

Practical WIRELESS

MAY
1973

20p


8 PAGE SUPPLEMENT

EXTRA
INSIDE

SIMPLE PROJECTS
FOR THE HOME



RADIO ALARM CLOCK

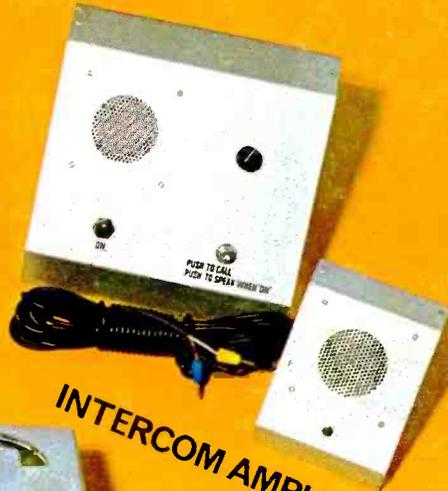


INTERCOM AMPLIFIER



BABY ALARM



TAPE TUNER

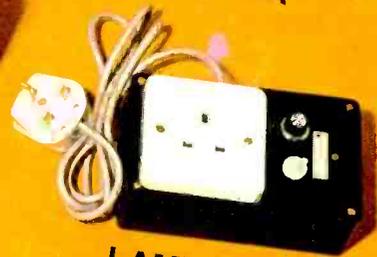

LAMP DIMMER



WATER LEVEL DETECTOR



LIGHT
POWERED
RADIO




TWO TONE DOOR BELL

PLUS ALL THE REGULAR FEATURES

look! electronics really mastered

... practical
... visual
... exciting!

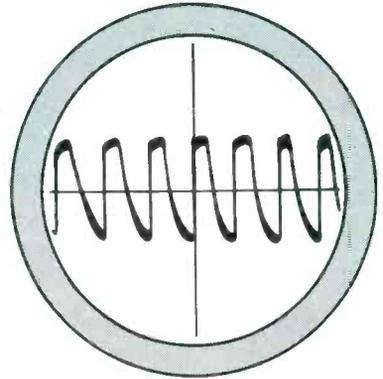no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

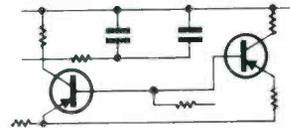2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL53

special free gift also to all our students

PRACTICAL WIRELESS

VOL. 49 NO. 1

ISSUE 795

MAY 1973

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Morris A. Colwell

ASSISTANT EDITOR

Lionel E. Höwes, G3AYA

ART EDITOR

Peter Metalli

TECHNICAL EDITORIAL

Eric Dowdeswell, G4AR

NEWS & PRODUCTION

Colin R. Riches

SECRETARIAL

Jenny Phelps

Jill Alflatt

Telephone 01-634 4292

ADVT. MANAGER

Roy Smith

Telephone 01-634 4293

CLASSIFIED ADVTs.

Colin R. Brown

Telephone 01-634 4301

SUBSCRIPTIONS

Subscription Rates for one year to any part of the world £2.65 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477 Binders and indexes can be supplied by the Binders Dept. at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of *Practical Wireless* and *Television* only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 22 SUPPORT SERVICE—Leader article and June preview
- 23 NEWS . . . NEWS . . . NEWS
- 37 PRACTICALLY WIRELESS—Light hearted view by Henry
- 42 TELEVISION—This month's attractions
- 48 NEXT MONTH in *Practical Wireless*
- 56 PRODUCTION LINES—New products reviewed
by Colin Riches
- 60 ON THE AIR—Reports on Broadcast Bands:
- 60 Short Wave—*Malcolm Connah*
- 63 Medium Wave—*Charles Molloy*
- 63 V.H.F./F.M.—*Simon David*
- 64 Amateur Bands, Short Wave—*David Gibson G3JDG*
- 68 HOTLINES on recent developments—*Ginsberg*

● CONSTRUCTIONAL

- 24 V.H.F. REGEN. RECEIVER—*R. H. Longden*
- 33 EXPERIMENTERS CORNER—Ideas for further development:
- 33 6-9 volt Stabilised Supply—*J. Rowley*
- 34 Two Versatile Transistor Amplifiers—*C. E. Miller*
- 46 RECEIVER MATCHING UNIT—*F. G. Rayer G3OGR*
- 49 "P.W. TRICOLOUR" Mood Lighting System, Part 2—
Jurek Budek
- 57 160-80 METRES CONVERTER—*R. A. Penfold*
- 67 TAKE 20 No. 48 Pulse Generator—*Julian Anderson*

● OTHER FEATURES

- 29 FETRONS Semiconductor substitutes for valves
- 38 SPECIAL VALVES Part 1 Communications—*M. K. Titman*
- 45 I.C. OF THE MONTH, NE555 Precision Timer—
L. A. J. Ireland
- 71 TRANSISTOR CIRCUITRY FOR BEGINNERS—
H. W. Hellyer and M. Hollier
- 75 GOING BACK Equipment of yesteryear—
Colin Riches and Arthur Dow

★ SUPPLEMENT Extra eight centre pages

SIMPLE PROJECTS FOR THE HOME

Two Tone Door "Bell"; Intercom Amplifier; Water Level Detector; Tape Tuner; Radio Alarm Clock; Lamp Dimmer; Baby Alarm; Light Powered Radio

PACKAGE PRICE R.S.C. STEREO PACKAGE OFFERS

FOR ILLUSTRATED UNITS

ONLY £39-95

Carr. £1.00
Or deposit £8.95
and 9 monthly
payments £4.22
(Total £44.98).



Individual Rec. Retail Prices:
LINEAR 505 5 + 5 Watt Amplifier *£17.50
GARRARD 2025 Autochanger + K840A Cartridge *£13.58
Teak Veneer Plinth with Transparent Plastic Cover *£8.10
Pair A55 LOUDSPEAKERS (Inc 8" x 5" 10,000 Gauss) *£11.50
TOTAL £48.68

SAVE £31-60

MONARCH SPEAKERS

GOLDRING GL72



SEND S.A.E. FOR FREE COLOUR BROCHURE

'SUPER 30' AMP

HIGH FIDELITY UNITS

PACKAGE PRICE **£99-95** Carr. £1.75

FOR ILLUSTRATED UNITS

Or deposit £15.00 and 12 monthly payments £8.00 (Total £111.00)
Individual Rec. Retail Prices:
GOLDRING GL72 *£11.00
Transcription Turntable - P.U. *£31.99
GOLDRING G800 *£12.21
Magnetic Cartridge *£10.50
DE-LUXE PLINTH with Roll-over Cover *£10.50
Pair R.S.C. MONARCH LOUDSPEAKERS line magnet. R.S.C. SUPER 30 *£38.70
MK III AMPLIFIER *£38.75
TOTAL £131.55

FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams, Frequency *£9-95 free Impedance 8-15 ohms.

Or Dep. £2.25 and 9 mthly pmtnts. £1 (Tot. £11.25)

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.
DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. *£9-45 Carr. 40p.
MONARCH Size 19 x 10 1/2 x 9in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible P.V.C. cone surround, long throw voice coil magnet. High flux pressure tweeter. Handsome design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. See 'package offers' for illustration. Carr. 50p **£19-35**

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ±12db. Treble Control ±13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs.



COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS **£11.50** Carr. 40p
OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £14.99 or dep. £2.20 and 9 monthly payments £1.70 (Total £17.60).

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.
J8 Size 15 1/2" x 10 1/2" x 9". SE8 For optimum performance with any 8in. *£6-47
8in. Hi-Fi speaker. Hi-Fi spkr. Size 19 x 10 1/2 x 9in. *£6-47
SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter. Size 25 1/2 x 16 x 9in. *£7-87
SE10 For outstanding results with 10in. Hi-Fi spkr. Size 25 1/2 x 16 x 9in. *£6-74
9in. P'td. *£7-87

AUDIOTRINE HIGH FIDELITY SPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.
Exceptional performance at low cost.

*HF808T	8"	10W	£2.98	HF120D	12"	15W	£4.99
*HF102D	10"	10W	£3.40	HF128	12"	15W	£5.75
HF120	12"	15W	£4.50	HF128D	12"	15W	£6.25

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω.
PLEASE STATE IMPEDANCE WHEN ORDERING *£3-85
MODEL 803T 8" 15w. with parasitic Tweeter. £4.95
Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15.



R.S.C. BATTERY/MAINS CONVERSION UNITS



TYPE BML An all-dry battery eliminator. Size 5 1/4 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v and 90v, to battery radio where A.C. mains 200/250v. 50cfs is available. ASSEMBLED READY FOR USE **£3-75**

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5-95** Carr. 30p
OR SENIOR 15 WATT INCLUDING **£6-95** Carr. 35p
HF126 15,000 LINE SPEAKER

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'Lift and cut' controls. 3 Input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7-75** Carr. 40p.
OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£10-95**

ASTERISK * INDICATES UNITS WHICH UP TO APRIL 1st INCLUDED PURCHASE TAX

With effect from the same date other items will bear VAT at 10% (i.e. 10p in the £1)

In the event of the March Budget announcing an alteration in the rate of VAT the appropriate adjustment will be made

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50c/s. Screened

MIDGET CLAMPED TYPE 21 x 21 x 2 1/2 in. 250v., 60mA, 6-3v. 2a. 90p 200-0-250v., 60mA 6-3v. 2a. £1.05	TOP SHROUDED DROP-THRO' TYPE 250-0-250v. 70mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-35 250-0-250v. 100mA, 6-3v. 3a. £1-55 250-0-250v. 100mA, 6-3v. 2a., 0-5-6-3v. 1a. £1-60 250-0-250v. 80mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-65 250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20 300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20 300-0-300v. 130mA, 6-3v. 4a., c.t., 6-3v. 1a. £2-60 Suitable for Mullard 610 Amplifier £2-60 300-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-60 350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-60	SELENIUM RECTIFIERS F.W. (Bridged) All 9/12v. D.C. output. Max. A.C. input 18v. 1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 6a. 80p.
FULLY SHROUDED UPRIGHT MOUNTING 250-0-250v. 60mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-40 250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20 300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20 300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a. £2-65 For Mullard 610 Amplifier £2-65 350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-20 350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2-65 425-0-425v. 200mA, 6-3v. 4a., c.t., 6-3v. 3a. £4-95 425-0-425v. 200mA, 6-3v. 4a., 6-3v. 3a., 5v. £5-10 425-0-425v. 200mA, 6-3v. 4a., c.t., 6-3v. 3a. £5-10 350-0-450v. 250mA, 6-3v. 4a., c.t., 6-3v. 3a. £5-60	CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. 99p; 2 1/2a. £1.10; 3a. £1.25; 5a. £1.45; 6a. £1.65; 8a. £2.00 AUTO (Step UP/step DOWN) TRANSFORMERS 0-110/120v. 200-230-250v. 50-80 watts £1.10 150 watts, £1.90 250 watts £2.75; 500 watts £5.75 OUTPUT TRANSFORMERS Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 50p Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 83p Push-Pull 10 watts 6V6, EL86 to 3, 5, 8 or 15 Ω £1.37 Push-Pull EL84 to 3 or 15 Ω 10-12 watts. £1.35 Push-Pull Ultra Linear for Mullard 510, etc. £2.20 Push-Pull 15-18 watts sectionally wound 6L6, KT66, etc. for 3 or 15 Ω £1.99 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £3.30	SMOOTHING CHOKES 150mA, 7-10H, 250 Ω 70p ; 100mA, 10H, 200 Ω 80p; 80mA, 10H, 350 Ω 90p ; 60mA, 10H, 400 Ω 25p.
FILAMENT or TRANSISTOR POWER PACK Type 6-3v. 1.5a. 49p; 6-3v. 2a. 54p; 6-3v. 3a. 79p; 6-3v. 6a. £1.30; 12v. 1a. 65p; 12v. 3a. or 2 1/2v. 1.6a. £1.95-0-18v. 1 1/2a. £1.10-0-12v. 2 1/2a. 2a. £1.78.		

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
Only high grade components by leading manufacturers

- Push Button Selector Switching
- Jack Socket for Headphones
- Neon Indicator
- Satin Silver Finish Metal Fascia
- Solid State Circuitry
- Twenty Silicon Transistors
- Four Diodes, Four Rectifiers

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8 Ω. Frequency Response 7 Hz to 70 KHz ± 1 1/2 dB.



COMPLETE KIT (less cabinet). Carr. 65p. Cabinet if req. £5 extra. **£25**

Send S.A.E. for full descriptive leaflet.


R.S.C. STEREO FM TUNER. Visually matches Super 30 Mk. III **£44-95**

FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £3-99 (Total £42-91). **£38-75**


'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in. approx.
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more Carr. 65p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-47 (Total £26-83). **£23**

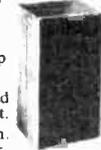

RSC GROUP/DISCO UNITS

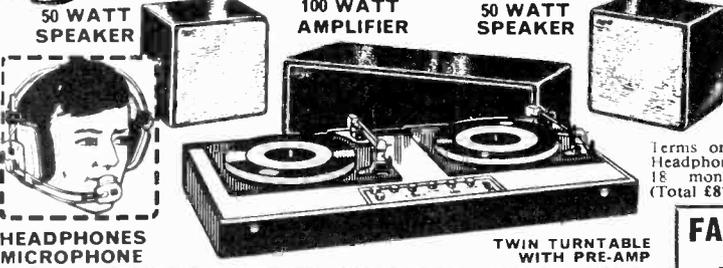

HEADPHONES MICROPHONE

TWIN TURNTABLE WITH PRE-AMP

PACKAGE OFFER

- Units listed below
 (a) 100w POWER AMPLIFIER
 (b) PAIR OF HI-FI HEADPHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to headphones)
 (d) PAIR 50 WATT SPEAKERS Black/Rexine covered
- Size approx. 18" x 18" x 8"
£72-85
 Carr. £1-25

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 Mk.III turntables and Sonotone or Acos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Rexine covered Cabinet with lid. see illus. on left

Or Dep. £13-25 and 9 mthly pymts £8-88
 (Total £275-17) or Dep. £15 and 18 mthly payments £3-82 (Total £80-16).

£67-10

Terms on Amplifier, Speakers and Headphone/Mike £15 and 18 monthly payments of £4-00 (Total £87-00).

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/150	15" 60 Watt 14,000 gauss 8/150	12" 50 Watt 13,000 gauss 150
£22-95	£12-90	£10-90
Dep. £8 and 9 mthly payments £2-20 (Total £25-80)	Dep. £3-30 and 9 mthly payments £1-30 (Total £16)	Dep. £2 and 9 mthly payments £1-20 (Total £12-80)

PAIR SUITABLE ALL PURPOSES FOR BASS GUITAR, ELECT. ORGAN, ETC.

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair
 TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C132 30-40 WATTS Fitted two 15" 11,000 lines 15 watt speakers. Overall size approx. 58x14x9in
 Packed for 12 months' GUARANTEE. Carr. 65p
£19-95
 Terms: Dep. £3 and 9 mthly payments £2-22 (Total £22-88)

TYPE C4125 50 WATTS Fitted four 12" 11,000 lines 15 watt speakers. Overall size approx. 58x14x9in
 Packed for 12 months' GUARANTEE. Carr. 75p
£31
 Terms: Dep. £4 and 9 mthly payments £2-37 (Total £34-33)

TYPE C4100 100 WATTS Inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 58x16x10". Acoustically damped and pressurised. Terms: Dep. £11 and 12 mthly. pmts. £5-18 (Total £73-18). Carr. £1

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output. Hum level -70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, E186, ECC83, EL34, EL24, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. for mixing purposes. 200-250v. 50 c/s A.C. mains. For 4 and 15 ohm speakers. Twin-handled perforated cover £1-90. 12 MONTHS' GUARANTEE. Carr. 65p

£19-75
 TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22-90). Send S.A.E. for leaflet.

LINEAR T40/60D 50W GROUP/DISCO AMPLIFIER

- ★ FULL MONITORING FACILITIES
- ★ Individual Bass and Treble controls
- ★ Twin Jack output sockets for speakers
- ★ Input sockets for medium or high impedance
- ★ Microphones or Guitar P.U.s and Crystal or Ceramic Gram. P.U.s
- ★ Frequency response 30-20,000 Hz.
- ★ Output overload protection plus double fusing

FRONT PANEL (Jack inputs) Gram, Gram, Microphone/Guitar P.U.; plus monitoring socket.
 CONTROLS Vol. (1) (2) (3) and (4). Bass, Treble, Master Vol., Monitor Selection Switch (Gram (1) or (2), Mains Switch).

Simulated black rexine, plastic bonded metal case.
£49-50 Carr. 75p
 Or Deposit £7-50 and 9 monthly payments £5-37 (Total £65-85)

ALSO STOCKED-LINEAR T80/100D £69-75

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Control. Protective circuit to guard against damage from accidental shorts. Output for Speakers/5 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 60 watts music rating.
 Or deposit £7-25 and 9 monthly payments £3-55. Total £39-20.
£34-95 Carr. 75p

RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.

For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle.
 Terms: Deposit £8-95 and 9 monthly payments £6 (Total £82-95). Carr. £1-50
ONLY £55-95

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free
£6-75 or Dep. £1-25 and 9 mthly payments 75p (Total £8-00)

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95	PACKAGE PRICE
PR. FANE POP 25/2 25W L/SPEAKERS	£13-80	£45 carr. £1
Terms: Deposit £6-80 and 9 monthly payments of £4-92 (Total £60-78)	£48-45	
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95	PACKAGE PRICE
PR. FANE POP 50 L/SPEAKERS	£21-80	£52 carr. £1
Terms: Deposit £10 and 9 monthly payments of £5-37 (Total £68-33)	£68-75	
F.A.L. PHASE 50 MK.III AMPLIFIER	£34-95	PACKAGE PRICE
PAIR L12/25 25W L/S in cabinets	£23-90	£56 carr. £1-25
Terms: Deposit £10 and 9 monthly payments of £5-88 (Total £68-92)	£68-85	
F.A.L. PHASE 100 AMPLIFIER	£61-95	PACKAGE PRICE
4 FANE POP 50 L/SPEAKERS	£43-80	£99-95 carr. £2
Terms: Deposit £10-73 (Total £112-82)	£105-55	

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH

L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50
 Or deposit £5-50 and 9 monthly pmts. of £3-70. Total £38-80

L12/20 12" 20-25 WATT 13,000 lines
 L13 13" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State impedance required. Carr. 40p

£34-50
£11-95
£5-25

CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

VAT FOR INFORMATION ON PRICES MARKED WITH * SEE OPPOSITE PAGE

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.
 ★ Two extra heavy duty 12in. 50v Loudspeakers.
 ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet.
 Credit Terms: Deposit £15 & 9 monthly payments of £6-25.
£65 Carr. £2 (Total £71-25)

NOW FIVE NEW BRANCHES

- BOLTON** open shortly
NOTTINGHAM 19/19A MARKET STREET
SUNDERLAND 5 MARKET SQUARE
STOCKPORT 8 LITTLE UNDERBANK
COVENTRY 17 SHELTON SQUARE
- NEW LARGER PREMISES AT **HULL**, **DARLINGTON** & **NEWCASTLE** See Addresses

RSC GP30 HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group

A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator.
 For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 9 monthly payments of £2-45.
£23-50 Carr. 65p (Total £26-45)

RSC

HI-FI CENTRES LTD.
 MAIL ORDERS & EXPORT ENQUIRIES TO:
 ADDIO HOUSE, HENCONNER LANE, LEEDS, 13. Tel: Pudsey (09735) 77831.
 TERMS C.W.D. or C.O.D. No C.O.D. under £1.
 POSTAGE 25p EXTRA UNDER £2. 30p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED.
 S.A.E. PLEASE WITH ENQUIRIES.
 SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS


R.S.C. Branches operate a 5-day week Open all day Saturday

- BRADFORD** 10 North Parade (Closed Wed.) Tel. 25349
BLACKPOOL (Agent) O & C Electronics 227 Church Street
BIRMINGHAM 30/31 Great Western Arcade, Tel. 021-236 1279 (Closed Wed.)
COVENTRY 17 Shelton Square, The Precinct
DERBY 26 Osaston Rd., The Spot (Closed Wed.) Tel. 41361
DARLINGTON 19 Northgate (Closed Wed) Tel 68043
EDINBURGH 101 Lothian Rd. (Closed Wed.) Tel. 229 9501
GLASGOW 326 Argyle St. (Closed Tues.) Tel. 248 4158
HULL 7 Whitefriargate Tel. 20505
LEICESTER 32 High Street (Closed Thurs.) Tel. 56420
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.) Tel. 28252
LIVERPOOL 73 Dale St. (Closed Wed.) Tel. 236 3573
LONDON 238 Edgware Road, W.2. (Closed Thurs.) Tel. 723 1629
MANCHESTER 60A Oldham Street, (Closed Wed.) Tel. 236 2778
MIDDLESBROUGH 106 Newport Rd. (Closed Wed.) Tel. 47096
NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.) Tel. 21469
NOTTINGHAM 19/19A Market Street (Closed Thurs.) Tel. 48068
SHEFFIELD 13 Exchange Street (Castle Market Bldg.) (Closed Thurs.) Tel. 20716
STOCKPORT 8 Little Underbank. Tel: 480-0777.
SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 70573

TOP QUALITY — LOW COST




AMATEUR RADIO EQUIPMENT

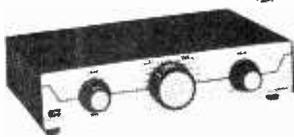


P.R.40
SOLID STATE
R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supercedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee ...

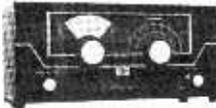

MULTIBAND-6
SOLID STATE
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery). Stamp brings illustrated leaflets.

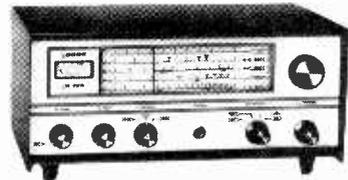

CR70A
COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

Complete ready built.

SEND FOR YOURS TODAY!

NOTE: These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers. Some portable receivers being advertised as Communication Receivers do not meet these requirements.



ON THE DESIGN STAFF—
G3SZM G3IRE

CODAR®

TELECOMMUNICATIONS AND ELECTRONIC
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX
Tel. 090-63-61901 BN15 - 8TZ



The Pictorial Method

**BASIC ELECTRICITY (5 vols)
ELECTRONICS (6 vols)
TELEVISION (3 vols)**

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR
100%
GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

WHAT READERS SAY

... after studying them for a while, I came to the conclusion there is only one word to describe these manuals—BRILLIANT.
E.J. Southampton.

Their appeal is in their simplicity.
E.P. Basingstoke.

An ordinary person like me can soon acquire a first rate understanding of the subject.
C.B. Maidstone.

I have passed my theory exam. on electronics with the help of your manuals. *D.F.F. Ely.*

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £4.50
- BASIC ELECTRONICS 6 parts £5.40
- BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS

FULL POSTAL.....


ADDRESS

POST NOW FOR THIS OFFER!

Cool lighting **for hot parties.**

Velvet dim to full brightness at a touch of the finger. Off/on and infinitely variable.

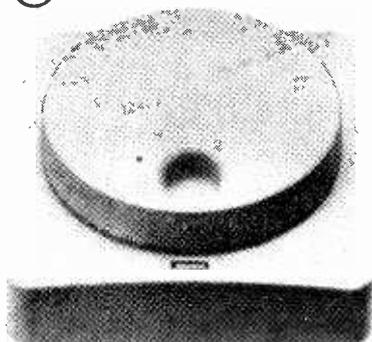Beta light glow makes switch easy to find in the dark and consumes no current.



Economical too!

As the light is progressively dimmed, so the current consumption drops – think of it as an electric tap. 300 watt capacity, straight replacement for standard light switch.

Complete kit of parts £2.80 or made up £2.90.



Hot Ignition for cold mornings.

The Jermyn capacitor discharge ignition system.

Instant starting in all weathers. Even with a near flat battery, the unit will produce a full sized spark.


Just one of the many advantages of an electronic ignition system, the others are:

High energy spark even at maximum revs.

Smoother running. Less strain on battery and starter. Lower petrol consumption. Long plug life with infrequent adjustment (typically 20,000 miles, gapped at .050").

No contact breaker arcing giving long life and less adjustment (typically 20,000 – 25,000 miles)

STATE + or – earth when ordering.

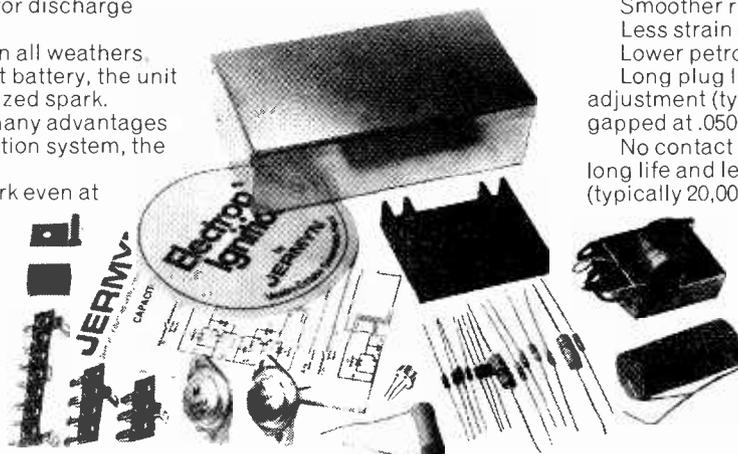

Complete set of parts to build it yourself for only £7.75, as described in Practical Wireless and fully approved by the author.

Save 55p
Buy both for £10.00

Reprints of the two part feature are available at 25p.

To Jermyn Industries, 85 Vestry Estate, Sevenoaks, Kent.

Please despatch return of post ... light dimmer kit ... light dimmer ...
Ignition Kits + or – earth ... £10 pair. Enclose cheque or postal order.

BLOCK CAPITALS

NAME

ADDRESS

JERMYN

Another!
winner!

fane **MODE ONE**

**HIGH FIDELITY
LOUDSPEAKER KIT**



**ONLY
£9.59**

Post free
Price includes
VAT rate of 10%.
Any applicable
reduction will
be made to
accord with
the Mar.
1 9 7 3
Budget.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

SPECIFICATION OF UNITS

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	½"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	10kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. **SIZE** 15½" x 10½" x 9".

*When used with above cabinet.

Please send S.A.E. for fully descriptive leaflet.

Distributors to the wholesale and retail trade
LINEAR PRODUCTS LTD.
Electron Works, Armley, Leeds
LS12 3SA. Tel. 630126

Manufactured by
FANE ACOUSTICS LTD.
Hick Lane, Batley, Yorkshire.
Tel. Batley 6431

ERSIN

Multicore
5 CORE SOLDER

for fast, easy
reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

**EASY-TO-USE
DISPENSERS**



Size 5
Savbit alloy
18 swg, 18p
(illustrated).
Size 19A
60/40 alloy
18 swg, 18p
Size 15
60/40 alloy
22 swg, 22p

**IDEAL FOR HOME
CONSTRUCTORS**


Size 1 cartons in 40/60, 60/40
and Savbit alloys
in 7 gauges 25p



Size 12
for Service
Engineers and
Electricians.
75ft of 18 swg
Savbit alloy. 75p



NEW! BIB WIRE STRIPPER AND CUTTER

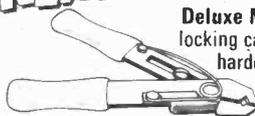

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to **Multicore Solders Ltd.**, Hemel Hempstead, Hertfordshire HP2 7EP

**4 CHANNEL STEREO
CONVERTER**



TRANSFORMS
YOUR STEREO
SYSTEM INTO
SENSATIONAL
QUADRAPHONIC
SOUND

Create a new dimension in sound — sound that engulfs you with natural realism from every corner of your room. Simply wired to your amplifier or Tuner/Amp. speaker outputs and again into 4 speakers. Neat styling with brushed effect console panel. Peak input power 50w into 8 ohms. Front Hi/Low Level 6dB. Phone jacks for input and output. Size: 6" x 3½" d. x 2" h. Guaranteed.

INTRODUCTION PRICE

£7.50


CCIL LTD

(Dept. PW 5), 43 BARTHOLOMEW CLOSE,
LONDON, EC1A 7HP. Tel. 01-600 3211.

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.

**INTER-LOCKING
PLASTIC STORAGE DRAWERS**

NEAT!
HANDY!
TIDY!

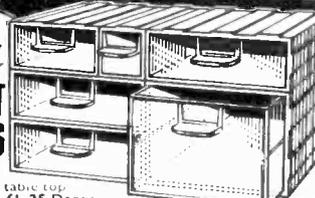

**DISCOUNT
PRICES**

SINGLE UNITS (5" x 2½" x 2½") £1.25 Dozen
DOUBLE UNITS £2.15 Dozen
TREBLE (3D) £2.20 for 8
DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.25 for 8 extra large size (6D1) £3.10 for 8, carriage 35p orders over £6. £10 postage free
QUANTITY DISCOUNTS! 5% in £1 for orders over £6. 7½% over £10. 10% over £20. Quotation for large quantities.
PLEASE ADD VAT TO TOTAL REMITTANCE.

**IVORYET
LIMITED**

Dept. PW5) 124 CRICKLEWOOD BROADWAY,
LONDON N.W.2 01-450 4844

**5 SIZES
ALL INTERLOCK**

**LARGE STOCKS
ATTRACTIVE DISCOUNTS
DEPENDABLE SERVICE**

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power 60p
AC153K npn germanium low power 32p
AC176K npn germanium low power 32p
AD161 npn germanium medium power 42p
AD182 pnp germanium medium power 40p
AF139 pnp germanium UHF 35p
BCN 107 12p; BC108 12p; BC109 13p; } npn
BC167 10p; BC168 9p; BC169 10p }
BC177 15p; BC178 14p; BC179 15p; } pnp
BC257 9p; BC258 8p; BC259 9p }
Standard groupings available.
BD135 npn med power 30p
BD136 pnp med power 30p
DIODES
OA90, OA91, OA95 each 8p
OA200 9p; OA202 10p
Other semiconductor
AC128 17p; AP117 35p
BFY61 19p

Full lists and technical data will be found in Catalogue No. 6.


SIEMENS' THYRISTORS

0-8A 400V 58p, 600V 70p
3A 400V 60p, 600V 88p

ZENER DIODES full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 286F) 4p.

DIN PLUGS & SOCKETS

by Hirschmann, 4A rating

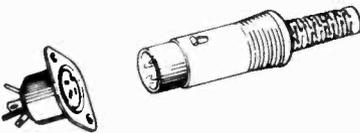


2 way LS—socket 10p; plug 12p. 3 way scr. socket 10p; plug 12p. 5 way scr. socket 12p; plug 15p.

TRANSISTOR ACCESSORIES

To3 cover 7p
Heat sinks 1°C/W, type 6W1, un drilled 60p

SWITCHES

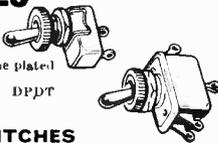1011C SPST toggle 20p
409 DPDT toggle 29p. (These are chrome plated 2.6A rating)
7201 Sub-miniature DPDT 250V a.c./2A 48p




ROTARY SWITCHES

Radiospares Miniature Make-switch (in assembly kit form) Shaft 48p
Wafers, MRB-2P5W, 1P11W; RBM-1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each, 32p

WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, each 24p

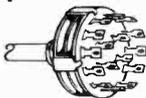

ELECTROLYTIC CAPACITORS

AXIAL LEAD

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity μ F								
0.47							7p	7p
1.0						7p	7p	7p
2.2					7p	7p	7p	7p
4.7				7p	7p	7p	7p	7p
10				7p	7p	7p	7p	7p
22				7p	7p	7p	7p	7p
47	7p			7p	7p	7p	7p	7p
100	7p	7p		7p	7p	7p	7p	7p
220	7p	7p		7p	7p	7p	7p	7p
470	7p	7p		7p	7p	7p	7p	7p
1000	9p	12p	15p	17p	20p	23p	24p	41p
2200	14p	18p	22p	25p	30p	36p	40p	
4700	23p	28p	37p	40p				
10,000	37p	40p						

Polycarbonate —5% Tolerance

250V up to 0.1 μ F: 100V/0.1 μ F and above.
0-01; 0-012; 0-015; 0-018; 0-022; 0-027; 0-033; 0-047; 0-056; each 4p.
0-068; 0-082; 0-1; 0-12; 0-15 each 4p.
0-18; 0-22; each 5p.
0-27; 0-33; 6p; 0-39 7p; 0-47 8p; 0-56 10p; 0-68 11p. 1 μ F 13p.

SILVERED MICA non-polarised capacitors in 34 values from 2.2 pF to 680 pF, each 6p

RESISTORS 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 μ p
C	1/20W	5%	82 Ω - 220K Ω	E12	9	8	7.5
C	1/8W	5%	4.7 Ω - 470K Ω	E24	1	0.9	0.75 nett
C	1/4W	10%	4.7 Ω - 10M Ω	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 Ω - 10M Ω	E24	1.2	1	0.8 nett
C	1W	10%	4.7 Ω - 10M Ω	E12	2.5	2	1.6 nett
MO	1/2W	2%	10 Ω - 1M Ω	E24	4	3	2 nett
WW	1W	10% \pm 1/20 Ω	0.22 Ω - 3 Ω	E12	7	7	6
WW	3W	5%	1 Ω - 10K Ω	E12	7	7	6
WW	7W	5%	1 Ω - 10K Ω	E12	9	9	8

Codes: C—carbon film, high stability, low noise.
MO—metal oxide, Electrofil TR5, ultra low noise.
WW—wire wound, Pleseley.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.


Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order).

★ Please remember to add V.A.T. to your order if it is going to reach us after March 31.

EVERYTHING BRAND NEW, GUARANTEED TO MAKERS SPEC. NO SECONDS OR REJECTS


KNOBS

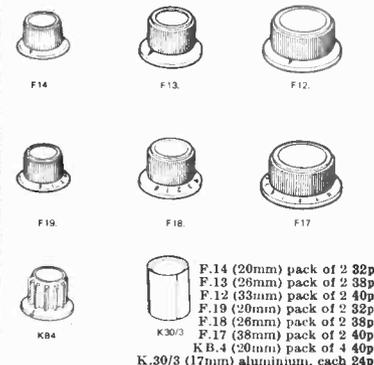All grub screw fitting for 1" shafts. Black. For other types—see Catalogue No. 6, P.54



F.14 (20mm) pack of 2 32p
F.13 (25mm) pack of 2 38p
F.12 (33mm) pack of 2 40p
F.19 (20mm) pack of 2 32p
F.18 (26mm) pack of 2 38p
F.17 (38mm) pack of 2 40p
K.B.4 (20mm) pack of 4 40p
K.30/3 (17mm) aluminium, each 24p

POTENTIOMETERS

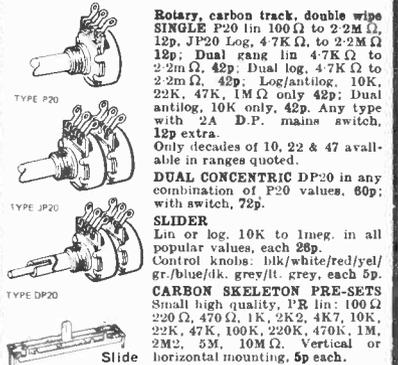

Rotary, carbon track, double wipe
SINGLE P20 lin 100 Ω to 2.2M Ω , 12p. JP20 Log, 4.7K Ω , to 2.2M Ω , 12p; Dual rang lin 4.7K Ω to 2.2M Ω , 42p; Dual log, 4.7K Ω to 2.2M Ω , 42p; Log/antilog, 10K, 22K, 47K, 1M Ω only 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.
Only decades of 10, 22 & 47 available in ranges quoted.
DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.
SLIDER
Lin or log, 10K to 1Meg. in all popular values, each 26p.
Control knobs: blk/white/red/yl/gr./blue/dk. grey/lt. grey, each 5p.
CARBON SKELETON PRE-SETS
Small high quality, PR lin: 100 Ω , 22K, 47K, 10K, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 3M, 10M Ω . Vertical or horizontal mounting, 5p each.

IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 180's of semi-conductors, ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc. Information and equivalent tables, etc. Well illustrated (96 pages 5 1/4" x 8 1/4") 25p. post free with refund voucher for 25p. allowable on orders over 25 or more.

with 25p refund voucher

All items offered for sale in accordance with our stated terms of business, copy of which available on request. Prices quoted DO NOT include V.A.T.
Orders received after March 31st must be accompanied by an additional 10% of nett value for V.A.T.

DISCOUNTS Not allowed on nett price items. 10% on orders for 25 or more, 15% on orders for 150 or more. Prices subject to alteration without prior notice.

POSTAGE AND PACKING FREE SURCHARGE 10p on small mail orders under 22. Overseas orders carriage and insurance charged at cost.

ELECTROVALUE

(Dept. P.W. 5) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 3603 Telex 264475

ENG. REG. NO. 1047768. R.O. 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB


SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES
FOR DOMESTIC & COMMERCIAL USE

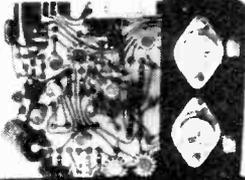New Versions using 3A
'Plastic Power' Driver
Transistors Now Available



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2-95 carr. free

25 WATTS RMS. 7 transistors 7 diodes

SA35 £4-45 carr. free

35 WATTS RMS. 7 transistors 7 diodes

SA100 £10-90 carr. free

100 WATTS RMS. 11 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000 Hz ± 1dB
Distortion	0.2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	25-45 volts SA25/35 40-70 volts SA100
Size	4 1/2" x 4" x 1" (SA100) 4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR

THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilized supply for 2 SA25/35	£4-90
PU70	Unstabilized supply for one or two SA100	£7-75 carr. 40p
PS45	Stabilized module for 2 SA25's or two SA35's	£3-50 carr. free
MT45	Transformer for above, heavy duty	£2-85 carr. 20p
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3-50 carr. 20p
PS70	Stabilized supply module for one or two SA100's	£4-90 carr. free
MT70	Transformer for PS70	£4-90 carr. 40p

ALL MODULES ARE BUILT ON
GLASS FIBRE P.C. BOARD
AND ARE SUPPLIED FULLY TESTED

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE £13-90 + 20p carr. or with supply
£18-95 + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

SPECIFICATION

Power output	120 watts into 8 ohms
Freq. response	20-20,000 Hz ± 2dB
Input sensitivity	200 mV into 10K
Construction	Fibreglass board
Size	8" x 4" x 4" (5" with supply)
Low distortion parallel push-pull output stage.	




NEW 160 watt version & supply **£27-90**

SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

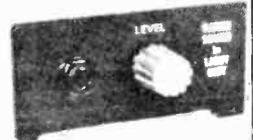Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.




£8-90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in Tough Steel case for free mounting or panel fixing. Fully guaranteed.

£19-75 carr. 30p

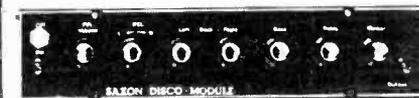MONO VERSION £6-50 carr. 20p (As illustrated, S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



£15-80 carr. 30p


SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. **THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B. -Stereo only has mic input.)

COMPLETE AMPLIFIERS

The CSE 100. £34-90 carr. free

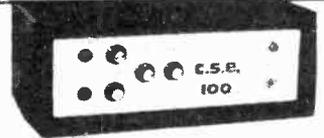This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.



The SAXON 100 £48-50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

600 Watt 3 colour Light Boxes Smart Resine finish £15 carr free.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5-95 carr. 30p. 15" 50W.8/15 ohm £14-50 carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11-50 carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use.
D11 DHL IDEAL DISCO MIKE ONLY £9-45 (rrp £11-00).

SEND SAE FOR OUR AKG PRICE LIST. DISCOUNTS ON ALL MICS.

All prices subject to VAT at standard rate

CALLERS & MAIL ORDER:

327-331 Whitehorse Road,
W. Croydon, Surrey
CRO 2HB 01-664 6385

CALLERS ONLY:

OUR NEW
DISTRIBUTORS

CIRCLE SOUND,
328-330 The Banks, Rochester.
Medway 464198

BUSINESS HOURS:

9.30 a.m.
to 5.30 p.m.

TERMS OF BUSINESS:

C.W.O. or C.O.D. (35p extra)
All cash in regd. envelopes please!
Telephone orders to our CROYDON BRANCH.
TRADE & EXPORT enquiries invited.

COMET HI-FI discount warehouses



NEW LOW PRICES

	Rec. Retail Price	Comet Price
STEREO AMPLIFIERS		
AKAI AA5200	87-45	64-95
AKAI AA5500	109-45	80-95
AKAI AA5800	164-45	121-95
ALBA UA 700	41-72	27-95
ALPHA 212 by Highgate	41-53	25-95
AMSTRAD IC 2000	50-88	30-95
AMSTRAD Integra 4000	39-05	23-95
ARMSTRONG 521	64-90	48-50
FERRROGRAPH F307 Mk II (cased)	74-80	49-95
GLIXOR MW3000, 15 watts RMS per channel	54-45	25-95
GOODWIN RH 25 25	65-95	49-95
JVC Nivico VN 300	63-80	52-95
JVC Nivico MCA 104Z	93-50	74-95
MCA 105E	143-55	119-95
MCA V5E/VN550		
Quadrasonic	97-90	81-95
MCA V9E/VN880		
Quadrasonic	162-80	136-95
KELETRON KSA 700	31-90	19-95
KELETRON KSA 1500	42-90	26-50
LEAK Delta 30 (cased)	76-89	51-95
LEAK DELTA 70 (cased)	94-45	62-95
METRO SOUND ST20E	43-45	26-95
METRO SOUND ST20E	77-00	50-95
PHILIPS RH521	119-90	98-95
PIONEER SA500A	51-81	35-95
SA600A	105-03	65-95
SA800	139-21	99-95
SA1000	171-40	107-95
Quadrasonic QL600		
Converter	130-85	93-95
QD 210 Quadrasonic decoder	47-14	32-95
QA 800A Quadrasonic	Sp. Price	159-95
QC800A Pre-amp	Sp. Price	133-95
QM600A Pow. amp.	Sp. Price	135-95
Reverberation 202w	60-45	43-50
RANK ROTEL 210	38-39	28-50
RANK ROTEL 310	57-20	39-95
RANK ROTEL 610	86-35	56-95
RANK ROTEL RA 810	116-05	83-50
RANK ROTEL RA 1210	141-90	101-95
ROGERS Ravensbourne	77-00	59-50
Ravensbourne (cased)	82-50	64-95
Ravensbrook Mk. II	57-75	44-95
Ravensbrook (cased) Mk. II	63-25	48-50
SINCLAIR 2000	38-50	27-75
3000	49-50	34-95
PROJECT 605	32-95	23-75
SOLARVOX 20, 10 watts RMS per channel	43-95	26-95
SOLARVOX 30, 15 watts RMS per channel	51-65	35-95
SOLARVOX MA801 2 x 8 watts RMS plus MATRIX 4 channel	42-30	29-75
SOLARVOX MA813 2 x 18 watts plus MATRIX 4 channel	56-52	42-95
TANDBERG TA300	76-89	59-95
TANDBERG TA300M	87-45	72-50
WHARFEDALE Linton amplifier	71-50	50-95
Amplifiers listed all take both ceramic cartridges.		
TUNERS		
AKAI AT550 AM/FM/MPX/FET	84-10	61-95
AKAI AT580 AM/FM/MPX/MOS. FET	131-09	96-95
AMSTRAD Multiplex 300 FM	37-55	26-95
ARMSTRONG M8 Decoder	10-45	7-75
*DULCI MCT 7 FM	22-96	14-90
JVC Nivico MCT V5E/VT500 AM/FM	80-96	62-95
MCT V7E AM/FM	115-25	94-95
LEAK Delta FM	74-43	52-95
LEAK Delta AM/FM	83-79	62-25
METRO SOUND FMS 20	51-70	36-95
PHILIPS RH 690	45-66	33-50
PHILIPS RH 621	102-61	78-80
PIONEER TX500A AM/FM	72-47	49-95
PIONEER TX900 AM/FM	100-35	68-95
RANK ROTEL 320	55-91	39-95
RANK ROTEL 620	87-86	62-95
ROGERS Ravensbourne in Teak Case	61-05	44-95
Ravensbrook (cased)	46-75	34-95
SINCLAIR 2000	42-44	28-95
3000	42-44	28-95
Project 60 Tuner (stereo)	23-57	16-95
All Tuners listed are complete with MPX Stereo Decoder except where stated.		
TUNER/AMPLIFIERS		
AKAI CR80T AM/FM Tuner Amplifier with built in Eight Track Tape Recorder	140-78	84-95
AKAI AA8030	131-09	96-95
AKAI AA8080	115-25	94-95
AKAI AS8100S Quadrasonic	243-85	181-95
AKAI AA8500	235-97	166-95
AKAI 6300	130-31	74-95
ARENA 2600	104-62	55-95
ARMSTRONG M8 Decoder	10-45	7-75
ARMSTRONG 525	84-96	66-50
ARMSTRONG 526	95-31	74-95
GOODMANS Module 90, 35w. RMS	87-55	66-95
Module 80 Compact	158-16	119-95
Module 90	112-04	85-95
Module 110 FM/MW/LW/SW/100w. RMS	130-86	99-95
GOODMANS Module 110, Compact	230-65	175-95

These prices are effective April 1st, 1973 and are calculated assuming a V.A.T. rate of 10%. Should the V.A.T. rate differ, please check prices before ordering.

	Rec. Retail Price	Comet Price
TUNERS/AMPLIFIERS—continued		
JVC Nivico 4MM 1000 Quadrasonic	149-93	124-95
JVC Nivico VR 550/5501 AM/FM..	93-68	75-95
VR 5521L AM/FM and SEA	164-74	135-95
4VR 5414 Quadrasonic	211-82	176-95
KYOTO 1000 AM/FM Tuner/Amplifier with built in Stereo Cassette Recorder. Complete with two speakers and two microphones	79-90	57-95
LEAK Delta 75	163-83	123-95
PHILIPS RH 720	202-41	154-95
PIONEER SX525	134-86	92-95
SX626	154-72	126-95
SX828	184-72	152-95
QX 4000 Quadrasonic	285-21	196-95
QX 8000 Quadrasonic	216-81	150-95
ROTEL RX 150A	274-69	190-95
ROTEL RX200A	65-68	47-95
ROTEL RX 400A	84-10	61-95
ROTEL RX 600A	101-12	74-95
ROTEL RX 800A	140-01	103-95
ROTEL RX 800A	178-07	131-95
ROTEL RX 154A Quadrasonic	121-68	89-95
SOLARVOX TAM 1105 2 x 5 watts RMS AM/FM Multiplex comp. with 2 speakers and featuring Matrix 4 channel	36-28	28-95
TANDBERG TR200 MPX	99-79	83-95
TANDBERG TR1000 FM MPX (teak)	146-86	124-95
TANDBERG TR1010 AM/FM MPX	159-09	133-95
TELETON CR55	118-06	84-95
TELETON R8000 AM/FM	39-74	20-95
WHARFEDALE LINTON WF40	107-66	81-95
All Tuner/Amplifiers listed take magnetic cartridges except Teleton R8000 and Kyoto 1000 which take ceramic only. All include MPX Stereo Decoder with the exception of Armstrong where M8 decoder is extra.		
TURNTABLES		
CONNOISSEUR BD1 Kit	12-65	10-50
CONNOISSEUR BD2 Chassis	31-02	24-95
CONNOISSEUR BD2 P/C/SAU2	39-16	32-25
GARRARD SP25 Mk. II	145-25	97-75
GARRARD 40B	12-85	9-50
GARRARD SL65B	18-78	12-95
GARRARD SL95B	46-40	30-60
GARRARD 401	40-43	27-50
GARRARD SL72B	30-73	20-25
GARRARD AP76	26-82	16-95
GARRARD Zero 100A	51-57	37-25
GARRARD Zero 100S	47-44	34-25
GOLDRING G101P/C	28-05	19-50
GOLDRING GL72 Chassis	29-70	20-25
GOLDRING GL75	38-61	28-50
GOLDRING GL75P	39-60	26-50
GOLDRING GL75P/Cover	48-84	33-50
GOLDRING GL85P/Cover	82-50	55-50
LEAK Delta	65-07	49-95
JVC Nivico SRP 473 Quadrasonic, including plinth and cover	65-88	52-95
McDONALD MP70	13-96	9-25
McDONALD 610	17-71	12-25
McDONALD HT70	19-49	13-50
PHILIPS GA212 Electronic	64-95	50-95
PIONEER PL12D with base and cover	47-19	32-50
PIONEER PL61 with base and cover	170-53	114-95
THORENS TD125 Mk. II	77-00	62-95
THORENS TD125AB Mk. II with TP 16 arm	116-05	95-50
THORENS TD 160C including base and cover	65-04	53-50
WHARFEDALE Linton	35-11	25-95

The following Turntables are complete with base, plinth, plastic cover and cartridge. Fully wired and ready for use. All at special prices.

GARRARD SP25 Mk. III with Goldring G800 Special Price 17-75

McDONALD MP80 with Goldring G800 Special Price 17-25

McDONALD MP60 with SHURE M 44/7 Special Price 18-25

McDONALD HT70 with Goldring G800 Special Price 24-25

GARRARD AP76 with Goldring G800 Special Price 25-95

GARRARD AP76 with Shure M55E Special Price 28-95

GARRARD AP76 with Shure M75EJ Special Price 31-25

GARRARD 2025TC with Sonotone 9TAHC Special Price 12-10

GOLDRING GL75 with G800 Special Price 36-95

GOODMANS TD100 with G800E 73-94 48-95

	Rec. Retail Price	Comet Price
SPEAKERS		
AKAI SW 155	70-95	50-95
AMSTRAD ACOUSTA 1500 (pair)	44-00	25-95
AMSTRAD ACOUSTA 2500 (pair)	55-00	32-95
AMSTRAD 138 (pair) Teak	28-60	15-50
B and W Model 70	175-45	125-95
B and W DM2	65-89	46-95
B and W DM4	46-75	35-95
B and W D5 (pair)	55-99	41-95
CELESTION COUNTY (pair)	46-13	34-50
Ditton 120 (pair)	52-80	37-95
Ditton 15	35-20	25-50
Ditton 25	71-50	51-95
Ditton 44	59-40	42-95
Ditton 66	100-90	78-75
Ditton 86	104-50	75-95
FERRROGRAPH S1 Inc. stand	46-33	34-95
Havant (pair)	53-77	38-50
Magister	72-19	46-75
Double Maxim (pair)	63-45	45-95
Mezzo 3	39-27	26-95
Magnum K2	60-50	41-95
Dimension 8	79-68	54-95
DIN 20 NT Kit (pair)	22-95	16-50
KELETRON KS4 (pair)	22-66	14-50
KS6 (pair)	28-16	17-95
KS8 (pair)	36-23	23-95
KS10 (pair)	44-68	30-50
KS15 (pair)	69-85	44-95
KS20 (pair)	78-76	50-95
LEAK 150 (pair)	46-82	35-95
LEAK 250 (pair)	60-85	46-50
LEAK 600	54-45	38-50
METRO SOUND HFS 103 (pair)	27-17	19-95
202	23-65	16-95
Diplex 15	35-20	26-95
Diplex 25	61-60	42-95
PIONEER CS53	51-39	34-95
SINCLAIR Q16	8-47	6-20
TANDBERG Tan 7	27-78	22-25
Tan 11 (pair)	37-66	29-95
TL 12 Teak (pair)	52-25	42-95
TL 25 Teak (pair)	67-32	55-50
TL 50 Teak	74-80	58-75
TELETON 8000 (pair)	19-87	11-50
THORPE GRENVILLE TG100 (pair)	31-85	25-50
TG200 (pair)	46-15	28-50
TG300 (pair)	61-55	34-50
WHARFEDALE Denton Mark II (pair)	39-32	27-50
Denton Mark II (pair)	48-68	34-50
Trilon III (pair)	60-85	42-50
Melton Mark II	38-50	26-95
Dovedale 3 Mark II	52-25	35-95
Rosedale	75-90	52-95
Unit 3 speaker kit (pair)	23-40	16-50
Unit 4 speaker kit (pair)	41-80	29-25
Unit 5 speaker kit (pair)	60-50	42-50
PICK UP ARMS AND HEADS		
AUDIO Technica AT 1005 Mk. II	17-85	12-95
AUDIO Technica L2 lifts	2-46	1-90
CONNOISSEUR SAU2	13-86	11-25
GOLDRING Lenco 75	13-20	8-95
GOLDRING Lenco L69	9-90	6-25
GOLDRING PH6 Head Shell for 69/75	2-81	
GOLDRING PH7 Head Shell for 85	3-47	2-40
GOLDRING PH8 Head Shell for 101	0-92	0-70
SME 3009 ser. 11 Improved	34-65	25-95
SME 3009-52 ser. 11 Improved	37-95	28-95
SME S2 Head Shell	2-77	1-90
CHASSIS SPEAKERS		
GOODMANS Twin-axiom 8	8-58	6-25
Twin Axium 10	9-47	6-90
Axiom 401	19-45	13-95
Axiom 8P	5-17	3-75
Axiom 10P	5-62	4-10
Axiom 12P	14-30	10-40
Axiom 15P	23-10	16-50
Axiom 18P	39-27	27-95
Axiom 100 40 watts din.	13-20	9-50
ARU 172	4-95	3-60
Axent 100	7-59	5-40
Midax 650	4-10	2-95
Attenuator	14-95	10-95
Crossover network XQ/950	8-55	5-95
WHARFEDALE 8 in. Bronze/RS/DD	4-44	3-20
Super 8/RS/DD	7-95	5-75
Super 10/RS/DD	13-11	9-45
CARTRIDGES		
AMSTRAD 900C	5-02	3-15
AMSTRAD 900D	7-63	4-75
AMSTRAD 900 EX	11-23	7-75
AUDIO TECHNICA AT 66	5-98	3-30
AUDIO TECHNICA AT 66	5-78	4-75
*CONNOISSEUR Ceramic SCU1	5-78	2-95
GOLDRING G850	Sp. price	3-75
GOLDRING G800	Sp. price	6-50
GOLDRING G800E	Sp. price	12-50
GOLDRING G800 Super E	11-00	7-50
GOLDRING G820	16-50	11-40
GOLDRING G820E	58-00	52-00
GOLDRING G820 Super E	52-50	37-95
EMPIRE 1000ZE/X	41-79	26-95
EMPIRE 999VEIX	24-58	16-25
EMPIRE 999TEIX	19-86	12-95

OVER 1000 ITEMS ALWAYS IN STOCK

All items brand new and fully Guaranteed and backed by after-sales service

— latest models in manufacturers' sealed cartons



COMET for after-Sales Service THROUGHOUT THE U.K.

Service Departments at Hull, Birmingham, Bridlington, Dagenham, Doncaster, Edinburgh, Eastleigh, Gool, Macclesfield, Hayes, Jarrow, Leeds, Leicester, Nottingham, Rotherham, Rochdale, Rochester, Sheffield, Telford, Wigan, with engineers covering York and Scarborough

	Rec. Price	Retail Price	Comet Price
CARTRIDGES SPEAKERS—cont.			
EMPIRE 999E/X	15.40	10.30	
EMPIRE 909E/X	12.03	7.95	
EMPIRE 90E/X		6.20	
SHURE M3DM	Sp. Price	3.60	
SHURE M44-G	Sp. Price	4.60	
SHURE M44-7	Sp. Price	4.20	
SHURE M-44C	Sp. Price	4.60	
SHURE M44E	Sp. Price	4.60	
SHURE M55E	Sp. Price	7.90	
SHURE M75G	Sp. Price	4.95	
SHURE M75-6 (S)	Sp. Price	7.10	
SHURE M75-6	Sp. Price	8.25	
SHURE M75EJ	Sp. Price	10.10	
SHURE M75EJ	Sp. Price	12.15	
SHURE M91E	Sp. Price	24.95	
SHURE V15-11	Sp. Price	3.53	1.30
SONOTONE 9TACH Diam/Saph Cartridges listed are magnetic—except those starred which are ceramic			

	Rec. Price	Retail Price	Comet Price
BASES AND COVERS			
CONNOISSEUR Plinth BD1	5.28	4.30	
CONNOISSEUR Cover	3.96	3.20	
CONNOISSEUR P.U. Mount Board	0.88	0.70	
GARRARD WB1 Base	3.56	2.70	
GARRARD WB4 Base	5.28	3.90	
GARRARD SPC1 Cover	3.47	3.00	
GARRARD SPC4 Cover	4.13	3.00	
Special Offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500			
	Sp. Price	2.50	
Special offer of base and cover to fit McDONALD MP60 and 610			
	Sp. Price	3.50	
GOLDRING Plinth 75	9.24	6.40	
GOLDRING Plinth 72	8.91	6.20	
GOLDRING Covers for 72P	4.46	3.10	
Cover for 75P De Luxe	4.95	3.40	
Cover for 85P	6.60	4.60	
THORENS TX 25 (for TD125AB)	8.25	6.40	
THORENS TX11 Cover	4.18	3.40	
SME Plinth System 2000 with motor-board			
	43.56	34.95	
MOTORBOARDS only			
	5.51	4.00	
SME P1 Spacer			
	0.92	0.70	

	Rec. Price	Retail Price	Comet Price
HEADPHONES			
AMSTRAD HPS5A	8.25	4.30	
HP56A with volume control	11.77	7.40	
HP5 7A bass and treble controls	15.35	10.90	
AKAI ASE9	7.98	4.70	
AKAI ASE22	13.09	7.95	
AKG K180	30.80	18.70	
AKG K60	16.50	9.90	
AKG 100	8.80	5.50	
AKG 120	11.00	4.95	
KOSS HV1	22.00	17.60	
KOSS ESP-9 Electrostatic	75.90	58.25	
KOSS ESP-6 Electrostatic	49.50	38.50	
KOSS K2 plus 2 Quadrafone	49.50	39.95	
KOSS PRO-5 LIC	33.00	26.50	
KOSS PRO-4AA	30.80	23.25	
KOSS KO-727B	18.15	13.75	
KOSS 747	22.00	16.50	
KOSS K-711	11.00	8.50	
KOSS K6	13.75	10.50	
KOSS K6/LC (with volume control)	15.40	11.95	
KOSS K6/CO Quadrafone	22.00	18.75	
PIONEER SE 50	24.09	14.50	
PIONEER SE 30A	13.86	9.25	
PIONEER SE 20A	8.67	5.50	
PIONEER SEL 20	11.58	7.50	
PIONEER SEL 40	19.17	12.50	
SOUND MD806	7.15	3.10	
WHARFEDALE DD1	13.75	9.75	
WHARFEDALE Isodynamic	21.95	16.50	

	Rec. Price	Retail Price	Comet Price
BLANK TAPES			
SCOTCH DYNARANGE CASSETTES			
C80	0.77	0.40	
C90	1.08	0.55	
C120	1.63	0.80	

	Rec. Price	Retail Price	Comet Price
BLANK TAPES—continued			
SCOTCH HIGH ENERGY COBALT CASSETTES			
C50	1.20	0.75	
C90	1.54	0.95	
SCOTCH CASSETTE HEAD			
CLEANER	0.61	0.40	
SCOTCH Low Noise 8-TRACK BLANK CARTRIDGES			
40 mins.	1.65	0.99	
30 mins.	1.98	1.20	
MAGCAM 8-track 80 mins.			
	Sp. Price	0.75	
SCOTCH Hi-Fi DYNARANGE SPOOLED TAPES			
5" L.P. 900	2.02	1.25	
5" L.P. 1200	2.37	1.45	
7" L.P. 1800	3.18	1.99	
SCOTCH Hi-Fi DYNARANGE DOUBLE PLAY			
5" D.P. 1200	3.41	1.55	
5" D.P. 1800	3.41	2.15	
7" D.P. 2400	4.37	2.75	
Postage—5p per order. Packs of ten post free.			

	Rec. Price	Retail Price	Comet Price
HI-FI STEREO SYSTEMS—COMPLETE			
BUSH A1005	66.25	47.95	
BUSH 1006 with radio	89.06	64.25	
DANSSETTE 4005	67.73	43.95	
DECCA SOUND 613	Sp. Price	47.50	
DECCA SOUND 614	Sp. Price	51.95	
DECCA COMPACT 2 with radio	Sp. Price	72.95	
DECCA 403	Sp. Price	40.95	
FERGUSON 3450 B with Radio (new Model)	75.35	55.95	
FERGUSON 3451 B with Radio (new Model)	101.42	75.95	
FERGUSON 3454	39.34	29.95	
FIDELITY UA1 Music Master with Radio			
	95.52	66.95	
FIDELITY UA2 Music Master			
	40.98	27.95	
FIDELITY Stereo Nine			
	Sp. Price	21.95	
FIDELITY UA3 incl. stereo radio			
	59.73	41.95	
	74.89	52.95	
GROSVENOR MPX 8400 AM/FM/MPX Tuner/Amplifier, magnetic player with speakers			
	65.75	36.95	
HMV 2451	115.64	85.95	
HMV 2452	62.57	47.95	
HMV 2455	165.89	122.95	
T.T. 1025 with 662 speakers and radio	45.72	33.95	
T.T. 2250 with 659 speakers and radio	136.98	99.95	
PHILIPS 808	99.53	69.95	
PHILIPS 825	46.92	32.95	
PHILIPS 826	71.09	49.95	
PHILIPS 835 with radio	65.88	46.50	
PHILIPS 836 with radio	90.05	63.50	
ULTRA 6027	54.50	40.95	
ULTRA 6028	56.83	42.50	
ULTRA 6450 B (new model) with radio	75.35	55.95	
ULTRA 6451	75.35	55.95	
ULTRA 6455	39.19	28.95	
ULTRA 6454	36.83	27.95	

	Rec. Price	Retail Price	Comet Price
TAPE RECORDERS			
AKAI 1721L	93.87	66.95	
AKAI 4000 DS	93.50	68.95	
AKAI X201D	168.30	123.95	
AKAI X1810	215.18	159.95	
AKAI GX221D	215.18	159.95	
AKAI GX1900D	224.57	166.95	
AKAI GX370D	328.95	244.95	
AKAI CR80D 8-track stereo tape deck	79.90	53.95	
AKAI CR80 8-track stereo recorder	117.02	66.95	
AKAI CR80DS Quadraphonic	149.88	109.95	
AKAI CR80T 8-track stereo recorder and tuner amplifier	140.78	84.95	

	Rec. Price	Retail Price	Comet Price
TAPE RECORDERS—continued			
AKAI CR81T 8-track cartridge stereo recorder and tuner amplifier	145.65	107.95	
AKAI CR81	102.89	75.95	
AKAI CR81D	84.10	61.95	
FERGUSON 3258 4-track	66.77	47.00	
FERROGRAPH 702/704 Dolby	267.30	226.95	
FERROGRAPH 702H Dolby	278.30	235.95	
FERROGRAPH 722/724 Dolby	305.80	258.95	
FERROGRAPH 725H Dolby	316.80	268.95	
FERROGRAPH 702/704	220.00	167.95	
FERROGRAPH 722/724	258.50	194.95	
FIDELITY Braemar 4-track	32.64	17.95	
GROSVENOR 8-track record, play-back deck	51.15	36.95	
GROSVENOR MPX 8400 AM/FM MPX Tuner/Amplifier, magnetic input, built-in 8-track cartridge player with speakers			
	65.75	36.95	
GRUNDIG TK 121 (twin-track)	53.09	37.95	
GRUNDIG TK 141 (4-track)	58.60	42.95	
GRUNDIG TK 147 (4-track auto)	92.87	69.95	
GRUNDIG TK 148 (4-track auto speed)	63.54	52.95	
GRUNDIG TK 246 4-track stereo deck	115.25	92.95	
GRUNDIG TK 3200 Hi-Fi (Battery)	135.15	94.75	
MARCONI 4248 4-track, 2 speed	49.66	33.00	
PHILIPS 4307 4-track	47.40	33.95	
PHILIPS 4308 De Luxe 4-track	55.92	39.95	
PHILIPS 4414 4-track stereo	113.75	77.95	
PHILIPS 4416 4-track stereo recorder	137.46	98.95	
PHILIPS 4418 4-track stereo	189.59	137.95	
PHILIPS 4450 4-track stereo	279.64	199.95	
TANDBERG 3341X 4-track stereo deck	122.11	102.95	
TANDBERG 6041X 4-track stereo	187.62	153.95	
TANDBERG 9021X 2-track stereo deck	216.20	182.95	
TANDBERG 9041X 4-track stereo deck	216.20	182.95	

	Rec. Price	Retail Price	Comet Price
TAPE RECORDERS (CASSETTE)			
AKAI CS35D tape deck	75.13	49.95	
AKAI CS35 Stereo incl. Speakers	105.71	77.95	
AKAI GXC 400 tape deck	89.74	65.95	
AKAI GXC 40	105.71	75.95	
AKAI GXC 40T recorder, tuner/amplifier	157.40	116.95	
AKAI GXC 45D tape deck	112.28	83.95	
AKAI GXC 46 Dolby tape recorder	143.30	106.95	
AKAI GXC 46D Dolby tape deck	131.09	96.95	
AKAI GXC 65D Dolby auto-reverse deck	145.18	107.95	
BUSH TP 66 Battery/Mains	26.70	19.50	
FERGUSON 3253 (mains)	41.15	25.00	
FERGUSON 3256 (mains)	36.60	22.50	
FERGUSON 3257	53.51	37.95	
FERGUSON 3257/7 speakers for above	15.15	11.25	
GEC CR200 AM/FM Cassette/Radio, Battery/Mains with slide controls			
	Sp. Price	32.95	
GRUNDIG C210 Battery/Mains			
	46.00	34.95	
HARVARD Elite Cassette/AM/FM Radio (battery/mains)			
	Sp. Price	21.50	
JVC Nivico 9420 LS with AM/FM radio, battery/mains			
	57.84	38.95	
JVC Nivico 1710 Radio/Cassette, AM/FM			
	Sp. Price	34.95	
PHILIPS 2202/2203	22.59	16.50	
PHILIPS 2204 battery/mains	28.25	21.95	
PHILIPS 2405 Stereo with 2 RH401 L/S	67.78	50.95	
PHILIPS 3302	20.24	14.95	
PIONEER CT 4141 Dolby Deck	143.97	98.95	
PYE 9116 Stereo	85.80	47.95	
PYE 9140	20.24	14.95	
WHARFEDALE Dolby DC9 Mk. II	111.41	82.50	

FREE Technical Advisory Service. If in doubt ask us! Price list on request. Comet guarantees that all prices quoted are genuine. All offers subject to availability. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) **OR, IF SECURICOR DELIVERY REQUIRED add £1.95 only.** Make cheques, Money Orders payable to 'COMET'.

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

OPEN DAILY TO THE PUBLIC FROM:
9am-4pm Monday
9am-1pm Tuesday
9am-4pm Wednesday
9am-4pm Thursday
9am-4pm Friday
9am-3.30pm Saturday

- BIRMINGHAM: Heeley Road, Selly Oak, B29 6EY. Tel: 021-472 6181
- BIRMINGHAM: Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley B26 1BJ. Tel: 021-706 0684
- LONDON, DAGENHAM: Rainham Road South, Dagenham, RM10 8ST. Tel: 01-595 5111
- EDINBURGH: 1 Newhaven Road, EH6 5QX. Tel: 031-554 4454 (9 lines)
- LEEDS: Reservoir Road, Clough Road, HU6 7QD. Tel: 0482 46441 (6 lines)
- HULL: 78 Armley Road, LS12 2EF. Tel: 0532 40551
- SHEFFIELD: The Mill, 1 Loxley Road, Main Bridge, S6 4TN. Tel: 0742 341721/6
- STOCKTON: Teesway, Portrack Lane, Teesside, TS18 2RH. Tel: 66132/65215
- ROCHDALE: Corner of Well Lane and Queensway. Tel: 50606
- LEICESTER: Syston Street. Tel: 0533 52236
- WIGAN: Wharf Mill, Princess Street, WN3 4EZ. Tel: 0942 34741
- LONDON, HACKBIDGE (Nr. Croydon): 190 London Road, Hackbridge, Wallington, Surrey. Tel: 01-669 0271
- SUNDERLAND: 4-7 St. Thomas Street, Sunderland, SR1 1HR. Tel: Sunderland 59993
- RENFREW: Blythswood Trading Estate, Argyle Avenue, Renfrew, RA4 9EL. Tel: 041 886 5731
- JARROW: 56/64 Ellison Street, Jarrow, NE32 3MT. Tel: 0632 892211
- LONDON, HAYES: Silverdale Road, Pump Lane, Hayes. Tel: 01-573 1841
- SANDIACRE: 121 Town Street, Sandiacre, Nottingham, NG10 5DW. Tel: Sandiacre 6116
- EASTLEIGH: Chickenhall Lane, Eastleigh, SO5 5ZQ. Tel: Eastleigh 4722
- LONDON, ROCHESTER: Maidstone Road, Rochester. Tel: Medway 49171

SECURICOR
 SPECIAL DELIVERY SERVICE
 All in-stock items delivered by SECURICOR within 72 hours.
 (Add £1.95 only for Securicor delivery)
 ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILE IN TRANSIT

Would you spend an hour a day to earn more money in Electronics- Television-Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and our wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics - in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments).

With ICS you study at home - at your own pace, when you choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

ICS your key to the door
of opportunity

Tick or state subject of interest and post to:
International Correspondence Schools, Dept. 23211,
Intertext House, Stewarts Road, London SW8 4UJ.

Subject of interest _____

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name _____

Address _____

Occupation _____

Age _____

Accredited by the Council for the Accreditation of Correspondence Colleges



ELECTRONIC ORGAN KITS

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT, ELECTRICAL HOUSEHOLD APPLIANCES AND MUSICAL INSTRUMENTS.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE ROAD, LONDON, S.W.18
TEL: 01-870 4949

NEW VALVES! GUARANTEED AND TESTED 24-HOUR SERVICE

1R5	25	30P19	53	ECC82	17	EL33	54	PCF86	44	PY801	80
1R5	21	30PL1	54	ECC83	21	EL41	52	PCF801	27	R19	27
1T4	14	DAF91	21	ECC85	31	EL84	20	PCF802	28	U191	54
2R4	24	DAF96	35	ECH35	48	EM80	35	PCF805	55	U251	60
3V4	46	DF91	14	ECH42	58	EM81	35	PCL82	28	U329	65
6/30L2	53	DF96	35	ECH81	26	EM84	30	PCL83	53	U801	73
6AT6	18	DH77	15	ECL80	27	EY86	27	PCL84	31	UABC80	29
6AQ5	21	DK91	25	ECL82	27	EZ80	19	PCL85	38	UBF89	28
6BW7	48	DK96	43	ECL86	32	EZ81	21	PCL86	35	UCC85	32
6F1	57	DL92	24	EF29	36	KT61	54	PL200	49	UCH42	58
6F23	64	DL94	46	EF41	58	KT66	75	PL36	45	UCH81	28
6F25	49	DL96	38	EF80	22	N78	£1.00	PL81	41	UCL82	30
12AU7	17	DY86	21	EF55	26	PC86	42	PL82	29	UF41	49
25L6GT	18	DY87	21	EF86	27	PC88	42	PL83	31	UF89	28
30C15	58	DY802	28	EF89	24	PC97	38	PL84	28	UL41	52
30C17	73	EABC80	28	EF91	12	PC900	28	PL500	59	UL84	27
30C18	55	EBC33	38	EF92	26	PCC84	27	PL504	59	UY41	37
30F5	60	EBC41	47	EF183	25	PCC89	41	PY81	23	UY85	22
30FL1	59	EBF89	27	EF184	27	PCC189	46	PY82	23	WX7	42
30FL14	67	ECC81	15	EH90	33	PCF80	25	PY800	30	Z77	18

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no callers.

GERALD BERNARD 83 Osbaldeston Road,
Stoke Newington, London N.16

poly-planar

20-Watt Full Range Speaker

Completely replaces the
conventional cone speaker
Super-thin construction
permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance:
8 ohms. Operating temperature range: -20°F to +175°F. Size
(WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£6.50 each Stereo pair £12.50
post free

web europa

P.O. Box 162, Watford WD1 1AA



Build yourself a TRANSISTOR RADIO

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 33p extra.

Total building cost

£9.35

P. P. & Ins. 52p

(Overseas P. & P. £1.05)



ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL




7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9" x 7" x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 33p extra.

Total building cost **£7.68** P. P. & Ins. 47p.
(Overseas P. & P. £1.05)

ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9" x 7" x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 33p extra.

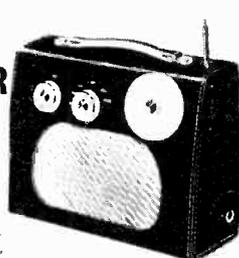
Total building costs **£6.58** P. P. & Ins. 47p.
(Overseas P. & P. £1.05)



ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9" x 5 1/2" x 2 1/2in. approx. Easy build plans and parts price list 25p (FREE with parts).

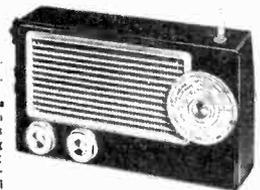Total building costs **£4.38** P. P. & Ins. 31p
(Overseas P. & P. £1.05)



POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes. Super-sensitive ferrite rod aerial. Fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2.50** P. P. & Ins. 24p
(Overseas P. & P. 65p)



TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning, condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2" x 4 1/2" x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2.75** P. P. & Ins. 25p
(Overseas P. & P. 65p)




TRANS EIGHT

8 TRANSISTORS AND 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9" x 5 1/2" x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

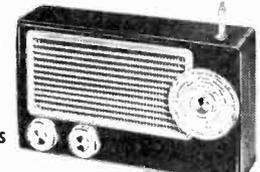Total building costs **£4.95** P. P. & Ins. 33p
(Overseas P. & P. £1.05)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY TO FOLLOW DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets. Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.
Parts price list and easy build plans 25p (FREE with parts).

All parts including Case and Plans **£6.05** P. P. & Ins. 33p

(Overseas P. & P. £1.05)

RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367
Reg. no. 788372

I enclose £ _____ please send items marked.

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for _____

Name _____

Address _____

FULL AFTER SALES SERVICE

* Callers side entrance "Lavelis" Shop
* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.
PLEASE NOTE: ALL PRICES NOW INCLUDE VAT

PW 53

ESSENTIAL BOOKS FOR RADIO AMATEURS

New Edition A GUIDE TO AMATEUR RADIO

by Pat Hawker
G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.
90p post paid

New Book TELEVISION INTERFERENCE MANUAL

by B. Priestley
G3JGO

The causes of interference to TV receivers are examined, and ways in which they can be overcome are suggested in this latest RSGB publication.
90p post paid

RAE MANUAL

by G. L. Benbow
G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination.
90p post paid

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's UK origin ensures easy availability of components. Complete coverage of technical and constructional fields.
£4.10 post paid

These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send s.a.e. for complete list

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 4V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. £0.40.

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £14.40 plus P. & P.

INTERCOM BABY ALARM



OUR PRICE ONLY £3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 14p. P. & P. £0.25.

TELEPHONE AMPLIFIER



£2.99

Why not boost business efficiency with this incredible De-Juxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.5)
160 KENSINGTON HIGH STREET, LONDON, W.8.

EX COMPUTER PRINTED CIRCUIT PANELS

2 x 4 in. packed with semi-conductors and top quality resistors, capacitors, diodes etc. Our price 10 boards 50p (8p). With a guaranteed min. of 35 transistors—data included.

SPECIAL BARGAIN PACK

25 boards for £1 (25p).

ELECTROLYTICS

10,000µ 75v, 68,000µ 16v, 10,000µ 35v, 4½ x 2½ in. dia., 25,000µ 25v, 20,000µ 30v, 8,000µ 55v, 40,000µ 10v, 4½ x 3 in. dia. 50p (12p). 15,000µ 15v, 4½ x 2 in. dia. 20p (10p). 2,000µ 25v wire ended, 3 x 1 in. dia. 15p (5p) or 12 for £1.50 (15p).

250 MIXED CAPACITORS 60p (8p)

250 MIXED RESISTORS 60p (8p)

200 SI PLANAR DIODES 50p (5p) untested

SUB. MIN. CO-AX PLUGS & SKTS. 4 pairs 50p (5p)

MINIATURE GLASS NEONS 12 for 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES, MIXED 8 for 50p (8p)

PAPST EXTRACTOR/BLOWER FANS 100 cfm 4½ x 4½ x 2 £3.50 (28p)

QUARTZ HALOGEN BULBS 12v 55w 50p (5p)

Postage and package for each item shown in brackets.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8.

01-478 8499

SAVE TIME AND MONEY

LIST PRICE £6.25 | OUR PRICE £4.84

PLUS V.A.T.



As supplied by us to SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21½" x 11½" x 6½". Size of drawers 6½" x 2½" x 1½". Other sizes available. Callers welcome Mon.-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. NEW as illustrated OUR PRICE ONLY £4.84 plus 35p carriage on orders less than £10. Money back guarantee. SEND FOR FREE LISTS.

TRADE AIDS

(DEPT. PW10), 111 CHILTERN DRIVE,
BERRYLANDS, SURBITON, SURREY

01-399 4383

100 yds. Berrylands Railway Station.

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p
AC107	22	AD161	36†	BC146	40†	BD133	71†	BF182	44	MAT120	21	2G308	38†	2N2148	62†
AC113	22	AD162	36†	BC147	11	BD135	44	BF183	44	MAT121	22	2G309	38†	2N2160	66
AC115	25†	AD161	&	BC148	11	BD136	44	BF184	27†	MPF102	46	2G333	22	2N2192	38†
AC117K	22	AD162	(MP)	BC149	13	BD137	40†	BF185	33	MPF104	40†	2G339A	17†	2N2194	38†
AC122	13	ADT140	60†	BC150	20	BD138	55	BF186	44	MPF105	40†	2G344	20	2N2194	38†
AC125	18†	AF114	28†	BC151	22	BD139	60†	BF194	13	OC19	38†	2Q345	17†	2N2217	24
AC126	18†	AF114	28†	BC152	18†	BD140	66	BF195	13	OC20	69†	2G371	17†	2N2218	22
AC127	18†	AF115	26†	BC153	31	BD155	88	BF196	15†	OC22	42	2G371B	13	2N2219	22
AC128	18†	AF116	26†	BC154	33	BD175	66	BF197	15†	OC23	46	2G373	18†	2N2220	24
AC132	15†	AF117	28†	BC157	20	BD176	66	BF200	49†	OC24	41	2G374	18†	2N2221	24
AC134	15†	AF118	38†	BC158	13	BD177	71†	BF202	104†	OC25	42	2G377	33	2N2222	22
AC137	15†	AF124	33	BC159	13	BD178	71†	BF207	49†	OC26	27†	2G378	17†	2N2268	18†
AC141	15†	AF125	27†	BC160	49†	BD179	77	BF258	66	OC28	55	2G381	17†	2N2269	15†
AC141K	18†	AF126	31	BC161	55	BD190	77	BF269	93†	OC29	55	2G382	17†	2N2269A	15†
AC142	15†	AF127	31	BC167	13	BD185	71†	BF282	60†	OC35	46	2G401	33	2N2411	26†
AC142K	18†	AF139	33	BC168	13	BD186	71†	BF283	60†	OC36	55	2G414	33	2N2412	26†
AC151	16†	AF178	33	BC169	13	BD187	77	BF270	38†	OC41	22	2G417	27†	2N2446	51†
AC154	22	AF179	55	BC170	13	BD188	77	BF271	38†	OC42	26†	2N388	38†	2N2711	23
AC156	22	AF180	55	BC172	15†	BD199	82†	BF272	38†	OC44	16†	2N388A	60†	2N2712	23
AC157	26†	AF186	49†	BC173	15†	BD195	93†	BF274	38†	OC45	14	2N404	22	2N2713	23
AC165	22	AF239	40†	BC174	15†	BD196	93†	BF275	38†	OC70	11	2N404A	31	2M2904	18†
AC166	22	AL102	71†	BC175	24	BD197	99	BF279	66	OC71	11	2N524	46	2N2904A	23
AC167	22	AL103	71†	BC177	21	BD198	99	BF289	24	OC72	15†	2N527	54	2N2905	22
AC168	26†	AS726	27†	BC178	21	BD199	104†	BF292	33	OC74	18†	2N588	46	2N2906A	23
AC169	15†	AS727	33	BC179	21	BD200	104†	BF293	33	OC75	16†	2N589	49†	2N2906	16†
AC178	22	AS728	27†	BC180	26†	BD205	88	BF287	26†	OC76	16†	2N696	14	2N2906A	20
AC177	26†	AS729	27†	BC181	26†	BD206	88	BF288	26†	OC77	27†	2N697	14	2N2907	22
AC178	31	AS750	27†	BC182	11	BD207	104†	BF290	22	OC81	16†	2N698	26†	2N2907A	24
AC179	31	AS751	27†	BC182L	11	BD208	104†	BF291	22	OC81D	16†	2N699	38†	2N2923	15†
AC180	18†	AS752	27†	BC183	11	BD209	110	BF292	22	OC82	16†	2N706	9	2N2924	15†
AC180K	22	AS754	27†	BC183L	11	BD215	99	BF293	22	OC82D	16†	2N706A	10	2N2925	15†
AC181	18†	AS755	27†	BC184	13	BF17	49†	BF295	16†	OC83	22	2N707	13	2N2926	14
AC181K	22	AS756	27†	BC184L	13	BF18	77	BF296	16†	OC84	22	2N711	33	2N2926(Y)	12
AC187	24	AS757	27†	BC186	31	BF19	77	BF297	16†	OC89	22	2N713	38†	2N2926(B)	11
AC187K	22	AS758	27†	BC187	31	BF121	49†	BF298	16†	OC139	22	2N718	26†	2N2926(R)	11
AC188	24	AS721	44	BC207	12	BF123	55	BF299	16†	OC140	22	2N718A	55	2N2926(D)	11
AC188K	22	BC107	10	BC208	12	BF125	49†	BF300	16†	OC170	27†	2N725	31	2N3010	77
AC197	27†	BC108	10	BC209	11	BF127	49†	BF301	16†	OC171	27†	2N727	31	2N3011	15†
AC198	22	BC109	11	BC212L	12	BF152	60†	BF302	16†	OC172	27†	2N743	22	2N4058	30
AC199	22	BC113	11	BC218L	12	BF153	49†	BF303	20	OC201	31	2N744	22		
AC200	22	BC114	16†	BC214L	15†	BF154	49†	BF304	20	OC202	31	2N914	15†	AAL19	9
AC201	22	BC115	16†	BC225	27†	BF155	77	BF305	20	OC203	27†	2N915	33	AA120	9
AC202	17†	BC116	16†	BC226	38†	BF156	53	BF306	20	OC204	27†	2N929	23	AA129	9
AC207	19†	BC117	16†	BCY30	28†	BF157	60†	BF307	20	OC205	38†	2N930	23	AA230	10
AC208	21	BC118	11	BCY31	28†	BF158	60†	BF308	14	OC209	44	2N131	22	AA231	11
AC209	38†	BC119	33	BCY32	33	BF159	66	BF309A	14	OC271	47†	2N132	24	AA300	11
ACY30	31	BC120	88	BCY33	24	BF160	44	BU105	22	ORP12	47†	2N1302	15†	BA116	23
ACY31	31	BC125	13	BCY34	27†	BF162	44	BU11E	55	ORP60	44	2N1303	15†	BA126	24
ACY34	23	BC126	20	BCY70	15†	BF163	44	C400	33	ORP61	44	2N1304	18†	BA148	15†
ACY35	23	BC132	13	BCY71	20	BF164	44	C407	27†	P346A	22	2N1305	18†	BA154	15†
ACY36	31	BC134	20	BCY72	15†	BF165	44	C424	22	P397	46	2N1306	23	BA155	15†
ACY40	18†	BC135	13	BCZ0	22	BF167	34	C425	55	ST140	14	2N1307	23	CG2	14
ACY41	38†	BC136	16†	BCZ1	27†	BF173	24	C426	38†	ST141	18†	2N1308	25†	BY100	16
ACY44	38†	BC137	16†	BCZ11	27†	BF176	38†	C428	22	TI843	33	2N1309	25†	BY101	13
AD130	42	BC139	44	BD121	66	BF177	38†	C441	33	UT46	30	2N1613	22	BY105	18†
AD140	53	BC140	33	BD123	71†	BF178	33	C442	33	2G301	21	2N1711	22	BY114	18
AD142	53	BC141	33	BD124	66	BF179	33	C444	38†	2G302	21	2N1889	35	BY126	15
AD143	42	BC142	33	BD131	55	BF180	33	C450	24	2G303	21	2N1890	49†	BY127	16†
AD149	55	BC143	33	BD132	66	BF181	33	MAT100	22	2G304	26†	2N1893	40†	BY128	16
								MAT101	22	2G306	44	2N2147	79	BY130	17†

Cut these 3 pages out and keep for reference

DIODES AND RECTIFIERS

9	BY133	23	OA70	7†
9	BY164	55	OA79	7†
6	BYX38/30	46	OA81	7†
10	BYZ10	38†	OA85	10
33	BYZ11	33	OA90	6†
33	BYZ12	33	OA91	6†
27	BYZ13	27†	OA95	7†
44	BYZ17	44	OA200	6†
38†	BYZ18	38†	OA202	7†
31	BYZ19	31	SD19	5†
31	CG2	31	IN34	7†
5†	(OA91 Eq.)	5†	IN34A	7†
6†	CG651	6†	IN914	6†
6†	(OA70-OA79 Eq.)	6†	IN916	6†
5†	OA5	5†	IN414B	6†
25	OA55L	25	18021	11
16	OA10	16	18951	6†
17†	OA47	17†		

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. count by weight	0-55
C 2	200	Capacitors mixed values approx. count by weight	0-55
C 3	50	Precision Resistors -1%, -01% mixed values	0-55
C 4	75	1/4 W Resistors mixed preferred values	0-55
C 5	5	Pieces assorted Ferrite Rods	0-55
C 6	2	Tuning Gangs, MW/LW VHF	0-55
C 7	1	Pack Wire 50 metres assorted colours	0-55
C 8	10	Reed Switches	0-55
C 9	3	Micro Switches	0-55
C10	15	Assorted Pots & Pre-Sets	0-55
C11	5	Jack Sockets 3 x 3.5m 2 x Standard Switch Types	0-55
C12	40	Paper Condensers preferred types mixed values	0-55
C13	20	Electrolytics Trans. types	0-55
C14	1	Pack assorted Hardware - Nuts/Bolts, Grommets etc.	0-55
C15	4	Mains Toggle Switches, 2 Amp D/P	0-55
C16	20	Assorted Tag Strips & Panels	0-55
C17	10	Assorted Control Knobs	0-55
C18	4	Rotary Wave Change Switches	0-55
C19	3	Relays 6-24V Operating	0-55
C20	4	Sheets Copper Laminate approx. 10" x 7"	0-55

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19 & C20.

Component Lists for mail order available on request

JUMBO COMPONENT PAKS MIXED ELECTRONIC COMPONENTS

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 30 items in weight. Price incl. P. & P. 21.65 only.



BRAND NEW POST OFFICE TYPE TELEPHONE DIALS
ONLY 83p each

THE NEW S.G.S. EA 1000 AUDIO AMP MODULE *Guarantee

3 Watts R.M.S. ONLY £2.89 each

Module Tested and Guaranteed.
Qty. 1-9 £2.89; 10-25 £2.50 Price each. Larger quantities quoted on request. Full book-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

SYSTEM 12 STEREO

Each Kit contains two Amplifier Modules, 3 watts RMS, two loudspeakers, 15 ohms, the pre-amplifier, transformer, power supply module, front panel and other accessories, as well as an illustrated stage-by-stage instruction booklet designed for the beginner.

ONLY £18.64 FREE P. & P.

NOW-TURN OVER FOR MORE FANTASTIC OFFERS

The largest selection

NEW LOW PRICED TESTED S.C.R.'s

PIV 1A	5A	5A	7A	10A	18A	30A
T05 T06 T07 T08 T09 T10 T11 T12 T13 T14 T15 T16 T17 T18 T19 T20 T21 T22 T23 T24 T25 T26 T27 T28 T29 T30 T31 T32 T33 T34 T35 T36 T37 T38 T39 T40 T41 T42 T43 T44 T45 T46 T47 T48 T49 T50						
50	0.26	0.28	0.39	0.39	0.52	0.55
100	0.28	0.37	0.52	0.52	0.55	0.64
200	0.39	0.41	0.64	0.54	0.63	0.87
400	0.48	0.62	0.62	0.74	0.83	1.19
600	0.59	0.63	0.75	0.75	0.85	1.07
800	0.70	0.77	0.88	0.88	0.99	1.32
1000	0.70	0.77	0.88	0.88	0.99	1.32

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.06	0.06	0.08	0.16	0.23	0.66
100	0.04	0.07	0.06	0.15	0.18	0.26	0.83
200	0.06	0.10	0.07	0.16	0.22	0.27	1.10
400	0.07	0.15	0.08	0.22	0.30	0.41	1.38
600	0.08	0.18	0.11	0.25	0.38	0.50	2.05
800	0.11	0.19	0.12	0.28	0.41	0.51	2.20
1000	0.12	0.28	0.16	0.33	0.51	0.70	2.75
1200	—	0.37	—	0.42	0.63	0.83	—

TRIACS		
VBO	2A	6A 10A
TO-5 TO-66 TO-48		
2p	2p	2p
100	83	55 82½
200	85	86 99
400	77	82½ 1.21

DIACS
FOR USE WITH TRIACS
BR100 (D32) 40p each

FREE
One 50p Pak of your own choice free with orders valued £4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1374 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G417 AF117

All 55p each pak

D1699 NPN SILICON DUAL TRANSISTOR
(Similar to 2N2060)
1 25 100+
0.27 0.25 0.23

ND 180 NIXIE DRIVER TRANSISTOR
Suitable replacement for BSX 21, C 407, 2N 1893 120vcb.
1 25 100+
0.18 0.16 0.15

Sil. trans suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 51p each. Any Qty

GP 100 TO3 METAL CASE GERMANIUM
V_{beo}=80V. V_{ceo}=50V. I_C=10 amps. P_{tot}=30W. h_{fe}=30-170.
Replaces the majority of Germanium power transistors in the OC, AD and NKT range.
1 25 100+
0.47 0.44 0.39

GP 300 TO3 METAL CASE SILICON
V_{beo}=100V. V_{ceo}=60V. I_C=15 amps. P_{tot}=115W. h_{fe}=20. 100T. =1MHz. Suitable replacement for 2N 3055, BDY 11 or BDY 20.
1 25 100+
0.55 0.58 0.50

2N3055
115 WATT SIL PWR NPN 55p EACH

ADI61/162 PNP M/P COMP GERM TRANS.
OUR LOWEST PRICE OF 80p PER PAIR

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-33V. 400mV (DO-7 Case) 15p ea. 1½W (Top Hat) 25p ea. 10W (SO-10 Stud) 35p ea.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each

50 AMP. BRIDGE RECTS.
2.5V RMS 35p each
100V RMS 40p ..
400V RMS 50p ..
Size 16 mm x 16 mm.

UT 46 UNJUNCTION TRANSISTORS
Direct replacement for TR18 43rand BEN 3000 also electrically equivalent to 2N2646 Ep
1 25 100+
0.30 0.27 0.22

CADMIUM CELLS
ORP12 47p
ORP60, ORP61 44p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N708/8. BSY-27/28/85A. All usable devices up open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.
20 For 0.55
50 For 1.10
100 For 1.92
500 For 8.25
1000 For 14.30

SIL. G.P. DIODES 2p
300mW 30 0.55
40PIV(Min.) 100 1.65
Sub-Min. 500 8.50
Full Tested 1,000 9.90
Ideal for Organ Builders.

R 2400 TO3 NPN SILICON HIGH VOLTAGE
V_{beo}=250V. V_{ceo}=100V. I_C=6 amps. P_{tot}=30W. h_{fe}=typ.20 IT=5MHz.
1 25 100+
0.55 0.49 0.44

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	5p
U 2	60 Mixed Germanium Transistors AF/RF	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.55
U 4	40 Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 Sil. Planar Trans. NPN like B8795A, 2N706	0.55
U 7	18 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0.55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.55
U 10	20 BAY50 charge storage Diodes DO-7 Glass	0.55
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.55
U 12	12 Silicon Rectifiers Epoxy 600mA up to 800 PIV	0.55
U 13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0.55
U 14	150 Mixed Silicon and Germanium Diodes	0.55
U 15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.55
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000V PIV	0.55
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.55
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.55
U 19	25 Silicon NPN Transistors like BC108	0.55
U 20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0.55
U 23	30 MADD'S like MHz Series PNP Transistors	0.55
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 390 PIV	0.55
U 25	25 300 MHz NPN Silicon Transistors 2N708, B8Y27	0.55
U 26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U 27	12 NPN Germanium AF Transistors TO-18 like AC127	0.55
U 29	10 1 Amp BCR's TO-5 can, up to 600 PIV CIR1/25-800	1.10
U 30	15 Plastic Silicon Planar Trans. NPN 2N2924	0.55
U 31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0.55
U 32	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0.55
U 33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.55
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0.55
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.55
U 36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.55
U 37	30 Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0.55
U 38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.55
U 39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0.55
U 40	10 Dual Transistors 8 lead TO-5 2N2060	0.55
U 41	25 RF Germanium Transistors TO-1, OC45, NKT72	0.55
U 42	10 VHF Germanium PNP Transistors TO-1 NKT867, AF117	0.55
U 43	25 Sil. Trans. Plastic TO-18 AF. BC113/114	0.55
U 44	20 Sil. Trans. Plastic TO-5 BC115/116	0.55
U 45	7 3A SCR. TO66 up to 600PIV	1.10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP x25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1.24 25 99 100 up Price each 49p 44p 89p

F.E.T.'S
2N3819 31p 2N5468 35p
2N3820 55p 2N5459 44p
2N3821 89p BFW10 66p
2N3823 31p MPP105 41p

NEW 6th EDITION
TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each.

LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

BIP 19/20 TO3 NPN PLASTIC SILICON
V_{beo}=100V. V_{ceo}=50V I_C=10 amps. P_{tot}=60W. h_{fe}=typ. 100 IT=3MHz BIP 19/20 Matched Pair.
1 25 100+ 1 25 100+
0.37 0.35 0.32 0.88 0.80 0.55

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0.55
Q2	16 White spot R.F. transistors PNP	0.55
Q3	4 OC 77 type transistors	0.55
Q4	6 Matched transistors OC44/45/81/81D	0.55
Q5	4 OC 75 transistors A.F. B. P. coded.	0.55
Q6	5 OC 72 transistors	0.55
Q7	4 AC 128 transistors PNP high gain.	0.55
Q8	4 AC 126 transistors PNP	0.55
Q9	7 OC 81 type transistors	0.55
Q10	7 OC 71 type transistors	0.55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0.55
Q12	3 AF 116 type transistors	0.55
Q13	3 AF 117 type transistors	0.55
Q14	3 OC 171 H.F. type transistors	0.55
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0.55
Q16	2 GET860 low noise Germanium transistors	0.55
Q17	5 NPN 2 x ST.141 & 3 x ST.140.	0.55
Q18	4 MADD'S 2 x MAT 100 & 2 x MAT 120	0.55
Q19	3 MADD'S 2 x MAT 101 & 1 x MAT 121	0.55
Q20	4 OC 44 Germanium transistors A.F.	0.55
Q21	4 AC 127 NPN Germanium transistors	0.55
Q22	2 NKT transistors A.F. B. P. coded.	0.55
Q23	10 OA 202 Silicon diodes sub-min.	0.55
Q24	8 OA 81 diodes	0.55
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.55
Q26	8 OA95 Germanium diodes sub-min IN89	0.55
Q27	2 10A PIV Silicon rectifiers IB425B	0.55
Q28	2 Silicon power rectifiers BYZ 13	0.55
Q29	4 Silicon transistors 2 x 2N698, 1 x 2N697, 1 x 2N698	0.55
Q30	7 Silicon switch transistors 2N706 NPN	0.55
Q31	6 Silicon switch transistors 2N708 NPN	0.55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.55
Q33	3 Silicon NPN transistors 2N1711	0.55
Q34	7 Silicon NPN transistors 2N2989, 500MHz (code P397)	0.55
Q35	3 Silicon PNP TO-5. 2 x 2N2904 & 2N 2905	0.55
Q36	7 2N3646 TO-18 plastic 500 MHz NPN	0.55
Q37	3 2N3053 NPN Silicon transistors	0.55
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0.55

ELECTRONIC SLIDE-RULE
The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and f of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and e Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. Must for every electronic engineer and enthusiast. Size: 2 cm x 4cm. Complete with case and instructions. Price each: £3.68

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC09	-12 x 7400	0.55	UIC46	-5 x 7448	0.55	UIC86	-5 x 7486	0.55
UIC01	-12 x 7401	0.55	UIC47	-5 x 7447	0.55	UIC90	-5 x 7480	0.55
UIC02	-12 x 7402	0.55	UIC48	-5 x 7448	0.55	UIC91	-5 x 7491	0.55
UIC03	-12 x 7403	0.55	UIC50	-12 x 7480	0.55	UIC92	-5 x 7492	0.55
UIC04	-12 x 7404	0.55	UIC51	-12 x 7481	0.55	UIC93	-5 x 7493	0.55
UIC05	-12 x 7405	0.55	UIC53	-12 x 7483	0.55	UIC94	-5 x 7494	0.55
UIC06	-8 x 7406	0.55	UIC54	-12 x 7484	0.55	UIC95	-5 x 7495	0.55
UIC07	-8 x 7407	0.55	UIC60	-12 x 7480	0.55	UIC96	-5 x 7496	0.55
UIC10	-12 x 7410	0.55	UIC70	-8 x 7470	0.55	UIC100	-5 x 74100	0.55
UIC13	-8 x 7413	0.55	UIC72	-8 x 7472	0.55	UIC121	-5 x 74121	0.55
UIC20	-12 x 7420	0.55	UIC73	-8 x 7473	0.55	UIC141	-5 x 74141	0.55
UIC30	-12 x 7430	0.55	UIC74	-8 x 7474	0.55	UIC181	-5 x 74181	0.55
UIC40	-12 x 7440	0.55	UIC75	-8 x 7475	0.55	UIC184	-5 x 74184	0.55
UIC41	-5 x 7441	0.55	UIC76	-8 x 7476	0.55	UIC193	-5 x 74193	0.55
UIC42	-5 x 7442	0.55	UIC80	-5 x 7480	0.55	UIC196	-5 x 74196	0.55
UIC43	-5 x 7443	0.55	UIC81	-5 x 7481	0.55	UIC199	-5 x 74199	0.55
UIC44	-5 x 7444	0.55	UIC82	-5 x 7482	0.55	UICXI	-25 Assorted	
UIC45	-5 x 7445	0.55	UIC83	-5 x 7483	0.55			74's 1-68

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES— 18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593.

OPEN MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.

Please add 10p postage and packing per order. Cash with order please. Orders to BI-PAK SEMICONDUCTORS, P.O. BOX 6, WARE, HERTS.

- the lowest prices!

74 Series T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

	1	25	100+	1	25	100+		1	25	100+	
SN7400	0.17	0.16	0.13	SN7450	0.17	0.16	0.13	SN74141	0.74	0.71	0.64
SN7401	0.17	0.16	0.13	SN7451	0.17	0.16	0.13	SN74145	21.65	21.54	21.43
SN7402	0.17	0.16	0.13	SN7453	0.17	0.16	0.13	SN74150	23.30	23.07	22.75
SN7403	0.17	0.16	0.13	SN7454	0.17	0.16	0.13	SN74151	21.10	21.05	0.99
SN7404	0.17	0.16	0.13	SN7460	0.17	0.16	0.13	SN74153	21.32	21.21	21.05
SN7405	0.17	0.16	0.13	SN7470	0.32	0.29	0.27	SN74154	21.98	21.87	21.76
SN7406	0.39	0.34	0.31	SN7472	0.32	0.29	0.27	SN74155	21.54	21.43	21.32
SN7407	0.39	0.34	0.31	SN7473	0.41	0.39	0.36	SN74156	21.54	21.43	21.32
SN7408	0.20	0.19	0.18	SN7474	0.41	0.39	0.36	SN74157	22.09	21.98	21.87
SN7409	0.20	0.19	0.18	SN7475	0.50	0.48	0.46	SN74160	21.98	21.87	21.76
SN7410	0.17	0.16	0.13	SN7476	0.41	0.39	0.36	SN74161	21.98	21.87	21.76
SN7411	0.28	0.27	0.26	SN7480	0.74	0.71	0.64	SN74162	24.40	24.13	23.85
SN7412	0.39	0.34	0.31	SN7481	21.32	21.27	21.21	SN74163	24.40	24.13	23.85
SN7413	0.32	0.29	0.27	SN7482	0.96	0.95	0.94	SN74164	22.43	22.37	22.31
SN7416	0.48	0.44	0.42	SN7483	21.21	21.16	21.08	SN74165	22.43	22.37	22.31
SN7417	0.48	0.44	0.42	SN7484	21.10	21.05	0.99	SN74166	22.85	22.85	23.30
SN7420	0.17	0.16	0.13	SN7485	23.98	23.85	23.74	SN74174	22.53	22.42	22.31
SN7422	0.55	0.53	0.50	SN7486	0.85	0.82	0.82	SN74175	21.76	21.65	21.54
SN7423	0.55	0.53	0.50	SN7489	26.05	25.78	25.50	SN74176	22.75	22.64	22.53
SN7425	0.55	0.53	0.50	SN7490	0.74	0.71	0.64	SN74180	22.20	21.76	21.54
SN7426	0.50	0.46	0.44	SN7491	21.10	21.05	0.99	SN74181	26.05	25.50	25.23
SN7427	0.50	0.46	0.44	SN7492	0.74	0.71	0.64	SN74182	22.20	21.98	21.76
SN7428	0.77	0.72	0.68	SN7493	0.74	0.71	0.64	SN74183	22.20	21.98	21.76
SN7430	0.17	0.16	0.13	SN7494	0.85	0.82	0.82	SN74190	22.15	22.09	22.04
SN7432	0.50	0.48	0.44	SN7495	0.85	0.82	0.82	SN74191	22.09	22.04	21.98
SN7433	0.88	0.83	0.77	SN7496	0.96	0.93	0.86	SN74192	22.15	22.09	22.04
SN7437	0.71	0.68	0.66	SN74104	21.32	21.27	21.21	SN74193	22.15	22.09	22.04
SN7438	0.71	0.68	0.66	SN74105	21.07	21.04	0.97	SN74194	22.97	22.88	22.75
SN7440	0.17	0.16	0.13	SN74106	21.07	21.04	0.97	SN74195	22.20	22.09	21.98
SN7441	0.74	0.71	0.64	SN74107	0.44	0.42	0.40	SN74196	22.20	22.09	21.98
SN7442	0.74	0.71	0.64	SN74110	0.61	0.59	0.58	SN74197	21.98	21.87	21.76
SN7443	21.43	21.38	21.32	SN74111	21.38	21.27	21.21	SN74197	21.98	21.87	21.76
SN7444	21.43	21.38	21.32	SN74118	21.10	21.05	0.99	SN74198	26.05	25.50	24.95
SN7445	21.98	21.95	21.93	SN74119	21.49	21.38	21.21	SN74199	26.05	25.50	24.95
SN7446	21.07	21.04	0.97	SN74121	0.44	0.41	0.38	Terminal Post Volt Reg. TO.3			
SN7447	21.10	21.07	21.06	SN74122	21.54	21.43	21.21	21.21	Plastic O/P 1.5 Amps. μ A7905		
SN7448	21.10	21.07	21.06	SN74123	23.08	22.97	22.86	5V. & μ A7812 12V. μ A7805			

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type	Price	1	25	100+
EP930	15p	12p	11p	
BP932	14p	13p	12p	
BP933	14p	13p	12p	
BP935	14p	13p	12p	
BP936	14p	13p	12p	
BP944	14p	13p	12p	
BP945	27p	26p	24p	
BP946	13p	12p	11p	
BP948	27p	26p	24p	
BP951	71p	69p	60p	
BP962	13p	12p	11p	
BP993	44p	42p	38p	
BP994	44p	42p	38p	
BP997	44p	42p	38p	
BP999	44p	42p	38p	

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only)

LINEAR I.C.'s—FULL SPEC.

Type No.	1-24	25-99	100 up
BP 201C—SL201C	69p	58p	49p
BP701C—SL701C	89p	55p	49p
BP 702C—SL702C	89p	55p	49p
BP 702—72702	58p	49p	44p
BP709—72709	39p	37p	33p
BP 709P— μ A709C	89p	37p	33p
BP 710—72710	48p	46p	44p
BP 711— μ A711	49p	47p	44p
BP 741—72741	81p	28p	28p
TAA 283	77p	66p	60p
TAA 293	96p	82p	77p
TAA 350	21.87p	21.74p	21.65p

S.G.S. EA1000 22-89p

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than 0.1% at 1KHz.

★ Signal to noise ratio 80dB.

ONLY
£3.58p each

★ Supply voltage 10-35 Volts.

★ Overall size 63mm × 105mm × 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm × 105mm × 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £3.25**

TRANSFORMER BMT80 £2-14½ p. & p. 27½p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response 20Hz — 20KHz \pm 1dB
Harmonic Distortion better than 0.1%
Inputs : 1. Tape Head
2. Radio, Tuner
3. Magnetic P.U.
1.25 mV into 50K Ω
35 mV into 50K Ω
1.5 mV into 50K Ω

All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within \pm 1dB from 20Hz to 20KHz.

Bass Control \pm 15dB at 20Hz
Treble Control \pm 15dB at 20KHz
Filters : Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than — 65dB
Input overload + 26dB
Supply + 35 volts at 20mA
Dimensions 292mm × 82mm × 35mm

ONLY £13-14½

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25-30 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail.

Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minttron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2.3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	21.87	21.70	21.09

All indicators 0.9 + Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each
Epoxy TO-5 case	1-24 25-99 100 up
uL900 Buffer	38p 36p 29p
uL914 Dual 2/p gate	38p 36p 29p
uL923 J-K flip-flop	55p 51p 49p

Date and Circuits Booklet for IC's
Price 8p.

DUAL-IN-LINE SOCKETS.

14 & 16 Lead Sockets for use with DUAL-IN-LINE I.C.'s. TWO RANGES PROFESSIONAL & NEW LOW COST.

PROF. TYPE No. 1-24 25-99 100up
T80 14 pin type 38p 30p 27p
T80 16 " " 38p 35p 33p

LOW COST No.

BPS 14 16p 14p 12p
BPS 16 17p 15p 13p

DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

GARRARD SP25 Mk III
Special Purchase.
Limited number available
Garrard SP25 Mk. III
Goldring G800
Teak plinth and tinted cover
All leads supplied.
Please add £1.25 P. & P. & Ins.

£17.45

AMPLIFIERS

Please add 85p P. & P. & Ins.

Amstrad 8000 Mk. II	£14.95
Amstrad IC2000	£27.50
Amstrad Integra 4000	£21.45
Armstrong 521 (Teak cased)	£43.90
Alpha Highgate 212	£24.85
Alpha Highgate FA300	£32.25
Alpha Highgate FA400	£35.65
Leak Delta 30	£44.85
Leak Delta 70	£54.90
Metrosound ST20E	£24.20
Metrosound T60	£45.95
Pioneer SA600 & 610	£57.25
Pioneer SA500A	£31.95
Pioneer SA1000	£96.95
Rogers R/brook (Chassis)	£37.95
Rogers R/brook (Cased)	£41.50
Rogers R/bourne (Chassis)	£49.95
Rogers R/bourne (Cased)	£52.75
Sinclair PR060 2 X Z30/PZ5	£14.70
Sinclair PR060 2 X Z30/PZ6	£16.70
Sinclair PR060 2 X Z50/PZB/Trans	£22.95
Sinclair AFU (Filter Unit)	£4.20
Sinclair 605	£18.25
Sinclair 2000 Mk. II	£21.50
Sinclair 3000 Mk. II	£28.00
Wharfedale Linton	£42.95
Teleton SAQ 307	£22.95
Rotel RA310	£34.95
Rotel RA610	£52.95

TURNTABLES

Please add 75p P. & P. & Ins.

Connoisseur BD1 Chassis	£12.75
Garrard SP25 Mk. III	£9.90
Garrard AP76	£17.20
Garrard SL65B	£13.95
Garrard 401	£28.75
Garrard Zero 100 (Auto)	£36.90
Garrard Zero 100 (Single)	£35.80
BSR MP60	£9.40
Goldring GL72	£20.90
Goldring GL72/P	£27.45
Goldring GL75	£26.85
Goldring GL75/P	£34.95
Goldring 101/P.C.	£20.00
Wharfedale Linton + cart.	£25.90
Thorens TD125AB Mk. II.	£27.95
Thorens TD150 Mk. II	£91.45
Thorens TD160 AB & C	£53.95

TUNERS

Please add 85p P. & P. & Ins.

Amstrad Multiplex 3000	£38.75
Armstrong 523	£39.50
Armstrong 524	£31.45
Rogers R/brook FET4 (Chassis)	£37.25
Rogers R/brook FET4 (Cased)	£43.50
Rogers R/bourne FET4 (Chassis)	£45.00
Rogers R/bourne FET4 (Cased)	£49.50
Sinclair PR060 (Module)	£17.45
Sinclair 2000/3000 Tuner	£29.90
Leak Delta FM (Cased)	£53.60
Leak Delta AM/FM (Cased)	£63.75
Alpha Highgate FT150	£37.95
Metrosound FMS 20	£38.70
Philips RH 690	£33.00

TUNER/AMPLIFIERS

Please add £1 P. & P. & Ins.

Alpha Highgate 150	£48.95
Armstrong 525 (Teak cased)	£69.45
Armstrong 525 AM/FM (Teak cased)	£77.25
Leak Delta 75	£119.00
Teleton 2100	£32.50
Goodmans One Ten	£98.90
Goodmans Mod 90	£87.95
Rotel 150	£49.50
Rotel 400	£75.50
Rogers Ravensbrook (Teak cased)	£77.00
Rogers R/brook (Chassis)	£72.00
Alpha FR 3000. New product	£72.00

SPEAKERS

Please add £1.50 per pair P. & P. & Ins. Price per pair

Amstrad I38	£13.90
Wharfedale Denton 2	£29.50
Wharfedale Linton 2	£35.85
Wharfedale Melton 2	£45.90
Wharfedale Doveedale 3	£59.80
Celestion Ditton 120	£38.40
Celestion Ditton 15	£30.90
Celestion Ditton 25	£84.50
Celestion County (new prod.)	£34.50
Goodmans Double Maxim	£47.40
Goodmans Mezzo 3	£45.95
Goodmans Magister	£82.95

Special bulk purchase

£2.90



Plus 65p P. & P. & Ins. Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25, 2025TC, 3000, 1025; 2000; 2500; 3500; 5100; AT65; SL65B; Also for BSR, McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B*. £4.20 + 65p. P. & P. & Ins. Also finished in walnut to match Japanese equipment—at no extra.

CARTRIDGES

Please add 10p P. & P. & Ins.

Goldring G850	£3.75
Goldring G800	£4.70
Goldring G800E	£7.50
Goldring G800 Super E	£14.15
Shure M3D	£3.70
Shure M44E	£4.75
Shure M55E	£5.55
Ortofon SL15	£15.85
Sonotone 9TAMC	£1.35

All prices Correct at time of press E. & O. E. and are subject to alterations.



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept: (PW5) 174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.


Open Monday to Saturday 9.30 a.m. to 6 p.m. **LATE NIGHT FRIDAY 7 p.m.**

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card)

2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

PHOTOELECTRIC KIT

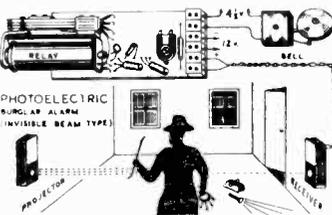CONTENTS: P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



PHOTOELECTRIC KIT £2.85

Postage and Pack. 15p (U.K.) Commonwealth
SURFACE MAIL 25p
AIR MAIL £1.40
Australia, New Zealand, S. Africa, Canada and U.S.A.
Also Essential Data Circuits and Plans for Building 10 advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1.45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Large Lenses, Filter, etc. Price £2.10. Postage 15p (U.K.) Commonwealth: Surface 20p, Air Mail £1.15.

BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.
CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4.75 postage and pack. 25p (U.K.). Commonwealth: Surface 30p, Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT


Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.
CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3.25, postage and pack. 15p (U.K.) Commonwealth: Surface 25p, Air Mail 75p.

YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects.

Stereo radio from your existing tuner.

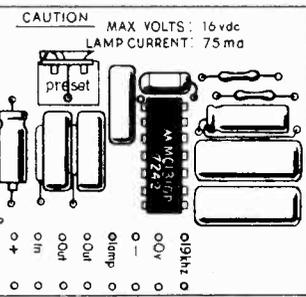

A complete set of parts from Jermynto build a stereo decoder module that will convert your existing mono tuner for stereo reception whilst maintaining a high standard of reproduction.

The distortion is very low (typically 0.3% at 560 mV RMS composite input signal) with 40dB channel separation.

The stereo switching is automatic and there is a light emitting diode which acts as a stereo beacon.

The kit requires no coil and there are no alignment problems.

Fitting. The module requires a 10-16 volt power supply which can normally be tapped off the existing tuner. The signal input is taken off before the de-emphasis circuit which in practice means disconnecting one, or at the most, two capacitors. Any radio engineer will be able to spot these capacitors, but if you're really stuck send the circuit with a SAE to us and one of our engineers will indicate the output point. (This is the full extent of our involvement, no hardware please). Of course, if you have a modern mono tuner with a multiplex output our module simply plugs in.

The outputs go via a screened twin cable to the tuner inputs of your stereo amplifier.

And the cost? £4.90 for the Kit with 100% tested integrated circuit. Also available assembled and aligned, checked and ready for use at £6.90 (includes 12 month guarantee). Beat that!

To Jermynto Industries
83 Vestry Estate
Sevenoaks
Kent
Block Capitals Please

Please rush me Kit(s), made up Stereo decoders.
I enclose cheque/postal order for £

Name
Address

Why take the risk?

of damage to expensive transistors and integrated circuits, when soldering?

Use Antex low-leakage soldering irons

All prices exclusive of V.A.T.



220-240 Volts or 100-120 Volts

Model X25

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with it's truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 3/32".
2 other bits available 3/32" and 3/16".

Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be removed

PRICE: £1.75 (rec. retail)
Suitable for production work and as a general purpose iron

Model CCN

220 volts or 240 volts

The 15 watt miniature model CCN. also has negligible leakage.

Test voltage 4000v. A.C.

Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"

4 other bits available
1/8", 3/16" 1/4" and 1/16"

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8"

PRICE: £1.95 (rec. retail)

A SELECTION OF OTHER SOLDERING EQUIPMENT.



MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24
PRICE: £1.70 (rec. retail)

MODEL CN2


Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.
PRICE: £1.70 (rec. retail)



MODEL G

18 Watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.
PRICE: £1.83 (rec. retail)

MODEL SK.1 KIT

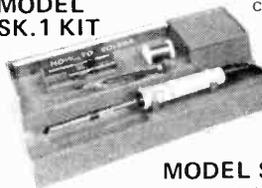

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £2.75
(Rec. retail)

MODEL SK.2 KIT

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder and booklet "How to Solder"



PRICE £2.40
(Rec. retail)

MODEL MES.KIT



Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder."

PRICE £1.95
(Rec. retail)



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from: —
ANTEX LTD. FREEPOST
(no stamp required) **Plymouth**
PL1 1BR Tel: 0752 67377
Reg No: 393594

- Please send the ANTEX colour catalogue.
 Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME _____

ADDRESS _____

PW/5


UNISOUND FOR THE NEW SOUND



AT
£26.12
INC.
VAT

It's the RT-VC system that screws together to save you pounds! Unisound comprises two superb speakers and an amplifier/record deck plinth—all beautifully finished in simulated teak. The stereo amplifier (4 watts per channel into 8 ohms) is based on the famous Mullard Uniex system brought up-to-date by RTVC using integrated circuits. Turntable is the proven Garrard 2025 TC complete with stereo cartridge and tinted acrylic cover. Speakers are big EM1 Twin-cone units all ready for mounting in their elegant cabinets, which simply need screwing and glueing together. Easy step-by-step instructions. **£26.12 complete plus £1.40 packing + £1.40 post. Diamond Stylus £1.25 extra.** Stereo headphones with adaptor £4 extra. Send for leaflet.

AN RTVC EXCLUSIVE DESIGN

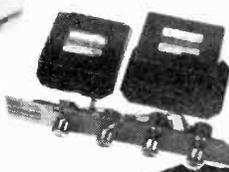


UNISOUND MODULES ONLY £6.95 + 50p. p. & p.

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion at all power levels over the audio spectrum.

RTVC No price in

If you can solder on printed circuit board you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions

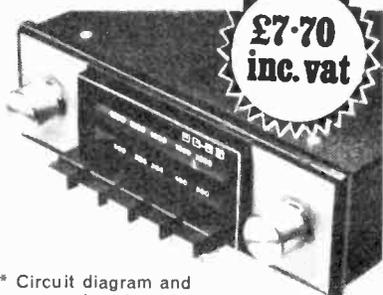THE TOURIST PB CAR RADIO KIT AN INCREDIBLE BUY ONLY FROM **RTVC**



£7.70
inc. vat

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.


Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7" wide, 2" high and 4½" deep.

* Circuit diagram and comprehensive instructions 50p free with parts.

* Fully retractable lockable car aerial £1.25 post paid.

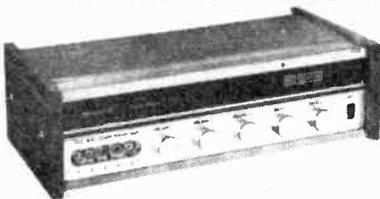PRICE ONLY £7.70 p. and p. 55p
Speaker with baffle and fixing strips £1.50. 25 p. & p., post free if bought with the kit. Send for leaflet.



RELIANT Mk IV

A GOOD QUALITY AMPLIFIER—12 Watts £10.50 (inc. VAT). 20 Watts £13.50 (inc. VAT)

*5 Electrically Mixed inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors).


*Solid State Circuitry. *Attractive Styling INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs. 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.)

All 250mV sensitivity.
Size approx. 12½ x 6 x 3½ ins.

12W 3 ohms only version **£10.50** plus 60p
20W 8-15 ohms version **£13.50** p & p

SOUND 50

50 WATT AMPLIFIER. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19½ x 10½ x 8ins. Amplifier **£31.35** plus £1.50 p. and p. (inc. VAT)

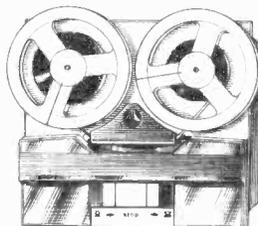

PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tap deck, less heads. Cater up to 7ins. spools. Unused but store soiled hence no warranty. plus £1 p & p

Increase* with VAT!

VISCOUNT III AUDIO STILL ONLY £52* COMPLETE

14 + 14w. r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10w. at 1kHz - 0.1%. This is real value for money! We have designed 2 systems and the heart of them both is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect, transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tinted acrylic cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PRICES: SYSTEM I


Viscount III R 101 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£15.40 + £2.20 p & p
Garrard SP25 Mk.III with MAG. cartridge plinth & cover	£25.00 + £1.75 p & p
total	£64.60

Available complete for only **£52*** +
£3.50 p. & p.

PRICES: SYSTEM 2

Viscount R 101 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£35.20 + £3.30 p & p
Garrard SP25 Mk. III with MAG. cartridge plinth & cover	£25.00 + £1.75 p & p
total	£84.40

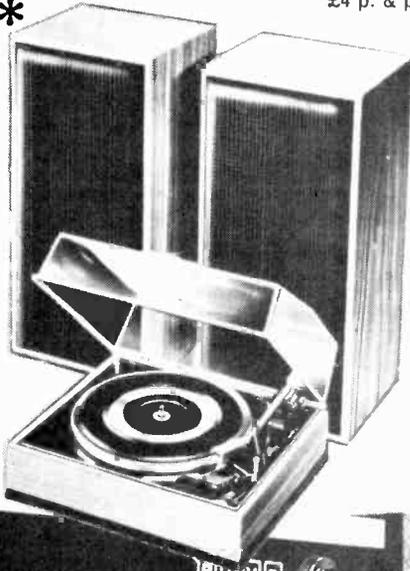Available complete for **£69*** +
£4 p. & p.



SPEAKERS: Duo Type II Size approx. 17in. x 10½in. x 6½in. Drive unit 13in. x 8in. with parasitic tweeter. Max. power 10 watts ohms. Simulated Teak cabinet. £15.40 a pair (inc. VAT), £3.30 p. and p. Duo Type III Size approx. 23½in. x 11½in. x 9½in. Drive unit 13½in. 8½in. with H.F. speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet.

SPECIFICATION R101: 14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms.) Total distortion @ 10W 1kHz @ 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within idB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Signal-to-noise ratio: (all controls at max.)—P.U.1. and radio - 65dB, P.U.2 - 58dB. Cross talk better than -35dB on all inputs. Size approx. 13½in. x 9in. x 3½in. Send S.A.E. for fully illustrated brochure. 12 month's written guarantee.

ONLY FROM US

TIMES OF OPENING: Acton—Mon.—Sat. 9.30-5.
Closed all day Wed.
Edgware Rd.—Mon.—Sat. 9.30-5. Closed all day Thurs.

VISIT OUR SHOWROOMS

RTVC

Radio and TV Components (Acton) Ltd.
71c High Street, Acton, London W3 6NG
323 Edgware Road, London W2
Mail orders to Acton. Terms C.W.O.
Goods not despatched outside U.K.
All enquiries S.A.E.

SUPPORT SERVICE

WHY did you buy this copy of *Practical Wireless*? Were you influenced by advanced publicity or advertising; are you a regular reader with a devotion to follow our activities month by month; or are you one of many thousands who pick up this magazine to seek guidance on what makes radio and electronics tick? It has been said that people read *Practical Wireless* to learn something about the subject. After all, it is a technical field that demands some education and understanding and it is really this aspect that makes most people read.

To supplement professional career requirements there is a growing band of people who are bank clerks, clergymen, accountants, businessmen, as well as students and technicians who are seeking part time courses on the practical side of radio and electronics. Some colleges are able to offer facilities, subject to minimum class size, but we have heard of cases where they cannot find enough qualified engineers who are willing to spend extra time in the evenings to instruct these students. It is a pity because it often means that a course has to be dropped because of this.

So we come back to magazines; *Practical Wireless* is used in schools and colleges to a great extent because it provides an excellent support service to instructors, many of whom cannot always find sufficient time in addition to their everyday jobs to make full preparation for classes. *Practical Wireless* is a leader because its articles and designs are "down-to-earth" and, in spite of competition from elsewhere, we still offer the greatest constructional project support to instructors, technicians and engineers, while encouraging the confidence of newcomers.

This month we have rubber-stamped this policy by giving you for the first time a unique supplement containing eight extra straightforward constructional projects for the home, attractively presented with abundant illustrations and a full colour cover picture. To make it easier for you to find this supplement and worthwhile to keep for reference, we have printed it on a pleasant shade of "apple-green" coloured paper—another first for *Practical Wireless*.

Don't let this divert your curiosity too far from our other usual features because you will also find much more to interest you in this issue. For the benefit of quick and easy reference you will also find our contents list just inside the front cover, together with information on many aspects of our service. And watch out for next month's issue too for more special attractions, some of which are mentioned in this issue.

M. A. COLWELL—Editor

The June issue, on sale May 4th, will include a new easy competition to win a Digital Multi-meter, a special feature on what to look for when buying Hi-Fi Equipment, and "Special Valves in Electronics", plus the usual abundance of constructional projects.

Further details on page 48.

NEWS...

B.R.C.

change their name

BITISH Radio Corporation Limited announced on the 1st April that it has changed its name to Thorn Consumer Electronics Limited. It continues to manufacture and market audio and TV products under the Ferguson, HMV, Ultra and Marconiphone brands and remains a wholly-owned subsidiary of Thorn Electrical Industries Ltd.

VAT

To the best of our knowledge, the prices quoted in this issue were correct at the time of going to press.

As from April 1st, 1973, there is no purchase tax but a large number of goods carry Value Added Tax.

The "N.F.A.C."

THE National Federation of Aerial Contractors Limited is making an attempt to "clean up" the aerial contracting industry.

The Ministry of Posts and Telecommunications listed 55,000 complaints of bad reception in their recent annual report. Out of 32 listed causes of complaints, the largest numbers were for "inefficient aerial installations" and the N.F.A.C. feels that it can help this state of affairs by alerting the consumer and all who employ aerial contractors that there are in existence a very large number of "Rooftop Racketeers".

Plans currently being considered by the Federation include random inspections of members' installations and a system whereby new companies applying for membership will have their work inspected in addition to the trade references that are already required. A special Standards Committee will hear reports of faulty workmanship.

By this system, the N.F.A.C. hopes to assist in narrowing the field of consumer complaints and possibly convince dealers that they mean to play their part in cleaning up the aerial contracting industry.

Mullard film on I.C. design

MULLARD Ltd. have announced a new 16mm colour film lasting 18 minutes. It's called *The Computer-Aided Design of Integrated Circuits* and is available on free loan from the Mullard Film Library, 269 Kingston Road, Merton Park, London, SW19 3NR.

The film, which was shot mainly on location at the Mullard semiconductor plant at Southampton, describes in detail the use of the computer and its peripheral equipment in such functions as IC design and layout, mask-making and testing at every stage of production.

Tandberg in the jungle

SERGEANT J. Murtagh of the Royal Signals is seen in the picture using a Tandberg Series 11 portable tape recorder. This machine and a TP4-1 portable radio accompanied a recent British Trans-Americas expedition which took in 18,000 gruelling miles from Alaska to the tip of South America. The purpose of the journey was to survey a road through the uncrossed 300 miles of swamp and jungle bordering the Panama canal which blocks the Pan American highway system.

During the trip, the expedition kept in touch with the outside world with the TP4-1 receiver, picking up BBC news broadcasts and weather reports.

In the jungle and swamps, the electrical equipment was carried in man-packs or by ponies and although it was partially immersed in water, rolled on several times by the ponies and carried through thick mud, it continued to function without a fault.



Sgt. Murtagh of the Royal Signals.

Signals "piped" through waveguide

THE core of a system which, when fully implemented, will transmit 300,000 phone conversations or 200 colour TV signals at the same time through a waveguide "pipe" is now operating at the GEC-Marconi works at Great Baddow.

This equipment will be used by Post Office engineers in a field trial system to be installed between the Post Office Research Station at Martlesham, Suffolk and a Post Office site at Wickham Market, 15 kilometres away.

The new "pipe" is a 50mm diameter circular waveguide capable of supporting signals throughout the frequency band from about 32 to 110GHz. The photograph shows 32-50GHz channel separating filters and band-branching assembly.



Texan reprints

REPRINTS of the "Texan" 20+20W Stereo Amplifier are available.

They may be obtained by sending 35p (30p+5p) postage/packing to "Texan" Reprint, c/o Chief Cashier, Practical Wireless Tower House, Southampton Street, London WC2E 9QX.

World Radio Club

FURTHER to the item on the World Radio Club in the March issue, we have been informed by the programme Producer that an extra broadcast in the BBC World Service will be made each week at 20.30 GMT on Thursdays.

The midday edition has now been moved to 13.30 GMT on Wednesdays. The other Friday and Sunday transmissions remain unaltered. BBC, Bush House, P.O. Box 76, Strand, London WC2B 4PH.

Some S.E.R.T. meetings


THE Society of Electronic and Radio Technicians, Faraday House, 8-10 Charing Cross Road, London, W.C.2. will be holding the following meetings:

April 11: "Test Equipment" by B. Ellison from Tektronix. Venue is The Conference Theatre, I.B.A., 70 Brompton Road, London, S.W.3 and the lecture commences at 7.00 p.m.

April 5: "Colour TV Forum and Exhibition". This will be held in the Byng Kendrick Suite, University of Aston, Birmingham, commencing at 7.00 p.m.

April 24: "The CVC5 Colour Receiver" by A. E. Thomas from ITT. This will be held in the Cleveland Scientific Institution, Corporation Road, Middlesborough. Meeting starts at 7.30 p.m.

VHF Regen Receiver

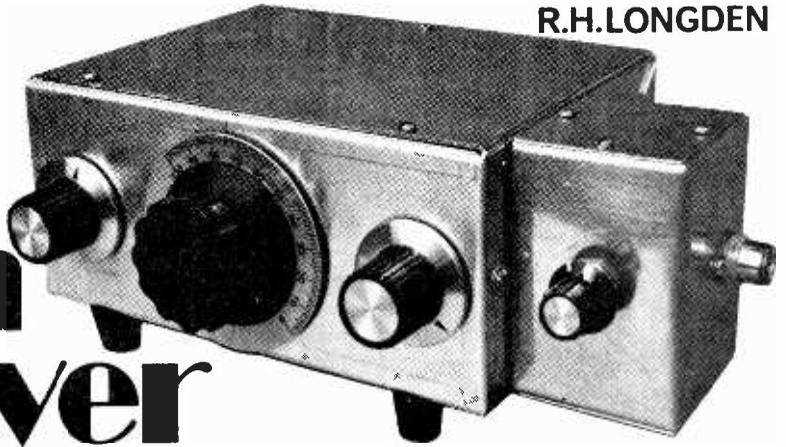

THIS is a self-contained receiver which may be used over the range 115-150MHz, or 140-190MHz, according to the coil fitted. It was actually found to maintain good efficiency even up to 210MHz. A vertical telescopic aerial or improved aerial system will provide reception on the internal speaker, an outlet being present for headphones when required. An optional preamplifier is also described.

The receiver has a superregenerative detector, which is a great advantage from the point of view of simplicity. This type of detector is highly sensitive, and it should be possible to copy a signal of under $1\mu\text{V}$. There is also only one tuned circuit, so no alignment or ganging difficulties arise. The bands include the 2-metre amateur band (144-146MHz). In terms of sensitivity, most signals which can be well received with the simpler type of converter-communications receiver combination can also be received satisfactorily with this receiver.

A disadvantage sometimes encountered with this type of receiver is tricky tuning and hand-capacity

effects. These do not arise here, due to sound construction and a metal case and so actual use of the receiver is easy.

Circuit Details

Fig. 1 is the circuit, employing a junction f.e.t. in the first stage. The rod or other aerial is coupled by L1, and L2 is tuned by VC1. The network R2, C4, R3 and C5 gives a suitable quench frequency and regeneration is controlled by VR1. To modify the tuning range, L2 only need be changed.

A three-stage audio amplifier assembled on a separate circuit board follows. Tr2 is the first audio amplifier, Tr3 the driver, and Tr4/5 the output pair, operating a small speaker in the case. The outlet takes a jack plug for an external speaker or phones, if wanted, and VR2 is the volume or audio gain control. R12 is a small pre-set potentiometer, which allows working conditions for the output pair to be suitably adjusted.

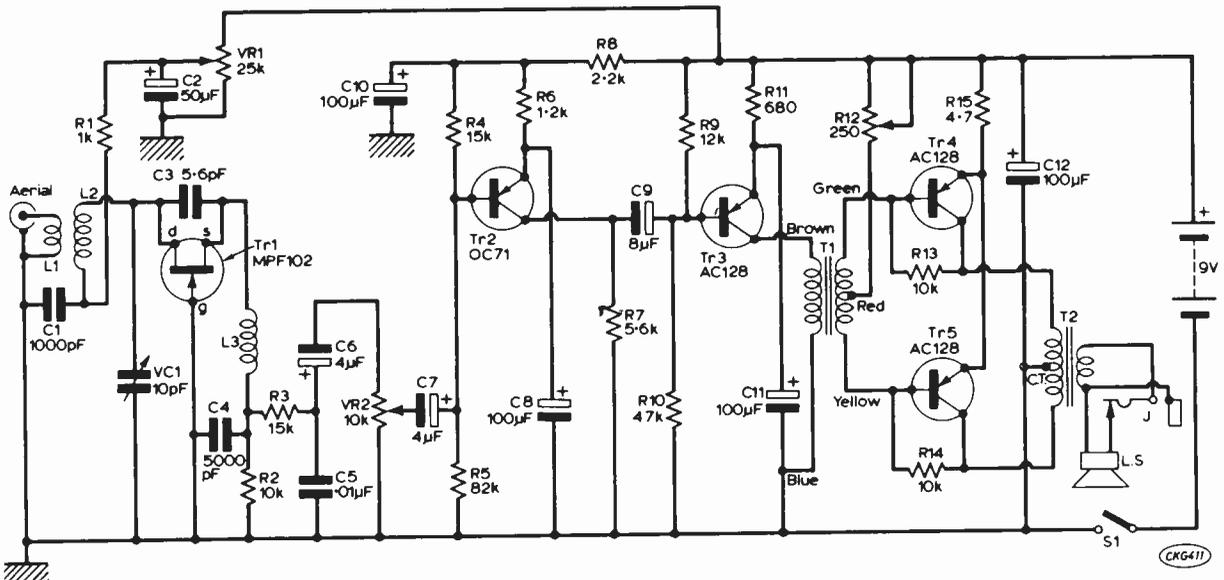


Fig. 1: Circuit of the main receiver. The circuit of the pre-amplifier is shown in Fig. 4. The heading photograph shows the two units bolted together.

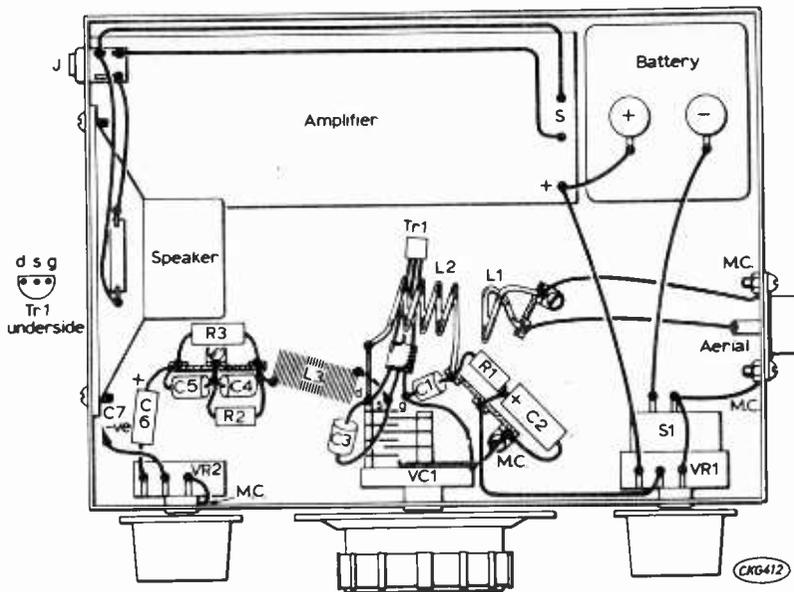


Fig. 2: Layout of the main components and audio amplifier board within the cabinet. When the preamplifier is fitted the coaxial aerial socket is removed and used on the preamplifier box.

Photograph looking into the top of the receiver which may help when locating components as in Fig. 2 above.

Cabinet Construction

Flanged universal chassis members 7 x 3in form the front and back, and similar parts 5 x 3in are the sides. The top and bottom are 7 x 5in flat plates.

The front member is drilled for VC1, VR1 and VR2, as in Fig. 2. Also punch or drill holes for a co-axial socket on the right hand side, or for an insulated terminal or socket, if a co-axial feeder is not required here.

An opening is cut in the left member for the speaker, taking care that this will clear the amplifier and other parts. Perforated zinc or expanded metal is placed over the aperture, and the speaker is bolted on. The jack outlet is placed as shown.


The four flanged members are then assembled by bolts through the holes present in them. Four holes are drilled in one 7 x 5in plate, these are marked through so that the flanges can be drilled to suit. The case bottom can then be attached. Two rubber feet were placed on the front bolts, to raise the front of the receiver slightly.

It is easier to assemble the receiver if the sides and back are left off until later. When all construction is finished, the top 7 x 5in flat plate is fixed with four self-tapping screws.

Detector Stage

This is wired as in Fig. 2. A 3-lead holder is used for Tr1. This avoids possible damage from heating while soldering, and also allows the transistor to be changed, if necessary. The MPF102 is listed as having a top frequency of 200MHz. Some were found to perform satisfactorily at well above this, but others, not up to specification, would only operate at relatively low frequencies.

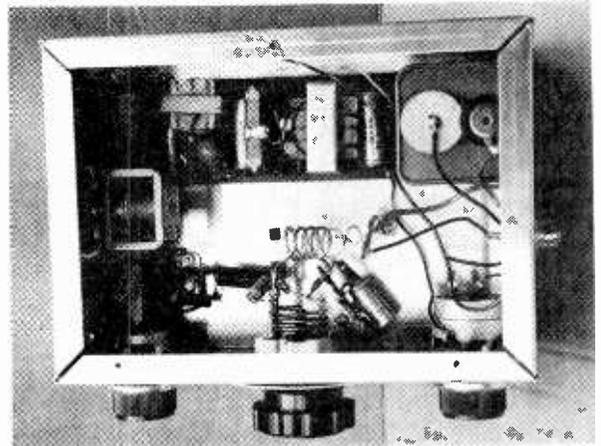The holder drain tag is soldered directly to the lower fixed plates pillar of VC1. The leads of C3 are cut short, and this item is soldered from the source tag, to the top pillar of VC1. A stout wire is also soldered to this pillar, projecting back about 1/2in so that L2 can be changed without unsoldering other items.



A stout lead from the gate tag goes to the moving plates contact of VC1, just clearing the moving plates. The tag strip holding R1 and C2 is raised on a long bolt, so that wires from C1 are as short as possible. A wire projects upwards about 1/2in to take the other end of L2.

L1 is a single turn of insulated wire. Coupling can be adjusted by rotating this small tag strip slightly on its fixing bolt, but it is not very critical.

L3 is self-supporting, and is 30 turns of 26swg enamelled wire, wound on a 1/4in diameter object which is afterwards removed. Turns are closewound. One end is soldered to the tag supporting R2, C4 and R3, and the other end is soldered to the source tag of Tr1 holder.

The potentiometers and other parts can then be wired as in Fig. 2. A lead will run from VR2 under the speaker to the input pin of the audio amplifier.

Audio Amplifier

This is assembled on Veroboard 5 x 1 1/4in, as in Fig. 3. First drill two holes for the chassis bolts, position the board in the case, and mark and drill

matching holes in the metal bottom. Tags held with the bolts form earthing points, Fig. 3. The bolts are $\frac{1}{2}$ in long, so that extra nuts hold the assembly clear of the metal case, lock-nuts underneath securing the amplifier. A piece of card $5 \times 1\frac{3}{4}$ in may be put between the amplifier and case bottom, though shorts to the metal will not arise if joints are kept close to the board.

Coils

These are self-supporting, wound with 18swg, 20-swg or other stout wire, with spaced turns. A coil having 4 turns, $\frac{1}{2}$ in outside diameter, and $\frac{7}{16}$ in long, was found to tune 115-150MHz. This is suitable for 2 metre reception.

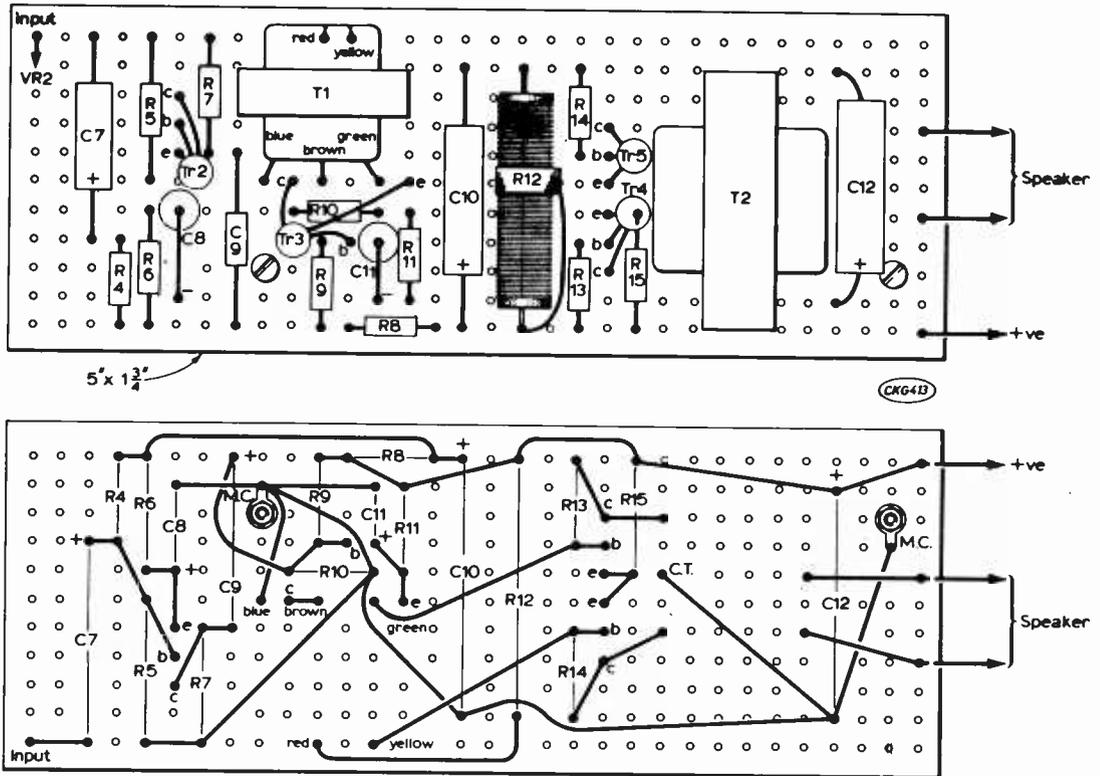


Fig. 3: Diagrams of the component layout and wiring of the audio amplifier board.

Take care to fit the electrolytic capacitors as indicated. With a unit of this kind, it is helpful to place black 1mm sleeving on the negative line leads, and red sleeving on positive leads. With another colour for other wiring, it will be easy to check connections if this should prove necessary.

The amplifier may be tested before fixing it. Place the slider of R12 at about the central position. Connect the speaker and a 9V battery, negative to one of the chassis tags. Either place a meter in one battery lead and move the slider of R12 for a current of 10mA, or adjust R12 to place just enough resistance in circuit for speech to sound normal. If R12 is at a very low value, current drawn will be small but cross-over distortion will be present.

For this test, input can be from any convenient source; a signal generator, diode tuner, pick-up, or from the first stage of the completed receiver. If VR2 is not in circuit, avoid overloading the amplifier by the test signal.

The amplifier is fitted as shown, negative return being through the metal case. Connect the speaker leads and amplifier to the jack so that the contacts which open silence the speaker, when phones or an external speaker are in use.

A coil $\frac{1}{2}$ in long and $\frac{7}{16}$ in in diameter, having three turns, tuned 192-150MHz, while a similar coil having two turns allowed 216MHz to be reached.

Stray circuit capacitances and the length of connecting leads influence the frequencies tuned. The frequency can be raised by reducing the number of turns, or by stretching the coil to separate turns, or by reducing the overall diameter.

Operating notes

When VR1 is advanced, a position should be found where a strong hiss begins. This is roughly the correct setting for VR1, though it will be found that further slight adjustment may be helpful, depending on the strength of the signal tuned in.

The hiss should cease when any signal of sufficient strength is tuned in, provided VR1 has not been turned too far. VR2 adjusts volume in the usual way, and can probably be advanced about half way, for the internal speaker.

If superregeneration is impossible on some part of the band, move L1 a little further from L12. This

★ components list

Resistors

R1 1kΩ	R9 12kΩ
R2 10kΩ	R10 47kΩ
R3 15kΩ	R11 680Ω
R4 15kΩ	R12 250Ω miniature slide pot.
R5 82kΩ	R13 10kΩ
R6 1.2kΩ	R14 10kΩ
R7 5.6kΩ	R15 4.7Ω All ½W, 5%
R8 2.2kΩ	
VR1 25kΩ linear pot. with switch	
VR2 10kΩ log. pot.	

Capacitors

C1 1000pF disc ceramic	C7 4μF 4V
C2 50μF 10V	C8 100μF 10V
C3 5.6pF	C9 8μF 6V
C4 5000pF	C10 100μF 10V
C5 0.01μF	C11 100μF 10V
C6 4μF 4V	C12 100μF 10V
VC1 10pF variable Jackson C804	

Transistors

Tr1 MPF102	Tr3 AC128
Tr2 OC71	Tr4/5 2xAC128

Miscellaneous

Case: Two 5x3in. and two 7x3in. flanged universal chassis members, and two 5x7in. flat plates (Home Radio, Mitcham); KN2 2½in. dial and knob (Home Radio); Two 1in. knobs; tag strips, etc.; T1 Osmor driver transformer; T2 Output transformer, 2xAC128 type to 2/3 ohms; 2½in. 3Ω speaker; Jack socket with break contacts; 3-lead transistor holder, co-axial socket.

is not critical, but tight coupling will tend to prevent regeneration, while very loose coupling will reduce signal strength.

Aerials

There is room for considerable experiment here. Some local transmissions (range about 10 miles) were received with about 6in of wire projecting from the socket, which shows how sensitive this type of circuit can be.



This view of the receiver shows the positioning of the internal loud-speaker and the socket for an external loudspeaker or headphones.

With a telescopic aerial extending to three feet, a considerable number of transmissions were received, including amateurs over 50 miles away. This aerial performed poorly with the receiver and aerial near a metal window, but was better in the centre of a downstairs room, and even better in an upstairs room. Reducing the length to about two feet made almost no difference, and sliding the sections up and down did not give any notably best or critical resonant length.

Best results of all on 2 metres were obtained with a dipole made from ¼in aluminium tubing, 38½in overall, with a centre co-axial feeder. This aerial was mounted out of doors on a light pole. A long or lossy feeder would tend to lose much of the advantage such an aerial can give.

The angle and slope (polarisation) of all these aerials had some influence on results. No doubt an improved VHF aerial would increase signal strength, but some means of rotating it would be needed, and this was not felt justified.

Pre-amplifier

The receiver has high sensitivity, but in some circumstances there are advantages to be obtained by adding an r.f. stage. This stage will materially reduce radiation from the superregenerative detector, and also help isolate the aerial to avoid dead spot or damping effects on some frequencies. In fact, these are the most important advantages, and much gain must not be expected from the r.f. stage at frequencies over 150MHz or so.

Fig. 4 is the circuit, the f.e.t. being used in a grounded-gate arrangement which does not need neutralising. L1 is peaked by the small capacitor VC1. Tuning is flat, and needs no adjustment over a small band.

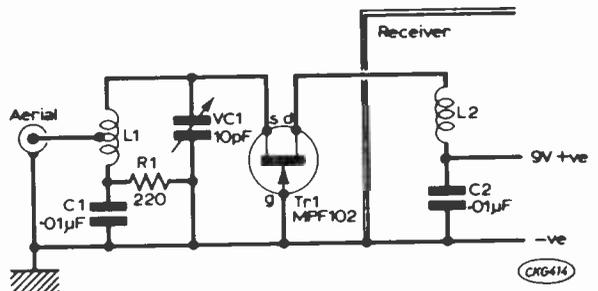


Fig. 4: Circuit of the pre-amplifier and connections to the input circuit of the main receiver.

The f.e.t. drain circuit is to the coupling loop L2, which was originally used for aerial coupling in the receiver. Alternatively, a broadly resonant winding can be used here, resulting in better gain over a narrow band of frequencies.

Cabinet

The box is 3 x 2 x 2in and is bolted on the metal side of the receiver case. It is made from a flat piece of aluminium 7 x 2in and one 7 x 3in flanged "universal chassis" member.

The long flanges are cut 2in from each end, a 90° piece being removed. A piece of wood about

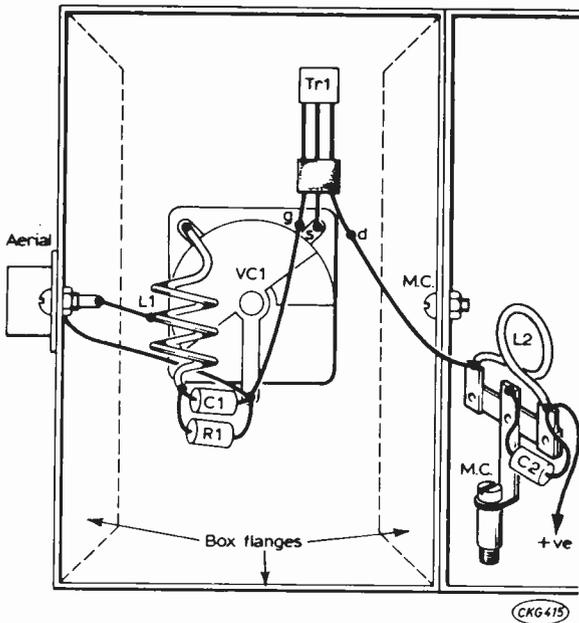


Fig. 5: Positioning of the few components within the preamplifier box.

3 x 2in and 1/2in or so thick is then placed between the flanges, and another piece of wood is placed level with this, and the whole gripped tightly in a vice. The 7 x 3in member is then bent into a 3 x 2 x 2in box, with the flanges inwards. Fig. 5 shows this part from behind. The front is drilled for VC1, and one side for the co-axial or other aerial socket. Three holes are also drilled in the other side, to match up with the holes which are exposed when the co-axial socket is removed from the receiver.

The 7 x 2in piece is bent at 2in from each end, in the same manner, so will fit on to enclose the box. It is held with a number of self-tapping screws.

Pre-amplifier Wiring

The transistor holder (or transistor) is soldered directly to VC1, as in Fig. 5. All leads are as short as possible.

L1 is wound with 18 or 20swg copper wire, and is similar to the coil in the receiver, but will generally have to be stretched somewhat, or have

★ components list

R1 220Ω 1/2W, 5%
 C1 0.01μF
 C2 0.01μF
 VC1 10pF or similar miniature variable, or pre-set.
 Tr1 MPF102 Holder optional

Universal Chassis flanged side 7x3in. (Home Radio)
 Aluminium 7x2in.
 Knob, tag-strip, etc.

The components listed above for the pre-amplifier are additional to those required for the main receiver.

about one less turn. If maximum volume is with VC1 fully open, this shows that L1 should be changed, by removing a turn, spacing turns further apart, or winding a new coil of smaller diameter.


The position of the aerial tapping depends somewhat on the use of a co-axial fed dipole or similar aerial, or a short vertical rod type aerial. This tapping can usually be about one-quarter to one-third the total number of turns from the C1 (earthed) end.

Two bolts fix the r.f. stage to the side of the receiver, and a lead from Tr1 drain passes through the original aerial socket hole to L2.

Receiver Changes

The tag strip holding L2 is replaced by one having two insulated tags. A lead from one tag is run to a positive pin on the a.f. amplifier and C2 is connected from this tag to the chassis tag, as in Fig. 5. The drain lead is taken to the other tag.

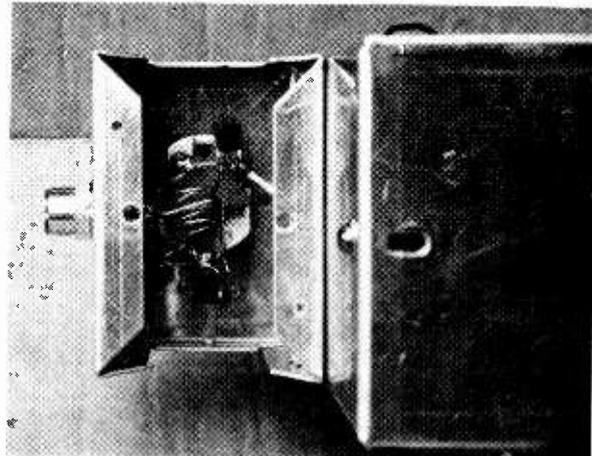L2 is one turn of insulated wire, positioned near the detector coil. Coupling is adjusted for best regeneration, by bending the loop L2 to adjust the distance to the detector coil, as with the original circuit.



Rear view of the completed pre-amplifier bolted to the receiver.

It was found that results were better with coupling in one phase. To check for this, twist L2 180°, to change its sense with relation to the detector coil.

As mentioned, L2 can be resonant over a narrow band. This increases gain, but makes it a little more troublesome to change coils or cover a wide band of frequencies. If this method is to be tried, wind L2 with one or two extra turns, compared with the detector coil, using insulated wire to avoid shorts. It is then necessary to stretch or compress L2, or change the number of turns, until it is found to peak up signals in the wanted frequency range. The resonant effect is quite flat, but these adjustments, and the degree of coupling with the detector coil, and position of the aerial tapping, can make quite a difference to reception. ■

Because superregenerative receivers are notorious for their radiation it is strongly recommended that the pre-amplifier be fitted as an essential part of the receiver. Complete screening, as described by the author, is very important.

SPECIAL PRODUCT REPORT

FETRONS

FETRONS

THE field effect transistor (FET) is currently being used in the front end of a.f. and r.f. circuits, as well as being developed into simplified forms of logic circuitry for micro-miniature applications such as wrist watches and pocket calculators. Aside from the manufacturers of such luxury items, our attention is turned here to more domestic matters such as television receivers, radio transmitters and receivers. Where thermionic valves are still being used, there is some reluctance to effect a total conversion to semiconductor techniques. We can have the best of both worlds because we can now replace valves in some circumstances with direct equivalent improved performance transistors. Particular areas of application also include unattended relay stations, and telecommunications terminals, as well as domestic receivers.

TRIODE EQUIVALENT

These transistors, called "fetrons," have emerged from the military applications stable and are being made available for other applications, although very little is generally known about the performance so far. The fetron is basically an arrangement of two n-channel field effect transistors (Fig. 1) connected to provide the equivalent working characteristics of a triode valve but with a much better frequency response at both ends of the spectrum. This is because the fetron has an extremely low channel resistance and inter-electrode capacitance. Furthermore, since there are

no heaters, operation is immediate on switch-on.

OTHER FEATURES

The life of the fetron is likely to be much greater than the thermionic valve under normal working conditions and the degradation of operational characteristics is minimal. Other important features include a higher amplification factor (almost ten times that of a valve) and a lower noise figure. Since no heaters are used, power requirements are simplified to just one high tension supply.

PENTODE CHARACTERISTIC

Both the thermionic valve and the FET are voltage controlled devices, hence design equations are virtually the same. Although the pentode anode voltage-current characteristics are similar to the drain characteristics of the fetron, the latter are more clearly defined at the cut-off region

or "knee" and exhibit stable current drain for various drive conditions (Fig. 2).

Since the main purpose of the fetron is to act as a direct replacement for the triode valve, it is essential that it should withstand high voltages and have a matched gm. The single junction FET cannot do this, but when two specially selected FETs are cascaded the problem is overcome. It is also possible to reduce the Miller (gate to source capacitance) effect by using a low capacitance, small signal, high gm FET at the input circuit, coupled with a high voltage output FET.

With the arrangement shown in Fig. 1, the output FET acts as a voltage dropper for the input FET and the Miller effect capacitance of each is in series. The output impedance is also greater than in a valve pentode, resulting in the excellent characteristics shown in Fig. 2. Since the input gate circuit is effectively a reversed bias junction, it presents a very high resistance load to the signal source.

Fig. 3 shows the transfer characteristic of a fetron which has been made

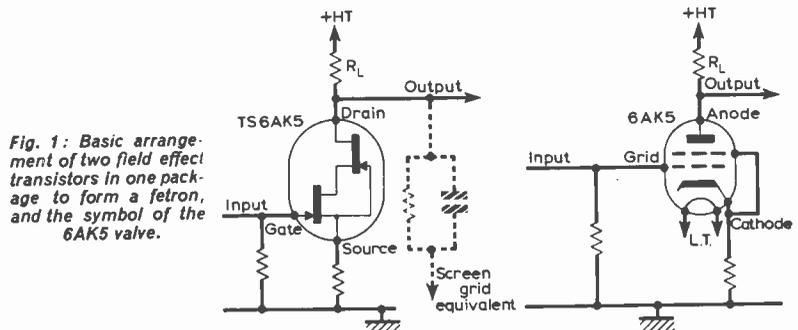



Fig. 1: Basic arrangement of two field effect transistors in one package to form a fetron, and the symbol of the 6AK5 valve.

TABLE 1:

TYPICAL PENTODE DEVICE CHARACTERISTICS— Rk=200 Ω, Eb=120V		
PARAMETER	6AK5	TS6AK5
Plate voltage breakdown	350V	350V
Plate resistance	0.5MΩ	5.0MΩ
Transconductance	5,000μmhos	4,500μmhos
Plate current (Rk=200Ω)	7.5mA	7.0mA
Grid voltage for Ib=10μA	-8.5V	-5.0V
Amplification factor	2,500	22,500
Input capacitance	4.0pF	6.5pF
Output capacitance	0.02pF	0.02pF
Useful frequency limit	400MHz	600MHz

TABLE 2:

TYPICAL TRIODE DEVICE CHARACTERISTICS (EACH SIDE)—Rk=2-70 Ω, Eb=130V		
PARAMETER	12A7	TS12A7
Plate voltage breakdown	400+V	350V
Plate resistance	15kΩ	250kΩ
Transconductance	4,000μmhos	3,000μmhos
Plate current (Rk=240Ω)	5.0mA	9.0mA
Grid voltage for Ib=110μA	-7.0V	-7.0V
Amplification factor	60	750
Input capacitance	2.2pF	25pF
Output capacitance	1.5pF	3.5pF

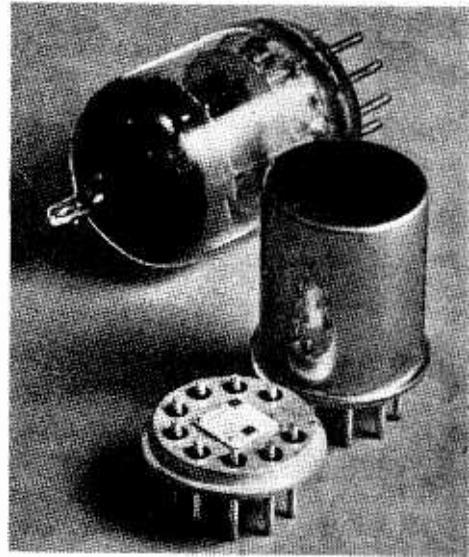

up from selected FETs to approximate closely that of a particular valve (shown dotted) operating within the same limits. If special requirements include partial operation beyond this FET cut-off then clearly a more appropriate FET device must be selected for this, perhaps providing a higher current for the same control voltage. The gm or transconductance ratio of the fetron gives a true square law property with consequent harmonic distortion figures of an extremely low order. In fact, harmonics beyond second order are claimed to be negligible.

Although the simulation of the "screen grid" principle can be effected within the fetron package, the similarity of the transfer curves to those of a pentode must not be taken as an assumption that the fetron is an ideal replacement for the pentode, even though the noise figure may be lower. The fetron has a markedly improved performance over the triode due to square law operation.

POWER REQUIREMENTS

Power supplies can be greatly simplified: first by the elimination of low voltage lines; secondly by the use of less stringent h.t. regulation. Current requirements are similar to or slightly higher than for a triode, but surge currents of up to about 1,000 times can be tolerated. Due to the lack of heating requirements the fetron will operate at more comfortable temperatures around 65°C. The case is ruggedised by using a deep-drawn steel cap welded to a large diameter header, using the same pin arrangement for connections.

Fetrons that have been made so far include replacements for the 6EW6, 6JC6, 6AK5 and 12A7 but with ready made FET junctions currently available it is expected that the majority of common types can be simulated. More familiar types such as 6V6 and 6AQ5 are next on the list. The type number given to fetrons consists of the equivalent valve number but prefixed TS. Hence the

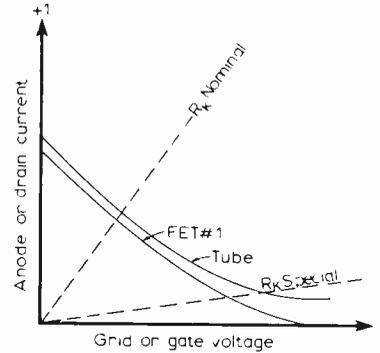


Fig. 3: Transfer characteristic of a fetron compared with a valve.

fetron for replacing the 12A7 is TS12A7.

The manufacturer who has announced these activities in fetrons is the American company Teledyne Semiconductors, who are selling in the U.K. via the distributors GDS Sales Ltd. of Slough. Prices are higher than for valves but this is offset by the long term performance advantages described. GDS Sales quotes £8 for the TS12A7 and £6.50 for the TS6AK5 for orders of 1 to 99, these being the first available in the U.K. Although this price is high the long term advantages of reliability and performance are compensatory. Small orders for these devices are being handled by the subsidiary company Best Electronics (Slough) Ltd, Michaelmas House, Salt Hill, Bath Road, Slough, Bucks, SL1 3UZ.

Elsewhere in this issue we are taking a closer look at some of the valves that still have a unique role to play in radio and electronics. Look out for our special feature "Special Valves for Communications".

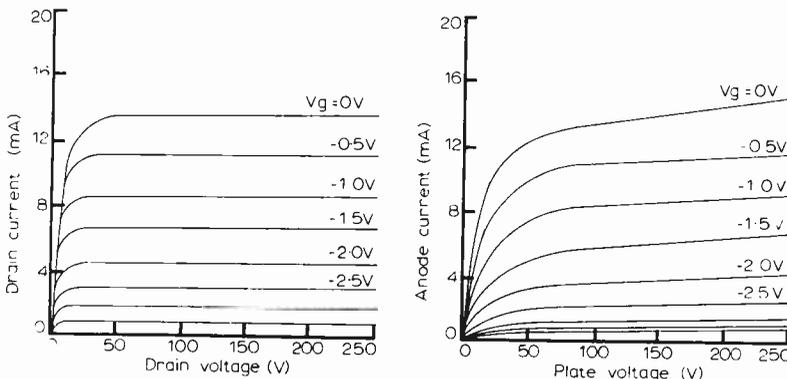


Fig. 2: Comparison of output drain characteristics with those of the 6AK5 anode.

instruments for your test bench at prices you can afford

**under
£15**



Portable VVM
£13.80

The Heath range of low-cost testers and instruments in kit form fulfils the many and varied requirements of the practical hobbyist, the engineer and others engaged in a wide range of electronic activities.

**under
£5**



Portable transistor tester
£13.80




Transistor/diode checker
£3.90




R and C substitution boxes
£4.80 and £3.90



R.F. probe
£3.50

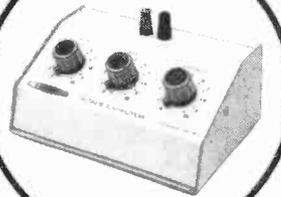

Decade capacitance box
£9.80

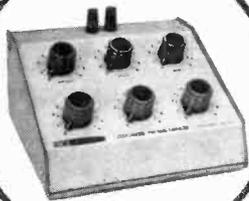

Decade resistance box
£14.80



Power supply
£9.80

No deposit terms up to

£30

Budget plans also available



Signals tracer
£13.80

Kit prices quoted

free catalogue

Our jumbo sized Heathkit catalogue is full of good things. Stereo amplifiers, tuner amplifiers, tuners, loudspeakers and audio accessories, electronic calculator, metal detectors, shortwave receivers, intercoms... even a powerful battery charger kit.

Please send me a FREE Heathkit catalogue

Name _____

Address _____

Heath (Gloucester) Limited, Department PW/5/73
Gloucester GL2 6EE. Telephone 0452 29451



(Mail order prices and specifications subject to change without notice)



Heath (Gloucester) Limited, Gloucester GL2 6EE.

BRAND NEW


SEMICONDUCTORS & COMPONENTS

GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

2C301	0.15	2N2925	0.12	2N5174	0.08	AF116	0.25	BC307	0.10	BF271	0.21
2C302	0.15	2N2925	0.12	2N5174	0.08	AF117	0.25	BC307A	0.10	BF272	0.21
2G303	0.05	Green	0.10	2N5175	0.08	AF118	0.25	BC307V1	0.10	BF273	0.21
2G304	0.05	Green	0.10	2N5176	0.08	AF121	0.25	BC308	0.09	BF274	0.21
2G306	0.30	Yellow	0.10	2N5245	0.08	AF122	0.25	BC308B	0.09	BF455	0.05
2G309	0.30	Orange	0.10	2N5190	0.08	AF126	0.19	BC309	0.10	BF459	0.05
2G344A	0.25	2N3053	0.21	2N3181	0.07	AF127	0.25	BC309A	0.10	BF459	0.05
2G345B	0.25	2N3054	0.47	2N5192	1.84	AF139	0.58	BC309B	0.10	BF459	0.05
2H871	0.15	2N3054	0.46	2N5193	1.01	AF170	0.25	BC313	0.30	BF621	0.20
2G374	0.15	2N3055	0.60	2N5194	1.10	AF172	0.25	BC327	0.84	BF661	0.27
2G381	0.22	2N3390	0.20	2N5195	1.46	AF178	0.55	BC328	0.22	BF698	0.27
2G417	0.20	2N3391	0.20	2N5245	0.08	AF179	0.45	BC337	0.19	BF710	0.21
2N1094	1.40	2N3392	0.22	2N5457	0.55	AF180	0.40	BC338	0.19	BF711	0.21
2N174	0.75	2N3392	0.18	2N5458	0.48	AF186	0.40	BCY30	0.40	BF715	0.25
2N176	0.75	2N3393	0.18	2N5459	0.38	AF200	0.35	BCY31	0.40	BF715	0.25
2N274	0.75	2N3394	0.12	2N5128	0.68	AF259	0.41	BCY32	0.60	BF729	0.25
2N285	0.75	2N3402	0.17	2N138	1.85	AF240	0.72	BCY33	0.75	BFX30	0.25
2N301	0.95	2N3403	0.19	2N139	1.85	AF279	0.64	BCY34	0.84	BFX37	0.20
2N375	1.00	2N3404	0.24	2N140	0.92	AF280	0.64	BCY34	0.85	BFX44	0.23
2N384	1.00	2N3405	0.21	2N141	0.91	AF282	0.64	BCY36	0.40	BFX63	2.48
2N388A	0.40	2N3414	0.10	2N142	0.58	AF211	0.55	BCY39	1.05	BFX68	0.50
2N404	0.48	2N3415	0.10	2N143	0.75	AL102	0.75	BCY40	0.60	BFX84	0.24
2N466	0.75	2N3416	0.15	2N152	0.92	AL103	0.70	BCY42	0.15	BFX85	0.29
2N456A	0.75	2N3417	0.21	2N153	0.81	ABY26	0.80	BCY43	0.15	BFX86	0.24
2N457A	0.80	2N3870	1.25	2N154	0.84	ABY27	0.88	BCY58	0.21	BFX87	0.25
2N491	0.20	2N3871	1.12	2N159	1.17	ABY28	0.28	BCY69	0.22	BFX88	0.20
2N564	0.28	2N3872	0.97	2N161	0.90	AF249	0.24	BCY76	0.22	BFY10	0.45
2N591	0.84	2N3702	0.10	2N200	3.49	ABY26	0.20	BCY84	0.67	BFY10	0.45
2N696	0.15	2N3703	0.10	2N201	1.05	ABY56	0.35	BCY70	0.17	BFY11	0.45
2N697	0.16	2N3704	0.14	4K521	0.55	BCY71	0.22	BCY71	0.22	BFY17	0.20
2N698	0.25	2N3705	0.10	4K500	0.78	AL103	1.25	BCY72	0.18	BFY18	0.25
2N699	0.25	2N3706	0.09	4K501	0.81	BC107	0.14	BCY78	3.47	BFY19	0.25
2N706	0.12	2N3707	0.09	4K502	0.78	BC108	0.13	BCY80	2.15	BFY20	0.20
2N706A	0.12	2N3708	0.70	4K509	0.88	BC109	0.18	BCY89	0.85	BFY22	0.40
2N708	0.18	2N3709	0.09	4K510	0.80	BC113	0.18	BCZ10	0.85	BFY27	0.20
2N709	0.88	2N3710	0.12	4K516	0.50	BC114	0.12	BCZ11	0.50	BFY41	0.48
2N711	0.30	2N3711	0.80	4K518	0.92	BC115	0.15	BD116	0.75	BFY43	0.82
2N718	0.80	2N3712	0.85	4K522	0.92	BC116	0.15	BD118	0.75	BFY60	0.18
2N720	0.60	2N3714	1.15	4K530	0.46	BC117	0.21	BD123	0.82	BFY62	0.18
2N721	0.55	2N3715	1.28	4K531	0.48	BC118	0.11	BD124	0.87	BFY65	0.15
2N914	0.92	2N3716	1.80	4K563	0.88	BC119	0.27	BD130	0.57	BFY66	0.84
2N916	0.17	2N3773	2.35	4K589	0.46	BC121	0.28	BD131	0.40	BFY66	0.41
2N918	0.20	2N3774	4.25	4K594	0.56	BC122	0.29	BD132	0.50	BFY75	0.40
2N919	0.20	2N3775	4.25	4K594	0.56	BC125	0.20	BD136	0.48	BFY77	0.24
2N929	0.14	2N3776	5.95	4K595	0.50	BC126	0.20	BD136	0.48	BFY77	0.24
2N930	0.14	2N3777	4.84	4K602	0.44	BC132	0.80	BD137	0.55	BFY78	0.84
2N1090	0.28	2N3778	2.25	4K608	0.50	BC134	0.11	BD138	0.63	BFY90	0.80
2N1091	0.24	2N3779	3.15	4K609	0.52	BC135	0.11	BD139	0.71	BFY90	0.80
2N1121	0.20	2N3780	4.50	4K610	0.58	BC136	0.15	BD140	0.88	BDX19	0.18
2N1132	0.20	2N3781	8.27	4K611	0.58	BC137	0.15	BD140	0.88	BDX19	0.18
2N1184	1.27	2N3782	8.27	4K611	0.58	BC138	0.20	BDY11	1.50	BDX21	0.20
2N1302	0.16	2N3789	1.76	4K614	0.55	BC140	0.84	BDY17	1.50	BDX26	0.34
2N1303	0.16	2N3790	2.20	4K647A	0.89	BC141	0.89	BDY18	1.75	BDX27	0.34
2N1304	0.20	2N3791	2.08	4K648A	0.44	BC142	0.84	BDY19	1.97	BDX28	0.25
2N1305	0.20	2N3792	2.00	4K660	0.60	BC143	0.21	BDY20	0.92	BDX29	0.47
2N1306	0.22	2N3794	1.10	4K661	0.49	BC144	0.24	BDY20	0.92	BDX30	0.47
2N1307	0.22	2N3819	0.37	4K661	0.49	BC145	0.21	BDY60	0.80	BDX59	0.73
2N1308	0.25	2N3820	0.47	4K662	0.46	BC147	0.11	BDY61	0.86	BDX60	0.54
2N1309	0.25	2N3823	0.82	4K664	0.56	BC148	0.10	BDY62	0.75	BDX61	0.42
2N1483	0.80	2N3824	0.75	4K636	1.10	BC149	0.13	BP116	0.28	BDX76	0.15
2N1507	0.24	2N3826	0.28	4K673	0.50	BC153	0.18	BP117	0.48	BDX77	0.20
2N1613	0.20	2N3834	0.16	AC1107	0.85	BC154	0.18	BP119	0.55	BDX78	0.25
2N1631	0.85	2N3834A	0.16	AC1107	0.85	BC157	0.14	BP121	0.88	BDW70	0.28
2N1637	0.80	2N3855	0.16	AC1113	0.18	BC158	0.18	BP123	0.27	BDY24	0.20
2N1638	0.27	2N3855A	0.16	AC1117	0.20	BC159	0.14	BP125	0.25	BDY25	0.15
2N1671	1.25	2N3856	0.16	AC1121	0.13	BC160	0.37	BP127	0.27	BDY26	0.20
2N1701	0.15	2N3856A	0.16	AC1126	0.25	BC163	0.13	BP130	0.80	BDY27	0.15
2N1702	2.15	2N3857	0.16	AC1127	0.25	BC168	0.11	BP154	0.18	BDX38	0.15
2N1711	0.17	2N3858A	0.16	AC1128	0.25	BC169	0.13	BP158	0.16	BDY39	0.15
2N1893	0.84	2N3859	0.16	AC1134	0.25	BC189	0.13	BP159	0.27	BDY51	0.25
2N2102	0.80	2N3859A	0.16	AC142K	0.25	BC170	0.11	BP160	0.28	BDY52	0.25
2N2147	0.70	2N3860	0.16	AC151Y	0.16	BC171	0.11	BP161	0.85	BDY53	0.25
2N2148	0.20	2N3866	0.70	AC152Y	0.17	BC172	0.12	BP165	0.85	BDY54	0.20
2N2192	0.40	2N3877	0.25	AC153	0.22	BC182	0.10	BP166	0.85	BDY58	0.79
2N2192A	0.40	2N3877A	0.25	AC153K	0.25	BC182L	0.12	BP167	0.18	BDY65	0.15
2N2193	0.40	2N3878	1.22	AC154	0.16	BC183	0.09	BP173	0.10	BDY78	0.40
2N2193A	0.42	2N3878	1.91	AC1176	0.18	BC183L	0.09	BP177	0.25	BDY79	0.40
2N2194	0.27	2N3900	0.20	AC176K	0.20	BC184	0.11	BP178	0.25	BDY79	0.40
2N2194A	0.20	2N3900A	0.21	AC187K	0.20	BC184L	0.11	BP185	0.85	BU104	0.09
2N2195	0.27	2N3901	0.92	AC188K	0.20	BC186	0.25	BP180	0.85	BU105	0.25
2N2195A	0.18	2N3903	0.20	AC197	0.25	BC187	0.25	BP181	0.85	C111	0.58
2N2218A	0.30	2N3904	0.17	ACY18	0.20	BC204	0.11	BP182	0.80	D40N3	0.52
2N2219	0.37	2N3905	0.21	ACY19	0.20	BC205	0.10	BP183	0.40	DET111	0.46
2N2219A	0.31	2N3906	0.22	ACY20	0.20	BC206	0.11	BP184	0.17	DET112	0.20
2N2220	0.20	2N4035	0.68	ACY21	0.18	BC207	0.10	BP185	0.17	DET113	0.20
2N2221	0.20	2N4036	0.68	ACY22	0.18	BC208	0.09	BP194	0.14	DET111	0.20
2N2222	0.31	2N4039	0.09	ACY28	0.18	BC209	0.10	BP195	0.15	GT1115	0.50
2N2222A	0.41	2N3089	0.90	ACY30	0.55	BC211	0.80	BP196	0.15	GT1119	0.85
2N2368	0.11	2N4060	0.11	ACY40	0.17	BC212K	0.10	BP197	0.15	GT1210	0.25
2N2369	0.29	2N4061	0.11	ACY41	0.17	BC212L	0.16	BP198	0.15	GT1210	0.25
2N2370	0.17	2N4062	0.10	ACY42	0.17	BC214L	0.23	BP199	0.15	GT1210	0.25
2N2646	1.50	2N4302	0.25	ACY44	0.21	BC236	0.18	BF200	0.85	GT1538	0.20
2N2647	1.20	2N4303	0.32	AD136V	0.86	BC237	0.09	BF224J	0.14	GT1538	0.20
2N2711	0.12	2N4913	0.80	AD140	0.55	BC238	0.09	BF225J	0.19	GT1873	0.12
2N2712	0.12	2N4914	0.87	AD142	0.50	BC239	0.09	BF227	0.22	GT1880	0.80
2N2713	0.17	2N4915	0.95	AD143	0.45	BC252	0.20	BF238	0.22	GT1883	0.20
2N2714	0.17	2N4916	0.90	AD149	0.86	BC253	0.18	BF244	0.15	GT1887	0.20
2N2904	0.18	2N4917	0.17	AD149V	1.26	BC257	0.09	BF245	0.48	GT1890	0.22
2N2904A	0.25	2N4918	0.50	AD149V	1.26	BC258	0.09	BF247	0.48	GT1890	0.22
2N2905	0.28	2N4919	0.53	AD181	0.87	BC258	0.09	BF247	0.48	GT1890	0.22
2N2905A	0.28	2N4920	0.6								

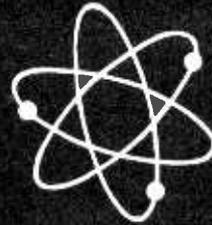

6-9V STABILISED SUPPLY

THIS inexpensive unit will enable cassette recorders, portable radios, portable record players and the like requiring 6 to 9V to be run from a 12V car battery, in or out of the car. This not only saves their internal batteries but ensures that they run at peak efficiency.

CIRCUIT

In the basic circuit, Fig. 1, the reference voltage is determined by a zener diode ZD which controls the output voltage. Tr1, a power transistor, takes a small current from the zener diode, amplifies it, and feeds the resulting current to the output circuit.

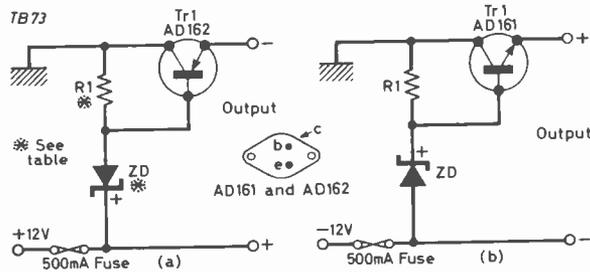


Fig. 1: Basic stabilising circuits for a) negative and (b) positive "earth".

With the output circuit left open Tr1 remains off, but as soon as a load is connected the current will increase until the voltage at the output is a little less than that of the zener diode. If for any reason the output voltage increases the voltage across Tr1's base-emitter decreases causing the collector current to drop. Conversely, if the output voltage decreases the base-emitter voltage will increase, raising the collector current. The overall effect being that the output voltage will remain constant despite varying load currents.

OVERLOAD

Although the basic circuit will work quite satisfactory, if the output leads are accidentally shorted together a heavy current will flow which may damage the transistor before the fuse can blow. To insure against this the circuit can be modified to the form shown in Fig. 2. Here, no matter what the load, even a short circuit, no more than 330mA will flow. Under normal loads the voltage across R2 will be less than the 500mV or so required to start Tr2 conducting, so the circuit will work as in Fig. 1.

J. ROWLEY

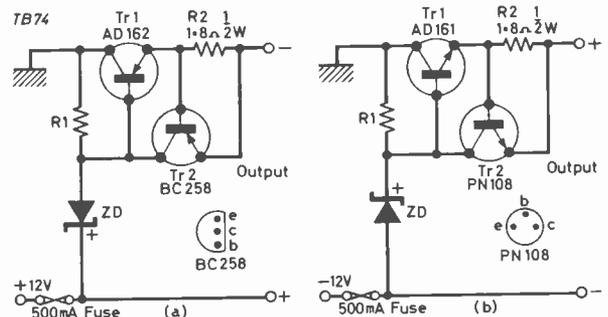


Fig. 2: Protected circuits for negative or positive "earth".

However when the current exceeds 280mA this will no longer obtain and Tr2 will start to draw current from the zener diode. At first this will have no effect, but if the voltage across R2 increases further Tr2 will draw more and more current until finally the zener will stop conducting, thus enabling the output voltage to fall to a level where no more than 330mA flows.


Output Voltage	ZD (400mW)	R1 (1/4W)
6V	6.2V	680Ω
7.3V	7.5V	390Ω
9V	9.1V	220Ω

CONSTRUCTION

The unit is built into an aluminium box approx. 3x2x2in. (Type AB12) the power transistor being bolted to the box after applying silicone grease. The few components are connected directly to the pins of the power transistor. Since the quiescent current is only about 13mA no on-off switch is fitted.

BACK NUMBERS

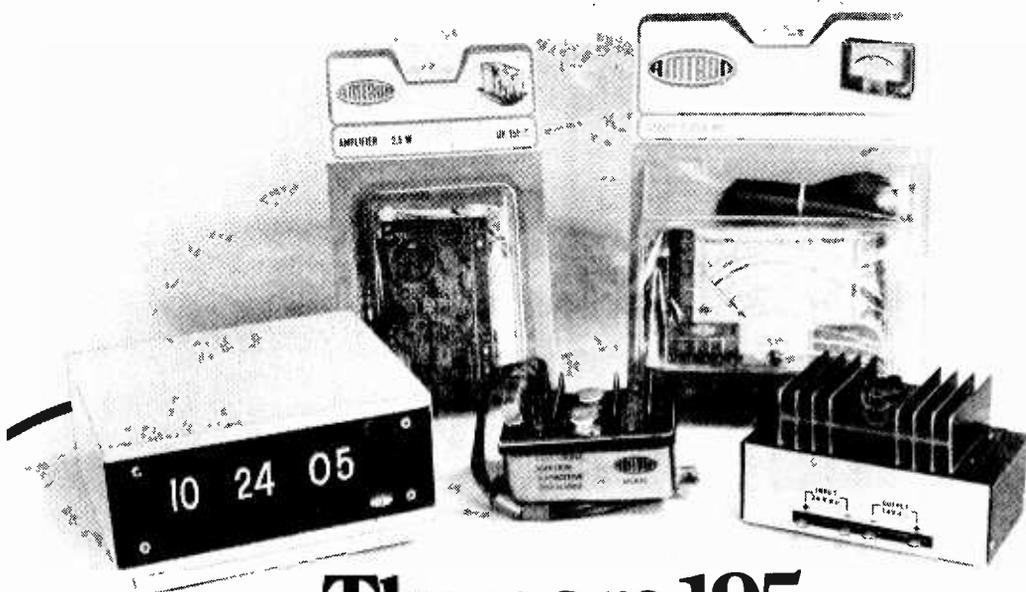We regret that the back numbers department of P.W. has now closed and consequently we are unable to supply these. Requests for specific back issues can usually be included in our 'CQ' section; there is no charge for this but it is a service between readers and P.W. is unable to meet any of these requests.



There are 195 other good reasons for buying AMTRON electronic kits

Apart from the five items shown above, there are another 195 kits to choose from in the vast AMTRON range of electronic kits.

A few examples of equipment you can construct from AMTRON kits are:

Power supplies, preamplifiers, amplifiers, L.F. instruments, accessories for musical instruments, amateur and radio control transmitters and receivers, battery chargers, electronic car accessories, psychedelic lighting equipment, measuring instruments, tuners, receivers, I.C. digital equipment.

Only 1st class fully guaranteed components are used – solder is included with every kit.

Prices range from £1.10 to £80 and each kit is sold in protective blister pack containing complete instructions.

Should you experience any difficulty in obtaining AMTRON Kits please contact us direct.

PLEASE SEND FOR BROCHURE



TRADE & EDUCATION ENQUIRIES WELCOME

AMTRON U.K. 4 & 7 CASTLE STREET HASTINGS SUSSEX TELEPHONE HASTINGS 2875

Why pay more - look at our Fantastic Bargain Offer!

PENTHOUSE

A COMPLETE AUDIO SYSTEM

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder, 4 wavebands Long/Medium/Short/VHF, 8 watts per channel (music power) output. The latest BSR CI29 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.

OUR PRICE £63.00




Credit terms £6.30 deposit plus £2.00 p. & p. followed by 12 payments of £5.32. Total Credit Terms £70.14 SEND £8.30 TODAY.


TRANSEUROPEAN

A TRANSISTORISED HI-FI STEREO RADIOGRAM SYSTEM AT LESS THAN HALF-NORMAL PRICE

The system includes elegantly styled solid state Teak finish cabinet tuner/amplifier. Push-button selection, 4 waveband VHF/FM, short, medium & long wavebands. The latest 4-speed B.S.R. Mono/Stereo record changer with two 10in. X 6in. matching elliptical speakers. Supplied ready for housing. **EASILY FITTED - NO TECHNICAL KNOWLEDGE NECESSARY. OUR PRICE £39.95.** Credit Terms of first payment of £3.95. 10 payments of £4.10. Total credit price £44.95, p. & p. £2. SEND £5.95 TODAY

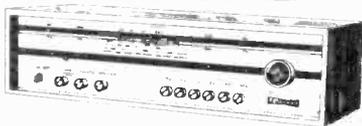

THE AVON AUDIO SYSTEM

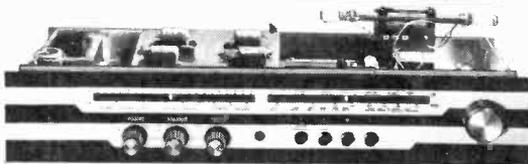

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz. **BSR 4 SPEED STEREO/MONO RECORD CHANGER** plays all types or 7in., 10in., and 12in. Mono of Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £37.00. Credit Terms £3.70 deposit plus £2 Post & Packing followed by 12 payments of £3.15 (Total Credit Terms £41.50) Don't miss this bargain.

SEND £5.70 TODAY

ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

Please send me free details of your range

Name

Address

PWS/73

LEWIS radio 100, Chase Side London N14
Tel: 01-886 3733/9666

Post coupon NOW for...
FREE leaflets

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. £2.10p.

B.F.W. 10 Fet. New (unmarked) 5 for £1.00p.

PINNACLE LOW NOISE CASSETTES C60—50p/C90—75p C120—£1.

P.C BOARDS (not computer panels).

1 off 6 transistors single wave band.

1 off 4 transistor audio

1 off 3 transistor £1.50 the three.

Encapsulated bridge rectifier (itt usd 3 3mdh) 100 PIV 2 amps. 50p each, 3 for £1.25.

Transistor F.M. Stereo Multiplex Decoder. Size: 5 1/2 x 2 1/4 x 1 1/2. As used in well known British stereo units with circuit. £3.75.

GARRARD SP25 MK. 11 less Cartridge. £10.50.

10 VOLUME CONTROLS consisting of 2 off each.

100K log. ganged L/S—20K log. ganged L/S.

470K log. D/P Switch—10K lin. L/S—50K lin. L/S. £1.25.

4 PHONO SOCKETS ON PANEL. 10 panels for £1.25.

12 PLASTIC KNOBS. Chrome and Gold, 3 types—4 off each—spring clip £1.25.

10 COMPUTER PANELS packed with components including one panel with 2 Power Transistors. £1.00.

SLIDER CONTROLS (less knobs)

25K Log or Lin single 30p.

10K—100K Log ganged 50p.

100K—100K Log ganged 50p.

PLEASE ADD 10% V.A.T. AFTER 1st APRIL.

All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.12. DAF96, DF96, DK96, DL96, 4 for £1.55.

1R5	-28	30C17	-76	EAF42	-50	EM80	-38	PCF808	-68	U801	-75
1R5	-22	30C18	-57	EB91	-12	EM81	-36	PCL82	-30	UABC80	-31
1T4	-16	30F5	-64	EBC33	-40	EM84	-32	PCL83	-55	UAF42	-50
384	-26	30FL1	-65	EBC41	-49	EM87	-50	PCL84	-38	UBC41	-45
3V4	-47	30FL12	-89	EBC81	-30	EY51	-36	PCL85	-38	UBF80	-34
6U4G	-31	30FL14	-68	EBC90	-22	EY86	-29	PCL86	-37	UBF89	-32
6V4C	-35	30L1	-29	EBF80	-32	EY87	-29	PCL88	-80	UCC84	-38
6X3GT	-30	30L15	-70	EBF83	-39	EZ40	-39	PCL800	-89	UCC85	-85
5Z4G	-35	30L17	-70	EBF89	-29	EZ41	-39	PCL905	-88	UCF80	-30
6/30L2	-54	30P4	-54	ECC81	-17	EZ80	-21	PEN44	-77	UCH42	-59
6AM6	-13	30P12	-69	ECC82	-20	EZ81	-22	PEN36C	-70	UCH81	-80
6AQ5	-22	30P19	-54	ECC83	-35	EZ90	-25	PFL200	-51	UCL82	-52
6AT6	-20	30P21	-58	ECC85	-34	GZ30	-34	PL36	-48	UCL83	-55
6AU6	-20	30P13	-69	ECC804	-54	GZ32	-40	PL81	-43	UP41	-52
6BA6	-20	30P14	-80	ECC80	-30	K741	-77	PL81A	-47	UF89	-30
6BE6	-21	35L6GT	-45	ECCF82	-28	K761	-65	PL82	-31	UL41	-53
6BJ6	-41	35W4	-25	ECH35	-55	K766	-78	PL83	-38	UL84	-80
6BW7	-50	35Z4GT	-25	ECH42	-59	LN319	-68	PL84	-30	UM64	-22
6F14	-35	50C26G	-68	ECH81	-29	LN329	-80	PL500	-63	UY41	-39
6F23	-68	807	-49	ECH93	-38	LN339	-65	PL504	-63	UY85	-25
6P25	-50	AC/VP2	-77	ECH84	-35	N78	£1.05	PM84	-30	VP4B	-77
6J5GT	-20	B349	-70	ECL80	-30	P61	-40	PX25	-95	W77	-43
6J7G	-24	B729	-54	ECL82	-29	PABC80	-31	PY32	-52	Z77	-22
8K7G	-12	COH35	-67	ECL86	-35	PC86	-44	PY33	-52	Transistors	
6K8G	-36	CY31	-28	EPF39	-38	PC88	-44	PY81	-25	AC107	-17
6Q7G	-35	DAF91	-22	EP41	-27	PC89	-42	PY82	-25	AC127	-18
68L7GT	-32	DAF96	-38	EP80	-23	PC97	-38	PY83	-26	AD140	-37
68N7GT	-32	DF91	-16	EF85	-28	PC900	-29	PY88	-33	AF115	-20
6V6G	-28	DF96	-36	EP86	-30	PC834	-29	PY800	-31	AF116	-20
6V6GT	-28	DH77	-20	EP89	-26	PCC85	-23	PY801	-31	AF117	-20
6X4	-23	DK32	-33	EP91	-13	PC838	-38	R19	-30	AF125	-17
6X5GT	-25	DK91	-28	EP92	-27	PC899	-45	IZ20	-70	AF127	-17
10P13	-53	DK92	-50	EP98	-65	PCC189	-45	UZ5	-75	OC26	-26
12AT7	-17	DK96	-45	EP183	-27	PC805	-70	UZ6	-26	OC44	-18
12AU7	-20	DL35	-40	EF184	-29	PCF80	-26	U47	-73	OC45	-12
12AX7	-22	DL92	-26	EH90	-36	PCF82	-33	U49	-70	OC71	-12
19B6RG	-75	DL94	-47	EL33	-55	PCF86	-48	U52	-31	OC72	-12
20E2	-67	DL96	-38	EL34	-48	PCF800	-69	U75	-24	OC75	-12
20P3	-75	EY86	-24	EL41	-54	PCF801	-28	U91	-55	OC81	-12
25L6GT	-19	EY86	-24	EL84	-23	PCF801	-28	U93	-31	OC81D	-12
25U4GT	-57	DY87	-24	EL90	-26	PCF802	-39	U251	-61	OC82	-12
30C1	-26	DY802	-33	EL95	-33	PCF805	-57	U301	-38	OC82D	-12
30C15	-58	EABC80	-32	EL500	-62	PCF806	-56	U329	-68	OC170	-28

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Minimum post/packing on 1 valve 7p., on each additional valve,

(3p. per valve extra)

Any parcel insured against damage in transit 3p extra.

practically wireless

commentary by

HENRY

No. 99

Age cannot
wither them

WHERE wireless engineers foregather, talk inevitably veers toward: 'I remember ...'

It is either a model with such idiosyncracies that a catalogue of 'common faults' would have called for an appendix to the service manual, a manufacturer whose crass perfidy extended to an invoice before the goods arrived—or worse, so long afterwards that one had to guess at the cost of the spares before one dared complete the repair—or a customer.

But my subject today is not so much the trials and tribulations of the working engineer as this 'harking back' tendency we all evince, once we converse with fellows of like mind. Go to a meeting of the RSGB, the SERT, the BARTG or even your local Gramophone Society and before the last strains of the demonstration or mutters of the lecture have died away, everybody is avidly recounting his or her personal experiences.



... a donkey-driven gramophone.

Watching two members of the Royal Television Society taking coffee last week reminded me of Ralph Richardson and John Gielgud in the Royal Court Theatre production of *Home*. Parallel tracks of reminiscence, meeting rarely at some way-station. From the few words I caught in that BBC Hospitality Room, member A was waffling on about videotape while the other had some bee in

his bonnet about phase-lock loop and pulse-code-modulation.

Henry was dying to know how Mr. B allied the two subjects, but couldn't find out because the charming production assistant he was trying to chat up with his memories of Marconi would insist on relating her opinions of Arthur Negus every time I had to pause for breath.

All this is brought on by hearing about the Fetron.

The Fetron is a genuine solid state substitute, mounted in a case like a valve, with pin formation and characteristics of the valve it is meant to replace.

You can read the ins and outs of it in the "Special Product Report" elsewhere in this issue, if it grips your curiosity like it did mine. Suffice it to say on this page that all those "everlasting" relay stations, built around valves designed to run forever, could not die without putting up a fight first.

Use of the Fetron saves major circuit modification when a valve-change is needed. Ain't science wunnerful?

Trouble is, Henry took a look at the types available and found there listed the dear old 12AT7. Now the TS12AT7 sounds a good idea until you remember some of those old 'universal' radiograms, and one or two series-heated television sets that used them.

What happens if you plug in a Fetron? Have they made a resistive heater 'bridge', or do we have to solder a resistor across the socket? And, if we do, shouldn't there be a thermistor provided? Should we not also protect the h.t. line because the Fetron is operative immediately?

So many questions... reminds Henry of that unfortunate chap in an electronics magazine who offered a simpler way of getting over some stabiliser problems. Only snag was, somebody had to remember to turn the control back to zero after use unless the

next chap along blew the thing up—you know, the way your loudspeaker creases when you have left the amplifier gain up high and a 'friend' flicks your stylus!

Well, the upshot of this poor chap's sensible economy was that



... and the inevitable happened.

electronic geniuses wrote in, both calling him gormless and detailing complicated protection circuits that would automatically switch off, from any given function. I wonder if Mrs. Mary W. would like one built into every TV?

I remember one TV we could never switch 'Off' because the maker had fitted too-substantial suppressors across the contacts.

We all tend to hark back. You should see the glee with which Colin Riches unearths a donkey-driven gramophone. At the wedding of a friend's daughter, hardly out of her teens, one of the speakers, Marketing Director of a worldwide Telecommunications company, had to remind the reception that his first acquaintance with the charming Sally was when she sat in his lap—at eighteen months—and the inevitable happened.

He might, at least, have reminded them of the days when he was hawking cheap radios round the council estates. It is just as funny a story. Remind me to tell it to you, one day ...

Special Valves

PART 1 COMMUNICATION TYPES

M.K.TITMAN B. Sc(Eng), C. Eng , MIEE.

THERMIONIC devices still have a wide range of applications in modern electronic circuits and, despite the semiconductor takeover, they remain essential components in a variety of applications from high power r.f. amplifiers to electro-optical transducers.

The requirement for valves for u.h.f. and s.h.f. has led to the development of special techniques. The following valves were all developed from the necessity to exploit new ways to enable communication systems to use the wide bandwidths available at u.h.f. and microwave frequencies. The principles used are mathematically complex but their operation can be readily understood.

DISC SEAL VALVES

The form of construction used for both triode and tetrode configurations is illustrated in Fig. 1. The structure consists of a thimble-like cathode, spaced from a parallel wire grid further separated from a disc anode. The structures are very rigidly held by the ceramic space discs and because of the annular configuration co-axial input and output terminations can be used. The advantage of this system is that high power operation with reasonable efficiency in the GHz region is possible.

Disc seal triodes are used for amplifier and oscillator applications from 0.5GHz to 4GHz frequencies, at power levels of 1W to 600W. Typical values of g_m are 6mA/V to 25mA/V. At lower power levels

(<25W) the envelope is designed for convection cooling but forced air cooling is used for the higher power levels. Examples of this valve type are the ES157 at 2W, and TDO4-20 at 12W.

KLYSTRONS

Klystrons are also essentially microwave valves which operate as oscillators in the frequency range from u.h.f. to more than 100GHz. Generally they are available for discrete commercial frequencies such as 6, 7, 8 or 9GHz and mechanical tuning by micrometer adjustment is possible.

The klystron consists of a cavity (or for power devices, multiple cavities) through which a stream of electrons is beamed from a normal electron gun assembly, as shown in Fig. 2. The electrons are velocity modulated by a field produced by a toroidal modulating structure known as a rhumbatron. The electrons therefore become bunched in regions of high electron density and rarified in low density regions, as they travel through a further section known as the drift space. Consequently if critical frequencies are utilised the bunching allows resonant oscillation to occur in a mode controlled by the rhumbatron.

Power levels for high frequencies are in the region of 1kW with special u.h.f. power devices operating at 460 to 1000MHz at levels of 20kW. The electronic tuning range for such devices is from 30 to 100MHz,

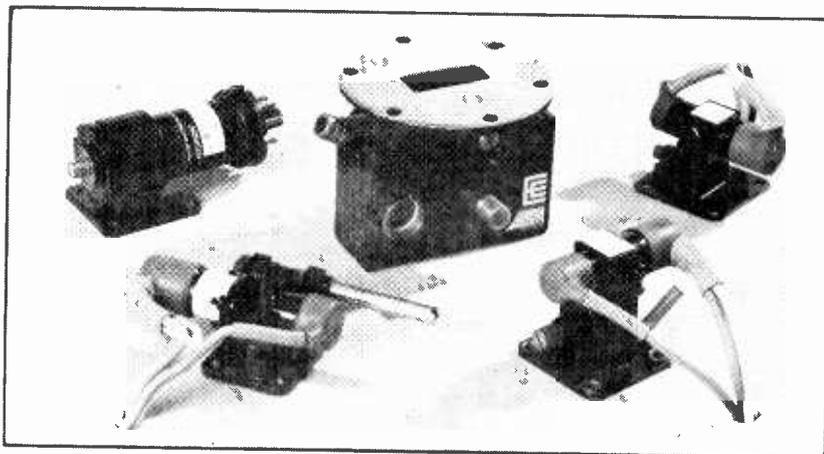


Fig. 1: at left, shows the general configuration of a disc seal valve. The picture shows a collection of oscillator klystrons, the centre one being used in communications relay equipment. The others are used in radar local oscillators.

ELECTROKIT

Now available from one company are kits for many of the articles published in the Electronics, Radio and TV Journals. Examples of our range are:

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971) £9.50. This kit includes all the parts for the assembly of this popular and reliable system. The hardware and the construction data are included.

DRILL SPEED CONTROLLER (E.E. Aug. 1972) Kit consists of resistors, rectifiers, thyristors and tag board as specified in the article, price **£1.15**. Kit with M.K. box, switch and plate included **£2.30**.

ELECTRONIC PIANO (P.E. Sept. 1972)
We can supply the various sections for this article in kit form:—

POWER SUPPLY £6.60, including all semiconductors, resistors, capacitors, transformer, heat sink and hardware less P.C.B.

PREAMP AND TREMELO £3.20, complete with switches hardware and electronic components, less P.C.B.

MAIN AMP £4.20, complete with IC-12, electronic components and P.C.B.

13 PITCH BOARDS £39.50. Kit contains all the resistors, capacitors and semiconductors as published, but not the P.C.B's or the inductor.

LIGHT DIMMER. Kit contains all parts including circuit and construction data, 480 watts, fully suppressed. Price **£2.10**.

MUSIC MAKER ELECTRONIC ORGAN (P.W. Nov. 1972) complete kit **£4.40** or kit less resistors, P.C.B. and plastic box **£2.80**. Stylus not supplied.

MIGHTY MIDGET (P.W. Jan. 1973) kit contains all parts, less the battery, box and knob, **£2.25**.

TRIFFID RADIO (P.E. Feb. 1973). Kit includes all parts listed, less "tuning coil" and "miscellaneous components". **£4.95**. Ferrite rod and wire, optional extra at **50p**, P.C.B. optional extra at **65p**.

We shall be offering kits for most articles published in the popular electronics magazines and will be pleased to quote prices.



Send for details of kits available (please enclose S.A.E.)

All kits sent POST FREE within the limits of U.K.

Please Note. We reserve the right to withdraw kits without prior notification.

Please note, prices shown do not allow for VAT. Please add 10% to your order.

ELECTROKIT

12 Lauderdale Road, London, W.9
Telephone 01-286 0011

Mon.-Fri. 9.30-5.30 Thurs. 9.30-6.30

TV's 19" NOW £11.95

TWO YEARS' GUARANTEE
ALL MODELS

405/625: 19" £25.95

FREE 23" £35.95



CATALOGUE CARR £1.95

COLOUR TV 19" £145
OR 25" £185

LIMITED SUPPLY, REGRET PERSONAL CALLERS ONLY
A SELECTION OF RECENT YEARS MODELS
U.K. MANUFACTURE

TV TUBES REBUILT
GUARANTEED 2 YEARS

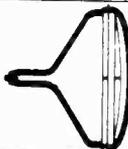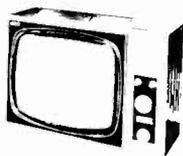17" and 19" £5.95, 21" and 23" £6.45
Exchange Bowls carr. 55p



COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 22p.
Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p.
Record Player Cabinets. £3.75p. Designed for the modern auto-changer. Size 17" x 15" x 7 1/2". p.p. 55p.
Radio: £3.95. 8 transistor LW/MW. Free case, battery. Post 15p.
Precision Tape Motors: £1.95. 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature. AM. Post free.
Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p.
Press Button VHF Tuner 75p. Brand new, takes PCF806, PCC89. Post 25p.
Valve £1.80 50p.

SPECIAL OFFER
Pots: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg. 100. KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg.

DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12. Phone 01-478 6001-2-3

BARGAIN PARCELS 14lb at £1.45 plus 32 1/2p p.p.; 28lb at £2.75 plus 52 1/2p p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save ££s. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 09J 4 1/2 in. dia. Length 15in. Also 7BP7. All unused as new. Price £1.40 post paid.

NEW HEAVY COAX CABLE dia. 1/2" 70 ohms approx. 50ft. lengths £1.40. p. & p. 30p. 100 ft. lengths £2.70. p. & p. 50p.

AERIALS. New Condition Whip Type, 4ft. 20p; 11ft. 75p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above. 62 1/2p. p. & p. 25p.

CRYSTALS AS NEW. Hc 6u, 5,345; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s. 50p each plus 8p p.p.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2 P. & P. 25p. minimum order of six.

ANY HEIGHT AERIAL TUBULAR SECTIONS 3/4" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 20p p. & p. 5p each. Minimum order 6.

AS NEW AERIAL TUNER UNIT No. 6 RF, consisting of 1 1/2 inch 500 mico/ampmeter 3 gang tuner 75 PF geared BNC type socket size 5 1/2" x 4 1/2" x 5". Price £1.50, p. & p. 25p.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft 47 1/2p. 100ft. 55p, p. & p. 20p.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition. £1 each section. Carriage 35p each section. 1/2" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1 + 30p p.p.

AS NEW 500ua PENNY SIZE METERS complete with jack plug price £1 each, p. & p. 10p.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

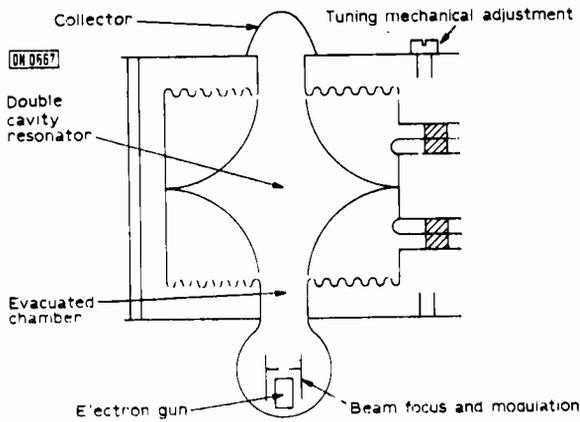


Fig. 2: Internal arrangement of a klystron valve.

whilst the mechanical range is considerably more. Typical device types are the KS6, 7, 9 family and YK1010 to 1090. Most of these utilise waveguide outputs but some have coaxial probes. The higher power devices require forced air cooling, whilst the u.h.f. power units need a cooling water supply.

TRAVELLING WAVE TUBES

These are microwave power amplifier valves used extensively in communication systems particularly for microwave links. The basic construction is shown in Fig. 3 and consists of an electron gun assembly, a modulating helix structure and a collector electrode. The electron gun forms a narrow electron beam focused by means of the grid and anode. The beam passes along the axis of an accurately formed helix structure and is continually focussed by a magnet system. The modulating microwave frequency is passed along the helix and travels at approximately the same speed as electrons in the beam. Thus the r.f. field produces an electric field which velocity modulates the electron beam as it travels along the helix axis. After modulation the electron beam bombards the collector electrode which is often water cooled.

For low power valves the helix is of wire but for power devices a ring bar structure is used. As the helix is in a long glass envelope, heat dissipation is by radiation and thus the power is limited, especially since the mechanical helix structure must be very accurate. For very high power devices a ring-bar helix system is used and is a development of the

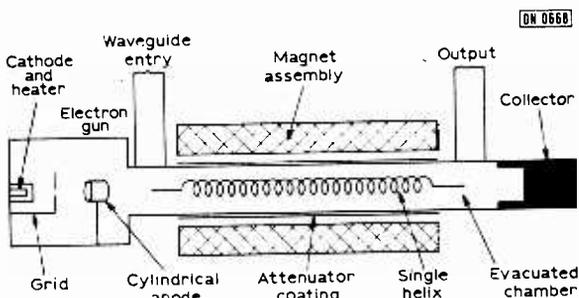


Fig. 3: Diagram to illustrate the construction of a travelling wave tube.

cross-wound opposite band helix system. Where very high power is necessary the ring bar structure is supported by annular beryllium insulators of high thermal conductivity.

Travelling wave tubes are very efficient microwave amplifiers which produce amplitude modulated output signals. The frequency range is determined by the mechanical structure and the helix in particular and, for the simple helix, it is roughly an octave about the centre frequencies from 1 to 9GHz.


Power levels for continuous operation are usually 1 to 10W but kilowatts are possible while operation in pulsed modes can result in peak power levels in the megawatt region. The band-width at high power levels is usually reduced to as low as 10% or 400MHz at 4GHz.

Both forward and backward wound helices are used and typical gains in the X band are in the region of 30 to 40dB, with noise factors of 20 to 28dB. Generally they are designed to fit into special mountings which incorporate the permanent magnet systems. The input and output are usually taken directly from waveguide connections, with the forward wave tubes operating as amplifiers and the backward wave tubes as oscillators. Typical forward wave types are LB4-20 and 30, at 4GHz and LB6-15 to 25 at 6GHz, with backward wave oscillators like the YH1100 and BA16.


MAGNETRONS

These are essentially high efficiency oscillator valves and are used for producing fixed frequency, fixed amplitude oscillations and, in a pulsed mode, are widely used in radar equipment. The normal frequency is in the X band (5.2 to 10.9GHz) although other bands are covered.

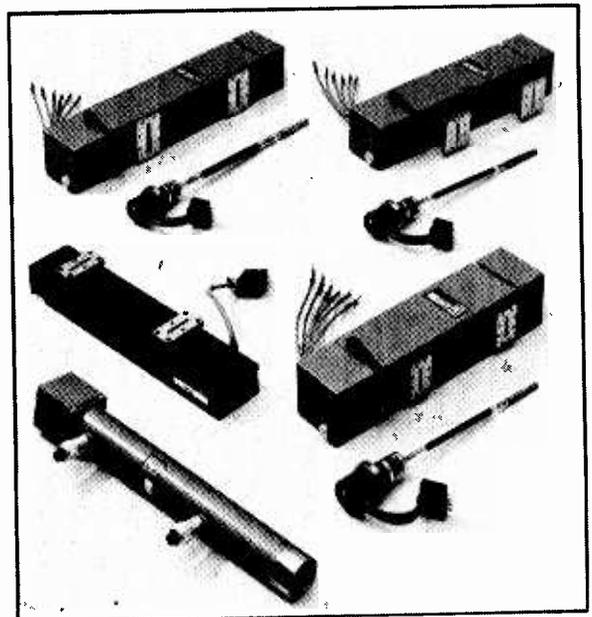The magnetron, as illustrated in Fig. 4, consists of one or more very carefully machined cylindrical cavities with a cathode adjacent to the cylinder and formed of a thin wire. A permanent magnet provides



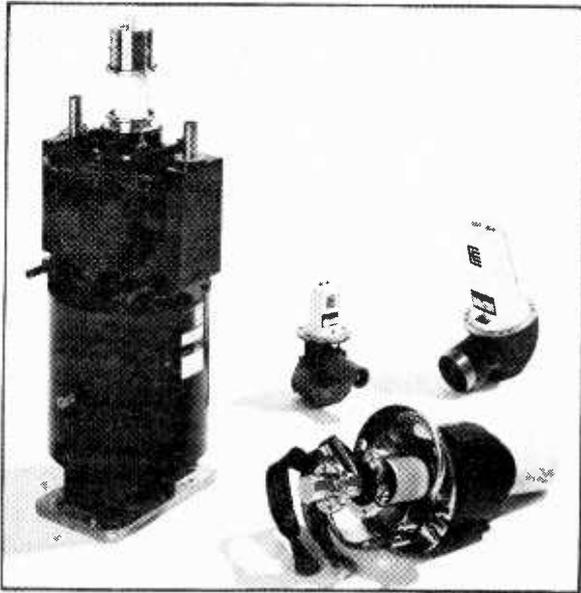A selection of travelling wave tubes used for communications in the S, C and X-bands. Three are replaceable types, shown beside their mounts.



In this collection of magnetrons the large one is an L-band 2.3MW tunable pulse magnetron intended for high power surveillance radar. In the foreground is a 25kW CW model for industrial use. The remaining two magnetrons are rated at 50kW and 900kW pulse operation in the S-band.

a magnetic flux at right angles to the cylinder and thus at right angles to the electric field formed by the diode. Electrons released from the cathode travel in a circular path and at a given frequency just graze the anode. The oscillation frequency is determined by the physical characteristic of the cylinder and therefore is often fixed. Slight tuning is however provided with some magnetrons.

Continuous-wave magnetrons are available in the frequency range 8 to 9.5GHz at power levels of 6W to 20W. Typical operating conditions are $V_a=1kV$, $I_a=50mA$, $V_h=6.3$ and I_h starting at 1A. Typical types are JPT 9-01 and JPG 8-01.

Pulsed magnetrons are designed for short pulse durations in the region 1 to $5\mu s$ for X band devices at approximately 9GHz. Power outputs range from 25W to 50kW with devices such as JPT9-02 and YJ1050. The lower frequency 1.25GHz (L Band) and 5.5GHz (C Band) devices operate at higher power levels up to 1,000kW.

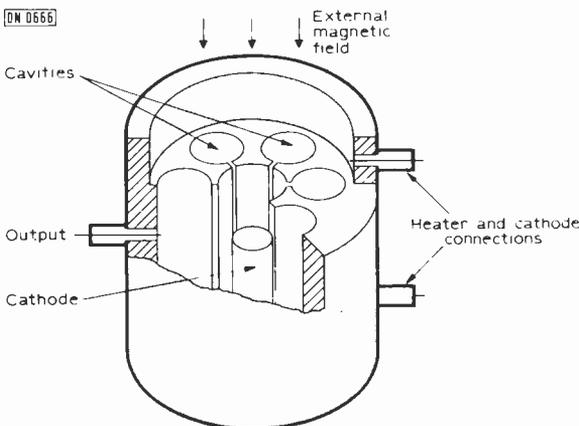


Fig. 4: General arrangement of a multiple cavity magnetron.

FUTURE TRENDS

Although trends continue towards the use of semiconductor devices, the power transmitter valve at all frequencies cannot yet be replaced directly. Thus power valves at all frequencies are still of very considerable use and development continues to improve all these designs.

A trend which undoubtedly will continue is the replacement of high power microwave transmitters by low power solid state components such as varactor chains. This has been made possible by improved receiver and aerial design.

We are indebted to the English Electric Valve Co. of Chelmsford for permission to reproduce the photographs in this article.

TO BE CONTINUED

TELEVISION

MAY ISSUE

THE LID OFF VARICAPS

What exactly is a varicap tuner, how does it work and what goes wrong with it? This month Keith Cummins looks at all aspects of varicap tuners and sums up the pros and cons. Including an insight into the tricky servicing problems that can arise with their use.

TRANSISTOR IF PREAMPLIFIER

It is often worthwhile converting dual-standard sets to single-standard operation and fitting a modern transistor u.h.f. tuner. When this is done it is convenient to remove the v.h.f. tuner, but this usually means the need for extra gain between the u.h.f. tuner and the i.f. strip. A simple transistor i.f. pre-amplifier that has been used in converting sets such as the BRC 850 chassis is featured this month.

ASSESSING COLOUR RECEIVER PERFORMANCE

In the concluding article in his series E. J. Hoare provides a detailed account of how to assess the colour performance of receivers—purity and convergence etc. and the operation of the colour circuits.

SERVICE NOTEBOOK

Amongst the items in George Wilding's Service Notebook this month is a detailed procedure for tackling that common condition, lack of e.h.t.

PLUS ALL THE REGULAR FEATURES

ON SALE APRIL 16

(★ All prices include V.A.T.)

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and you might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPER-SEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use. We're almost giving them away at only **£19.47**—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! ★ Send quickly, after receiving goods test 7 days, refund if not delighted. Elegant black & chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! The Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space communications. **Yes, EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. **VHF: FM/USW, AM: MW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world!** Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!) Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for ultra perfection of reproduction and tone! Press-button dial tuning—available anywhere—runs economically on standard batteries or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE 14ins x 10ins x 4ins overall approx.** Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram, **ONLY £19.47** (with mains/battery eliminator £1.62 extra). **BOX, POST, ETC. 55p. BUT WAIT, for only 50p extra you get the sensational "COMPUTERISED" WORD TUNING GUIDE** (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K., when abroad. (NO GUESSING! NO MESSING!) PLUS Standard "longlife" batteries PLUS ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.)

THOUSANDS OF MILES REDUCED TO INCHES?
1973 RUSSIAN RADIO TECHNOLOGY
SHRINKS THE WORLD! *COMPUTERISED?



BRAND NEW FABULOUS ASTRAD 17
PORTABLE RADIO & COMMUNICATIONS RECEIVER



28 TRANSISTORS AND DIODES!
WAVEBANDS:
 STANDARD LONG and MEDIUM
 Plus 5 SHORT WAVEBANDS
 Plus ULTRA SHORT WAVES
 (V.H.F. AM: FM, MW, LW, USW.)
£19.47 BOX POST ETC. 55p
 MAINS/BATTERY ELIMINATOR £1.62 extra

FIRST TIME EVER!
 NOW AVAILABLE WITH **FABULOUS COMPUTERISED WORLD TUNING GUIDE!**
 NO MORE GUESSWORK—INSTANT DATA at your fingertips—enables you to **TUNE IN A FLASH** to transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £21.60 NOW!**
fabulous BRAND NEW SOLID STATE
BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER
 This equipment's got EVERYTHING!
RECOMMENDED RETAIL PRICE £44
OUR PRICE £22.40 CARR. ETC. 39p
 WITH REMOTE CONTROL MICROPHONE

FIRST TIME EVER! SAVE £15.21!
BRAND NEW AC/DC BATTERY/MAINS
Cassette TAPE RECORDER & PLAYER
FIRST CLASS MAKERS
 With remote control microphone.
WE COULD CHARGE UP TO £26.97!
OUR PRICE £11.76 POST ETC. 34p

(★ All prices include V.A.T.)
Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined!** & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play anything, anywhere! **RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE!** Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! ★ Separate ON/OFF and HI-LO volume controls! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker sockets! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in approx.). Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. **AND the amazing built-in full circuit VHF, AM/FM Radio** gives you superb clarity of tone, incredible regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player ALONE! £22.40, carr. etc. 39p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand, **WITH WRITTEN GUARANTEE**. Send quickly, after receiving goods test 7 days, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 28p extra if required.

(★ All prices include V.A.T.)
THE ONE STEP FORWARD EVERYONE HAS WAITED FOR: NOW a superb ultra portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £11.76!** Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "PIANO KEYBOARD CONTROL PANEL for latest MASTER SWITCH control) AND **AUTOMATIC LEVEL CONTROL**. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or outside! Runs on standard batteries AND 220/240V AC mains. Separate out for remote control microphone, etc. Size 9 1/2in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Recommended selling price £26.97!) **OUR PRICE ONLY £11.76**, post etc. 34p. ★ Send quickly, after receiving goods test 7 days—refund if not delighted. **BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries AND microphone stand all for 55p extra, if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn store.)

SHOPERTUNITIES LTD.

Dept. WP/30, 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON, W12 8AQ (Thurs. 1, Late Night shopping Fri. 7).


Also at 37/39 HIGH HOLBORN (opp. Chancery Lane), LONDON, W.C.1 (Thurs 7 p.m.). BOTH OPEN MON TO SAT 9 A.M. TO 6 P.M.

TERMS Retail mail order subject to £1.00 minimum order.
 Cash with order only. Trade and educational establishments
 M/AC on application (minimum £5.00).
 Postage 10p inland, 25p. Europe
 GUARANTEE: All goods carry full manufacturer's
 warranty. Get in touch today for a complete
 run-down of devices available from SCS (include SAE)



SCS COMPONENTS, P.O. Box 26
 Wembley, Middlesex HA0 1YY
 The 'Professional' Amateur Supplier

device of the month ZN414

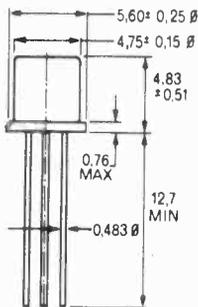


The Ferranti ZN414 is a complete a.m. radio circuit which operates from 1.1 to 1.8 volts and requires only battery, earphones and antenna plus a tuning capacitor and two decoupling capacitors. The ZN414 features: medium and long waveband, good stability on assembly, no setting up of IF coils, plus much more.

a complete a.m radio circuit for just

£1.20

compatible device MFC4000

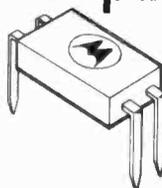


The Motorola 1/4-Watt Audio Amplifier is designed for the output stage of battery powered portable radios.

- * 250 mW of Audio Output Power
- * Low Standby Current— 3.5 mA typical
- * Low Harmonic Distortion
- * Reduces Component Count in Portable Radios by Two Transformers and Two Transistors
- * Eliminates Costly Component Matching Requirements

motorola 1/4 watt
 audio amplifier
 MFC4000

50p

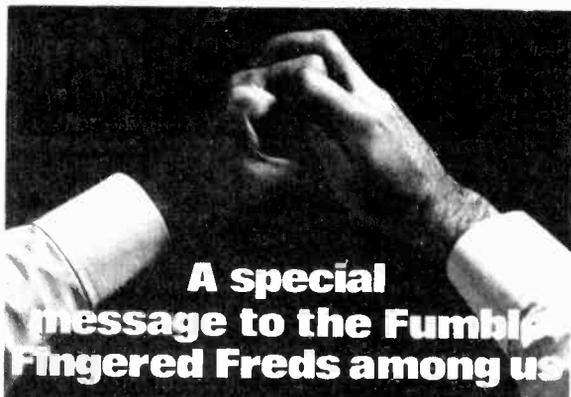

A special message to the Fumbling Fingered Freds among us

NEW STEPHENSPEAKERS

A new range of loudspeaker kits and cabinets with a style and specification for every purpose. You'll be cheating a bit if you tell your friends "made it myself". We supply superb craftsmen built fully finished cabinets in beautiful stain and scuff resistant vinyl in white or teak.

Just fit the speaker cloth (supplied) and screw in your speaker.

HIGH QUALITY
 AT LOW COST

Send for our free booklet
 "Choosing a Speaker"



STEPHENSPEAKERS,
 WILMSLOW AUDIO, Dept. 'PW', Swan
 Works, Bank Square, Wilmslow SK9 1HF

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDEGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 4285

The T.V. Graveyard of the North, as seen on T.V. Close to the Motorway. Plenty of Free Parking Space. Est. 1935.

STUDENTS WIRELESS PROCEDURE TRAINING SET. Comprising Mike, Single LR Phone and connector. In small wood case. In good condition, but untested. A gift, £1.35. Post paid.

NEW TOP QUALITY MAINS TRANSFORMERS. 250v-250v at 80ma. 6-3v at 4 Amp. Not to be missed at £1.80. Post paid. Weight 10 lbs.

COMPLETE UNTESTED T.V. SETS. With back and all valves. BBC1 & ITV. 17" 90° Tube £1. 17" 110° Tube £2.20. 19" £3.30. Carr. and Ins. on any set £1.65.

RECLAIMED T.V. TUBES, all with 12 months Guarantee. AW43/88 £1.65. AW43/80 £1.65. MW43/69 £1.10. Carriage and Ins. on any Tube £1.65.

1/2CWT. OF EX GOVERNMENT ELECTRONIC SCRAP. Resistors, Panels, Gears, etc. 30p. Carr. 80p

19" UNTESTED BBC2 SETS. When available £6. Carriage and Ins. £1.65.


SPEAKERS. Removed from T.V. sets. all 3 ohm. 7 x 4", 8 x 2 1/2", 6 x 4" 27p, post 11p.

TOP QUALITY TAPE. Reel to reel. 5" ST. 44p. 5" LP. 55p. 5 1/2" LP. 60p. 7" ST. 66p. 7" LP. 80p. Post on any Tape 11p. Tapes Cassette Type. C60 35p. C90 45p. C120 55p.

JAP EARPIECE. 8 ohm Magnetic 2-5 12p. 3-5 12p.

EX EQUIPMENT VALVES. All tested on our Mullard Valve Tester before despatch. 3 months guarantee on all Valves. Single Valves Post 3p. Over post paid.

ARPI2	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	14p	U191	20p
EBF89	15p	PCL83	15p	68W7	12p
ECC81	12p	PCL84	15p	6U4	12p
ECC82	12p	PL82	10p	6F23	20p
EF91	5p	PL83	10p	20P1	15p
EY86	22p	PL36	17p	20P3	12p
EF183	20p	PY81	10p	30F5	12p
EF184	20p	PY801	17p	30FL1	20p
		PY800	17p		

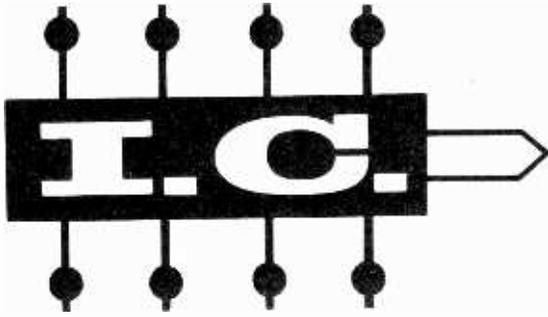

OF THE MONTH

L.A.J. IRELAND

Number 37

SGS NE555 Precision Timer

A highly stable timing device, type NE555, recently released by SGS, is the topic for this month's article. It allows precision timing from microseconds to hours with a mere handful of components; its uses however are not limited solely to the timing field as it can also find wide application in such diverse spheres as pulse generation, frequency division, pulse-width modulation, etc., to mention but a few. Such versatility coupled with low cost should make it an attractive i.c. to the amateur experimenter and a few of its more interesting features and applications will be outlined in the following notes.

Applications

A block diagram of the NE555 is shown in Fig. 1 and the first application to be considered is its use as an accurate timer, Fig. 2. The timing period is set by one additional resistor capacitor network with additional terminals allowing control over the triggering and resetting of the device. The external

pulse is applied to pin 2 the flip-flop changes state and biases off Tr1 thereby allowing C1 to charge via R1. The time constant associated with R1C1 determines the rate at which C1 charges and when its voltage reaches $\frac{2}{3}V_{cc}$, the threshold comparator

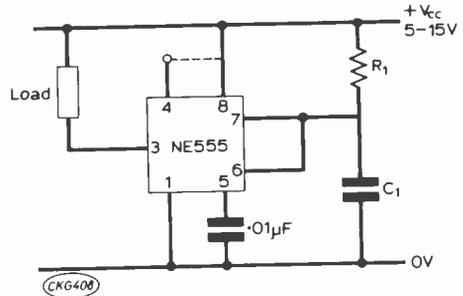


Fig. 2: Typical application of the NE555. The values of R1 and C1 for a delay of 1 second would be 1MΩ and 1µF.

resets the flip-flop and discharges C1 in addition to providing an output pulse at pin 3. One of the great advantages of this type of circuit is that the timing rate, for all practical purposes, is independent of the supply voltage. Timing periods from as short as 1 microsecond to as long as 1 hour may be obtained with this rather simple arrangement.

Multivibrator

Another interesting application of the NE555 is obtained when pins 2 and 6 are joined together as illustrated in Fig. 3. Here the device is operated as

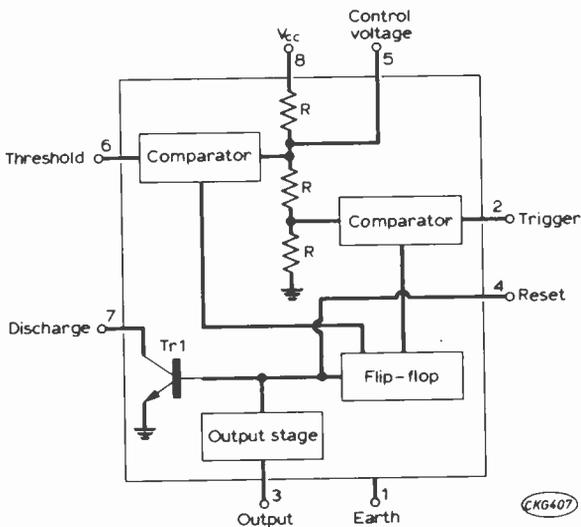


Fig. 1: Block diagram of the NE555 timing device.

capacitor connected between pin 7 and earth is initially held discharged by the short circuit path of the saturated transistor Tr1. When a negative trigger

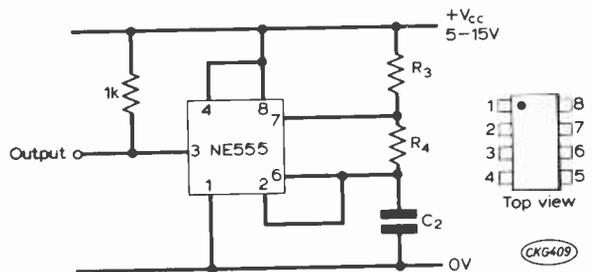


Fig. 3: In this circuit the NE555 is used as a free-running multivibrator.

a free-running multivibrator with the frequency and duty-cycle set by the R3-R4-C2 arrangement. The combined value of R3 and R4 in conjunction with C2 determines the frequency while the duty cycle is set by the ratio R3/R4. As the transistors fabricated in the silicon chip are of the highest quality excellent square waves are obtained from the output at pin 3. Once again, in this arrangement the operating frequency is independent of the power supply voltage.

Pulse-width modulator

The final application of the NE555 to be considered is its use as a pulse-width modulator. Here an external square wave generator's output is connected to pin 2 with the modulating signal applied to pin 5 as indicated in Fig. 4. (Incidentally, another NE555 operated in the astable mode will function quite well

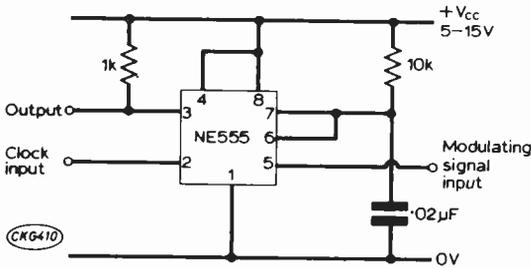


Fig. 4: Yet another application is as a pulse-width modulator.

as the clock generator.) As the control voltage on pin 5 increases, it affects the threshold voltage of the comparator resulting in an increase of the pulse width. The exact opposite occurs as the modulating voltage decreases so the output train of pulses obtained at pin 3 has a frequency identical to the clock input frequency with the pulse width controlled by the modulating signal.

A few of the more interesting applications of the NE555 i.c. have been reviewed in this article and further uses of the device are left to the ingenuity of the experimenter. The NE555 is available from Quarndon Electronics Ltd., Slack Lane, Derby.

Receiver Matching Unit

F. G. RAYER

AN end-connected wire of random length is often used as a short wave aerial and this can, in fact, give good results if reasonably high and clear of earthed objects. At some frequencies, when the aerial length is a half wave or multiple of a half wave, the end impedance at the receiver can be very high, over 1000 ohms. At the other frequencies (a quarter wave or odd number of quarter waves) the impedance is low, probably under 50 ohms. Therefore, for an efficient transfer of energy from the aerial to the receiver at all fre-

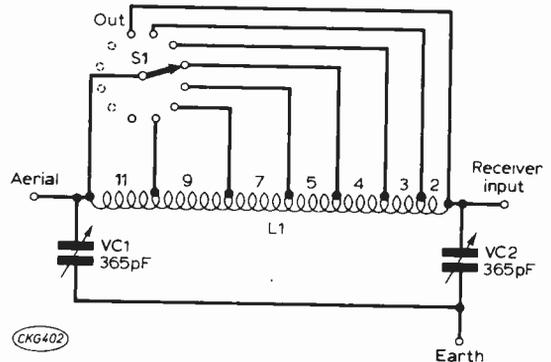


Fig. 1: above, shows the circuit of the receiver matching unit. When switched to "Out" the two variable capacitors should be turned to minimum capacity.

quencies, some matching device is needed. The one described here covers about 3.5MHz to 30MHz, and it is over this range that such an accessory is most likely to prove useful.

THE PI NETWORK

In the circuit, Fig. 1, the tapped inductor L1 has a variable input capacitor VC1 and variable output capacitor VC2. A 12 position rotary switch S1 allows turns to be selected as follows—0, 2, 5, 9, 14, 21, 30, and 41, the last four positions remaining unused. This switch and adjustment of VC1 and VC2 allows a wide range of aerials to be matched to the receiver.


Many communications receivers have a nominal aerial input impedance of about 75 ohms while others, and especially some popular older models, are 600 ohms. On some frequencies the aerial may chance to match the receiver. The Receiver Matching Unit will then give no improvement in signal strength, but can be left in circuit by setting VC1



TUT! TUT!!

Improving VHF Radio April PW

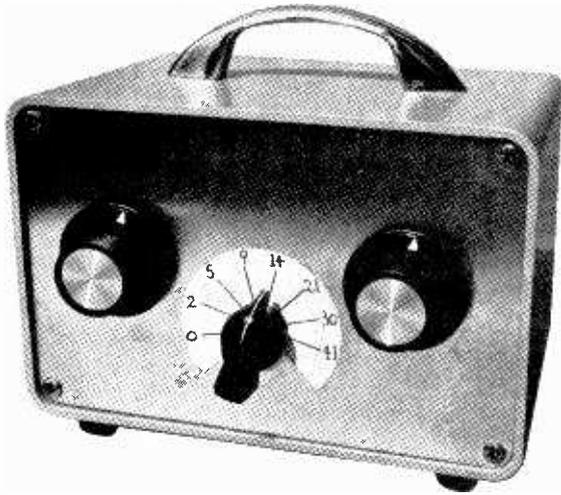
Although our information was taken from a normally reliable valve and transistor manual the connections for the BF200 transistor in Fig. 6 were incorrect. They should read, clockwise from the tag: emitter, base, collector and shield.



and VC2 at minimum and the switch at "0".

At other frequencies the switch is progressively rotated to bring more turns into circuit, each time adjusting VC1 and VC2 for best results. This is merely a matter of peaking the matching unit controls for best volume, or best S-meter reading. Where the mis-match is bad, quite a significant improvement should be had. If peaking the signal by ear, switch off the receiver a.g.c. or choose a weak signal or adjust for maximum general noise picked up by the aerial.

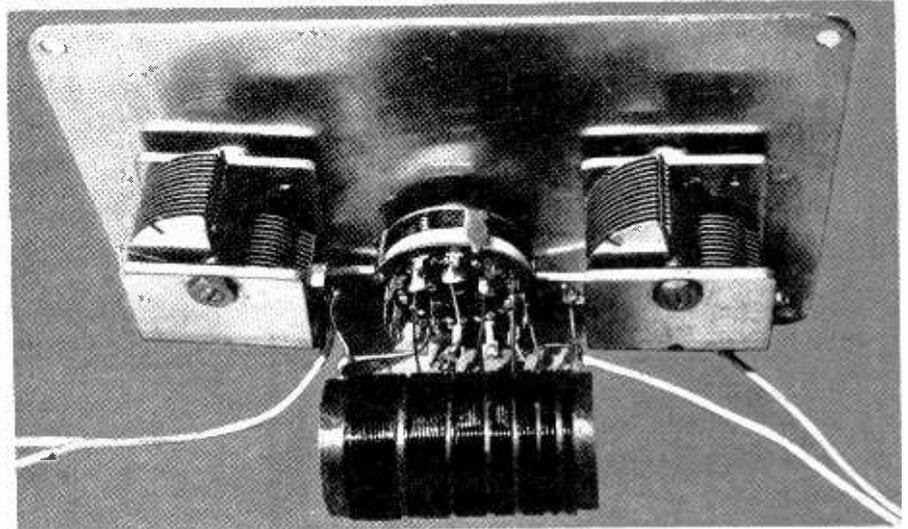The photograph, right, shows the author's prototype unit. The multiple leadouts from the coil are sufficient to hold it firmly on the switch.



The coil is wound with 22 s.w.g. enamelled wire on a paxolin tube 1in. in diameter and about 2in. long. Anchor the wire through small holes near one end. Wind 2 turns side by side, and twist a small loop. Leave a space of about $\frac{1}{8}$ in. and wind 3 turns, making a further loop. Continue in this way, adding 4, 5, 7, 9 and 11 turns, with a small space between each section. Scrape all the loops and solder on leads for the switch.

Solder the leads to the switch so that the first position shorts the whole coil, subsequent positions leaving 2 turns, 5 turns, 9 turns, and so on, in circuit, position 8 having no connection so that the whole coil is in use.

VC1 and VC2 are each 365pF miniature air-spaced

capacitors. Solid dielectric components are not recommended. A value of 350pF or so is useful for the lower frequencies, but for the h.f. bands only 200pF or even 150pF capacitors may be suitable, if to hand.

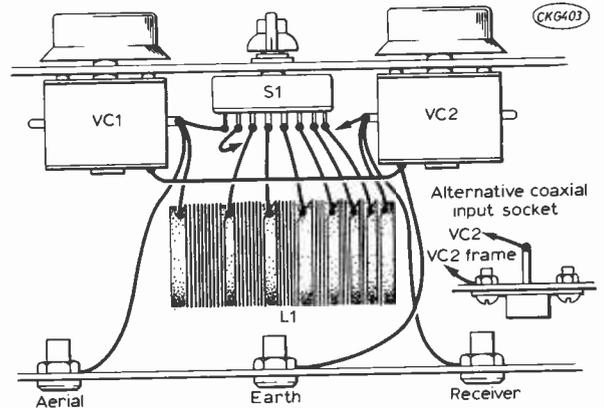


Fig. 2: Wiring diagram of the matching unit. Unused positions on the switch have been ignored.

Fig. 2 shows construction, the coil being supported by its leads. The plastic case used was 6×4×4in. but had no removable back, so flying leads were left just long enough to reach Aerial, Receiver, and Earth terminals fitted at the rear. Communication receivers often have a 75 ohm co-axial aerial input socket when a co-axial socket can be fitted to the

back of the matching unit. The inner conductor of the co-axial lead to the receiver will be the aerial lead, and the outer braiding will act as the earth connection no earth being needed on the unit.

The switch has a scale showing the number of turns in circuit. The lowest frequency reached depends on the aerial and receiver, but can extend down to 1.5MHz in some cases. On some ranges, the unit is useful in reducing second channel interference. If a numbered dial is fitted to each capacitor a very useful chart can be made up showing dial readings and switch positions for the various amateur and short wave broadcast bands, which will considerably shorten the time taken to tune the unit to any particular frequency. ■

IN NEXT MONTH'S

PRACTICAL WIRELESS

STEREO HEADPHONES REMOTE CONTROL UNIT

Listen to your stereo records and radio programmes in the comfort of your armchair, perhaps several feet away from the amplifier. Settle down and enjoy the music in the "ideal stereo" position. You don't have to get up to adjust volume or balance controls because you have this small unit on your lap to do it remotely, with balance meter and socket for private listening on stereo phones. Easy construction details given next month.



FREE COMPETITION
4 DIGITAL MULTIMETERS
WORTH £200
TO BE
WON!



OPEN TO ALL READERS OF P.W.
FULL DETAILS AND ENTRY FORMS IN
THE JUNE ISSUE—ORDER NOW

ALL IN THE JUNE ISSUE
ON SALE 4th MAY. PRICE 20p.

SIMPLE MEDIUM WAVE RECEIVER

This small easy to build radio is designed to include the 160 metre band and local radio stations on the medium wave. It is easily converted for the long wave 1500 metres by adding one component. Ideal for bedroom, garage or holidays.

REGULATED POWER SUPPLIES FOR TRANSISTOR RADIOS

Save battery costs at home. Run your pocket radio from a mains power unit. This unit replaces small 9 volt batteries for radios drawing up to 50mA current.

MANY OTHER CONSTRUCTIONAL ARTICLES, SPECIAL FEATURES AND REGULAR COLUMNS



Two Tone Door Bell

This oscillator produces a pleasing tone, different in frequency for either of two doors. By using a suitable centre-tapped transformer T1, the collector circuit of each transistor can drive the base of the other transistor.

Assembly is on a perforated srbp board and wired as in Fig. 2. This board is fitted in the speaker cabinet or to a flat speaker panel fitted across the corner of the room.

One push-button switch is wired to A, and the other to B. The return leads of both switches go the common terminal C. When one switch is operated both R1 and R2 are in circuit, while with the second push R2 only is present. Wires A-C can run to the front door, and B-C to the back door.

The note can be altered by changing the resistance of R1 or R2 or the capacitance of C1, C2 or C3.

Connections for OC81, NKT271: collector wire nearest spot, then base, emitter.

components

- R1 resistor 1.2kΩ ±10% ¼w
 - R2 resistor 220Ω ±10% ¼w
 - R3 resistor 47kΩ ±10% ¼w
 - R4 resistor 47kΩ ±10% ¼w
 - C1 capacitor 0.047µF polyester
 - C2 capacitor 0.047µF polyester
 - C3 capacitor 0.047µF polyester
 - Tr1 transistor OC81 or NKT271
 - Tr2 transistor OC81 or NKT271
 - T1 transformer 9.2:1 CT primary, type T/T7 Repanco
- Loudspeaker 3Ω 5in. and wooden board 12in. x 9in.
 Battery 9V type PP6 or PP9 with connectors
 Perforated srbp component board
 Nuts and bolts 6BA, soldering tags, pvc wire

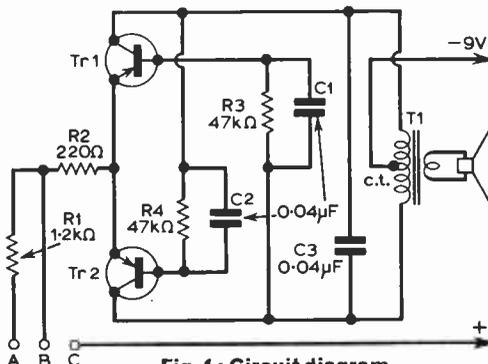


Fig. 1: Circuit diagram


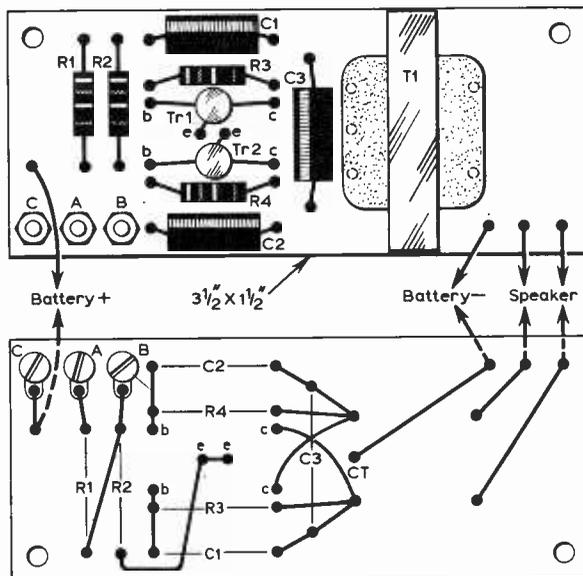


Fig. 2: Component layout and wiring

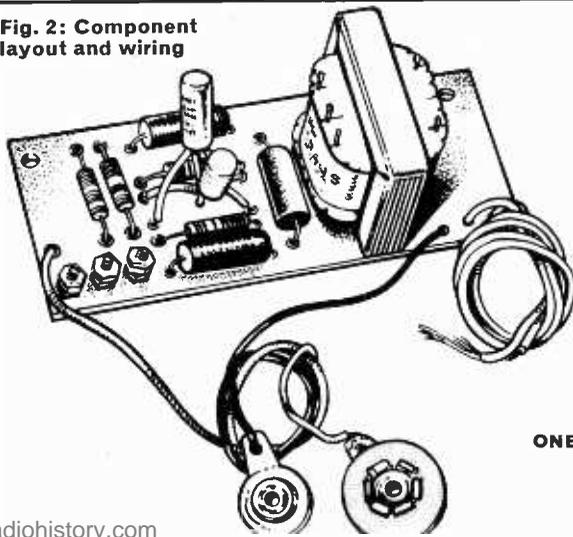



Ready-made amplifier module used to give press-button calling and communication in both directions. Fig. 1 is the complete circuit.

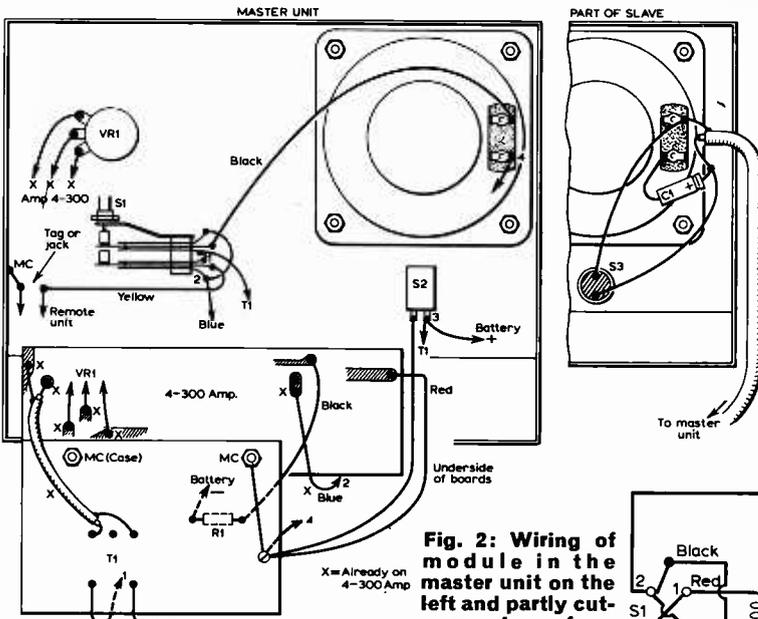
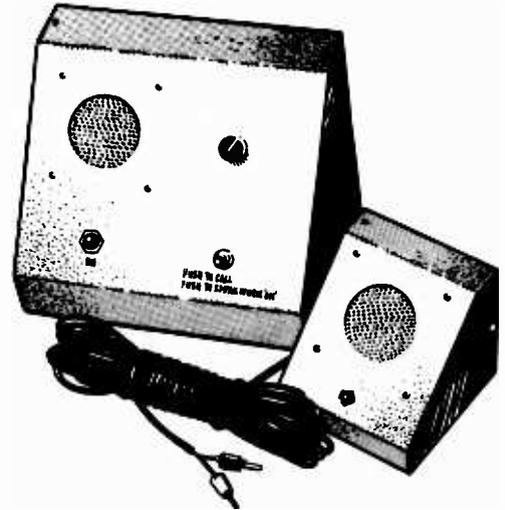


Fig. 2: Wiring of module in the master unit on the left and partly cut-away view of remote unit

components

- R1 resistor 150Ω ±10% ¼ watt
- VR1 potentiometer supplied with amplifier module
- C1 capacitor 50μF 12V electrolytic
- T1 transformer 9:2:1 CT primary, type T/T7 Repanco
- S1 2-pole, changeover spring loaded push button, type S746 with S768 operator, or type S415 Bulgin
- S2 single-pole, on-off toggle switch
- S3 single-pole, on-off push button
- Loudspeakers 3Ω 2½in. or 3½in.
- Battery 9V type PP6 or PP9 and connectors
- Amplifier module type 4-300
- Component board srpb 3½in. × 2½in.
- Case 8in. × 6in. × 6in. (Master unit)
- Case 4in. × 4in. × 4in. (Remote unit)
- PVC connecting wire and knob
- Nuts and bolts 6BA and 4BA
- Soldering tags 6BA

S1 is the "push-to-call and push-to-speak" switch. When it is pressed, the circuit is completed in such a way as to cause an audio tone (R1 limits current in this condition). S2 switches the unit on so that the master position may speak to the remote position, or vice versa. S3 at the remote unit causes a tone at the master unit, to gain attention.

At the master unit, press S1 a few times to gain attention, then close S2, with S1 released to listen. Press S1 again to speak. Switch off with S2 when contact is finished. At the remote unit, press S3 a few times to call master unit and await reply. VR1 is set to a suitable volume level, and is ready wired to the 4-300 unit.

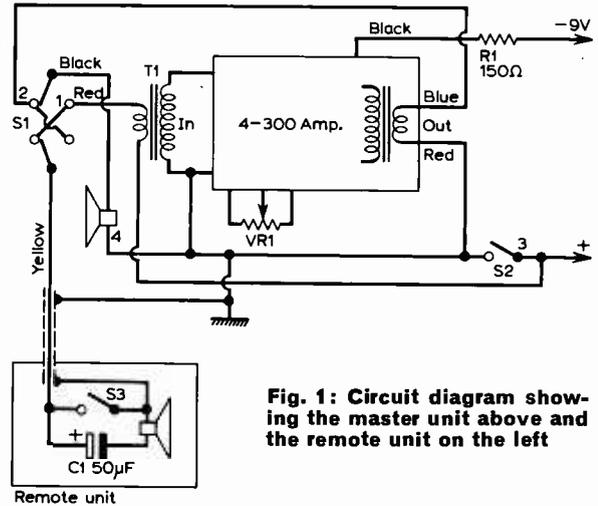


Fig. 1: Circuit diagram showing the master unit above and the remote unit on the left

Numbers 1 to 4 in Fig. 1 refer to connection points 1 to 4 in Fig. 2. Fig. 2 shows the master unit. Two 6BA bolts secure the 4-300 amplifier and also the srpb board for T1 and R1. Solder coloured leads to S1 as indicated before fitting this item. Input and output circuits and T1 are

continued on page three

A sensor, on the end of twin flexible lead, can be placed in a water tank, swimming pool, bath or wash-boiler. A buzzer sounds when the water level reaches the sensor.

The minimum battery current drain is about 0.3mA; rises to about 400mA when water reaches the sensor.


Fig. 1 shows the circuit. The presence of water shorts the sensor probe and allows base current to flow through R1, resulting in a collector current of about 40-50mA to close the relay. The buzzer sounds until the sensor is removed from the water, or the device is switched off.

Fig. 2 shows all wiring, in a case made from aluminium. The tag strip (shown detached) is mounted vertically in the adjacent corner of the case. Space is left for a flat 3-cell 4.5 volt battery.

components

- R1 resistor 10kΩ ±10% ½ watt
- Tr1 transistor OC76 or any high gain pnp type
- S1 single-pole, on-off switch
- RLA relay 100Ω coil, single-pole on-off contacts, 3-6V operation
- Battery 4½ to 6V depending on relay obtained
- Buzzer 4½ to 6V
- Sensor probe (see text)
- Case 6in. × 4in. × 2in. aluminium box or chassis with lid.



Fig. 1 (right): Circuit diagram
Fig. 2 (below): Component layout and wiring

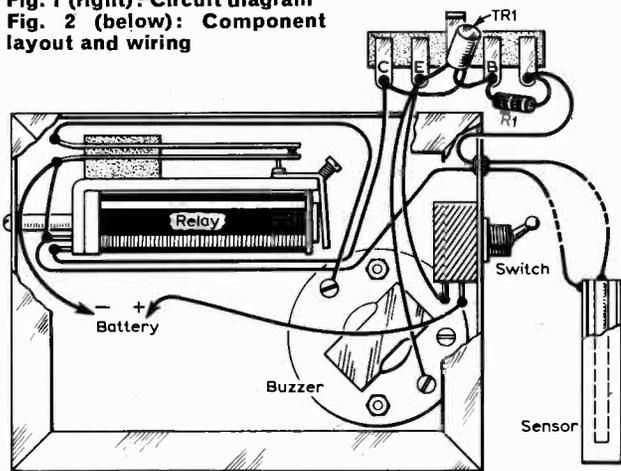

Water Level Detector

The sensor is made in coaxial form to avoid any accidental short (and wrong indication) by metal items. It has an outer metal tube about 2in. long by 3/8in. diameter, with a slightly shorter internal pin (actually a length of 4BA threaded rod). The inside part is fixed by a tight binding of insulating tape, or by an insulated sleeve. The sleeve and pin must not touch. Several feet of thin twin flex are soldered on, the sensor inner part going to R1.

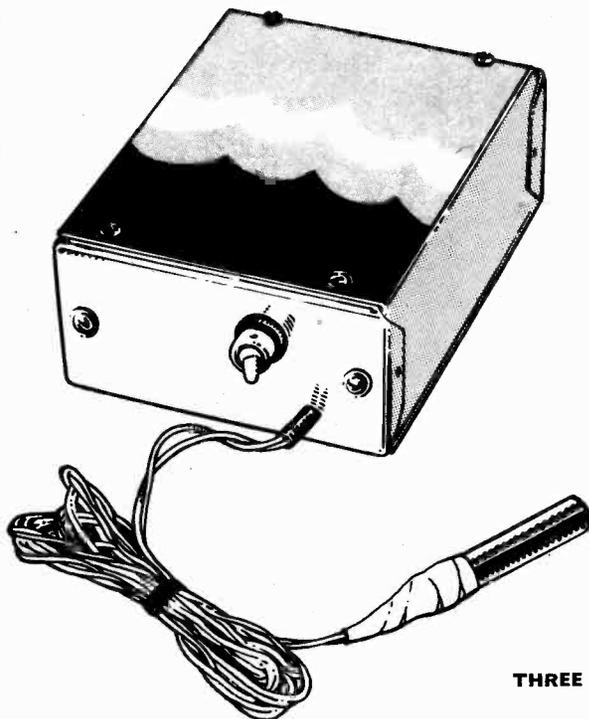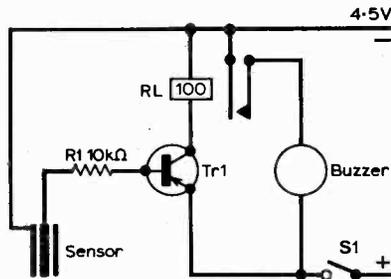An alternative probe can be a coaxial plug as used for TV aerial wire, although it must be kept free from corrosion.



INTERCOM AMPLIFIER


continued from page two

positioned to avoid feedback which would cause instability. In addition to VR1, the 4-300 has a preset sensitivity control, which can be left at about the middle of its travel.

Easy connecting of a remote unit lead can be by a jack plug and socket, the outer conductor being the common positive return. Do not connect or disconnect while battery is switched on.

The equipment will operate as a baby alarm by placing the remote unit near the cot and closing S2.

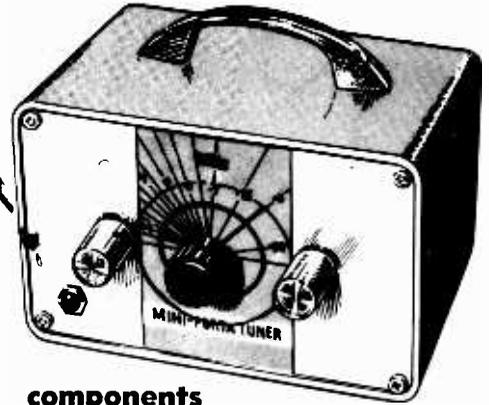Connections to the 4-300 amplifier module are shown in Fig. 2, indicating appropriate copper pads used for connections. MC indicates connection made to the metal case by soldering tags. S1 does not necessarily need to resemble that shown in Fig. 2 but can be any style with the operation as in components list.



components

Resistors

- R1 18kΩ
- R2 15kΩ
- R3 2.7kΩ
- R4 1kΩ
- R5 47kΩ
- R6 120kΩ
- R7 330kΩ
- R8 390Ω
- R9 27kΩ
- R10 1.5kΩ
- R11 3.9kΩ

All resistors $\pm 10\% \frac{1}{2}$ watt

Potentiometer

- VR1 10kΩ log.

Diode

- D1 AA119 or OA91

Capacitors

- C1 0.01μF mica or ceramic
 - C2 0.02μF mica or ceramic
 - C3 180μF mica or ceramic
 - C4 2μF electrolytic
 - C5 0.01μF mica or ceramic
 - C6 0.1μF polyester
 - C7 200μF 9V electrolytic
 - C8 0.01μF polyester
 - C9 0.5μF polyester
- (Note: C9 not required if used only with IC-12 audio amplifier)

Variable Capacitors

- VC1 & VC2 208+ 176pF with trimmers type 00 Jackson (slow motion optional)

Preset Trimmers

- TC1, TC2 fitted to VC1, 2

Transistors

- Tr1 BF194 Tr2 BF195 Tr3 BF195

Coils

- L1, L2 Medium wave ferrite rod aerial coil type MW/FR5 Denco
- L3 Oscillator coil type TOC1 Denco

Transformers

- T1 I.F. transformer type IFT13 Denco
- T2 I.F. transformer type IFT13 Denco
- T3 I.F. transformer type IFT14 Denco

Switch

- S1 Single-pole, on-off toggle switch

Miscellaneous

- Perforated srbp, 0.15in. matrix 4½in. x 2½in.
- Control panel and bracket 4½in. x 2in. aluminium
- Nuts and bolts 6BA, pvc wire
- Case, insulated, of wood or plastic

This portable medium wave tuner gives an output for a tape recorder or amplifier.

Note that the AA119 diode has a *black* mark to denote plus polarity; wrong polarity here will upset avc action. Components are positioned as in Fig. 2 and wired as shown in

grey. The perforated srbp board is bolted to the metal bracket carrying VR1, VC1/2 and S1. MC is the metal case connection.

A bracket, srbp strip, and strip of card wrapped round the rod and drawn tight with a

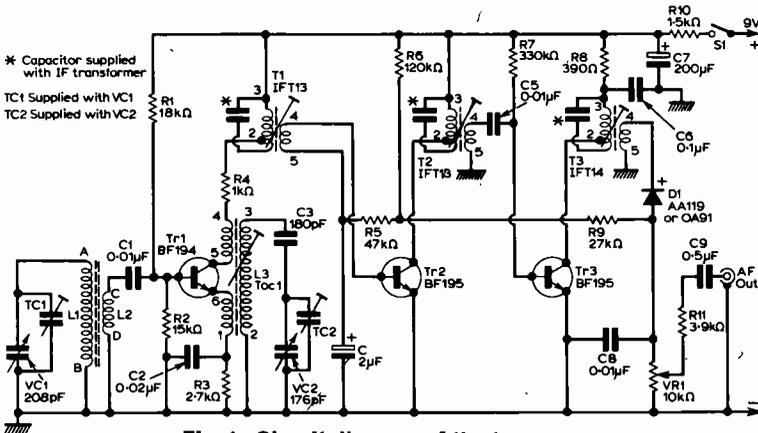


Fig. 1: Circuit diagram of the tuner

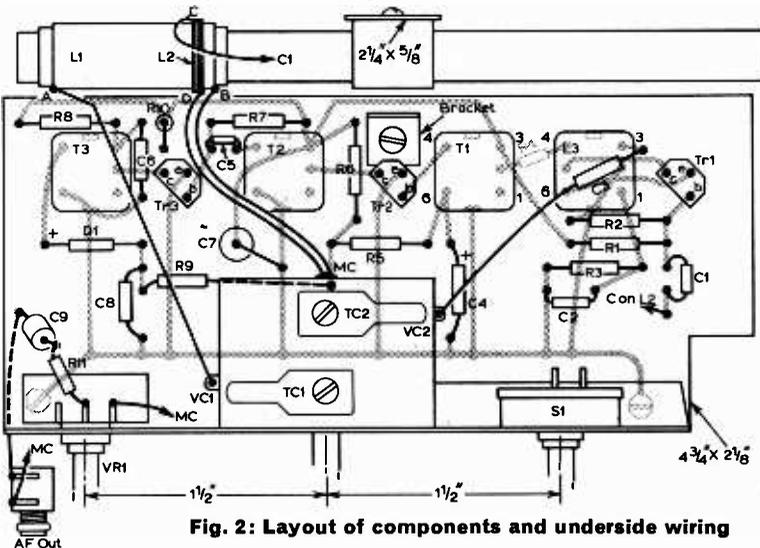


Fig. 2: Layout of components and underside wiring

This radio alarm is designed to awaken you at a preset time set on the clock movement, and to switch off automatically if required.

Use the "Tape Tuner" (page four of this supplement) with an integrated circuit audio amplifier. The synchronous clock runs from 250V a.c. mains and is supplied with contacts which are set by a front mounted control. A second control sets the duration, then automatically switching off. (A minute timer ringer is also provided, but is not used in this circuit.)

The master or programming switch, which is arranged as in Fig. 1 and shown in two views in Fig. 2, allows the radio to be switched on irrespective of the clock settings, or switched off separately, giving complete freedom of operation without any need to change clock settings.



components

Tape tuner as described on page four of Supplement Amplifier i.c. type "Super IC12" with heat sink (Sinclair)

Electric programmer clock as illustrated with switch contacts glass and bezel (various advertisers)


Loudspeaker 8Ω to match IC12

Switch single pole, 3-way to select operation

Connection block, 3-way for mains connection

Fabric or expanded aluminium speaker grille

Case approx. 10in. x 7in. x 4½in.

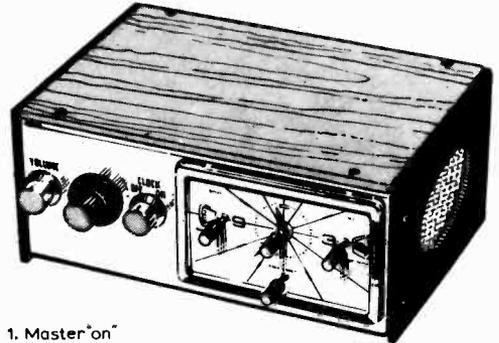

A mains connector joins mains leads and clock leads.

The i.c. amplifier is mounted on brackets. The whole unit is powered by a PP9 9V battery. A mains unit could be fitted instead and several proprietary brands can be purchased or the reader can make his own. All units can be mounted in a suitable wooden case.

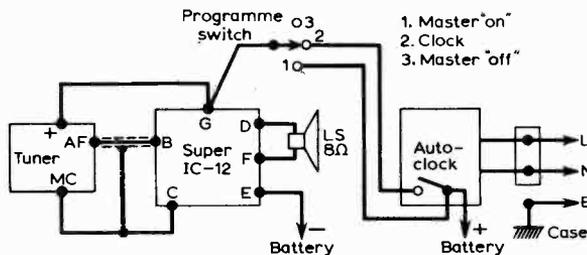


Fig. 1 (left): Circuit diagram

Fig. 2 (below): Component layout and wiring (the programme switch is shown twice for wiring detail)


TAPE TUNER

continued from page four
nut and bolt hold the ferrite rod aerial.

The i.f. transformers T1, T2, T3 are pre-aligned but the effect of slight core adjustment can be tried. Adjust TC1 and TC2 at the high frequency (200 metres) end of the band, and the core of L3 (if necessary). The position of L1/L2 on the ferrite rod is adjusted at the low frequency end of the band.

Note that the specified case is insulated material, not metal to avoid screening the ferrite rod aerial. Audio output should be heard on high impedance phones connected to the output jack socket. The output is of high impedance and should be fed into the high impedance input of a tape recorder via screened cable (but see also the Radio Alarm Clock). Transistor connections as indicated by top view in Fig. 2.

Transistor connections as indicated by top view in Fig. 2.

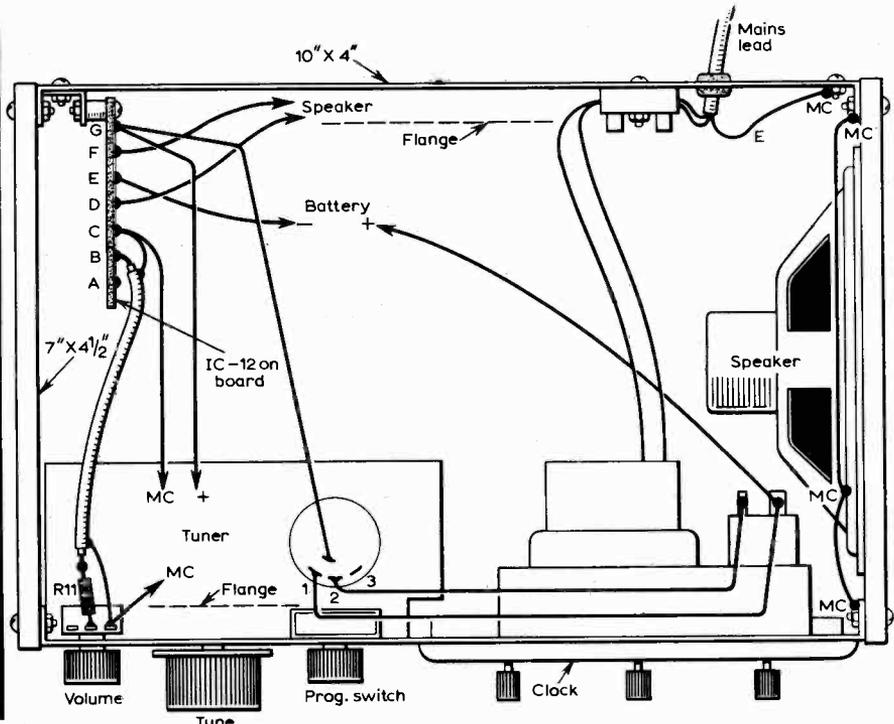

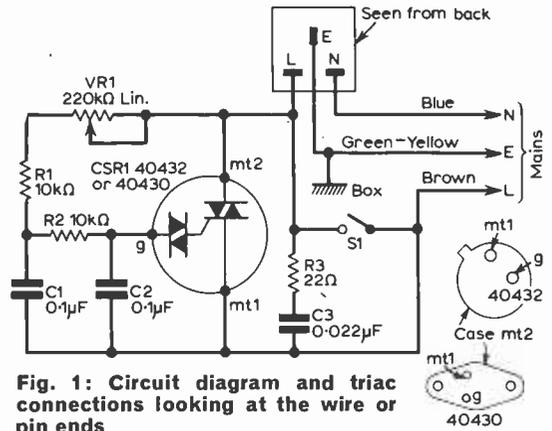
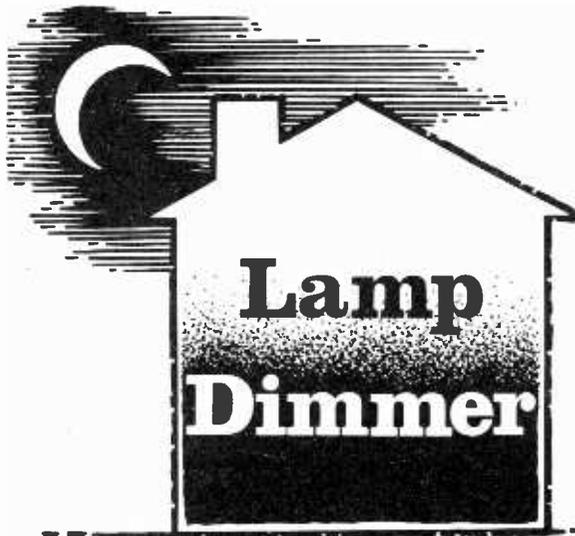


Fig. 1: Circuit diagram and triac connections looking at the wire or pin ends


This lamp dimmer is constructed in an electrical switch box. The 40432 triac is rated at 0.5A without a heat sink, or 1A with the type 5F clip-on heat sink shown. With 240V a.c. mains, this is suitable for lamp loads of 120 watts and 240 watts respectively. An alternative triac type 40430 can also be used.

The dimmer can be fitted in place of an ordinary lamp switch. With the portable unit shown, the dimmer box and a 13A type outlet are assembled in a larger box. A table or standard lamp can be plugged into it, or it can be used for heat control of a soldering iron. This unit is not rated for power drills and is not suitable for them nor for fluorescent lamps.

Fig. 1 is the circuit, with wiring to integral 13A type outlet. The metal box, Fig. 2, provides screening. Complete closure by a metal plate was not found necessary. The triac case is connected, via a soldering tag bolted to the heat sink or case, to VR1. It must be insulated from the box and any other metal part. Flexible leads to VR1 and S1 allow these to be positioned in the front holes.

Assure proper earthing is maintained right up to any appliance controlled by the unit. The mains plug is fitted with a 3A fuse.

Triac connections shown in diagram.

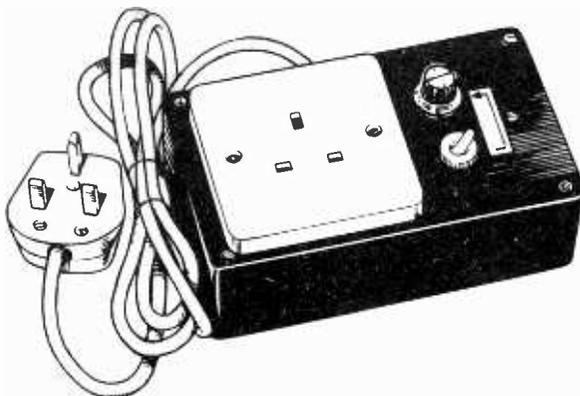

components

- R1 resistor 10kΩ ±10% ½ watt
- R2 resistor 10kΩ ±10% ½ watt
- R3 resistor 22Ω ±10% ½ watt
- VR1 potentiometer 250kΩ linear
- C1 capacitor 0.1μF 1,000V d.c. or 300V a.c.
- C2 capacitor 0.1μF 1,000V d.c. or 300V a.c.
- C3 capacitor 0.022μF 1,000V d.c. or 300V a.c.
- CSR1 triac type 40432 with heat sink clip type 5F or triac type 40430
- S1 Single-pole, on-off toggle switch 250V a.c. Metal electrical switch box 2½in. × 2½in. × 1½in. or 6½in. × 3½in. × 2in. with 13A mains socket Tag strip 8-way, knob, pvc wire, rubber grommet

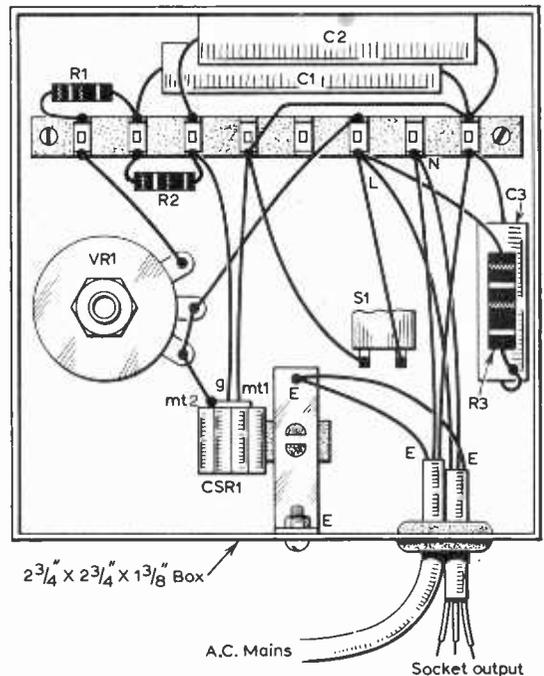


Fig. 2: Component layout and wiring

The input transducer is a small loudspeaker, followed by Tr1 and Tr2 as amplifiers. VR1 is a sensitivity control, allowing adjustment of the sound level at which the unit operates.

All components except the speaker and VR1 are mounted on the perforated srpb board in Fig. 2. Underside wiring is shown in grey. Points A, B and C carry connecting wires to VR1. Wires A and C are connected so that sensitivity increases as the control knob is rotated from the "off" position in the usual way. The case is an aluminium box or chassis.

Test by connecting a meter to the output terminals. A brief pulse of current is indicated when switching on, due to C5. The reading should then remain at zero, rising to 100-250mA while snapping the fingers or speaking quietly.

Place the unit adjacent to the source of sound. Where extraneous sounds may operate the unit, reduce sensitivity by turning back VR1 just enough to avoid this.

Twin bell wire or a long twin flexible lead run from the output terminals to the bell or relay. A diode 1N4148 should also be connected across the output terminals to suppress back e.m.f. through Tr4; diode plus to collector.

Connections for OC71, OC81: Collector nearest spot, then base, emitter.

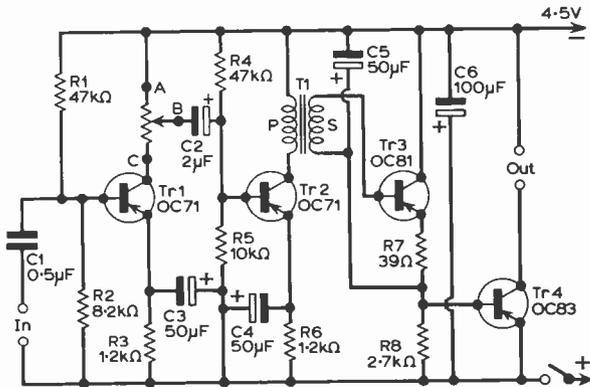


Fig. 1: Circuit diagram of the amplifier

components

Resistors

R1 47kΩ	R5 10kΩ
R2 8.2kΩ	R6 1.2kΩ
R3 1.2kΩ	R7 39Ω
R4 47kΩ	R8 2.7kΩ

All ±5% ¼w

Potentiometer

VR1 5kΩ with switch S1 attached

Capacitors

C1 0.5μF polyester	C4 50μF 6V electrolytic
C2 2μF 6V electrolytic	C5 50μF 6V electrolytic
C3 50μF 6V electrolytic	C6 100μF 6V electrolytic

Transistors

Tr1 OC71	Tr3 OC81
Tr2 OC71	Tr4 OC83

Transformer

T1 9:2:1, CT primary, type T/T7 Repanco

Miscellaneous

- Miniature 40 ohm speaker
- Perforated srpb board 4in. × 2½in.
- Screw terminals or sockets
- Case, aluminium or wood, 10in. × 4in. × 3in.



This alarm gives a warning by means of a bell, buzzer or lamp, so it can be used as a baby alarm, or as an extension for a door-bell or telephone bell. As it is sound operated, no direct connection is necessary to a telephone or other equipment.


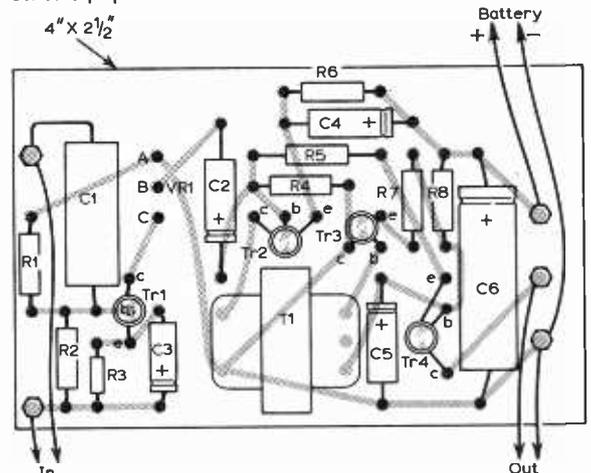


Fig. 2: Component layout and underside wiring shown grey

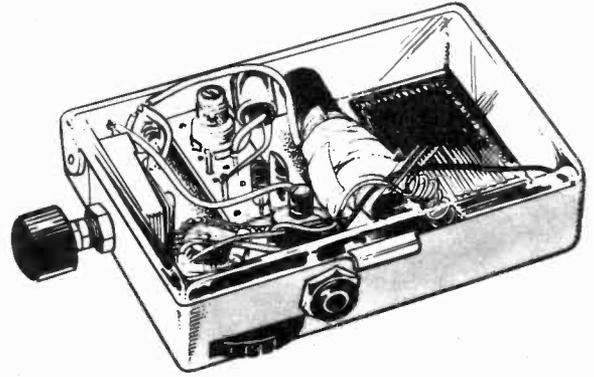



components

- R1 resistor 270Ω ±10% ¼ watt
- VR1 potentiometer 20kΩ miniature edge control with switch S1
- C1 capacitor 0.1μF low voltage
- C2 capacitor 2μF 6V or higher electrolytic
- VC1 variable capacitor 300pF mica dielectric
- TC1 trimmer capacitor 2-10pF screw driver control
- Tr1 transistor AF117 or similar pnp type
- RFC R.F. cored choke 5mH
Ferrite rod ⅜in. diameter, 2in. long
Wire 26 s.w.g. enamelled copper wire for tuning coil
- Phones high impedance with jack plug and socket
- Solar cell 0.5volt or dry cell 1.5V
- Component board 1⅜in. × ⅝in. and box
PVC connecting wire

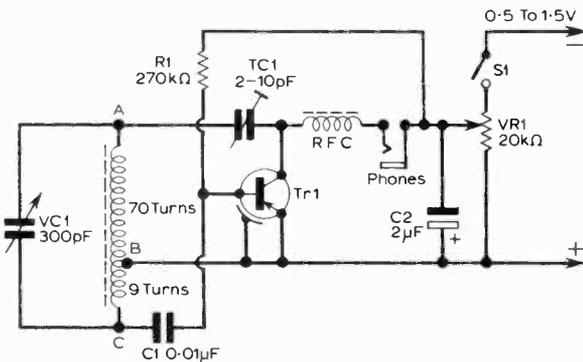


Fig. 1: Circuit diagram

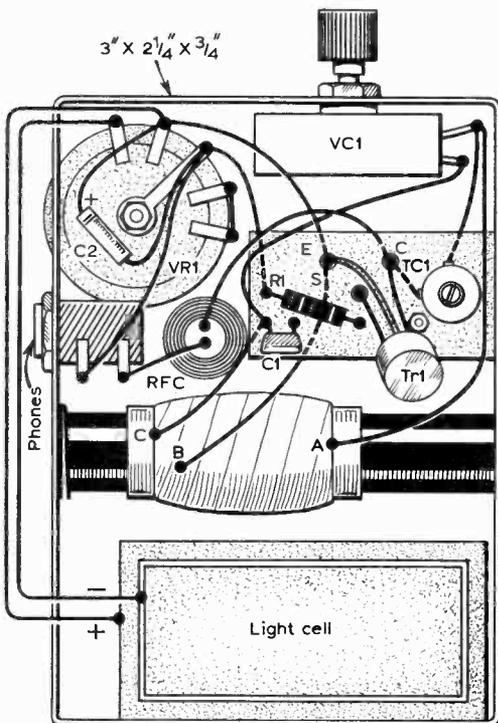


Fig. 2: Component layout and wiring

Simple regenerative receiver providing headphone reception of local medium wave stations only. Power derived from a mercury cell when energised from daylight or good artificial light. A 1.5 volt dry cell can be used instead.

Tuned circuit consists of 79 turns of 26 s.w.g. enamelled copper wire (A to C) close wound on ferrite rod ⅜in. diameter, in parallel with small tuning capacitor VC1. This coil has a tapping (B) nine turns from one end (C). Trimmer capacitor TC1 controls regeneration and is set so that oscillation is just possible with VR1 near maximum voltage setting when using a single 0.5V solar cell.

Tuning coil is wound on thin card or thick paper tube so that it can be moved along ferrite rod for best reception. A few feet of flexible wire aerial connected at A may help reception. Phones should be high impedance 2,000 ohms or more and connected via jack socket on box. Small components are mounted on perforated srpb board and wired underneath. Keep wires short. Minimum recommended box size 3in. x 2⅜in. x ⅝in. Connections for AF711: collector wire nearest spot, then screen, base, emitter. ●

COMPONENT SUPPLIES

Components should be readily available from several of our advertisers including the following: Arrow Electronics, Chromasonic Electronics, Elektrokit, Electrovalue, Henry's Radio, Home Radio (Components), A. Marshall & Son, Trannies, J. Bull (Electrical) and others.

Sub-standard, unmarked or other components that are not as specified in components lists cannot be guaranteed as suitable substitutes. Constructors should satisfy themselves before buying.



TRICOLOUR

Mood Lighting System

PART TWO

JUREK BUDEK*



THE P.W. Tricolour provides a versatile but straightforward form of colour lighting effect that is much improved on earlier designs, due largely to the use of the principle of zero voltage switching. Last month's article explained how this was done so now it is time to do the construction and see the results.

Construction

In the P.W. Tricolour lighting system, the bass frequencies are 'presented' by the red lamps, middle frequencies by the green lamps and treble frequencies by the blue lamps. The control unit referred to in the following text is the P.W. Tricolour filter and control unit.

The construction of the control unit is not complicated if care is taken to follow the drawings and assembly notes. Before connecting any mains supply to any unit, double-check all wiring against the circuit diagrams (last month) and wiring diagrams, making quite sure that all thyristors, triacs and diodes are correctly connected.

It is recommended that sockets are used for mounting the integrated circuits. Do not solder the I.C.'s directly to the printed circuit board.

Assemble the eight way socket to the back panel in such a manner that when plug is inserted the five core cable to the lamps leads horizontally away from the fuse assembly.

The lights output socket is a Bulgin type P552 and the plug to fit this (for the lamps unit lead) is a Bulgin P551.

Attach the fuse holders, rubber grommets and speaker socket to the back panel. Assemble the components on to the printed circuit board, making sure that no accidental solder bridges occur across adjacent copper pads. The heat sink for the triacs is "live" and should not be connected to, or allowed to come in contact with, any metal part except the triac mountings, which are also the connections to their "main terminal 2". For safety connect this, the "zero" voltage indicated on the mains transformer, to the neutral terminal of the mains, and connect the control unit chassis to earth on the mains plug.

Insert the rubber grommet for the l.e.d. lamp

indicator into the front panel. Switches S1, S2, S3 and S4 are as used in the Texan amplifier.

The mains switch shown on the front panel uses detachable connecting clips, but any suitably rated mains switch is suitable. The front panel is mounted on the front of the chassis frame with spacers so that clearance of the control fixing nuts provides a neat and uncluttered appearance to the panel. The assembly

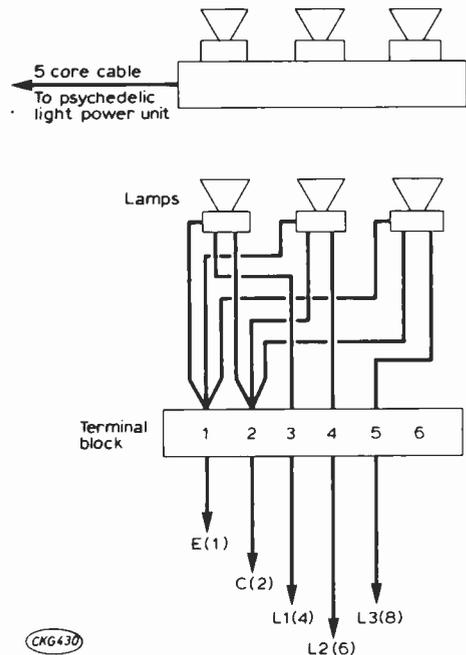


Fig. 13: The simplest arrangement in which one control unit drives three lamps, each 100 to 150 watts. E represents the earth or chassis connection via tag 1 on the Bulgin 8 pin plug/socket arrangement. The figures in parenthesis are the pin numbers. C is the common lead to the lamps—which is the 240V live lead. L1, L2 and L3 are the leads to the respective lamps shown as LP1, LP2 and LP3 (Fig. 12 last month).

* TEXAS INSTRUMENTS LIMITED

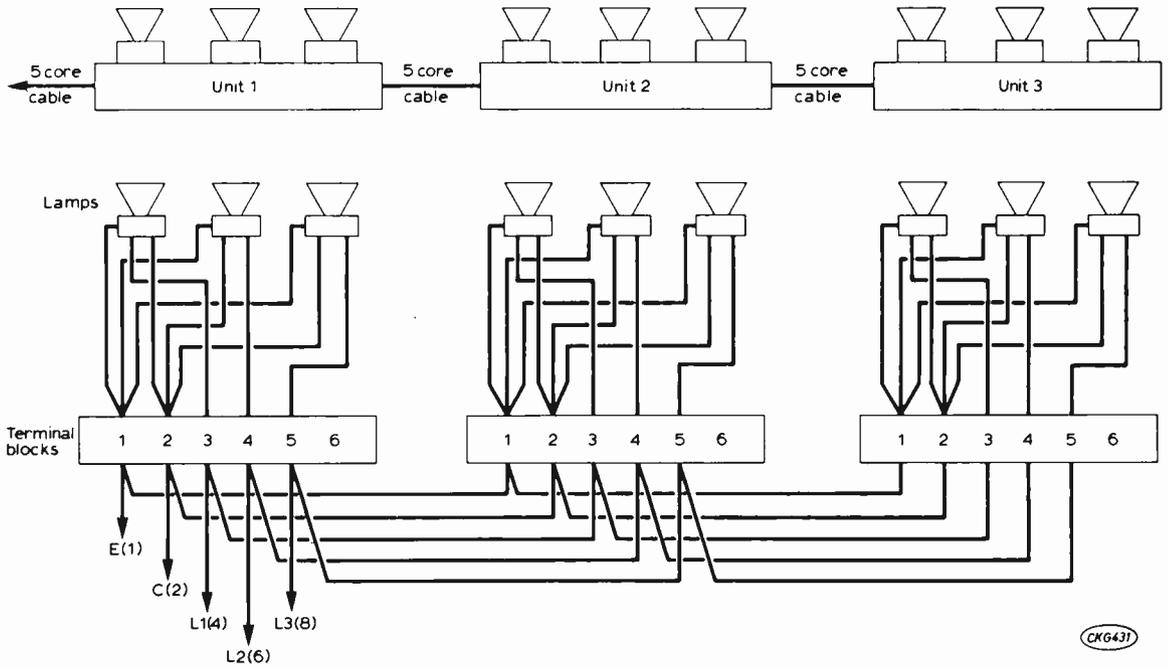


Fig. 14: Three banks of lamps, each 100w maximum, driven from one control unit.

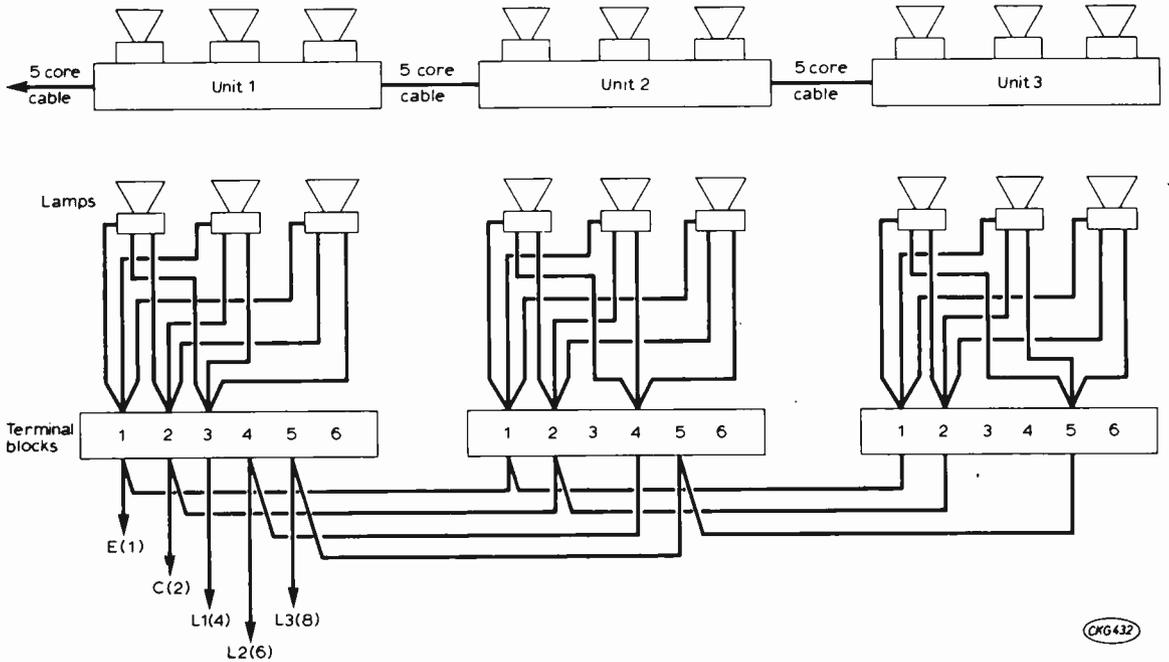


Fig. 15: Three banks of lamps, each 100W maximum, controlled by one frequency range.

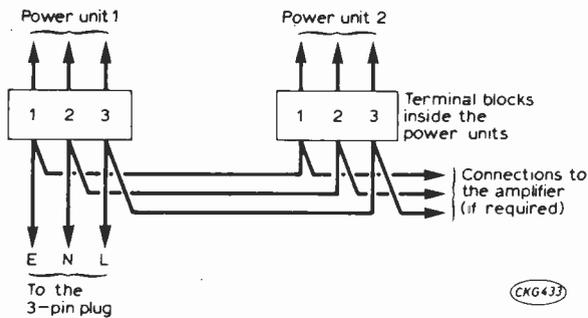


Fig. 16: Mains terminal block connections when using two control units.

uses 6BA nuts and bolts.

The three triacs and their associated heat sink uses 4BA nuts and bolts.

Fuses FS1, FS2 and FS3 are in the bass (red lamp), middle (green lamp) and treble (blue lamp) circuits respectively.

Unit Arrangement

The equipment consists of two units. One unit contains the control for the psychedelic lights, the filter circuits and the necessary power supply. It is advisable, but not essential, that this unit is located near to the 13A power socket and amplifier. The second unit is mobile and consists of three colour lamps mounted on a panel with a five core flexible cable attached to it. This unit can be hung on the wall, left on the table, or placed in some other convenient position.



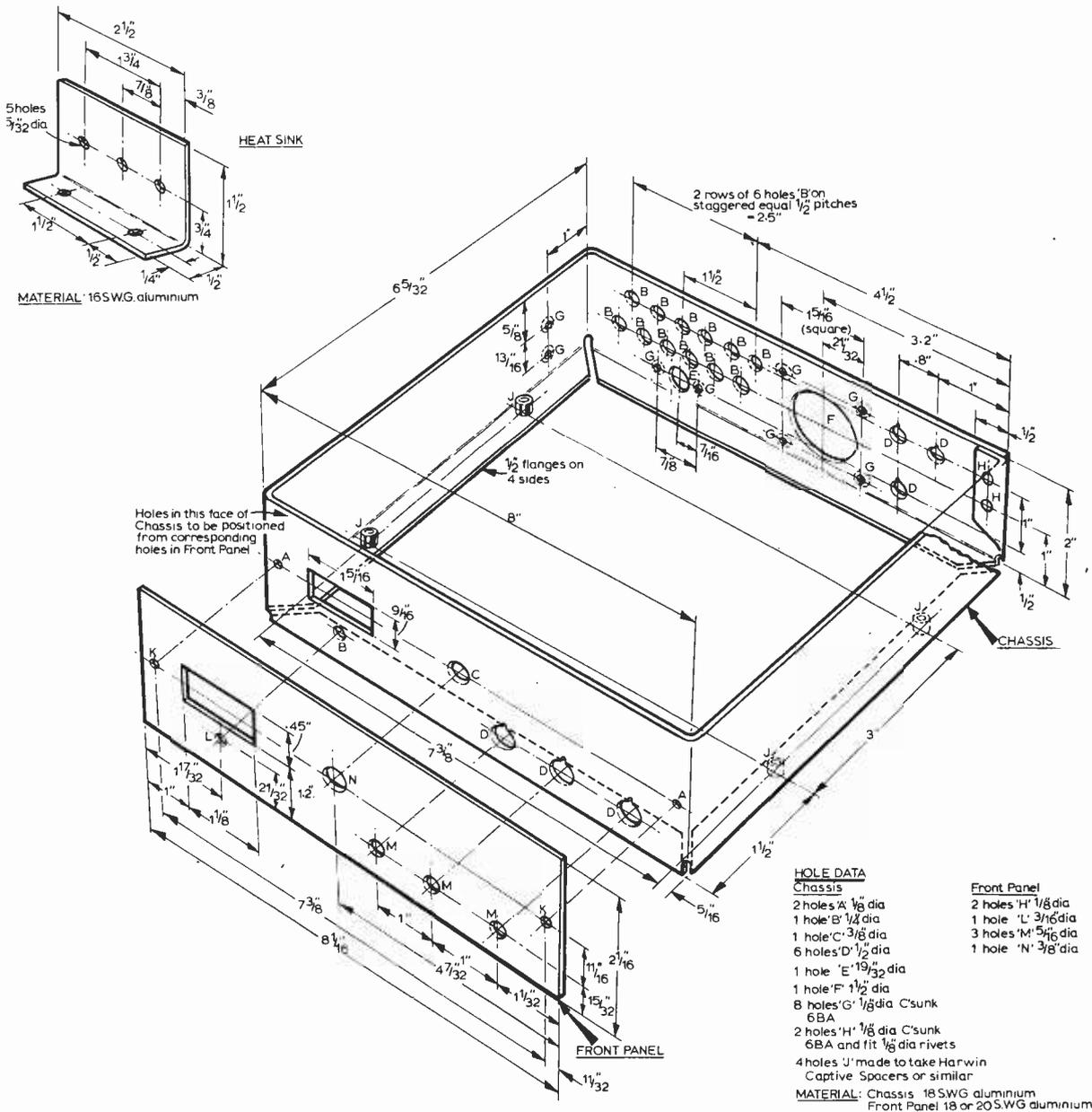


Fig. 17: Details of chassis construction and drilling with the heat sink shown top left, front panel left.

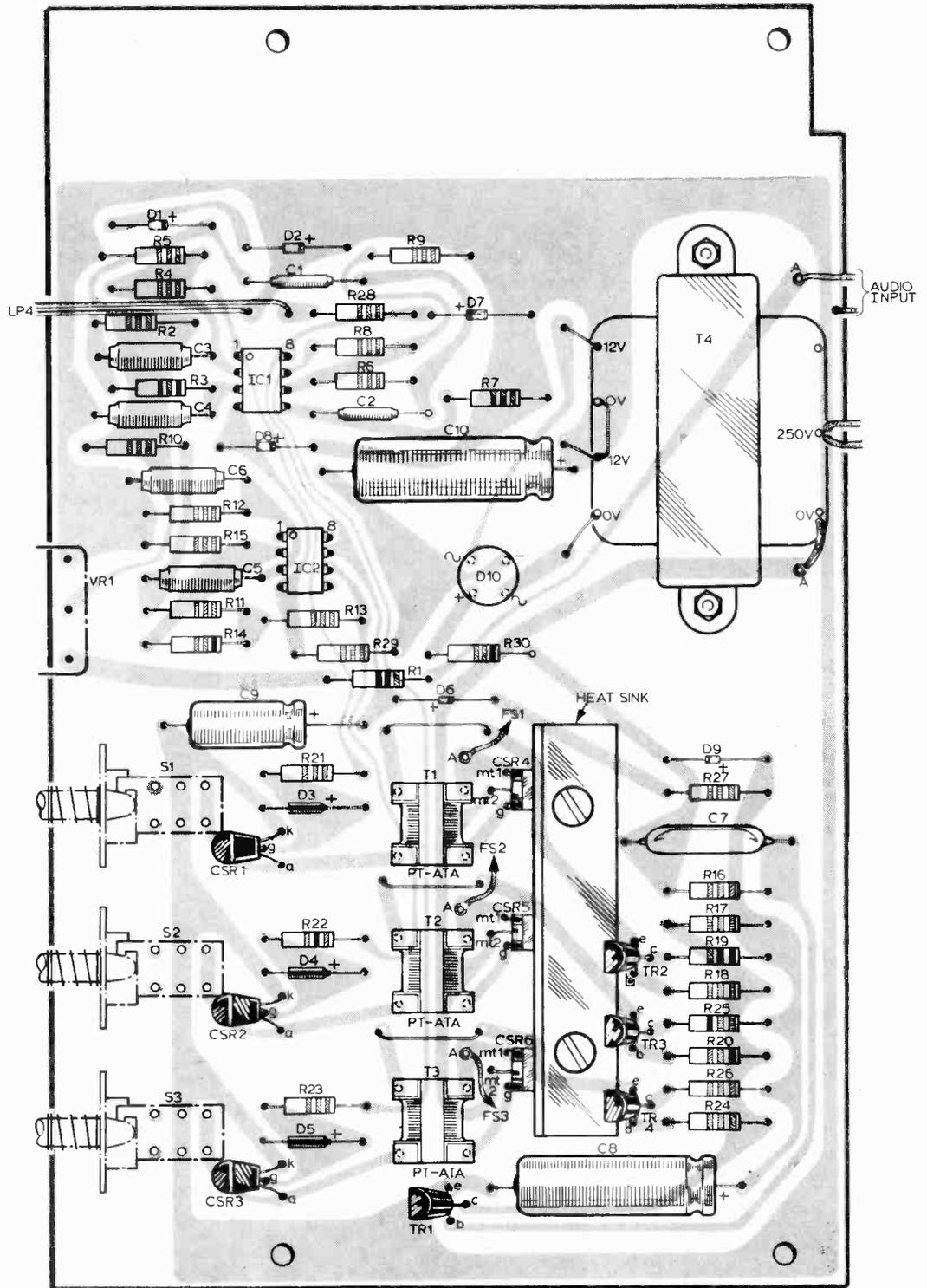

⊙ Indicates solder pins
in 5 positions A

Fig. 18 : Component layout and wiring to the printed circuit board. It will be observed that there are two leads from the 250V tag on T4. One lead is the live (L) lead from the mains terminal block. The other lead goes to tag 2 on the lights output socket.

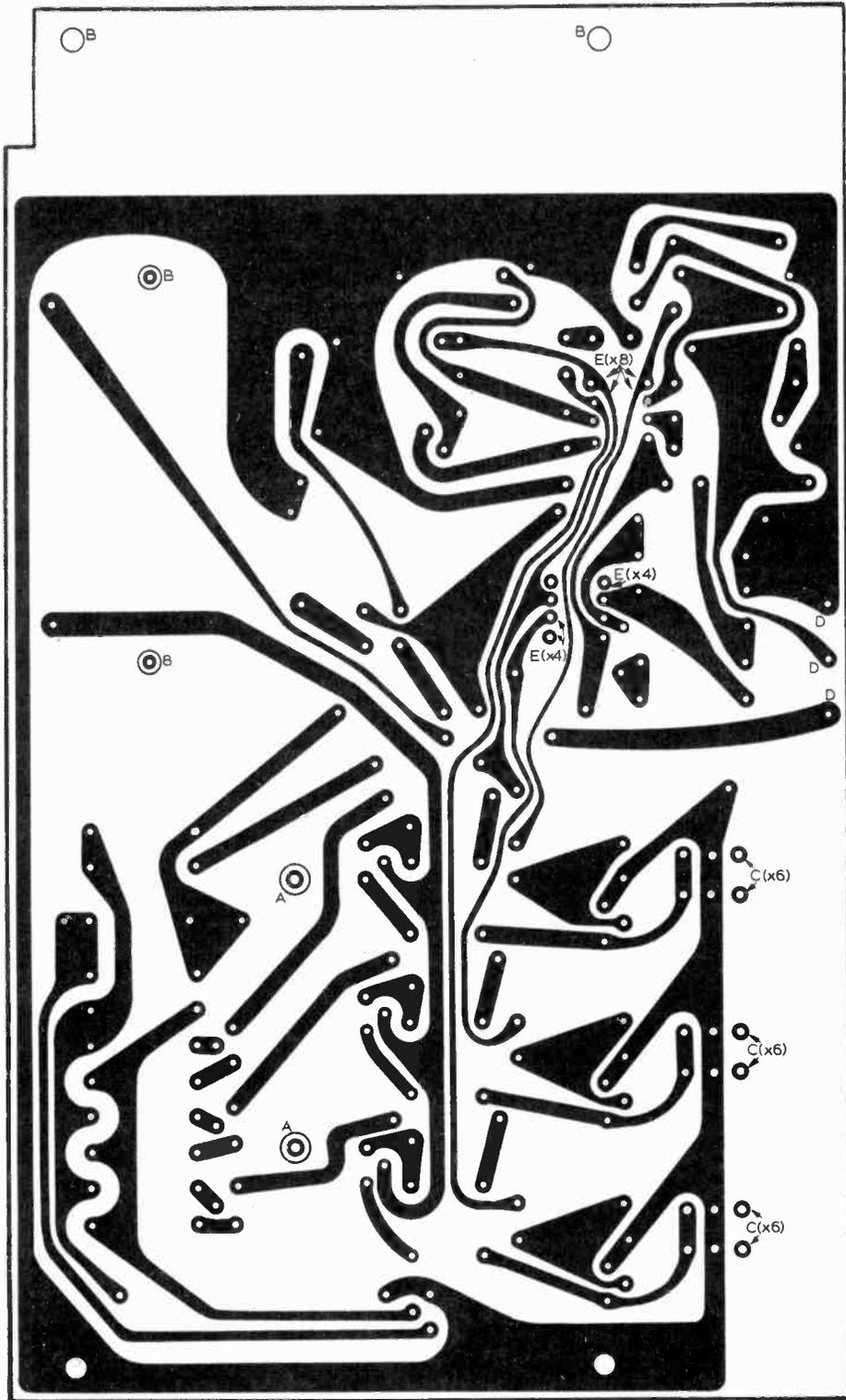

HOLE DATA

2 holes 'A' $\frac{7}{32}$ " dia 3 holes 'D' 1.8mm dia
 6 holes 'B' $\frac{1}{8}$ " dia 16 holes 'E' $\frac{1}{32}$ " dia
 18 holes 'C' 1.3mm dia
 All other holes 1.0mm dia

Fig 19: Full size pattern and drilling positions of the printed circuit board.

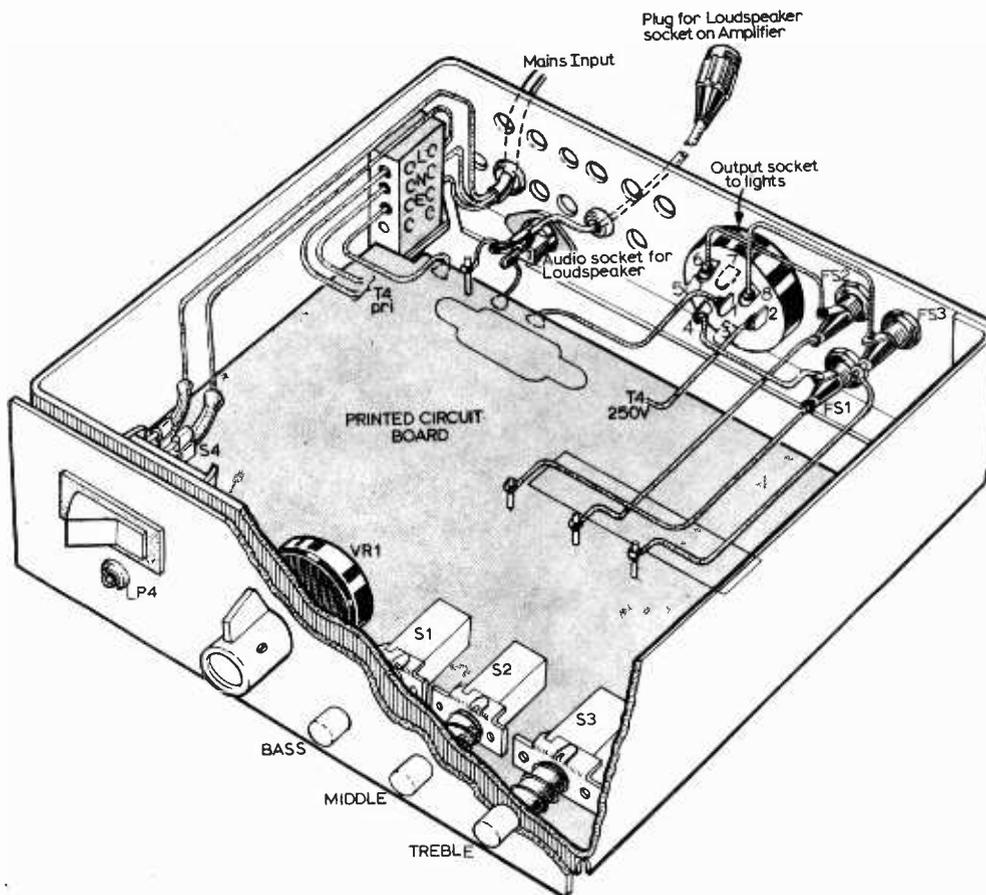


Fig. 20: Wiring of chassis mounted components to the printed circuit board. Tag 1 on the lights output socket goes to chassis (and mains earth). The live lead (L) from the mains terminal block goes to the 250V tag on T4 transformer.

The power control unit is capable of supplying three of these lamp units in parallel, each with its three coloured 100 watt lamps, i.e. a total power capability of 3×300 watts. Each lamp unit has a six way terminal block for interconnecting as shown in the diagrams.

Fig. 13 shows the connections for a single lamp unit. The five core cable is terminated with a plug suitable for connecting to the control unit. The figures in brackets show the pin numbers on the plug used. Connected thus, the three lamps will flash in accordance with frequency ranges present in the music.

Fig. 14 shows a triple unit arrangement, where each unit is connected in the same way as shown in Fig. 13. Here, however, the overall light level is increased and flexibility of lamp positioning is allowed, each lamp unit maintaining its three frequency range response.

A great deal of experimentation of lamp arrangement is worthwhile to achieve the best effect to suit your room and music. Fig. 15 gives another arrangement, using three lamp units, which is basically similar to that shown in Fig. 14, except that here each lamp unit will flash according to one frequency range.

The interconnections between speaker, amplifier and control units are also straightforward. Simply connect the speaker's DIN plug into the control unit and then plug in the cable from the control unit, now terminated with a DIN plug, into the amplifier. This should be done while all power is switched off. The amplifier should be connected via the control unit to a suitable loudspeaker before switching on.

The arrangement for a stereo system is very simple. Two control units and two lamp sets are required. A three core cable from a 13A socket is connected to the terminal board of control unit 1. From the same terminal board the second three core cable is connected to control unit 2 as shown in Fig. 16.

The advantage of this arrangement is obvious, i.e. only one 13A plug is used for both control units. If required, the power supply to the amplifier can also be taken from the terminal board of control unit 2 as shown in Fig. 16, thus achieving further simplification.

The interconnections between the control units, amplifier and speakers are similar to that described for the mono system but duplicated. Connect one speaker DIN plug into control unit 1 and then plug in the cable from it into the amplifier socket. This is repeated for the second speaker and control unit.

The effectiveness of the association of the light and music can be further improved if the lamps are placed near the speaker from which they are actuated. It is extremely effective when standing each lamp unit on or behind each speaker cabinet and projecting the lights up the walls behind.

The printed circuit board shown in this issue is for the zero voltage control version of the P.W. Tricolour only. A different printed circuit board, alternative components and slight alterations to the metalwork will be required for the version with lamp dimming facilities.

TO BE CONTINUED



designed for the discerning mind

Everything you need in the way of Discotheque equipment. Our 4 Disco Studio Centres with full light and sound facilities offer a comprehensive range of DJ Electronics equipment – apart from being appointed stockists for AKG, Reslo Sound, Beyer, etc., etc.

Our equipment is designed to provide maximum flexibility of operation. We have a range of versatile component units suited for the enthusiast and professional alike.

In fact you decide the specification and we provide the system. Amplifiers – Speaker Systems – Microphones – Discotheques – Sound to Light Units – Effects Projectors – Strobes. All you need including a wide range of sliders with ready cut panels.

Send for our new catalogue – you can mail order with no-deposit credit terms.

Our Studio Centres are open Monday to Saturday.

DISCOSCENE
536 Sutton Road, Southend, Essex – (0702) 611577

DISCOSOUND
122 Balls Pond Road, London, N.1 – (01) 254 5779

HENRY'S DISCO
309 Edgware Road, London, W.2 – (01) 723 6963

DISCOSOUND
90-98 Shaftesbury Avenue, London, W.1. – (01) 437 5832

PRODUCTION LINES

colin riches

ADJUSTABLE SPANNER

The picture shows a self-adjusting spanner suitable for all nut sizes from $\frac{7}{16}$ in. to $\frac{1}{2}$ in. A.F.

The end of the tool is placed over the nut and turned until the "tongue" of the spanner locks onto the nut.

It is constructed from chrome-vanadium steel and weighs $5\frac{1}{2}$ ozs. Finish is either matt (£1.49) or polished (£1.79). *Thunder Screw Anchors Ltd., Victoria Way, Burgess Hill, Sussex, RH15 9NF.*



TUAC EQUIPMENT

Tuac Ltd., are marketing a new range of ready-assembled modules and complete units. They are a "waa-waa" unit, fuzz box, disco "auto fade", octave doubler and a phase-splitter.

Leaflets which are issued in conjunction with Tuac kits can be obtained on receipt of a 3p stamp from: *Transistor Universal Amplification, Co. Ltd., 163 Mitcham Road, London, SW17 9PG.*


COMPONENT HOUSING TYPE LK8

Logikontrol Ltd., announce a compact component housing. It is made from high impact polystyrene and measures 90 x 50 x 37m.m. and at 25.4m.m. to the inch, you can work it out for yourselves! The internal volume is 10c.c. and it has facility for 2 printed circuit boards on which the components can be mounted.

Printed circuit connections and a snap-fit lid eliminate the need for a special plug and socket.

These units which are available in five different colours may be obtained from large component suppliers or in quantities of 10 upwards from Logikontrol direct, the 10 off price being 22p each. *Logikontrol Ltd., 17 Little Edward Street, London, NW1 4AT.*

AUTO GROOVE-KLEEN

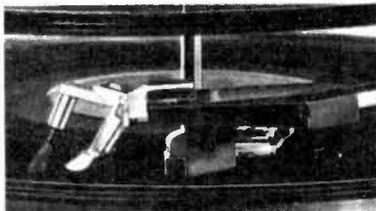

If you have an autochanger record playing unit, you have not been able up to now, to use a groove-cleaning brush to remove the dust and dirt from the records.

Bib seem to have solved this problem with their model 45 unit which just sticks onto the cartridge housing. Obviously to avoid any increase in stylus weight, the tone-arm should be re-balanced or the calibration control reduced by two grammes.

Due to the design, the velvet shoe and brush will not drag across the record when the tone arm moves from the end of one record to the outside of the record stack.

After the records have been played, the velvet shoe can be lifted off for cleaning with the separate brush supplied.

The price of this unit is 98p plus tax. *Bib Sales, P.O. Box 78, Hemel Hempstead Herts.*



GUIDE TO SEMICONDUCTORS

Motorola Semiconductors Ltd. have published a "master selection guide". It includes in its 150 pages brief technical details of 17 diode families from 4-layer to zener, hybrid circuits, microwave devices, optoelectronic components, rectifiers, triacs, diodes, linear integrated circuits and much more than we can describe here. The guide, which is free of charge, may be obtained from *Motorola Semiconductors Ltd., York House, Empire Way, Wembley Middlesex.*


TRANSISTOR TESTER

Transistor tester type TT169 has been announced by Avo. It is designed for GO/NO-GO in-circuit testing of p.n.p. and n.p.n. signal or power transistors. The tester is battery operated and small enough to be held in the hand. Front panel lights show whether a device is faulty or OK.

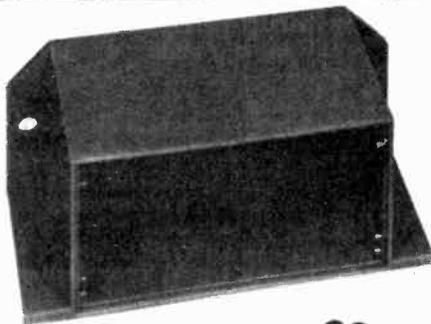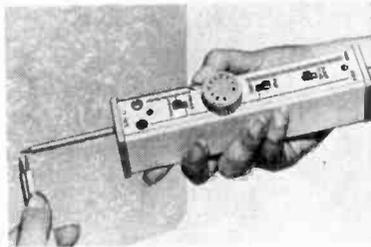
The TT169 comes with all the necessary leads and connector in a plastic case. The price is £17.50 plus VAT and readers may obtain them from the usual retailers and distributors. *Avo Limited, Avocet House, Dover, Kent.*



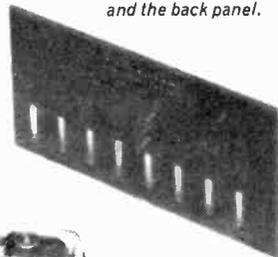(left) The plastic housing and the back panel.



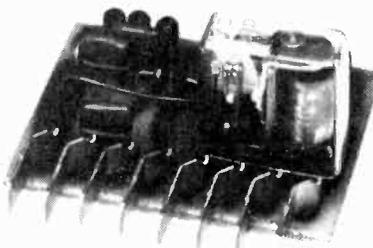(right) A component board which can be slotted into the housing



160-80 metre CONVERTER

R.A. PENFOLD

THIS is a simple device which is easy to construct and which when placed ahead of a medium wave receiver will enable it to cover the 80 and 160 metre amateur bands. The unit is self contained, and is housed in a diecast box measuring $4\frac{3}{4}$ in \times $3\frac{3}{4}$ in \times $2\frac{5}{8}$ in. An external long wire aerial and an earth are required.

Only two transistors are used, including a field-effect type in the mixer stage. Frequency stability is excellent as the oscillator is crystal controlled.

Heterodyne Principle

What is required of the converter is to receive a signal in either the 160 or 80 metre band and change this signal to a frequency which lies in the MW band. This can be achieved by heterodyning.

This is a process in which two signals are mixed to produce at the output, (a) the original two frequencies, (b) the sum of the two, and (c) the difference between the two. By the use of tuned circuits in the output, whichever of the two new frequencies produced is required can be selected.

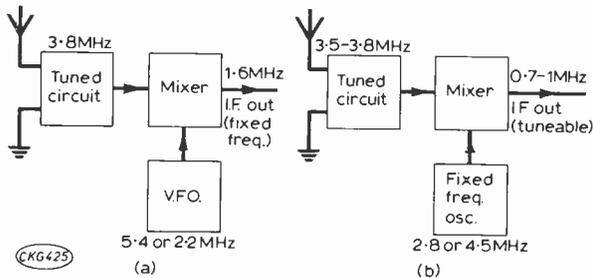


Fig. 1: Diagrams showing methods of converting a signal to a fixed or variable intermediate frequency.

The manner in which this process can be used in a converter is shown in Fig. 1. In the type of converter shown in Fig. 1a, the circuit is arranged so that the frequency to which the tuned circuit at the input is tuned is different from the operating frequency of the oscillator by the i.f. The tuning capacitors for the aerial tuned circuit and the oscillator would be ganged.

An example is given in the diagram of how a 3.8MHz signal is converted to a 1.6MHz i.f. There are two oscillator frequencies which will allow this ($3.8 - 1.6 = 2.2$ MHz, or $3.8 + 1.6 = 5.4$ MHz). In this type of converter the receiver is tuned to the i.f., and the tuning is carried out on the converter.

A second type of converter is shown in Fig. 1b. This type is often used in 2 and 4 metre VHF

amateur band converters. This time the tuning is carried out on the receiver, the oscillator on the converter being at a fixed frequency. The aerial tuned circuit should either be a broadband unit i.e. resonant over the entire band which is to be tuned, or should be tuneable over this range. Again there are two possible oscillator frequencies ($3.8 - 1 = 2.8$ MHz, $3.5 - 0.7 = 2.8$ MHz, $3.8 + 0.7 = 4.5$ MHz, $3.5 + 1 = 4.5$ MHz).

This type of converter has the advantage that the oscillator can be crystal controlled, simplifying alignment and giving very good stability. This type is also very much more simple and inexpensive. The system does have drawbacks as discussed later but the author's converter, which is of this type, has proved very successful.

Practical Circuit

A circuit diagram of the converter is shown in Fig. 2. Tr2 is operated as a Pierce oscillator the crystal being used on its parallel resonant frequency. The primary winding of the oscillator r.f. transformer, L5, forms the collector load for Tr2. R2 biases the transistor, C3—C5 produce a centre tap on the crystal, this centre tap being earthed.

Tr1 is the f.e.t. mixer stage. L1 is the aerial input coupling winding and L2 the aerial tuned winding. This can be tuned over the range 70-230 metres by VC1. Tr1 is used in the common-source mode, source bias being provided by R1 and C1 is its decoupling capacitor. Tr1's source and R1 are connected via the

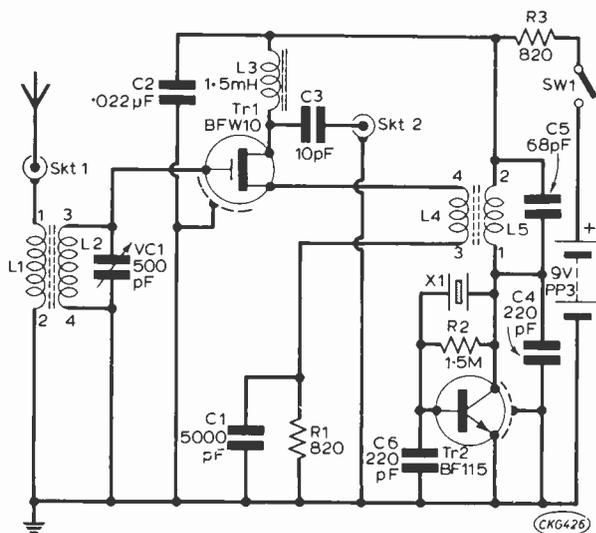


Fig. 2: Complete circuit of the converter unit.

secondary winding on the transformer, L4. The voltage across L4 modulates Tr1's drain and source voltages and thus mixes the oscillator signal and the input signal. A small r.f. choke, L3, forms the drain load for Tr1, the mixed output being coupled to the receiver via C3.

SW1 is the on-off switch, and R3 reduces the 9V supply to the required level. C2 is the supply decoupling capacitor.

The crystal frequency is chosen so that it can be used to convert signals in both the 80 and 160 metre bands to the MW band, the desired band being selected by tuning VC1—L2 to the correct frequency. Using a 2.8MHz crystal the 80 metre band will be converted to 0.7 - 1MHz ($3.8 - 2.8 = 1, 3.5 - 2.8 = 0.7$), and the 160 metre band will be converted to 0.8 - 1MHz ($2.8 - 1.8 = 1, 2.8 - 2 = 0.8$).

It is not essential for the crystal to operate exactly on 2.8MHz, as if it is a little either side of this frequency the converter will still operate but the tuning range on the receiver over which the amateur bands are covered will be slightly altered. A 2.794MHz crystal was used on the prototype.

Construction

The circuit is housed in an STC diecast box. The wiring is broken into two sections, a 5-way tagstrip on which the oscillator is constructed, and a 6-way tagstrip on which the mixer is built.

Diagrams illustrating the wiring of these two tagstrips are shown in Fig. 3 (mixer) and Fig. 4 (osc.). These two diagrams also show all other wiring of the converter. All the wiring is quite straightforward and should present no difficulty, even to a beginner. The only point which should be noted is that the screen lead of Tr1 is too short to reach to the appropriate tag unless a short piece of insulated wire is used to lengthen it.

Figure 5 shows the interior layout of the unit and also gives details of the mounting bracket of the crystal. This bracket is constructed from 18-22 swg sheet aluminium. The two tagstrips are mounted by $\frac{1}{2}$ in 6BA bolts, a stand-off insulator $\frac{1}{4}$ to $\frac{3}{8}$ in long being used to hold them clear of the sides of the case.

The battery is held in place by being trapped between the front, and rear of the case. A pad of expanded polystyrene, foam rubber or a similar material should be glued to the rear of the case where the battery would otherwise come into contact with it. This is to make it fit more firmly and to insulate the battery terminals from the case.

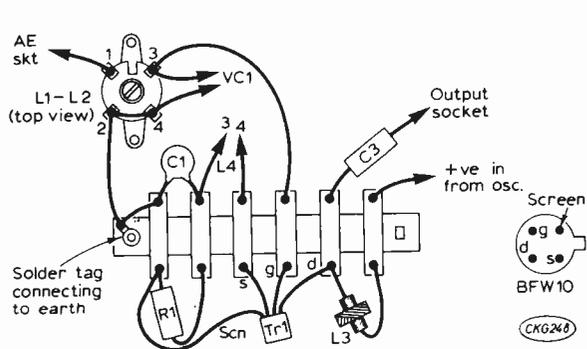


Fig. 3: Method of wiring the mixer stage components.

★ components list

Resistors

R1 820Ω
R2 1.5MΩ
R3 820Ω } All $\frac{1}{4}$ W, 5 per cent types

Capacitors

C1 5000pF
C2 0.022μF polystyrene etc.
C3 10pF ceramic or silver mica
C4 220pF polystyrene or silver mica
C5 68pF polystyrene or silver mica
C6 220pF polystyrene or silver mica

Semiconductors

Tr1 BFW10 or similar f.e.t.
Tr2 BF115

Miscellaneous

L1/2 Repanco RA3; L3 miniature r.f. choke, about 1.5mH; L4/5 Repanco RO3; SW1, on-off switch; STC diecast box, size 2 ($4\frac{1}{2} \times 3\frac{1}{2} \times 2\frac{1}{2}$ in.); HC6U crystal, about 2.8MHz with holder (see text) (Henry's Radio); 1-off each 5-way and 6-way tag strip; 2-off coax sockets; Knob; Battery and clip.

As supplied, the exterior finish of the diecast box is rather rough and dirty. If the case is to be painted it will be necessary to thoroughly clean it first with a scouring pad. If preferred it can be cleaned in this way, and then polished to a bright natural finish.

Using the Converter

An external aerial is required; this merely consists of a length of wire which is mounted as high as possible and is as long as possible. An earth of some sort is essential for the correct operation of the circuit, although this does not necessarily have to be a very efficient one. The prototype is fitted with coaxial sockets for the aerial, earth and output connections.

Ideally the converter should be used in conjunction with a broadcast receiver which requires an external aerial. The receiver and the converter are connected by a short screened cable. In this way there is a minimum of interference picked up on the MW band directly by the receiver.

It was found possible to use the converter with an

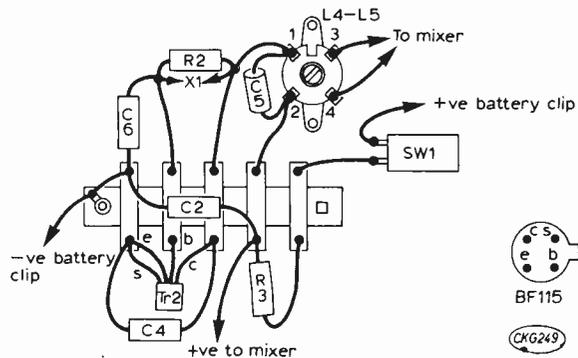


Fig. 4: Tagstrip construction of the oscillator stage.

ordinary transistor receiver. C3 should be removed, and a piece of wire connected in its place. It is then merely necessary to take a short lead from the converters output socket, and to place this alongside the receiver's ferrite aerial.

In this way it was found possible to receive a number of amateur stations on both the 80 and 160 metre bands. MW stations received directly by the receiver can prove bothersome, especially after dark.

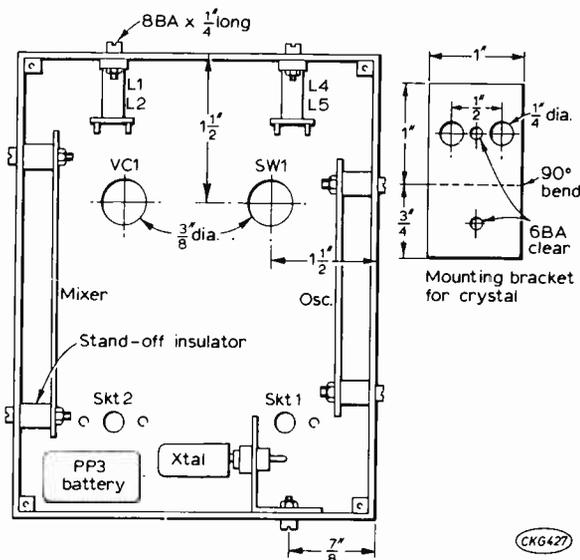


Fig. 5: Layout of components and tagstrips inside the die-cast box.

Operating the controls on the converter is very simple, as there are only two. SW1 is the on-off switch. VC1 tunes the converter to the desired band. With this control turned almost fully anti-clockwise it should be found possible to tune the 80 metre band and with it turned almost fully clockwise it should be possible to tune 160 metres.

With VC1 approximately adjusted in this way, it should be possible to receive a few signals. VC1 can then be peaked for maximum sensitivity. A simple dial can be marked around the control knob of VC1 showing the areas over which the amateur bands are tuned.

Results

Using the converter with a 132ft. longwire aerial at about 20ft., in conjunction with a 6 transistor MW portable receiver, a large number of amateur stations have been heard. The 160 metre band is of course used mainly for local working, and a.m. is still used to a certain extent. Stations up to about 50 miles distant have been received on this band without too much difficulty.

Due to its simplicity, the circuit does have one drawback. Top Band is not only used for amateur transmissions but also for maritime ones. These transmissions are fairly powerful and occasionally when tuning the 80 metre band transmissions from ships in the nearby Thames estuary did break through. Conversely, a local amateur using a powerful SSB transmitter on 80 metres did tend to break through on the 160 metre band.

COMPARE OUR PRICES

Speaker Bargains		Microphone Bargains	
E.M.I. 13 x 8 in 3, 8 & 15 OHMS	£2.00	MIC45 "ACOS" metal case, crystal hand	95
PLAIN	£2.25	CM 20 Crystal Hand	45
WITH TWEETER	£2.25	DX143 Dynamic, cassette-type stick	£1.00
Type 350-20 watt with Tweeter	£2.25	CM70 PLANET stick metal, switch crystal	£1.45
8. OHM p. & p. 37p.	£7.25	DM160 Dynamic uni-dir, ball metal	£3.75
TWIN TWEETER	£3.50	UD130 50K/600 OHM uni-dir, ball metal	£4.50
8 x 5 in 3, 8 & 15 OHMS	£1.30	TW209 LESSON DUAL IMP ball metal, uni-dir.	£5.75
7 x 4 in 3 & 8 OHMS	£1.05	CONDENSER MIKE uni-dir.	£7.95
FANE 2" 8. OHM DUAL CONE	£2.30	GIUITAR MIKE	45
CELESTION 8" 15. OHM	£1.50	POSTAGE 17p each.	40
BAKER GROUP 25 12" 25 WATT 8 or 15. OHM	£5.75		
2 1/2" 8 or 64 OHM p. & p. 10p.	50		
POSTAGE 25p per SPEAKER			
Kit-Form Cabinets Teak (17" x 10" x 6") with a 13" x 8" or 8" CUT OUT	£2.75		
(12" x 12" x 6") with a 8" x 5" or 8" CUT OUT	£2.25		
(PLEASE SPECIFY CUT OUT)			
Add 35p per Cabinet for p. & p.			
Cartridges with standard fittings & styli			
GOLDRING G850	£3.25	Battery Eliminators	
GOLDRING G800	£4.95	240v input 6 or 9v d.c. output at 150 mA	£1.99
ACOS GP91/25C or GP91/35C STEREO COMPATIBLE	£1.05	240v input 6, 7 1/2 or 9v output at 300 mA	£2.99
ACOS GP94 STEREO CER.	£1.75	12v d.c. input (for cars) 6, 7 1/2 or 9v d.c. output at 300 mA P. & P. 10p	£2.99
ACOS GP95 STEREO CRYST.	£1.35		
ACOS GP96 STEREO CER.	£1.75	Tapes - "MYLAR" base finest quality British made.	
9THAC SONOTONE STEREO CERAMIC (DIAMOND)	£1.95	5" 600 ft 36p	5 1/2" 1800 ft 85p
9THAC/S SONOTONE STEREO CER. (DIAMOND) SLIMLINE	£1.95	5" 900 ft 45p	7" 1200 ft 55p
ACOS GP87/2C MONO CRYST.	.65	5" 1200 ft 60p	7" 1800 ft 80p
ACOS GP101 COMP. CRYST.	.75	5 1/2" 900 ft 49p	7" 2400 ft 95p
19-TI. SONOTONE STEREO CRYSTAL	.90	5 1/2" 1200 ft 55p	
POSTAGE 5p per CARTRIDGE		POSTAGE 9p each.	
		PLASTIC LIBRARY CASES	
		for 5in Reels 16p	
		5 1/2in Reels 19p	
		7in Reels 21p	
		P. & P. 5p each	

THIS MONTH'S SPECIAL OFFER
AMSTRAD STEREO HEADPHONES
 Model HPS 5A with v. controls. Recommended retail price £6.95.
 Our Price £3.95. P. & P. 25p.

SEND 25p FOR COMPLETE CATALOGUE
 Slight price alterations due to VAT will effect certain of our items after April 1st

RIVERSDALE ELECTRONICS
 Mail Order Department W5/73, P.O. Box 470, Manchester M60 4BU
 ALL OUR MERCHANDISE IS FULLY GUARANTEED



become
a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

WBS3
 BLOCK CAPS please



BROADCAST BANDS

SHORT WAVE RECEIVER CHOICE by MALCOLM CONNAH

By far the largest portion of my mailbag consists of letters from readers asking my advice on the choice of a receiver. I have often said that this is a very difficult subject on which to give advice, partly because the letters give very little information and partly because "one man's meat is another man's poison".

In order to assist the less technically minded reader to select a receiver to meet his requirements I am going to devote this article to discussing the various features of receivers which are important for good short wave reception.

1. Frequency Coverage: The most common type of receiver is the General Coverage Receiver. This type of receiver usually tunes from 540kHz to 30MHz in four bands. One of these bands covers the medium wave band leaving three bands of short wave coverage.

Due to the number of stations on the bands it is very desirable to have a separate bandspread, or fine tuning, control. This control has the effect of expanding a small portion of the tuning scale making it much easier to tune in a particular station. The much-advertised transistor portable receivers are usually lacking in this respect.

An alternative method of frequency coverage is found in the more expensive receivers which have a number of bands each covering 500kHz of the spectrum. These receivers usually cover the Amateur bands only but can be ordered with coverage of the Broadcast bands. The tuning of these receivers is so fine that a separate bandspread control is not required.

In general the listener must ensure that the receiver covers the bands in which he is interested and that the tuning can be finely controlled.

2. Number of Conversions: The number of conversions that a receiver has is the number of different i.f.'s (Intermediate Frequencies) that it has. The normal single conversion receiver has a single i.f. usually in the range 455-470kHz, although 1.6MHz is sometimes used. The double conversion receiver has two different i.f.'s. In general, the more i.f.'s a receiver has, the better the selectivity and image rejection will be.

3. RF Stages: Some of the simpler receivers available have no r.f. stage and the signal is passed from the aerial to the mixer stage directly. The addition of an r.f. stage will increase the sensitivity of the receiver and also improve the image rejection of a single conversion set. As mentioned last month this problem can be overcome by adding a preselector between the aerial and the receiver.

4. Operating Modes: The Broadcast Bands listener is usually only interested in amplitude modulated (a.m.) signals and this mode of operation is, therefore, essential. If the set is also to be used for reception of Amateurs provision should be made for code (c.w.) reception, this also allows reception of single sideband (s.s.b.) transmissions. However, the provision of a product detector gives much better s.s.b. reception. If the provision also exists for manual selection of the upper or lower sideband this facility can be used during the reception of a.m. signals to avoid interference and fading effects.

5. Selectivity: The selectivity of a receiver is its ability to separate stations on adjacent frequencies. It is extremely useful to have the facility of varying the selectivity of the receiver. When interference is heavy a narrow selectivity can be used to cut out the interference. Mechanical or crystal filters help to improve the selectivity of a receiver.

6. Stability: It is essential for a good receiver to be stable in operation. With some valve receivers the heating effects involved caused frequency drift and other annoying effects. The introduction of transistors and, in particular, field-effect transistors has greatly improved the situation due to the low heating effects associated with these devices.

7. Valves vs. Transistors: Apart from improving stability, as mentioned above, transistors have many advantages in communication receivers. They have a longer life, require simpler power supplies and are low cost. The benefits of this are that transistor receivers tend to be smaller, lighter in weight, less expensive and also have the option of being operated from an external battery.

8. Automatic Volume or Gain Control (a.v.c. or a.g.c.) Almost every receiver has some form of a.v.c. or a.g.c. which adjusts the gain of the receiver to compensate for changes in signal strength. A receiver with variable a.v.c. or a.g.c. is to be preferred as the optimum setting can then be used.

9. Extras: Most receivers have various extras of which the following are the most useful. (a) The provision of a headphone socket. (b) An aerial trimmer to match the aerial to the set. (c) A signal strength meter (S-meter) to assist with tuning. (d) A crystal calibrator to check the dial accuracy. (e) A noise limiter which should be variable if possible. (f) A notch filter to reduce heterodynes.

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. **BRANDED FROM TEXAS I.T.T. FAIRCHILD**



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
BN7400	0-20	0-18	0-18	BN7400	0-20	0-18	0-18	BN74148	1-50	1-40	1-30
BN7401	0-20	0-18	0-18	BN7401	0-20	0-18	0-18	BN74150	3-36	2-95	2-15
BN7402	0-20	0-18	0-18	BN7403	0-20	0-18	0-18	BN74151	1-10	0-95	0-90
BN7403	0-20	0-18	0-18	BN7404	0-20	0-18	0-18	BN74153	1-36	1-27	1-20
BN7404	0-20	0-18	0-18	BN7405	0-20	0-18	0-18	BN74154	2-00	1-75	1-65
BN7405	0-20	0-18	0-18	BN7406	0-20	0-18	0-18	BN74155	1-56	1-47	1-35
BN7406	0-30	0-27	0-25	BN7407	0-30	0-27	0-25	BN74156	1-56	1-47	1-35
BN7407	0-30	0-27	0-25	BN7408	0-20	0-19	0-18	BN74157	1-80	1-70	1-55
BN7408	0-20	0-19	0-18	BN7409	0-45	0-42	0-35	BN74160	2-60	2-40	2-25
BN7410	0-20	0-18	0-18	BN7411	0-28	0-22	0-20	BN74161	2-60	2-40	2-25
BN7412	0-48	0-44	0-40	BN7413	0-48	0-44	0-40	BN74162	3-40	3-25	3-20
BN7414	0-30	0-27	0-25	BN7415	0-48	0-44	0-40	BN74163	3-40	3-25	3-20
BN7416	0-30	0-27	0-25	BN7417	0-30	0-27	0-25	BN74164	2-76	2-80	2-10
BN7418	0-30	0-27	0-25	BN7419	0-48	0-44	0-40	BN74165	4-00	3-85	3-00
BN7420	0-30	0-27	0-25	BN7421	0-30	0-27	0-25	BN74166	4-00	3-85	3-00
BN7422	0-48	0-44	0-40	BN7423	0-48	0-44	0-40	BN74167	6-25	6-50	6-10
BN7424	0-20	0-18	0-18	BN7425	0-48	0-44	0-40	BN74170	4-10	3-55	3-10
BN7426	0-48	0-44	0-40	BN7427	0-48	0-44	0-40	BN74172	2-00	1-75	1-30
BN7428	0-48	0-44	0-40	BN7429	0-48	0-44	0-40	BN74175	1-85	1-27	1-15
BN7430	0-20	0-18	0-18	BN7431	0-48	0-44	0-40	BN74176	1-80	1-35	1-20
BN7432	0-42	0-39	0-35	BN7433	0-42	0-39	0-35	BN74177	4-00	3-85	3-00
BN7434	0-70	0-61	0-44	BN7435	0-70	0-61	0-44	BN74180	1-85	1-20	1-20
BN7436	0-48	0-44	0-40	BN7437	0-48	0-44	0-40	BN74181	7-00	6-00	5-50
BN7438	0-48	0-44	0-40	BN7439	0-48	0-44	0-40	BN74182	1-00	0-80	0-60
BN7440	0-20	0-18	0-18	BN7441	0-20	0-18	0-18	BN74184	2-40	2-00	1-80
BN7442	0-75	0-72	0-70	BN7443	0-75	0-72	0-70	BN74185A	2-60	2-30	2-00
BN7444	0-75	0-72	0-70	BN7445	2-00	1-75	1-60	BN74190	1-95	1-85	1-75
BN7446	2-00	1-75	1-60	BN7447	1-75	1-60	1-45	BN74191	2-00	1-90	1-80
BN7448	1-75	1-60	1-45	BN7449	1-75	1-60	1-45	BN74192	2-00	1-90	1-80
BN7450	0-20	0-18	0-18	BN7451	0-20	0-18	0-18	BN74193	2-00	1-90	1-80
BN7452	0-48	0-44	0-40	BN7453	0-48	0-44	0-40	BN74194	2-60	2-25	1-90
BN7454	0-48	0-44	0-40	BN7455	0-48	0-44	0-40	BN74195	1-85	1-70	1-60
BN7456	0-48	0-44	0-40	BN7457	0-48	0-44	0-40	BN74196	1-80	1-40	1-30
BN7458	0-48	0-44	0-40	BN7459	0-48	0-44	0-40	BN74197	1-60	1-40	1-30
BN7460	0-48	0-44	0-40	BN7461	0-48	0-44	0-40	BN74198	4-80	3-70	3-55
BN7462	0-48	0-44	0-40	BN7463	0-48	0-44	0-40	BN74199	4-80	3-70	3-55
BN7464	0-48	0-44	0-40	BN7465	0-48	0-44	0-40	BN74200	4-80	3-70	3-55
BN7466	0-48	0-44	0-40	BN7467	0-48	0-44	0-40	BN74201	4-80	3-70	3-55
BN7468	0-48	0-44	0-40	BN7469	0-48	0-44	0-40	BN74202	4-80	3-70	3-55
BN7470	0-48	0-44	0-40	BN7471	0-48	0-44	0-40	BN74203	4-80	3-70	3-55
BN7472	0-48	0-44	0-40	BN7473	0-48	0-44	0-40	BN74204	4-80	3-70	3-55
BN7474	0-48	0-44	0-40	BN7475	0-48	0-44	0-40	BN74205	4-80	3-70	3-55
BN7476	0-48	0-44	0-40	BN7477	0-48	0-44	0-40	BN74206	4-80	3-70	3-55
BN7478	0-48	0-44	0-40	BN7479	0-48	0-44	0-40	BN74207	4-80	3-70	3-55
BN7480	0-48	0-44	0-40	BN7481	0-48	0-44	0-40	BN74208	4-80	3-70	3-55
BN7482	0-48	0-44	0-40	BN7483	0-48	0-44	0-40	BN74209	4-80	3-70	3-55
BN7484	0-48	0-44	0-40	BN7485	0-48	0-44	0-40	BN74210	4-80	3-70	3-55
BN7486	0-48	0-44	0-40	BN7487	0-48	0-44	0-40	BN74211	4-80	3-70	3-55
BN7488	0-48	0-44	0-40	BN7489	0-48	0-44	0-40	BN74212	4-80	3-70	3-55
BN7490	0-48	0-44	0-40	BN7491	0-48	0-44	0-40	BN74213	4-80	3-70	3-55
BN7492	0-48	0-44	0-40	BN7493	0-48	0-44	0-40	BN74214	4-80	3-70	3-55
BN7494	0-48	0-44	0-40	BN7495	0-48	0-44	0-40	BN74215	4-80	3-70	3-55
BN7496	0-48	0-44	0-40	BN7497	0-48	0-44	0-40	BN74216	4-80	3-70	3-55
BN7498	0-48	0-44	0-40	BN7499	0-48	0-44	0-40	BN74217	4-80	3-70	3-55
BN7500	0-48	0-44	0-40	BN7501	0-48	0-44	0-40	BN7502	0-48	0-44	0-40

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX

LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SN 74 HO } Now in stock - send
LOW POWER SM 74 LOO } for list No. 36

A SELECTION OF SPECIAL-CONDUCTORS FROM STOCK

AAY30 10p	BC147 12p	BU105 2-25	OC44 15p	T1843 35p	2N3055 55p
AZ42 15p	BC190C 12p	BU106 15p	OC45 15p	V405A 25p	2N3440 75p
AZ13 10p	BC182 10p	BY126 15p	OC77 15p	ZTX108 15p	2N3442 75p
AC107 85p	BC214 15p	BY127 15p	OC71 15p	ZTX200 15p	2N3525 75p
AC126 25p	BCY32 75p	BZ13 35p	OC72 25p	ZTX201 15p	2N3614 65p
AC127 25p	BCY34 35p	C106D 65p	OC77 45p	ZTX202 15p	2N3615 75p
AC128 25p	BCY39 100p	GET111 55p	OC81 25p	ZTX241 20p	2N3702 10p
AC176 25p	BCY42 30p	GET116 55p	OC83 25p	ZTX260 15p	2N3704 10p
AC187 25p	BCY43 25p	GET880 45p	OC140 55p	ZTX203 17p	2N3711 85p
AC188 25p	BCY55 2-50	LM309K	OC170 25p	2G301 30p	2N3714 1-75
ACY17 20p	BCY70 15p	(T03) 1-87	OC171 80p	2N404 20p	2N3771 1-75
ACY20 20p	BCY71 20p	MAT121 25p	OC200 45p	2N527 35p	2N3773 2-25
ACY21 20p	BCY72 15p	MJE340 50p	OC201 75p	2N598 15p	2N3790 2-25
ACY39 55p	BCY87 2-99	MJE370 70p	OC202 80p	2N599 15p	2N3819 25p
AD140 50p	BCZ11 50p	MJE920 75p	OC203 50p	2N793 10p	2N3820 50p
AD149 50p	BD124 80p	MJE2855	OC271 1-25	2N930 20p	2N3865 85p
AD161 35p	BD131 75p	1-10	ORP12 50p	2N987 45p	2N3903 15p
AD162 35p	BD132 80p	MJE3055	ORP60 40p	2N1131 25p	2N3906 12p
AF117 20p	BF115 25p	75p	P346A 20p	2N1132 25p	2N4061 12p
AF118 50p	BF167 25p	MFP105 40p	RA8310AF	2N1302 18p	2N4062 12p
AF124 25p	BF173 25p	NKT214 20p	RA8508AF	2N1304 25p	2N4126 15p
AF139 30p	BF179 30p	NKT216 40p	RA8508AF	2N1305 25p	2N4271 35p
AF186 40p	BF180 30p	NKT217 40p	55p	2N1307 25p	2N4547 30p
AF239 40p	BF194 15p	NKT403 70p	TAA263 75p	2N1308 25p	2N5777 55p
AS927 30p	BF195 15p	NKT404 50p	T1209 39p	2N1613 20p	28001 1-00
AS928 25p	BF196 15p	OA5 50p	TIP29A 50p	2N1671 1-00	28012 10-00
B102 30p	BF197 25p	OA10 35p	TIP30A 60p	2N2147 75p	28018 8-25
B115 7p	BFX13 25p	OA81 10p	TIP31A 60p	2N2150 59p	28026 9-00
B145 15p	BFX34 75p	OA91 7p	TIP32A 70p	2N2217 25p	28301 50p
BAX13 5p	BFX37 30p	OA200 7p	TIP33A	2N2221 20p	28303 65p
BAX16 7p	BFX68 20p	OA202 10p	1-00	2N2222A	28324 95p
BC107 10p	BFY50 20p	OC116 75p	TIP34A	25p	40250 50p
BC108 10p	BFY51 20p	OC20 85p	1-50	2N2369A	40380 40p
BC109 10p	BFY32 20p	OC23 35p	TIP35A	1-50	40392 50p
BC109C 12p	BFY64 50p	OC25 40p	2-50	2N2906 20p	40362 50p
BC113 15p	BFY90 50p	OC28 55p	TIP36A	2N2926 (all	40408 50p
BC117 20p	BSX20 15p	OC35 50p	3-00	cols)	40486 75p
BC143 35p	BSY27 15p	OC36 65p	TIP41A 75p	2N3053 20p	40636 1-10
		OC42 40p	TIP42A 85p	2N3054 50p	40430 1-00

VAT Prices DO NOT include Value Added Tax. From 1st April, 1973 10% must be added and shown separately to your total order (inclusive Post/packing). Help us to help you receive your order without delay. **E. & O. E.**

QUANTITY DISCOUNTS

10% 12+ ; 15% 25+ ; 20% 100+ ; 25% 250+ ; ANY ONE TYPE
From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value £1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SPECIAL-CONDUCTORS

BFY90 1000 MC/S	59p	2N2926 10p	All Colours
25 + 50p		25 + 9p	
100 + 45p		100 + 8p	
500 + 40p		500 + 6p	
		1000 + 5p	
AF117 Mullard 25p		2N3819 Texas 35p	
25 + 17p		25 + 30p	
100 + 15p		100 + 25p	
500 + 12p		500 + 20p	
		1000 + 15p	
OC170 Mullard 25p		BC107, BC108, BC109 10p each	
25 + 20p		All Makes	
100 + 18p		25 + 8p	
500 + 15p		100 + 7p	
1000 + 13p		500 + 6p	
		1000 + 5p	
BY127 Mullard 15p		AD161, AD162 35p each	
25 + 12p		25 + 32p	
100 + 10p		100 + 28p	
500 + 9p		500 + 25p	
1000 + 8p		1000 + 22p	
OA202 10p		2N3053 20p	
25 + 8p		25 + 18p	
100 + 7p		100 + 15p	
500 + 6p		500 + 12p	
1000 + 5p		1000 + 10p	
OC35 Mullard 50p		2N3055 55p	
25 + 45p		25 + 50p	
100 + 40p		100 + 45p	
500 + 35p		500 + 38p	
1000 + 30p		1000 + 33p	

PLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier SL403D

Complete with 8-page booklet, circuits and data. **£1.50** each



TRIACS

Type	Volts	Price
3 AMP RANGE	P.I.V. 1-11	
BC35A	100	75p
BC35B	200	79p
BC35D	400	85p
6 AMP RANGE (T048)		

BAKER 12in MAJOR £9



30-14500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly flux density 145000 gauss. Bass resonance 40 c.p.s. 20 watt RMS.

MAJOR MODULE KIT £11-50

30-17000 cps. with tweeter, crossover and baffle.

Baker Loudspeakers full range			
Regent 12in	£8	Superb 12in	£15
Major 12in	£9	Auditorium 12in	£14
Deluxe 12in	£10	Auditorium 15in	£20
		Group 25 12in	£8
		Group 35 12in	£9
		Group 50 15in	£20

Baker Loudspeaker Co., Bensham Manor Passage,
Thornton Heath, Surrey. Tel. 01-684 1665

FERRANTI *Radio i.c.*

ZN414

only £1.32

WITH FREE DATA

BF859	15p	ZTX300	12p	ZTX502	17p	Z8178	38p
BF860	20p	ZTX301	13p	ZTX503	14p	Z8270	11p
BF861	20p	ZTX302	17p	ZTX504	43p	Z8272	18p
BF896	15p	ZTX303	14p	ZTX530	21p	Z8374	19p
BF897	23p	ZTX304	21p	Z8142	33p	Z8279	26p
BF898	20p	ZTX310	9p	Z8170	10p	Z8278	37p
ZTX107	8p	ZTX330	15p	Z8171	13p		
ZTX108	8p	ZTX384	18p	Z8172	16p		
ZTX109	11p	ZTX500	12p	Z8174	17p		
ZTX214	15p	ZTX501	13p	Z8176	23p		

* Zeners *
K8030A to K8180A 19p

All devices top grade, brand new, fully guaranteed. We specialize in Ferranti semiconductors and can supply any device. Postage & Packing 10p. Free over £2. Send S.A.E. for full list and data. All prices include V.A.T.

DAVIAN ELECTRONICS

PO BOX 38, OLDHAM, LANCS. OL2 6XJ

GUNTON ELECTRONIC IGNITION KIT £9.35

inc. V.A.T.

PRINTED CIRCUIT BOARD DESIGN. ALL METALWORK READY-DRILLED

READY BUILT UNIT GUARANTEED 5 YEARS £11.55 inc. V.A.T.

Patents pending. 12 volt only—state pos. or neg. earth
Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- ★ Continual Peak-Tuned Performance
- ★ Up to 20% reduced fuel consumption
- ★ Easier All-weather Starting
- ★ Increased Acceleration and Top Speed
- ★ Longer Spark Plug Life
- ★ Increased Battery Life
- ★ Elimination of Contact Breaker Burn
- ★ Purer Exhaust Gas Emission



Kit includes absolutely everything for assembly: Case, Cables, Coil Connectors, Silicon Grease, etc. 8 page illustrated Instructions cover fitting of all Types of Tachometers. Call in for a Workshop Demonstration. S.A.E. all enquiries please or Phone 33652 (many letters from satisfied customers)

ALUMINIUM BOXES

Complete with baseplate and screws

At direct from manufacturer prices with return of post service

Type No.	L	W	D	Price
7*	5½	2½	1½	44p
8*	4	4	1½	44p
9*	4	2½	1½	44p
10*	5½	4	1½	53p
11	4	2½	2	44p
12	3	2	1	39p
13	6	4	2	59p
14	7	5	2½	68p
15	8	6	3	88p
16	10	7	3	96p

*THESE SIZES ACCEPT STANDARD VEROBOARD RANGE ALL PRICES INCLUDE V.A.T.
20% DISCOUNT ON ORDERS FOR 10 OR MORE BOXES

DEPT. PW 4 ELECTRONICS DESIGN ASSOCIATES
82 BATH STREET, WALSALL WSI 3DE

TEXAN 20+20 WATT. STEREO AMPLIFIER

Electro Spares can now supply all the components to build the "Texan" Amplifier, featured in *Practical Wireless* May/June 1972. All components are brand new with fibre glass p.c. board, all metalwork, knobs, finished silver trim front panel, etc. etc.

TOTAL COST OF COMPLETE COMPONENTS ONLY £27.85—POST FREE!

All components are available separately, to enable the constructor to obtain just what parts he requires at any one time. Please send S.A.E. for free list.

SPECIAL CONTEMPORARY STYLE SLIMLINE METAL CASE WITH WOODEN END CHEEKS IS NOW AVAILABLE FOR THIS AMPLIFIER—DETAILS INCLUDED WITH ALL LISTS, OR AVAILABLE ON RECEIPT OF S.A.E.

P. E. 'GEMINI' STEREO AMPLIFIER

30 Watts (R.M.S.) per Channel into 8 Ohms !!
Total Harmonic Distortion 0.02% !!
Frequency Response (-3 dB) 20Hz-100kHz !!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but it is well within the capabilities of the ambitious constructor.

We can now supply a reprint of the articles in booklet form, price 55p plus 4p postage, with free complete component price list.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.


All parts available separately.



ELECTRO SPARES

21 BROOKSIDE BAR,
CHESTERFIELD, DERBYSHIRE.
QUALITY • SERVICE • VALUE

RAYMER MICROCHIP RE500

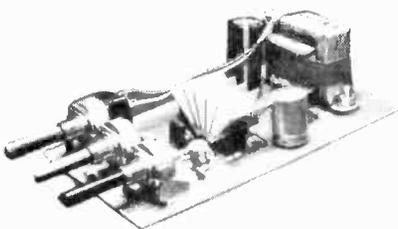

This advanced high-fidelity integrated amplifier is completely self-contained and only requires connecting to mains, speaker and input.

Ideally suited for:
MONO RECORD PLAYERS
MONO CONVERSION TO STEREO
STEREO CONVERSION TO QUADRAPHONIC (x 2 Microchip + Decoder)
T.V. AMPLIFIER
TAPE AMPLIFIER
P.A. INSTALLATIONS
AUDIO ALARM ETC.

SPECIFICATIONS
OUTPUT 5 watt RMS (10w peak)
FREQUENCY RESPONSE 10Hz to 50kHz ± 3db
TOTAL HARMONIC DISTORTION less than 1%
LOAD IMPEDANCE 4 to 16 ohms
INPUT IMPEDANCE 100k ohm Nominal
POWER GAIN 40db Typical
SIZE 140 x 80 x 45mm

With free instruction sheet.
PRICE £6.93 (inc. VAT) plus 25p p. & p.
Guaranteed 12 months against failure in normal use.

TRADE ENQUIRIES WELCOMED

NAME
ADDRESS
.....
Please send
.....
I enclose P.O./Cheque/Money Order
RAYMER ELECTRONICS LTD, STANLEY RD. CAMBRIDGE CB5 8LB
Reg. Bus. 1031205



COMMERCIAL RADIO

by CHARLES MOLLOY

COMMERCIAL radio in the UK has come a step nearer with the start of medium wave tests in the London area by the Independent Broadcasting Authority. Kevin Peel (Hornchurch Essex) has heard the IBA on 557kHz with transmissions of music and announcements stating that the tests were being made by the IBA for an indefinite time. The choice of frequency is a surprise as the two IBA London stations are expected to be on 1151kHz (London News) and 1546kHz (London Entertainment). The first regular broadcasts from the IBA are scheduled to start this year with the opening of the London stations to be followed in 1974 by others in the provinces.

Harold Emblem (Mirfield, Yorkshire) has logged a number of medium wave stations in the Persian Gulf area between 0230hrs and 0300hrs GMT. He reports Kuwait on 539kHz; Tabriz, Iran on 645kHz; Bagdad 760kHz; 'The Voice of the Arab Emirates' Dubai 1250kHz with an Arabic religious programme followed by pop music at 0300hrs; Teheran 1325kHz; Kuwait 1345kHz. Harold mentions that Kuwait

539kHz can be heard during the evening under Budapest, which uses the same frequency. Bagdad on 760kHz is also audible in the evening.

Commercial radio is well established in Spain where several chains of low power locals operate alongside the government owned Radio Nacional Espana networks. The commercial stations are allocated call signs and about 150 of these outlets can be found all over the band. Those most frequently heard in the UK are EAJ5 Radio Sevilla on 809kHz; EAJ1 Radio Barcelona on 827kHz; EAJ2 Radio Espana (Madrid) 917kHz; EAJ29 Radio Intercontinental 953kHz; EAJ8 R. San Sebastian 1025kHz; EFE14 La Voz de Madrid 1097kHz; EAJ15 Radio Reloj (Barcelona) 1124kHz; EFJ43 Radio Juventud Bilbao 1133kHz; ECS11 Radio Centro Madrid 1385kHz; EAJ20 Radio Sabadell 1475kHz; EFE25 La Voz de Calabria 1570kHz. The common channels 1106kHz, 1133kHz, 1394kHz, 1412kHz, 1430kHz, 1475kHz, 1502kHz, 1520kHz and 1570kHz are crowded with stations. They sign-off for the night from 2300hrs GMT onwards and at this time the DXer can hear one station after another dominate a channel only to close down and leave the frequency free for a weaker occupant. Many a rare catch can be had at this time.

L. J. Hook asks for information about the MW Command receiver. Also known as the BC946 it was part of the ARC5 aircraft communications equipment used in the last war. It performs very well on the medium waves but it does require some modification as it was designed to work from a 28 volt aircraft supply.

IBA ON VHF

by SIMON DAVID

THIS new v.h.f. section will be a regular feature giving news and views on transmissions usually found on the 88 to 108MHz dial, but may be extended to include related topics. VHF is generally taken to include transmissions between 30 and 300-MHz, i.e. below 10 metres, but since this area is also covered in David Gibson's Short Wave column, this section has been specially started to provide some information more appropriate to broadcasting.

Since f.m. broadcasts began in the U.K. on a regular basis, it has been continually predicted that the medium wave band was due for banishment. This has not come about however and the medium wave is in fact still being exploited. What is expected is that the new Independent Broadcasting Authority Stations will use the upper reaches of the f.m. dial for stereo programmes, but will not necessarily use the same transmitters as the BBC. Receivers within close proximity of a BBC transmitter and collecting signals of around 100µV may find that they will be able to pick up a 20mV signal from the local IBA station.

One of the main headaches is expected to come from cross modulation effects due to emergency services being tuned in close to the commercial channels. This will undoubtedly result in a number of semi-redundant old tuners, although there is no fear of upsetting their present usefulness for BBC programmes. Whether politics come into this we are not too sure, but it is strange how the commercial side of broadcasting frequently has to accept second rate operational conditions.

In order to help find space for the new IBA com-

mercial radio stations, the BBC will be nudging its local stations along the v.h.f. tuning scale a little, changing the operating frequencies of Radios London, Medway, Oxford, Brighton, Bristol, Leicester, Nottingham, Stoke, Humberside, and Sheffield. These adjustments are expected later this year when the appropriate details should be given in the local Press and *Radio Times*.

The new station at Carlisle is still expected to "appear" on 95.6MHz, but it looks as if Swaledale will be "lost" for want of a suitable site for a relay station.

Although some way off yet, it is not a bad idea to look into the needs and possibilities of incorporating very sharp rejection filters to suppress adjacent local transmitters. The use of a field effect transistor at the front end will also help to reduce cross modulation effects. Several tuners have automatic gain control and since this would not be helpful in this situation it is worth incorporating a switch so that it can be cut out of service as necessary.

Furthermore, the mixer stage design becomes critical and the noise generated here must be at a very low level. This will mean that the r.f. circuit will not have such a high gain as in the past but this can be made up by increasing the gain through the i.f. stages.

The use of phase-lock integrated decoders will provide tuners with lower distortion and better frequency response, both of which have become necessary for good stereo reception.

We shall always be pleased to hear of readers' experiences of v.h.f. reception, especially those who listen in to continental stations. Please be brief and confine your letters to stations received, aerial and tuner used and the effect of interfering transmissions.



SHORT WAVES

by DAVID GIBSON, G3JDG

THIS month's postbag has been conspicuous by the very marked absence of 14MHz logs. It seems that the twenty-metre-only addicts are as dead as their band these days. Meanwhile, back at the eighty-metre ranch it's been a right merry r.f. square dance. The amount of DX on eighty has been quite remarkable with west coast W stations romping in at times. In fact, stations further down the globe have also put in an almost regular appearance on this band; Mexico, Brazil and Argentine, etc. Some real goodies have put in an appearance for the persistent enthusiast. Callsigns like DU1EJ and VS6DO have shown that your receiver dial need not read above 4MHz in order to log some rewarding DX signals both on phone and c.w.

News from VE land. An enthusiastic band of Canadian Amateurs are building a large ocean-going trimaran. Their object is to put the 40 most "wanted" countries on the air. I will pass on information about their ports of call as soon as I hear.

Great hopes that an Amateur station will be allowed on Clipperton Island. Callsign to listen for will probably be FO8C. Anyone heard the station reported to be located in the Spanish Sahara yet?

Time to pass on to some queries, curses and comments. Michael Green (Cheshire) uses a UR1A. The drawing of his antenna system bears a harrowing resemblance to the national grid. (Bet he's the only s.w.l who tunes topband in rubber gloves and wellies). Michael queries queer callsigns heard in the wee small hours on 80 metres s.s.b.; Rudolph, Scrooge, Virgin Mary and Snowman. Michael's problem is simply, "How do I QSL them?" (Perhaps the nearest Asylum is licensed?).

Letter from a long way off bears the signature of Lindsay Pennell and the post mark Hong Kong (Ah, those were the days, Chow Mein butties and cocoa on the Kowloon ferry). Lindsay wonders why so few G s.w.l.s hear the Hong Kong throng signing VS6. There are some 40 licensed Amateurs many of them being very active into Europe. Confess now, you're all logging VS6's and not telling your Auntie David.

Simon Baines (Hitchin) reports a number of W stations including W5NMA, heard on forty metres s.s.b. Gear is a five-valve receiver, transistor b.f.o. and 30ft of wire end fed.

M. Harrison (Derby) sends in a log of numerous G stations heard on topband. Incidentally, a good non-G to listen for on 1.8MHz is WIBB/1 whose stalwart support and interest in topband is well known all over the world. It is interesting to note that PY1DVG has been heard on 1.8MHz.

Kevin Smith is thirteenth summers old and lives in Brighton. (Wish I was and did.) Whereas most boys of 13 are the proud possessors of pieces of string and marbles, Kevin settles for a CR100 and a 215ft long wire end fed. His best areas on topband were: DL8PC, GI3GRD, GM4BBL, GW3ZQN all on s.s.b., and OK1ATP on c.w. His log for 28MHz reads: CN8BF, CN8CF, CR4BS, CR7AF, CR7IZ, CT2AT, ET3USF, ET3USP, KV4CF, ST2SA, VP2LAF, WB4WOI/P, ZE4JW, ZS6AD, Z4ME, 6W8DL, 7Q7RM, 9G1HE, 9H4D, 9J2AY, 9J2DT all s.s.b.

Best times for listening on eighty metres are from midnight to around 0300 hours according to Alan Smith (Lancs). He bemoans the Lids who test incessantly by blowing into the mike (it's unhygienic but they can't touch you for it). Alan has a JR31, 60ft end fed and an a.t.u. Heard on eighty: EP2TW, K1UAT, K2LQA, KP4AN, KV4CI, PY4BTK, VE1ADV, VP2LI, VP7ND, W1GEY, W2BXA, W3WGH, W4AG, ZB2CF, ZS1MH, ZS3GH, 9H1CW, 9V1RE. A cheap day excursion to 14MHz s.s.b. raised: EP2ES, HZ1AB, KG6JBE, KL7HFA, KX6BQ, LUIDAC, MP4TEE, VE1ASJ, VE3MO, VK3ADR, YK1AA, ZL1KN, ZL1WE, ZL2AVE, ZL2BQC, ZL3QN.

David Sharred (Birmingham) had a quick tour of eighty metres. Main listening times were "after my paper-round", and the gear is a CR150/2 with a V-shaped antenna (60ft each leg). Goodies bagged on 3.5MHz: CN8BF, JY1, K5PFL, KV4AM, OA6NCT, P11ROS, VE3CDP/W9, W2HCW, W4MYA, W9QLD, WA5JMK, WB4MCI/P4, ZK2BO, ZL4BT, ZL4KF, ZS3GH, 3A2EG, 5U7AX. On twenty metres David's best were VK5RN and VK6XO.

Where are all you v.h.f. types hiding? No logs at all for lonely little 70MHz and only one for 144MHz. Michael Prescott (Lancs.) uses a Roamer 10 receiver and a two metre dipole. He reports signals from the following: G3AHD/A, G3PVC, G3VIM, G3XIM, G3VME, G8EYO/A, G8ESU, G8GYS, G8VLE and G8XDL. Well done Michael, you've kept the v.h.f. flag flying—just.

For the contest and Rally enthusiasts, April is a busy, busy month. Jottings from my Events diary read: April 1, White Rose Mobile Rally at Leeds; 1, WAB phone contest (l.f.); 8, WAB c.w. l.f. contest; 8, eighty metre QRP (low power) contest; 15, four metre portable contest (no excuse now for not sending in a log); 21-22, Bermuda contest (phone); 29, Rugby DF qualifying round; May 5-6, two metre and 70cm open contest (another chance for the v.h.f. s.w.l.s to shine); 5-6, Bermuda contest (c.w.); 6, Spalding Tulip Time Mobile Rally.

BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

Medium Waves Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.


VHF Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4 4AD.

AMATEUR BANDS

Short Wave/VHF

Logs in alphabetical order please by 15th of the month to David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.

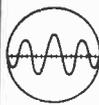MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.



TUAC

TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD.
163 MITCHAM ROAD, LONDON SW17 9PQ
01-672 3137/9080

ARE PROUD TO ANNOUNCE AN ENTIRELY NEW RANGE OF PROFESSIONAL STANDARD DISCOTHEQUE EQUIPMENT AND AUDIO MODULES

TUAC DISCOTHEQUE MIXER FEATURING AUTO FADE



£20.00 Complete PSU £2.95
p. & p. 50p. p. & p. 25p.

FEATURES: Mic input with volume and tone control. Two deck inputs for ceramic/crystal P.U.'s. Tape input with volume control. Master volume, treble and bass controls. Automatic mic override, with adjustable fade depth; fades the music down when you make your announcements, then the music automatically returns to its original level. Automatic/manual override switch. Full headphone facilities. Panel mounting, satin enamel finish. 40V D.C. operation. IV low impedance output.


CONTROLS: Mic vol, mic tone. Override depth. Tape vol. Left deck fader, right deck fader. Deck vol, treble, bass. Master vol. Headphone vol, left/right fader. Auto/manual override switch. Power on/off switch.

TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last



£49.50 p. & p. £1.00
CELESTION, GOODMAN'S & FANE speakers, condenser and dynamic mics, mic stands, headphones—all readily available.

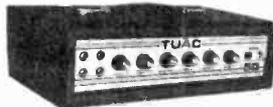100 Watt RMS Sine Wave Slave Amplifier. Suitable for use with above mixer. Slave input, gain control, slave output, Hi/Lo sensitivity switch. Rugged circuit. Rugged leather-cloth covered case. Short and open circuit protection. Over 200 watts peak output. 8Ω output impedance. FULLY FUSED speakers.



£41.25 p. & p. £1.00
100 watt version £60.50 p. & p. £1.00.

50 Watt RMS Sine Wave General Purpose Amplifier. Suitable for Disco, PA, Guitar. 4 inputs, 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leather-cloth covered case, short and open circuit protection. Tone control specification as VA08 pre-amp. FULLY FUSED

TUAC MICROPHONE MIXERS—battery operated—all steel construction



£14.12 p. & p. 40p

FEATURES: 4 inputs with adjustable sensitivity, volume and extra wide range tone control on each input. 2 outputs, stereo or mono use. Max. output 2V. Low noise silicon transistor line up. 18V. D.C. operation.



£8.25 p. & p. 35p.

FEATURES: 2 inputs with adjustable sensitivity, volume and extra wide range tone control on each input. Single output. Mono use max. output 2V. Low noise silicon transistor line up. 18V. D.C. operation.


TUAC COMBO AMP.



£60.00 complete.

25 Watt RMS Sine Wave Ideal for small groups, clubs and studio use. 4 inputs, 2 vol. controls. Master vol, treble, middle and bass controls. Heavy duty Celestion 12" speaker. Available May

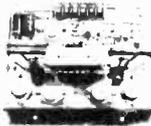TUAC POWER AMPLIFIER MODULES—TP 100W now with 4 RCA 150 watt output transistors TP 50W now with 2 RCA 115 watt output transistors



TP100W T.H.D. at full power 2"

All output power ratings are R.M.S. continuous sine wave using specified supply. Each circuit incorporates a robust driver transformer stage with thermal overload protection and is short and open circuit proof. Full power response 10Hz-20KHz ±2dB. Input sensitivity 30mV into 3KΩ. Hum and noise better than -70dB. Output impedance 8Ω. Constructed on glass fibre P.C. board. O/P matching transformer 4-8-16-60-100Ω £8.00 p. & p. 40p. An additional Heatsink is required. An aluminium chassis is ideal, just bolt the module Heatsink on.

TP100W 100 watts RMS output into 8Ω £15.18 p. & p. 45p.
PS100 Power supply and transformer £9.10 p. & p. 50p.
PS100/100 Supply for two TP100W modules £18.00 p. & p. 65p.
TP50W 50 watts RMS output into 8-15Ω £10.36 p. & p. 40p.
PS50 Power supply and transformer £6.86 p. & p. 50p.
PS50/50 Supply for two TP50W modules £11.95 p. & p. 65p.
Two TP100W modules can be wired in a bridge output circuit to give a single 200W R.M.S. output into 8Ω using PS100/100 supply. Use phase splitter PS201 to drive modules.

TUAC PRE-AMPLIFIER MODULES 30mV O/P into 3K.

40V D.C. operation except where stated.
VA06 Suitable crystal/ceramic P.U., Mic., guitar, radio tuner, vol., treble & bass controls. Sensitivity 8mV for 30mV O/P Treble +22 -15dB @ 12KHz. Bass ±18dB @ 40Hz.

VA08 As VA06, but with extra middle control. Treble +28dB @ 18KHz. Middle +20 -15dB @ 4KHz. Bass +20 -10dB @ 40Hz. Sensitivity 4mV.

SVA01 As VA08 but stereo with bal. control.

MVA01 Suitable for disco, mic., tape input. 2 inputs, with Vol. & tone control on each input. Sensitivity 2mV. +25dB @ 12KHz to +20dB @ 40Hz.

MEVA01 Magnetic Cartridge equalisation. Connects to input of VA06 or VA08 with volume control.

SIPAM Master volume and presence control. High treble boost of +15dB @ 15KHz.

EFVA01 Increases the output of any of the above to 1V. RMS. Low impedance emitter follower output.

NEW RANGE

Includes 3 guitar effects units!

HPA01 Headphone Amplifier. 8-15Ω 200mV output. Left right fader. Volume control. 200mV 1MΩ I/P. Adjustable sensitivity.

AMF01 Auto Fade Unit. Feed deck and Mic. Pre-amps in, output to power module. Fade depth and Master Vol. Control. 30mV operating Level. Spec. as disco mixer.

PS201 Phase Splitter unit to drive two TP100W modules in bridge O/P.

WAA01 WAA-WAA Module. This is an exceptional unit, producing a superb WAA-WAA for guitars. Pedal soon available. 18V D.C. operation.

FUZ01 Fuzz Module. Professional standard Volume, tone & fuzz sustain controls. Case soon available. 9V D.C. operation.

FXD01 Frequency Doubler Module. Doubles the frequency of any sinusoidal wave, such as that obtained from the WAA-WAA module. 9V D.C. operation.

TUAC LIGHT MODULATORS



3 Channel SILMB illus.

Constructed on glass fibre P.C. board, individually tested.

Three channel light modulator will control three separate sets of lights, up to 1000 watts each set. One channel responds to the bass, one to the middle, and one to the high frequencies. Input sensitivity only 0.5 watt! Three individual controls allow for adjustment of the three channels, and a master sensitivity control allows for input levels up to 100 watts to be safely accommodated. Full interference suppression. Full wave control. Isolating input transformer does not affect Amplifier operation. Fully Fused.

SILMB 3 Channel £17.45 p. & p. 35p.

Single Channel version, SILMB Increased capacity of 1800 watts. Sensitivity control. Isolating input transformer does not affect amplifier operation.

SILMB 1 Channel £6.47 p. & p. 25p.


PRE-AMP POWER SUPPLY UNIT

For use with all pre-amp modules and discotheque mixer. Not necessary if PS100 or PS50 supply is used. Output 40V D.C. 250mA. Mains fuse also incorporated. £2.95 p. & p. 25p.

All TUAC Modules are ready assembled on glass fibre P.C. board and are individually tested.

POSTAGE AND PACKING 20p EA. ALL PRICES ARE INCLUSIVE OF V.A.T.

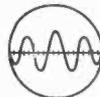ALL TUAC KITS ARE SUPPLIED COMPLETE WITH EASY TO FOLLOW WIRING INSTRUCTIONS AND CIRCUIT DIAGRAM. CALL FOR A DEMONSTRATION OF ANY OF THE ABOVE UNITS. SPEAKERS AND CABINETS ALSO SUPPLIED.



TUAC

LARGE S.A.E. WITH ALL ENQUIRIES PLEASE.

OUR TECHNICAL STAFF WILL BE PLEASSED TO ADVISE YOU ON ANY PROBLEM. ALL TUAC EQUIPMENT CARRIES A 12 MONTH GUARANTEE. TRADE AND EXPORT ENQUIRIES WELCOME.

VALVES		All prices in pounds and new price	
1BA6	25 6J6	20 7C5	£1-18
1BE6	30 6J7M	45 7C6	75
1BH6	75 6J7G	30 7D5	60
1A7GT	45 6B36	50 6J7GT	45
1D5	50 6K6QT	45 6K6GT	60
1H5	50 6BR7	90 6K7M	60
1N6GT	55 6BR8	70 6K7G	35
1R5	40 6B7	£1-30 6K7GT	35
1B4	30 6B6W	85 6K8M	60
1B5	30 6B7	80 6K8G	40
1T4	30 6C4	33 6K8GT	50
3A4	40 6C5G	35 6K25	75
3Q4	50 6C6	25 6L18	50
3Q5	50 6C6G	£1-25 6L18	45
3B4	25 6C6H	60 6Q7G	40
3V4	45 6C6W4	65 6Q7GT	43
6R4G	45 6E5	£1-00 6S7M	40
5U4G	85 6E5	£1-00 6S7M	75
5V4G	45 6F1	70 6S7M	40
5Y3GT	40 6F6G	90 6S7M	40
5Z4G	40 6F6G	35 6S7GT	30
6J30L2	80 6F8	50 6S7GT	40
6A7	75 6F11	40 6S7GT	35
6A8G	40 6F12	45 6S7GT	35
6A8S	35 6F23	85 6S7GT	35
6AM5	35 6F24	75 6S7GT	35
6AM6	35 6F25	£1-00 6S7GT	35
6AQ5	38 6F28	65 6V6G	60
6A8G	35 6G6	35 6X4	35
6AT6	35 6H6	23 6X5G	40
6AU6	25 6J5	35 6X5GT	40
6B4G	£1-00 6J5G	20 7B6	70
6B8G	20 6J6GT	30 7B7	50
128R7	40 37	40 DAF91	80
14E7	50 42	50 DAF96	45
19AQ5	50 50R5	50 EC90	£1-35
20D1	50 50R5	50 EOC31	35
20P2	70 50R5	50 DF33	55
20P4	£1-10 75	50 DF33	45
20P5	£1-10 75	50 DF33	45
20P6	£1-10 75	50 DF33	45
20P100	£1-10 75	50 DF33	45

Transistors		Integrated Circuits	
1N914	07 2N2219	20 BY100	15 NKT713
1S113	25 2N2369A	20 BZY88	15 OA70
1B202	23 2N2444	£1-91 AD149	50 GET102
2G302	22 2N2646	45 AF115	25 GJ7M
2G371	22 2N2904	20 AF117	25 KJ300A
2N404	20 2N2926	10 ASY26	25 MJE520
2N697	15 2N3055	75 BC107	10 MJE2955
2N706	10 2N3702	10 BC108	10
2N1132	25 2N3819	35 BC109	10
2N1305	22 2N4147	75 BC169C	10
2N1560	60 AC126	20 BFY50	22 NKT223
2N2218	20 AC127	25 BFY51	20 NKT251
AC128	20	BY100	15
ACY20	20	BZY88	15
ACY39	50	CRS1-40	47
AD140	50	DP003	15
AD149	50	GET102	30
AD151	37	GT0882	25
AF115	25	GJ7M	37
AF117	20	KJ300A	25
AS226	25	MJE520	87
AS227	25	MJE520	87
AS228	25	MJE520	87
AS300	25	MJE520	87

RST VALVE MAIL ORDER CO. TELEX 946708 Open to callers 9am-5pm Mon-Sat. Closed Saturday from 1pm-3pm. From 1st April 1973 all orders subject to V.A.T. at applicable rate. This must be added to your order including postage.

16a WELLFIELD ROAD, LONDON SW16 2BS Send large S.A.E. for list. Phone 677 2424 (4 lines) Express postage 1p per transistor, over 10 post free. Integrated Circuits & Valves 5p, plus 1p for each additional item, over £5-00 post free.

FREE!

FULLY ILLUSTRATED CATALOGUE

AMAZING QUALITY
Our superb catalogue is printed in easily read type. It has dozens of clear pictures and illustrations of thousands of the kinds of components you use.

SPEEDY SERVICE
Write now and we will be delighted to forward a copy to you by return of post.

PHONE ANY TIME
You can phone for your free catalogue whenever it suits you. Out of office hours leave your name and address on our answering machine.

£1 FREE
When you receive your catalogue you will find out how you can obtain one pounds worth of goods absolutely free!

PLUS
Free post and packing in U.K.
Every item sold guaranteed brand new and marked by the manufacturer.

Phone 037 42 79033 or Write:—
MAPLIN ELECTRONIC SUPPLIES
P.O. BOX No. 3
RAYLEIGH
ESSEX
SS6 8LR

S-DECS AND T-DECS
S-DECS £1.44
T-DECS £2.88
µ-DEC A £3.00
16 dit IC carriers £1.20

IC RADIO CHIP TBA651
As featured in July Practical Wireless IC of the month feature. Contains RF Amp, oscillator, mixer, IF Amps, detector, voltage stabilizer and wide range AGC circuitry. With data £2-10

SINCLAIR EQUIPMENT
IC12 £2.00
Z50 £4.25
PZ5 £3.97
Z30 £3.50
Project 60 tuner £16-80
AFU £4.50
stereo 60 £7-80
Sinclair Executive Calculator £55 00
New Sinclair Digital Multimeter £44-00
System 2000 Amplifier £22-00

DELUXE KIT FOR THE IC12
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £14.5. Stereo version with balance control £33-00

POWER UNITS FOR THE IC12
A set of components to construct a 23V 0.5 Amp power supply £2-27. Also suitable Sinclair PZ5 fully constructed £3-97.

PREAMPLIFIER KITS FOR THE IC12
Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1-20. Stereo model £2-20. Type 2 for ceramic or crystal pickups. Mono 6p. Stereo £1-20.

PROJECT 60 KIT £2-50
Our extremely popular kit contains the extra capacitors. DIN plugs and sockets, cables and fuse holder needed to complete Project 60.

SWANLEY ELECTRONICS
32 Goldsel Road, Swanley, Kent
Mail order only. Postage 10p per item. Lists 10p
*** Add 10% extra to all prices for V.A.T. ***
Official credit orders from schools etc. welcome.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER
Complete kit—price £3-80 (post & packing 20p.). Customer writes: "I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. **EXCITING COMPETITION for Short-Wave listeners.** Send stamped envelope for details.

"I.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

ALTHOUGH the prices of unijunctions have not taken the normal course of falling in cost, they are cheap enough to be used in one of our circuits.

The unijunction transistor bears little resemblance to the conventional transistor; it doesn't amplify, has only limited use and doesn't even have a collector. The connections are to an emitter, base 1 and base 2. In fact the best thing that the unijunction is good for is as a relaxation oscillator, as in Fig. 1.

Operation

When a voltage is applied to the circuit, the capacitor C1 starts to charge up through R1 and VR1. Initially the emitter of Tr1 will be at negative potential but as the capacitor charges, the voltage at this point rises. When it reaches a certain point, b₁ and b₂ are virtually short circuited and current will pass through R2, R3 and Tr1. At the same time C1 will be discharged through R3 and the device will become open circuit again. The same process will start all over again so that a series of pulses appears across R3 via C2. Since the output will be a series of pulses whose rise and fall times are very rapid, only a low value capacitor is necessary despite the low value of R3. The output will be in the form of a positive-going pulse; if a negative-going pulse is required this capacitor should be connected to b₂. A sawtooth waveform is available from the emitter but it should only be connected to a high impedance load otherwise the operation of the relaxation oscillator will be affected.

The frequency of the pulses depends on the relationship of the resistance made up from VR1 and R1 and the capacitor C1. Resistor R1 limits the current

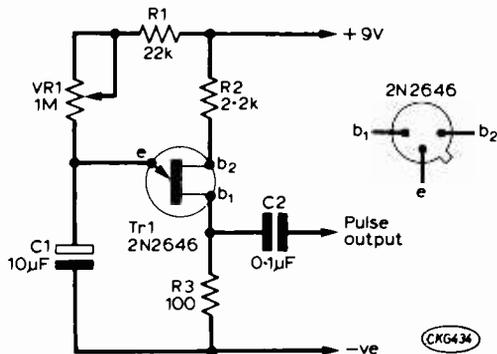


Fig. 1: Circuit and suggested valves for the pulse generator.

No. 48 PULSE GENERATOR

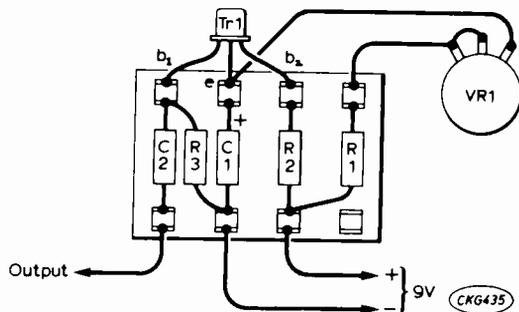


Fig. 2: Practical layout of components on a piece of tagboard.

through the emitter so that it cannot be connected directly to the positive line; this would cause damage to the device.

Experimenting

There is room for experiment here; C1 can be altered in value from 500µF down to 0.01µF. The high value will produce pulses with very long intervals; it is difficult to say how long as the natural leakage through the electrolytic will play a major role. If a low leakage device is used the time interval can be a minute or more. Using the low value capacitors the pulses could extend to ultrasonic frequencies.

★ components list

R1	22kΩ ½W, 5 per cent	1p
R2	2.2kΩ	1p
R3	100Ω	1p
VR1	1MΩ linear pot	12p
C1	10µF 12V	5p
C2	0.1µF mylar, etc.	4p
Tr1	2N2646	40p
		64p

Prices are those recently advertised and may have changed. No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

Modifications

The output can be taken to an amplifier to act as a metronome. In fact if only a low level output is required, a high impedance loudspeaker (50Ω to 80Ω) can take the place of R3; in this case of course C2 will not be needed.

A suggested layout is shown in Fig. 2 making use of a small piece of tag board; this is far from critical and almost any layout may be used.

HOTLINES

ON RECENT DEVELOPMENTS

Do you ever have that feeling that you are being watched? Well, maybe you are at that and have been for the past 13,000 years. A theory has been put forward that we are getting intelligent messages from space. To be more precise, from an interstellar "thingy" which is buzzing round the earth—probably in an orbit which is similar to that of the moon. (Good gracious, Holmes).

LONG WAY ROUND

Before you rush out and wave your hanky at the sky, hear what the experts have done about it. It is all tied in with things called long-delayed echoes. These were observed as far back as 1928. A transmitter using 15kW on 9550kHz was radiating its Morse signal which in turn was being received by a number of receiving stations. A Morse signal was being sent and received almost instantaneously. Now a signal can go two ways—direct to the receiver by the shortest route and also in the opposite direction. This latter signal can quite easily travel right round the world before it is received by our receiver. Thus two signals are heard; the direct one, and the one which goes the "long" way round. The latter takes about one seventh of a second and is heard as an "echo" of the direct signal which, because it travels direct (therefore less distance) arrives almost instantaneously i.e., with negligible delay.

So far so good. But imagine the effect on the minds of the listeners when other echoes were heard—not delayed by one seventh of a second but at various intervals varying from about three seconds to 15 seconds! These long-delayed echoes were also noticed independently at other times, on other dates, by different receiving stations listening to a different transmitter and on a different frequency.

Then, someone plotted a graph of one of these echo sequences and another piece of the intriguing jigsaw came to light. The plotted points bore a striking likeness to the constellation Bootis. Other echo sequences were plotted and produced patterns which were clearly

identifiable with other constellations.

The hypothesis has been put that the long-delayed echoes are being returned to Earth from a space probe; a probe which arrived from the Bootis constellation 13,000 years ago. Moreover, the probe was sent to search for evidence of intelligent life in the form of radio transmissions.

People who are in doubt about the validity of all this should bear in mind that all the evidence so far corroborates this hypothesis. So closely, in fact, that EMI engineers are to set up a high-power transmitter and high gain antenna (probably around 144MHz) in order to put the hypothesis to the test. Are they just being starry-eyed? I do not think so.

ERNIE

Apart from driving the fastest milk cart in the west, Ernie has achieved fame in other ways. For example, he painstakingly avoids selecting your premium bond number every month without a single complaint or grumble. To date, his selections have paid happy punters prizes amounting to some £350 million—none of which has yet reached your scribe!

So it is with ageing joy and renewed hope that I report a new Ernie who will produce the monthly list of prize-winners in under three hours. The old Ernie used to take ten days to complete the same task.

Before we non-winners get too elated, let us examine what we are up against. Just what (or who) is Ernie and how does he choose winners?

First, Ernie comes from Ernie Harrison, Managing Director of Rascal, whose idea it was. Ernie himself (the number picker) has been described as the most advanced electronic system in the world for generating numbers in a completely random fashion. How does he fit go about the task?

The first job is to monitor the noise level of a pair of zener diodes (actually, a pair for each digit). Each "pair" noise is amplified and then compared with a reference voltage. Because of the nature of noise there are peaks, and each time one of these exceeds the set reference level it is counted and used in the production of a digit.

Once a complete digit is generated it is safely entrusted to the memory of a computer. Here, it is checked to see if it is eligible. If it is, then it will be stored in the computer's memory, if it is not, it will be discarded.

Ernie presses on until the memory or store has 60 numbers in its care. These are then "written" onto magnetic tape and this is then "played" to another computer for checking and finally linking the lucky numbers to the bondholders' names and addresses.

I am already making the most careful measurement of the noise generated by a pair of zener diodes—well, you never know.

TRANSISTORISED TED?

How about an electronic government, a big computer tucked away beneath Parliament in a Guy Fawkes-proof vault? Maybe not yet, but in America the computer has managed to secure itself a small governmental foothold.

The House of Representatives is to vote by computer. Problem has been the 435-name list of members and the time wasted in correcting attendance errors. Other little hitches like finding a vote recorded from a member who wasn't even there were also proving annoying. The mind boggles.

The new system means that each member has a small plastic "card". He can use this card to vote at any one of some 50 stations located at various points about the House. Behind the Speaker's seat is a scoreboard which gives the latest updated score on how the voting is going. Electronic voting is reckoned to save at least 50 per cent of the time previously taken for such a task. The computer will also give written records of votes simultaneously plus an instant breakdown of these into States or Parties as required.

Look out members of Parliament—you might be replaced by a pair of zener diodes one day—they're cheaper, smaller and generate less noise!

Ginsberg

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

ONLY 95p
POST & PACKING 35p EACH
TELEPHONE DIALS
Standard Post Office type.
Guaranteed in working order.

ONLY 25p
POST & PACKING 15p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H28	20	OC2001/2/3 PNP Silicon uncodded TO-5 can	50p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types.	50p
H39	10	Integrated Circuits, 6 Gates B7C 962, 4 Flip Flops B7C 945	50p
H40	20	BFYS02, 2N696, 2N1613 NPN Silicon uncodded TO-5	50p
H41	2	Sil Power transistors comp pair BD131/132	50p

UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN14 and IN16 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BS795A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW, Zener Diodes OC-7 Mix. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

MAKE A REV COUNTER FOR YOUR CAR

The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OVER 1,000,000 TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BC170 etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 50p for £3, 1,000 for £5, 10,000 for £40 P. & P. 10p/1,000.

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.

TYPE "B" PNP Silicon, plastic encapsulation.

TYPE "E" PNP Germanium AF or RF.

TYPE "G" NPN Silicon plastic encapsulation.

TYPE "G" NPN silicon similar ZTX 300 range

TYPE "H" PNP silicon similar ZTX 500 range

8 RELAYS FOR VARIOUS TYPES £1 P & P 25p

VALUE ADDED TO YOU

ON ORDERS OF £4 OR OVER

SEE BELOW

Please read very carefully. We will give a discount to customers who send in an order for £4 or over. This discount will be equal to the V.A.T. rate current at this time. If your order does amount to £4 or over, all you need to send is the total cost of goods and postage as stated in this advertisement. No addition for V.A.T. is needed.

V.A.T. for orders under £4: If the total cost of goods plus postage and packing is less than £4, kindly add 10% (10p in the £) to your remittance. Incorrect amounts will delay your order.



A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

100,000 Plastic Power Transistors in stock, more on way!

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms. Range 1. VCE. Min 15. HFE Min 15.

40 Watt 1-12 13-25 26-50

90 Watt 20p 18p 16p

Range 2. VCE. Min 40. HFE Min 40.

40 Watt 1-12 13-25 26-50

90 Watt 30p 28p 26p

Complementary pairs matched for gain at 3 amps. 10p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile 16 pin type at 18p each. } type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes; 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.

The Hife Radio Valve & Transistor Data Book 9th Edition; 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Postage and Packing 21p.

Send for lists of publications

N.B. Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF
TELEPHONE: SOUTHEND (0702) 46344

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	33p
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	36p
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	36p
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	36p
Rod Aerial	RA2W		72p
Driver Transformer	LFD4/1		58p
Output Transformer	OPT1		58p
Printed Circuit	PCA1		58p

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	39p
T41/2E	2nd I.F. Transformer	39p
T41/3T	3rd I.F. Transformer	57p
T41/3T	B.F.O. Coil	57p

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

WEYRAD (ELECTRONICS) LIMITED
SCHOOL STREET, WEYMOUTH, DORSET

P. C. BOARDS



Reverberation Unit PCB.

FOR P.W. PROJECTS

All PCB's Fibreglass, Drilled, Roller-Tinned
Circuit and Layout Diagrams free with each PCB

REVERBERATION UNIT (Nov/Dec 1972)

PCB (2in x 11in). Specially designed to also hold Slider Pots with spacing compatible with published front panel £1.20
SET of R's, C's, S/C's, Slider Pots, Transformer £6.80

8 WATT AMPLIFIER (Nov 1972)

PCB (Mono—2in x 3in) 60p
R's, C's, Semiconductors: Stereo Set £7.70, Mono Set £3.90

PRE-AMPLIFIER (Nov 1972)

PCB (Stereo—3in x 7in) Specially designed to also hold all Pots, either rotary or slider, plus Selector Switch £1.50
R's, C's, Rotary Pots, Selector Switch, Semiconductors:
Stereo Set £5.20, Mono Set £2.50

LOUDHAILER & SIREN (Dec 1972)—PRE-AMP & SIREN GENERATOR

Set of R's, C's, Pot, Semiconductors PCB (2in x 2in) £2.20

VIBRASONIC GUITAR PRE-AMP (Sept 1970)

PCB (4in x 13in) for Mic Pre-Amp, 2-Guitar Pre-amp, Tremulant & Tone Controls, Master Volume. Specially designed to also hold Rotary or Slider Pots £2.30
Set of S/C's, R's, C's, Rotary Pots, LDR, Lamp, Coupling Transformer £7.75 Power Supply £2.80

DIGITRONIC DIGITAL CLOCK (Feb. 1973)

PCB (1in x 3in) for 6-digit read-out 60p
POSTAGE: U.K. 10p any order. OVERSEAS at cost.

P.E. DESIGNS ALSO AVAILABLE—S.A.E. FOR FREE LIST.
ALL PRICES V.A.T. EXCLUSIVE

PHONOSONICS

DEPT. PWS, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
MAIL ORDER ONLY

BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON S.W.17 01-672 3984

CARTRIDGES—Stereo Sonotone 9TA H/C Diamond £2.40, Ronette S105 Medium Output £1.40, S106 High Output £1.40, Acos GP93/1 Sapphire £1.90, GP94/1 Sapphire £2, Japanese equivalent to B.S.R. TC8s £1.75. P. & P. 7p on each.

CARTRIDGES—Mono GP91 Stereo Compatible £1.25, B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7p.

HI-FI STEREO HEADPHONES Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms, frequency range 20-20,000 Hz 6ft. cord and standard stereo plug. Only £2.57. P. & P. 27p.



STEREO HEADPHONE JUNCTION BOX
Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only £1.50. P. & P. 13p.

VYNAIR Widths from 50 to 54in., 75p yd. off roll. P. & P. 10p, 1/2 yard 40p. P. & P. 10p. Send 5p stamps for samples.

LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed—
build as you learn with
the exciting new
'Technatron' kit. No
Extras. Tools, transistors,
meter etc. All supplied
You could build a
radio in weeks.

SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV,
ELECTRONICS, C & G, TELECOMS ETC.

Dept. BPW15 Aldermaston Court, Reading RG7 4PF

Name

Address


.....

.....

..... Age CV



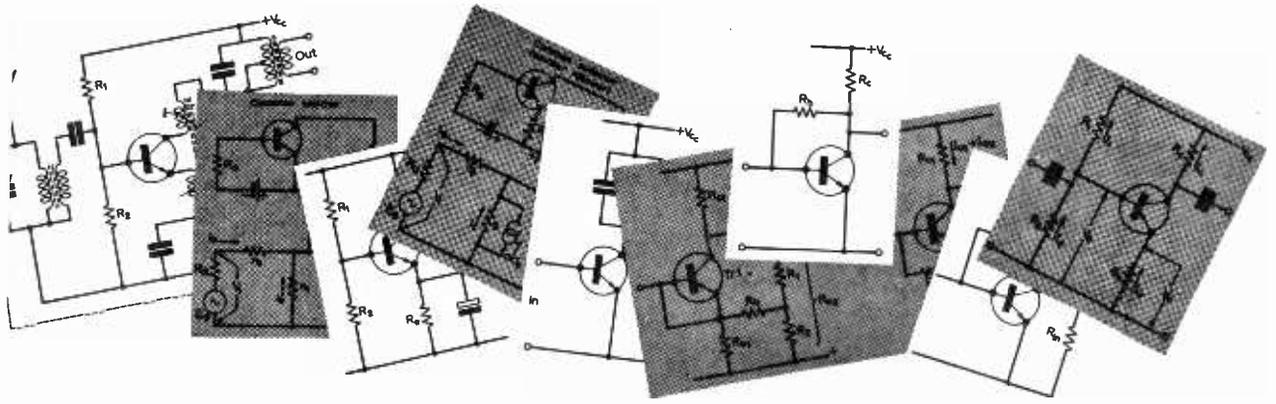BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



TRANSISTOR CIRCUITRY for beginners

PART 16

H.W. HELLYER & MICHAEL HOLLIER

Practicalities

A BC109 is chosen to give an open-loop gain of 260, with an input of about 30mV at 1kHz. We shall aim to keep this level constant for further tests. Connecting the two resistors of Fig. 76 to the input, we have the virtual earth type of circuitry. This has been discussed at some length in previous articles. It can now be simplified to the triangle of Fig. 77,

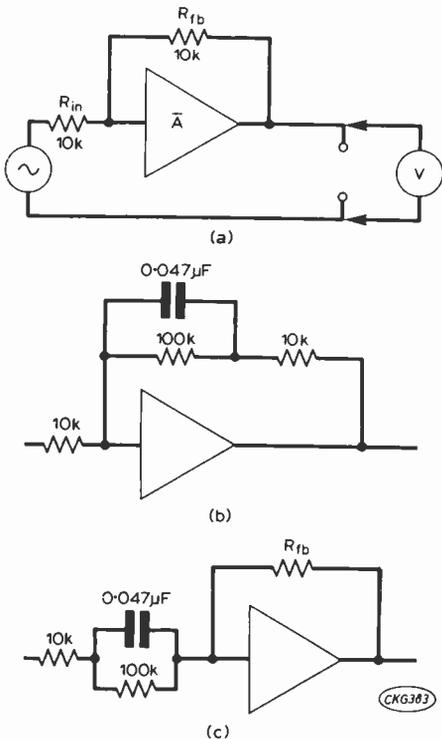


Fig. 77: (a) Simplified representation, with the symbols denoting an inverting amplifier. (b) a frequency-dependent development, and (c) the bass cut variation, with the frequency-selective portion before the feedback loop.

the input shown conventionally at the blunt end; the output at the sharp end (i.e., the 'arrow' points the way the signal is going). Fig. 77 is a simplified diagram, the letter A within its triangle denoting that it is an amplifier.

Previously you will have noted reference to an 'inverter'. By this, is meant that the input is 180° antiphase to the output. In Fig. 77, we see a bar over the A, denoting an inverter. For the benefit of old-timers like me, this can be regarded as exactly parallel to valve technology: a positive-going waveform at the grid produces a negative-going waveform at the anode.

If previous articles have been followed, it will be noted that the closed loop gain, which is the circuit gain calculated after feedback has been applied, is derived from the formula: $G_c = R_{fb}/R_{in}$.

If we now make R_{in} equal to 10kΩ and R_{fb} also 10kΩ, the closed loop gain is unity, i.e., 10/10. In practice, we shall measure 0.8 rather than 1. If, with R_{in} at 10kΩ and R_{fb} at 100kΩ, giving a theoretical gain of 10, we were again to measure, we should find the answer more like 7.7. Carrying this experiment a little further—and please do not merely take our word for this; try it and see for yourself—we find that with R_{in} at 100kΩ and feedback resistors varying between 10kΩ and 1MΩ, the closed loop gain varies between 0.1, via 0.98 (at 100kΩ) and 5.8. Which only goes to prove that the actual gain is always less than calculated, and, secondly, the lower the circuit impedance, the greater the error.

Practically, therefore, it would seem that our circuit was not the best. But, as it is typical of the majority of commercial designs, we make no apology. It has to be remembered that the tone control circuitry does not have to contribute a lot of gain. We do not normally need a gain at any frequency of more than 'times 10', plus a stage gain of around 4, and so a maximum gain of about 40. Refinements will be added, never fear . . .

Reverting to Fig. 77 (a) and making R_{in} 10kΩ, with a similar value for R_{fb} , we obtain a gain of 0.98, and the virtual earth point is at the junction of the two resistors. If we insert a resistor as shown at

Fig. 77(b) we reduce the gain somewhat, 0.96, but let's return to that later, the important point being that we can arrange the gain that we require by choice of R_{in} and R_{fb} .

Here I part with Mike and assert that many modern circuits are resolved and arranged (rather than designed) by what are euphemistically called 'empirical methods'; more cynically described as 'hit or miss'. With the basis of existing circuits and a mass of mathematics that go to support them, the modern designer takes for granted the previous researches, and builds upon them. Exceptions, like John Linsley Hood, who question every fact and do their own research, are as rare as gold nuggets in a leadmine.

All of which digression leads me to Fig. 77(b). Here we have R_{in} at 10kΩ with a similar feedback resistor R_{fb} in series with a 0.047μF capacitor (itself, practically, paralleled by 100kΩ). The impedance of the feedback network can, if you want to be meticulous, be calculated at any point in the frequency range.

This is all very fine, but, in practice, we can say that at very high frequencies the capacitor will be an effective short-circuit. In these circumstances, the circuit becomes effectively R_{in}/R_{fb} having unity gain. Lowering the frequency raises the reactance X_c until it eventually becomes an open-circuit, and, in comparison with the 100kΩ previously mentioned, the gain will be nearly 11. Theory gives us 110/10, practice a little less, hence my question-begging formula. We shall settle for a gain of around 20dB, which is ten times the input voltage.

In the frequency range that C is effective we will have an impedance change in the feedback network giving us a slope of 6dB/octave. At frequencies below where unity gain is produced, the slope will flatten, so that further reduction of frequency does not change the output from unity gain. At frequencies above where the effective R_{fb} is 110kΩ, i.e., for a theoretical gain of x11, the curve again flattens. The transitions from slope to flat are not sudden and our dotted curves show the practical results obtained.

Turnover

Reference has already been made to f_t , and by this we mean the turnover frequency, (in the case of Fig. 75 we have two turnover points, at 3dB positive or negative position on the curve, depending on the way the calculations are carried out, as should become apparent).

The f_t points can be calculated from the formula $f_t = \frac{1}{2\pi CR}$ where the frequency is in hertz; the

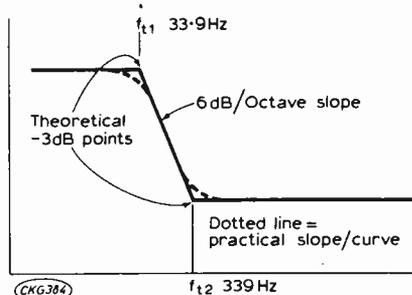


Fig. 78: The bass lift curve in theory (solid line) and in practice (dotted line).

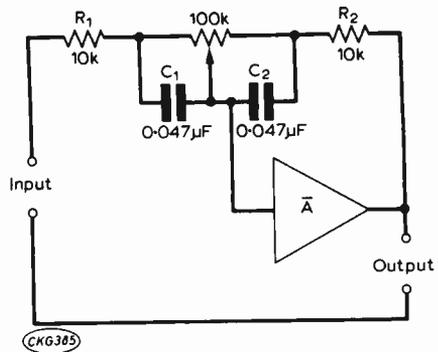


Fig. 79: A combined bass lift and cut circuit.

constant 2π can be taken as 6.28, C is in farads and R in ohms. Taking the component values of Fig. 77(b), we obtain a lower frequency turnover point of 33.9Hz while the upper frequency turnover point works out to 339Hz.

In practice, of course, the points are not definite. The plotted curve, as can be shown later, follows rather the dotted than the hard line of Fig. 78. Plotting the curve obtained from a 'hook-up' replica of Fig. 76, we get the actual curve of Fig. 78, from a generator with a 600Ω source impedance, and reading across the 'open' output with a high impedance valve-voltmeter. (Amendment, please: our habit these days is to use the battery-powered millivoltmeter so the use of the term 'valve-voltmeter' is mostly a matter of habit—although we certainly continue to use our old faithful instruments where the low value of hum and noise will not prove an embarrassment.)

One of the reasons for the smoothing of a theoretical curve is, of course, that other circuit considerations take effect. In theory, we take the two extremes, when the 0.047μF capacitor is in parallel with the 100kΩ resistor and the 10kΩ resistor is not effective, and when the capacitor is in series with the 10kΩ resistor, the effect of the 100kΩ resistor then being ignored. In practice, of course, it cannot be ignored: its real effect is to modify our 10kΩ to 9kΩ under these circumstances.

Taking the worked theoretical examples:

$$f_t = \frac{1}{2\pi CR} = \frac{10^6}{6.28 \times 0.047} \times 10k\Omega \dots\dots\dots (1)$$

$$\text{and } \frac{10^6}{6.28 \times 0.047} \times 100k\Omega \dots\dots\dots (2)$$

$$(1) = 339\text{Hz and } (2) = 33.9\text{Hz}$$

These figures agree very nearly with our practical measurements. This, from the curve of Fig. 78., gives us our Bass Lift circuit.

Bass cut

If we now reverse the networks R_{in} and R_{fb} as depicted in Fig. 77(c), we get an inverse of the previous curve. That is to say, we get bass cut instead of bass lift, because the feedback is now resistive, while the input circuit, up to the 'virtual earth point', is frequency-dependent.

Combining both these circuits, as in Fig. 79, we get bass cut and lift according to the position of the slider of the control. With the slider on the left, C1 is effectively short-circuited and we are left with

—continued on page 76

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £10-50. P. & P. 25p.

DE LUXE STEREO AMPLIFIER



A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate u.a. e. something with negligible hum. Valve line up:- 2 x ECL86 Triode Pentodes, 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £8-92 P. & P. 45p.

POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp continuous (1 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 5 1/2" x 2 1/2". Suitable for Transistor Radio, Tape Recorders, Amplifiers etc. etc. Ready PRICE £4-50. P. & P. 35p. built and tested.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T03, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" 6p for 50p P. and p. 13p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amp full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £1-85 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri 200/240v. Sec. 9-0-9 at 500mA. 85p. P. & P. 13p. Pri 200/240v. Sec. 12-0-12 at 1 amp. 95p. P. & P. 13p. Pri 200/240v. Sec. 10-0-10 at 2 amp. £1-45. P. & P. 30p.

British made solid state all silicon stereo amplifier. 15 watts rms per channel output. Fre. res. 20Hz to 20KHz. Suitable for magnetic or ceramic pickup tape mic. etc. built in switchable scratch filter, rumble filter and loudness control. 60 m/m slider controls for bass, treble and volume. 10 way push button function, selector switch. This amplifier has specification and performance usually only found in amplifiers costing twice as much. Each amplifier supplied, tested and fully guaranteed. Finished in the most attractive contemporary style teak cabinet. Size 16 1/2in. x 6 1/2in. x 4 1/2in. Makers recommended price £42-15. Our price (while stocks last) £32-50 + 75p. p. & P. + V.A.T. Send SAE for full details of specification. **CENTRE ZERO MINIATURE MOVING COIL METER.** 100uA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER
For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 12Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 85p. P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

VAT. Prices in this advertisement (incl. p. and p.) will be subject to VAT as from 1st April, 1973.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge 28-97 Carr. 50p. With stereo cartridge 27-97 Carr. 50p. **GARRARD SP25 Mk III** with heavy precision machined die cast turntable £10-85, carr. 50p.

SPECIAL BARGAIN OFFER!

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). **NOW ONLY £4-50. P. & P. 35p.**

LATEST ACOS GP91/18C mono compatible cartridge with 1/2 stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

SONOTONE STARC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond and Stereo LP and Sapphire 78. ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £3-85 P. & P. 40p.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £3-25 P. & P. 50p.

SPECIAL OFFER ! HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 8" deep. Fitted with P.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £8-40 Carr. 65p
Cabinet Available Separately £4-50 Carr. 60p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8-50 Carr. 65p

LOUDSPEAKER BARGAINS

5in. 3 ohm £1-05. P. & P. 15p. 7 x 4in. 3 ohm £1-15. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1-62. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3-20. P. & P. 30p. B.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4-20. P. & P. 30p.

EMI Ceramic magnet heavy duty tweeter. Approx 3 1/2". Available 3 or 8 or 15 ohms. £1-25 + 15p p. & p.
BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly £5-75. Guitar models: 25w. £6-75, 35w. £8-50. P. & P. 38p



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS

With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £2-75. P. & P. 25p.

12in. "RA" TWIN (ONE LOUSPEAKER. 10 watts peak handling 3, 8 or 15 ohm £2-20. P. & P. 30p. 25 ohm SPEAKERS 3i) only 63p P. & P. 13p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5-95 each. P. & P. 25p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usual, £1-75 yd., our price 75p yd. length. P. & P. 15p per yd (min 1 yd.) S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-cups. Wired and fitted with standard stereo 3 1/2 jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £2-95. P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES.
OUR PRICE £1-05. P. & P. 8p

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knob, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback of 18dB over main amp. Power required for 100% modulation: 12W x 8" d. x 1.0 amp. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT ... £10-50 P. & P. 15p
(Magnetic input components 30p extra)
POWER PACK KIT ... £3-00 P. & P. 30p
CABINET ... £3-00 P. & P. 30p

(Post Free if all units purchased at same time)
Full after sales service
Also available ready built and tested £21-00. Post Free.
Note: The above amplifier is suitable for feeding two mono stereo into inputs (e.g. mike, radio, turn error decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.



3-VALVE AUDIO

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on double plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 44 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4-95. P. & P. 35p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4-10. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECC83 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. **£2-95**
P. & P. 35p BARGAIN PRICE

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully brushed section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EZ80 and EZ80 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £2-97 P. & P. 55p. Also available ready built and tested £10-97 P. & P. 60p.

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Hold this
while I
solder it.



BAND-AID* Washproof Plasters.

© Johnson & Johnson
LTD

* TRADE MARK

HARTLEY TYPE 13A

ONLY £18.00
DOUBLE BEAM
OSCILLOSCOPE

TB2Hz-750kHz. Band width 5-5MHz. Sensitivity 33mV/cm. Calibration markers 100kHz and 1MHz. A completely reliable general purpose oscilloscope. Supplied with CIRCUIT DIAGRAM and Mains lead. Carr. £1-50.

As above. Complete with all accessories. £25-00. Carr. £1-50. Many other oscilloscopes available.

FIRST TIME EVER at £42-50
Solartron CD711S2 Double Beam Oscilloscope d.c.-9MHz; 3mV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carriage £1-50.

GRATICULES, 12cm x 14cm in High Quality plastic. 30p ea. P. & P. 5p.

MODERN TELEPHONES type 706. Two tone grey, £3-75 ea. The same but black, £2-75 ea. P. & P. 25p ea.

AS NEW type 706 **BLUE**, £5 ea. P. & P. 25p.

Also **TOPAZ YELLOW** £4-50 ea. P. & P. 25p.

STANDARD GPO DIAL TELEPHONE (black) with Internal bell, 87p ea. P. & P. 50p. Two for £1-50. P. & P. 75p. All telephones complete with bell and dial.

20Hz to 200kHz WB SINE AND SQUARE GENERATOR

Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8-85 each. P. & P. 25p. (Not cased, not calibrated.)

Open 9 a.m. to 7.30 p.m. any day.

CHILTMHEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916

WOBBULATOR

Sweeps 8 to 45MHz ready to use. 6-3V a.c. required. £9 each. P. & P. 25p. (Not cased, not calibrated.)

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 17p. **POTS**—10 different values. Brand new—50p. P. & P. 17p.

COMPONENT PACK consisting of 2-2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors $\frac{1}{2}$ and $\frac{1}{4}$ watt, many high stabs, etc. Fine value at 50p per pack. P. & P. 17p.

P.C.B., pack S & D. Quantity 2 an ft—no tiny pieces. 50p plus P. & P. 20p. **FIBRE GLASS** as above £1 plus P. & P. 20p.

5 **CRYSTALS** 70 to 90kHz. Our choice, 50p. P. & P. 15p.

Matched pairs, 50p per pair. P. & P. 15p.

TRIMMER PACK, 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. **ALL BRAND NEW**, 25p the lot. P. & P. 10p.

ELECTRONIC TIMER UNITS—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2-50 incl. carriage.

AMERICAN SCOPE type USM24. A 10 meg scope—all min valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore £20-00. Carr. £1-50.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 30p ea. Holder 1p ea. Information 5p. **PHOTOCELL** equ OCP71—15p ea. **PHOTO-RESIST** type Clare 703. Two for 50p.

DELIVERED TO YOUR DOOR

1 cwt of Electronic Scrap chassis boards, etc. No Rubbish. FOR ONLY £3-50.

Ever had Component Problems?

1. Problems of choosing your components?
2. Problems of getting them quickly?
3. Problems of locating a supplier?



HOME RADIO (COMPONENTS) LTD
have created a catalogue and an organisation that between them solve your problems simply & economically

PUT US TO THE TEST

FIRST YOU'LL NEED THE CATALOGUE. SEND COUPON with 75p CHEQUE or P.O. YOU'LL NEVER SPEND 15 BOB BETTER!

The price of 75p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

Please write your Name and Address in block capitals



Name _____

Address _____



HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PW, 234-240 London Road, Mitcham CR4 3HD

GOING BACK...

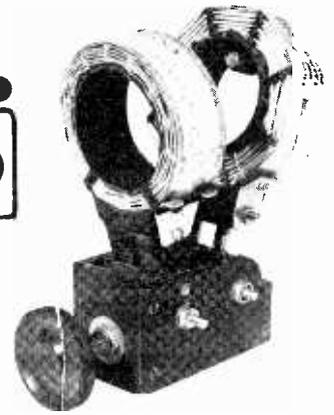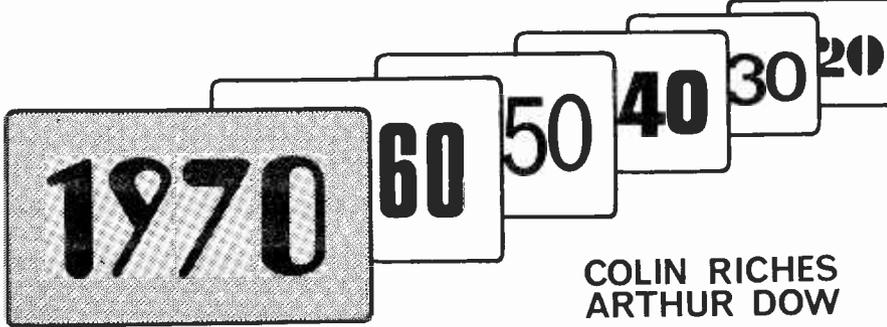

COLIN RICHES
ARTHUR DOW

QUITE a large number of letters addressed to us involve queries or seek information on the date or origin of bits and pieces of old wireless equipment or valves. So this month we thought that we would try to give some very broad indications of the form of construction and appearance of domestic wireless sets at the interesting stage of their development. This should enable readers to date a piece of apparatus, if called upon to express an opinion, or if an interesting bit of gear is found in a junkshop.

History

From the turn of the century when Marconi was experimenting with the first tuned spark transmitter, until 1922 when the first official broadcast was made and valve circuits had been developed to the extent that they were no longer regarded as freak, the amount of equipment produced was comparatively small and that which remains is mostly in safe hands.


Once broadcasting had begun the boom in home constructed receivers got under way very rapidly since there were few commercial receivers available at that time. It is this period from about 1922 until the mid-30's that is probably of most interest to

those who specialise in collecting vintage wireless equipment and with which we will concern ourselves here.

Components

There were many firms supplying components such as coils and holders, tuning condensers, audio transformers and valves as well as ebonite panels and associated hardware. Basket-wound or wave-wound coils were frequently home-made and plugged into holders which were adjustable from the panel to vary the coupling between the coils. Resistors looked like cartridge fuses and were pushed in to clips. The grid-leak was often changed to suit the 'softness' of the detector valve or it might be a panel-mounted variable resistance.

'Spaghetti' resistors had the resistance wire wound on a flexible core and looked like a piece of string with end tags. These could be connected directly between terminals of components. Most components such as audio transformers, valveholders and condensers etc. had terminals, usually 6BA, often with a soldering tag. Sets of this period were characterised by the great effort that went into the wiring up.

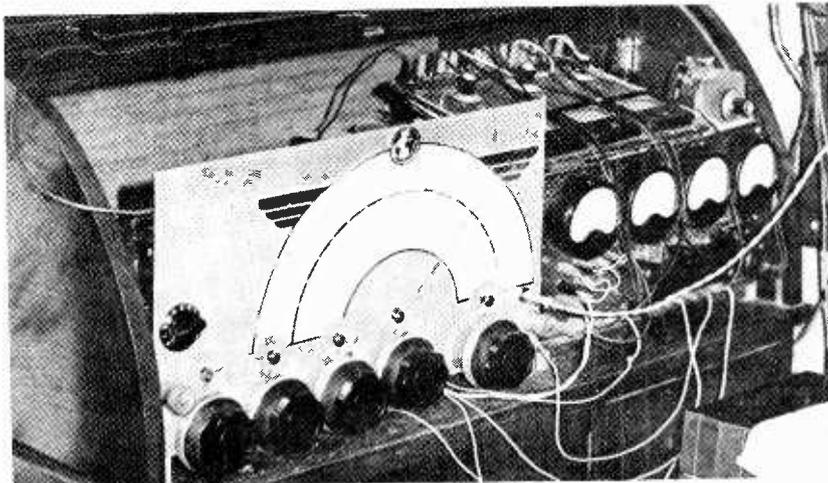

We don't want to start an argument but we think that Mr. A. Rea of Hull could be our oldest reader, at 80 years plus. Wireless is still his hobby and he is very proud of the John Scott-Taggart ST900, shown above, built many years ago, probably about 1937. He can feed the output of the receiver into a tape recorder or into a valved amplifier using a pair of PX25's which feeds no less than five loudspeakers around the place.

Square sectioned copper wire was common, always arranged with neat corners or angles and straight parallel runs and neat loops under the terminals. The need for short, direct wiring was not appreciated then, and indeed, was probably of little importance where only medium and long waves were concerned and stage gains were very low.

Construction

Such receivers were built on a wooden baseboard to which the components were fixed with wood-screws and an ebonite panel was fixed to one edge of the board. Along the back edge was a row of terminals, mounted on a strip of ebonite, for connecting the set to the accumulator, high tension battery, grid bias battery, aerial and earth and headphones or speakers. Incidentally, the cabinets for these sets were also given a great deal of attention and often were works of art in themselves to ensure that they fitted in with the rest of the furniture. Indeed, the receiver was often built in to an existing piece of furniture. The panels of sets of this period were a mass of knobs and controls with possibly a rheostat for each filament, variable grid-leaks, tuning condensers for each stage, coil coupling controls and reaction controls. Later, when shorter wavelengths were in use, metal panels were employed in order to prevent 'hand capacity' effects which upset the rather critical tuning.

Valves

Valves can be dated fairly accurately from a study of their physical characteristics. At the beginning of the period we are discussing, say 1922-24, the Marconi-Osram R valve was common along with the Mullard ORA and the Cossor P1 all of which were bright emitters with tungsten filaments. Generally they had a metal sleeve base and a pinch on top of the glass envelope, formed during the evacuation process. 1924-25 saw the introduction of the dull emitter valves using oxide-coated filaments such as the MO DE5, Mullard DO6 and the Cossor WR1. These valves still had the pinch on top but the bases were the more familiar moulded type.

Between 1925 and 1927 saw the advent of the now famous Mullard PM range of valves which were dull emitters with filament voltages from two to six volts. The pinch was now concealed in the base of the valve thus eliminating a very vulnerable feature of the older valves.

The first 'mains' type valves emerged in 1927 with the heaters, usually four volts, being run from a mains transformer instead of accumulators or batteries. In the early 30's r.f. type valves appeared with sprayed-on metallic coating for screening purposes and the glass envelopes, especially for the audio amplifier valves, developed a waisted section at the top of the envelopes intended to support the mica discs of the electrode assembly and thus reduce any tendency to microphony.

For those that are really interested in these old radios there is no finer pastime than trying to get one of them to work even if it means using equivalent modern components as replacements for faulty parts. Our CQ column is open to those readers who wish to appeal to other readers for old components if it is felt that only a 100% genuine vintage receiver is acceptable.

the effective bass lift circuit of Fig. 77(b). With the slider to its right we get the alternative condition, with C2 short-circuited and the bass cut circuit of Fig. 77(c).

Balance

Take the case of the slider at its middle position. Then, the input and output circuits are identical and balanced. That word, BALANCED is important. It is the basis of the Baxandall tone control circuit—one of the most elegant solutions to an audio problem yet posed, and not to be under-rated. In the full circuit, the impedance change with the slider moved (a change in frequency-dependence, looked at in the basic way of our approach) is exactly balanced with the movement of the slider in the other

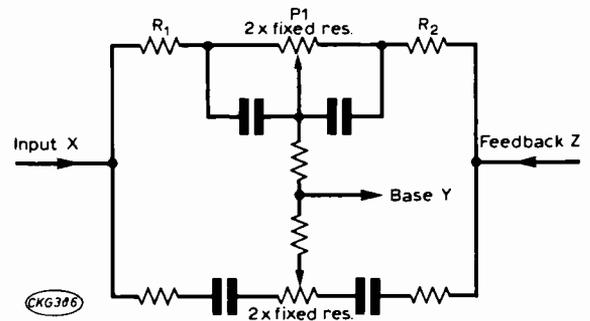


Fig. 80: The eventual network to be inserted in the feedback loop, giving bass and treble lift and cut.

section of the ganged potentiometer. It remains only that the ganged potentiometers themselves shall be within at least 1dB of linearity.

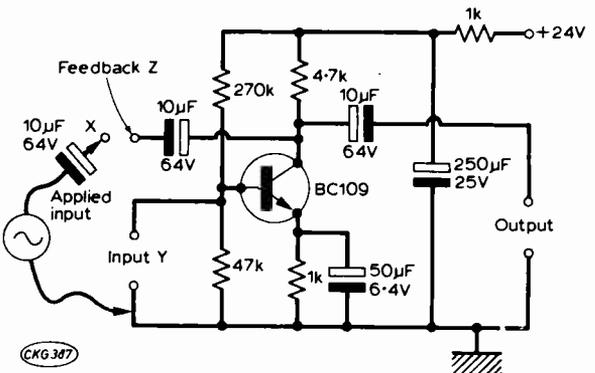


Fig. 81: The basic amplifier circuit over which the feedback is applied.

From the simple experiments we have already carried out, we know that when the input resistance, R_{in} is equal to the feedback resistance R_{fb} , then the theoretical gain is unity. In practice, findings are not far removed from the theoretical. At intermediate positions of the sliders, we shall get variations from the theoretical norm, between maximum bass and maximum cut.

ZN414 £1.25 POST FREE

The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets

Dual in-line or Zig Zag (Duit), 14 and 16 pin
Our Price 1p per pin

VDR's & Thermistors

A15B	75p	GL23	£1.00	VA1005	15p
CZ1	15p	R53	£1.32	VA1026	13p
CZ4	13p	R54	£1.46	VA1033	13p
CZ13A	13p		VA1040	10p	
E298 ED/A258	10p		VA1053	10p	
E298 ZZ/06	10p		VA1055S	10p	
GL16	£1		VA1034	10p	

Potentiometers



5KΩ	50KΩ	500KΩ	
10KΩ	100KΩ	1MΩ	
25KΩ	250KΩ	2MΩ	

log or lin less switch (& 1KΩ lin) 12p
log or lin with switch 24p
dual less switch 40p
dual with switch 10K, 100K & 1M log only 52p
10K log 10K antilog less switch 40p

Capacitors

disc ceramic		low voltage	
0.1μF 18v	5p	0.1μF 30v	5p
0.22μF 18v	5p	0.22μF 6v	5p
0.47μF 12v	5p	0.47μF 3v	5p
ceramic plate		30V	
1000pf	10p	4700pf	10p
2200pf	10p	10,000pf	10p

Ceramic - plate		63V (C333)	
1.8pf	8.2pf	33pf	120pf
2.2pf	10pf	39pf	150pf
3.3pf	12pf	47pf	180pf
3.9pf	15pf	56pf	220pf
4.7pf	18pf	68pf	270pf
5.6pf	22pf	82pf	330pf
6.8pf	27pf		00pf
all 5p. each			

mylar film		100V	
1000pf 2p	0.1μF 3p	0.68μF 4p	5p
2000pf 2p	0.2μF 3p	1μF 5p	4p
5000pf 2p	0.4μF 3p	2μF 5p	5p
	0.5μF 3p		

polystyrene		160V	
10pf to 10,000pf In multiples of 10, 15, 22, 33, 47 & 68			

metallised polyester		250V (C280)	
0.1μF 3p	0.68μF 3p	4.7μF 8p	
0.15μF 3p	1μF 4p	68μF 1p	
0.22μF 3p	1.5μF 4p	100μF 1p	
0.33μF 3p	2.2μF 5p	1.5μF 20p	
0.47μF 3p	3.3μF 6p	2.2μF 24p	

metallised polyester		400V (C281)	
0.1μF 4p	0.47μF 6p	22μF 10p	
0.15μF 4p	0.68μF 6p	33μF 10p	
0.22μF 4p	1μF 7p	47μF 15p	
0.33μF 5p	1.5μF 8p		

silvered mica 1% (-50pf) 500V			
2.2pf-820pf	7p	4.7nF-5600pf	19p
1nF-2.2nF	9p	6800pf-0.1μF	22p
2.7nF-3.6nF	16p		

mixed dielectric		600V	
0.1μF 7p	0.47μF 7p	22μF 16p	
0.22μF 7p	0.68μF 8p	47μF 24p	
0.33μF 7p	1μF 8p	1μF 33p	

Slider Pots


Single	Dual	log
10K	10 + 10K	or
25K	25 + 25K	lin
50K	50 + 50K	
100K	100 + 100K	Knobs
30p	50p	10p

Resistors

1/2 watt 5% Carbon Film - low noise
Hi-Stabs
All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value

1 W 10% Carbon Composition 3p each
2 W 10% Carbon Composition 6p each
2 W 5% Wire wound 9p each
5 W Wire wound 9p each
10 W Wire wound 10p each
plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25

Eliminators

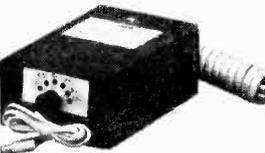

9 volt @ 20mA (PP3)	£1.25
6 volt @ 50mA	£1.50
9 volt @ 50mA	£1.50
6 - 6 volt, 50mA	£2.50
9 - 9 volt, 50mA	£2.50
7 1/2 volt for cassette recorders	£2.00
6, 7 1/2 or 9 volt	£3.00
Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts	£3.99
(p. & p. 15p on all types)	£4.99


NEW LIST
LOUDSPEAKERS
COILS AND INDUCTORS
TRANSFORMERS
(postage 5p)

Diodes & Rectifiers

AA119	9p	BA156	15p	BY176	£1.50
AA120	9p	BA243	56p	BY182	£1.50
AA129	9p	OA47	10p	BY250	23p
BA102	25p	OA79	9p	IN4001	6p
BA115	17p	OA90	7p	IN4002	7p
BA130	10p	OA91	7p	IN4003	8p
BA145	20p	OA200	10p	IN4004	8p
BA148	20p	BY100	15p	IN4005	10p
BA154	13p	BY126	15p	IN4006	12p
BA155	14p	BY127	15p	IN4007	15p

8776 ZENER SERIES (p. 40)

SGS

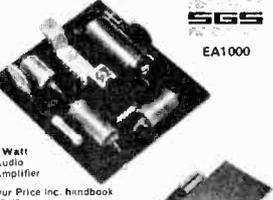

EA1000
3 Watt Audio Amplifier
Our Price inc. handbook £2.49



FM TUNER chassis fully transistorised 9 volt operation
OUR PRICE £6.25
Matching stereo decoder £4.97
Ask for model list No. 11.

10 - less 15%
25 - less 25%
100 - less 33%
5 Watt Audio Amplifier
Our Price £3.99
Less quantity discount.

Presets



Vertical or Horizontal	
0.1 watt 5p	0.25 watt 7p
100 1K Ω	10K Ω 1M Ω
250 2.5K Ω	25K Ω 250K Ω 2.5M Ω
500 5K Ω	50K Ω 500K Ω 5M Ω

mylar film		100V	
1000pf 2p	0.1μF 3p	0.68μF 4p	5p
2000pf 2p	0.2μF 3p	1μF 5p	4p
5000pf 2p	0.4μF 3p	2μF 5p	5p
	0.5μF 3p		

polystyrene		160V	
10pf to 10,000pf In multiples of 10, 15, 22, 33, 47 & 68			

metallised polyester		250V (C280)	
0.1μF 3p	0.68μF 3p	4.7μF 8p	
0.15μF 3p	1μF 4p	68μF 1p	
0.22μF 3p	1.5μF 4p	100μF 1p	
0.33μF 3p	2.2μF 5p	1.5μF 20p	
0.47μF 3p	3.3μF 6p	2.2μF 24p	

metallised polyester		400V (C281)	
0.1μF 4p	0.47μF 6p	22μF 10p	
0.15μF 4p	0.68μF 6p	33μF 10p	
0.22μF 4p	1μF 7p	47μF 15p	
0.33μF 5p	1.5μF 8p		


silvered mica 1% (-50pf) 500V			
2.2pf-820pf	7p	4.7nF-5600pf	19p
1nF-2.2nF	9p	6800pf-0.1μF	22p
2.7nF-3.6nF	16p		

mixed dielectric		600V	
0.1μF 7p	0.47μF 7p	22μF 16p	
0.22μF 7p	0.68μF 8p	47μF 24p	
0.33μF 7p	1μF 8p	1μF 33p	

MAIL ORDERS: Where no p. & p. charge is shown a minimum of 7p applies. p. & p. on overseas orders is charged at cost.
ADDRESS TO: Component Dept.
56, Fortis Green Road, London N10 3HN
Telephone 01-883 3705

CHROMASONIC electronics

Heat Sinks

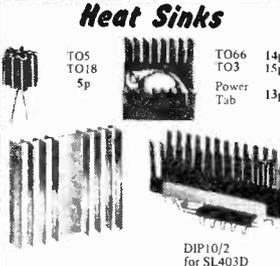

TOS	5p	TO66	14p
TO18		TO3	15p

Power Tab 13p
DIP10/2 for SL403D 15p
10D 50p

Transistors & Integrated Circuits


AC107	25p	BC147	10p	BF196	15p	OC81	19p	2N1304	22p	2N5172	15p
AC126	17p	BC148	10p	BF197	15p	OC140	20p	2N1711	25p	LO05T1	£1.50
AC127	15p	BC149	10p	BF272	53p	OC170	23p	2N1893	30p	LOG	£1.50
AC128	15p	BC157	12p	BFY50	24p	OC171	30p	2N2926	all 10p	LOG	£1.50
AC176	15p	BC158	10p	BFY51	21p	ZTX107	15p	2N3053	23p	MC1330L	£1.75
AC187	25p	BC159	12p	BRY39	38p	ZTX108	12p	2N3054	56p	MC1330	80p
AC187K	25p	BC169	15p	BSX21	26p	ZTX109	15p	2N3055	49p	MC1350	75p
AC188	25p	BC268	15p	BSY65A	14p	ZTX300	12p	2N3056	12p	MC1351	£1.00
AC188K	25p	BD115	67p	BUI10502	£1.75	ZTX301	15p	2N3703	12p	MC1359	£1.00
ACY20	20p	BD131	70p	MUE340	87p	ZTX302	20p	2N3704	10p	MFC4000B	48p
AD140	40p	BD136	70p	MPF192	40p	ZTX303	20p	2N3705	10p	MFC4010A	55p
AD149	40p	BD137/2M P		MPF103	37p	ZTX304	25p	2N3706	10p	LM380	£1.45
AD181	60p	BF160	21p	MPF105	46p	ZTX305	15p	2N3707	15p	PA234	£1.99
AD182	11p	BF167	20p	MPF106	45p	ZTX501	15p	2N3709	12p	TAD100	£1.50
AF115	18p	BF172	20p	OC28	40p	ZTX502	20p	2N3710	12p	FILTER LP175	£1.50
AF118	18p	BF196	25p	OC35	40p	ZTX503	17p	2N3711	12p	μA709C	34p
AF117	18p	BF191	30p	OC44	15p	ZTX504	50p	2N3819	35p	μA710	45p
AF139	28p	BF194	25p	OC48	15p	ZTX531	25p	2N3963	15p	μA720C	95p
BC107	10p	BF185	25p	OC71	11p	2N697	18p	2N3904	17p	μA741C	47p
BC108	10p	BF194	15p	OC72	17p	2N706	12p	2N3905	21p	μA748C	60p
BC109	10p	BF195	15p	OC76	15p	2N708	15p	2N3906	12p		

Veroboard

Copperclad		Plain	
0.1"	0.15"	0.15"	
2 3/8" x 1"	6p	6p	
2 3/8" x 3 3/8"	20p	16p (9)	10p
2 3/8" x 5"	24p	21p (7)	12p
3 3/8" x 3 3/8"	24p	21p (8)	
3 3/8" x 5"	27p	27p (10)	17p
1 7/8" x 2 3/8"	67p	50p	37p
1 7/8" x 3 3/8"	90p	70p	52p
1 7/8" x 5"			75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

THE TEXAN

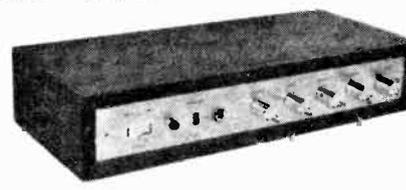

Complete Kit (inc. Teak Case) **£28.50** ~~£50~~ **45p**

20 Watts per channel integrated stereo amplifier developed by engineers of 'Texas Instruments Ltd. This designer approved kit, has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 Hz at -3db. The semiconductor complement of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistor, 4 rectifiers and 2 zeners. Controls include: bass, treble, volume, balance, 'on/off', 'on' indicator, headphone sockets, scratch filter, rumble filter, inputs for magnetic phono, tuner, aux. or tape; tape head etc. input, selector; mono/stereo switch.

The construction of this kit was featured in 'Practical Wireless' May/Aug 1972.

NEW LISTS
BOXES, CHASSIS, etc. No. 7
TRANSISTORS, I.C.'s, etc. (soon)

Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2 3/8"	5 3/8"	1 1/8"	35p	8p
(8)	4"	4"	1 1/8"	35p	8p
(9)	4"	4 3/8"	1 1/8"	35p	8p
(10)	4"	5 3/8"	1 1/8"	40p	8p
11	4"	2 3/8"	2"	35p	8p
12	3"	2"	1 1/8"	32p	9p
13	6"	4"	2"	50p	10p
14	7"	5"	2 3/8"	58p	12p
15	8"	6"	3"	75p	18p
16	10"	7"	3 3/8"	85p	20p

Mullard B Siemens Electrolytics

CAP		VOLTAGE						
μF		4	6.3	10	16	25	50	63
1.5								5p
2.2								6p
3.3								6p
4.7								6p
6.8								6p
10								6p
15								6p
22								6p
33								6p
47	6p							6p
68								10p
100	6p							12p
150	6p							12p
220	6p							18p
330	6p							18p
470								18p
680								21p
1000	10p							40p
1500								40p
2200								55p
3300								55p
4700	21p							83p

Hi-Volt Electrolytics

CAP		VOLTAGE			
μF		18	25	50	64
500					33p 40p
1250					50p
1600					75p
2000					75p
2500					90p
3200					90p
4000					90p
5000					90p

Quantity Prices on application

SEW PANEL METERS

CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

- LOW COST
- QUICK DELIVERY
- OVER 200 RANGES IN STOCK
- OTHER RANGES TO ORDER

Type SW.100 100 x 80 mm.

50µA	£3.80
50-0-50µA	£3.80
100µA	£3.80
100-0-100µA	£3.70
500µA	£3.50
1mA	£3.40
20V. D.C.	£3.40
50V. D.C.	£3.40
300V. D.C.	£3.40
1 amp. D.C.	£3.40



5 amp. D.C. £3.40
300V. A.C. £3.40
VU Meter £4.15

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts

50mA	£3.10
100mA	£3.10
500mA	£3.10
1 amp.	£3.10
5 amp.	£3.10
15 amp.	£3.10
30 amp.	£3.20
20V. D.C.	£3.10
50V. D.C.	£3.10
150V. D.C.	£3.10
300V. D.C.	£3.10
15V. A.C.	£3.10
300V. A.C.	£3.10
8 Meter 1mA	£3.15
VU Meter	£3.95
5 amp. A.C.*	£3.10
1 amp. A.C.*	£3.10
10 amp. A.C.*	£3.10
20 amp. A.C.*	£3.10
30 amp. A.C.*	£3.10

Type MR.38P. 1 21/32 in. square fronts

200mA	£1.75
300mA	£1.75
500mA	£1.75
750mA	£1.75
1 amp.	£1.75
2 amp.	£1.75
5 amp.	£1.75
10 amp.	£1.75
3V. D.C.	£1.75
10V. D.C.	£1.75
15V. D.C.	£1.75
20V. D.C.	£1.75
50V. D.C.	£1.75
100V. D.C.	£1.75
150V. D.C.	£1.75
300V. D.C.	£1.75
500V. D.C.	£1.75
750V. D.C.	£1.75
15V. A.C.	£1.85
50V. A.C.	£1.85
150V. A.C.	£1.85
300V. A.C.	£1.85
500V. A.C.	£1.85
8 Meter 1mA	£1.85
VU Meter	£2.30

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts

1 amp.	£2.15
5 amp.	£2.15
15 amp.	£2.15
30 amp.	£2.15
50 amp.	£2.15
5V. D.C.	£2.15
10V. D.C.	£2.15
20V. D.C.	£2.15
50V. D.C.	£2.15
150V. D.C.	£2.15
300V. D.C.	£2.15
50mV. D.C.	£2.40
100mV. D.C.	£2.40
30V. A.C.*	£2.20
50V. A.C.*	£2.20
150V. A.C.*	£2.20
300V. A.C.*	£2.20
500V. A.C.*	£2.20
500mA	£2.15
1 amp. A.C.*	£2.15
5 amp. A.C.*	£2.15
10 amp. A.C.*	£2.15
20 amp. A.C.*	£2.15
30 amp. A.C.*	£2.15
500mA	£2.15
VU Meter	£3.40

Type SD.830 82.5mm x 110mm Fronts

10mA	£2.50
50mA	£2.50
100mA	£2.50
500µA	£2.50
1 amp.	£2.50
5 amp.	£2.50
10 amp.	£2.50
5V. D.C.	£2.50
10V. D.C.	£2.50
20V. D.C.	£2.50
50V. D.C.	£2.50
300V. D.C.	£2.50
15V. A.C.	£2.75
300V. A.C.	£2.75
VU Meter	£3.00

Type MR.52P. 2 1/2 in. square fronts

50µA	£2.40
50-0-50µA	£2.35
100µA	£2.35
100-0-100µA	£2.75
500µA	£2.75
1mA	£2.20
10mA	£2.20
50mA	£2.20
100mA	£2.20
500mA	£2.20
1 amp.	£2.20
5 amp.	£2.20
10V. D.C.	£2.20
20V. D.C.	£2.20
50V. D.C.	£2.20
300V. D.C.	£2.20
15V. A.C.	£2.30
300V. A.C.	£2.30
8 Meter 1mA	£2.30
VU Meter	£3.50
1 amp. A.C.*	£2.20
5 amp. A.C.*	£2.20
10 amp. A.C.*	£2.20
20 amp. A.C.*	£2.20
30 amp. A.C.*	£2.20

Type MR.45P. 2 in. square fronts

50µA	£2.50
50-0-50µA	£2.30
100µA	£2.30
100-0-100µA	£2.95
500µA	£2.95
1mA	£1.85
5mA	£1.85
10mA	£1.85
20mA	£1.85
50mA	£1.85
100mA	£1.85
150mA	£1.85
5 amp.	£2.50
10V. D.C.	£1.85
20V. D.C.	£1.85
50V. D.C.	£1.85
300V. D.C.	£1.85
15V. A.C.	£2.00
300V. A.C.	£2.00
8 Meter 1mA	£2.05
VU Meter	£2.50
1 amp. A.C.*	£1.85
5 amp. A.C.*	£1.85
10 amp. A.C.*	£1.85
20 amp. A.C.*	£1.85
30 amp. A.C.*	£1.85

Type S-80 80 mm. square fronts

50µA	£3.50
50-0-50µA	£3.40
100µA	£3.40
100-0-100µA	£3.30
500µA	£3.30
1mA	£2.50
5mA	£2.50
10mA	£2.50
20mA	£2.50
50mA	£2.50
100mA	£2.50
500mA	£2.50
1 amp. D.C.	£2.85
300V. D.C.	£2.85
VU Meter	£3.70

Type SD.640 63.5mm x 85mm Fronts

50µA	£2.60
50-0-50µA	£2.55
100µA	£2.55
100-0-100µA	£2.55
200µA	£2.55
500µA	£2.35
1mA	£2.35
5mA	£2.35
10mA	£2.35
50mA	£2.35
100mA	£2.35
500µA	£2.35
1 amp.	£2.35
5 amp.	£2.35
10 amp.	£2.35
5V. D.C.	£2.35
10V. D.C.	£2.35
20V. D.C.	£2.35
50V. D.C.	£2.35
300V. D.C.	£2.35
15V. A.C.	£2.40
300V. A.C.	£2.40
VU Meter	£2.70

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts

50µA	£3.70
50-0-50µA	£3.00
100µA	£3.00
100-0-100µA	£2.80
500µA	£2.80
500-0-500µA	£2.65
1mA	£2.40
5mA	£2.40
10mA	£2.40
20mA	£2.40
50mA	£2.40
100mA	£2.40
500mA	£2.40
1 amp.	£2.40
5 amp.	£2.40
10 amp.	£2.40
15 amp.	£2.40
20 amp.	£2.40
30 amp.	£2.40
50 amp.	£2.75
5V. D.C.	£2.40
10V. D.C.	£2.40
20V. D.C.	£2.40
50V. D.C.	£2.40
150V. D.C.	£2.40
300V. D.C.	£2.40
15V. A.C.	£2.55
50V. A.C.	£2.55
150V. A.C.	£2.55
300V. A.C.	£2.55
500V. A.C.	£2.55
8 Meter 1mA	£2.60
VU Meter	£2.70
1 amp. A.C.*	£2.40
5 amp. A.C.*	£2.40
10 amp. A.C.*	£2.40
20 amp. A.C.*	£2.40
30 amp. A.C.*	£2.40

Type PE.70. 3 1/2 x 1 1/2 in. x 2 1/2 in. deep

50µA	£3.40
50-0-50µA	£3.30
100µA	£3.30
100-0-100µA	£3.20
200µA	£3.20
500µA	£3.20
1 amp.	£3.85
5 amp.	£3.85
10 amp.	£3.85
20 amp.	£3.85
30 amp.	£3.85
500µA	£3.05
1mA	£2.70
300V. A.C.	£2.70
VU Meter	£3.75

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. Each instrument has a mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50µA	£5.50
100µA	£5.10
1mA	£4.85
50-0-50µA	£5.10
1-0-1mA	£4.85
1A d.c.	£4.85
1A d.c.	£4.85
10V. d.c.	£4.85
20V. d.c.	£4.85
50V. d.c.	£4.85
300V. d.c.	£4.85
Dual range 500mA/5A d.c.	£5.10
5V/50V d.c.	£5.10

Type SD.460 46mm x 59.5mm Fronts

50µA	£2.40
50-0-50µA	£2.35
100µA	£2.35
100-0-100µA	£2.35
200µA	£2.35
500µA	£2.20
1mA	£2.15
5mA	£2.15
10mA	£2.15
50mA	£2.15
100mA	£2.15
600µA	£2.15
1 amp.	£2.15
5 amp.	£2.15
10 amp.	£2.15
5V. D.C.	£2.15
10V. D.C.	£2.15
20V. D.C.	£2.15
50V. D.C.	£2.15
300V. D.C.	£2.15
15V. A.C.	£2.30
300V. A.C.	£2.30
VU Meter	£2.55

Type MR.52P. 2 1/2 in. square fronts

50µA	£2.30
50-0-50µA	£2.20
100µA	£2.20
100-0-100µA	£2.20
500µA	£2.20
1mA	£2.20
5mA	£2.20
10mA	£2.20
20mA	£2.20
50mA	£2.20
100mA	£2.20
500µA	£2.20
1 amp.	£2.20
5 amp.	£2.20
10 amp.	£2.20
15 amp.	£2.20
20 amp.	£2.20
30 amp.	£2.20
50 amp.	£2.75
5V. D.C.	£2.20
10V. D.C.	£2.20
20V. D.C.	£2.20
50V. D.C.	£2.20
150V. D.C.	£2.20
300V. D.C.	£2.20
15V. A.C.	£2.30
50V. A.C.	£2.30
150V. A.C.	£2.30
300V. A.C.	£2.30
500V. A.C.	£2.30
8 Meter 1mA	£2.30
VU Meter	£3.50
1 amp. A.C.*	£2.20
5 amp. A.C.*	£2.20
10 amp. A.C.*	£2.20
20 amp. A.C.*	£2.20
30 amp. A.C.*	£2.20

"SEW" EDGWISE METERS

Type PE.70. 3 1/2 x 1 1/2 in. x 2 1/2 in. deep

50µA	£3.40
50-0-50µA	£3.30
100µA	£3.30
100-0-100µA	£3.20
200µA	£3.20
500µA	£3.20
1 amp.	£3.85
5 amp.	£3.85
10 amp.	£3.85
20 amp.	£3.85
30 amp.	£3.85
500µA	£3.05
1mA	£2.70
300V. A.C.	£2.70
VU Meter	£3.75

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. Each instrument has a mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50µA	£5.50
100µA	£5.10
1mA	£4.85
50-0-50µA	£5.10
1-0-1mA	£4.85
1A d.c.	£4.85
1A d.c.	£4.85
10V. d.c.	£4.85
20V. d.c.	£4.85
50V. d.c.	£4.85
300V. d.c.	£4.85
Dual range 500mA/5A d.c.	£5.10
5V/50V d.c.	£5.10

***MOVING IRON— ALL OTHERS MOVING COIL**
Please add postage

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1 in. dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.15 P. & P. 10p.
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.65 P. & P. 15p.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £1.85 P. & P. 15p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS
Excellent quality · Low price · Immediate delivery

6-260 General Purpose Bench Mounting

1 Amp	£7.00
2.5 Amp	£8.05
5 Amp	£11.75
8 Amp	£15.90
10 Amp	£22.50
12 Amp	£23.80
20 Amp	£49.00
25 Amp	£58.00
40 Amp	£82.50

6-260B Panel Mounting

1 Amp	£7.00
2.5 Amp	£8.05

Please add postage
ALL MODELS
INPUT 230 V 50/60 CYCLES
OUTPUT VARIABLE 0-260 VOLTS
Special discounts for quantity

AUTO TRANSFORMERS
0/115/250V. Step up or step down. Fully shrouded.

80 W	£2.10	P. & P. 18p
150 W	£2.70	P. & P. 18p
300 W	£3.80	P. & P. 23p
500 W	£5.25	P. & P. 33p
1000 W	£7.50	P. & P. 43p
1500 W	£10.20	P. & P. 43p
2280 W	£17.25	P. & P. 50p
8000 W	£35.00	P. & P. £1

MCA.220 AUTOMATIC VOLTAGE STABILISER

Input 88 125 VAC or 175 250VAC. Output 120V AC. or 240 VAC. 200 VA. rating. £11.97, carr. 50p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 5 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40) Quantities available.

BH.001 HEAD SET AND BOOM MICROPHONE

Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. £4.82. P. & P. 15p.

240° Wide Angle 1mA Meters

MW 1-6 80mm square £3.97
MW 1-8 80mm square £4.97
P. & P. extra

RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V AC. Size 185 x 85 x 105mm. £8.97 P. & P. 25p.

PS.200 REGULATED P.S.U.

Solid state. Variable output 5-20 volt D.C. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V A.C. Size 7 1/2" x 5 1/2" x 3 1/2". £14.97. P. & P. 25p.

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 1.5 amp. Meter to monitor current. Input 220/240V AC. Size 4" x 3 1/2" x 6 1/2". £11.97. P. & P. 25p.

230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RPH CW; 60p each Post 12p.


LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1

MULTIMETERS for EVERY purpose!



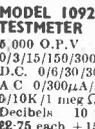
TS60 POCKET MULTIMETER
High-precision at low-cost.
Ranges: D.C. 15V, 150V, 1,000V (10,000 opv). A.C. 15V, 150V, 100V (1,000 opv). D.C. Current 150mA. Resistance 100k ohms.
\$1.85. Post 15p.



MODEL 1092 TESTMETER
5,000 O.P.V.
0/3/15/150/300/1200 V.
D.C. 0/6/30/300/600 V.
A.C. 0/300/1200 MA
1/10K/1 meg Ω
Decibels 10 to +16dB
\$2.75 each +15p P. & P.



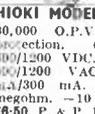HIKIOI MODEL 720X
20,000 O.P.V.
Overload protection
10/5/150/500/1000 V.D.C.
10/5/250/1000 V.A.C.
50μA/250mA. 20K/2 meg
ohms. -5 to +62dB
\$4.97. P. & P. 15p




HIKIOI MODEL 730X
30,000 O.P.V. Overload
protection. 6/30/60/300/
600/1200 V.D.C. 12/60/120/
600/1200 V.A.C. 60μA/30
mA/300 mA. 2K/200K/2
megohm. -10 to +63dB
\$5.80. P. & P. 15p



KAMODEN 72.200 MULTITESTER
High sensitivity tester.
200,000 o.p.v. Overload
protection. Mirror scale.
Ranges:
0 / -06 / -3 / 3 / 30 / 120 /
600 / 1200V. D.C.
0 / 3 / 12 / 60 / 300 /
11, 200V. A.C.
0 / 6μA / 1-2mA / 120mA /
600mA / 12A. D.C.
0 / 12A. A.C.
-20 to +63dB.
0 / 2K / 200K / 2 meg /
200 meg ohms.
\$16.95. Post 30p



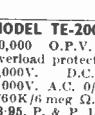MODEL TE-200
20,000 O.P.V. Mirror scale,
overload protection. 0/5/25/125/
1,000V. D.C. 0/10/50/250/
1,000V. A.C. 0/50 μA/250 mA/
0/60K/6 meg Ω. -20 to +62dB.
\$3.95. P. & P. 15p.




MODEL 500
30,000 O.P.V. with overload
protection mirror scale
0/5/2.5/10/25/100/250/500/
1,000V. D.C. 0/2.5/10/25/
100/250/500/1,000V. A.C.
0/50μA/5/50/500mA. 12
amp. D.C. 0/60K/6 Meg/
60 Meg Ω.
\$8.87. Post paid.



HIKIOI MODEL 750X
50,000 o.p.v. 43 ranges 0-0.3
to 1,200V D.C. 0-3 to 1,200V
A.C. 0-300μA/300mA. 0-3K/30
meg ohms. -10 to +17dB.
\$8.97. Post 20p.



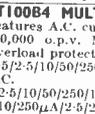HT10084 MULTI-METER
Features A.C. current ranges.
100,000 o.p.v. Mirror Scale,
Overload protection.
0/5/2.5/10/50/250/500/1000 V
D.C.
0/2.5/10/50/250/1000 V. A.C.
0/10/250μA/2.5/25/250 MA/
10 Amp. D.C.
10 Amp A.C. 0/20K/200K/
2 MEG/20 MEG. -20 +62dB.
\$12.50. P. & P. 25p.



370 WTR MULTI-METER
Features A.C. current ranges.
20,000 o.p.v. 0/5/2.5/10/50/
250/500/1000 V. D.C.
0/2.5/10/50/250/500/1000V A.C.
0/50μA/1/10/100mA/1/10 Amp
D.C.
0/100mA/1/10 Amp A.C.
0/5K/50K/500K/5 MEG/ 50
MΩ.
-20 +62dB.
\$15. P. & P. 25p.



RUSSIAN 22 RANGE MULTIMETER
Model U437 10,000 o.p.v.
A first class versatile instrument
manufactured in
U.S.S.R. to the highest
standards. Ranges: 2.5/10/
50/250/500/1000V. D.C. 2.5/
10/50/250/500/1000V. A.C.
DC Current 100mA/1/10/
100mA/1A. Resistance
300 ohms/3/30/300K/3M Ω.
Complete with batteries,
test leads, instructions and
sturdy steel carrying case.
OUR PRICE \$5.97. P. & P. 25p

ROUND SCALE TYPE PENCIL TESTER MODEL Y.58
Completely portable, simple
to use pocket sized tester.
Ranges 0/3/30/300V AC
and DC at 2,000 o.p.v.
Resistance 0-20K ohms.
ONLY \$1.97 P. & P. 13p.




LT601 MULTIMETER
New style 20,000
o.p.v. pocket multi-
meter. 5/25/50/250/
500 / 2500 V. D.C.
10 / 50 / 100 / 500 / 1000V.
A.C. 50μA / 250mA. 4K / 6
meg ohms. -20 to +22 dB.
\$3.75. Post 20p.



MODEL TH-12
20,000 o.p.v. Overload
protection Blade switch selector
0 / -25 / 2.5 / 10 / 50 / 250 /
1000V. D.C. 0 / 10 / 50 / 250 /
1000V. A.C. 0 / 50μA / 25 /
250mA. D.C. 0 / 3K / 30K /
300K / 3 meg -20 to +50dB
\$4.97. Post 15p.



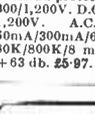MODEL TE-300
30,000 O.P.V. Mirror scale,
overload protection 0/5/3/15/60/
300/1,200V. D.C. 0/6/30/120/600/
1,200V. A.C. 0/30μA/60/600/
60mA/300mA/600mA. 0/8K/
80K/800K/8 meg. ohm -20 to
+63 db. \$5.97. P. & P. 15p.



MODEL PL436
20k Ω/Volt D.C. 8k Ω/
Volt A.C. Mirror scale.
-6/3/12/30/120/600 V
D.C. 3/30/120/600 V
A.C. 50/600μA/60/600
mA. 10/100K/1 Meg/10
Meg Ω -20 to +48db.
\$6.97. P. & P. 12p.




TMK MODEL TW-50K
46 ranges, mirror scale,
50K/Volt. D.C. 5K/Volt A.C.
D.C.: Volts -125, -25, -1.25,
2.5, 5, 10, 25, 50, 125, 250,
500, 1000V. A.C. Volts: 1.5,
3, 5, 10, 25, 50, 125, 250, 500,
1000V. D.C. Current: 25,
50μA, 2.5, 5, 25, 50, 250,
500mA, 5.10 amp. Resistance:
10K, 100K, 1 MEG, 10 MEG
Ω. Decibels: -20 to +81.5db
\$8.60. P. & P. 17p.




MODEL K228A
Taut band
suspension.
Overload
protection.
Polarity
reversing
switch. 30,000 o.p.v.
0 / 5 / 2.5 / 15 / 50 / 250 /
500 / 1000 / 2500V. D.C. 0 / 15 / 50 / 150 /
500 / 1000V. A.C. 0 / 50μA / 5 / 50 / 150 /
500mA. 1.5 D.C. 0 / 3K / 300K / 3 meg.
\$8.95. Post 20p.



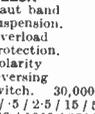HIKIOI MODEL 700X
100,000 O.P.V. Overload
protection. Mirror scale.
3/6/1-2/1-5/3/6/12/30/60/
120/300/600/1200V DC
1.5/3/6/12/30/60/150/300/600/
1200 V. A.C.
15/30μA/3/6/30/60/150/300mA
6/12 AMP. DC. 2K/200K/2
Meg/20 Meg ohm -20 to
+63dB. \$13.50. P. & P. 20p.



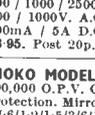MODEL C-7080 EN
Giant 6" mirror scale.
20,000 o.p.v. 0 / 25 / 1 /
2.5 / 10 / 50 / 250 / 1000 /
5000V. D.C. 0 / 2.5 / 10 /
50 / 250 / 1000 / 5000V.
A.C. 0 / 50μA / 1 / 10 / 100 /
500mA / 5 D.C. amp. D.C.
0 / 2K / 200K / 20 meg
-20 to +50 dB.
\$13.95. Post 35p.



U4312 MULTIMETER
Extremely sturdy instrument for general
electrical use. 667 o.p.v.
0/3/1-5/3/30/60/150/300/
600/900 VDC and 75V. V.
0/3/1-5/7.5/30/60/150/300
600/900 VAC.
0/300μA/1-5/6/15/60/150
600mA/1-5/5 AMP. D.C.
0/1-5/15/60/150/600mA/
1-5/5 AMP. A.C.
0/200 Ω/3K/30K Ω.
Accuracy DC 1%. AC 1.5%.
Knife edge pointer, mirror scale. Complete
with sturdy metal carrying case, leads and
instructions. \$9.50 plus P. & P. 25p.

Selected TEST EQUIPMENT

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring
A, B and ICO. NPN or PNP.
Equally adaptable for check-
ing diodes. Supplied complete
with instructions, battery and
leads.
\$7.50. Post 20p.



TE-16A TRANSISTORISED SIGNAL GENERATOR

An inexpensive instrument
for the handyman.
Operates on 9v battery.
Wide easy to read scale.
800kHz modulation.
5 1/2 x 5 1/2 x 3 1/2 in.
Complete with instruc-
tions and leads. \$7.97. Post 25p.



A new portable
bridge offering ex-
cellent range and
accuracy at low
cost. Ranges: R.
10 1/11 meg Ω
6 Ranges ± 1%
L1 μ H - 111
6 Ranges ± 2%
HENRY'S 0 Ranges 2 to 20. C.10pF ± 1110mPd
1:1/100. G Ranges ± 1%. Bridge voltage at
1,000 cps. Operated from 9 volts. 100μA.
Meter indication. Attractive 2 tone metal
case. Size 7 1/2 x 5 x 2 1/2 in. \$20. P. & P. 25p.


Model S-100TR TRANSISTOR TESTER

100,000 o.p.v. mirror scale/
overload protection. 0/12/
-6/3/12/30/120/600 V DC
0/6/30/120/600. V AC. 0/12/
600μA/ 12/300mA/12 AMP
DC. 0/10 K/1 MEG/100MEG.
-20 to +60db. 0-01-2 MFD.
Transistor tester measures
Alpha, beta and Ico. Complete
with batteries, instructions
and leads. \$18.50. P/P 25p.




MODEL 449A IN CIRCUIT TRANSISTOR TESTER

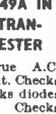Checks true A.C.
beta in/out. Checks
Icbo. Checks diodes
in / out. Checks
SCR, etc. Beta
HI 10 - 500.
LO 2 - 50. Icbo 0-5000μA. 220/240 V A.C.
operation
\$17.50. Post 25p.



TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

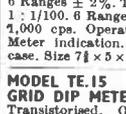
A new portable
bridge offering ex-
cellent range and
accuracy at low
cost. Ranges: R.
10 1/11 meg Ω
6 Ranges ± 1%
L1 μ H - 111
6 Ranges ± 2%
HENRY'S 0 Ranges 2 to 20. C.10pF ± 1110mPd
1:1/100. G Ranges ± 1%. Bridge voltage at
1,000 cps. Operated from 9 volts. 100μA.
Meter indication. Attractive 2 tone metal
case. Size 7 1/2 x 5 x 2 1/2 in. \$20. P. & P. 25p.



MODEL TE 15 GRID DIP METER
Transistorised. Operates as
Grid Dip, Oscillator, Absorp-
tion Wave Meter and Oscil-
lating Detector. Frequency
range 440Kc/s-280Mc/s in
6 colls. 500μA Meter. 9V
battery operation. Size 180 x
80 x 40mm.
\$12.50. Post 20p.

KAMODEN HM. 720B F.E.T. V.O.M.

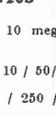Input impedance 10 meg
ohms.
Ranges:
0 / 25 / 1 / 2.5 / 10 / 50 /
250 / 1000V. D.C.
0 / 2.5 / 10 / 50 / 250 /
1000V. A.C.
0 / 25μA / 2.5 / 25 / 250
MA D.C.
-20 to +62dB
0/5K/50K/500K/5meg/
500meg ohms.
\$14.95. Post 30p



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18 x 200,000 Hz; Square 18 x 50,000 Hz
Output max.
+10 dB.
(10 K ohms)
Operation in-
ternal batteries
Attractive 2-
tone case 7 1/2
x 5 x 2 1/2 in.
Price \$17.50.
Carr. 17p.



MODEL MG-100 SINE SQUARE WAVE AUDIO GENERATOR
Range 19-220,000Hz
Sine Wave 19-200,000Hz
Square Wave 19-200,000Hz
Output Sine or Square
Wave 10V. P. to P.
Size 180 x 90 x 90mm.
Operation 220/240V. A.C.
\$17.50. Post 37p


MODEL L-55 FET V.O.M.

Input impedance 10 meg
ohms. 0 / 3 / 1.2 / 6 / 30 /
120 / 600V. D.C. 0 / 3 /
12 / 60 / 120 / 600V. A.C.
0 / 120μA / 120mA D.C.
0 / 1K / 100K / 10 meg
/ 100 meg ohms
\$15.97. Post 15p.




CI-5 PULSE OSCILLOSCOPE

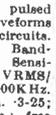For display of pulsed
and periodic waveforms
in electronic circuits.
VERT. AMP. Band-
width at 100KHz VRMS/
mm. -1.25; HOR. AMP. Bandwidth 600KHz.
Sensitivity at 100KHz. V. RMS/mm. -3.25;
Preset triggered sweep 1-3,000μsec.; free
running 20-200,000Hz in nine ranges.
Calibrator pipe. 220 x 360 x 430mm.
115-230V. AC operation.
\$39.00. Carr. paid.



TO-3 PORTABLE OSCILLOSCOPE

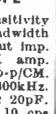3in. tube. Y amp. Sensitivity
0.1v p-p/CM. Bandwidth
1-5 cps-1.5 MHz. Input Imp.
2 meg Ω 25pF X amp.
sensitivity 0.9v. p-p/CM.
Bandwidth 1-5cps-800KHz.
Input Imp. 2 meg Ω 20pF.
Time base. 5 ranges 10 cps
300 kHz. Synchronization.
Internal/external. Illuminated
scale 140 x 215 x 330 mm. Weight 13lb.
220/240V. A.C. Supplied brand new with
handbook. \$47.50. Carr. 50p.



MODEL AT201 DECADE ATTENUATOR
Frequency range 0-
200KHz. Attenuator
0-111db step.
Impedance 600 ohms.
Max. input power
30dbm. Size 180 x 90 x 55mm.
\$12.50. Post 37p



TE-65 VALVE VOLTMETER
28 ranges D.C. volts
1.5-1,500V. A.C. volts
1.5-1,500V. Resistance up
to 1,000 megohms. 200/
240V. A.C. operation
Complete with probe and
instructions.
\$17.50. P. & P. 30p.
Additional probes avail-
able: R.F. \$2-12; H.V.
\$2.50.



MODEL U4311 SUB-STANDARD RANGE VOLT AMMETER
Sensitivity 330 ohms/Volt
AC and DC. Accuracy
5% D.C. 1% AC. Scale
length 165mm. 0/300/750μA/
1.5 / 3 / 7.5 / 15 / 30 / 75 /
150 / 300 / 750mA / 1.5 / 3 /
7.5AMP DC 0 / 3 / 7.5 / 15 /
30 / 75 / 150 / 300 /
750mA / 1.5 / 3 / 7.5
AMP AC 0 / 7.5 / 150 /
300 / 750mV / 1.5 / 3 /
7.5 / 15 / 30 / 75 / 150 / 300 / 750V DC
0/750mV/1.5/3/7.5/15/30/75/150/300
/750V AC. Automatic cut out. Supplied com-
plete with test leads, manual and test certifi-
cates. \$49.00. Post 50p.



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE
5 mc/s Pass Band. Separate
Y1 and Y2 amplifiers.
Rectangular 5in. x 4in.
C.R.T. Calibrated trig-
gered sweep from 2 μsec.
to 100 mill-sec. per cm.
Free running time base 50 cps-1 mc/s. Built-
in time base calibrator and amplitude
calibrator. Supplied complete with all
accessories and instruction manual
\$87. Carr. Paid.

G. W. SMITH
& CO (RADIO) LTD.
Also see opposite page
and next two pages

KAMODEN HM.350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and DC current. Amplification factor of NPN, PNP, transistors, diodes, SCR's etc. 4" x 4 1/2" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.




KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1000 Meg-ohms, 500 Volt. Battery operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. £19-95. Post 30p



ARF-300 AM/RF SIGNAL GENERATOR

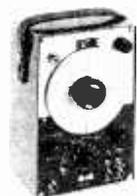

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine / square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. AC. Complete with instructions and leads. £29-95. Post 50p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt. current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2% ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1-999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing. Full scale adjustment against an internal reference voltage. Overload: to 100v. D.C. Input: Fully floating (3 poles). Input power: 110-230v. A.C. 50/60 cycles. Overall size: 5 1/2in. x 2 1/2in. x 8 3/16in. AVAILABLE BRAND NEW AND FULLY GUARANTEED. £35-50. Carr. 50p.



HAND HELD 2-WAY WALKIE TALKIES

Industrial quality in robust metal cases. Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases. 2 channel £52-50 Pair. Post 50p. 3 channel £79-50 Pair. Post 50p. 2 watt.



EMI LOUSPEAKERS

Model 350. 1 1/2" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £27-25 each P. & P. 37p. Model 450. 1 1/2" x 8" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £32-62 each. P. & P. 25p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2" x 9" x 7 1/2". 8 ohms. 8 watt RMS. 16 watt peak. Complete with DIN lead. £12-95 pr. Carr. 50p.

EA.41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2" x 8 3/4" in. £5-97. P. & P. 15p.



UNR-30 RECEIVER

4 Bands covering 550Kc/s-30Mc/s. B.F.O. Built-in Speaker 220/240v A.C. Brand new with instructions. £15-75. Carr. 37p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550Kc/s-30Mc/s. FET 8 Meter. Variable BFO for SSB, Built-in Speaker, Bandspread, Sensitivity Control. 220/240v. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.

SKYWOOD CX203 COMMUNICATION RECEIVER

150-400Kc/s. 550 Kc/s-30Mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter. S Meter. Bandspread, RF Gain. 18" x 9 1/2" x 8 1/2". 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £50. Carr. 50p.



LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400Kc/s. 550 Kc/s-30Mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter. S Meter. Bandspread, RF Gain. 18" x 9 1/2" x 8 1/2". 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £50. Carr. 50p.



TRIO 9R59DS COMMUNICATION RECEIVER

4 band covering 150Kc/s to 30 Mc/s. continuous and electrical bandsread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. S meter. Sep. bandsread dial. 1F frequency 456 Kc/s. audio output 1.5w. Variable RF and AF gain controls 115/250v. A.C. Size: 7" x 13" x 10" with instruction manual. £49-50. Carr. Paid.



HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Inputs 5MU/100MU. Output 50mW. £5-97. P. & P. 15p.



1021 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2-25. P. & P. 15p.



MP7 MIXER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3" Inputs Mics: 3 x 3mV 50K : 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8-97. P. & P. 20p.



HI-FI EQUIPMENT SAVE UP TO 33 1/3% OR MORE


SEND S.A.E. FOR FULL DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



FANTASTIC OFFER!

NIKKO TRM 50 STEREO AMPLIFIER

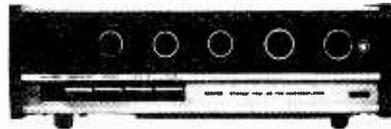17 + 17 watts rms stereo amplifier with inputs for Magnetic and Crystal phono, Tuner, Tape, Aux and Tape Monitor. Outputs for two pairs of stereo speakers and Tape. Stereo headphone socket. Full range of controls including loudness control, scratch filter, etc. Size 13" x 9 1/4" x 3 1/2". Unrepeatable offer—limited stocks!



List price £59-50

OUR PRICE

£39-95

Carriage 50p

AKAI BARGAINS!



AA6300 AM/FM STEREO TUNER AMPLIFIER

20+20 watts rms. FM 88-108 MHz. AM 535-1605 kHz. Dual stereo speaker outputs. Headphone socket. (Rec. List Price £117-46)

OUR PRICE £61-95 P & P 75p

AKAI AA6300 SYSTEM

20+20 watt AM/FM stereo tuner amplifier. Garrard AP76, plinth and cover. G800 cartridge, pair of Mezzo III speakers. Carriage & Pack. £2-00

OUR PRICE £132-50

WHARFEDALE LINTON SYSTEM

Wharfedale Linton Amplifier, Linton Turntable, pair of Linton 2 speakers and all leads.

OUR PRICE £95-95 Carr. and Ins. £1-25

LINTON RECEIVER SYSTEM £125-00. Carr. & Ins. £1-25.

AMSTRAD 8000 II SYSTEM

Amstrad 8000 II 7 + 7 watt amplifier. BSR MP60, plinth and cover. Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE £45-50 Carr. £1-00

NIKKO TRM.50 SYSTEM



NIKKO TRM50 17 + 17 watt rms. stereo amplifier Garrard AP76, plinth & cover. Goldring G800E cartridge, pair of Linton 2 speakers and all leads.

OUR PRICE £93-95

Carr. and Ins. £1-50

LEAK DELTA 30 SYSTEM



Leak Delta 30 stereo amplifier, Goldring GL75, plinth, cover and G800 cartridge. Pair of Leak 150 speakers and all leads.

OUR PRICE £109-95

Carr. and Ins. £1-50

TELETON SAQ206B SYSTEM



Teleton SAQ206B 8 + 8 watt Amplifier, BSR MP60, plinth & cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE £51-50

Carr. £1-50



B.S.R. TD85 8-TRACK STEREO TAPE PLAYER DECK Integrated preamps (output 125 mV) to feed into any stereo amplifier. Automatic and manual programme selector. 4 pole synchronous motor. 210/240 V. £12-75 Post 50p

G. W. SMITH & CO (RADIO) LTD. Also see previous pages and opposite page

SINCLAIR IC-12



List Price £2-98
OUR PRICE £1-80
 P. & P. 10p

SINCLAIR PROJECT 60 PACKAGE DEALS



2x230/Stereo 60/PZ5. £15-95. P. & P. 37p.
 2x230/Stereo 60/PZ6. £18-00. P. & P. 37p.
 2x250/Stereo 60/PZ8. £20-25. P. & P. 37p.
 Transformer for PZ5 £2-97 extra.
 Active Filter Unit. £4-45 extra.
 Pair of Q16 Speakers. £10-97. P. & P. 37p.
 Sinclair Project 605. £20-97. P. & P. 37p.
 All other Sinclair Products in stock.

TRANSISTORISED FM TUNER



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £5-95. P. & P. 12p. Stereo multiplex adaptors £4-97.

AUDIOTRONIC ACR 3500 CAR RADIO



Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker, mounting brackets and instructions.
 OUR PRICE **£5-25** P. & P. 50p

AUDIOTRONIC ACP-8 8 TRACK CAR PLAYER



Attractive black and silver finish. 12v neg. earth. Slider controls for volume, tone and balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.
 ONLY **£12-50** P. & P. 40p

TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms.
 £1-97. P. & P. 15p.

HOSIDEN DH-085 DE-LUXE STEREO HEADPHONES



Features unique mechanical 2 way units and fitted adjustable lever, controls 8 ohm impedance 20-20,000cps. Complete with spring lead & stereo jack plug
 £7-97. P. & P. 12p.

TE-1035 STEREO HEADPHONES



Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance 25-18,000 Hz. With lead and stereo jack plug. ONLY £1-97. P. & P. 12p.

ROTEL BARGAINS!

All brand new and guaranteed



RA210 Amp	£22-50
RA310 Amp	£34-95
RA610 Amp	£51-95
RX150 Receiver	£36-95
RX200 Receiver	£46-50
RX400 Receiver	£57-95

P. & P. 50p extra any item.

ROTEL RA210 SYSTEM



8 + 8 watt amplifier, BSR MP60, plinth and cover, G800 cartridge, pair of Medway T138 speakers and all leads.
 OUR PRICE **£54-50** Carr. & Ins. £1-25

ROTEL RX150 SYSTEM



AM/FM 71 + 71 watt stereo tuner amplifier, BSR MP 60, plinth and cover, G800, pair of Denton 2 speakers and all leads.
 OUR PRICE **£76-50** Carr. & Ins. £1-25

MONATONE 6750 SYSTEM



AM/FM 4 + 4 watt stereo tuner amplifier, Garrard 2025 T/C, plinth and cover, stereo cartridge, pair of matching speakers and all leads.
 OUR PRICE **£30-50** Carr. £1-00

SPECIAL OFFER! ROTEL RH700 STEREO HEADPHONES



20-20,000Hz. 8-16 ohm. (List £9-95). OUR PRICE **£8-75**. P. & P. 25p.

KOSS SP.3XC STEREO HEADPHONES



Response 10-15,000Hz. Impedance 4-6 ohms. Brand new. Boxed & fully guaranteed. (List £9.50). OUR PRICE **£8-50**. P. & P. 25p.

HOSIDEN DH-025 STEREO HEADPHONES



Wonderful value and excellent performance combined. Adjustable head-band. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug. ONLY **£2-37**. P. & P. 12p.

AKAI BARGAINS



CASSETTE (P. & P. 50p)

CS35D Deck	£44-95
CS35 Recorder	£57-75
CS83/CSS8 Speakers	£67-95
GX C40D Deck	£57-75
GX C40 Recorder	£87-95
GX C40T Deck/Receiver	£101-25
GX C45 Deck	£78-25
GX C46D Dolby Deck	£84-30
GX C48 Recorder	£90-75
GX C60D Deck	£87-65
GX C63D Dolby Deck	£93-40

CARTRIDGE (P. & P. 50p)

CR81 Deck with amps.	£86-20
CR81D Deck	£54-10
CR81T Recorder/Receiver	£93-70
CR8088 4 channel Recorder	£114-25
CR8088 4 channel Recorder	£94-95

TAPE (P. & P. 75p)

4000DS Deck	£59-95
4000DS Recd Cover	£3-95
1721L Recorder	£80-35
X201D Deck	£82-50
X201D Deck	£105-20
GX220D Deck	£123-95
GX221D Deck	£138-40
GX280D	£196-50
GX370 Deck	£211-50

TAPE/CASSETTE (P. & P. 750)

GX1900D Deck	£144-50
---------------------	---------

TAPE/CARTRIDGE (P. & P. 75p)

X1810D Deck	£138-40
--------------------	---------

TAPE/CASSETTE/CARTRIDGE (P. & P. 75p)

X2008D Recorder	£180-75
------------------------	---------


MICROPHONES (P. & P. 50p)

ADM 11 Dynamic (pair)	£7-50
------------------------------	-------

RECEIVERS (P. & P. 75p)


AA6300 20 + 20 watt	£81-95
AA8030 25 + 25 watt	£92-50
AA8080 40 + 40 watt	£117-50
AA8500 65 + 65 watt	£150-50

DOLBY SYSTEM NOISE REDUCTION UNIT

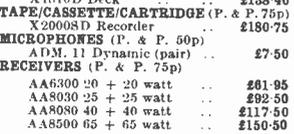

Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 15kHz ± 1dB 19kHz -35dB. Size 15 1/2" x 9" x 3 1/2". AC 200/250V.
 OUR PRICE **£32-50** Carr. 50p.

LOW NOISE TAPE CASSETTES

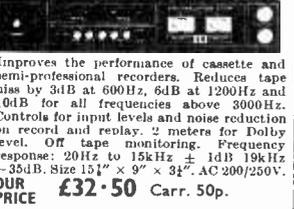

Top quality in library cases

C60	£1-29	£2-53	£5-99
C90	£1-85	£3-62	£8-59
CU20	£2-29	£4-48	£10-63

P. & P. Post Post
 15p Free Free

TAPE HEAD CLEANER 30p each.

SPECIAL OFFER OF NEAT EQUIPMENT

(Buy now while stocks last)

PICK UP BARGAIN! NEAT G30J



Identical specification to Neat G30 static balance arm but two-tone chrome and black finish. Complete with head shell, pick up rest and plug-in phono leads. Brand new and fully guaranteed.
 OUR PRICE **£7-50** P. & P. 25p

Neat G30B Arm £8-40. P. & P. 25p.
 Neat V70 Cartridge (Original Pack) £2-15
 Neat V70 Cartridge (Bulk Pack) £1-50
 Neat V70E Cartridge £3-35
 Neat V60M Cartridge £2-15
 P. & P. 12p extra

RECORD DECKS

Carriage and Packing 50p

B.S.R. McDONALD

CL14 Mini	£3-95
CL29 Mono	£5-50
CL37	£7-00
510/TPD1	£13-95
610	£9-90
610/TPD1	£14-85
710	£19-20
810	£24-50
710/810 Plinth and Cover	£8-35
MP60	£7-85
MP60/G800	£10-25
MP60/TPD1	£12-60
MP60/TPD2	£11-25
HT70	£10-97
HT70/G800	£15-95
HT70/TPD1	£15-95

CONNOISSEUR

BD1 Kit	£8-65
BD1 Chassis	£10-75
BD1/SAU2/Plinth/Cover	£26-15
BD2/SAU2/Chassis	£21-15
BD2/SAU2/Plinth/Cover	£26-75

GARRARD

2025 T/C Stereo	£6-40
SP25 III	£8-50
SP25 III/Acos GP104 Ceramic	£8-50
SP25/MP26	£13-90

PLINTHS & COVERS

Carriage & Packing 50p

Budget SP25 etc.	£2-95
Budget AP76/Zero 1008	£3-85
Budget B.S.R.	£2-95
SME 2000 System	£26-40

RECORD DECK PACKAGES

Carriage & Packing 75p

Complete unit with stereo cartridge ready wired in plinth with cover.

GARRARD

2025 T/C/9TAHCD	£10-85
SP25 III/G800	£15-95
SP25 III/M44-7	£17-25
SP25 III/M44-7	£16-75
SP25 III/M35E	£18-25
SP25 III Module/M75-6	£18-99
AP76/G800	£23-95
AP76/G800E	£25-95
AP76/M445	£24-85
AP76/M35E	£25-25
AP76/M75ED	£31-70
AP76/M75EJ	£27-85
AP76 Module/M75-6	£28-95
AP96 Module/M75-6	£30-40
ZERO 1008 Module/M93E	£41-85

B.S.R. McDONALD

210/8C7M	£8-85
MP60/G800	£15-50
MP60/TPD1/G800	£15-20
MP60/M44-7	£16-75
HT70/TPD1/G800	£18-60

GOLDRING

GL75/G800	£32-25
GL75/G800E	£34-95

GOODMANS

TD100/G800 Teak	£42-95
TD100/G800 White	£44-75

LEAK

Delta/M75-6	£43-95
--------------------	--------

PHILIPS

GA105/GP200	£13-80
GA100/GP200 Teak	£20-00
G1212/GP400	£45-25

PIIONEER

PL12D (Less cartridge)	£29-60
PL15C (Less cartridge)	£41-25
PL14D (Less cartridge)	£39-25
PL50 (Less cartridge)	£38-90
PLA1	£102-75
PLA35	£68-60

WHARFEDALE

Linton/M44-7	£23-70
---------------------	--------

WARRANT INFORMATION

All prices are subject to 10% V.A.T. (10p in £)
 This must be added to total value of goods ordered (including postage/carriage) and enclosed with all mail orders. PLEASE PRINT NAME AND ADDRESS CLEARLY.

CREDIT TERMS FOR CALLERS
 ACCESS & BARCLAYCARD WELCOME

G.W.SMITH & CO (Radio) LTD

Personal Callers Welcome - All Branches Open 9-6 Mon. to Sat.

10 TOTTENHAM CT. RD. LONDON, W.1
 22 TOTTENHAM CT. RD. LONDON, W.1
 287/288 TOTTENHAM CT. RD. LONDON, W.1
 3 LIBLE STREET, LONDON, W.C.2
 34 LIBLE STREET, LONDON, W.C.2
 311 EDGWARE ROAD, LONDON, W.2

Tel 01-837 2232
 Tel 01-838 3715
 Tel 01-850 0870
 Tel 01-837 6260
 Tel 01-437 8156
 Tel 01-262 0387

All Mail Orders to
 1112, Paddington Green
 London W.2
 Tel 01 262 6562



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 65p. Postage 20p for first one then 10p for each one ordered.

MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely 65p each or 5 for £2.50. Send for list of titles. We can't repeat when sold out.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, 35p each, £3.50 doz.



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system, 88p each or 10 for £3.42.



12 VOLT 1/4 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2.00, plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps — maximum load 250W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on lead. Silicon rectifiers and smoothing by 3,000mF. Price £5.75 plus 65p post.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole change-over relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. (100% British Make. Unused. Size approx. 1 1/2" x 1". Open construction.

Single pole 25p each 10 for £2.25
Treble pole 35p each 10 for £3.15

DOOR INTERCOM

Know who is calling and speak to them without leaving bed or chair. Output comprises microphone with call push button, connectors and master intercom. Simply plugs together. Originally sold at £10. Special snip price £3.50 plus 20p postage.



TYPE 25 RELAYS

These are miniature relays. Size approx. 1 3/16" high x 1 1/4" in. wide x 1 in. deep, 4 change over silver/gold contacts. Contact rating lamp 100V. D.C. Fitted with a plastic cover. Coil operates approx. 250mV. P.C. Available with the following coils:

28 ohm for 1-2.5v. 45 ohm for 4-7.5v. 52 ohm for 4-9.6v. 90 ohm for 5.5-11.5v. 130 ohm for 10-15v. 530 ohm for 17-36v. 1250 ohm for 27-44v. 2500 ohm for 31-65v. 5800 ohm for 27-44v. 75p each, 10 for £6.75. Also one with 16,500 ohm coil but this has only 2 heavy duty change-over gold contacts. Price 85p.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 20p each £1.80 for ten, your assortment.



REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature, 1" long x approximately 1/4" diameter. Will make and break up to 4A up to 300V. Price 13p each, £1.20 dozen.

Standard, 2 1/2" long x 1/4" diameter. This will break currents of up to 1A, voltage up to 250V. Price 10p each, 90p per dozen.

Flat. Flat type, 2 1/2" long, just over 1/4" thick, flattened out, so that it can be fitted into a smaller square or a larger quantity may be packed into a square solenoid. Rating 1A 200V. Price 30p each, £3 per dozen.

Small ceramic magnets to operate these reed switches 9p each, 90p dozen.

Dry Reed Relays. Solenoids on moulded bobbins within magnetic shields—printed circuit, or panel mounting.

Ref.	Coil Resistance	Reed Switches	Price
71005	2 K	1 normally open	25p
81916	5 K	1 normally open	25p
		1 normally closed	75p
05003	4 K	1 normally open	25p
62040	1500 & 500 ohms	1 normally open	35p
Multiple Reed Relay. Ref. 53001. Contains 13 normally open reeds within a solenoid. Operates on 600 mW. Coil resistance 9K ohms. Price £1.95 each.			
Multiple Reed Relay. Ref. 631. 2 normally open 1 normally closed coil resistance 30 ohms. Price 75p.			




MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output 65p. Model 1172 750mW power output 85p. Model EP9000 4 watt power output £1.85. EP9001 twin channel or stereo pre amp. £1.60 10% discount if 10 or more ordered.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing fux smoke when soldering etc., etc. A real bargain at £1.85.

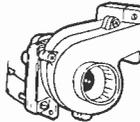

GOOD COMPANION I.C. VERSION

We can now offer these again in I.C. version using Ferranti ZN414 and Mullard AF Module 1172. Cabinet size approx. 11in. wide x 8in. high x 3in. deep. Complete assembly instructions—Excellent tone wood cabinet £5.75 + 25p post & ins.




MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January '73. All electronic parts £2 post paid.

THIS MONTH'S SNIP 10 AMP DIMMER/CONTROLLER

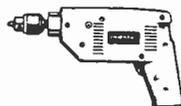For the control of lighting of stage or studio or portable equipment in workshops etc. This has socket outlets each controlled by 5 AMP Solid State regulator. Also fitted with master switch fuse and neon indicator and terminating with 6 feet of flex. Overall length 17in. 3 1/4in. x 1 1/4in. deep. £7.50, plus 25p P. & P.



PORTABLE ELECTRIC DRILL

Very superior quality made by a famous Dutch Toolmaker. Model No. ASM 830. 300w - 2 speed 2200/3000. With 3/8" chuck and chuck key, also separate side handle and hammer facility for dealing with concrete, etc. An equivalent British made drill would cost £15-00. £9.95—similar model but without the hammer attachment £7.85. Have either model on approval for 7 days.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp. sockets in metal box to take standard 13 amp. fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2.25 plus 20p post and ins.



CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for an improved and even more efficient version (Practical Wireless, June). Price £5.95 plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board etc. £6.95.

ELECTRONIC IGNITION


24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. £2.50 post and ins, 25p. Additional time contacts 60p pair.



THYRISTOR LIGHT DIMMER

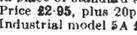For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95, plus 20p post and insurance. Industrial model 5A £3.



BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of these are zinc carbon types but also mercury manganese-nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £2.25 plus 20p postage.



SPIT MOTOR

200-250v. Induction Motor, driving a carter gear box with 1 1/2" of output drive shaft running at 5 revs per minute. Intended for roasting chickens, also suitable for driving models—windmills, coloured disc lighting effect, etc. etc. £1.85 plus 20p post and insurance.



DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50, 13p post and p. Made up model also available. £2.50.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 5v. 12 volts for up to 600mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip only £1.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24" x 18" £1.40
13" x 10" £1.00




PP3 BATTERY CHARGER

Almost 3 times the life can be obtained from PP3 battery if you re-charge it from the mains. This ready to use charger with instructions only 50p.

15A ELECTRICAL PROGRAMMER

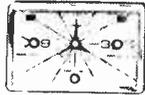Learn in your sleep: Have radio playing and kettle boiling as you awake on switch on lights to ward off intruders — have a warm house to come home to. All these and many other things you can do



by famous maker with 15 amp. on/off switch. Switch on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £1.95 + 20p p. & p. or with glass front, chrome bezel, 75p extra.

BAKELITE INSTRUMENT CASE

Size approx. 9 1/2" x 3 1/2" x 2" deep with brass inserts in four corners. This is a very strong case suitable to house instruments and special rigs, etc. Price 45p each. Fixolin lid 10p extra.



TELEPHONES

Complete as illustrated. Save your legs, time and temper, simply by putting in some telephones. Ex. G.P.O. not new — but guaranteed in good condition and serviceable. Supplied with diagram and instructions showing how to connect. Price £1 each + 50p post or 2 for £2.50 post paid. Also available separately, dials and handsets 50p each + 20p post.



RADIO ALARM CLOCK, LAMP DIMMER, INTERCOM-AMPLIFIER, LIGHT POWERED RADIO, BABY ALARM, TWO TONE DOOR BELL, TAPE TUNER, WATER LEVEL DETECTOR. To receive kits for these and other projects featured in this issue send S.A.E. for PW Kits List.

ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1" 8p each, 10 for 72p.



SLIDE SWITCHES

Slide Switch, 2-pole changeover panel mounting by two 9B.A. screws. Size approx. 1in. x 1in. rated 250V 10amp. 6p each, 10 for 54p, 100 for £5.10, 500 for £24. Ditto as above but for printed circuit 5p each, 10 for 45p, 100 for £4.25. Sub Miniature Slide Switch. DPDT 19mm (1 1/2in approx.) between fixing centres. 18p each or 10 for £1.08, 8P Change over spring return 250V 1 amp. 10p.



SPRING COIL LEADS

as fitted to telephones, 4 core 15p each, 10 for £1.35, 3 core 10p each 10 for 90p.



V.A.T. Please add V.A.T. 10% on total order after April 1st.

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

BSR LATEST SUPERSLIM STEREO & MONO



Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 18 1/2 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in.

with STEREO and MONO XTAL £8-25 Post 25p

ANOTHER RCS BARGAIN! 4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watts output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make.

Size 8" wide x 4" deep x 3" high. Price £5-95 post 25p.

Suitable 7" x 4" Speaker £1-00.

RCS DE-LUXE 3 WATT AMPLIFIER

Ready made, tested. Printed circuit, 3 watts output. Tone and volume controls. Complete with output valve and rectifier, two knobs, and high performance loudspeaker. Double wound fully isolated mains transformer. A.C. mains 200/250V. Response 50-12,000 cps. Sensitivity 300mV. £4 Post 25p

BSR SINGLE PLAYER



Heavy duty 4-speed motor with separate pick-up arm fitted LP 78 stereo comp. £5-50 Post 25p

HI-FI PICK UP CARTRIDGES

Stereo/Mono VTA £2-50; GP84 £2-50; GP88 £2. Sapphire Mono GP91 £1-50; Powerpoint LP78 60p.

GARRARD DECCA DISCO DECK



Single play Stereo/Mono Deram transcription head and arm. Four speeds. 10 1/2 in. turntable. Anti-rumble filter. Bias compensation. Laboratory motor.

SPECIAL PRICE £18-50 Post 25p

METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R. Most will play with cover in position. 12", 14", 7 1/2 in. Covered in black leatherette. Post 35p

£4-95

ALSO AVAILABLE IN SOLID NATURAL MAHOAGANY WAX POLISHED FINISH—AT SAME PRICE

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH



Single pole two-way Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights etc. Variable knob Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes or 0 to 6 hours. Fully insulated. Makers last list price £4-50. Brand new and fully guaranteed.

OUR PRICE £1-50 P. & P. 15p or £3 pair. (STATE TYPE A OR B WHEN ORDERING.)

BLANK ALUMINIUM CHASSIS

18 s.w.g. 2 1/2 in. sides. 6 x 4 in. 45p; 8 x 6 in. 55p; 10 x 7 in. 65p; 12 x 8 in. 85p; 14 x 9 in. 90p; 16 x 6 in. 80p; 12 x 3 in. 50p; 16 x 10 in. £1.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 9p; 8 x 6 in. 11p; 14 x 8 in. 16p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 23p; 16 x 6 in. 28p; 14 x 9 in. 34p; 12 x 12 in. 40p; 16 x 10 in. 50p.

RADIO BOOKS (Post 3p)

- Handbook of transistor equivalents 40p
- Handbook of Simple Transistor Circuits 35p
- Master colour code folder 15p
- Boys' book of crystal sets and simple circuits 18p
- Universal tram motor speed indicator 3p
- Fish fidelity loudspeaker enclosures 40p
- Practical Stereo handbook 30p
- Sound and Loudspeaker Manual 50p
- Coil design and construction manual 30p
- Radio, TV and electronics data book 25p
- Handbook of tested Transistor Circuits 40p
- 38 Practical Tested Diode Circuits 35p
- Hi-Fi P.A. and Doo Amplifier Design 75p
- Practical Transistor Novelty Circuits 40p
- Resistor colour code calculator 10p
- Engineers' and Machinists' reference tables 20p
- TV fault finding 50p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2-20 Post 15p Details S.A.E. Size 3 1/2 x 1 1/2 in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300 V.C. operation. Size 1 1/2" x 1 1/2" x 1". Response 25 c.p.s. to 25 Kc/s, 25 db gain. Full use with valve or transistor equipment. 99p Full instructions supplied. Details S.A.E.

MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12v 90p
250-0-250 80 mA. 6-3 v. 3-5 a. 6-3 v. 1 a. or 5 v. 2 a. £2-50
350-0-350 80 mA. 6-3 v. 3-5 a. 6-3 v. 1 a. or 5 v. 2 a. £3-00
300-0-300 v. 120 mA. 6-3 v. 2 a. C.T.; 6-3 v. 4 a. £2-25
MINIATURE 200 v. 20 mA. 6-3 v. 1 a. 2 1/2 x 2 1/2 in. 75p
MIDGET 220 v. 45 mA. 6-3 v. 2 a. 2 1/2 x 2 1/2 in. 90p
HEATER TRANS. 6-3 v. 3 a. 60p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2-25
1 amp., 6, 8, 10, 12, 18, 20, 24, 30, 35, 40, 45, 60 £2-25
2 amp., 6, 8, 10, 12, 18, 15, 20, 24, 30, 35, 40, 45, 60 £2-25
3 amp., 6, 8, 10, 12, 18, 20, 24, 30, 35, 40, 45, 60 £2-75
5 amp., 5, 8 and 18V £1-00
5 amp., 5, 8 and 18V £1-20
3 amp., 3, 5, 8, 10, 13 and 5-0-5V £1-30
5 amp., 3, 5, 8, 10, 13 and 5-0-5V £1-50
AUTO TRANSFORMERS. 115v to 250v or 230v to 115v. 150w. £2-25; 500w. £2-50; £10; 1000w. £16.
CHARGER TRANSFORMERS. Input 200/250V. Output for 6 or 12v. 1 1/2 amp. £1-50; 2 amp. £1-80; 4 amp. £2-50
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp. £2; 4 amp. £4; 5 amp. £4-50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.
LUCAS 2DS50 Full wave Bridge 70v. 5 amp. 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240v. Secondary 0-240v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with air feet. £10 Carr. Famous make. (Value £19) OUR PRICE 50p Can be used as 800 watt auto transformers 600-110V.

NEW TUBULAR ELECTROLYTICS CAN TYPES

2/350V 14p	250/25V 14p	50+50/350V 35p
4/350V 14p	500/25V 20p	60+100/350V 55p
8/450V 14p	1000/25V 35p	32+32/250V 18p
16/450V 18p	1000/50V 47p	32+32/450V 33p
32/450V 20p	8+8/450V 18p	350+50/325V 50p
25/25V 10p	8+16/450V 20p	32+32+32/350V 43p
50/50V 10p	16+16/450V 25p	100+50+50/350V 48p
100/25V 10p	32+32/350V 25p	

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 15, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 85p.
5000mF 6V 25p; 12V 42p; 25V 70p; 35V 85p; 50V 95p.

CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2p to 5000pF, 4p. FERAPIC 350V-0.1 caps 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%, 2.2-500pF 8p; 560-2,200pF 10p; 2,700-5,600pF 20p; 6,800pF-0.01, mid 30p each. TWIN GANG. "0-0" 208pF+178pF, 65p; Slow motion drive 385pF+385pF with 25pF+25pF, 50p; £1-60. 500pF standard 45p; small 3-gang 500pF £1-60. SHORT WAVE SINGLE. 10p, 30p; 25pF, 65p; 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers. 50p each

Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS. 250V AC/DC Amber, 20p. RESISTORS. 1/2 w., 1 w., 20%, 1p; 2 w. 5p. 10 to 10M. HIGH STABILITY, 1 w. 2%, 10 ohms to 6 meg., 10p. Ditto 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt, 10 ohms to 100K, 10p each; 2w 5 ohm to 8-2 ohms 10p. TAPE OSCILLATOR COIL. Valve type, 35p.

WEYRAD P50 - TRANSISTOR COILS

RA2W Ferrite Aerial. 72p
Osc. P50/LAC 38p
I.F. P50/200 470 kc/s. 35p
3rd I.F. P50/300 35p
P51/I or P51/S 35p
P50/SV 38p
Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 20p.
Spare Cores 3p
Driver Trans. LFDT4. 68p
Printed Circuit, PCA1. 68p
F.B. Tuning Gang 65p
Weyrad Booklet 10p
OPT1 1000mF 68p

VOLUME CONTROLS 80 Ohm Coax 4p yd.

BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1-40; 60 yd. £2.
FRINGE LOW LOSS 10p yd
Ideal 625 and colour. p yd
1 1/2 inch DIAMETER WAVELENGTH SWITCHES, 25p. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way, 25p each. 1 p. 1. 2-way, or 4 p. 2-way, or 4 p. 3-way, 25p.
TOGGLE SWITCHES, sp. 14p; dp. 22p; dp. dt. 22p.
Sub-miniature, sp. 30p; dp. 37p; dp. dt. 45p.

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 15p.

RADIO COMPONENT

Illustrated Colour Brochure, Radio Books & Component Lists 10p. Written guarantee.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters. £4-50
And crossover, 10 watt, State 3 or 8 or 15 ohm. As illustrated. Post 25p

With flared tweeter cone and ceramic magnet, 10 watt. £2-75
Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p

TEAK CABINET 18 x 10 x 9 in. Modern Design £5-50

Post 25p

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns, Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 24-00. Suitable Tweeter £2-00.

£4

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt, 3 ohm or 15 ohm models. £1-90 Post 10p
Crossover 95p.

GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps. £4-50

LOUDSPEAKERS P.M. 3 OHMS. 7 1/2 in. £1 25; 6 in. £1 50; 8 x 5 in. £1 60; 8 in. £1 75; 10 x 6 in. £1 90; 10 in. £2-00. SPECIAL OFFER: 8 ohm, 2 1/2 in. £1. 2 1/2 in. 35 ohm, 2 in.; 3 in.; 5 in. 25 ohm, 2 1/2 in. dia.; 3 in. dia.; 15 ohm. £1 TYPE 3 1/2 in. dia.; 5 in. /6 x 4 in.; 7 x 4 in.; 8 x 8 in. £1 TAPE 3 ohm, 2 1/2 in. 2 1/2 in. 3 1/2 in. 5 in. dia. 6 x 4 in., 8 ohm, £1-50. RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. diameter 4 watt; 10 in. diameter 5 watt; 12 in. diameter 6 watt, 3 or 8 or 15 ohm models £2-20 each. Post 15p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kc/s, 8W 8 ohm or 15 ohm £1-95. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £2. TWO-WAY 3,000 c.p.s. CROSSOVERS 8, 8 or 15 ohm 95p.

FM/VHF TUNING HEART

88 to 108 M/Cs British made. 2 Transistors ready aligned—requires 10-7 M/Cs IF. Complete with tuning gang. Connections supplied but some technical experience essential. OUR PRICE £3-95

VALVE OUTPUT TRANS. 25p.
MIKE TRANS. mv metal 100-1 £1-25.
5 WATT MULTI RATIO. 3, 8 and 15 ohms, 80p.
PUSH-PULL VALVE OUTPUT TRANSFORMERS. 50 watt £2-50 100 watt £12-50

STEREO / MONO HEADPHONES



New Model with new type alder volume controls. Stereo/Mono switch. 8 ohms. £10.
High Quality with tweeters and volume controls. 8 ohm. £7.
Budget Model. 8 ohm. £3-25.
HEADPHONE JUNCTION BOX with switch £1-75.
Mono Stethoscope. 8 ohms. 65p.
EAR PIECES. Crystal. 25p.
Magnetic. 25 ohms. 18p.
Magnetic. 250 ohms. 23p.
ACOS. 1000 ohms. 53p.

BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 9 1/2 x 6 1/2 in. Pre-aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100uV input. Full instructions for any FM Tuner. Some technical experience essential. £6-50 Post 15p

DIPLO LEFT AERIAL £1-50. CABLE 4p yard.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET SOCKETS, SURFACE OR FLUSH 25p. BALANCED TWIN RIBBON FEEDER 300 ohms, 5p yd. Magnetic. 14p. open circuit 14p. closed circuit 25p. Chrome Lead Socket 45p. Phono Plug 5p. Phono Socket 5p. JACK PLUGS 84d. Chrome 15p; 3-5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 8p; CANS 5p.

E.M.I. WOOFER AND TWEETER KIT

£5.75 THE PAIR. Post 25p.
(Available separately.
Woofer 24 25; Tweeter
£1 90).

Comprising a fine example of a Woofer 10 1/2 - 6 1/2 in. with a massive Ceramic Magnet, 440z. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condensers and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps
SUITABLE ENCLOSURE 20 13 9 in.
MODERN DESIGN. TEAK WOOD FINISH.



£9.90
Post 25p

8in. or 10in. ELAC HI-FI SPEAKER



Dual cone plasticised roll surround. Large ceramic magnet, 50 18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts. **£3.75**
10in. model. 12 watts music power. Post 25p

TEAK VENEER SPEAKER CABINET

Fluted Wood Front

MODEL "A" 20 13 9 in.
For 12in. dia. or 19 Post
10in. speaker. 25p

MODEL "B" 16 10 8 in.
For 13 8in. or 15 Post
8in. speaker. 25p

MODEL "C" 16 8 6 in.
For 8 5in. or 14 Post
6in. speaker. 25p



LOUDSPEAKER CABINET
WADDING 18in. wide. 15p ft.

BARGAIN AM TUNER.

Medium Wave.
Transistor Superhet
Ferrite aerial. 9 volt. **£4.95**



BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output 9 volt battery operated. **£3.95**



STEREO VERSION OF ABOVE

BARGAIN FM TUNER. 88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 5 4 in. **£14.85**



BARGAIN FM TUNER. **£9.85**

As above less cabinet.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9 volt battery operated. **£4.50**



THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V Leaflet S.A.E. **£2.50** Post 15p



WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 in. Operating voltage 200/250V a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes driers, towel rails ideal for airing cupboards. Ideal for anti-frost device for the garage preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1 50)

ALL POST PAID Discounts for quantity

BAKER 12in. MAJOR £10

Post 25p



30-14,500 c.p.s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. NOTE: 3 or 8 15 ohms must be stated.

Module kit, 30-17,000 c.p.s. with tweeter. crossover. 8affe and instructions. **£12.50**
Post 25p

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£8.80**
12in. 25 watt
3, 8 or 15 ohms. Post 25p

GROUP "35" **£9.90**
12in. 35 watt
3, 8 or 15 ohms. Post 25p

GROUP "50" **£22**
15in. 50 watt
8 or 15 ohms. Post 25p



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music 4-way mixing. Response 10 30,000 cps. Matches loudspeakers 8/15ohm. A.C. 200/260V. Separate Treble and Bass controls Guaranteed. Details S.A.E. **£49** Post Free



CALLERS ONLY: DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version. 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. **£55**

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

1/2 in. Round 88p	1 1/2 in. Round 98p	Key "B" for above 8p
3/4 in. Round 75p	1 in. Round 98p	2 1/2 in. Round 22 05
Key "T" for above 5p	1 1/4 in. Round 98p	2 3/4 in. Round 22 30
1/2 in. Round 83p	1 1/2 in. Round 1 05	Key "C" for above 12p
3/4 in. Round 83p	1 3/4 in. Round 1 05	2 1/2 in. Round 44 10
1 in. Round 88p	1 1/2 in. Round 1 10	2 3/4 in. Round 25 25
1 1/4 in. Round 88p	1 3/4 in. Round 1 10	3 in. Round 28 10
1 1/2 in. Round 90p	1 1/2 in. Round 1 25	Key "E" for above 18p
Key "A" for above 5p	1 1/2 in. Round 1 43	1 in. Square with key 1 63
	1 3/4 in. Round 2 1 50	

SLIDER VOLUME CONTROLS

Mono LOG or LINEAR
Size 3 1/2 x 1 1/2 in. with knobs.
5K, 10K, 25K, 50K, 100K, 250K, 500K, 1 MEG, 2 MEG. **65p EACH**



E.M.I. TAPE MOTORS. 120 volts AC each. 1,200 r.p.m. 4 pole or 2 in series 240 volts AC. Size 3 1/2 x 2 1/2 in. (illustrated). Post 15p. **£1**

BALFOURGRAM MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 7/32. Size 2 1/2 x 2 1/2 in. Post 15p. **85p**

E.M.I. GRAM MOTORS. 120V or 240V AC. 2,400 r.p.m. 2-pole 70mA. Spindle 1/2 in. **£1** Post 18p

BAKER HI-FI SPEAKERS

HIGH QUALITY - BRITISH MADE

REGENT

12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models.

£8 Post 25p




DE-LUXE Mk II

12in 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£10 Post 25p

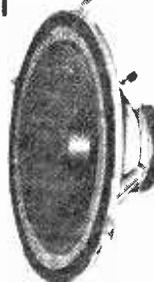

SUPERB

12in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£15 Post 25p




AUDITORIUM

12in. 25 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs Ideal for Hi-Fi and Discos.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£14 Post 25p

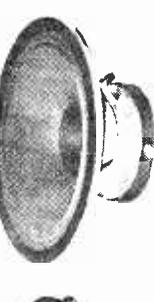

AUDITORIUM

15in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discos, etc. Electric instruments and the home hi-fi.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£20 Post 25p



Hi-Fi Enclosure Manual containing 20 plus details, crossover data and cubic tables. 12p Post Free.

ALL PRICES INCLUDE VAT

SPECIALISTS

(Export: Remit cash and extra postage.)

OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m.


(closed for lunch 1.15 to 2.30)

337 WHITEHORSE ROAD CROYDON

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

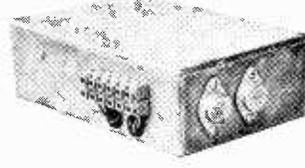PRACTICAL ELECTRONICS
"SCORPIO"
ELECTRONIC IGNITION
SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required. Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision. Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7 1/2in x 4 1/2in x 2in approx. Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P.

DABAR LIGHTING EFFECTS

NEW! NEW! NEW! NEW! NEW! NEW! NEW!



SINGLE CHANNEL
SOUND TO
LIGHT UNIT
STL/1

Single channel "Sound to Light" unit with slider fader controls for audio trigger level and background load dimmer. Switchable for response to High, Mid and Low frequency audio input signals selected by fascia control. D.J. Pulse-Flash push button fitted to fascia for manual flashing of lamp load. Neon load indicator fitted. Constructed on glassfibre printed circuit material with attractive black anodised fascia panel. Input and load connections via Cinch printed circuit connector. Maximum Load 1kW at 250V 50Hz. R.F.I. filtered. Price: £13 each post free U.K.

S.A.E. All Enquiries please



THREE CHANNEL
SOUND TO
LIGHT UNIT
STL/3

Three channel "Sound to Light" unit with slider fader controls for audio trigger level and background load dimmer. An attractive unit with independent control of High, Mid and Low frequency audio trigger levels. Slider fader background or dimmer controls on each channel. D.J. Pulse-Flash push buttons on each channel together with neon load indicators. Constructed on glassfibre printed circuit material with attractive black anodised fascia panel. Input and load connections at rear so unit is ideally suited for mounting into disco-console. Maximum Load 1.5kW per channel at 250V 50Hz. R.F.I. filters incorporated. Price: £38.50 each post free U.K.

Trade enquiries Welcome

PSYCHEDELIC LIGHTING
UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source. The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 carr. paid.

ALL PRICES SUBJECT TO VAT
ADJUSTMENT

DABAR ELECTRONIC PRODUCTS
 98a Lichfield Street, Walsall
 Staffs. WS1 1UZ
 TELEPHONE: WALSALL 34345
 TELEGRAMS: DABELEC Walsall Staffs.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants (Closed Wednesday)



F.M. TUNER AMPLIFIER for 88-102 MHz. Self-powered for 200-250V. a.c. Valves ECC85, EF89, EF80, ECC82, 2 diodes, metal rect. Chassis 10" x 6" x 6". Audio amp. module giving 3W. into 16-ohm. Price £14 (post 50p).

Kit and wiring instra. for 12V windscreen wiper delay control (metal box 3 1/2" x 1 1/2" x 1 1/2" with fixing strap, relay and all compnls. £1.50 (post 20p).

MAINS TRANSFORMERS. 240-250v. input Deduct 10% from total bill for more than one transformer.

- B. Charger 12v. at 1A. 60p (20p)
- E. 250v. at 50 m.a. & 6.3v. at 1 1/2A. 50p (20p)
- H. 90v. at 100m.a. & 220v. at 60m.a. 85p (20p)
- J. 37v. 2A, 24-0-24v. 150m.a. £2.50 (50p)
- K. 250-0-250v. 150m.a. 20v. 1/2A. 15v. 1A. 6.3v. 5A. £2 (50p)
- L. 275-0-275v. 60m.a. 6.3v. 2 1/2A & 6.3v. 1/2A, 75p (25p)
- M. 110v. input; 200-0-200v. 60m.a. 6.3v. 1 1/2A. 60p (25p)
- N. 220v. 60m.a. 6v. 1A. 45p (25p)



STEREO AMPLIFIER 2 x 3W. Printed circuit. Valves E280 & 2 ECL82. Liquidated stock of well-known manufacturer. Front panel 12" x 2". Chassis 9" x 3". Controls on-off, balance, ganged vols, ganged tones; for 200-250v. a.c. Output transformers for 3-ohm speakers. With knobs. Also available for 110v. a.c. Only £8 (p. & p. 50p) 110v. type £5 plus post.

TRANSISTOR RADIO PARTS

Gang capacitors. Min. 180pf+180pf 20p (8p); 150+110pf 30p (10p) 250+250pf direct cover 30p (8p); 250+250p dust cover, slow motion 20p (5p); triple 33pf direct driver with slow motion 60p (10p).

Driver transformers. 2.5 to 1+1 20p (8p); 5.7 to 1+1 20p (8p); Output traas. 2x OC81 to 3-ohm 25p (5p); 2x OC82 to 3-ohm 20p (5p); Edgewise pots (s.p.) 1" dia 2.5K or 5K 15p (5p); 2.5K 1" dia 25p (5p); pots with 5/64" dia spindle 2.5K 1" long spindle 15p (5p) with knob; 2.5K 1 1/2" pin. 15p (5p) with knob; all pots with s. pole switch.

Osc. coil & 3 i.f. trans. replacement for P50 IAC range set of 4 for 80p, post pd.

1 lb (min. 100) high stab resistors 1W to 1W up to 2.5M 50p (10p post); 1 lb mixed tag strips 2 to 12v approx. 75 for £1 (10p post); spring back telephone cable, 10' coil ext. to 6ft, 4-core 15p (10p post) or 7 for £1 post pd.; **AUDIO CONNECTORS.** PLUGS 2-pin speaker 10p; 3-pin DIN 14p; 5-pin 17p; phono 5p; 1" jack 12p; 2.5mm & 3.5mm 8p; METAL phono 12p; 1" 12p; 2.5mm 10p; 3.5mm 12p; **SOCKETS** 2-pin speaker 10p; 3 & 5 pin DIN 9p; phono single 5p; double 7p; treble 10p; 4-way 12p; 1" jack open 15p; moulded 20p; stereo open 20p; moulded 25p; **LINE SOCKETS** speaker, 3-pin & 5-pin DIN 17p; phono metal 12p; co-ax. T.V. plug 8p; car radio plug 6p; either socket 8p. Post 10p any order.

FELSTEAD ELECTRONICS (PW 68)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only—No C.O.D. or Caller service. Charges (Min. 7p) in brackets after all items apply to G.B. and Eire only. Regret orders under 25p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas Orders welcomed.

RECORDING TAPE: Finest quality/value British Nylon available: STANDARD 5" 600ft. 40p, 5" 900ft. 55p; 7" 1200ft. 82p; LONG PLAY 5" 900ft. 55p; 5" 1200ft. 62p; 7" 1800ft. £1.00 (Charges for 5" and 5 1/2", singles 9p, two to four 8p each; five and over 33p the lot. For 7", one or two 11p each reel, 3, 4 and 5 reels 33p the lot, 6 reels and over 39p the lot.) Other sizes and accessories in list. **CASSETTES** in lib cases new type highly improved quality C60 55p, C90 72p, C120 99p (under 5, 9p each; 5 for 17p the lot; any quantity over 5, 28p the lot).

CARTRIDGES all with standard fittings and styli. Stereo-compatible Mono GP91/SC 98p; STEREO GP93 £1.35, Stereo Ceramic GP94 £1.75. (All at 7p each.) Comparatives shown in List, with more types inc. Sonotone 9TAHC, Stereo Ceramic Diamond £1.70 (7p). **DIAMOND STYLUS:** single tip types: Acos GP37, GP59, GP65/67, GP71, BRR TCS/LP/ST; COLLARO O.P. and DC284, GARRARD GC2, GC8, GC810, GCE12, RONETTE BF40, O.P. and T. PHILIPS 3201 (3060), 3065, 3302, 3304), 3010/12/13/16; SONOTONE 1ST/20T ALL AT 38p each (7p). **SAPPHIRE 16p** (7p) **DIAMOND DOUBLE TIP TURNOVER TYPES** (78 sp. on other side). For ACOS GP73, GP91 (for DOUBLES GP93, GP94 etc.) GP918C (for stereo compat. types) GP104 BSR ST4 (3T3, 8T5), 8T9 (8T8), ST12/14/15, SONOTONE 8TA, 9TA, 9TAHC. PHILIPS 3306 3310, 3224, 3228/32 GP280, GARRARD GCM21, and 22, GC823, GK825 and 26, GCM21T and 22T, GCM24T GC823, GK825T and 26T, GCM31, GC836, GC836, GC838, K840A, K841B ETC. ALL AT 68p (7p). **SAPPHIRE 32p** (7p). **DOUBLE DIAMOND STYLUS:** same dia ST/DP up each side: no 78) All types £1.35 (7p). **SAPPHIRE DOUBLE STYLUS/TIPPED 32p** (7p). **PICK-UP WIRE:** super thin hex screened, sheathed, TWIN 7p per yard, 4-core 13p per yard (either up to 6 yds. 7p). Over, charges paid. **MICROPHONES:** CRYSTAL: LAPEL 1 1/2", clip/hand, lead 3.5mm jack plug 39p (9p). CM20 Cream Plastic hand 58p (9p); CM70 "PLANET" Metal, tapered with neck cord, adaptor for stand £1.65 (11p); "MIC 45". Curved metal hand grip £1.10 (11p) ALL with leads. **DYNAMIC:** 209 Cardiod Ball, 50K/600 Q built in volume control, on/off switch, special 20ft lead, the best value any; where at £6.80 (33p); UD130, uni-dir mesh ball 50K/600 Q jack plug, cable, adaptor, £5.28 (22p); DM160, omni-dir, Ball mesh, 50K, cable adaptor, jack plug, £4.29 (33p) each. **SPEAKERS:** Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) £2.08 (33p) or pair for stereo £4.65, charges paid. **SMALL 2 1/2"**, 3 Q, 8 Q or 64 Q (state which) 36p (8p). More speakers in List. **HEADPHONES:** High resistance 2000 Q adjustable £1.10 (11p). **EARPIECES:** with lead and min. 2.5mm or 3.5mm (state which) Jack plug. **MAINSTREAM 11p.** CRYSTAL (3.5mm plug only) 29p (up to 6 for 9p any size). **SOLDERING IRON:** Slim, modern, British high speed, 8 1/2", all parts replaceable, highest quality, fully guaranteed £1.29 (11p). **TRANSFORMERS:** Sub-min 1 1/2 x 1 1/2mm. OUTPUT (3 coils for OC72, etc.) 16p or DRIVER 17p (Up to 12 for 7p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5yds. Ass'd. coils. **SOLID CORE 16p** (7p). **FLEXIBLE CORE 18p** (9p). **SUPER THIN** flexible for transistor wiring, etc. 18p (7p) **RETRACTABLE FLEXIBLE LEADS (CURLIES):** With phono plug, each encl, 6ft 20p, 12ft 44p. With phono plug/phono socket other encl. 6ft. 20p, 12ft 50p (5p lead up to 6 for 9p any size). **VIBRATORS:** 12v/4 pin non-synch 121H/4, 2 1/2" ex. pins, 23p. SAME but 3 1/2" ex. pins, USA 18p; 12v/2 pin synch. (12SR7) 2 1/2" ex. pins, 72p (9p any type). **MAINS NEONS,** 7y leads 11p. **NEON SCREWDRIVER** (pocket tester) 19p (7p either). **MAINS BATTERY ELIMINATOR.** Input 240v-A.C. Output 3, 4 1/2, 6, 7, 9 and 12v D.C. by switch selector. On/off switch, pilot lamp, leads, plug to suit most cassette recorders, £4.13 (27p). Highly suitable for all transistor receivers.

All above prices have been adjusted to include V.A.T. Our LIST (see heading) with Cartridge and Styli equivalents etc., contains details of very many more components, Accessories and Units at most reasonable prices, of great interest to the constructor and amateur.

TRANSISTORS

1 DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)

ALL PRICES INCLUDE VAT

£19.50 ELECTRONIC DIGITAL CLOCK

(For complete kit of parts including case.)



This 4 digit 24 hour clock is available to readers at this special price for 1 month only. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

74 Series TTL

SN7400	16p	15p	SN7423	55p	50p	SN7450	16p	15p	SN7489	6.05p	5.85p
SN7401	16p	15p	SN7424	55p	50p	SN7451	16p	15p	SN7490	74p	72p
SN7402	16p	15p	SN7427	49p	46p	SN7453	16p	15p	SN7491	1.10p	1.04p
SN7403	16p	15p	SN7428	77p	72p	SN7454	16p	15p	SN7492	74p	72p
SN7404	16p	15p	SN7430	16p	15p	SN7456	16p	15p	SN7493	74p	72p
SN7405	18p	15p	SN7432	39p	46p	SN7457	33p	28p	SN7494	85p	72p
SN7406	38p	35p	SN7433	94p	82p	SN7458	33p	28p	SN7495	85p	72p
SN7407	38p	35p	SN7437	72p	69p	SN7473	41p	38p	SN7496	95p	82p
SN7408	20p	18p	SN7408	22p	69p	SN7474	41p	38p	SN74100	1.80p	1.75p
SN7409	20p	18p	SN7440	16p	15p	SN7475	50p	47p	SN74104	1.09p	1.06p
SN7410	17p	15p	SN7441	74p	70p	SN7476	44p	43p	SN74105	1.09p	1.06p
SN7411	27p	25p	SN7442	74p	70p	SN7480	73p	70p	SN74107	44p	42p
SN7412	38p	35p	SN7443	1.43p	1.37p	SN7481	1.32p	1.26p	SN74110	61p	58p
SN7413	32p	29p	SN7444	1.43p	1.37p	SN7482	97p	95p	SN74111	1.37p	1.27p
SN7416	47p	43p	SN7445	2.00p	1.82p	SN7403	1.20p	1.15p	SN74118	1.10p	1.05p
SN7417	47p	43p	SN7446	1.07p	1.02p	SN7484	1.10p	1.05p	SN74119	1.47p	1.37p
SN7420	16p	15p	SN7447	1.10p	1.03p	SN7485	3.08p	3.85p	SN74121	44p	41p
SN7422	55p	50p	SN7448	1.10p	1.03p	SN7486	36p	35p	SN74122	1.54p	1.49p

* Devices may be mixed to qualify for Price Breaks
* 100 Plus less 10% off 25 plus break

Linear Integrated Circuits

301 DIL	50p	72p	DIL	89p
301 TO99	55p	72p	TO99	89p
301 8 PIN DIL	46p	74p	8 PIN DIL	38p
301A DIL	69p	74p	14 PIN DIL	38p
301A TO99	69p	74p	TO99	41p
301A 8 PIN DIL	69p	74p	DIL	46p
307 DIL	69p	74p	DIL	39p
307 TO99	69p	74p	TO99	41p
307 8 PIN DIL	69p	74p	TO99	41p
308 TO99	6.45p	143p	DIL	1.27p
308A TO99	6.40p	143p	TO99	1.27p
709c DIL	31p	304p	DIL	84p
709c TO99	35p	750p	DIL	1.27p



Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	6½p	15µF	6½p	47µF	6½p
100µF	6½p	33µF	6½p	100µF	9p
220µF	6½p	68µF	6½p	150µF	10p
330µF	6½p	150µF	8p	220µF	10p
1000µF	13p	220µF	9p	470µF	11p
4700µF	29p	680µF	17p	680µF	25p
		1000µF	17p	1000µF	25p
		1500µF	25p	2200µF	44p
		2000µF	43p		
6.3 VOLT		25 VOLT		63 VOLT	
33µF	6½p	10µF	6½p	1µF	6½p
68µF	6½p	22µF	6½p	2.2µF	6½p
150µF	6½p	47µF	6½p	4.7µF	6½p
470µF	11p	100µF	8p	6.8µF	6½p
680µF	13p	150µF	10p	10µF	6½p
1500µF	18p	220µF	10p	22µF	6½p
2200µF	18p	470µF	13p	4.7µF	6½p
3300µF	26p	680µF	13p	6.8µF	6½p
		1000µF	22p	10µF	6½p
		2200µF	39p	22µF	6½p
		5000µF	68p	68µF	10p
				100µF	11p
				150µF	13p
				220µF	13p
				330µF	22p
				470µF	26p
				1000µF	44p
				1500µF	20p
				2200µF	24p

BARGAIN PACKS

Unmarked Packs	55p
BC108	55p
BC107	55p
(Plastic can)	
BC109	55p
BC169	55p
2N2646	55p
2N2926	55p
2N2926	55p
2N3055	33p
2N3055	27p
AD161, AD162	M/P
BC107-BC108	8p
BC109	9p
BC110	9p
BC111	6½p
BC121L-3-4-212-4	9p
BC122	8p
AC127 or AC128	13p
100 plus	12p
100 plus	11p
ZENER DIODES	
400 M/W 5%	
Miniature BZY 88 Range	
All voltages 3-33 Volt	9p each
1 watt 5%	
All voltages 6.8-300 Volt	14p each
10 watt 5%	
All Voltages 7.5-100 Volts	51p each

Transistors

AC107	16p	BC138	36p	BF260	29p	OC44	14p
AC126	14p	BC142	33p	BF229	18p	OC45	14p
AC127	15p	BC143	33p	BF230	18p	OC70	23p
AC128	15p	BC144	33p	BF240	37p	OC72	14p
AC142K	22p	BC145	26p	BF284	25p	OC72	14p
AC141K	20p	BC147	9p	BF285	35p	OC81	14p
AC176	15p	BC148	9p	BF286	35p	OC83	22p
AC187	15p	BC149	9p	BF287	28p	OC84	28p
AC187K	20p	BC155	16p	BF288	20p	TIP29A	53p
AC188	15p	BC154	17p	BF290	21p	TIP30A	64p
AC188K	20p	BC157	13p	BF251	17p	TIP31A	64p
AC17	24p	BC158	12p	BFY52	17p	TIP32A	73p
AC171	21p	BC159	14p	BFY54	30p	TIP33	£1-05
AC178	25p	BC167	13p	BFY90	72p	TIP34A	18132
AC1720	22p	BC168	11p	BFY20	19p	TIP35A	£1.54
AC1721	25p	BC169	11p	C407	22p	TIP36A	£2.53
AC1722	18p	BC177	15p	C426	33p	TIP36A	18940
AC1723	69p	BC179	15p	C428	31p	TIP41A	79p
AD140	40p	BC182L	9p	C450	17p	TIP42A	81p
AD142	44p	BC183L	9p	MPR111	36p	TIP42A	81p
AD143	39p	BC184L	9p	MPR112	35p	TIP42A	81p
AD149	35p	BC185	35p	MPR121	33p	TIP42A	81p
AD150	60p	BC212L	11p	MPR121	33p	TIP42A	81p
AD161	29p	BC213L	11p	MPR122	44p	TIP42A	81p
AD162	29p	BC214L	11p	MPR123	50p	TIP42A	81p
AD M/P	50p	BC258	9p	NKT211	28p	TIP42A	81p
AF114	14p	BC259	9p	NKT212	28p	TIP42A	81p
AF115	14p	BC276	14p	NKT213	28p	TIP42A	81p
AF116	14p	BC277	14p	NKT214	28p	TIP42A	81p
AF117	14p	BC300	40p	NKT261	23p	TIP42A	81p
AF118	92p	BC301	32p	NKT271	20p	TIP42A	81p
AF124	27p	BC302	30p	NKT274	20p	TIP42A	81p
AF139	39p	BC303	50p	NKT275	25p	TIP42A	81p
AF239	41p	BC304	40p	NKT403	71p	TIP42A	81p
AL300	77p	BC370	15p	NKT465	85p	TIP42A	81p
AL102	66p	BCV71	37p	NKY603P		TIP42A	81p
AL103	55p	BCV72	17p			TIP42A	81p
ASV26	31p	BD123	66p	NKT613G	28p	TIP42A	81p
ASV27	40p	BD130	50p			TIP42A	81p
AF103	99p	BD131	68p	NKT674	26p	TIP42A	81p
AO110-110	BD132	90p		NKT676		TIP42A	81p
AO111	77p	BD133	25p	OC28	24p	TIP42A	81p
BC107	9p	BD136	50p	NKT713	32p	TIP42A	81p
BC108	9p	BD141	£1.87	NKT732	77p	TIP42A	81p
BC109	9p	BD142	50p	OC19	55p	TIP42A	81p
BC113	15p	BF159	33p	OC20	55p	TIP42A	81p
BC116	16p	BF173	29p	OC23	33p	TIP42A	81p
BC125	16p	BF177	25p	OC25	25p	TIP42A	81p
BC126	25p	BF178	25p	OC28	33p	TIP42A	81p
BC132	16p	BF179	35p	OC29	33p	TIP42A	81p
BC134	16p	BF194	15p	OC35	38p	TIP42A	81p
BC135	16p	BF195	17p	OC36	38p	TIP42A	81p
BC137	16p	BF244	27p	OC41	14p	TIP42A	81p

Diodes & Rectifiers

IN914	8p
IN916	8p
IN4148	8p
IN44	8p
IN4007	22p
IN113	17p
IN120	17p
IN121	15p
IN130	9p
IN131	11p
IN132	11p
IN133	11p
IN200	11p

MULLARD POLYESTER'S

MULLARD POLYESTER CAPACITORS C280 SERIES	
250V P.C. mounting:	0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF,

Sinclair Project 60

Now—the Z.50 Mk.2


with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50. Circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual
£5.48

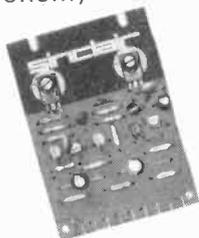Z.30 the power amplifier for quality and economy



with free manual
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/8 x 1/2). Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.


Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

Brilliant new technical specifications

Input impedance 100 K Ω
Input (for 30w into 8 Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8 Ω . See curve
Frequency response 10Hz to more than 200 KHz \pm 1dB
Max. supply voltage 45v (4 Ω to 8 Ω speakers) (50v 15 Ω speakers only)
Min. supply voltage 9v
Load impedance — minimum : 4 Ω at 45v HT
Load impedance — maximum : safe on open circuit

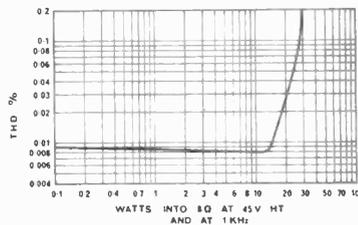

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 1.2V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43


F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

sinclair

SINCLAIR RADIONICS LTD., R.O. London Road, St. Ives, Huntingdonshire, PE17 4HJ (Phone St. Ives 4311) Reg. No. 699483 England

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit

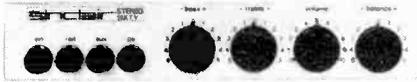

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio — up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve ± 1 dB. 20 to 25,000 Hz. Ceramic p.u. — up to 3mV. Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to -12dB at 10KHz. BASS +12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed **£9.98**

Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7 μ V for lock-in over full deviation. **Squelch level:** Typically 20 μ V. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz — 15KHz (± 1 dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

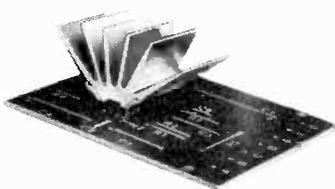Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC.12 make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 8 watts RMS continuous (12 watts peak). 6–8 Ω . **Frequency Response:** 5Hz to 100KHz ± 1 dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.


Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Power Supply Units

The new PZ.8 Mk.3

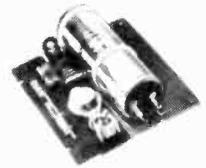

The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage—45.

PZ.8 Mk.3—£7.98

(Mains transformer, if required) £5.98

PZ.5 30v. un stabilised

(not suitable for Project 60 tuner) £4.98

PZ.6 35v. stabilised

(not suitable for IC.12) £7.98

Project 605



the easy way to buy and build Project 60 without soldering

Project 605 in one pack contains one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free

£29.95

All you need for a superb 30 watt high fidelity stereo amplifier

Order form

Please send

Enclose cash/cheque/money order.

Name _____

Address _____

PWS

SINCLAIR RADIONICS LTD., R.O. London Road,
 St. Ives, Huntingdonshire, PE17 4HJ

sinclair

Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Service Sheets

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS" Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

Books and Publications

DENCO CLACTON LIMITED

355-7-9 Old Road

Clacton-on-Sea, Essex

Catalogue 20p post paid

S.A.E. all enquiries

Radio BOOKS

Handbk of Transistor Equip and Substitutes	45p
Handbook of Tested Transistor Circuits	45p
Rad & Electr Colour Codes and Data Chart	20p
Ht Ft PA & Disco Amplifier Design Hbk	80p
Boys' Bk of Crystal Sets and Simple Circuits	23p
How to make FM & TV Aerials, Bands 1,2,3	23p
Radio Servicing for Amateurs	25p
High Fidelity Loudspeaker Enclosures	45p
Practical Tape Recording Handbook	35p
Practical Stereo Handbook	35p
Practical Radio Inside Out	45p
Transistor Circuits Manual No. 1	20p
Transistor Circuits Manual No. 2	20p
Transistor Test Equip and Servicing Manual	35p
Radio TV and Electronics Data Book	30p
Transis Circuits for Radio Controlled Models	45p
Pract Transistor Audio Amplifiers, Book 1	25p
Handbook of Simple Transistor Circuits	40p
Modern Transistor Circuits for Beginners	45p
Sound and Loudspeaker Manual	55p
Resistor Colour Code Disc Calculator	15p
Manual Transistor Audio Amplifiers	45p
Practical Car Radio Handbook	35p
Radio TV and Industrial Tube & Valve Equip	45p
Practical Transistor Novelty Circuits	45p
Television Servicing Vol. 1	95p
Television Servicing Vol. 2	95p
Television Servicing Vol. 3	70p
Television Servicing Vol. 4	80p
Using an Oscilloscope	85p
Servicing Transistor Radio Receivers	85p
Television Timebase Circuits	£1.10
Pal-D Colour Receiver Questions & Ans	78p

All prices include postage & packing
FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

SHORT WAVE MAGAZINE, now in its 36th year and published monthly, covers the whole field of Radio Amateur transmission and reception including regular news features (DX, VHF, Clubs and SWL) and the design, construction and operation of AMATEUR Radio equipment of every type. Cover price 25p at newsagents. Specimen copy 30p post free, first class. Annual subscription £3.00 (or £2.75 second class posting) year of 12 issues.—Circulation Dept. (P.), Short Wave Magazine Ltd., 55 Victoria Street, London SW1H 0HF. (Tel: 01-222 5341/2)

DIGITAL COMPUTER LOGIC and Electronics. Four volume self-instructional course. £2.95 including p & p. Money back assurance. Cambridge Learning (PW), 8a Rose Crescent, Cambridge.

TRANSISTOR DATA THE INTERNATIONAL TRANSISTOR DATA MANUAL

1973 EDITION is now ready. Data on upwards of 18,000 transistors of international origin. £5.25 plus 35p post & packing in the UK. Brochure available. Order direct from

SEMICON INDEX LTD.,
Freepost, Wokingham, Berks. RG11 2AY.

★ **KILRIMONT BOOKS** ★
Understanding Electronic Components £3.50
Practical Wireless Circuits £1.20*
Audio Technicians Bench Manual £3.00
Using an Oscilloscope £0.70*
Mazda Book of PAL Receiver Servicing £3.80
Beginners Guide to Radio £1.00*
Computer Science £2.00
Colour T.V. Picture Faults (111.) £2.50
* Please enclose 5p postage on orders less than £2.00. Lists gladly sent on application.
Kilrिमont Books (A), Kilrिमont House, London Road, Braintree, Essex. CM7 8QL

Aerials

Direct from the Manufacturers

U.H.F. AERIALS

EASY ASSEMBLY KITS

TO Element **SAVE 40%** on normal retail price

£1.25

14 Element 18 Element
£1.50 £1.75

Rapidly assembled and 20p above 35p carriage and packing. Please state which channels or group.

APEX AERIALS (E.M.)
ALSAN WORKS, MARY ST. JOHNSTONE, HENFRESHIRE



BAINES for High Frequency Aerials

UHF Multibeams by J. Beam

MBM 10 £2.20 MBM 18 £2.90 MBM 30 £3.90
MBM 46 £6.00 MBM 70 £11.00

VHF FM Aerials
Dipole £1.40, FM/H £2.00, FM3 £3.00, FM4S £5.55, FM6S £7.80

Meathead Pre-amps
Single Stage £5.00, Two stage £8.00, Wideband £7.00
Accessories: SAE for full list. Co-ax 5p, low loss 9p

11 Dale Cres., Tupton, Chesterfield S42 6DR

GENUINE FULL SIZE 18 element TV aerial

as used by leading TV companies

FOR ONLY **£1.99** + 25p C&P

Guaranteed Perfect Pictures. Save 2.25. We supply this genuine U.H.F. aerial for only £1.99 can be fitted out side or inside. Quality made, technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions advice.

Money Back Refund Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters.

Send direct to Dept PW10, 219 Mansfield Rd., Nottingham.



IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists

DIRECT FROM MANUFACTURER—a comprehensive catalogue of UHF & VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (PW), 261 Hardess Street, London, S.E.24.

★ SERVICE SHEETS • MANUALS • BOOKS ★

SERVICE SHEETS OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK | **SERVICE SHEET** ON RADIOS, TV, R. PLAYERS AND T. RECORDERS, ETC. | **SERVICE SHEET** 30p + Postage PLEASE ENCLOSE S.A.E. WITH ENQUIRIES... | Catalogue 20p.

NEW BOOKS AND PUBLICATIONS	PRICE
AUDIO TECHNICIANS BENCH MANUAL by John Earl. 182 pages 114 Illustrations.	£3.00
RADIO TECHNICIANS BENCH MANUAL by H.W. Hellyer. 215 pages 131 Illustrations.	£3.00
BEGINNERS GUIDE TO RADIO by G.J. King. 7th Edition. 204 pages. Illustrated.	£1.00
ELECTRONICS IN MUSIC by F.C. Judd. Circuit designs. 169 pages. Illustrated.	£3.15
FOUNDATIONS OF WIRELESS AND ELECTRONICS by M.G. Scroggie. 552 pages.	£3.00
F.M. RADIO SERVICING HANDBOOK by G.J. King. 2nd Edition. 206 pages.	£3.00
FAULT LOCATION EXERCISES IN RADIO & TV SERVICING by K.J. Bohlman. Vol. 1.	£0.80
SERVICING WITH THE OSCILLOSCOPE by G.J. King. 176 pages. Illustrated.	£1.80
WORLD RADIO-TV HANDBOOK 1973. Immense amount of tabulated matter listed.	£3.00
50 PHOTOELECTRIC CIRCUITS AND SYSTEMS by P.S. Smith. 88 pages. Illustrated.	£2.30

NOTE. Postage on all books is now 5p up to £1. ORDERS OVER £1.00 POST FREE. (UK only)
Send large S.A.E. for FREE booklists and book pamphlets on Radio, Television & Electronics.
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good prices paid.

BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorks. Tel. 0423-86844

Educational

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs') RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 732MI INTERTEXT HOUSE,
STEWARTS RD., LONDON, SW8 4UJ

RADIO, TV, RTEB Certs., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book—FREE, BIET (Dept ZL BPW 26), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

CIE, AMSE, City & Guilds, etc. Thousands of exam successes. Postal courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept ZL BPW 37), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Situations Vacant

TEKTRONIX U.K. LIMITED

have vacancies for

Product Service Technicians

to repair and recalibrate our range of oscilloscopes and other products at our Harpenden office.

A good knowledge of basic electronics is necessary and a flair for fault-finding would be an advantage.

We offer good working conditions, profit sharing, non-contributory life assurance and pension schemes.

Please write or telephone:

R. M. Garrett,

Tektronix U.K. Limited,

36/38 Coldharbour Lane,

Harpenden, Herts.

Telephone: Harpenden 61251 Ext. 25

ASSISTANT CHIEF ELECTRONICS ENGINEER. Duties will include servicing of all types of audio domestic appliances, plus sample specification reports on imported Hi-Fi equipment. The use and familiarisation of test equipment. Experience on FM/MPX and tape recorder techniques is essential. Successful applicant will work in close liaison with the chief service engineer. Remuneration according to experience and qualifications. Three weeks' holiday per year. Tel: 01-594 1473. Personnel Manager, Harris Overseas Ltd., Harvard House, 14 Thames Road, Barking, Essex.

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators
Training Centre

M97, Oxford House

9-15, Oxford Street, W.1.

Telephone: 01-734 2874

127, The Piazza, Dept. M97.

Piccadilly Plaza, Manchester 1.

Telephone: 061-236 2935

Wanted

TOP PRICES PAID for NEW VALVES
popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),

367 Kensington Street, Bradford 8,

Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

WANTED: Built or partly built Heathkit A.F.M.2 Tuner. 64, Green Lane, Coventry.

For Sale

BBC 2 TV'S 7.50 Including Delivery

Thorn 850 Chassis with UHF Tuner. Ex-rental sets sold complete but un-serviced, with repolished cabinets. Rush £7-50. Cash with Order.

U.H.F. TUNERS

For Ferguson 850, 900 Chassis, but adaptable for most D/STD Chassis. £2-50 each. Plus 50p P&P. C.W.O.

Send S.A.E. for list of TVs, Tubes, Valves, etc. Allow 10-14 days delivery.

TRADE DISPOSALS (PW),

Midlands & North: 1043 Leeds Road, Bradford 3.

Scotland: Unit 5, Peacock Cross Industrial Estate, Burnbank Road, Hamilton.

Cornwall: Pencoys, Four Lanes, Redruth.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

Receivers and Components

TV LINE OUTPUT TRANSFORMERS Tidman Mail Order Ltd., 236 Sandycombe Rd., Richmond, Surrey. TW9 2EQ. 01-948 3702.

THE

TEXAN

NOW ON DEMONSTRATION



Designer approved Kit only £28-50
Instructions only 35p

Pack 1. RESISTORS 80p
Pack 2. SMALL CAPS £1-50
Pack 3. LARGE CAPS £1-40
Pack 4. SUNDRIES £1-90
Pack 5. SWITCHES 90p
Pack 6. CONTROLS £1-45
Pack 7. SEMI COND. £8-25
Pack 8. TRANSFORMER £4-95
Pack 9. P.C. BOARD £2-50
Pack 10. CHASSIS, etc. £4-20

Post extra—parts available separately
Send for list and technical spec.

Kits also available for

- ★ Radio Control Systems
- ★ Digital Clock Systems
- ★ Integrated Circuit Amplifiers (to 50W)
- ★ Hi-Fi Pre-amps
- ★ Stabilized Power Supply Units

TELERADIO HI FI, 325 Fore Street,
Edmonton, London N.9 01-807 3719

CLOSED ALL DAY THURSDAY

BUILD THE

TREASURE TRACER

MK III Metal Locator



- Varicap tuning
- Excellent sensitivity and stability
- Weighs only 22oz
- Speaker and earphone operation
- Knocks down to only 1in.
- Prebuilt search coil assembly
- Ministry approved design
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- Completely new design
- Send 3 a.c. for leaflet

Complete £8-90 Built tested and guaranteed £12-50
Post 30p Post 30p

MINIKITS ELECTRONICS, 35a LANGLEY DRIVE, WAINSTED,
LONDON E11 2LW (Mail order only)

MINI MAINS PACK KIT. Safe double wound mini transformer, silicon rects., 1000F smoothing. Delivers 9V d.c., 120mA. Components with data sheet; pack buildable to size of PP6 etc. battery. £0-90+U.K. post 5p. By mail only from AMATRONIX LTD., 396 SELSDON RD., SOUTH CROYDON, SURREY, CR2 0DE.

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0-47, 1, 2-2, 4-7, 10 mfd—4p, 22, 47—4½p (50V-5p) 100—5½p (50V-7p). Subminiature bead-type tantalums 0-1/35V, 0-22/35V, 0-47/35V, 1/35V, 2-2/35V, 4-7/35V, 10/16V—8p. Mylar Film 100V—0-001, 0-002, 0-005, 0-01, 0-02—2p, 0-04, 0-05—3p, 0-1—3½p. Polystyrene 63V E.12 series, 10 pF—10,000 pF—2p. Miniature Highstab resistors E.12 series. 5% carbon film 10-10MΩ (10% over 1 Meg.) Metal Film ½W 100-2-2MΩ and 1W-270-10MΩ all ½p ea. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

CASED AMPLIFIERS

2xEC83, EL84, EZ80. 20µV 1/P sensitivity 2 watts Op/P into 7 x 4" 3" Speaker. All contained in polished cabinet with non-standard single motor deck. Tested with circuit £3 (£1). Suitable cassettes £1 (20p); spare heads 40p.

COMPUTER PANELS

Lots of Transistors inc. Power Types, Diodes, R's, C's, Pot Cores, etc. Some boards broken, but good value at 3lbs. £1 (20p), 7lbs. £2 (40p).

1,000 R's & C's £3.00. Amazing Variety of resistors, including Carbon Film, Metal Oxide, Hi-Stabs, 1, 2 & 5%, 1, 1/2, 1/4 and 1W From a few ohms to a few Megohms. Also Mica, Ceramic, Foil, Paper, Electrolytic, Polystyrene Capacitors. About 1000 Components £3 (30p).

FERRIC CHLORIDE

Anhydrous Technical Quality in sealed 1lb packs 40p (15p), 10lbs £3.50 (50p).

COMPONENTS: BC107-8-9, 8p ea., 14 for £1; 709C 25p; 741C 25p; 742C 40p; 2N3055 55p; IN4003 7p; IN4008 11p; Croton 1610 Light Guide; 60 Filament 1p per metre, 5 + 80p, 10 + 70p. SURPLUS CAPACITORS MFD/V: 0.47/350 6p; 2/160 2p; 8/350 8p; 8/450 10p; 25/25 5p; 500/50 18p; 550/8 8p; 1000 + 500/18 12p—Lots of others. Lots of Odd Units, Sockets, Meggers, Avo's, Sig. Gen's, etc. at above for callers. SAE List. Post in brackets, small parts 8p.

GREENWELD (PW12)

24 Goodhart Way, West Wickham, Kent. Tel: 01-777 2001. Shop at 1 Deptford Broadway, S.E.3. Tel: 01-692 2009.

U.K. ADD VAT TO ORDER TOTAL.
MICROCIRCUITS: 709 28p; 710 36p; 723 57p; 741 28p; 748 37p; PA230 70p; SL402A £1.00; PET Op.Amp. £1.62. TRANSISTORS: 2N696 14p; 2N697 14p; 2N708A 11p; 2N1613 15p; 2N1711 15p; 2N2218 19p; 2N2219 19p; 2N2219A 19p; 2N2904 17p; 2N2928 18p; 2N2928 18p; ORANGE 7p; YELLOW 8p; GREEN 9p; 2N3053 15p; 2N3054 40p; 2N3055 35p; 2N3702 10p; 2N3703 10p; 2N3704 10p; 2N3705 9p; 2N3706 9p; 2N3709 8p; 2N3710 9p; 2N3711 9p; 2N4058 12p; 2N4059 9p; 2N4061 11p; 2N4062 11p; AC107 28p; AC126 28p; AC127 12p; AC176 15p; ACY17 23p; ACY21 17p; AF114 14p; AF115 14p; AF116 14p; AF117 14p; AF124 22p; BC107A 7p; BC107B 8p; BC108A 8p; BC108B 8p; BC108C 9p; BC109B 7p; BC109C 7p; BLY41A 40p; BC147A 9p; BC167A 10p; BC168B 9p; BC169B .0p; BC171 13p; BC178 12p; BC179 16p; BCY70 15p; BCY71 22p; BD142 35p; BF115 20p; BF194 13p; BFX29 24p; BFX84 20p; BFX86 15p; BFX87 24p; BFX88 15p; BFY50 15p; BFY51 15p; BFY52 15p; BLY41A 40p; BSX20 12p; OC4 12p; OC45 12p; OCT1 12p; OCT2 12p; OCT8 18p; OCT8 24p; ME SERIES AVAILABLE. RECTIFIERS: 1 AMP: 50V 34p; 100V 4p; 200V 41p; 400V 5p; 800V 6p; 1000V 7p. ZENERS BZY88 SERIES 2.7V to 33V 8p each. DIODES IN916 4p; CA90 6p; CA200 7p; CA202 8p. SCR IR122D (400V SA) £1.15. LED PANEL LAMP WITH BUSH AND DATA 40p. CARBON FILM 1/4W 5% RESISTORS E12 values 22 to 2.2M 1p EACH or 7p per 10 of ONE VALUE DALO ETCH RESIST FILLED FIBRE TIP PEN 80p. MINIATURE METAL GLAZE RESISTORS 1/16W 5% 41p each. 1K THERMISTOR 9p. 2N3819 26p. TESTED TRANSISTOR CIRCUITS BOOKLET 40p. ITT POCKET MULTIMETER 27 ranges £17. C.W.O.

(Above prices on Feb. 12. Check our list) J.F. ELECTRONICS (P.W.5) York House 12 York Drive, Grappenhall, Warrington WA4 2EJ. Mail Order Only. P & P at Cost—10p minimum per order. List Free.

DISC Ceramics 100 55p. Resistors 100 40p. Lists and samples 20p. Plus postage. Derwent Radio, Scarborough.

IRISH READERS! Up to 20% off stereo amplifiers, tuners, decks, speakers etc. FREE catalogue Berne Bros, Auburn Terrace, Athlone, Co. Westmeath, Ireland.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 incl. postage C.W.O. to Caledonian Components, Forsterton Firs, Strathore Road, Thornton, Fife.

VALVE BARGAINS any 5—Give Free ECC82 EF183-EF184. PCF80. PCL82 PY800. PL36. When buy TVS. 19in. U.H.F./V.H.F. TV £6:50 carriage £1:50. Slotmeters. Perfect working. £1:50. Post Free. MIR Radio & TV, 193 Ramsey St., Rochdale, Lancs. Tel. 40599.

Trampol electronics

ALL BRAND NEW, no rejects. Money back warranty. 5V DIGITAL INDICATOR. 0-9DP socket and filter £1.45. LED TYPE 1/4" 0-9DP DIL £2.25 ea. LIGHT EMITTING DIODES. All with data and panel clip. TIL 209 1/4" dia 25p. Red 1/4" dia type 35p. Green 70p. INFT RED beam LEO £1.10. T65 GAS detector £1.69. ULTRASONIC TRANSDUCERS £2. DALO PCB resist marking pen 60p. Copper board 12" x 6" BRBP 40p FeC etch PAK 19p. INTEGRATED CIRCUITS: with data if required. IC LITE SWITCH: Photo amp/trigger 40ma / 11-20 relay or TTL 87p. DIL relay £1.10.



IC digital clock

MOS/LSI type 28 pin 4 or 6 digit 12/24 hr. Chip with socket £13. PCB £1.99. KIT £21.49. 741 DIL 8 pin 25p. 709 14p. DIL 25p. 748 25p. 710 35p. 555 TIMER mono/stable osc. clock 95p. REGULATORS: 1A 5 to 20V £1.49. 723 57p. RECEIVER 2N414 1.19. Mini Rk xlt £1.99. 1310 stereo decoder for tuners £2.69. Kit £3.45. 74N TTL: Gates 7400 etc. 14p ea. 7413 27p. 7441 75p. 7447 £1.09. 7490 69p. 7492 67p. 74121 45p. DIL SOCKETS: lo or hi profile 8/14/16 pin 13p. SEMICONDUCTORS: 2N3055 40p. BC107 8p. BC108 8p. BC109 8p. BC147/8/9 10p. BC167/8/9 15p. BC182/3/4 10p. BC192/3/4 11p. BCY70/72 13p. BD131/2 55p. BFX60/61/52 13p. TIS43 UJT 24p. 2N706 11p. 2N2969 12p. 2N2926 OY 8p. 2N2646 40p. 2N3053 17p. 2N3614 55p. 2N3702/3/4/5/6/7/8/9/10/11 All 9p ea. FETS: 2N3819 27p. 2N3823 29p. SCR 400V 1A 25p. 4A 55p. TRANSFORMER: 1A 6 & 12V £1. CAPACITORS: Disc 22p to 0.1µF 4p. 25V electrolytic 10, 50, 100 µF 6p, 1000 µF 15p. PRESETS 5p ea. RESISTORS 1/4W. 5 11p ea. CARBON POTS 12p ea. Dual 40p. Switch + 12p.

FLUORESCENT LIGHTS 12VOLT @ 2.70

13" 8 watt fully built with diffuser.



TRIO

All TRIO equipment available 1e. 9R-5908 Rx £49.50. JR310 Rx. £75. Also GODAR gear PR40 £8.90. Multiband Rx kit £13.80. CR70A Rx £27.50. V.A.T. You must add 10% (1/10) to all prices. FREE CAT. S.A.E. Data sheets. 8p ea. P.&P. 8p CWO. P.O. BOX 29, BRACKNELL, BERKS.

World-wide acclaim, the incomparable

GLOBE-KING V.H.F. & S.W. KITS

Precision standard, inexpensive, low-cost valve and transistor Kits for Short-Wave 10-350 m. V.H.F. 80-180 M/cs. Ideal for beginners with unique "Easy-Build" diagrams and simplified instructions. Send to-day for free literature price list and order form, kindly enclose stamped addressed envelope (Overseas: Int. Reply Coupon). Direct to the sole manufacturers:

JOHNSONS (RADIO) SHAW ST., WORCESTER. WR1 3QQ

Please note new address, city centre. Pioneers in DX radio—Established for over 30 years.

(A JOHN BANNER COMPANY)

S-N-CHANNEL FETs 3819E—£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.

Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LIMITED

45 Station Road, Gerrards Cross, Bucks. Mail Order only

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 + p.&p 10p U.K. only.

Illustrated catalogue of selected kits and components. 15p P&P free.

Galleon Trading Co, 12, Burras Way, Corringham, Stanford-Le-Hope, Essex. SS17 9DE

PRECISION

POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0.47µF: ±5% 80p; ±2% 40p; ±1% 50p
1.0µF: ±5% 40p; ±2% 50p; ±1% 60p
2.2µF: ±5% 50p; ±2% 60p; ±1% 70p
4.7µF: ±5% 70p; ±2% 90p; ±1% 115p
6.8µF: ±5% 95p; ±2% 115p; ±1% 140p
10µF: ±5% 110p; ±2% 130p; ±1% 160p
15µF: ±5% 160p; ±2% 220p; ±1% 270p

TANTALUM BEAD CAPACITORS

Values available 0.1-0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p, 14 for £1. Special pack 6 of each value (78 capacitors) £5.

NEW—TRANSISTORS. BC107, BC108, BC109, All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178—42p each; 3 for £1.

POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1. IN916—9p each, 6 for 50p, 14 for £1. IS44—5p each, 11 for 50p, 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners—Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13, 15V. Tol. ±5% at 5 mA. All new and marked. Price 10p each, 6 for 50p, 14 for £1.00. Special offer 6 of each voltage (66 zeners) £4.50

RESISTORS. Carbon film 1/4W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 9p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS. 0.1µF, size 1 1/2in x 1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47µF, size 1 1/2in x 1/2in, 35p; 1.0µF, size 2in x 1in, 45p; 2.0µF, size 2in x 1in, 75p each.

SILICON PLASTIC RECTIFIERS 1.5 Amp Brand new wire-ended DO27. 100P/IV at 8p each or 4 for 30p; 400P/IV at 9p each or 4 for 34p; 800P/IV at 14p each or 4 for 50p. 5p post and packing on all orders below £5. 10% V.A.T Effective April 1st.

MARCO TRADING (formerly V. Attwood) Dept. W.5. The Maltings, Station Road, Wem, Salop

13A SCOPE. Handbook with Circuit Diagram — £2.00. Complete range spares, probes, transformers, chokes, potentiometers, graticules, etc. Cheap. SAE or phone. CT.316 Scope. Handbook with Circuit Diagram — £2. SPEAKES, 12 Kenley Avenue, Shrewsbury. Tel. 56949.

NEW RECEIVER MODULE RM-A

A small circuit board, wired, tested and aligned and requiring only addition of tuning capacitor, coils and controls (not included) to make a complete AM/CW/SSB superhet RX for up to 30 MHz. Headphone output. Runs off 6v to 15v. PP9 suitable. Contains RCA IC (equiv. 14 transistors) plus BFO, FET local osc. and 2 double-tuned IPT's at 465 kHz. Full instructions and colour coded leads make connection simple, even for beginners—£7.85 post paid. Provides good stable reception of DX on CW/SSB or can be used with HF or VHF converters as double superhet. Suitable add-on RF and Audio Amp modules also available from £2. SAE details.

P. R. GOLLEDGE G3EDW Glen Tor, Torrington, Devon. Tel: 08-052 2411

VISIT AUTO TRACTION. Thousands of bargains in surplus radio equipment. Meters, motors, relays, TR/TX, telephone equipment, aircraft equipment. SAE enquiries. 27A, Arragon Road, Twickenham, Middx. 892 9489.

TAPE HEADS

For valve and transistorized recorders from £2 ea.

Send stamp for lists.
R.D.I. Ltd.
Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

Miscellaneous

Darned Electronic Wizardry

by Dewtron

Famous kits, e.g. waa-waa complete kit £2.95; Fuzz kit £4.75, auto rhythm modules P & P 20p mm. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

ONE CHIP CALCULATOR MOS INTEGRATED CIRCUIT

- Add, subtract, multiply, divide
- 12-digit display
- Fixed decimal point at 0.2, 3 or 4
- Automatic lockout of "unsure" repeat operation
- True credit balance sign display
- Automatic overflow indication
- Leading zero suppression
- Data Sheet 50p (refund on purchase)

£12.50
p & p inc.

O'Driscoll, 68 Hammer Hill,
Haslemere, Surrey, GU27 3QZ
Tel: 0428-2058

GLASS FIBRE P.C. BOARD. Large supplies available in single sided one ounce copper 2p per 3 sq. inches (under 1 foot). 75p per sq. ft. (over 1 foot). In double sided one ounce copper 1p per sq. inch (under 1 ft.), £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd. Stratford-on-Avon, Warwick.

MANUFACTURER'S SURPLUS, RECORD PLAYER Cabinets with motor board £3-00. Radio Cabinets make ideal speaker cabinets 13in x 7in x 5in 50p, AM/FM gang condensers with S/M drive 25p. UHF/IF Transformers, set including sound discriminator, 75p with data. F/M Tuner with valve £1-50. All items new includes P & P. ARCHER, 9 Pine Grove, Maidstone, Kent.

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

EXPERIMENTERS! Hundreds of unusual items cheap. 1973 catalogue 5p. Grimsby Electronics, 64 Tennyson Road, Cleethorpes, Lincs. (Mail Order Only).

"AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS"

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECKET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.80 (inc. VAT) NOW
'(S.A.E. for details)' 'MAIL ORDER ONLY'
TO: 'BOFFIN PROJECTS'
DEPT. KW2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwicks.

BEDFORD ELECTRONICS

2 Grove Place, Bedford
Bedford S1961

YOUR LOCAL
COMPONENTS SUPPLIER
Free catalogue on request

ENGRAVING. Give your Fascia Panels that professional look. Have the letters machine engraved. 3p per letter, minimum order 50p. Plus P & P. Colourstones, 9 Broadway Close, Harwell, Berkshire.

CONSTRUCTION AIDS—Screws, nuts, spacers etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd., Stratford on Avon, Warwicks.

Ladders

LADDERS. 20ft, £7.80; 24½ft £9.80. Carr. 80p. Leaflet. (Dept. WLS) Home Sales Ladder Centre, Baldwin Road, Stourport, Worcs. Tel. 029-93 5222.

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30—
ECC82, ECL80, EB91, EF89, EF80, EF85, EF183, EF194, EY89, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15.

19" UHF/VHF (BBC2) £8.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—85p

‡ to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Capacitors up to 500MFD—£1.10 (our choice).

BARGAINS PARTS

Transistor UHF Tuners—£2.00, 500K-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2.25. Brand New Transformers BF15, BF173, BC174, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order Money back guarantee. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

The BATTERIES That Won't Let You Down! RECHARGEABLE

Mallory Cells in U2, U11 and Penlite U7 sizes, Kestrel Battery Charging Unit



Uses:
Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you must have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestrel Charging Unit which has been specially designed for these new type batteries.

PRICES
Batteries U2 equiv. £1.38
Penlite U7 equiv. 50p
U11 equiv. £1.03
Charging unit £3.99 with one battery holder

KESTREL

Bush & Meissner

Send to:
275 WEST END LANE
LONDON, N.W.8
01-704 9611

TRANSFORMERS

DOUGLAS GUARANTEED
12 or 24 volts

Output V. & Amps.	Ref. No.	Add 10% V.A.T.
12V x 2 250 mA x 2	MT111 CS*†	£0.91 9p
12V x 2 500 mA x 2	MT213 CT*†	£1.18 16p
12V x 2 1A x 2	MT 71 AT*†	£1.48 24p
12V x 2 2A x 2	MT 18 AT	£2.06 30p
12V x 2 3A x 2	MT 70 AT	£2.59 32p
12V x 2 4A x 2	MT 108 AT	£3.29 34p
12V x 2 5A x 2	MT 72 AT	£3.33 42p

30 Volts. All tapped at 0-12-15-20-24-30V
Out- Ref. No. Price P.P. Out- Ref. No. Price P.P.

put Amps.	put Amps.	put	put
500 mA MT 112 CT†	1.12 16p	3A MT 20 AT	2.64 32p
1A MT 79 AT†	1.55 29p	4A MT 21 AT	3.10 40p
2A MT 3 AT	2.23 30p	5A MT 51 AT	4.31 42p
50 volts. All tapped at 0-19-25-33-40-50V.			
500 mA MT 102 AT†	1.45 24p	3A MT 105 AT	3.91 41p
1A MT 103 AT	2.00 32p	4A MT 106 AT	5.06 41p
2A MT 104 AT	3.10 32p	6A MT 107 AT	7.47 50p
60 Volts. All tapped at 0-24-30-40-48-60V.			
500 mA MT 124 AT†	1.48 30p	2A MT 127 AT	3.16 41p
1A MT 126 AT	2.24 32p	3A MT 125 AT	4.59 41p

AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 113 CT	£0.89 16p
75 VA		MT 61 AT	£1.72 30p
150 VA	0-115-200-220-240	MT 4 AT	£2.15 32p
200 VA		MT 65 AT	£2.90 32p
400 V. Output at 50 Hz. Ref. IT3 AT			
C-D Ignition system by R. M. Marston			Price P. & P. £2.30 29p

EQUIPMENT RANGE

Sec. Output (r.m.s.)	Ref. No.	Price P. & P.
3-0-3 V. 200 mA	MT 238 CS*†	£0.89 8p
9-0-9 V. 100 mA	MT 13 CS*†	£0.91 8p
12-0-12 50 mA	MT 239 CS*†	£0.91 8p
20-0-20 30 mA	MT 241 CS*†	£0.91 8p
0-20 x 2 300 x 2	MT 214 CT*†	£1.21 16p
0-8-0 x 2 500 mA x 2	MT 207 CT*†	£1.48 19p
0-15-0 x 2 500 mA x 2	MT 205 AT*†	£2.12 29p
0-15-37 x 2 1A x 2	MT 203 AT*†	£2.48 29p
0-15-37 x 2 1A x 2	MT 204 AT*†	£3.42 30p
10-12-0-12-20 700 mA (d.c.)	MT 221 AT*	£1.11 26p

AT Indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; * with interwinding screen; † untapped 240V Primary; ‡ Primary tapped at 210-240V. other Primaries tapped at 200-220-240V.
Over 200 types in stock through agents or direct. Send for lists.

DOUGLAS ELECTRONICS INDUSTRIES LTD.
(Dept. MO.18PW), Thames St., LOUTHE, Lincs. LN11 7AD

AUDIO POWER AMPLIFIERS

10W £4.00 } 1
25W — £8.00 } OFF
50W — £11.00 } PRICES

GENEROUS QUANTITY DISCOUNTS AVAILABLE

DETAILS FROM:
PHOTAIN CONTROLS LTD.

Randalls Road, Leatherhead, Surrey

PRICES DO NOT INCLUDE VAT

Tel: 72776/75517 STD CODE 037-23

Due to Warehouse Clearance we have a few low powered F.M. VHF Wireless Station Type A. AFV. No. 88. Contained in two units (1) Transmitter/Receiver, (2) 12 Volt Power Unit and L.F. Amplifier.

The TX and RX are contained in a waterproof diecast Alloy case, using a total of 14 Valves, operates on four switched channels which are Crystal controlled. All 8 Crystals are supplied, and are the same in each set. Therefore all sets will transmit and receive to each other, provided each are switched to the same channel out of the four. The Stations are supplied with Mounting Carriers, 2 Vertical Whip Aerials, plus Aerial Base, Spare Valves, Bulbs, Mounting Screws, Connectors, etc. Including the Operating Manual giving all details, plus circuits of the Wireless set. All above items are individually boxed and wrapped, placed in original Transit case.

Absolutely brand new. Made by Echo for the Government, no expense spared, few only available at £8.50, carr. £2.

Radio Telescope Terminal Set. A. type, AN/SGGTA latest Government release of these sought after units, housed in metal case, approx. size 8" x 19" x 16" deep. Using a total of 11 Valves, Supply Voltage 115 Volts 50 c/s.

Containing meter switched for checking, send and receive Bias, Send and Receive Level, Loop and Plate current, in fair used ex Government condition. Few only available at £7.50, carr. £1.50.

Large quantity of Teletypewriter Paper. Available, sprocket fed, contained in sealed packs, each pack containing 4 separate wads, price 60p per pack of four pads, post 25p, or wooden crate containing 5 packs = 20 wads £2, carr. 50p.

Signal Generator TF801A. 10/300 m/cfs with Spare Valves in Wooden Transit Case as New, £28, carr. £2. Signal Generator Marconi TF144G MK3 (Grey). Probably the latest of this type, 85 K/cfs-25 m/cfs, supplied in Wooden Transit Cases with Leads Grade 1 condition £15, carr. £3.

Advanced Constant Voltage Transformer. 190/250V voltage in, 230V out, 250 watts, £12, carr. £2.

Power Supply Unit Rectifier No. 7. For Teletypewriters, Input 100/240V, A.C. or 12V D.C. Output 70/100V twice D.C. 30mA, plus 35/45 A.C., 40 mA, plus 11.5/14W D.C. 0.2/0.4 amps outputs, very conservatively Government Rated, in small case size 7" x 9 1/2" x 7" Brand New £3, carr. 50p.

Ediswan Stabilised Power Unit Type R1280. 2 independent adjustable outputs (1) 0-300V 150 mA. (2) 0-300V 75 mA, 2 square type Meters used, one for each output, an additional output of 200V, plus 2 L.T. outputs of 6.3V at 4 amps G.T. enclosed in metal case made for Rack Mounting size 19" x 8 1/2" x 17". £15 carr. £2.

Regulated Power Supply Model 500 made by All Power Transformers Ltd., output adjustable 200/600V D.C. 350 mA, and 6.3V at 10 Amps, plus unregulated output, one Square Meter indicating Output current and Voltage, Housed in Metal Case, made for Rack Mounting. Size 19" x 10 1/2" x 13" Price £15 carr. £2.

L.T. Power Units. (1) Output 28V or 34V D.C. 10 amps, 2 Square Meters for Voltage and Current, semi Stabilised, Current overload Trips, for 19" chassis Mounting 19" x 10 1/2" x 14" £14 carr. £2. (2) 28V at 10 amps, adjustable with Current Trip, fully Transistorised Output indicated on 2 Meters Voltage and Amps. 19" Rack Mounting by 10 1/2" x 16" £14 carr. £2.

Advanced Chassis Mounting Power Units. Output 24/25V 10 amps, £10 carr. £2.

Avo Valve Tester No. 3 with Book in Transit Case £15 carr. £2.

Oscillator No. 2 (Air Mek) 20/80mc/s, F.M. or A.M. Mains or 12V D.C. input £15 carr. £2.

Minihred Frequency Analyser D669A with Manual £13 carr. £2.

Terms C.W.O. or uncrossed P.O.s in case stocks run out, so we can refund same.

Johns Radio 424 BRADFORD RD., BATLEY YORKS. Phone: BATLEY 7732



LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8/15 ohm	£21.45
Fane Pop 60 watt 15" 8/15 ohm	£12.26
Fane Pop 50 watt 12" 8/15 ohm	£10.17
Fane Pop 25/2 25 watt 8/15 ohm	£5.94
Fane Pop 15 12" 15 watt 8/15 ohm	£4.40
Fane 122/10a or 122/12	£9.90
Fane Crescendo 15" 8 or 15 ohm	£27.50
Fane Crescendo 12" 8 or 15 ohm	£24.20
Fane 8" d/cone 808T 8 or 15 ohm	£2.64
Fane 8" d/cone, roll surr. 807T 8 or 15 ohm	£3.16
Baker Group 25 3, 8 or 15 ohm	£6.00
Baker Group 35, 3, 8 or 15 ohm	£7.50
Baker De Luxe 12" d/cone	£9.62
Baker Major	£7.50
EMI 13 x 8 3, 8 or 15 ohm	£2.25
EMI 13 x 8 type 150 d/cone 3, 8 or 15 ohm	£2.58
EMI 13 x 8 type 450 t/w 3, 8 or 15 ohm	£3.85
EMI 13 x 8 type 350 8 ohm	£8.25
EMI 6 1/2 93850 4 or 8 ohm	£2.80
Elac 9 x 5 59RMLO9 15 ohm	£2.53
Elac 9 x 5 59RMLL4 8 ohm	£2.53
Elac 6 1/2 d/cone 6RM220 8 ohm	£2.59
Elac 6 1/2 d/cone, roll surr. 6RM171 8 ohm	£3.22
Elac 4" tweeter TW4 8 or 15 ohm	£1.21
Celestion PS8 for Unilex	£2.16
Celestion MFL000 25 watt horn 8 or 15 ohm	£10.45
Elac 5" 3 ohm	£1.75
Elac 7" x 4" 3 or 8 ohm	£1.52
Elac 8" x 5" 3, 8 or 15 ohm	£1.93
Wharfedale Bronze 8 RS/DD	£5.50
Wharfedale Super 8 RS/DD	£9.80
Wharfedale Super 10 RS/DD	£3.80
Goodmans 8P 8 or 15 ohm	£4.49
Goodmans 10P 8 or 15 ohm	£11.55
Goodmans 12P 8 or 15 ohm	£17.05
Goodmans 15P 8 or 15 ohm	£29.70
Goodmans 18P 8 or 15 ohm	£6.79
Goodmans Twinaxiom 8	£7.61
Goodmans Twinaxiom 10	£6.60
Eagle DT33 dome tweeter 8 ohm	£4.95
Eagle HT15 tweeter 8 ohm	£3.46
Eagle CT5 tweeter 8 ohm	£1.21
Eagle MHT10 tweeter	£3.30
Eagle CT10 tweeter	£1.92
Eagle Xovers CN23, 28, 216	£1.10
Kef T27	£4.67
Kef T15	£5.50
Kef B110	£6.16
Kef B200	£7.42
Kef BL39	£10.72
Kefkitt 2	£24.75
Richard Allan 12" d/cone 3 or 15 ohm	£2.20
Richard Allan 8" 3, 8 or 15 ohm 10" x 6" 3, 8 or 15 ohm	£2.27
8" x 5" 3 or 8 ohm	£1.92
7" x 4" 3 or 8 ohm	£1.38
3" 8 ohm or 80 ohm	£1.38
24" 64 ohm	£.65
24" 64 ohm	£.65
Speaker matching transformer 3, 8 or 15 ohm	£1.10
Adasta Hiten 10" 10 watt 8 or 15 ohm	£2.80
Adasta Top 20 12" 25 watt 8 or 15 ohm	£6.32

Stephenspeaker kits and cabinets—send for illustrated brochure and list of recommended speakers.

Car stereo speakers—ask for leaflet.

PA/Disco amplifiers (carr. and ins. £1.00):

Baker 100 watt ... £46.00

Linear 30/40 ... £25.00

Linear 40/60 ... £30.00

Linear 80/100 ... £50.00

FREE with speaker orders over £7 "Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect.

Carriage and insurance 25p per speaker.

(Tweeters and Crossovers 15p each.)

All prices quoted inclusive of V.A.T.

WILMSLOW
AUDIO, Dept. PW
Swan Works, Bank Square,
Wilmslow, Cheshire, SK9 1HF

U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS
7 element 2.25. 11 element 2.75.
14 element 3.25. 18 element 3.75.

WALL MOUNTING c/w WALL ARM & BRACKET

7 element 3.25. 11 element 3.75. 14 element 4.25. 18 element 4.75. CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT. 7 element 4.00. 11 element 4.50. 14 element 4.75. 18 element 5.25. MAST MOUNTING arrays only. 7 element 2.25. 11 element 2.75. 14 element 3.25. 18 element 3.75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 99p yd. KING TELEBOOSTERS from 3.75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7.50. State clearly channel number required on all orders. P.p. on all aerials 50p. Accs. 15p C.W.O. Min. C.O.D. charge 25p.

BBC—ITV—FM AERIALS
BBC (band 1) WALL S/D 2.00. LOFT inverted 'TV' 1.25. EXTERNAL 'H' array only 3.00. ITV (band 3) 5 element loft array 2.50. 7 element 3.00. COMBINED BBC—ITV, loft 1+5 2.75. 1+7 3.50. WALL & CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from 3.75. COMBINED U.H.F.—V.H.F. aerials 1+5+9 4.00. 1+5+14 4.50. 1+7+14 5.00. F.M. RADIO loft S/D 1.00 3 element 3.25. 4 element 3.50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P.p. all aerials 50p. Accs. 30p. C.W.O. Min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS
40-41 MARONCH PARADE, LONDON
ROAD, MITCHAM, SURREY
Telephone 01-648 4884

B.H. COMPONENT FACTORS LTD.
VAT: Please add V.A.T. at the standard rate after April 1st.

SPECIAL RESISTOR KITS. (1W or 1/4W 5% Carbon Film) 10E12KIT, 10 each. £12 value, 10ohms-1M 25E12KIT, 25 each. £12 value, 10ohms-1M

A total of 1625. £6.50 net
MULLARD POLYESTER C280 250V. (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 3p, 0.068, 0.1, 0.15, 4p, 0.22, 2p, 0.33, 7p, 0.47, 8p, 0.68, 10p, 1.0, 18p, 1.5, 20p, 2.2, 3p.

MULLARD POLYESTER C296: 160V. (µF) 0.01, 0.015, 0.022, 2p, 0.047, 0.068, 3p, 0.15, 0.22, 4p, 0.33, 5p, 0.47, 6p, 0.68, 1.0, 1.5p, 400V: (µF) 0.001, 0.0015, 0.0022, 0.0033, 0.01, 2p, 0.015, 0.033, 3p.

MULLARD ELECTROLYTIC C426. 5p, each. (µF/V) 0.64/64, 1.6/25, 3.2/10, 4/40, 10/40, 10/16, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/16, 4, 125/16, 125/10.

HI-VOLT ELECTROLYTIC: 8/350, 12p 16/350, 17p, 32/350, 22p, 50/250, 15p, 32/350, 22p, 100/600, 80p, 1000/12, 10p, 1000/25, 2000/12, 2500/12, 15p, 1000/50, 35p, 2000/25, 25p, 2500/25, 30p, 3000/50, 65p, 5000/50, 85p, 2500/50, 55p, 1000/100, 80p.

CARBON FILM RESISTORS. 1/4W, 5% 10ohms-22M; 1/4W 5% 22Ω-1M 1p, each or 100 for 5p.
METAL FILM RESISTORS. 1W 5% 27Ω-10M 1p each or 100 for 21.

VEROBOARD 0-1 0-15 CARBON POTS
2 1/2" x 6" 25p 5K-2M Log and Lin
2 1/2" x 3 1/2" 23p 17p single 15p, dual
3 1/2" x 5" 29p 30p with SW. 24p, single
3 1/2" x 3 1/2" 25p 25p 42p

5 Pin DIN Plug 15p, Skt. 10p Single SHREED WIRE
3 Pin DIN Plug 13p, Skt. 10p 9p, stereo 9p, quad
5 Pin DIN Plug 18p, Skt. 12p. 19p.
Red Panel Neon 240V. 15p.
Preset Skeleton Pots 1K-1M 5 for 20p
Neon Bulb 90V, wire ended 5 for 20p
1N4001, 6p, 1N4002, 7p, 1N4003, 8p, 1N4004, 9p
1N914, 6p, 7400N, 15p, 7401-7410-7430, 15p
2N700, 10p, µL914, 30p, BC108, 11p, BFY51, 20p
C.W.O. ps 10p. Discount £10-10%. The above items are only a few taken from our catalogue which is available free. Money back refund.

Dept. PW, 61 CHEDDINGTON RD., PITSTONE
LEIGHTON BUZZARD, BEDS., LU7 9AQ.
Tel.: Cheddington 688446 (STD Code 0298)

SPECIAL OFFER !!!

SMALL ELECTROLYTICS

Ref. No.	Capacity	Voltage	Price	Ref. No.	Capacity	Voltage	Price
H8/1	1µf	150v	4p	H7/4A	64µf	35v	5p
H8/1A	2µf	150v	2p	H7/5	80µf	15v	5p
H8/2	2-2µf	25v	4p	H7/6	100µf	25v	5p
H8/2A	3-3µf	25v	4p	H7/6A	100µf	15v	4p
H8/3	3µf	50v	4p	H7/7	100µf	25v	4p
H8/3A	4µf	50v	4p	H7/8	125µf	16v	5p
H8/4	4-7µf	25v	4p	H7/8A	100µf	35v	6p
H8/4A	5µf	64v	4p	H7/9	100µf	63v	6p
H8/5	5µf	10v	4p	H7/10	125µf	4v	6p
H8/5A	5µf	150v	4p	H7/10	125µf	25v	5p
H8/6A	10µf	10v	4p	H7/10A	160µf	2-5v	3p
H8/7	10µf	70v	4p	H7/11	160µf	25v	6p
H8/8	16µf	35v	4p	H7/11A	150µf	16v	5p
H8/8A	16µf	16v	4p	H7/13A	200µf	25v	8p
H8/9	20µf	6v	2p	H7/14	220µf	50v	10p
H8/9A	20µf	70v	4p	H7/14A	220µf	16v	6p
H8/10	22µf	50v	4p	H7/15	220µf	25v	5p
H8/10A	22µf	100v	4p	H7/15A	220µf	35v	10p
H8/11	25µf	12v	4p	H6/1A	250µf	4v	3p
H8/11A	24µf	275v	4p	H6/2	250µf	25v	3p
H8/12	32µf	15v	4p	H6/3A	320µf	2-5v	3p
H8/12A	30µf	10v	4p	H6/4	320µf	10v	4p
H8/13A	32µf	50v	4p	H6/5	330µf	15v	5p
H8/14	40µf	25v	5p	H6/5	330µf	25v	10p
H8/14A	40µf	16v	4p	H6/5A	330µf	35v	15p
H8/15	47µf	50v	4p	H6/7	400µf	15v	5p
H8/15A	40µf	35v	4p	H6/8	470µf	25v	10p
H7/1	50µf	6v	3p	H6/8A	470µf	35v	20p
H7/1A	50µf	10v	4p	H6/9	500µf	15v	4p
H7/2	50µf	50v	4p	H6/10A	400µf	40v	20p
H7/2A	64µf	2-5v	2p	H6/10	750µf	12v	5p
H7/3A	64µf	25v	4p	H6/13A	1000µf	25v	16p
H7/4	64µf	15v	4p	H5/2A	2200µf	16v	15p

POSTAGE: 15p PER ORDER

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series		Working Voltage Vdc.	Capacitance µF	Max. Ripple Current at 50°C	Weight	Price
071 15332	16		3300	2-4 amps	1oz	15p
071 15472	16		4700	3-9 amps	1oz	17p
071 15682	16		6800	5-8 amps	1½oz	22p
071 15103	16		10000	7-9 amps	2½oz	27p
071 18222	63		2200	5-8 amps	3oz	37p
072 15752	16	7500 + 7500		10-5 amps	4½oz	49p
072 15113	16	11000 + 11000		13-8 amps	4½oz	49p
071 16222	25		2200	2-2 amps	1oz	15p
071 16472	25		4700	5-4 amps	1½oz	22p
072 16502	25	5000 + 5000		9-6 amps	3½oz	37p
072 16752	25	7500 + 7500		12-6 amps	4½oz	49p
072 17342	40	3400 + 3400		9-1 amps	3½oz	37p
072 17502	40	5000 + 5000		12-0 amps	1oz	15p
071 18681	63		680	2-1 amps	1oz	15p
072 18172	63	1650 + 1650		7-8 amps	3oz	37p

106 and 107 Series		Capacitance	Weight	Price
106 15103	16	10000	7 amps	2½oz 65p
106 16223	25	22000	17 amps	10oz £1.12
106 17103	40	10000	12 amps	7½oz 94p
106 18153	63	15000	28 amps	18oz £1.79
107 10222	100	2200	10 amps	5½oz 74p

Type No.	Voltage	Capacitance	Weight	Price
102 15163	16	16000	8oz	20p
104 90003	20	39000	16oz	30p
102 16802	25	8000	7oz	25p
104 17562	40	5600	5oz	20p
104 90001	45	20000	16oz	50p
104 18332	63	3300	5oz	25p

A further 10% discount on lots of 100 of any one type.
Please calculate the weight of your order and include appropriate postage.

Not over	Ordinary Parcels	Not over	Ordinary Parcels
14lb	16p	10lb	37p
21b	21p	14lb	47p
41b	25p	18lb	57p
61b	29p	22lb	67p

ALL GOODS PLUS 10% V.A.T.

£1 100 ½ WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

£1 1 VERO-BOARD CUTTER
5 ½ in. x 1 in. x .15 BOARDS
50 SQ. INS. "ODD PIECES"
VERO

£1 20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108 ETC.

£1 6 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS &
CAPACITORS

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

£1 1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT

£1 100 RESISTORS
100 CERAMIC CAPACITORS
(ASSORTED TYPES)

INDEX TO ADVERTISERS

Amtron U.K.	35
Antex Ltd.	19
Apex Aerials	90
Arrow Electronics Ltd.	39
Astro Electronics	82
B.H. Components Factors Ltd.	94
Baines, R.	90
Baker Loudspeakers Co.	62
Bedford Electronics	93
Bell's Television	90
Bernard, Gerald	12
B.I.E.T.	70, Cov iii
Bi-Pak Semiconductors	15, 16, 17
Bi-Pre-Pak Ltd.	69
Boffin Projects	93
British National Radio & Electronic School	Cov ii, 59
Broadway Electronics	70
Bull, J. (Electrical) Ltd.	83
Bush & Meissner	93
C.C.I.L. Ltd.	6
Caranna, C.	90
Chilmead Ltd.	74
Codar	4
Colomor Electronics Ltd.	82
Comet High Fidelity Discount Warehouses	10, 11
Chromasonic Electronics	77
D.E.W. Ltd.	93
Dabar Electronic Products	86
Davian Electronics	62
Denco	90
Discosound	55
Douglas Electronic Industries Ltd.	93
Duke & Co. (London) Ltd.	40
Electrokit	40
Electronic Design Associates	62
Electronic Mail Order (Bury) Ltd.	93
Electrospares	62
Electrovalue	7
Elvins Electronic Musical Instruments	12

Felstead Electronics	86
Future Technatics Ltd.	82
Galleon Trading	92
Gladstone Radio	86
Global Audio Discount Warehouse	18
Golledge P.R.	92
Greenweld Electronics	92
HAC Short-wave Products	66
Harverson Surplus Co. Ltd.	73
Heath (Gloucester) Ltd.	31
Henry's Radio Ltd.	61, Cov iv
Home Radio (Components) Ltd.	74
I.C.S.	12, 91
Imperial Trading	90
Ivoryet Ltd.	6
Jef Electronics	92
Jermyn Industries	5, 18
Johns (Radio) Ltd.	92, 94
Johnson & Johnson Ltd.	74
K.V.A. Electronics	94
Kensington Supplies	91
Keytronic	14
Kilrimont Books	90
Lasky's Radio Ltd.	8
Lewis Radio	36
Linear Products Ltd.	6
London Computer Operators Training Centre	91
Maplin Electronic Supplies	66
Marco Ltd.	92
Marshall, A. & Son	32
Milward G. F.	95
Minikit Electronics	91
Multicore Solders Ltd.	6
O'Driscoll	93

Padgetts Radio Store	44
Partridge Electronics Ltd.	8
Pembridge College	82
Photain Controls	94
Phonosonics	70
Radio Component Specialists	84, 85
Radio Book Services	90
Radio Exchange Co. Ltd.	13
Radio & T.V. Components (Acton) Ltd.	20, 21
Radio Society of Great Britain	14
Raymer Electronics Ltd.	62
Readers Radio	36
Redhawk Sales	92
Riversdale Electronics	59
RDI	93
RSC (Hi-Fi Centres) Ltd.	2, 3
R.S.T. Valve Mail Order Co.	66
S.C.S. Components	44
Saxon Entertainments	9
Scientific & Technical	8
Selray Book Co. Ltd.	4
Semicon Index Ltd.	90
Sinclair Radionics Ltd.	88, 89
Shopertunities Ltd.	43
Smith, G. W. & Co. Ltd.	78, 79, 80, 81
Surplelectronics	36
Swanley Electronics	66
Tektronix	91
Teleradio Co. Ltd.	91
Thacker, A. H. & Sons Ltd.	40
Tidman Mail Order	91
Trade Aids	14
Trade Disposals	91
Trampus Electronix	92
Trannies	87
Tuac Ltd.	65
Web Europa	12
West London Direct Supplies	14
Weyrad Electronics Ltd.	70
Wilmslow Audio	44, 94
York Electrics	18
Z & I Aero Services Ltd.	96

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*. Write to B.I.E.T. Dept. BPW04 Aldermaston Court, Reading RG7 4PF.

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-534 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2-65.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

MECHANICAL	Man. Prod.—cont.	Constructional-cont.
A.M.S.E. (Mech.) <input type="checkbox"/>	Quality Control <input type="checkbox"/>	Building <input type="checkbox"/>
Boiler Inspect. <input type="checkbox"/>	Salesmanship <input type="checkbox"/>	Building Drawing <input type="checkbox"/>
C & G Eng. Crafts <input type="checkbox"/>	Storekeeping <input type="checkbox"/>	Build. Foreman <input type="checkbox"/>
C & G Fabricat. <input type="checkbox"/>	Work Study <input type="checkbox"/>	Carpentry & Join. <input type="checkbox"/>
Diesel Eng. <input type="checkbox"/>	Works <input type="checkbox"/>	Civil & Municipal <input type="checkbox"/>
Eng. Inspection <input type="checkbox"/>	Management <input type="checkbox"/>	Engineering <input type="checkbox"/>
Eng. Metallurgy <input type="checkbox"/>	DRAUGHTSMANSHIP <input type="checkbox"/>	Constructional <input type="checkbox"/>
Inst. Eng. & Tech. <input type="checkbox"/>	A.M.I.E.D. <input type="checkbox"/>	Engineering <input type="checkbox"/>
Inst. Motor Ind. <input type="checkbox"/>	Design of Elec. <input type="checkbox"/>	Construction <input type="checkbox"/>
Mainten. Eng. <input type="checkbox"/>	Machines <input type="checkbox"/>	Surveyors <input type="checkbox"/>
Mechanical Eng. <input type="checkbox"/>	Die & Press Tool <input type="checkbox"/>	Institute <input type="checkbox"/>
Sheet Metal Work <input type="checkbox"/>	Design <input type="checkbox"/>	Clerk of Works <input type="checkbox"/>
Welding <input type="checkbox"/>	Electrical <input type="checkbox"/>	Council Eng. <input type="checkbox"/>
	Draughtsmanship <input type="checkbox"/>	Geology <input type="checkbox"/>
	Gen. Draughtsmanship <input type="checkbox"/>	Health Eng. <input type="checkbox"/>
ELECTRICAL & ELECTRONIC	Jig & Tool Des. <input type="checkbox"/>	Heat & Vent. <input type="checkbox"/>
A.M.S.E. (Elec.) <input type="checkbox"/>	Tech. Drawing <input type="checkbox"/>	Hydraulics <input type="checkbox"/>
C & G Elec. Eng. <input type="checkbox"/>	RADIO & TELE-COMMUNICATIONS <input type="checkbox"/>	Inst. of Builders <input type="checkbox"/>
C & G Elec. Inst. <input type="checkbox"/>	Colour TV <input type="checkbox"/>	Inst. Works & <input type="checkbox"/>
C & G Elec. Tech. <input type="checkbox"/>	C & G Radio/TV/ <input type="checkbox"/>	Highway Sup. <input type="checkbox"/>
Computer Elect. <input type="checkbox"/>	Electronics <input type="checkbox"/>	Painting & Dec. <input type="checkbox"/>
Elec. Maths <input type="checkbox"/>	C & G Telecomm. <input type="checkbox"/>	Public Hygiene <input type="checkbox"/>
Elec. Science <input type="checkbox"/>	Tech. <input type="checkbox"/>	Road Engineer. <input type="checkbox"/>
Electronic Eng. <input type="checkbox"/>	Prac. Rad. Elec. <input type="checkbox"/>	Structural Eng. <input type="checkbox"/>
Electrical Eng. <input type="checkbox"/>	(with kit) <input type="checkbox"/>	Surveying <input type="checkbox"/>
Install. & Wiring <input type="checkbox"/>	Radio Amateurs <input type="checkbox"/>	GENERAL
Meters <input type="checkbox"/>	Exam. <input type="checkbox"/>	Agricultural Eng. <input type="checkbox"/>
& Measuring <input type="checkbox"/>	Radio Servicing <input type="checkbox"/>	Council of Eng. <input type="checkbox"/>
Instruments <input type="checkbox"/>	& Repairs <input type="checkbox"/>	Farm Science <input type="checkbox"/>
MANAGEMENT & PRODUCTION	Radio & TV Eng. <input type="checkbox"/>	General Educat. <input type="checkbox"/>
Auto. Control <input type="checkbox"/>	Trans. Course <input type="checkbox"/>	Gen. Plastics <input type="checkbox"/>
Computer Prog. <input type="checkbox"/>	TV Main. & Serv. <input type="checkbox"/>	Pract. Maths <input type="checkbox"/>
Electronic Data <input type="checkbox"/>	AUTO & AERO <input type="checkbox"/>	Pract. Slide Rule <input type="checkbox"/>
Processing <input type="checkbox"/>	Aero Eng. <input type="checkbox"/>	Pure & Applied <input type="checkbox"/>
Estimating <input type="checkbox"/>	A.M.I.M.I. <input type="checkbox"/>	Maths <input type="checkbox"/>
Foremanship <input type="checkbox"/>	A.E.C. Cert. <input type="checkbox"/>	Refrigeration <input type="checkbox"/>
Inst. Cost & Man <input type="checkbox"/>	Auto Engineer. <input type="checkbox"/>	Rubber Tech. <input type="checkbox"/>
Accountants <input type="checkbox"/>	Auto Repair <input type="checkbox"/>	Sales Engineers <input type="checkbox"/>
Inst. Marketing <input type="checkbox"/>	C & G Auto. Eng. <input type="checkbox"/>	Tech. Report <input type="checkbox"/>
Management <input type="checkbox"/>	Garage <input type="checkbox"/>	Writing <input type="checkbox"/>
Metrication <input type="checkbox"/>	Management <input type="checkbox"/>	Timber Trade <input type="checkbox"/>
Motor Trade Man. <input type="checkbox"/>	MAA/IMI Dipl. <input type="checkbox"/>	University Ent. <input type="checkbox"/>
Network Plan. <input type="checkbox"/>	Motor Vehicle <input type="checkbox"/>	
Numerical Cont. <input type="checkbox"/>	Mechanics <input type="checkbox"/>	
Operational <input type="checkbox"/>	CONSTRUCTIONAL <input type="checkbox"/>	
Research <input type="checkbox"/>	A.M.S.E. (Civil) <input type="checkbox"/>	
Personnel Man. <input type="checkbox"/>	Architecture <input type="checkbox"/>	
Planning Eng. <input type="checkbox"/>		
Production Eng. <input type="checkbox"/>		

Coaching for many major exams. including ONC, C & G, etc.

G.C.E.

58 'O' & 'A' LEVELS SUBJECTS

Over 10,000 group passes

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW04 Aldermaston Court, Reading RG7 4PF

QN BPW04

NAME _____

Block Capitals Please

ADDRESS _____

OTHER SUBJECTS _____ AGE _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

BUILD THE TEXAN

★ FREE TEAK CABINET with complete kits!

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector; Mag. P.U Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).
Constructional details Ref. No. 21 30p

SPECIAL KIT PRICE

£28-50

P & P 45p

COMPLETE WITH FREE TEAK CABINET
Designer approved kits distributed by Henry's!

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



★ SLIM DESIGN WITH SILVER TRIM
Overall chassis size 14 1/2" x 6" x 2" high

ELECTRONIC KITS
Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

IC RECEIVER
ZN414 Radio integrated circuit as featured in Practical Wireless, January 1973, Practical Electronics, February 1973. Price £1 20.

BATTERY TAPE DECK
Garrard 9 volt Tape Deck with heads, etc. As previously advertised. Limited quantity. £9 50, post 30p.

LEARN A LANGUAGE
Recorded Cassettes with step by step phrase books. French, German, Spanish Italian. £16 course. £5 00 per set of four.

DISCO SPOTBANK
3 channel Disco Spotbank for use with any psychodelic lighting display. £12 75, p. & p. 35p.

HI-FI EQUIPMENT
Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES. FREE—24 page detailed brochure (Ref. No. 17). You can see the savings!

HIGH QUALITY CASSETTES
The best UK low noise tapes but at a special price. Living Sound cassettes meet the highest international standard (IEC 94A). Fantastic price savings.

	RRP each	3 for	6 for	10 for
C60	70p	1 00	1 80	2 80
C90	97p	3 32	5 74	2 20
C120	1 47	1 62	3 15	5 00

Full guarantee. Post paid.
Made by EMI especially for Henry's. See earlier page of this magazine for transistors and semi-conductor devices.

ULTRASONIC TRANSDUCERS
Operate at 40Kc up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits. £5 90 per pair. Post 10p.

MARRIOTT TAPE HEADS
4 TRACK MONO or 2 TRACK STEREO
'17' High Impedance £2 00
'18' Med. Impedance £2 00
'36' Med.-Low Imp. £3 50
Erase Heads for above 75p
'63' 2 track mono—Hi Imp. £1 75
'43' Erase Head for above 75p

7 SEG & NIXIE TUBES
(Post 15p per 1 to 6)
XN3, XN13, GN6 0-9 side view with data, 85p.
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
3015F 7 seg £2 each. £7 per 4 with data.
12 and 24 hour clock circuits Ref. No. 31 15p.

Miniature Amplifier
5 transistor, 300mW o/p. Fitted volume and sensitivity control, 9 volt operated. £1 75 each P/P 15p.

Quality Slider Controls
60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K. 1 meg. Log and Lin. 40p each, 10K, 25K, 50K, 100K, 250K, Log and Lin ganged. 60p each.

LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt 3, 8 or 15 ohms £2 20. Post 22p.
TYPE 152 TC Twin cone version £2 75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3 85. Post 25p.
TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7 70. Post 28p.



POLISHED CABINETS 150, 150TC 450 £4 60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 ohms)
SERIES 6 (Assembled 150 T/C) per pair £16 50. Post 70p
SERIES 8 (Assembled 450) per pair £18 95. Post 70p

TEST EQUIPMENT

Just a selection!
SE250B Pocket Pencil Signal Injector £1 90
SE500 Pocket Pencil Signal Tracer £1 50
THL33D Robust 2K/Volt £4 55 with case £4 95
TE15 Grid Dip Meter 440 KHz-280 mHz £13 45
500 30 K/V Multimeter £9 25
200H 20K/V Multimeter £4 20. With case £4 95
AF105 50K/V Multimeter £8 50. With case £9 50
U4341 A/C/D Multimeter with transistor tester with steel case £10 50
TE20D RF Generator 120KHz-500MHz £15 95. Carr. 35p
TE22D Audio Generator 20Hz-200KHz £17 50. Carr. 35p
CL5 3" Pulse Scope 10Hz-10MHz £39 00. Carr. 50p
TE65 Valve Voltmeter 28 ranges £17 50. Carr. 40p
ALL NOMBREX MODELS IN STOCK



ML-3 MW/LW TUNER to BUILD
Use Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4 85. Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD
Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning. 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7 98. p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

PA-Disco-Lighting
UK's Largest Range—Write phone or call in. Details and demonstrations on request.
DJ30L 3 Channel sound to light unit, 3KW. £29 50
DJ40L 3 channel Mic (built-in) to light, 3kW. £38 75
DJ70S 70 watt Disco amp/mixer. £49 75
DISCOAMP 100 watt amp/mixer. £68 85
DJ105S 30 watt Disco amp/mixer. £32 25
Anti-Feedback Quality Mic. £11 50
DJ500 50 watt PA Amplifier £43 95
DJ700 70 watt £52 75
GROUP 300 150 watt rms "Group" Valve Amplifier £86 00
FIBRE OPTICS LIGHTING. — MICS. EFFECTS. PROJECTORS. SPOTS. DIMMERS — STANDS. MIXERS. SPEAKERS.
Everything for PA—Disco—Lighting.
FREE Stock List Ref. No. 18
● PORTABLE DISCOS—DETAILS ON REQUEST
● CREDIT TERMS FOR CALLERS

BUILD THIS VHF FM TUNER
5 TRANSISTORS 300 kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.
TOTAL £6 97, p.p. 20p. Decoder Kit £5 97.
Tuning meter unit £1 75
Mains unit for Tuner and/or Decoder PS6/12 £3 25. Post 20p

SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!
Z30 £3 57; Z50 £4 37
STEREO 60 PZ5 £3 97
£7 97; PZ8 £4 77
PZ6 £6 37;
Transformer for PZ8 £2 95
Active Filter Unit £4 45
Stereo FM Tuner £16 95
IC12 £1 80; Q16's £15 pr.
Post etc. 20p per item

PACKAGE DEALS
Post 25p
2xZ30, Stereo 60, PZ5 £15 95
2xZ30, Stereo 60, PZ6 £18 00
2xZ50, Stereo 60, PZ8 £20 25
Transformer for PZ8 £2 95
PROJECT 60S KIT £19 95

CATALOGUE
Fully covered and illustrated detailing every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.
PRICE 55p Post Paid (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS
Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to "303" see above.

VAT Prices DO NOT include Value Added Tax. From 1st April, 1973 10% must be added and shown separately to your total order (inclusive Post/packing). Help us to help you receive your order without delay. E. & O.E.

Henry's LIMITED

EDGWARE ROAD, W2

454-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open: 9 am-6 pm
6 days a Week
(303 closed Thursday)
All stores open all day Saturday