

PRACTICAL WIRELESS

JUNE
1975

30p

digital waveform generator




also



DIRECT CONVERSION RECEIVER

& REPAIRING HI-FI AMPLIFIERS

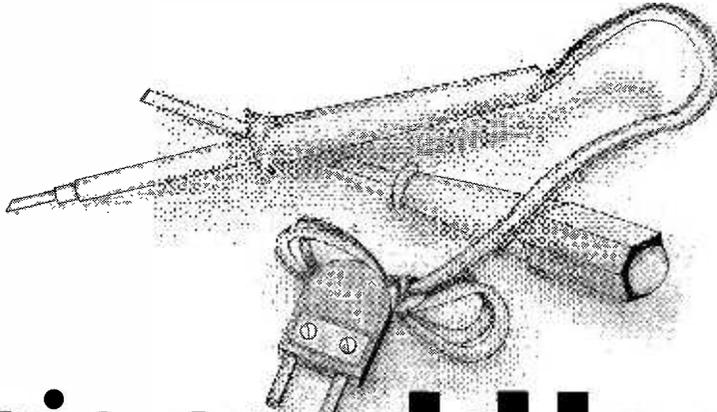

This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1


Build an oscilloscope.

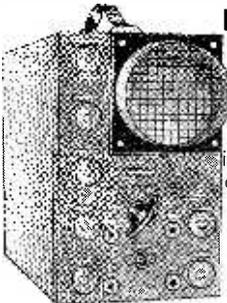

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2

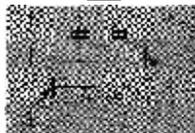Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

Carry out over 40 experiments on basic circuits.



We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS



FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WL/65
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)

PRACTICAL WIRELESS

VOL. 51 NO. 2

ISSUE 820

JUNE 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metall

TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

PRODUCTION & NEWS EDITOR

Colin R. Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder
Susan King

ADVERTS MANAGER

01-634 4293

Roy Smith

CLASSIFIED ADVERTS

01-634 4301

Collin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £5.00 and to the rest of the world £5.00 (\$13.50 USA/CAN) including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.90) and Indexes 30p (Inc. VAT) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 112 LEGISLATION—Editor's comment
- 113 NEWS . . . NEWS . . . NEWS . . .
- 130 HOTLINES on recent developments by *Ginsberg*
- 131 NEXT MONTH IN PRACTICAL WIRELESS
- 140 PRODUCTION LINES by *Colin Riches*
- 146, 147 LETTERS—Readers comment
- 148 ON THE AIR
- 148 Amateur Bands—*Eric Dowdeswell, G4AR*
- 149 Broadcast Bands—Short Waves—*Derek Bell*
- 150 Broadcast Bands—Medium Waves—*Charles Molloy*
- 158 TELEVISION—coming in the June issue

● CONSTRUCTIONAL

- 114 DIRECT CONVERSION RECEIVER—*R. H. Longden*
- 126 P.W. 'EASYBUILD' ELECTRONIC ORGAN—Part 4—*M. J. Hughes, M.A., C.Eng., MIERE*
- 132 DIGITAL WAVEFORM GENERATOR—Part 1—*John Smith*
- 137 P.W. 'APOLLO' Series—Sweep Oscillator Techniques—Part 2—*W. Poel*
- 153 EXPERIMENTAL WORKSHOP—No. 15—*M. J. Hughes, M.A., C.Eng., MIERE*

● OTHER FEATURES

- 121 IC OF THE MONTH—SN76023N Audio Amplifier
- 125 TECHNICROSS—No. 9
- 142 REPAIRING HI-FI AMPLIFIERS—*H. Leeming, G3LLL*
- 145 GOING BACK—Earlier days of Wireless—*Colin Riches*

HUGE DISCOUNTS

ON LEADING BRAND HI-FI ALL RSC PRICES INCLUDE VAT
LOW DEPOSIT CREDIT TERMS

Full labour and material guarantees for 12 months

	Rec. Price	RSC Price
LINEAR 202 Amplifier	£39-23	£24-95
LINEAR 505 Amp 5 + 5w	£19-75	£16-95
AUDIO FIDELITY Model 60 Amp	£59-95	£45-95
WHARFEDALE LINTON Amp	£68-04	£49-95
LEAK 2100 Amplifier	£119-75	£92-95
LEAK 2002 Cassette	£139-50	£108-95
LEAK 2030 L/ Speakers	£94-50 Pr	£69-00
LEAK 2060 L/ Speakers	£83-50 Ea	£57-50
LEAK 2000 Tuner/Amp	£193-50	£149-50
ROTEL RX150A Tun/Amp	£84-50	£59-95
ROTEL RX152 Tun/Amp	£94-50	£67-95
ROTEL RX202 Tun/Amp	£107-50	£77-95
ROTEL RX402 Tun/Amp	£145-00	£104-95
ROTEL RT222 Tuner	£59-90	£42-50
ROTEL RT322 Tuner	£84-50	£59-95
WHARFEDALE Denton I L/Spkr	£33-78 Pr	£22-95
WHARFEDALE Denton II L/Spkr	£47-50 Pr	£31-95
WHARFEDALE Linton II L/Spkr	£59-75 Pr	£39-95
FANE Ambassador 35 L/Spkr	£89-00 Pr	£69-50
FANE MARQUESS 30 L/Spkr	£75-00 Pr	£49-95
FANE Model One Spkr Kit	£23-98 Pr	£18-95
WHARFEDALE Linton II Kit	£28-90 Pr	£19-50
WHARFEDALE WHD20 Cassette	£103-68	£76-95

BASF CASSETTES (Carr. Free)

LH CASSETTES in Snap Pack		SUPER SM CASSETTES in Snap Pack	
Rec. Price	RSC Price	Rec. Price	RSC Price
C60 98p	65p	3.00	4.99
C90 1-36	90p	3.99	6.99
C120 1-87	1-20	5.50	9.90
		1-08	80p
		1-05	4-75
		1-94	1-46
		6-75	12-95

Also Shure Cartridges, Bass Tape, Koss H/Phones, etc. Prices of above correct at April 7 1975

RSC G66 MkII 6.6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 — 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT BOARD AND INSTRUCTIONS £12.95 Carr. 40p



OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.95 or Dep. £2-12 and 8 monthly payments £2-12 (Total £10-08).

AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE. Exceptional performance at low cost.

HF808T	8"	10W	£2-85	HF180D	12"	15W	£5-50
HF102D	10"	10W	£3-50	HF180L	12"	15W	£7-95
HF120	12"	15W	£5-95	HF180D	12"	15W	£8-50

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET

Only high grade components by leading manufacturers

- * Push Button Selector Switching
- * Jack Socket for Headphones
- * Neon Indicator
- * Satin Silver Finish Metal Fascia
- * Solid State Circuitry
- * Twenty Silicon Transistors
- * Four Diodes, Four Rectifiers

Send S.A.E. for leaflet



COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £22-95. £4-90 extra.

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.	TOP SHROUDED DROP-THERO TYPE
250v., 60mA, 6.3v. 2a. £1-50	250-0-250v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a. £2-25
250-0-250v., 60mA, 6.3v. 2a. £1-60	250-0-250v. 100mA, 6.3v. 3a., £2-50
	250-0-250v. 100mA, 6.3v. 2a., 0-5-6.3v. 1a. £2-50
	350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. £2-75
	250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-75
	300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-75
	300-0-300v. 100mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-75
	300-0-300v. 130mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-50
	350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-75
	350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-50
	350-0-350v. 150mA, 6.3v. 4a., c.t., 5v. 3a. £2-50
	425-0-425v. 200mA, 6.3v. 4a., Twice 5v. 3a. £2-70
	450-0-450v. 250mA, 6.3v. 4a., c.t., 5v. 3a. £2-90

AKAI TAPE UNITS

	Rec. Price	RSC Price		Rec. Price	RSC Price
CS30D	£91-23	£64-95	GXC75D	£209-89	£149-95
CS33D	£111-08	£79-95	GXC510D	£199-39	£135-95
GXC36D	£116-24	£72-50	CR81D	£98-10	£69-95
GXC38D	£144-23	£102-95	GXR82D	£128-77	£92-95
GXC38	£154-53	£109-95	1722L	£146-37	£105-95
GXC40T	£195-35	£139-95	4000DS	£136-59	£97-95
GXC46D	£165-47	£115-95	4000DB	£196-27	£139-95
GOLDRING GL72 T/Table & G800	£29-95				
GOLDRING GL75 T/Table & G800	£34-95				
PIONEER PL12D T/Table on plinth & cover	£41-75	List £61-90			
T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER					
GARRARD SP25 MK IV with G850	Special Price £23-95	(Carr. £1)			
RANK BD2000	Rec. Price £67-25	RSC Price £48-95			

FANE HIGH FIDELITY SPEAKERS

Limited number at approximately half list prices.

Model	Special Price	Model	Special Price
5" 501	8 ohms £5-20	12" 122/14*	8 & 15Ω £11-50
8" 804*	8 ohms £3-65	12" 122/14LR	8Ω £12-95
10" 1005LR	15Ω £5-75	12" 122/17*	8 & 15Ω £12-95

Available by Mail Order carr. free or may be ordered through Branches *Basic models made to individual specification of equipment manufacturers


HI-FI 7 Watt LOUDSPEAKERS fitted Parasitic Tweeter Imp 8Ω

8" x 5" £1-25 ea. 6 1/2" £1-45 ea. 8" £1-85 Carr. 20p

HI-FI SPEAKER ENCLOSURES

Simulated Teak finish Sizes approx. Carr. 50p per enc.

ME8 13 x 9 1/2 x 6 1/2 in.	£3-95	Both cut for 8in. speaker	£8-95
JE8 16 x 11 x 9 in.	£5-95	Cut for 10in. and Tweeter	£8-95
SE10 25 x 16 x 9 in.		Cut for 12in. and Tweeter	£8-95
SE12 25 x 16 x 9 in.			

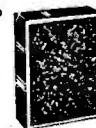

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 Gauss 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. OR SENIOR 15 WATT INCLUDING HF123 13,000 GAUSS SPEAKER

£6-95 Carr. 45p
£8-95 Carr. 50p

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operation. Response 30-20,000 c.p.s. -2dB. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm speakers. Max. sensitivity 5mV. O/P rating I.H.F.M. Enclosed enamelled case 9 1/2 x 2 1/2 x 6 1/2 in. Silver finish fascia 10 1/2 x 3 1/2 in. COMPLETE KIT, wiring diagrams and instructions. £7-95 Carr. 40p. FACTORY BUILT £10-95

AUDIO FIDELITY MODEL 80 HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 8-15 Ω. £5-40 ea. £7-98 pr.

MODEL 83 8" 15w. with parasitic Tweeter. £6-99 ea. £10-95 pr. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 8-15Ω.

AUDIO FIDELITY FRI SPEAKER KIT

Response 30 Hz-15 KHz. Rating 15 watts in sealed cabinet. Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material. Screws. Terminal Panels. Carr. Free. SPECIAL OFFER £15-99 Pair Carr. 50p



SELENIUM RECTIFIERS F. W. (Bridged)	CHARGER TRANSFORMERS	OUTPUT TRANSFORMERS
All 6 1/2in. D.C. output. Max. A.C. input 18v.	0-9-15v. 1 1/2a. £1-75	0-110/120v. 200-250v. 50-80 watts £2-50
1a. 85p. 2a. 49p. 3a. 65p. 4a. 81p. 6a. 87p.	2 1/2a. £1-95; 3a. £2-00; 4a. £2-25; 5a. £2-50	150 watts, £4-50; 250 watts, £5-50; 500 watts, £7-50
L.F. CHOKES	AUTO (Step UP/step DOWN) TRANSFORMERS	350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. £2-75
150mA, 7-10V. 250 Ω £1-10; 100mA, 10H, 200 Ω 95p; 60mA, 10H, 400 Ω 85p.	350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-75	300-0-300v. 100mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-75
	300-0-300v. 100mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-75	300-0-300v. 130mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-50
	350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-50	350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-50
	350-0-350v. 150mA, 6.3v. 4a., c.t., 5v. 3a. £2-50	350-0-350v. 150mA, 6.3v. 4a., c.t., 5v. 3a. £2-50
	425-0-425v. 200mA, 6.3v. 4a., Twice 5v. 3a. £2-70	425-0-425v. 200mA, 6.3v. 4a., Twice 5v. 3a. £2-70
	450-0-450v. 250mA, 6.3v. 4a., c.t., 5v. 3a. £2-90	450-0-450v. 250mA, 6.3v. 4a., c.t., 5v. 3a. £2-90

RSC 100 watt DISCO SYSTEM

50 WATT SPEAKER **50 WATT SPEAKER**

TWIN TURNTABLE WITH PRE-AMP and POWER AMPLIFIER

AT FANTASTIC LOW PRICES!

Complete with lid **HEADPHONES MICROPHONE**

- Units listed below
- (a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier
 - (b) PAIR OF HI-FI HEAD- PHONES
 - (c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
 - (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"
- (a) (b) (c) & (d) Carr. £3-90 **£159-95**

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BBE MP60 type turntables and Sonotone Acco Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid. Terms of illustration on left.

Or DEP. £9-00 and 18 fortnightly pymts. £4-61 (Total £91-98) Carr. £1-50

£79-95

DEP. £19-95 & 18 fortnightly payments of £9-11 (Total £183-93).

STEREO VERSION of Above System Or DEPOSIT £28-95 and 18 fortnightly pymts. £11-11 (Total £229-95) Carr. £3-50 **£199-95**

TD2S STEREO VERSION OF ABOVE Terms DEPOSIT £15 and 18 fortnightly payments £8-51 (Total £152-18) Carr. £1-60 **£115-00**

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £109-95 Carr. £2-50

Garrard SP25 or McDonald MP60 turntables. Sonotone or Acco cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £12-95 and 18 fortnightly payments £8-31 (Total £128-53)

STEREO VERSION £145 (Total £186-70). Carr. £3

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Vynide and Vynair

TYPE C38 40-50 WATTS Incorporating three exceptionally efficient 8" speaker units. Terms: DEP. £2-95 and 8 monthly payments £2-87 (Total £23-91) Carr. 65p. **£21-95**

TYPE C370 70 WATTS Fitted three 12" 25 watt highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5-11 & 8 monthly pymts. £5-11 **£39-95** (Total £45-99) Carr. 85p

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
£31-95	£17-95	£13-95
Dep: £5-80 and 8 monthly payments £2-80 (Total £38-20)	Dep. £3-17 and 8 monthly payments. £2-17 (Total £20-53)	Terms for pairs Dep £6-90 & 8 mthly pymts £2-16 Total £21-18

FOR BASS GUITAR, ELECT. ORGAN, ETC. **PAIR SUITABLE FOR ALL PURPOSES**

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: DEPOSIT £8-75 and 8 monthly payments £8-00 (Total £20-73) Carr. free **£26-73**

FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

'POP' 25/T 12" 25W. Dual cone. 15 ohm Imp. (Not for Bass Guitar use) **£9-95**

PH50 HIGH POWER TWEETER £6-65 with 2 to 4 mfd. Non elect. filter available 55p. Rating 80 Watt Imp 8Ω Response 3KHz 20KHz

D40 FULL RANGE 40 WATT POWER SPEAKER KIT £21-00

Consisting of 12" 40 watt Bass Unit, HPX1 200w Cross-over and PH50 Tweeter. Rating 40w R.M.S. Imp. 8 ohms. Terms: Deposit £5-99 and 8 mthly payments £2-50. (Total £25-99).

TITAN GROUP/DISCO SPEAKERS

as advertised elsewhere in this issue

FULL RANGE AT DISCOUNT PRICES

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE VYNIDE AND VYNAIR FINISH

L12/2 50 WATT Fitted pair of 12" 30 watt high flux speakers for conservative use. Impedance 8-15 ohms. Carr. £1-50

Orating: Output 25-11 and 8 monthly parts. of £3-11. Total £25-99

L12/250 15" 25 WATT 13,000 lines 15 ohm. Terms for Pairs: Dep £3-32 & 8 mthly pymts £2-32 **£12-95** (Total £29-88) Carr. 65p.

L12/10 10-15 Watt Vynide cabinet 12" unit 8-15 ohm. Approx. 14" x 14" x 9". Dep. £3-5p. Terms for Pairs. Dep. £2-05 & 8 mthly pymts £2-05 (Total £18-45). **£7-95**

FAL MAESTRO COMBINED 30W AMP. AND 12" SPEAKER £48-60 Carr. Free

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size Fitted carrying handle. Deposit £2-60 and 8 mthly payments £5-75 (Total £54-60)

RSC 'PHANTOM 50' Rating 50 watts, 3 inputs, 2 vol. controls. Bass, Treble, Presence Terms: Deposit £8-00 & 8 mthly. pymts. £8-76 (Total £28-08). £55-00 Carr. £1-50

FAL PHASE 50 Mk. III AMPLIFIER 50 WATT £48-60 Carr. Free

Solid state. 4 separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speaker's 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or Deposit £8-60 & 8 monthly payments £5-75. Total £24-60. Carr. Free

REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 60w Peak O/P rating. Not for Bass Guitar.

★ Two Fane heavy duty high flux 12in. spkrs.

★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or 'mikes'. Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £9-95, & 18 fortnightly payments of £4-15 (Total £284-65). Carr. £2-50 **£74-95**

REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-40 & 18 fortnightly payments £4-61. £79-95 (Total £91-98). Carr. £2-50

FAL DISCO PRE-AMPLIFIER T/Table mixing inputs Monitoring. Mic. Jack & Tape inputs. Independent Vol. Control. Std. 200-250v A.C. Mains operation £18-50

GP30 AMPLIFIER £29-95 Carr. 75p

For Guitar, Vocal or Instr. Group, Gram, Radio or Tape. 4 inputs. 2 Vol. Controls. Current Valves. Peak o/p rating. Strong Vynide covered cabinet with carrying handles. Black/Silver Facia. Neon Indicator. For 200-250v A.C. For 3 of 15 Ω speakers. Send SAE for leaflet. Terms: Dep £5-58 & 8 mthly pymts £3-58 (Total £24-22) Carr. 75p

LIQUID WHEEL from PROJECTORS £24-75

COMPLETE £99-95 PULSAR

'SOUND TO LIFE' SYSTEM

AT A WORTHWHILE SAVING ON INDIVIDUAL UNITS purchased separately. Terms: Deposit £11-48 and 18 fortnightly payments £3-74. (Total Credit Price £114-80). Super SL Unit. 1000 watt per channel. Manual override buttons, 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd and 10 yd leads, fitted plugs. Units sold sep.

NOW AVAILABLE I.S.E. CA 127

JINGLE MACHINES £79-95

Terms: DEPOSIT £9 and 18 fortnightly payments £4-61 Total £91-98

Barclaycard and Access accepted

All items subject to availability. Prices correct at 7.4.75 E. & O.E.

NEW BRANCHES AT BOLTON, DONCASTER, and PRESTON

- OPEN ALL DAY SATURDAYS (5 Day Week)**
- BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349
- BOLTON** 23 Deansgate. (Closed Wed.). Tel. 33512
- BIRMINGHAM** 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).
- COVENTRY** 17 Shelton Square, The Precinct. Tel. 25983
- DERBY** 97 St. Peter's Street. (Closed Wed.). Tel. 41361
- DARLINGTON** 19 Northgate (Closed Wed.). Tel. 68043

HI-FI CENTRES LTD.

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs). Tel. 63069

EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501

GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158

HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505

LIVERPOOL 32 High Street (Closed Thurs.). Tel. 56420

LEEDS 5-7 County (Mecca) Arcade, Briggsate. (Closed Wed.). Tel. 452852

LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573

LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

- MAIL ORDERS & EXPORT ENQUIRIES TO:-**
- AUDIO HOUSE, HENCONNER LANE, LEEDS. 18.** Tel: Pudsey (09735) 77831
- MAIL ORDERS MUST NOT BE SENT TO SHOPS** TERMS C.W.O. or E.O.D. No G.O.D. under £1. POSTAGE 40p PER ORDER OR AS QUOTED. TRADE SUPPLIED. S.A.E. PLEASE WITH ENQUIRIES.
- MANCHESTER** 60A Oldham Street (Closed Wed.).
- MIDDLESBROUGH** Tel. 236 2778
- 106 Newport Road (Closed Wed.).** Tel. 47096
- NEWCASTLE UPON TYNE** 24 Newgate Shopping Centre (Closed Wed.). Tel. 21489
- NOTTINGHAM** 19/19A Market Street (Closed Wed.). Tel. 48068
- PRESTON** (Closed Thurs.). Tel. 51979
- 41 Friargate Walk, St. Georges Shopping Prec. Tel. 51979**
- SHEFFIELD** 13 Exchange Street (Castle Mkt. Blds.)
- STOCKPORT** (Closed Thurs.). Tel. 20716
- 8 Little Underbank (Closed Thurs.).** Tel. 480-9777
- SUNDERLAND** 5 Market Sq. (Closed Wed.). Tel. 70573

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX

All prices inclusive of V.A.T.

Telephone 4743

0B9	.40	6BA6	.35	6L1	2.00	12K5	1.00	35W4	.50	DM70	.60	ECH63	.44	EY87/s	.33	PCF806	.50	UBC81	.45	Transistors	AF117	.21	PSY11A	.25	
0Z4	.47	6BC6	.60	6L6GT	.55	12K7GT	.50	DM71	1.50	EF40	.75	ECH84	.44	EY88	.40	PCF200	.35	UBF80	.40	1N4744	.15	AF121	.23	PSY41A	.25
1A3	.45	6B7	.55	6L7	.55	12K8GT	.45	35Z4GT	.75	DY87/s	.85	ECL82	.54	EZ40	.50	FCL33	.45	UBL21	2.00	2N494	.20	AF124	.23	QAG9	.16
1A9GT	.50	6BH6	.60	6L15	.55	12K9C7	.50	35Z5GT	.75	DY80A	.85	ECL83	.70	EZ41	.55	PCL84	.40	UC92	.45	2N7666	.58	AF126	.20	QAG7	.17
1A7GT	.65	6B7A	.55	6L19	2.00	12K9GT	.40	42	.50	H80CC	2.20	ECL84	.60	EZ80	.25	PCL85	.47	UC94	.75	2N1756	.55	AF128	.53	QAG0	.17
1BSGT	.50	6BK7A	.60	6L20	.75	12K9T	.35	43	1.00	E90F	1.40	ECL85	.60	EZ81	.29	PCF805	.55	UC95	.45	2N1217	.94	AF128	.61	QAG3	.17
1HSGT	.60	6BQ7A	.55	6N7GT	.60	12K9T	.44	50B25	.85	E83F	1.30	ECL86	.40	EY90	.70	PCF845	.80	UCF86	.70	2N2297	.25	BA115	.15	QAG9	.16
1L4	.23	6BR7	1.00	6Q7G	.50	12K9T	.44	50B25	.85	E83F	1.30	EF92	1.50	GZ32	.50	PCF45DD	2.00	UCF87	2.00	2N2297	.25	BA116	.10	QAG1	.10
1N6GT	.65	6BR8	1.50	6Q7GT	.60	12K9T	.75	50B25GT	1.25	EP2CC	.60	EF90	.75	GZ33	1.25	FCL83	.80	UCF88	.45	2N3053	.30	BA119	.14	QAG5	.10
1R6	.45	6B7A	1.40	6Q7M	.55	12K9T	.55	50R16	.75	E10F	1.90	EF92	.70	GZ37	1.00	PCF453DD	2.00	UCF89	.33	2N3702	.21	BA123	.17	QAG1	.10
1R4	.53	6B7A	.80	6Q7G	.60	12K9T	.55	50R16GT	.65	E12CC1	.25	EF92	.50	H80C80	.60	2.00	UCF93	.55	2N3709	.23	BC107	.14	QAG9	.10	
1U7A	.60	6B7W	.70	6R7M	.75	12K9T	.55	50R16	.60	E1145	.53	EF92	.80	H80C80	.60	2.00	UCF94	.70	2N3709	.23	BC108	.14	QAG9	.10	
1U5	.75	6BZ6	.49	6SA7	.44	19A45	.50	58A2	.50	E1145	.53	EF92	.80	H80C80	.60	2.00	UCF95	.70	2N3709	.23	BC109	.14	QAG9	.10	
2D21	.45	6C4	.40	6S07GT	.33	20P2	.75	90A7	2.50	E47E	1.00	EF182	.30	KT41	1.00	PL84	.40	UY45	.35	AC122	.22	BCY34	.25	OC76	.17
2GKb	.55	6C6G	.50	68G7	.44	20L1	1.10	90C1	2.50	EABCO	.80	EF184	.55	KT66	2.55	PL84/500	1.00	UY10	1.00	AC124	.22	BCY38	.25	OC76	.17
2X2	.60	6C8	.40	68H7	.44	20P2	.75	90C3	2.40	EACD1	.75	EF904	1.25	KT61	5.00	.75	H80	.45	KT61-50	PL505	1.45	UY10	2.50	AC127	.22
2A4	.50	6C9	1.00	68T	.55	20P2	1.00	150B2	.75	EAF2	.75	H80	.45	KT61-50	PL505	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17	
2D4	.40	6CD6G	1.25	68K7GT	.44	20P2	1.80	12158G	.50	EAF2	.75	H80	.45	KT61-50	PL505	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17	
2Q4	.60	6C8A8	.75	68K7GT	.44	20P2	1.80	12158G	.50	EAF2	.75	H80	.45	KT61-50	PL505	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17	
2Q6GT	.55	6C16	.65	6V6G	.17	25A6G	.60	5072	1.00	E91	.20	EL34	1.00	KT62-100	MHL6	51	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	
2B4	.40	6CL8A	.80	6V6GT	.45	25V6G	.70	5763	1.50	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3V4	.70	6CMT	.75	6X4	.40	25Z4G	.40	6897	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3C8B	.55	6C8U	.75	6X5GT	.45	25Z4	.50	6903	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3G8	.60	6C9	.75	6X5GT	.45	25Z4	.50	6903	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3R4GY	.80	6D7	.75	7B7	.70	28D7	1.00	7193	.52	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3U4G	.40	6D7A	.75	7B7	.70	28D7	1.00	7193	.52	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3V4G	.50	6E76	.75	7B7	.70	28D7	1.00	7193	.52	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3Y3GT	.45	6E5	1.00	7Y4	.75	30C17	.30	ACCPEN	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3Z3	.75	6E1	.75	7Y4	.75	30C17	.30	ACCPEN	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3Z4G	.45	6E4G	.50	10P7	.75	30C17	.30	ACCPEN	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3Z4GT	.45	6E13	.70	10C2	.65	30P12	.57	AC/TH1	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3/20L3	.60	6F14	.75	10DR	.75	30P12	.57	AC/TH1	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A8G	1.25	6F15	.65	10F1	.75	30P12	.57	AC/TH1	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A7	.49	6F15	.65	10F1	.75	30P12	.57	AC/TH1	1.00	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A8G	.87	6F23	.70	10F15	.65	30P14	.70	A21	.25	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A8G	.60	6F24	.85	10L1D1	.70	30L15	.70	A23	.30	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.65	6F26	1.00	10P7	.75	30L17	.65	A24	.30	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.40	6F28	.67	10P14	2.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17
3A15	.60	6F32	.50	12A6	1.00	30P4MR	.60	BL63	.20	EBC41	.75	EL37	2.50	PL1	.50	PL509	1.45	UY10	2.50	AC127	.22	BCY38	.25	OC76	.17

no extras
all prices inc VAT
FREE delivery



ALL ITEMS SUBJECT TO
MANUFACTURERS INCREASE
AND AVAILABILITY

**Personal
Callers are
Welcome!**



**High Quality
Construction
Kits, stocked
at all branches
Send for
catalogue!**

AMPLIFIERS
Rotel RA211 £43.95
RA311 £54.95
RA611 £86.95
Sansui AU101 £48.25
AU505 £74.95
Sinclair 4000 £50.00
Linton Mk. II £59.95

TUNERS & RECEIVERS
Sinclair 4000 Tuner £43.95
Rotel RT222 £42.75
Pioneer SX434 £99.00
Rotel RX150A Tuner/
Amp. £59.95
Rotel 152 £69.95
Sansui
210 AM/FM/MPX £75.50
310 AM/FM/MPX £99.50
441 AM/FM/MPX £91.95

RECORD DECKS (Ins. 50p)
Garrard SP25 MkIV £14.75
BSR MP60 £12.95
Garrard
SP25 MkIV P & C G/800 £25.00
Goldring GL78 P & C/
G800E £59.95
Rank Domus BD 2000/
Rex 999 Cart. £50.00
Connoisseur
BD1 Kit £13.50
BD2 Chassis/SAU2 £32.50
SAU Arm £14.25
SCUI Cartridge £5.95
Pioneer PL12D £43.50

TAPE DECKS (Insurance 2.00)
Akai
4000DS Reel to Reel £97.95
4000DB Reel to Reel
Dolby £149.50
GXC36D £85.00
GXC38D £107.95
CS33D £82.95
Akai CR81D 8-track Rec.
player £85.95
GXC82D £95.95

SPEAKERS
Chassis Speakers
EMI (Plain) 13in x 8in,
3 or 8 ohm Bass unit £2.50
with Single Tweeter
(only 8 ohm) £2.75
with Tweeter and Cross-
over 3, 8 or 15 ohm £4.25
Type 350 Kit 15 watt 8 ohm £8.25
13in x 8in Bass unit 15 watt
8 ohm or 15 ohm £5.45
8in x 5in 5 watt 3, 8 or
15 ohm £1.70
8in x 5in 10 watt
Dualcone 8 ohm £2.95
6 1/2" 10 watt 8 ohm £2.65
8in 10 watt 8 ohm £4.50
8in 4 or 15 ohm £2.25
7in x 4in 3 or 8 ohm £1.30
Elac 6 1/2" 8 ohm Dualcone £2.65
Elac 8in 8 ohm Dualcone £2.70
Elac 10in 8 ohm Dualcone £3.75
Baker Group 25 12in 8 or
15 ohm £8.25

Adastra 'Top 20' 12in
25 watt 8 or 15 ohm £8.25
Adastra 'Hi-Ten' 10in
10 watt 8 or 15 ohm £3.70
Also 5in 8 ohm speaker £0.95
2 1/2in 8 or 64 ohm
speaker 60p

**WHARFEDALE SPEAKER
BARGAINS**
Denton 1 pr. £26.75
Denton 2 pr. £32.00
Linton 2 pr. £40.75
Glendale 3 pr. £60.95
Kingsdale 3 ea. £64.95
Dovedale 3 ea. £44.95

KITS
Linton 2 pr. £20.95
Glendale 3 pr. £35.95
Dovedale £55.50

**SPEAKER CABINETS IN
KIT FORM (Teak Veneer)**
(Ins. 50p. per pair)
12in x 8in x 6in
(8 x 5 or 7 x 4 cutout) £3.50
14in x 12in x 9in
(10", 8 x 5, 8", 6 1/2" & 3 1/2") £4.25
18in x 11in x 9in
(8" x 3" or 13 x 8) £5.50
22in x 14in x 9in
(12" & 3" or 13 x 8) £7.25

TWEETERS & CROSSOVERS
Cone Tweeter 10 watt
8 or 15 ohm (K2006) £2.95
Cone Tweeter 3 watt
8 ohm (K2003) £1.55
Horn Tweeter 8 ohm
(K2007) £6.50
Dome Tweeter 8 ohm
(K2011) £5.75
2-way Crossovers (CN23,
CN28, CN216) £1.40
3-way Crossover (CN38) £2.85

CARTRIDGES & STYLII

	Cart. £	D/D Styli £
ACOS		
GP91/2SC or 3CS (ster. comp)	1.10	1.25
GP93/1 or 95/1 ster. cryst.	1.35	1.25
GP94/1 or 96/1 ster. ceram.	1.75	1.25
GP101 cryst. comp.	90	—
GP104 ster. ceram.	1.95	1.25
BSR		
X5M or X5H cryst. comp.	1.95	1.25
SX6M or SX6H cryst. ster.	2.10	1.25
SC5M ster. ceram.	2.85	1.25
SONOTONE		
9TAHC or 9TAHC/G (Diam.)	1.95	1.25
3509 Magnetic	1.95	1.25
AUDIO TECNICA		
AT55	1.95	—
EMPIRE 999 REX	3.95	—
GOLDRING		
G850	3.10	1.95

G800 4.25 1.95
G800H 4.25 1.95
G800E 7.25 3.95
SHURE
M44G 4.95 3.95
M55E 6.25 4.95
M75ED Type 2 11.75 8.25
M15EJ Type 2 9.75 6.25
V15 Type 3 32.25 —

MICROPHONES
UD130 50K/600 ohm
uni-dir. ball metal £6.75
UD147 £9.25
Condenser Mic. 600 ohm
uni-dir £9.50
Cassette Stick Mic. with
R/Control £1.65
Cass. Stieck Mic. with
R. control (Philips type) £2.00
Mic-Mixers Mono/stereo £5.50

HEADPHONES
Rotel
RH430 £4.75
RH 630 £7.75
RH 700 £11.50
Koss
K711 £11.50
KR0711 £10.95
K6 £13.00
K6LC £14.95
K0727B £16.75
K0747 £21.50
HVI £21.95
PRO4AA £29.25
PRO54 £29.95
K6LCQ £26.00
Sansui SS10 £16.75
*Headphone adaptor
(Junction box) £2.75
extension lead 2ft curly £1.50

CASSETTES

	C40	C60	C90	C120
Low Noise	35p	45p	55p	55p
Philips	55p	75p	110p	110p
Memorex	65p	79p	110p	155p
Ampex (360)	45p	55p	75p	99p
Ampex (20-20+) Chromium Dioxide	59p	65p	99p	135p
Chromium Dioxide	99p	140p	—	—
Cassette Head Cleaner	—	—	45p	—
Ampex Head Cleaner/Demag	—	—	£1.65	—
BIB Stereo Test Cassette	—	—	£2.15	—
Cassette Racks (hold 6)	—	—	£0.45	—
Cassette Rotating Racks (hold 20)	—	—	£3.50	—
Cassette Carrying Case (hold 18)	—	—	£1.95	—
8-Track Cartridge Blanks				
C40 C64 C80				
Ampex	80p	95p	£1.10	—
8-track H/Cleaner Demagnetiser	—	—	£1.90	—
8-track Carrying Cases (BIB)	—	—	£1.65	—

TAPES

	Stnd	LP	DP	Cases
5"	55p	65p	1.00	20p
5 1/2"	65p	86p	1.35	25p
7"	80p	110p	1.85	30p
High frequency/Ampex	—	1.40p	—	1.55p
5"	—	1.90p	—	2.95p
AKAI Metal Reel 7"	—	—	—	£2.10

CALCULATORS
Sinclair Cambridge Build £12.95
Sinclair Cambridge with
memory £17.95
Scientific £19.95

SINCLAIR PROJECT 80
Stereo Pre-amp. £12.95
Active Filter Unit £7.25
Z40 15 watt Amp £5.75
Z60 25 watt Amp £7.25
P25 Power Supply for 240 £5.45
P26 Power Supply for 240 £8.45
P28 Power Supply for 260 £8.25
FM Tuner £12.95
Stereo Decoder £8.45
Q16 Speaker £7.75
IC20 Stereo Amp. Kit £7.45
PZ20 Power Kit £5.25

PORTABLE RADIOS
Meridian Mk. II £12.25
Vega Jade £5.95
Vega Sapphire £8.75
Vega VEF206 £15.50
Selena LM/MW/FM/SSW
Murphy £22.50
B833 MW/VHF £9.95
BA838 LW/MW/VHF
M/Batt £18.50
MA5003 Head Set
Radio LW £7.95
Bush
VTR165 LW/MW/VHF £22.00
VTR127 LW/MW/VHF £15.50
VTR 175 LW/MW/VHF £13.95
VTR188 LW/MW/VHF/
2SW M/Batt £31.95
BY5661 LW/MW/VHF £14.95
Selga 2 wave band with
leather case £5.50

CLOCK RADIOS
Bush CR128 LW/MW £13.60
Bush CR232 MW/VHF £24.95
Murphy MV5600
MW/VHF £22.95
Vega Signal 2 wave band
£9.95

CASSETTE RECORDERS
Bush TP66 M/Batt £25.75
Murphy BA200 M/Batt £22.75
Bush BT8504 (miniature) £25.50
Mains Battery Cass. £15.50

RADIO CASSETTES
(Mains/Batt.)
Murphy BA209 MW/VHF £33.50

**STEREO RECORD PLAYER
& SYSTEM**
Bush A1005 £56.50
Hanimex HRC5060 8-track
AM/FM/MPX+Speaker £116.95

CAR AUDIO
Hitachi Car Radio
WM702R LW/MW £16.50
KM1510 LW/MW/VHF £32.50
Hitachi Car Cassette
CS114 £45.00
Hitachi AM/FM & Cassette
CSW 217 £57.00
Battery Eliminators 240 in
6, 7.5 or 9 volt output £2.95

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART
ELECTRONICS**

Mail Order Dept PW/6
Belmont St, Monton,
Eccles, Manchester.
Tel: 061-789 5268

Manchester
30-32 Shudehill. tel 061-832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738

Marshall's

A. Marshall & Son (London) Limited Dept. PW
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161
& 85 West Regent Street Glasgow G2 2QD Tel: 041-332 4133

Everything you need is in our new 1975 catalogue. Available now price 25p

Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linear

CA3018A	85p	CD4043	£1.80	NE565	£4.48	SN7448	90p	SN74157	95p
CA3020A	£1.80	CD4044	£1.80	SL414	£1.80	SN7450	16p	SN74160	£1.10
CA3028A	75p	CD4045	£2.65	SL610C	£1.70	SN7451	16p	SN74161	£1.10
CA3035	£1.37	CD4046	£2.84	SL611C	£1.70	SN7453	16p	SN74162	£1.10
CA3046	70p	CD4047	£1.45	SL612C	£1.70	SN7454	16p	SN74163	£1.10
CA3048	£2.11	CD4049	81p	SK620C	£2.60	SN7460	16p	SN74164	£2.01
CA3052	£1.62	CD4050	66p	SL621C	£2.60	SN7470	33p	SN74165	£2.01
CA3089E	£1.96	LM301A	48p	SL623C	£4.59	SN7472	26p	SN74166	£4.10
CA3090Q	£4.23	LM308	£2.50	SL640C	£3.10	SN7473	36p	SN74174	£1.25
CD4000	36p	LM05TL	£1.50	SN7400	16p	SN7474	36p	SN74175	90p
CD4001	36p	LM300	£1.10	SN7401	16p	SN7475	50p	SN74176	£1.44
CD4002	36p	LM381	£2.20	SN7401AN	36p	SN7476	35p	SN74180	£1.40
CD4006	£1.58	LM702C	75p	SN7402	16p	SN7480	50p	SN74181	£1.95
CD4007	36p	LM709	38p	SN7403	16p	SN7481	£1.25	SN74190	£2.30
CD4008	£1.63	BD1L	45p	SN7404	19p	SN7482	75p	SN74191	£2.30
CD4009	£1.18	14D1L	40p	SN7405	19p	SN7483	95p	SN74192	£1.15
CD4010	£1.18	LM710	47p	SN7406	45p	SN7484	95p	SN74193	£1.15
CD4011	36p	LM723C	90p	SN7407	45p	SN7485	£1.25	SN74196	£1.50
CD4012	36p	LM741C	40p	SN7408	19p	SN7486	32p	SN74197	£1.58
CD4013	66p	BD1L	40p	SN7409	22p	SN7490	45p	SN74198	£2.25
CD4014	£1.72	14D1L	38p	SN7410	16p	SN7491	85p	SN74199	£2.25
CD4015	£1.72	LM748	£1.72	SN7411	25p	SN7492	45p	SN7603N	£2.92
CD4016	66p	LM748	60p	SN7412	25p	SN7493	28p	SN7603N	£2.92
CD4017	£1.72	14D1L	73p	SN7413	35p	SN7494	82p	SN7603N	£1.95
CD4018	£2.55	LM3900	70p	SN7416	35p	SN7495	72p	SN7603N	£1.60
CD4019	86p	LM7805	£2.00	SN7417	35p	SN7496	75p	SN7603N	£2.92
CD4020	£1.91	LM7812	£2.50	SN7420	16p	SN74100	£1.25	TAA263	£1.10
CD4021	£1.72	LM7815	£2.50	SN7423	29p	SN74107	36p	TAA300	£1.80
CD4022	£1.64	LM7824	£2.50	SN7425	29p	SN74118	£1.00	TAA350A	£2.10
CD4023	36p	MCI3031	£1.50	SN7427	29p	SN74119	£1.92	TAA550	60p
CD4024	£1.24	MCI318P	£2.59	SN7430	16p	SN74121	37p	TAA611C	£2.18
CD4025	32p	MCI330P	90p	SN7432	28p	SN74122	50p	TAA621	£2.03
CD4027	43p	MCI351P	80p	SN7437	35p	SN74123	60p	TAA651B	£1.22
CD4028	£1.50	MCI352P	80p	SN7438	35p	SN74141	85p	TBA461B	£2.25
CD4029	£3.50	MCI466L	£3.50	SN7440	16p	SN74145	90p	TBA461B	£2.25
CD4030	87p	MCI469R	£2.75	SN7441AN	85p	SN74150	£1.50	TBA651	£1.69
CD4031	£5.19	NE555V	70p	SN7442	65p	SN74151	85p	TBA800	£1.40
CD4037	£1.93	NE556	£1.30	SN7446	95p	SN74153	85p	TBA810	£1.40
CD4041	£1.86	NE560	£4.48	SN7447	95p	SN84154	£1.50	TBA820	£1.15

PW TELE TENNIS KIT £42.50 + VAT Reprint 75p

TRY OUR GLASGOW SHOP

POPULAR SEMICONDUCTORS

2N696	22p	2N3906	27p	AF139	65p	BD139	71p	MPSA56	31p
2N697	16p	2N4037	42p	AF239	65p	BD140	87p	OC28	76p
2N698	83p	2N4038	90p	AF240	90p	BD141	36p	OC35	60p
2N699	59p	2N4058	18p	AF279	70p	BF117	55p	OC42	50p
2N706	14p	2N4062	15p	AF280	79p	BF154	20p	OC45	32p
2N708	17p	2N4289	34p	AL102	£1.00	BF159	27p	TIP29A	49p
2N916	28p	2N4920	£1.10	BC107	14p	BF180	35p	TIP29C	58p
2N918	32p	2N4921	83p	BC108	14p	BF181	36p	TIP31A	62p
2N1302	18p	2N4923	£1.00	BC109	14p	BF184	30p	TIP32A	74p
2N1304	26p	2N5245	47p	BC147B	14p	BF194	12p	TIP33A	£1.01
2N1306	31p	2N5294	48p	BC148B	15p	BF195	12p	TIP34A	£1.51
2N1308	47p	2N5296	48p	BC149B	15p	BF196	13p	TIP35A	£2.90
2N1711	45p	2N5457	49p	BC157A	16p	BF197	15p	TIP36A	£3.70
2N1202	60p	2N5458	49p	BC157B	16p	BF198	16p	TIP42A	£0.90
2N1217	78p	2N5459	49p	BC167B	15p	BF244	21p	TIP2955	98p
2N1218	94p	2N6027	45p	BC168B	15p	BF257	47p	TIP3055	50p
2N2218A	22p	3N128	73p	BC169B	15p	BF258	53p	TIS43	28p
2N2219A	26p	3N140	£1.00	BC182	12p	BF259	55p	ZTX300	13p
2N2220	25p	3N141	81p	BC182L	12p	BF562	27p	ZTX301	13p
2N2221	18p	3N200	£2.49	BC183	12p	BF598	25p	ZTX500	15p
2N2222	20p	40361	40p	BC183L	12p	BFR39	24p	ZTX501	13p
2N2369	20p	40362	45p	BC184	13p	BFR79	24p	ZTX502	18p
2N2646	55p	40406	44p	BC184L	13p	BFX29	30p	IN914	7p
2N2904	22p	40407	35p	BC212A	16p	BFX30	27p	IN3754	15p
2N2905	25p	40408	50p	BC212LA	16p	BFX84	24p	IN4007	10p
2N2906	19A	40409	52p	BC259B	16p	BFX85	20p	IN4148	7p
2N2907	22p	40410	52p	BC214LB	18p	BFX88	25p	IN5404	22p
2N2924	20p	40411	£2.00	BC237B	16p	BFY50	22p	IN5408	30p
2N2926G	12p	40594	74p	BC238C	15p	BFY51	23p	AA119	8p
2N3053	25p	40595	84p	BC239C	15p	BFY52	20p	BA102	25p
2N3054	60p	40636	£1.10	BC257A	16p	BRY39	48p	BA145	18p
2N3055	75p	40673	73p	BC258B	16p	ME0402	20p	BA154	12p
2N3391	28p	AC162	20p	BC259B	17p	ME0412	18p	BA155	12p
2N3392	15p	AC127	20p	BC301	34p	ME4102	11p	BB103B	23p
2N3393	15p	AC128	20p	BC307B	17p	MJ480	95p	BB104B	45p
2N3440	59p	AC151	27p	BC308A	15p	MJ481	£1.20	BY126	12p
2N3442	£1.40	AC152	49p	BC309C	20p	MJ490	£1.05	BY127	15p
2N3635	15p	AC173	83p	BC327	32p	MJ491	1.45	BY211	12p
2N3705	15p	CI776	30p	BC328	22p	MJ2955	£1.00	BVZ12	51p
2N3703	13p	AC187K	35p	BCY70	17p	MJ340	48p	OA47	6p
2N3704	15p	AC188K	40p	BCY71	22p	MJE370	65p	OA81	18p
2N3706	15p	AD143	68p	BCY72	15p	MJE371	75p	OA90	6p
2N3708	14p	AD161	50p	BD121	£1.00	MJE520	60p	OA91	6p
2N3714	£1.38	AD162	50p	BD122	82p	MJ521	70p	WO21A20P	12p
2N3716	£1.80	AF106	40p	BD123	67p	MJE2955	£1.20	BY164	32p
2N3771	£2.20	AF109	40p	BD131	40p	MJE3055	75p	BY164	57p
2N3773	£2.65	AF115	35p	BD132	50p	MP8113	47p	ST2diac	20p
2N3789	£2.06	AF116	35p	BD135	43p	MPF102	39p	40669	£1.00
2N3819	37p	AF117	35p	BD136	47p	MPSA05	25p	TIC44	29p
2N3820	64p	AF118	35p	BD137	35p	MPSA06	31p	C106D	65p
2N3904	27p	AF124	30p	BD138	63p	MPSA55	31p	ORP12	60p

Prices correct at May 1975, but all exclusive of VAT. P. & P. 25p.

ELECTROVALUE

The best of all!

CATALOGUE 7 ISSUE 3

with 25p refund voucher

Up-dated Price & Product Information

112 pages plus cover As comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more SEND NOW FOR YOUR COPY BY RETURN 30p paid (it's an investment in practical money-saving and reliability)

PRICES as shown in our latest catalogue (No. 7, issue 3) were due for review by April 1st. In fact these have remained unchanged since January, reviewed only at 3-monthly intervals as from July 1st next. This is instead of making day-to-day price changes.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders list value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Section 2/5, 28, ST. JUDES RD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB, Telephone Egham 3603, Telex 264475. Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours: Daily 9-5.30 pm; 9-1 pm Sats.



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL Dept. W.B. 65 P.O. Box 156, JERSEY

NAME: _____ ADDRESS: _____

BLOCK CAPS please

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- | | | | |
|-------------------------------------------------------------|---------------|---------------|-------------------------------------------------------------------------------------------------------------------------------------------|
| SA35
35W RMS 25-50V
7 transistors, 7 diodes | £6-60 | Carriage free | ★ 25Hz-25kHz
★ 0.2% distortion
★ Noise—80dB
★ 500mV into 20K
★ 4-16 ohms
★ Simple wiring
★ Short and open circuit proof |
| SA50
50W RMS 25-65V
7 transistors, 7 diodes | £8-50 | Carriage free | ★ Continuously rated
★ Top-grade components |
| SA100
100W RMS 45-70V
10 transistors, 7 diodes | £12-50 | Carriage free | |

120 watt module complete with built-in supply—extra heavy duty £24-75 Carr. 60p



THE SA100 MODULE


POWER SUPPLIES

- | | | | |
|---------------------------------------------|---------------------------------|--------------|---------------|
| UNSTABILISED—READY WIRED & FUSED | | | |
| PU45 | Suits 2 SA35 or 1 SA50 (4 ohm) | £6-50 | Carriage 50p |
| PU70 | Suits 2 SA50 (8 ohm) or 2 SA100 | £9-50 | Carriage 60p |
| STABILISED | | | |
| PS45 | Suits 2 SA35 or 1 SA50 (4 ohm) | £5-50 | Carriage free |
| MT45 | Transformer for above | £3-90 | Carriage 50p |
| PS70 | Suits 2 SA100 | £6-50 | Carriage free |
| MT70 | Transformer for above | £5-50 | Carriage 60p |

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £29-50

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep. Carr. 60p

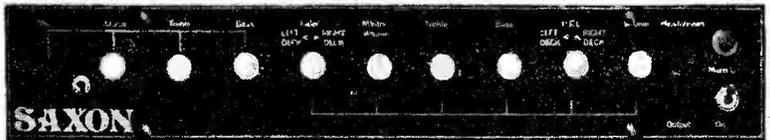

DISCO MODULE £12-50

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep. Carr. 50p



3-CHANNEL SOUND-LITE £24-75

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford! Carr. 50p



SINGLE CHANNEL VERSION £7-90 Carr. free
High sensitivity compact handles 1kW. Full wave operation.


ADD 8% VAT TO ALL ORDERS

MULTI-PURPOSE MIXERS


M4HL £25-00 Carr. 60p	M6HL £35-00 Carr. 60p
----------------------------------------	----------------------------------------

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

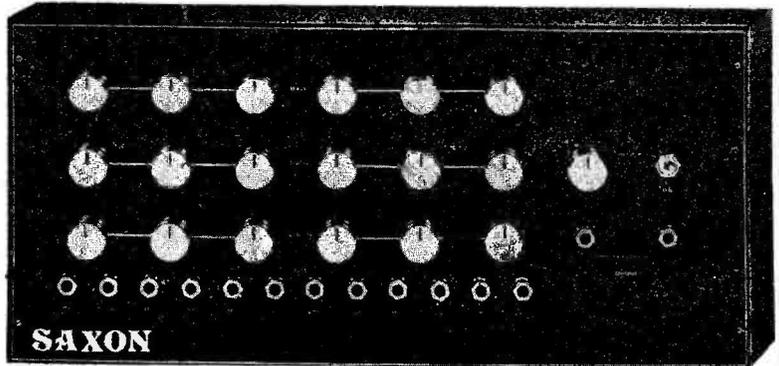VA30 CHANNEL MODULE £3-90 Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



SAXON CSE 100 COMPLETE AMPLIFIER
100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vyndie case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.
£39-90 Carr. 60p

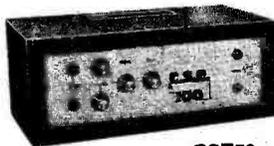

CSE50
£33-00 Carr. 60p

NEW !!

SAXON MULTIMIX 100 £57-00 carr. £1-00

100W rms four inputs slider controls plus master slider. Wide range bass and treble controls. Fantastic value, ideal for complete disco's, groups, clubs etc. **SAXON MULTIMIX 50**—Exactly as above but 50W rms. **£45-00.**

CALLERS AND MAIL ORDER

SAXON ENTERTAINMENTS LIMITED

327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)
SHOP HOURS: 9 a.m.-5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.-3 p.m.
24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 10p FOR OUR 26 PAGE MANUAL—(all circuits & details).
TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.
Please send S.A.E. with all enquiries.
VAT @ 8% must be added to all orders including carr. charges.



GIRO NO. 331 7056. Access accepted. C.V.O. only, P. & P. 10p on orders below £5. Discount: £10-10%, £20-15% (except net items). Export Order enquiries welcome (VAT free).

Official Orders accepted from Educational, Government and Departments. ALL PRICES INCLUDE VAT AT 8%.

SPECIAL RESISTOR KITS (Prices include post & packing)

- 10E12 1/4W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
 - 10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.95 net
 - 25E12 1/4W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
 - 25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
 - 5E12 1/4W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £3.45 net
- Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3 1/2p, 0.068µF, 0.1µF, 4 1/2p, 0.15µF, 5p, 0.22µF, 6p, 0.33µF, 7p, 0.47µF, 10p, 0.68µF, 13p, 1µF, 15p, 1.5µF, 24p, 2.2µF, 27p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 3p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3 1/2p, 0.047µF, 0.068µF, 0.1µF, 4 1/2p, 0.15µF, 7p, 0.22µF, 9p, 0.33µF, 13p, 0.47µF, 15p.
160V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 4p, 0.1µF, 4 1/2p, 0.15µF, 5 1/2p, 0.22µF, 6p, 0.33µF, 7p, 0.47µF, 9p, 0.68µF, 13p, 1µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2 1/2p, each, 0.1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 4 1/2p.

RESISTORS

W. Type Range	CF—High Stab Carbon Film, 5%	MF—High Stab Metal Film, 5%	Size mm
1	1-99	100-999	1000+
2	1-99	100-999	0-60
3	1-99	100-999	0-60
4	1-99	100-999	0-60
100	1-99	100-999	0-60

VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0-25V Vertical or horizontal 7p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω.
SUB-MIN 0-05V Vertical, 100 Ω to 220K Ω 7p each.

B. H. COMPONENT FACTORS LTD.

(P.W.) LEIGHTON ELECTRONICS CENTRE, 59 NORTH ST., LEIGHTON BUZZARD, BEDS. Tel: LEIGHTON BUZZARD 2316 (STD. Code 05253) CATALOGUE No. 4 20p

Miniature Mullard Electrolytics

1.0µF 63V	7p	100µF 25V	7p
1.5µF 63V	7p	100µF 63V	7p
2.2µF 63V	7p	150µF 16V	7p
3.3µF 63V	7p	150µF 63V	17p
4.0µF 40V	7p	220µF 6-4V	7p
4.7µF 63V	7p	220µF 10V	7p
6.8µF 63V	7p	220µF 16V	8p
10µF 25V	7p	220µF 63V	25p
10µF 63V	7p	330µF 16V	14p
15µF 16V	7p	330µF 63V	28p
15µF 63V	7p	470µF 6-4	8p
16µF 40V	7p	470µF 40V	25p
22µF 25V	7p	680µF 16V	17p
22µF 63V	7p	680µF 40V	28p
32µF 10V	7p	1000µF 16V	28p
33µF 16V	7p	1000µF 25V	28p
33µF 40V	7p	1500µF 6-4	17p
47µF 10V	7p	1500µF 16V	28p
47µF 25V	7p	2200µF 10V	28p
68µF 16V	7p	3300µF 6-4	28p
68µF 63V	14p		
100µF 10V	7p		

VEROBOARD 0.1 0.15

2 1/2 x 5"	36p	36p
2 1/2 x 3 1/2"	39p	25p
3 1/2 x 5"	42p	46p
3 1/2 x 3 1/2"	36p	36p
2 1/2 x 1 1/2"	10p	9p
2 1/2 x 5" (Plain)	—	19p
2 1/2 x 3 1/2" (Plain)	—	19p
2 1/2 x 3 1/2" (Plain)	—	19p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 50	22p	22p

TRANSISTORS

AC127	21p	BC212L	13p
AC128	22p	BC213L	13p
BC107	12p	BC214L	13p
BC108	12p	OC44	19p
BC109	13p	OC71	13p
BC148	13p	OC81	17p
BC149	13p	OC170	29p
BC182L	13p	2N2926	13p
BC183L	13p	2N3702	14p
BC184L	14p		

POTENTIOMETERS

Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17 1/2p Dual Gang 48p. Log single with switch 28p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001	6p	DIN 2 Pin	12p
IN4002	7p	5 Pin 180°	13p
IN4003	9p	5 Pin 180°	16p
IN4004	9p	Std. Jack	20p
IN4005	12p	2.5mm jack	13p
IN4006	14p	Phono	7p
IN914	7p	SOCKETS	
IN916	7p	DIN 2 Pin	10p
BA100	10p	DIN 2 Pin	10p
OA5	42p	5 Pin 180°	12p
OA47	9p	Std. Jack	18p
OA81	11p	2.5mm jack	13p
OA200	8p	Phono	7p

ELECTROLYTIC CAPACITORS. Tubular & Large Case
(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100, £1.10, 2000/25, 35p, 2000/100, £1.20, 2500/25, 38p, 2500/50, 68p, 5000/25, 69p, 5000/50, £1.20.

HI-VOLT: 4/350, 20p, 8/350, 23p, 100/100 27p, 16/350, 35p, 100/100, 27p, 100/250, 40p.

METALLISED PAPER CAPACITORS
250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7 1/2p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 0.22µF, 0.25, 7p, 0.5, 1000V: 0.01, 12p, 0.022, 13p, 0.047, 0.1, 19p, 0.22, 28p, 0.47, 36p.

PLEASE NOTE OUR NEW ADDRESS
Our new Electronics Centre is now open in Leighton Buzzard and all callers are welcome. As well as our normal stock of over 2000 product lines, we have a large range of surplus equipment, Bargains, Calculators, etc. OPEN 6 DAYS 9 to 5 (shut 12.30 to 1.30).

NEW KIT
5E12 1/4W Metal Film, 5 each value 10Ω-1M, total of 305 £3.75 net.

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator 20,000Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—5Ω—1MΩ in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465 KHz (A.M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8.64 net p & p 50p.

MULTIMETER U4341
27 Ranges plus Transistor Tester, 17,000Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 6 ranges.
Idc—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2KΩ—2MΩ in 4 ranges.
Accuracy—dc—2%, ac—4% of F.S.D.
hfe—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.88 net p & p 50p.

MULTIMETER U4313
33 ranges, Knife edge with mirror scale, 20,000Ω/Volt. High accuracy, mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ldc—0.6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db accuracy—10 to 4 (2db).
Accuracy—dc—1%, ac—2 1/2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net p & p 50p.

NEW CAPACITOR KITS

C280 Kit—PC Mounting polyester 250V, 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF, 2 of 0.47, 1µF, £1.40 net.

C296 Kit—Tubular polyester, 400V, 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF, 2 of 0.47, 1µF, £1.40 net.

Ceramic Kit—square plate, 50V, 5 each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0.01µF, £1.40 net.

250V Paper Kit—Tubular metal case, 3 of each value: 0.05, 0.1, 0.25, 0.5, 1µF, £1.00 net.

500V Paper Kit—Tubular metal case, 3 of each value: 0.025, 0.05, 0.1, 0.25, 0.5µF, £1.00 net.

1000V Paper Kit—Tubular metal case, 3 each value: 0.01, 0.025, 0.05, 0.1µF, £1.20 net.


MULTIMETER U4324
34 Ranges, High sensitivity, 20,000Ω/Volt. Overload protected.
Vdc—0.6—1000V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25Ω—5MΩ in 5 ranges.
Accuracy—dc and R—2 1/2% of F.S.D. ac and C—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £10.64 net p & p 50p.

MULTIMETER U4313
33 ranges, Knife edge with mirror scale, 20,000Ω/Volt. High accuracy, mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ldc—0.6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db accuracy—10 to 4 (2db).
Accuracy—dc—1%, ac—2 1/2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net p & p 50p.


MULTIMETER U4313
33 ranges, Knife edge with mirror scale, 20,000Ω/Volt. High accuracy, mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ldc—0.6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db accuracy—10 to 4 (2db).
Accuracy—dc—1%, ac—2 1/2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net p & p 50p.

MULTIMETER U435
32 Ranges, High Sensitivity, 20,000Ω

SHEER SIMPLICITY!

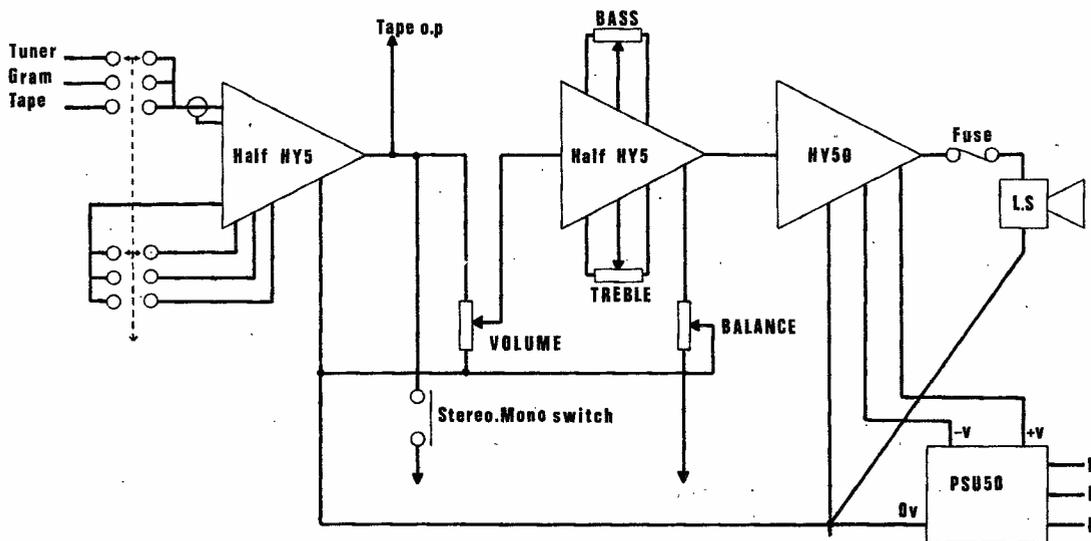

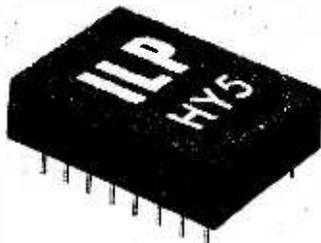MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION
Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 5-100mV; Input Impedance 47kΩ at 1kHz. **Outputs:** Tape 100mV; Main output 0db (0-775V RMS). **Active Tone Controls:** Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. **Distortion:** 0.5% at 1kHz; **Signal/Noise Ratio:** 68db. **Overload Capability:** 40db on most sensitive input. **Supply Voltage:** ± 15-25V.


PRICE £4.50 + 36p VAT
 P. & P. free



The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION
Output Power: 25W RMS into 8Ω. **Load Impedance:** 4-16Ω. **Input Sensitivity** 0db (0-775V RMS). **Input Impedance:** 47kΩ. **Distortion:** Less than 0.1% at 25W typically 0.05%. **Signal/Noise Ratio:** Better than 75db. **Frequency Response:** 10Hz-50kHz ± 3db. **Supply Voltage:** ± 25V. **Size:** 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT
 P. & P. free

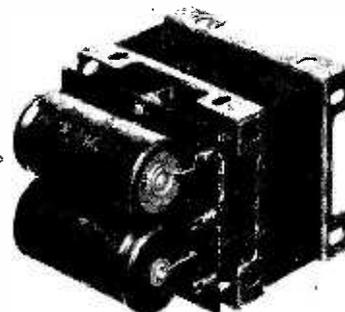

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS
Output voltage: 50V (25-0-25V). **Input Voltage:** 210-240V. **Size:** L.70. D.90. H.60mm.

PRICE £6 + 48p VAT
 P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD

Tel (0227) 63218

Regd. V.A.T. No. 202141535

Please supply,

Total Purchase price

I Enclose, Cheque Postal Orders Money Order


Please debit my Access account Barclaycard account

Account number

Name & Address

Signature

BIG Discounts

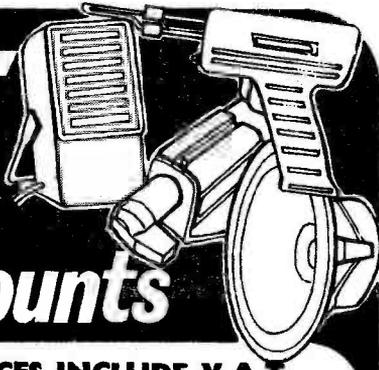

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£	£
P. & P. 40p per speaker			
EMI 13" x 8" or 8 ohm Plain	2-20	ELAC 6 1/2" 8 ohm Dualcone	2-25
With Co-Axial Tweeter		ELAC 5" 8 ohm Dualcone	2-50
8 ohms only	2-30	ELAC 10" 8 ohm Dualcone	3-50
Tweeter & Crossover 3, 8		10 watt	3-55
or 15 ohm	3-95	ADASTRA 10" 8 or 15 ohm,	3-55
Type 350		10 watt	
20 watt	7-95	BAKER GROUP 25 12" 8 or	7-95
6 1/2" 8 ohm, 10 watt	2-60	15 ohm, 25 watt	
8" 8 ohm, 10 watt	4-50	Following speakers 15p P. & P.	
12" 8 ohm, 20 watt	6-70	2 1/2" 8 ohm or 64 ohm	55
8" x 5" C/Mag. 3, 8 or		5" 8 ohm, c/mag.	85
15 ohm 5 watt	1-40	7" x 4" 3 or 8 ohm	1-20
8" x 5" Dualcone			
8 ohm, 10 watt	2-55		

TWEETER & CROSSOVER		£	£
Cone Tweeter 8 or 15 ohm,		Crossovers CN23 (3 ohm),	
10 watt	2-80	CN28 (8 ohm), CN216 (16	
Cone Tweeter 8 ohm, 3 watt	1-45	ohm)	1-30
Horn Tweeter 8 ohm, 20 watt	8-40	P. & P.	10
Dome Tweeter 8 ohm, 30 watt	5-80		

KIT FORM CABINETS TEAK VENEER		£	£
12 x 12 x 8 with 8" x 5" or		18 x 11 x 9 with 8" x 1 1/2" or	
6 1/2" and 3 1/2" cut out.	3-50	13" x 8" cutout for EMI 350	4-95
17 x 10 x 9 with 8" or 13" x 8"		P. & P. ea.	50
cutout	4-50		

MICROPHONES		£	£
CM70 Planet stick metal,		TW209	5-75
switch crystal	1-55	CONDENSER MIKE 600 ohm,	9-35
DM160 Dynamic omni-dir.		Cassette Stick Mike with R.	
ball metal	4-90	Control on/off switch	1-50
UD130 50K/600 ohm, uni-dir		(2-5 & 3-5mm J/Ply)	30
ball metal	6-40	P. & P.	

SOLDERING IRONS		£	£
ANTEX CN240 15 watt	2-10	X25 25 watt (low	2-19
SK 1 KIT (15 watt iron		leakage)	15
2 spare Bils etc.)	3-40	P. & P.	

CARTRIDGES & STYLII		£	£
ACOS GP91/2SC or 3SC ster.		SONOTONE	
comp.	1-00	9TAHC or 9TAHC/G Diam.	1-90
GP93/1 or 95/1 ster.		3509 Ster. ceram. Diam.	1-90
cryst.	1-35	GOLDRING G850	2-95
GP94/1 or 96/1 ster.		G800	3-95
ceram.	1-75	G800E	6-90
GP101 cryst. comp.	0-80	P. & P.	15
GP104 ster. ceram.	1-80	D. Diamond Stylil for above	1-25
R/SR X5M or X5H cryst. comp.	1-80	G800/G850	1-85
SX6M or SX6H cryst.		G800E	3-95
comp.	1-95	P. & P.	05
SCSM ster. ceram.	2-70		

CALCULATORS SINCLAIR		£	£
Cambridge	12-95	Scientific	19-95
Cambridge with memory	17-95		

BATTERY ELIMINATORS		£	£
240v input 6, 7.5 or 9	2-95	12v input, 6, 7.5, 9 output, 1 amp	4-25
		P. & P.	15

TAPES		£	£
5"	50p	LP	DP
5 1/2"	85p	80p	1-00p
7"	80p	1-10p	1-80p

LOW NOISE CASSETTES		£	£
C80	1-5	6-10	11-20
C90	35p	33p	30p
C120	45p	43p	40p
	55p	52p	50p

SIB ACCESSORIES		£	£
Tape Editing Kit Ref. 23	1-35	WHAFFEDALE SPEAKER	
Recording Tape		BARGAINS	
Splicer Ref. 20	1-15	Linton 2 Kit (pr)	1-95
Cassette Tape, editing Ref. 24	1-50	Glendale 3 Kit (pr)	2-00
Cassette Salvage Kit Ref. 29	45	Dovedale 3 Kit (pr)	52-00
Stylus Balance Ref. 32A	1-20	Denton 2 Speaker (pr)	30-00
Spirit Lever Ref. 46	50	Linton 2 Speaker (pr)	39-50
Hi-Fi Stereo Test Cassette	2-18	Dovedale 3 Speaker	2-50
Groove-Kleen Record Cleaner	1-90	(each)	42-00
P. & P.	15p	Glendale 3 Speaker (pr)	57-00
		Kingsdale 3 Speaker	3-50
		(each)	59-95
			4-00

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

Riversdale Electronics

Mail Order Department PW6

P.O. Box 470, Manchester M60 4 BU.

★ ELECTRONIC PIANO KIT

★ SYNTHESISER KIT

★ ELECTRONIC ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D-I-Y. enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements which will compare with organ commercially built costing double the price.

Portable organ with 4 octave keyboard. £145-29. ★ Console organ with 5 octave keyboard, £250-93. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board, £470-65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board, £680-00. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board, £960-00. ★ W/W Sound Synthesiser Kit, £130. ★ W/W Touch Sensitive Electronic Piano, £100. 2 speed Leslie type speaker units Hi-Fi Horn unit £70. Mid-range speaker unit £60. Base unit £50.

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc.

Send 60p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

12, Brett Rd., Hackney, London E8 1JP. Tel. 01-986-8455. 8, Putney Bridge Rd., London SW18 1HU. Tel. 01-870-4949. 40a/42a, Dalston Lane, Dalston Junction, London E8. Tel 01-249-5624.

Business Hours:— Open 10am-7pm Monday to Saturday
Closed all day Thursday
Open 10am-1pm Sunday

PC ETCHING KIT

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO Etch-resist Pen, abrasive cleaner, etching dish and instructions £3-30.

FERRIC CHLORIDE

Anhydrous to Mil-Spec In 1lb double sealed packs. 1lb 90p, 3lb £1-80, 10lb £4-65.

COMPUTER PANELS

Large quantity always available. 3lbs assorted £1-60, 7lb £2-85, 56lb £15. Pack with 20 multitrans trimmings plus other parts £1-10. Pack with 10 200V 1A SCR's plus 120 other parts £1-10.

7lb BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, switches, pots, plus PC Boards with transistors and diodes, also loads of odds and ends. Contents always changing. Only £2-60.

POWER SUPPLY UNIT

G101: Mains transformer, 2A thermal cut-out, bridge rect. with fuse, 7 to 10-15V output with 2 extra capacitors (provided). With data £1-30.

RESISTORS & CAPACITORS

400 assorted carbon resistors £1-30; 250 Hi-Stabs, 1, 2 & 5%. Very good variety £1-20. 100 wirewounds, 7W-15W £1-80. 200 small value poly. ceramic, mica capacitors £1. 15 trimmers, airspaced and compression from a few pF to 1250pF £1. Polyester C280 caps. .01 to .47mfd. 250 & 400V 100 £1-15. 500 £4-25. Miniature electrolytics, transistor type 015/8 but mostly unmarked 200 for £1-25.

All prices include 8% VAT and UK Postage. SAE list, enquiries.

GREENWELD (PW6)

51 Shirley Park Rd., Southampton SO1 4FX. Tel: 772501.

Also callers at 21 Deptford Bdy. SE8 (692 2909) & 35 Lower Addurcombe Road, Croydon. (688 2950)

8 PIN DIL 741's

10+ 26p, 25+ 23p, 100+ 21p, 250+ 20p

555 TIMERS

3+ 60p, 10+ 50p, 25+ 46p, 100+ 43p

1N4001, 2, 3, 4, 5, 6, 7

10 of each type—all marked and full spec. 70 diodes for £3-50
15, 18, 20, 24 or 30V @ 1A, also 12-0-12

2N3055's FULL SPEC

10+ 35p, 25+ 32p, 100+ 30p

7 SEGMENT LEDS

14 pin DIL package 19 x 11mm TTL compatible (7447 driver) 4 for £3-60, 6 for £5-20.

VEROBOARD

About 8 pieces, total 100 sq ins assorted sizes and pitches £1-15.

TRANSFORMERS

All mains primary. 6-0-6V @ 100mA 85p; 9-0-9V @ 100mA 90p; 12-0-12V @ 100mA 95p; 24-0-24V @ 50mA £2; 17V @ 1A £1-80; 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V @ 1A, also 12-0-12 or 15-0-15V £2-70, 2 amp version £3-90

HEAT SINKS

6 x 5 x 3" finned aluminium with 2xOC29/35 Only £1-20.
DG19E Display Tubes. No info. £1

TRANSISTORS ETC.		
AC127 20p	BC148 10p	BC548 10p
AC128 20p	BC149 10p	BCY70 15p
AC178 20p	BC157 10p	BCY71 15p
AC187 25p	BC158 10p	BCY72 10p
AC188 25p	BC159 10p	BF173 20p
AD161 40p	BC182 10p	BF181 25p
AD162 40p	BC183 11p	BF194 10p
BC107 10p	BC184 12p	BF195 10p
BC108 10p	BC212 11p	BFY52 15p
BC109 10p	BC213 12p	OC45 10p
BC116A 15p	BC214 13p	OC71 10p
BC143 25p	BC267 12p	2N2346 50p
BC147 10p	BC328 15p	2N2928 12p

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

10p for 1 Valve. Each additional Valve add 2p.

DM70	0-61	ECL83	0-66	GY501	1-18	PL82	0-48	30C1/PCF80	
DY51	0-80	ECL86	0-64	GZ34	0-80	PL83	1-04	30C15/	0-54
DY80/7	0-41	EF80	0-42	PC88	0-95	PL84	0-68	30C15/	
DY802	0-46	EF83	0-88	PC88	0-85	PL500	0-90	PCF800	1-01
EAB30	1-03	EF85	0-48	PC89	0-57	PL504	0-90	30C17	1-01
EB91	0-64	EF86	1-16	PC89	0-54	PL508	1-24	30C18/	
EB91	0-78	EF89	1-14	PC88	0-88	PL509	1-56	PCF805	1-00
EBF80	0-56	EF91	1-00	PC89	0-86	PL602	1-40	30F5/PCF818	
EBF83	0-59	EF92	1-87	PC89	0-64	PY33	0-65		1-03
EBF89	0-63	EF95	1-47	PC89	0-80	PC881/800	0-49	30FL1/	
EC86	0-78	EF183	0-63	PCF82	1-22	PC882	0-57	PC8500	1-00
EC88	0-76	EF184	0-63	PCF86	0-64	PCF82	0-56	30FL2	0-80
EC90	0-88	EF187	0-85	PCF90	1-00	PCF82	1-02	30FL2	1-13
EC97	0-40	EL34	0-92	PCF201	1-00	PCF82	1-02	30FL4	1-00
EC98	0-47	EL36	1-01	PCF801	0-64	PCF82	1-02	30FL4	1-00
EC98	0-44	EL81	0-86	PCF802	0-70	U191	0-88	30L1/PC84	
EC98	0-47	EL84	0-47	PCF806	0-64	U193	0-54	30L1/	0-54
EC98	0-44	EL85	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL86	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL87	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL88	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL89	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL90	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL91	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL92	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL93	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL94	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL95	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL96	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL97	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL98	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL99	0-86	PCF82	1-22	U193	0-54	30L1/	0-54
EC98	0-44	EL00	0-86	PCF82	1-22	U193	0-54	30L1/	0-54

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0-75	EF89	1-25	MU14	1-00	PY88	0-58	6J5M	0-65
AZ31	0-60	EF80	0-35	N78	3-50	6Y50	1-10	6J5G	0-45
CB131	1-40	EF85	0-45	OA2	0-45	6Y81	0-55	6J7G	0-30
CL33	1-50	EF86	0-50	OB2	0-45	6Y81	0-55	6J7M	0-30
CV31	0-60	EF89	0-35	PC86	0-65	6Y81	0-55	6K7G	0-30
DAF91	0-40	EF91	0-40	PC88	0-65	6Y81	0-55	6K7M	0-30
DAF96	0-60	EF92	0-50	PC97	0-55	6Y81	0-55	6K7M	0-30
DC90	1-35	EF95	0-45	PC90	0-55	6Y81	0-55	6K7M	0-30
DF91	0-60	EF98	0-80	PC84	0-85	6Y81	0-55	6K7M	0-30
DF96	0-60	EF183	0-40	PC88	0-82	6Y81	0-55	6K7M	0-30
DK91	0-60	EF184	0-40	PC89	0-55	6Y81	0-55	6K7M	0-30
DK92	1-00	EL32	0-60	PC89	0-85	6Y81	0-55	6K7M	0-30
DK96	0-75	EL33	2-50	PCF80	0-40	6Y81	0-55	6K7M	0-30
DL92	0-60	EL34	0-70	PCF82	0-42	6Y81	0-55	6K7M	0-30
DL94	0-48	EL36	0-80	PCF86	0-65	6Y81	0-55	6K7M	0-30
DL96	0-45	EL37	2-50	PCF80	0-40	6Y81	0-55	6K7M	0-30
DY86	0-45	EL41	0-90	PCF80	0-40	6Y81	0-55	6K7M	0-30
DY87	0-45	EL42	1-65	PCF80	0-40	6Y81	0-55	6K7M	0-30
DY802	0-47	EL84	0-35	PCF806	0-80	6Y81	0-55	6K7M	0-30
EAB30	0-38	EL95	0-60	PCF808	1-00	6Y81	0-55	6K7M	0-30
EAF42	0-70	ELL80	2-00	PC82	0-45	6Y81	0-55	6K7M	0-30
EB91	0-60	EM80	0-55	PC83	0-70	6Y81	0-55	6K7M	0-30
EB93	1-00	EM81	0-80	PC84	0-80	6Y81	0-55	6K7M	0-30
EB94	0-75	EM84	0-40	PC85	0-50	6Y81	0-55	6K7M	0-30
EB98	0-40	EM85	1-00	PC86	0-50	6Y81	0-55	6K7M	0-30
EBF80	0-40	EY1	0-45	PC86	0-50	6Y81	0-55	6K7M	0-30
EBF83	0-40	EY86	0-45	PC86	0-50	6Y81	0-55	6K7M	0-30
EBF89	0-32	EZ40	0-60	PC86	0-50	6Y81	0-55	6K7M	0-30
EBL91	2-00	EZ41	0-75	PC86	0-50	6Y81	0-55	6K7M	0-30
ECC81	0-45	EZ42	0-80	PC86	0-50	6Y81	0-55	6K7M	0-30
ECC82	0-38	EZ80	0-30	PC86	0-50	6Y81	0-55	6K7M	0-30
ECC83	0-38	EZ81	0-31	PC86	0-50	6Y81	0-55	6K7M	0-30
ECC84	0-35	GY601	0-80	PC86	0-50	6Y81	0-55	6K7M	0-30
ECC85	0-45	GZ20	0-65	PC86	0-50	6Y81	0-55	6K7M	0-30
ECC88	0-50	GZ22	0-65	PC86	0-50	6Y81	0-55	6K7M	0-30
EOH35	1-50	GZ34	0-75	PC86	0-50	6Y81	0-55	6K7M	0-30
ECH42	0-85	GZ37	1-25	PC86	0-50	6Y81	0-55	6K7M	0-30
ECH81	0-35	HN309	1-50	PC86	0-50	6Y81	0-55	6K7M	0-30
ECH83	0-50	K761	2-50	PC86	0-50	6Y81	0-55	6K7M	0-30
ECL80	0-60	K766	2-95	PC86	0-50	6Y81	0-55	6K7M	0-30
ECL82	0-48	K781 (7C5)	1-30	PC86	0-50	6Y81	0-55	6K7M	0-30
ECL83	0-75	K781	1-30	PC86	0-50	6Y81	0-55	6K7M	0-30
ECL86	0-55	K781	1-75	PC86	0-50	6Y81	0-55	6K7M	0-30
ECLL800	3-50	KT88	3-25	PC86	0-50	6Y81	0-55	6K7M	0-30
EF37A	1-20	KTW61	1-50	PC86	0-50	6Y81	0-55	6K7M	0-30

TRANSISTORS-INTEGRATED CIRCUITS

EXPRESS POSTAGE

10p per order.

AA119	0-07	BD124	0-80	QA200	0-08	ZTX600	0-15	2N2904	0-20
AA123	0-10	BD131	0-85	QA202	0-10	ZTX601	0-15	2N2904A	0-25
AA215	0-10	BD132	0-60	OC16	1-00	ZTX603	0-18	2N2905	0-28
AC107	0-25	BF115	0-25	OC20	2-00	ZTX631	0-25	2N2905A	0-25
AC126	0-25	BF167	0-25	OC23	1-25	ZTX650	0-18	2N2906	0-20
AC127	0-25	BF173	0-28	OC25	0-40	IN914	0-06	2N2926	0-10
AC128	0-20	BF179	0-28	OC28	0-70	IN4001	0-06	2N3053	0-20
AC176	0-25	BF180	0-35	OC25	0-25	IN4002	0-07	2N3055	0-20
AC187	0-20	BF181	0-35	OC26	0-25	IN4003	0-08	2N3525	0-20
AC188	0-20	BF194	0-13	OC27	0-25	IN4004	0-08	2N3514	0-20
AC191	0-22	BF195	0-13	OC28	0-25	IN4005	0-10	2N3515	0-25
AC192	0-22	BF197	0-15	OC29	0-25	IN4006	0-12	2N3702	0-11
AD140	0-50	BF200	0-25	OC30	0-25	IN4007	0-12	2N3703	0-12
AD149	0-40	BF561	0-25	OC31	0-25	IN4008	0-12	2N3704	0-14
AD161	0-39	BF572	0-25	OC32	0-25	IN4009	0-12	2N3705	0-15
AD162	0-39	BF573	0-25	OC33	0-25	IN4010	0-12	2N3706	0-16
AF116	0-25	BFX29	0-28	OC34	0-25	IN4011	0-12	2N3707	0-13
AF117	0-25	BFX29	0-28	OC35	0-25	IN4012	0-12	2N3708	0-13
AF118	0-25	BFX29	0-28	OC36	0-25	IN4013	0-12	2N3709	0-14
AF119	0-25	BFX29	0-28	OC37	0-25	IN4014	0-12	2N3710	0-14
AF120	0-25	BFX29	0-28	OC38	0-25	IN4015	0-12	2N3711	0-14
AF121	0-25	BFX29	0-28	OC39	0-25	IN4016	0-12	2N3712	0-14
AF122	0-25	BFX29	0-28	OC40	0-25	IN4017	0-12	2N3713	0-14
AF123	0-25	BFX29	0-28	OC41	0-25	IN4018	0-12	2N3714	0-14
AF124	0-25	BFX29	0-28	OC42	0-25	IN4019	0-12	2N3715	0-14
AF125	0-25	BFX29	0-28	OC43	0-25	IN4020	0-12	2N3716	0-14
AF126	0-25	BFX29	0-28	OC44	0-25	IN4021	0-12	2N3717	0-14
AF127	0-25	BFX29	0-28	OC45	0-25	IN4022	0-12	2N3718	0-14
AF128	0-25	BFX29	0-28	OC46	0-25	IN4023	0-12	2N3719	0-14
AF129	0-25	BFX29	0-28	OC47	0-25	IN4024	0-12	2N3720	0-14
AF130	0-25	BFX29	0-28	OC48	0-25	IN4025	0-12	2N3721	0-14
AF131	0-25	BFX29	0-28	OC49	0-25	IN4026	0-12	2N3722	0-14
AF132	0-25	BFX29	0-28	OC50	0-25	IN4027	0-12	2N3723	0-14
AF133	0-25	BFX29	0-28	OC51	0-25	IN4028	0-12	2N3724	0-14
AF134	0-25	BFX29	0-28	OC52	0-25	IN4029	0-12	2N3725	0-14
AF135	0-25	BFX29	0-28	OC53	0-25	IN4030	0-12	2N3726	0-14
AF136	0-25	BFX29	0-28	OC54	0-25	IN4031	0-12	2N3727	0-14
AF137	0-25	BFX29	0-28	OC55	0-25	IN4032	0-12	2N3728	0-14
AF138	0-25	BFX29	0-28	OC56	0-25	IN4033	0-12	2N3729	0-14
AF139	0-25	BFX29	0-28	OC57	0-25	IN4034	0-12	2N3730	0-14
AF140	0-25	BFX29	0-28	OC58	0-25	IN4035	0-12	2N3731	0-14
AF141	0-25	BFX29	0-28	OC59	0-25	IN4036	0-12	2N3732	0-14
AF142	0-25	BFX29	0-28	OC60	0-25	IN4037	0-12	2N3733	0-14
AF143	0-25	BFX29	0-28	OC61	0-25	IN4038	0-12	2N3734	0-14
AF144	0-25	BFX29	0-28	OC62	0-25	IN4039	0-12	2N3735	0-14
AF145	0-25	BFX29	0-28	OC63	0-25	IN4040	0-12	2N3736	0-

RTVC

* COMPLETE STEREO SYSTEM

System 1a. £62.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel (40 watts peak). All systems include:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/ stereo, on/off function and bass and treble filters. Plus headphone socket.

Specification:

20 wats per channel into 8 ohms 40W peak. Total distortion @ 10W @ 1kHz 0.1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV at 1kHz into 47K. equalised within ± 1 dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

Garrard SP 25 deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type IIa matched speakers - Enclosure size approx. 19 $\frac{1}{4}$ " x 9 $\frac{1}{2}$ " x 7 $\frac{1}{2}$ " in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling. 30 watts peak.

Complete System with these speakers £62.00 + £5.50 p & p.


System 2. £82.00

Viscount III amplifier (As System 1a)

Garrard SP 25 deck (As System 1a)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 $\frac{1}{2}$ " Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS. 8 ohms frequency range - 20 Hz to 18,000 Hz.

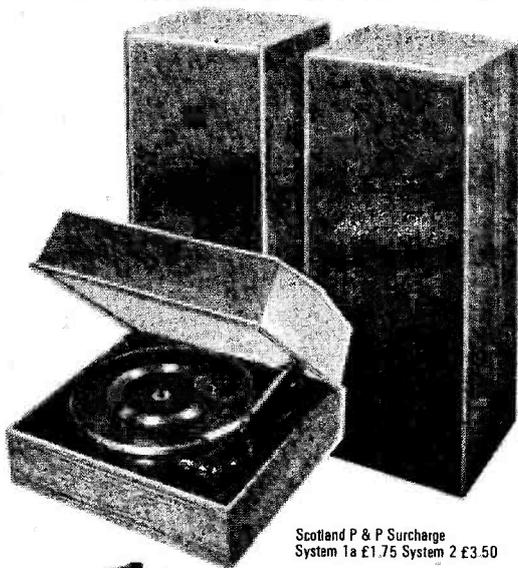Complete System with these speakers £82.00 + £6.50 p & p.



Scotland P & P Surcharge
System 1a £1.75 System 2 £3.50



PRICES: SYSTEM 1a

Viscount III R102 amplifier £27.00 + £1.60 p & p

2 Duo Type IIa speakers £26.00 + £5.50 p & p

Garrard SP 25 with Mag. cartridge de luxe plinth and cover £21.00 + £2.80 p & p

Total if purchased separately: £74.00

Available complete for only: **£62.00**
+ £5.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier £27.00 + £1.60 p & p


2 Duo Type III speakers £39.00 + £6.40 p & p

Garrard SP 25 with Mag. cartridge de luxe plinth and cover £21.00 + £2.80 p & p

Total if purchased separately: £87.00

Available complete for only: **£82.00**
+ £6.50 p & p

EMI SPEAKERS AT FANTASTIC REDUCTIONS

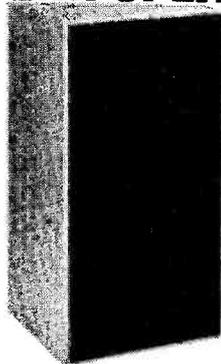

LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification - Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz - 20 KHz.


Our Price £29.00
(normally £56.97) + £5 p & p.

EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

Complete with crossover. Components and circuit diagram **£5.50** + £1 p & p.

20 WATT SPEAKER SYSTEM *

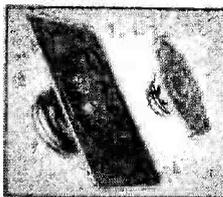

System consists of a 13" x 8" (approx.) elliptical woofer unit with a 8" x 5" (approx.) mid-range unit incorporating parasitic tweeter and crossover components and circuit diagram

Technical Specification: Bass Unit: Flux density - 100 K, speech coil - 1 $\frac{1}{2}$ ". Cone. Triple laminated paper with P.V.C. surround. Mid-Range Unit: Flux density - 33 K, speech coil - 1" with parasitic tweeter. Power handling: 20 watts RMS. Impedance - 8 ohms. frequency response - 20 Hz to 18,000 Hz.


Our Price £7.50
Complete + £1.35 p & p.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 $\frac{1}{2}$ " tweeter and matching crossover.

Easily put together with just a few basic tools.
Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS. (30 watts peak). Response 20-20,000Hz. Size 20" x 11" x 9 $\frac{1}{2}$ " approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

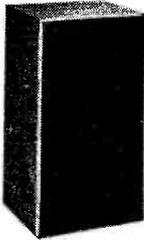
£18.95 pair complete
+ £4.50 p & p. Complete with crossover Components and circuit diagram



DECCA STEREO AMPLIFIER CHASSIS

Specification: 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47K (for magnetic cartridges). AC Mains only 240V. Controls - volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" x 5 $\frac{1}{2}$ " x 3 $\frac{1}{4}$ " approx.

£5.95 + £1 p & p.

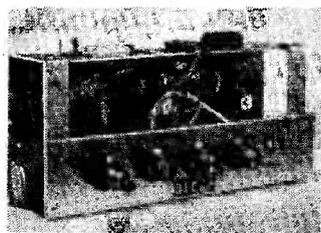

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high

and 4½" deep approx. **£8.00**+90p. p & p. Speaker including baffle and fixing strip **£1.65**+37p p & p. Car Aerial Recommended — fully retractable **£1.37**+32p p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £7.00**+90p p & p.

*STEREO 21 QUALITY SOUND FOR LESS THAN £20.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications — For the technically minded:

Input sensitivity 800mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutoff. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs.


Overall Dimensions. Speakers approx 15½" x 8" x 4". Complete deck and cover in closed position approx. 15½" x 12" x 6".

Complete only £19.95 + £2.60 p & p.

Extras if required. Optional Diamond Stylus **£1.37**.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£5.00**.

*DISCO AMPLIFIER

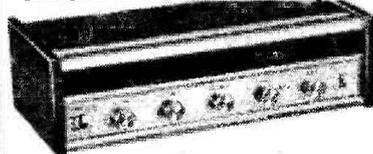

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12½" x 6" x 3½"

£17.00 + £1.15 p & p.

*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. Yours for only

£12.95 + £1.45 p & p.




BUILD YOUR OWN *STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£9** + £1.50 p & p. **£7.64** + 90p p & p.

PORTABLE DISCO CONSOLE*

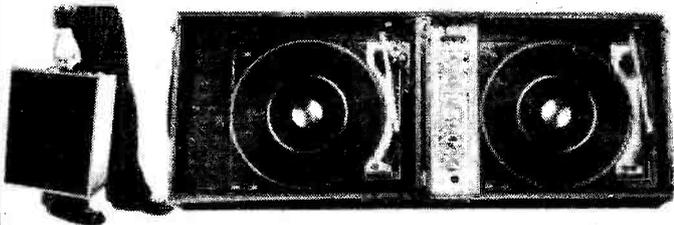

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV. Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation. Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalle meter). Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17½" x 13½" x 8½" (app.)
Unit Open — 35½" x 13½" x 4½" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £49.00 + £5.60 p. & p.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st April 1975 and subject to change without notice. All prices include V.A.T. at 8% rate.



21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs.
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

ESSENTIAL BOOKS FOR RADIO AMATEURS

NBFM MANUAL
by
R. S. Hewes, G3TDR
and
G. R. Jessop, G6JP

The use of frequency modulation by radio amateurs as a communication system has generally been confined to the vhf and uhf bands. When used for this purpose it is essentially a narrow band mode radically different from that used for high fidelity broadcasting. Until now references to narrow band frequency modulation equipment have been confined to articles appearing in various journals, but this manual is intended to present complete coverage of the subject from one source.

It is hoped that it will encourage the home construction of equipment which is truly narrow band, using the frequency or phase methods of modulation and taking full advantage of the mode by the use of the correct demodulator.

The relative freedom from interference to television, radio and audio equipment, and the excellent rejection of impulse noise, makes the mode attractive and economic for both fixed and mobile operation.
60 pages

Price: £1.10 inc p & p

AMATEUR RADIO TECHNIQUES
(5th edition)

by **Pat Hawker, G3VA**

Basically an ideas and source book, this ever-popular work brings together a large selection of new circuits and devices and many constructional and fault-finding hints. In this new edition some 50 pages of new material have been included and other sections have been revised and expanded.

304 pages Price £2.35 inc p & p Over 700 diagrams

**RSGB AMATEUR RADIO
CALL BOOK 1975**

Incorporates new call signs and amendments notified between August 1973, when the previous edition closed, and August 1974.

Also includes valuable operating data such as band plans, beacons, amateur radio prefixes in country order, ITU-zone list, beam headings and QSL Bureau sub-managers, and a list of RSGB affiliated societies, clubs and groups.

160 pages

Price £1.25 inc. p & p

These are just three of a complete range of technical publications, log books and maps for the radio amateur. Send a large stamped self-addressed envelope for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



250w Light Dimmers **£2.60 (15p)**
TRANSISTORS (p. & p. 10p.)

All new and full spec.
BC107/8/9, BC147/8/9, BC157/8/9 all 9p
BF180 25p, BF182/3 40p, BF184 17p,
BF187 13p, BFW10 55p, 741 8DIL 34p,
BF336 35p, 2N3771 £1.10, 2N3441 50p,
BD131 40p, 2N3055 45p, NE555 67p.

EX COMPUTER PC PANELS
4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards **£1.10 (35p)**

ELECTROLYTICS
2,200µ 63v **35p (11p)**
2,000µ 50v with clip **35p (11p)**
4,700µ 63v **60p (13p)**
68,000µ 16v **65p (32p)**
30,000µ 25v **65p (32p)**
3,600µ 40v 4 x 2" **55p (32p)**

5,000µ 35v **40p (15p)**
20A 100 piv Si recs 4 for **£1 (13p)**
3A 100 piv Si recs 4 for **50p (10p)**

250 mixed resistors **60p (15p)**
250 mixed capacitors **60p (15p)**
150 mixed HI-STABS **60p (13p)**
200 Si planar diodes **60p (9p)**
QH bulbs 12v 55w **50p (8p)**

2N3055 EQUIV 4 for **£1 (12p)**
SMALL ELECTROLYTICS
2.2µ 10/16v, 10µ 35v, 50µ 40v, 100µ 40v,
100µ 6v, 150µ 10v, 64µ 10v 12 for **45p (7p)**.

PRESETS 100mW "PIHER"
220Ω 470Ω 4k7 10k 100k 12 for **50p (7p)**.
Postage and packing shown in brackets
ADD 8% VAT TO TOTAL

KEYTRONICS


(Mail Order only)

**44 EARLS COURT ROAD
LONDON W8. 01-478 8499**

CENTURION

INSTRUMENT

CASES

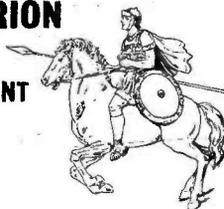

Model Nos. 119 and 121 two part aluminium construction base front and back unit finished in white gloss, hooded cover finished in blue hammer stove enamel.

Model D	W	H
119	152mm	127mm 89mm
121	152mm	203mm 76mm

£1.80 ea
£2.25 ea

Model Nos. 221F and 222F flat packs. Front & Rear panels aluminium case mild steel front panel finished in white gloss other parts finished in blue hammer stove enamel.

221F	152mm	203mm	152mm	£3.05 ea
222F	197mm	254mm	159mm	£3.65 ea

Prices include P & P U.K.
Add 8% V.A.T. U.K. only.
Send S.A.E. for full range brochure.

Manufactured by

Arbour Electronics Limited

Unit 13 East Hanningfield Ind. Est.
Nr. Chelmsford, Essex CM3 5BG
Tel. Chelmsford (0245) 400700.

Sheet metal work wiring assembly service available

4-STATION INTERCOM



£16.15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 65p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £23.75 per pair P. & P. 65p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY

£11.95

+ V.A.T. 96p


Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £19.95 + V.A.T. £1.04 P. & P. 65p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW8)
169 KENSINGTON HIGH STREET, LONDON, W8

Crescent Quality Components

BARGAIN CAPACITOR 2,000MFD at 50v. DC wkg. Size = 2" x 1 1/2" diameter. Tag ended. All new and unused. Our price 85p.

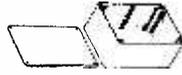BARGAIN PROJECT BOX
A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied). An ideal box to give a small project a professional finish. SIZE (Internal) 81mm x 51mm x 28mm. OUR PRICE 40p.



JB11D STEREO JUNCTION BOX

The most popular stereo junction box. Facility for two pairs of headphones and two speakers. 3 position switch selects headphones, loudspeakers or both. A bargain at 22-50



LIGHT EMITTING DIODES

TL209 (Red) With Clip 22p each
TL209 (Green) With Clip 35p each
TL209 (Yellow) With Clip 90p each
Mled 500 T092 Type 16p each

LED READOUTS

Litronic
DL707 3 Character 14 Pin Dtl. 22-00
DL701 as above but ± 1 22-00
DL747 6 Character 22-62
Mintron
3015 7 Segment 16 Pin Dtl 41-18
3015G as above but ± 1 41-18
Clock Chip
CR7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet 24-95
Circuits and Information Sheet 15p
Lit 704 Led Display for above 41-10
Or 4 for 44-20

WAFER SWITCHES

1 Pole 12 Way
2 Pole 2 Way
2 Pole 3 Way
2 Pole 4 Way
2 Pole 6 Way
3 Pole 4 Way
4 Pole 3 Way
22p each



POTENTIOMETRES

All types 1" and less diameter
Singles Dual
5K Log or 5K
10K Lin Less 10K
25K Switch 25K Less
50K 17p each 50K Switch
100K 100K 48p each
250K Double 250K
500K Pole 500K
1M Switch 1M
2M 2M 2M

PRE SETS

Sub Miniature Skeleton Type 0-1 Watt Horizontal Mounting 100, 250 and 500 ohm, 1k, 2-5k, 5k, 10k, 20k, 50k, 100k, 250k, 500k, and 1M ohm 6p each

MAINS TRANSFORMERS

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high
Fixing centres: 2 1/2" max.
TR1 20-0-20v 100 m/a
TR2 12-0-12v 100 m/a All
TR3 9-0-9v 100 m/a 240 Volt
TR4 0-0-0v 100 m/a Primary
TR5 9-0-9v 100 m/a
Our Price 21-23 each

500/850v MAINS RELAY

Heavy duty contacts 9-500 ohm coil. All new and unused D.P.D.T. mains relays 50p, Carr. Free. Special quantity 44p per 100 off.

MINIATURE RELAYS

Brand new range of British made Relays, Size 1 1/2" x 1" x 1/2". All two changeovers with 250v 1-5A contacts and suitable for fitting on 1m Veroboard.
Type Volts Current Ohms
27/A 12v 17M/A 700 All
21/A 12v 28M/A 430 21-30
12/A 6v 33M/A 185 each

MONO/STEREO MICROPHONE MIXER

9 volt. High impedance input. Gold finish with four black plastic chrome tipped level control knobs. On/Off switch and stereo/mono switch. 4 Input sockets.

SPECIFICATIONS:-

Input Imp = For XTAL Mics etc.
Gain = Approx 3.D.B.
Max Input Sig = 1 volt
Max Output Sig = 1-3 volt
Noise Ratio = -60DB
Supply = 9 volt
OUR PRICE = 25-25p

POWER SUPPLY UNITS

PP1 switched 3, 4, 6, 7 1/2, 9 and 12 volts at 500 m/a, with on/off switch and pilot light. Size: 130mm x 95mm x 75mm. ONLY 24-00.
PP2 Switched 6 - 7 1/2 - 9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders 22-25
PP3 Car converter. From 12v Pos. or Neg. to = 6 - 7 1/2 - 9 volt. Easy to fit and transistor regulated 22-90



VEROBOARD

2 1/2 x 3 1/2	.15	.15	Plain .15
2 1/2 x 5	24p	24p	15p
3 1/2 x 3 1/2	34p	34p	18p
3 1/2 x 5	34p	34p	
3 1/2 x 8	49p	49p	
17 x 2 1/2	1-06p	77p	60p
17 x 3 1/2	1-45p	1-16p	75p
17 x 5	1-85p		1-10p
Pin insertion tool			72p
Spot face cutter			52p
Pkt. 25 pins (state -1 or -15)			25p

LOUDSPEAKERS

2 1/2" 8 ohm 50p
2 1/2" 40 ohm 50p
2 1/2" 80 ohm 50p
5" 8 ohm ceramic 11-25
6 1/2" 8 ohm dual cone ceramic 22-50
10" 8 ohm dual cone ceramic 23-75
7" x 4" 8 ohm ceramic 21-60
8" x 4" 8 ohm Permatan Magnet 41-00
*EMI 13" x 8" 450 Kit 44-10
3 8 - 15 ohm 44-10
*EMI 13" x 8" 350 Kit 8 ohm 27-50



10 inch DUAL CONE L/S Manufactured by "ELAC" to a very high standard these loudspeakers are a real bargain. SPEC:- Size=10" Dual Cone. Power=10 Watts Frequency=40-12000Hz Our Price = 23-75p each

MAINS KEYNECTOR

Keynetor connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage demonstrations, etc. Multi connections can be made (max. load 13A fused). 22-25p.



ALUMINIUM BOXES

Metal project boxes give your work a professional finish

AB7	L	W	H	54p
AB8	2 1/2	5 1/2	1 1/2	63p
AB9	4	4	1 1/2	54p
AB10	4	5 1/2	1 1/2	63p
AB11	4	2 1/2	2	54p
AB12	3	2	1	46p
AB13	6	4	2	69p
AB14	7	5	2 1/2	84p
AB15	8	6	3	99p
AB16	10	7	3	11-25
AB17	10	4 1/2	3	11-02
AB18	12	5	3	11-20
AB19	12	8	3	11-50

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1005 = 105mm x 73mm x 45mm = 51p
1006 = 150mm x 75mm x 47mm = 66p
1007 = 184mm x 124mm x 60mm = 96p
1021 = 106mm x 74mm x 45mm (sloping front) = 50p

BARGAIN BOARD5

Components galore for the experimenter Ex Computer boards with Resistors, Capacitors and useful Transistors—at least 4 transistors per board. Five boards 41-00.

CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.

ME6 = 0 to 50 micro amp Full Scale
ME7 = 0 to 100 micro amp Full Scale
ME8 = 0 to 500 micro amp Full Scale
ME9 = 0 to 1 m/a Full Scale
ME10 = 0 to 5 m/a Full Scale
ME11 = 0 to 10 m/a Full Scale
ME12 = 0 to 50 m/a Full Scale
ME13 = 0 to 100 m/a Full Scale
ME14 = 0 to 500 m/a Full Scale
ME15 = 0 to 1 amp Full Scale
ME16 = 0 to 50 volts
ME17 = 0 to 300 volts A.C. Full Scale
ME18 = "8" Meter
ME19 = "VU" Meter



OUR PRICE 22-00

ADD LUXURY TO YOUR CAR

with a motor driven car aerial

SPEC:-
★ 5 section
★ extended length 100cm
★ Length under fender 40cm
★ Cable length 120cm

DECON DALO 33PC ETCH RESIST PFM
The Decon Dalo 33PC is a unique instrument for the professional and amateur electronics engineer, enabling him to prepare in minutes a perfect printed circuit board

OUR PRICE 86p
WIRE WOUND VOLUME CONTROL
250ohm Only 25p EACH. Approx 1" Diameter. Long standard spindle.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

★ Completely Portable
★ Heats in 5 seconds
★ Solders up to 150 joints or more per charge
★ Recharges automatically in its own stand
★ No AC leakage or induced current to damage delicate components
★ Heats to 700 deg. F
★ Fine Tip for delicate and general purpose soldering
★ Only 8" long and weighs just 6 ozs.
OUR PRICE 29-75 (spare bits are available)

STOP PRESS

BHA0002 15 watt Amp Module 22-50
NE555 Timer I.C. 78p
MC1310P Stereo Decoder I.C. 22-00
7805 Regulator 41-40
TIP 29A 55p
TIP 30A 63p
BC107 10p
BC108 10p
BC109 10p



L.C. SOCKETS
D.I.L.
8 pin
14 pin
16 pin 14p

BARGAIN TRANSFORMERS

12-0-12 volt 500m/a
240 volt primary transformer bargain.
approx size = 60mm x 40mm x 50mm
fixing centres = 75mm
Our Price = 21-20.

18 volt 500m/a
240 volt primary
approx size = 60mm x 40mm x 50mm
fixing centres = 75mm
Our Price = 21-00.

LOW NOISE LOW PRICE CASSETTES

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C80 = 81p
C90 = 42p
C120 = 53p
10% Discount on ten or more cassettes of one type

U.K. POSTAGE 20p UNLESS OTHERWISE STATED
V.A.T. Please add 8% to all Totals

CRESCENT RADIO LTD. P.W.
All mail to 11 MAYES ROAD, WOOD GREEN, LONDON N22 6TL
Phone: 01-888 3206
Callers Welcome at 15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct You should own one.
CRESCENT CATALOGUE
Price 30p.


12 inch MODELS

T12/35 Rated Power 35 WATTS

Centre Pole Diam. 1 1/2" Imp. 8-15Ω
Twin Cone. Range: 50-17000Hz
Ceramic Magnet
Weight: 600 Gms

Rec. Price

£10.50

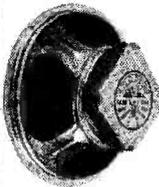

T12/60 Rated Power 60 WATTS

Centre Pole Diam. 2" Imp. 8-15Ω
Range: 60-9000Hz
Ceramic Magnet
Weight 1150 Gms.

Rec. Price

£17.50




T12/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp 8-15Ω
Range: 40-5000Hz
Ceramic Magnet
Weight: 1250 Gms

Rec. Price

£29.00

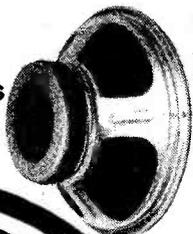

All Rec. Prices inc. VAT

15 inch MODELS

T15/70 Rated Power 70 WATTS

Centre Pole Diam. 2" Imp 8-15Ω
Ceramic Magnet
Weight: 1150 Gms
Range: 50-4000Hz

Rec. Price

£19.00



T15/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp. 8-15Ω
Ceramic Magnet
Weight: 1250 Gms.
Range: 50-4000Hz

Rec. Price

£32.75

18 inch MODEL

T18/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp. 8-15Ω
Ceramic Magnet
Weight: 1250 Gms.
Range: 35-4000Hz

Rec. Price

£37.50



Wholesale, Retail and Export enquiries to Sole Distributors:-

AUDIO EQUIPMENT LTD.

102 Henconner Lane, Leeds 13

S.A.E. please for trade terms or leaflet

NEW

PRACTICAL PAPERBACKS FROM FOULSHAM-TAB

THE COMPLETE SHORTWAVE LISTENERS

HANDBOOK by Hank Bennet **£2.10**

ELECTRONICS & PHOTOGRAPHY by Robert M Brown & Mark Olsen **£1.85**

GETTING THE MOST OUT OF YOUR ELECTRONIC CALCULATORS by William L Hunter **£1.85**

INDEXED GUIDE TO MODERN ELECTRONIC CIRCUITS by Robert L Goodman **£1.90**

MODEL SAIL AND POWER BOATING . . . by remote control by George Siposs **£1.80**

RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD edited by Wayne Green **£1.95**

AMATEUR FM CONVERSION & CONSTRUCTION PROJECTS by Ken Sessions, Jnr **£2.10**

CAR STEREO SERVICE & INSTALLATION by Paul Dorweiler & Harry Hansen **£1.95**

COLOUR TV TROUBLES (FACTBOOK) by The Editors of Electronic Technician/Dealer **£2.30**

ELECTRONIC TEST EQUIPMENT—and how to use it by Joe Risse **£1.85**

ELECTRONICS UNRAVELLED—A new common-sense approach by James Kyle **£1.90**

SIMPLIFIED COMPUTER PROGRAMMING—The easy RPG way by Kelton Carson **£1.95**



FOULSHAM-TAB LTD.
YEOVIL ROAD, SLOUGH, BERKS

GUEST ELECTRONIC DISTRIBUTION LIMITED

Guest, normally supplying electronic components to industry, are making available packs of specially selected components for the home constructor. These components are of professional quality at hard to beat prices.

PACK 1—CAPACITOR PACK

30 Miniature vertical mounting electrolytic capacitors 50V working.

5 x 0.47μF	5 x 10μF	£2.00 (one pack)
5 x 1.0μF	3 x 22μF	£3.50 (two packs)
5 x 2.2μF	2 x 33μF	
5 x 3.3μF		

PACK 2—RESISTOR PACK

Pack of 200 medium power (0.75 & 1W) resistors.

Assorted values throughout E24 range 5%. **£2.00 (one pack)**

PACK 3—POTENTIOMETER PACK

Pack of skeleton potentiometers linear 1/4W.

4 x 250Ω	4 x 10KΩ	
4 x 500Ω	4 x 50KΩ	£2.50 (one pack)
4 x 1KΩ	4 x 100KΩ	
4 x 2.5KΩ	4 x 2.5MΩ	

PACK 4

A special pack designed for the constructor who is "stocking up" generally and seeks excellent value.

Comprising:

- Selection of electrolytic capacitors (30+)
 - Comprehensive selection of medium power resistor (5%) E24 series (100+)
 - Selection of skeleton potentiometers (32+)
 - Selection of lampholders (5+) with bulbs
 - Miniature 250V 2A toggle switches, 3 or 4 poles (2+)
- £5.50 (one pack)**

All prices include VAT and Post and Packing.

Please send cheque/P.O./Cash, clearly stating pack required and address to:

BRIAN WOODS

(REF: B.D.) Marketing Services, Guest Distribution, Redlands, Coulsdon, Surrey CR3 2HT

NEW ITEMS THIS MONTH

The bargains in this column are just some of the items which appeared in the April supplement to our catalogue. You can receive this catalogue and the next 12 supplements by sending 21.

Miniature microswitch with roller, Cherry ref. no. E52, size approx. $1\frac{1}{2}$ " long x $\frac{1}{2}$ " high x $\frac{1}{4}$ " thick with steel roller on $\frac{1}{4}$ " long actuating lever. 35p each.

Triac, ex unused computer American "GE" ref. no. 8C 40D, this is a 600v 12 amp triac. A snip at £1.40.

Rectifier, American "GE", 100v 10 amp. 65p each. **Computer condensers**, American made Sangamo, their type DCM-21, 500 mfd, 35v DC working with mounting clip and terminal sockets. Price £1 each + 25p post.

Reel to reel tapes, pre-recorded with classic and light music, new in perspex type storage box, 10 different titles (our assortment). 45 the lot, which makes them worth buying even if you do not like the music recorded on them. Please add 80p post. 50 all different £25.

Multi-voltage transformer 13 watts, an extremely versatile transformer and it is quite surprising the number of different voltages which may be obtained by using its two windings or parts of these windings in assisting or opposing modes. In addition to these, such voltages as 20-0-20 or 25-0-25 or 130-0-130 may be obtained. The two secondary windings are (1) 50v tapped at 30v and (2) 260v tapped at 240, 220, 200 and 130. Special snip price, only £1.30p post.

Ring main cable Springtime is the time for alterations at home and if you are contemplating any lighting or heating alterations, then note we have good quality ring main cable 13 amp twin and earth, price 15p per metre, cut to your length, or £11.75 per 100 metres + £1 post.

Diode for light bulbs Springtime is the time for length, or £7.75 per 100 metres. Also for ring mains etc. we have junction boxes at 14p each, 13 amp ring main sockets, flush mounting, white, at 40p each, brown at 25p each or brown switched at 80p each. 13 amp 2 gang sockets, brown, unswitched, at 60p each. 5 amp 3 pin sockets, white at 25p each. Switches in white and grey boxes 20p each—white spur with 13 amp socket 50p. 3KW tantalum heaters. We have had a further small delivery of these and can once again supply. Price, a little up unfortunately, now £4.80 + 60p post. Control switch 55p. Knob for same 25p.

Break-down unit contains a large range of most useful parts some of which are as follows—66 silicon diodes equivalent OA91. 68 resistors, mostly 1 watt 5% covering a wide range of values. 4 x .1 mfd 400v condensers. 15 x .01 mfd 100v condensers. 2 RF chokes. 8 x B9 valve holders. 1 x 4H choke. 1 x 21v transformer. 1 heated unit containing 4 delay lines. Tag panels, trimmer condensers, suppressors, all mounted up on a useful chassis sized approx. 9" x 5" x 7". Offered at only 75p—the 66 diodes would cost at least 10 times this amount, so this is obviously a snip not to be missed. Post and packing 50p.

Waterproof 3 core leads for lawn mowers etc., new colour code, 5A rating, this is a perfectly standard pvc circular flex which will cost you 15p per metre in your local shop. Offered at the special price of £1.85 per 25 metre length + 30p post. Fits a 13 amp socket to a cable drum, wind this lead round the drum to terminate with 3 amp rubber covered plug (available, price 40p) and you have a very useful extension lead.

Aquarium thermostat, in a sealed glass tube, but adjustable over the tropical fish range. Price £1 each.

Computer boards with ICs, We guarantee each board have at least 15 ICs, the boards are in tip top condition, as far as we know they were never put into service. Price 75p each.

Computer cooling fans, the famous Plannair, these are a six bladed 4 1/2" fan rotating at approx. 3000 revs per minute. In a die cast case sized approx. 5 1/2" square with 4 fixing holes and cable entry box. Now new, but any not in perfect working order would be replaced. Price £3 each + 30p post.

Double-ended mains motors, special snip this month! It has a normal induction motor, not high powered but quite suitable for operating a fan in a heater or cooker hood or similar. This has the advantage that having a spindle from each end thus any fan blade should be right. Another feature is that this has 4 mounting feet. Special price, only 55p each.

Slot meter, Another special bargain this month because of its high and useful breakdown value is the slot meter. (a) It is in a useful box with lock, size approx. 8" x 3" x 4" (b) it has a Sangamo motor of 1 rev per hour which the makers price in excess of £3 (c) it has a digit counter and (d) it has a coin switch mechanism. Undoubtedly an unrepeatable bargain at £2 + 30p post.

High power battery motor, 12v operated, strong enough to power a motor mower, go-cart or similar. Speed easily variable. These motors can also be used as a brake for any rotating machine, simply by coupling the spindle to the machine and short-circuiting the windings by a variable resistance, price £2.50.

Transistor type 2N3065, thoroughly checked, for high gain, suitable for fluorescent lighting in verters etc. 45p each.

Relay "olasta" Swiss, made with watchmaker's precision, 1600 ohm coil operates heavy duty gold or silver contacts, one set changeover and two other sets open or relay closing. A really high-class relay, supplied in a transparent plastic box which can be used as a dust cover. Do not miss this bargain at 55p. **2 circuit toggle switch** normal panel mounting through 3/8" hole, one circuit changeover, the other circuit simply on-off. 80p each.

MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this:

1 Unilex Amplifier	Ref. EP.9000	£1.60
1 Unilex Amplifier	Ref. EP.9000	£1.60
1 Unilex Pre-Amp	Ref. EP.9001	£1.98
1 Unilex Power Unit	Ref. EP.9002	£2.35
1 Control panel kit with spun aluminium faced knobs		£2.80

Pair of 15 ohm speakers made by Goodmans are also available if required, price £3.80 the pair. No extra postage if ordered with the above, otherwise add 25p.

SPECIAL PRICES TO COLLEGES AND INSTITUTIONS WISHING TO INCLUDE THIS KIT IN THEIR CURRICULUM.



SMITHS CENTRAL HEATING CONTROLLER



Push button gives 10 variations as follows:—(1) continuous hot water and continuous central heating (2) continuous hot water but central heating off at night (3) continuous hot water but central heating on only for 2 periods during the day (4) hot water and central heating both on but day time only (5) hot water all day but central heating only for 2 periods during the day (6) hot water and central heating on during the day time only—then for summer time use with central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off. A handsome looking unit with 24 hour movement and the switches and other parts necessary to select the desired programme of heating. Supplied complete with wiring diagram. Originally sold, we believe, at over £15—we offer these, while stocks last, at £5.95 each, post 30p.

WALL THERMOSTATS

Wall mounting and in a handsome plastic case. (Cream and beige). Adjustable by slider (lockable) and may be set to control temperature from around freezing through to 50°C. The slide panel is engraved and indicates (frost), (warm), (very warm), etc. The thermostat will control heaters, etc., up to 15 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse, etc. Price £1.65. Don't miss this.

THIS MONTH'S SNIP

Latest BSR Record Changer with ceramic Stereo Cartridge £6.95 and if purchased at the same time teak veneered wooden plinth and Perspex cover for only £4.00 instead of £4.95 P.&P. £1 on one or both items.

TRANSISTOR ASSISTED CAR IGNITION

This system which has proved to be efficient and reliable, was described in the April *Wireless World*. We can supply kit of parts. Price £5.55 plus 30p post. When ordering please state whether for positive or negative systems.

RADIO STETHOSCOPE

Easiest way to fault find, traces-signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal earpiece, £2.20 twin stetho-set insns. 20p.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.75 plus 40p P. & P.

1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a large clear dial, size 4 1/2" x 3 1/2", which can be set in 1 minutes up to 1 hour. After preset period the bell rings. Ideal for processing a memory jogger or, by adding simple lever, would operate micro-switch. £1.26.

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 30 metre bands—kit contains chassis front panel and all the parts, £1.25—crystal ear-phone 50p.

INSTANT START FLUORESCENT LIGHTING BARGAINS

Starters—control gear, complete with tube ends and tube clips for window lighting, signs, fascias, etc. 4 ft. 40 w. £1.50; 5 ft. 65w. £1.60; 5 ft. 80w. £1.75; 6 ft. 80w. £1.95; and for pairs as follows:—twin 2 ft. 20w. £2.55; twin 3 ft. 30w. £2.75; twin 4 ft. 40w. £2.95; twin 5 ft. 65w. £3.25; twin 5 ft. 80w. £3.95; twin 8 ft. 125w. £4.50. These are about one half of maker's current prices and can't be repeated once stocks are cleared. Please add 30p per piece to cover postage or carriage.

TERMS:—

ADD V.A.T.
Send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 30p.

MAINS TRANSFORMERS

All standard 230-250 volt primaries.

		£	p
1v	1 amp (special)	1.75	
2.4v	5 amp	.85	
6.3v	2 amp	1.00	
6.3v	3 amp	1.50	
9v	1 amp	.85	
9v	3-5 amp	1.95	
12v	11 amp	1.50	
12v	1 amp	1.00	
6.5v-0.6 5v	1 amp	1.35	
18v	1 amp	1.25	
20v	1 amp	1.00	
24v	1 amp	1.50	
24v	3 amp	1.50	
12-0-12v	50mA	1.20	
6-0-6v	50mA	1.20	
8-0-8v	1 amp	1.25	
18-0-18v	2 amps	3.50	
25v	1 1/2 amp	1.85	
50v 2 amp & 6.3v	1 amp	4.50	
60v 5 amp & 5v	1 amp	7.50	
27v	3 amp	4.50	
30v	37 amp	22.00	
80v tapped 75v & 70v	4 amp	5.50	
230v-60mA & 0-3v	1.5 amps	1.75	
275-0-275v at 90mA & 6-4v	3 amps	2.25	
EBT Transformer 5000v			
23mA	(intermittent)	5.50	

Charger Transformers			
6v and 12v	2 amps	1.25	
6v and 12v	3 amps	2.25	
6v and 12v	5 amps	3.50	

DEDUCT 10% IF YOU ORDER 10 OR MORE OF ONE TYPE, ADD 85p PER TRANSFORMER IF NOT COLLECTING.

RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable or closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. 35p each. Resistor and rectifier 20p extra.

BLACK LIGHT

As used in discotheques and for stage effects, etc. Virtually no white light appears until the rays impinge on luminous paint or white shirts, etc. We offer 12" 8w tube complete with starter, choke, lamp-holders and starter-holder. Price £2.75 + 30p post. Tubes only £2 + 30p post.

TAPE DECK

In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 3 1/2". Mains operated on metal platform with tape head and guide. Not new but guaranteed good working order. Price £1.95 plus £1 post and insurance.

LIGHT SWITCH

Automatically switches on lights at dusk and off at dawn. Can also be used where light and dark is a convenient way to stop and start an operation. Requires only a pair of wires to the normal switch. In bakelite box, normal switch-plate size. 1 amp model £2.95.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.20.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in Box all ready to work. £7.95 plus 95p VAT and postage.

MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heaters, etc. New and perfect. Snip at 75p Postage 30p for first one, 10p for each one ordered. 1" stackmotor £1.04. 1 1/2" stackmotor £1.20.

AUTO-ELECTRICAL CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £6.95 plus 25p post and insurance.

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.), 103 TAMWORTH ROAD,
CROYDON CRO IX

ERSIN

Multicore

5 CORE SOLDER



for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Erskin Multicore Solder contains a trace of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Erskin Multicore Savbit Solder in a dispenser 7ft 6 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Erskin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints

Dispensers of Erskin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Erskin Multicore Solder.

Size 19A 34p



NEW BIB WIRE STRIPPER & CUTTER



Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B. 80p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.


Size 18 90p

Bib Hi-Fi Accessories Limited,
 56/6 J.K. Sales Corporation Ltd, 10, Bow Rd, Harnley, Herts. HP2 4RH

Prices shown are recommended retail including V.A.T. from Electrical and Hardware Shops. If unavailable, send for P.O. Prices and specifications subject to change without notice.

LISTEN TO CODAR® THE WORLD!

★ CR70A

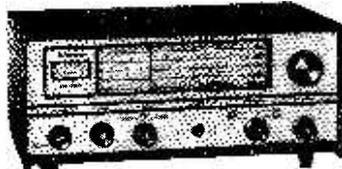

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, international broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ IMPORTANT NOTE
 This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

*** Special discounts for Educational Authorities and Senior Citizens.**



★ MADE TO ORDER!

£37-15!

VAT PAID CARR. 85p

★ P.R.40 ★



£10-93!

VAT PAID CARR. 32p

R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1-5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee ...

MULTIBAND-6 ★

SHORT WAVE RECEIVER KIT

£16-90! CARR. 43p

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual. fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST (STAMP APPRECIATED)

ON THE DESIGN STAFF—G3SZM G3IRE

CODAR®

TO COPE WITH INCREASING DEMAND—PLEASE NOTE NEW SALES OFFICE TEL No. BRIGHTON 38345 MON-THURS-9.30 a.m.-4.30 p.m.

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE. **BN15-8TZ**

MAPLIN

ELECTRONIC SUPPLIES

Get your 1975 CATALOGUE!

132 Big Pages

Includes dozens of useful & interesting circuits you can build; data; hundreds of pictures, transistor equivalents list and hundreds of new lines. Packed with information. Only 40p.

NEW SHOP NOW OPEN, details below

SUPERSONIC SAME-DAY-SERVICE - MEANS QUALITY COMPONENTS - FAST!

● RESISTORS

CARBON FILM

1/4W 1.0 to 1M: 5%, 1M2 to 10M: 10% E12
1/2W 1.0 to 10.0: 5%, 1M2 to 10M: 10%
E12 11.0 to 910k: 5% E19 & E24 1p each

METAL OXIDE

1/4W 10.0 to 1M: 2% E12 & E24 4p each

WIREWOUND

3W 0.25Ω, 0.27Ω, 0.33Ω, 0.47Ω: 10%, 1Ω: 5%, 10Ω: 5%, 100Ω: 5%, 1k: 5%, 10k: 5%, 100k: 5%, 1M: 5%
1.2Ω to 270Ω: 5% E12 14p each
Other ranges stocked. See our catalogue for details.

E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

● POTENTIOMETERS

Rotary miniature carbon track 1/4" spindle.
Values available: 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M.

Log. Single-gang 17p
Lin. Single-gang (+ 1K) 17p
Log. or Lin. Single-gang with switch 36p

Log. or Lin. Dual-gang without switch 54p
Slider 60mm track. Metal-cased: overall length 86-15mm (knob extra 7p)

Values available: 1k; 5k; 10k; 25k; 50k; 100k; 250k; 500k; 1M. Single Gang 38p
Log Single Gang 42p
Lin or Log Dual Gang 49p

Presets: 0-1W Vertical or Horizontal.
100Ω, 220Ω, 470Ω, 1k, 2k, 4k, 7k, 10k, 22k, 47k, 100k, 220k, 470k, 1M 7p each

● CAPACITORS

Sub-miniature

Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1	63	63	63
1.5	63	68	16
2	63	68	63
3	63	100	4
4	63	100	10
6	63	100	25
6.8	63	100	40
10	25	100	63
10	63	150	63
15	16	150	16
15	40	150	25
15	63	150	40
22	10	150	63
22	25	220	4
22	63	220	10
33	6	220	16
33	16	220	25
33	16	220	63
33	40	330	4
47	4	330	10
47	10	330	16
47	25	330	25
47	0	330	63
47	63	330	220
		4700	4

● MAINS CONNECTORS

P360 3-pin 1.5A Chassis Plug with Line Socket 40p
SA2190 3-pin 5A Chassis Plug 28p
SA1862 Line Socket for SA2190 32p
P437 3-pin 5A Chassis Socket with Line Plug 77p

● TRANSISTORS & DIODES

AC127	18p	BY126	13p
AC128	18p	BY127	13p
AC176	17p	BY164	49p
AD161/162 MP	BZY68 series		
BA100	83p	MFF102	38p
BA145	22p	OA91	6p
BC107	10p	OA200	7p
BC108	17p	OC71	20p
BC109	13p	OC146D	35p
BC109C	15p	T1843	28p
BC142	28p	W005	30p
BC143	26p	W04	38p
BC147	10p	IN914	4p
BC148	10p	IN4001	6p
BC149	12p	IN4002	6p
BC168C	12p	IN4003	6p
BC169C	12p	IN4004	7p
BC173	17p	IN4005	8p
BC182L	10p	IN4006	8p
BC183L	12p	IN4007	9p
BC184L	12p	IN4148	49p
BC212L	14p	2N1392	20p
BC213L	15p	2N1303	20p
BC214L	18p	2N1304	30p
BC271	22p	2N1711	24p
BD131	45p	2N2219	25p
BD132	54p	2N2646	45p
BD131/BD132	2N2905	35p	
MP	£1.20	2N2926or	18p
BD135	36p	Ye	18p
BD139	49p	Gn	13p
BD140	69p	2N3053	18p
BF258	85p	2N3055	49p
BF259	85p	2N3819	22p
BFX29	80p	2N5459	51p
BFX30	33p	7400	16p
BFX84	30p	7413	38p
BFX85	36p	7447	£1.10
BFX87	30p	7473	54p
BFX88	25p	7474	45p
BFY50	20p	7490	45p
BFY51	22p	7493	98p
BFY52	20p	74121	39p
L.E.D. RED	2mcd 1/2" only		15p
Panel mtg. chip	(Other colours and 7-seg. displays in our catalogue)		5p

● INTEGRATED CIRCUITS

CA3046 (14-pin DIL)	69p
LM10042C (TO99)	£4.25
MC1310P (14-pin DIL)	£2.50
MC1495 (U4796) (14-pin DIL)	78p
MFC4000B	59p
MFC6040	85p
NE555V (8-pin DIL)	65p
SC1495 (14-pin DIL)	£2.70
SG3402 (14-pin DIL)	£1.60
TBA1808	£1.00
µA741C (8-pin DIL)	36p
µA741C (14-pin DIL)	45p
µA747C (14-pin DIL)	£1.05
µA749C (8-pin DIL)	89p
ZN414 (TO18)	£1.20

VOLTAGE REGULATORS

LA7805 5V 1.5A (TO3)	£1.75
LA7815 15V 1.5A (TO3)	£1.75
MV8 5V, 12V, 15V, 500mA (TO3)	£1.60
µA78M05 5V 500mA (Plastic power)	£1.05
µA78M15 15V 500mA (Plastic power)	£1.05
µA78L05 5V 100mA (TO92)	80p
µA78L15 15V 100mA (TO92)	80p
µA723C Variable 2 to 37V (TO99 or 14-pin DIL)	75p

Our catalogue contains applications circuits and data for all the above I.C.'s and many more

● DISCOUNTS

Details in our catalogue. Start collecting MES Discount Vouchers NOW!

● SWITCHES

Rotary adjustable stop. 1 pole, 2 to 12 way; 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way 40p each
Slide Sub-min DPDT 10p
Slide Min. DPDT 14p
Push to make Non-locking SPST 14p
Push-on, Push-off Locking DPST 250V 4A 86p
Rocker White DPST 250V 10A 42p
Rotary Mains DPST 250V 2A 29p
Toggle with ON/OFF plate DPDT 250V 1.5A 26p

BCD OUTPUT SLIDE SWITCH
Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue. £1.88

● PLUGS & SOCKETS

DIN	PLUG	CHASSIS SOCKET
2-pin	8p	7p
3-pin	8p	8p
4-pin	10p	8p
5-pin A (180°)	12p	8p
5-pin B (240°)	12p	8p
6-pin	12p	8p

JACK PLUGS
1in. Std. Mono Plastic Barrel 13p
1in. Std. Mono Metal Barrel 18p
1in. Std. Stereo Plastic Barrel 18p
1in. Std. Stereo Metal Barrel 18p
2.5mm Plastic Barrel 10p
2.5mm Metal Barrel 15p
3.5mm Plastic Barrel 10p
3.5mm Metal Barrel 15p

JACK CHASSIS SOCKETS
2.5mm Open-type metal 9p
3.5mm Open-type metal 9p
1/2" Std. Mono Open-type metal 14p
1/2" Std. Mono Moulded with 2 break contacts 16p
1/2" Std. Stereo Open-type metal 18p
1/2" Std. Stereo Moulded with 3 break contacts 81p

PHONO
Plastic-topped Plug 7p
Screened Plug 12p
Chassis Socket Single 5p
Chassis Socket Twin 8p

● TRANSFORMERS

LT700 min. output. Pri. 1k2; Sec. 5Ω 200mW	55p
Sub-min mains 6.0-6V 100mA	£1.05
12-0-12V 50mA	£1.03
(Size both approx. 30 x 27 x 25mm)	
0-6V 500mA, 0-6V 500mA	£1.88
0-12V 250mA, 0-12V 250mA	£1.88
0-20V 150mA, 0-20V 150mA	£1.88
0-24V 125mA, 0-24V 125mA	£1.88
Mains MT3AT; Sec: 12-15-20-24-30V 2A	£4.33
Mains MT306AT; Sec: 0-15-20V 1A, 0-15-20V 1A	£3.88

● ORGAN CONSTRUCTION

A Full Scale Electronic Organ that you can Build to Your Own Specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS

Leaflet MES 51: Price 15p, describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.
Leaflet MES 52: Price 15p continues the description of the MES 50 series organs and shows you how to add a second keyboard with lots more stops.

● THE AMAZING DMO2

A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4k to 8k (highest) or 2k to 4k or 1k to 2k, etc. right down to 16Hz to 32Hz! And this new comparable design is even smaller—only 3.5in x 3.7in including gold-plated edge connexion.

DMO2T includes built in variable depth and rate frequency shift tremulant.
SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.16.
Keyboards high quality, fully sprung. £15-95
Flat-front 48-note F to E £15-95
SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.16.
Keyboards high quality, fully sprung. £15-95
Flat-front 48-note F to E £15-95
SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.16.
Keyboards high quality, fully sprung. £15-95
Flat-front 48-note F to E £15-95
SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw-tooth. £1.80 each or 6 for £9.94 or 12 for £18.16.
Keyboards high quality, fully sprung. £15-95
Flat-front 48-note F to E £15-95
SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107 0-22	AD161 & 0-22	BC151 0-22	BD133 0-72	BF184 0-28	MJE8440 0-55	2G302 0-21	2N1893 0-41	2N3053 0-19	2N4058 0-13
AC113 0-20	AD162(MP) 0-20	BC152 0-19	BD135 0-44	BF185 0-38	MFF102 0-46	2G303 0-21	2N2147 0-79	2N3054 0-51	2N4059 0-11
AC115 0-26	AF125 0-55	BC153 0-81	BD137 0-59	BF187 0-30	MFF104 0-41	2G304 0-27	2N2148 0-63	2N3055 0-45	2N4060 0-18
AC117K 0-32	AF114 0-27	BC154 0-33	BD138 0-55	BF188 0-44	MFF105 0-30	2G306 0-44	2N2160 0-66	2N3059 0-16	2N4061 0-13
AC122 0-13	AF115 0-27	BC157 0-20	BD138 0-55	BF194 0-13	OC10 0-10	2G308 0-38	2N2192 0-39	2N3084 0-18	2N4062 0-18
AC125 0-19	AF116 0-27	BC158 0-18	BD139 0-61	BF195 0-12	OC20 0-70	2G309 0-48	2N2193 0-39	2N3085 0-16	2N4063 0-13
AC126 0-19	AF117 0-27	BC159 0-13	BD140 0-66	BF196 0-16	OC22 0-52	2G319 0-22	2N2194 0-39	2N3088 0-16	2N4064 0-13
AC127 0-20	AF118 0-27	BC160 0-50	BD165 0-88	BF197 0-16	OC23 0-64	2G339A 0-18	2N2217 0-24	2N3089 0-16	2N4065 0-13
AC128 0-20	AF124 0-33	BC161 0-55	BD175 0-66	BF200 0-50	OC24 0-62	2G344 0-20	2N2218 0-22	2N3089 0-16	2N4066 0-13
AC129 0-16	AF125 0-33	BC162 0-13	BD176 0-66	BF222 0-105	OC26 0-42	2G346 0-18	2N2219 0-22	2N3402 0-23	2N4067 0-13
AC134 0-16	AF126 0-31	BC163 0-13	BD177 0-72	BF257 0-50	OC28 0-32	2G371 0-18	2N2220 0-24	2N3403 0-23	2N4068 0-13
AC137 0-16	AF127 0-31	BC165 0-13	BD178 0-72	BF258 0-66	OC28 0-55	2G371B 0-18	2N2221 0-22	2N3405 0-46	2N4069 0-13
AC141 0-20	AF130 0-33	BC170 0-13	BD179 0-77	BF259 0-94	OC29 0-55	2G373 0-19	2N2222 0-22	2N3405 0-46	2N4071 0-13
AC141K 0-32	AF178 0-55	BC171 0-18	BD180 0-77	BF262 0-61	OC35 0-46	2G374 0-19	2N2268 0-19	2N3414 0-17	2N4072 0-13
AC142 0-20	AF179 0-55	BC172 0-18	BD185 0-72	BF263 0-61	OC36 0-55	2G377 0-18	2N2369 0-16	2N3416 0-17	2N4073 0-13
AC142K 0-28	AF180 0-55	BC173 0-18	BD185 0-72	BF270 0-39	OC41 0-22	2G378 0-18	2N2369A 0-16	2N3416 0-17	2N4074 0-13
AC151 0-17	AF181 0-55	BC174 0-16	BD187 0-77	BF271 0-39	OC42 0-22	2G381 0-18	2N2411 0-27	2N3417 0-21	2N4075 0-13
AC154 0-22	AF186 0-55	BC175 0-24	BD188 0-77	BF272 0-83	OC44 0-17	2G382 0-18	2N2412 0-27	2N3425 0-22	2N4076 0-13
AC155 0-22	AF239 0-41	BC177 0-21	BD189 0-83	BF273 0-89	OC45 0-14	2G401 0-33	2N2546 0-52	2N3425 0-22	2N4077 0-13
AC166 0-22	AL102 0-72	BC178 0-21	BD190 0-83	BF274 0-89	OC70 0-11	2G414 0-33	2N2711 0-23	2N3415 0-22	2N4078 0-13
AC157 0-27	AL103 0-72	BC179 0-21	BD195 0-84	BF275 0-89	OC71 0-11	2G417 0-23	2N2712 0-23	2N3416 0-17	2N4079 0-13
AC158 0-22	AS236 0-55	BC180 0-27	BD196 0-84	BF280 0-30	OC74 0-16	2N388 0-89	2N2714 0-23	2N3416 0-17	2N4080 0-13
AC166 0-22	AS237 0-33	BC181 0-27	BD196 0-84	BF284 0-24	OC74 0-16	2N388A 0-81	2N2714 0-23	2N3416 0-17	2N4081 0-13
AC187 0-22	AS238 0-28	BC182 0-16	BD198 0-99	BF285 0-33	OC76 0-17	2N390 0-22	2N2904 0-19	2N3702 0-18	2N4082 0-13
AC168 0-27	AS239 0-28	BC182L 0-16	BD199 0-105	BF286 0-24	OC76 0-17	2N404A 0-81	2N2905 0-23	2N3703 0-18	2N4083 0-13
AC169 0-16	AS240 0-28	BC183 0-16	BD200 0-105	BF287 0-27	OC77 0-28	2N404A 0-81	2N2906 0-23	2N3703 0-18	2N4084 0-13
AC176 0-22	AS251 0-28	BC183L 0-16	BD200 0-88	BF288 0-24	OC81 0-17	2N404A 0-81	2N2906 0-23	2N3706 0-18	2N4085 0-13
AC177 0-27	AS252 0-33	BC184 0-22	BD206 0-88	BF290 0-22	OC81D 0-17	2N404A 0-81	2N2906A 0-23	2N3707 0-18	2N4086 0-13
AC178 0-31	AS254 0-28	BC184L 0-22	BD207 0-105	BF291 0-22	OC82 0-17	2N404A 0-81	2N2907 0-23	2N3708 0-18	2N4087 0-13
AC179 0-31	AS255 0-28	BC185 0-21	BD207 0-105	BF292 0-22	OC82 0-17	2N404A 0-81	2N2907 0-23	2N3708 0-18	2N4088 0-13
AC180 0-22	AS256 0-28	BC187 0-31	BDY20 0-110	BF293 0-19	OC83 0-22	2N404A 0-81	2N2908 0-23	2N3709 0-18	2N4089 0-13
AC180K 0-32	AS257 0-28	BC207 0-12	BF115 0-27	BSX19 0-17	OC83 0-22	2N404A 0-81	2N2909 0-23	2N3710 0-18	2N4090 0-13
AC181 0-32	AS258 0-28	BC208 0-13	BF117 0-50	BSX20 0-17	OC83 0-22	2N404A 0-81	2N2910 0-23	2N3711 0-18	2N4091 0-13
AC181K 0-32	AS259 0-28	BC209 0-13	BF118 0-50	BSX21 0-17	OC83 0-22	2N404A 0-81	2N2911 0-23	2N3711 0-18	2N4092 0-13
AC187 0-24	AS271 0-44	BC212L 0-14	BF119 0-77	BSY26 0-17	OC83 0-22	2N404A 0-81	2N2912 0-23	2N3711 0-18	2N4093 0-13
AC187K 0-25	BC107 0-9	BC213L 0-14	BF119 0-77	BSY26 0-17	OC83 0-22	2N404A 0-81	2N2913 0-23	2N3711 0-18	2N4094 0-13
AC188 0-24	BC108 0-9	BC214L 0-14	BF121 0-50	BSY27 0-17	OC83 0-22	2N404A 0-81	2N2914 0-23	2N3711 0-18	2N4095 0-13
AC188K 0-25	BC109 0-9	BC225 0-28	BF125 0-50	BSY29 0-17	OC83 0-22	2N404A 0-81	2N2915 0-23	2N3711 0-18	2N4096 0-13
AC17 0-28	BC113 0-11	BC226 0-29	BF127 0-55	BSY38 0-20	OC83 0-22	2N404A 0-81	2N2916 0-23	2N3711 0-18	2N4097 0-13
AC18 0-28	BC114 0-11	BC227 0-29	BF129 0-61	BSY39 0-20	OC83 0-22	2N404A 0-81	2N2917 0-23	2N3711 0-18	2N4098 0-13
AC19 0-28	BC115 0-17	BC228 0-29	BF131 0-61	BSY40 0-20	OC83 0-22	2N404A 0-81	2N2918 0-23	2N3711 0-18	2N4099 0-13
AC20 0-22	BC116 0-17	BC229 0-27	BF132 0-61	BSY41 0-20	OC83 0-22	2N404A 0-81	2N2919 0-23	2N3711 0-18	2N4100 0-13
AC21 0-22	BC117 0-20	BC230 0-27	BF133 0-61	BSY42 0-20	OC83 0-22	2N404A 0-81	2N2920 0-23	2N3711 0-18	2N4101 0-13
AC22 0-18	BC118 0-21	BC231 0-27	BF134 0-61	BSY43 0-20	OC83 0-22	2N404A 0-81	2N2921 0-23	2N3711 0-18	2N4102 0-13
AC23 0-20	BC119 0-22	BC232 0-27	BF135 0-61	BSY44 0-20	OC83 0-22	2N404A 0-81	2N2922 0-23	2N3711 0-18	2N4103 0-13
AC24 0-21	BC120 0-22	BC233 0-27	BF136 0-61	BSY45 0-20	OC83 0-22	2N404A 0-81	2N2923 0-23	2N3711 0-18	2N4104 0-13
AC25 0-21	BC121 0-22	BC234 0-27	BF137 0-61	BSY46 0-20	OC83 0-22	2N404A 0-81	2N2924 0-23	2N3711 0-18	2N4105 0-13
AC26 0-21	BC122 0-22	BC235 0-27	BF138 0-61	BSY47 0-20	OC83 0-22	2N404A 0-81	2N2925 0-23	2N3711 0-18	2N4106 0-13
AC27 0-21	BC123 0-22	BC236 0-27	BF139 0-61	BSY48 0-20	OC83 0-22	2N404A 0-81	2N2926 0-23	2N3711 0-18	2N4107 0-13
AC28 0-21	BC124 0-22	BC237 0-27	BF140 0-61	BSY49 0-20	OC83 0-22	2N404A 0-81	2N2927 0-23	2N3711 0-18	2N4108 0-13
AC29 0-21	BC125 0-22	BC238 0-27	BF141 0-61	BSY50 0-20	OC83 0-22	2N404A 0-81	2N2928 0-23	2N3711 0-18	2N4109 0-13
AC30 0-21	BC126 0-22	BC239 0-27	BF142 0-61	BSY51 0-20	OC83 0-22	2N404A 0-81	2N2929 0-23	2N3711 0-18	2N4110 0-13
AC31 0-21	BC127 0-22	BC240 0-27	BF143 0-61	BSY52 0-20	OC83 0-22	2N404A 0-81	2N2930 0-23	2N3711 0-18	2N4111 0-13
AC32 0-21	BC128 0-22	BC241 0-27	BF144 0-61	BSY53 0-20	OC83 0-22	2N404A 0-81	2N2931 0-23	2N3711 0-18	2N4112 0-13
AC33 0-21	BC129 0-22	BC242 0-27	BF145 0-61	BSY54 0-20	OC83 0-22	2N404A 0-81	2N2932 0-23	2N3711 0-18	2N4113 0-13
AC34 0-21	BC130 0-22	BC243 0-27	BF146 0-61	BSY55 0-20	OC83 0-22	2N404A 0-81	2N2933 0-23	2N3711 0-18	2N4114 0-13
AC35 0-21	BC131 0-22	BC244 0-27	BF147 0-61	BSY56 0-20	OC83 0-22	2N404A 0-81	2N2934 0-23	2N3711 0-18	2N4115 0-13
AC36 0-21	BC132 0-22	BC245 0-27	BF148 0-61	BSY57 0-20	OC83 0-22	2N404A 0-81	2N2935 0-23	2N3711 0-18	2N4116 0-13
AC37 0-21	BC133 0-22	BC246 0-27	BF149 0-61	BSY58 0-20	OC83 0-22	2N404A 0-81	2N2936 0-23	2N3711 0-18	2N4117 0-13
AC38 0-21	BC134 0-22	BC247 0-27	BF150 0-61	BSY59 0-20	OC83 0-22	2N404A 0-81	2N2937 0-23	2N3711 0-18	2N4118 0-13
AC39 0-21	BC135 0-22	BC248 0-27	BF151 0-61	BSY60 0-20	OC83 0-22	2N404A 0-81	2N2938 0-23	2N3711 0-18	2N4119 0-13
AC40 0-21	BC136 0-22	BC249 0-27	BF152 0-61	BSY61 0-20	OC83 0-22	2N404A 0-81	2N2939 0-23	2N3711 0-18	2N4120 0-13
AC41 0-21	BC137 0-22	BC250 0-27	BF153 0-61	BSY62 0-20	OC83 0-22	2N404A 0-81	2N2940 0-23	2N3711 0-18	2N4121 0-13
AC42 0-21	BC138 0-22	BC251 0-27	BF154 0-61	BSY63 0-20	OC83 0-22	2N404A 0-81	2N2941 0-23	2N3711 0-18	2N4122 0-13
AC43 0-21	BC139 0-22	BC252 0-27	BF155 0-61	BSY64 0-20	OC83 0-22	2N404A 0-81	2N2942 0-23	2N3711 0-18	2N4123 0-13
AC44 0-21	BC140 0-22	BC253 0-27	BF156 0-61	BSY65 0-20	OC83 0-22	2N404A 0-81	2N2943 0-23	2N3711 0-18	2N4124 0-13
AC45 0-21	BC141 0-22	BC254 0-27	BF157 0-61	BSY66 0-20	OC83 0-22	2N404A 0-81	2N2944 0-23	2N3711 0-18	2N4125 0-13
AC46 0-21	BC142 0-22	BC255 0-27	BF158 0-61	BSY67 0-20	OC83 0-22	2N404A 0-81	2N2945 0-23	2N3711 0-18	2N4126 0-13
AC47 0-21	BC143 0-22	BC256 0-27	BF159 0-61	BSY68 0-20	OC83 0-22	2N404A 0-81	2N2946 0-23	2N3711 0-18	2N4127 0-13
AC48 0-21	BC144 0-22	BC257 0-27	BF160 0-61	BSY69 0-20	OC83 0-22	2N404A 0-81	2N2947 0-23	2N3711 0-18	2N4128 0-13
AC49 0-21	BC145 0-22	BC258 0-27	BF161 0-61	BSY70 0-20	OC83 0-22	2N404A 0-81	2N2948 0-23	2N3711 0-18	2N4129 0-13
AC50 0-21	BC146 0-22	BC259 0-27	BF162 0-61	BSY71 0-20	OC83 0-22	2N404A 0-81	2N2949 0-23	2N3711 0-18	2N4130 0-13
AC51 0-21	BC147 0-22	BC260 0-27	BF163 0-61	BSY72 0-20	OC83 0-22	2N404A 0-81	2N2950 0-23	2N3711 0-18	2N4131 0-13
AC52 0-21	BC148 0-22	BC261 0-27	BF164 0-61	BSY73 0-20	OC83 0-22	2N404A 0-81	2N2951 0-23	2N3711 0-18	2N4132 0-13
AC53 0-21	BC149 0-22	BC262 0-27	BF165 0-61	BSY74 0-20	OC83 0-22	2N404A 0-81	2N2952 0-23	2N3711 0-18	2N41

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS Coded and Guaranteed

Pak No.	EQVT
T1 8 2G3713	OC71
T2 8 D1374	OC75
T3 8 D1216	OC81D
T4 8 2G381T	OC81
T5 8 2G382T	OC82
T6 8 2G344B	OC44
T7 8 2G345B	OC45
T8 8 2G378	OC78
T9 8 2G399A	2N1302
T10 8 2G417	AF117

All 54p each pak

ND 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for BSX 21, C 407, 2N 1893 120Veb.

1	25	100+
0.19	0.17	0.16

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX800 6p each. Any Qty.

GP 100 TO3 METAL CASE GERMANIUM

V_{beo}=80V. V_{ceo}=50V. I.C.=10 amps. P_{tot}=30W. h_{fe}=30-170. Replaces the majority of Germanium power transistors in the OC, AD and NKT range.

1	25	100+
0.47	0.44	0.40

GP 800 TO3 METAL CASE SILICON

V_{beo}=100V. V_{ceo}=60V. I.C.=15 amps. P_{tot}=115W. h_{fe}=20. 100fT=1MHz. Suitable replacement for 2N 3065, BDY 11 or BDY 20.

1	25	100+
0.55	0.53	0.51

NEW 9th EDITION

Over 300 pages TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. £2.30 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE IN STOCK. SEND FOR FREE LIST.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N706/8, 2N738/9/5A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. TO 2N2906, BCY70. When ordering please state preference NPN or PNP.

20	For	0.54
50 <td>For</td> <td>1.08</td>	For	1.08
100 <td>For</td> <td>1.92</td>	For	1.92
500 <td>For</td> <td>8.25</td>	For	8.25
1000 <td>For</td> <td>14.30</td>	For	14.30

SIL. G.P. DIODES

300mW 30 0.55
40PIV(Min.) 100 1.65
Sub-Min. 500 5.50
Fully Tested 1,000 9.90
Ideal for Organ Builders.

ADI61/162

M/P COMP. GERM. TRANS. OUR LOWEST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS

PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-33V. 400mW (DO-7 Case) 8p ea. 1W (TO-9 Case) 18p ea. 10W (SO-10 Stud) 32p ea.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0.54
Q2	16 White spot R.F. transistors PNP	0.54
Q3	4 OC 77 type transistors	0.54
Q4	6 Matched transistors OC44/45/61/61D	0.54
Q5	4 OC 75 transistors	0.54
Q6	5 OC 72 transistors	0.54
Q7	4 AC 128 transistors PNP high gain	0.54
Q8	4 AC 126 transistors PNP	0.54
Q9	7 OC 81 type transistors	0.54
Q10	7 LC 71 type transistors	0.54
Q11	3 AC 127/128 Complementary pairs	0.54
Q12	3 AF 116 type transistors	0.54
Q13	3 AF 117 type transistors	0.54
Q14	3 OC 171 H.F. type transistors	0.54
Q15	7 2N2926 Sil. Epoxy transistors	0.54
Q16	5 NPN 2xST141 & 3xST140	0.54
Q18	4 MADT's 2xMAT 100 & 2xMAT 120	0.54
Q19	3 MADT's 2xMAT 101 & 1xMAT 121	0.54
Q20	4 OC 44 Germanium transistors A.F.	0.54
Q21	4 AC 127 NPN Germanium transistors	0.54
Q22	20 NKT transistors A.F. R.F. coded	0.54
Q23	10 OA 202 Silicon diodes sub-min	0.54
Q24	8 OA 81 diodes	0.54
Q26	15 IN914 Silicon diodes 75 PIV 75mA	0.54
Q28	8 OA95 Germanium diodes sub-min	0.54
Q28	10 PIV Silicon rectifiers 180V/80	0.54
Q29	2 Silicon power rectifiers BYZ 13	0.54
Q29	4 Silicon transistors 2x 2N696, 1x 2N697, 1x 2N698	0.54
Q30	7 Silicon switch transistors 2N708 NPN	0.54
Q31	6 Silicon switch transistors 2N708 NPN	0.54
Q32	3 PNP Silicon transistors 2x 2N1191, 1x 2N1192	0.54
Q33	3 Silicon NPN transistors 2N1711	0.54
Q34	7 Silicon NPN transistors 2N2369, 500MHz (code P397)	0.54
Q35	3 Silicon PNP TO-5 2x 2N2904 & 1x 2N2905	0.54
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0.54
Q37	3 2N3063 NPN Silicon transistors	0.54
Q38	7 NPN transistors 3x 2N3703, 2x 2N3702	0.54

555 I.C. 65p each

All prices include V.A.T.

MAMMOTH I.C. PAK

APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS MANY CODED also SOME UNKNOWN TYPES - YOU TO IDENTIFY
PAK NO. M.I.C. 200
PRICE £1.25 per PAK including p & p & V.A.T.

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
UTC00=	12x 7400	0.54
UTC01=	12x 7401	0.54
UTC02=	12x 7402	0.54
UTC03=	12x 7403	0.54
UTC04=	12x 7404	0.54
UTC05=	12x 7405	0.54
UTC06=	8x 7407	0.54
UTC07=	8x 7407	0.54
UTC10=	12x 7410	0.54
UTC20=	12x 7420	0.54
UTC30=	12x 7430	0.54
UTC40=	12x 7440	0.54
UTC41=	8x 7441	0.54
UTC42=	8x 7442	0.54
UTC43=	8x 7443	0.54
UTC44=	8x 7444	0.54
UTC45=	8x 7445	0.54

Pak No.	Contents	Price
UTC46=	5x 7446	0.54
UTC48=	5x 7448	0.54
UTC50=	12x 7450	0.54
UTC51=	12x 7451	0.54
UTC53=	12x 7453	0.54
UTC54=	12x 7454	0.54
UTC60=	12x 7460	0.54
UTC70=	8x 7470	0.54
UTC72=	8x 7473	0.54
UTC73=	8x 7473	0.54
UTC74=	8x 7474	0.54
UTC76=	8x 7476	0.54
UTC80=	8x 7480	0.54
UTC81=	5x 7481	0.54
UTC82=	5x 7482	0.54
UTC83=	5x 7483	0.54
UTC86=	5x 7486	0.54

1975 CATALOGUE NOW READY 10p

NEW LOW PRICED TESTED S.C.R.'s

Pak No.	Contents	Price
UTC90=	5x 7490	0.54
UTC91=	5x 7491	0.54
UTC92=	5x 7492	0.54
UTC93=	5x 7493	0.54
UTC94=	5x 7494	0.54
UTC95=	6x 7495	0.54
UTC96=	5x 7496	0.54
UTC100=	5x 74100	0.54
UTC121=	5x 74121	0.54
UTC141=	5x 74141	0.54
UTC151=	5x 74151	0.54
UTC154=	5x 74154	0.54
UTC183=	5x 74183	0.54
UTC199=	5x 74199	0.54
UTCIX1=	25 Assorted	74's £1.65

2N3055

116 WATT SIL. POWER NPN 45p EACH

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.54
U 2	60 Mixed Germanium Transistors AF/RF	0.54
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.54
U 4	40 Germanium Transistors like OC81, AC128	0.54
U 5	60 200mA Sub-Min. Silicon Diodes	0.54
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0.54
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 0.54	
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.54
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.54
U10	20 BAY56 charge storage Diodes DO-7 Glass	0.54
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.54
U13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0.54
U14	150 Mixed Silicon and Germanium Diodes	0.54
U15	25 NPN Sil. Planar Trans. TO-5 like BFY751, 2N697	0.54
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.54
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.54
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.54
U19	25 Silicon NPN Transistors like BC108	0.54
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.54
U21	30 AF Germanium Alloy Transistors 20300 Series & OC71	0.54
U23	30 MADT's like MHz Series PNP Transistors	0.54
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.54
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0.54
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.54
U29	10 I Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1.08
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.54
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.54
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0.54
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.54
U36	25 Silicon Planar NPN Transistors TO-18 2N2906	0.54
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 2S322	0.54
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.54
U39	30 R.F. Germ. PNP Transistors 2N1303/5 TO-5	0.54
U40	10 Dual Transistors 6 lead TO-5 2N2080	0.54
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.54
U44	20 Sil. Trans. Plastic TO-5 BC115/116	0.54
U45	7 SA SCR, TO66 up to 600PIV	1.08
U46	20 Unijunction transistors similar to T1848	0.54
U47	10 TO220AB plastic triacs 50V 5A	£1.08
U48	9 NPN Sil. power transistors like 2N3055	£1.08
U49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	£1.08

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

FREE

One 55p Pak of your own choice free with orders valued £4 or over

CADIUM CELLS

ORP12 48p

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A		
50	0.05	0.06	IN4001	0.05	0.08	0.15	0.21	0.80	
100	0.05	0.07	IN4002	0.06	0.10	0.17	0.23	0.70	
200	0.06	0.10	IN4003	0.07	0.12	0.22	0.25	1.00	
400	0.08	0.15	IN4004	0.08	0.15	0.30	0.35	1.35	
600	0.09	0.17	IN4005	0.10	0.18	0.36	0.45	1.95	
800	0.12	0.19	IN4006	0.11	0.20	0.38	0.55	2.80	
1000	0.14	0.19	IN4007	0.12	0.25	0.48	0.65	2.50	
1200	-	-	-	-	-	0.80	0.58	0.75	3.00

DIACS

FOR USE WITH TRIACS BR100 (D3C) 25p each

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each

TRIACS

VBOM	2A	6A	10A
TO-5	TO-6	TO-4	TO-8
	p	p	p
100	38	55	83
200	55	66	99
400	77	83	1.21

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 20p Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

2 Amp. BRIDGE RECTS.

50 v RMS	35p each
100 v RMS	40p
200 v RMS	45p
400 v RMS	50p
1,000 v RMS	55p

Size 16 mm x 16 mm.

D1699 NPN SILICON DUAL TRANSISTOR

(Similar to 2N2060)

1	25	100+
0.28	0.26	0.23

LINEAR INTEGRATED CIRCUIT PAKS MANUFACTURERS FALL-OUTS

ULIC709	10 x 709	0.54
ULIC710	7 x 710	0.54
ULIC741	7 x 741	0.54
ULIC747	5 x 747	0.54
ULIC748	7 x 748	0.54



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible. Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).


So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

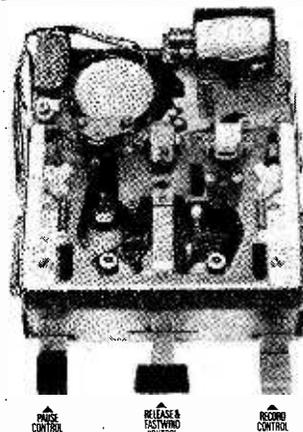Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.



GARRARD CT4'S MK III STEREO CASSETTE PLAYER & RECORDER

has full facilities for record, play-back, pause, erase, rest, fast forward and reverse wind, automatic tape end stop and cassette release.

Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo, cassette players, HI-FI stereo cassette recorders, industrial and many other applications.

Send cheque or Postal Orders for **£19.98** (£18.50 + 8% VAT) (includes post and packing) to:

BOTHWELL ELECTRIC SUPPLIES.
(Glasgow) LIMITED
431 Sauchiehall Street
GLASGOW G2 3LG Tel: 041-332 6184
Scotland's Leading Electronics Centre

ALLARD ELECTRONICS

New Branded Components—Full Specification—Guaranteed

Transistors	LC's	Price ea.	SPECIAL OFFER	
Price ea.	709C (DIL or TO)	0.87	This month only	
AC125/6/7/8	728C (DIL or TO)	0.60	NE555	
AD140/149	741C TO	0.48	Price each 0.49	
AD161/162	741C DIL	0.35	POTENTIOMETERS—CARBON TRACK	
AF114/6/7	748C TO	0.44	Lin. or Log. 1" Bush—Spindle 2" F.M.P.	
AF118	LM309K	2.00	5K to 2 Meg Single 0.16 ea.	
BC107/8/9	TLA500	0.95	5K to 2 Meg Dual with D/P sw. 0.22 ea.	
BC147/8/9	2N414	1.05	10K to 2 Meg Dual with D/P sw. 0.42 ea.	
BC157/169	S.O.R.'s		Log. only 0.62 ea.	
BC168	CRS1/05	0.80	T.T.L.'s	
BC132/8/4	CRS1/10	0.58	Price ea.	
BC222/8/4	CRS1/20	0.60	7400/1/2/3 0.14	
BC070/1/2	CRS1/40	0.45	7404/5 0.12	
BD181/182	CRS3/40	0.55	7406/7 0.38	
BF194/5/6	ZENERS		7408 0.15	
BFY50/1/2	BZY88 all voltages	0.09	7416/7 0.34	
MJE370	BZX61 series 1.3v	0.17	7428/8 0.37	
MJE371	ALI-BOXES		7432/3 0.36	
2N2218	2 1/2 x 5 1/2 x 1 1/2" 0.44		7435 0.27	
2N2906	4 x 4 x 1 1/2" 0.44		7437/2AN 0.45	
2N2926 all 0-09	4 x 2 1/2 x 1 1/2" 0.44		7470/72 0.27	
2N3053	4 x 2 1/2 x 2" 0.44		7473/74 0.38	
2N3054	4 x 4 x 2" 0.60		7475 0.44	
2N3055	4 x 4 x 3" 0.60		7476 0.47	
2N3702/3/4	7 x 5 x 2 1/2" 0.70		7482 0.75	
2N3706/6	VEROBOARD		7483 0.38	
2N3707/8/9	1 Matrix	Price ea.	7484 0.00	
2N3819	2 1/2 x 2 1/2" 0.30		7485 0.37	
TIP29a	2 1/2 x 2 1/2" 0.34		7486 0.20	
TIP30a	2 1/2 x 3" 0.53		7487 0.20	
TIP31a	2 1/2 x 1 1/2" 0.35		7488 0.20	
TIP32a	2 1/2 x 1 1/2" 1.25		7489 1.85	
TIP41a	Pins 25 per pack	0.15	7490 0.90	
TIP42a			7491 0.90	
			DIL SOCKETS	
			DIL 8 pin 0.14	
			16 pin 0.15	
			14 pin 0.18	
			16 pin 0.18	
			DIODES	
			1N914/ 0.15	
			1N4148 0.05	
			1N4001/8 0.08	
			SPEAKERS	
			7" x 4" FANE 0.85 each	
			8-8-15 ohm	
			0.85 each	
			Send for FREE CATALOGUE.	
			Listing over 2,000 Items.	
			S.A.E. please. Quantity Discounts	
BRIDGE RECTIFIERS			DEPT. W.6, 299/301 BALLARDS LANE,	
P.V.	1A	2A	4A	LONDON N12 8NP
50V	0.30	0.30	0.45	MAIL ORDER ONLY. Cash with order.
100V	0.30	0.35	0.48	Orders under £8 plus 15p. P. & F. Add VAT to total
200V	0.25	0.40	0.54	
400V	—	0.43	0.60	
600V	0.25	0.45	0.70	

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CPW 06
READING RG7 4FP

CPW06

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.


Name

Address

POST CODE

BIET

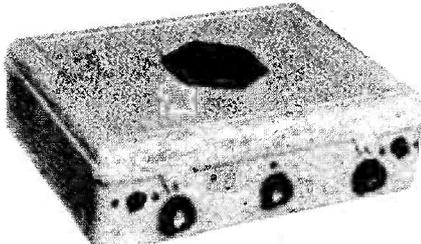HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 8 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator.
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

Total Building Costs
£7-23 P P & Ins. 55p
 (Overseas Seamail P & P £3-40)
 (+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 55p free with parts.

ROAMER TEN Mk 2


WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket.

10 Transistors. Latest 4-2 watt Ferrite Magnet Loudspeaker.

9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

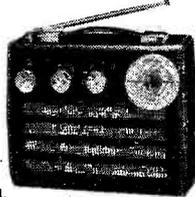

Total building costs **£9-50** P P & Ins. 65p
 (Overseas Seamail P & P £3-50)
 (+ 8% VAT 76p)

POCKET FIVE

NOW WITH 3" LOUD-SPEAKER

3 Tunable wavebands, M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List free with parts.



Total Building Costs **£2-95** P P & Ins. 38p
 (+ 8% VAT 24p)
 (Overseas Seamail P & P £2-30)

ROAMER EIGHT Mk 1

NOW WITH VARIABLE TONE CONTROL


7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car Aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4 in. approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.



Total building costs **£6-98** P P & Ins. 65p
 (Overseas Seamail P & P £3-50)
 (+ 8% VAT 56p)


NEW JIFFY TESTER

Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Also for checking short circuits of capacitors, tuning capacitors and many other uses not listed here. See instruction sheet free with kit. Complete with earpiece, jack plug and socket, resistors, capacitors, components, etc. Parts Price List and Easy Build Plans free with Parts. **Total Building Costs**

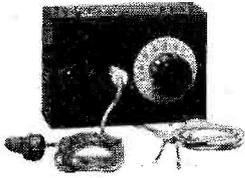

£2-25 (+ 8% VAT 18p)
 P P & Ins. 22p
 (Overseas Seamail P. & P. £1-70)

NEW EVERY-DAY SERIES SIX

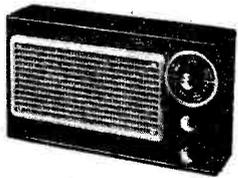


Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

Total Building Costs **£3-98** P P & Ins. 50p
 (Overseas Seamail P & P £2-30)
 (+ 8% VAT 32p)

TRANS EIGHT


8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 5in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

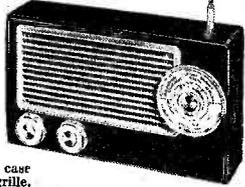

Total building costs **£4-48** P P & Ins. 50p
 (+ 8% VAT 36p)
 (Overseas Seamail P & P £2-50)

"EDU-KIT"

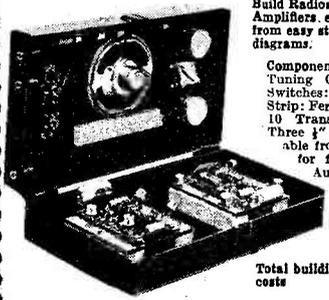

Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

Total building costs **£5-50** P P & Ins. 50p
 (Overseas Seamail P & P £3-40)
 (+ 8% VAT 44p)

Prices are subject to alteration without notice.

★ Callers side entrance "Lavelle's" shop.
 ★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA

Tel. : 0234 52367. Reg. No. 788372.

I enclose £..... for

- ROAMER TEN EV6
- ROAMER EIGHT TRANS EIGHT
- JIFFY TESTER MAJOR EDU-KIT
- POCKET FIVE EDU-KIT

Parts

Name

Address

(Dept. PW6)

FOLLOWING our recent comments on the reception of privileged transmissions and the illegal use and sale of walkie-talkie type radios, we have, as a result, acquired quite a postbag from many of our readers. We apologise for the fact that we may have been unable to answer all your individual comments, but we are publishing a small selection of them in our Letters pages.

Comments have been wide and varied and much controversy has been aroused. Readers may judge for themselves whether or not our comments were justified. One particular point has arisen over the sale of "non UK licensable walkie-talkies" and this also applies to the sale of equipment that is licensable. This is the ease by which transmitting/receiving equipment, portable or otherwise, may be quite openly acquired. Anyone may purchase a transmitter/receiver without any formality whatsoever, simply by passing the cash over the counter, or ordering by post from a multitude of sources.

A considerable amount of radio interference, much of which is deliberate, is being caused to licensed users by other "sources". There is no evidence, so far, to support some views that deliberate interference is being caused by licensed stations.

It is the unlicensed operator and the indiscriminate sales of transmitters/receivers to these persons that must be checked. It is essential that a measure of control be introduced to stop sales to non licence holders.

One suggestion that certainly meets with our approval, is that it should be a legal requirement that intending purchasers should produce the necessary licence before equipment of this nature is sold, and that the sale be recorded and registered. Of course, this will raise the battle-cry, "shades of 1984" but what is the alternative? After all, purchasers of TV receivers, firearms etc have their purchases recorded and the details are passed to the appropriate government licensing dept. It is quite clear that appropriate legislation is long overdue.

LIONEL E. HOWES—Editor

THE NEW TELEVISION

Next month we have a surprise for you! A new, bigger and better *Television* magazine, starting with the July issue. The page size will be larger, and there will also be more pages. We have been experiencing increasing difficulty in getting all we want into each month's issue of the magazine in its present form. Colour servicing, for example, calls for the inclusion of more and more complicated circuitry. This has been tending to squeeze out some of the other features we feel should be included. But with larger and more pages we consider we will be able to provide the service we aim to give.

NEWS...

18th Longleat Mobile Rally

THIS annual event, organised by the City of Bristol Group of the R.S.G.B., will take place at Longleat House, Longleat Park, near Warminster, Wiltshire, on Sunday, June 29th, 1975.

As in previous years the trade stands will be housed in spacious marquees. The rally starts at 10 a.m. and talk-in stations will be operational. 160 metres (G6YB/P) 1920kHz. 80 metres (G3JMY/P) 3755kHz. 2 metres (G3TAD/P) 145.00, 145.50MHz plus VFO.

There will be a walking DF hunt starting at 3 p.m. on 160 metres. Bring your DF equipment or your transistor radio converted to top band and join in the fun. All members of the family can take part in this.

As well as the trade stands there will be the grand raffle, RSGB book stand, bring and buy stand (no rubbish please), all goods to be marked with the price and name and call sign of the person selling the article. Refreshments will be available on site.

There is something for everyone in the grounds. The wild life park, the stately house, the gardens, children's zoo and pet corner with plenty of space to picnic, park the car or just "rag-chew."

Overnight camping as from 6 p.m., Saturday, June 28th, 1975.

Details from **Brian Croker** G3ULJ, 36 Portland Street, Staple Hill, Bristol, BS16 4PT.

AVAILABLE NOW!

REPRINT OF PW's

**TELE-TENNIS
SERIES**

July-November 74

Send 75p + 7p (post & packing) to:
Chief Cashier (PW Tele-Tennis),
IPC Magazines,
Tower House, Southampton St.,
London, WC2E 9QX

Plessey distributor

PLESSEY Semiconductors have recently appointed Semiconductor Specialists as distributors for the Plessey range of IC's in the UK and North America.

Semiconductor Specialists are situated at *Premier House, Fairfield Road, Yiewsley, West Drayton, Middx.*, and state that they will hold stocks in the UK., so that buyers can obtain their supplies of both Plessey and U.S. components from a single source.

Although large stocks of UK franchised products are held at the West Drayton depot, the firm further states that U.S. franchised products in stock at the company's Chicago warehouse are shipped to the UK every weekend and can be delivered in four working days.

New book

THE new book is written by Robert Brown and Mark Olsen entitled 'Experimenting with Electronic Music'. It's contents cover exactly what the title suggests and includes details on the construction of tone generators, a small electronic organ and a series of electronic modifiers such as tremolo, reverberation, and a chime device. Price is £1.50.

Other useful publications to help the novice understand the various aspects of electronics, comprise: 'Basic Maths Course' by Henry Jacobowitz, 'The oscilloscope' by George Zwick, and '199 TV Tough Dog Problems Solved' by Art Margolis. Price for these books is £1.40, £1.75 and £1.75 respectively and are all available from the publishers Foulsham-Tab Ltd., Yeovil Road, Slough, SL1 4JH.

Pyser look-out for antiques

PYSER LIMITED, sole UK distributors of Marantz high fidelity equipment, are in the market for "antiques". The company wishes to purchase certain "classic" high fidelity units in first-class condition, and at present the list (with prices offered) is: Marantz 7C, £100; McIntosh MC-275, £100; McIntosh

BREMA news

NEWs now from BREMA (British Radio Equipment Manufacturers Association) which must surely emphasise the economic climate that envelopes us all. They state that deliveries of colour TV's, whether UK-made or imported, dropped in Dec. '74 by 23% over the same period in '73. This brought the total for the year to 2.2 million, a fall of 20% compared with 1973. This may all sound pretty bad, but for the monochrome TV its even worse! A total fall of 42% for the year's deliveries, resulting in a mere 810,000 sets being delivered.

This dramatic fall, however, is not limited to TV's; audio systems fell by 17% and radio receivers by 28%. It must be seen that if this trend continues, many people in the TV/radio industries will be redundant. This not only hits these people hard but, indirectly, thousands of others.

The MC 14435

THE MC 14435 $3\frac{1}{2}$ digit DVM i.c. is the latest addition to the rapidly growing Semicomps Ltd. CMOS family and contains the logic for use in a dual slope integration A/D converter system. The device consists of $3\frac{1}{2}$ digits of BCD counters, 13 memory latches and multiplexed BCD outputs. An internal clock oscillator is provided which needs only a single external capacitor.

In order to complete the system use is made of the MC 1505L dual-ramp generator and comparator. Only one external capacitor and two calibration potentiometers are required. Further gen from Semicomps Ltd., Northfield Industrial Estate, Beresford Avenue, Wembley, Middx. HA0 1SD.

C-22, £90; JBL SA660, £90; JBL SA600, £50.

In addition, Pysers would like to hear from audiophiles who would like to sell other "classic" Marantz units in good condition. contact *Malcolm Blockley, Electronics Division, Pyser Limited, Fircroft Way, Edenbridge, Kent.*

Books received**Use of Microphones**

By Alec Nisbett

Shows one how to choose microphones to suit various jobs, how to position them, move them, balance and control them etc.

Price: £1.75

Focal Press Limited, 31 Fitzroy Square, London W1P 6BH

Dictionary of Data Processing

By Jeff Maynard

A dictionary for those wishing to keep abreast of current data processing terminology. More than 4,000 terms are defined.

Price: £3.90

Newnes Butterworths Limited, 88 Kingsway, London WC2B 6AB

Television

By Heinz Kurth

The author takes the whole concept of television to pieces and shows how a TV camera takes pictures, how the image is broadcast, how the receiver works, how colour TV works, what goes on in the studio etc.

Price: 95p

World's Work Limited, The Press, Kingswood, Tadworth, Surrey

Colour Television Servicing (2nd edition)

By Gordon J. King

Deals with the servicing of PAL receivers in a down-to-earth manner and with a minimum of mathematics. It is divided into three sections the first looking at colour TV systems as a whole, the second studies the elements involved such as picture tubes, conversion systems, chroma channels etc. The third section is devoted exclusively to matters of servicing.

Newnes Butterworths Limited, Borough Green, Sevenoaks, Kent TN15 8PH

Principles and Calculations for Radio Mechanics (Part 2)


By R. A. Bravery & A. P. Gilbert

The second of two volumes designed to meet the needs of students studying principles and calculations as part of the City & Guilds Radio Mechanics' Course 22.

Price: £1.90

Newnes Butterworths, 88 Kingsway, London, WC2B 6AB

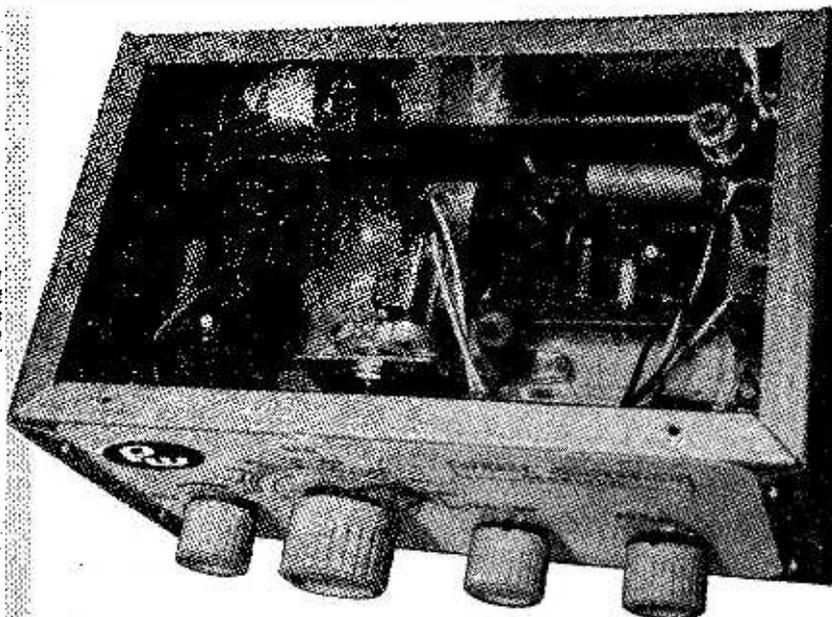Inside the receiver with the oscillator/mixer board to the right with input coils at extreme right. Oscillator coils L3/4 are positioned near the main tuning capacitor. The audio amplifier board is on the left.



CW signals can be found in the direct conversion receiver. This omits the frequency changer, intermediate frequency amplifier, product detector and carrier or heterodyne oscillator of the communications superhet. Instead, conversion of the incoming signal to an audio signal takes place directly.

★ components list

Resistors

R1 47k Ω	R5 1.8k Ω	R9 15k Ω
R2 27k Ω	R6 1.8M Ω	R10 100 Ω
R3 4.7k Ω	R7 100k Ω	R11 1.8k Ω
R4 220 Ω	R8 56k Ω	R12 100 Ω

All 5% $\frac{1}{4}$ or $\frac{1}{2}$ W

VR1 10k Ω log-pot with switch S2

Capacitors

C1 50pF SM	C9 4.7nF
C2 100pF SM	C10 4 μ F 6V
C3 20 μ F 6V	C11 4.7nF
C4 0.047 μ F	C12 800pF SM 5%
C5 0.01 μ F	C13 800 pF SM 5%
C6 220 μ F 12V	C14 680pF SM
C7 0.25 μ F	C15 5pF SM
C8 100 μ F 12V	C16 0.5 μ F
TC1 30pF pre-set	VC1 25pF variable (Jackson C804)

VC2 100pF variable (Jackson C804)

Semiconductors

Tr1 40673	Tr3 BC107
Tr2 BC108	Tr4 BC109

Miscellaneous

Coilformers 10mm ($\frac{3}{8}$ in.) diameter, with cores (4). Ferrite beads FX115 (2). Ball slow motion drive (Jackson 4511/DRF). Knobs (4). S1 2-pole 2-way wafer switch. Jack socket, insulated. Case, flanged members 203 x 101mm (8 x 4in.) (2), 127 x 101mm (5 x 4in.) (2), 203 x 76 (8 x 3in.) (1), flat plates 203 x 127 (8 x 5in.) (2) (Home Radio). Aerial and earth sockets. Rubber feet

BANDS USED


Of the amateur bands available, the 80 metre band (3.5 to 3.8MHz), will probably be of most interest for general reception of amateur signals, likely to be available at any time, while at weekends and evenings there is usually a great deal of activity. So the receiver is primarily intended for this band. However, Top Band, 160m (1.8 to 2MHz) coverage is also included, as this band carries Slow Morse, local and other transmissions.

Both these bands are influenced by seasonal, daily and other propagation changes, but it is unusual for 80m, in particular, to lack all amateur signals as this band is much used for regular Nets and other contacts.

RECEIVER CIRCUITS


In the circuit in Fig. 1. L1 tunes 160m and L2 tunes 80m, VC1 with C1 in parallel providing suitable coverage. VC1 is panel operated and is peaked for best reception. Aerial coupling is via TC1, which can be set to suit long or short aerials. Pole S1a of the switch selects either L1 or L2 as required. Tr1 is the converter stage signal passing to gate 1 of the 40673 which is internally diode protected, and thus much less liable to damage than an unprotected insulated gate transistor. For the reception of CW, Tr4 acts as a heterodyne oscillator, with injection to gate 2 of Tr1 via C15. When receiving CW, the pitch of the audio tone depends on the difference in frequency between the received signal and oscillator Tr4.

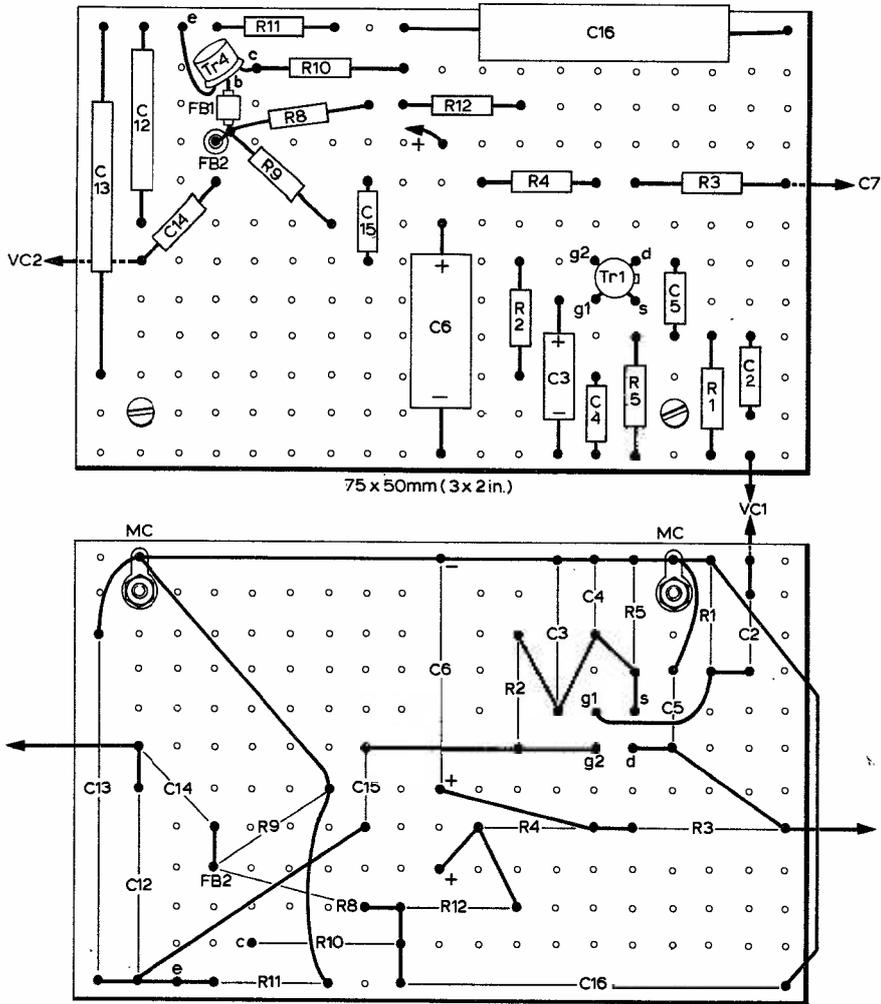During SSB reception, Tr4 performs as the conversion oscillator, resulting in an audio signal appearing at the drain of Tr1. This audio is resolved into intelligible speech when Tr4 is so tuned that it is able to replace the carrier suppressed during transmission. If Tr4 is tuned to the wrong side of the SSB signal, the speech is inverted and unintelligible.



002

Fig.2: above, gives details of the construction of the oscillator/mixer board. Fig.3, below, shows the audio amplifier board. Both boards are 0.15in. matrix.

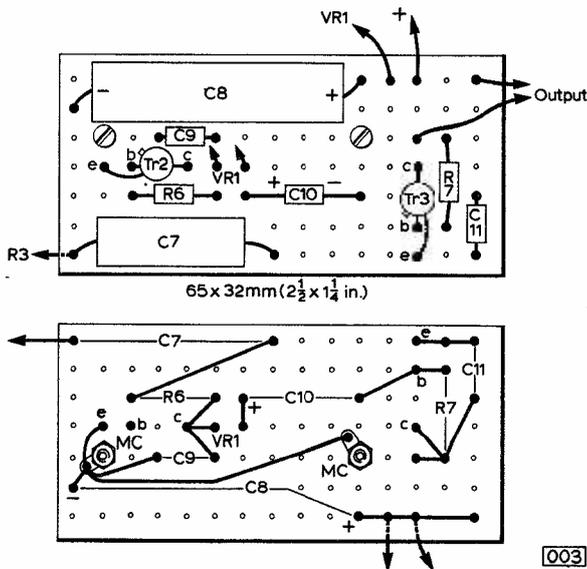

003

The second section of the switch, S1b, selects L3 for 160m, and L4 for 80m with VC2 giving approximately correct coverage. C12 and C13 are 1% or 2% silver mica capacitors and no adjustment is required, except to the coil cores, to bring the oscillator into the band.

Ferrite beads FB1 and FB2 are to avoid VHF parasitics, although this oscillator circuit was found to be very stable and reliable.


Audio signals from Tr1 are taken to a simple two-stage audio amplifier Tr2/3. Capacitors C3 and C4 by-pass the source of Tr1 at audio frequencies. VR1 is the audio volume control the output from the final audio amplifier Tr3 going to a jack socket.

INDUCTORS

The coils are all wound on 10mm ($\frac{3}{8}$ in.) diameter formers with adjustable cores. L1, L2 and L3 are wound with 32SWG enamelled wire, L4 is wound with 24SWG enamelled wire.

L1 has 70 turns, wound in a compact pile. L2 has 40 turns, L3 has 32 turns and L4 has 20 turns, all close wound.

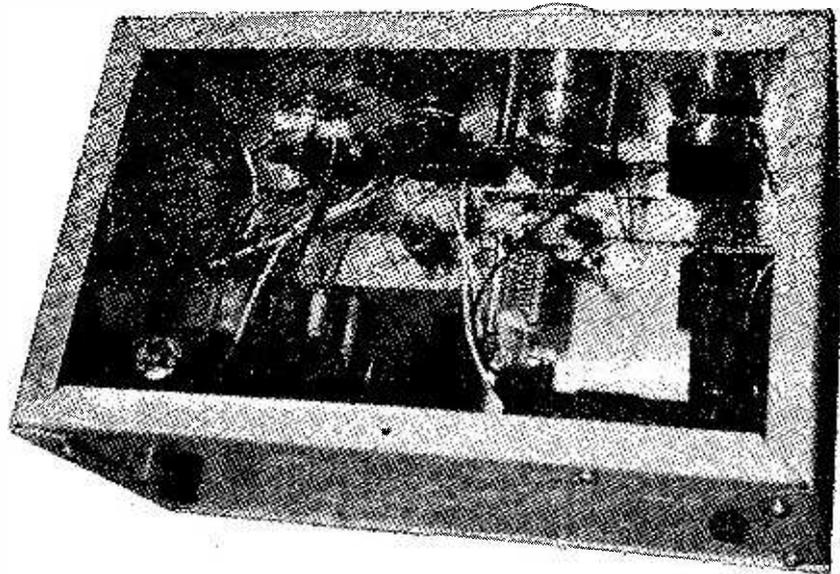View from the rear of the completed receiver. If the potentiometer VR1 has a metal spindle it is important to check that it is isolated from the track, see Fig.1. If not, insulating panel bushes must be used. Leads between the coils and their respective tuning capacitors should be rigid and as short as possible.



Each winding is begun as near to the top of the coil former as possible. The wire can be secured with a little quick-setting adhesive, or with a turn or two of cotton or thread to which a little adhesive has been applied. After winding, the end of the coil is secured in the same way. A few touches of an adhesive, such as Bostick 1, can be applied to keep turns in place, but the whole windings should not be painted, varnished or waxed.

The bottom end of each winding is soldered to a tag. This will be held by one of the fixing bolts in contact with the metal chassis. The top end of each winding is cut to a suitable length to reach S1.

The cores of L3 and L4, in particular, should be fixed against further movement after adjusting them, by wax or thin elastic placed between core and former.

OSCILLATOR MIXER BOARD

The board is approximately 75 x 50mm (3 x 2in) and components are positioned as in Fig. 2. Begin by drilling holes for two 6BA bolts, which secure the tags MC. Later, additional nuts on these bolts will allow the board to be secured to the metal chassis, with a little clearance for underside wiring.

In most places the wire ends of components will be long enough to reach the various connecting points. Elsewhere, 22SWG tinned copper or other connecting wire can be used, with insulated sleeving where necessary.

No special care is necessary when fitting Tr1, except to avoid lengthy heating of the leads, as with any transistor. Other dual-gate FET's may be used in this circuit, but if they are not gate-protected it is

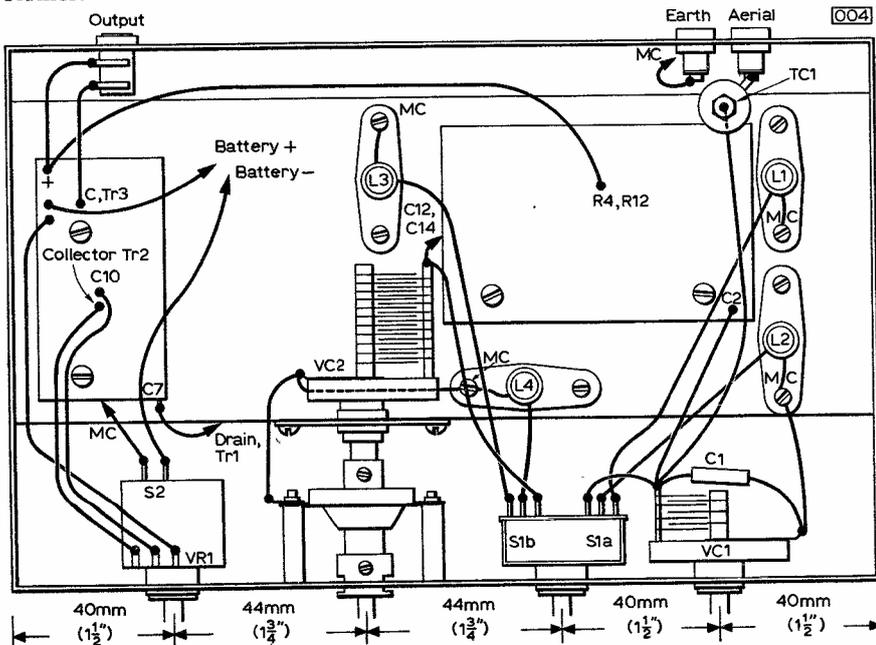


Fig.4: Layout of components on sub-chassis and panel. The aerial and earth sockets are shown displaced for clarity but their actual positions are not important. Both circuit boards are raised off the sub-chassis to avoid short-circuits.

absolutely essential that the shorting wire supplied round the leads is **not removed** until R1, R2 and R5 are connected, at least.

When fitting Tr4, take the collector lead to R10 and the emitter lead to R11, as in Fig. 2. A piece of insulated sleeving slightly longer than the ferrite bead is put on the base lead, and bead FB1 is added. R8 and R9 are then soldered in place, with very short leads at the base. Bead FB2 is then fitted in the same way, and the base lead is taken through the board to C14.

Some flying leads are provided, for connecting later. One runs from C2, to C1, VC1 and S1a. A short projecting wire passes from the junction of C12 and C14, for VC2 and S1b. A connection is also provided from the drain of Tr1, R3 and C5, to go through the chassis to the audio amplifier. A red lead from R4 and R12 is the positive connection. The negative circuit is completed by the bolts MC.

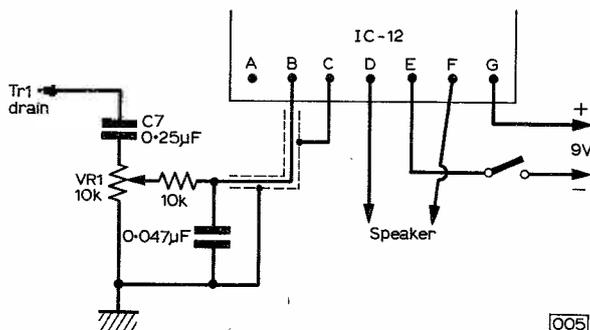


Fig.5: If a separate audio module is available stages Tr2 and Tr3 can be omitted. Connections for the Sinclair IC2 are shown here.

AUDIO AMPLIFIER

The board 65 x 32mm (2½ x 1¼in.) is assembled in a similar way, as in Fig. 3, with bolts MC again providing a connection to the metal chassis. The wire end of C7 can be taken through the board, then bent up to provide a connecting point for the lead from Tr1 drain circuit. A pin is inserted for the positive connecting point. Leads from here run to R4/R12, output jack and battery positive, the latter going through a hole in the board, with a clip soldered to the end of the flex.

Three leads run to VR1. That from C10 positive goes to the centre tag of VR1, while the outer tags go to Tr2 collector and positive line. Switch S2 is connected to the chassis and to a flexible lead with a negative battery connector.

Leads from Tr3 collector and positive run to the output jack. This must be an insulated type, giving complete isolation from the metal.

CONSTRUCTION

The flanged members form a rigid assembly and make a good case for the receiver when top and bottom are closed with flat plates. The general layout of items will be seen from Fig. 4.

The internal 205 x 75mm (8 x 3in.) member is raised about 32mm (1¼in.), and is set back about 40mm (1½in.) to clear the drive, VR1 and other panel controls. It is necessary to place the member forming the panel **inside** the flanges of the sides.

Front, back and sides are secured together with the 4BA bolts provided, using the holes already punched for this purpose. Holes are drilled to take bolts to secure the internal member.

Fit VC1, S1 and VC1 about 40mm (1½in.) from the bottom of the panel. The drive for VC2 is 50mm (2in.) from the bottom edge, so that VC2 clears the chassis. A clearance hole is punched for the drive, which is fixed with spacing sleeves and long bolts. VC2 is attached to a bracket, or to a piece of scrap metal which is bolted to the front flange of the chassis. The drive and VC2 should be lined up correctly, so that tuning is smooth and easy. If needed, large or elongated holes can be provided on the bracket, to allow a little adjustment for this purpose.

If a different drive is employed, it should have a fairly high ratio, or tuning will be rather critical. The cursor is attached by two small screws.

Fix the two circuit boards in the way described, taking care that no short circuits can arise to the metal. Leads can then be taken to the two sections of the bandswitch, etc., as shown in Fig. 4. C1 is soldered directly across VC1. Insulated sockets provide for aerial and earth connections, the earth socket being connected to the metal.

ALIGNMENT

The cores can be provisionally located with each about 4 or 5 turns down from the top of the former, but this will have to be adjusted to secure band coverage.

If no other means of adjustment is available, each band can probably be located fairly readily at a time when there is plenty of amateur activity, such as on a Sunday morning. With the receiver switched to 80m, set the core of L4 so that amateur signals are heard throughout almost the whole swing of VC2. Tuning from the maximum capacitance position for VC2, CW signals should be heard for about the first one-third of rotation, and SSB signals for about the other two-thirds.

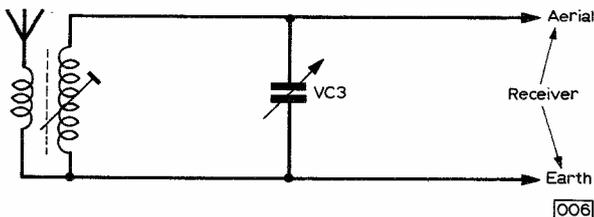


Fig.6: A bandpass input can be formed by adding the above circuit but TC1 must be reduced in value, see text.

Should it be possible to borrow a communications-type receiver, place a temporary wire from its aerial socket to near VC2 and adjust L4 so that the carrier picked up by the receiver can be tuned from about 3.5 to 3.8MHz. In the same way, adjust L3 for about 1.8-2.0MHz. Otherwise adjust L3 to bring amateur activity within the range tuned by VC2.

Subsequently, it is only necessary to adjust L1 on the 160m band, and L2 on the 80m band, so that VC1 can be peaked for best volume, throughout both bands. Here, TC1 will have some influence on tuning. With other than short aerials, TC1 should be unscrewed to quite a low value.

Should a signal generator be available, it can of course provide a means of adjusting the circuits for correct coverage.

continued on page 158



Already we know of 22,000 people who like our ideas.

In October of last year we ran several ads announcing a brand-new service for amateur electronics enthusiasts.

The new service was called Doram.

And it promised the first-ever professional electronics service for amateurs.

We said that if you didn't get your order within seven days we'd refund your money. So you'd have no long wait.

We said that we'd only give you top quality, big-name components.

We said that we'd give you a no-quibble guarantee and replace any component which arrived faulty.

And finally we said that we'd offer you a choice of millions of components on over 4,000 product lines.

Buy the Doram catalogue for 25p, we said, and you'll get a fantastic electronic component mail

order service.

We were as good as our word.

And your letters of thanks flooded in. Thousands tried our service. Hundreds went out of their way to write congratulating us.

'Your storeman must be power assisted,' you said.

'I think you are a good firm and live up to your advertisement well,' you said.

'How nice to find a firm which actually stocks all the items in its catalogue,' you said.

And an awful lot more we'd blush to admit.

The Doram catalogue is still available, price 25p.

To encourage you to try us we'll give a £10 voucher to the first catalogue buyer out of the post bag on 30th June. And a £5 voucher to the next 19 new buyers.

Similarly, on 31st July, we'll give a £10 voucher to the first new

catalogue buyer. And a £5 voucher to the next 19 new buyers.

Use the coupon now while the offer lasts. Only these coupons are eligible, and all unsuccessful coupons from the June draw will also be entered for the July draw.

**£10 VOUCHERS AND
£5 VOUCHERS TO BE WON**

I enclose 25p and look forward to receiving my Doram catalogue.

**Doram Electronics Ltd., PO Box TR8,
Wellington Road Industrial Estate,
Leeds LS12 2UF**

Name _____

Address _____

DORAM PW/6/75

POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5A mains plug.
2 metre output lead with 4-way multiplug giving 2-1 and 2-5 mm sockets and 3-5 mm plugs.
Price £2.30. Post 10p.



2" and 4" PANEL METERS

SIZE: 60mm Wide x 45mm High x 40mm Deep.	I.E. Movement	Ohms	SIZE: 110mm Wide x 82mm High x 45mm Deep.	I.E. Movement	Ohms
0-50 micro A.	1250	0-50 micro A.	1400	0-100 micro A.	580
0-100 micro A.	580	0-100 micro A.	290	0-500 micro A.	170
0-1 mA	170	0-1 mA	260	0-5 mA	170
0-5 mA	170	0-5 mA	200	0-10 mA	6
0-10 mA	6	0-10 mA	6	0-50 mA	0.5
0-50 mA	0.5	0-50 mA	0.5	0-100 mA	0.5
0-100 mA	0.5	0-100 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5	0-2 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5	0-25 Volt	15K
0-25 Volt	15K	0-25 Volt	15K	0-50 Volt	50K
0-50 Volt	50K	0-50 Volt	50K	0-300 Volt	300K
0-300 Volt	300K	0-300 Volt	300K	"g" Meter	170
"g" Meter	170	"g" Meter	200	VU Meter	5250
VU Meter	5250	VU Meter	5250		

VU Meters are complete with detectors. Modern wide view. Price 2" £2.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set.

1/2 watt CARBON FILM RESISTORS
1/2 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 95p per 100.

C1000 MULTIMETER

Special Offer
Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt.
Ranges:
AC Volts 0-15, 50, 250, 1000 V
DC Volts 0-10, 50, 250, 1000 V
DC Current 0-1 mA, 0-100 mA
Resistance 0-150K ohms
Size 90 x 24 x 90 mm
Complete with Batteries, Test Prods.
Instructions. Special price £3.30 Post 25p.



C1001 MULTIMETER

Input Resistance 20,000 ohms per volt
Overload protection
150 μA movement, clear scale
Ranges—AC Volts 0-10, 50, 250, 1000V
DC Volts 0-5, 25, 125, 500, 2500V
DC Current 0-50 mA
Resistance 0-60 Kohms, 0-6 Mohms
Decibels -20 to +22 dB.
Carrying Case, Test Prods and Batteries included.
Size: 11.5 x 8.3 x 2.7 cm.
Price £3.85. Post 20p.

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 3-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA (watts)	Ref. No.	Price Cased	Price Plugs	Price 2 Pin + 1 Earth	Price Open Post
60	149	3.35	0.88	4.37	0.86
100	150	3.15	0.88	4.90	0.84
200	151	11.45	0.88	8.14	0.80
250	152	12.90	0.88	9.80	0.88
350	153	16.50	0.88	11.88	0.95
500	154	17.25	0.88	13.62	1.13
750	155	27.10	1.10	20.59	O.A.
1000	156	36.40	1.10	27.15	O.A.
1500	157	48.90	1.10	38.37	O.A.
2000	158	49.75	2.64	37.10	O.A.
3000	159	78.15	2.64	58.55	O.A.

12 & 24 Volts Prim. 200-240V.

Amps	Ref. No.	Price	Post
12V 24V			
0.3	0-15	242	1.58
0.5	0-25	111	1.38
1	0-5	213	1.74
2	1	71	2.30
4	2	18	2.96
6	3	70	4.18
8	4	108	4.56
10	5	72	5.20
12	6	116	5.51
16	8	17	7.90
20	10	115	10.42
30	15	187	13.25
40	20	232	14.85
60	30	226	16.88

30 Volts

Amps	Ref. No.	Price	Post
0.5	112	1.90	0.47
1	79	3.40	0.56
2	3	3.50	0.56
3	20	4.50	0.64
4	21	5.15	0.72
5	51	6.40	0.73
6	117	7.16	0.88
8	88	9.55	0.95
10	89	9.67	0.95

AUTO TRANSFORMERS

VA	Ref. No.	Price Cased	Price Plugs	Price Open	Post
Tapped at 115, 220, 240 Volts					
20	113	3.85	0.20	1.71	0.47
Tapped at 115, 200, 220, 240 Volts					
150	4	6.38	0.20	4.18	0.56
200	65	7.94	0.20	4.95	0.64
300	68	8.00	0.20	5.81	0.72
500	67	10.99	0.20	8.85	0.88
750	83	13.82	0.25	10.60	0.95
1000	84	17.27	0.25	13.68	1.13
1500	93	21.87	0.25	18.31	O.A.
2000	95	33.11	1.90	24.25	O.A.
3000	73	47.84	2.10	35.10	O.A.

50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.

Amps	Ref. No.	Price	Post
0.5	102	2.58	0.47
1	103	3.48	0.50
2	104	5.03	0.64
3	105	5.81	0.72
4	106	7.58	0.88
6	107	12.30	0.95
8	118	13.20	1.13
10	119	17.02	O.A.

60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 48, 60V.

Amps	Ref. No.	Price	Post
0.5	124	2.30	0.50
1	126	3.41	0.56
2	127	5.09	0.72
3	125	7.52	0.80
4	123	8.75	0.86
5	40	9.75	0.95
6	130	11.20	1.01
8	121	15.00	1.19
10	122	18.20	O.A.
12	189	18.50	O.A.

MINIATURE AND EQUIPMENT

Prim. 240V with screen.

Sec. 1 Volts	Sec. 2	Milliamps	Ref. No.	Price	Post
3-0-3	—	200	238	1.50	0.25
0-6	0-6	500	234	1.38	0.25
0-6	0-6	1000	212	1.90	0.47
9-0-9	—	100	13	1.40	0.25
0-9	0-9	330	235	1.50	0.25
0-9-9	0-9-9	500	207	1.98	0.34
0-9-9	0-9-9	1000	208	2.75	0.47
15-0-15	—	40	240	1.85	0.25
0-15	0-15	200	236	1.38	0.25
20-0-20	—	30	241	1.85	0.25
0-20	0-20	150	150	237	1.38
0-15-20	0-15-20	500	205	2.75	0.56
0-20	0-20	300	300	214	1.38
0-20	—	3500	NO SCREEN	1116	3.20
20-12-0-12-20	—	700 (D/C)	—	221	3.20
0-15-20	0-15-20	1000	1000	206	3.50
0-15-27	0-15-27	500	500	203	3.00
0-15-27	0-15-27	1000	1000	204	3.85

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 20p	60 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 85p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 55p	100 P.I.V. 70p
200 P.I.V. 35p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 85p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 80p

ADD 10p P & F PER ORDER



PLEASE ADD 8% FOR VAT

POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5 and 12 volts at 500 mA D.C., Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc Size 7.5 x 5.0 x 14.0cm. Price £3.95. Post 25p.



MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation. Price: Packet of 10 for 60p. Postage 15p.

A.S.P. LTD.

DEPT PW6, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436



ELECTRONIC KITS

requires reliable firms well connected in own markets for handling exclusive sales in countries where no organisation yet exists.

Send enquiries to:

AMTRON
Casella Postale 4160, Milano, Italy

VALVE BARGAINS

Any 5 50p, 10 75p, 50 £3.30, 100 £6.40. Your choice

from the following list:

ECC82, ECL80, EB91, EF80, EF183, EF184, PC86, PC88, PC97, PC900, PCC84, PCC89, PCC189, PCF80, PCF802, PCF805, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14

Colour Valves 25p each
PL508, PL509, PY500/A

Press 4 Button UHF Tuners £2.50.

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11 — For Stereo and Standard VHF Radio

B12 — For the older VHF Television, please state

BBC1 & ITV Channels.

B45 — For mon. or colour


this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit.

Price £3.40 each

Prices include V.A.T. P. & P. under £1/15p, £1 to £3/20p over £3/25p.

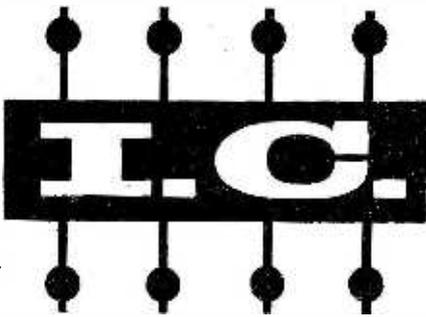ELECTRONIC MAILORDER LTD., 62 Bridge Street, Ramsbottom, Bury, Lancs 1.



OF THE MONTH

Number 51 SN76023N AUDIO POWER AMPLIFIER

THE Texas Instruments SN76013N and SN76023N IC audio amplifiers can provide a continuous output power of typically 5W RMS into an 8Ω loudspeaker when it is driven from a 24V power supply. The minimum output power before clipping obtainable from any device of either type is 4W into an 8Ω load or 3W into a 16Ω load using a 24V supply.

The absolute maximum permissible power supply voltage is 28V, but it is wise to regard the upper limit as about 24V so as to allow a suitable margin of safety.

The minimum recommended load impedance is 8Ω.

Both ICs incorporate a finned heat sink made of extruded aluminium providing a total effective area of about 75 square centimetres in a small space. Its efficiency can be appreciated by the fact that the absolute maximum continuous output power rating into an 8Ω load is 8W RMS at 25°C, or 6W at 70°C.

The quiescent power supply current at zero signal is about 10mA at a power supply voltage of 24V.

AVAILABLE TYPES

The only difference between the SN76013N and the SN76023N is in the feedback circuit. No internal feedback components are included in the SN76023 device and suitable external components must therefore be employed. This increases the versatility of the device, since tone controls can be used as part of the feedback circuit.

The SN76013 contains two internal feedback resistors which minimise the number of external components required. The gain of this device can be reduced of necessity.

The SN76013 and SN76023 are each available in either a dual-in-line package which has a gap in the centre of each line of pins or a quad-in-line encapsulation in which alternate pins on each side are bent so that one can see four lines of pins when the device is viewed from one end. The same gap is present at the centre of each line of pins.

The SN76013ND is electrically identical to the SN76013N but has no metal fins, possessing instead a metal tab at the centre of each of the two lines of pins. It provides a minimum output power of 3W into a 15Ω load, but the use of a load of smaller impedance may result in the device overheating owing to the absence of cooling fins. It can be used in the same circuits as the SN76013N, but will not be discussed further here.

SN76023N AMPLIFIER CIRCUIT

A typical circuit for the use of the SN76023N as a power amplifier is shown in Fig. 1.

The bias voltage at pin 2 is smoothed by R2 and C2 to remove mains hum or any other signals on the power supply line which reach pin 2. The bias is then applied via R1 to the input pin 1. The value of this bias voltage determines the mean output potential at pin 6.

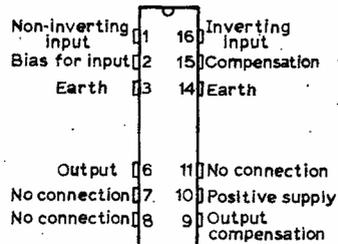
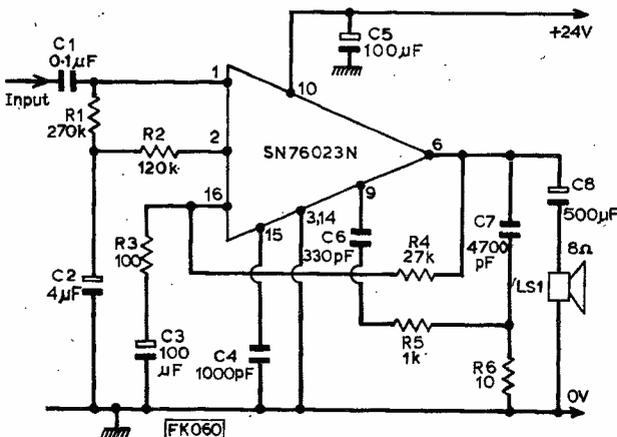


Fig. 1: Typical circuit using the SN76023N integrated circuit as an audio amplifier. The pin functions are shown to the right (viewed from above).

If a well-smoothed power supply is employed, C2 may be reduced to $0.1\mu\text{F}$. There is no point in increasing its value above about $10\mu\text{F}$, especially as the use of a large value will result in a short time delay at switch-on whilst this capacitor charges.

The input impedance of the circuit is approximately equal to R1, since the input impedance of the integrated circuit itself is well over one megohm.

The optimum value of C5 depends on the type of power supply employed. If a well-regulated mains power pack is used, C5 may be as low as $0.1\mu\text{F}$, but for the other types of supply it should have a value of at least $100\mu\text{F}$ —preferably considerably more when batteries are used. C5 should be soldered as close to the integrated circuit as possible. Alternatively a $0.1\mu\text{F}$ capacitor may be soldered directly between pin 10 and ground and a larger electrolytic capacitor in parallel with it at a more convenient point.

Frequency compensation is provided by C4. The value shown will provide low distortion at frequencies approaching 100kHz . Instability may occur if the value of this component is made too small in an attempt to raise the upper frequency limit for non-audio applications.

The value of C6 is not at all critical; this component maintains high frequency stability on negative going half cycles by compensating for the difference between two internal complementary transistors.

The low frequency response is mainly determined by the value of C8. This component prevents the loudspeaker from taking a steady current from the output of the amplifier. The filter C7-R6 compensates for the inductance of the speaker.

VOLTAGE GAIN

The voltage gain of the circuit is equal to $(R4 + R3)/R3$. If the values shown are used, the gain is about 270 or about 48dB. If R3 is increased to 470Ω , the voltage gain falls to about 57 or about 35dB. R3 should not be increased above about $1\text{k}\Omega$ (at which value the gain is 28 or about 29dB) unless an additional capacitor is connected between pins 1 and 16 to reduce the gain at very high frequencies and thereby maintain stability.

The value of the feedback resistor R4 can be increased to give a very high gain, but this will result in increased distortion and the circuit will be more prone to instability. In addition, there will be a delay at switch-on as C3 charges through R4.

THE SN76013N CIRCUIT

The SN76013N may be used in the same type of circuit, but the following modifications must be made to the circuit of Fig. 1.

- The feedback resistor R4 is omitted, since an internal $25\text{k}\Omega$ resistor is connected between pins 6 and 16 of the SN76013N device.
- The SN76013N contains an internal 100Ω resistor which functions as R3 of Fig. 1. The inverting input is not connected directly to pin 16, but via the 100Ω resistor.

If a voltage gain of 250 (about 48dB) is required, C3 is connected directly between pin 16 and ground. If a lower gain is required, an additional resistor is connected between pin 16 and the upper end of C3. This additional resistor will be in series with the internal 100Ω resistor.

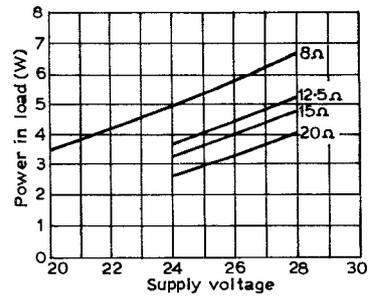


Fig. 2: Output power plotted against supply voltage for a distortion of one per cent.

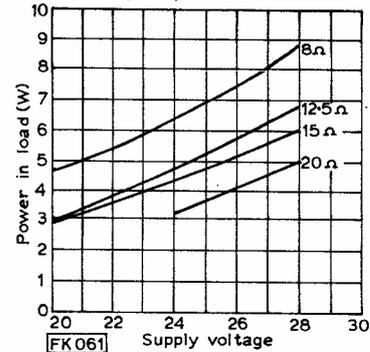


Fig. 3: Output power plotted against supply voltage for a distortion of ten per cent.

PERFORMANCE

The output power from these devices is plotted against the power supply voltage for distortion levels of one and ten per cent in Figs. 2 and 3 respectively.

The minimum supply voltage at which the devices will function satisfactorily at low power is about 8V.

Although a speaker of impedance greater than 8Ω may be used, the power delivered to the speaker at any given value of the supply voltage will be reduced as shown in the graphs.

The power dissipated in these devices can reach about 3.8W with a 24V supply or 5.4W with a 28V supply when an 8Ω loudspeaker is used. The corresponding figures for a 15Ω speaker are about 2.1W and 2.6W .

RADIO RECEIVERS

The writer has used the SN76023N in the circuit of Fig. 1 with an input from a t.r.f. radio receiver using the ZN414 device. The supply voltage was 9 to 12V .

It was found that the gain was rather too high and therefore the value of R3 of Fig. 1 was increased to 330Ω . This comment will probably apply to the use of the Fig. 1 circuit with most radio tuners. It would have been necessary to increase the power supply voltage if the output of 5W had been required.

These audio amplifiers can also be used with super-heterodyne IC radio receivers such as the TBA 651, LM1820, $\mu\text{A}720$, etc.

USE IN RECORD PLAYERS


The circuit of Fig. 4 shows how the SN76023N can be used with a record player employing a ceramic cartridge. This relatively simple circuit includes separate bass and treble controls and a volume control.

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, eucutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £12-50. P. & P. 55p.

DE LUXE STEREO AMPLIFIER

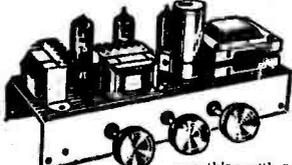

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving a d.c. smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4 1/2" h. Overall height including valves 8". Ready built & tested to a high standard. £10-75. P. & P. 85p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v, and 9v, and 13v, at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built & tested. PRICE £5-20 P. & P. 55p.

VINYL & REKINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1-50 yd. length. P. & P. 30p per yd. (min. 10 yd.). S.A.E. for samples.

HARVERSONIC SUPER MONO AMPLIFIER

A super quality grain amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. PRICE £4-20 P. & P. 60p BARGAIN PRICE

FEW ONLY! High grade mains transformer with grain orientated lamination. Primary 200/240 Secondary 18.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2 1/2" h x 2 1/2" w x 2" d overall. £1-35 plus 35p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-10-15-20-25-30-35-40-50-60v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2-60 P. & P. 65p.

MAINS TRANSFORMER. For transistor power supplies. Ptl. 200/240v. Sec. 0-0-9 at 500 mA. £1-25. P. & P. 30p. Ptl. 200/240v. Sec. 12-0-12 at 1 amp. £1-40. P. & P. 30p. Ptl. 200/240v. Sec. 10-0-10 at 2 amp. £2-00. P. & P. 40p.

3 VOLT RELAY 100 mA/4 single pole normally closed. 3 for 60p + 15p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 10Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price 1-20p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 100's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

5 Reference Encyclopedias for Electronic Engineers and Designers, covering between their transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents, 90p; Transistor Equivalents, £1-00; Transistor Characteristics, £1-80; POST FREE All three together, £3-00

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias £1-00, Post Free 8 pole 3 way 2 bank low loss Walex type switches 1 1/2" sections. Standard spindle. 2 switches 64p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday. All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to 'lock-on' station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form).

PRICE £23-00 Post and Packing £1-00.

STEREO-DECODER SIZE 2" x 3" x 1" ready built. Pre-aligned and tested. Sens. 20-500 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5-40 plus 15p. P. & P. Stereo beacon light if required 40p extra.



SPECIAL BARGAIN OFFER! Limited number of BBR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £28-00 + p. & p. 80p.

LATEST Hi Sensitivity Uni-directional slim-line condenser microphone as used by many professionals. Very low acoustic feedback. Available hi impedance or low impedance. States which required. £13-50 plus 25p P. & P.

LATEST ACOS GP91/180 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1-46. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal Mounting brackets and armover stylus, 70mV per channel output. ONLY £1-75 + 15p P. & P.

SONOTONE STAIC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-27 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2-78. P. & P. 15p.

LATEST BERTHO T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £1-80 P. & P. 15p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer. EOC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 5in. deep x 6in. high. Ready built and tested. PRICE £5-50. P. & P. 75p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6-70. P. & P. 75p.

HI-FI LOUSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive double front. Size 18 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (estate which). **OUR PRICE £9-50** each Carr. £1-25. Cabinet Available Separately £5-00, Carr. £1-10. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8-00, Carr. £1-25.

LOUDSPEAKER BARGAINS

5in. 3 ohm £1-25. P. & P. 15p. 7 x 4in. 3ohm £1-40. P. & P. 25p. 10 x 6in. 3 or 15 ohm £2-10. P. & P. 35p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1-70. P. & P. 25p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3-50. P. & P. 35p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network £4-65. P. & P. 35p. P.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £1-30 + 25p. P. & P.

BRAND NEW Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly 27-50. Guitar models: 25w £7-50. 35w, £8-50. P. & P. 75p.

"POLY FLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.R. for full details. Only £6-60 each. P. & P. 60p.

NOW ALSO AVAILABLE: 8", 10 watts, r.m.s. 20 watt peak 40Hz-20,000Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cans. £4-32 + 40p P. & P.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 16 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000 Hz. Sensitivity: better than 60mV into A.C. Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to -10dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp. Overall Size 12" w x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £13-96 P. & P. 50p (Magnetic input components 35p extra)

POWER PACK KIT £4-82 P. & P. 55p
CABINET £4-82 P. & P. 50p
(Post Free if all units purchased at same time)

Full after sales service

Also available ready built and tested £28-08. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc. and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4 1/2" x 4 1/2" h. Incorporates EOC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £6-50. P. & P. 70p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5-50 P. & P. 70p.

10/14 WATT HI-FI AMPLIFIER KIT

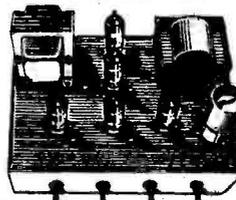

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ohm speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up: 2 EL84s, EOC83, EF86 and E280 rectifier. Simple instruction booklet 16p + 8AE (Free with parts) All parts sold separately. ONLY £10-25 P. & P. £1-00. Also available ready built and tested £14-00 P. & P. £1-00.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3 1/2 inch plugs. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3-50. P. & P. 25p.


PRICES INCLUDE VAT

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station. SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

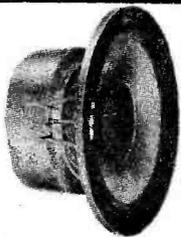(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. OF OVERSEAS ORDERS CHARGED EXTRA.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7-75
Baker Group 35 3, 8 or 15 ohm	£8-50
Baker Group 50/12 8 or 15 ohm	£12-50
Baker Deluxe 12" d/cone	£10-75
Baker Major	£8-50
Baker Regent	£7-75
Baker Superb	£14-50
Baker Auditorium 12	£12-50
Celestion MH1000 horn	£10-95
Celestion P5T3 for Unilex	£2-35
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00
Coral 6 1/2" d/cone roll surr. 8 ohm	£2-50
Coral 8" d/cone roll surr. 8 ohm	£2-25
EMI 13 x 8 3, 8 or 15 ohm	£2-25
EMI 13 x 8 150 d/c 3, 8 or 15 ohm	£2-25
EMI 13 x 8 type 350 8 or 15 ohm	£8-25
EMI 13 x 8 20 watt base	£6-60
EMI 6 1/2" 93850 4 or 8 ohm	£3-00
EMI 5" 98132CP 8 ohm	£2-50
EMI 8 x 5 d/cone, roll surr 10 watt	£2-85
EMI 5 1/2" tweeter 97492A	£1-65
Eagle DT33 30 watt tweeter	£5-45
Eagle HT15 horn tweeter	£3-80
Eagle CT5 cone tweeter	£1-75
Eagle CT10 tweeter 8 or 16 ohm	£2-55
Eagle MHT10 horn tweeter	£3-80
Eagle crossover CN23, CN28, CN216	£1-58
Eagle FR4	£5-30
Eagle FR65	£8-35
Eagle FR8	£10-65
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2-80
Elac 6 1/2" 6RM171 d/c roll surr.	£3-50
Elac 6 1/2" 6RM220 d/cone	£2-85
Elac 4" tweeter TW4	£1-21
Elac 10" d/cone 10RM239 8 ohm	£2-65
Elac 8" 8CS175 3 ohm	£2-50
Fane Pop 15 watt 12"	£5-25
Fane Pop 25/2 25 watt 12"	£7-25
Fane Pop 40 watt 10"	£3-50
Fane Pop 50 watt 12"	£12-00
Fane Pop 55 12" 60 watt	£12-50
Fane Pop 60 watt 15"	£13-25
Fane Pop 70 watt	£15-95
Fane Pop 100 watt 18"	£24-50
Fane Crescendo 12A 100 watt 12"	£29-00
Fane Crescendo 12B bass	£29-00
Fane Crescendo 15" 100 watt	£36-00
Fane Crescendo 18" 150 watt	£51-95
Fane 80T 8" d/c roll surr.	£7-00
Fane 80T7 8" d/c roll surr.	£3-85
Fane 808T 8" d/c	£2-75
Fane 701 twin ribbon horn	£35-00
Fane 910 horn	£12-75
Fane 920 horn	£33-00

Goodmans 8P 8 or 15 ohm	£5-00
Goodmans 10P 8 or 15 ohm	£5-30
Goodmans 12P 8 or 15 ohm	£12-95
Goodmans 12P-D 8 or 15 ohm	£16-75
Goodmans 12P-G 8 or 15 ohm	£15-75
Goodmans Audiomax 12AX 100 watt	£37-50
Goodmans Audiomax 15AX	£40-25
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Mldax 750	£16-00
Goodmans Axent 100 tweeter	£7-25
Goodmans Audiom 100 12"	£12-00
Goodmans Axiom 401 12"	£17-25
Goodmans Twinaxiom 8	£8-25
Goodmans Twinaxiom 10	£9-80
Kef 127	£5-25
Kef T15	£6-00
Kef B110	£7-25
Kef B200	£8-25
Kef B139	£14-25
Kef DN8	£2-00
Kef DN12	£4-95
Kef DN13	£3-90
STC4001G super tweeter	£8-19
Richard Allan CG8T 8" d/c r/surr.	£6-35
2 1/2" 84 ohm, 70mm 80 ohm, 70mm 8 ohm	£5
2 1/2" 75 ohm	£5-50
7" x 4" 3 or 8 ohm	£1-40
8" x 5" 3 or 8 ohm	£1-50
10" x 6" 3, 8 or 15 ohm	£2-30
Complete Radferd range in stock	

SPEAKER KITS

Baker Major Module	each £10-75
Goodmans Mezzo	pair £45-00
Goodmans DIN 20	each £9-75
Helme XLK 25	pair £22-00
Helme XLK 30	pair £14-95
Helme XLK 50	pair £39-95
Keffil 1	each £20-95
Keffil 3	each £36-75
Richard Allan Twinkit	each £8-95
Richard Allan Triple 8	each £13-75
Richard Allan Triple	each £19-95
Richard Allen Super Triple	each £23-75
Wharfedale Linton 2 kit	pair £19-25
Wharfedale Glendale 3 kit	pair £34-50
Wharfedale Dovedale 3 kit	pair £52-50

PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£49-75
Linear 30/40	£30-00
Linear 40/60	£35-00
Linear 80/100	£58-95
Linear 100 watt slave	£44-00
Eagle PA range in stock—ask for catalogue.	

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 39p each, 12" and up, 50p each. Speaker kits 75p each (£1.50 pair) tweeters and crossovers 25p.

ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
Discount Radio, PA, Hi-Fi: 10 Swan St. Wilmslow
Send stamp for free booklet "Choosing a Speaker"



AGFA Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!

	1	5	10
C60	37p	£1-30	£3-50
C90	50p	£2-48	£4-95
C120	63p	£3-10	£6-29

AGFA HIGH DYNAMIC SUPER

	1	5	10
C60+8	50p	£2-40	£4-70
C90+8	68p	£3-35	£6-60
C120	99p	£4-90	£9-80

AGFA STEREO-CHROM CHROMIUM DIOXIDE

	1	5	10
C60	85p	£4-20	£8-30
C90	£1-08	£5-35	£10-60

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PW)

10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

tecknowledgegy;

Ambit has something different to offer the modern electronics enthusiast - amateur or professional.

Tecknowledgegy - the sort of data and information service that simply cannot be matched by any other component source. With today's new products in electronics, you need a new approach to buying to make certain that you get best advantage from the vast amount of data and information that is being published to complement the modern technology.

Our speciality is wireless. AMBIT has all the semiconductor and inductors for all types of receiver up to 200MHz. VHF FM stereo is covered by various modules for tunerhead, IF and decoder applications. Larsholt 7252 FM tunerhead: A complete varicap tuned head+IF, with 1uV for 26dB S/N, 0.1% THD, muting, AFC, meter drive audio preamps Ready built £20.00.

Linear Phase FM IF system, with mute, AFC, AGC, meter drive. Twin IF filters and 0.1% THD. Built and aligned on a R&S Polyskop for £9.00.

EF5603 MOS and Varicap FM tunerhead from TOKO. The best in the range £8.40.

EC3302 FET and varicap FM tunerhead for lower cost systems. £5.00.

The ALL Electric Wireless.....

A UNIQUE varicap tuned AM radio unit with IC, ceramic filter IF, and three stage tuning. Covering the medium wave in one sweep. Kit £8.00, built for £9.95.

A Unique 150mm track length slider for AM/FM varicap tuners, and any other application for a precision 50k linear WW potentiometer. £3.00 ea. 6 Button preset varicap control unit from IMI. Inc fixing bracket £3.40.

993090 MPX PLL decoder. A superb unit with pilot tone filter, audio preamps, LED beacon. Kit £6.40 - built £7.60.

91310 Low cost MPX decoder module. No corner cut though, and price includes LED beacon and TOKO pilot tone filter. Kit for £5.10, built £5.90.

We also carry a wide range of linear ICs for audio and radio

EG The LM381N stereo preamp £1.85
The NE560,561,562,563 PLL £3.19 ea
CA3089E FM IF subsystem inc coil £1.94
CA3090AQ stereo decoder inc coil £3.75

And stacks of TOKO coils and filters for radio and MPX. SAE for our free shortform lists.

Shortform price list and product summary FREE with an SAE. Full catalogue folder cost is 40p (inc), and contains more info on TOKO and up to the minute linears than ever.

from

Ambit international
37 High Street
Brentwood, Essex.
CM14 4RH
Tel: 216029 Tlx: 995194
VAT EXTRA: P&P 20p

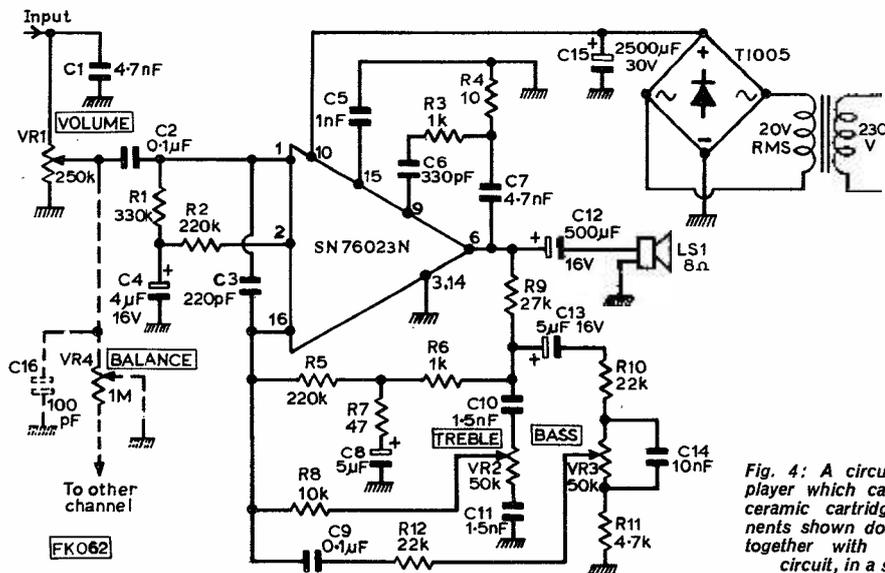


Fig. 4: A circuit for a record player which can be fed from a ceramic cartridge. The components shown dotted are required, together with another identical circuit, in a stereo system.

If a stereo system is required, the additional components shown dotted may be employed to provide a channel balancing control. The lower end of VR4 would be connected to the slider of the volume control in the other identical channel.

The 27kΩ resistor R9 is the main feedback resistor which passes the feedback current to the tone control network.

A power supply unit is shown in Fig. 4 which is also suitable for use with the circuit of Fig. 1. If the lead to pin 10 is not short, an additional 0.1µF capacitor should be soldered close to the integrated circuit between pin 10 and ground. It will provide a low impedance at high frequencies and will thus preserve stability.


AVAILABILITY

AVAILABILITY

The SN76013N and the SN76023N are available from S.D.S. Components Ltd., Hilsea Industrial Estate, Portsmouth, PO3 5JW at £1.57 each plus V.A.T. plus 20p packing and postage.



PW TECHNICAL CROSS PUZZLE No. 9

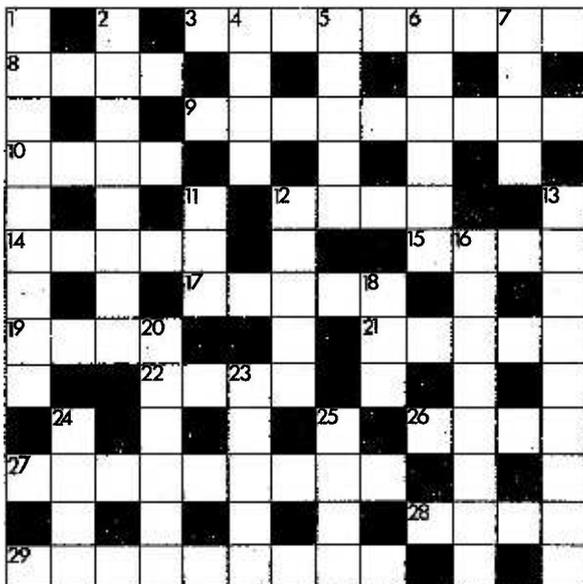

ACROSS

- 3 The airman's voice in stereo? (5, 4)
- 8 A tester set this short one . . . (4)
- 9 . . . and essences to test this mike distortion! (9)
- 10 Cable erosion joins don't look straight (4)
- 12 Put unclean material on the air? (4)
- 14 Echo irking the group inside (5)
- 15 Box handled only with gloves on? (4)
- 17 Stationary selector? (5)
- 19 The law for resistance units? (4)
- 21 Non-transmitters (5)
- 22 Six to one it's such a triode! (4)
- 26 Head of a solid state for oiling? (4)
- 27 Solar orbit makes speakers hum? (5, 4)
- 28 Shorten aerial for a bit of opera? (4)
- 29 Annoyed about such a network? (9)

DOWN

- 1 Quite a dish with open-air Mike! (9)
- 2 A graphic account of a signal success (8)
- 4 One girl got me to switch up, boss . . . (4)
- 5 . . . and another's ring is radioactive! (5)
- 6 Rough ways to make L.P.'s? (6)
- 7 Component between arm and head (4)
- 11 Painting transistors back and front only! (3)
- 12 It's groovy before you hear a sound! (3,2)
- 13 Tape device to rub out the chief! (5,4)
- 16 Modulators containing liquid? (8)
- 18 Short value with ship-to-shore link? (3)
- 20 America is solid with them (6)
- 23 Reception's not so hot in this house? (5)
- 24 Den a beginner on this broadcasting? (4)
- 25 The magnetism of that Rod! (4)


FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH

PW 'Easybuild' ELECTRONIC ORGAN

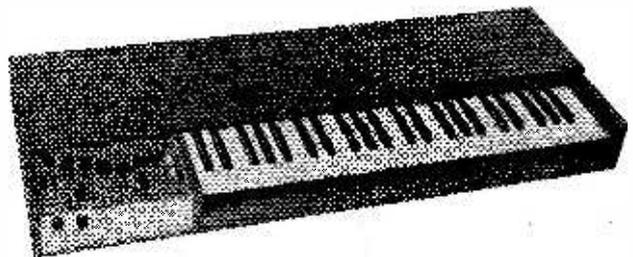PART 4

M. J. HUGHES M.A., C. Eng. MIERE

This, the fourth and final part of the PW Easybuild Organ, covers in detail the construction of the cabinet, the dimensions required to cut out the aluminium cover plate, and the final wiring of the keyboard and pitch switches.



AS with the rest of this project, follow the details of the cabinet very carefully to prevent any problems which might arise with parts not fitting exactly. The cabinet design has been kept as simple as possible avoiding any fancy carpentry. Most of the structure is held together with butt joints, pins and resin glue. Chipboard, plywood and softwood battens are the basic materials required but the final attractive appearance is obtained with iron-on wood veneer which also covers the less attractive details of the assembly!

place. Make sure that these pieces are accurately located otherwise the keyboard will not fit properly.

Stage two is to make and fit the supporting battens for the two printed circuit boards. These are glued and pinned into position as shown in Fig. 14. The main printed board should fit snugly into the back left hand corner of the cabinet and be supported on all edges. The power supply need only be supported along its two longer edges. Make sure that the battens are not too high otherwise the top of the transformer might protrude.

CABINET CONSTRUCTION

Stage one is to make the basic structure which is, in effect, a shallow tray comprising a base made from 6mm ($\frac{1}{4}$ in) plywood with 12.5mm ($\frac{1}{2}$ in) chipboard ends and back, Fig. 14. An elliptical aperture for the speaker is cut at one end of the back, using a coping saw, while a recess can be cut in the outer surface if one wishes to use an inlaid loudspeaker grill which will give the back surface of the finished organ a nice flush appearance. No details of this grill are shown because it is felt that readers can use their own initiative here. The prototype used a commercial grill made from thin strips of wood glued to hessian.

The two sides and back are glued and pinned into position and a strip of softwood is similarly fixed along the front edge, giving extra strength to the edge and finishing off the gap which would otherwise be under the keys. A notch has to be cut in one end of this batten for the aluminium cover which is fitted later.

A long batten is fixed towards the rear of the tray to which the keyboard hinge is screwed, likewise two short blocks are required at either end of the keyboard so that it can be firmly screwed down into

FITTING INTERNAL COMPONENTS

The third stage is to fit the internal component parts into place. Start with the keyboard. The hinge should be opened up horizontally, and when resting on the long batten, the two side support blocks should just fit under the end flanges of the keyboard sub frame. Ensure that the busbars are short enough at the ends not to foul on these blocks! The front edge of the keys should be just about flush with the front edge of the cabinet, they should be inset rather than proud. Hinge the keyboard firmly to the long batten but do not, at this stage, screw the end flanges down to the support blocks.

Place the main PCB in position and when satisfied that it is seated correctly, screw it down on all four sides. Hinge the keyboard up and carefully lay the bunch of wires, that will form the loom, under the keyboard and then shut the keyboard down on them for the time being. There should be sufficient clearance for the wires to run between the hinge batten and the left-hand end support block.

Next screw the power supply PCB and loudspeaker

into position. Cut to shape, but do not fix, the two keyboard cheeks. These are made from softwood and veneered to match the cabinet Fig. 15. Note that the left-hand cheek has a recess along two edges to match the recess in the end of the front strip, for locating and fixing the aluminium cover plate. The cheeks will ultimately be fixed into position from the underside of the cabinet with long thin screws. They take very little strain and really only serve to finish off the appearance.

At this stage, cut, bend and grain (with wire wool) the aluminium cover plate, shown in Fig. 16. Fix the three switches and two jack sockets into position and make any adjustments so that it will fit over the slider controls of the main PCB, without fouling. This can now be put to one side because the connections to it will be made later. Finally assemble the lid which is designed to fit on to the top of the cabinet and be fixed with three screws, one in each end and one in the centre of the back. To finish the cabinet, veneer all visible exterior surfaces, not forgetting the inside surfaces of the two ends.

LOOM CONNECTIONS

First connect the three leads from the power supply board to the three corresponding terminals on the main PCB. Run leads from the OV and LS1 pins of the main board to the loudspeaker and mains leads to S1 and the power supply board. Now complete the loom wiring by hinging up the keyboard.

Take a piece of twine about 1.85m (6ft) long and gently bundle the 60 wires together about 50mm (2in) away from the main PCB. Do not put too much strain on them and make sure there are no kinks. They should give the appearance of long hair con-

verging to the top end of a plait. Instead of plaiting the wires they should be kept as straight and as parallel as possible once they have been formed into the bunch. Use the twine to tie the bunch securely and then tie a tight loop of twine round the wires approximately every 25mm down their length while forming the loom round and under the keyboard.

When the corner has been negotiated and the loom is close to the tags for bottom "C", locate the wire which carries the flag number 31 and cut it to length so that it can be neatly soldered to the tag which carries RK2. After soldering into position tie another loop around the loom and then cut and solder wire

CABINET DIMENSIONS		
accurate dimensions in metric, imperial to nearest $\frac{1}{16}$ in		
A (2 off)	355 x 84 x 10mm	(14 x 3 $\frac{1}{4}$ x $\frac{3}{8}$ in.)
B	925 x 84 x 10mm	(36 $\frac{3}{8}$ x 3 $\frac{1}{4}$ x $\frac{3}{8}$ in.)
C	945 x 355 x 6mm	(37 $\frac{1}{4}$ x 14 x $\frac{1}{4}$ in.)
D (2 off)	103 x 31 x 25mm	(4 x 1 $\frac{1}{4}$ x 1in.)
E	720 x 45 x 25mm	(28 $\frac{3}{8}$ x 1 $\frac{3}{8}$ x 1in.)
F	657 x 32 x 17mm	(25 $\frac{3}{8}$ x 1 $\frac{1}{4}$ x $\frac{5}{8}$ in.)
G (2 off)	322 x 35 x 10mm	(12 $\frac{5}{8}$ x 1 $\frac{3}{8}$ x $\frac{3}{8}$ in.)
H (2 off)	205 x 35 x 10mm	(8 x 1 $\frac{3}{8}$ x $\frac{3}{8}$ in.)
I (2 off)	80 x 12.5 x 10mm	(3 $\frac{1}{8}$ x $\frac{1}{2}$ x $\frac{3}{8}$ in.)
J	190 x 12.5 x 10mm	(7 $\frac{1}{2}$ x $\frac{1}{2}$ x $\frac{3}{8}$ in.)
K	945 x 250 x 10mm	(37 $\frac{1}{4}$ x 9 $\frac{7}{8}$ x $\frac{3}{8}$ in.)
L (2 off)	152 x 12.5 x 10mm	(6 x $\frac{1}{2}$ x $\frac{3}{8}$ in.)
M	665 x 12.5 x 10mm	(26 $\frac{1}{8}$ x $\frac{1}{2}$ x $\frac{3}{8}$ in.)
N	50 x 12.5 x 10mm	(2 x $\frac{1}{2}$ x $\frac{3}{8}$ in.)
P	925 x 44 x 22 mm	(36 $\frac{3}{8}$ x 1 $\frac{1}{2}$ x $\frac{7}{8}$ in.)
Q	205 x 7 x 7mm	(8 x $\frac{5}{16}$ x $\frac{7}{16}$ in.)
R		} see Fig. 15
S		

AM0347

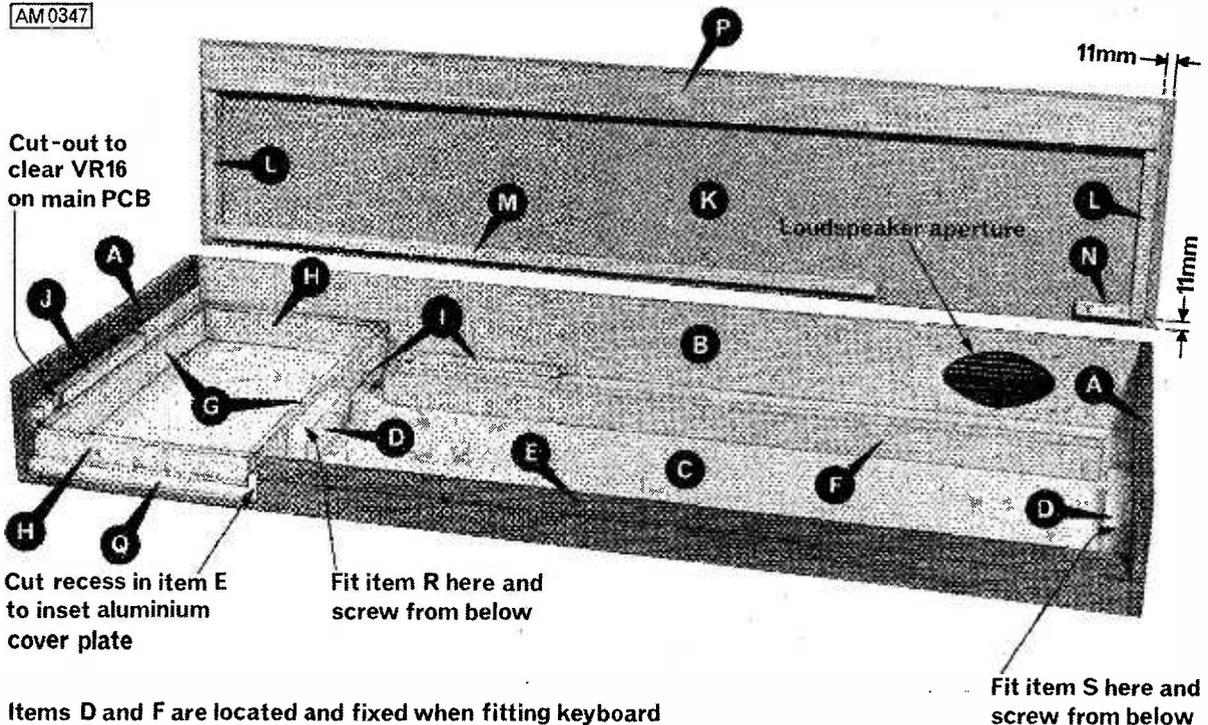


Fig. 14: The complete cabinet, showing internal construction and the veneer on exposed surfaces. Sizes for the individual sections are obtained by noting the relevant letter on the section and referring to the table immediately above this figure.

56 to the next tag; tie another loop and then work steadily down the keyboard referring all the time to the wiring schedule, connecting one wire at a time and carefully and neatly tying the loom tightly after each soldering operation.


After the first two or three connections it will be found to be quite a simple operation and it has the distinct advantage that it gets easier as the loom gets thinner. If this step is done neatly, a great deal of satisfaction will be gained from the end result. It will look neat and professional, but more importantly, will give a strong, reliable job.

BUSBAR CONNECTIONS

The next stage in the construction is to connect the busbars via the switches to the main PCB, Fig. 17. Use screened pick-up lead for this and make sure the screen is earthed exactly as shown. Two of the connections go straight to the board while two go via S2 and S3. A little loose cable can be left under the aluminium cover plate so that it can be readily lifted out of position without the leads restraining its movement (do not forget the solder tag under one of the switch fixing screws). The screened leads should roughly follow the same routing as the loom and, if wished, could be anchored to the loom with twine to stop them flopping about under the keyboard.

TESTING

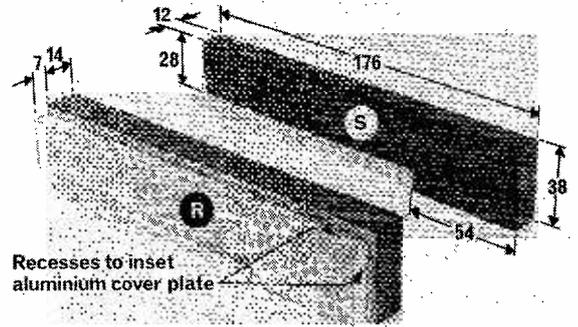The organ can now be tried out properly and final tests and adjustments carried out as follows:—



All dimensions are in millimetres (mm)

AM0348

Fig. 15: Annotated photograph of the cheeks, which are placed at either end of the keyboard when cabinet construction is completed.

Assuming that the main PCB is exactly as it was left after the initial tests it should be possible to apply power, and with the vibrato at minimum and volume at maximum, be able to advance each "voice" for each of the two pitches in turn and get a sound from the loudspeaker for every note on the keyboard as the keys are depressed. There will be much less volume than previously because the keyboard series resistors have been introduced which reduce the output level to about 1/50 of the original. It is possible to compensate for this by increasing the gain of the busbar pre-amplifiers and, if that is not enough, by means of VR15.

Check that every note sounds correct at each pitch. If not, check for bad connections in the line for that note. Try playing several notes at the same time and then a tune. It may be that you will hear a

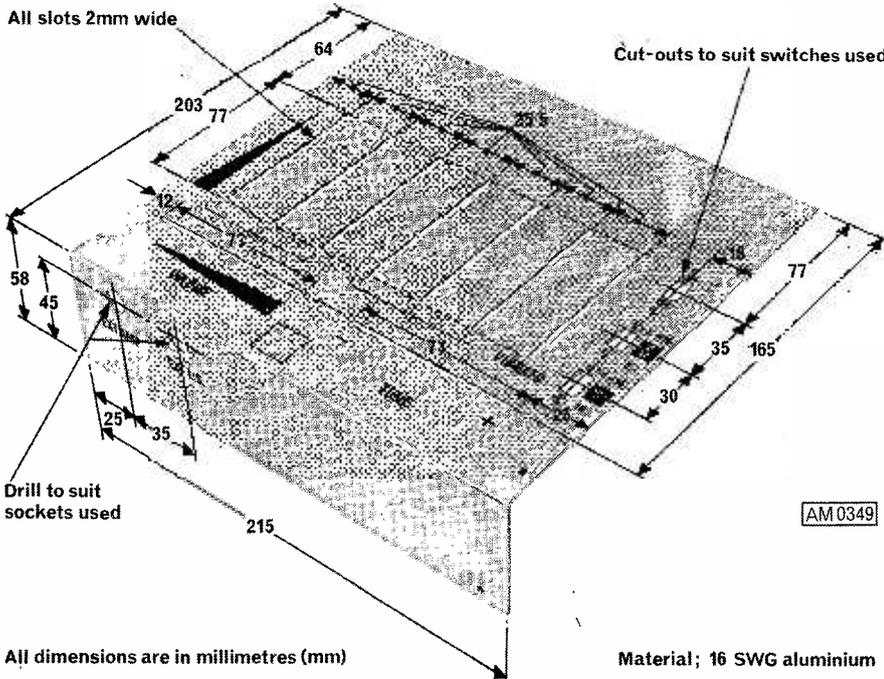


Fig. 16: Aluminium cover plate, giving drilling and cutting dimensions of the slots and holes required for the organ controls.

AM0349

All dimensions are in millimetres (mm)

Material; 16 SWG aluminium

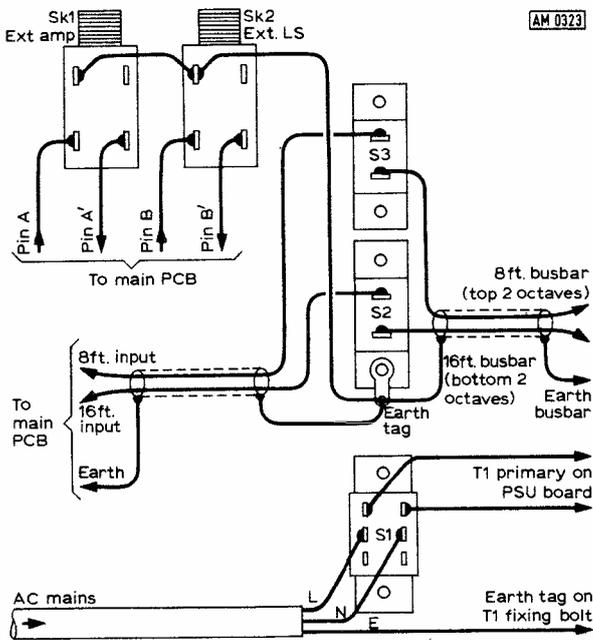


Fig. 17: Pitch controls and jack socket wiring for the underside of the cover plate.

sort of click as you play some notes. This is to be expected and is most likely caused by the key contacts making before they break through the earth busbar. For a fraction of a second the whole busbar will be shorted to earth as the offending keys are pressed.

To correct this, methodically go through every 'b' wire of the contact while listening to sounds at 8ft pitch only. Press bottom "C" and keep it pressed; very slowly depress C# next to it, and if the sound of bottom 'C' disappears at a certain depression of C# then it means that the 'b' wire of the C# contact block furthest away from the 'a' wire must be moved. A pair of forceps helps make this a very simple operation.

Having cured C#, move on to 'D' while listening to C#, and adjust the 'b' wire for note 'D'. Carry on like this for every note on the keyboard and then start again by adjusting the 'c' wire while listening to notes at 16ft pitch. It sounds a formidable job but in actual fact is very quick and quite interesting and curiously relaxing!

OUTPUT MATCHING

The keyboard can now be screwed down via its end flanges and the end cheeks fixed into position which hide the flanges from view. It is now necessary to break the shorting links at A/A¹ and B/B¹ on the main circuit board and connect the output jack sockets as shown in Fig. 17. Before fixing the cover plate into position permanently, test the phono output by feeding from the correct jack socket to a radio tuner or ceramic cartridge input of a hi-fi system. Set the volume control of the main amplifier to the level normally used and try playing a tune. The output may be lower or higher than expected, in

which case use VR15 in the organ to set the output to match the levels normally associated with the volume setting of the hi-fi system. This action however, may cause the loudspeaker inside the organ to be either overloaded or too weak. In order to overcome this problem leave all the preset controls as they are and change the value of R29.

This can be done by reducing its value (to prevent the loudspeaker overloading when the volume control is set to maximum) by shunting it with another similar value resistor and keep reducing the value of this shunt resistor until a satisfactory state of affairs is reached. If however the output from the internal loudspeaker is too weak after all the adjustments to match the hi-fi system have been made, the value for R29 should be increased. This is achieved by carefully cutting one of R29's leads on the top side of the board and inserting another similar value resistor in-series with it.

COMPLETION

The organ is now complete and the aluminium cover plate can be screwed into position; fix the top and give the veneer a polish with good quality wax. Finally check that everything is working satisfactorily, the fine tuning, the vibrato, the keyboard splitting switches and then, if you are anything like the author, get some lessons on how to play it! Or start on another one for your neighbour!

Notes

It has been brought to our attention that the connections of certain manufacturers' 747 IC's (IC14 & IC15) do not conform to those used by the author. We therefore advise all constructors to check the positive supply to pins 9 and 13. The IC's used by the author, and the subsequent circuit board published, assumed that all 747's had pins 9 and 13 internally shorted. This is not always the case. Link pins if necessary.

H. L. Smith, 287 Edgware Road, London, W2 have agreed to supply the cover plate. Material used will be 16SWG aluminium and it will be bent and cut to size with the control slots machined out. Price is 75p or £1.06 by post. Both prices are inclusive of VAT.

Studio Electronics, PO Box 18, Harlow, Essex. Tel: 0279 416771 have informed us that they will be able to supply ready-built cabinets and all components including the keyboard, IC's and pcb's. Prices on request.

Integrated circuits, transistors and diodes are also available from Marshalls, 42 Cricklewood Broadway, London, NW2. Tel: 01-452 0161.

Another manufacturer who is willing to supply both main and power supply printed circuit boards for the Easybuild Organ is WKF Electronics, Welbeck Street, Whitwell, Worksop, Notts. Price for both boards, which are constructed from fibre glass and roller tinned is £5.50 plus 20p p & p.

For the more adventurous constructor, PW is offering a full-size paper drawing of the main PCB, showing track layout. For those who require one of these, please write, marking envelope 'Easybuild Organ' to Practical Wireless, Fleetway House, Farringdon Street, London EC4A 4AD enclosing a PO or cheque for 25p and a 10 × 8in S.A.E.

HOTLINES

ON RECENT DEVELOPMENTS

TAKE NOTE

It's getting harder and harder these days to make a dishonest living. Take forgery of banknotes as an example. In this field, electronics is making it really difficult. Onto the US scene has just come a midget bank note forgery detector—and it's hand held, too.

Far from being a leg pull, the device is quite ingenious and has certain patented ideas within it. Basically, all US notes are printed in an ink which contains certain ferrous oxides. What the detector does is to magnetize these inks as its read/write head (rather like a tape recorder's) is passed over the note. On stroking the detector back across the note again, it will immediately flash a light if the note is genuine. On its return path, the read/write head is detecting the residual magnetic field on the finely engraved lines of the money. If the light fails to flash, it's a forged note. The unit itself is less than half the size of a one dollar note, requires only a single activating button to be depressed to operate it, and it runs from a 9V battery.

ORGANITIS

Exponents and enthusiasts of the electronic organ will delight in hearing about a new IC from SGS Ates, the Italian semi-conductor manufacturer. The new chip, called an arpeggio/chord generator makes even the beginner sound like an accomplished organ player. For while he plays a simple one note melody on the top keyboard, the new IC will produce the correct chord for accompaniment and the bass notes also. So with a single note playing, you get the correct chord accompaniment and bass—all from a single chip.

Also from SGS Ates come two new rhythm generator chips. Eight instruments and twelve rhythms are offered but two of these rhythms can be used at the same time thus offering a wide variety—again from a single chip. I suppose the ultimate will be when some semiconductor manufacturer brings out a complete electronic organ on a chip; all you'll have to connect will be a keyboard and a set of tabs/switches to select voices and rhythms.

"KEEPING CHEQUE"

Talking about money (Ginsberg's favourite topic) I note with interest the launch of a "computer check book". It's not available in the UK yet but it seems a very good idea. The entire unit is about the size of a cheque book case and it quite simply keeps the balance of your bank account continually in its mind—figuratively speaking. It'll do this for about a year. The device utilises a shift register type of memory and requires very little current indeed. What a wonderful idea—just have a super overdraft and let a shift register worry about it! (Dare I suggest that this might register a shift in responsibility?).

LASER LINK

I see that yet another application has arrived for the laser. This time it's Xerox who is using in its latest facsimile (fax) machine. This is a unit which can be connected to the telephone, and documents, letters or photographs etc. can be transmitted to one of the terminal stations at the other end of the telephone link. What is remarkable is that the new copier takes only 120 seconds of line time to transmit the document. Besides employing a helium-neon laser and being very fast it has another interesting "plus". Most copiers need special paper, but this telecopier uses plain, unsensitised paper.

At the 120 second speed, resolution is around 6,200 picture elements to the square inch, but if you run at 180 seconds this can be improved on. Don't bank on having one as a toy—the price stands at around the equivalent of £3,400 although leasing one works out at £78/month plus extra charges per document sent over a certain number.

VIDEO DISC

A German manufacturer has launched a TV video disc system, which is compatible with US, French and Japanese standards. The system is currently offered for sale in West German radio and TV stores for around the £250 mark. At present, there are around 50 different records to choose from but this should increase to about 300 plus by the

end of this year. Titles include, children's programmes, education and entertainment. The records last for about 10 minutes (in colour) and cost something like £1.60p each. Perhaps, in the near future, you'll be able to see as well as hear a performance when you buy a record?

BUG FINDER

Are there bugs in your house? Not the hairy, creepy kind, the electronic sort? If there is a bug about, the new development from Britain's EMI will sniff it out. Designated Bloodhound, the device is a wide-band receiver. Most of the listening bugs around consist of an f.m. solid state transmitter with a range of a few hundred yards at best. The microphones in these devices can normally detect conversation at anything up to about 30ft.

Unfortunately for this type of bug Bloodhound's sensitive little ear-holes can listen over a very wide band—300MHz and it can soon ferret out listening devices, even those attached to telephones or mains wiring. So if something's bugging you, this could be the answer.

FOURIER CHIPS

The quest to pack more and more on a single IC chip continues. The latest to catch my eye has been one which carries out things called Fourier transformations. This is a method of analysing a signal into its many component parts and is very useful in military/security applications where one can identify a wanted signal from a masking signal etc. The new chip will perform fast Fourier transforms in a few milliseconds—something that normally takes a digital computer. Perhaps the most impressive thing is the density of packing on the device. The chip size is only a meagre 270 thou. by 350 thou. and the manufacturers have managed to pack what amounts to a 13,000 transistor capability in this tiny area. Makes that tiny transistor portable of yours that you thought was small look a bit silly doesn't it?


UPDATE

pw **YOUR**

TEXAN stereo amplifier...

IN NEXT MONTH'S

PRACTICAL WIRELESS

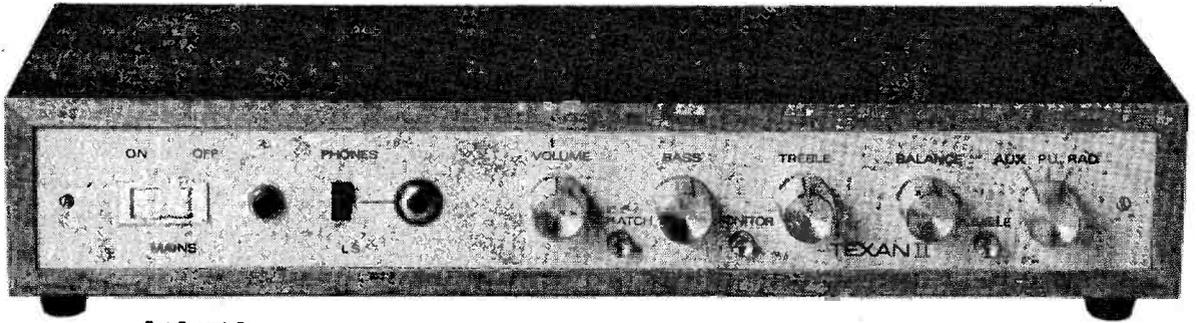

...with the

TEXAN II

Improve the performance with a few simple modifications. New toroidal-wound mains transformer gives higher power output per channel. Reduced susceptibility to mains-borne interference. Plus-optional tape monitoring facility.

VARICAP AM/FM STEREO TUNER



All electric tuner using varicaps . . . double linear phase filter IF strip . . . stereo decoder with low-pass filter and stereo beacon. Modular construction allows choice of FM or AM facilities, or both.

DON'T MISS THIS EXCITING ISSUE!

ON SALE IN JUNE

PW TELE-TENNIS SOUND EFFECTS UNIT

Five cheap ICs and a handful of components are all that you need to make this unit. Tones indicate the success, or otherwise, of your shots! A highly desirable addition to our popular game.

DIGITAL WAVEFORM

TO anyone possessing an oscilloscope, a waveform or function generator is a very useful but expensive, item of test gear. There are a number of excellent commercial instruments available, the least expensive of these being in the Heathkit range of generators. The instrument described in this article is cheaper than any of the commercially available units and gives a very useful performance. Some sacrifices have of course been necessary, but in general these do not detract from the instruments' usefulness for the majority of applications.

PERFORMANCE

The generator provides selected sine, sawtooth or square waveforms having a maximum peak amplitude of 10 volts. The calibrated frequency range is 0.1Hz to 100kHz with an additional "high" range giving useful signals up to 1MHz. An unusual feature of the instrument is the decade switching giving "period" or time, instead of frequency. If for example, the decade switches were set to a "period" of 10 μ Sec, this represents the time interval between the signal peaks. Frequency is given by the reciprocal of this period i.e. $1/10 \cdot 10^{-6} = 1/10^{-5} = 100\text{kHz}$. A period-to-frequency conversion chart will be given later. This form of presentation together with a "decimal point" using light emitting diodes (LED) makes the instrument particularly useful when employed with a modern oscilloscope. A DC shift control is also provided, capable of shifting the signal ± 5 volts. By this means the signal may be either positive going 10 volts, negative going 10 volts or symmetrical about earth ± 5 volts. An attenuator is also provided so that the signal and DC shift may be used at low levels.

Unloaded, the attenuator gives the following approximate peak voltages 10V, 2V, 1V, 200mV, 100mV, 20mV, 2mV and 1mV. Loads as low as 600 ohms can be driven with reasonable accuracy on the 1 to 20mV ranges. On the higher ranges loads must be greater than 100k Ω in order to maintain attenuator accuracy. If accuracy is unimportant the instrument will drive 2k Ω on the higher ranges and even smaller loads, less than 600 ohms, on the low ranges.

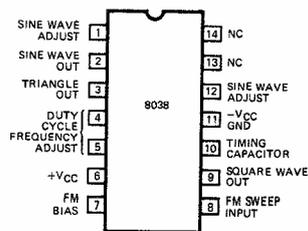
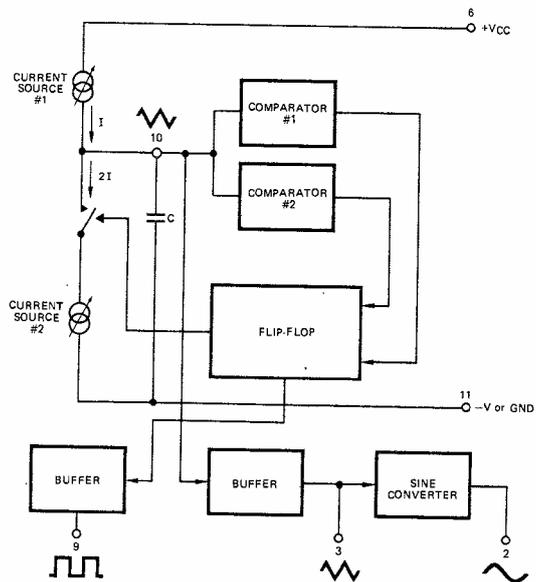


Fig. 1: Block diagram of the Intersil 8038 waveform generator IC. The lower diagram shows the pin designations.

GENERATOR

John Smith C. Eng. PART ONE

SPECIFICATION

Frequency Range:— 0.1Hz to 100kHz
100kHz to 1MHz (uncalibrated)

Waveforms:— Sine, Triangle and Square

Output:— 10V peak (attenuated to 1mV)

DC Shift:— $\pm 5V$

CIRCUIT DESIGN


The generator design is based on the Intersil 8038 IC waveform generator (see Fig. 1) capable of producing sine, square or triangular waveforms. Two types are available, the 8038CC, which is the cheaper version, and the 8038BC, which has a superior performance; another model the 8038AC has a military specification, but is rather expensive for use in this application. The 8038BC has been selected for this instrument. However, some users may be able to make do with the cheaper unit. A certain amount

of component selection is necessary to achieve the best from the circuits.

The constructor has a number of options open to him with regard to performance and simplicity thus:—

1. 8038 BC with component selection (gives maximum performance)
2. 8038 BC with components as designed (gives a reduced performance)
3. 8038 CC with component selection
4. 8038 CC without component selection
5. 8038 BC with a simplified circuit
6. 8038 CC with a simplified circuit.

The performance gets worse as one approaches option Number 6, but for those people who want waveforms, but are not particularly concerned about accuracy, then option 6 is the cheapest. Options 5 and 6 use a simplified circuit which will be dealt with in a later article.

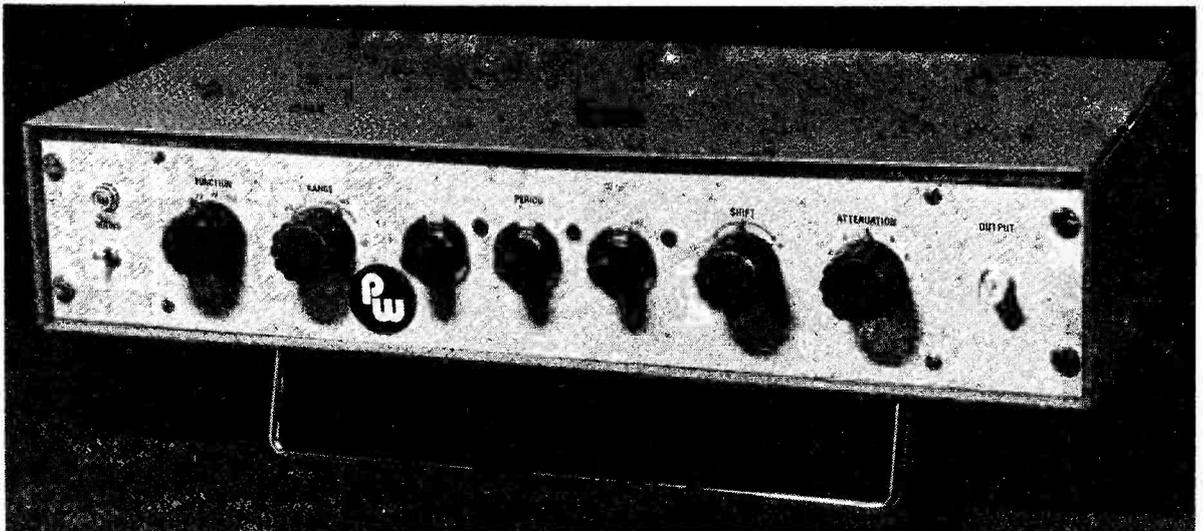

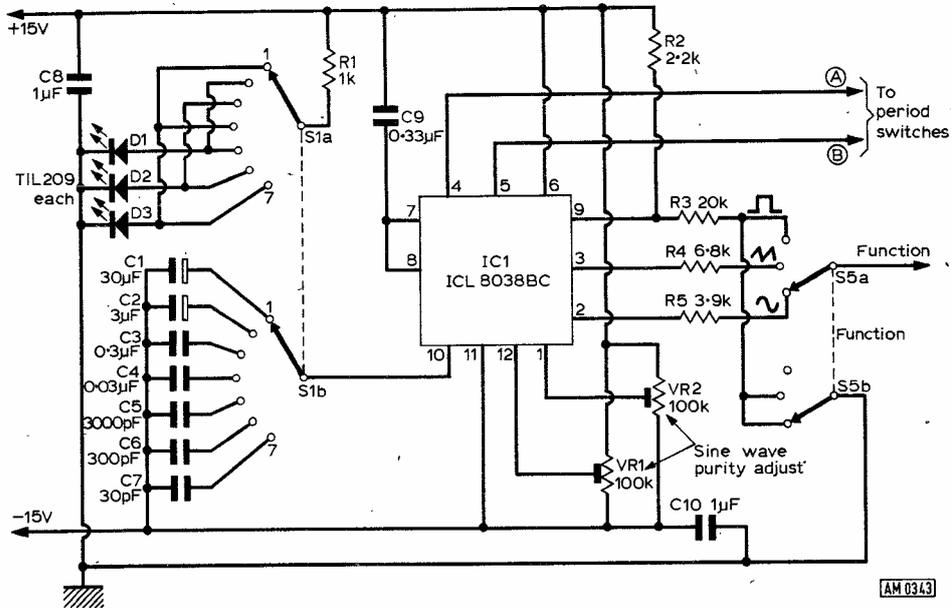


Fig. 2: Circuit diagram of the main generator section of the waveform generator. The light emitting diodes D1-D3 are the decimal point indicators on the front panel. The capacitors C1-C7 are nominal values and must be adjusted for required accuracy.

The circuit diagram is given in Figs. 2 to 5. Frequency or period range is controlled by capacitors C1 to C7 selected by switch S1a. Switch S1b operates the LED decimal point indicator. Position 1 is the seconds range where the first LED (D3) is lit. The maximum period which may be set on this range is 9.99 seconds (0.1Hz). Position 2 is calibrated in milliseconds and the last LED (D1) is lit. This means that the switches can be set to 999 milliseconds, i.e. 1Hz approximately but 1Hz can be obtained precisely on range 1 by setting the switches to 1.00 seconds. However, in practice this fine distinction is outside

the capability of the instrument. The period adjustment is carried out on switches S2 to S4 connected to pins 4 and 5 of the 8038 (Fig. 3).

Capacitors C8 and C9 are decoupling components which must be mounted close to the IC for optimum performance. R1 is a current limit resistor for the light emitting diodes and may be reduced in value to give more current in the diodes if necessary. R2 is a load for the 8038 whilst R3 to R5 set the voltage levels for each of the output waveforms. VR1 and VR2 are used to adjust the purity of the sine wave output. C10 is a decoupling capacitor

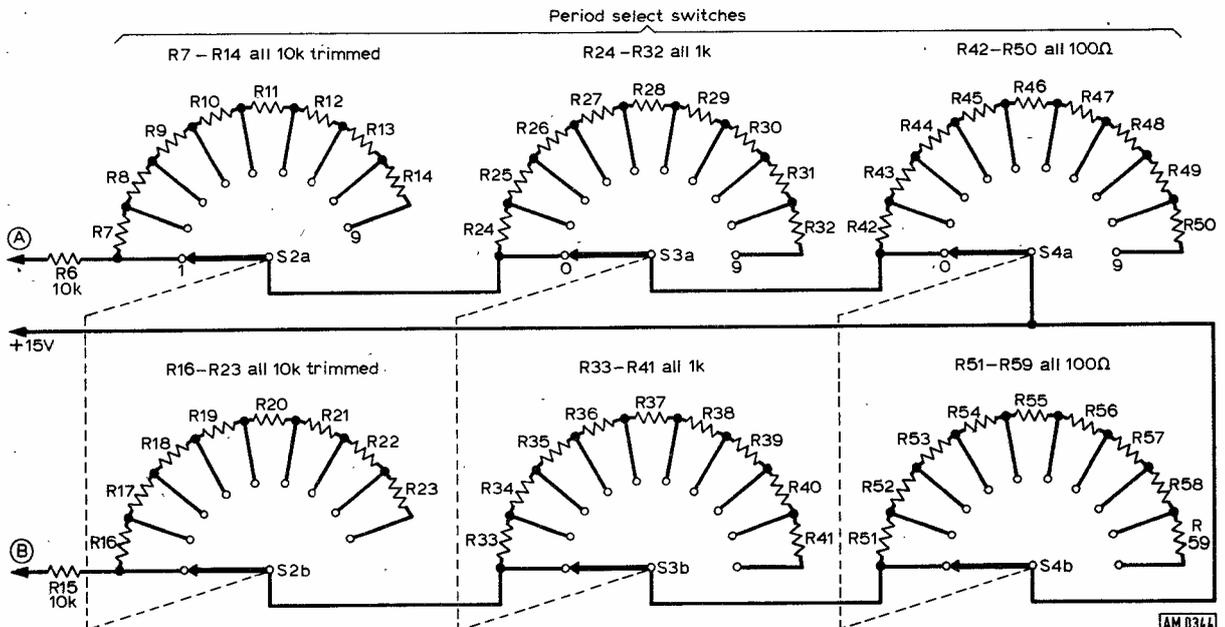


Fig. 3: Wiring of the three period select switches. These allow period to be varied over a range of 1000 to 1.

★ components list

Resistors

R1	1 kΩ	R65	1kΩ
R2	2-2kΩ	R66	6-8kΩ
R3	20kΩ	R67	2-4kΩ
R4	6-8kΩ	R68	2-4kΩ trim
R5	3-9kΩ	R69	2kΩ
R6	10kΩ	R70	200Ω
R7-R14	10kΩ	R71	8kΩ (4-7k + 3-3k)
R15	10kΩ	R72	1kΩ
R16-R23	10kΩ	R73	800Ω (470 + 330)
R24-R32	1kΩ	R74	100Ω
R33-R41	1kΩ	R75	80Ω (47 + 33)
R42-R50	100Ω	R76	10Ω
R51-R59	100Ω	R77	8Ω (4-7 + 3-3)
R60	6-8kΩ	R78	1Ω
R61	10kΩ	R79	1Ω
R62	4-7kΩ	R80	1-2Ω } 2-5W wire-wound
R63	560Ω	R81	1-2Ω }
R64	110Ω		

All ± 2% 1/4W unless otherwise stated
 VR1, VR2 100kΩ preset (2 off)
 VR3 100Ω preset
 VR4 1kΩ carbon

Capacitors

C1	30μF 25V	C10	1μF
C2	3μF	C11	10pF
C3	0-3μF	C12	1000pF
C4	0-03μF	C13	1000μF 50V elect.
C5	3000pF	C14	0-22μF 50V
C6	300pF	C15	100μF 25V elect.
C7	30pF	C16	1000μF 50V elect.
C8	1μF	C17	0-22μF 50V
C9	0-33μF	C18	100μF 25V elect.

Capacitors and resistors marked "trim" are nominal values and should be trimmed to working values using the method to be described in the text.

Semiconductors

IC1	8038BC (see text)
IC2, IC3	MVR15V (RS)
D1-D3	TIL209 light emitting diode (3 off)
D4, D5	REC76 (RS) or similar 200V, 2A bridge rectifier (2 off)
Tr1-Tr3	BC184 (3 off)
Tr4	BC214

Switches

S1	2 pole 7 way	S5	2 pole 3 way
S2	2 pole 9 way	S6	1 pole 9 way
S3	2 pole 10 way	S7	Double pole mains switch
S4	2 pole 10 way		

Miscellaneous

T1	Mains primary, 0-20V 0-20V 30mA secondary (RS)
LP1	Mains neon indicator
Sk1	BNC socket

Instrument case 432 x 200 x 88mm (RS type 4) with tilt bail (RS type D), knobs 28mm (4 off), Knobs 14-5 mm (3 off), Veroboard 0-1in matrix 330 x 70mm (13 x 2 1/2 in), 80mm 4BA studding (4 off), 25mm stand-off (4 off), finned heatsink 50 x 50 mm (2 x 2 in) (2 off), capacitor clips, 14 pins DIL socket.

Note

Please note that RS Components will not supply direct to the public, but components can be ordered from them through a retailer. The MVR15V, case, REC76 and transformer are available from Doram, PO Box TR8, Wellington Road Industrial Estate Wellington Bridge, Leeds LS12 2UF. Order numbers are 305-399, 509-620, 261-592, 196-319 respectively (see catalogue). Switches S1 to S6 can be made from RS Makaswitch components. The 8038 is available from Ambit, Technomatic or Trampus.

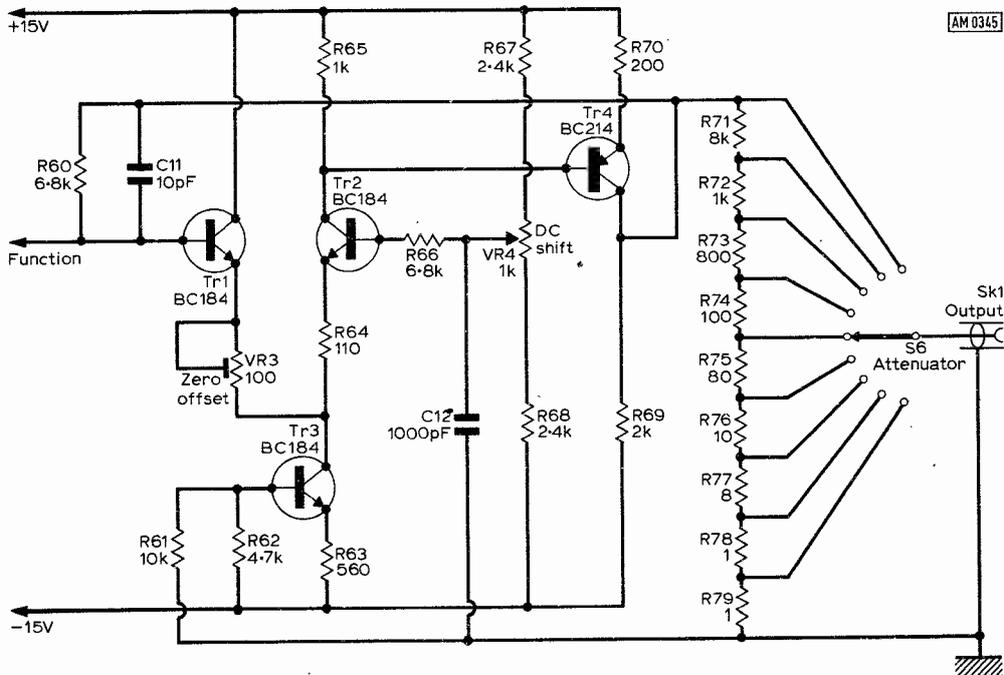


Fig. 4: Circuit diagram of the differential amplifier used in the waveform generator to give up to 10V peak output.

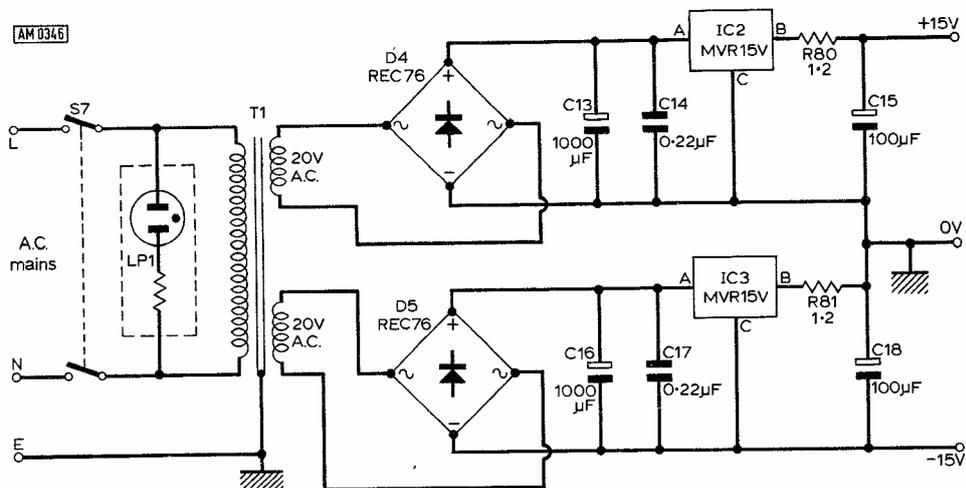


Fig. 5: Circuit diagram of the power supply which gives the required +15 and -15V supply rails.

which must also be mounted close to the 8038. C1 to C7, R3 to R5, R6 to R23 are marked for selection. These are the components which must be adjusted to obtain the highest accuracy of options 1 and 3.

The three output waveforms from the 8038 function generator are fed via S5 to a differential amplifier (Fig. 4). S5b is necessary to short the pulse waveform to earth when the sine or triangular waveform is selected. This prevents the pulse interfering with these two functions through the switch stray capacitance. If possible, a large, low capacity switch should be employed in this position together with another pole to short the triangle waveform to earth when the generator is switched to sine operation.


The differential amplifier Tr1, Tr2, Tr3 couples the selected waveform to Tr4, an emitter follower output stage. Tr1 and Tr2 form the differential amplifier proper with feedback in the emitter and a constant current "tail" formed by Tr3. VR3 is used

to adjust the calibration of the DC shift potentiometer VR4 at zero. A small portion of the output signal is fed back to the input of Tr1 via R60. C11 is a stabilising capacitor. Emitter follower Tr4 is coupled to a simple output attenuator which is capable of driving the loads already specified.

POWER SUPPLY

The power supply (Fig. 5) uses a transformer having two 20 volt windings. DC is obtained from bridge rectifiers D4 and D5 smoothed by 1000 μ F capacitors C13 and C16. The DC voltage from the two capacitors is applied to voltage regulators contained in a TO5 package IC2 and IC3. C14, C15, C17, C18, R80 and R81 are stabilising components which prevent the regulators from oscillating.

To be continued

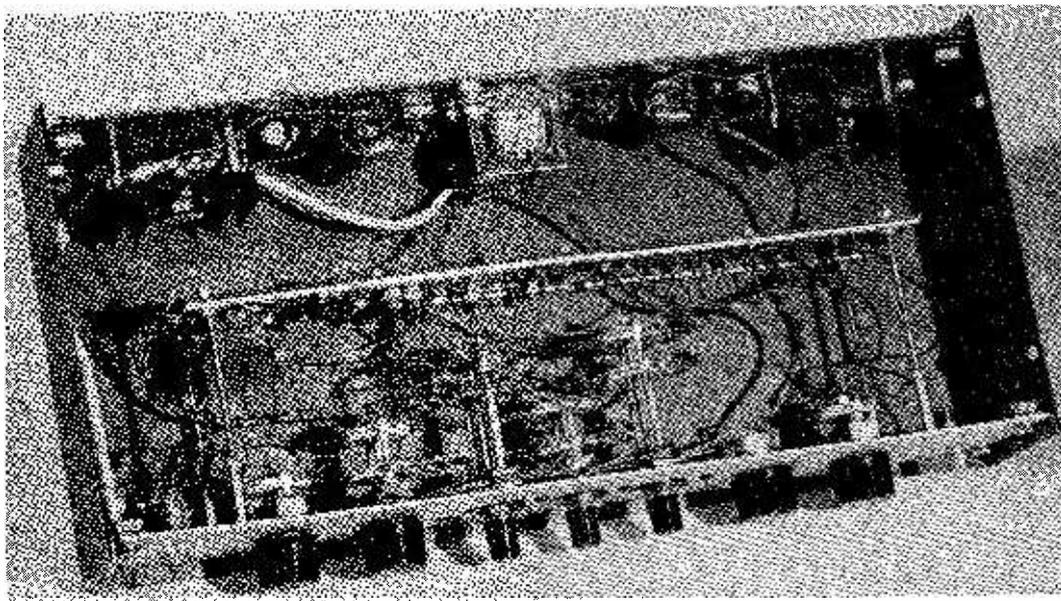

The completed waveform generator with the top cover plate removed to show the disposition of the components within the case. The power supply is built on the back panel and the rest of the generator on the long panel in the centre of the case.

Pw APOLLO series

Part 2

TRIPLE VARICAP BIASING METHODS : SWEEP OSCILLATOR TECHNIQUES

W. POEL *

HAVING introduced the two new Motorola diodes for AM tuning in Part 1, this month's feature examines and explores the possibilities and potential that this breakthrough in price represents for the art of radio and electronics in general.

BIASING TECHNIQUES

Both the new diodes, the MVAM1 and MVAM2, employ a negative voltage to perform the tuning function, so with the almost universal adoption of negative earth circuitry techniques, this presents a few problems.

A solution is proposed in Fig. 2.1 which shows how a 27V bias can be used to keep the varicap reverse biased as the tuning voltage is varied from 0V to 25V. Until such time as the manufacture of a diode for direct negative earth applications is completed, this method is the best compromise.

The +27 volts still have to be found from somewhere in the circuit. In mains equipment, this will be another tapping on the transformer—or possibly a simpler arrangement via a voltage doubler from the main winding. In battery portable equipment, the only solution is a separate battery supply, or a DC to DC converter.

* Ambit International

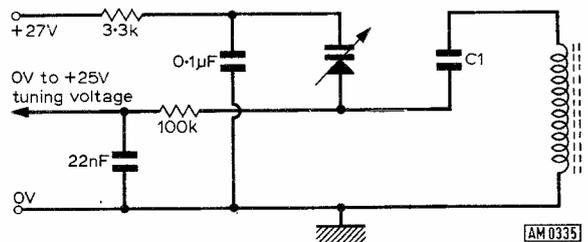


Fig. 2.1: By using a separate 27V bias voltage the common cathode varicap diode can be tuned using a variable voltage from 0 to 25V.

DC TO DC CONVERTER

In the application of tuning a varactor, there is little actual current required, apart from that required to operate the voltage stabilisation circuitry. The principle is simple. An AC voltage is derived from an oscillator, and this can then be transformed up to the required level, and rectified with the earth in any sense that may be required.

The preferred means of deriving the AC in this type of application is with a sinewave oscillator. Square wave circuits will inevitably radiate many harmonics that will probably interfere with the AM radio, and nonetheless, the sinewave oscillator should be carefully screened to prevent unwanted radiation occurring.

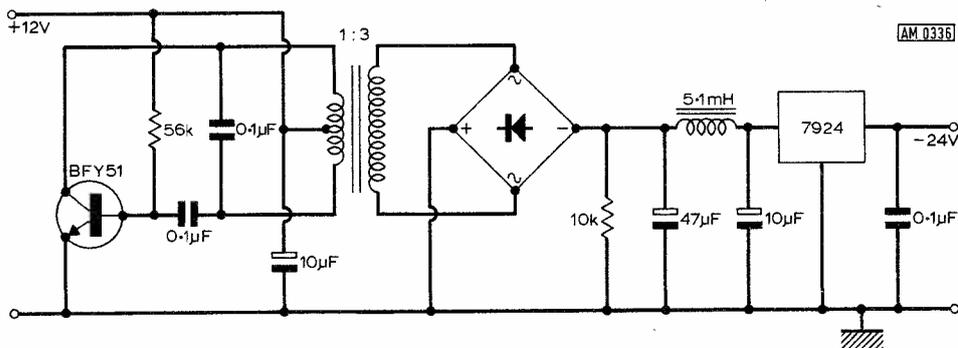


Fig. 2.2: A generalised circuit diagram for an inverter to give -24V from a +12V source. The 12V is fed to a one transistor oscillator, the resultant A.C. is then rectified and regulated.

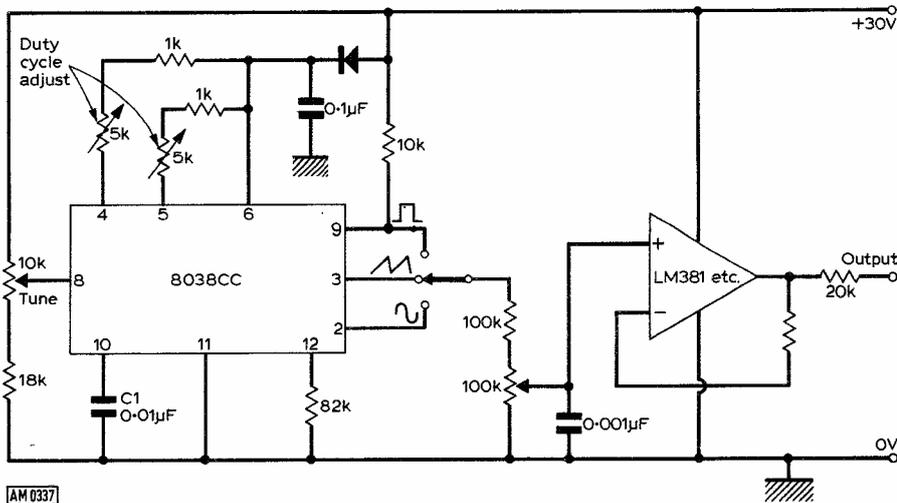


Fig. 2.3 The 8038CC can be used as a simple square wave generator. The output can be amplified by an I.C. amplifier such as the LM381 to give a sweep of the required amplitude.

A general circuit is shown in Fig. 2.2, employing just a single transistor and inverter inductor. The turns ratio of the primary to secondary will determine the voltage step up—so from 12V to 36V, 1 to 3 is necessary.

The output from this inverter is carefully decoupled and filtered to prevent any residual remains of the AC signal being present by the time the voltage gets to the tuning diodes.

The inductor used can be of the bobbin, pot core or iron cored variety, but should be suitable for operation at the selected frequency of the inverter. Iron cored inductors may not be suited to frequencies above 20kHz.

The current that can be taken from the circuit will depend on the rating of the inductor—the overall efficiency for such a configuration is in the region of 40 to 50 per cent, given the correct components.

For simplicity, the method of voltage stabilisation is the three terminal 7924 (24V fixed negative regulator). A cheaper alternative can no doubt be devised using a Zener diode and a resistor, but the 7924 maintains better stability and has a far greater degree of supply rejection.

SQUARE LAW

When biasing any single varicap in the radio frequency circuit, remember that the law of the tuned circuit scale will be the "square law", so to obtain a scale of uniform linearity, the potentiometer should have an inverse square law.

Such a potentiometer is not presently widely available, but it is anticipated that a special long slider will be available with this feature designed specifically for radio tuning applications.

The two trimmers at the extremities of the main tuning pot are an important feature when aligning the scale. Although the various tuning diodes in the same package are matched to one another to a close degree of tolerance, this is not necessarily so between different samples.

It is also wise to remember that the lowest value of the tuning voltage should not be permitted to fall below two or three volts. This is because there is a chance that the oscillator circuit in the receiver will have an RF voltage that could exceed the total

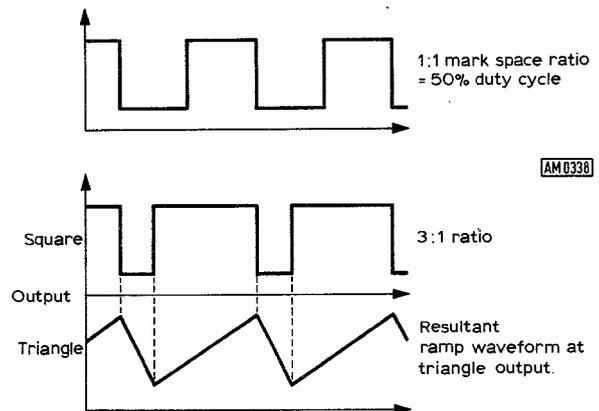



Fig. 2.3b: Waveforms associated with the circuit of Fig. 2.3. The upper waveform is that appearing at pin 9 when the duty cycle is adjusted to 50%. With a 3:1 mark space ratio (75% duty cycle) the waveforms at pins 9 and 3 appear as shown.

reverse bias on the diode tuning it. The result is that the oscillator RF gets rectified, and ceases to function at low frequencies with various audible manifestations of the instability. This can also be the case with an RF stage that is handling a very high level signal—this may become rectified, and will then modulate the supply to the other diodes on the same tuning bias supply.


OTHER APPLICATIONS AND FACILITIES

Anywhere that one uses a conventional variable capacitor of the mechanical variety, the varicap can be used for greater layout flexibility.

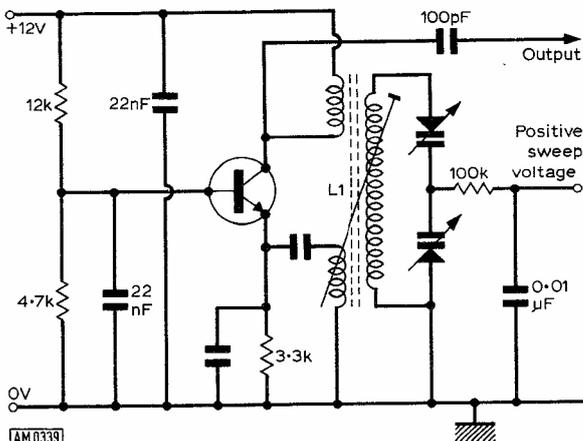There are a couple of qualifications, based on the effect of strong signals becoming rectified by the diodes; so the devices would not, for instance, be suited to transmitter power circuitry; but in test gear, they certainly have many applications.



AM 0339
 Fig. 2.4: The circuit diagram for a basic wobbulator or voltage controlled oscillator. The sweep voltage is used to vary the capacitance of the varicaps and hence the tuned frequency of the one transistor oscillator.

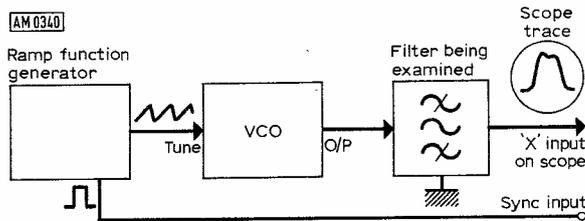

AM 0340
 Fig. 2.5: The ramp generator of Fig. 2.3 and the VCO of Fig. 2.4 can be combined as shown in order to display the response characteristics of a tuned circuit.

SWEEP OSCILLATORS

Sweep oscillators are used extensively for radio tuned circuit alignment, and are known under various guises as panoramic adapters, wobbulators, spectrum analysers, etc. They all employ the same basic principle, namely that an RF oscillator is varied in frequency in synchronism with an oscilloscope trace.

The circuit under test is fed with the output of the oscillator and the performance of the tuned circuit is then assessed by the visible display of the amplitude response. Fig. 2.3 details a simple form of sweep voltage generator, and in conjunction with the oscillator of Fig. 2.4 a basic wobbulator is formed. Fig. 2.5 shows how this combination is used in conjunction with an oscilloscope for displaying the response characteristics of a tuned circuit.

SWEEP GENERATOR

The 8038 function generator IC is used to provide the basic waveform generation. It is a fascinating device in its own right, in that the single chip provides triangle, square and sine wave outputs simultaneously with a fixed phase relationship.

The duty cycle (Fig. 2.3b) can be simply adjusted with the potentiometers on pins four and five, and the actual frequency of the sweep is again set by a potentiometer.

As an audio oscillator, the 8038 can be swept by up to 1000:1 by the application of a suitable sweep voltage at pin 8. However, the sweep voltage is basically a low duty cycle triangle wave—or ramp voltage and the amplitude of this, direct from the chip is approximately one third of the supply voltage.

With a 30V supply, this gives 10 volts, so to increase this, an operational amplifier is employed to amplify to around 28V peak to peak.

The values shown on the circuit allow the frequency of sweep to be varied from 20Hz to 20kHz. By switching additional capacitance across the timing capacitor at pin 10 the frequency can be lowered, though to fully appreciate the capability of the 8038, reference should be made to the very comprehensive manufacturer's data sheet.

The square wave output from the 8038 can then be employed as the trigger for the oscilloscope time-base, to ensure that the sweep voltage and the trace start simultaneously.

SCAN WIDTH SELECTION


Applying the whole voltage to the varicap diodes will result in a very large sweep being achieved—but this is not the only factor, since it is desirable to be able to select a specific area of the spectrum for examination. Fig. 2.6 shows how this is accomplished by simply adding the sweep voltage into the main tuning voltage. This technique is often employed in VHF varicap tuners, where it is desirable to be able to control all the tuned circuits at once, rather than just the local oscillator.

Adjusting the amplitude of the sweep voltage will vary the width of the scan. Remember that the sense (polarity) of the tuning voltage for the single ended MVAM diodes should be considered when testing equipment, as separate power supplies may need to be employed.

EXISTING RECEIVERS

It is a relatively simple matter to append the spectrum analyser feature to an existing receiver design by simply adding the MVAM diodes across the various sections of the tuning capacitor. The scale linearity of the main receiver will suffer—but if used in conjunction with a signal generator to provide marker reference points, the result will be fascinating at least, and probably very useful as well.

By monitoring the diode voltage at the detector, one will obtain a frequency/amplitude plot on the oscilloscope trace—giving a visible display of signals present within the swept part of the band, as shown in Fig. 2.7.

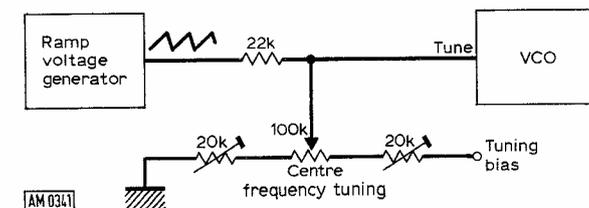

AM 0361
 Fig. 2.6: To investigate a specific area of the spectrum the sweep voltage is added to the main tuning voltage. Adjusting the amplitude of the sweep voltage will vary the width of the scan.

continued on page 158

PRODUCTION LINES

colin riches

RADIO CONTROL COMPONENTS

Home Radio inform us that they can supply the following components for the Radio Control Monitor: VC1 (Cat. No. VC26D); TC1 (Cat. No. VC62); PHF3 coil (Cat. No. CO84C); OA90 (Cat. No. OA90); C1-0.047 μ F (Cat. No. 2CN155); 3.5mm jack socket (Cat. No. JH18) and 100 Microamp meter (Cat. No. TG76). Total price including post, packing and VAT is £5.88 — Home Radio (Components) Ltd., 234-240 London Road, Mitcham, Surrey.


INSTRUMENT CASES

Arbour Electronics Limited have sent us details of their 'Centurion' instrument cases. The two shown in our picture are the 222F and 321F.


Model 222F (left) comes packed flat. The front and rear panels are of aluminium and the case of mild steel. The front panel is finished in white gloss and the other sections in blue hammer stove enamel. Price of the 222F (197 x 254 x 159mm) is £3.40 plus VAT (postage paid).

Model 321F (203 x 406 x 165mm) has an aluminium front panel. The case and rear panel are of mild steel. The front panel is finished in white gloss and the other sections are a black 'crackle' finish. This cabinet is finished with top and bottom aluminium trim. Price of the 321F is £5.80 plus VAT post paid.

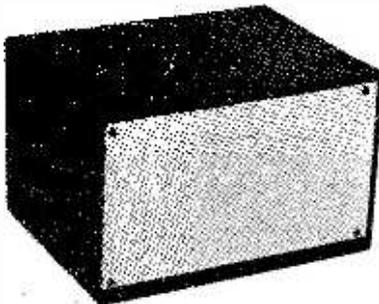Further information on these instrument cases or the sheet metal work service run by Arbour, contact them at Unit 13, East Hanningfield Industrial Estate, Nr. Chelmsford, Essex. Tel. Chelmsford (0245) 400700.




TRIMMER POTS

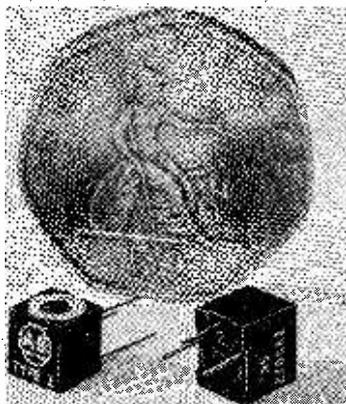

The Allen Bradley single trim type Z trimmer potentiometer is ideal for use in miniature equipment for it only measures a 6.35mm cube.

Power rating is 0.5W at 70°C and terminations are by pins with the option of vertical or horizontal mounting. High power rating is achieved by cermet technology in the 50 Ω to 1M Ω range.

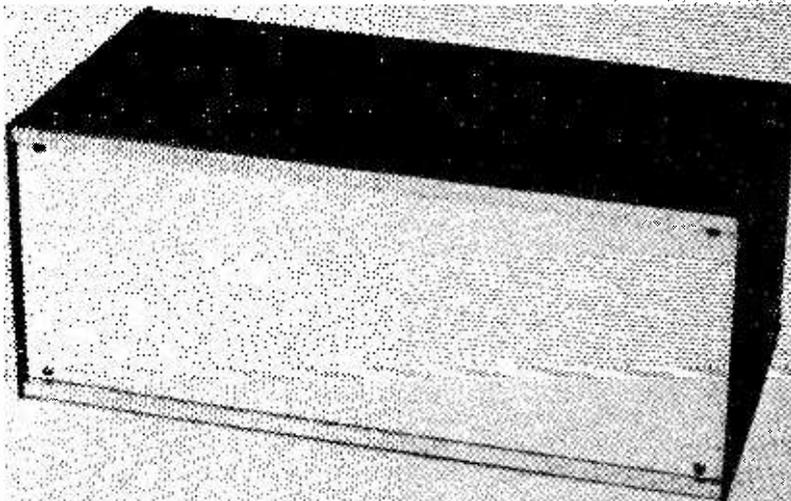Both vertical and horizontal types are available in 10% tolerance (price 95p each for 25 off) ex-stock from Jermyn Industries, 74 Vestry Estate, Sevenoaks, Kent.



TELE-TENNIS REPRINTS


These are still available from:

Chief Cashier (P.W. Tele-Tennis) IPC Magazines, Tower House, Southampton St., WC2E 9QX. Price is 75p + 7p postage.

THE DANAMETER

Dana Electronics have developed a "personal" volt-ohmmeter which features a 3½-digit liquid crystal display. A single 9V transistor radio battery will last a year with normal use.

Sixteen ranges are available on the switch: four each of d.c. volts, a.c. volts, d.c. current and ohms. Both a.c. and d.c. volts scales are 2, 20, 200 and 1kV; d.c. current is measured from 20 μ A through 2mA, 200mA to 2A, and ohms from 200 through 20k Ω , 2M Ω to 200M Ω . Reading accuracies vary from $\pm(0.5\%$ of reading + 0.05% of range) (2V d.c. range) to $\pm(8\%$ of reading + 0.05% of range) (200M Ω range). When 'd.c. volts' is selected the input resistance is 10M Ω , and the impedance for a.c. volts is 2M Ω . Switch

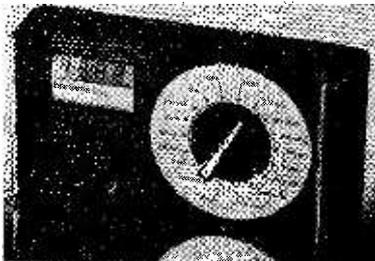

position 17 is for internal battery checks, and position 18 is 'Off'.

The Danameter costs £99.50. Further information may be obtained from Dana Electronics Ltd., Collingdon Street, Luton, Beds.

LARSHOLT VHF TUNERSET

The constructor who feels that making a VHF receiver is a bit too complicated a venture will welcome the Larsholt "TunerSet" made by Larsen and Hoedholt in Denmark. It will also appeal to the experienced constructor who may not have too much spare time on his hands.

This elegant and well-constructed unit is only 168 x 65 x 25mm (6 $\frac{5}{8}$ x 2 $\frac{1}{2}$ x 1in.) with clearly numbered pins for connecting to the external circuitry. The input accommodates 75 or 300 Ω feeders and provides around 330mV of audio at medium impedance at the output with signals greater than 2 μ V. Gate-protected 40822 and 40823 MOSFET'S are used in the RF and mixer stages and a BF224 in the local oscillator. All three stages are varicap tuned by an external stabilised voltage which can be fed into the unit by the conventional push-button panel. A voltage from 2.3 to 12 volts will provide a frequency range from 87.5 to 104.5 MHz. The recommended stabilised main supply is 20 volts, taking 65mA.

The signal at the usual IF of 10.7MHz passes through a double ceramic filter to a CA3089E limiting stage and an LM3900 IC. Quadrature detection, muting and AFC facilities are provided. Two sections of the LM3900 are unused and their input and output connections brought out to pins so that they can be used as additional audio amplifiers. With stereo, the audio output signal can be routed via an external decoder IC, such as the CA3090AQ or MC1310 or KB4400, the two channels then being fed back to the two spare sections of the LM3900 for further amplification.

Simple external circuits connected to the appropriate pins will provide a signal strength meter, centre-zero

tuning meter as well as muting and AFC switching. A frequency scaled meter can be linked to the varicap tuning voltage if desired.

The technical specification adequately meets today's requirements and a first-class receiver can be quickly built around the TunerSet. The accompanying technical literature is clear and provides all the necessary information to accomplish this. Indeed, the frills can be left to later and the tuner made to work initially with just the 20V power supply and a couple of PP3 batteries across a potentiometer for the tuning voltage, the output being fed into some audio amplifier such as a Hi-fi set-up. All necessary tuning and alignment points are clearly marked but it is suggested that these be left alone until the final alignment when the finished receiver is working properly.

Full information on the TunerSet can be had from *Ambit International*, 37a High Street, Brentwood, Essex.

RIVLIN POT.

Rivlin for many years have been known for their quality precision wirewound resistors and resistive standards.

The new Rivlin Type WS150 potentiometer is developed from experience gained during the last 2 years of producing a 60mm Carbon Slide Potentiometer, which has been much praised for its price and technical merit.

This latest pot is the first of their WS range and features a wirewound 50k Ω , 150mm track, of near professional standards. It is being used in our P.W. "Apollo" m.w. tuner/receiver featured in P.W. This component is intended to satisfy a need in the Audio and lighting industry where a linearity of 0.1% and resolution of 0.03% are required. Further developments in the range will incorporate varying track lengths as market dictates. For further information, please send a stamped addressed envelope to: *Rivlin Instruments Ltd., Dept. P.W., Doman Road, Camberley, Surrey GU15 3DJ.*



HAVE TOOLS—WILL TRAVEL

The Link-MK service engineer's cabinet and tool case is a neatly adapted standard small-parts cabinet. It comprises a Link-MK cabinet containing four sizes of transparent drawer in various combinations, together with a wooden tray for larger tools, all housed in a lockable simulated leather carrying case.

When open, the rigid front of the case folds down to make a convenient platform for tools. All the drawers can be subdivided to hold large or small items (an assortment of dividers is supplied) and each drawer has a label slot.

The cabinet, measuring 15in x 12 $\frac{1}{2}$ in x 8in, is intended to meet the needs of both professional service engineers and hobbyists of all sorts, from DIY enthusiasts to modellers and photographers.

It is obtainable from storage specialists at a recommended price of £14.80 plus VAT. Names of local stockists will be provided by the manufacturers on request. *Link-Hampson Ltd., Bone Lane, Newbury, Berkshire.*



ELECTRONI-KITS

Electroni-kit, the UK distributor for Denshi Block Mfg. Co. Ltd., tell us that they can supply the SR Series of educational electronics kits.



The one shown in our photograph is the SR-3A de-luxe kit from which one can build 105 projects including things like a solar-battery-operated transistor radio, three-transistor intercom, amplifiers, electronic sirens, metronomes, organs, etc., etc.

These kits are very good for youngsters to learn the basic elements of radio and electronics for all components plug into a circuit board. No soldering is needed. For further information and prices write to *Electroni-kit, 408 St. John's Street, London EC1B 1LJ.*

Repairing HI-FI AMPLIFIERS

H. LEEMING G3LLL

IN the "good old days" of valve equipment it was quite surprising what one could get away with, and many engineers who really hadn't much idea what was going on, managed to execute quite successful repairs by trial and error. As we shall see, this kind of approach with directly-coupled transistorised equipment can do far more harm than good, and it is hoped that this article will, at the very least, indicate to readers how not to repair equipment! Let us imagine that an amplifier has blown its fuse and has come in for service. How does Fred, the bodger, tackle the job?

First, Fred replaces the fuse which immediately blows again, to give himself a chance to find the fault he fits a larger fuse! Noting that this also blows he decides to check the output transistors on a tester and sure enough, one of them seems faulty. Fred swops the transistor, switches on, and blows another fuse! Fred next decides to isolate the two channels, and so disconnects the supply voltage from the left hand one, and sure enough the right hand channel functions satisfactorily without the destruction of any more fuses. Fred is now convinced that one of the output transistors is still faulty, but just to prove the point he decides to swop over the power amplifier boards which, fortunately, plug in. Soon the amplifier works on neither channel, blows mains as well as low voltage fuses, and so, in desperation, Fred sends the amplifier back to the manufacturers.

When the bill arrives, Fred's customer finds that he has to pay for eight transistors, four rectifier diodes, a mains transformer and several sundry parts which, together with Fred's time, and carriage amounts to over £30. Fred assures the customer that it wasn't his fault as the amplifier had so many faulty components that he just hadn't a chance! What went wrong?

WRONG APPROACH

In the first place Fred made a totally wrong approach to the job. Transistorised amplifiers, unlike their valve counterparts, are invariably directly-coupled devices, and this really does throw a spanner in the "lucky dip" type of approach to servicing, as faults in one stage can often damage components, as well as affecting voltages, in other stages. In the case in question, the only original fault could well have been incorrect quiescent current brought about

by the setting of VR1 in Fig. 1 or that one of the transistors was faulty. The fuse had blown to protect the equipment, and the real trouble did not start until a larger fuse was fitted. With Tr8 and Tr9 incorrectly biased the supply current surged up blowing all the output and driver transistors.

As the circuit boards do not include the output transistors, swopping the boards around connected a good board to a faulty pair of output transistors and a faulty board to a good pair of output transistors. This resulted in another collection of blown components. In the end, so much current was drawn that the rectifier went short-circuit taking the mains transformer with it. We might well laugh at Fred's approach, but how does one go about tracing faults in transistorised equipment?

REGAINING SUPPLY VOLTAGE

With a transistorised amplifier that blows fuses, one has a real problem, as, without power, not many meaningful tests can be made. Simple faults, such as the mains rectifier or smoothing capacitor being short circuited will blow the mains fuse and can be found by ohmmeter tests. But faults causing excessive current to be drawn in the amplifier section do not usually respond to such a simple approach. The first problems when dealing with a case of a blown LT fuse, is to get the amplifier into some kind of working order without destroying more components in the process. There are two possible answers here.

1. Restrict the voltage applied to the equipment.
2. Restrict the maximum LT current possible.

In the first approach the amplifier is connected to a supply derived from a variable voltage transformer or Variac with a milliammeter connected in place of the LT fuse. The amplifier is switched on with the applied volts at zero, this is then gradually increased until the meter measures, say, 100mA. This method works quite well, but does not protect the amplifier or the test meter against any sudden avalanche of current, should the amplifier suddenly break down at some particular applied voltage. This method also ties up a valuable meter and necessitates the use of a variable AC supply which might not always be available.

The second approach, shown in Fig. 1 is the best one. Here a resistor RX is used to replace the LT fuse, its value being calculated so that under short-circuit conditions the possible current is limited to

a safe value. The value of the resistor is not particularly critical and if a resistor of around 250Ω is fitted this will ensure that under conditions of even a dead short, the current will not exceed a few hundred milliamps. Note that under short-circuit conditions the resistor could get hot so it should be rated at 10 or 20W depending upon the supply voltage. Having connected the resistor, the amplifier can be switched on safely and under fault conditions, only a small voltage will appear at point Y (if the amplifier was not faulty the voltage at point Y, with the amplifier drawing only its standing current, would only be a few volts below normal). Having got a small voltage at point Y it is now possible to do a little fault tracing, and to find out just where the excessive current is going.

The first point to ascertain is which channel is the faulty one, and under low voltage conditions this might not be at all obvious, as sometimes the channel which appears to have the queerest voltages turns out to be the good one! The certain way to tell where the current is going, is to disconnect the LT supply separately from each channel; but sometimes a quick dodge is to feel the temperature of the transistors, as the warmest ones will usually be those which are passing most current.

FAULT TRACING

Having got the amplifier into some sort of operating condition and established which channel is faulty we are ready to apply some logical fault tracing techniques—or are we? Practice shows that the slowest way to trace faults in a transistorised directly-coupled power amplifier is to try and trace them logically! A few shots in the dark are very well worthwhile.

The first items to test are the output transistors and, if in doubt, checks on these made by an ohmmeter or a simple transistor tester should be compared against tests made on known good samples. Silicon output transistors should show no noticeable leakage, but often good germanium transistors will register quite high leakage. With amplifiers where it is possible to swap over the circuit boards, it is very simple to tell whether the fault is in the board or the output transistors by swapping them over, but in this case ensure that RX is fitted and not a fuse. One point to note here is that confusion can be caused if, as quite frequently happens, in addition to there being a faulty output transistor there is also a fault on the driver board.

Presuming that the output transistors are found to be in good condition, or are made so, but that the amplifier still tries to draw excessive current, the next components in order of their likelihood of being faulty are; Tr8, Tr9, Tr6, Tr7 and C34. This order seems to apply to all of the many transistorised amplifiers which use circuit arrangements similar to that shown in Fig. 1 and in 95% of cases the fault will lie in one of these components. If the fault does not appear to be due to a transistor or an output capacitor, a considerable amount of time may have to be spent tracking it down, remembering all the time to try and separate cause from effect. In the case of amplifiers where the driver boards containing all the power amplifier components, with the exception of the output transistors, are removable, it might be advisable to swap the whole board. If it is necessary

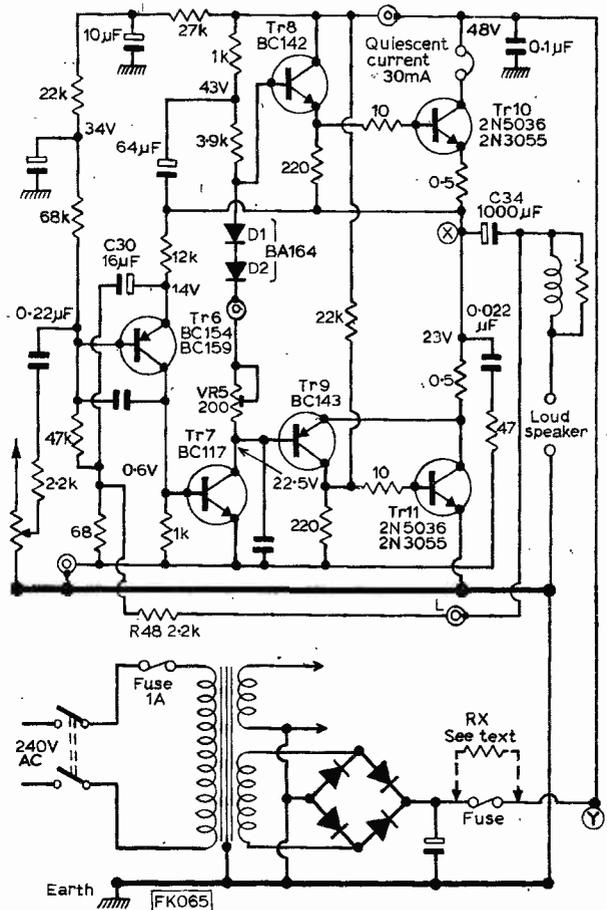


Fig. 1: Output stage of a typical hi-fi amplifier, showing component values and theoretical voltages.

to trace the trouble without outside help, here are a few tips which may be of use:—

1. When things are working correctly, the output stage current is determined by the difference between the base voltages of Tr8 and Tr9. This, in turn, is controlled by the voltage drop across D1, D2 and VR5. D1/D2 stabilize the voltage, whilst VR5 adjusts it to the correct value depending upon the current through Tr7. If any fault occurs which tends to increase the voltage between the bases of Tr8, Tr9, such as an open-circuit diode or potentiometer, this will result in excessive current.
2. In a correctly functioning stage using NPN silicon transistors, the base will always be about 0.6V more positive than the emitter (using PNP transistors the voltage will be about the same but negative, whilst germanium transistors will be found to have about 0.1V between base and emitter). More voltage than this indicates that the transistors base/emitter junction is open circuit, whilst less voltage indicates that there is insufficient bias.
3. The amplifier's DC stabilisation will be completely upset by the low supply voltage which is applied under test conditions. In these circumstances it is no use at all trying to scale down voltage readings from those given in the service manual, and any voltage checks in a stereo amplifier should be made by comparison with the known good channel.

LOW OUTPUT AND DISTORTION

Having discussed the faults which can cause excessive current to flow let us now have a look at other troubles which can occur. In a normally operating amplifier point X should be at about half the LT supply voltage, and any departure by more than, say, 10% from this indicates trouble. Such a departure from the correct voltage would usually result in low output or audible distortion, and when trying to track down such troubles, checking the centre voltage between the output transistors is one of the first tests that should be made. In many amplifiers this voltage is adjusted by a pre-set potentiometer in the base circuit of Tr6, while others use self-stabilising circuits. In either case, the trouble can be caused by almost any component and checking through from the output transistors backwards, as previously suggested, is as good an approach as any.

If low output or excessive distortion in the power amplifier section occurs without any apparent centre voltage deviation, it is quite possible that there is a lack of quiescent current and this should be checked and re-set if necessary by adjusting VR5, or its equivalent, according to the makers' instructions. When checking quiescent current it is wise to solder a resistor of about ten times the milliammeter's internal resistance across the measurement point; otherwise, should the test leads drop off, or the meter cut-out blow, Tr8 will be destroyed as it will try to take over the work of the output transistor.

If, upon checking, the standing current is found to be too low or non-existent but is not adjustable, the fault will possibly lie in either D1 or D2 being short-circuit, as, whilst there are exceptions, a faulty transistor will usually upset the centre voltage reading.

OTHER FAULTS

Up to now we have confined ourselves to looking at DC faults in the directly-coupled power amplifier section, as this type of trouble is exclusive to transistorised equipment. More normal "valve type" faults occur however, and there is no reason why some unwanted effect should not turn out to be an open-circuit capacitor or a resistor "gone high". To be fair, such faults are rare and 95% of troubles in the power amplifier section are of such a nature that they affect the DC operating conditions.

"What is the trouble with my amplifier?" asked our customers. "Oh, it will be either the output transistors, the input transistor, or somewhere in between," replied our service engineer, and believe it or not, he was right! This may sound a little facetious, but just as the output transistors are the most failure-prone devices in the power amplifier section, so the input transistors are the most troublesome component in the pre-amplifier section. Lack of gain, or distortion, in the input stage can usually be traced by simple voltage checks, once again noting the magic figure of 0.6V which should appear between base and emitter on any amplifier using modern silicon devices. Whilst measuring this voltage do not forget to allow for the loading effect of the test meter, as the base voltage of an input transistor, which should be 4V for instance, would be wildly out if an attempt was made to measure it using the 5V range of a 1000 Ω /V test meter.

Hissing or spluttering is invariably caused by noisy

transistors and the offender can often be found by the application of a little heat or cold, and a marked change in the level of the noise will normally result if the offending transistor is approached with the tip of a soldering iron or is squirted with aerosol freezing fluid. In any case, if in doubt about the goodness of a transistor, substitution is the final test.

REPLACEMENT TRANSISTORS

Many transistors are basically very similar, different types being picked out by a selection process during production. The BC109 for instance, is guaranteed to have high gain and low noise, but the makers do not guarantee a very high voltage rating. The BC107 however has a guaranteed higher voltage rating but does not claim as good a noise or gain performance. These characteristics are guaranteed for the sake of users who want a transistor which they know will work without the need for further tests.

In workshop practice for instance, by carrying only the BC109 in stock, it is quite possible to select individual transistors that will replace the BC107, the BC108 or the BC109, or for that matter nearly any other NPN small signal transistor. The gain of transistors can be checked to sufficient accuracy with quite cheap transistor checkers. As well as voltage and gain ratings the power rating of transistors also has to be taken into account, but to some extent this can be judged from physical size. In a service department almost all faulty small-signal silicon audio transistors end up being replaced by a BC109!!


Output and driver transistors come in a multitude of shapes, and sizes but many are interchangeable. If an NPN silicon output transistor is required for an amplifier which is rated at 30W and which has a 60V supply rail, it is almost certain that another NPN output transistor which is the same physical size, and which is used in another makers' 45W amplifier with a 70V rail, will be a more than adequate replacement. Likewise the driver transistors of the larger amplifier can more than likely be used quite successfully with the smaller amplifier.

This approach of using transistors which exceed the specification of the original items fitted might seem extravagant, as it entails fitting a more expensive replacement. It does, however, much reduce delay and the number of parts carried in stock, and in the end it makes sound economics, even where it is felt desirable to replace both output or driver transistors to ensure a matched pair, instead of waiting weeks or months whilst a reluctant maker deems to deliver replacements.

FINAL TESTS

As a final check, all amplifiers should preferably be checked to their original specification for power output and distortion and should also be checked with an oscilloscope for performance on square waves. If, due to lack of the requisite test equipment, this is not possible, a fairly reliable comparison test can be made using a mono signal. This is fed into both channels of the amplifier and set to balance each other out by carefully adjusting the balance and tone controls. Any distortion existing in one channel alone will not balance out, and, if excessive, will indicate that further attention is required.

GOING BACK...

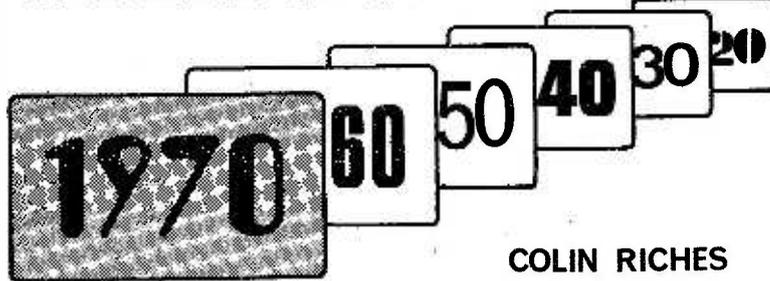

The Fultograph

ANGUS Kennedy, who is aged 12½ and lives in Ludlow, Shropshire, recently sent me a cutting from a 1928 newspaper and asks if anyone can advise on a machine called the "Fultograph".

If any other readers can help us out on this one—information, a picture of a built unit or anything, we shall be pleased to mention it in "Going Back".

The newspaper item is entitled "Forecasting the Fultograph—Pictures to be broadcast" and is described as the "wonderful new feature of the BBC transmissions".

Readers were told that extraordinary interest was attached to the then recent announcement by the British Broadcasting Corporation of their plans for the prospective broadcasting of pictures. A new and more entertaining type of programme was to be expected and wireless would be afforded a fresh and entirely new dimension. News pictures of events within a few hours of their happening, illustrations of childrens' stories, latest Paris fashions, winning race horses, football favourites, weather charts, portraits of missing people—these were but a few of the possible subjects that could be transmitted—not only from

COLIN RICHES

English stations but some of the more powerful continental stations.

The Fultograph was described as being "not only for the wealthy few". By the cheapness of the apparatus, pictures by wireless would be at the disposal of a vast majority of wireless owners in England to whom its utter simplicity would appeal. It only had to be connected to any ordinary wireless set capable of working a loudspeaker and it operated automatically, requiring no tuning, no additional batteries and no more current than for one ordinary valve. In roughly three minutes the complete picture would be reproduced on specially-prepared paper and just to watch it evolve would be not the least fascinating feature of the device. On the paper's removal from the instrument no fixing or developing by photographic means would be required.

The Fultograph system was described as being used by the British Broadcasting Corporation and was an invention perfected only after years of research and experiment. Long before 1928 a less-effective instrument could have been put on the market but it was decided to wait until the device described had been fully perfected.

The apparatus was to have

been marketed by Wireless Pictures (1928) Limited. It was obviously some form of facsimile machine which would have been available to everyone and was, basically an exceedingly good idea. It was probably dropped because of the development of the television receiver but—does anyone know the inside story on the "Fultograph"? We would be very pleased to hear from you if you do.

Wireless Museum


THE Vintage Wireless Museum of the Wireless Preservation Society has been transferred from South Lincolnshire to the Isle of Wight, and is to be established in Arretton Manor, which is open to visitors throughout the year. It is the Home of Count and Countess Slade de Pomeroy, and already houses a folk museum and exhibition of domestic and agricultural by-gones, many of which were collected on the Island. There is also a superb collection of dolls, dolls' houses and toys of past ages.


The Wireless Preservation Society was established some three years ago, and is exclusively devoted to the collection, preservation and restoration of wireless, electronic and sound reproducing equipment, including television receivers, for purely cultural, educational and historical purposes. It is an entirely non-profit-making organisation, and all its officers are honorary.

The Hon/secretary and curator, Mr. Douglas Byrne, G3KPO, is now living at No. 32 Luccombe Road, Shanklin, IOW (Tel. 098-386 2586), from whom further information can be obtained.

Revolution?

GOING back through my photographic files the other week I came across this Mullard photograph, released back in the '60's. Its caption reads: "The Trons are forced to retreat as they are overwhelmed by armies of Semicons". It is very interesting to see how their photographer envisaged the transistor "revolution". I am sure however, that amongst our Going Back readers there are many thousands that feel the valve will live for ever!

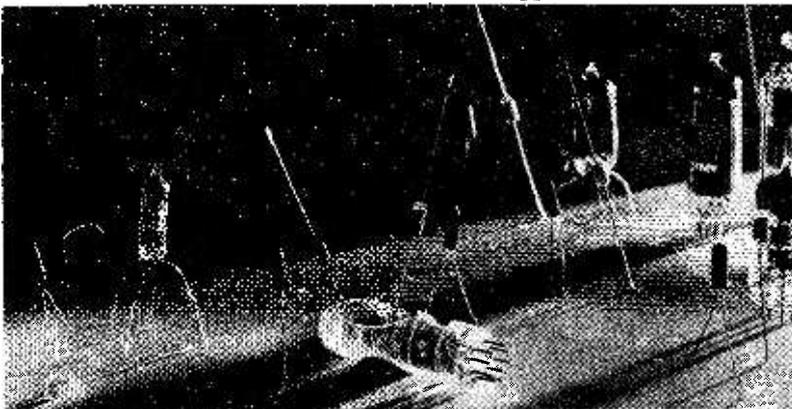

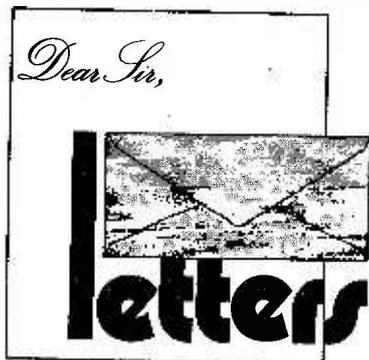

The Law is an Ass!

The law which states that the public must not listen to certain wavelengths or use the dial pointer over certain parts of the radio scale is as ludicrous as it is archaic; and is typical the backward thinking of British politicians as was the law requiring a man carrying a red flag to walk in front of every motor car. Further to your Editorials in the March and April issues, I feel it is not the public nor the small print that needs to be looked at, but the Law; this unrealistic aspect of it should be rescinded, and the sooner the better!

I draw the distinction, however, between the use of the air and the use of on-the-spot "bugging" devices for the surreptitious eavesdroppings of private conversations. This is quite a different matter and should be prohibited out of common respect and decency, backed (so far as necessary) by law.

But the air should be free whether we breathe it or listen to it (at any frequency).

Those who are brave enough to preach democracy should be brave enough to practise it.—**Peter W. Feese** (London)

Naughty!!

I would be grateful if you could let me know if it is possible to convert a pocket transistor radio to receive Public Service Transmissions.

I would be quite content if the conversion meant that I would receive PST only.—**J. Bonnar** (Scotland)

Sorry this is just not on. You have not been reading my recent editorials!—Ed.

Designers—take note

As a reader of PW for the past 25 years, I would like to say how excellent your magazine is, and to further state how pleased I am that you have kept to the sensible "zig-zag" sign for resistors instead of the "oblong box" symbol of foreign origins. In particular I'm grateful for new equipment designs using IC's and varicap tuning.

May I however, make a plea, and beg for an article which deals with a varicap-tuned, digital frequency readout communication receiver, covering frequencies from 10kHz to 30MHz. Also a digital readout frequency meter, covering the range 10kHz to 30MHz and 30MHz to 100MHz.

Preferably the RF, Osc., and IF stages of the 10kHz to 30MHz communications receiver should have FET's of MOS FET's, and should be able to receive NBFM, SSB and CW. Sensitivity should be at least $1\mu\text{V}$ for 50mW output on all ranges. Power should be derived from a 12V source to enable the set to be completely portable.

The equipment that I have just described costs "a bomb" if bought commercially, so surely PW could publish a design that would enable the home constructor to build one, at a fraction of the cost of the ready-made article.—**G. B. Corry** (West London)

PW in Parliament?

In a recent letter to my MP (Neil Macfarlane—Sutton and Cheam) regarding the continual erosion of individual liberty, I cited the Home Office's deplorable behaviour in sending letters to editors as reported in your March editorial. My MP, in reply, said he had not seen a copy of the letters sent, and asked for a sight of one if I wished him to take the matter up with the Home Secretary.

As this is a clear case of a Govt. Dept. misusing an Act of Parliament and trying to limit individual rights I would ask if you are prepared to supply a copy of the letter in question for me to pass on to my MP.

I have already put it to him that the Home Office is a totally unsuitable Dept. to overlook communications and that in any event the Act in question should

be repealed or amended as it attempts to deny an undeniable human right to receive magnetic waves—radio frequencies being no different from light and heat from the sun.

It is up to those who desire secrecy to apply that little extra to obtain it by coding or scrambling.—**SM Sugden** (Surrey)

Whose kidding who!

We at the Gullibalivsky Institute of Leggapullov are dismayed at the pirating of our research work, as described in your April issue. The device was invented by us and we called it a "Bogatron". It was not envisaged by us to be used at radio-frequency, (which is testimony to its versatility), but at extremely low frequencies, barely above D.C.

At these frequencies of about 5 cycles per day, it was enormously successful in flushing out phonies. (Would you like to buy a couple?)—**George W. Spray** (Isle of Wight)

From the many enquiries on the Unitron article (April issue), it would appear that many readers enjoyed the joke—Ed.

Problem solved!

I was interested to read in the March 1975 issue of your magazine an article on building a Sinclair Scientific Calculator. In the last paragraph the author says "On the other hand the most annoying omission is a "clear last entry" key. Having to repeat a lengthy calculation because you push a wrong button can be very frustrating." Well, fret no more! I bought one of these calculators, ready-built I am ashamed to say, and have also found the lack of this particular key annoying. So I worked out this key sequence to effect the same operation.

Example Say we wish to multiply 1.2345 by 6.7890 and we accidentally key in 6.7990 then we can clear this number by keying E, -, 9, 9, + this has the effect of adding 6.7990×10^{-99} to 1.2345 which gives 1.2345, then key in the correct value and continue the calculation.

I hope you, and all other Sinclair Scientific users will find this useful.—**W. S. McBriar** (Cambridge)

Illegal sales

Having read your magazine for many years, I can't recall anyone writing to you regarding "public enemy No 1"—the imported walkie-talkie. I'm sure every reader knows that these sets are illegal, yet a walk up the Edgware Road will show a selection of these sets on display to the general public. Granted most have written in the sales literature, in small print, "not licensable in the UK", but I was horrified when I visited a well known shop and overheard the sales chat of one of the salesmen.

He was telling a potential customer of a walkie-talkie set, costing in excess of £50, that it would be virtually impossible to trace the signal due to the high density of the buildings in London.

This of course it utter rubbish, as with todays sophisticated tracing equipment, it wouldn't pose much of a problem for the GPO. The salesman further went on to explain, that in the event of a "10,000 to one" chance of being traced he would probably be ticked-off or suffer a maximum £5 fine. Unfortunately the salesman neglected to say that his £50 worth of equipment would also be confiscated.

In my opinion the law should be changed, so that it would be illegal to sell any transmitting device, without first obtaining proof that the buyer has a licence to use the set in question, and that the set conforms with the regulations.—**D. Lane** (London)

Think negatively

Having constructed the PW electronic ignition circuit, published June 1971, and successfully used it on two Ford Escort cars in the last 2½ years, I've found one fault in the system—and this is due to the car manufacturers! What happens if a positively earthed vehicle is changed for a negatively earthed one? Is the ignition circuit obsolete?

In my particular case, the vehicle earthing did change, as above, which necessitated only four alterations to the circuitry. These were to remove the supply from the transformer centre tap, and transfer it to the link connecting the collectors of Tr1 & 2 to R2/R3. An earth was then placed on the transformer centre tap; D5 was removed altogether,

and D4 reversed, so that its anode was connected to R7/R6. Finally, Tr1 and Tr2 were insulated from the chassis.—**C. A. Emms** (Suffolk).

Attention Hoarders!

We are trying to assemble a small collection of old electrical equipment, mainly radios, record players, etc. As we rely on donations, we have so far been limited to equipment no more than 40 years old. If anyone in the Belfast area has any old, unused, or damaged equipment (the condition is immaterial) we would be very glad to hear from him.

There are two particular items for which we are looking: an old valve portable radio (with DF91 and similar valves), and an old "Cat's Whisker" crystal set.—**C. J. Steenson** (Annedale Grammar School, Belfast).

Wake-up, Home Office

Having been a reader of *P.W.* for over 20 years I have gained a lot of knowledge and enjoyment from it. But the time has come when I can no longer restrain myself from writing to your columns for the very first time.

Your editorial article in the March '75 issue really makes one wonder. When will the powers that be, i.e., the Home Office, wake up from their 1900 era of thinking and acting? Where, might I ask them, can the public obtain a copy of the Terms, Provisions and Limitations, that we must abide by since a licence to use a radio receiver for the reception of Wireless Telegraphy is no longer required?

No doubt the Home Office would point out, if a situation arose that required taking a person to court for breach of Section 5 of the "Wireless Telegraphy Act, 1949", that ignorance of the law does not exempt a person from being prosecuted under it! Even if, and it is a big **IF**, the public had access to the aforesaid mentioned Act, etc., how many would actually read it, and further, how many would really digest it or understand it?

Like most small print in any document it is written in a pedantic style of wording, appropriate to the year 1900. Again, I wonder how many people have read Clause 4 of the Television Broadcast Receiving Licence, and of those who have read it, how many have understood it? Especially as

it refers to "messages" unintentionally received. What about "visual images?"

With reference to no licence being required for a radio receiver, again I think the powers that be are doing the BBC a grave injustice in taking money away from them; they say that more money is lost collecting a licence fee than is gained. What a ridiculous statement, have they not got any brains, or are they just too lazy to use them?—**H. H. Berry** (Cheshire).

Unavailable licence?

Your editorials on walkie-talkies etc were long overdue. For years this equipment has been sold without restraint, aided and abetted more recently by the Home Office who seem to have insisted that advertisers add a note that such equipment needs a licence for use in the UK or, even more ludicrous, that a licence is required but is not generally available to the public!

The advertisers must be laughing their heads off! Tell everyone that it will be illegal to listen to such-and-such transmissions on their XYY Superset and they'll rush round in their hundreds to buy one! Surely the answer is simple, no licence, no sale!—**A. Smith** (Romford, Essex).

Modified or not?

I am writing in response to your editorial in the March edition—regarding the Home Office claim that it is illegal to listen to private communication channels under Section 5 of the Wireless Telegraphy Act.

I am quite sure that this Act was modified at the time FM broadcasting by the BBC was introduced on VHF; purely because breakthrough was inevitable and it was not possible not to hear Public Service Transmissions.

I think Barlow on TV was correct in his statement that it was not illegal to listen to Public Service Broadcasts because I am sure the modified section of the Wireless Telegraphy Act made it, not illegal to listen, but illegal to **act on, or pass on** any information received in this way.

Unfortunately, I cannot put a date on this modification but I am sure it happened and I would welcome any comment from legal advisers.—**D. H. Myers G8AYG** (Cheshire).



by Eric Dowdeswell G4AR

LET'S give a big cheer this month to regular correspondent **Tim Charles** (Colchester) who has heard New Zealand on Top Band! That's just about the ultimate in DX'ing, combining maximum distance with the lowest of our HF band allocations. Tim was aroused by the activity of many G stations around the DX 'window' of 1825 to 1835kHz at 0647 on 9 March last. He tuned up to 1872, the usual frequency for ZL's, and heard ZL3RB calling CQ DX although he was only RST 349 and disappeared in a couple of minutes. It is not known if any positive QSO's resulted but now is the time to try, as we approach the bottom of the sunspot cycle.

Tim suggests, and I think correctly, that G2PU worked a ZL about 12 years ago when we were around the bottom of the last cycle. With the improvements in technique which have been made by Top Band enthusiasts over the last few seasons I should not be surprised to hear of several QSO's being made with ZL in the near future. Let's hope that Tim can now get a QSL from ZL3RB. That would be something really worth having on the wall of the shack!

While in the southern hemisphere I should mention an interesting letter received from **David Down** in Christies Beach, South Australia. An ex-Royal Australian Navy operator David sticks to CW. He has taken his examination for a licence so he ought to be on the air very soon now. His list of stations heard on 7, 14 and 21MHz does not contain any G's, unfortunately, seemingly due to the unfavourable times that he has been listening, as far as G operation is concerned. I have asked him to keep a lookout for Europeans on 160m!

John Porter (Baslow Derbys) and family got a bit fed up with tripping over radio equipment scattered around the house so he moved it into an outside shack where I am sure he will be very happy! He was able to get his 10, 15 and 20m dipoles connected to his FR50B without any difficulties. He was pleased to copy KC4USG/MM2 on 14MHz SSB. This is the US icebreaker Glacier which itself was trapped in thick ice in the Antarctic, after damaging a propeller. On 10 March the Daily Express reported that the scientists and crew aboard the Glacier had been flown out. **Andrew Swiffin** (Cheadle) was kind enough to send me details of his crystal-controlled converter mentioned last month. It first appeared in QST and uses a 6AK5 RF stage with another 6AK5 as mixer. A 6J6 double triode uses a single crystal on 6.2 or 8.3MHz, or thereabouts, harmonics being selected according to the band required. It is very versatile when used in front of a general coverage receiver.

A brief letter from **Tom Proctor**, aged 16, who lives in Bristol and uses a No. 19 set on which he copies SSB signals. No mean achievement with that equipment! **Michael Connolly** (Yeovil) joins the column for the first time, using a CR70A and PR40 and a dipole on 80m. He can also copy on 2m with a Sentinel converter fed from a halo aerial in the loft. **Gary Edge** (Culcheth, Warrington) stuck to 80m SSB like so many others, using his 9R59DS and 150ft wire plus a whip aerial. A PS says 'have sold my 9R5 and bought an HA500'. We all hope you will both be very happy!

Paul Barker (Sunderland) comes up with yet another VE oddity! CY6GQ special event station in Calgary, work ten CY6's for an award. Well, don't just sit there, go and get those CY6's! **Ian Moore** aged 14 has got a head start on most of you. His Dad is G3JQJ ex-DL2WM and he allows Ian to use the receiver part of his treasured FT200 provided Ian learns the Morse Code. What a clever Dad! But watch out Dad 'cos once Ian has his ticket you won't be able to get near your FT200!

Old friend **David Saul** A8723 hopes to leave us by the end of the year! He takes his RAE in May and looks forward to a nice new G4+3 call sign. We hate to lose you OM but sincerely hope you make it. **David Coupe** (Nr Middlesborough) joins us and says his main interest is 2m using a Microwave Modules converter into an Eddystone 888A at 28-30MHz. Input comes from a six element Yagi at about 22ft. A good clear path to the north has enabled him to hear many GM's on SSB with the odd ON and PA0 to the south. He has also logged many stations through Oscar 7.

Malcolm Sole (Lancaster) reports a quiet month but still managed good catches like ST2AY and KG4FO Guantanamo Bay on 80m SSB. **Ron Newall** (Richmond Sy) joins the column with a first log of stuff heard on 160 and 80m, presumably SSB. There can't be that number of stations still using double sideband and carrier! I deliberately omitted to say 'AM' because the statement would have been incorrect! It is quite surprising how many amateurs, and others, who talk and write about SSB and AM as if they were two completely different methods of modulation. They are both amplitude modulation or AM! It's just that SSB is the result of conventional 'AM' losing one sideband and its carrier. The methods of generation are quite different of course but that is another matter. I am surprised that those who still use the old style of AM do not incorporate all the refinements which have developed around SSB such as VOX, restricted audio bandwidth etc. There is no reason why they should be thought of as being peculiar to SSB.

Stephen Terry BRS35669 (Banbury) kept his log to the real goodies and a nice lot they are too, from 15 to 80m using his FR50B and a dipole fed 'off-centre'. Watch your matching OM, the impedance rises rapidly away from the centre and if you are using low impedance cable you could be losing some of the signal voltage developed on the aerial. Stephen doesn't say which band the dipole is cut for so it is probably rather ineffective on the other bands anyway. **Alan Doherty** (Portrush Co. Antrim) just beat the deadline with a log that concentrates on his favourite band, 20m, again with an FR50B fed from a 132ft aerial. One early morning stint was rewarded with KC6PS, quite a rare prefix.

Log extracts

J. Porter:— 80m HP4HCU TG8AU 20m CE8AA KC4USG/MM2 (see text) KV4AA ZD8TM ZS2PR (Marion Is) 15m 5L2JJR (Liberia)

A. Swiffin:— 80m FG7AO PZ1AP UI8MV VP2DM 20m KL7IEU TA2SC VS5LH ZS3TP 15m CE6EZ OA4O VP2A (Antigua) VP2EEE (Anguilla)

T. Charles:— 160m VE1BCZ ZL3RB (see text) 80m HP1CWP VP2DAJ YB2AU ZL1AHI ZL3FZ ZL4FB 40m CO2SM VK7CH ZL1BN ZL2AGY 20m CR4BS TR8VE VP2LAW ZS3DO 2m via Oscar 7 from 70cm DJ2IF DJ2RE DL1JV ON4DY

M. Bennett:— 20m CP1OY CR3AH P29MI 15m JY9CR VS9MB ZS4MZ

M. Connolly:— 80m CT2AE P11VKL 20m CR4BS TU2FG ZD7SD 8P6BU

G. Edge:— 80m EP2VJ M1I TZ1AC YB0ABV ZS5LB 7X5AH

S. Budd:— 20m C5AU (Gambia) TA1BW VQ9MC 15m VQ9HCS (Astove Is)

P. Barker:— 40m VU2AIK 20m FL8DN PJ2RC Z29FV VP2VBG 5T5GS

I. Moore:— 20m HR1KS VQ9DC 40m VP2A

D. Saul:— 80m EA8CR VP2AC VP2DM VP2KX VP2MDB (VP Club Net) 20m ET3USE FLOJN FP8DH TR8BJ


D. Coupe:— 20m HH2FW VQ9NB 2m via Oscar 7 DJ9DL F9FJ LA1FH OE2CAL PA0GCA plus W2 W6 W8 and W0.

M. Sole:— 80m A9XH (Bahrein) KG4FO ST2AY UA9VH/JT1 (Ulan Bator) ZL2BT 8Q6AB (Maldiva Is) 40m HI8XKP VK7DJ

S. Terry:— 80m VQ9M ZL3PX 8Q6AB 9M2DQ 20m C5AR VP8NP ZD7SD 5T5CJ 15m EA9AQ ZP5WM 7P8AT

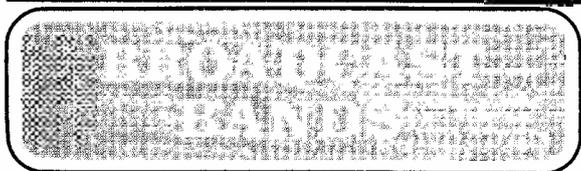A. Doherty:— 80m HS5ABD VU2GDG 20m C5AR FY0BHI HR3JJR KC6PS P29CW VP5GT VQ9HCS VQ9MC YS1JWD 5L2FW

All stations are SSB except those in bold which are CW.



SHORT WAVE BROADCASTS

by Derek Bell

SEVERAL letters recently improved me for referring to a megahertz when I should have said kilohertz. This was in the item on using 300,000 to find wavelength or frequency. The answer I offer is that MHz has long been preferred to describe frequencies, so that instead of saying "five thousand kilohertz" we say "five megahertz" while for values under one megahertz the frequency is referred to in kilohertz.

Recently I asked for info on DX shows, in order to compile a list for you. I am glad to say that shoals of letters arrived giving not only days and times but four or five frequencies for each station. This is because of the practice of many stations of putting out signals on several frequencies at the same time. This posed an insoluble problem, namely which frequency would be audible here on any given day? Last year was, it is agreed, one of the worst years in memory for the short wave DXer, due to solar storms. So which frequency do I select when there is every chance that it may be blotted out by noise or that it may not be carrying DX at all?

In order to get round this I selected one frequency and one alternate and the list is as follows:—

Mondays	Japan	1640	11815	5990
	Norway	0810	11850	15175
Tuesdays	Finland	1800	9550	11755
	Hungary	1615	21505	17890
Wednesdays	Prague	1900	7245	7345
	S. Africa	2226	11970	7270
Thursdays	Holland	1842	6085	6020
	Bonaire	0045	11815	—
Fridays	Bulgaria	1930	6070	9700
	Rumania	1930	6150	7225
Saturdays	Israel	2030	9395	9495
	Monaco	0920	7230	9640
Sundays	Lisbon	0935	9670	—
	Austria	0915	9770	—

The first set of figures, that is the time, is the advertised start of transmission and you will realise that the DX shows are slotted into the session for a particular target area and that this session may be of an hour or so duration. The second set, the frequencies, are those in English, since some stations repeat the show in more than one language. My thanks go to among others, Messrs Mead, Chowanietz, James and Forkin for taking the trouble to help me compile the list. There are of course other stations that do DX shows, for instance BBCs World Service, that are crowded out through space problems, but your World Radio and TV Handbook will give more information on these.

John Godwin of Rugeley sends some detailed information for the new European service of Radio Sri Lanka. This starts every evening at 1900 on 15120 and 11800 and comprises talks, requests and news and John says that for a QSL the DXer should write to:—

English Services
Sri Lanka Broadcasting Corp.
PO Box 1510
Colombo, Sri Lanka

We have at last lured into the column one of the licensed amateur operators. Part of the condition of the amateur ticket is the right to listen to time-signal stations and G. F. Painter G3CFO sends a comprehensive list of unusual stations that he has heard. One in particular, LOL Buenos Aires, "popped up", as Mr. Painter puts it, on 5MHz while he was doing something irrelevant to the rig, at his house in Chipping Norton.

John Haines has his rig in the living room with his aerial made of five feet of cable suspended from the curtain rail. This and the Heathkit SW717G he runs brought in Radio Nacional de Brazil on 11780 at 2135, John Higginbotham of Holyhead, however, goes in for a fifty foot long wire in the loft and has an ITT Euromarine dangling on the end of it. John has been fortunate enough to pull in

Voice of Nigeria on 7275 at 1530
Radio Norway on 9590 at 1300
RSA on 11900 at 2100

John hopes to take possession shortly of an ex-RAF 1132A. This is a fine example of the full coverage ex-service set that can be bought very reasonably, if you are lucky. The trouble is that there are so very few



of them ever come on the market! From the charming town of High Wycombe **Terry Gilbert** sends a logging of a very rarely reported station, Radio Afghanistan on 15195 at 1130. This goodie was pulled in via a Codar CR70A and Joystick, coupled to a Hamgear preselector ATU. Terry very kindly says that this column gets read first in PW and wonders if anyone can fill him in on the Heathkit GR78, as he is looking for a set to take on holiday (*We shall be reviewing this kit in the July PW-Ed.*)

The other month I featured a set bought in a jumble sale, but this month one that was actually given away because it apparently did not work! This happy event happened to **J. Sharmen** of London

MEDIUM WAVE DX

by **CHARLES MOLLOY**

F. WILDMAN (Bournemouth) has been trying the medium waves with his Codar CR70 and 75ft outdoor aerial. He reports excellent reception of WINS New York City on 1010kHz at 2345 on the 4th March, both Hilversum on 1007kHz and Mainz/Wolfheim on 1016kHz having signed-off at 2300 to leave a clear space for the North American. Another outlet in NYC—WNEW on 1130 kHz—was logged on the 7th March at 0620. Reception was very good with occasional interference from Brussels on 1124kHz, and lasted until 0650 which was well past daybreak.

Fred Dinning pulled-in a good bag of Canadians at his QTH at Dunlop in Scotland using a Hammerlund SP600 and medium wave loop. DX logged includes VOXM St John's Newfoundland on 590kHz; CKCM Grand Falls, Nfld 620kHz; CFCY Charlottetown, Prince Edward Island 630kHz; CBN St John's 640kHz; CJCN Grand Falls 680kHz; CBNM Marys-town, Nfld 740kHz; CBH Halifax, Nova Scotia 860kHz; CJCH Halifax 920kHz; CJON St John's 930kHz; CHER Sydney, N.S. 950kHz; CHNS Halifax 960kHz; CKBW Bridgewater, N.S. 1000kHz; CBA Monoton, New Brunswick 1070kHz; CBD Saint John N.B. 1110kHz; CKEC New Glasgow, N.S. 1320kHz. Newfoundland, which is located approx. 2,200 miles west of the U.K. and 3½ hours behind GMT in time is the first part of North America to fade-in (some 4 to 5 hours after sunset in the U.K.), followed shortly afterwards by the eastern seaboard states of Canada (GMT-4) and the United States (GMT-5). Even

who was given a Pye five band set by his grandmother. He does not tell us the aerial type but he has managed to log:

Radio Peace and Progress on 9800 at 1415

Vatican Radio on 9645 at 1500

Radio Cairo on 9455 at 2315

We will all, I am sure, want to wish **Alan Crookes** of Deepcar, Sheffield a "get well soon". He had an accident at work which will, as he says, put him "out of circulation" for a spell. Nothing daunted he turned to his Murphy B40 and hooked this on to the PW aerial tuner unit which sucks the signals from a redundant TV aerial. This set up brought in, among others, Radio Australia on 11840 at the unusual time of 1710 along with another rarity the Gospel station ETLF Ethiopia on 11830 at 2215.

To wind up this month's items a quick look around the stations. WDXC report that Adventist World Radio plan to broadcast from the Deutsche Welle Malta relay by the summer, while FEBA plan to put into action a 100kW transmitter which they test on 15325 from 1230 to 1500.

in midsummer the outlets logged by Fred can be heard in the U.K. for an hour before sunrise. Reception is often very good as dawn approaches—a reward for the keen DXer who tunes round the band at this hour.

Harlod Emblem reports again from Mirfield in Yorkshire. Using an Eddystone 730 and medium wave loop he logged Kabul, Afghanistan on 1280kHz with sign-on at 0200; CKVO the new outlet at Clarenville, Newfoundland on 710kHz and Radio Caribbean on 840kHz. (Radio Caribbean transmits with a power of 10kW from Castries on the island of St. Lucia). Listen for medium wave broadcasts from the Caribbean between 0100 and sunrise during the summer. Stations to search for that are logged regularly in the U.K. are Radio Surinam, Paramaribo on 725kHz; Point Galina, Jamaica 750kHz; Radio Demerara, Guyana 760kHz; Trans World Radio, Bonaire 800kHz; Radio Antilles, Montserrat 950kHz; Radio Victoria, Aruba now on 960kHz; Radio Paradise, St. Kitts 1265kHz; Radio Bahamas in Nassau on 1540kHz.

A. J. Fenton (Warley) has heard a Russian station on 254kHz after the close down of Lahti, Finland at 2130. Yerevan, Armenia is on this frequency until 2200 while Dushanbe, Tadzhikistan signs-on at 2300. Either of these is capable of being logged in the U.K. **David Blair** (Airdrie, Scotland) asks if an Aerial Tuning Unit would improve reception on the medium waves. An ATU is inserted between the aerial and receiver and is adjusted to give a good match between the two. In many cases this will bring a considerable increase in signal strength. Partridge Electronics, who advertise in Practical Wireless, can supply a Joymatch ATU suitable for use on the medium waves.

BROADCAST BANDS

Short Wave Reports by the 15th of the month to Derek Bell, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the middle of the month to **Eric Dowdsawell G4AR**, Silver Fir, Leatherhead Road, Ashstead, Surrey, KT21 2TW.

Complete the coupon and we'll send you our new catalogue. Completely free.



The new Heathkit catalogue is now out. Full as ever with exciting new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now and we'll send you your free copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

So, when you receive your catalogue you should have hours of pleasant reading.


And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

At either one you'll be able to see for yourself the one thing the catalogue can't show you.


Namely, how well a completed Heathkit performs.

Heath (Gloucester) Limited, Dept. PW-65, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

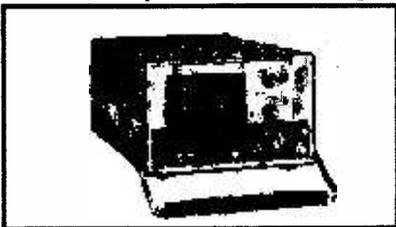
A new oscilloscope from the Heathkit range.



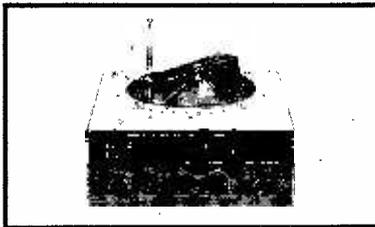Marine direction finder with digital read-out.



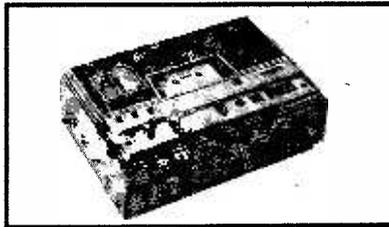Stereo cassette deck with built-in Dolby.



The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. PW-65, Gloucester, GL2 6EE. Please send me my free Heathkit catalogue.

Name _____ Address _____

Postcode _____

Remember easy terms are available with the Heathkit Monthly Budget Plan.



**Fully guaranteed
Individually packed
VALVES**

A1065 £1.25	ECL80 55p	GZ34 70p	FY80 40p
AR3 55p	ECL82 55p	GZ37 £1.00	FY81 40p
ATP4 50p	ECL83 70p	KT30 £2.50	FY82 40p
B12H £3.00	ECL86 50p	KT88 £2.20	FY83 40p
CY31 50p	EF36 65p	MH4 75p	FY88 45p
DAF96 55p	EF37A 70p	ML6 65p	FY500 £1.00
DF96 55p	EF40 70p	OA2 45p	FY800 45p
DK96 70p	EF41 75p	OS2 45p	FY801 50p
DL32 40p	EF42 75p	PABCS0 40p	QV03-10
DL6 60p	EF80 30p	PC37 50p	AD 192
DY86/87 40p	EF83 £1.25	PC800 50p	ADZ 11
DY802 45p	EF85 35p	PC84 40p	ADZ 12
ES8CC/07 £1.20	EF86 35p	PC85 40p	ADZ 11
EL180CC 70p	EF89 30p	PC88 60p	BCY 31
EL18CC 70p	EF92 50p	PC89 60p	BCY 33
EA50 40p	EF95 40p	PC91 60p	BCY 72
EABC80 40p	EF183 35p	PC980 40p	BF 115
EAF42 75p	EF184 35p	PCF83 40p	BF 167
EB91 30p	EFL200 75p	PCF84 60p	BF 185
EC33 £1.00	EL33 £2.50	PCF86 60p	BF 51
EC41 35p	EL34 70p	PCF200 75p	BFY 52
EC83 £1.00	EL36 60p	PCF201 75p	BFY 90
EB41 75p	EL37 £1.80	PCF802 50p	
EBF80 40p	EL41 30p	PCF805 50p	
EBF83 50p	EL81 60p	PCF806 75p	
EBF89 40p	EL84 30p	PCF808 80p	
EC92 35p	EL85 60p	PCF809 80p	
EC81 35p	EL86 45p	PCL81 55p	
EC83 35p	EL90 45p	PCL82 55p	
EC84 35p	EL904 80p	PCL84 45p	
EC85 40p	EM31 60p	PCL86 50p	
EC86 80p	EM30 55p	PCL86 50p	
EC88 50p	EM84 40p	PCL86 50p	
EC89 40p	EM87 £1.00	PL200 70p	
ECF80 70p	EY51 45p	PL81 50p	
ECF82 40p	EY81 45p	PL82 45p	
ECF91 30p	EY86 40p	PL83 45p	
ECH35 £1.40	EY88 50p	PL84 45p	
ECH42 40p	EZ10 75p	PL904 50p	
ECH81 35p	EZ80 30p	PL908 £1.00	
ECH83 45p	EZ81 30p	PL909 £1.35	
ECB84 45p	EY501 75p	PY33 60p	

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavailable.

TRANSISTORS, DIODES etc.

AC 113	AF 139	BSY 27	OA 202	OC 200	2N 3053
AC 126	AF 178	BSY 38	OA Z 200	OC 206	2N 3054
AC 127	AF 186	BSY 95A	OC 22	OC 22	SX 754
AC 128	AFZ 12	BVZ 16	OC 25	OC 25	ZR 11
AC 176	ASV 26	CRS 1/10	OC 26	OC 26	ZR 21
AC 178	ASV 27	CRS 1/20	OC 28	OC 28	1N 23A
AC 19	ASV 28	CRS 1/30	OC 29	OC 29	1N 25
AC 20	ASV 28	CRS 1/40	OC 35	OC 35	1N 30A
AC 21	BC 103	CRS 1/40	OC 36	OC 36	1N 38A
AC 23	BC 118	CRS 3/10	OC 42	OC 42	1N 43
AC 29	BC 119	CRS 3/20	OC 44	OC 44	1N 70
AC 30	BC 136	CRS 3/30	OC 45	OC 45	1N 277
AC 34	BC 137	CRS 3/40	OC 70	OC 70	1N 415C
AD 161	BC 148A	GRT 115	OC 73	OC 73	1N 414S
AD 162	BC 172	GRT 116	OC 73	OC 73	1N 456A
ADZ 11	BC 172A	GEX 66	OC 78	OC 78	2N 708
ADZ 12	BC 212A	NKT 222	OC 81	OC 81	2N 918
AF 114	BCY 31	OA 5	OC 82	OC 82	2N 1304
AF 115	BCY 33	OA 7	OC 82D	OC 82D	2N 1305
AF 116	BF 115	OA 7	OC 82DM	OC 82DM	2N 1307
AF 117	BF 167	OA 71	OC 83	OC 83	2N 1309
AF 118	BF 167	OA 73	OC 139	OC 139	2N 2062
AF 124	BF 185	OA 79	OC 140	OC 140	2N 2147
AF 125	BFY 51	OA 91	OC 170	OC 170	2N 2411
AF 126	BFY 52	OA 91	OC 172	OC 172	2N 2989
AF 127	BFY 90	OA 200	OC 172	OC 172	2N 2989



ALL valves guaranteed

68C7GT 40p	25L6GT 70p	6064 60p
68C7 50p	30C15 11.00	6065 £1.00
68C7 50p	30C17 11.00	6067 70p
68J7GT 35p	30C18 11.00	6080 £2.30
68K 57 50p	30F5 11.00	6146 £2.35
68L7GT 50p	30FL1 11.00	6146B £2.35
68N7GT 50p	30FL12 11.00	6200 £5.00
68Q7 55p	30FL14 11.00	9001 25.00
68VGT 50p	30FL15 11.00	9002 50.00
68WGT 50p	30P19 11.00	9004 35p
624 65p	30P11 95p	9006 85p
630L2 90p	30P13 95p	
7B7 80p		
7Y4 80p	30P14 11.00	GR. Tubes
9D6 40p	35L6GT 75p	DG7-5
11E2 26.00	35W4 50p	£12.00
12A6 55p	35Z4GT 70p	
12AT6 45p	50C3 60p	MW13-35
12AT7 40p	50C6G 60p	£35.00
12AU7 85p		VCR13A
12AV6 50p	75 11.00	28.00
12AX7 35p	75C1 28.00	3B1 24.00
12BA6 45p	75 75p	3B2 29.00
12BE6 50p	78 70p	3B3 28.00
12BH7 50p	80 75p	38L 29.00
12C5 55p	85A2 28.00	
12E1 28.50	728a/b 28.00	Special
12K5 11.00	803 26.00	Valves
12K7GT 50p	805 214.00	CV239
12K9GT 70p	807 65p	
12Q7GT 70p	813 26.00	M503-242
12SA7GT 70p	931A 26.00	£45.00
12S67 55p	954 50p	K301 27.00
12S7 55p	955 50p	KRN2A
12Y4 40p	956 50p	26.00
145T 11.00	957 50p	OY4-230
19A05 65p	1305 20p	£19.00
19G3 28.00	1629 70p	TY4-500
19G6 26.00	2051 11.00	230.00
19H5 214.00	5933 23.00	735A 233.00
20P3 60p	6087 75p	2J/192
20P4 11.00	6090 70p	£140.00

V.A.T.
Please add 8% to all orders

UF85 45p	1R5 40p	6BG6G 90p	6H6 35p
UF89 50p	1R4 30p	6B7B 65p	6J4WA 85p
UL41 70p	1R4 30p	6B7C 80p	
UL84 40p	1X2A 60p	6BR7 £1.20	6J5 65p
UY41 45p	1X28 75p	6BW6 £1.00	6J5GT 50p
UY85 40p	2D21 50p	6BW7 £1.00	6J6 30p
VR105/30 2E25 29.00	2E25 29.00	6C4 40p	6J7 60p
	844 60p	6C4 40p	6J7 60p
	844 60p	6C6 50p	6J7G 40p
VR150/30 3D6 40p	5ZAGT 55p	6C8B 50p	6J8GT 80p
	6AB7 60p	6C8B 50p	6J8GT 80p
	6AB7 60p	6C8B 50p	6J8GT 80p
X61M £1.40	3V4 85p	6C8B 50p	6J8GT 80p
X66 65p	58/254M 24.50	6D6 55p	6K5GT 30p
Z900U 22.70	5B255M 24.50	6E8 85p	6K25 £1.00
	2801U 22.70	6AX5GT 11.00	6L6 21.90
	2801U 22.70	6F8 70p	6L6G 60p
	5R4GY 90p	6F8 70p	6L7G 40p
IA3 55p	5U4G 50p	6G8 70p	6L7G 40p
IA4 25p	5V4G 55p	6B8A 35p	6F82 75p
	5V4G 55p	6B8B 40p	6F83 23.50
	5V4G 55p	6B8C 40p	6F83 23.50

MINIMUM POSTAL ORDER 5L. PERSONAL CALLERS WELCOME. OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Postage Up to £2 12p, £2-23 22p. Over £23 post free. C.O.D. 25p extra.

29/41FT. AERIALS each consisting of ten 3ft., 3/4in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the sections. Fin, rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag. £7.50 new. Carriage £1.50.

Colomor (Electronics) Ltd.
170 GOLDHAWK ROAD, LONDON W12.
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

**Quality
Loudspeaker
Systems**

Direct from manufacturer as supplied by us to the trade.
Finished in natural Teak veneer 15 watt 8 ohm bass reflex speaker system containing Goodmans 8" bass with HF speaker. Frequency response 50 Hz - 19000 Hz. Complete with leads and DIN plug. Cabinet size 17" x 10" x 7" deep.
Price £17.00/pair including VAT plus £1.90 packing, carriage and insurance (U.K. mainland).
*Bulk discounts available for trade enquiries. Please send cash with order direct to:-
Forward Marketing, 30 Ridgeway, Stanground, Peterborough.



INVERTERS
240v-50Hz. from your 12v car battery.
25 watt-£3.90 + 30p p & p.
40 watt-£6.80 + 35p p & p.
75 watt-£9.95 + 75p p & p.
All above inverters are in kit form but may be purchased built up & ready for use. Price list sent on receipt of stamped addressed envelope.

P.W. AUTOMATIC EMERGENCY SUPPLY
250v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 73 P.W. Complete kit of parts (excluding meter) £22.50 + £1.10 p & p.

COMPLETE FLUORESCENT LIGHT INVERTOR KIT
8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for, factories, hotels etc. 12"-8 watt £2.90 + 25p p & p. 21"-13 watt £3.30 + 30p p & p.

TRANSFORMERS & COILS
Both high volume & small order capacity available for Mains, R.F., & I.F. Transformers. Before you buy elsewhere let us quote you and see what you save.
V.A.T. at 8% included.

TRADE & EXPORT ENQUIRIES WELCOMED
ASTRO ELECTRONICS, 10A SPRINGBANK RD., CHESTERFIELD, DERBYSHIRE

ELECTRONI-KIT
... educational kits of exceptional quality ...
(AUDIO mag. Dec. 1974)

BUILD AND REBUILD ANY NUMBER OF TIMES:
Radios, microphones, burglar alarms, inter-comms, ferrite detectors, solar cell, photoelectric cell, voice relay, electronic cats, birds, guns, organs, illuminometers, voltmeters, meters of all types, etc., etc., plus your own circuit designs.

COMPLETELY SAFE-suitable for all, from beginners on. 30 different projects £10-45, 100 different projects £20-45, over 150 £33-95. Add-on kits, spares, available too.

Prices include Manuals, Battery, p & p, VAT, etc. Cheque/PO (or 7p for catalogue) to DEPT. PW.

Satisfaction guaranteed.
ELECTRONI-KIT LTD, 408 St. John's Street, London, EC1. [01-278 4579]

EXPERIMENTAL WORKSHOP

M. J. HUGHES
M.A., C.Eng., MIERE.

LEARNING BY PRACTICAL PROJECT STEPS

PART 15—RF OSCILLATORS

SO far in this series we have concerned ourselves only with oscillators that use resistors and capacitors to introduce frequency selective feedback. Oscillators using RC frequency determining components are usually restricted to the lower frequencies, up to a few hundred kilohertz. Above these frequencies we enter into the area of **Radio Frequencies** and it is usual to find the frequency selective networks using capacitors and inductors instead of resistors. The reasons are various, e.g. resistors are usually rather temperature sensitive and consequently the time constants of the circuits could change from time to time; the quality factor or "Q" of RC circuits is not usually as high as for LC circuits at the higher frequencies and often we require inductive coupling to help with feedback control.

One of the most common LC oscillators is the Hartley oscillator which we shall be describing and using this month. The basic circuit is shown in Fig. 108a. To prevent experimental problems we shall be making this circuit oscillate with frequencies in the range of 500kHz to about 1MHz, i.e. over the medium wave band. This allows us to use any conventional transistor radio, having a medium wave tuning range, to detect oscillation and, at the same time, the frequencies are not so high to give us problems with parasitic capacitance and layout.

Tr1 is operated in a very similar mode to the simple feedback biased audio amplifier stages described previously, but note that its emitter is not returned direct to the earth rail. Imagine that L1 and C1 had been left out of the circuit as we have drawn it; L2 would act as an emitter load to the transistor. Any signal that we applied through C2 to the base of the transistor would cause collector current to vary through R2 and L2. This gives rise to voltage variations at the collector of the transistor. There will be pretty insignificant voltage variations at its emitter but there will be reasonable levels of current flowing through the windings of L2. These currents cause varying magnetic fields within the windings and these magnetic variations are used to generate our feedback to make the circuit provide self-sustained oscillation.

Now let's see what happens when we introduce L1 to the circuit. This winding is coupled electrically to the top end of L2 and is wound on the same magnetic axis. We shall be using a ferrite rod on

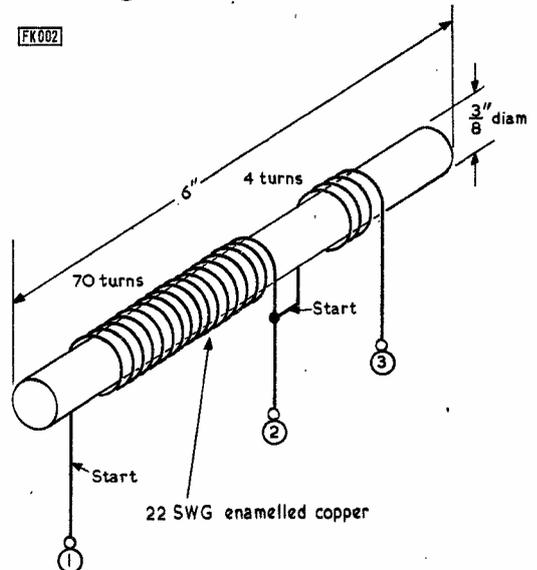
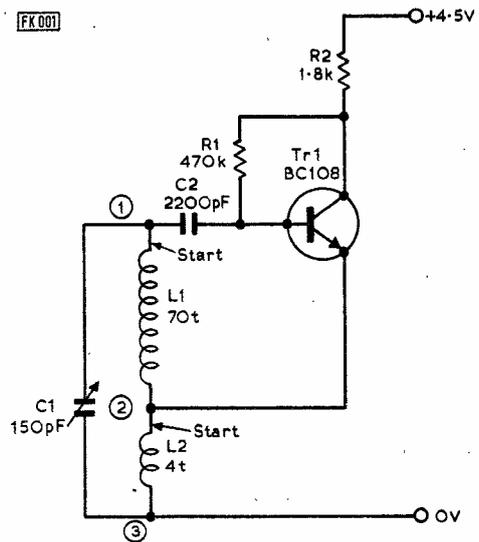


Fig. 108a, top: Shows the basic Hartley oscillator circuit. Fig. 108b, bottom, gives the details of the coils L1 and L2, wound on a ferrite rod.

which to wind the coils as this helps increase the magnetic coupling between the two coils. By adding the extra turns for L1 on the same core that we are using for L2 gives us the equivalent of an **Auto-transformer**. If an AC signal was applied between the top end of L2 and earth it would induce a signal across the top of L1 and earth having a higher voltage. The voltage increase would be proportional to the ratio of turns.

$$V_{out} = V_{in} \times \frac{\text{Turns on L1} + \text{Turns on L2}}{\text{Turns on L2}}$$

This simple turns ratio expression does not make allowances for losses but is sufficiently accurate to give an indication of what is happening. In our case we get voltages at the top end of L1 that are approximately 20 times greater than are applied across L2. We must, however, remember that something has to go to allow this voltage magnification and, of course the current is reduced by a factor of 20. In other words we can say that the impedance across L1 and L2 in series is higher than that across L2 on its own.

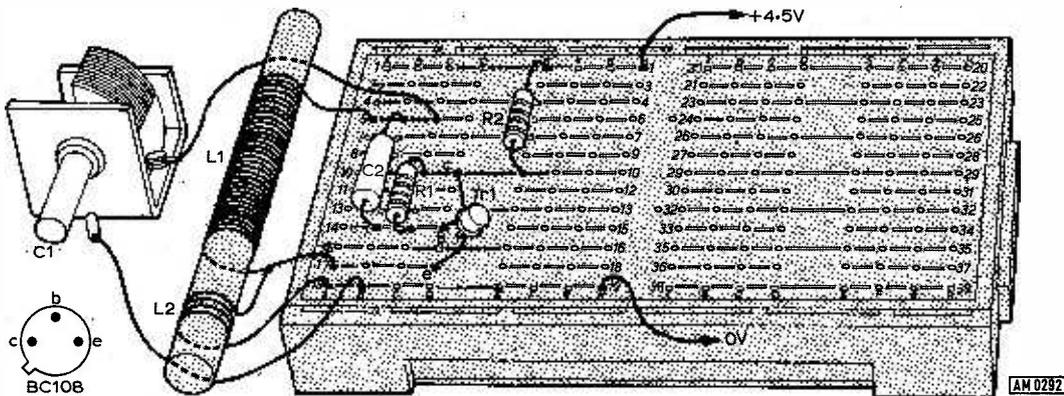


Fig. 109: Shows the practical layout of Fig. 108a assembled on S-dec.

If we now connect the top end of L1 to C2 we shall be feeding back a higher voltage to the base that was generated at the emitter. Provided the transistor has a high enough current gain (greater than the current loss factor caused by the transformer action) the feedback voltage will produce a voltage change back at the emitter at least as great as the original signal that set the ball in motion. Provided we get our phasing right we can provide positive feedback with the necessary amplification to produce self-sustained oscillation but don't worry about its frequency at present. Provided that both the windings of L1 and L2 are wound on the same core with the same sense, i.e. in the same direction, and the starts of each winding are as shown in Fig. 108a, any voltage applied across L2 will be presented across L1 and earth in the **same phase** and, of course, at a higher level. We already know, from emitter follower action, that voltages at the base of a transistor appear at its emitter with no phase shift so consequently we shall get positive feedback in our circuit if we obey the foregoing points.

We now have to consider how to get oscillation at a predetermined frequency and this is where C1 comes into play. C1 with L1 and L2 form what is called a **parallel tuned circuit**. For a given frequency we can select values for C1 and the total inductance of L1 and L2 together so that the reactance of the

capacitor exactly equals the reactance of the inductor. For given values of inductance and capacitance the frequency at which this state of affairs occurs is given by:—

$$\text{Capacitive reactance} = \text{Inductive reactance}$$

$$\text{or } \frac{1}{2\pi \times f \times C} = 2\pi \times f \times L$$

$$\text{or } f = \frac{1}{2\pi \sqrt{LC}}$$

where f is in hertz, L in henrys and C in farads.

Remember, in our circuit, the value for inductance is obtained from the **total** inductance of L1 and L2 together!

It is a feature of a parallel tuned circuit that when the two reactances are equal the impedance of the parallel circuit becomes extremely high, the limiting value of this impedance being set by the Q factor of the coil. This means, in real terms, that at resonance we shall see the highest values of AC voltage appearing across the tuned circuit. At all other frequencies, whether higher or lower, the

voltage across C1 will be less. It should, therefore, be quite obvious that we shall get higher values of feedback voltage at the resonant frequency than at any other and the circuit will prefer to oscillate at the resonant frequency.

By making C1 a variable component we can alter the frequency of oscillation to suit ourselves. The inductor we shall use is identical to the ferrite aerial coil one would use for a simple transistor radio set. After all, the input stages of a medium wave radio have to tune to the same frequencies we are hoping to generate so it should seem only right that the inductance and capacitance values should be the same. Wind L1 and L2 with 22SWG enamelled copper wire on about a 6in length of 3/8in diameter ferrite aerial rod. They should be close wound and there should not be more than about 1/8in gap between L1 and L2, Fig. 108b. Make sure that you start each winding at the right place and keep the same winding sense.

Now wire up the circuit of Fig. 108a according to the given layout, Fig. 109, and apply power from a 4.5V battery. Lay (do not connect) a piece of insulated wire close to Tr1 and connect the other end of the wire to the aerial input socket of a medium wave radio. If there is no aerial socket the chances are that there is a ferrite rod inside the radio; if so it should be sufficient, for our experiment, to

continued on page 157

NEW SINCLAIR IC20 10+10 Watt stereo amplifier kit with free 16 page booklet and printed circuit £6.99 (82p)
IC20 P220 power supply kit for above £4.45 (66p)
 VP20 stereo volume, tone control and preamp kit £4.95 (72p)

SINCLAIR CALCULATORS AND MULTIMETERS

Sinclair Digital Multimeter DM2 £58.95 (£5.26)
 Scientific calculator assembled £15.03 (£1.57)
 Cambridge Calculator assembled £10.07 (£1.13)
 Cambridge Memory Assembled £13.96 (£1.44)
 Oxford 100 £10.50 (£1.20), Oxford 200 £16.95 (£1.70), Oxford 300 £24.95 (£2.40)

CALCULATOR POWER SUPPLY
 This 6V 500MA model runs any Sinclair or other 9V calculator from the mains. £3.30 (65p)

FERRANTI ZN414
 IC radio chip with data £1.20 (25p). Also available kit of extra parts to complete a radio £2.55 (47p). Send sae for free leaflet

SINCLAIR PROJECT 80
 Stereo 80/2 Z40/P25 £24.40 (£2.40)
 Stereo 80/2 Z40/P26 £26.70 (£2.67)
 Stereo 80/2 Z60/P28 £28.66 (£2.87)
 AFU £6.38 (78p)
 Z40 £4.87 (68p)
 Z60 £6.38 (78p)
 Q16 £5.70 (65p)
 P25 £4.62 (73p)
 P26 £7.41 (94p)
 P28 £7.25 (90p)
 Decoder £7.46 (89p). Trans for P28 £3.75 (70p).
 Tuner £11.43 (£1.42), Stereo 80 £11.43 (£1.42).
 Project 80S £28.95 (£3.30), Project 80SQ Quad Decoder £15.95 (£1.28)

SINCLAIR SUPER IC12
 6 Watt IC power amp and preamp. With 44 page booklet and printed circuit £1.80 (43p)

DELUXE KIT FOR THE IC12
 Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.80 (31p). Stereo model with balance control £3.90 (49p)

IC12 POWER KIT
 Supplies 28V 0.5 Amps £3.07 (62p)

PREAMP KITS FOR THE IC12
 Type 1 for magnetic pickups, mics and tuners. Mono model £1.50 (30p), Stereo model £2.70 (35p). Type 2 for ceramic or crystal pickups. Mono 80p (23p), Stereo £1.80 (30p)

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAINS
 The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 500 mA. £3.90 (50p).
 Other eliminators stocked:—
 250mA—3 way switched model giving 6, 7½ and 9V £2.50 (65p).
 50mA— 4½V £2.40 (40p), 6V £2.40 (40p), 9V £2.40 (40p), 7½V cassette type £2.80 (60p), Double 4½V + 4½V £2.95 (50p), 6V + 6V £2.95 (50p), 9V + 9V £2.95 (50p).
 500mA— Heavy duty deluxe models 6V £3.30 (65p), 7½V £3.30 (65p), 9V £3.30 (65p)

S-DECS AND T-DECS
 S-DeC £1.98 (36p)
 T-DeC £3.63 (52p)
 M-DeC A £3.99 (56p)
 M-DeC B £6.99 (86p)
 IC carriers:—
 16 pin plain 81p (18p) with socket £1.77 (28p)
 10 TO5 plain 78p (18p). With socket £1.68 (27p)

SWANLEY ELECTRONICS
 PO BOX 68, SWANLEY, KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and new VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back up service to ensure your success. VHF and UHF Modulator kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes and focus/scan coil assemblies. Ready built cameras also available. Complete kits available for P.W. tele-tennis game. Send 5" x 7" S.A.E. for full details, or come along for a demonstration and a chat with our technical staff.

CROFTON ELECTRONICS
 124 Coine Road, Twickenham, Middlesex, TW2 6QS
 Tele: 01-898 1569
 Telex 934642
 Cadanac LDN

BETTER GET 'SET'

FAMOUS NO. 19 SET TRANS/RECEIVER
 TR50/51 2-8 MHZ in 2 bands. 11 valve. 807 PA Power reqs 12VLT 275-VHT REC 500VTM. Rebuilt £12.50, Carr. £1.50.
 Complete station 12 VDC PSU. Mic. Cables £23.50, Carr. £3.00.

POWER UNIT RECTIFIER No. 19 (Heavy Duty)
 Mains 100/250V AC Tapped input 12 or 24Vdc 6/7 amps output. Excellent for driving No. 19 and other equipment, also battery charger. Size 19" x 6 x 7. Only £8 50. Carr £1 50.

TE76/CT52
 A superb Miniature Oscilloscope £25, Carr. £2.50. Mains operation.

RE102 42/MAST
 12-3" 6" x 2" sections WIRE GUYS STRAINERS in carry holdall £23.50 Carr. £3.50.

AERIAL RODS
 3' x 1" screwed M & F ends 10 £2.25. Post 75p, 25 £5, Carr £1 00.
AE101. Telescopic mast 20p antenna £3.75. Carr. £1.25
 List 25p refundable with purchase.

XTAL CALIBRATOR
 No. 10
 1/10MHZ Harmonics 30 MHZ £3.50 Post 50p.
No. 62 RC/TM 1.5-10MHZ £15 Carr. £2.
 Add VAT 8% Prices and Carriage

Surplus Electronic Trading
 P.O. BOX No. 19, HITCHIN, HERTS. SG4 6TN

Wire Wound Resistors. Our selection of mixed values. 30 for £1 50. 100 for £4.00.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.50.

Ferguson Stereogram chassis Model 3357, all transistor, medium long, VHF/FM. 3 watts per channel S/M. with connection data, less tuning scale, £20. Post paid.

Crystals HC6U: 52-03333 MHZ: 52-02500: 52-01667: 51-56667: 51-58330: 37-76250: 37-75000: 12-895-8: 12-891-6: 12-700-0: 9-456-25: 9-455-55: 9-533-33: 9-531-94: 9-530-55: 9-090-62: 9-087-5 50p each.

Electrolytics, 32/32/32/μF, 325v, 2" x 1 1/2" 35p: 80μF 150vt 1 1/2" x 1" 20p; 2000μF 30v, 2 1/2" x 1" 25p; 2000μF 35v 3" x 1" 30p; 470μF 100v 3" x 1 1/2" 25p; 2000/2000μF 25v 2" x 1 1/2" 35p; 700μF 200v 3 1/2" x 1 1/2" 30p; 16/16μF 275v 1 1/2" x 1" 20p; 40/40/20μF 275v 3" x 1" 20p; 4500/900/900μF 30v 2 1/2" x 1 1/2" 50p; 2500μF 40vt 2 1/2" x 1 1/2" 40p; 4000μF 18v 2" x 1" 20p; 470μF 25v 1 1/2" x 1 1/2" 15p; 4,000μF 25v 3" x 1 1/2" 40p.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5". 8 x 5 8" ohms ceramic, 5 watts RMS. Complete with din leads. £11.00 pair.

Thorn TV IF chassis, 950 series (less valves), £1.75.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, £3.25.

Light Dependent Resistors (RCA sq3536) 30p each, 4 for £1.00.

P-C Boards (not computer panels) 1 off 6 transistor single wave band, 1 off 4 transistor audio, 1 off 3 transistor £1.60, three boards.

Repenco Transformers AF1, AF2, TT45, 46, 47, 49, 53, 55, 20p each.

L/M, M/W, VHF Tuner 5 transistor in kit form, complete with full assembly instructions. 9vt supply, positive earth. O/pout 100mw. Built-in A.M. aerial. 88-108 Mcs. £5.75.

Stereo Decoder using MC1310. Fully assembled, can be used with our tuner kit. With data, £4.25.

Mains Droppers, 10 mixed values, £1.00.

Edgewise Level meters, 200μA, size 1 1/2" overall, 50p.

Chrome Plastic knobs, 3 types, 4 off each with spring clip, £1.25.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 70p: 10" x 7 1/2" x 2 1/2" 85p. 11" x 7 1/2" x 2 1/2" 95p.

BSR P128, similar to HT70 single play, with heavy die cast turntable, less cartridge, £11.00.

Circuit Diagram supplied with VHF tuner £3.25.

Ferguson Stereogram Chassis. MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £28.50. Post paid

5 ASSORTED SWITCHES £2.00. 50-3 way to 7 way TAG STRIPS, £1.25. ALMA REED RELAY TYPE DRH. 3 VOLTS, 55p.

REPANCO & DENCO COILS. NEW/BOXED OUR SELECTION—5 FOR £1.25

Goods not despatched outside UK 15p Handling charge on orders under £1.00. Please add 10% for post and packing on all items except gram chassis. All items include VAT.

SURPLECTRONICS
 216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

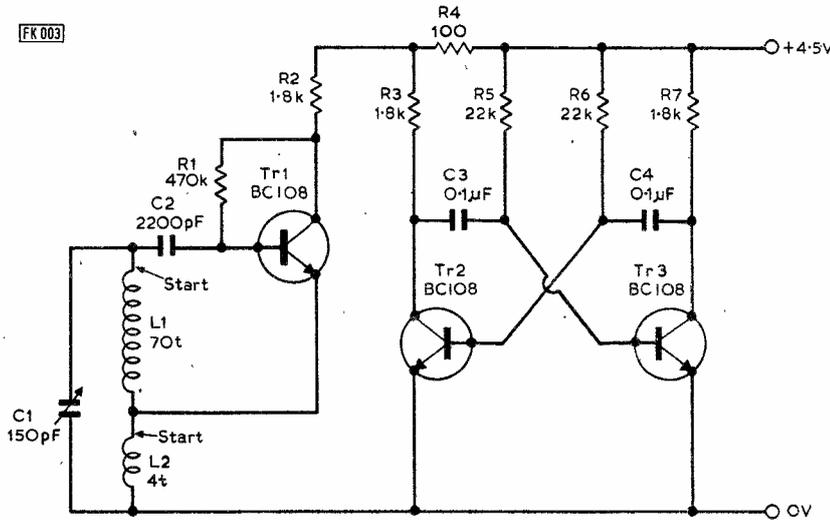


Fig. 110: An audio tone is generated by multivibrator Tr2/3, modulating the carrier produced by oscillator Tr1.

place the radio close to the ferrite rod of our oscillator. Tune in a broadcast station on the radio and then adjust C1 of our oscillator. At one setting you should hear a very loud whistle changing in pitch as you adjust C1. This is **heterodyning** or beating of the signal we are generating and the signal coming in from the distant station.

Try different positions on the tuning scale of the radio and you should be able to check the range of frequencies our oscillator generates. It is easiest to beat this signal against incoming signals otherwise you will hear no noise from the loudspeaker when in tune, apart, perhaps, from a slight reduction in background hiss as the AGC circuits of the radio come into operation.

If the level of positive feedback is too great Tr1 might be driven into saturation and instead of getting a pure sinewave signal we will get a clipped signal. This clipping introduces high order harmonics and you might find in the case of excessive feedback, spurious signals occurring all over the tuning range of the radio. You can increase the level of feedback by increasing the value of C2 and vice versa. With too little feedback the circuit will, of course, not oscillate. Ideally the value for C2 should be selected to enable the circuit to **just** oscillate. Try altering the number of turns for L1. Reducing the turns makes the circuit operate at higher frequencies,


shorter wavelengths, because we are reducing its inductance, and vice versa.

The circuit we have just made produces what is called an RF carrier signal. It is a pure, constant amplitude sinewave and, as such, carries no intelligible information. However, in the case of broadcasting we need just such a signal but need to impress audio information upon it so that we can get an intelligible signal from the loudspeaker of our radio. The simplest way of doing this is by a process known as amplitude modulation, AM. This entails altering the level of signal our oscillator produces in proportion to the amplitude of audio signal we wish to transmit.

Fig. 110 shows a simple modification that allows us to modulate our carrier signal with a square wave produced by the multivibrator, Tr2 and Tr3. Resistors R3 and R4 form the collector load for Tr2 and we use the junction of these two components to provide the power rail voltage to our RF oscillator. As the waveform at the collector of Tr2 rises and falls so does the voltage driving the oscillator and the amplitude of the resulting carrier will be amplitude modulated at the frequency of the multivibrator. A clear tone should be detectable over the medium wave range of the radio as C1 is adjusted. Such a circuit can form the basis of a test signal generator. The layout is shown in Fig. 111.

Fig. 111: Layout of components used in Fig. 110.

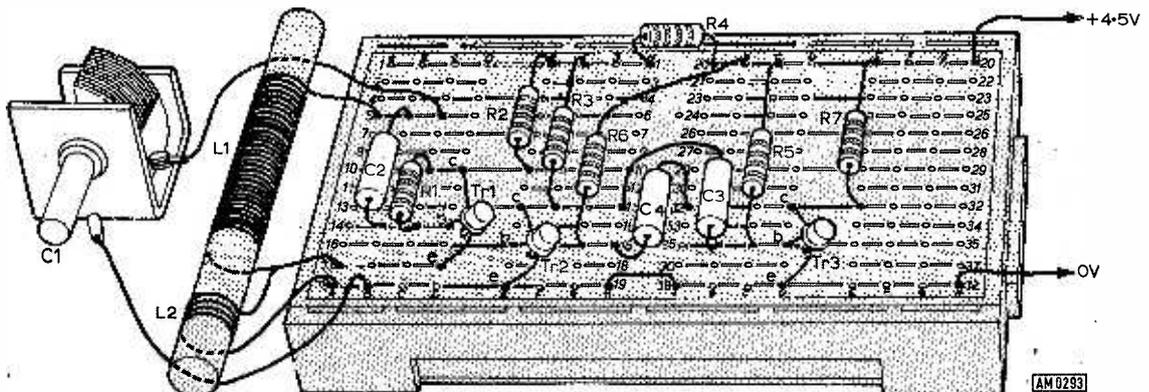Next month: Simple radio receiver circuits.



IN USE

When receiving SSB signals, accurate tuning is absolutely necessary, since small errors will influence the quality of the signal. No resolution of speech is possible if the oscillator is on the wrong side of the signal. This will soon become apparent in use.

For CW reception, the oscillator may be either side the signal, as is found to give best reception. Tuning slightly either way will change the pitch or audio tone.

The receiver is not intended for conventional AM reception as AM signals produce a continuous heterodyne except when tuning of the oscillator agrees exactly with the carrier frequency.

The output stage is suitable for headphones of medium or high impedance type with a resistance of about 100Ω to 1.5kΩ. Battery current is about 7mA with 1.5kΩ phones and 20mA with 100Ω phones, the latter providing greater volume.

MODIFICATIONS

Other audio amplifiers could be used, omitting Tr2 and Tr3. An example is the Sinclair IC-2, which can be connected as in Fig. 5.

C7 and VR1 are already present. The additional resistor and capacitor are a high frequency filter, to help produce a frequency response more suitable for the purpose. The amplifier is operated from its own 9V battery and a 3 to 15Ω speaker can be used.

When using this or other Class B amplifiers it is essential to prevent frequency modulation of Tr4 at syllabic rate from a common battery supply. The simplest method is to use separate batteries, as mentioned. The alternative is a decoupled and regulated supply for Tr1 and Tr4. The amplifier in Fig. 1 gives excellent headphone volume with many signals, but it is not really intended for a loudspeaker.

BANDPASS INPUT

If a resonant aerial or tuning unit is not available, the coil and capacitor in Fig. 6 may be added near the receiver aerial socket.

VC3 can be 100pF or larger, if one coil is to cover both bands. The tuned winding resembling L1 or L2 in the receiver. For the aerial coupling winding, use about one-third as many turns as the tuned winding. TC1 is almost fully opened providing top-capacitance coupling between the tuned circuits. PW

Television

from **JULY** issue onwards

bigger pages—more pages

more of your favourite subjects

Look for it—in June

TELEVISION

IN THE JUNE ISSUE

THYRISTOR TESTER

Thyristors are now commonly used in solid-state receiver stabilised power supplies. Unfortunately they are inclined to be troublesome. Other applications are in the line output stage of many imported colour receivers and as over-voltage protection crowbar trips. So there is increasing need to be able to test them. Simple checks are not reliable: the only satisfactory method of testing involves the use of high voltages and currents. This is the basis of Alan Willcox's useful tester, which complements his recent transistor tester.

FAULT-FINDING: GEC SERIES 1 AND 2

John Law's latest fault-finding guide deals with the timebase sections of the GEC Series 1 and 2 chassis.

RANK'S REMOTE CONTROL SYSTEM

Channel changing techniques have altered a great deal in recent times. The latest approach is to use touch tuning in conjunction with a varicap tuner unit, with an integrated circuit to switch between the tuning potentiometers. This arrangement lends itself readily to remote control and Rank have exploited the possibilities to produce an ingenious low-cost cordless remote control system which is a standard feature of the latest range of Bush colour receivers. A detailed description of the system will be given.

APOLLO—continued from page 139

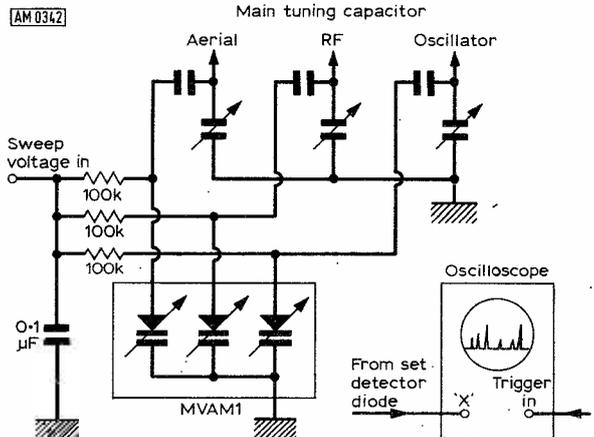


Fig. 2.7: Using this set-up one may obtain a visible display of signals present within the swept part of the band.

If in any doubt about one's proficiency to undertake such a modification to an existing set, take great care to become accustomed to using the varicaps, and the techniques necessary to avoid damaging them through over-voltage when coupling to an existing circuit.

NEXT MONTH: A VARICAP AM/FM STEREO TUNER

**ALL MAIL ORDER BY
RETURN.C.O.D.SERVICE
WELCOME**

C. T. ELECTRONICS

V.A.T.
Unless otherwise stated all prices are EXCLUSIVE of V.A.T.
Please add 8% to all orders.
Carriage: orders under £10 plus minimum 35p. Over £10 post free.

All mail order and enquiries to 270 Acton Lane, Chiswick, London W4 5DG Tel: 01-994 6275

SEMICONDUCTORS

AC107	35p	BCY32	95p	MM1712	60p
AC125	35p	BCY34	65p	MM1702	45p
AC126	25p	BCY38	65p	MPF103	
AC127	27p	BCY39	£1.00	(2N5457)	35p
AC128	25p	BCY55	£1.50	MPF104	
AC176	25p	BCY70	22p	(2N5458)	35p
AC188	30p	BCY71	22p	MPF105	
AC194	25p	BCY72	22p	(2N5459)	40p
ACY18	30p	BD121	75p	OA47	10p
ACY19	30p	BD123	75p	OA70	10p
ACY20	25p	BD124	65p	OA79	10p
ACY21	30p	BD131	40p	OA81	10p
AD140	60p	BD132	50p	OA90	10p
AD142	60p	BD153	75p	OA91	10p
AD149	60p	BD155	75p	OA200	10p
AD161	44p	BDY11	£1.40	OA202	10p
AD162	44p	BDY17	£1.60	OA210	10p
AF114	25p	BDY19	£1.96	OA211	10p
AF115	25p	BDY20	£1.40	OC16	90p
AF116	25p	BF152	20p	OC19	85p
AF117	25p	BF194	14p	OC22	55p
AF118	60p	BF195	15p	OC26	65p
AS221	30p	BF196	15p	OC28	65p
AS222	30p	BF197	15p	OC35	65p
BA102	33p	BF200	30p	OC36	65p
BA112	30p	BF224J	30p	OC42	40p
BA114	15p	BFX29	30p	OC44	20p
BA155	15p	BFX34	30p	OC45	25p
BC107	12p	BFX35	30p	OC70	15p
BC108	12p	BFX86	30p	OC71	15p
BC109	14p	BFX98	30p	OC72	15p
BC113	15p	BFY10	15p	OC75	25p
BC115	15p	BFY44	50p	OC76	25p
BC116	15p	BFY29	30p	OC77	40p
BC117	20p	BFY51	25p	OC81	25p
BC147	11p	BFY52	25p	OC83	25p
BC148	11p	BFY95	25p	OC89	30p
BC149	12p	BSW63	65p	OC170	25p
BC153	14p	BSV68	65p	OC171	25p
BC157	14p	BY127	20p	OC201	60p
BC158	15p	BY164	65p	OC202	60p
BC169	15p	IS100	15p	TIP29A	40p
BC182	12p	IS103	15p	TIP30	55p
BC184	14p	MJ340	50p	TIP31A	57p
BC196	25p	MJ481	95p	TIP32A	69p
BC212	14p	MJ2801	£1.25	TIP33A	£1.00
BC212L	14p	MJ2901	£1.95	TIP34A	£1.40
BC213	16p	MJE340	50p	TIP35A	£1.50
BC214	14p	MJE370	75p	TIP36A	£3.50
BC301	25p	MJE371	90p	TIP39A	£3.50
BC302	25p	MJE380	65p	TIP41A	70p
BC303	40p	MJE2955	£1.20	TIP42A	85p
BCY30	40p	MJE3055	75p	TIP29B	54p
BCY31	55p	MM1613	45p	TIP30B	60p

QTY. DISCOUNTS: 12+ 10%; 25+ 15%; 100+20%

S.C.R.s

TIP31B	65p	2N2218	25p
TIP32B	77p	2N2219	25p
TIP33B	£1.06	2N2222	20p
TIP34B	£1.06	2N2224	25p
TIP35B	£2.71	2N2306	75p
TIP36B	£3.50	2N2477	30p
TIP41B	78p	2N2640	50p
TIP42B	95p	2N2846	£1.50
TIP28C	60p	2N2904	25p
TIP30C	72p	2N2906	25p
TIP31C	80p	2N2907	25p
TIP32C	£1.00	2N2926	12p
TIP33C	£1.20	2N3053	25p
TIP34C	£1.80	2N3054	25p
TIP35C	£3.00	2N3055	50p
TIP36C	£3.74	2N3232	70p
TIP41C	90p	2N3252	95p
TIP42C	£1.00	2N3643	30p
TIS50	40p	2N3702	14p
ZTX107	15p	2N3703	12p
ZTX300	15p	2N3704	12p
ZTX500	16p	2N3705	12p
ZTX501	20p	2N3706	12p
ZTX504	50p	2N3707	12p
ZTX531	30p	2N3708	12p
ZTX550	25p	2N3709	12p
IN659	8p	2N3771	£1.70
IN914	8p	2N3772	£2.00
IN916	8p	2N3773	£2.50
IN4001	8p	2N3775	35p
IN4002	9p	2N3320	25p
IN4003	9p	2N3366	85p
IN4004	10p	2N3904	22p
IN4005	12p	2N3905	25p
IN4006	14p	2N4058	12p
IN4007	16p	2N4059	12p
IN4145	7p	2N4287	15p
2N686	25p	2N4061	12p
2N687	20p	2N4126	17p
2N698	25p	2N4286	15p
2N706	12p	2N4287	15p
2N805A	15p	2N4288	15p
2N806	15p	2N4289	15p
2N890	20p	2N4290	15p
2N1132	25p	2N4444	£1.90
2N1302	16p	2N4871	35p
2N1303	16p	2N4903	£1.10
2N1304	23p	2N5069	£1.10
2N1305	25p	2N5191	25p
2N1306	25p	2N5194	£1.10
2N1307	25p	40360	50p
2N1308	25p	40361	50p
2N1309	25p	40362	50p
2N1513	25p	40669	90p
2N1711	25p	40671	70p
2N2147	40p	D151	£1.00
2N2160	65p		Microwave Diode
2N2217	25p		

TRIACS

CRS1/05	40p
CRS1/10	56p
CRS1/20	65p
CRS1/40	65p
CRS1/60	90p
CRS1/10	62p
CRS2/30	82p
CRS3/40	82p
CRS7/400	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.60
C106B	45p
C106D	70p
40669	90p
2N3525	95p
2N4444	£1.90
BT10/500A	90p

BRIDGE RECTIFIERS

W02 1A 200V	38p
BY164 1-4A 200V	57p
MDA952/2 6A	57p
100V	80p

ZENER DIODES

BZY88 Series	
400mW	
3-3V-33V, 5% 11p	
1-5W range	25p
10W range	45p
TL1209	38p
HP5082	28p
MA2082R	20p

L.E.D.

ORP12	60p
NE555 Timer	80p

TO3 VOLTAGE REGULATORS

L005 5V 650mA	
L036 12V 600mA	
L037 15V 450mA	

VEROBORD

2 1/2 x 3 1/2	0-1	0-15
2 1/2 x 3	32p	23p
2 1/2 x 5	35p	35p
3 1/2 x 3 1/2	35p	35p
3 1/2 x 5	40p	41p
17 x 2 1/2	£1.05	79p
17 x 3 1/2	£1.43	£1.12
17 x 5	£1.84	

PIN INS. TOOL

S.P.F. CUTTER	52p	52p
100 PINS SS	30p	30p
100 PINS DS	30p	30p
500 PINS SS	£1.55	£1.55
500 PINS DS	£1.55	£1.55

ALSO STOCKED

Electrolytic Capacitors, Mullard, Sprague, Lorlin, etc. Polyester, Polystyrene, Silver Mica Capacitors, etc. Resistors 1/8W-10Watt. Potentiometers: carbon, wirewound, Preset, Rectilinear multiturn, Antex Soldering irons. switches, rotary, slide, toggle, etc. Cable, veroboard.

POTENTIOMETERS

Linear or Log	Single	Double
Rotary Pots	17p	45p
Rotary Switched	25p	—

★★SPECIAL OFFERS★★

MINIATURE MAINS TRANSFORMER.
PRI 240V. SEC. 12V, 100MA. Manuf. Hinchley
Size: 36 x 45 x 40mm. F.C. 53mm.
Price 1-65p. 100-60p ea. 1,000-50p ea. 10,000-40p ea.

3 CORE PVC INSULATED MAINS CABLE. GREY ML6650, 3x7/0-2mm. Price 100m-£4.50, 1000m-£35, 10,000m-£330.

0.47 mfd. 50V MYLAR FILM CAPACITOR.
Size 1" x 0.35" x 0.65" P.C. Mount. Price 100-4p ea. 1000-3p ea.

240V. A.C. SOLENOID. Reversible operation; twin coil. Size approx. 2 1/2 x 1 1/2 x 1 1/2in. 75p.

30 unmarked OC71 transistors £1.00
25 Unmarked 250V Zener diodes, 4-7V, 5-1V, 6-2V, 7-5V, 9-1V, 10V, Measured and tested £1.00

Please state voltage required.
50 GE Diode OA47 equivalent. £1.00

TRANSFORMER: DOUGLAS PRI, 0, 115, 200, 220, 240 SEC. 25-0-25-0-6V, 2 1/2A, £4.50 + 50p p.p.

TRANSFORMER
PRI, 0, 115, 160, 205, 225, 245. SEC. 35-0-35, 1-2A £4.50 + 50p p.p.

MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)
Type 092 0-8-2-2p
801 0-8-2-2p
991 0-5-1-3p } Price 10p ea.

QUANTITY DISCOUNTS PLEASE TELEPHONE
1000pF Feedthrough capacitor 5p ea.
Miniature tubular P.C. trimmers
3-5-13pF
6-30pF
4p c/o Varley 700Ω relay 10p ea.
50p ea.

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROBORD WITH BASE & P.K. SCREWS

AB7	2 1/2" Long	5 1/2" Wide	1 1/2" High	55p
AB8	4"	4"	1 1/2"	55p
AB9	4"	2 1/2"	1 1/2"	55p
AB10	4"	5 1/2"	1 1/2"	55p
AB11	4"	2 1/2"	2"	65p
AB12	3"	2"	1"	50p
AB13	6"	4"	2"	75p
AB14	7"	5"	2 1/2"	90p
AB15	8"	6"	3"	£1.16
AB16	10"	7"	3"	£1.32
AB17	10"	4 1/2"	3"	£1.10
AB18	12"	5"	3"	£1.32
AB19	12"	8"	3"	£1.80

ALUMINIUM BOXES WITH SLOPING TOP PANEL—IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20 8" Long 9" Wide 3 1/2" High at back £2.20
2" High at front 6" Slope to front
With P.K. Screws

AB21 As above but 10" long £2.20
AB22 As above but 12" long £2.60

20 CORE CABLE + SCREEN, SIZE 14/0076
60p + VAT per yard Phone for postage rate

LARGE SELECTION OF MOVING IRON METERS IN STOCK
From 5A-300 Amp. Send for list.

TEAK VENEERED SPEAKER CABINET
Suitable for 8" + Tweeter. Approx. size 8" x 12" x 8".
Price £5.50 + 70p P. & P. each.

TEAK VENEERED SPEAKER CABINET
Suitable for 12" + Tweeter. Approx. size 15" x 18" x 9".
Price £9.00 + £1.00 P. & P. each.

★ ★ SPECIAL OFFERS ★ ★

MULTICORE CABLE. 25-way, individually screened, 14/0076. £1.00 per yard + V.A.T. Postage by weight.

IMHOFF 19" RACKING CABINETS. 13 1/2" high, 22" wide, 13" deep. Brand new. £10.00 each + V.A.T. Carriage £1.00.

SIEMENS CONTACTORS. Over 1,000 in stock. All types. Phone or write for details.

METAL OXIDE RESISTORS TR4/5/6 in stock. All values. 1-off price 3p each. Discount on quantity.

10 TURN TRIMPOTS by Bourns, Mec, Painton, etc. All values in stock. 50p each. Discount on quantity.

9-WAY FULLY STABILISED BATTERY CHARGERS.
24" L, 7 1/2" H, 7" D. Price £14.00 each. Carriage £1.00 + V.A.T.

4-WAY BATTERY CHARGER. Type CC 999. Charges up to 8 of the above battery cassettes. Price £14.00 + V.A.T.

12-WAY BATTERY CHARGER. Type CC 999. Charges up to 12 of 13-4V DEAC batteries. Metered battery condition check. Price £25.00 + V.A.T.

We are open from 9.30 a.m.—6.00 p.m. Monday-Saturday.

We have the largest retail selection of components available. Phone or write if you are in difficulties obtaining a particular component.

C.O.D. service welcome. All mail order by return. Official orders welcome to Government establishments, Education Authorities, etc.

01-994-6275

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO AND MONO

Plays 12", 10" or 7" records
Auto or Manual. A high
quality unit backed by BSE
reliability with 12 months*
guarantee. AC 500/250V.
Size 18 1/2 x 11 1/2 in.
Above motor board 8 1/2 in.
Below motor board 8 1/2 in.
With STEREO/MONO CARTRIDGE



£7-95 Post 45p.

PORTABLE PLAYER CABINET

Modern design. Size 18" x 15" x 7" reline
covered. Large front grille. Hinged Lid. Chrome
fittings. Motor board out for Garrard deck.
Few only, in red and black.

£4-50

Post 45p.

SOLID MAHOGANY PLINTH

With P.V.C. Cover. Cut out for most
B.S.E. or Garrard decks.
Size 12 1/2 x 14 1/2 x 7 1/2 in.


£6-50

Post 45p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with
separate pick-up arm fitted
LF/78 turnover mono
compatible cartridge.

£4-95 Post 45p

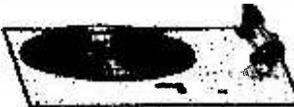

R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/compat. cartridge. Base-
plate. Size 11 1/2 x 8 1/2 in. Turntable. Size 7 in diameter. A/C
mains. 220/250V motor has a separate winding 14 volt to
power a small amplifier.

£6-50 Post 45p

COMPLETE STEREO SYSTEM

Two full size loudspeakers 18 1/2 x 10 x 8 1/2 in. Player
unit clips to loudspeakers making it extremely compact.
Overcut size only 18 1/2 x 10 x 8 1/2 in. 3 watts per
channel, plays
all records 33
rpm 45 rpm.
Separate vol-
ume & tone
controls 240V
AC mains

Attractive
Teak finish
Weight 10lbs.



Bargain Price
£25
85p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES

Single pole two-way Surface mounting
with fixing screws. Will replace existing
wall switch to give light for return home,
garage, automatic anti-burglar lights etc. Variable knob
Turn on or off at full or intermediate settings.
Fully insulated. Makers last list price £4-50. Brand new and
fully guaranteed. OUR PRICE **£2-20** Post 35p.



CASSETTE RECORDER MOTOR ONLY. 6 Volt.
Will replace many types. Ideal for models. £1-25.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in sides
6 x 4 in 45p; 8 x 4 in 53p; 10 x 7 in 65p; 12 x 8 in 85p;
14 x 9 in 90p; 16 x 6 in 90p; 12 x 8 in 50p; 16 x 10 in £1.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 12p; 8 x 6 in 19p;
14 x 8 in 29p; 10 x 7 in 24p; 12 x 8 in 25p; 12 x 8 in 34p;
16 x 6 in 34p; 14 x 9 in 40p; 12 x 12 in 47p; 16 x 10 in 60p.

1 1/2 inch DIAMETER WAVECHANGE SWITCHES 45p. EA.
2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way.
1 p. 1 2-way, or 4 p. 2-way, or 4 p. 2-way.
TOGGLE SWITCHES, sp. 20p; dp. 25p; dp. dt. 30p.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape P.U., Guitar, etc. Can be used with
Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size
1 1/2 x 1 1/2 x 1 1/2. Response 25 c.p.s. to 25 Kc/s, 26 db gain.
For use with valve or transistor equipment. **£1-25** Post
Full instructions supplied. Details S.A.E. 20p

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V 15p	250/25V 14p	16+16+16/275v 45p	
4/350V 14p	500/25V 50p	50+50/300V 50p	
8/350V 18p	100+100/275v 65p	32+32/450V 60p	
16/350V 25p	150+200/275v 70p	100+50+50/350V 85p	
32/500V 50p	8+8/450V 25p	32+32+32/850 65p	
25/25V 10p	8+16/450V 25p	900MFD/350V 95p	
50/50V 10p	16+16/450V 40p	4700/63V 85p	
100/25V 10p	32+32/350V 40p		

LOW VOLTAGE ELECTROLYTICS.
22, 25, 50, 68, 150, 470, 500, 680, 1500, 2200, 3300, mid
all 2 volt 10p.
22, 25, 50, 68, 150, 200, 220, 330, 470, 680, 1000, 1500,
2200, mid all 10 volt 10p ea.
220, 330, 1000, 4700, mid all 4v. 10p ea.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 25p; 50V 47p; 100V 70p.
2000mF 4V 25p; 25V 45p; 50V 57p; 4700/63V 95p.
2500mF 50V 85p; 3000mF 25V 47p; 50V 85p.
5000mF 6V 25p; 12V 42p 25V 75p; 35V 85p; 50V 95p.
500V-0-001 to 0-05 4p; 0-1 10p; 0-25 12p; 0-47 25p.
CERAMIC 1pF to 0-01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V-01 7p; 0-5 15p; 1mF or 2mF 150V 15p.
MICRO SWITCH pole changeover 20p
MICRO SWITCH sub min 25p.
TWIN GANG. "0-0" 208pF +178pF, £1-10.
Slow motion drive 385pF + 385pF with 25pF + 25pF, 50p;
500pF standard twin gang 75p. 120 PF twin gang 50p.

ELAC 9 x 5 in. HI-FI SPEAKER. TYPE 59RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE

£2-95

NEON PANEL INDICATORS. 250V AC/DC Amber, 30p
RESISTORS 1 w., 1/2 w., 1/4 w., 20%, 1p; 2 w. 5p. 10 Ohm to 10M-
HIGH STABILITY. 1/2 w. 2% 10 ohms to 8 meg., 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg. 4p.
WIDE-WAUGE RESISTORS. 5 watt, 10 watt, 15 watt,
10 ohms to 100K, 10p each to 8-2 ohms 10p.
TAPE OSCILLATOR COIL. Valve type, 35p.
FERRITE ROD 8" x 1/2" 20p; 6" x 1/2" 20p; 3" x 1/2" 10p.

MAINS TRANSFORMERS ALL POST 40p each

250-0-250V 80MA. 6-3-2A 22-50.
250-0-250 80 mA. 6-3 2-5 A. 6-3 v. 1a. or 5 v. 2 a. £4-00
250-0-350 80 mA. 6-3 v 3-5 A. 6-3 v. 1a. or 5 v. 2 a. £5-00
300-0-300 v. 120 MA. 6-3 v. 4 A. C.T. 6-3 v. 2 a. £6-00
MINIATURE 200 v. 20 MA., 6-3 v. 1 a. 2 1/2 x 2 1/2 in. 75p
MIDGET 220 v. 45 mA., 6-3 v. 2 a. 2 1/2 x 2 1/2 in. 80p
HEATER TRANS. 6-3 v. 3 amps. £1-20 1 amp. 55p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs
at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £4-00
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £4-00
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £6-00
3 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £7-50
5 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £9-75
3, 5, 8, 10, 12, 15 or 2-5 v. 5 amp. £1-80 0-0-5 v. 500 mA
90p 9 v. 1 amp. 95p 12 v. 300 mA 75p 12 v. 500 mA
85p 12 v. 750 mA 95p. 40 v. 2 amp. tapped 10v. or 30 v.
£2-50. 20V 3 amp. £2. 40V 3 a. £2-50. 22V 0 22V 4 a. 23.
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v.
150w. £4-00; 500w. £7-50; 750w. £16-00; 1000w. £18-00.
CHARGER TRANSFORMERS. Input 200/250V.
for 6 or 12v. 1 amp. £1-50; 2 amp. £1-80; 4 amp. £2
BATTERY CHARGERS. Ready built with leads and clips
4 amp. £4; 5 amp. £4-50.
FULL WAVE BRIDGE CHARGER RECTIFIERS:
6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240v. Secondary 0-240v. 3 amps. 720
watts. Insulated terminals. Varnish impregnated. Fully
enclosed in steel case with fixing feet.
Famous make. (Value £10) OUR PRICE **£12** Carr.
Suitable for outside use. 95p

SET OF 3 MOTORS FOR COLLARO STUDIO 115 volt TAPE DECK £1-50 Post 50p.

VOLUME CONTROLS 80 Ohm Coax 5p. yd.
5 K. ohms to 2 Meg. LOG or
LIN. L/S 20p. D.P. 35p.
STEREO L/S 55p. D.P. 75p.
Edge 5K. S.P. Transistor 25p

BRITISH AERIALITE
AERIAL-ALIE SPACED
40 yd. 22p. 60 yd. 23.
FRINGE LOSS LOSS 10p per
yd Ideal 625 and colour.

Wiresound controls 1 1/2 in. diam. 3 watts. 10 ohms to 100K
British made with long spindles 1/2 in. dia 80p ea.
DUAL CONCENTRIC POT 500K LOG + 500K LIN D.P.
switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in. 75p.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters.
And crossover. 10
watt. Size 3 or 8
15 ohm. As illustrated. Post 35p

With sized tweeter cone and ceramic
magnet. 10 watt.
Bass res. 45-60 cps.
Flux 10,000 gauss,
Size 3 or 8 or 15 ohm. Post 35p



Bookshelf Cabinet £6-60

Fluted wood front 16 x 10 x 7 1/2 in. Teak Veneer Post 45p

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet
Special Rubber cone surround.
Frequency response 30-15,000 cps.
Ideal P.A. Columns,
Hi-Fi Enclosure Systems, etc.
Suitable cabinet 12 x 8 x 6 £4-00.
Suitable Tweeter £2-00.



ELAC CONE TWEETER

The moving coil diaphragm gives a good
radiation pattern to the higher frequencies
and a smooth extension of total response
from 1,000 cps to 18,000 cps. Size 8 1/2 x
3 1/2 x 2 1/2 in. deep. Rating 10 watt, 8 ohm.
Crossover £1-60
Post 20p **£1-90**

GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone.
Heavy ceramic magnet. Bass
resonance 35 cps. Frequency
response 30-8,000 cps.
Ideal bass unit for £3-75
Hi-Fi systems



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1-25; 6 in. £1-50;
8 x 5 in. £1-60; 8 in. £1-75; 10 x 6 in. £1-90; 10 in. £2-00.
SPECIAL OFFER LOUDSPEAKERS! All Brand New.
3 ohm. 2 1/2 in; 3 1/2 in; 5 in. 3 ohm. 2 1/2 in; 2 1/2 in; 5 in x 3 in;
5 in. 15 ohm. 3 1/2 in; 5 in; 6 x 4 in; 5 in x 3 in; 7 x 4 in; 8 x 5 in.
25 ohm. 2 1/2 in; 3 in; 5 in; 5 in. 35 ohm. 8 in; 5 in.
80 ohm. 2 1/2 in; 2 1/2 in. 120 ohm. 3 in. **£1 EACH.**

LOUDSPEAKER VOLUME CONTROL 15 ohm 10 watt with lin lock threaded bush for wood panel mounting 65p.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in.
diameter 4W £2-50 10 in. diameter 6W £2-95; Post 25p.
12 in. diameter, 6W, £3-50; 3 or 8 or 15 ohm models.
SPEAKER COVERING MATERIALS. Samples large S.A.M.
Horn Tweeters 2-16Kc/s. 10W 8 ohm or 16 ohm £2-60.
De Luxe Horn Tweeters 2-18 Kc/s. 15W, 8 ohm 44-00.
TWO-WAY 3,000 c.p.s. CROSS OVERS 3, 8 or 16 ohm £1-60.
3-WAY CROSSOVER 850 cps and 3000 cps (25 watt) £1-95.

GOODMANS CONE TWEETER 18,000 cps. 25 watts. 8 ohm. Price **£3-30.**

ELECTRO MAGNETIC PENDULUM MECHANISM

1-5v d.c. operation over 250 hrs. continuous on SP2 battery.
Fully adjustable swing and speed. Ideal for any teaching
electro magnetism or for metronome; strobe etc. 95p, Post 20p

R.C.S. VALVE AMPLIFIER
2 Stage Triode Pentode valve, 3 watts 8 ohm output. Volume
on/off and tone controls AC mains. Complete and tested.
With Loudspeaker. **£4-50** Post 35p.

WEYRAD COILS		
P50/1A0-60p.	E24W 85p.	Twin Gang £1-10.
P50/2CC-40p.	OFT1 85p.	Printed Circuit 85p.
P50/3CC-40p.	LEDT4. 65p.	

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p
OUTLET BOXES, SURFACE MOUNTING 85p.
BALANCED TWIN RIBBON FEEDER 200 ohms, 7p yd.
JACK SOCKET 8id. open-circuit 15p, closed circuit 25p;
Chrome Load Socket 45p. Phone Plugs 10p. Phone Socket 8p
JACK PLUGS 8id. Chrome 20p; 3-5mm Chrome 15p. DIN
SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS
Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p.
VALVE HOLDERS 5p; CHASSIS 10p; GANS 5p.

FM/VHF AERIAL FEEDER CABLE

800 ohm suitable for stereo 7p per yard.

BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors.
ready aligned—requires 10-7
Mc/s I.F. Complete with tuning gang.
Connections supplied but some
technical experience required.
SUITABLE I.F. STRIP £4-95. **Our Price**
£3-95 Post 20p.

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 30p. CALLERS WELCOME

RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p. Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

£5-75 THE PAIR. Post 45p.
(Available separately.
Woofer £4-25; Tweeter
Post 45p
£1-90).
Comprising a fine example of a Woofer
1 1/2" x 6 1/2" with a massive Ceramic
Magnet. 44oz. Gauss 13,000 lines.
Aluminium Cone centre to improve
middle and top response. Also the E.M.I.
Tweeter 3 1/2" square has a special
lightweight paper cone and magnet flux
10,000 lines. Crossover condenser and
full instructions supplied.
Impedance Standard 8 ohms
Maximum power 13 watts
Useful Response 25 to 18,000 cps
Bass Resonance 45 cps
SUITABLE ENCLOSURE 20 x 13 x 9in.
MODERN DESIGN, TEAK WOOD FINISH.



£10-50
Post 75p

ELAC 8in. or 10 x 6in. HI-FI SPEAKER



Dual cone plasticized roll sur-
round. Large ceramic magnet.
50-16,000 cps. Bass resonance
55 cps. 8 ohm impedance.
8in. 10 watts **£3-75**

**TEAK VENEER HI-FI SPEAKER CABINETS
Fluted Wood Fronts**

MODEL "A". 20 x 13 x 12in.
For 12in. dia. Post
10in. speaker. **£14-00** 75p

MODEL "B". 16 x 10 x 7in.
For 13 x 8in. or Post
8in. speaker. **£6-60** 45p

LOUDSPEAKER CABINET
WADDING 18in. wide, 90p ft.

BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft.
HI-FI CABINET £18-50. Carr. £2 each. Few only.
Size 30 x 20 x 12in. Teak Finished Fluted Front.

TEAKWOOD LOUDSPEAKER FRONT GRILLS
Modernize your cabinets with the grooved look. Sizes—
12 1/2" x 10 1/2"—75p. 10 1/2" x 7 1/2"—45p.

**BARGAIN 4 CHANNEL
TRANSISTOR MONO
MIXER.** Add musical
Highlights and sound effects
to recordings. Will mix
Microphones, records, tape
and tuner with separate
controls into single output.
9 volt battery operated.
£4-50
STEREO VERSION OF ABOVE £6-50.



**R.C.S. STEREO FM TUNER
BRITISH MADE**



This completely cased mains powered Hi-Fi
Tuner with brushed aluminium face is British
made using the latest circuitry. Bargain **£23**
Post 45p.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor
Push-Pull Ready built with volume, treble and
bass controls. 18 volt battery operated. **£3-50**

**WAFER HEATING ELEMENTS
THIN**

OFFERING 1001 USES for every type of heating and
drying applications in the home, garage, greenhouse,
factory (available in manufacturing quantities). Approx.
size 1 1/2" x 3 1/2" x 1/4". Operating voltage 200/250V, a.c.
250 watts approx. Printed circuit element enclosed in
asbestos fitted with connecting wires. Completely flexible
providing safe Black heat. British-made for use in photo-
copiers and print drying equipment.
Ideal for home handymen and experimenters. Suitable
for Heating Pads, Food Warmers, Convector Heaters, etc.
Must be clamped between two sheets of metal or asbestos,
etc., to make efficient clothes dryers, towel rails—ideal for
siding cupboards. Ideal for anti-frost devices for the garage
—preventing frozen radiators or acting as oil sump heater.
Use in the greenhouse for seed raising and plant protection.
Invaluable aid for bird houses, incubators, etc., etc. Can
be used in series for lower heat. Or in parallel for higher
heat applications.

ONLY 40p EACH (FOUR FOR £1-50)
ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £8-50



30-14,500 c/s. Post 40p
12in. double
cone woofer and tweeter cone
together with a BAKER
ceramic magnet assembly
having a flux density of
14,000 gauss and a total flux
of 145,000 Maxwells. Bass
resonance 40 c/s Rated 20
watts. NOTE: 8 or 8 or
15 ohms must be stated.

Module kit, 30-17,000 c/s
with tweeter, crossover, baffles
and instructions. **£10-95**

Please state 8 or 8 or 15 ohms. Post 45p

**"BIG SOUND"
BAKER SPEAKERS**

Robustly constructed to stand up to
LONG periods of electronic power.
As used by leading groups and discos
Useful response 30-13,000 cps.
Bass Resonance 55 cps.

GROUP "25" £7-75
12in. 25 watt
8, 8 or 15 ohms.

GROUP "35" £8-50
12in. 35 watt
8, 8 or 15 ohms.

GROUP "50" £16-50
15in. 50 watt
8 or 15 ohms.

GROUP 50/12in. £12-95
50 watt 8 or 15 ohms

Post 50p
Group + PA Cabinets in stock
Send for Leaflet.



**MAJOR 100 WATT
ALL PURPOSE
TRANSISTOR
AMPLIFIER**

All purpose transistorized.
Ideal for Groups, Disco and P.A.
4 inputs speech and music. 4 way
mixing. Output 8/15 ohm. a.c. Mains.
Separate treble and bass controls.
Guaranteed. Details SAE. **£49**
Carr. £1-00



NEW MODEL—MAJOR 50 WATT £39-95
Carr. £1.

4 inputs 2-way mixing. 2 outputs separate treble
and bass controls. Ideal disco or P.A. amp.

**DE LUXE 100 WATT
VALVE AMPLIFIER CHASSIS**

4 input 10 wide range controls. For Mikos, Discos, Organs
Guitars, etc. 4, 8 & 15 ohm loudspeakers matching 200-00.

THE "INSTANT" BULK TAPE
ERASER & HEAD DEMAGNETISER.
Suitable for cassettes, and all sizes of
tape reels. A.C. mains 200/250V.
Leaflet S.A.E. **£3-75** Post
80p



QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 2in thick wood cabinet. Size
18 1/2in x 18 1/2in x 8 1/2in. Weight 23lbs. This
cabinet features a wide mesh Silver Grill
covering a separate compartment for mount-
ing Tweeters or Mid-Range Horn. The fully
sealed bass compartment is cut out for
6 1/2inch Woofer. £7-50 Carr. 85p.
Rosewood Version £9-50 Carr. 85p.
Baffle could be cut to take larger speaker.



SPECIAL OFFERS

100 Ohm 20 watt Rheostat 2 1/2in diam. Ceramic Former.
Screw Terminals 1/4in. diam. spindle. **95p**. Post 25p.
AC mains relay 3 pole change over **75p**.

REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 48 Watt.
spindle 1 1/2" x 7/32", size 3 1/2" x 3". **£2-25**
As illustrated. 240v. AC mains. Post 35p

E.M.I. TAPE MOTOR
4 pole, 240 v. 135 mA. Size 3 1/2" x 2 1/2" x 2 1/2". **£1-85**
1200 rpm. Spindle 1/2in diameter.
120v version 21. Post 30p

**BAKER HI-FI SPEAKERS
HIGH QUALITY — BRITISH MADE**

**REGENT
12in. 15 watts**

An inexpensive unit for the
beginner in high fidelity and
for general purposes. May be
used to improve any Radio,
Amplifier, Hi-Fi or Television
receiver.
Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps
8 or 15 ohm models.

£7-75 Post
40p

**DE-LUXE Mk II
12in 15 watts**

Especially designed to provide
full range reproduction at an
economical cost. Suitable for
use with any high fidelity
system. Built-in concentric
tweeter cone.
Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£9-75 Post
40p

**SUPERB
12in. 20 watts**

A high quality loudspeaker,
its remarkable low cone
resonance ensures clear
reproduction of the deepest
bass. Fitted with a special
copper drive and concentric
tweeter resulting in full
range reproduction with
remarkable efficiency in the
upper register.
Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£13-80 Post
50p

**AUDITORIUM
12in. 25 watts**

A full range reproducer for
high power, Electric Guitars,
public address, multi-speaker
systems, electric organs.
Ideal for Hi-Fi and Disco-
theques.
Bass Resonance 35cps
Flux Density 16,000gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£12-9 Post
50p

**AUDITORIUM
15in. 35 watts**

A high wattage loudspeaker
of exceptional quality with a
level response to above
2,000 cps. Ideal for Public
Address, Discotheques, Elec-
tronic instruments and the
home HI-FI.
Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£16-50 Post
50p

Hi-Fi Enclosure Manual containing plans, designs, cross-
over data and cubic tables. 60p. Post 3p.



CUSTOMERS FREE CAR PARK

OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-2-30

SPECIALISTS 337 WHITEHORSE ROAD . GROYDON

(Exports Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

Another!
winner!

fane **MODE ONE** Mk II

HIGH FIDELITY LOUDSPEAKER KIT



Mk II VERSION

Consisting of a Fane Model 805 ultra-low resonance 8" speaker unit with PVC cone surround, and a Model 303/8 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

NO SOLDERING REQUIRED

Recommended
retail price

£11.99
including
V.A.T.

SPECIFICATION OF UNITS

	Model 805	Model 303/8
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	2"
Magnet Flux Density	11,000 gauss	8,000 gauss
Frequency response	30Hz-8kHz	2kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

*When used in sealed cabinet

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

AMBASSADOR '35' LOUDSPEAKER UNITS

Rating 30 Watts. Employing 12" Bass and 8" x 5" Mid-range speaker plus Dome Pressure Tweeter.

£89
Pair

MARQUESS '30' LOUDSPEAKER UNIT

Rating 30 Watts. Inc. Deep Cone ultra low resonance 13" x 8" Bass Speaker and Dome Pressure Tweeter.

£75
Pair

Distributors to the wholesale
and retail trade

LINEAR PRODUCTS LTD.
Electron Works, Armley, Leeds
LS12 3SA. Tel. 630126

Manufactured by

FANE ACOUSTICS LTD.
286 Bradford Rd., Batley, Yorks.
Tel. Batley 6431

Please
send S.A.E.
for fully
descriptive
leaflet.

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- | | | |
|-------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------|-------------------------------------------------------------------------|
| <input type="checkbox"/> Build-As-You-Learn
PRACTICAL RADIO
AND ELECTRONICS
(with kit) | <input type="checkbox"/> Electronic
Engineering | <input type="checkbox"/> CITY AND GUILDS
Installations and
Wiring |
| <input type="checkbox"/> Electrical
Engineering | <input type="checkbox"/> Computer Electronics | <input type="checkbox"/> CITY AND GUILDS
Electrical
Technicians |
| <input type="checkbox"/> Electrical Installations
and wiring | <input type="checkbox"/> Computer
Programming | <input type="checkbox"/> CITY AND GUILDS
Telecommunications |
| <input type="checkbox"/> Electrical
Draftsmanship | <input type="checkbox"/> General Radio and
TV Engineering | <input type="checkbox"/> Radio Amateurs' Exam
etc. etc. |
| <input type="checkbox"/> Electrical
Mathematics | <input type="checkbox"/> Radio Servicing,
Maintenance and
Repairs | |
| | <input type="checkbox"/> Transistor
Technology | |

To ALDERMASTON COLLEGE Dept. EPW-04, Reading RG7 4PF **EPW. 04**

NAME (Block Capitals Please) _____

ADDRESS _____

POST CODE _____

Other subjects _____ Age _____
Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

QUALITY* STEREO SOUND

ALMOST **1/2 PRICE OFFER!** SOLENT AUDIO SYSTEM



*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £3.00. Send £8.00 today.

Chassis only available for cash at £35.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every complete order.

LEWIS radio PW/6/75 100 CHASE SIDE SOUTHGATE
LONDON N14 5PL Telephones: 01-882-1644

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

TRANSISTOR PACKS ALL AT 50p EACH TESTED & GUARANTEED

B79	4	IN4007 Sil. Rec. diodes, 1,000PIV 1 amp. plastic	H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC945
B81	10	Reed Switches, 1 long 2" dia. High-speed P.O. type	H41	2	BD131/BD132 Complementary Plastic Transistors
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	H65	4	40361 Type NPN Sil. Transistors TO-5 can comp. to H66
H38	30	Short lead, NPN Silicon Planar Ex Equipment.	H66	4	40362 Type PNP Sil. Transistors TO-5 can comp. to H65

UNMARKED & UNTESTED

B1	50	Germanium Transistors PNP, AF and RF	H6	40	250mV zener diodes. At least 20 good.
B66	150	Germanium Diodes Min. glass type	H15	30	Silicon rectifiers 750mA assorted. Top-hat type.
H68	10	Experimenter's pack of I.C.s, D.T.L. and T.T.L. (some marked)	H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	H67	10	3819N Channel FET's plastic case type

PLASTIC POWER TRANSISTORS

40 WATT SILICON				
Type	Polarity	Gain	VCE	Price
40N1	NPN	15	15	20p
40N2	NPN	40	40	30p
40P1	PNP	15	15	20p
40P2	PNP	40	40	30p

90 WATT SILICON				
Type	Polarity	Gain	VCE	Price
90N1	NPN	15	15	25p
90N2	NPN	40	40	35p
90P1	PNP	15	15	25p
90P2	PNP	40	40	35p

NEW X-HATCH GENERATOR Mk. 2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 2". Operates from 3 U.2 type batteries (extra).

P/P add 30p Complete kit **£7-93** Ready built unit-only **£9-93**

TO CLEAR

Hundreds of various portable transistor radio chassis with FM & AM tuning. Ideal for experimenters. All in going order, but no instructions or tuning drives. A cheap way to make a portable. Each £1.

SUNDRY

Capacitor Discharge Ignition Kit £7-50. 8 assorted relays £1-00. Rev counter device (for cars) £1-00. U.H.F./TV Tuner Units £2-50. L.M.380 Audio I.C. £1-00 and technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. This must be added to total value of your order including postage at current rate. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 20p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED



challenging values!

Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.

AMPLIFIER MODULES

Pre-amplifiers; tone control

- SS.100 Active tone control unit to provide bass, treble, balance and volume controls **£1-60**
- SS.101 Pre-amp for ceramic cartridge, tape and radio **£1-60**
- SS.102 Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction ± 1 dB at 1K **£2-25**

POWER AMPLIFIERS

- SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6 to 22. Size 3 1/2" x 2" **£1-75**
- SS.103-3 Stereo version of above using one I.C. on each channel **£3-25**
- SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2 1/2" x 1 1/2" **£1-95**
- SS.110 Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26 to 32V. **£2-40**
- SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0.15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms **£3-60**

BUILD A STEREO FM TUNER!

- SS.201 Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V. **£6-25**
- SS.202 I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4.5 to 14V. **£5-25**
- SS.203 Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c. **£5-62**








POWER SUPPLY STABILIZER

- SS.300 Add this to an un stabilised supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential on your audio and special systems. Money saving and very reliable **£3-25**

ALL MODULES TESTED AND GUARANTEED WITH INSTRUCTIONS

MAINS TRANSFORMERS FOR ABOVE

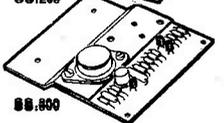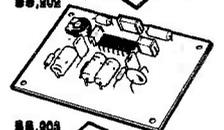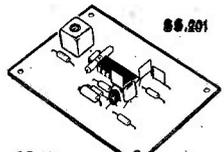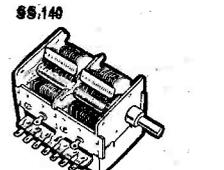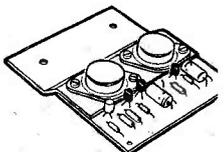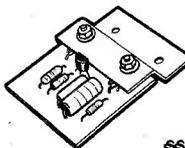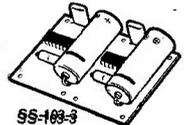- Add 35p per transformer for PIP
- Type A 18V/1A (Suit SS.103) **£1-50**
- Type B 25V/2A (Suit SS.110) **£2-00**
- Type C 30V/2A (Suit SS.140) **£3-25**
- Bridge Rectifiers—Type A 27p. Types B & C 38p



To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose

Name

Address

PW6

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

Prr. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £
07	20	1 8	7.0 x 6.0 x 6.0	2.80 38
149	60	3 12	9.9 x 7.7 x 8.6	4.37 45
150	100	5 0	9.9 x 8.9 x 8.6	4.89 45
151	200	8 0	12.1 x 9.3 x 10.2	8.13 53
152	250	13 12	12.1 x 11.8 x 10.2	9.83 73
153	350	15 0	14.0 x 10.8 x 11.8	11.88 73
154	500	19 8	14.0 x 13.4 x 11.8	13.65 91
155	750	29 0	17.2 x 14.0 x 14.0	20.51 * *
156	1000	38 0	17.2 x 16.6 x 14.0	29.15 * *
157	1500	46 0	21.6 x 13.4 x 18.1	33.23 * *
158	2000	60 0	21.6 x 15.3 x 18.1	37.07 * *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.67 30
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.90 38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	4.12 45
66	300	6 4	9.9 x 9.6 x 8.6	"	5.82 53
67	500	12 8	12.1 x 11.2 x 10.2	"	8.82 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	13.68 91
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.31 * *
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.20 * *
73	3000	40 0	21.6 x 13.4 x 18.1	"	35.09 * *

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets, 20VA £3.23 pp 8p
500VA £10.45 pp 8p 1000VA £17.51 via B.R.S.

TRANSFORMERS

PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £
111	0.5	1 4	4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.47 30
213	1.0	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	2.74 30
71	2	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.29 38
78	4	2 2	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.86 38
70	6	3 3	8.9 x 8.0 x 7.7	0-12V at 3A x 2	4.12 45
108	8	4 5	9.9 x 8.9 x 8.6	0-12V at 4A x 2	4.56 45
72	10	5 8	9.9 x 9.6 x 8.6	0-12V at 5A x 2	5.14 60
116	12	6 6	12.1 x 10.2 x 8.6	0-12V at 5A x 2	5.52 53
17	16	8 8	12.1 x 9.9 x 10.2	0-12V at 8A x 2	7.28 60
115	20	10 11	14.0 x 9.6 x 11.8	0-12V at 10A x 2	10.39 73
187	30	15 15	15.8 x 14.0 x 11.8	0-12V at 15A x 2	13.59 85
226	60	30 32	17.2 x 15.3 x 14.0	0-12V at 30A x 2	16.83 * *

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.81 30
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.40 38
3	2.0	3 4	8.9 x 7.7 x 7.7	"	3.49 38
20	3.0	4 8	9.9 x 8.3 x 8.6	"	4.53 45
21	4.0	6 4	9.9 x 9.6 x 8.6	"	5.13 53
51	5.0	6 12	12.1 x 8.6 x 10.2	"	6.41 53
117	6.0	8 0	12.1 x 9.3 x 10.2	"	7.16 60
88	8.0	12 0	12.1 x 11.8 x 10.2	"	9.90 67
89	10.0	13 12	14.0 x 10.2 x 11.8	"	9.87 73

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.58 30
103	1.0	2 12	8.3 x 7.4 x 6.1	"	3.38 38
104	2.0	5 8	8.3 x 8.9 x 8.6	"	4.68 45
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.81 53
106	4.0	10 0	12.1 x 10.5 x 10.2	"	7.60 67
107	6.0	12 0	14.0 x 10.2 x 11.8	"	12.10 67
118	8.0	18 0	14.0 x 12.7 x 11.8	"	12.98 85
119	10.0	25 0	17.2 x 12.7 x 14.0	"	16.99 * *

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.33 38
126	1.0	3 4	8.9 x 7.7 x 7.7	"	3.41 38
127	2.0	6 4	9.9 x 9.6 x 8.6	"	5.08 45
125	3.0	8 12	12.1 x 9.9 x 10.2	"	7.32 60
123	4.0	13 12	12.1 x 11.8 x 10.2	"	8.75 67
40	5.0	12 00	14.0 x 10.2 x 11.8	"	9.75 73
120	6.0	15 8	14.0 x 12.1 x 11.8	"	11.30 85
121	8.0	25 00	14.0 x 14.7 x 11.8	"	15.00 * *
122	10.0	25 00	17.2 x 12.7 x 14.0	"	17.52 * *
189	12.0	29 00	17.2 x 14.0 x 14.0	"	19.98 * *

MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA	Weight lb oz	Size cm.	VOLTS	P & P £
238	200	2 2	2.8x2.6x2.0	3-0-3	1.54 10
212	1A, 1A	1 4	6.1x5.8x4.8	0.6-0.6	1.84 30
13	100	1 4	3.9x2.6x2.9	9-0-9	1.41 13
235	330,330	4	4.8x2.9x3.5	0.9, 0.9	1.56 19
207	500, 500	1 00	6.1x5.4x4.8	0.8-9, 0.8-9	1.92 30
208	1A, 1A	1 12	7.0x6.4x6.1	0.8-0.8-9	3.30 38
232	200, 200	1 4	4.8x2.9x3.5	0.15, 0.15	1.43 19
214	300, 300	1 4	6.1x5.8x4.8	0.20, 0.20	1.93 30
221	700 (D.C.)	1 8	7.0x6.1x6.1	20-12-0-12-20	2.17 38
206	1A, 1A	2 12	8.3x7.7x7.0	0-15-20, 0-15-20	3.46 38
203	500, 500	2 4	8.3x7.0x7.0	0-15-27, 0-15-27	3.00 38
204	1A, 1A	3 4	8.9x7.7x7.7	0-15-27, 0-15-27	3.85 38

* Carriage via BRS

PLEASE ADD 8% FOR V.A.T.
INCLUDING P. & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* + VE AND - VE GROUND

Here's the new, improved version of the original Scorpio Electronic Ignition System - with a big plus over all the other kits - the Electro Spares Kit is designed for both positive and negative ground automotive electrical systems. Not just -ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car or motor cycle.

When your Scorpio Mk. 2 is installed, you instantly benefit from all these Scorpio Mk. 2 advantages:

- ★ Easier starting from cold ★ Firmer even with wet or oiled-up plugs ★ Smoother running at high speed ★ Fuel saving
- ★ More power from your engine ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £10.85 inc. VAT and p & p.
Ready Made Unit £13.65 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

PE FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits, Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

PE GEMINI STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

★ All components as specified by original authors, and sold separately if you wish.

★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 9p postage.

★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North

288 ECCLESALL RD., SHEFFIELD S11 8PE(B)

Tel: Sheffield (0742) 668888




TRAMPUS

Electronics Ltd.
WINDSOR, BERKS
58/60 GROVE RD.
SENB. C.W.O. ADD VAT TO ALL PRICES IN U.K. P&H 15p. EXPORTS 50p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS... LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.
CATALOGUE/LIST FREE SEND SAE.
BARCLAYCARD & ACCESS * POST

Digital Displays

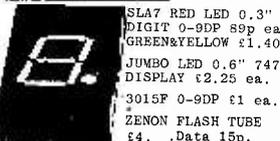

LEDS red 13P

LEDS 209 STYLE ONLY 13p ea
TIL 209 WITH CLIP RED 15p ea
TIL 211 & CLIP GREEN 20p ea
LARGE 0.2" CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR 2" ORANGE 30p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81P

TEC12 PHOTO AMP/SCMITT/RELAY
DRIVER or LED TTL INTERFACE 81p

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MM5311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder
with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 DIL14	29p	LM377	2x2Wt 2.87
555 TIMER	54p	LM380	2W AF 89p
703 RF/IP	28p	LM381	2xPre £2
709 T099	23p	LM3900	4XOPAE9p
709 DIL 14	28p	MC1303	£1.20
710 DIL 14	34p	MC1306	49p
723 Reg.	54p	MC1310&LEDE2	65
741 DIL 8	27p	MC1312 SQ	£2.10
741 DIL 14	29p	MC1330	89p
741 T099	29p	MC1339	2xPre £1
747 2x741	70p	MC1350	55p
748 DIL 8	33p	NE536	fetOPA £2
7805 5V	£1.40	NE540	Driver £1
7812 & 15	£1.40	NE550	2vRef 79p
76013 6W AF	£1	NE555	Timer 55p
8038 SIG GEN	£3	NE556	2x" £1.20
CA3028	£1	NE560	PLL £3.15
CA3045	55p	NE561	PLL £3.15
CA3048	£2	NE562	PLL £3.19
CA3052	£1.50	NE565	PLL £2.69
CA3054	£1	SN72709	709 28p
LM300	2-20V £2	SN72741	741 26p
LM301 OPA	45p	SN72748	748 33p
LM304 0-40V	£3	SN76690	IF £1
LM307 OPA	49p	SN76611	IF£1.25
LM308 HiBo	95p	TAD110	WAF £2
LM308K 5V	£1.48	TBA810	7&F 99p
LM372 IP	£1.80	ZN414	RX £1.09

SPECIAL OFFERS

2N3055 FULL HIGH SPEC	115W 37p
741C 8PIN DIL 27p	MFC4000B 33p
NE555 TIMER	55p. ZN414 RX £1.09
BC109 9p.	2N3819e 16p. BFY51 15p

740 TTL

7400 GATES	13p	7473/74/76	29p
7404 INVERT	17p	7475	45p
7401/2/10etc	14p	7490	52p
7413 SCMITT	31p	7491/2/3/4	59p
7440 BUFFER	14p	74100	74175 £1
7447 DRIVER	89p	74121	32p
7470 & 7472	29p	74123	35p
		74141(7441)73p	

TRANSISTORS & DIODES

Price each			
AC197 & 128	16p	MATCHING	16p
AC187 & 188	19p	INS. BUSH SET	10p
AD149	43p	TIP 41	70p
AD161 & 162	33p	TIP 42	88p
BC107 & 108	9p	TIP 2955	90p
BC109	10p	TIP 3055	55p
BC147/8/9	10p	TI843	see 2N2646
BC157/8/9	12p	ZTX109&301	13p
BC167/8/9	12p	1N4001	4p
BC177/8/9	18p	1N4004 & 7	7p
BC182/3/4&L10p		1N4148 & 914	4p
BC12/3/4&L11p		2N697	14p
BCY70/1/2	17p	2N7068	11p
BD131 & 132	39p	2N2646 UJT	32p
BFR51		2N2904 & 5	20p
BFR50/51	23p	2N2926royg	9p
BFR50	23p	2N3053	37p
BFR48	250V 29p	2N3055	115W 37p
BFY50/1/2	15p	2N3563 & 64	16p
BSX19/20/21	16p	2N3614	49p
MJE2955	90p	2N3702 & 3	9p
MJE3055	65p	2N3704 & 5	10p
MPU131 PUT	49p	2N3706 & 7	9p
OA91 OA81	6p	2N3708 & 9	8p
OA81 & OA91	6p	2N3710 & 11	10p
TIP 29 & 30	52p	2N3819E	FET 17p
TIP 31 & 32	69p	2N3823E	FET 17p
		2N3904/5/6	15p

FULL SELECTION IN OUR FREE LISTS.

NEW TRAMPUS FULL SPEC PAKS

PAK A	10 RED LEDS our choice	£1	
PAK B	4 741 OP AMP	£1	
PAK C	4 2N3055 £1.12	BC109 £1	
PAK D	10 BC162 £1.17	11 2N3704 £1	
PAK E	8 BFY51 £1.14	9 2N3819e £1	
PAK J	9 2N3053 £1.14	4 1N914 £1	
BZY88	400mW	1A/50V SCR	36p
ZENER DIODES	9p	TAG1/40V	55p
BRIDGE RECT		C106 & 7 SCR	D1
1A 50V	20p	4A/400V	53p
BR100 DIAC	25p	SC146D TRIAC	
		10A 400V	75p

vero

VERO PINSx36 28p
COPPER CLAD VEROBOARD 0.1"
2 1/2"x5" 29p 2 1/2"x3 1/2" 26p. 3 1/2"x3 1/2" 31p.
3 1/2"x5" 31p 3 1/2"x17" £1.50
DIL IC's BOARDS 6x4 1/2" £1.50
24 way edge connector 60p.
36 way 90p. PLAIN 3 1/2"x17" £1.
FACE CUTTER 45p. REC ETCH PAK 50p

Dalopen 69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 59p
HEATSINKS
5F/T05 & 18F/T018 5p ea. TV4 15p.
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.
TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 20pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf in
10V 5p. 25V 6p. 50V 8p. 2uf/10v 5p.
1000 uf/25v 18p. 200/500 25v 9p.
POTENTIOMETERS (POTS) AB or EGIN
LIN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6P. RESISTORS 14p
SWITCHES: SPST 18p. DPDT 25p.
DIN PLUGS ALL 12p. SOCKETS 10p.
ALL CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v/6v or 12v/12v
Only £1.34. 100mA type CT 75p.

Oil sockets

TEXAS GOLD
LOW PROFILE ea
8,14, & 16 PIN 13p
SOLDERCON STRIPS:
100 PINS 50p. 1K £3

THE FLEA THAT ROARS!!!

A Good Transmitting Aerial IS A Good Receiving Aerial!—Accepted Radio Thinking and Simple Logic—If you can't hear 'em you sure can't work 'em!! Read what the **DX ITSELF** has to say about the "**FLEA**" POWERED **230CM LONG V.F.A.**—operated continuously under "**IMPOSSIBLE**" conditions. A stamp secures the evidence!

PARTRIDGE have a complete **VFA SYSTEM**, correctly terminated for your equipment ranging from modern communications gear to a modest solid state radio. Don't be satisfied with anything less than the **PARTRIDGE WORLD RECORD ANTENNA SYSTEM!** Make your selection from the list below:-

- (Each **SYSTEM** consists of the elegant gold stove enamelled 7' 6" VFA and a matching finish **JOYMATCH A.T.U.**, despatched direct by parcel post—our risk). (All prices delivered—our risk). Prices subject to alteration without notice.
- SYSTEM 'A'** for modern Communications Receivers £28-61
- SYSTEM 'D'** for other S.W. and M.W. receivers, all types £21-02
- SYSTEM 'J'** for TXs and TCVRs up to 500w PEP 160 thru 10m (pa inpt) £35-78
- JOYMATCH A.T.U.** kit (1.6 continuous to 30 mHz) £6-27
- JOYMATCH A.T.U.** kit (500 kHz continuous to 30 mHz) £6-27
- Either kit fully assembled £7-58
- JOYMATCH "Aerial Bandswitch"** tuned aerial. MW & SW £6-27
- SUPER SENSITIVE** general coverage DX-CRYSTAL SET that REALLY WORKS, not a toy, complete with Aerial and a sensitive matching Earpiece £3-95
- COMMUNICATIONS HEADPHONES**, 8 ohms, matches most modern Comm. Rxs. £4-02
- VFA Stack Lashing (Massive VFA support on chimney stack) £2-17
- JOYMATCH** Artificial Earth (ground) switch tuned £6-27
- A.G.T.U. Artificial Earth D.I.Y. add on unit for your A.T.U. £0-63
- Radials for the A.G.T.U. cut to required band, each £0-63
- "**INVISIBLE AERIAL**" wire tough PVC covered tinned copper 22swg per 10m £0-63
- A.G.T.U. supplied fitted to **JOYMATCH A.T.U.'s** (less radials) £0-83
- FIELD STRENGTH METER**, (Japanese) £1-83
- VALVES**, complete set for 9R59DS & 9R59DE, including OA2 stabiliser £5-28

PARTRIDGE SUPER PACKAGE COMPLETE RADIO STATION FOR ANY LOCATION

Comprising:—Trio QR666 Gen. Cov. RX, Headphones, V.F.A., System 'A', all connecting cables, del. (our risk) **£158-00**



Phone 0843 62535
or 62839
(after office hours)
G3CED G3VFA



CHROMASONIC electronics

Dept. 1 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

RECTIFIERS

V	1A	3A	6A	12A
50	IN4001	6p	IN5400	15p
100	IN4002	7p	IN5401	16p
200	IN4003	9p	IN5402	17p
400	IN4004	9p	IN5404	22p
600	IN4005	11p	IN5406	26p
800	IN4006	13p	IN5407	28p
1000	IN4007	16p	IN5408	31p

BRIDGES

V	1A	2A	6A
50	20p	35p	75p
100	20p	40p	78p
200	22p	45p	90p
400	25p	50p	£1.05
600	25p	50p	£1.20
1000	38p		

TRIACS

V	4A
25v	2N6068 45p
50v	2N6069 52p
100v	2N6070 58p
200v	2N6071 63p
400v	2N6073 68p
600v	2N6075 £1.49

SOLDERING

Desolder Braid Reel 64p

Multicore
18 awg size 5 32p
22 awg size 15 36p
carton size 1 50p
" 12E1.57

Adcola Invader

L706 19 watt 1/8" bit £2.88
L646 20 watt " bit £3.13

DIN CONNECTORS

Pins	Plugs	Sockets	Line Connectors
2	9p	7p	11p
3	10p	7p	11p
4	11p	7p	11p
5 (180)	11p	8p	11p
5 (240)	11p	8p	11p
6	11p	9p	11p
7	13p	9p	11p

4mm.

Available in seven colours

Terminals 15p

Plugs 13p.

Transistor covers

TO 3	10p
TO 66	10p

HEAT SINKS

TV2 (TO66)	15p
TV3 (TO 3)	16p
TV4 (TO 126)	14p
TV5 (TO 220)	14p
5F (TO 5)	7p
173 for SL414 SL415 SL416	18p
AY-1-4	35p
10D N 400-4	

CO-AXIAL

Plug - Screened	11p
Plastic	9p
Sockets	
Chassis	10p
Surface	11p
Coupler	25p

PHONO

Sockets	
1 way	5p
2 way	7p
3 way	7p
4 way	8p
Plugs:	
Plastic Moulded	7p
Chrome Screened	12p
Coupler screened	15p

JACK

Plugs	Sockets
2.5mm *	20p 12p
3.5mm *	20p 12p
standard *	25p 15p
stereo *	27p 21p
side entry standard	48p

AUDIO I.C.'S

A brand New Audio I.C. Leaflet with Circuits and pin connections for ALL the I.C.'s listed below FREE with orders over £1.00 or 10p without



I.C. SOCKETS

UI (TBA800)	16p
UI (TBA810S)	16p
U2 (TBA810AS)	16p
U2 (LCA940)	16p
U3 (TDA2020)	35p
10D N 400-4	47p

I.C. PIN SOCKETS

I.C. pins in strips of 100. Just snip off what you need. 65p per strip

P.C. CONNECTORS

0-1" pin centres	24 way + key	supplied with ends	64p
------------------	--------------	--------------------	-----

SWITCHES

High Quality 250v 1A	Rotary 2A Mains Switches
S.P.S.T. 25p	35p
D.P.D.T. 45p	
Render	Bulgin
Subminiature Toggle S.P.D.T. 48p	push-to-make 25p
Slide D.P.D.T. 12p	
Eng Dill Switches	
1 pole 8 way 99p	
2 pole 4 way 85p	
4 pole 2 way £1.24	
Lorlin Water Switches 27p	
1 pole 12 way; 3 pole 4 way;	4 pole 2 way; 4 pole 3 way

POWER OUTPUT Watts	Supply Volts	Load Ohms	Power I.C.	Price	Pre-Amplifiers	Supply Volts	
0.25	9 16 C	MFC40008	78p		Dual Low Noise +24	A LM381	£2.16
0.5	9 8 E	MC1306P	68p		Dual Low Noise +14	A LM382	£2.19
1	9 8 F	TAA300	£1.76		Dual Pre-Amp +13	A MC1303L	£1.59
2	12 8 G	TBA820	74p		Dual Low Noise +12	A MC1339P	£1.31
2	18 8 A	LM380	£1.08		Dual Low Noise +15	A TBA231	88p
2 1/2 + 2 1/2	24 8 A	LM377	£2.91		General	MFC5040	83p
3	18 8 J	SL414	£1.72		D.C. Controlled attenuator	3 stage G.P. amp.	8
3	24 16 J	SL415	£2.24		Bi-Fet	TAA263	80p
5	24 8 H	TBA800	99p		Tape Pre-Amp.	F TAA310	£1.34
7	16 4 H	TBA810S	£1.07		Bi-Fet	TAA320	97p
7	16 4 K	TBA810AS	£1.07		Hear/Aid Amp 1.3v	I TAA370	£2.05
10	20 4 M	TCA940	£1.94		PPL stereo decoder(1)	A MC1310	£2.14
15	30 3 O	BHA0002	£2.60		4 channel SQ " (1)	A MC1312	£2.42
15	25 8 F	NE540L	£1.08		" pre-amp (1)	16 MC1314	£4.05
35 driver	+15 4 N	TDA2020	TBA		CBS SQ Logic (1)	16 MC1315	£5.37

MAINS TRANSFORMERS

secondaries	1A	2A	4A
6-0-6v, 100mA 97p	£1.95	£2.27	£2.64
9-0-9v, 100mA 97p	£2.48	£4.15	-
0-24-30-40-48-60v	£5.18	£7.02	-
12-0-12v, 100mA 97p	£A	1A	2A
18-0-18v, 200mA plus	£2.70	£3.40	£4.53

RENDAR INSTA-POWER

safe; inexpensive; quick, A.C. mains connector. A 13 amp plug top containing snap connectors £1.75

(i) & (ii) Separate leaflets available free only with purchases over £1

VAT INCLUSIVE PRICES AT 8%

OVERSEAS CUSTOMERS DEDUCT VAT INVOICES ON REQUEST P&P On UK Orders. 15p Overseas Orders at Cost

CHROMASONIC electronics

Dept. 1
56, Fortis Green Road, London, N10 3HN.
telephone: 01-883 3705

RESISTORS

The standard ranges of Resistors stocked are either E12 or E24 and the values are all in multiples of ten times the decade shown below. The E12 items are only those in bold type. The E24 items are both those in bold and light type.

10	18	33	56
11	20	36	62
12	22	39	68
13	24	43	75
15	27	47	82
16	30	51	91

CARBON FILM $\frac{1}{2}$ watt $\pm 5\%$ tol. 2p ea.
E12 Series 10 Ω to 330K Ω

CARBON FILM $\frac{1}{2}$ watt $\pm 5\%$ tol. 13p ea.
E24 Series 10 Ω to 10M Ω

'CERMET' THICK FILM $\frac{1}{2}$ watt $\pm 2\%$ tol. 8p ea.
E12 series 56 Ω to 150K Ω

METAL OXIDE FILM $\frac{1}{2}$ watt $\pm 2\%$ tol. 43p ea.
E12 series 10 Ω to 1M Ω

CARBON COMPOSITION $\frac{1}{2}$ watt 43p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; ± 0.5 tol.
5.6 ; 6.8 ; 8.2 $\pm 10\%$ tol.

CARBON COMPOSITION 1 watt 53p ea.
2.2 ; 2.7 ; 3.3 ; 3.9 ; 4.7 ; ± 0.5 tol.
5.6 ; 6.8 ; 8.2 $\pm 10\%$ tol.

CARBON FILM 1 watt $\pm 5\%$ tol. 33p ea.
E12 series 10 Ω to 10M Ω

CARBON FILM 2 watt $\pm 5\%$ tol. 63p ea.
E12 series 10 Ω to 10M Ω

WIREWOUND $2\frac{1}{2}$ watt $\pm 5\%$ tol 0.22 to 0.47 Ω 15p
E12 series $\pm 10\%$ " 1 to 270 Ω 13p

WIRE WOUND 5 WATT 13p ea.

1	25	250	1.5K
1	30	270	1.8K
1.8	39	300	2K
2.2	50	330	2.2K
2.7	60	350	2.5K
3.3	68	400	2.7K
3.9	75	470	3K
4.7	82	500	3.3K
5	100	560	3.5K
5.6	125	600	3.9K
6.8	133	680	4.7K
8.2	150	750	5K
10	180	820	5.6K
15	200	1K	6.8K
21	220	1.2K	8.2K

WIRE WOUND 10 watt 14p ea.
All the values shown in bold in the 5 watt range

WIRE WOUND 10 watt $\pm 5\%$ tol. 20p ea.
10K ; 15K ; 20K ; 25K

WIRE WOUND 15 watt 133p ea.
All the values from 10 Ω upward shown in bold in the 5 watt range.

POTENTIOMETERS



5K 250K Log or Lin Less Switch (and 1K Lin) 14p
10K 500K Log or Lin with Switch 26p
25K 1 Meg Dual Less Switch 46p
50K 2 Meg 1 Meg Log only 57p
100K 10K Log $\pm 10K$ Antilog Less Switch

Sliders



10K Single 33p
25K DUAL 55p
100K

Preset

Vertical or Horizontal
.1 Watt 5p .25 Watt 7p

100	1K	10K	100K	1Meg
250	2.5	25K	250K	2.5 Meg
500	5K	50K	500K	5Meg

Cermet

100 2.5K 25K 250K
500 5K 50K 500K
1K 10K 100K 1Meg
40p

CAPACITORS

Ceramic Plate

Mullard C333 Series 63 Volts Wkg.

all of 53p each

± 0.25 pf	1.8 pf	$\pm 2\%$	12 pf	$\pm 2\%$	68 pf
2.2 pf	15 pf		82 pf		
3.3 pf	18 pf		100 pf		
3.9 pf	22 pf		150 pf		
4.7 pf	27 pf		150 pf		
5.6 pf	33 pf		180 pf		
6.8 pf	39 pf		220 pf		
8.2 pf	47 pf		270 pf		
10 pf	56 pf		330 pf		

Mullard 630 series 40 volts $\pm 10\%$ tol.

629 series 100 volts

all of 53p each

390 pf	1000 pf	3300 pf
470 pf	1200 pf	3900 pf
560 pf	1500 pf	4700 pf
680 pf	1800 pf	* 10 nf
820 pf	2200 pf	* 22 nf
	2700 pf	

Eric Monolithic Ceramic 30 Volts Wkg.

27 nf 11p; 47 nf 13p; 100 nf 17p

Low Voltage Disc Ceramics

all of 53p each

0.01 uF	18v	0.1 uF	30v
0.022 uF	18v	0.22 uF	6v
0.047 uF	18v	0.47 uF	3v

Mylar Film 100 Volts Wkg.

1000 pf	23p	0.05 uF	33p
2000 pf	23p	0.068 uF	5p
5000 pf	23p	0.1 uF	5p
0.01 uF	33p	0.2 uF	63p
0.02 uF	33p	0.47 uF	7p
0.04 uF	33p		

MULLARD C295 Series 63 volts

Tolerance $\pm 1\%$ Polystyrene

6,800pf	(6.8nf)	C295 AH/D6K8	11p
8,200pf	(8.2nf)	C295 AH/D8K2	11p
13,000pf	(13nf)	C295 AH/D13K	15p
18,000pf	(18nf)	C295 AH/D18K	15p
20nF	(.02uF)	C295 AH/D20K	15p
30nF	(.03uF)	C295 AH/D30K	18p
39nF	(.039uF)	C295 AH/D39K	18p
51nF	(.051uF)	C295 AH/D51K	25p

Polystyrene 160 volts Wkg.

Tolerance $\pm 1\%$ up to 33p; $\pm 5\%$ 47p up.

10 pf to 10,000 pf (0.01 uF) in multiples of:

10 ; 15 ; 22 ; 33 ; 47 ; 68.

Wima MKS 0.22uF $\pm 5\%$ 100v 11p

Mullard C280 Series. 250 Volts Wkg.

Metallised Polyester Film

0.01 uF	33p	0.22 uF	53p
0.015 uF	33p	0.10 uF	7p
0.022 uF	33p	0.47 uF	9p
0.033 uF	33p	0.68 uF	12p
0.047 uF	33p	1.0 uF	14p
0.068 uF	4 p	1.5 uF	23p
0.1 uF	4p	2.2 uF	26p
0.15 uF	4p		

Mullard C281 series 400 Volts Wkg.

Metallised Polycarbonate Film $\pm 10\%$

0.01 uF	5p	0.1 uF	8p
0.015 uF	5p	0.15 uF	9p
0.022 uF	5p	0.22 uF	11p
0.033 uF	6p	0.33 uF	15p
0.047 uF	6p	0.47 uF	16p
0.068 uF	6p		

VDR's &

Thermistors



CZ1 17p
CZ4 18p
CZ13A 18p
CZ19 18p
E298CDA258 13p
E298EDA258 13p
E298EDA260 13p
E298EDA262 13p
E298EDA265 13p
E298EDP268 13p
E298Z205 13p
E298Z206 13p
E299DDP336 14p
E299DDP338 14p
E299DDP342 14p
E299DDP348 14p

G116 E1.21
G123 E1.21
R53 E1.49
R54 E1.61

VA1005 16p
VA1026 16p
VA1033 16p
VA1034 16p
VA1039 16p
VA1040 16p
VA1053 16p
VA1055S 16p
VA1056S 16p
VA1066S 17p
VA1067S 19p
VA1067S 19p
VA1077 21p
VA1098 31p
VA1104 29p
VA1107 29p

CAPACITORS



Silvered Mica 350V.

Tol. $\pm 0.5\%$ 11p each

2.2 pf	18pf	30pf
3.3 pf	20pf	33pf
5 pf	22pf	39pf
10 pf	25pf	47pf

Tol. $\pm 1\%$ 11p each

50pf	150pf
56pf	82pf
68pf	100pf
75pf	120pf

12p each

250pf	330pf	560pf
270pf	390pf	680pf
300pf	470pf	820pf
	500pf	

17p each

1000 pf 1500pf 220pf

26p each

2700pf	3600pf	5000pf
	4700pf	

33p each

6800pf 8200pf 10000pf

Mixed Dielectric 600 Volts Wkg.

0.01 uF	8p	0.1 uF	9 p
0.022 uF	8p	0.22 uF	17p
0.033 uF	8p	0.47 uF	26p
0.047 uF	8p	1 uF	36p
0.068 uF	9p		

Mixed Dielectric 1000 Volts Wkg.

1000 pf	63p	0.022 uF	11p
2200 pf	53p	0.047 uF	13p
3300 pf	7p	0.1 uF	13p
4700 pf	7p	0.22 uF	24p
0.01 uF	10p	0.47	33p

Solid Tantalum Beads

all at 16p

0.1 uF	35v	10 uF	6.3v
0.22 uF	35v	10 uF	16v
0.47 uF	35v	10 uF	25v
1.0 uF	35v	22 uF	16v
2.2 uF	35v	47 uF	6.3v
4.7 uF	35v	100 uF	3v

Feed-through Ceramics

1000 pf 350v 6p

Disc Ceramic 750 Volt Wkg.

all of 53p each

470 pf; 1000 pf; 5000 pf; 0.01 uF

Tubular H1-K Ceramics 750 Volts Wkg.

1000 pf	53p	3000 pf	53p
1500 pf	53p	5000 pf	53p
2000 pf	53p	0.01 uF	53p

Pulse Ceramics all at 10p each

12 kv D.C. Wkg	8kv D.C.
10pf	120pf
22pf	140pf
68pf	150pf
82pf	180pf
100pf	200pf
	220pf
	250pf
	270pf
	300pf

VAT INCLUSIVE PRICES AT 8%

OVERSEAS CUSTOMERS REDUCT
VAT INVOICES ON REQUEST
P&P On U.K. Orders 15p Overseas Orders at Cost

RIVLIN RESISTORS

Standard T.C. Values for all types shown (UNIVERSAL RANGE 1) are better than 10 p.p.m. between 10°C and 70°C. Lower T.C.'s may be specified over the full resistance range. However, if a specific T.C. is required, the temperature at which that T.C. is expected to operate, must be stated. Wire for any given application can usually be selected from a wide range in stock from 2 p.p.m. to 6000 p.p.m. All precision wirewound resistors manufactured by Rivlin Instruments are measured in absolute ohms and are expressed as deviations from National Physical Laboratory certified master standards held by Rivlin. These standards have an accuracy of better than 0.0002% and the precision measuring equipment has a discrimination better than 1 p.p.m. over the entire range of resistance values offered by Rivlin. Rivlin can provide accurately matched sets of resistors. The stability of ALL types is considered to be better than 100 p.p.m. per year under normal operating conditions. It should be pointed out that all resistors are manufactured in a similar manner and the choice of a low accuracy of RESISTANCE in no way prejudices the high order of long term STABILITY of that component. The limit on the component temperature with no power being dissipated is 130°C.

RIVLIN POTENTIOMETERS

400 SERIES. A preset wirewound potentiometer conforming to BSI 3081 for printed circuit applications. The rugged construction ensures stable settings under vibration and shock conditions and reduces the risk of damage handling to a minimum.

CARBON SLIDE POTENTIOMETERS

60mm Single Track including Black Knob, 60mm Twin Track including Black Knob, 60mm Quad Slide Potentiometers—1K, 5K, 10K, 25K, 50K, 100K, 500K ohms Log, Lin, Antilog. Metal Case. 3.2db Matched Track, 15mV Nominal Noise (B.S.2122). Life exceeds 20,000 cycles. Fixing Holes 2 x M3 on 80mm Centres.

Prices on application.

Designed, manufactured and supplied by: **RIVLIN INSTRUMENTS LTD.** Doman Road, Camberley, Surrey. GU15. 3DJ. Tel: **CAMBERLEY (0276) 21107.**

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: **British National Radio & Electronics School, Dept W.C. 65 P.O. Box 156, Jersey, C.I.**

Please send **FREE BROCHURE** to

NAME Block

ADDRESS Caps.

..... Please

BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL

IRON POWDER TOROIDAL CORES

CORE No.	2 Mix Red 50k-30MHz $\mu = 10$	6 Mix Yellow 10-90 MHz $\mu = 8$	10 Mix Black 30-150 MHz $\mu = 7$	12 Mix Grn/White 60-200 MHz $\mu = 5$	OD"	ID"	TH"
T-200	£1.35	£1.90			2.000	1.250	.550
T-130	.90	1.12			1.300	.780	.437
T-106	.45	.70			1.060	.560	.437
T-80	.30	.40			.795	.495	.250
T-68	.22	.28	£0.34		.690	.370	.190
T-50	.20	.22	.26	£0.28	.500	.303	.190
T-37	.18	.20	.21	.24	.370	.205	.128
T-25	.14	.16	.18	.20	.255	.120	.128

TOROID CORE KITS

TK-101 contains 8 T-50-2 7 T-68-2, £2.40

TK-102 contains 7 T-50-6 6 T-60-6, £2.45

TK-103 contains 4 T-50-2 4 T-50-6 3 T-68-2 3 T-68-6, £2.40

Balun kit makes a 1:1 or 4:1 1kW balun, with instructions, £2.00

Data Sheets available upon receipt of a S.A.E.

Terms: C.W.O. Mail order only. S.A.E. with all enquiries. P & P 20p on all orders

T.M.P. ELECTRONIC SUPPLIES

3 BRYN CLYD, LEESWOOD, MOLD, CLWYD, CH7 4RU

Tel.: Pontybodkin 846 STD 035 287

If you have difficulty in obtaining

PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£5.00) to:—

**Subscription Department,
Practical Wireless,
Tower House, Southampton Street,
London, WC2E 9XQ**

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 12p per word (minimum 12 words), box number 30p extra. Semi-displayed setting £10.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Receivers and Components

BRAND NEW COMPONENTS by return. Electrolytics, 15V, 25V, 50V 0.47, 1, 2, 2.4, 4.7, 10 Mfd.s.—4p, 22, 47—4½p (50V—5p), 100—5½p (50V—7p), 220—6p (50V—9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V—9p. Mylar Film 100V 0.001, 0.002, 0.005, 0.01, 0.02—2½p, 0.04, 0.05—5p. Mullard Tubular Polyester 400V E6 series, 0.001-0.022—3p, 0.033-0.1—4p. Mullard miniature C333 ceramics E.12 series 2% 1.8pf-47pf.—2½p, 56pf-330pf.—3p. Polystyrene 63V, E12 series 10pf-1,000pf.—2½p, 1,200pf-10,000pf.—3½p. Miniature Highstap Carbon Film Resistors ½W E12 series 5% 10-10MΩ (10% over 1 Megohm)—1p. Postage 10p. Prices VAT inclusive. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

BETA DEVICES FOR BETTER PRICES

TRANSISTORS	DIODES & RECT.	BEHIND REEFT
AC187/5 PR 0-40	IN914 0-04	1A 100V 0.20
BC107/8/9 0-09	IN4148 0-04	1A 200V 0.25
BC108C 0-11	BY127 0-14	1A 600V 0.30
BC147/8 0-10	IN4001/2 0-05	25A 200V £2.00
BCY70/71/720-13	IN4003/4/5 0-06	ZENERS
BFY88 0-20	IN4008/7 0-08	BZY88C 3-3-
BFY90 0-18	IN5401 0-11	33V 5% 0-09
BFY91/52 0-12		1 watt 6.8-
OC28 0-45	SEG DISPLAYS	200V 5% 0-15
OC38 0-85	3015F £1.00	L.E.D.
2N2846 0-80	DL707-LED £1.70	200V-RED 0-17
2N2905A 0-81	DL747-LED £2.45	LED CLIP 0-02
2N3053 0-14		OP. AMP. 10's
2N3055 0-38	D.I.L. SOCKETS	708C T099 0-80
TIP29A 0-49	8 Pin 0-12	709C D.I.L. 0-30
TIP30A 0-87	14 Pin 0-12	741C T099 0-88
TIP31A 0-81	16 Pin 0-14	741C D.I.L. 0-88
TIP32A 0-74		728C D.I.L. 0-80
TIP41A 0-74		747C D.I.L. 0-88
TIP42A 0-80	V.A.T. INC.	748C D.I.L. 0-88
7400N 0-16	74 SERIES T.T.L.	7474N 0-87
7401N 0-18	7420N 0-18	7400N 0-68
7402N 0-18	7427N 0-28	7492N 0-68
7404N 0-19	7430N 0-18	7412N 0-50
7408N 0-23	7440N 0-18	74122N 0-70
7410N 0-18	7447N £1.00	74128N £1.28
7413N 0-29	7472N 0-22	74141N £1.18

C.W.O. PLUS P.P. 15p TO BETA DEVICES

Abbey Chambers, 4, Highbridge Street, Waltham Abbey, Essex.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

250mA. Cartridge Fuses 1½" 90p per 100. Unused Carbon Resistors. 100 different 50p. Unused W/W Resistors. 100 assorted £1.10. 100 Capacitor Mixture, 85p. 2ib. 8 to 2BA. Nut & Bolt mixture 22p. Brass 38p. 18 Assorted Potentiometers Unused £1.15 Ex Government Standard Jack Plugs 4 for 50p 6 volt 38 or 18 watt Bulbs. SEC. 70p per doz. Earphones Ex Govt. 85p per pair. New Meter or Cassette Cases, stiff imitation leather 6½" x 3½" x 4". Only 55p. Ex T.V. Speakers. Perfect. 3Ω elliptical 55p. 300mA Meters New. £1.75p. 7" Tape Spools 15p each. All postage in U.K. included in price

SOUND SYSTEMS OF SUFFOLK
876 Foxhall Rd., Ipswich, Suffolk IP3 8NQ

MULLARD 10W RMS AMPLIFIER MODULES. Absolutely complete. £2.65 inclusive. LTE, 46 Minehead Road, South Harrow, Middx.

ELECTROLYTICS 6½p DESPATCH BY RETURN

2.2uF, 4.7uF, 63V. 10uF, 22uF, 47uF, 100uF-25V. ALL 8.5p (inc. Vat) + 10p p&p Discount: 10% on totals over £3, 15% over £6. C.W.O. BUG SOUND ELECTRONICS, THE SHOP BLACKMORE END, BRAINTREE, ESSEX

MULTI-BAND RADIOS. Grundig Satellit, 13 band, £129; Koyo, marine, aircraft, PSB, FM, SW1, SW2, MW, LW, batt/mains, £44; 4-band, MW, FM, aircraft, PSB, £14. SAE lists. Langtons Radio, High Street, Rocester, Staffordshire. 088 923 388.

Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1uF (1½" x 1")	50p	0.47uF	50p	48p
0.25uF (1½" x 1")	58p	1.0uF	60p	50p
0.5uF (1½" x 1")	62p	2.2uF	80p	55p
1.0uF (2" x 1")	71p	4.7uF	£1.30	£1.05
2.0uF (2" x 1")	75p	6.8uF	£1.54	£1.08
5.0uF (2" x 1")	80p	10.0uF	£2.00	£1.40
10.0uF (2" x 1")	91p	15.0uF	£2.75	£2.15

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8uF at 15V/25V or 35V; 10.0uF at 16V/20V or 25V; 22.0uF at 6V/10V or 16V; 33.0uF at 6V or 10V; 47.0uF at 6V or 8V; 100.0uF at 2V. ALL at 10p each, 10 for 85p, 50 for £4.

TRANSISTORS: BC183/183L 11p BFY60 20p BC107/8/9 9p BC184/184L 12p BFY51 20p BC114 12p BC219/215L 14p BFY92 20p BC147/8/9 10p BC547/558A 12p AF178 30p BC158/7/8 12p BF194 12p OC71 15p BC182/182L 11p BF197 12p 2N3055 50p

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 90p; IN915 5p, 6 for 45p, 14 for 90p; 1S44 5p, 11 for 50p, 24 for £1.00, 1N4001 6p, 6 for 37p, 12 for 68p; 1N4001 6p; 00A 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p. **LOW PRICE ZENER DIODES**—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.8V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 6 for 38p, 14 for 59p. SPECIAL OFFER: 100 Zeners for £5.50.

RESISTORS—High stability, low noise carbon film 5%, ½W at 40°C, ¼W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 55.

BRIDGE RECTIFIERS—1.5 amp, brand new wirewound DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 500V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 8p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2.5MΩ, 5MΩ. PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SRA/AIRMAIL.

PLEASE ADD 8% V.A.T. TO ORDERS. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. W6).
The Old School, Edginston, Nr. Wem, Shropshire.
Tel: Whixall 464/465 (STD 094 872)
(Proprs. Mintoast Trading Ltd.)

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc., Sample pack 65p incl. postage or send stamp for list. Redhawk Sales Ltd., 10 Maple Lodge Close, Rickmansworth, Herts. Mail Order Only.

INFLATION? PRICE INCREASES? SGS.ATES 7 watt IC TBA810AS, only 99p. Send £1.98+20p post for two, data included. PC Boards 55p each, post 10p. 7 watt IC kit, all parts £2.25, post 20p. Ready Built 7 watt IC modules using TBA810AS overload protected size 3¼ x 2½ x ¾, £2.50 each, (stereo) 2 for £4.60, (quad) 4 for £8.50. Post 25p per order. Send mail order to Watson, c/o 131 Buxton Street, London E1.

TAPE HEADS

Send stamp for lists.

R.D.I. Ltd.
Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

For valve and transistorized recorders from £2 ea.

Wanted

WANTED. Communication receiver (540-10 metres). 8 metre band spread or vernier also (2-10 metre) receiver. Age immaterial, good working order, reasonable price. Hindhead 5605.

TOP PRICES PAID FOR NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C).
367 Kensington Street, Bradford 8, Yorkshire.

"Radio & TV Servicing" books wanted from 1961 onwards. Any quantity. £2.00 paid per copy by return of post.—Bell's Television Services, 190 Kings Road, Harrogate, Yorkshire. Tel. (0423) 55885.

WANTED. Old Pye Radio or Radiogram. Condition immaterial.—Collins, 131 Hazleton Way, Horndean, Hants. Horndean 591725. Reverse charge evenings or weekends.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

TELEPHONES WANTED, candlestick type or older (foreign and English). 01-722 4151.

Ladders

LADDERS, timber and aluminium. Tel: Telford 586644 for brochure.

ELECTRONIC CRAFTSMEN

Is your present job routine and uninteresting ?

We are a research establishment and our craftsmen are engaged on a wide variety of work in the fields of prototype and small batch wiring and assembly, test and inspection, maintenance fault finding and repair. Why not join us and enjoy working in first class conditions in the country.

You can expect gross earnings including overtime of £45 per week, and we can offer good housing at low rental (for applicants who reside outside the radius of our Assisted Travel Area) together with 3 weeks paid holiday with holiday bonus, free pension and excellent sick benefit scheme.

Applicants who should have served a recognised apprenticeship or have had equivalent training together with experience in one of the fields detailed should 'phone Tadley 4111 (ST.D 073.56.4111) Ext. 5230, or write to:

**Industrial Recruitment Officer
(PA/78/PW) Procurement Executive
Ministry of Defence
AWRE Aldermaston
Reading, Berks
RG7 4PR**

RADIO ENGINEER/TECHNICIAN FOR CENTRAL AMERICA

Needed to work with the Radio Schools Movement in Guatemala, training a team of Guatemalans in the maintenance and repair of station equipment. A British Volunteer Post.

Information:
**Paddy Coulter,
Overseas Volunteers CIIR
41 Holland Park, London, W11 3RP**

**MEN!
£90 p.w.
can be yours**

Jobs galore? Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

**London Computer Operators
Training Centre
Y24, Oxford Hse.,
9-15 Oxford St. W1. Tel: 01-734 2874**

Educational

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

**INTERNATIONAL
CORRESPONDENCE SCHOOLS,
Dept 732, Intertext House, London SW8 4UJ.
Or Phone 01-822 9911 (All Hours)**

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on Sept. 15th.

Prospectus from: London Electronics College, Department B6, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

Service Sheets

SERVICE SHEETS for Radio, TV, etc., 50p and SAE. Catalogue 20p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
ALL AT 50p EACH

" PLEASE ENCLOSE LARGE S.A.E WITH ALL ENQUIRIES & ORDERS "
Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA

**71 BEAUFORT PARK
LONDON, N.W.11 6BX**

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 20p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

BELL'S TELEVISION SERVICES for Service Sheets, Manuals, Books on Radios, TVs, etc. Service Sheets 50p plus SAE. Free booklists on request. Back issues of PW, PE, EE, TV available 25p plus 9p post. SAE with enquiries.—BTS (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

Books and Publications

THE McCOURT T.V. REPAIR MANUALS MAKE REPAIRS SIMPLE AS A.B.C.

Set out in the easiest to follow style, showing symptom, cause and cure for every common fault and virtually every possible one, for every British standard or portable set plus many foreign. Contained in 4 large manuals, only £12 set or send your model, make and £3.35 for the correct manual by return. Colour manuals £3.35 each, full details from:—

T.V. TECHNIC, 76 CHURCH STREET, LARKHALL, LANARKS.

Technical Books — Radio & Electronics

World's Radio & TV Stations (International Edit).....	£0.68
Audio Amplifiers.....	£0.70
Boys Book of Crystal Sets & Simple Circuits.....	£0.33
Television Timebase Circuits.....	£1.15
Radio TV and Industrial Tube & Valve Equip.....	£0.68
How to get the best out of your Tape Recorder.....	£1.67
Modern Electronic Troubleshooting.....	£1.55
Jack Darr's Service Clinic.....	£1.55
Transistor Circuits for Modern Test Equipment.....	£0.88
Rad & Electr Colour Codes and Data Chart.....	£0.20
Handbk of Transistor Equip. and Substitutes.....	£0.48
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0.87
Radio Servicing Problems.....	£0.75
Electronic Circuits for the Amat Photographer.....	£0.68
Handbook of Simple Transistor Circuits.....	£0.40
TV Fault Finding.....	£1.10
Sound and Loudspeaker Manual.....	£0.60
TV Technicians Bench Manual.....	£2.80
Radio Amateur Operator's Handbook.....	£0.85
Towers International Transistor Selector.....	£3.30
Television Servicing Vol. No. 2.....	£1.27
Television Servicing Vol. No. 3.....	£0.75
Television Servicing Vol. No. 4.....	£1.00
Radio Technicians Bench Manual.....	£3.30
Servicing Transistor Radio Receivers.....	£0.90
1st Book of Hi Fi Loudspeaker Enclosures.....	£0.68
2nd Book of Hi Fi Loudspeaker Enclosures.....	£0.68
Manual of Electronic Circuits for the Home.....	£0.60
Modern Crystal Set Circuits for Beginners.....	£0.40
Electronic Novelties for the Motorist.....	£0.58
2nd Book of Transistor Equip. & Substitutes.....	£1.07
Handbook of Electronic Musical Novelties.....	£0.40
Transistorised Novelties for Hi Fi Enthusiast.....	£0.95
Fault Location Exercises in Rad. & TV Vol. 1.....	£1.55
Fault Location Exercises in Rad. & TV Vol. 2.....	£2.70
Colour TV Picture Faults.....	£2.70
Practical Transistor Novelty Circuits.....	£0.48
Boys Book of Practical Radio & Electronics.....	£0.68
Radio Receiver Construction using ICs & Transis.....	£0.68
ICs & Transistor Gadgets Construction Handbk.....	£0.85
Integrated Circuits Equip. & Substitutes Hbk.....	£3.30
Audio Technicians Bench Manual.....	£3.30
Improving your Hi-Fi.....	£3.30
Guide to Printed Circuits.....	£2.80
Receiving Pal Colour Television.....	£3.35
World Radio TV Handbook 1975.....	£3.80

All prices include Postage & Packing

RADIO BOOK SERVICE

40 Elwill Way, Beckenham BR3 2RZ

"UNDERSTANDING SOLID-STATE ELECTRONICS" is the simplest, easiest-to-follow book yet on the subject. Includes 12-lesson self-teaching course with "quizzes". 242 pages, technical glossary with each chapter. And only £1.20 post paid. Send a cheque/P.O. for your copy now to: Texas Instruments Ltd., Book Sales, MS21 PW1, Manton Lane, Bedford, MK41 7PA.

Aerials

GENUINE FULL SIZE 18 element TV aerial as used by leading TV companies



IMPERIAL TRADING (LTD.)
Quality & Reliability

J. & A. TWEEDY (Electronic Supplies) LTD.
79 Chatsworth Road, Chesterfield, S40 2AP
We have in stock a good range of Jaybeam TV and FM aerials. As well as these we have a good stock of accessories. A SAE will bring more details.
Multibeam: MBM 28 £5.00, MBM 28-00, MBM 70 £12.50, JBM 18 £4.00, Rotators AR 30 £27.00, AR 40 £32.00, CD 44 £24.00, Stereobeam: SBM2 £3.00, SBM 3 £4.00, SBM 4 £5.00, SBM 5 £8.95, NEW 9 element £19.00.
VAT included on all prices.
Masthead amplifiers £11.00, Setback £5.50. State group required on all aerials and amplifiers. Carriage is paid on all aerial orders but extra on accessories.

Miscellaneous

LOWEST COST IC SOCKETS. Use Soldercon IC socket pins for 8 to 40 pin DIL's. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price), 70p for strip of 100 pins, £1.50 for 3 x 100, £4 for 1000, 10p p&p for orders under £2. Add 8% VAT. Instructions supplied—send sae for sample. SINTEL, 53n Aston Street, Oxford. Tel: 0865 43203.

FELSTEAD ELECTONICS (PW92)

Longley Lane, Gatley, Cheadle, Cheshire, SK8 4EE.

for low price

Styli, cartridges, leads, cassettes, tape, plugs, sockets, components and accessories &c. (by post only). Send S.A.E. for list incl. illus. stylus chart.

All items also available to callers in Manchester at Trionix, 177, School Lane, (Kingsway Corner), East Didsbury. 19.

UFO CHARTS: Wave Prediction, 54p; Daily Flight Pattern, 50p; TV Doppler Detection, 65p; Propulsion Theory, 55p; "Anti-Gravity", 55p. Map 50p. Circuits: Transistor Optical Detector, 66p; Radiation/Optical, 44p; Crystal Radiation Counter/Timer/Stopclock, 85p. R. & E. Highlands, Needham Market, Suffolk.

TAPER, hand-reamer (with T-bar). Invaluable tool for all constructors. Saves time and temper! Reams 1/8 in to 1/2 in dia., 4in long. Guaranteed. Only £1.45 post free. Gemini Services, 44 Beechwood Ave., Kew, Surrey TW9 4DE.

TRIACS (plastic) 10A/400V, 64p (60p for 3+); Diac 19p; NE555V 58p (55p for 3+); LEDs 0.2in dia. Red 20p, Amber Green Yellow 25p. P&P 10p. Add VAT. CWO. TK Electronics, 106 Studley Grange Road, London W7 2LX.

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4 1/2 p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

12 VOLT 21" 13 Watt Fluorescent Lighting (by Thorn/AEL) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT
SALOP ELECTRONICS 23 Wyle Cop, Shrewsbury, Shropshire
Tel. 53396

COPPER CLAD laminate for printed circuits. 1/16in double-sided epoxy glass in assorted sizes (average 5in x 10in), £1 per lb (approx. 200 sq in), including postage and packing. Minimum order £1. Cash with order please. Midland Circuits Limited, 76-78 Cato Street North, Birmingham B7 5AN.

MINI ACCUMULATORS



LOW COST IC MOUNTING. 100 IC pin sockets, 60p. Quantity rates. SAE details and sample. 7 and 8 hole plastic supports 5p/pair (P&P 8p/order). LED (MLED500), 20p each, post free (quantity rates). PKG Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters'!

★ Pocket-sized **MAXI-VOLT** Big 3inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £1.90 for your Maxi-Volt now!

★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £6.90 for yours now!

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £2.90 now! (all prices include V.A.T., packing & postage.)

Send remittance to:
BOFFIN PROJECTS,
4 CUNLIFF ROAD,
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)
Or for more details, send 20p for lists

SINTEL

Add 10p P. & P. for orders under £2. Data, and circuits where appropriate supplied with orders, or available separately (send 9p 4in S.A.E.) **ADD VAT at 8%.**

- DL707 Red 0-3in LED 7 seg display C. Anode £1.35
- DL747 Red 0-6in LED Jumbo display C. Anode £2.45
- Economy DL704 Red 0-3in 7 seg LED C. Cath. 95p**
- NSN33 Type 0-12in 3 digit LED C.C. Red £1.85
- MKS0250N Alarm Clock IC £5.80
- CT7001 Clock/Calendar/Timer IC £5.95
- MK/704-6 MKS0250N 6 digit Alarm Clock Kit £16.85 (complete less case, transformer, switches, LS)
- SOLDERCON I.C. Socket Pins 100 pins for 50p** (Nylon supports available) 300 pins for £1-50
- Send s.a.e. for pin sample 1000 pins for £3-50
- Other displays, IC's, etc. are available; also **RCA CMOS** at new low prices:
- Phone (9.30 to 7) or send s.a.e. for lists.

SINTEL, 53N ASTON STREET OXFORD
Tel. (0865) 43203

VALVES. Radio, TV, transmitting, industrial. 1950 to 1975. Many obsolete. 2,000 types stocked. List 20p. We wish to purchase new and boxed valves. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 0233.

VALVES. New, boxed, and reclaimed types. S.A.E. for lists. Al Radio Components, 14 The Borough, Canterbury, Kent, CT1 2DR.

BULK OFFERS

All goods full spec. and marked

1N4001	£2-50/100	1N4002	£2-80/100
1N4003	£3-20/100	1N4004	£3-50/100
1N4005	£4-30/100	1N4006	£4-70/100
1N4007	£5-00/100	1N4148	£3-00/100
BC182	£7-00/100	BC183	£7-50/100
BC184	£8-00/100	BC212	£7-50/100
BC213	£8-00/100	BC214	£8-50/100
BC108	£7-50/100	BC109	£7-50/100
BC116A	£8-00/100	BC161	£10/100
BC267	£6-00/100	741C	£19/100
NE555V	£39-00/100	2N4055	£27-50/100

400mW Zeners £5/100, most values.
Assorted Computer panels £25/cwt.
Assorted small value capacitors—mica ceramic, poly etc. £26/10,000
Assorted C200 caps £4/1000 (cosmetic faults)
Assorted 015/016/017 electrolytics—mostly OK, but very few are marked, so only £19/10,000.
Ferric Chloride £30/100 1lb bags.
Miniature mains transformers, all 100mA set: 6-0-6V £5/10; 9-0-9V £5-50/10; 12-0-12V £6/10.
Veroboard Outputs £22/10lb.
1000mfd 63V wire ended 1TT £25/100
Minimum Order £5; cart free; Add VAT @ 8%.

JUNIPER ELECTRONICS (PW2)
PO BOX 61 SOUTHAMPTON



TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Comp. kit £10-90 Built & tested £15-25
Post 50p P&P VAT(8%) P&P 10p — 23-27 VAT(8%)

MINIKITS ELECTRONICS,
63 CLEVELAND ROAD,
LONDON, E14 2AN (Mail order only)

PRINTED CIRCUIT manufacturer's offer, ready drilled PCBs for PW and PE projects published after June 1974, at one price 70p. E.g. Orion amp, telephone exchange. Also full sets for: Tele-tennis £3-50; PE CCGTV £1-40p. Power slaves £1-35p. Scorpio ignition and Ferret locator 60p. CWO. Please add 15p per 40 sq in P&P. Production space available for PCB production, design, silk-screen printing, electroplating, tinning plus all graphic/art and photographic masters. Estimates by return post or phone. WKF Electronics, Welbeck Street, Whitwell, Worksop, Notts. Tel: Whitwell 695 (Derbys.).

DIGITAL CLOCK CHIP, AY-5-1224, with data & circuit diagram, £3-66 + VAT, 'Jumbo' LED digits (16mm high), type DL-747, only £2-04 each + VAT, post free.—Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside. L62 5AG.

P.W. CRATA F.M. TUNER. Set of five P.C. boards £3, p&p 20p. Other components available. S.A.E. for lists. Teleradio, 325 Fore Street, Edmonton, London N9 0PE.

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronics and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Largest choice at highly competitive prices, why pay more. Fast despatch. Free literature, (stamp would be appreciated), Bazelli, Department No. 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

**SIMPLE TO FORM
NON-MAGNETIC RUST PROOF
MILL FINISH**

ALUMINIUM

FLAT MINI SHEETS

10ins. x 14ins. 20 swg (0.90mm.)

6 sheets for £2 plus 30p P & P

OTHER SIZES AVAILABLE

**For general car repairs,
trims, kick plates, etc.**

**BAYKIN
ENGINEERING LTD.**

(Dept. PW)
GREVILLE ROAD, BEDMINSTER,
BRISTOL, BS3 1LL

AERIAL WIRE. High quality PVC covered multi-strand copper, 50ft 60p (10p); 75ft 87p (13p); 100ft £1-20 (15p); 150ft £1-80 (24p); 200ft £2-39 (26p); 250ft £2-96 (28p); 300ft £3-54 (31p). P & P in brackets. Longer lengths available. SAE all enquiries. Al Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

BLUE PCB INK
(ETCH - RESIST)
USE WITH ANY
£1.75 PEN! (175cc)
VAT & Post FREE
CWO Please to -
JFH SUPPLIES, 30 BAKER ST. LONDON W1M



Business Opportunities

Run your own hi-fi store

A unique opportunity to run your own hi-fi superstore and become the outright owner of a franchise that's the only one of its kind in Britain

Tandy Corporation (Branch UK), a division of The Tandy Corporation of America, where its 'Radio Shack' operation has over 2,000 retail outlets, arrived in Britain late in 1973 and has already opened 100 audio superstores in England. During 1975, the same fast rate of growth will be maintained and openings will commence in Scotland. Every major town and city will have at least one Tandy Store.

The product range consists of exclusive Tandy brands of radio, audio and communications equipment plus components, accessories and kits offering the highest possible quality at competitive prices.

This ensures high volume sales with substantial profits. Previous trade experience is not necessary. Tandy's 50 years experience assures realistic training of the Franchisee and covers everything from your Grand Opening, to everyday routines, plus regular newspaper advertising, full merchandising and promotional support.

A minimum investment of £17,000 is required.

For further information please write in confidence to the Senior Vice President, Mr. Richard N. O'Brien.

TANDY

Tandy Corporation (Branch UK)
Bilston Road, Wednesbury, WS10 7JN, Staffs.

Synthesiser "Sounds Supreme"

by Dewtron (V-T extra.)

Famous kits, e.g. waa-waa complete kit £3-50; Fuzz kit £5-50. P & P 25p under £10. Ring Modulator modules £9. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

OSCILLOSCOPE TUBES for engineers in electronics. New boxed, Mullard E13-10GH. Callers only £8-50. Components, valves, etc. Rogers, 31 Nelson Street, Southport.

GLASS FIBRE PCBs for all projects. Drilled and tinned. Send master print and 30p per board plus 5p per square inch. Electro Circuits, 4 Highcliffe Way, Wickford, Essex.

FANTASTIC NEW MICROTEST 80

MEASURES
ONLY
90x70x18 mm
ELECTRONIC ZERO Ω

Amazing Value at **£11.95**
8 fields of measurement
and 40 ranges

PRINTED CIRCUIT BOARD IS
REMOVABLE WITHOUT SOLDERING

Volts D.C. 6 ranges: 100mV - 2V, -10V, -50V, -200V-1000V. (20k Ω /V) \pm 2% precision on DC and AC
Volts A.C. 5 ranges: 1.5V, -10V, -50V, -250V, -1000V. (4k Ω /V)
Amp. D.C. 6 ranges: 50 μ A - 500 μ A - 5mA - 50mA - 500mA - 5A
Amp. A.C. 5 ranges: 250 μ A - 2.5mA - 25mA - 250mA - 2.5A
Ohms 4 ranges: Low Ω - Ω x 1 - Ω x 10 - Ω x 100 (from 1/10 Ω until 5 Mega Ω)
V Output 5 ranges: 1.5V, -10V, -50V, -250V, -1000V
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB
Capacity 4 ranges: 25 μ F - 250 μ F - 2500 μ F - 25,000 μ F



SUPRETESTER 680R ICE
20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields
Scale width and small case dimensions (128 x 95 x 32mm)
Accuracy and stability (1% in D.C. 2% in A.C.) of indicated reading
Simplicity and ease of use and readability
Full ranges of accessories
1000 times overload
Printed circuit board is removable without de-soldering
More ranges than any other meter. Ask for free catalogue **£18.50**

Accessories (extra) available to convert Microtest 80 & Supretester 680R into following: LIGHT-METER GAUSS METER, ELECTRONIC VOLT-METER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100k Multiplier, SIGNAL INJECTOR—Send for details.

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324
A-DC 0-96-3A - 6 Ranges.
A-AC 0-3-3A - 5 Ranges.
V-DC 0-6-1200V - 9 Ranges.
V-AC 3-900V - 8 Ranges.
Freq.: In the range of 45 to 20kHz.
Resistances: 500 Ohm to 5 M Ω - 5 Ranges. Decibel: 10 to +12dB.
Accuracy: \pm 2.5% DC, \pm 4% AC.
Dimensions: 167 x 98 x 63 mm.



only **£8.85**

ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including \star 170v-21mA \star All d.c. operation \star Uniform, continuous line characters of equal height \star Memory with simple solid state drive circuits \star Readability in high ambient light \star 200 footcandle brightness \star Long life with no loss of brightness \star Character height 2 1/2 in.



Price only **99p** each plus 16p P/P.
Bases for above 60p each.

JUST ARRIVED !!

NUMERIC INDICATOR TUBES
Ultra-long life, high quality, 0-9 and 2 Independent decimal points. Supply voltage 200V D.C. Current 14mA, Pulse duration 100 μ s. Character height 0.51, overall size 1.4.
Brand new, guaranteed. Surplus to manufacturers requirements. Type B585Set
1-25 \pounds 1.10 25+ 90p 100+ 80p
1000+ price on application
Adv. 8% VAT to all items + 35p P & P
ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

For Sale

MICROPHONES: AKG D109, £12.65; AKG D202EI, £43.45; AKG D190C, £18.70; AKG D190E, £20; AKG D224 £55; Sennheiser MD211N, £49.50; Sennheiser MD413N, £29.70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manorwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

COPPER CLAD LAMINATE

FOR
PRINTED CIRCUITS
Single sided 1/16" paper base—1.0p/sq. Inch.
Single sided 1/16" glass-epoxy—1.5p/sq. Inch.
Any rectangular sizes cut to your requirements.
Please send cash with order.
Price includes postage and packing.
From: **SINTECH ENGINEERING LTD**
VOLUNTARY PLACE
WANSTEAD
LONDON E.11. 01-530-4240.


ENTHUSIAST CLEARING component stock, for list s.a.e. to Fretter, 56 Antony Gardens, Plymouth PL2 3SB.

FOR SALE. Marconi Electra Marine Receiver with 889A power supply unit. £40 ono and Guillimot Transmitter, £20 ono, both in working order. 01-283 1030 ext. 429.

SOUNDLIGHT CONVERTERS from £9; strobes from £21; loads more. Free catalogue. Aaryak Lighting, 98A(P), West Green Road, London N15 5NS. 01-800 8656.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

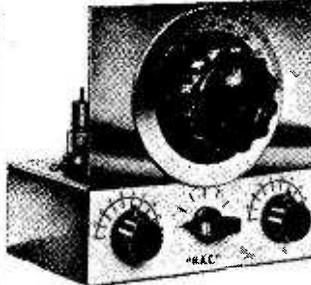

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1974 "DX" RECEIVER
Complete kit—Price £4.60 (incl. p. & V.A.T.). Customer writes: "Australia, India and America at loud volume." "I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver."
This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits and components.
Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX No. 16, EAST GRINSTEAD, SUSSEX RH19 3SN

Everest Instruments Ltd.

34, Shakespeare St., Nottingham. Tel: (0802) 45468
All prices quoted include P&P & VAT, min order £1, C.W.O. only. 12x10 S.A.E. for full lists. Trade enquiries invited.

Transformers			240/110v	£ p
Volts	Amps	£ p	autos -	30 watts 2.42
6-3	1-5	1.66	50 "	3.33
8-8	3-0	1.90	100 "	4.78
9-0	1-0	1.66	150 "	6.07
12-0	1-5	1.90	200 "	7.85
12-0	3-0	2.74	300 "	15.47
8-0-6	0-5	1.78	Bulk tape eraser	3.21
9-0-9	0-5	1.78	15-8-3 ohm 12 watt	
9-0-9	1-0	2.03	matching	1.55
10-0-10	2-0	2.73	Transistor driver	
12-0-12	1-0	2.02	4:1+1	0.24
12-0-12	2-0	2.85		
12-0-12	3-0	3.83		
15-0-15	1-0	2.62		
18-0-18	2-0	3.93		
0-10-12-14-16-18	4-0	4.17		
0-5-20-30-40-60	2-0	5.95		
Battery charger transformers				
6 & 12v	1-0	2.14		
	2-0	2.98		
	4-0	3.93		

Speakers	SWR 50 swr & power
2 1/2" EMI 8 ohm tweeter 97492AT	twin meter 12.20
3" Goodmans 8 ohm tweeter 51C4D	illuminated (12v) edge meter 1300uA
3" Audax 8 ohm tweeter 6-5TWB18	5 x 7 led alpha numeric matrix 14 ddi
5" Audax 8 ohm bass HF13E8	BB113 triple varicaps 0.30
5" EMI 8 ohm bass 3472BV	Dual reed relays 35 ohm coil 2 reeds N.O.
5" EMI 8 ohm 14A/584B	BC117 complimentary to BC107
6 1/2" EMI d/cone 8 ohm 93850CC	10K 1in stereo pots 0.30
7 x 4 EMI 15 ohm 99850AN	100K log stereo pots + D.P. switch
8 x 5 EMI d/cone 4 ohm 8 ohm 10 watt 93870KG/H	250 ohm 1in pots + S.P. switch 1/2 shaft
10 x 6 EMI 8 ohm mid-range 93870CH	110v solenoids 0.25
10 x 8 EMI 8 ohm 93870CH	8280A BCD decade counter
10 x 8 EMI 8 ohm 93870CH	Twin tuning 300 + 250pf with ganged 100K pot for varicap tuning
10 x 8 EMI 8 ohm 93870CH	3-7-70pf disc comp. precision trimmers
10 x 6 Eiac 8 ohm d/cone 610RM59	0-47mfd @ 100v polycarbonate
8" Eiac 8 ohm 8RM/306	1-0mfd @ 100v polycarbonate
8" Celestion 8 ohm d/cone P58 9858	0-01mfd @ 160v tubular polyester
12" EMI 25 watt 8 ohm 14A/1200CP	0-04mfd @ 600v 0-04
13 x 8 EMI 20 watt 8 ohm 92390GK/H	0-0033mfd @ 1500v 0-04
13 x 8 EMI 25 watt 8 ohm 92390GF/H	250ml plastic bottles for etching solution
	250v C280 capacitors
	0-01, 0-015, 0-022, 0-047
	0-1 0-02
	0-3 0-03
	1-0 0-06
	0-12 0-12
	2-2 0-20

Miscellaneous	Electrolytics. Tubular with axial leads except where stated.
SWR 10 swr single meter	
Mfd	Volts Pence
47	4 7
100	4 7
330	4 7
33	6-3 7
68	6-3 7
470	6-3 9
1000	6 11
22	10 7
25	10 7
47	10 7
100	10 7
220	10 7
330	10 9
15	16 7
33	16 7
68	16 7
220	16 9
330	16 12
1000	16 20
10	25 7
22	25 7
47	25 7
100	25 7
150	25 9
200	25 11
470	25 15
1250	25 25
5000	25 65
1000+1000	30 32
2500	30 40
8-8	40 7
15	40 9
100	40 24
1000	50 35
1	63 7
1	63 7
2	63 7
4	63 7
10	63 7
15	63 7
22	63 7
32	63 9
800	63 32
2500	63 85
4700	63 145

SPARKRITE MK 2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

"Sparkrite MK 2" is a high performance, high quality, capacitive discharge, electronic ignition system. Sparkrite completely eliminates problems of the contact breaker. Misfire due to contact breaker bounce is electronically eliminated, contact breaker burn is eliminated, the condition of the contacts is not relevant to the performance of the ignition, and the system is no longer dependant on the dwell period for recharging.

Sparkrite will give you: Up to 20% better fuel consumption, instant all weather starting, cleaner plugs, faster acceleration, higher top speed, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

The Kit comprises everything needed. All ready drilled and guaranteed components and parts.

Prices: D.I.Y. assembly kit £10.93*. Ready built unit £13.86*. (Both to fit all vehicles with coil/distributor ignition up to 8 cylinders.) Switch for instant changeover from "Sparkrite" Ignition to conventional ignition £2.79*. R.P.M. limiting control £2.42*. Details of more specialised units on request.

*Inc. V.A.T., p & p. CALL IN AND SEE US FOR A DEMONSTRATION.



ORDER NOW

TO **Electronics Design Associates**
Dept PW6
82 Bath Street, Walsall, WS1 3DE
Phone 33652.

FROM Name
Address

QTY Please Supply
SPARKRITE MK 2 DIY Assembly kits to build Neg. or Pos. @ £10.93
SPARKRITE MK 2 Ready Built Negative earth @ £13.86
SPARKRITE MK 2 Ready Built Positive earth @ £13.86
Ignition changeover switches @ £2.79
R.P.M. Limit systems in the above units @ £2.42
Fluorescent light assembly kits @ £3.19
Fluorescent light built units @ £3.78
Diffusers for the above @ 59p
of number alum. boxes ☐
of number alum. boxes ☐

I enclose cheque/P.O.s for £.....

Cheque No.
(Send SAE if brochure only required)

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

Prices include lids, screws and V.A.T. (@ 8%). Add 18p to the total order value for postage and packing.

No. 7	5 1/2" x 2 1/2" x 1 1/2" high	47p
No. 8	4" x 4" x 1 1/2" high	48p
No. 9	4" x 2 1/2" x 1 1/2" high	48p
No. 10	5 1/2" x 4" x 1 1/2" high	48p
No. 11	4" x 2 1/2" x 2" high	48p
No. 12	3" x 2" x 1" high	38p
No. 13	6" x 4" x 1 1/2" high	58p
No. 14	7" x 5" x 1 1/2" high	73p
No. 15	8" x 6" x 1 1/2" high	80p
No. 16	10" x 8" x 1 1/2" high	£1.14

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12v, 8w, fluorescent light. Everything needed is supplied: white enameled ready drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, end caps, cable, the fluorescent tube, nuts bolts washers, and simple assembly and operating instructions. Prices: Assembly kit £3.46*. Ready built £4.10*. Diffuser 59p*.
*Inc. V.A.T. p. and p.

INDEX TO ADVERTISERS

Allard Electronics	110
Ambit International	124
Amtron Electronics	120
Arbour Electronics Ltd.	102
A.S.P. Ltd.	120
Astro Electronics Ltd.	152
A.W.R.E. (Ministry of Defence)	170

Barrie Electronics	164
Baykin Engineering Ltd.	172
Bentley Acoustic Ltd.	92
Beta Devices	169
B.H. Component Factors Ltd.	96
Bi-Pak Semiconductors	108-109
Bi-Pre-Pak Ltd.	163
Bib Hi-Fi Accessories Ltd.	106
Boffin Projects	171
Bothwell	110
British Institute of Engineering Technology	110, 162, cover iii
British National Radio & Electronics School	cover ii, 94, 168
J. Bull (Electrical) Ltd.	105
Bug Sound Electronics	169

C. Caranna	170
Chromasonic Electronics	166-167
C.J.L. Ltd.	92
Codar	106
Colomar (Electronics) Ltd.	152
Combined Precision Equipment	155
Crescent Radio Ltd.	103
Crofton Electronics	156
C.T. Electronics	159

D.E.W. Ltd.	172
Doram Electronics Ltd.	119

Electronic Brokers	173
Electronic Design Associates	175

Electronic Mail Order Ltd.	120
Electroni-Kit	152
Electrospares	164
Electrovalve Ltd.	94
Elvins	98
Everest	173

Felstead Electronics	171
Forward Marketing	152
Foulsham-TAB Ltd.	104

Garfields	171
Greenwell Electronics	98
Guest International	104

H.A.C. (Shortwave) Products	173
Harversons Surplus Co. Ltd.	123
Heath (Gloucester) Ltd.	151
Henry's Radio Ltd.	cover iv

J.L.P. Electronics Ltd.	97
Imperial Trading	171
Intertext (I.C.S.)	170

J.F.H. Supplies	172
Juniper Electronics	172

Kensington Supplies	169
Keytronics	102

Lewis Radio	162
Linear Products Ltd.	162
London Computer Operators Training Centre	170
London Electronic College	170
Lowe Electronics	155

Maplin Electronic Supplies	107
Marco Trading	169
Marshall, A. & Son	94
Minikits Electronics	172

Newmart Electronics	93
Paddy Coulter	170
Partridge Electronics Ltd.	165
Pembridge College of Electronics	92

Radio Book Services	171
Radio Component Specialists	160-161
Radio Exchange Ltd.	111
R.D.I. Ltd.	169
Radio Society of Great Britain	102
Rivlin	168
R.S.C. (Hi-Fi) Centre Ltd.	90-91, 104
R.S.L.	96
R.S.T. Valve Mail Order Co.	99
R & TV Components Ltd.	100-101
Riversdale Electronics	98

Salop Electronics	171
Saxon Entertainments Ltd.	95
Sintech Engineering Ltd.	173
Sintel	172
Sound Systems of Suffolk	169
Studio Electronics	96
Surpletronics	156
Surplus Electronics Trading	156
Swanley Electronics	156

Tandy Corporation	172
Technomac Ltd.	176
Texas Instruments Ltd.	171
T.M.P. Electronic Supplies	168
Trampus Electronics Ltd.	165
TV Technic Publications	171
Tweedy (J. & A.)	171

Watford Electronics	174
West London Direct Supplies	102
Wilmslow Audio	124

Z & I Aero Services	176
---------------------	-----


Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

AC/DC MULTIMETERS

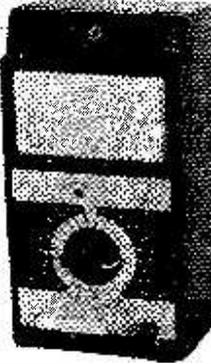

TYPE U4313

39 ranges:
600µA to 1.5A A.C.,
60µA to 1.5A D.C.,
1.5V to 600V A.C.,
75mV to 600V D.C.
Resistance up to 1MΩ
Capacity up to 0.5µF
Level up to 12db

Accuracy: 1.5% D.C.,
2.5% A.C.

Sensitivity: 20kΩ/V D.C.,
2kΩ/V A.C.

Mirror scale: 86mm long

Dimensions: 115 x 215 x
90mm

PRICE, incl. steel carrying
case, leads and manual
£13.80*

TYPE U4315

42 ranges:
500µA to 2.5A A.C.,
50µA to 2.5A D.C.,
1V to 1000V A.C.,
75mV to 1000V D.C.,
Resistance up to 1MΩ
Capacity up to 0.03µF
Level up to +2db.

Accuracy: 2.5% D.C.,
4% A.C.

Sensitivity: 20kΩ/V D.C.,
2kΩ/V A.C.

Plain scale: 86mm long

Dimensions: 115 x 215 x
90mm.

PRICE, incl. steel carrying
case, leads and manual
£10.00*

LINEAR INTEGRATED CIRCUITS

— Please note reductions in prices —

Mullard TAA263. Direct coupled three stage low level amplifier for use from DC to 600 kc/s. Supply voltage 6-8v. Typical power gain 77 db into 150Ω load. Output power 10mW. TO72 four-lead encapsulation **£0.65***

Mullard TAA293. Medium frequency amplifier with frequency response of 600kc/s. Nominal supply voltage 6v. Typical power gain 89db. Maximum power dissipation 160 mW. Power output 10 mW. into 150Ω load. TO74 ten lead-encapsulation **£0.65***

Mullard TAA320. Metal oxide silicon low frequency pre-amplifier consisting of a MOST stage followed by a bi-polar transistor. Gate to source voltage 9-14v. Total power dissipation 200 mW. Drain current 1 µA. Output conductance 0.65 mmho. TO18 3-lead encapsulation **£0.60***

Type 741 Operational Amplifiers, 8-dual-in-line encapsulation **£0.30***

L.E.D. TYPE HP5082/4850

Red Light GASP Light Emitting Diodes giving bright diffused light of 0.8 mcd at forward voltage of 1.6V and DC current of 20 mA. Plastic wide angle lens 0.200in. diameter. Ideal for panel lights, etc. Price for 12 pieces **£1.75** incl. VAT and p.&p

OUR NEW 1975 ILLUSTRATED CATALOGUE/PRICE LIST covering VALVES, TUBES, SEMICONDUCTORS, PASSIVE COMPONENTS AND TEST EQUIPMENT IS NOW READY. PLEASE SEND **£0.20** FOR YOUR COPY.

* ALL PRICES EXCLUSIVE OF V.A.T. WHEN REMITTING CASH WITH ORDER PLEASE ADD **£0.50** PER MULTIMETER AND **£0.15** IN £ FOR OTHER ITEMS—SUBJECT TO A MINIMUM CHARGE OF **£0.20**—TO COVER HANDLING AND POSTAGE. NO C.O.D. ORDERS ACCEPTED:

TTL 74 I.C.s. 7400 13p 7441 65p 7485 140p 7401 14p 7442 65p 7486 34p 7402 14p 7447 75p 7489 270p 7403 16p 7448 70p 7490 40p 7404 16p 7450 15p 7491 80p 7405 14p 7451 16p 7492 50p 7408 16p 7453 16p 7493 40p 7410 13p 7454 22p 7494 75p 7413 32p 7470 30p 7495 70p 7414 80p 7472 25p 7496 75p 7416 30p 7473 32p 7497 45p 7420 14p 7474 32p 74121 34p 7422 25p 7475 32p 74141 65p 7425 30p 7476 32p 74142 250p 7427 37p 7480 65p 74154 150p 7430 14p 7481 95p 74154 130p 7432 25p 7482 76p 74192 120p 7437 27p 7483 95p 74193 120p 7440 16p 7484 95p		LINEAR I.C.'s CA3046 Transistor Array 50p CA3048 4 Independent Amplifiers 230p IC13038 VCO Fun. Gen. 14 pin DIL 275p LM301A Op. Amp. with ext. comp. 36p LM381 Audio Amplifier 90p LM381 Stereo Pre Amp. 150p LM3900 Quad Op. Amp. 70p MC1310 Colless FM Stereo Dec. 225p MC1312 SQ Quadrasonic Dec. 220p MC1314 SQ Quadrasonic Dec. 360p MC1315 SQ Quadrasonic Dec. 430p MFC4000 4W Audio Amp. 50p MFC6040 Electronic Attenuator 90p MFC8070 Zero Voltage Switch 250p NE536 FET Op. Amp. 250p NE555 Timer 8 pin DIL 45p		NE556 Dual 555 14 Pin DIL 100p NE560 PLL 18 Pin DIL 325p NE561 PLL with AM Demod. 16 Pin 325p NE562 PLL with VCO 16 Pin 325p NE563 PLL FM/IF Demod. 16 Pin DIL 300p NE565 PLL 14 Pin DIL 325p NE566 Function Generator 8 Pin DIL 200p NE567 PLL Tone Decoder 8 Pin DIL 250p TBA570 AM/FM Radio receiver 160p TBA800 5 Watt Audio Amp. 80p TBA810 7 Watt Audio Amp. 100p TBA820 2 Watt Audio Amp. 80p ZN414 TRF Radio Receiver 110p Data sheets on above I.C.'s 70p each.		Popular Op Amps 709 OPA with ext. comp. 8/14 pin DIL 28p 710 Diff. Comparator 14 pin DIL 35p 741 OPA with int. comp. 8 pin DIL 25p 747 Dual 741 14 pin DIL 70p 748 OPA with ext. comp. 8 pin DIL 38p 5001 12 Digit Calculator Chip 28 pin DIL 485p PC Keyboard 0-9, decimal, 4 function, C, K, keys. Size: 2-36" x 3-76" x 0-45" 400p					
DIL Sockets by Texas 8 pin 12p, 14 pin 13p, 16 pin 14p Mica + 2 bushes for TO3 & TO66 5p		VOLTAGE REGULATORS (PLASTIC) 723 1amp +Ve -Ve 14 pin DIL 45p 5v 7805 140p 7905 250p 12v 7812 140p 7912 250p 15v 7815 140p 7915 250p 18v 7818 140p — 24v 7824 140p — Data Sheets on Vol. Regs. 10p each		SCR-THYRISTORS 1A 50v 100v 400v 600v 2N3525 91p 1A 40p 42p 50p 70p 2N4444 185p 3A 43p 49p 75p 100p 2N5080 40p 7A — 80p 80p — 2N5062 65p 16A — 82p 88p — 2N5064 50p Other BT106 140p, C106D 45p, MCR101 25p BR100 BI-DIRECTIONAL TRIGGER FOR SCRs and TRIACS ... 21p		TRIACS 100v 400v 500v 3A 85p 95p 120p 6A 88p 120p 150p 10A 109p 154p 185p 16A 145p 180p 200p Other 40430 90p, 40486 85p, 40669 95p					
Transistors AC126/7 11p BC214 13p AC128 11p BC115 55p AC176 11p BD124 75p AC187 12p BD131 42p AC188 11p BD132 45p AD149 43p BF115 22p AD181 36p BF167 23p AD182 36p BF173 25p AF114/5 13p BF184 22p AF116/7 13p BF194 11p AF139 41p BF195 12p AF239 44p BF196 14p BC107/8 9p BF197 12p BC109 10p BFR39 78p BC147/8 11p BFY29/30 30p BC149 8p BFX84/5/6 BC157 13p 25p BC158 12p BFX88 24p BC159 14p BFX50/1/2 BC169C 12p BC177 18p BRY39 15p BC178 17p MJE340 45p BC179 18p MJE2855 95p BC182/3 10p MJE3055 65p BC184 11p MPSU06 55p BC212 11p OC26 47p		OC28 55p OC35 48p OC36 52p OC41/2 15p OC44/5 11p OC44/5 11p OC70/1/2 11p OC73 60p OC81/2 12p OC83/4 28p TIP295/5 TIP295/6 11p TIP41A 65p TIP42A 72p ZTX300 12p ZTX300 12p ZTX500 15p ZTX500 15p 2N364 11p 2N364 11p 2N370/5 11p 2N370/5 11p 2N3706/7 11p 2N3706/7 11p 2N3708 9p 2N3708 9p 2N3772 161p 2N3772 161p 2N3775 220p 2N3775 220p 2N3903 15p 2N3903 15p 2N4058 15p 2N4058 15p 2N4060 13p 2N4060 13p 40361 40p 40361 40p 2N1613 20p 2N1613 20p 40361 40p 40361 40p		40362 43p 40362 43p BY100 15p BY100 15p BY126 12p BY126 12p BY127 12p BY127 12p OA47 7p OA47 7p OA79 8p OA79 8p OA81 7p OA81 7p OA85 9p OA85 9p OA90 6p OA90 6p OA91 7p OA91 7p OA95 6p OA95 6p OA200 20p OA200 20p O2302 7p O2302 7p IN014 4p IN014 4p IN4001 5p IN4001 5p IN4004 6p IN4004 6p IN4007 7p IN4007 7p IN4148 4p IN4148 4p		LED TIL209 16p ZENERS 3-3V to 33V 400mW 9p 1-3W 18p A Tunnel AEY11 50p Varicap BB105 30p Noise ZIJ 75p		C-MOS LOGIC CD4000AE 19p CD4001AE 19p CD4002AE 19p CD4009AE 67p CD4011AE 21p CD4013AE 63p CD4016AE 63p CD4017AE 163p CD4018AE 229p CD4022AE 169p CD4024AE 116p CD4024AE 116p CD4027AE 91p CD4028AE 140p CD4029AE 195p CD4046AE 202p CD4047AE 157p CD4054AE 195p CD4055AE 195p CD4060AE 229p CD4071AE 26p CD4081AE 26p CD4501AE 120p CD4501AE 250p CD4528AE 120p		OPTO-ELECTRONICS ORP12 50p OCP70 30p ORP60 60p OCP71 90p ORP61 60p 2N5777 40p LEDS TIL209 with clip 16p Green/Yell. with clip 35p SEVEN SEGMENT DISPLAYS 3015F 0-35 in DIL 120p LIT704 0-33 in DIL 130p LIT707 0-33 in DIL 135p LIT747 0-68 in DIL 210p MAN-3M 0-127 in PCB 120p MAN-4 0-19 in DIL 180p NEW I.C. CA3130S COSMOS OP. AMP. WITH MOSFET INPUT. Ideal for single supply applications. 8 pin DIL in TO-5 Data 20p plus S.A.E. 100p	
MOSFETS 40803 58p 40803 58p 40763 58p 40763 58p 3N128 75p 3N128 75p 3N140 85p 3N140 85p 3N141 75p 3N141 75p		BRIDGE RECTIFIERS 50V 100V 400V 600V 0-25A — 20p — — 1A 22p 24p 27p 29p 2A 30p 35p 45p 48p 4A — 55p — — 6A 55p 60p — —		DIODES BY100 15p BY126 12p BY127 12p OA47 7p OA79 8p OA81 7p OA85 9p OA90 6p OA91 7p OA95 6p OA200 20p O2302 7p IN014 4p IN4001 5p IN4004 6p IN4007 7p IN4148 4p		UJTS TIS43 25p 2N2160 70p 2N2646 35p 2N4781 31p OAS1 OA85 9p OA90 6p OA91 7p OA95 6p A2002 7p IN014 4p IN4001 5p IN4004 6p IN4007 7p IN4148 4p					

Minimum order £2. P & P 20p. MAIL ORDER ONLY
Please add 8% VAT to total Govt., Colleges, etc, orders welcome

TECHNOMATIC LTD. 54 SANDHURST ROAD, LONDON, NW9
Tel. 01-204 4333

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes



Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit**. Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

CUT OUT THIS COUPON
 Tick or state subject of interest. Post to address below.

<input type="checkbox"/> ELECTRICAL ENGINEERING	Practical Radio & Electronics (with self-build kit)	<input type="checkbox"/> Construction Surveyor's P.U.I.
<input type="checkbox"/> City & Guilds	Radio Amateurs' Exam	<input type="checkbox"/> Clerk of Works Diploma
<input type="checkbox"/> Wiring and Installations		<input type="checkbox"/> C. & G. Building Quantities
<input type="checkbox"/> C. G. Electrical Tech-Primary	<input type="checkbox"/> ELECTRONIC ENGINEERING	<input type="checkbox"/> General Building Heating, Ventilating & Air Conditioning
<input type="checkbox"/> Gen. Electrical Eng.	Gen. Electronic Eng.	<input type="checkbox"/> Carpentry & Joinery
<input type="checkbox"/> AERONAUTICAL ENGINEERING	Practical Electronics (with kit)	<input type="checkbox"/> Painting & Decorating
Air Registration Board Certificates	<input type="checkbox"/> AGRICULTURAL ENGINEERING	<input type="checkbox"/> Plumbing
Gen. Aero Engineering		<input type="checkbox"/> C.E.I. (Part 1, 2, 3)
<input type="checkbox"/> AUTO ENGINEERING	REFRIGERATOR SERVICING	<input type="checkbox"/> Inst. Cost & Management
City & Guilds Auto Engineering	<input type="checkbox"/> MECHANICAL ENGINEERING	<input type="checkbox"/> Accountants Works Management etc. etc.
<input type="checkbox"/> Practice	Society of Engineers	
<input type="checkbox"/> Inst. Motor Industry	Inst. Engineers and Technicians	
<input type="checkbox"/> M.A.A./I.M.I. Management Diploma	General Mechanical Eng.	
<input type="checkbox"/> Gen. Auto Engineering	Welding	
<input type="checkbox"/> Auto Diesel Maintenance	Maintenance Eng.	
<input type="checkbox"/> Motor Mechanics	General Diesel Eng.	
<input type="checkbox"/> Service Station and Garage Management	<input type="checkbox"/> DRAUGHTSMANSHIP	
<input type="checkbox"/> TELECOMMUNICATIONS	Institute of Engineering Draughtsmen & Designers	
City & Guilds Telecommunications	General Draughtsmanship	
<input type="checkbox"/> Architectural Draughtsmanship	Technical Drawing	
<input type="checkbox"/> RADIO & TV	<input type="checkbox"/> CONSTRUCTION & BUILDING	
Gen. Radio and TV Eng.	Institute of Building	
<input type="checkbox"/> Radio Servicing, Maintenance and Repairs		

G.C.E.
 —58 'O' & 'A'
 Level Subjects
 —over 10,000
 Group Passes!

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College,
 Dept. TPW06, Reading RG7 4PF.

NAME.....
 Block capitals please
 ADDRESS.....
 POSTCODE.....

OTHER SUBJECTS.....
 AGE.....

Accredited by C.A.C.C. Member of A.B.C.C.

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course".
 Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.
 "My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to


ALDERMASTON COLLEGE
 Dept. TPW06, Reading RG7 4PF.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Publisher's subscription rate (including postage): for one year UK £5-00, Overseas £5-00 (\$13-50 USA/Canada) International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's Radio

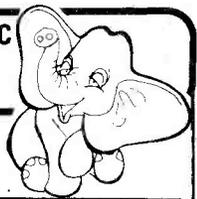LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES—MEAN LESS VAT.



You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIER

Features glass fibre PC board, Gardners low field transformer 6-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and, P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 153" x 23" x 66" mains operated. Free teak sleeve with every kit. **£31.00 (Carriage 50p).** (also built and tested **£37.50**)



HENELEC STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 23" x 66". Complete kit with teak sleeve. (also built and tested **£24.95**) **£21.00 (Carriage 50p).**



JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

NEW SPECIAL PURCHASE MULLARD TYPE LP1179 AND LP1171 AM/FM TUNER MODULES

These two modules together form a high quality AM/FM tuner covering the long, medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete. Supplied with circuits and spec. data

LP1179 FM Coverage 87-108 MHz
Bandwidth 300 KHz
Selectivity 1 dB
Signal to noise at limiting threshold 40 dB
Audio output 75 mV with built in tuning gang



LP1171 AM Bandwidth 6-5 KHz
Sensitivity 1 μV
Built-in AGC LP1171
Supply 6V negative earth
LP1179 and LP1171 £4 each or £7.50 pr.
Suitable Ferrite aerial £0.75
£4.00 each or £7.50 pair



Mullard Modules
LP1157 AM/Type 2-50
LP1185 10-7 F.F. Unit 4-30
LP1186 10-7 FM Tuner 4-85
Gortler Perm. F/M Tuner 4-20

Amplifiers with controls
E1210 12 volt 2 1/2 + 2 1/2 watts 8 ohms 8-25
SAC14 Mains 7 + 7 watts 8 ohms 11-75
SAC30 Mains 15 + 15 watts 8 ohms 14-95
CAO38 9 volt 1 1/2 + 1 1/2 watts 8 ohms 6-95
CAO68 12 volt 3 + 3 watts 8 ohms 10-50

FM and AM Tuners and Decoders
FM5231 (tu 2) 6 volt fm tuner 7-95
TU3 12 volt version (FM use with Decoder) 7-95
SD4912 Stereo Decoder for Tu 3-12 volt 7-95
SP62H 6 volt stereo FM tuner 14-80
A1007 9 volt MW-AM 4-95
A1018 9 volt FM tuner in cabinet 13-95
A1005M (S) 9-12 volt Stereo decoder FM for above 7-50
1062 12 volt Stereo decoder general purpose 6-50

Power Supplies Mains Input ('chassis-rest case)
470C 6 7/8/9V 300 MA with adaptors 2-25
P500 9 volt 500 MA 3-20
HC244R 3 1/8/7 1/2/9V. 400 MA stabilised 5-50
*P11 2v. 3 amp. 3-30
*P15 28v. 3 amp D 3-30
*P1080 12V 1A 4-70
*P1081 45V 0.9A 7-80
P12 4-12V. 0.4-1 amp 7-15
SE101S 3 1/8/9/12V. 1 amp stabilised 12-75
P1076 3/4/9/12V. 1/2 amp 4-20
SE800A 1-15 VOLT 0-1A stabilised 17-50

SINCLAIR MODULES & KITS

SINCLAIR PROJECT 80
ST80 Stereo preamplifier 11-95
Audio Filter Unit 6-95
Z40 15 Watt Amplifier 5-45
Z60 25 Watt Amplifier 6-95
P25 Power Supplies for 1 or 2 Z40

P26 Power Supplies (S Tab) for 1 or 2 Z40 7-98
TRANSFORMER FOR PZ8 4-00
FM TUNER 11-95
STEREO DECODER 7-95
IC20 power amp kit 7-95
PZ20 power supply for 1 or 2 P26 5-45

PACKAGE DEALS (carr./packg 35p)

2 x Z40 ST80 PZ5 25-00
2 x Z60 ST80 PZ6 27-75
2 x Z60 ST80 PZ8-trans 34-40
805 Kit 35-95

Sinclair Special Purchases

*Project 80 stereo preamp £6.75 (post 20p)
*Project 605 Kit £19.95 (post 25p)

EMI SPEAKERS SPECIAL PURCHASE

13 In. x 8 in. chassis speakers (Carr./packing 30p ea. or 50p pr.)
*150 TC 10 watts 8 ohms twin cone £2-20
450A Built in tweeter £3-85
8 ohms
EW 15 watt 8 ohms with tweeter £6-25
350 20 watt 8, 15 ohm with tweeter £8-95 each
*Polished wood cabinet £4-80 carr., etc. 35p each or 50p pair.



UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation. Brand new. (Post packing 25p. each).
TYPE A variable tuning slow motion drive £3-00
TYPE B 4-button push-button (adjustable) £3-50
TYPE C variable tuning £2-50
TYPE D 6 Button UHF/VHF £4-50

PA-DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt 'U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc.

FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF at HENRY'S DISCO CENTRE, 309 EDGWARE ROAD. TEL. 01-723 6963

TEST EQUIPMENT MULTIMETERS

Carr/packing 35p) £ p
U4324 20kΩ/V with case 9-85
U4312 20kΩ/V with case 13-80
U4317 20Ω/V with case 17-00
U4341 33kΩ/V plus transistor steel case 11-00
U4323 20kΩ/V plus 1kHz OSC with case 8-00
U4311 Laboratory meter £52-00
U4312 20kΩ/V with case £10-75
U4315 20kΩ/V with case £10-00
U4317 20kΩ/V with case £17-00
ITI-2 20kΩ/V slim type 5-95
THL33D (L33DX) 2kΩ/V Robust 7-50
TP55N 20kΩ/V (Case £2) 10-75
TP105 20kΩ/V 8-50
TW205 20kΩ/V 13-00
TW50K 50kΩ/V 14-50
S100TR 100kΩ/V plus transistor tester 22-50



ALL PRICES SUBJECT TO 8% VAT

FREE:— SEND NOW FOR OUR FREE LIST NO. 36 FOR OUR COMPLETE RANGE OF OVER 10,000 SEMICONDUCTOR DEVICES AT NEW LOW PRICES.

EXTRA DISCOUNTS

Semiconductors—Any one type or mixed SN74 Series IC's, 12—extra 10%; 25—extra 15%; 100—extra 20%.

TRANSISTORS & INTEGRATED IC'S

TTL "7400 series" IC's from 16p each
Cosmos "4000 series" IC's from 25p each
Linear Op-Amps from 40p each
Signetics Phase Lock IC's; RCA Linear IC's; TOS Power Devices in PNP and NPN; BC107 and "BC range" from 12p
Range of OC Types 18p
Plastic Power Devices, Rectifiers, Zener, Power Regulator IC's and many others.
Diodes up to 10 watts

DIL SOCKETS

8 PIN 14p
14 PIN 15p
16 PIN 17p
24 PIN £1-15
28 PIN £1-25



NEW REVOLUTIONARY SUPERTESTER 680R

£ p
680R Multi-tester 18-50
†TE40 AC Multivoltmeter 19-75
†TE15 Grid dip meter 19-50
440kHz-28mHz
†TE65 28 Range valve voltmeter 22-50
†TE20D RF Generator, 120kHz-500mHz 18-95
†TE22D AF Generator 20Hz-200kHz 19-95
*HM350 in circuit transistor tester 19-50
*C3025 Deluxe meter 1-300mHz 6-95
*TT145 Compact transistor tester 14-75
†G3-36 R/C osc. 20Hz-200Hz 19-75
*SE30A De-luxe signal tracer 12-95
*SE400 Mini-lab all in one tester 15-50
CI-5 Scope 500,000KHz carrier tester 43-00
Radio activity counter 0-10r (carr. £1) 9-97
Mains unit for above (carr. 50p) 3-75

TAPE HEADS

Marriot XRPS/17 1/2 Track High 2-50
Marriot XRPS/18 1/2 Track Med. 3-50
Marriot XRPS/36 1/2 Track Med. 5-00
Marriot XRPS/63 1/2 Track High 1-75
Marriot Erase Heads for XRSP 17/18/36 (XES11) 75p
Marriot BXIZE 343 1/2 Track erase 75p
R/RP Rec'd/Play 1 Track 45p
HRP S'glo Trk/Rec/Play 35p
Bogen Type UL280 Erase 1-50
Miniature Stereo Cassette Rec/Play 2-25

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max. DC operation, complete with data. Price £1-50 each or 2 for £2-85.



Printed Circuit Panels 50p.

8 DIGIT POCKET ELECTRONIC CALCULATORS

Sinclair Cambridge Built £11-00
Cambridge Kit £9-00
Cambridge Memory Built £17-50
Scientific Built £16-00
Scientific Kit £13-50



NOMBREX TEST EQUIPMENT

Model 35 Stabilised Power Supply

A short circuit proof power supply delivery up to 30 volts at 1 Amp. Built-in Volts and ammeters **£34-00**

Model 40 Wide Range Audio Signal Generator

A high stability signal generator using the low distortion Wien bridge principle. **£34-00**

Model 41 RF Signal Generator

Covering 150 KHz to 220 MHz in 8 ranges. Built in AF mod. Output up to 50mV. **£38-00**

Model 42 Wide Range RF Signal Generator

Covering 150 KHz to 300 MHz in 8 ranges. Highest range on harmonic. **£24-50**

Model 43 RC Bridge

Null indicating bridge for resistors and capacitors. Resistance range 10R to 10M ±2% at Centre Scale. **£23-50**

Model 44 Inductance Bridge

Measures 1μH to 100H in 4 ranges ±5% accuracy. Q measurement from 0.1-1,000 ±10%. **£34-00**

Model 45 Direct Reading Frequency Meter

10Hz to 100 KHz in 4 ranges. Input from 10MV to 5V **£36-00**

ELECTRONIC FOOTBALL & TENNIS WITH THE VIDEO SPORT FABULOUS ON YOUR OWN TV

Play three exciting electronic ball games ● FOOTBALL ● TENNIS ● HOLE IN THE WALL on your own TV. Just insert Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.

OUR INCREDIBLE PRICE **£34.72 + VAT**

DEMONSTRATIONS NOW IN ALL HI-FI CENTRES

All models except Model 35 are internally powered from 9V battery (extra). Carriage and packing all models 37p.

NOW OPEN—SUPERMARKET

Come and browse round the new components supermarket at 404 Edgware Road, Bargins galore. Goodie Bags. Components, etc. WATCH FOR FURTHER DEVELOPMENTS!

Henry's Radio

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Hi Fi and Electronics Centres Open 9 am - 6 pm

Prices correct at time of preparation. Subject to change without notice. E.&O.E