

PRACTICAL WIRELESS


OCTOBER
1975

30p



**EXTRA
INSIDE
8-PAGE
SUPPLEMENT**

SIMPLE HOME PROJECTS

No.1

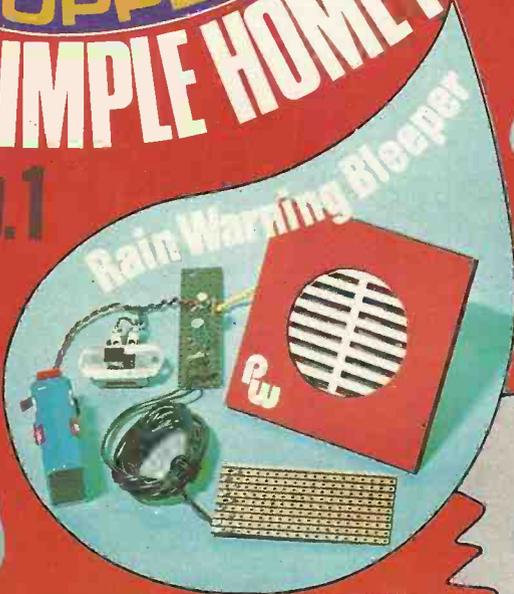

**MEMO
Reminder**

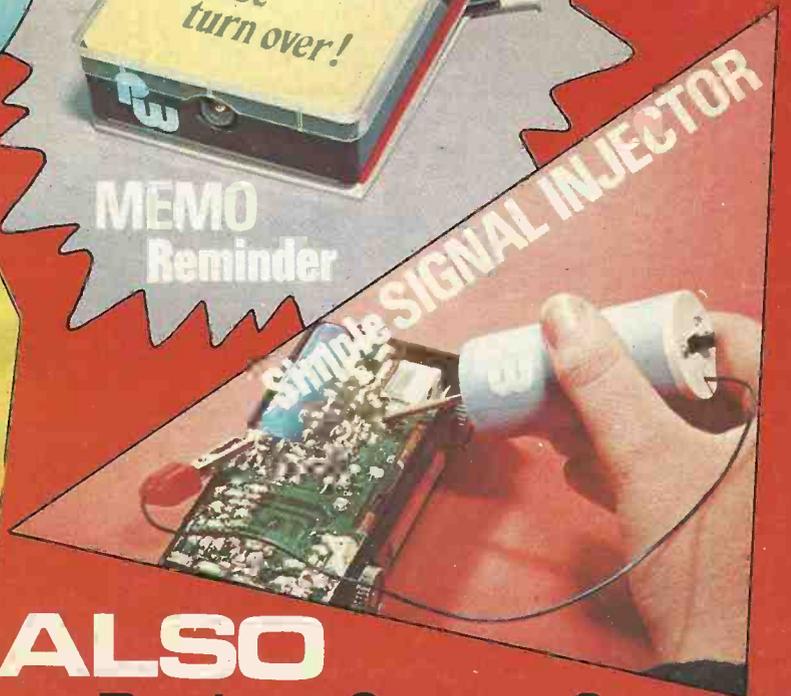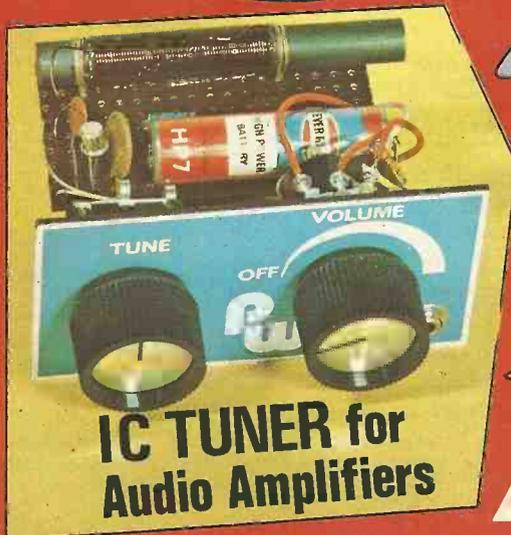

ALSO

STARTING: Improve your Budget Stereo System

**ALL MAIL ORDER BY
RETURN.C.O.D.SERVICE
WELCOME**

C.T. ELECTRONICS

Tel: 01-994 6275

All mail order and enquiries to 270 Acton Lane, Chiswick, London W4 5DG

V.A.T.
Unless otherwise stated all prices are exclusive of V.A.T. Please check whether the goods you are ordering are 25% or 8% V.A.T. Carriage orders under £5 please add 33p. Order over £10 post free in U.K. only. This to be at our discretion.

SEMICONDUCTORS

AAZ12	25p	BC214	14p	IS100	15p
AC107	35p	BC214L	15p	IS103	15p
AC125	25p	BC238	15p	MJ340	50p
AC126	25p	BC239	15p	MJ461	95p
AC127	25p	BC300	30p	MJ2801	£1.25
AC128	25p	BC301	30p	MJ2801	£1.95
AC176	25p	BC302	30p	MJE340	50p
AC187	27p	BC303	35p	MJE370	75p
AC188	27p	BCY31	35p	MJE371	90p
ACY17	25p	BCY32	35p	MJE520	65p
ACY18	25p	BCY33	30p	MJ2855	£1.20
ACY19	25p	BCY34	65p	MJE3055	75p
ACY20	25p	BCY38	65p	MM1813	45p
ACY21	25p	BCY39	95p	MM1712	65p
AD140	60p	BCY55	£1.50	MPF102	45p
AD142	60p	BCY70	20p	MPF103	45p
AD161	45p	BCY71	20p	(N25457)	35p
AD182	45p	BCY72	20p	MPF104	45p
AF114	25p	BD121	75p	(N25458)	35p
AF115	25p	BD123	85p	MPF105	45p
AF116	25p	BD124	70p	(N25459)	40p
AF117	25p	BD131	40p	OA47	15p
AF118	50p	BD132	50p	OA70	10p
AF124	30p	BD135	50p	OA79	10p
AF239	60p	BD136	50p	OA81	10p
BA102	30p	BD139	75p	OA90	10p
BA112	50p	BD140	87p	OA91	10p
BA114	16p	BD153	80p	OB200	10p
BA155	16p	BD156	80p	OA202	10p
BA156	15p	BDY17	£1.50	OA210	35p
BC107	13p	BDY18	£1.75	OA211	35p
BC108	12p	BDY19	£1.90	OC16	90p
BC109	14p	BDY20	£1.20	OC19	85p
BC109c	16p	BF166	10p	OC24	10p
BC113	13p	BF166	10p	OC26	65p
BC114	13p	BF178	35p	OC28	60p
BC115	15p	BF180	35p	OC35	60p
BC116	15p	BF194	16p	OC36	65p
BC117	20p	BF195	16p	OC42	40p
BC118	15p	BF196	16p	OC44	20p
BC119	30p	BF197	16p	OC45	25p
BC143	25p	BF200	30p	OC70	15p
BC147	12p	BF224	18p	OC71	12p
BC148	12p	BF244J	18p	OC72	20p
BC149	12p	BF245	45p	OC75	25p
BC149c	14p	BF259	35p	OC76	25p
BC157	14p	BFX32	30p	OC77	40p
BC158	14p	BFX34	30p	OC81	25p
BC159	15p	BFX35	30p	OC83	25p
BC167	14p	BFX36	30p	OC84	25p
BC168	14p	BFX38	30p	OC139	30p
BC169	14p	BFY10	35p	OC170	30p
BC169c	15p	BFY44	50p	OC171	30p
BC172	13p	BFY50	25p	OC200	60p
BC182	12p	BFY51	25p	OC201	60p
BC182L	12p	BFY52	25p	OC202	75p
BC183	12p	BFY53	25p	TIP29A	45p
BC183L	12p	BFY90	25p	TIP30	55p
BC184	12p	BSW68	70p	TIP41A	77p
BC184L	12p	BSW63	65p	TIP32A	69p
BC185	35p	BSW68	80p	TIP33A	£1.00
BC186	27p	BSX19	15p	TIP34A	£1.40
BC212	12p	BSX20	15p	TIP35A	£3.20
BC212L	12p	BY127	20p	TIP36A	£3.50
BC213	12p	BY127	20p	TIP41A	77p
BC213L	12p	BY164	65p	TIP42A	85p

QTY. DISCOUNTS: 12+ 10%; 25+ 15%; 100+20%

TIP29B	54p	2N2369A	50p
TIP30B	60p	2N2477	30p
TIP31B	65p	2N2646	30p
TIP32B	77p	2N2846	£1.50
TIP33B	£1.06	2N4904	25p
TIP34B	£1.62	2N2805	30p
TIP35B	£2.71	2N2906	25p
TIP36B	£3.50	2N2907	25p
TIP41B	78p	2N2926	25p
TIP42B	85p	2N3053	25p
TIP29C	65p	2N3055	50p
TIP30C	72p	2N3232	£1.35
TIP31C	80p	2N3252	£1.10
TIP32C	£1.00	2N3553	£1.40
TIP33C	£1.20	2N3643	30p
TIP34C	£1.80	2N3702	12p
TIP35C	£3.00	2N3703	12p
TIP38C	£3.74	2N3704	12p
TIP41C	90p	2N3705	12p
TIP42C	£1.00	2N3706	12p
TIS50	40p	2N3707	12p
ZTX107	15p	2N3708	14p
ZTX300	15p	2N3709	14p
ZTX501	20p	2N3771	£1.60
ZTX502	20p	2N3772	£1.60
ZTX504	50p	2N3792	£1.80
ZTX531	30p	2N3794	30p
ZTX550	25p	2N3819	35p
IN659	8p	2N3821	55p
IN614	8p	2N3823	79p
IN616	8p	2N3866	85p
IN4001	8p	2N3904	22p
IN4002	9p	2N3905	25p
IN4003	9p	2N3906	25p
IN4004	10p	2N4014	80p
IN4005	12p	2N4036	82p
IN4006	14p	2N4037	44p
IN4007	16p	2N4058	14p
IN4148	7p	2N4059	14p
2N696	25p	2N4080	12p
2N697	25p	2N4081	12p
2N698	25p	2N4082	12p
2N706	12p	2N4126	18p
2N706A	14p	2N4286	25p
2N708	15p	2N4287	25p
2N929	22p	2N4288	27p
2N930	20p	2N4314	30p
2N1132	25p	2N4290	32p
2N1302	30p	2N4291	32p
2N1303	30p	2N4302	45p
2N1304	30p	2N4444	£1.90
2N1305	30p	2N4871	35p
2N1306	30p	2N4803	£1.30
2N1307	30p	2N4819	90p
2N1308	30p	2N5069	£1.30
2N1309	30p	2N5191	96p
2N1613	30p	2N5192	£1.10
2N1711	30p	2N5194	£1.20
2N1890	60p	2N5195	£1.40
2N2146	15p	2N2147	90p
2N2147	90p	2N5245	45p
2N2160	80p	2N5286	55p
2N2170	25p	2N5293	50p
2N2217	25p	2N5457	35p
2N2219	25p	2N5458	35p
2N2222	20p	2N5459	40p
2N2222A	20p	2N5485	55p
2N2306	70p	2N5489	55p
2N2306	70p	2N5555	50p
2N5777	40p	2N5777	40p

CRS1/05	40p
CRS1/10	50p
CRS1/20	60p
CRS1/40	65p
CRS1/60	90p
CRS1/80	62p
CRS2/30	62p
CRS3/40	90p
CRS7/400	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.60
C106B	45p
C106D	70p
40669	90p
TIC44	35p
2N4444	£1.90
BT10/500A	90p

BRIDGE RECTIFIERS	
W02 1A 200V	38p
BY164 1-4A 200V	57p
MDA952/2 6A 100V	80p
ZENER DIODES	
BZY85 Series	£1.25
3-3V-33V, 5% 11p	
1-5W range	25p
10W range	45p

L.E.D.	
TIL209	38p
HP5082	28p
MAZ082R	20p

L.D.R.	
ORP12	60p
NE555 Timer	80p
TO5 VOLTAGE REGULATORS	
L005 5V 600mA	30p
L036 12V 600mA	30p
L037 15V 450mA	£1.60 ea.

VEROBOARD	
2 1/2 x 3 1/2	0-15
2 1/2 x 5	23p
3 1/2 x 3 1/2	35p
3 1/2 x 5	35p
1 1/2 x 2 1/2	40p
1 1/2 x 3 1/2	79p
1 1/2 x 5	£1.12
1 1/2 x 8	£1.84
PIN INS. TOOL	72p
S.P.F. CUTTER	52p
100 PINS SS	30p
100 PINS DS	30p
500 PINS SS	£1.55
500 PINS DS	£1.55

BNC PLUGS at 35p each.
UHF (N) PLUGS at 50p each.

U.H.F. V.S.W.R. probes as U.H.F. transmitters £5 each + 8% VAT.
All the above are new in original packets. Please add 8% VAT P & P 30p.

POTENTIOMETERS	
Linear or Log	Single Double
Rotary Pots	17p 45p
Rotary Switched	25p

★★SPECIAL OFFERS★★

MINIATURE MAINS TRANSFORMER.
PRI 240V. SEC. 12V. 100Ma. Manuf.: Hincinley
Size: 36 x 45 x 40mm. F.C. 53mm.
Price 1-65p. 100 60p ea. 1,000 50p ea. 10,000
40p ea. 8% VAT.

MINIATURE MAINS TRANSFORMER.
Primary 115/240V Sec. 18v/250 Ma at 80p ea.
+ VAT & postage 33p. 8% VAT.

MULLARD POT CORE TYPE FX2241 at 60p ea. + 33p p.p. 8% VAT.

24V D.C. SOLENOID by MAGNETIC DEVICES 60p each. 2 1/2 long x 3/4 x 1/4 in. + 8% VAT.

240V. A.C. SOLENOID. Reversible operation; twin coil. Size approx. 2 1/2 x 1 1/2 x 1 1/2 in. 90p.

30 unmarked OC71 transistors £1-00
25 Unmarked 250mW Zener diodes. 4-7V, 5-1V, 6-2V, 7-5V, 9-1V, 10V. Measured and tested! £1-00

Please state voltage required. £1-00
D.I.L./TO99 45p
741C Op Amp 8/14
747C Dual Op Amp £1-20
748C Op Amp 75p

30F 800V WKG PAPER CAPACITORS, ideal for Strobe Constructors £1-50 each + 8% VAT + 33p post.

Many other values of **PAPER CAPACITORS** in stock. Phone for details.

JACKSON AIRSPACED CAPACITORS to suit 3in. spindle:
1000P Two Gang at 55p + 25% VAT
500pF Two Gang at 75p + 25% VAT

MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)
Type 092 0-8-2-2p
801 0-8-2-2p Price 10p ea.
991 0-5-1-3p

QUANTITY DISCOUNTS PLEASE TELEPHONE
1000pF Feedthrough capacitor 5p ea.
Miniature tubular P.C. trimmers 50p ea.
3-5-13pF
6-30pF 10p ea.
4p c/o Varley 700 Ω relay 50p ea.

Gold Flashed professional TRANSISTOR SOCKETS. To suit small signal TO18, etc. 30 for £1-00 + 8% VAT.

W. WOUND POTS 1Ω-100KΩ at 30p each
Colvern or Reliance styles + 25% VAT

VERO EDGE CONNECTOR 24 way 1" pitch 30p each + 8% VAT. All the other sizes in stock.

SIEMENS VARLEY RELAY 4P C/O 100Ω 24V 50p each.

PLESSEY RELAY 2 P C/O 6V operation 40p each.

MODERN DISC CERAMICS £1-00 a hundred, £3-00 a thousand + 25% VAT. Phone or write for list.

ACCESSORIES
DIL SOCKETS, 8 pin 14p, 14 pin 14p, 16 pin 14p. Mica Washers + 2 Bushes (TO3 or TO86) 4p.

METAL BOXES

ALUMINIUM BOXES IDEAL FOR VEROBOARD WITH BASE & P.K. SCREWS

AB7	2 1/2" Long	5 1/2" Wide	1 1/2" High	55p
AB8	4"	4"	1 1/2"	55p
AB9	4"	2 1/2"	1 1/2"	55p
AB10	4"	5 1/2"	1 1/2"	55p
AB11	4"	2 1/2"	2"	65p
AB12	3"	2"	1"	50p
AB13	6"	4"	2"	77p
AB14	7"	5"	2 1/2"	80p
AB15	8"	6"	3"	£1-16
AB16	10"	7"	3"	£1-32
AB17	10"	4 1/2"	3"	£1-10
AB18	12"	5"	3"	£1-32
AB19	12"	8"	3"	£1-80

ALUMINIUM BOXES WITH SLOPING TOP PANEL—IDEAL FOR PRE-AMPS, ETC., USING SLIDER CONTROLS

AB20 8" Long 9" Wide 3 1/2" High at back £2-20
2" High at front 6" Slope to front
With P.K. Screws

AB21 As above but 10" long £2-20
AB22 As above but 12" long £2-60

★ SPECIAL OFFERS ★

MULTICORE CABLE. 20 way 14/0076 + Screen at 70p per yard+ postage by weight.

MULTICORE CABLE. 25-way, individually screened. 14/0076. £1-00 per yard+V.A.T. Postage by weight.

3 CORE PVC INSULATED MAINS CABLE. GREY ML6850, 3x7/0-2mm. Price 100m-£4-50, 1,000m-£35, 10,000m-£330.

METAL OXIDE RESISTORS TR4/5/6 in stock. All values 1-off price 3p each. Discount on quantity.

10 TURN TRIMPOTS by Bourns, Mec, Painton, etc. All values in stock. 50p each. Discount on quantity.

KOKUSAI MECHANICAL FILTER. 455 Kc/S. 6 Kc/S overall. Ideal for A.M. £5 each INC VAT. Postage 33p each.

TRANSFORMER 240V A.C. Primary 1185-0-1185V at 360Ma Secondary £12+8% VAT+£1-50 postage.

OMRON OCTAL REL

PRACTICAL WIRELESS

VOL. 51 NO. 6

ISSUE 824

OCTOBER 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

PRODUCTION & NEWS EDITOR

Colin R. Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Susan King

ADVERTS MANAGER

01-634 4293 Roy Smith

CLASSIFIED ADVERTS

01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

Binders (£1.90) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at Carlton House, 66-68 Great Queen Street, London, WC2 5DD.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of *Practical Wireless* and *Television* only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

Practical Wireless, October 1975

● NEWS & COMMENT

454 MAKING LIFE EASIER—Editor's comment

455 NEWS . . . NEWS . . . NEWS . . .

459 HOTLINES on recent developments by *Ginsberg*

479 NEXT MONTH IN PRACTICAL WIRELESS

484 CQ! CQ! CQ! CQ! CQ!

488 PRODUCTION LINES by *Colin Riches*

501 LETTERS—Readers' views

502 ON THE AIR—

502 Broadcast Bands, SW—*Derek Bell*

505 Broadcast Bands, MW—*Charles Molloy*

506 Amateur Bands—*Eric Dowdeswell, G4AR*

506 TELEVISION—the October issue

● CONSTRUCTIONAL

456 ADD-ON 'Q' MULTIPLIER—*R. A. Penfold*

460 TELE-TENNIS BALL SPEED CONTROL—*R. S. Girdwood*

469 MINIATURE 2m EQUIPMENT—Part 2: Preamplifier—
W. H. Bond, F.R.C.S., G3XGP

474 TAKE 20 No. 72—Trafficator Audio Repeater—*David Andrews*

480 IMPROVE YOUR BUDGET STEREO SYSTEM—Part 1—
B. Barnard

485 AIDS TO IMPROVED RECEPTION—Part 1—*C. Heath*

490 VARICAP ABSORPTION WAVEMETER—*H. S. Wood, T. Eng. (CEI) MITE, G8SX*

● OTHER FEATURES

465 YOUR CONTINENTAL HOLIDAY RECEPTION

466 TECHNICROSS No. 11—Puzzle

477 GOING BACK—Equipment of Yesteryear—*Colin Riches*

493 ELECTRONIC WRISTWATCHES—*J. B. Dance*

509 IC OF THE MONTH No. 54—Motorola MC14440 CMOS Clock

**SPECIAL EXTRA! —8-PAGE SUPPLEMENT —
SIMPLE HOME PROJECTS No. 1**

HUGE DISCOUNTS ON LEADING BRAND HI-FI

Full labour and material LOW DEPOSIT CREDIT TERMS

	Rec. Price	RSC Price
LINEAR 202 Amplifier	£45.40	£28.95
LINEAR 505 Amp 5 + 5w	£22.85	£19.95
AUDIO FIDELITY Model 60 Amp	£69.45	£53.95
WHARFEDALE LINTON Amp	£78.85	£57.95
LEAK 2100 Amplifier	£138.60	£107.95
LEAK 2002 Cassette	£161.46	£125.95
LEAK 2030 L/ Speakers	£109.38 Pr	£85.95
LEAK 2060 L/ Speakers	£96.65 Ea	£74.95
LEAK 2000 Tuner/Amp	£223.96	£172.95
ROTEL RX152 Tun/Amp	£109.39	£79.95
ROTEL RX202 Tun/Amp	£124.42	£89.95
ROTEL RX402 Tun/Amp	£169.93	£120.95
ROTEL RT224 Tuner	£72.50	£51.95
ROTEL RT324 Tuner	£92.50	£66.95
WHARFEDALE Denton I L/Spkr	£39.10 Pr	£26.95
WHARFEDALE Denton 2XP L/Spkr	£57.29 Pr	£43.95
WHARFEDALE Linton 3XP L/Spkr	£79.69 Pr	£59.95
FANE Ambassador 35 L/Spkr	£103.00 Pr	£79.95
FANE MARQUESS 30 L/Spkr	£86.75 Pr	£57.50
FANE Model One Spkr Kit	£27.75 Pr	£21.95
WHARFEDALE Linton II Kit	£33.45 Pr	£22.50
WHARFEDALE WHD20 Cassette	£120.00	£89.95

BASF CASSETTES in Snap Pack CARR. FREE

LH CASSETTES		SUPER SM CASSETTES	
Rec. Price	RSC Price	Rec. Price	RSC Price
C60	98p	65p	3.00
C90	1.36	90p	3.99
C120	1.87	1.20	5.50

Also Shure Cartridges, Basf Tape, Koss H/Phones, etc. Prices of above correct at Aug 19 1975

AKAI TAPE UNITS

	Rec. Price	RSC Price
CS30D	£105.59	£77.50
CS34D	£137.50	£99.95
GXC39D	£186.50	£132.95
GXC39	£205.50	£144.95
GXC75D	£258.50	£181.95
GXC310D	£113.00	£79.95
GXR82D	£162.50	£116.95
4000DS	£619.50	£122.95

TURNTABLES

GOLDRING GL75 with G800 As above but with Plinth and Cover	£39.95	£51.95
PIONEER PL12D with Plinth and Cover	£48.50	£48.50
BSR MP60 with Plinth and Cover plus G850 Goldring Cartridge	£22.95	£22.95
GARRARD SP25 Mk. IV with Plinth and Cover plus G850 Cart.	£29.95	£29.95

PLINTH AND COVER



for Garrard SP25 or BSR MP60
£3.75
Carr. 50p

TITAN GROUP/DISCO SPEAKERS

	Rec. Price	RSC Price
T12/35 12" 35w	£13.00	£10.95
T12/60 12" 60w	£20.00	£14.95
T12/100 12" 100w	£35.00	£27.95
T15/70 15" 70w	£27.00	£19.95
T15/100 15" 100w	£38.50	£27.95
T18/100 18" 100w	£42.50	£29.95

DISCO SYSTEM

40 WATT



Consisting of Twin BSR T/table Console with Pre-amp and built-in Power Output. Sep. vol. controls for each T/table. H/phone monitoring facilities. Sep. Bass and Treble controls. Mic. Vol. control. Neon Mains Indicator. Plus Pair 12" 25w Spkrs. in matching Rexine covered cabinets.
£99.99
carr. £3

Terms: Dep. £15.99 and 18 fortnightly paymts. £5.38. (Total £112.83)

MOBILE DISCO CONSOLE




MIC., JACK, PHONE JACK, MONITOR VOL. CONTROL, MONITOR SELECTOR DECK (1) Vol. Control, DECK (2) Vol. control, Mic. Vol. Control, Treble Control, Bass Control and ON/OFF Switch, Neon Indicator, BSR T/tables.
£59.95
Carr. £3

Terms: Dep. £7.95 and 18 fortnightly paymts. £3.33 Total £67.89.

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

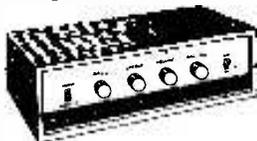Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db.



Treble Control ± 13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 - 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and INSTRUCTIONS **£14.99** Carr 40p

COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £19.50.


HI-FI SPEAKER ENCLOSURES

Simulated Teak finish. Sizes approx. Carr. 50p. per enc.

ME8 13x9 1/2 x 6 1/2 in.	£4.50
JE8 16x11x9 in.	£6.95
SE10 25x16x9 in.	£10.25
SE12 25x16x9 in.	£10.25

Both cut for 8in. speaker.
Cut for 10in. and Tweeter
Cut for 12in. and Tweeter

POWER (SLAVE) AMPLIFIER 100 WATT

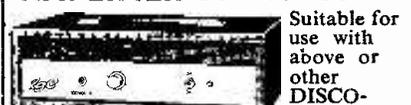

Suitable for use with above or other DISCO-Consoles. Also for increasing output of lower-powered Amplifiers.

£39.95
carr. £1

Terms: Dep. £5.11 and 8 mthly paymts of £5.11 (Total £45.99)

AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE. Exceptional performances at low cost.

HF808T 8" 10W	£2.95	HF120D 12" 15W	£7.50
HF102D 10" 10W	£3.95	HF126 12" 15W	£9.25
HF120 12" 15W	£6.95	HF126D 12" 15W	£9.95

AUDIO FIDELITY FRI SPEAKER KIT

Response 30 Hz-15 KHz. Rating 15 watts in sealed cabinet. Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material, Screws.

Terminal Panels. **£13.64** each Carr. Free.
SPECIAL OFFER **£18.50** Pair Carr. 80p



AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 Gauss 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range **£7.95** Carr. 45p.
OR SENIOR 15 WATT INCLUDING **£10.25** Carr. 50p.
HF123 13,000 GAUSS SPEAKER

AUDIO FIDELITY MODEL 80 HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 8-15 Ω. **£9.25** pr.
MODEL 83 8" 15w. with parasitic Tweeter. £7.99 ea. **£12.50** pr.
Response 25 Hz to 15 KHz. Gauss 13,000 Imp 8-15 Ω

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

ALL PRICES INCLUDE V.A.T.	
MIDGET CLAMPED TYPE	
250v. 60mA 6.3v. 2a.	£1.75
250-0-250v. 60mA 6.3v. 2a.	£1.95
FULLY SHROUDED UPRIGHT MOUNTING	
250-0-250v. 60mA 6.3v. 2a. 0-5-6.3v. 2a.	£2.60
250-0-250v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4.35
300-0-300v. 130mA 6.3v. 4a. C.T. 6.3v.	
1a. for Mullard 510 Amplifier	£5.20
350-0-350v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4.35
350-0-350v. 150mA 6.3v. 4a. 0-5-6.3v. 3a.	£5.20
425-0-425v. 200mA 6.3v. 4a. C.T. 5v. 3a.	£9.95
425-0-425v. 200mA 6.3v. 4a. 6.3v. 4a. 5v. 3a.	£10.00
450-0-450v. 250mA 6.3v. 4a. C.T. 5v. 3a.	£10.45

FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50c/s. Screened

TOP SHROUDED DROP-THROUGH TYPE	
250-250v. 70mA 6.3v. 2a. 0-5-6.3v. 2a.	£2.60
250-0-250v. 100mA 6.3v. 3-5a.	£2.90
250-0-250v. 100mA 6.3v. 2a. 6.3v. 1a.	£3.20
350-0-350v. 80mA 6.3v. 2a. 0-5-6.3v. 2a.	£3.20
250-0-250v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4.35
300-0-300v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4.35
300-0-300v. 130mA 6.3v. 4a. 0-5-6.3v. 1a suitable for Mullard 510 Amp.	£5.20
350-0-350v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4.35
350-0-350v. 150mA 6.3v. 4a. 0-5-6.3v. 3a.	£5.20
FILAMENT OR TRANSISTOR POWER PACK	
Type: 12v. 1a. £1.10, 6.3v. 1.5a. £1.06, 6.3v. 2a. £1.10	
6.3v. 3a. £1.70, 6.3v. 6a. £2.60, 12v. 3a. or 24v. 1.5a. £2.60	
0-9-18v. 1.2a. £2.26, 0-12-25-42v. 2a. £3.19	

SELENIUM RECTIFIERS F. W. (Bridged)	
All 6/12v. D.C. output. Max. A.C. input 18v.	
1a. 45p. 2a. 57p.	
3a. 65p. 4a. 85p.	
5a. £1.15.	
L.F. CHOKES	
150mA, 7-10H, 250 Ω	£1.28; 100mA, 10H, 200 Ω
£1.10; 60mA, 10H, 400 Ω	£1p.

RSC 100 WATT DISCO SYSTEM

50 WATT SPEAKER

AT FANTASTIC LOW PRICES!

50 WATT SPEAKER

TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER Complete with lid

HEADPHONES MICROPHONE

- Units listed below
- (a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier
 - (b) PAIR OF HI-FI HEAD PHONES
 - (c) MATCHING 'MIKE'
 - (d) PAIR 50 WATT SPEAKERS Black Roxine covered Cabinets Size approx. 18" x 18" x 8"
- £169-99**

RSC TDI DISCO CONSOLE

Incorporating twin BSR MP60 type turntables or Sonotone or Accos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control. Black Vynide covered Cabinet with lid.

Or DEP. £9-95 and 18 fortnightly pmts. £89-95

£5-11 (Total £101-93) Carr. £1-50

DEP. £19-99 & 18 fortnightly. Payments of £9-75 (Total £195-49).

STEREO VERSION
Of Above System
Or DEPOSIT £34-95 and 18 fortnightly pmts. £209-95

£11-19 (Total £238-87) Carr. £3-50

TD2S STEREO VERSION OF ABOVE
Terms DEPOSIT £20 £125-00 and 18 fortnightly payments £6-71 Carr. £1-60 (Total £120-78)

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £119-95

Twin McDonald MP60 type turntables. Sonotone or Accos cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £13-95 and 18 fortnightly payments £6-78 (Total £135-99)

or DEPOSIT £25 and 18 fortnightly pmts £8-30 (Total £174-40). Carr. £3

STEREO VERSION £155

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100Watt 14,000 gauss 8/15Ω	15" 60 Watt 13,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 8/15Ω
£35-95	£18-95	£13-95

Dep. £7-95 and 8 mthly payments £4-00 (Total £29-95)

Dep. £4-17 and 8 monthly payments £2-17 (Total £21-63)

FOR BASS GUITAR, ELECT. ORGAN, ETC.

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Vynide & Vynair

TYPE CI32 40-50 WATTS £27-95
Incorporating two exceptionally efficient 13" x 8" speaker units. Dep. £3-95 and 8 monthly payments £3-50 (Total £31-95) Carr. 65p

TYPE CG70 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £8-11 & 8 mthly pmts. £5-11 £39-95 (Total £43-99) Carr. 85p

'POP' 25/T 12" 25W HIGH POWER TWEETER PH50

Dual cone. 15 ohm imp. (Not for Bass Guitar use). Terms for Pairs: Deposit £3-90 and 8 mthly pmts of £2-75 (Total £25-60).

Response 3KHz-20KHz with 2 to 4 mld. Non elect. filter available 55p. Rating 50 Watt Imp 8Ω

£6.65

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphones and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed, Tremolo Intensity. Terms: DEPOSIT £7-73 and 8 monthly payments £3-40 (Total £34-93) Carr. free

£29-99

D40 50 WATT DISCO KIT ALL PURPOSE FULL RANGE

Consisting of 12" 13,000 Gauss Bass Unit, HPX1 Cross over and PH50. Tweeter as above. Imp 8/15Ω (Bass Guitar requires pair in one cabinet). Terms: Dep. £3 x 8 mthly. pmts. £2-75 (Total £25)

£21-50

FAL MAESTRO COMBINED 30W AMP. AND 12" SPEAKER £55-95

Free Carr. For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size Fitted carrying handle. Deposit £9-25 and 8 monthly payments £6-78 (Total £68-33)

HIGH QUALITY LOUDSPEAKER UNITS

ALL 2-TONE VYNIDE and VYNAIR FINISH L1/2 2 50-WATT Fitted pair of 12" 30 watt high flux speakers. Imp. 8-15 ohms. Car. £1-50. Terms: Dep. £5-11 and 8 monthly pmts. of £5-11. Total £45-99.

L12/50 12" 50 WATT 13,000 lines 15 ohms. Terms: Dep. £3-95 and 8 monthly pmts. £3-37 (Total £30-91) Carr. 55p.

£39-95

£25.95

PHANTOM 50

Rating 50 watts. 3 inputs, 2 vol. controls. Bass, Treble, Presence

Dep. £7-95 & 8 mthly. pmts. £7-48 (Total £67-79). Carr. £1-50

£59-95

JINGLE MACHINES I.S.E. CA127 £79-95

DEPOSIT £9 and 18 fortnightly payments £4-61. Total £91-98

FAL PHASE 50-4 AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protection against serious o/p overloading. G/p for spkrs. 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. O/p 50w Music. Deposit £3-60 & 8 mthly. payments. £5-75. Total £48-60. Carr. Free.

£48-60

REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P rating. Not for Bass Guitar.

★ Two Fane heavy duty high flux 12in. spkrs. ★ Four Jack Inputs and Two Volume Controls for instant use of up to four pick-ups or 'mikes'. Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £9-95 & 18 fortnightly payments of £4-15 (Total £48-85). Carr. £2-50

£74-95

REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-00 & 18 fortnightly payments £4-61. (Total £41-98). Carr. £2-50 **£79-95** FAL DISCO PRE-AMPLIFIER Table mixing inputs. Headphone Monitoring, Mic, Jack & Tape inputs. Independent Vol. Control. Std. 200-250v. A.C. Mains operation **£18-50**

LIQUID WHEEL from PROJECTORS £24-75

'SOUND TO LIFE' SYSTEM PULSAR special price £99-95

complete kit Dep. £11-48 and 18 fortnightly pmts. £5-74. (Total £114-80). Super SL Unit. 1000 watt per channel. Manual override buttons, 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd. and 10 yd. leads, fitted plugs. Units sold sep.

FAL SOUND-TO-LIFE UNIT £21-60

3-WAY SPOT BANK Excluding Bulbs Each £16-20

COMPLETE SYSTEM Incl. 2 Spotbanks and bulbs. Carr. £1-50 £55

NEW BRANCHES AT BOLTON, DONCASTER, and PRESTON

RSC

HI-FI CENTRES LTD.

EDINBURGH 101 Lothian Rd. (Closed Wed.) Tel. 229 9501

GLASGOW 326 Argyle St. (Cl'd Tues.) Tel. 248 4158

HULL 7 Whitefriargate (Closed Thurs.) Tel. 20505

LEICESTER 32 High Street (Closed Thurs.) Tel. 56420

LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.) Tel. 458252

LIVERPOOL 73 Dale St. (Closed Wed.) Tel. 236 3573

LONDON 238 Edgware Road, W.2. (Closed Thurs.) Tel. 723 1629

MANCHESTER 60A Oldham Street (Closed Wed.) Tel. 236 2778

MIDDLEBROUGH 106 Newport Road (Closed Wed.) Tel. 47096

NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.) Tel. 21469

NOTTINGHAM 19/19A Market Street (Closed Thurs.) Tel. 46088

PRESTON 41 Friargate Walk, St. Georges Shoppg Prec. Tel. 51979

SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.) Tel. 20716

STOCKPORT 8 Little Underbank (Closed Thurs.) Tel. 480-0777

SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 70573

MAIL ORDERS & EXPORT ENQUIRIES TO— AUDIO HOUSE, HENCONNER LANE, LEEDS. 18. Tel: Pudsey (08735) 7781.

MAIL ORDERS MUST NOT BE SENT TO SHOPS TERMS C.W.O. or O.O.D. No O.O.D. under £1. POSTAGE 40p PER ORDER OR AS QUOTED. TRADE SUPPLIED S.A.E. REQUIRED FOR LEAFLETS OR WITH ENQUIRIES.

Barclaycard and Access accepted

All items subject to availability. Prices correct at 19.8.75 E. & O.E.

OPEN ALL DAY SATURDAYS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.) Tel. 25349

BOLTON 23 Deansgate. (Closed Wed.) Tel. 33512

BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)

COVENTRY 17 Shelton Square, The Precinct. Tel. 25983

DERBY 97 St. Peter's Street. (Closed Wed.) Tel. 41361

DARLINGTON 19 Northgate (Closed Wed.) Tel. 68043

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.) Tel. 63069

ELECTROLYTIC CAPACITOR OFFER

10000/63 £1.88	2200 6.3 20p	220/63 18p
5000/50 £1.58	1000 180 63p	160/25 8p
5000/70 75p	1000 30 25p	100/12 7p
5000/50 75p	1000 25 25p	8/450 16p
5000/35 50p	470 63 23p	16/450 25p
5000/12 25p	470 35 16p	50/450 30p
3000/25 30p	330 100 30p	32+32/450 38p
2500/70 63p	250 64 20p	50 50 8p

DIGITAL I.C.s

Large range of 7400 series in stock. Prices from 18p.

INTEGRATED AUDIO POWER AMPS

20W RMS, 1 off £6.38, Stereo pair £11.95.
30W RMS 1 off £7.95, Stereo pair £14.80.
50W RMS 1 off £12.38 Stereo pair £22.76.

The 30 and 50W types have internal electronic protection and all types may be used on either single rail or + and - power supplies. Freq. resp. 20Hz-100kHz (all types). THD 0.5% at full power (all types). O P load 8 ohms.

50W RMS (4Ω) amp. kits complete with building and application details. Suitable for instruments, disco, hi-fi, etc. £8.95.

ZN414 IC Radio, £1.20

741 56p.
IC sockets DIL, all 26p.
Complete range of components held in stock.
Resistors C.F. 0.5W and 0.25W all 2p.
Metal Oxide 0.5W, 5p.
MYLAR Caps.

1nF, 2nF, 5nF, 6p; 10nF, 20nF, 30nF, 40nF, 47nF, 8p; 0.1μF, 0.2μF, 12p.

C280. Polyester 250V
10nF, 22nF, 4p; 33nF, 47nF, 4p; 68nF, 5p; 0.1μF, 0.15μF, 5p;

0.22μF, 6p; 0.33μF, 9p; 0.47μF, 10p; 0.68μF, 14p; 1.0μF, 17p; 1.5μF, 25p; 2.2μF, 28p.

1N4002 6p CRS1/40 89p
1N4003 6p CRS3/40 £1.08
1N4004 7p CRS7/40 £1.38
1N4005 8p CRS1/60 £1.25
1N4006 8p CRS7/60 £1.80
1N4007 9p 40669 £1.18

1N4148 5p Zener Diodes
OA90 8p 400mW 16p
OA91 8p 1 watt 19p

SEMICONDUCTORS

AC141 57p	BC167 14p	BD124 97p	MJ3001 £2.80	2N3053 26p
AC142 42p	BC168 14p	BD131 52p	MJ4200 £5.88	2N3054 66p
AD161 62p	BC169 15p	BD132 64p	MJE2955 £1.48	2N3055 59p
AD162 62p	BC182 13p	BD135 56p	MJE3055 75p	2N3702-2N3711 14p
BC107 13p	BC212 16p	BD136 63p		
BC108 12p	BC301 32p	BFY50 23p	TIP29A 69p	
BC109 16p	BC302 56p	BFY51 22p	TIP30A 96p	40361 55p
BC147 14p	BC303 37p	BFY52 24p	TIP31A 87p	40362 69p
BC148 12p	BCY70 18p	MJ481 £1.36	TIP32A 99p	40406 55p
BC149 14p	BCY71 50p	MJ491 £1.52	TIP41A 72p	40407 40p
BC157 14p	BCY72 16p	MJ2500 £2.75	TIP42A £1.27	40408 63p
BC158 12p	BD115 67p	MJ2501 £2.85	TIP2955 £1.38	40409-40410 85p
BC159 12p	BD121 £1.48	MJ3000 £2.68	TIP3055 75p	

"ALL PRICES INCLUDE VAT"

P. & P. 25p on all orders. Hundreds of other types of semiconductors held in stock. S.A.E. with all inquiries.

E B A

(Elliott Blunt Audio Ltd.)

40 YORK STREET, TWICKENHAM, MIDDX.

Tel. 01-891 1692

Opening hours 9.30 a.m. to 6 p.m. Monday—Saturday

VALVE BARGAINS

Any 5 64p, 10 99p, 50 £4.
Your choice from the following list: ECH84, ECC82, ECL80, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14.

Colour Valves 25p each
PL508 PL509, PY500/A

Press 4 Button Transistor UHF Tuners £2.50

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11—For Stereo and Standard VHF Radio Television, please state BBCI and ITV Channels.

B45—For mon. or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit.

Price £3.90 each

BARGAIN PACKS

All Components in the Bargain Packs are unused and marked.

Pack 1—Polyester (C280) Axial Leads Capacitors—250V/W & 400V/W, very good mixed selection from 0.01 UF to 2.2 UF. Price 100 £1.25, 1000 £10.00 (our choice).

Pack 2—50 AC128 untested but marked Transistors. Price 50 £1.50.


Pack 3—Plugs Plastic Insulated Type. (Prices in brackets for ten).

**Co-Ax Plug—8p (70p).
Jack Plugs—Standard 17p (£1.50), 2.5mm 10p (85p), 3.5mm 10p (85p).**

Din Plugs—2 Pin 12p (£1.00), 3 Pin 14p (£1.20), 5 Pin 18p (£1.50).

Prices include V.A.T. P. & P. under £1/10p, £1 to £3/15p, above £3/20p. Overseas at cost. Money back guarantee on all orders.

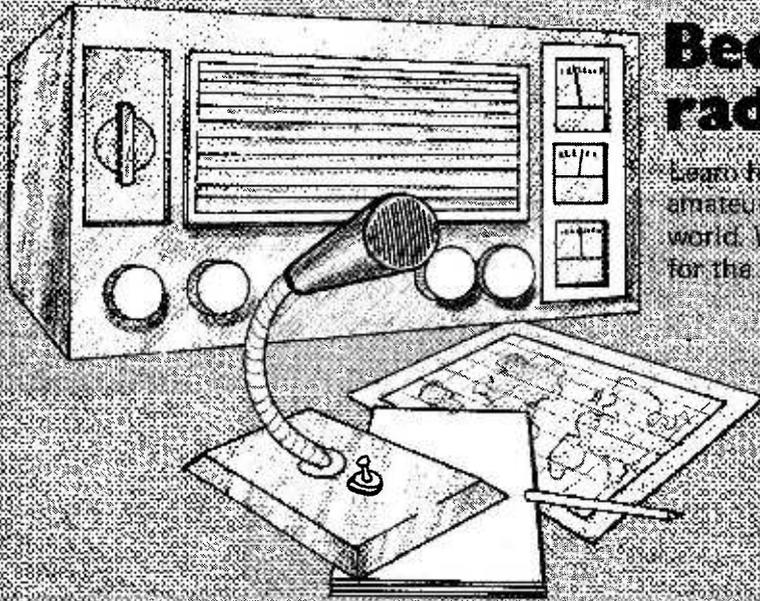ELECTRONIC MAILORDER LTD., 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCS. Tel. Rams. 3036.



Become a radio amateur.

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure, without obligation to:

**To: BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. W.C: 105
P.O. Box 156, Jersey, Channel Islands.**

NAME _____

ADDRESS _____

Block caps please


Free!

Crescent Quality Components

TWO-WAY STEREO ADAPTOR. Stereo Jack Plug to Two Free Sockets. For connecting two stereo inputs into one. A Bargain at 80p + VAT 25%.

BARGAIN PROJECT BOX

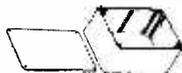A plastic box with moulded extrusion rails for PC or Chassis Panels with metal front plate fitted with four screws (all supplied). An ideal box to give a small project a professional finish. SIZE (Internal) 81mm x 51mm x 28mm. OUR PRICE 40p. +8%



JB11D STEREO JUNCTION BOX

The most popular stereo junction box. Facility for two pairs of headphones and two speakers. 3 position switch selects headphones, loudspeakers or both. A bargain at £2.50 +25%



LIGHT EMITTING DIODES -8%

	RED	GREEN	YELLOW	AMBER
0.2 inch	17p	27p	29p	27p
0.16 inch	24p	29p	30p	29p
0.125 inch	15p	25p	30p	25p

For orders of 10 and more LEDs 10% discount. (All LEDs supplied with free plastic mounting clip).

LOW COST SEVEN SEGMENT DISPLAYS -8 INCH +8%

Model	Color	Com. Anode	Left Dec.	Right Dec.	Price
CR72R	Red	Com. Anode	Left Dec.		£1.35
CR52G	Green	Com. Anode	Left Dec.		£1.35
CR82Y	Yellow	Com. Anode	Left Dec.		£1.35
CR74R	Red	Com. Cathode	Right Dec.		£1.35
CR54G	Green	Com. Cathode	Right Dec.		£1.35
CR84Y	Yellow	Com. Cathode	Right Dec.		£1.35

For full information on low cost displays please send 15p.

Clock Chip +8%
 CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet £4.95
 Circuits and Information Sheet 15p
 Lit 704 Led Display for above £1.10
 Or 4 for £4.20

WAFER SWITCHES

- 1 Pole 12 Way
 - 2 Pole 2 Way
 - 2 Pole 3 Way
 - 2 Pole 4 Way
 - 2 Pole 6 Way
 - 3 Pole 4 Way
 - 4 Pole 3 Way
- 25p each +8%



POTENTIOMETERS

All types 1" and less diameter

Single	Dual	Price
5K Log or	5K	
10K Lin Less	10K	
20K Switch	20K	Less
60K 17p each	60K	Switch
100K	100K	53p each
250K Double	250K	+25%
500K Pole	500K	
1M Switch	1M	
2M 87p each	2M	

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed one pound poly packs. Our Price 50p + P/P + VAT @25% per lb.

MAINS TRANSFORMERS

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high

Fixing centres: 25/32"

TR1	20-0-20v 100 m/a	
TR2	12-0-12 v 100 m/a	All
TR3	9-0-9 v 100 m/a	240 Volt
TR4	6-0-6 v 100 m/a	Primary
TR5	3-0-3 v 100 m/a	

Our Price £1.23 each +8%

MONO/STEREO MICROPHONE MIXER
 9 volt. High impedance input. Gold finish with four black plastic chrome tipped level control knobs. On/Off switch and stereo/mono switch. 4 Input sockets.

SPECIFICATIONS:-
 Input Imp = For X.TAL Mics etc.
 Gain = Approx 3.D.B.
 Max Input Sig = 1 volt
 Max Output Sig. = 1.3 volt
 Noise Ratio = -60DB
 Supply = 9 volt
OUR PRICE = £5.25p +25%

POWER SUPPLY UNITS

PP1 switched 3, 4, 6, 7, 9 and 12 volts at 500 m/a, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm. ONLY £4.00.
 PP2 Switched 6-7-9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders £3.25
 PP3 Car converter. From 12v Pos. or Neg. to = 6-7-9 volt. Easy to fit and transistor regulated £3.00 +8%



NEW VEROBOARD PRICES

Size	Price	Plain Price
3/4" x 3 1/2"	25p	15p
2 1/2" x 4 1/2"	41p	20p
3 1/2" x 8 1/2"	41p	20p
3 1/2" x 6"	40p	20p
1 1/2" x 3 1/2"	1.24p	89p
1 1/2" x 5 1/2"	1.86p	87p
1 7/8" x 5"	E.15p	1.37p

Pin insertion tool Spot face cutter Pkt 36 pins (state -1 or -15)

LOUDSPEAKERS +25%

- 2 1/2" 8 ohm 50p
- 2 1/2" 40 ohm 50p
- 2 1/2" 80 ohm 50p
- 5" 8 ohm ceramic £1.25
- 6 1/2" 8 ohm dual cone ceramic £2.50
- 10" 8 ohm dual cone ceramic £3.75
- 8" x 5" 8 ohm Permat's Magnet £1.60
- 3-8-15 ohm
- *EMI 13" x 8" 350 Kit 8 ohm £7.50 + 50p Carr.



10 inch DUAL CONE L/S Manufactured by "ELAC" to a very high standard these loudspeakers are a real bargain SPEC:- Size=10" Dual Cone. Power=10 Watts Frequency=40-12000Hz +25% Our Price = £3.75p each

MAINS KEYNECTOR

Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage demonstrations, etc. Multi connections can be made (max. load 13A fused). £3.25p. +8%



ALUMINIUM BOXES +8%

Metal project boxes give your work a professional finish

Model	L	W	H	Price
AB7	3 1/2"	4 1/2"	1 1/2"	54p
AB8	4"	5 1/2"	1 1/2"	48p
AB9	4"	6 1/2"	1 1/2"	34p
AB10	4"	7 1/2"	1 1/2"	69p
AB11	4"	8 1/2"	1 1/2"	54p
AB12	5"	5 1/2"	1 1/2"	45p
AB13	5"	6 1/2"	1 1/2"	69p
AB14	5"	7 1/2"	1 1/2"	54p
AB15	5"	8 1/2"	1 1/2"	69p
AB16	10"	7 1/2"	3"	£1.23
AB17	10"	8 1/2"	3"	£1.08
AB18	12"	8 1/2"	3"	£1.23
AB19	12"	9 1/2"	3"	£1.50

ABS PLASTIC BOXES -8%

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

- 1005 = 105mm x 73mm x 45mm = 65p
- 1006 = 150mm x 75mm x 47mm = 72p
- 1007 = 184mm x 124mm x 60mm = £1.28
- 1021 = 106mm x 74mm x 45mm (sloping front) = 55p

TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket. Fully extended = 43" Fully closed = 7" Our Price 50p + P/P + VAT @ 25%

CLEAR PLASTIC PANEL METERS
 Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.

- ME6 = 0 to 50 micro amp Full Scale
- ME7 = 0 to 100 micro amp Full Scale
- ME8 = 0 to 500 micro amp Full Scale
- ME9 = 0 to 1 m/a Full Scale
- ME10 = 0 to 5 m/a Full Scale
- ME11 = 0 to 10 m/a Full Scale
- ME12 = 0 to 50 m/a Full Scale
- ME13 = 0 to 100 m/a Full Scale
- ME14 = 0 to 500 m/a Full Scale
- ME15 = 0 to 1 amp Full Scale
- ME16 = 0 to 50 volts
- ME17 = 0 to 300 volts A.C. Full Scale
- ME18 = "S" Meter
- ME19 = "VU" Meter



OUR PRICE £3.00 +8%

WIRE WOUND VOLUME CONTROL
 250ohm Only 25p EACH. Approx. 1" Diameter. Long standard spindle. +8%

MINIATURE RELAYS

Brand new range of British made Relays. Size 1 1/2" x 1" x 3/4". All two changeovers with 250v 1.5A contacts and suitable for fitting on .1m Veroboard. Type Volts Cur- Ohms

- 27/A 12v 17M/A 700
 - 21/A 12v 28M/A 430
 - 12/A 6v 33M/A 185
- All £1.30 each +8%

DECON DALO SSPC ETCH RESIST PEN

The Decon Dalco SSPC is a unique instrument for the professional and amateur electronics engineer, enabling him to prepare in minutes a perfect printed circuit board

OUR PRICE 80p +8%

CABLE LESS SOLDERING IRON

- * Completely Portable
 - * Heats in 5 seconds
 - * Solders up to 150 joints or more per charge
 - * Recharges automatically in its own stand
 - * No AC leakage or induced current to damage delicate components
 - * Heats to 700 deg. F
 - * Fine Tip for delicate and general purpose soldering
 - * Only 8" long and weighs just 6 ozs.
- OUR PRICE £9.75 +8% (spare bits are available)

STOP PRESS +25%

- BHA0002 15 watt Amp Module £3.50
- NE555 Timer I.C. 75p
- MCI310P Stereo Decoder I.C. £1.40
- 7805 Regulator 55p
- TIP 29A TIP 30A 65p
- BC107 10p
- BC108 10p
- BC109 10p

I.C. SOCKETS +8%

- D.I.L.
- 8 pin = 13p
- 14 pin = 14p
- 16 pin = 14p
- 24 pin = 24p
- 28 pin = 28p
- 36 pin = 36p

BARGAIN TRANSFORMERS

12.0-12 volt 500m/a
 240 volt primary transformer bargain. approx size = 60mm x 40mm x 50mm fixing centres=75mm
 Our Price =£1.20 +8%

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design
 Contents = Plastic etching dish.
 Sample copper clad board.
 Laminate Cutter.
 1 lb Ferric Chloride.
 Large Plastic Spoon.
 Etch Resist Pen.
 Full Etching Instructions.
 Complete and Big Kit Value at £3.75p +8%

LOW PRICE LOW PRICE CASSETTES +8%

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
 C60 = 31p C90 = 45p C120 = 53p
 10% Discount on ten or more cassettes of one type

U.K. POSTAGE 20p UNLESS OTHERWISE STATED

VAT-All prices are excluding VAT. Please add to each item the VAT rate indicated.

CRESCENT RADIO LTD. P.W.

All mail to No. 1 ST. MICHAELS TERRACE WOOD GREEN, LONDON N22 4SJ. Phone: 01-888 3206

Callers Welcome at 15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct You should own one.

CRESCENT CATALOGUE
 Price 30p.


12 inch MODELS

Guaranteed
for 5 years

T12/35 Rated Power 35 WATTS

Centre Pole Diam. 1½" Imp. 8-15 Ω
Twin Cone. Range: 50-17000Hz
Ceramic Magnet
Weight: 600 Gms

Rec. Price **£13·00**

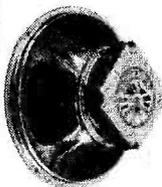

T12/60 Rated Power 60 WATTS

Centre Pole Diam. 2" Imp. 8-15 Ω
Range: 60-9000Hz
Ceramic Magnet
Weight 1150 Gms.

Rec. Price **£20·00**



T12/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp 8-15 Ω
Range: 40-5000Hz
Ceramic Magnet
Weight: 1250 Gms

Rec. Price **£35·00**



Power Ratings
R.M.S.
Continuous

All
Rec.
Prices
inc. VAT


15 inch MODELS

Guaranteed
for 5 years

T15/70 Rated Power 70 WATTS

Centre Pole Diam. 2" Imp 8-15 Ω
Ceramic Magnet
Weight: 1150 Gms
Range: 50-4000Hz



Rec. Price **£27·00**

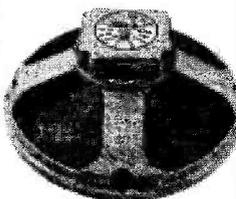

T15/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp. 8-15 Ω
Ceramic Magnet
Weight: 1250 Gms.
Range: 50-4000Hz

Rec. Price **£38·50**

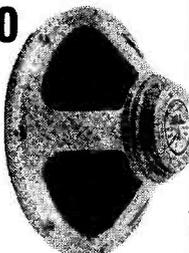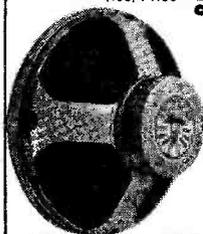

18 inch MODEL

T18/100 Rated Power 100 WATTS


Centre Pole Diam. 3" Imp. 8-15 Ω
Ceramic Magnet
Weight: 1250 Gms.
Range: 35-4000Hz

Rec. Price **£42·50**

Manufacturers, Wholesale, Retail and
Export enquiries to sole Distributors:-

AUDIO EQUIPMENT LTD.
102 Hencorner Lane, Leeds 13

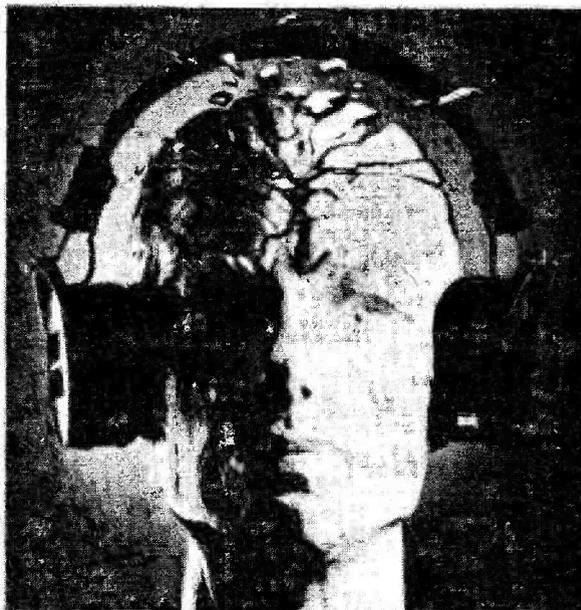S.A.E. please for
trade terms or leaflet
Prices correct at Aug. 6, 1975



AUDIO FAIR '75

The truest sounds you'll ever hear

Choose the right hi-fi and you're constantly rewarded. Choose the wrong hi-fi and you live with a costly mistake.

Audio '75 helps you arrive at the right buying decision, by bringing together under one roof, the finest equipment for you to see, hear and compare.

Audio Fair '75 lets you become acquainted with new products, new ideas and new refinements in your price range.

Don't miss Audio Fair '75 - it could save you a lot of money and anxiety.

Sponsored by **THE OBSERVER**

THE 1975 INTERNATIONAL AUDIO FESTIVAL & FAIR.

OLYMPIA LONDON: 20th-26th OCTOBER.

Admission 75p (live-theatre show FREE)

LASKYS FOR CHOICE

SEW PANEL METERS

STOCKED AT
481 Oxford Street 311 Edgware Road
42 Tottenham Court Rd. 3 Lisle Street
branches or by mail order.

USED EXTENSIVELY BY
INDUSTRY, GOVERNMENT
DEPARTMENTS, EDUCATIONAL
AUTHORITIES ETC.

Over 200 ranges in stocked—other ranges to
order. Quantity discounts available. Send
for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£4.20	10V DC	£4.05
100uA	£4.15	20V DC	£4.05
200uA	£4.10	50V DC	£4.05
500uA	£4.05	300V DC	£4.05
50-0-50uA	£4.15	15V AC	£4.15
100-0-100uA	£4.10	30V AC	£4.15
1mA	£4.05	VU Meter	£4.95
5mA	£4.05		
10mA	£4.05		
50mA	£4.05		
100mA	£4.05		
500mA	£4.05		
1A DC	£4.05		
5A DC	£4.05		
10A DC	£4.05		
5V DC	£4.05		



CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm


50uA	£5.05	150V AC	£4.90
100uA	£4.95	300V AC	£4.90
500uA	£4.75	VU Meter	£6.25
50-0-50uA	£4.95		
100-0-100uA	£4.90		
1mA	£4.75		
1A DC	£4.75		
5A DC	£4.75		
20V DC	£4.75		
50V DC	£4.75		
300V DC	£4.75		



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

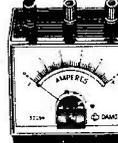A range of high quality
moving coil instruments
ideal for school experi-
ments and other bench
applications. 3" mirror
scale. The meter move-
ment is easily accessible
to demonstrate internal
working.



50uA	£9.35	20V DC	£8.40
100uA	£8.70	50V DC	£8.40
50-0-50uA	£8.70	300V DC	£8.40
1mA	£8.40	800mA/5A DC	£9.50
1-0-1mA	£8.40	5V/50V DC	£9.50
1A DC	£8.40	5V/15V DC	£9.50
5A DC	£8.40	1A/15A DC	£9.50
10V DC	£8.40		
15V DC	£8.40		

CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.85	5V DC	£3.65
100uA	£3.80	10V DC	£3.65
200uA	£3.75	20V DC	£3.65
500uA	£3.70	50V DC	£3.65
50-0-50uA	£3.80	300V DC	£3.65
100-0-100uA	£3.75	15V AC	£3.80
1mA	£3.65	30V AC	£3.80
5mA	£3.65	VU Meter	£4.65
10mA	£3.65		
50mA	£3.65		
100mA	£3.65		
500mA	£3.65		
1A DC	£3.65		
5A DC	£3.65		
10A DC	£3.65		



*Items with asterisk are Moving Iron
type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4.75	10V DC	£4.50
100uA	£4.65	20V DC	£4.50
200uA	£4.60	50V DC	£4.50
500uA	£4.55	300V DC	£4.50
50-0-50uA	£4.65	15V AC	£4.60
100-0-100uA	£4.60	30V AC	£4.60
1mA	£4.50	VU Meter	£5.80
5mA	£4.60		
10mA	£4.60		
50mA	£4.50		
100mA	£4.50		
500mA	£4.50		
1A DC	£4.50		
5A DC	£4.50		
10A DC	£4.50		
5V DC	£4.50		



CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm


50uA	£3.55	15V AC	£3.40
100uA	£3.50	30V AC	£3.40
200uA	£3.45	5 Meter 1mA	£3.75
500uA	£3.40	VU Meter	£4.30
50-0-50uA	£3.50	1A DC	£3.25
100-0-100uA	£3.45	5A DC	£3.25
500-0-500uA	£3.25	10V DC	£3.25
1mA	£3.25	20V DC	£3.25
5mA	£3.25	50V DC	£3.25
10mA	£3.25	300V DC	£3.25
50mA	£3.25		
100mA	£3.25		
500mA	£3.25		
1A DC	£3.25		
5A DC	£3.25		
10V DC	£3.25		
20V DC	£3.25		
50V DC	£3.25		
300V DC	£3.25		



CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.45	10V DC	£3.05
100uA	£3.40	15V DC	£3.05
200uA	£3.30	20V DC	£3.05
500uA	£3.25	50V DC	£3.05
50-0-50uA	£3.40	100V DC	£3.05
100-0-100uA	£3.30	150V DC	£3.10
500-0-500uA	£3.05	300V DC	£3.10
1mA	£3.05	500V DC	£3.15
1-0-1mA	£3.05	750V DC	£3.15
5mA	£3.05	15V AC	£3.15
10mA	£3.05	20V AC	£3.15
20mA	£3.05	50V AC	£3.15
50mA	£3.05	150V AC	£3.15
100mA	£3.05	300V AC	£3.15
150mA	£3.05	500V AC	£3.30
200mA	£3.05	5 Meter 1mA	£3.50
300mA	£3.05	VU Meter	£4.10
500mA	£3.05		
750mA	£3.05		
1A DC	£3.05		
2A DC	£3.05		
10A DC	£3.05		
3V DC	£3.05		

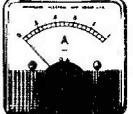

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm


50uA	£6.00	50V DC	£5.75
100uA	£5.95	150V DC	£5.75
200uA	£5.90	300V DC	£5.75
500uA	£5.80	15V AC	£5.85
50-0-50uA	£5.95	30V AC	£5.85
100-0-100uA	£5.90	5 Meter 1mA	£6.85
500-0-500uA	£5.65	VU Meter	£7.10
1mA	£5.75	1A AC	£5.75
1-0-1mA	£5.75	5A AC	£5.75
5mA	£5.75	10A AC	£5.75
10mA	£5.75	20A AC	£5.75
50mA	£5.75	30A AC	£5.75
100mA	£5.75		
500mA	£5.75		
1A DC	£5.75		
5A DC	£5.75		
15A DC	£5.75		
30A DC	£5.95		
10V DC	£5.75		
20V DC	£5.75		



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.55	5V DC	£4.45
100uA	£4.50	10V DC	£4.45
200uA	£4.45	20V DC	£4.45
500uA	£4.30	50V DC	£4.45
50-0-50uA	£4.50	15V AC	£4.45
100-0-100uA	£4.45	30V AC	£4.45
1mA	£4.25	VU Meter	£5.50
5mA	£4.25		
10V DC	£4.25		
30V DC	£4.35		
VU Meter	£5.50		

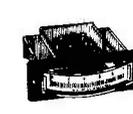


POSTAGE / PACKING & INSURANCE 15p

BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm


50uA	£4.95	10V DC	£4.95
100uA	£4.90	20V DC	£4.90
500uA	£4.60	50V DC	£4.90
50-0-50uA	£4.80	300V DC	£4.90
100-0-100uA	£4.85	15V AC	£4.95
1mA	£4.60	30V AC	£4.95
1A DC	£4.60	VU Meter	£5.95
5A DC	£4.60		
20V DC	£4.80		
50V DC	£4.80		
300V DC	£4.60		
300V AC	£4.75		
VU Meter	£5.95		

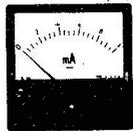

CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£4.10	5 Meter 1mA	£4.20
100uA	£3.85	VU Meter	£4.85
500uA	£3.70	1A AC	£3.65
50-0-50uA	£3.85	5A AC	£3.65
100-0-100uA	£3.70	10V DC	£3.65
1mA	£3.65	20V DC	£3.65
5mA	£3.65	50V DC	£3.65
10mA	£3.65	300V DC	£3.65
50mA	£3.65	15V AC	£3.65
100mA	£3.65	30V AC	£3.65
1A DC	£3.65		
5A DC	£3.65		
10V DC	£3.65		
20V DC	£3.65		
50V DC	£3.65		
300V DC	£3.65		
15V AC	£3.65		
30V AC	£3.75		

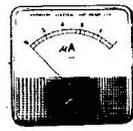

BAKELITE MODEL MR 65 Size: 80 x 80mm


25uA	£5.80	30V DC	£3.95
50uA	£4.40	30V AC	£3.95
100uA	£4.35	50V AC	£3.95
500uA	£4.05	1A AC	£3.95
50-0-50uA	£4.35	5A AC	£3.95
100-0-100uA	£4.30	10A AC	£3.95
500-0-500uA	£3.95	20A AC	£3.95
1mA	£3.95	30A AC	£3.95
1-0-1mA	£3.95	50A AC	£3.95
5mA	£3.95	100V DC	£3.95
10mA	£3.95	15V DC	£3.95
50mA	£3.95	20V DC	£3.95
1A DC	£3.95	50V DC	£3.95
2A DC	£3.95	100V DC	£3.95
5A DC	£3.95	15V DC	£3.95
10A DC	£3.95	30V DC	£3.95
15A DC	£3.95	50V DC	£3.95
30A DC	£3.95	100V DC	£3.95
50A DC	£4.20	150V DC	£3.95
5V DC	£3.95		
10V DC	£3.95		
15V DC	£3.95		
30V DC	£3.95		
50V DC	£3.95		
100V DC	£3.95		



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£4.35	300V DC	£4.10
100uA	£4.25	1A AC	£4.10
200uA	£4.20	5A AC	£4.10
500uA	£4.15	10A AC	£4.10
50-0-50uA	£4.25	20A AC	£4.10
100-0-100uA	£4.20	30A AC	£4.10
500-0-500uA	£4.10	50A AC	£4.10
1mA	£4.10	100A AC	£4.10
1-0-1mA	£4.10	200A AC	£4.10
5mA	£4.10	300V DC	£4.10
10mA	£4.10	15V DC	£4.10
50mA	£4.10	20V DC	£4.10
100mA	£4.10	50V AC	£4.10
500mA	£4.10	150V AC	£4.10
1A DC	£4.10	15V DC	£4.10
5A DC	£4.10	20V DC	£4.10
10A DC	£4.10	50V DC	£4.10
15A DC	£4.10	150V DC	£4.10
20A DC	£4.20		
30A DC	£4.25		
50A DC	£4.10		
5V DC	£4.10		
10V DC	£4.10		
15V DC	£4.10		
20V DC	£4.10		
50V DC	£4.10		
150V DC	£4.10		


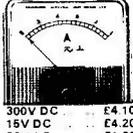


BATTERY/LEVEL PANEL INDICATOR

18mm
18mm Panel
mounting.

OUR
PRICE
95p P/P

& Ins 15p Discounts for quantity.

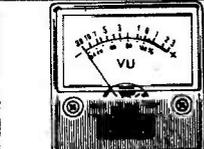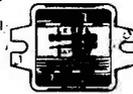

VU METER TYPE 3
250uA Size: 33mm x 20mm.
£1.55 P/P & Ins 15p

REDUCED TO CLEAR

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input:
230V 50/60Hz. Output 0-260V

MODEL S260 BENCH MOUNTING

P/P & Ins

1A	£7.30-£1.50
2.5A	£10.25-£1.50
5A	£12.95-£1.50
8A	

IT MAKES SENSE TO

HIOKI 730X
30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 60µA/30mA/300mA. 2K/200K/2 Meg Ohm. -10 to +63dB.
OUR PRICE £8.10 P/P & Ins 30p



U4312 MULTIMETER
extremely sturdy instrument for general electrical use. 667 opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0.7/300µA/1.5/6/15/150/60/600mA/1/1.5/6A DC. 0.1/1/5/15/60/150/300/600mA. 1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1% AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.
OUR PRICE £11.60 P/P & Ins 60p



MODEL AS.100D VOM
1000.00v opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10µA/6/60/300mA/12 Amp. 0/2k/200k/2M/200 Meg Ohm. -20 to -17dB.
OUR PRICE £18.90 P/P & Ins 60p



KAMODEN HM720B FET VOM
Input impedance 15 Megohms. Ranges:- 0/25/1/2.5/10/50/100V DC. 0/2.5/10/50/250/500V AC. 0/25µA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms.
OUR PRICE £24.30 P/P & Ins 60p



LB4 TRANSISTOR TESTER
Tests PNP or NPN transistors. Audio indicator. Operates on two 1.5V batteries. Complete with instructions etc.
OUR PRICE £4.85 P/P & Ins 20p



U4323 MULTIMETER
20,000opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.06/0.5/5/50/500µA/5mA/50mA/100mA/1.0. x 10, x 100, x 1,000, x 10,000 (50k, 800k, 5kΩ, 50kΩ centre scale). Battery operated. Size: 180 x 97 x 40mm. Supplied in carrying case complete with test leads.
OUR PRICE £8.60 P/P & Ins 60p



HIOKI 750X VOLT-OHM-MILLIAMETER
43 ranges: 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1200V DC. 0/0.3/0.6/1.5/3/6/12/30/60/150/300/600/1200V AC. Current: 0-30/60µA/1.5/3/15/30/150/300mA. Resistances: 0-3/300k/30Mhms. Decibels: -10 to +17dB. Output: -0-3/6/15/30/60/120/300V. Accuracy: 3% DC, ±4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.
OUR PRICE £12.90 P/P & Ins 60p



KAMODEN 360 MULTIMETER
High sensitivity to DC 100kohm/V AC 10kohm/V 5" mirror scale, overload protected. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 5/10/50/250/500V AC. AC Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100M ohms. DC current: 10/250µA/2.5/25/250 mA/10A. AC current: -0-10A. -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc.
OUR PRICE £18.90 P/P & Ins 60p



SWR METER Model SWR3
Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52Ω Indicator 100µA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.
OUR PRICE £4.55 P/P & Ins 60p



MODEL TE15 GRID DIP METER
Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz - 280MHz in six coils. 500µA meter. 9V battery operation. Size: 180 x 80 x 100mm.
OUR PRICE £18.90 Ins 30p



TMK 200 MULTIMETER KIT
Build yourself a quality 20000 opv multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test prods and instructions. Ranges: 0/0.6/3/30/120/600/1200V DC. 0/6/30/120/600/1200V AC. Current: 0/0.6/6/60/600mA. Resistance: 0/10/100K/1/10 Meg ohms. Decibels: -20 to +63dB. Size: 90 x 150 x 35mm
OUR PRICE £9.65 P/P & Ins 30p



TMK MODEL TW50K
46 ranges, mirror scale. 50k/V DC 50k/V AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts 1.5/3/5/10/25/50/125/250/500/1000. DC current 25/50µA/2.5/5/25/50/250/500mA/5/10A. Resistance: 10/100k/1 Meg/10 Meg ohms. -20 to +81.5dB.
OUR PRICE £13.50 P/P & Ins 60p



Model HT100B4 MULTIMETER
Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/50/250/1000 Volts AC. DC resistance 0-20/200k/2/20 Meg. ohms. DC current: 10/250µA/2.5/25/250 mA/10A. AC current: -0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.
OUR PRICE £21.50 P/P & Ins 60p



U4341 Multimeter & Transistor Tester
27 ranges. 16,700opv. Overload protected. Ranges: 0.5/2.5/10/50/30/60/150/300/600V DC. 1.5/7.5/30/150/300/750V AC. Resistance: 0.06/0.6/6/60/600mA AC. 0.3/3/30/300mA AC. Resistance: 0.06/0.5/2/20/200k ohms/2 Mhms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.
OUR PRICE £11.85 P/P & Ins 60p



SINCLAIR DM2 DIGITAL MULTIMETER
Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply.
DC VOLTS: 1v, 10, 100v, 1000v. AC VOLTS: 1v, 10v, 100v, 1000v. DC CURRENT: 1mA, 10mA, 100mA, 1000mA. AC CURRENT: 1mA, 10mA, 100mA, 1000mA. RESISTANCE: 1k, 10k, 100k, 1000k.
OUR PRICE £63.70 P/P & Ins 50p



MODEL C7208FM
30,000 opv DC. 15,000 opv AC. 6/3/15/60/300/600/1200V DC. 6/30/120/600/1200V AC. DC Resistance x 1, x 10, x 100, x 1000 (50k centre scale). DC Current 30µA/3/30/600mA. -20 to +63dB.
OUR PRICE £9.65 P/P & Ins 30p



MODEL AF.105 VOM
50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V AC. 0/30µA/6/60/300 mA. 12 Amp. 0/10k/1m/10m/100 Meg Ohms. -20 to -17dB.
OUR PRICE £13.50 P/P & Ins 60p



370WTR MULTIMETER
Features AC current ranges. 20,000 opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50µA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.
OUR PRICE £21.50 P/P & Ins 60p



KAMODEN TT35 TRANSISTOR TESTER
High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.
OUR PRICE £18.90 P/P & Ins 60p



TRANSISTORISED L.C.R. AC BR/8 MEASURING BRIDGE
A new portable bridge offering excellent range and accuracy at low cost. Reistance: 6 ranges: 0.1 ohm-11.1 megohm ± 1% Inductance: 6 ranges: 1 microhenry-111 henries ± 2% Capacity: 6 ranges: 10p-1110 mfd ± 2% Turns Ratio: 6 ranges: 1:1/1000-1:11100 ± 1% Bridge Voltage at 1,000cps. Operated from 9 volt battery. 100 microamp meter indication. Size 73 x 5" x 2".
OUR PRICE £29.70 P/P & Ins 60p




U4324 MULTIMETER
High sensitivity. 20,000opv. Ranges: 0.5/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.05/0.6/6/60/600mA/3A DC. 3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mhms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.
OUR PRICE £10.60 P/P & Ins 60p



MODEL 500
30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50µA/5/50/500mA. 12A DC. 0/60k/6 meg/60 megohms.
OUR PRICE £15.05 P/P & Ins 60p



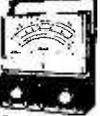MODEL C7080EN
Giant 6" mirror scale. 20,000 opv. 0/0.25/1/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500V AC. 0/2.5/10/50/250/1000/5000V DC. 0/2.5/10/50/250/1000/5000V AC. 0/50µA/1/10A/100/500mA/10A DC. 0/2k/200k/20 Meg. -20 to +50dB.
OUR PRICE £21.50 P/P & Ins 60p



S100TR MULTIMETER TRANSISTOR TESTER
100,000opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/12/600µA/12/300mA/6/12A DC. 0/10k/1 Meg/100 Meg. -20 to +50dB. 0.01-0.2MFD Transistor tester measures Alpha, Beta and Ico. Complete with instructions, batteries and leads.
OUR PRICE £22.65 P/P & Ins 60p



TE-200 RF SIGNAL GENERATOR
Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable RF attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.
OUR PRICE £24.30 P/P & Ins 60p



U91 Clamp VOLT AMMETER
For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.
OUR PRICE £15.10 P/P & Ins 60p



U4317 MULTIMETER
High sensitivity instrument for field and laboratory work. Knife edge pointer. 85mm. mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50µA/0.5/1.5/10/50/250mA/1.5A DC. 0.25/1.5/10/50/250mA/1.5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.
OUR PRICE £18.35 P/P & Ins 60p



KAMODEN 72.200 Multitester
High sensitivity tester. 200,000 opv Overload protected. Mirror scale. Ranges: -0/0.6/3/3/60/120/600/1200V DC. 0/3/12/60/300/1200V AC. 0/6/60/300mA/12A DC. 0/12A AC. -20 to +56dB. 0/2k/200k/2 Meg/200 Megohms.
OUR PRICE £24.30 P/P & Ins 60p



C15 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz V/RMS/mm: 0.1-25; HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz V/RMS/mm: 0.3-25 Preset triggered sweep 1-3000µsec. Free running 20-200 kHz in nine ranges. Calibrator pips. 220 x 350 x 430mm. 115-230V AC.
OUR PRICE £47.50 P/P & Ins £1.60



ALL PRICES INCLUDE VAT

AMERICAN RADIO a service that makes sense!

EXPORT Personal exports arranged for overseas visitors. Goods specifically packed, insured and despatched to all parts of the world at minimum cost exclusive of VAT. Payment by bank transfer, certified cheque, postal order or money order in any currency.

CUSTOMER SERVICES Our Customer Services Division at Head Office will answer all your enquiries - just ring 01-200 1321

BUY AT LASTKYS

ALL PRICES INCLUDE VAT

TE22 SINE SQUARE WAVE AUDIO GENERATOR
Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.
OUR PRICE £26.90 P/P & Ins £0p



HANIMEX HDC 1900 DIGITAL ALARM CLOCK
240V operation with large clear numbers, night light and 'snooze' switch. Attractively finished in white and silver.
OUR PRICE £8.10 P/P & Ins £1.00



T. T. C. SPRITE STEREO HEADPHONES
Feather weight (5oz). Dynamic stereo headphones providing high quality reproduction at a budget price. Soft removable ear pads and adjustable headband. Speaker size: 28mm. Impedance: 8 ohms. Frequency response: 30-13000 Hz.
OUR PRICE £2.40 P/P & Ins 30p



SAVE £9.35

ELIZABETHAN OCR26 DIGITAL CLOCK RADIO
A smaller than usual digital clock AM/FM radio, measuring only 8 1/2" x w 3 1/2" d x 4" h. The DCR is finished in simulated teak veneer and is fitted with a pre-set sleep timer switch that will turn on the radio at the precise time chosen (Mains operated) List Price £24.25
OUR PRICE £14.90 P/P & Ins. £1.35



HIGH QUALITY CONSTRUCTION KITS

ALL PRICES REDUCED TO CLEAR

LIMITED STOCKS AT Oxford Street. 42 & 17, Fleet Street.
311 Edgware Road. CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.

Post and Packing Ins. 15p per kit.

ARF 300 AF/RF SIGNAL GENERATOR
All transistorised compact fully portable. AF sine-wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/Sine wave 10V. P/P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.
OUR PRICE £40.50 P/P & Ins 60p



NEW GOLDRING G102 KIT
Belt-drive 2-speed turn table in kit form complete with pick up arm and head shell. P/P & Ins.
OUR PRICE £21.15 Ins £1.00



WALKIE TALKIES SKYFON NV7
Super low cost transmitter/receivers. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna.
OUR PRICE £43.60 per PAIR/P/P & Ins 50p
NOT LICENSABLE IN THE U.K.



SAVE £14.00

ELIZABETHAN 8/LZ-1
8-Track Stereo Player. Home 8-Track player with automatic and illuminated channel indicators for use with your hi fi system. Size 7 1/2" x 12" D x 2 1/2" h. List Price £28.90.
OUR PRICE £14.90 P/P & Ins. £1.35



AF20 Mono amplifier.....	£5.95
AF25 Mixer.....	£2.90
AF30 Mono pre-amplifier.....	£3.40
AF35 Emitter amplifier.....	£2.55
AF80 0.5W mic. amplifier.....	£5.10
AF305 Intercom.....	£8.45
AF310/2 Mono Amplifier.....	£7.95
M160 Multi-vibrator.....	£3.95
M1302 Transistor tester.....	£7.05
M191 VU Meter.....	£5.45
M192 Stereo balance meter.....	£7.10
LF380 Quadraphonic device.....	£11.45
AF75 Automatic light control.....	£7.55
AT50 Photo cell switch unit.....	£5.65
AT50 400W triac light dimmer/speed control.....	£24.35
AT56 2,200W triac light dimmer/speed control.....	£10.62
AT60 1 channel light control.....	£8.85
AT65 3 channel light control.....	£4.05
GU330 Tremolo unit.....	£3.40
HF61 Diode detector.....	£3.85
HF65 FM transmitter.....	£17.30
HF75 FM receiver.....	£22.95
HF310 FM tuner.....	£11.15
HF325 Deluxe FM tuner.....	£6.35
HF330 Decoder (HF310/325).....	£2.20
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£8.90
GP312 Circuit board.....	£2.25
GP304 Circuit board.....	£6.65
HF380 VU/vhf aerial amplifier.....	£8.25
HF395 broadband aerial amp.....	£8.80
NT110 Stabilised power supply 100mA, 9V.....	£6.60
NT300 Stabilised p. supply.....	£13.95
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2amps.....	£5.95
NT305 Voltage converter.....	£5.95
NT315 Power supply 240V AC 104.5/15V DC, 500mA.....	£12.75

MODEL TE20 RF SIGNAL GENERATOR
Six bands. 120kHz-250MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 190mm. Complete with test leads etc.
OUR PRICE £20.45 P/P & Ins 60p



SUPERB QUALITY LOW PRICES AUDIOTRONIC DIGITAL CLOCK RADIOS

ADC22
24-hour clock radio, covering MW/FM wavebands. 180-minute sleep timer. Choice of Grey or White cabinet. P/P & Ins.
OUR PRICE £17.50 Ins £1.00



SINCLAIR Project 80 Modules

Z40 Power Amp.....	£6.60	P/P & Ins. 15p
Z60 Power Amp.....	£8.95	P/P & Ins. 15p
Stereo 80 Pre-Amp.....	£13.10	P/P & Ins. 15p
Active Filter Unit.....	£7.40	P/P & Ins. 15p
FM Tuner.....	£13.10	P/P & Ins. 15p
Stereo Decoder.....	£8.40	P/P & Ins. 15p
P25 Power Supply.....	£4.65	P/P & Ins. 30p
P26 Power Supply.....	£6.40	P/P & Ins. 30p
P28 Power Supply.....	£7.90	P/P & Ins. 30p
Transformer for P28.....	£5.10	P/P & Ins. 30p

FREE

CATALOGUE

LASKYS 32 PAGE CATALOGUE AND PRICE LIST - absolutely free and available from all stores or by post (see coupon below). This exciting catalogue provides a comprehensive selection from the largest Hi-Fi Retailer in Europe - a MUST for every Hi-Fi and electronics specialist.

AF20 Mono amplifier.....	£5.95
AF25 Mixer.....	£2.90
AF30 Mono pre-amplifier.....	£3.40
AF35 Emitter amplifier.....	£2.55
AF80 0.5W mic. amplifier.....	£5.10
AF305 Intercom.....	£8.45
AF310/2 Mono Amplifier.....	£7.95
M160 Multi-vibrator.....	£3.95
M1302 Transistor tester.....	£7.05
M191 VU Meter.....	£5.45
M192 Stereo balance meter.....	£7.10
LF380 Quadraphonic device.....	£11.45
AF75 Automatic light control.....	£7.55
AT50 Photo cell switch unit.....	£5.65
AT50 400W triac light dimmer/speed control.....	£24.35
AT56 2,200W triac light dimmer/speed control.....	£10.62
AT60 1 channel light control.....	£8.85
AT65 3 channel light control.....	£4.05
GU330 Tremolo unit.....	£3.40
HF61 Diode detector.....	£3.85
HF65 FM transmitter.....	£17.30
HF75 FM receiver.....	£22.95
HF310 FM tuner.....	£11.15
HF325 Deluxe FM tuner.....	£6.35
HF330 Decoder (HF310/325).....	£2.20
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£8.90
GP312 Circuit board.....	£2.25
GP304 Circuit board.....	£6.65
HF380 VU/vhf aerial amplifier.....	£8.25
HF395 broadband aerial amp.....	£8.80
NT110 Stabilised power supply 100mA, 9V.....	£6.60
NT300 Stabilised p. supply.....	£13.95
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2amps.....	£5.95
NT305 Voltage converter.....	£5.95
NT315 Power supply 240V AC 104.5/15V DC, 500mA.....	£12.75

LASKYS make sense of Hi-Fi

ADC33 Deluxe
24-hour clock radio covering MW/FM wavebands. 180-minute sleep timer. Buzzer alarm. Tone control. P/P & Ins.
OUR PRICE £19.95 Ins £1.00



AUDIOTRONIC LOW NOISE CASSETTES

TYPE	6	10	25
C60	£1.70	£3.24	£7.65
C90	£2.42	£4.59	£10.80
C120	£2.95	£5.59	£13.22

P/P & Ins 4p each
3-10p: 4 and over 15p

FREE

CATALOGUE

LASKYS 32 PAGE CATALOGUE AND PRICE LIST - absolutely free and available from all stores or by post (see coupon below). This exciting catalogue provides a comprehensive selection from the largest Hi-Fi Retailer in Europe - a MUST for every Hi-Fi and electronics specialist.

AF20 Mono amplifier.....	£5.95
AF25 Mixer.....	£2.90
AF30 Mono pre-amplifier.....	£3.40
AF35 Emitter amplifier.....	£2.55
AF80 0.5W mic. amplifier.....	£5.10
AF305 Intercom.....	£8.45
AF310/2 Mono Amplifier.....	£7.95
M160 Multi-vibrator.....	£3.95
M1302 Transistor tester.....	£7.05
M191 VU Meter.....	£5.45
M192 Stereo balance meter.....	£7.10
LF380 Quadraphonic device.....	£11.45
AF75 Automatic light control.....	£7.55
AT50 Photo cell switch unit.....	£5.65
AT50 400W triac light dimmer/speed control.....	£24.35
AT56 2,200W triac light dimmer/speed control.....	£10.62
AT60 1 channel light control.....	£8.85
AT65 3 channel light control.....	£4.05
GU330 Tremolo unit.....	£3.40
HF61 Diode detector.....	£3.85
HF65 FM transmitter.....	£17.30
HF75 FM receiver.....	£22.95
HF310 FM tuner.....	£11.15
HF325 Deluxe FM tuner.....	£6.35
HF330 Decoder (HF310/325).....	£2.20
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£8.90
GP312 Circuit board.....	£2.25
GP304 Circuit board.....	£6.65
HF380 VU/vhf aerial amplifier.....	£8.25
HF395 broadband aerial amp.....	£8.80
NT110 Stabilised power supply 100mA, 9V.....	£6.60
NT300 Stabilised p. supply.....	£13.95
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2amps.....	£5.95
NT305 Voltage converter.....	£5.95
NT315 Power supply 240V AC 104.5/15V DC, 500mA.....	£12.75

AUDIOTRONIC HEADPHONES

LSH20 Individual volume controls. Mono/stereo switch. 19,000 Hz. 8 ohms.
OUR PRICE £6.25 P/P & Ins 50p



MINIATURE ORGAN MUSIC MASTER AM100
Spanning nearly two octaves, including semi-tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket. Size 229mm x 127mm x 64mm
OUR PRICE £9.95 P/P & Ins 50p



AUDIOTRONIC AHA101 Stereo Headphone Amplifier
All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.
OUR PRICE £10.65 P/P & Ins 30p



FREE

CATALOGUE

LASKYS 32 PAGE CATALOGUE AND PRICE LIST - absolutely free and available from all stores or by post (see coupon below). This exciting catalogue provides a comprehensive selection from the largest Hi-Fi Retailer in Europe - a MUST for every Hi-Fi and electronics specialist.

AF20 Mono amplifier.....	£5.95
AF25 Mixer.....	£2.90
AF30 Mono pre-amplifier.....	£3.40
AF35 Emitter amplifier.....	£2.55
AF80 0.5W mic. amplifier.....	£5.10
AF305 Intercom.....	£8.45
AF310/2 Mono Amplifier.....	£7.95
M160 Multi-vibrator.....	£3.95
M1302 Transistor tester.....	£7.05
M191 VU Meter.....	£5.45
M192 Stereo balance meter.....	£7.10
LF380 Quadraphonic device.....	£11.45
AF75 Automatic light control.....	£7.55
AT50 Photo cell switch unit.....	£5.65
AT50 400W triac light dimmer/speed control.....	£24.35
AT56 2,200W triac light dimmer/speed control.....	£10.62
AT60 1 channel light control.....	£8.85
AT65 3 channel light control.....	£4.05
GU330 Tremolo unit.....	£3.40
HF61 Diode detector.....	£3.85
HF65 FM transmitter.....	£17.30
HF75 FM receiver.....	£22.95
HF310 FM tuner.....	£11.15
HF325 Deluxe FM tuner.....	£6.35
HF330 Decoder (HF310/325).....	£2.20
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£8.90
GP312 Circuit board.....	£2.25
GP304 Circuit board.....	£6.65
HF380 VU/vhf aerial amplifier.....	£8.25
HF395 broadband aerial amp.....	£8.80
NT110 Stabilised power supply 100mA, 9V.....	£6.60
NT300 Stabilised p. supply.....	£13.95
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2amps.....	£5.95
NT305 Voltage converter.....	£5.95
NT315 Power supply 240V AC 104.5/15V DC, 500mA.....	£12.75

LSH30 Individual tone and volume controls. Mono/stereo switch. 30-20,000 Hz. 8 ohms.
OUR PRICE £8.95 P/P & Ins 30p



MINIATURE ORGAN MUSIC MASTER AM100
Spanning nearly two octaves, including semi-tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket. Size 229mm x 127mm x 64mm
OUR PRICE £9.95 P/P & Ins 50p



RANK AUDIO RA 210T STEREO AMPLIFIER
7 1/2 watts rms. Inputs for magnetic phono, tuner, tape and aux. Separate bass, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer. P/P & Ins.
OUR PRICE £21.85 Ins £1.00



FREE

CATALOGUE


LASKYS 32 PAGE CATALOGUE AND PRICE LIST - absolutely free and available from all stores or by post (see coupon below). This exciting catalogue provides a comprehensive selection from the largest Hi-Fi Retailer in Europe - a MUST for every Hi-Fi and electronics specialist.

AF20 Mono amplifier.....	£5.95
AF25 Mixer.....	£2.90
AF30 Mono pre-amplifier.....	£3.40
AF35 Emitter amplifier.....	£2.55
AF80 0.5W mic. amplifier.....	£5.10
AF305 Intercom.....	£8.45
AF310/2 Mono Amplifier.....	£7.95
M160 Multi-vibrator.....	£3.95
M1302 Transistor tester.....	£7.05
M191 VU Meter.....	£5.45
M192 Stereo balance meter.....	£7.10
LF380 Quadraphonic device.....	£11.45
AF75 Automatic light control.....	£7.55
AT50 Photo cell switch unit.....	£5.65
AT50 400W triac light dimmer/speed control.....	£24.35
AT56 2,200W triac light dimmer/speed control.....	£10.62
AT60 1 channel light control.....	£8.85
AT65 3 channel light control.....	£4.05
GU330 Tremolo unit.....	£3.40
HF61 Diode detector.....	£3.85
HF65 FM transmitter.....	£17.30
HF75 FM receiver.....	£22.95
HF310 FM tuner.....	£11.15
HF325 Deluxe FM tuner.....	£6.35
HF330 Decoder (HF310/325).....	£2.20
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£8.90
GP312 Circuit board.....	£2.25
GP304 Circuit board.....	£6.65
HF380 VU/vhf aerial amplifier.....	£8.25
HF395 broadband aerial amp.....	£8.80
NT110 Stabilised power supply 100mA, 9V.....	£6.60
NT300 Stabilised p. supply.....	£13.95
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2amps.....	£5.95
NT305 Voltage converter.....	£5.95
NT315 Power supply 240V AC 104.5/15V DC, 500mA.....	£12.75

LSH40 Two-way speaker system. Individual volume controls. 20-20,000 Hz. P/P & Ins 30p
OUR PRICE £10.75 P/P & Ins 30p



MINIATURE ORGAN MUSIC MASTER AM100
Spanning nearly two octaves, including semi-tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket. Size 229mm x 127mm x 64mm
OUR PRICE £9.95 P/P & Ins 50p

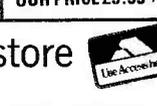

RANK AUDIO RA 210T STEREO AMPLIFIER
7 1/2 watts rms. Inputs for magnetic phono, tuner, tape and aux. Separate bass, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer. P/P & Ins.
OUR PRICE £21.85 Ins £1.00



FREE

CATALOGUE

LASKYS 32 PAGE CATALOGUE AND PRICE LIST - absolutely free and available from all stores or by post (see coupon below). This exciting catalogue provides a comprehensive selection from the largest Hi-Fi Retailer in Europe - a MUST for every Hi-Fi and electronics specialist.

AF20 Mono amplifier.....	£5.95
AF25 Mixer.....	£2.90
AF30 Mono pre-amplifier.....	£3.40
AF35 Emitter amplifier.....	£2.55
AF80 0.5W mic. amplifier.....	£5.10
AF305 Intercom.....	£8.45
AF310/2 Mono Amplifier.....	£7.95
M160 Multi-vibrator.....	£3.95
M1302 Transistor tester.....	£7.05
M191 VU Meter.....	£5.45
M192 Stereo balance meter.....	£7.10
LF380 Quadraphonic device.....	£11.45
AF75 Automatic light control.....	£7.55
AT50 Photo cell switch unit.....	£5.65
AT50 400W triac light dimmer/speed control.....	£24.35
AT56 2,200W triac light dimmer/speed control.....	£10.62
AT60 1 channel light control.....	£8.85
AT65 3 channel light control.....	£4.05
GU330 Tremolo unit.....	£3.40
HF61 Diode detector.....	£3.85
HF65 FM transmitter.....	£17.30
HF75 FM receiver.....	£22.95
HF310 FM tuner.....	£11.15
HF325 Deluxe FM tuner.....	£6.35
HF330 Decoder (HF310/325).....	£2.20
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£8.90
GP312 Circuit board.....	£2.25
GP304 Circuit board.....	£6.65
HF380 VU/vhf aerial amplifier.....	£8.25
HF395 broadband aerial amp.....	£8.80
NT110 Stabilised power supply 100mA, 9V.....	£6.60
NT300 Stabilised p. supply.....	£13.95
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2amps.....	£5.95
NT305 Voltage converter.....	£5.95
NT315 Power supply 240V AC 104.5/15V DC, 500mA.....	£12.75

your nearest store

CENTRAL LONDON (01) 493 8641	LEICESTER 45 Market Pl 537678
481 Oxford Street, W1	NORTHAMPTON 78 Abington Street 35753
10 Tottenham Court Rd. W1 637 2232	NOTTINGHAM 5-7 Lower Parliament St. 48987
33 Tottenham Court Rd. W1 636 2605	OXFORD 16 Westgate Centre 722870
42/45 Tottenham Ct. Rd. W1 636 0845	READING 6 Fnrns Walk, Friar Street
257/8 Tottenham Ct. Rd. W1 580 0670	RICHMOND 32 Hill Street 948 1441
3 Lisle Street, WC2 437 8204	ROMFORD 86 South Street 20218
118 Edgware Road, W2 723 9789	SOUTHEND 205/206 Churchill West 612241
193 Edgware Road, W2 723 6211	TUNBRIDGE WELLS 53/57 Camden Road 23242
207 Edgware Road, W2 723 3271	WOLVERHAMPTON

AERIALS

Telescopic, 15-120cm	£1.50
Telescopic, H & V Swivel, 15-80cm	£2.25
Indoor FM antenna, Compact design	£2.45
Loft mounting FM dipole antenna	£2.45

CAPACITANCE SUBSTITUTION BOXES

Single control for easy selection	
0001, 001, 0022, 01, 022, 047, 0.01, 0.22	£2.35

KEYNECTORS

Rapid connect to mains. Built-in plano switches, neon & 13A fuse	£3.50
--	-------

MULTIMETERS

Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA, R-150k	£4.95
---	-------

PRINTED CIRCUIT KITS

Contain all items necessary to produce printed circuits	£3.95
---	-------

SIGNAL INJECTORS

Audio through video signals, ideal -servicing amplifiers, radio & tv	£4.25
--	-------

TEST SWITCHES

5 miniature push to test switches	£1.00
-----------------------------------	-------

VERNIER DIALS

Positive logging to 1/10th of a degree, 8:1 ratio, clear scales	£2.45
---	-------

VU METERS

Calibrated -20 to +3, 0-100%, ideal -recording level or power output	£3.40
--	-------

**AUDIO PRODUCTS****AUDIO LEADS**

5p din plug to 5p din plug, 1.5m lead	£1.20
2p din plug to 2p din socket, 10m lead	£1.45
5 pin din plug to 2 phono plugs	£1.20

BIB HI-FI ACCESSORIES

GROOV-KLEENS-Ref. 42	£1.95
1/2" TAPE EDITING KITS-Ref. 23	£1.50
CASSETTE EDITING KITS-Ref. 24	£1.65
CASSETTE HEAD CLEANERS-Ref. 31	£0.65
HI-FI STEREO TEST CASSETTES-Ref. 53	£2.15

CASSETTE WALLETS (HOLD 6)-Ref. 39

£0.90

CASSETTE HEAD DEMAGNETISERS

Shaped pole piece-saves time	£3.65
------------------------------	-------

EARPHONES

Stethoscope style, 8 ohm dynamic	£1.20
Crystal earphone with lead & plug	£0.65
High resistance, 2000 ohm headphones	£3.20

FOOT SWITCHES

Push on-push off. Anti skid base	£2.70
----------------------------------	-------

INTERCOMS

2-station, ideal for the home-baby alarm, office, with cable & staples	£6.35
--	-------

Door-phone 'Answer door before opening' Completely weatherproof	£9.95
---	-------

MICROPHONES

Dynamic, remote start/stop, 200 ohms, 100-10kHz, 6mV output	£2.15
---	-------

MINIATURE TRANSISTOR MODULES

Microphone pre-amplifier	£2.45
Power amplifier	£2.70

(Each plug-in with mounting socket)

STEREO HEADPHONES

Superb stereo listening in comfort and privacy, 30-15kHz, 8 ohms	£4.85
--	-------

STEREO HEADPHONE JUNCTION BOXES

3 way switch unit selects phones only, speakers only or both	£2.30
--	-------

STEREO PRE-AMPLIFIERS

In: 3-30mV. Equalise: RIAA. Out: 200-800mV flat. 20-20kHz. Supply: PP3	£7.30
--	-------

SPEAKERS

Miniature, 75mm dia, 8 ohms	£0.95
-----------------------------	-------

TWEETERS & CROSSOVERS

Super Tweeters, 8 ohms, c/f 7kHz, For systems up to 30W RMS	£4.60
---	-------

Cone Tweeters, 8 ohms, c/f 3kHz, For systems up to 10W RMS	£2.35
--	-------

Crossovers, 8 ohms, c/f 800, 3kHz, 7kHz. For systems up to 40W RMS	£5.85
--	-------

Crossovers, 8 ohms, c/f 3kHz. For systems up to 15W RMS	£2.10
---	-------

BATTERY ELIMINATORS

Miniature AC adaptor-provides 9V at 50mA DC output from mains	£4.35
---	-------

POWER SUPPLY UNITS

P1 Switchable between 6 & 9V (200mA) Ideal-most small radios, etc.	£4.85
P2 Switchable to provide 6, 7.5, 9V at 400mA	£7.15

TRANSFORMERS

Mains (miniature), 2 secondaries	
0-6V, 0-6V RMS, 280mA	£2.70
0-12V, 0-12V RMS, 150mA	£2.70

Mains (sub miniature)	
6-0-6V RMS, 100mA	£1.45
12-0-12V RMS, 50mA	£1.45

PERSONAL RADIOS

Phillips RL077 with earphone & case	£6.00
Phillips RL020 with earphone & case	£7.50

**TOOLS****COMBINATION TRY & MITRE SQUARES**

Cabinet/Chassis/P.C.B. work. One tool combining Try & Mitre Square, Depth, Height and Marking Gauges, 300mm/12in Rule, Spirit Level/Plumb & Steel Scriber	£2.35
---	-------

--	--

--	--

HAND DRILLS

Laytool compact, 5/16" chuck, Gears totally enclosed, S/L bearings	£3.99
--	-------

SOLDERING IRONS

Antex 25W, X25, 240V, Low leakage, 1/8" interchangeable long life bit	£2.05
3/32", 1/8", 3/16" spare bits-each	£0.47

X25 Elements	£1.10
--------------	-------

Stands, ST3, High grade base, spring, sponges, accommodation-spare bits	£1.00
---	-------

SOLDER -In handy Bib dispenser	£0.43
--------------------------------	-------

WIRE STRIPPERS & CUTTERS

Bib BB, 8 gauge selector, automatic opening, easy grip handles	£0.85
--	-------

IMPROVE PETROL CONSUMPTION

Fit the Brilliant
New P.E. Scorpio Mk II
"Dual Polarity"
Capacitive Discharge
Electronic Ignition
System



★ Genuine Improvement in overall petrol consumption (independent report claims at least 8%-10%)

★ Much easier cold weather starting, less strain on your battery

★ Less use of choke—increases engine life

★ Smoother running at lower revs—makes your four cylinder car feel like a six cylinder

Together with the following 'Scorpio Mk II' plus features not previously available with other makes:—

★ Only one model used for both positive (+) and negative (-) earth vehicles—if you change your car, you can certainly transfer your 'Scorpio'.

★ Retains your original contact breaker points, which last their mechanical life—no points burn

★ Will drive electronic tachometers.

Send a stamped addressed envelope for our free interesting brochure, "Electronic Ignition—How it Works", containing circuit and itemised price list. Price for complete kit of parts, with easy to follow, comprehensive instructions, connecting wire, etc. ONLY £15.50, including V.A.T. and postage and packing. Ready made unit, fully tested, for immediate installation with easy to follow instructions, all leads, etc., ONLY £17.50, including V.A.T. and postage and packing.


THOUSANDS ALREADY IN USE—FULLY GUARANTEED.

ELECTRO SPARES, 288 ECCLESALL ROAD, SHEFFIELD S11 8PE

Tel: Sheffield (0742) 668888

Please allow 14 days minimum for delivery, for postal delays, cheque clearance, etc.

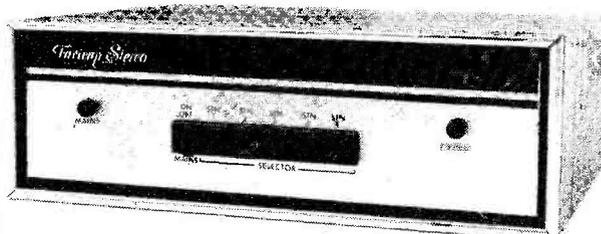P.E. 'VARICAP' STEREO PUSH BUTTON F.M. TUNER



The P.E. 'Varicap' Stereo Tuner uses the latest Mullard modules for R.F. and I.F. circuits—highly sensitive and pre-aligned for ease of construction. This superb kit has everything to enable you to construct this highly sensitive F.M. Stereo Tuner, with instant push button station selection, self contained regulated

power supply, stereo decoder, etc. etc. Easy to construct, highest quality reproduction. Price only £34.50 including V.A.T. and postage and packing. Please send stamped addressed envelope for our free brochure on the Varicap, which gives performance figures, detailed description, etc., etc.





P.E. 'GEMINI' STEREO AMPLIFIER

Output genuine 30W R.M.S. per channel! Distortion 0.01% (Maximum)! Frequency response -3dB, 20Hz to 100 kHz into 8 ohms! Fully comprehensive inputs, disc, tape, MIC etc.!


Yes, we are still supplying all components for this superb Stereo Amplifier, since we have not yet found a better one!

Fully comprehensive constructional booklet available, containing full specification, performance graphs, step-by-step, assembly instructions, photographs, fault finding guide, etc. etc. Price 55 pence plus 9 pence postage and packing.

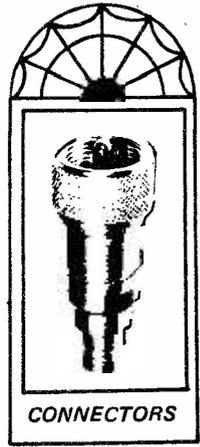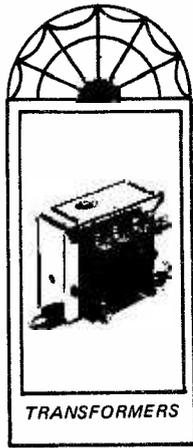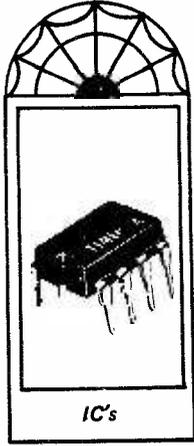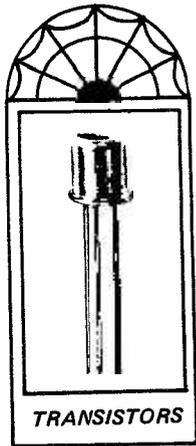For itemised price list only please forward stamped addressed envelope.



Use DORAM components for your project

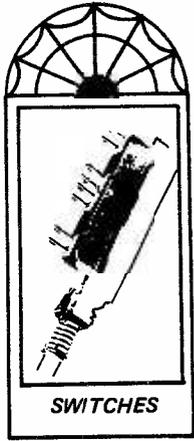

The doorway to Amateur Electronics



60^p

- ★ DORAM'S NEW CATALOGUE OFFERS THOUSANDS UPON THOUSANDS OF QUALITY ELECTRONIC COMPONENTS AND AUDIO ACCESSORIES FROM TRUSTED BIG NAME MANUFACTURERS.
- ★ ALL COMPONENTS ARE INDIVIDUALLY CODED AND PRICED - MANY NEW COMPONENTS ADDED FROM CUSTOMER REQUESTS.
- ★ 16 EXTRA PAGE DATA SECTION.
- ★ UNIQUE FREE UP-DATE PRODUCT INFORMATION SERVICE DURING LIFE SPAN OF CATALOGUE.
- ★ ALL COMPONENTS SENT BY RETURN OF POST.
- ★ POST AND PACKING FREE (only applies for Great Britain, N. Ireland and B.F.P.O. Nos. - overseas orders F.O.B.)
- ★ NO QUIBBLE REPLACEMENT PART SERVICE

The doorway to amateur electronics

DORAM

DORAM ELECTRONICS LIMITED
P. O. Box TR8
Leeds LS12 2UF

I enclose 60p. Please send me by return my new Doram Catalogue. (Overseas orders except for B.F.P.O., please add 30p for post and packing surface only).

PLEASE PRINT BLOCK CAPITALS  PW 10

NAME _____

ADDRESS _____

Post Code _____

POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA.
In moulded case forming a 2 pin 5A mains plug.



2 metre output lead with 4-way multiplex giving 2.1 and 3.5 mm sockets and 3-6 mm plugs.
Price £2.30. Post 10p.

2" and 4" PANEL METERS

2"		4"	
SIZE: 60mm Wide x 45mm High x 40mm Deep.	SIZE: 110mm Wide x 82mm High x 43mm Deep.	Movement	I.R. Ohms
0-50 micro A.	1250	0-50 micro A.	1400
0-100 micro A.	580	0-100 micro A.	730
0-500 micro A.	170	0-500 micro A.	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	6	0-10 mA	6
0-50 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-500 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	15K	0-25 Volt	15K
0-50 Volt	50K	0-50 Volt	50K
0-300 Volt	300K	0-300 Volt	300K
"g" Meter	170	"g" Meter	200
VU Meter	8250	VU Meter	8250

VU Meters are complete with detectors. Modern wide view.
Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set.

1/2 watt CARBON FILM RESISTORS
1/2 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 95p per 100.

C1000 MULTIMETER

Special Offer
Compact General Purpose Mini Multimeter.
Input Resistance 1000 ohms per volt
Ranges:
AC Volts 0-15, 50, 250, 1000 V
DC Volts 0-10, 50, 250, 1000 V
DC Current 0-1 mA, 0-100 mA
Resistance 0-150K ohms
Size 90 x 24 x 90 mm
Complete with Batteries, Test Prods, Instructions. Special price £3.90 Post 25p.



C1001 MULTIMETER

Input Resistance 20,000 ohms per volt
Overload protection
150 μA movement, clear scale
Ranges—AC Volts 0-10, 50, 250, 1000 V
DC Volts 0-5, 25, 125, 500, 2500 V
DC Current 0-50 mA
Resistance 0-60 Kohms, 0-6 Mohms
Decibels -20 to +22 dB.
Carrying Case, Test Prods and Batteries included.
Size: 11.5 x 8.3 x 2.7 cm.
Price £9.95. Post 20p.

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 3-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA	Ref. No.	Price Cased	Price Plugs	Price 2 Pin + 1 Earth	Price Open Post
60	149	8.95	0.88	4.37	0.56
100	150	9.15	0.88	4.80	0.64
200	151	11.45	0.88	8.14	0.80
250	152	12.90	0.88	9.80	0.88
350	153	15.50	0.88	11.88	0.95
450	154	17.25	0.88	13.62	1.13
750	155	27.10	1.10	20.59	O.A.
1000	156	35.40	1.10	29.15	O.A.
1500	157	42.00	1.10	33.37	O.A.
2000	158	49.75	2.64	37.10	O.A.
3000	159	73.15	2.64	58.55	O.A.

12 & 24 Volts Prim. 200-240V.

Amps	Ref. No.	Price	Post
12V	24V	£	£
0.2	0.15	2.42	1.58
0.5	0.25	1.11	1.88
1	0.5	2.13	1.74
2	1	7.1	2.50
4	2	18	2.96
6	4	30	4.18
8	4	108	4.56
10	5	72	5.20
12	6	116	5.51
16	8	17	7.00
20	10	115	10.42
30	15	187	13.25
40	20	232	14.55
60	30	226	16.93

30 Volts

Amps	Ref. No.	Price	Post
0.5	112	1.90	0.47
1	79	2.40	0.56
2	30	3.50	0.64
3	20	4.50	0.64
4	21	5.15	0.72
5	51	6.40	0.72
6	117	7.16	0.88
8	88	9.55	0.95
10	89	9.87	0.95

AUTO TRANSFORMERS

VA	Ref. No.	Price Cased	Price Plugs	Price 2 & 3 pin	Price Open Post
Tapped at 115, 220, 240 Volts	20	113	8.85	0.20	1.71
Tapped at 115, 200, 220, 240 Volts	150	4	6.88	0.20	4.12
	200	65	7.04	0.20	4.95
	300	66	8.00	0.20	5.81
	500	67	10.99	0.20	8.85
	750	83	13.82	0.85	10.80
	1000	84	17.27	0.85	13.68
	1500	93	21.87	0.85	18.31
	2000	95	33.11	1.60	24.25
	3000	73	47.94	2.10	35.10

50 Volts

Amps	Ref. No.	Price	Post
0.5	102	2.58	0.47
1	103	3.48	0.56
2	104	5.03	0.64
3	105	5.81	0.72
4	106	7.58	0.88
6	107	12.30	0.95
8	118	13.20	1.13
10	119	17.02	O.A.

60 Volts

Amps	Ref. No.	Price	Post
0.5	124	2.30	0.56
1	126	3.41	0.56
2	127	5.09	0.72
3	128	7.52	0.80
4	128	8.75	0.95
5	40	9.75	0.95
6	120	11.20	1.01
8	121	15.00	1.19
10	122	18.20	O.A.
12	189	18.50	O.A.

MINIATURE AND EQUIPMENT

Prim. 240V with screen.

Sec. 1	Volts	Sec. 2	Milliamps	Ref. No.	Price	Post
3-0-3	—	200	—	238	1.50	0.25
0-5	0-6	500	500	234	1.38	0.25
0-6	0-6	1000	1000	212	1.90	0.47
0-9	—	100	—	18	1.40	0.25
0-9-9	—	330	330	235	1.50	0.25
0-8-9	0-8-9	500	500	207	1.93	0.34
0-8-9	0-8-9	1000	1000	208	2.75	0.47
15-0-15	—	30	—	240	1.35	0.25
0-15	0-15	200	—	230	1.38	0.25
0-15-20	—	40	—	241	1.35	0.25
0-20	0-20	150	150	237	1.38	0.25
0-15-20	0-15-20	500	500	205	2.73	0.66
0-20	0-20	300	300	214	1.93	0.47
20-12-0-12-20	—	3500	NO SCREEN	1116	3.30	0.64
0-15-20	0-15-20	700	(D/C)	251	2.20	0.47
0-15-27	0-15-27	1000	1000	206	3.50	0.66
0-15-27	0-15-27	500	500	203	3.00	0.56
0-15-27	0-15-27	1000	1000	204	3.85	0.56

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 20p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 59p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
500 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p

ADD 10p P & P PER ORDER



PLEASE
ADD
VAT

POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5
9 and 12 volts at 500 mA D.C.,
Operates from 240 V mains,
suitable for Radios, Tape
Recorders, Record Players etc
Size 7.5 x 5 x 0.14-0cm. Price
£3.95. Post 25p.



MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation
Price: Packet of 10 for 60p. Postage 15p.

A.S.P. LTD.

DEPT PW9, SIMMONDS ROAD, WINCHEAP,
CANTERBURY, KENT. Tel: (0227) 52436

Send 25p for Catalogue

TONER ELECTRONICS

FOR

(Components, Transistors, Valves, Hi-Fi, all accessories, leads, etc., stocked. Speakers, Cartridges, Microphones, Tapes.)

Send 15p for price lists and our bargain page

(Callers Welcome).

38 MORGAN ST., WATERFORD, IRELAND
Phone: 051-32300

ELECTRONI-KIT

"... kits of exceptional quality" (AUDIO mag. Dec. 1974)
"... These kits are very good" (P.W. mag. June 1975)

BUILD AND REBUILD AND DESIGN YOUR OWN WORKING PROJECTS—NO SOLDERING

Radios, microphones, burglar alarms, inter-comms, ferrite detectors, solar cell, photoelectric cell, voice relay, electronic cats, birds, organs, illuminometers, voltmeters, meters of all types, etc., etc., plus your own circuit designs.

COMPLETELY SAFE—suitable for all, from beginners on.
30 different projects £10-45, 100 different projects £20-45, over 150 £33-95. Add-on kits, spares, available too.

Prices include Valuable Manuals, Battery, p. & p. VAT etc.
Cheque/P.O./Cash (or 11p for literature) to DEPT. PW


Satisfaction guaranteed

**ELECTRONI-KIT LTD, 408 St. John's Street,
London, EC1. (01-278 4579)**





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

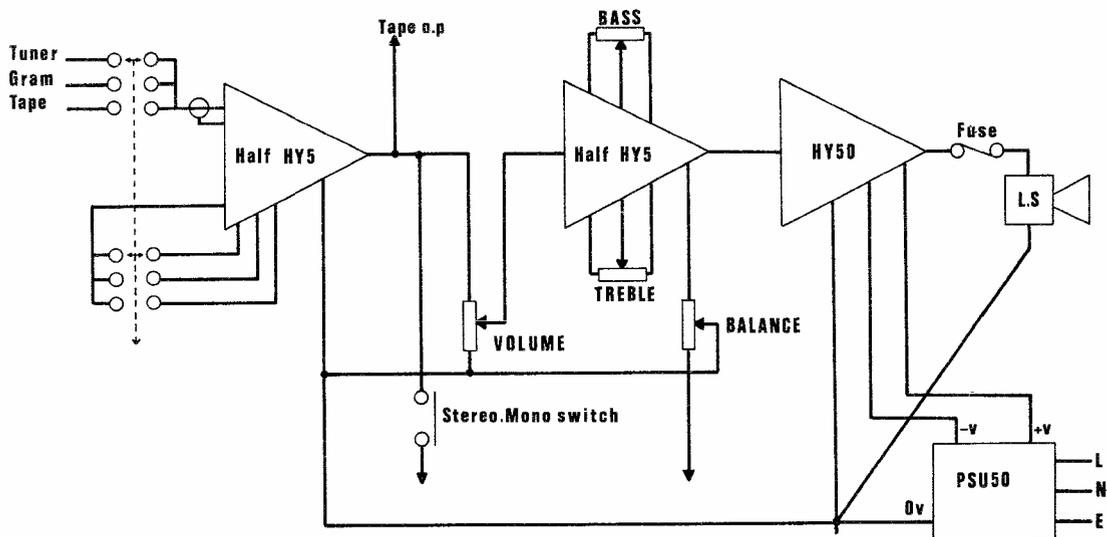

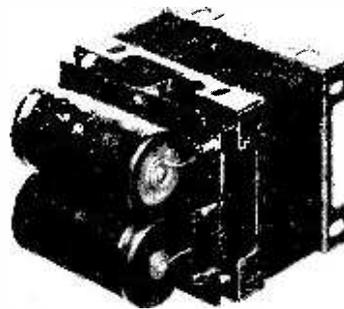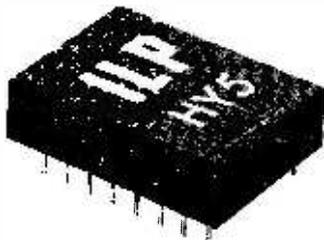MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxillary 3-100mV; input/Impedance 47kΩ at 1kHz. **Outputs:** Tape 100mV; Main output 0db (0.775V RMS). **Active Tone Controls:** Treble ± 12db at 10kHz; Bass ± 12db at 100Hz; Distortion: 0.5% at 1kHz. **Signal/Noise Ratio:** 68db. **Overload Capability:** 40db on most sensitive input. **Supply Voltage:** ± 16-25V.

PRICE £4.50 + 36p VAT
P. & P. free

The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8Ω. **Load Impedance:** 4-16Ω. **Input Sensitivity** 0db (0.775V RMS). **Input Impedance:** 47kΩ. **Distortion:** Less than 0.1% at 25V typically 0-05%. **Signal/Noise Ratio:** Better than 75db. **Frequency Response:** 10Hz-50kHz ± 3db. **Supply Voltage:** ± 25V. **Size:** 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT
P. & P. free

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: 50V (25-0-25V). **Input Voltage:** 210-240V. **Size:** L.70. D.90. H.60mm.

PRICE £6 + 48p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD

Tel (0227) 63218

Regd. V.A.T. No. 202141535

Please supply,

Total Purchase price

Enclose, Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number


Name & Address

Signature

RTVC

FOR SPEAKERS AT FANTASTIC REDUCTIONS

NEW!

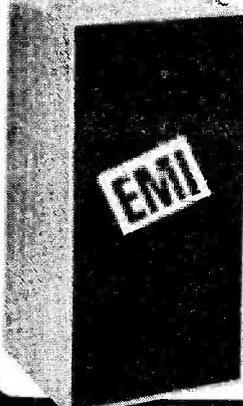

LE-4 SPEAKERS


Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.
Specification — Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz—20 KHz.

Our Price £34.00 each
 (normally £66.00)+£5.80 p & p.
 Scotland and the Orkneys
 P & P Surcharge £3.50

THE 'COMPACT'

EASY BUILD SPEAKER KIT


A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitred and professionally finished, simply apply glue, fold up around baffle board, and fix together with masking tape till glue dries. The cabinet measures 12" x 9" x 5" deep approx finished in simulated teak, incorporating a quality 7" x 4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia 7" magnet size 2 3/8" approx.

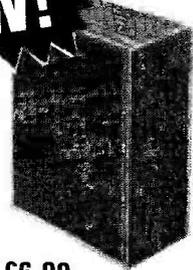


£6.00
 pair inclusive P & P £1.70

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 1/2" tweeter and matching crossover.
 Easily put together with just a few basic tools.
Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20—20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

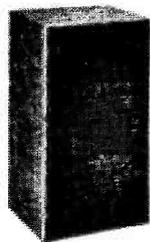

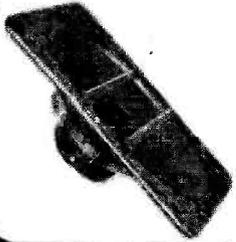£22.00 pair complete +£5.20 p & p.
 Complete with crossover Components and circuit diagram



EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

£6.50 +£1.20 p & p.
 Complete with crossover Components and circuit diagram

RTVC*

NEW!

VISCOUNT IV STEREO SYSTEM

System 1a. **£65.00**

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls — volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter. Front panel socket for stereo headphones. And a host of sockets at the rear — for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. — 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. — 50 millivolts @ 50 K ohms (R.I.A.A.); 3, 4, & 6. Tape Tuner/Aux. — 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone — 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than -50 dB on all inputs. **Tone control range:** Bass ±15 dB @ 50 Hz; Treble ±12 dB @ 10 KHz. **Power requirements:** 200-250V A.C. mains @ 60 watts. **Approx. size:** 15 1/4" x 3" x 10".

MP60 type deck with magnetic cartridge, de luxe plinth and cover.
Two Duo Type IIa matched speakers — Enclosure size approx. 19 1/4" x 10 3/4" x 7 1/4" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling. 30 watts peak.
Complete System with these speakers **£65.00** +£6.50 p & p.

System 2. **£81.00**

Viscount IV amplifier (As System 1a)
 MP60 type deck (As System 1a)

Two Duo Type III matched speakers — Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS. 8 ohms frequency range — 20 Hz to 18,000 Hz.

Complete System with these speakers **£81.00** +£7.60 p & p.

PRICES: SYSTEM 1a
 Viscount IV R103 amplifier £25.00+£1.90 p & p.
 2 Duo Type IIa speakers £30.00+£6.50 p & p.
 MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00+£3.30 p & p.
 Total if purchased separately: £75.00
 Available complete for only **£65.00** +£6.50 p & p.


PRICES: SYSTEM 2
 Viscount IV R103 amplifier £25.00+£1.90 p & p.
 2 Duo Type III speakers £46.00+£7.50 p & p.
 MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00+£3.30 p & p.
 Total if purchased separately: £91.00
 Available complete for only **£81.00** +£7.60 p & p.



20x20 SYSTEM

Scotland and the Orkneys P & P Surcharge
 System 1a £1.75 System 2 £3.50

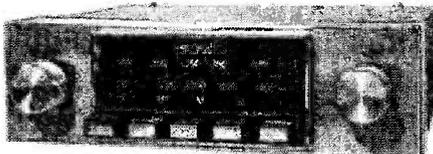PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO


Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high and 4 1/2" deep approx. **£9.50** +£1.05 p & p. Speaker including baffle and fixing strip **£2.00** +45p p & p. Car Aerial Recommended — fully retractable **£1.60** +40p p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** +£1.05 p & p.

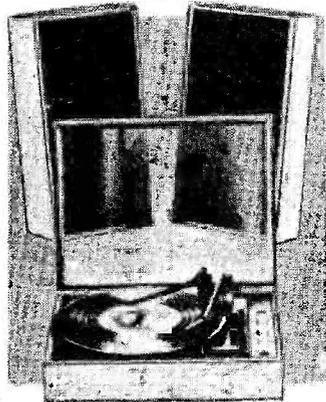*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications — For the technically minded:

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8—15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs.

Overall Dimensions. Speakers approx 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only £23.20 +£3.00 p & p.

Extras if required. Optional Diamond Styli **£1.60**. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

*DISCO AMPLIFIER




Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs — 4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic. guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains. 240V operation. Size approx: 12 1/2" x 6" x 3 1/2". **£20.00** +£1.35 p & p.

*8 TRACK HOME CARTRIDGE PLAYER

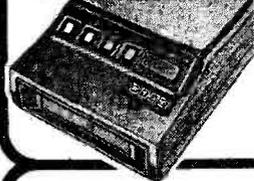

Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system. Unisound module and the Stereo 21. Technical specification Mains input. 240V. Output sensitivity 125mV.

Yours for only **£16.20** +£1.70 p & p.


BUILD YOUR OWN STEREO AMPLIFIER*



For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7"x4") **£10** + £1.75 p & p. **£8.95** + £1.05 p & p. Also available with the 'Compact' (see opposite page) easy build speaker kit **£13.50** + £2 p & p.

PORTABLE DISCO CONSOLE*

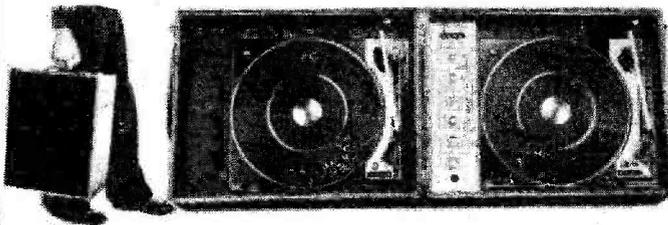

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV. Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation. Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter). Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17 1/2" x 13 1/2" x 8 3/4" (app.)
Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier. The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only **£49.00** +£6.50 p & p.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Aug 1975 and subject to change without notice.

All prices include VAT at current rates




21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

Lenco stereo cassette mechanisms from Goldring.


Lenco cassette mechanisms, as recommended by Practical Wireless for the Kempton and Ascot car stereo players, have major appeal for the enthusiast.

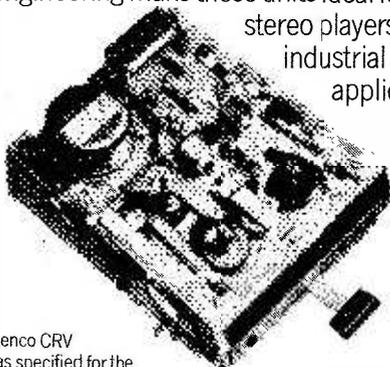Both units are based on the famous STAAR designs, and the robust construction and precision engineering make these units ideal for use in car stereo players, Hi-fi systems, industrial and many other applications.



Lenco CRV (as specified for the PW Ascot model). High quality unit, manufactured to hi-fi standards, with full facilities for both recording and playback. Features include fast forward, fast rewind, pause control, erase, auto stop and cassette ejection. £23.12 including packing, carriage and VAT.

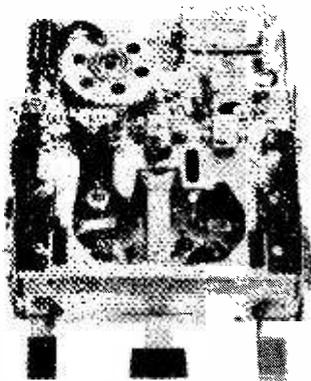Lenco FFR (as specified for the PW Kempton model). Cassette player with fast forward and rewind mechanism, auto stop and cassette ejection. £21.88 including packing, carriage and VAT.



To: Goldring Ltd., 10 Bayford Street, Hackney, London E8 3SE.

Please send me: Lenco FFR at £21.88

Lenco CRV at £23.12

I enclose PO, cheque for £ _____

NAME _____

ADDRESS _____

 **Goldring**

To order, complete coupon and enclose Cheque or Postal Order made out to Goldring Ltd. Please cross out on coupon unit not required.

ENGINEERS

FREE

YOURSELF FOR A
BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 76-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

- | | | |
|--|---|---|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Radio, Servicing & Repairs | <input type="checkbox"/> Painting & Decorating |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT) | <input type="checkbox"/> Radio Amateur's Exam. | <input type="checkbox"/> MECHANICAL |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> AUTO & AERO Motor Mechanics | <input type="checkbox"/> A.M.S.E. (Mech.) |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> C. & G. Motor V. Mechanics | <input type="checkbox"/> General Mech. Eng. |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> General Auto Engineering | <input type="checkbox"/> Inst. Engineers & Technicians |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Maintenance Engineering |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> Air Registration Board Certs. | <input type="checkbox"/> Welding |
| <input type="checkbox"/> RADIO & TELECOMMUNICATIONS | <input type="checkbox"/> M.A.A./I.M.I. Dip. | <input type="checkbox"/> MANAGEMENT & PRODUCTION |
| <input type="checkbox"/> Colour TV Servicing | <input type="checkbox"/> CONSTRUCTIONAL Heating, Ventilating & Air Conditioning | <input type="checkbox"/> Computer Programming |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> DRAUGHTSMANSHIP & DESIGN |
| <input type="checkbox"/> Radio & TV Engineering Course | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> General Draughtsmanship |
| | <input type="checkbox"/> Plumbing Technology | <input type="checkbox"/> A.M.I.E.D. |
| | <input type="checkbox"/> General Building | <input type="checkbox"/> Electrical Draughtsmanship |

POST NOW

G.C.E.

—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPW10, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals) _____

ADDRESS _____

Postcode _____

Other subjects of interest _____ Age _____

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY




TRAMBUS

Electronics Ltd.
WINDSOR, BERKS.
58/60 GROVE RD.
SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p EXPORTS 50p

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES CALLERS WELCOME
CATALOGUE/LIST FREE SEND SAE
BARCLAYCARD & ACCESS x POST.

Digital Displays

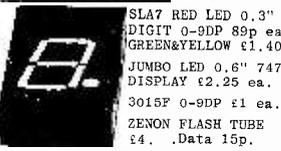


LEDS red 13p

LEDS 209 STYLE ONLY 13p ea
TTL 209 WITH CLIP RED 15p ea
TTL 211 & CLIP GREEN 29p ea
LARGE 0.2" & CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR 2" ORANGE 39p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81p

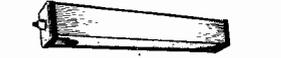TEC12 PHOTO AMP/SCM/TTL/RELAY
DRIVER OR LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK
& WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MM5311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder
with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 DIL14 29p	LM377 2x2W£2.87
555 TIMER 54p	LM380 2W AF 89p
733 RF/IF 28p	LM381 2xPre £2
739 TO99 23p	LM3900 4xOPA69p
709 DIL 14 28p	MC1303 £1.20
710 DIL 14 34p	MC1306 49p
723 Reg. 54p	MC1310&LED£2.65
741 DIL 8 27p	MC1312 SQ £2.10
741 DIL 14 29p	MC1330 69p
741 TO99 29p	MC1339 2xPre £1
747 2x741 70p	MC1350 55p
748 DIL 8 33p	NE536 fetOPA £2
7805 5V £1.40	NE540 Driver £1
7812 & 15 £1.40	NE550 2vRef 79p
78013 6W AF £1	NE555 Timer 55p
8038 SIG GEN £3	NE556 2x" £1.20
CA3028 £1	NE560 PLL £3.15
CA3046 55p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.19
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM300 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN7660 IF £1
LM307 OPA 49p	SN76611 IF£1.25
LM308 HiBo 95p	TAD110 &TF £2
LM309K 5V £1.48	TBA810 7WAF 99p
LM372 1F £1.80	ZN414 RX £1.09

SPECIAL OFFERS
2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p.MFC4000B 33p
NE555 TIMER 55p.ZN414 RX £1.09
BC109 9p.2N3819e 16p.BF511 15p

7400 TTL

7400 GATES 13p	7473/74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7490 52p
7413 SCHMITT 31p	7491/2/3/4 59p
7440 BUFFER 14p	74100 74175 £1
7447 DRIVER 89p	74121 32p
7470 & 7472 29p	74123 59p
	74141(&7441)73p

TRANSISTORS & DIODES

Price each	MATCHING	16p
AC127 & 128 16p	INS.BUSH SET10p	
AC187 & 188 19p	TIP 41 70p	
AD149 43p	TIP 42 80p	
AD161 & 162 33p	TIP 2955 90p	
BC107 & 108 9p	TIP 3055 55p	
BC109 10p	TIS43 see 2N3819e	
BC147/8/9 10p	ZTX109&301 13p	
BC157/8/9 12p	1N4001 4p	
BC167/8/9 12p	1N4004 & 7 7p	
BC177/8/9 18p	1N4148 & 914 4p	
BC182/3/4A&L10p	2N697 14p	
BC212/3/4A&L11p	2N706&8 11p	
BF770/1/2 17p	2N2646 UJT 32p	
BD131 & 132 39p	2N2904 & 5 20p	
BFR51 23p	2N2926royg 9p	
BFR50/51 23p	2N3053 17p	
BFR88 250V 29p	2N3055 115W 37p	
BFY50/1/2 15p	2N3563 & 64 16p	
BSX19/20/21 16p	2N3614 49p	
MJE2955 90p	2N3702 & 3 9p	
MJE3055 65p	2N3704 & 5 10p	
2N3706 & 7 9p	2N3708 & 9 8p	
2N3710 & 11 10p	2N3819E PFT 16p	
2N3819E PFT 16p	2N3823E PFT 17p	
2N3823E PFT 17p	2N3904/5/6 15p	
2N3904/5/6 15p		

NEW TRAMBUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice £1
PAK B 4 741 OP AMP " " £1
PAK C 4 2N3055 £1.D 12 BC109 £1
PAK E 10 BC182 £1.F 11 2N3704 £1
PAK G 8 BF51 £1.H 9 2N3819e £1
PAK J 9 2N3053 £1.K 40 1N914 £1

BZY88 400mW 1A/50V SCR 36p	
ZENER DIODES 9p TAG1/400 55p	
BRIDGE RECT C106 & 7 SCR D1	
1A 50V 20p 4A/400V 53p	
BR100 DIAC 25p SC146D TRIAC	
	10A 400V 75p

VERO

VERO PINSx36 28p.
COPPER CLAD VEROBOARD 0.1"
2 1/2"x5" 29p 2 1/2"x3 1/2" 26p.3 1/2"x3 1/2" 31p.
3 1/2"x5" 31p 3 1/2"x 1 1/2" £1.50
DIL IC'S BOARDS 6x4 1/2" £1.50
24 way edge connector 60p.
36 way 90p. PLAIN 3 1/2"x1 1/2" £1.
FACE CUTTER 45p.FEC ETCH PAK 50p

DALopen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 59p

HEATSINKS

5F/T05 & 18F/T018 5p ea.TV4 15p.
TV3/T03 16p.EXTRUDED 4" 4Y1 29p.
TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p,
ELECTROLYTIC:10/50/100 uf in
10v 5p.25v 6p.50v 8p.2uf/10v 5p.
1000 uf/25v 15p.200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LIN or LOG ROTARY 13p.SWITCH 14p
DUAL 45p.SLIDERS 29p.STEREO 57p
KNOBS 7p.PRESETS 6p.RESISTORS 14p
SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12p. SOCKETS 10p.
ALL CASES ABS/AB7 50p.AB13 65p.
TRANSFORMERS 1A 6v6v or 12v12v
Only £1.34.100mA type CT 75p.

OIL sockets

TEXAS GOLD ea
LOW PROFILE ea
8,14, & 16 PIN 13p
SOLDERCON STRIPS:
100 PINS 50p.1K £3.

QUALITY STEREO SOUND.

ALMOST **1/2 PRICE OFFER!** SOLENT AUDIO SYSTEM

£5-95 down

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM

OUR PRICE **£59.95**

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,00 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control Two matching elliptical speaker units.

Order early limited stocks available cash price £59.95. Credit Sale £5.95 deposit 9 monthly payments of £7.00 (Total Credit price £68.95). P. & P. £3.00. Send £8.95 today.

Chassis only available for cash at £42.00.

Full 12 months Guarantee. CALLERS WELCOME.

Stereo headphones supplied with every complete order.

LEWIS radio PW/10/75 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-882-1644

TOROIDAL TRANSFORMERS FOR THE TEXAN II

Designed by S.I.G.A. ELECTRONICS in conjunction with Texas Instruments for uprating Texan 20-20 Amplifiers. Pri. 220-240V; 50Hz; Screen; Sec. 25-20-0-20-25V, 1-5A. Fully impregnated; flying lead connections. Ref. T1295 Price £6.70 + 25% VAT post 50p. Ref. T1295/F with resin filled centre, 2BA clear hole. Price £7.10 + 25% VAT post 50p.


Toroidal transformers suitable for Audio Power Supplies Pri. 240V 50Hz; Screen; fully impregnated; flying leads

REF	SECONDARIES	O.D. (cms)	HT.	Price	Post
315	(a) 33-0-33V 2A	12.0	× 4.4	£8.50	£0.69
	(b) 25-0-25V 0.1A				
291	(a) 33-0-33V 4A	13.0	× 5.7	£10.69	£0.78
	(b) 25-0-25V 0.2A				
061	20-0-20V 1A	7.9	× 4.3	£4.87	£0.50
360	25-0-25V 1.5A	7.7	× 4.5	£6.26	£0.50
285	25-0-25V 2A	9.0	× 5.1	£6.37	£0.60
284	0-45V 1A	9.5	× 4.4	£5.15	£0.60
000	0-45V 2A	11.3	× 3.8	£6.64	£0.69

Terms: Cash with order, please add 25% VAT to goods only. Quantity discounts available on request.

Dept. PW 04
S.I.G.A. (ELECTRONICS) LIMITED
Sunderland Road, Sandy, Beds
SG19 1QY

LOWE ELECTRONICS

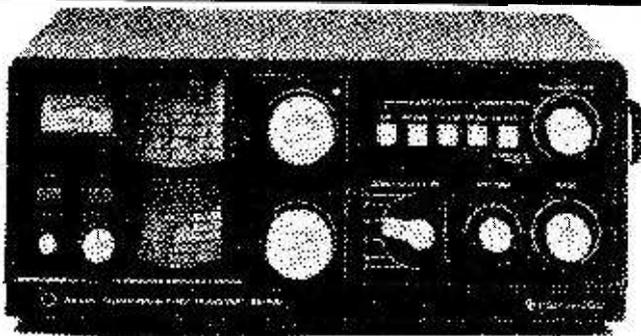

TRIO QR666

An all new receiver from the TRIO company providing general coverage reception 170kHz to 30MHz with calibrated bands for the amateur bands. Dual-gate MOSFETS for RF and mixer stages ensure high gain, good selectivity and first class A.G.C. characteristics.

Dual position selectivity gives two bandwidths to cater for all band conditions.

Use the QR666 at home, in the car or boat or truly portable; all catered for by the exclusive 3-way power supply.

PRICE £130 (VAT excl)

SPECIFICATION 170-410
 Frequency coverage 170-410kHz, 525-1250kHz, 1.25-3.0MHz,
 3-7.5MHz, 7.5-18MHz, 18-30MHz (Dual conversion)
 Bandspread 3-5.4MHz, 7-7.5MHz, 14-14.6MHz, 21-21.5MHz
 (Dual conversion), 28-30MHz (Dual conversion)
 Modes AM, USB, LSB, CW
 Selectivity 2 position wide/narrow
 Antenna 50-100Ω
 Sensitivity 1μV for 10dB S/N (SSB/CW)
 AF Output More than 1.5W into 8Ω. Internal speaker fitted
 Power supply 100/117/220/240V ac 50/60Hz, External 12V dc.
 Internal 12V batteries. Automatic changeover to
 internal supply in the event of mains failure
 Dimensions (mm) 362 wide x 163 high x 322 deep
 Weight 7.3kg (16.09 lbs)
 Options 500kHz marker QR6MK, FM broadcast tuner
 QR6FM

We stock a great many products apart from those advertised month by month—everything in fact for the radio amateur operator. If you need more information, our complete catalogues are available free to callers. If you require them sending by mail, postal charges being what they are today, please send us 20p in stamps because that's what it costs to send them to you!

HEAD OFFICE
BRANCH OFFICES
AGENTS

119 Cavendish Road, Matlock, Derbyshire. Tel. 2817 or 2430 9 a.m. to 9 p.m.

Goring Road, Steyning, Sussex. Tel. Steyning 814466

Soho House, 362-4 Soho Road, Handsworth, Birmingham. Tel. 021-554 0708

Alan GW3YSA. 35 Pen-Y-Waun, Efail Isaf, Nr. Pontypridd. Tel. Newton Llantwit 3809


John G3JYG. 16 Harvard Road, Ringmer, Lewes, Sussex. Tel. Ringmer 812071

Sim GM3SAN. 19 Ellismuir Road, Baillieston, Nr. Glasgow. Tel. 041-771 0364

OPENING HOURS: 9-5.30 TUESDAY TO SATURDAY INCLUSIVE

73 from BILL G3UBO/VE8DP, ALAN G3MME, JOHN G3PCY/5N2AAC, IAN G3ZYC

verobox

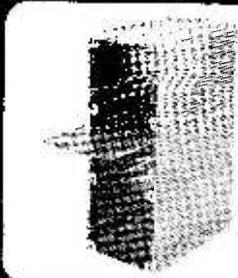

ALUMINIUM ENCLOSURES

- 8 standard sizes available from your local retailer.
- Made from precision extrusions with integral board guide slots.
- Flanged sides improve appearance and reduce heat.
- Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.

Eastleigh, Hants. SO5 3ZH

Tel: Chandler's Ford 2952 Telex: 47551

Subsidiaries and Agents
throughout the World

4-STATION INTERCOM



£16.15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 8 connecting wires each 66ft. and other accessories. P. & P. 65p.

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price ~~229.99~~ per pair P. & P. 65p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£11.95

+VAT 90p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £12.95 + VAT £1.04 P. & P. 65p, 10-day price return guarantee.

WEST LONDON DIRECT SUPPLIES (PWS)
 189 KENSINGTON HIGH STREET, LONDON, W8

GREENBANK ELECTRONICS

(Established 1970)

FREE!

Data and suggested circuits for AY-5-1224 & MK 50253 clock chips, details of P.C.B.s and component kits for AY-5-1224, data sheets for LED 0.3" and 0.6" displays.

NEW!

P.C.B.s to suit AY-5-1224 clock chip plus display (two types) **95p**
 50 Hz clock timebase suggested circuit (uses 3-2768 MHz Crystal), details free.

4 DIGIT CLOCK KITS

Kits include:—P.C.B., AY-5-1224 chip, 4 0.3" LED digits, transistors, diodes, resistors, capacitors, solder pins **£9.95** (0.6" digit version also available). Success guaranteed.

CLOCK CHIPS

AY-5-1224 4 digit 12/24 hr. Digital Clock Chip **£3.66**
 MK 50253 4/6 digit Alarm Clock Chip **£5.50**

LEDs (Economy Types)

DL-704E 0.3" Common cathode 7 seg. display **85p**
 DL-747E 0.6" Common anode 7 seg. display **£1.70**
 Single Red 0.2" LED indicator **12p**

Add 8% VAT to all prices, post etc. 10p + 8% VAT per order.

GREENBANK ELECTRONICS
 (Dept. W10P), 94 New Chester Road,
 New Ferry, Wirral, Merseyside, L62
 5AG Tel: 051-645 3391

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

10p for 1 Valve.
Each additional Valve add 2p in UK

DM70 0-89	EP86 0-53	PC900 0-65	PL504 1-02	30C15/
DY86/7 0-53	EP83 1-10	PC845 0-63	PL508 1-02	PCF800 1-22
DY802 0-53	EP85 0-53	PC85 0-90	PL509 1-77	30C17 1-29
EAB080 1-16	EP86 1-80	PC88 0-86	PL509 1-77	30C18/
EB91 0-78	EP89 1-80	PC89 0-86	PL509 1-77	30C19/
ERC81 0-89	EP91 1-35	PC189 0-91	PL509 1-77	PCF805 1-29
EBF80 0-83	EP92 1-51	PCF80 0-83	PL509 1-77	30F5/EP815
EBF83 0-86	EP96 1-63	PCF82 1-37	PL509 1-77	30F5/EP815
EBF89 0-50	EP183 0-69	PCF86 0-73	PL509 1-77	30F5/EP815
EC96 0-82	EP184 0-69	PCF200 1-13	PL509 1-77	30F5/EP815
EC88 0-86	EP189 0-81	PCF201 1-13	PL509 1-77	30F5/EP815
EC90 0-94	EL34 1-03	PCF801 0-78	PL509 1-77	30F5/EP815
EC97 0-69	EL37 1-15	PCF802 0-78	PL509 1-77	30F5/EP815
EC81 0-54	EL84 0-53	PCF806 0-73	PL509 1-77	30F5/EP815
EC82 0-53	EL86 1-06	PCF200 1-13	PL509 1-77	30F5/EP815
EC83 0-53	EL95 0-78	PCF201 1-13	PL509 1-77	30F5/EP815
EC84 0-53	EL96 0-78	PCF202 1-13	PL509 1-77	30F5/EP815
EC85 0-53	EL97 0-78	PCF203 1-13	PL509 1-77	30F5/EP815
EC86 0-53	EL98 0-78	PCF204 1-13	PL509 1-77	30F5/EP815
EC87 0-53	EL99 0-78	PCF205 1-13	PL509 1-77	30F5/EP815
EC88 0-53	EL00 0-78	PCF206 1-13	PL509 1-77	30F5/EP815
EC89 0-53	EL01 0-78	PCF207 1-13	PL509 1-77	30F5/EP815
EC90 0-53	EL02 0-78	PCF208 1-13	PL509 1-77	30F5/EP815
EC91 0-53	EL03 0-78	PCF209 1-13	PL509 1-77	30F5/EP815
EC92 0-53	EL04 0-78	PCF210 1-13	PL509 1-77	30F5/EP815
EC93 0-53	EL05 0-78	PCF211 1-13	PL509 1-77	30F5/EP815
EC94 0-53	EL06 0-78	PCF212 1-13	PL509 1-77	30F5/EP815
EC95 0-53	EL07 0-78	PCF213 1-13	PL509 1-77	30F5/EP815
EC96 0-53	EL08 0-78	PCF214 1-13	PL509 1-77	30F5/EP815
EC97 0-53	EL09 0-78	PCF215 1-13	PL509 1-77	30F5/EP815
EC98 0-53	EL10 0-78	PCF216 1-13	PL509 1-77	30F5/EP815
EC99 0-53	EL11 0-78	PCF217 1-13	PL509 1-77	30F5/EP815
EC00 0-53	EL12 0-78	PCF218 1-13	PL509 1-77	30F5/EP815
EC01 0-53	EL13 0-78	PCF219 1-13	PL509 1-77	30F5/EP815
EC02 0-53	EL14 0-78	PCF220 1-13	PL509 1-77	30F5/EP815
EC03 0-53	EL15 0-78	PCF221 1-13	PL509 1-77	30F5/EP815
EC04 0-53	EL16 0-78	PCF222 1-13	PL509 1-77	30F5/EP815
EC05 0-53	EL17 0-78	PCF223 1-13	PL509 1-77	30F5/EP815
EC06 0-53	EL18 0-78	PCF224 1-13	PL509 1-77	30F5/EP815
EC07 0-53	EL19 0-78	PCF225 1-13	PL509 1-77	30F5/EP815
EC08 0-53	EL20 0-78	PCF226 1-13	PL509 1-77	30F5/EP815
EC09 0-53	EL21 0-78	PCF227 1-13	PL509 1-77	30F5/EP815
EC10 0-53	EL22 0-78	PCF228 1-13	PL509 1-77	30F5/EP815
EC11 0-53	EL23 0-78	PCF229 1-13	PL509 1-77	30F5/EP815
EC12 0-53	EL24 0-78	PCF230 1-13	PL509 1-77	30F5/EP815
EC87 0-53	EL99 0-78	PCF305 1-13	PL509 1-77	30F5/EP815
EC88 0-53	EL00 0-78	PCF306 1-13	PL509 1-77	30F5/EP815
EC89 0-53	EL01 0-78	PCF307 1-13	PL509 1-77	30F5/EP815
EC90 0-53	EL02 0-78	PCF308 1-13	PL509 1-77	30F5/EP815
EC91 0-53	EL03 0-78	PCF309 1-13	PL509 1-77	30F5/EP815
EC92 0-53	EL04 0-78	PCF310 1-13	PL509 1-77	30F5/EP815
EC93 0-53	EL05 0-78	PCF311 1-13	PL509 1-77	30F5/EP815
EC94 0-53	EL06 0-78	PCF312 1-13	PL509 1-77	30F5/EP815
EC95 0-53	EL07 0-78	PCF313 1-13	PL509 1-77	30F5/EP815
EC96 0-53	EL08 0-78	PCF314 1-13	PL509 1-77	30F5/EP815
EC97 0-53	EL09 0-78	PCF315 1-13	PL509 1-77	30F5/EP815
EC98 0-53	EL10 0-78	PCF316 1-13	PL509 1-77	30F5/EP815
EC99 0-53	EL11 0-78	PCF317 1-13	PL509 1-77	30F5/EP815
EC00 0-53	EL12 0-78	PCF318 1-13	PL509 1-77	30F5/EP815
EC01 0-53	EL13 0-78	PCF319 1-13	PL509 1-77	30F5/EP815
EC02 0-53	EL14 0-78	PCF320 1-13	PL509 1-77	30F5/EP815
EC03 0-53	EL15 0-78	PCF321 1-13	PL509 1-77	30F5/EP815
EC04 0-53	EL16 0-78	PCF322 1-13	PL509 1-77	30F5/EP815
EC05 0-53	EL17 0-78	PCF323 1-13	PL509 1-77	30F5/EP815
EC06 0-53	EL18 0-78	PCF324 1-13	PL509 1-77	30F5/EP815
EC07 0-53	EL19 0-78	PCF325 1-13	PL509 1-77	30F5/EP815
EC08 0-53	EL20 0-78	PCF326 1-13	PL509 1-77	30F5/EP815
EC09 0-53	EL21 0-78	PCF327 1-13	PL509 1-77	30F5/EP815
EC10 0-53	EL22 0-78	PCF328 1-13	PL509 1-77	30F5/EP815
EC11 0-53	EL23 0-78	PCF329 1-13	PL509 1-77	30F5/EP815
EC12 0-53	EL24 0-78	PCF330 1-13	PL509 1-77	30F5/EP815
EC13 0-53	EL25 0-78	PCF331 1-13	PL509 1-77	30F5/EP815
EC14 0-53	EL26 0-78	PCF332 1-13	PL509 1-77	30F5/EP815
EC15 0-53	EL27 0-78	PCF333 1-13	PL509 1-77	30F5/EP815
EC16 0-53	EL28 0-78	PCF334 1-13	PL509 1-77	30F5/EP815
EC17 0-53	EL29 0-78	PCF335 1-13	PL509 1-77	30F5/EP815

SEMICONDUCTORS

COMPONENTS

CARBON RESISTOR PAKS

These Paks contain a range of Carbon Resistors, assorted into the following groups:

R1	50	Mixed	100 ohms-820 ohms	0-60
			1/8th W.	
R2	50	Mixed	1K ohms-8.2 Kohms	0-60
			1/8th W.	
R3	50	Mixed	10K ohms-82 Kohms	0-60
			1/8th W.	
R4	50	Mixed	100K ohms-820 Kohms	0-60
			1/8th W.	
R5	30	Mixed	100 ohms-820 ohms	0-60
			1/4 W.	
R6	30	Mixed	1K ohms-8.2 Kohms	0-60
			1/4 W.	
R7	30	Mixed	10K ohms-82 Kohms	0-60
			1/4 W.	
R8	30	Mixed	100K ohms-820 Kohms	0-60
			1/4 W.	

THESE ARE UNREPEATABLE PRICES

LOW COST CAPACITORS

500	µF	50V Elect	0-09	each
'01	µF	400V	0-08	each

REPANCO CHOKES & COILS

RF Chokes	CH1	2.5mH	0-27
	CH3	7.5mH	0-29
	CH5	1.5mH	0-28
	CH2	5.0mH	0-25
	CH4	10mH	0-31

COILS	DRX1	Crystal set	0-29	DRR2	Dual range	0-42
-------	------	-------------	------	------	------------	------

CARBON POTENTIOMETERS

Log and Lin	4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M.	
VC 1	Single Less Switch	0-14
VC 2	Single D.P. Switch	0-26
VC 3	Tandem Less Switch	0-43
VC 4	1K Lin Less Switch	0-14
VC 5	100K Lo gant-Log	0-43

HORIZONTAL CARBON PRESETS

0-1 Watt		0-08	each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M.			

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tappings 4V, 7V, 8V, 10V, 40V, 50V and 25V-0-25V.

Type	Amps	Price	P & P
MT50/1	1	\$1.79	0-45p
MT50/2	2	\$2.24	0-45p
		\$3.98	0-60p

COIL FORMERS & CORES

NORMAN 1/4" Cores & Formers	0-07p
1/2" Cores & Formers	0-09p

SWITCHES

DP/DT Toggle	0-28p
SP/ST Toggle	0-28p

FUSES

1 1/2" and 20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A QUICK BLOW
Anti-urge 20mm only

	★0-05p	each
	★0-07p	each

VEROBORDS

VB1	containing approx. 50 sq. ins. various sizes all 0.1 matrix	★0-60p
VB2	containing approx. 50 sq. ins. various sizes all 0.15 matrix	★0-60p

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen. Full instructions supplied with each pen. ★0-82p

BATTERY HOLDERS

Takes 6 H.P. 7s complete with terminal clip and lead ★0-81p each

CABLES

CP 1	Single lapped screen	Per Metre	★0-08
CP 2	Twin Common Screen		★0-11
CP 3	Stereo Screened		★0-12
CP 4	Four Core Common Screen		★0-21
CP 5	Four Core individually screened		★0-28
CP 6	Microphone Fully Braided Cable		★0-11
CP 7	Three Core Mains Cable		★0-11
CP 8	Twin Oval Mains Cable		★0-08
CP 9	Speaker Cable		★0-06
CP 10	Low Loss Co-Axial		★0-14

INSTRUMENT CASES



(In 2 sections, Black Vinyl covered top and sides and base)

No.	Length	Width	Height	Price
BV1	8"	5 1/2"	3"	★1-25
BV2	11"	6"	3"	★1-62
BV3	6"	4 1/2"	1 1/2"	★0-92
BV4	9"	5 1/2"	2 1/2"	★1-39

ALUMINIUM BOXES

No.	Length	Width	Height	Price
BA1	5 1/2"	3 1/2"	1 1/2"	★0-45
BA2	4"	4"	1 1/2"	★0-45
BA3	4"	2 1/2"	1 1/2"	★0-45
BA4	5 1/2"	4"	1 1/2"	★0-54
BA5	4"	2 1/2"	2 1/2"	★0-45
BA6	3"	2"	1"	★0-39
BA7	7"	5"	2 1/2"	★0-79
BA8	8"	6"	3"	★1-02
BA9	6"	4"	2"	★0-85

(Each complete with 1/4" deep lid & screws)
PLEASE ADD 20p POSTAGE AND PACKING FOR EACH BOX.


COMPONENT PAK

Pak No.	Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0-60
C2	150	Capacitors mixed values approx. count by weight	0-60
C3	50	Precision Resistors mixed	0-60
C4	75	1/8th width Resistors mixed preferred values	0-60
C5	5	Pieces assorted Ferrite Rods	0-60
C6	2	Tuning Gangs, MW/LW VHF	0-60
C7	1	Pak Wire 50 metres assorted colours	★0-80
C8	10	Reed Switches	0-60
C9	3	Micro Switches	0-60
C10	15	Assorted Pots & Pre-Sets	0-60
C11	5	Jack Sockets 3 x 3.5m, 2 x standard Switch Type	0-60
C12	30	Paper Condensers preferred types mixed values	0-60
C13	20	Electrolytic Trans. types	0-60
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets, etc.	0-60
C15	5	Mains Slide Switches, 2 Amp	0-60
C16	30	Assorted Tag Strips & Panels	0-60
C17	10	Assorted Control Knobs	0-60
C18	4	Rotary Wave Change Switches	0-60
C19	2	Relays 6-24V Operating	0-60
C20		Sheets Copper Laminate approx. 200 sq. ins.	★0-80

Please add 20p post and packing on all component packs, plus a further 10p on pack nos. C1, C2, C19 & C20.

AVDEL BOND

SOLVE THOSE STICKY PROBLEMS!
with

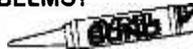

CYANOACRYLATE C2 ADHESIVE

The wonder bond which works in seconds—bond plastic, rubber, transistors, components permanently, immediately

OUR PRICE ONLY 60p for 2gm phial

BIB HI-FI ACCESSORIES

Ref.	Description	Price
B	Stylus and turntable cleaning kit	★31p
J	Tape head cleaning kit	★30p
P	Hi-Fi cleaner	★80p
9	Wire stripper/Cutter	★94p
31	Cassette head cleaner	★58p
32	Tape editing kit	★21.94
32A	Stylus balance	★12.94
36A	Record stylus cleaning kit	★39p
42	De Luxe Groov-Kleen	★21.94
43	Record care kit	★26.88
45	Auto changer groove cleaner	★88p
46	Spirit level	★68p
60	Hi-Fi stereo hints & tips	★88p
60	Chrome finish as above	★21.72

ANTEX EQUIPMENT

SOLDERING IRONS

X25	25 watt	★25-45
Model G	18 watt	★23-70
CCN 240	15 watt	★29-90
SK2	Soldering Kit	★33-90

BITS AND ELEMENTS

Bit No.	Price
102 for model CN240 3/32"	★42p
104 for model CN240 3/16"	★42p
110 for model CCN240 3/32"	★42p
1101 for model CCN240 3/16"	★42p
1102 for model CCN240 1/4"	★42p
1020 for model G240 3/32"	★42p
1021 for model G240 1/8"	★42p
1022 for model G240 3/16"	★42p
50 for model X25 3/32"	★1-35*
51 for model X25 1/8"	★1-35*
52 for model X25 3/16"	★1-35*

ELEMENTS

Model ECN 240	★1-10*
Model ECG 240	★1-35*
Model ECC 240	★1-55*
Model EX 25	★1-20*

SOLDERING IRON STAND

ST3 Suitable for all models	★1-10
Antex heat shunt	10p

PLUGS

PS 1	D.I.N. 2 Pin (Speaker)	0-10
PS 2	D.I.N. 3 Pin	0-11
PS 3	D.I.N. 4 Pin	0-14
PS 4	D.I.N. 5 Pin 100°	0-16
PS 5	D.I.N. 5 Pin 240°	0-16
PS 6	D.I.N. 6 Pin	0-18
PS 7	D.I.N. 7 Pin	0-17
PS 8	Jack 2.5mm Screened	0-17
PS 9	Jack 3.5mm Plastic	0-17
PS 10	Jack 3.5mm Screened	0-11
PS 11	Jack 1/2" Plastic	0-14
PS 12	Jack 1/2" Screened	0-20
PS 13	Jack Stereo Screened	0-38
PS 14	Phono	0-06
PS 15	Car Aerial	0-14
PS 16	Co-Axial	0-14

INLINE SOCKETS

PS 21	D.I.N. 2 Pin (Speaker)	0-13
PS 22	D.I.N. 3 Pin	0-12
PS 23	D.I.N. 5 Pin 180°	0-18
PS 24	D.I.N. 5 Pin 240°	0-18
PS 25	Jack 2.5mm Plastic	0-15
PS 26	Jack 3.5mm Plastic	0-15
PS 27	Jack 1/2" Plastic	0-18
PS 28	Jack 1/2" Screened	0-32
PS 29	Jack Stereo Plastic	0-28
PS 30	Jack Stereo Screened	0-38
PS 31	Phono Screened	0-17
PS 32	Car Aerial	0-10
PS 33	Co-Axial	0-20

SOCKETS

PS 35	D.I.N. 2 Pin (Speaker)	0-07
PS 36	D.I.N. 3 Pin	0-09
PS 37	D.I.N. 5 Pin 180°	0-09
PS 38	D.I.N. 5 Pin 240°	0-10
PS 39	Jack 2.5mm Switched	0-11
PS 40	Jack 3.5mm Switched	0-11
PS 41	Jack 1/2" Switched	0-19
PS 42	Jack Stereo Switched	0-28
PS 43	Phono Single	0-07
PS 44	Phono Double	0-09
PS 46	Co-Axial Surface	0-09
PS 47	Co-Axial Flush	0-19

P.C.B. KIT

PROFESSIONAL D.I.Y. PRINTED CIRCUIT KIT

PRICE £7-80
Containing 6 sheets of 6" x 4" single sided laminate, a generous supply of etchant powder, etching dish, etchant measure, tweezers, etch resistant marking pen, high quality pump drill with spares, cutting knife with spare blades, 6" metal ruler, plus full easy to follow instructions.

LOW-NOISE CASSETTES

C60		★33p
C90		★44p
C120		★58p
2 x quality marker pens, specifically		
..... line etchant		
resistant circuits on copper laminate.		
Complete with full instructions.		
		★1-53 per pair

AUDIO LEADS

S221	5 pin DIN plug to 4 phono plugs length 1.5m	★1-08
S222	5 pin DIN plug to 5 pin DIN socket length 1.5m	68p
S237	5 pin DIN plug to 5 pin DIN plug mirror image length 1.5m	★1-20
S238	2 pin DIN plug to 2 pin DIN socket length 5m	68p
S268	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 length 1.5m	★1-00
S270	2 pin DIN plug to 2 pin DIN socket length 10m	80p
S271	5 pin DIN plug to 2 phono plugs connected to pins 3 & 5 length 1.5m	68p
S275	5 pin DIN plug to 2 phono sockets connected to pins 3 & 5 length 23cm	68p
S318	5 pin DIN socket to 2 phono plugs connected to pins 3 & 5 length 23cm	68p
S404	Coiled stereo headphones extension cord extends to 7m	★1-40
S217	3 pin DIN plug to 3 pin DIN plug length 1.5m	80p
S219	5 pin DIN plug to 5 pin DIN plug length 1.5m	80p
S474	3.5mm Jack to 3.5mm Jack length 1.5m	68p
S600	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m	80p
S700	5 pin DIN plug to 3.5 Jack connected to pins 1 & 4 length 1.5m	80p

CROSSOVER NETWORK

K4007 1/P Impedance 8 ohms. Insertion Loss 3dB. Crossover Frequency 3 KHz. PRICE £1-12

H/PHONE JUNC. BOX

H1012 Enables change-over from loud (3-way) speaker to headphone listening. Also has a centre position for both outputs. PRICE £1-73

ALL PRICES EX
PLEASE ADD VAT
ITEMS EXCEPT THOSE
MARKED

GIRO NUMBER OR
383-7005

Postage & Packing
Add extra for airmail

HANDBOOKS

TRANSISTOR DATA BOOK
DTE 1 227 Pages packed with information on European Transistors. Full specification including outlines. Price £2-95 each

TRANSISTOR EQUIVALENT BOOK
BPE 75 256 Pages of cross references and equivalents for European, American and Japanese Transistors. This is the most comprehensive equivalents book on the market today and has an introduction in 13 languages. Price £2-68 each

DIODE EQUIVALENT BOOK
DE 74 144 Pages of cross references and equivalents for European, American and Japanese Diodes, Zeners, Thyristors, Triacs, Diacs and L.E.D.s. Price £1-98 each

MULLARD DATA BOOK 1974/75
MDB 74 The latest edition of this popular handbook contains information on Semiconductors, Integrated Circuits, Television Picture Tubes, Valves, Capacitors and Resistors. Included in the 161 informative pages are 21 pages on Semiconductor Comparables. Price £0-40 each

TTL DATA BOOK
DIC 75

PO BOX 6 WARE HERTS



AL 60

50w. PEAK (25w. R.M.S.)

ONLY £3.95

● Max Heat Sink temp 90°C. ● Frequency Response 20Hz to 100K Hz. ● Distortion better than 0.1 at 1KHz. ● Supply voltage 15-50 volts. ● Thermal Feedback. ● Latest Design Improvements. ● Load—3, 4, 5 or 16 ohms. ● Signal to noise ratio 80dB. ● Overall size 63mm x 105mm x 13mm. Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

STABILISED POWER MODULE SPM80



SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems. Public Address Intercom Units, etc. Handbook available 10p.

PRICE £3.00

TRANSFORMER ER BMT80 £2.60

STEREO PRE-AMPLIFIER TYPE PA100



Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls. PRICE £13.20

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets.

COMPLETE PRICE: £27.35 plus 45p postage

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16½" x 11½" x 3½", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets, etc.

KIT PRICE: £9.20 plus 45p postage

STEREO 30 COMPLETE AUDIO CHASSIS


7 + 7 WATTS R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This with only the addition of a transformer or overwind, will produce a high quality audio unit suitable for use with a wide range of inputs, i.e. high quality ceramic pickup, stereo tuner, stereo tape deck, etc.

Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse and fuse holder and universal mounting bracket, enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available.

Ideal for the beginner or advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty. Can be installed in 30 mins.) PRICE: £15.75 plus 45p postage and packing. TRANSFORMER: £2.45 plus 45p postage and packing. TEAK CASE: £3.65 plus 45p postage and packing.

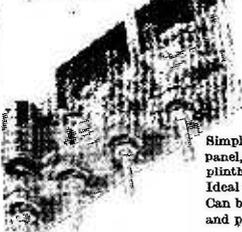INCLUDE VAT
AT 25% TO ALL
★ ADD 8%
≠ NO VAT
and 20p overseas
Minimum order 75p



SPEAKERS

E.M.I. LEK 350 Loudspeakers Enclosure Kit in teak veneer, including speakers. Rec. Retail Price £45.50 per pair. OUR SPECIAL PRICE £27.75 per pair — P. & P. £3.

AL10/AL20/AL30

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home. AL10 £2.30, AL20 £2.65, AL30 £2.95.

M.P.A.30

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new Bi-Pak M.P.A.30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

Used in the construction are 4 low noise, high gain, silicon transistors. It is provided with a standard DIN input socket for ease of connection.

Supplied with full, easy to follow instructions. PRICE £2.65

STORAGE/CARRIAGES ★

RECORD CASES

7 in E.P. 18½ in x 7 in x 8 in (50 records) ★£2.48
12 in L.P. 13½ in x 7½ in x 12½ in (50 records) ★£3.30

CASSETTE CASES

Holds 15. 10 in x 3½ in x 5 in. Lock and handle. ★£1.50

8-TRACK CARTRIDGE CASES

Holds 14. 13 in x 5 in x 6 in. Lock and handle ★£2.20
Holds 24. 13½ in x 8 in x 5½ in Lock and handle ★£3.20

CARTRIDGES

ACOS		
GP91-1SC	200mV at 1.2cms/sec	£1.11
GP93-1	280mV at 1cm/sec	£1.43
GP96-1	100mV at 1cm/sec	£2.81
TTC		
J-2005	Crystal/Hi Output	97p
J-2010C	Crystal/Hi Output Compatible	£1.11
J-2006S	Stereo/Hi Output	£1.52
J-2105	Ceramic/Med. Output	£1.81
J-2203	Magnetic 5mV/5cm/sec. including stylus	£4.78
J-2203S	Replacement stylus for above	£2.88
AT-55	Audio-technica magnetic cartridge 4mV/5cm/sec	£3.06

DYNAMIC MIC'PHONE

TYPE B1223. 200 ohms impedance. Complete with stand, on/off switch and 2.5mm and 3.5mm plugs. Suitable for cassette tape recorders. PRICE £1.67

JUST OUT!

STEREO FM TUNER

WRITE NOW FOR FULL DETAILS

Making Life Easier

THE 'heart' of the many constructional projects that appear month by month in this magazine is a circuit board design in one form or another.

Breadboard type wiring still remains a firm favourite with many constructors, both in the home and the workshop. For those constructors and designers that have the technical expertise and patience, the breadboard method is often the first design approach to many constructional projects.

When the constructor has completed the project—and possibly spent much time in carefully checking the wiring and assembly for possible mistakes, he will—with tongue in cheek—switch on! With breadboard wired projects it is quite easy to have built-in faults, overlook them on the final check and then switch on—often with disastrous results.

Where the constructional project is complex and a considerable amount of wiring interconnection is required, certainly the possibility of multiple wiring errors increases.

The printed circuit board, more commonly referred to as the 'p.c.b.' was introduced into the electronics industry many years ago and is now extensively used. The printed circuit board has numerous advantages—elimination of wiring errors; consistent and accurate reproduction of the 'circuit' wiring; uniformity of performance in multiple assembly work plus considerable saving in costs and assembly time.

The printed circuit board therefore, has many advantages for the home constructor and this has been confirmed by its use in the many constructional projects that have been featured in *Practical Wireless* over many years.

Practical Wireless intends to introduce a p.c.b. service whereby the printed circuit boards for selected P.W. constructional projects will be made available to readers and advertisers. There is no doubt whatsoever that the inclusion of this service will encourage many readers, who in the past, may have been reluctant to 'have a go' at constructional projects because of the wiring complexity.

We confidently anticipate—from the results of our p.c.b. survey—that this move will be widely welcomed. An announcement will be made in the November 1975 issue of this magazine, giving full details of the P.W. p.c.b. SERVICE to readers.

LIONEL E. HOWES, Editor

We welcome articles for publication on all aspects of electronics. They may either be handwritten or typed. However simple or complex your idea may appear, let us have brief details. We are prepared to pay for articles upon acceptance in certain instances and letters upon publication. Why not drop the Editor a line?

Once again it is regretted that due to increased paper and production costs, the price of this magazine will be increased to 35p with effect from the November issue

NEWS...

Forthcoming event

"How do we communicate . . . and some of the consequences?"

AN External Studies Course of nine lectures has been organised at the University of Kent, Canterbury, under the direction of Dr. K. L. Smith. The first talk will be at 7 p.m. on Thursday, 16 October, 1975. The fundamentals of modern Electronics communication systems and techniques will be discussed and demonstrated during the course, by various lectures. The final two lectures will deal with some political and social questions arising from the vast increase of information communicated by technical means.

For further information, contact Dr. A. T. Barbrook, External Studies Office, Rutherford College, University of Kent, Canterbury, Kent, CT2 7NT or Dr. K. L. Smith of the Electronics Laboratory.

BBC Stereo for the North East

THE BBC has announced the start of stereo transmissions from the Pontop Pike transmitting station. This brings the stereo services of Radios 2, 3 and 4 to some two and a half million people in Northumberland, Durham, Cleveland and North Yorkshire.

The stereo services are also rebroadcast from the Weardale and Whitby relay stations, but the quality and consistency of these transmissions will not be known until certain tests have been carried out.

BBC stereo is brought to Pontop Pike on a new programme link using pulse code modulation which, in addition to providing high-quality stereo, will mean better sound quality for mono listeners also.

Good progress is being made on the next extension of BBC stereo, to the Sandale station in Cumbria. It is hoped that an announcement about the opening of these services will be made in a few weeks' time.

Longleat mobile rally

THE City of Bristol RSGB Group held its Longleat Mobile Rally on Sunday June 29th 1975.

This year's event, the 18th, attracted an attendance of over 5,000, 4,123 signing in on arrival. A count of vehicles at 1430hrs was 2,166 with 12 coaches, there being 50 tents and caravans with visitors camping overnight.

The dealers, of which there were 27, reported complete satisfaction and brisk trading.

The GPO provided a TV Detector Van and their officers explained very fully how they carry out the detection of TV sets. The 30th Regiment of the Royal Signals provided an exhibition showing the means of communications now used in the armed service and provided a lot of fun for the juniors who were able to use portable equipment for talking to one another. Members of the Royal Navy ARS and the RAF-ARS were present to meet mem-

bers of their societies also the ARMS and the British Red Cross who look after the medical side at the rally each year.

Visitors to the rally came from England, Scotland and Wales also countries outside Great Britain. These included: 9GILZ, HB9AZX, F6DCW, VK3YET, VK6ZFL, VE6-ANO, WB2WOZ, ZD7PS.

The raffle was one of the main attractions, all tickets were sold and the 128 prizes were won and collected by the winners.

Talk-in facilities were operational on 160metres, 80metres and 2metres from 1000hrs and were in continual action. 160metres had 22 contacts, 80metres 40 contacts and 2metres 116 contacts which seems to speak for itself that many are changing over to 2 metres for mobile working.

The DF hunt being a walking one within the grounds of the rally proved a great success and drew a large entry, the winner finding the station in 12 minutes.

BBC Carlisle

TWO new low-power medium-wave transmitters at Brisco, Carlisle, started transmissions recently. One, on 285 metres (1052 kHz), provides Carlisle with an improved Radio 4 service, particularly at night when the service from Stagshaw (330 metres) is poor; the other carries BBC Radio Carlisle on 397 metres (755kHz) giving slightly better coverage than the temporary transmitter which it replaces.

Both transmitters serve an area to about 25 miles from Carlisle in the daytime but at night this distance is considerably reduced by interference.

The Radio 4 and BBC Radio Carlisle services on VHF from Sandale and the medium-wave BBC Radio Carlisle service from Whitehaven are unaffected by these changes.

Books received

Electronics — An Elementary Introduction for Beginners (S.I. Units)

By L. W. Owers C. Eng MIERE
Basic introduction to electronics for those meeting the subject for the first time.
£1.45

Publications Mailing Service, P.O. Box 6, Crawley, Sussex, RH10 6LH

Modern Crystal and Transistor Set Circuits for Beginners

By B. B. Babani
Brief constructional articles ranging from a crystal set to a two-transistor reflex receiver.
Price 35p

Babani Press & Bernards (Publishers) Limited, The Grampians, Western Gate, Shepherds Bush, London, W6 7NF

Beginners Guide To Transistors (2nd Edition)

By J. A. Reddihough and I. R. Sinclair

Takes reader from basics on how semiconductor work through audio frequency circuits and techniques, integrated circuits and finally some hints for fault-finding and servicing.
Price: £1.80

Butterworth Group, 88 Kingsway, London, WC2B 6AB

Component Show

THE 24th international London Electronic Component Show held at Olympia earlier this year defied the pundits of gloom and doom. Nearly 20,000 people including visitors from 61 different countries attended the show and though the overall figure was down on the 1973 LECS, trading and business conducted during the four-day event exceeded both expectation and previous records.

Chairman of the Radio and Electronics Manufacturers Federation Exhibition Committee, Mr. Sydney Brewell, MBE, echoed the sentiments of exhibitors when he said the 24th LECS had produced a "very high quality in terms of visitors despite the economic climate. Inquiries have been realistic and should result in considerable tangible trading in the future. From abroad interest has been particularly notable from Spain and Scandinavia. Generally exhibitors have been well satisfied with results and we can now look ahead with renewed

enthusiasm to the 25th international London Electronic Component Show to be held at Olympia from May 17-20, 1977."

On the AEG-Telefunken (U.K.) Limited's stand, Mr. Claud Cheeley, Sales Executive, reported the inquiry level high despite the lower attendance. He said that "the people who have attended have had a direct need for technical knowledge and have not been the casual peruser. We have been extremely busy and have taken some orders of real significant values".

The 24th London Electronic Component Show was sponsored by the Radio and Electronic Component Manufacturers Federation and organised by Industrial and Trade Fairs Limited.

"Radio Exchange"

Due to a printing error, the above advertiser's full-page advertisement space which appeared in the August issue, is incorrect. Prices quoted were at the old VAT rate. We apologise to all our readers for any inconvenience caused.

AMONG the most popular of all projects for the home constructor is the relatively simple transistor superhet short wave receiver. While most of these receivers have adequate sensitivity, their performance in other respects is often not all one would wish. The simple circuitry employed usually results in poor cross-modulation performance, poor image rejection and wide IF bandwidth.

The first two problems are not usually too bothersome and the use of an ATU and aerial attenuator can make a significant improvement in performance here. The last one can place severe limitations on the receiver, with today's crowded band conditions, and it can be difficult to radically improve the selectivity as this means adding some form of IF filter to the receiver. Some excellent filters are now available, but it is not always feasible to add such a filter due to lack of space in the receiver, and sometimes to lack of funds, as a good IF filter could easily cost more than the rest of the receiver!

of the coil. The quality of a parallel tuned circuit is termed 'Q', and is defined as the reactance of the inductor divided by the circuit resistance (XL/R).

The basic operation of a Q multiplier is shown in Fig. 1. At or near resonance the tuned circuit will exhibit relatively high impedance and, in consequence, will have little effect on the receiver. At frequencies significantly different from the resonant frequency its reactance will be low and signals at these frequencies will be attenuated by being shunted to earth. As the Q of the coil is not very high (about 100-150) it will not alter the receiver's IF passband a great deal on its own.

However, the tuned circuit is connected in an amplifier circuit which is used to apply positive feedback. A variable resistor or other circuit element enables the feedback level to be controlled. The purpose of adding the feedback is to sample and amplify a small amount of the signal in the tuned

ADD-ON Q MULTIPLIER


R.A.PENFOLD

Fortunately, there is a simple device known as a "Q Multiplier" which is inexpensive to construct and can be built as an external accessory to the receiver, thus needing no space inside the set. If space is available, it can be added inside the receiver. Such a unit gives a bandwidth which is variable from the normal IF bandwidth of the receiver, for the reception of good quality AM, to a very narrow peaked response, for the reception of CW. This is unlike other types of IF filter, normally designed for only one mode of reception.

CIRCUIT DESIGN

Basically a Q multiplier consists of a parallel tuned LC circuit resonant at the IF, connected between the tap on the primary of the first IFT and the chassis of the receiver. The tuned circuit theoretically has an infinite impedance at its resonant frequency, with a fairly low impedance at other frequencies.

This does not occur in practice as losses in the resistance of the coil have the effect of reducing the resonant impedance and broadening the bandwidth. If the signal in the circuit is coupled to an amplifier, as is the output of an IFT, this will have a damping effect on the quality of the tuned circuit. The quality of an unloaded tuned circuit will obviously be determined by the circuit resistance. The lower this resistance, the higher the quality

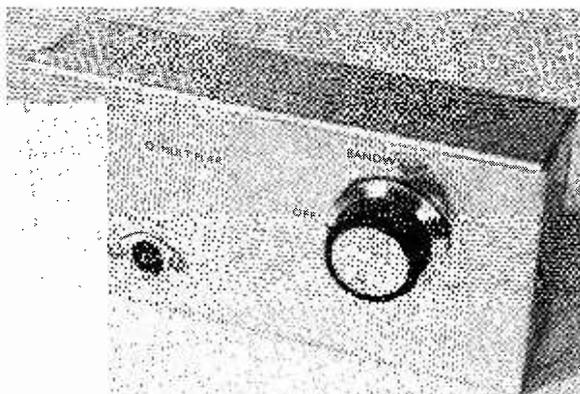

circuit and then to feed a controlled amount of this back to the tuned circuit. If we feed back to the circuit the same amount of signal as is lost due to circuit resistance, we will have the idealised tuned circuit with an infinite Q. This will then shunt to earth all signals except those very close to its

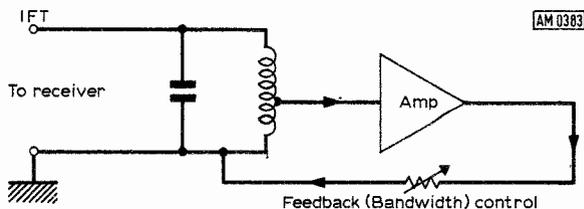


Fig. 1: Simple circuit to illustrate the operation of a Q-multiplier.

resonant frequency and this will result in the receiver having a very narrow bandwidth. The feedback control can be adjusted to give the coil any apparent Q higher than its actual Q value acting as a selectivity control for the receiver.

CONSTRUCTION

The circuit diagram of a very simple Q multiplier for use with an IF in the range 455 to 470kHz is shown in Fig. 2. This is basically the earthed base Colpitts oscillator with the feedback level controlled by VR1. The output of the unit is taken to SK1, a coax socket, via C4, a blocking capacitor.

The unit described is an independent unit external to the receiver, but decoupling components R6 and C1 are included so that the unit can be built into a receiver, obtaining its power from the receiver. Note that the parallel capacitor of L1 is part of the coil unit, as is its secondary winding, which is not used.

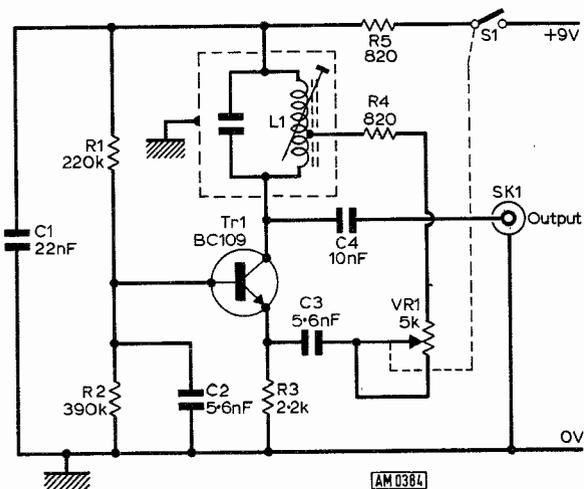


Fig. 2: above, circuit of the Q-multiplier described in the article. If the unit is fitted inside a receiver the output can go direct to the IFT, eliminating the socket. Fig. 3: right, shows the PCB and component layout. Plain veroboard with pins would be equally effective.

With the exception of the battery and SK1 all the components are mounted on a small PCB measuring 70 x 38mm (2¾ x 1½in). The copper backing pattern and components layout of the board are shown actual size in Fig. 3. The board is etched and drilled in the usual way. Before soldering VR1 to the PCB bend its connecting lugs so that they are at right angles to its spindle. It is then soldered to the panel so that when one is viewing it end on to the spindle, one can see the copper side of the PCB, see photograph. If it is connected the other way round it will not be possible to fit the unit in its case.

When all the components have been mounted the insulated lead between S1 and R6 on the PCB can be connected, as can the battery clip leads. Two insulated leads are connected to the board to form the leadouts to SK1.

The box used to house the unit is a commercially made one measuring 145 x 70 x 38mm (5¾ x 2¾ x 1½in). This has a removable lid which, in this application, becomes the front panel. Any similar box can be used as a housing for the unit provided it is metal and not plastic.

The layout has VR1 mounted towards the top RH

★ components list

Resistors



R1 220kΩ	R3 2.2kΩ	R5 820Ω
R2 390kΩ	R4 820Ω	VR1 5kΩ with S1
All resistors ½ or ¼W 10%		

Capacitors

C1 22nF plastic foil	C3 5.6nF polystyrene
C2 5.6nF polystyrene	C4 10nF ceramic, etc.

Miscellaneous

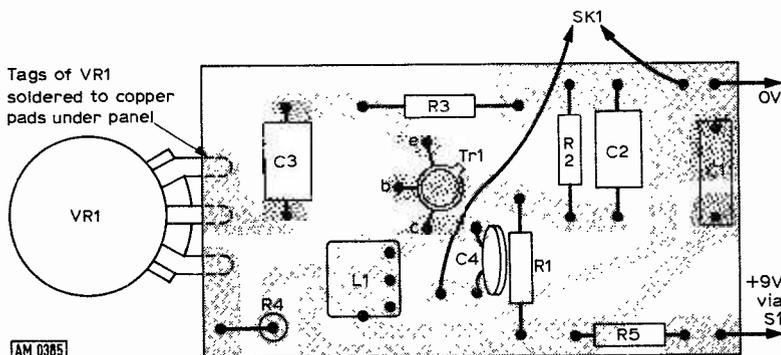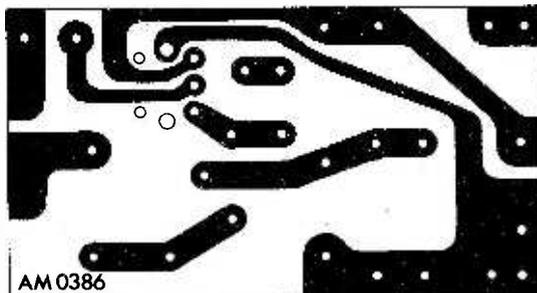Tr1, BC109. L1, Toko YHCS1A590R (Ambit Int.) or similar. Aluminium box, 145 x 70 x 38mm (5¾ x 2¾ x 1½in) or similar. PP3 battery and clips. PCB, see text. Coax socket. Coax cable and plugs.



side of the front panel with SK1 at the bottom left. The PCB is mounted on VR1. Some foam rubber can be used to hold the battery firmly in position in the case. When VR1, and SK1 have been mounted on the front panel the free ends of the leads connecting the PCB to SK1 can be cut to length and soldered to SK1.


RECEIVER MODIFICATIONS

The only modification required to the receiver is to fit a coax socket at some convenient point on the chassis. A length of coax cable is then used to connect this to the tap on the primary of the first IFT. The outer braiding of the cable is connected to the chassis. The author's receiver uses Denco transistor coils and with receivers of this type it is probably easiest to connect the coax inner to pin 8 of the Red oscillator coil (which is normally connected to

trimming tool, so as not to damage the core. If advancing VR1 still further produces this effect once again, then the core of L1 must again be adjusted to correct the tuning. The unit is then ready for use.

The further the control knob of VR1 is advanced the narrower the bandwidth of the receiver. This is true up to the point where there is sufficient feedback to cause the Q multiplier to break into oscillation. VR1 should always be kept below this point, as proper reception of AM and SSB is not possible with the circuit in this state.

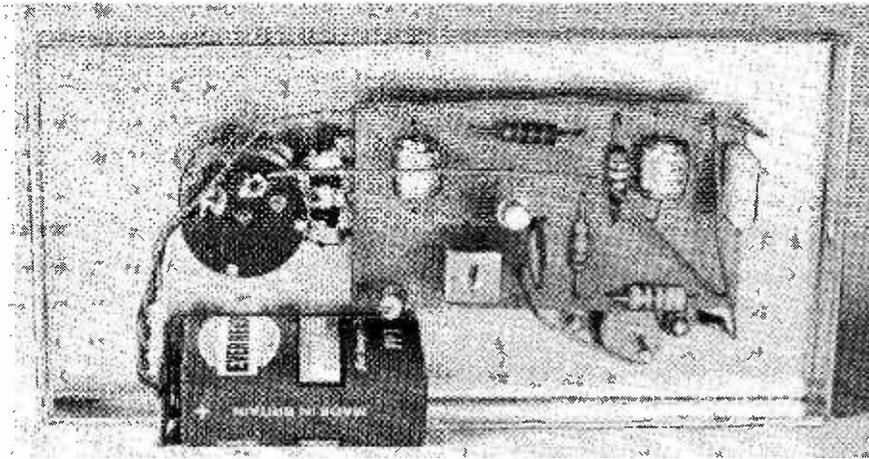For each reception mode aim at using the minimum bandwidth that gives an audio signal of satisfactory quality. In this way adjacent channel interference will be at a minimum. With VR1 adjusted for fractionally less than the minimum obtainable bandwidth, it will be found that AM cannot be received in the normal way. It can be received, however, by tuning the receiver slightly



The PCB is soldered to the tags on the bandwidth control which is fitted to the panel of the box.

the primary tap on the first IFT). A coax lead having a plug at each end is used to connect the Q multiplier to the receiver. Both coax leads should be as short as possible, only about 300mm or so long in total. If they are longer the capacitance of the cables may upset the IFT so that adjustment of its core will not give sufficient tuning adjustment to permit re-alignment.

ADJUSTMENT

Initially the unit should be removed from its box so that the core of L1 is accessible. Connect the unit to the receiver and re-align the first IFT. Tune to any broadcast station of reasonable strength giving a constant signal strength tuning as accurately as possible. If the Q multiplier is now turned on the receiver should operate in much the same way as it did before, until VR1 is advanced. If the core of L1 needs no adjustment (unlikely), as VR1 is advanced the audio signal from the receiver will lose the treble frequencies and, if advanced far enough, the middle frequencies as well. It is more likely though that as VR1 is advanced it will produce an effect similar to that obtained if the tuning of the receiver were slightly altered. This can be corrected by adjusting the core of L1 with a proper

either side of the central tuning position, so that one or other of the sidebands is received. This is very useful when conditions are noisy or if there is a heterodyne interfering with one sideband of the desired transmission.

A little experience will probably need to be gained with the unit before its full worth is realised, and then the unit should be found to be well worth the initial outlay.

PW

NEXT MONTH! FREE!

SUPPLEMENT No. 2

ON

SIMPLE HOME PROJECTS

Don't miss the

**NOVEMBER
issue**

HOTLINES

ON RECENT DEVELOPMENTS

OH! MY BACK!

PAIN is one of the unpleasant facts of life which everybody has suffered at one time or another and in varying degrees. Wouldn't it be nice if we could have a little switch somewhere so that when we got fed up with the pain we could simply turn the switch to "off" and stop it?

Things haven't quite come to that—yet, but the electronics and medical professions are working on it and have come a long way. The very latest item to emerge is the Stimtech EPS Mini Stimulator. This takes the form of a small (about two cigarette packets size) unit weighing only 340gm (12oz) complete with internal batteries. With this device it is claimed that you can control pain to a certain extent. More exactly, you don't control the actual pain itself but you can "block off" the connection between the pain and the "you" that feels it.

Small electrodes are attached to the skin (not surgically, just held in contact). Electrical impulses generated by the Mini Stimulator are then used to block the transmission of the pain messages through the nerve fibres. This is done by stimulating other fibres associated with the message carrying ones.

The Mini Stimulator cannot cure an ailment. What it does do is to "kill" the pain so that a happier, and in many cases, more active and useful life can result.

On test in America, electrical stimulation of this type was tried on a group of people suffering from chronic back troubles. Success in relieving the suffering was achieved



The Mini Stimulator—a small electronic unit which is used to block pain.



A new type of solar cell, 1cm. in diameter which produces 10W of electrical power. Sunlight is focused on to the cell by means of a concave reflector.

in 80% of the cases. In other tests, post-operative complications from abdominal surgery were reduced by an impressive amount—from one in three, to one in sixteen.

Sorry—you cannot go out and buy one and the British source of these units will only supply them on the recommendation and under the supervision of the medical profession. Cost, is £95 plus VAT.

SOLAR ENERGY

The search for a cheap and efficient form of energy continues. Solar cells are, of course, an obvious choice for future development. One American company has just launched an interesting solar cell which seems to be a giant step forward. One of the company's directors claims, "Other solar energy materials require 1,000 times the surface area to produce the same amount of energy". The new cell measures only about 1cm in diameter but it gives 10 watts of electricity directly from sunlight. The cells can be series connected. Larger series can be connected to give megawatt systems says the company.

Whilst most solar cell research to date has concentrated on silicon-based systems, these new cells are made from gallium arsenide. Secret of the system is to concentrate the sun's rays on the cell with a concave reflector.

It is interesting to note that the Plessey Company in England did similar work a year or two back but nothing further has been officially

announced. The U.S. company is already talking about arrays of cells, each cell with its own reflector, which would rotate to follow the sun. By doing this 40% more sunlight can be utilized compared to a flat, immovable panel of cells.

BEAMOS

You've heard of CMOS, but what about BEAMOS? It's for real and it stands for BEam Addressed Metal Oxide Semiconductor. An electron beam is used for access, and a special semiconductor target employed for very high density storage. The result is a semiconductor memory which is almost unbelievable. The first BEAMOS module (for military applications) has an access time of 30 millionths of a second and a transfer rate of ten million bits per second. The memory is capable of storing 32 million bits of information and the manufacturers reckon that the system could be made to store a million million bits.

Sixteen or more BEAMOS modules could be linked to provide 500 million bits of memory and such a system could be arranged to provide data transfer rates of 160 million bits per second.

Ginsberg

TELE-TENNIS

BALL SPEED CONTROL

R.S.GIRDWOOD

THE modifications to be described convert the Tele-Tennis game described in this magazine into a more interesting and skilful game.

MOD 1: BAT ANGLES

It was thought desirable to have the ball travel up the screen when the top of the bat was hit, and down when the bottom of the bat was hit. This gives the player the opportunity to direct the vertical direction of the ball.

MOD 2: VERTICAL SPEED CHANGE

As the horizontal speed of the ball is constant, any vertical speed change will vary the angle of the ball with respect to the horizontal.

The circuit produces a random vertical speed change so that the ball rebounds at different angles making it more difficult to assess the ball bat intersection point.

Both modifications fit on one printed circuit board which will fit "piggy-back" over one of the other boards. Of course, either or both modifications may be built with any surplus printed circuit board.

BALL ANGLE CIRCUIT

The circuit for the vertical ball direction change, when the ball hits the top or bottom bases is the same as the original but the ball/base gates are now type 7403 (open collector 7400) which allows several gates to be Wired-ored. The complete circuit is shown in Fig. 1.

A negative-going pulse on pin 13 IC7 sets the latch (IC7a and b) so that the ball goes up, and a negative-going pulse on pin 9 IC7 resets it for down. This latch is used instead of IC8 on board A. This 7400 can be used as IC14 on board D.

As the circuitry for both bats is the same, only the left bat will be described.

In order to detect where the ball hits the bat it is necessary to split the bat in half vertically. The

positive-going vertical "left bat" signal is inverted and triggers a monostable IC5, the timing of which is approximately half the vertical bat time.

The output of the monostable (normally 0 going to 1) is fed to pin 13 IC6 and in its inverted form to pin 10 IC2.

If a ball-hit-bat pulse (normally 0 going to 1) from IC14 board B arrives at pin 12 IC6 during this period, a negative-going pulse will appear at pin 11 IC6 setting the latch to the "ball up" position.

After the monostable time ends a 1 will be present on pin 10 IC2. As the vertical bat signal is still 1 (the remaining half of the bat), pin 8 IC2 goes to 0 and pin 6 IC2 to a 1. If the "ball-hit-bat" pulse arrives during this period a negative-going pulse will appear on pin 8 IC6 setting the latch in the "ball down" position. Therefore, the ball travels up the screen if the top of the bat is hit (monostable output) and down if the bottom is hit (vertical bat signal less the monostable output), plus, of course, the usual base/ball directions.

VERTICAL BALL SPEED CHANGE CIRCUIT

In order to effect a vertical speed change it is only necessary to switch a preset resistor in parallel with the "set speed" preset in the vertical integrator circuit on board D. The best time to achieve a speed change is when the ball hits the top/bottom base or bat.

The inputs to the vertical direction latch are normally 1 going 0 whenever a base or bat is hit. These two signals are fed to pin 1 and 2 IC8 and produce a positive-going signal on pin 3 IC8 when the top/bottom base is hit or any bat is hit, top or bottom.

The output of a multivibrator running at several kilohertz (the other two gates of IC1) is fed to pin 9 IC8 and in an inverted form to pin 13 IC8.

The positive-going pulse from pin 3 IC8 is fed to pins 10 and 12 IC8.

Now, depending on the output state of the multivibrator, when a pulse arrives from pin 3 IC8, either pin 11 IC8 or pin 8 IC8 will go to 0 either setting or resetting the following latch (IC7c and d). The output of the latch drives a DIL reed relay (RLA) which switches a 1M Ω preset in parallel with the 1M Ω preset in the vertical direction integrator circuit.

As the multivibrator frequency is in kilohertz, and the sample pulse occurs once in seconds, a fairly random speed change is thus produced.

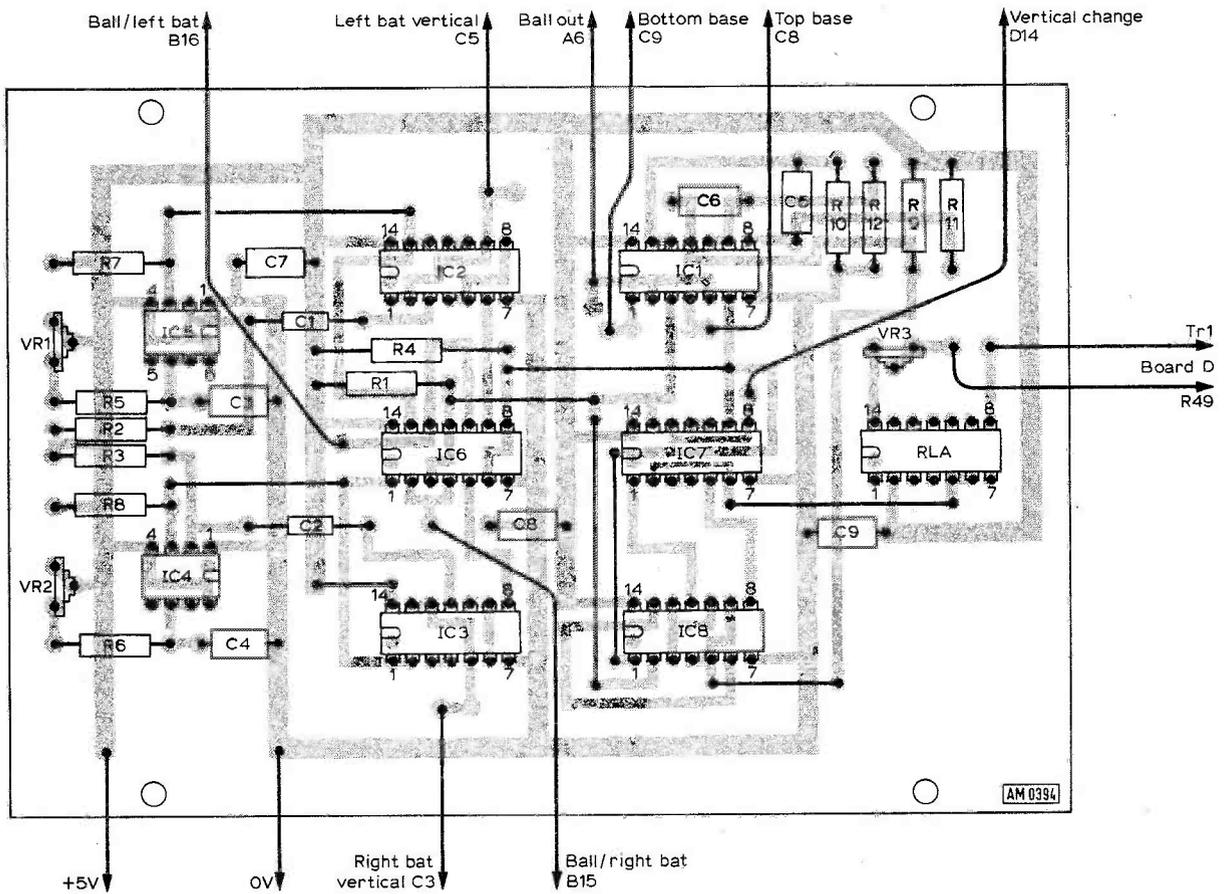


Fig. 2: Layout of the components on the printed circuit board

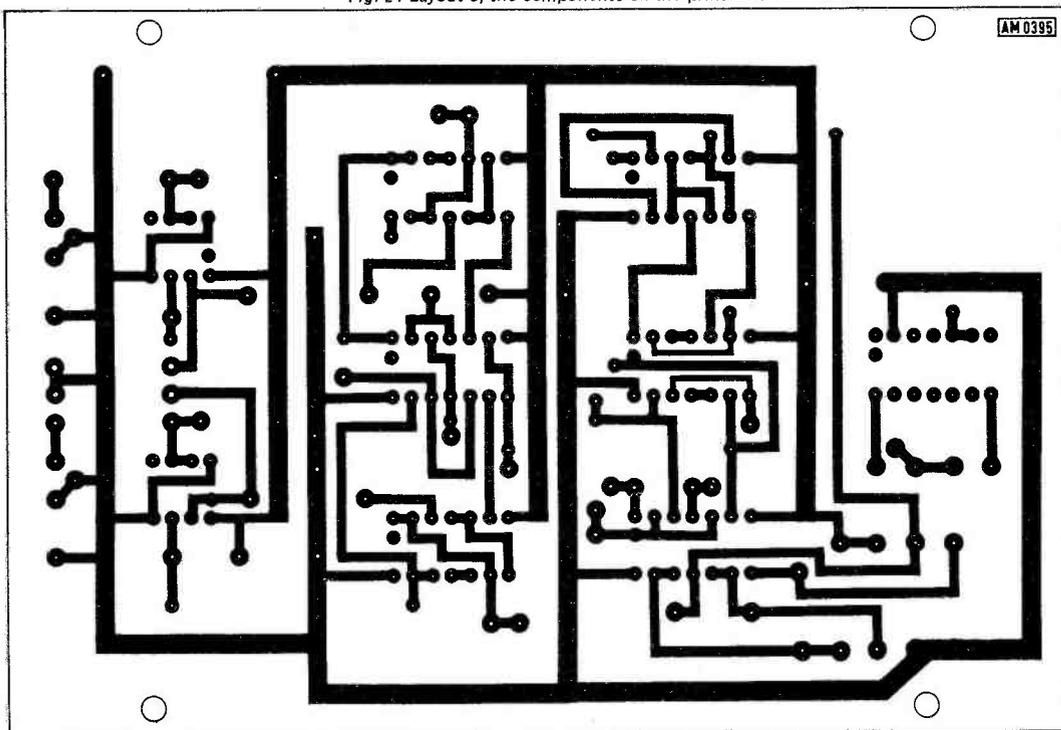


Fig. 3: Full size printed circuit layout for the Tele-Tennis Ball Speed Control

continued on page 497

Practical Wireless, October 1975

Complete the coupon and we'll send you our complete, new catalogue.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now (enclosing a 10p stamp for postage) and we'll send you your copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

**Easy to build -
a pleasure to own**

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.


So, when you receive your catalogue you should have hours of pleasant reading.

And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.


At either one you'll be able to see for yourself the one thing the catalogue can't show you.

Namely, how well a completed Heathkit performs. Heath (Gloucester) Limited, Dept. PW-105, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

DC-5 MHz, 100mV oscilloscope

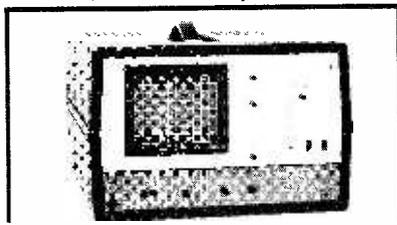

AM/FM 60 watt r.m.s. stereo receiver.

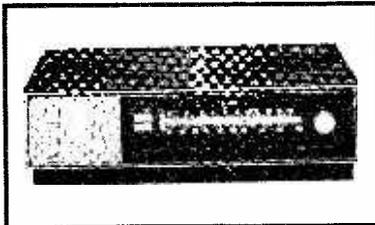

Deluxe digital alarm clock.



FREE
SOLDERING IRON
WORTH
£3.50
with all orders over £30

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. PW-105, Gloucester, GL2 6EE.
Please send me my Heathkit catalogue. I enclose a 10p stamp for postage.

Name _____ Address _____
Postcode _____

Full details in the catalogue. Offer available for limited period only.



Monthly subscription
available

HIGH POWER BATTERY MOTOR

12v operated, strong enough to power a motor mower, go-cart or similar. Speed easily variable. These motors can also be used as a brake for any rotating machine, simply by coupling the spindle to the machine and short-circuiting the windings by a variable resistance, price £2-50+ post and V.A.T. 75p. D/T 20 but 6/12v even more powerful as it's larger and is series wound £3-50+85p post and V.A.T.



FIRE ALARM SWITCHES

In cast iron case with break glass panel. These are red and engraved "Fire break glass"; they have hinged lid and second safety switch for testing purposes. Limited quantity. £1-75 each+post and VAT 46p.



DC HIGH CURRENT PANEL METERS

3 1/2" wound wide angle 240uA movement meters, flush mounting fitted with external shunts, made by Crompton Parkinson brand new, still in maker's cartons. These are a real bargain at £5-50 each. Reasonable quantities available in the following ranges: 0-10 amps, 0-20 amps, 0-30amps, 0-40 amps, 0-50 amps. Post and VAT 80p each.



EDGE MOUNTING MOVING COIL METER

Size 2 1/2" x 1" by Weston. 100uA movement scaled D.B., unseed still in original maker's cartons. £2-50 each + post and VAT 50p.



PERMEABILITY TUNERS

M.W. two stage ideal for use with 2N414 or similar circuit. Price 15p each + post and VAT 15p.



OVEN THERMOSTAT

Made by the famous Diamond H Company, this has a sensor joined by a capillary to a variable control and when fitted with a knob is ideal for many ovens or processes. 50p each + post and VAT 15p.



NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XN11 Price 90p each. 20p Post and VAT



WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make. £3-25 £1-00 post and VAT.



PORTABLE CABINET OFFER

A nicely made portable cabinet, soft padded black finish intended for portable stereo system. Dimensions as sketch. With motor board cut out for Garrard SP 25. This was obviously a very costly cabinet originally made for a deluxe record player. Offered at £1-95+£1-00 post and VAT, carriage free if bought with the Garrard or BSR record decks.



HIGHLY SENSITIVE MOVING COIL RELAY

panel mounting with glass window, this measures approx. 5 1/2" x 4" x 2 1/2", triggering current can be varied from a fraction of a milliamp to 5 milliamps by removing the front and adjusting the setting level. Price £3 each + post and VAT 95p.



SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in Rox all ready to work. £7-95 plus 80p VAT and postage.




AUDIO AMPLIFIER

Part of the famous Redifone background music system, secondhand, but believed in good order. However, no guarantee; we are selling for spare value only. These are 6 valve amplifiers, the output valves are 2x EL 84 in push/pull, complete with mains transformer, rectifier and ample smoothing equipment. The mains transformer alone, today would cost at least £4. Size is 8 1/2" x 5 1/2" x 4 1/2". Price only £2-00+postage and VAT £1-50.



BREAK-DOWN UNIT

Contains hundreds of useful parts some of which are as follows—86 silicon diodes equivalent OA 91. 63 resistors mostly 1/2 watt 5% covering a wide range of values. 4x1 mfd 400v indd condensers. 15x.01 mfd 100v condensers. 2 RF chokes. 8x B9 valve holders. 1x4H choke. 1x115v transformer. 1 boxed unit containing 4 delay lines also tag panels, trimmer condensers, suppressors, etc., on a useful chassis sized approx. 9" x 5" x 7". Only 75p (the 86 diodes would cost at least 10 times this amount). This is a snip not to be missed. Post and + VAT 75p.

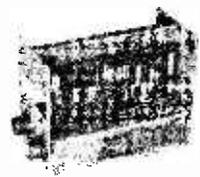

GPO PUSH BUTTON DIALLING UNIT

Will take the place of the normal rotating dial, has 10 numbered keys, so suitable for other digital systems. A desk mounting unit with rubber feet, this is a very intricate and expensive piece of apparatus. New and unused—our price only £9 each+£1.36 post and V.A.T.



24V POWER PACK

Normal mains input with a thermal safety device. 400 mA output, 4000 mfd of smoothing and full wave rectification, completely enclosed in plastic box and with flex for mains and terminal block for output. Price £1-75+£1 post and VAT.




8-SWITCH DISCO LAMP CONTROLLER

Mains motor driving a drum with adjustable trips operating 8 changeover 10 amp switches, so a total of 40K watts of lighting can be controlled enabling an unlimited variety of effects to be achieved and changed with the minimum of effort. This is a real snip a £7-50+£1.15 post and VAT.



HONEYWELL PROGRAMMER

This is a drum type timer device, the drum being calibrated to equal divisions for each setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control. Boiler firing. Dispensing and Venting machines. Display lighting animated and signs. Signalling, etc. Price from makers probably over £20 each. Special snip price £9-95 £1-00 Post and VAT. Don't miss this terrific bargain.

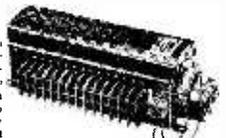

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated. Size 3in x 3in x 2in deep. Price £5-50. 80p Post and VAT, as illustrated but less case.



CENTRIFUGAL BLOWER

Miniature mains driven slower centrifugal type blower unit by Woods. Powerful but specially built for quick running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet, or for removing flux smoke when soldering, etc. etc. A real bargain at £2-50p. 55p Post and VAT.



SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 39 metre bands—Kit contains chassis front panel and all the parts. £1-25—crystal earphone 50p. 80p Post and VAT.



TERMS:

Where order is under £5 please add 30p surcharge to offset packing expenses.

J. BULL (ELECTRICAL) LTD.
(Dept. PW), 103 TAMWORTH RD.
CROYDON CRO IXX

WALL THERMOSTATS


Wall mounting and in a handsome plastic case. (Cream and beige). Adjustable by slider (lockable) and may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost), (warm), (very warm), etc. The thermostat will control heaters, etc., up to 15 amp at normal mains voltage and is ideal for living rooms, bedrooms, etc. Price £1-95, VAT & Postage 80p. Don't miss this.

INSTANT START FLOURESCENT LIGHTING BARGAINS

Startersless control gear, complete with tube ends and tube clips for window lighting, signs, fascias, etc. 4 ft. 40 w. £1-50; 5 ft. 65w. £1-00; 5 ft. 80w. £1-75; 6 ft. 80w. £1-95; and for pairs as follows—twin 2 ft. 20w. £2-55; twin 3 ft. 30w. £2-75; twin 4 ft. 40w. £2-95; twin 5 ft. 65w. £3-25; twin 5 ft. 80w. £3-95; twin 8 ft. 125w. £4-50. These are about one half of maker's current prices and can't be repeated once stocks are cleared. Please add 30p per piece to cover postage or carriage and 8% VAT.

15A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2-30, VAT & Postage 80p, or with glass front, chrome bezel, £1-00 extra.

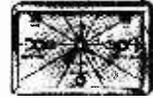

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 13 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1-50. VAT & postage 60p.


ONLY £1 FOR SEVEN ELECTRIC MOTORS

7 powerful batt. motors as used in racing cars & power models. Output & types vary for use in hundreds of different projects—Tools, toys, models, etc. All brand new reversible & for 1 1/2-12v. batts. Wiring diag. inc. VAT & Post 40p. FREE plan for min. power station.



EXTRACTOR FAN

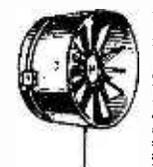Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector and fixing brackets. £3-75 VAT & Postage £1-25.



MAINS TRANSFORMERS

All standard 230-250 volt primaries		£ p
1v	1 amp (special)	1-75
2-4v	5 amp	85
6-3v	2 amp	1-00
6-3v	3 amp	1-50
9v	1 amp	95
9v	3-5 amp	1-95
12v	1 1/2 amp	1-50
12v	1 amp	1-00
6.5v-0-6.5v	1 amp	1-35
18v	1 amp	1-25
20v	1 amp	1-00
24v	1 amp	1-50
24v	3 amp	3-50
12-0-12v	50mA	1-80
6-0-6v	50mA	1-80
4-0-8v	1 amp	1-25
18-0-18v	2 amp	3-50
25v	1 1/2 amp	1-95
50v 2 amp & 6.3v	1 amp	4-50
60v 5 amp & 5v	1 amp	7-50
18v	1 amp	4-50
30v	3 amp	22-00
80v tapped 75v & 70v	4 amp	5-50
230v-60mA & 6-3v	1-5 amp	1-75
275-0-275v at 90mA & 6-4v	3 amp	2-25
EHT Transformer 5000v		
23mA	(intermittent)	5-50

Charger Transformers
6v and 12v 2 amp . . . 1-25
6v and 12v 3 amp . . . 2-25
6v and 12v 5 amp . . . 3-50
Add 30p per piece to cover postage and VAT 25%.

Your

Continental Holiday RECEPTION

BBC PROGRAMMES

MANY people are interested in listening to radio programmes in English when they are on holiday abroad. Apart from entertainment, these can provide news from home, as well as weather forecasts, road reports and other information about the area concerned. The following notes are intended as a guide to help listeners to know what they can expect to receive in different areas on receivers with and without short wave bands.

Details are given for each of the more popular holiday countries, and information is given about the BBC services that can be received, together with any special programmes in English that are broadcast for visitors by these countries. These tourist broadcasts can usually be heard on simple portable receivers.

Times mentioned are the local times in the countries concerned, except where otherwise stated.

Germany, Austria, Switzerland, Northern Italy

A medium wave portable or car radio will provide adequate reception only after dark, except in the nearer parts of West Germany. Radio 2 on 1500 metres can be heard in some parts during the day, but reception depends very much on the location. In towns where electrical interference is heavy, and this includes most continental capitals, signals may be overcome by the interference, but in rural areas acceptable reception is possible for long periods.

For consistently good reception, especially in the daytime, a receiver which covers at least some of the short wave bands is essential, and a receiver covering at least the 19 to 49 metre bands is desirable.

The 19, 25 and 31 metre bands should be used during the daytime, and the 31, 41 and 49 metre bands at other times. This will enable good reception of the BBC World Service to be obtained throughout the day and evening.

Northern France, Belgium, Holland

Listeners will find that an ordinary portable or car radio receiver covering the long and medium wave bands will prove quite adequate for listening to the BBC's domestic programmes.

Radio 2 on 1500 metres long wave, and Radio 4 on 285 metres or 330 metres medium wave, should be audible throughout most of the day and evening. The World Service in English is broadcast on 276 metres from 2300 to 0430 GMT.

Spain and Portugal

For reception in the daytime a short wave receiver is essential. This should cover at least the 19 to 49 metre bands. The general listening pattern is that during the daytime the 19 or 25 metre band should be used, and the 31, 41 or 49 metre band will give the best reception during the evening.

Late at night, the ordinary medium and long wave portable will often provide some recep-

tion. Listeners should try Radio 2 on 1500 metres long wave, and Radio 4 on 285 metres or 330 metres medium wave. BBC World Service on 276 metres medium wave can also give good results, especially in the more northerly parts.

Southern Italy and East Mediterranean

In all these areas a short wave receiver is essential, and to be sure of good reception at all times, the receiver will need to cover all bands from 13 to 50 metres. The general pattern is that the 13, 16 or 19 metre band will give best reception during daylight, and the 25, 31, 41 or 49 metre band during the evenings.

Denmark, Norway, Sweden

A medium and long wave portable will provide some reception at night-time. Radio 2 on 1500 metres, Radio 3 on 464 metres and Radio 4 on 330, 285 or 371 metres will probably provide the best signals. For early risers, the Radio 3 transmitter on 464 metres is used to carry BBC World Service programmes prior to 0730, or 0830 at weekends.

For reliable reception throughout the day, however, a short wave receiver is required, and an ideal receiver would cover the 19 to 49 metre bands. The 31, 25 or 19 metre band will give best reception during the daytime, and the 41 or 49 metre band will be best during the evenings.

LOCAL TOURIST BROADCASTS

Austria

From 0805 to 0810 daily a bulletin of news, weather and traffic reports is given in English on medium wave (293, 514, 577 metres) and on vhf.

Greece

On weekdays, news and weather bulletins are broadcast in English at 0815, 1310 and 2145 on 412 and 238 metres medium wave and on the local vhf channels. A weather forecast for shipping is also broadcast on these wavelengths at 0635 each day.

Italy

On weekdays from June to September at approximately 0800, news in English is broadcast on 188 and 219 metres medium wave and also on vhf.

Portugal

At approximately 0855 each day, tourist information is broadcast on the local vhf and medium wave transmitters in English, French and German. This programme can be heard on the wired radio systems which are available in many hotels.

Sweden

A summary of the news and weather forecast is given on the local Programme 3 vhf transmitters from 1800 to 1805 each day between July and September.

Switzerland

At 1215 and 1900 each day, listeners can hear the news in English on Line 1 of the Tele-diffusion service, broadcast over the telephone network. (This service is available in many hotels.)

SOME BBC WAVELENGTHS AND FREQUENCIES

Receiver dials are calibrated by wavelength (metres) or frequency (kHz or MHz). The following table may be useful:

		Wavelength	Frequency
Long wave	Radio 2	1500 metres	200 kHz
Medium wave	Radio 3	464 metres	647 kHz
	Radio 4	285 metres	1052 kHz
		330 metres	908 kHz
Short wave		371 metres	809 kHz
	World Service	276 metres	1088 kHz
	Broadcast Bands	13 metres	21 MHz
		16 metres	18 MHz
		19 metres	15 MHz
		25 metres	11 MHz
		31 metres	9 MHz
		41 metres	7 MHz
		49 metres	6 MHz

West Germany

From 1940 to 2030 Mondays to Saturdays inclusive, a varied programme of news, press reviews and general interest features is broadcast on 236 metres medium wave. This can be heard in most parts of Germany. Listeners in the Bonn area can hear a news broadcast in English, Mondays to Saturdays from 1940 to 1950 on 89.1MHz vhf.


A three minute news and

weather bulletin for listeners in Bavaria is broadcast at 1000, Mondays to Fridays on the local vhf transmitters.

In certain areas the British Forces Broadcasting Service is available on vhf throughout the day and evening.

The above information was supplied by the BBC Engineering Information Department, Broadcasting House, London W1A 1AA.

PW TECHNICAL PUZZLE No. 11

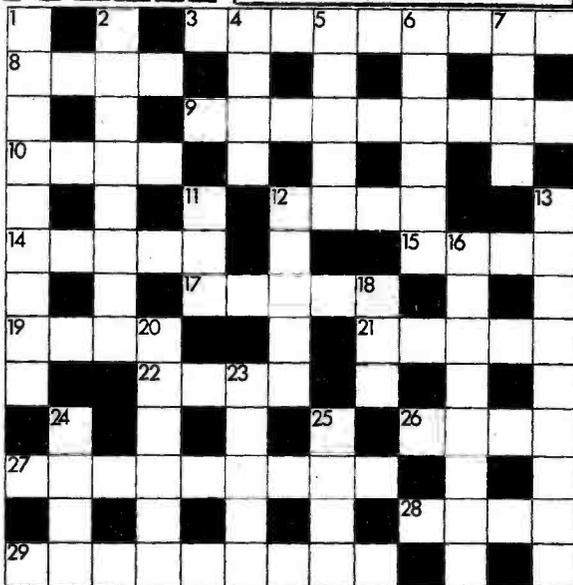

ACROSS

- 3 Impulsiveness in a storage system? (5-4)
- 8 Mid-ear connection is a thought! (4)
- 9 Part of electrical condensation? (9)
- 10 The pick-up with a saga involved! (4)
- 12 Get some sort of reception! (4)
- 14 Make an example of this turntable? (5)
- 15 An insult to smooth music! (4)
- 17 Scotsman in flower with this instrument? (5)
- 19 Graces often go with these tunes? (4)
- 21 Level of noise about a sports arena? (5)
- 22 All individually ache for modulation (4)
- 26 Specially built receivers for travellers (4)
- 27 Naturally flutes can be taped on them! (9)
- 28 You service what he employs inside? (4)
- 29 Military type of music transmitter? (9)

DOWN

- 1 A musical blow-out that's been stopped! (4-5)
- 2 Component in the rebuilt store, sir? (8)
- 4 Chorale containing a spoken part? (4)
- 5 Wipe out a seer with reform? (5)
- 6 A pull-out about these instruments? (6)
- 7 That's not overheating, anyway (4)
- 11 It's strung up headless against bombs! (3)
- 12 Organist and band-leader have common ground?
- 13 Play-group of all ages (9) (5)
- 16 Old-time player sat until replaced (8)
- 18 Top tunes to choose from? (3)
- 20 Not the first diatonic interval? (6)
- 23 Young officer acted as new arranger (5)
- 24 A Greek letter for the conductor, we hear (4)
- 25 Fingering found round old Ireland? (4)

FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH

BI-PRE-PAK

The people for component bargains




Makers of Stirling Sound audio equipment

ORIGINATORS OF PRE-PACKED COMPONENTS IN BRITAIN — AND STILL LEADING!


AUDIO MODULES — today's most challenging values!

POWER AMPS

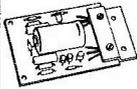

SS103
Compact I.C. amp. 3 watts R.M.S. Single channel (mono). On P.C.B. size 3 1/2" x 2". Needs 10-20V supply. **£1.75**

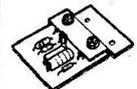SS103-3
Stereo version of above. (Two I.Cs.) **£3.25**
NEW! SS105 Mk. 2



A compact all-purpose power amp. Size 3 1/2" x 2". Useful 5W output (mono) into 3Ω using 12V. Two in bridge formation give 20W from 12V, for P.A. etc. **£2.25**

SS110 Mk. 2
Similar in size to SS105 but will give 10W output into 4Ω using 24V (mono). Two in stereo give first-class results, suitable for many domestic applications. **£2.75**

NOW—SS120 20W r.m.s. into 4Ω using 34V. 3 1/2" x 2" **£3.00**



SS140*
Beautifully designed. Will give up to 40W R.M.S. into 4Ω. Excellent S.N.R. and transient response. Fine for P.A., disco use, etc. Operates from 45V D.C. Two in bridge formation will give 80W R.M.S. into 8Ω. **£3.75**

PRE-AMP/CONTROL MODULES

SS100
Active tone control unit to provide Bass and Treble cut and lift. With full instructions (stereo). **£1.60**

SS101
Pre-amp for stereo ceramic cartridges, radio and tape. **£1.60**


SS102
Pre-amp for low-output stereo magnetic cartridges, radio and tape. **£2.25**

BUILD A STEREO F.M. TUNER

SS201
Front End assembly. Ganged tuning with well engineered slow-motion geared drive in robust housing. A.F.C. facility. Requires 6-16V. Excellent sensitivity. 88-108MHz. **£6.25**

SS202
I.F. Stage (with I.C.). Designed to use with SS201 uses I.C. Carefully checked before despatch. **£5.25**

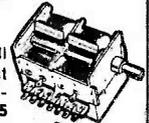SS203
Stereo Decoder. Designed essentially for use with SS201 and SS202, this excellent decoder can also make a stereo tuner of almost any single channel FM tuner. Supplied ready aligned. A.L.E.D. can easily be fitted. **£5.62**
Above 3 units together special price **£12.12**



SPECIAL OFFERS

LM 380 AUDIO IC (Marked SL60745). Brand new and to spec. 3 watts R.M.S.-out. With data. **£1.00**

2X SN7490. Brand new I.C. to spec. decade counters. **£1.00***

3XSN 7400 Quad 2 input Nan gate ICs. **50p***

SUNDRY

P.I. PAK—Approx. 170 short-lead semi-conductors and components. PNP, NPN, diodes, rectifiers, etc. on PCBs. At least 30% factory marked. Some data supplied. **50p***

UHF 625 line tuner, rotary. **£2.50**
Rev Counter (for cars) (8%). **£1.00***
Books by Bernard's Publications, Newnes-Butterworth's etc. No VAT.

THE FREE CATALOGUE

New edition better than ever. It's yours for free and well worth getting—only please send large S.A.E. with 10p stamp if we have to post it to you.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. **POST & PACKING** add 22p for UK orders unless marked otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. **PRICES** subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

NEW RANGE TRANSISTOR & COMPONENT PACKS

TP SELECTION

TP5 20 Transistors, PNP Germanium, Red Spot A.F.

TP6 20 Transistors, PNP Germanium, White spot RF.

TP7 1 2N174 150W 80Vce Power Transistor, with mounting assembly.

TP19 100 diodes, mixed Germanium, Gold-bonded, etc. Marked/Unmarked.

TP23 Twenty NPN Silicon uncodded T05. Similar to BFY502, 2N696, 2N1613, etc. Complementary to TP24.

TP24 Twenty PNP Silicon, uncodded T05. Similar to BFY64, 2N2904/5

TP29 8 power diodes 400V, 1-25A Silicon FST 3/4.

UT SELECTION

UT1 50 PNP's Germanium, AF & RF.

UT2 150 Germanium diodes, min. glass.

UT4 100 Silicon diodes, min. glass, similar to IN914, IN916.

UT5 40 250mW Zener diodes OA224 range; average 50% good.

UT7 30 Silicon rectifiers 750mA, mixed voltages, Top Hats, etc.

UT9 40 NPN Silicon planers. Similar to 2N3707-11 range. Low noise amps.

UT12 25 2N3702/3 Transistors, PNP Silicon, Plastic to 92.

CP SELECTION

CP1 Mixed bag of capacitors—Electrolytic, Paper, Silver Mica (Approx. 150—sold by weight).

CP2 200 (approx.) Resistors, various types, values, watts. (Sold by weight.)

CP3 40 Wire wound resistors, mixed.

CP4 12 pots—pre-set, w/wound, carbon, dual, with/without switches—all mixed.

CP7 Heat sinks, assorted, To fit SO-Z (OC72) TO-1 (AC128), etc.

ALL ABOVE PACKS—60p EACH.

TP Tested & Guaranteed; UT Untested, unmarked; CP Components.

CAPACITOR DISCHARGE IGNITION KIT

Simple to assemble and fit. Improves car performance, saves on fuel. P&P 30p. **£7.50***

BI-PRE-PAK X-HATCH GENERATOR Mk.2

Four-pattern selector switch 3" x 5 1/2" x 3" Ready-built and tested in kit form ***£9.93** ***£7.93**

Please add 35p for postage and packing. Is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact, self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case, instructions, but less batteries. (Three U2 type required.)

TV SIGNAL STRENGTH METER

Complete kit as described in "Television" **£10.50** plus 40p* for P&P

SS300 POWER SUPPLY STABILISER

Add this to your unregulated supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench etc. Money saving and very reliable. **£3.25***

PLASTIC POWER TRANSISTORS

40 WATT SILICON*

Type	Polarity	Gain	VCE	Price
40N1	NPN	15	15	25p
40N2	NPN	40	40	30p
40P1	PNP	15	15	25p
40P2	PNP	40	40	30p

90 WATT SILICON

Type	Polarity	Gain	VCE	Price
90N1	NPN	15	15	25p
90N2	NPN	40	40	35p
90P1	PNP	15	15	25p
90P2	PNP	40	40	35p

If you prefer not to cut coupon out, please mention PW10 when writing

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose inc. V.A.T.

Name

Address

PW10


BI-PRE-PAK LTD

Co. Reg. No. R267919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

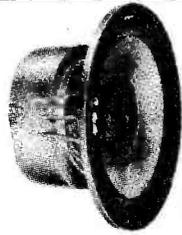WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£8-64
Baker Group 35 3, 8 or 15 ohm	£10-25
Baker Group 50/12 8 or 15 ohm	£14-00
Baker Deluxe 12" d/cone	£13-75
Baker Major	£11-87
Baker Regent	£10-00
Baker Superb	£18-12
Baker Auditorium 12	£16-25
Celestion MH1000 horn, 8 or 15 ohm	£10-95
Celestion PS8 for Unilex	£3-75
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00
EMI 13 x 8" 150 d/c 8 ohm	£22-94
EMI 13 x 8" type 350 8 or 15 ohm	£9-56
EMI 13 x 8" 20 watt base	£7-69
EMI 61" 93850 4 or 8 ohm	£4-37
EMI 8 x 5 d/cone, roll surr 10 watt	£3-44
EMI 21" tweeter 97492 A1	£8-31
Eagle CT33 30 watt tweeter	£7-40
Eagle HT15 horn tweeter	£8-12
Eagle CT5 cone tweeter	£2-06
Eagle CT10 tweeter 8 or 16 ohm	£3-00
Eagle MHT10 horn tweeter	£4-44
Eagle crossover CN23, CN28, CN216	£1-75
Eagle FR4	£6-12
Eagle FR5	£9-12
Eagle FR8	£12-31
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£3-44
Elac 61" 6RM171 d/c roll surr.	£4-06
Elac 51" 6RM220 d/cone	£12-12
Elac 4" tweeter TW4	£1-75
Elac 10" d/cone 10RM239 8 ohm	£3-12
Elac 8" 8CS175 3 ohm	£2-87
Fane Pop 15 watt 12"	£7-50
Fane Pop 25/2 25 watt 12"	£5-25
Fane Pop 50 watt 12"	£12-00
Fane Pop 55 60 watt 12"	£13-95
Fane Pop 60 watt 15"	£14-75
Fane Pop 100 watt 18"	£25-95
Fane Crescendo 12A 100 watt 12"	£34-50
Fane Crescendo 12B bass	£36-50
Fane Crescendo 100 watt 15"	£47-50
Fane Crescendo 150 watt 18"	£62-95
Fane 801T 8" d/c roll surr.	£8-12
Fane 807T 8" d/c roll surr.	£5-75
Fane 808T 8" d/c	£3-44
Fane 701 twin ribbon horn	£40-00
Fane 910 horn	£14-95
Fane 920 horn	£33-95
Goodmans 8P 8" or 15 ohm	£5-50
Goodmans 10P 8 or 15 ohm	£5-80
Goodmans 12P 8 or 15 ohm	£13-95
Goodmans 12P-D 8 or 15 ohm	£16-95

Goodmans 12P-G 8 or 15 ohm	£15-95
Goodmans Audiomax 12AX 100 watt	£36-50
Goodmans Audiomax 15AX	£40-25
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans H1dax 750	£16-00
Goodmans Axiom 100 tweeter	£28-44
Goodmans Audiom 100 12"	£13-90
Goodmans Axiom 401 12"	£20-00
Goodmans Twinaxiom 8	£10-14
Goodmans Twinaxiom 10	£10-75
Kef T27	£8-05
Kef T15	£8-94
Kef B110	£8-37
Kef B200	£9-50
Kef B139	£16-50
Kef DN8	£23-31
Kef DN12	£5-75
Kef DN13	£3-87
STC4001G super tweeter	£6-56
Richard Allan C68T 8" d/c r/surr.	£7-37
2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm	77
2 1/2" 75 ohm	55
3" x 4" 3 or 8 ohm	£1-65
8" x 5" 3 or 8 ohm	£1-75
10" x 6" 3, 8 or 15 ohm	£2-69

SPEAKER KITS

Baker Major Module	each £13-44
Goodmans Mezzo Twinkit	pair £47-19
Goodmans DIN 20	each £13-44
Helme XLK 25	pair £25-44
Helme XLK 30	pair £17-19
Helme XLK 50	pair £46-25
Keffit 1	each £48-44
Keffit 3	each £42-50
Richard Allen Twinkit	each £10-37
Richard Allan Triple 8	each £15-94
Richard Allan Triple 12	each £23-15
Richard Allan Super Triple	each £27-50
Wharfedale Linton 2 kit	pair £23-12
Wharfedale Glendale 3 kit	pair £40-60
Wharfedale Dovedale 3 kit	pair £63-12

PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£37-25
Linear 30/40	£30-00
Linear 40/60	£35-00
Linear 80/100	£58-95
Linear 100 watt slave	£44-00

Eagle PA range in stock—ask for catalogue.

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12" and up 50p each. Speaker kits 75p each (£1.50 pair) tweeters and crossovers 25p.

Including V.A.T. 25% on Hi Fi, 8% on PRO and PA

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow
Send stamp for free booklet "Choosing a Speaker"



Agfa Cassettes The best buy!

Agfa Low Noise Cassettes				
AT LESS THAN HALF PRICE!	C60	1 40p	5 £2-00	10 £3-98
	C90	54p	£2-70	£5-38
	C120	75p	£3-70	£7-38
AGFA HIGH DYNAMIC SUPER	C60+6	1 54p	5 £2-70	10 £5-35
	C90+6	70p	£3-50	£6-75
	C120	89p	£4-95	£9-85
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C60	1 90p	5 £4-50	10 £8-75
	C90	£1-10	£5-50	£10-90

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO
(DEPT. PW)
10 SWAN STREET, WILMSLOW,
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

Wire Wound Resistors. Our selection of mixed values. 30 for £1.40. 100 for £3.50.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.30 + post.

Ferguson Stereogram chassis Model 3357, all transistor, medium long, VHF/FM. 3 watts per channel S/M, with connection data, less tuning scale, £18.00. Post paid.

Crystals HC6U: 52-03333 MHz: 52-02500: 52-01667: 51-56667: 51-58330: 37-76250: 37-75000: 12-895-8: 12-891-8: 12-700-0: 9-456-25: 9-455-55: 9-533-33: 9-531-94: 9-530-55: 9-090-62: 9-087-5 50p each.

Electrolytics. 32/32/μF, 325v. 2" x 1 1/2" 35p: 80μF 150v 1 1/2" x 1" 20p: 2000μF 30v, 2 1/2" x 1" 25p: 2000μF 35v 3" x 1" 30p: 470μF 100v. 3" x 1 1/2" 25p: 2000/2000μF 25v 2" x 1 1/2" 35p: 700μF 200v 3 1/2" x 1 1/2" 30p: 16/16μF 275v 1 1/2" x 1" 20p: 40/40/20μF 275v 3" x 1" 20p: 4500/900/900μF 30v 2 1/2" x 1 1/2" 50p: 2500μF 40v 2 1/2" x 1 1/2" 40p: 470μF 25v 1 1/2" x 1 1/2" 15p: 4,000μF 25v 3" x 1 1/2" 40p. 32μF 450v 1 1/2" x 1" 30p: 8μF/16μF 450v 1 1/2" x 2" 30p: 1000μF 12v 1 1/2" x 1 1/2" 15p. 5000μF 50v 2" x 1 1/2" 50p: 150/200/200μF 300v 3" x 1 1/2" 50p: 4500μF 35v 2 1/2" x 1 1/2" 50p.

Try our parcel of small capacitors 20 mixed valves £1.50 + post.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5", 8 x 5 8" ohms ceramic, 5 watts RMS. Complete with din leads, £10.00 pair + post.

Thorn TV IF chassis, 950 series (less valves), £1.60 + post.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, circuit diagram supplied £3.00 + post.

P-C Boards (not computer panels) 1 off 6 transistor single wave band, 1 off 4 transistor audio, 1 off 3 transistor £1.40 + post, three boards.

Repanco Transformers AF1, AF2, TT45, 46, 47, 49, 53. 20p each + post.

L/M, M/W, VHF Tuner. 5 transistor in kit form, complete with full assembly instructions. 9vt supply, positive earth. Output 100mw. Built-in A.M. aerial. 88-108 Mcs. £5.25 + post.

Mains Droppers, 10 mixed values, £1.00 + post.

Edgewise Level meters, 200μA, size 3" overall. 50p + post.

Chrome Plastic knobs, 3 types, 4 off each with spring clip, £1.25 + post.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 65p + post: 10" x 7 1/2" x 2 1/2" 75p + post. 11" x 7 1/2" x 2 1/2" 85p + post.

BSR P128, similar to HT70 single play, with heavy die cast turntable, less cartridge, £10.00 + post.

Ferguson Stereogram Chassis. MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £26.25. Post paid 15 ASSORTED SWITCHES £1.90 + post. 50-3 way to 7 way TAG STRIPS, £1.15 + post. ALMA REED RELAY TYPE DRH. 3 VOLTS 50p + post.

REPANCO & DENCO COILS. NEW/BOXED OUR SELECTION—5 FOR £1.15 + post.

Please add 10% post and packing. Add 25% VAT to total order. Gram Chassis free postage. No goods despatched outside U.K.

SURPLECTRONICS
216 LEAGRAVE ROAD,
LUTON, LU3 1JD, BEDS.

Miniature

2m EQUIPMENT

part 2 : preamplifier

W. H. Bond F.R.C.S. G3XGP



aerial with the provision of a good earth, brought the world into the shack, and if one could not hear the signal this was always due to QSB or QRM. When however, a converter for the two metre band was made, the old aerial was no good and a special one had to be put up!

The aerial could be omnidirectional, or directional, the latter would bring in the one wanted signal magnificently but the other chap, off the beam heading, could hardly be heard. Using the omnidirectional aerial both signals went down so the RF gain was turned up, the signals reappeared but this time with a noise, making listening difficult and unpleasant.

NOISE

The noise is generated in the receiver and represents one essential difference between the lower frequencies and VHF. Below about 60MHz the dominant noise limiting the signal received is atmospheric, but above this frequency this falls, so that at VHF and

PROBABLY the majority of those interested in radio are not transmitting enthusiasts but listeners, some of whom may remember that on the lower frequencies, any piece of wire for an aerial

144-146MHz

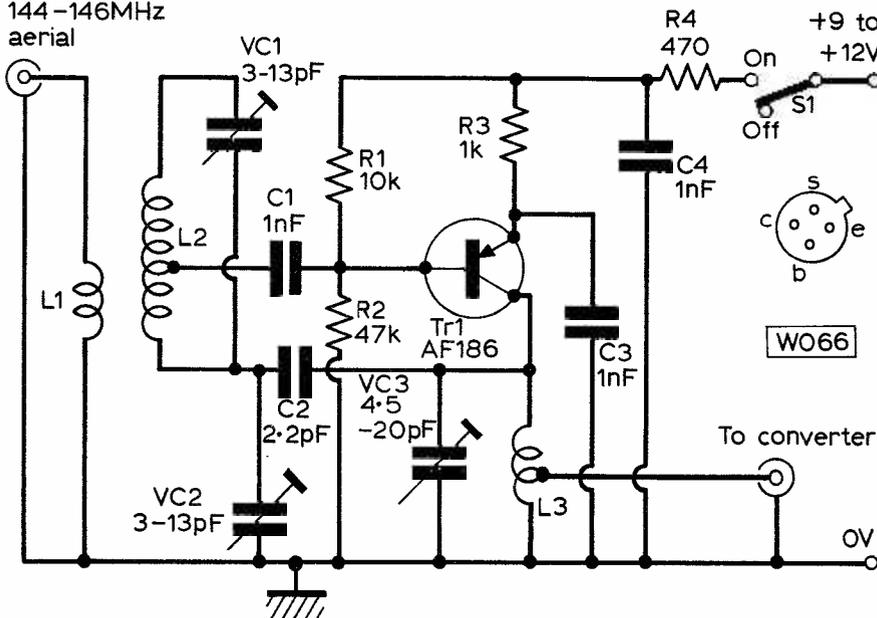


Fig. 1: Complete circuit diagram of the 2m Preamplifier. The AF186 is connected in common emitter configuration.

★ components list

Resistors	
R1 10k Ω	R3 1k Ω
R2 47k Ω	R4 470 Ω
All resistors 10% 1/4W	
Capacitors	
C1 1nF	C3 1nF
C2 2-2pF	C4 1nF
VC1 and VC2	3-13pF variable ceramic capacitor
VC3	4-5-20pF variable ceramic capacitor
C1-C4	disc ceramics
Semiconductor	
Tr1	AF186
Miscellaneous	
L1, 1½ turns enamelled 22SWG wound in first three turns of L2. L2, 7 turns 22SWG, tapped at second turn. L3, 7 turns 22SWG, tapped at first turn. Aluminium box 115x64mm (4½x2½in), Doram 509-939 or Eddystone 7134P. Single-sided copperclad fibreglass board 44 x 25mm (1½ x 1in). Four 5mm spacers. 2 coaxial sockets. S1, SPST switch.	

above, thermal and "shot" noise, predominates. Known as "white noise" it is random in frequency and time, and limits the lowest level of signal that can be demodulated in a receiver. Thermal noise depends on the bandwidth of the receiver, the resistance of the transistor used and two factors over which there is no control, Boltzmann's constant, and the absolute temperature. Shot noise on the other hand, depends on the rate of current flow through the device.

As the bandwidth cannot be reduced to a single cycle, a transistor has to be chosen that has the lowest inherent noise factor coupled with maximum gain at low current flow. The bandwidth, therefore, should be reduced to the minimum necessary, and the input resistance matched to the device resistance, in order that the maximum signal is transferred.

NEGATIVE FEEDBACK

There is, however, one other trick that can be employed after all these factors have been optimised, and that is negative feedback. Imagine a signal travelling through a transistor working in common emitter configuration with a positive signal changing into a negative one, or a 180° phase change. Now, as the signal travels through, random electron move-

ment adds some odd pulses (noise) first in the emitter base junction and then in the base where some electrons and holes combine, and, on the way out, in the base/collector junction.

These noise signals appear in a different phase from the main signal, some at 30°, some at 90°, but all out of phase with the input signal.

If the signal now returns from the collector to the base 180° out of phase and then the feedback signal reduced by a factor dependent on the gain of the transistor, no signal will appear at the collector. However, the noise generated in the transistor will still be audible because it is not 180° out of phase with the input signal. If the exact phase of the returned signal is altered there will be a point where the signal will be amplified, but the noise will be returned out of phase and not amplified. Both thermal and shot noise therefore being neutralised. This is the principle on which this pre-amplifier was designed, to amplify the signal but to neutralise the noise.


The input and output circuits are both tuned and lightly loaded so that the working Q is high and the bandwidth is kept to a minimum. The selected transistor is an AF186 with an inherently low noise factor and an FT of 900, chosen in preference to an FET, for those equal to it are twice as expensive and have less gain at VHF.

THE CIRCUIT

Because of both current and voltage gain, the transistor is run in common emitter configuration, Fig. 1 with the emitter being tied to the positive rail. The input coil is inductively coupled to L2 which is tuned by VC1. A tap on this coil matches the impedance of Tr1, the base being isolated by C1 from the bias chain R1 and R2. The emitter current is limited by R3, which is bypassed to earth by C3. L3 and VC3 in the collector lead, are tuned to the input frequency and a tap low down on L3 provides a low impedance output to match the following converter. C2 and VC2 is the neutralising phase shift circuit.

PCB CONSTRUCTION

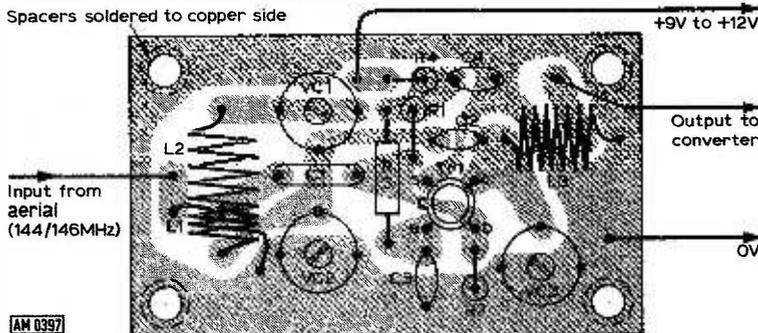Make a tracing of the board, Fig. 2. Stick this on a piece of single-sided copperclad fibreglass board, dot each of the component mounting holes with a centre punch, paint in the lines and etch. Clean and make the holes with a No. 60 drill, except for the



Component side view of PCB shown 1½ times actual size. All coils are wound on a 6.3mm (¼ in) drill for neatness, with L1 wound inside the first three turns of L2.

More than just a catalogue!

PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .


Really good value for money at just 40p.




The 3600 SYNTHESIZER

The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.

Please send S.A.E. for our price list.

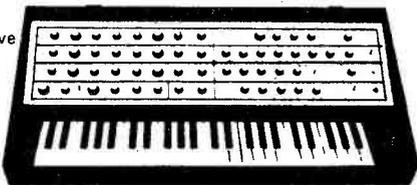


The 4600 SYNTHESIZER

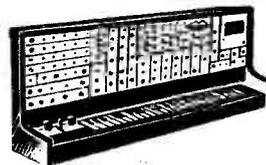

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or S.A.E. please for specification

GRAPHIC EQUALIZER

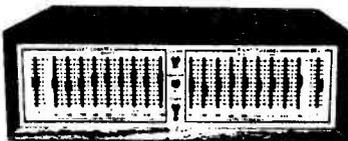A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's. S.A.E. for price list or complete reprint of article — price 15p.



ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range. Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, priced at 35p.



NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to

MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value _____ PW
For copy/copies of your Catalogue
Name _____
Address _____

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR.

Marshall's

A. Marshall (London) Ltd Dept. PW
42 Chislewood Broadway London NW2 3ET Tel: 01-452 0161/2
Telex: 21482

& 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133
& 1 Straits Parade Fishponds Bristol BS16 2LX
Tel: 0272 654201/2

& 27 Rue Danton Issy Les Moulineaux Paris 92 Tel: 642 2385
Catalogue price 25p Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linear

CA3018A	85p	CD4043	£1.80	NE555	£4.48	SN7448	90p	SN74157	95p
CA3020A	£1.80	CD4044	£1.80	SL414	£1.80	SN7450	16p	SN74160	£1.10
CA3028A	79p	CD4045	£2.65	SL610C	£1.70	SN7451	16p	SN74161	£1.10
CA3035	£1.37	CD4046	£2.84	SL611C	£1.70	SN7453	16p	SN74162	£1.10
CA3046	70p	CD4047	£1.65	SL612C	£1.70	SN7454	16p	SN74163	£1.10
CA3048	£2.11	CD4049	81p	SK620C	£2.60	SN7460	16p	SN74164	£2.01
CA3052	£1.62	CD4050	66p	SL621C	£2.60	SN7470	33p	SN74165	£2.01
CA3099E	£1.95	LM301A	48p	SL623C	£4.59	SN7472	26p	SN74167	£4.10
CD3090Q	£4.23	LM38	£2.59	SL640C	£3.10	SN7473	26p	SN74174	£4.10
CD4000	36p	LM051T	£1.50	SN7400	16p	SN7474	16p	SN74175	50p
CD4001	36p	LM380	£1.10	SN7401	16p	SN7475	50p	SN74176	£1.44
CD4002	36p	LM381	£2.20	SN7401AN	38p	SN7476	35p	SN74180	£1.40
CD4006	£1.38	LM702C	75p	SN7402	16p	SN7480	50p	SN74181	£1.30
CD4007	36p	LM709	38p	SN7403	16p	SN7481	£1.25	SN74190	£2.30
CD4008	£1.61	LM35	£1.35	SN7446	16p	SN7482	75p	SN74191	£2.30
CD4009	£1.18	14DL1	40p	SN7405	19p	SN7483	95p	SN74192	£1.30
CD4010	£1.18	LM710	47p	SN7406	45p	SN7484	95p	SN74193	£1.15
CD4011	36p	LM723C	90p	SN7407	45p	SN7485	£1.25	SN74196	£1.60
CD4012	36p	LM741C	40p	SN7408	19p	SN7486	32p	SN74197	£1.58
CD4013	66p	8DL	38p	SN7409	22p	SN7490	45p	SN74198	£2.25
CD4014	£1.72	14DL1	40p	SN7410	16p	SN7491	85p	SN74199	£2.25
CD4015	£1.72	LM747	£1.05	SN7411	25p	SN7492	45p	SN76003N	£2.92
CD4016	66p	LM748	60p	SN7412	28p	SN7493	45p	SN76013N	£4.95
CD4017	£1.72	14DL1	73p	SN7413	35p	SN7494	82p	SN76023N	£4.60
CD4018	£2.35	LM3900	70p	SN7416	35p	SN7495	72p	SN76033N	£4.60
CD4019	86p	LM7805	£2.00	SN7417	35p	SN7496	72p	SN76033N	£4.60
CD4020	£1.91	LM7812	£1.30	SN7446	16p	SN7497	£1.00	SN74100	£1.75
CD4021	£1.72	LM7815	£2.50	SN7423	29p	SN74107	36p	TAA263	£1.10
CD4022	£1.66	LM7824	£2.50	SN7425	29p	SN74118	£1.00	TAA360	£1.80
CD4023	36p	MC1303L	£1.50	SN7427	29p	SN74119	£1.92	TAA350A	£2.10
CD4024	£1.24	MC1318P	£2.59	SN7430	16p	SN74121	37p	TAA550	60p
CD4025	32p	MC1330P	90p	SN7432	38p	SN74122	85p	TAA611C	£2.18
CD4027	43p	MC1351P	80p	SN7437	28p	SN74123	85p	TAA621	£2.03
CD4028	£1.50	MC1352P	80p	SN7438	35p	SN74141	85p	TAA641B	£2.32
CD4029	£3.50	MC1466L	£3.50	SN7440	16p	SN74145	90p	TBA641B	£2.25
CD4030	87p	MC1499R	£2.75	SN7441AN	85p	SN74150	£1.00	TBA551	£1.69
CD4031	£2.19	NE555V	70p	SN7442	65p	SN74151	85p	TBA800	£1.40
CD4032	£1.93	NE555	70p	SN7443	65p	SN74152	85p	TBA810	£1.40
CD4037	£1.86	NE560	£4.48	SN7447	95p	SN84152	£1.50	TBA820	£1.15

BRISTOL 10% discount for callers at our new shop at I Straits Parade, Fishponds, Bristol, BS16 2LX producing a current issue of this mag. Tel: Bristol 654201/2

POPULAR SEMICONDUCTORS

2N696	22p	2N3906	27p	AF139	65p	BD139	71p	MPSA56	31p
2N697	15p	2N4037	42p	AF239	65p	BD140	87p	OC28	76p
2N698	82p	2N4036	67p	AF240	90p	BF115	36p	OC35	60p
2N699	59p	2N4037	67p	AF241	70p	BF117	36p	OC40	50p
2N706	14p	2N4062	15p	AF280	79p	BF154	20p	OC45	32p
2N708	17p	2N4289	34p	AL102	£1.00	BF159	27p	TIP29A	49p
2N716	28p	2N4920	£1.10	BC107	14p	BF180	35p	TIP29C	58p
2N717	28p	2N4921	83p	BC108	14p	BF181	36p	TIP31A	62p
2N722	18p	2N4922	83p	BC109	14p	BF182	36p	TIP31B	62p
2N1304	36p	2N5245	47p	BC147B	14p	BF194	24p	TIP33A	£1.01
2N1306	31p	2N5294	48p	BC148B	15p	BF195	12p	TIP34A	£1.51
2N1307	47p	2N5296	48p	BC149B	15p	BF196	13p	TIP35A	£2.90
2N1711	45p	2N5457	49p	BC157A	16p	BF197	15p	TIP36A	£3.70
2N1210	69p	2N5458	46p	BC159A	16p	BF198	8p	TIP32A	£0.90
2N147	75p	2N5459	49p	BC159B	16p	BF199	24p	TIP295	98p
2N148	94p	2N6027	45p	BC168B	15p	BF257	47p	TIP3055	50p
2N2218A	22p	3N128	73p	BC169B	15p	BF258	53p	TIS43	28p
2N2219A	26p	3N140	140p	BC182	12p	BF259	55p	ZTX300	13p
2N2220	25p	3N141	81p	BC182L	12p	BF561	27p	ZTX301	13p
2N2221	18p	3N200	£2.49	BC183	12p	BF598	25p	ZTX300	15p
2N2222	20p	40361	40p	BC183L	12p	BF599	24p	ZTX501	13p
2N2369	20p	40362	45p	BC184	13p	BF599	24p	ZTX502	18p
2N2466	55p	40406	44p	BC184L	13p	BF599	24p	IN914	7p
2N2904	22p	40407	35p	BC212A	16p	BFX30	27p	IN375A	15p
2N2905	25p	40408	30p	BC212LA	16p	BFX84	24p	IN4007	10p
2N2906	19p	40409	32p	BC213LA	15p	BFX85	30p	IN4148	7p
2N2907	22p	40410	32p	BC214LB	18p	BFX88	25p	IN5404	22p
2N2924	20p	40411	£2.00	BC237B	16p	BFY50	22p	IN5408	30p
2N2925C	12p	40594	74p	BC238C	15p	BFY51	23p	AA119	25p
2N2935	25p	40595	84p	BC239C	15p	BFY52	20p	BA102	8p
2N3054	60p	40636	£1.70	BC257A	16p	BFY59	48p	BA145	18p
2N3055	75p	40773	73p	BC258B	16p	ME0402	20p	BA156	12p
2N3059	28p	AC162	20p	BC259B	17p	ME4012	18p	BA155	12p
2N3392	15p	AC127	20p	BC301	34p	ME4102	11p	BB103B	23p
2N3393	15p	AC128	20p	BC307B	17p	MI480	95p	BB104B	45p
2N3440	59p	AC151	27p	BC308A	15p	MI481	£1.20	BY126	12p
2N3442	£1.40	AC152	49p	BC309C	20p	MI480	£1.05	BY127	15p
2N3638	15p	AC153	35p	BC327	23p	MI491	1.45	BY211	51p
2N3702	12p	AC176	30p	BC328	22p	MI2955	£1.00	BY212	51p
2N3703	13p	AC187K	35p	BCY70	17p	MJE340	48p	OA47	6p
2N3704	15p	AC188K	40p	BCY71	22p	MJE370	65p	OA81	18p
2N3706	15p	AD143	68p	BCY72	15p	MI3271	75p	OA90	6p
2N3708	14p	AD161	90p	BC121	90p	ME20	90p	OA91	6p
2N3714	£1.38	AD122	30p	BD123	82p	MI521	70p	WO21A200	32p
2N3716	£1.80	AF106	40p	BD124	67p	MI2955	£1.00	BY164	57p
2N3771	£2.20	AF109	40p	BD131	40p	MIE3055	75p	ST2diac	20p
2N3773	£2.65	AF115	35p	BD132	50p	MP113	47p	40669	£1.00
2N3789	£2.06	AF116	35p	BD135	43p	MPF102	39p	TIC	29p
2N3819	37p	AF117	35p	BD136	47p	MPSA05	25p	CI06D	65p
2N3820	64p	AF118	37p	BD137	55p	MPSA06	31p	ORP12	60p
2N3904	27p	AF124	30p	BD138	63p	MPSA55	31p		

Prices correct at Sept. 1975, but all exclusive of VAT. P. & P. 25p.

RELAY UNIT

Smart steel case 12 x 7 x 4 1/2" with 22 PO Type relays, most with at least 3 sets c/o contacts; 4 reed relays+coils, 2 pots, resistors, capacitors, 12BH7 valve, various diodes, tag board etc etc. Only £3.50

ETCHING KIT MK II

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO etch resist pen, abrasive cleaner etching dish and instructions. Now also includes 2 miniature drill bits. £3.50

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb 80p; 3lb £1.80; 10lb £4.65; 100lb £35.

COMPUTER PANELS

Large quantity always available. 3lb asstd £1.50; 7lb £2.85; 50lb £15. Pack with about 500 components inc. at least 50 transistors £1.

7lb BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches, + PCB boards with transistors and diodes also loads of odds and ends. Contents always changing. Only £3.00.

POWER SUPPLY UNIT

G101: Mains transformer, 2A thermal cut-out, bridge rect, will give 1.7-10.5V output with 2 extra capacitors (provided). With data, only £1.30

TRANSFORMERS

All mains primaries. 6.0-6V @ 100mA 96p; 9.0-9V 100mA £1.02; 12.0-12V 100mA £1.08. 24.0-24V 500mA £2.20. A multirap to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, also 12.0-12 or 15.0-15 £3.60. 2A version £4.40. 6.0-6.0V 500mA £1.45; 17V 1A £2; 9V 10A £3.00; sub-miniature 12.0-12V @ 50mA 80p.

Send 10p Stamp for Illustrated Multimeter Catalogue (Free with orders over £3).

All prices include UK postage VAT @ 8% or 25% as appropriate. SAE list, enquiries. Surplus components wanted for cash.

GREENWELD (PW10)

51 Shirley Park Road Southampton, SO1 4FX. Tel: (0703) 772501. Also callers welcome at 21 Deptford Bdy SE8 01-692 2009, & 38 Lower Addiscombe Rd, Croydon 01-688 2950

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit)	Electronic Engineering Computer Electronics Computer	Transistor Technology CITY AND GUILDS Installations and Wiring CITY AND GUILDS
Electrical Engineering	Programming Colour TV Servicing C&G Radio, TV & Electronic Mechanics	City and Guilds Technicians CITY AND GUILDS Telecommunications Radio Amateurs' Exam etc. etc.
Electrical Installations and Wiring	General Radio and TV Engineering Radio Servicing Maintenance and Repairs	

To ALDERMASTON COLLEGE Dept. EPW-08, Reading RG7 4PF **EPW 08**

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate London, EC2Y 5EJ Tel: 01-828 2721

NAME (Block Capitals Please) _____


ADDRESS _____

POST CODE _____

Other subjects _____ Age _____

Accredited by C.A.C.C. Member of A.B.C.C.

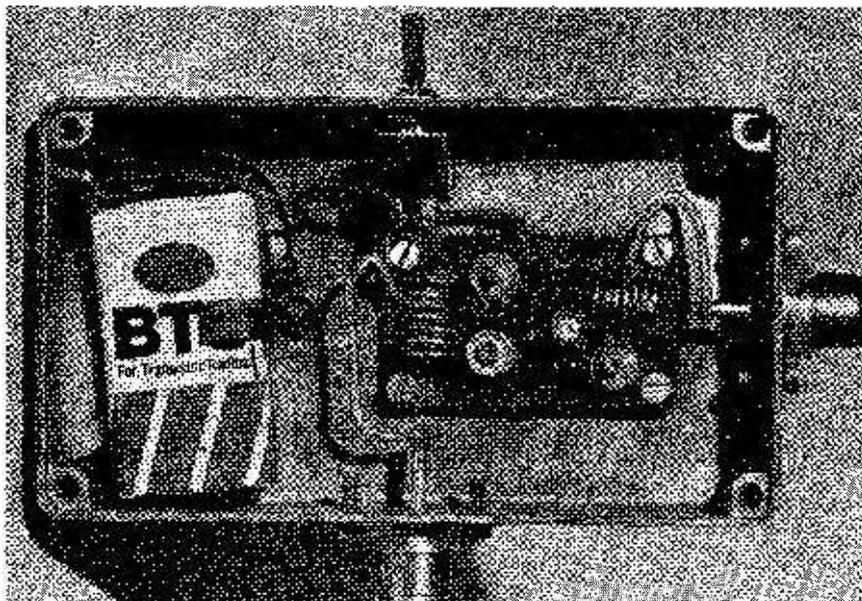HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



Interior photograph of the unit, showing details of the positioning of the PCB, the sockets and the on/off switch. The lid should be drilled to give access to VC1/VC3 for alignment purposes, as shown in the leading photograph.

mounting lugs of the variable capacitors, where a No. 52 drill must be used.

The coils should be close wound on a 6.3mm ($\frac{1}{4}$ in) drill, stretched to length before forming the leads and the taps fixed before mounting them as close as possible to the board. L1 should be wound inside the first three turns of L2 after the latter has been mounted on the board, putting the drill inside L2 as a former. Finally check the board for solder bridges, give a final clean.

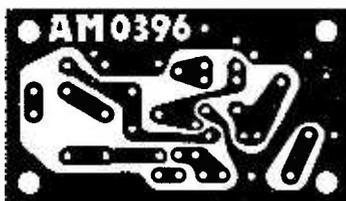


Fig. 2: Full size reproduction of the printed circuit board viewed from the underside. Holes for components are drilled with a No. 60 drill, while those for the variable capacitors are made with a No. 52 drill.

TESTING

Check that the current consumption lies between 1 and 1.5mA at 9 to 12V. If it is higher, adjust VC1 and VC2, for the chances are that the circuit is oscillating.

Fit the unit in a 115×64mm ($4\frac{1}{2}$ × $2\frac{1}{2}$ in) diecast box and complete the wiring to switch and co-axial sockets.

Neutralised preamplifiers are notoriously difficult to set up, but this unit has proved to be the exception. The simplest method requires a GDO as a test instrument, a normal converter and receiver together with a tuning wand. This is a thin rod of insulated material with ferrite on one end and brass on the other and is used to indicate whether more or less capacity should be used with a coil.

To begin, connect the aerial and converter to the unit, and, using the GDO dip L3 to the lower part

of the band using VC3, and then by adjusting VC1 and VC2, put L2 into the upper part of the band. Now switch on, use the GDO as a signal source and watching the S-meter of the receiver, adjust VC3 for maximum deflection, followed by VC2 and VC1. However, as all three adjustments are inter-dependent the optimum results are a matter for trial and error. Somewhere near the correct setting of VC1 the adjustment of VC2 will cause the signal to disappear completely and the correct setting of these two capacitors is when the output moves smoothly up and down as VC2 is moved to and fro. The tuning wand is a great help at this stage to indicate which way a capacitor should be moved, for when the setting is just right both brass and ferrite causes the same dip in the signal.

An off-air signal should be used for the final optimum setting of all three capacitors for optimum signal-to-noise ratio.

ALTERNATIVE METHOD

The second method requires a diode probe, a valve or FET voltmeter, a GDO and a source of RF. Load the input and output with 75Ω resistors and dip the coils as previously described. Now connect the diode probe to the *input* and feed a signal to the *output*, adjust VC2 and VC1 so that no output is indicated by the probe, dip the coils again and repeat the procedure until input and output are isolated and both coils on frequency. Final adjustments are made off-air.

There is still a final adjustment that can be made to improve the signal-to-noise ratio and this is by adjustment of the coupling between L1 and L2. In the prototype $1\frac{1}{2}$ turns seemed about right but it is worthwhile varying the coupling of the coils to find the position giving maximum signal and minimum noise.

THE NEXT ARTICLE IN THIS SERIES ON MINIATURISED 2m EQUIPMENT WILL CONTINUE WITH A LOW POWER FM TRANSMITTER.

TAKE 20

DAVID ANDREWS

No. 72 TRAFFICATOR AUDIO REPEATER

A series of simple transistor projects, using not more than twenty components.

WHILE some cars have trafficators which give out a strong clicking noise when they are activated quite a lot do not have this useful feature. If this is combined with the fact that on some cars the dashboard repeater lights are not very well positioned, or cannot be seen too clearly in bright sunlight, it should be apparent that there are lots of applications for this project which gives out a high pitched bleep whenever the trafficators are actuated. Although not excessively loud the sound emitted by the unit just cannot be ignored.

It is very easy to make and is simplicity to install, however, as is the case with a lot of car projects, it cannot cope for all types of car and therefore the unit will only work directly with negative earth cars with the flasher relay switch on the positive side of the dashboard repeaters.

Reference to Fig. 1 shows that the unit is a simple astable multivibrator which is directly coupled to a crystal microphone insert which is used, in this application, as a miniature loudspeaker. At the high audio frequency given out by the device a crystal insert proves very efficient. In theory any crystal insert will do but in practice there will be more output using a large diameter device. The prototype used an Acos type 43 which has the advantage of incorporating a smart gilt grille.

Diodes D1 and D2 are not seen frequently in multivibrators. They are there to protect the transistors from excessive emitter/base reverse voltages. D3 and D4 enable the unit to draw its power from either of the repeater lamps on the dashboard if the car is equipped with separate left and right hand indicators (the diodes are necessary to prevent interaction between the two sides). If the car has only a single repeater which operates whether turning right or left connect D3 to the lamp and omit D4 altogether.

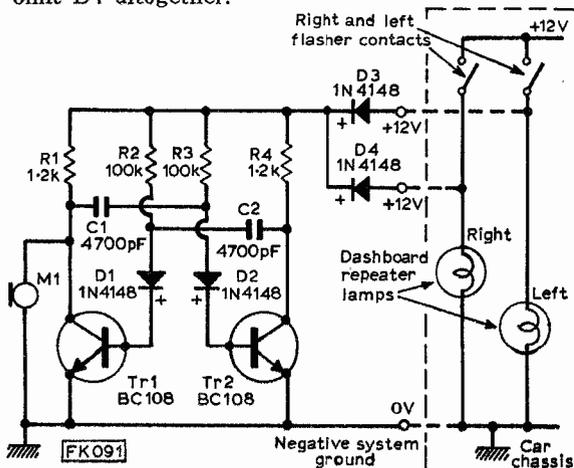


Fig. 1. Circuit of audio repeater and connections to trafficators.

When assembling the unit be careful to connect only the system earth to the aluminium box and make sure, if using the microphone insert specified that the earth connection (case) of the microphone is connected to the common emitter rail of the oscillator. The small board, Fig. 2, is bolted to the bottom of the box with 6BA bolts and spacing nuts.


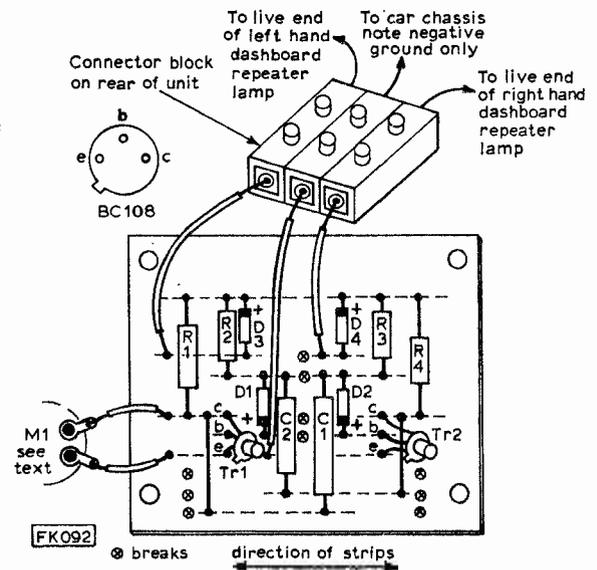


Fig. 2. Layout of components on Veroboard. NOTE: microphone case must be connected to chassis line.

For 6V systems the device will still work but the sound output will be slightly lower. It is quite easy to change the circuit to operate on positive earth systems by replacing Tr1 and Tr2 with a pair of general purpose pnp transistors (e.g. BCY70) and reversing the polarity on all four diodes.

★ components list

R1	1.2kΩ
R2	100kΩ
R3	100kΩ
R4	1.2kΩ
C1	4700pF
C2	4700pF
D1, D2, D3, D4	1N4148
Tr1	BC108
Tr2	BC108
M1	Acos Type 43 (Radio Component Specialists).
Connector block, Copper-clad Veroboard 0.1in matrix, 45 x 40mm. Aluminium box 75 x 50 x 25mm (3 x 2 x 1in) with lid.	

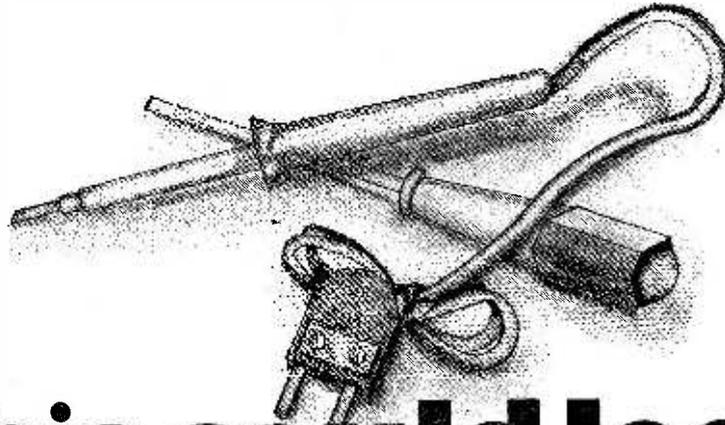

This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1

Build an oscilloscope.

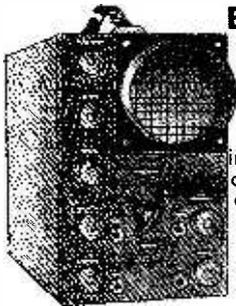

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2

Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

Carry out over 40 experiments on basic circuits.



We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS



FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WC/105
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)

DIABOLICAL LIBERTIES! With an antenna just 230 cm long!!—Only the WORLD RECORD PARTRIDGE VFA gets away with it—it works better in the clear ————— HONESTLY!!!

**These are VFA USERS claims, and remember, SWL's, A GOOD TRANSMITTING AERIAL IS AN EQUALLY GOOD Receiving AERIAL—You sure can't work 'em if you can't hear 'em!*

ZLIASY worked GC3EML on the 20m. band with **"JOYSTICK lying ON FLOOR OF SHACK!"**
G2BAH (ex G4CJN), Kendal, reports: "I happened to be listening on 80m. and heard someone in Manchester testing. We established a strength 8 qso each way. He had a *VFA laying on his kitchen table and was making tests to see if it would load up, etc. An old timer, a G2 and 2 letters, so he knew what he was doing."

G3ZDR worked a W3 on 20m. using a *VFA and a PM3A with 2 watts.

G3VFA worked WITW on 20m. using a *VFA and 750mW.

W6TYP worked WA6JPR over hundreds of miles on 40m. using *VFA and microwatts "equivalent to ONE MILLION!!! miles per watt of input power" (So says his WORLD RECORD achievement certificate).

P.W. "ON THE AIR" feature reports "Terry Gilbert sends a logging of a VERY RARELY reported station, Radio Afghanistan on 15195 at 1130. This goodie was pulled in via a Codar CR70A and "JOYSTICK!"

THE PARTRIDGE VFA SYSTEM to put YOU in the WORLD RECORD class is:—SYSTEM 'A' for modern Comm RX's **£32.76**: SYSTEM 'J' 500W P.E.P. 6 bands **£40.72**.

NEW! THE FLAT DWELLER'S ANSWER!! THE BIG BREAKTHROUGH—ENJOY THE ADVANTAGES OF OUTDOOR SPACE WITHOUT THE OUTDOOR SPACE!! SYSTEM RC1 (RX) £35.81; SYSTEM RC2 (TX/RX) £44.72: THIS IS ANOTHER PARTRIDGE FIRST—WRITE FOR DETAILS (7p).

(Each SYSTEM consists of the elegant gold stove enamelled 7' 6" VFA and a matching finish JOYMATCH A.T.U., despatched direct by parcel post—our risk). (All prices delivered—our risk). Prices subject to alteration without notice. COMMUNICATIONS HEADPHONES 8 OHMS **£4.82**; R.F. Field Strength meter (Jap) **£2.10** 9R59DS-DE, replacement valves incl. OA2 **£6.12**; A.G.T.U. Art earth **70p** plus radials **72p** each.

PARTRIDGE SUPER PACKAGE

COMPLETE RADIO STATION FOR ANY LOCATION. Comprising: Trio QR666 Gen. Cov. RX, Headphones VFA., System 'A', all connecting cables, del. (our risk)

£185.18

Send stamp for details and expert advice.


BOX 5



Phone 0843 62535
or 62839
(after office hours)
G3CED G3VFA



INVERTORS

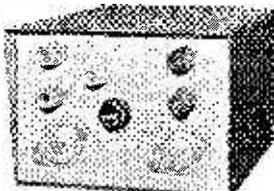

240v-50Hz from your 12v car battery.

25 watt—£4.20	150 watt—£18.10
40 watt—£7.35	300 watt (12v)—£29.85
75 watt—£10.71	300 watt (24v)—£23.75

All above invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) **£22.50+£1.10 p. & p.**

FLUORESCENT LIGHT INVERTOR KIT

8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats & secondary lighting for factories, hotels, etc.

12" x 9" watt—£2.90+25p p. & p. Built up **£4+25p.**

21" x 13" watt—£3.30+30p p. & p. Built up—**£4.50+30p.**


TRANSFORMERS & COILS

Both high volume & small order capacity available.

Special offer. Miniature mains transformer 12-0-12v-6V.A.—**35p** plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

ORION STEREO AMPLIFIER

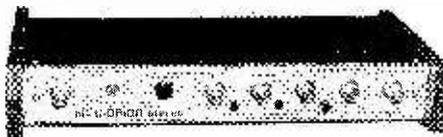


20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response ± 1 dB 20 Hz to 20 kHz. Hum level virtually nil with vol. full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner etc.

Complete kit of parts including slim line bookend case, silk screened front panel & knobs. **£43** incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

ASTRO IGNITION

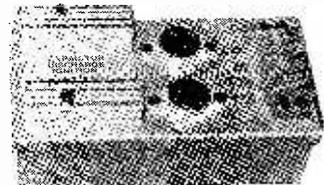


ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system **£9.50** incl. VAT. Ready built with only two connections to alter **£12.50** incl. VAT. Thousands have used this system both home and abroad. Consider these *advantages* more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker-burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

ASTRO ELECTRONICS,
Spring Bank Rd., West Park,
Chesterfield.

GOING BACK...

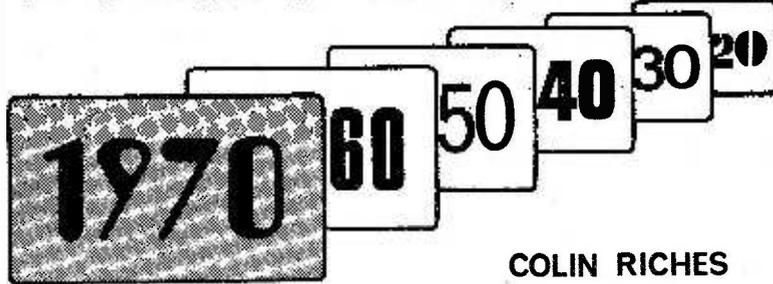

The Fultograph

THE Fultograph or picture receiving machine design was perfected by a Mr. Otto Fulton—hence its name and arrangements for a service were set up in October/November 1928 with the BBC.

The machine was designed so that it could be connected directly to the loudspeaker leads of a domestic radio receiver.

In earlier experiments at the broadcasting station, the picture to be transmitted was prepared as a transparency on a piece of film or as an ordinary black-and-white image. This was then attached to a cylinder and a fine pencil of light passed through it or directed on to it analysing it point by point by rotating the cylinder. The light which passed through the transparency or which was dispersed from the white parts of the photographic print was then directed on to a photocell which generated current according to the amount of

COLIN RICHES

light falling on to it. Thus, the black portions of a picture produced no potential at all, and the extreme white or transparent parts yielded maximum or constant potential.

The ensuing pulses of current representing the white areas on the transmitted image had then to be broken up into audio frequencies so that they could be fed through amplifiers and a modulator. This was accomplished either by putting a revolving serrated disc in the beam of light falling on the photograph or otherwise interrupting at audio frequency, the current flow which was controlled by the cell. This "carrier frequency" was intended to be one most suitable to LF amplification: 800-1000 Hertz. By this process, the image at the transmission end had to be in negative form, the cell becoming illuminated and the AF note sent out when it was required that a current should be obtained at the receiver for the purpose of recording the image.

As an alternative to using a photoelectric cell, the Fultograph system employed a transmitter in which a negative image in the form of an insulating gum deposit on a sheet of copper foil replaced the photograph or transparency.


The foil was wrapped round a cylinder and traversed line by line under a metal point so that the image was made to interrupt the current. Instead of a direct current, AC of 1 kilohertz was applied, introducing the necessary carrier frequency.

If one wished to use line illustrations which had no half-tones of white and grey, they appeared on the foil as insulating lines and areas.

In transmitting an actual photograph or a half-tone picture, the image was made on the copper through a line screen so that variations of light and shade were produced by a variation in the width of the lines in the same manner as the size of dots give black, white and variations of grey as we all know from newspaper photographs. Regarding the receiving end of the system, it can be seen that the HF signal was modulated in the same way as though a 1 kilohertz note were being made in front of a microphone, the light and shaded portions of the picture varying the intensity of the signal. After passing the receiver detector valve, the LF amplifier in the receiver was dealing with an AC of 1 kilohertz per second, varying in amplitude.

In the Fultograph receiving machine, the image was formed by the action of this current upon a chemical solution carried on an absorbent paper. As only DC could produce the desired chemical charge, rectification of the 1,000 Hertz AC accompanied by amplification was obtained by connecting the output terminals of the receiver to a rectifier valve. This valve, which was arranged as an anode-bend rectifier, suppressed half of the wave so the current in its anode circuit rose and fell in accordance with the changing light values occurring at the original picture.

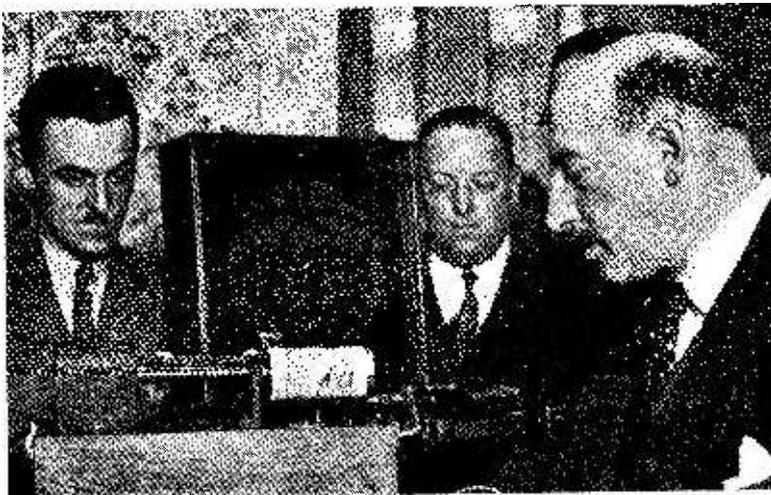A complete shutting off of the anode current of this rectifying valve, pending the arrival of the 1,000 Hertz note from the picture transmitter was obtained by supplying adequate grid bias. A milliammeter was fitted to Fultograph equipment for checking this



Otto Fulton, right, with some of his colleagues and early Fultograph apparatus.

adjustment which was normally accomplished by increasing the grid bias up to a point where the reading was almost at zero.

The electrolytic solution used, which was sensitive to current flow was potassium iodide. A current of a few milliamps applied for a brief period released sufficient free iodine which, in the presence of starch solution produced a deep blue colouring.


Similar screw threads on both transmitter and receiver gave a corresponding traverse of the revolving cylinders. A synchronising mechanism was included so that the cylinders revolved precisely in unison.

The following are notes from a Fultograph Instruction Manual:

Reception of Picture.— Just before the transmission an announcement will be made, following which there will be a tuning note lasting two minutes. As the Picture Receiver and loud speaker are connected in parallel, this tuning note will be reproduced on the loud speaker. It is now necessary to tune in the Receiver so that the strength is correct for picture reception. When the tuning note for picture reception is coming through, the reading on the milliammeter should be noted and the set should be detuned until the milliammeter reads 3 to 3.5, preferably by reducing reaction.

After the tuning note, three "V's" will be transmitted as follows: ···—, ···—, ···—. After the last "V" there is five seconds' interval, during which time the brake controlling the clockwork motor is released. This is effected by raising and giving a quarter turn to the round ebonite knob on the left-hand side of the Picture Receiver. The motor will then start. The drum, however, will not start revolving at once as this is automatically controlled from the transmitting station and the drum will only revolve when and while the picture transmission is in progress. The formation of the picture can now be watched while the Stylus travels slowly across the paper. It will be noted that the roller stops and starts once in each revolution. This is controlled by the transmitting station and ensures synchronisation.

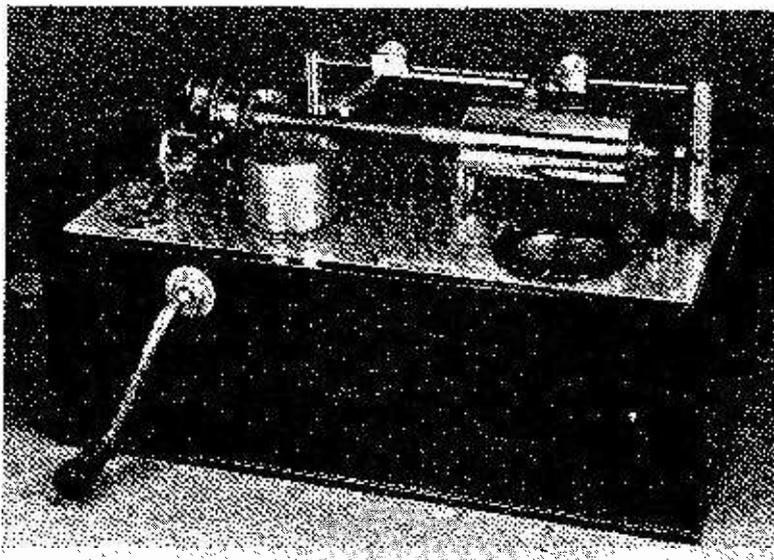Synchronisation Setting.— The setting of the motor speed control on the side of the Picture Receiver is not critical, but must be set so that the drum revolves rather faster than the drum at



Fultograph equipment constructed in the 1920's by one of our readers.

the transmitting station.

Fully wind up the motor. Put the switch on the Relay Panel in the "on" position. Remove the negative lead to the grid bias battery. The drum will now revolve continually. Count the number of revolutions per minute and adjust so that there are about 56 per minute.

When the setting is correct and a picture is being received, the drum should stop momentarily and start again once during each revolution. The pause should be very brief.

If the setting is too slow, the drum will revolve continually without this brief pause.

If the setting is too fast, the pause will be too long. The whole picture will be reproduced higher up on the paper so that the top of the picture may not appear at all, and in any case the whole picture will be elongated and distorted.

Speed adjustment need be made only once when the Fultograph is being used for the first time.

After Reception of a Picture.— At the conclusion of the picture, the drum stops revolving automatically and the switch on the Relay Panel should be moved to the "off" position, and *after this* the motor should be stopped by the knob on the left-hand side of the Picture Receiver.

The paper should then be removed and dried as quickly as possible. The ideal method is to put it before an electric fire so that in about two minutes it has

dried completely. A gas or coal fire may be used, but it is possible that the chemicals on the paper may be adversely affected by fumes. To increase the permanence of the picture it is advisable not to expose it immediately to very strong light, and it may also with advantage be kept between the leaves of a book until the following day.

The same procedure should be followed for the next picture and one minute will be given between each to enable you to wind up the motor and fix a fresh piece of paper to the drum. As about five minutes is required for drying, it is best to prepare the first piece about that time before the transmission begins. A fresh piece should then be prepared just before each picture, and can be left to dry while the picture is being received. It will then be ready for the next.

Trouble is sometimes experienced through low frequency oscillation. This may be due to run-down batteries or magnetic coupling between the Fultograph and the wireless set. The symptoms are continual rotation of the drum without pause while an attempt is being made to receive pictures and also, instead of a picture forming on the paper, the needle makes a continuous brown mark. The remedies are as follows:


- (1) Reverse the leads between the loud speaker terminals and the relay panel.

continued on page 501

Complete your
Hi-Fi system
with our

TV sound tuner

**IN NEXT MONTH'S
PRACTICAL
WIRELESS**

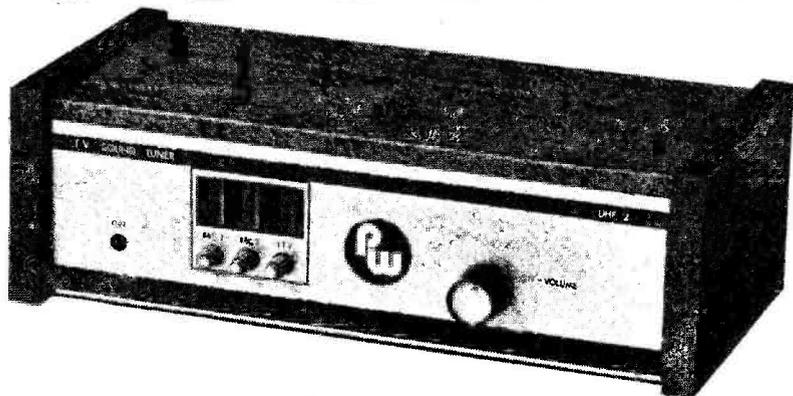

Does your TV sound let you down? Then build the PW TV Sound Tuner and get the full benefit of the broadcast sound. The Tuner uses a push-button varicap tuner for instant channel selection and provides an output level suitable for hi-fi amplifier or tape recorder. Needs no connection to the TV itself!

+ *another 8 page
supplement*

**SIMPLE HOME
PROJECTS No. 2**

FM TUNER DIGITAL READOUT



See at a glance the exact frequency to which your VHF tuner is set with the PW Digital Readout. Gives three figure accuracy and includes a special tuning aid for easy selection of main broadcast stations.

+

All your regular features

ON SALE IN OCTOBER

IMPROVE YOUR BUDGET STEREO SYSTEM

PART 1

B. BARNARD

FEW readers can afford the £300 to £400 worth of equipment that seems to be essential for true hi-fi. Many have to settle for something in the region of £100 and try to pretend that there is nothing better. But sooner or later we find it is not really good enough and we have the urge to start to try to bring our "budget" outfit up to a better standard. A serious snag about true hi-fi equipment, apart from its price, is that it represents the ultimate and the true enthusiast finds no challenge to his skill and ingenuity. All that is left is to keep up with the Rothschilds' and to trade-in hundreds of pounds worth of equipment and replace it with something more up to date, good for trade but murder for the pocket!

The author describes in some detail the cheap but effective improvements he was able to make to his Budget Hi-Fi System. Some or all of his ideas can be adapted for use on any similar system. Read and choose for yourself.

For all these reasons, but particularly the financial one, I chose and bought a unit audio system of well-known make. Unit audio because I prefer to have all the works in one box but mainly because I considered the styling to be outstandingly good. The recommended retail price at the time was £100 but I paid just £80 for it "cash and carry". For this not very princely sum I took home a LW, MW and FM radio, a Garrard SP25 playing deck and two attractively teak-housed two-unit loudspeakers.

FIRST IMPRESSIONS

Examining the specification I found that it included a stereo decoder (good), 6 watts per channel (sufficient for my purpose), ± 1.5 dB from 55Hz to 23kHz (quite good), a ceramic cartridge (not so good) and less than 1.5% total harmonic distortion (it all depends on what is meant by "less than"). I admired its appearance and tried a record or two. Pop records came across most impressively; there was terrific "presence" and with the volume control only halfway up we had almost reached the threshold of pain! The trouble with pop records is that one is never quite sure what the original sounded like so it was not possible at this stage to decide what sort of "fi" we were listening to. A visit to the room above

the one in which it was playing however quickly gave a clue to this. All one could hear was a regular "thump, thump" tuneless noise—"one note bass" is what they call it and not without reason.

At this stage, let me make it quite clear that there is no criticism of the manufacturer implied in all this. He had produced an instrument that did all he claimed for it, capable of giving first class entertainment. But the subtleties of Beethoven and Brahms were beyond it. I therefore set about upgrading and improving it so that I could listen to the kind of music I wanted, but always within a strict budget. I wanted the best possible results for a few pounds, for there is no point in spending, say, another £100 on such a project if you find the total exceeds the money you couldn't afford in the first place.

CHANGING THE CARTRIDGE

I am sure it is generally known that you cannot simply remove the ceramic cartridge and replace it with a magnetic one. If anyone is not convinced, I suggest they try it. The result will be very weak output, totally lacking in bass although, unless the ceramic was a very good one, there will already be the promise of greatly improved reproduction.

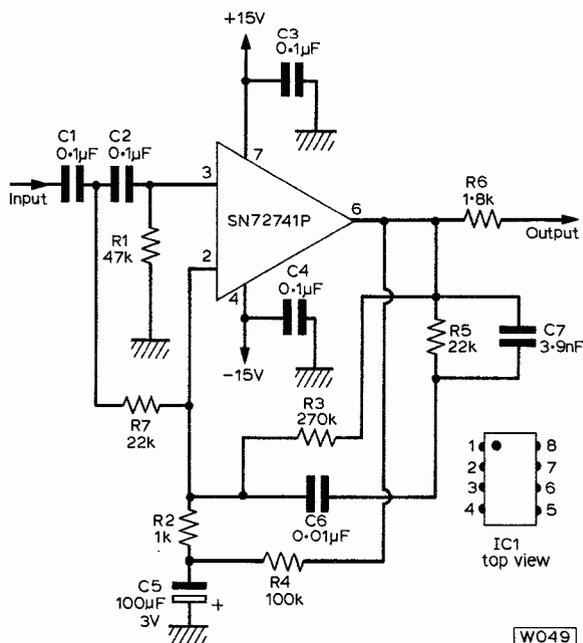


Fig. 1: Circuit of one channel of the new pre-amplifier added to the existing system.

Because of the much lower output and the electrical characteristics of the magnetic cartridge, a pre-amplifier is essential. This amplifier will not only boost the signal overall but is designed to give much greater amplification to the lower audio frequencies. The problem arises regarding space in the average unit audio for fitting extras like the preamplifier and its associated power supply. The central area of my chassis is quite unoccupied and leaves generous space for fitting additional units. The only real problem is headroom and one has to be extremely careful not to fix additional items in such a position that the record playing mechanism fouls them when the whole thing is reassembled.


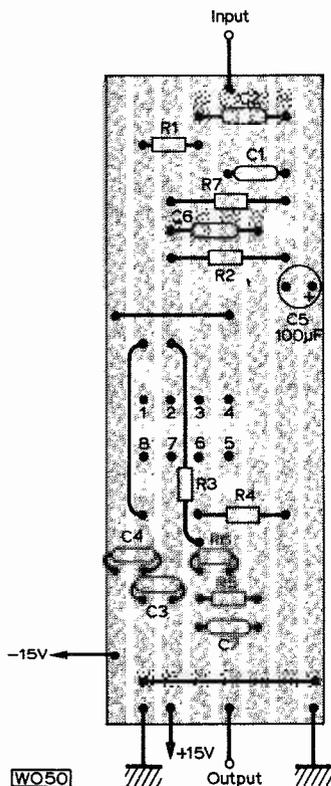


Fig. 2: Layout used by author for the pre-amplifier. Note that this layout is duplicated using a common board, see photograph.

The photograph shows the amplifier in place on the chassis held by 4BA bolts through holes drilled in the chassis. A sheet of insulating material (optional) is placed over them, nuts holding it in place, acting as spacers to prevent the print side of the amplifier board touching the chassis. The amplifier should be located to keep the input leads from the cartridge as short as possible.

POWER SUPPLY

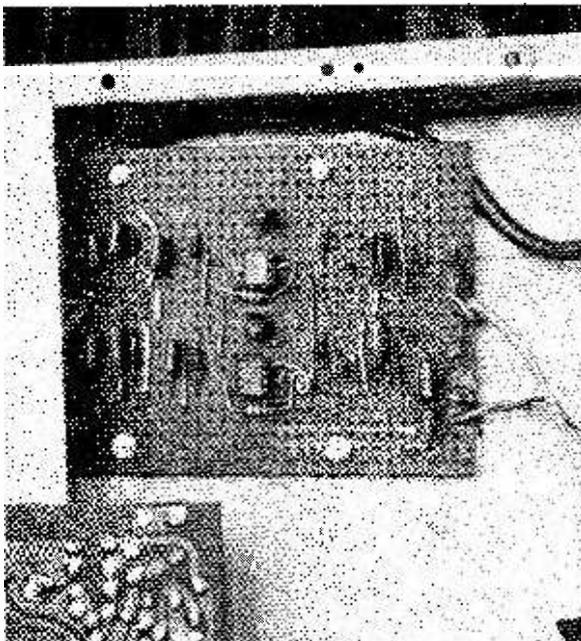The next item is the power supply unit for the preamplifier; +15 and -15 volts are required and it is seldom possible or wise to attempt to get this from the main supply system of the equipment. I used Veroboard for this as well. The circuit is given in Fig. 3. Notice that two zener diodes are used to prevent the DC volts rising above 15V as the ICs are rated at 18V maximum.



The finished stereo pre-amplifier board lucked away in an unused corner of the chassis.

The preamplifier circuit used is a direct copy of the PW "Texan" first stage except that I have wired in the rumble filter permanently. This is optional but I did it on the principle that any sounds emanating from the unit after the modification, below about 40Hz, were most likely to be undesirable and should be eliminated from the start. The circuit is shown in Fig. 1 and the amplifier is constructed on Veroboard, Fig. 2. I have used the 0.15in. board as I wanted to be able to make modifications and resoldering on fine pitch board is not easy. However, the IC holders do not fit into the Veroboard holes and wire connections have to be made to the pins, the holders then being bolted with 8BA nuts and bolts to the board. These connecting wires are then passed through the appropriate holes and soldered to the copper strips.


Constructors may prefer 0.1in. board, in which case both amplifiers can be accommodated on a piece of board about 85 x 75mm (3¹/₄ x 3in). Considerable liberties can be taken with this layout without affecting the performance of the amplifier.

Locate the power supply unit as close to the mains transformer of the equipment as is practicable. Apart from simplifying the wiring on the AC side, it is a source of AC magnetic field and it undoubtedly helps to have all such sources close together as will be clear later on when discussing the problems of mains hum. At this point connect the input and output of the amplifiers with screened leads to the cartridge (via tags on the gram deck) and the main amplifier respectively. Next connect the power supply unit taking the greatest care that the polarity is correct. The positive tag on both preamplifier and power unit should have been definitely identified and marked before connecting. A mistake at this stage will result in the immediate ruin of both ICs, so it is worth taking pains to get it right.

Before fixing the record playing deck into its normal playing position, some simple tests are required. Connect both loudspeakers and mains, switch on, putting the control switches or buttons in the "Gram" position. Check the +15V and -15V

circuits. If hum is present there is a fault condition unconnected with the work so far done and it must be found and cured at this stage.

Now switch to Gram and with the bass control at full boost and increasing volume slowly to maximum, listen for hum. As the cartridge coils are now disconnected they cannot contribute anything, so any hum is most probably coming from the input wiring of the preamplifier. Check that, where the input leads and output leads to and from the preamp protrude from their screens to make connections, they are **very** short and that the screens are properly earthed. If this does not produce a cure it may be necessary to make up a screen to cover the preamp. A screen of this type is not very difficult to construct but it should completely cover the preamp and be securely bolted to the chassis.

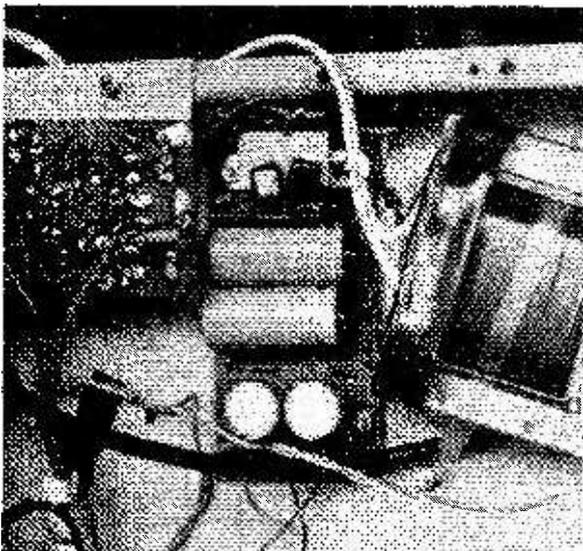

The power supply board is in the centre of the photograph. The mains transformer has been re-orientated to reduce hum, as described in the article.

Mu-metal is ideal for this as it is easily cut with tinsnips and bent to the required shape. A fairly reliable source of mu-metal is any ex-government surplus store selling screens used for radar tubes. This will give enough metal for this and any other screening that may be found necessary in future work. This screen will completely remove the small amount of hum that is present under these test conditions. It is essential to get rid of it, as every little helps, but it has of course not done anything on the main problem of hum pick-up by the magnetic cartridge. There are two obvious points of attack in curing cartridge hum pick-up. These are the mains transformer or the cartridge, or both.

CARTRIDGE HUM

I started with the cartridge, which is a Goldring G800 and already has a mu-metal screen included in its design. It seemed reasonable to suppose that if this screening were made complete, then the cartridge could be completely protected from the AC field. I made up a small rectangular screen from mu-metal that completely enveloped the cartridge body. It wrapped around the cartridge and "tucked-in" between the cartridge and its carrier. I also made up an even smaller screen to clip on the front, just

over the stylus. The additional weight was easily overcome by adjusting the counterbalance at the far end of the arm. The arm and cartridge mass was of course increased but as this tends to reduce the frequency at which it resonates with the compliance, it cannot be of any serious consequence.

The results were very enlightening and instructive but not sufficiently successful to warrant further work in this direction. There was unacceptable hum in the left-hand channel when the pickup arm was in the rest position; the hum disappeared completely during the tracking of most of an LP record but re-appeared loudly in the right-hand channel during the last few inches of the record grooves. Clearly, even this comprehensive screening of the cartridge left "windows" through which one coil or the other could "see" the 50Hz field. Despite this rather disappointing result, it was well worthwhile as it taught me a lot about the nature of the field in this application and of what to expect and what not to expect from metal screens.

TRANSFORMER TROUBLES


After this rather disappointing result, I shifted my attention to the obvious source of the trouble, the large mains transformer supplied in the equipment which supplies power to all stages except our newly-fitted preamplifier. I recalled that the external magnetic field was causing all the trouble but unfortunately, with unit radio, it is not possible to turn the transformer around to try different positions while the instrument is switched on and the playing deck is in its working position. However it is possible to achieve much the same thing by the following simple expedient.

The mains transformer is completely removed from the chassis. Primary and secondary leads are extended outside the instrument to the transformer which is now mounted with woodscrews to one end of a short piece of board. This piece of board is used



The mains transformer is fixed to a piece of wood and moved around outside, the best position noted being on the paper underneath.

as a "handle" to orientate the transformer in all directions, lateral and vertical. The transformer on its board is placed outside the cabinet but as close to its normal fixed position as possible. It is thus, in relation to the magnetic cartridge, only two or three inches disposed from its original position inside the instrument. A piece of plain white paper is placed beneath the transformer and extends to the cabinet side. The photograph shows the general arrangement and it may be noted that this is really a temporary arrangement of that already described for fitting the transformer permanently outside.

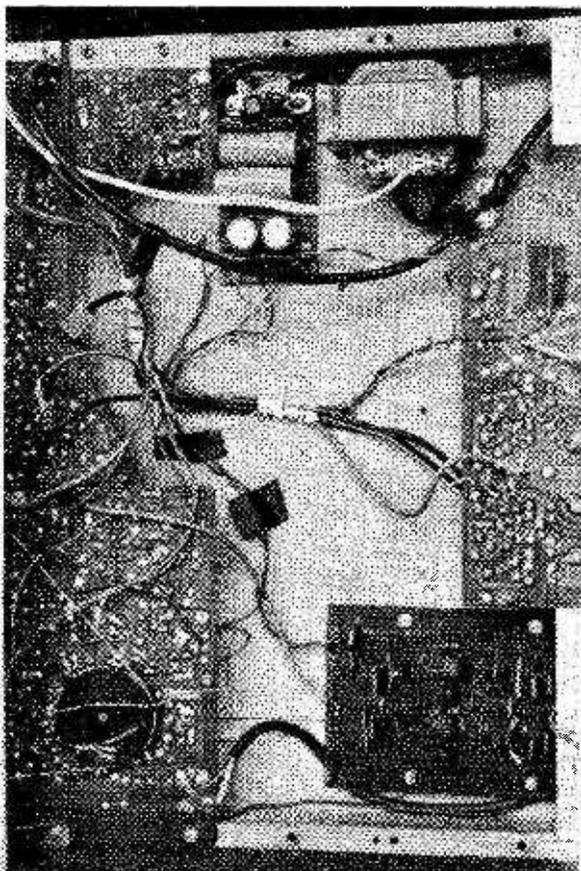

New power unit, top centre, and new preamplifier board, bottom right, fitted and tested before the experiments with the transformer.

Using the top edge of the board as a handle, turn the transformer first laterally, then vertically and with boosted bass and volume well up listen for the position of minimum hum. It is usually well-defined and holds for approximately ten to fifteen degrees of arc. Holding the transformer by its board in this position, mark on the paper with a pencil the angle the transformer casing makes with the cabinet side. At the same time note carefully the orientation of the transformer windings as this and the angle must be carefully reproduced when the transformer is remounted on the chassis inside the cabinet.

There are of course certain safety precautions to take when carrying out this work. The normal primary connections to the transformer are disconnected and taken to two terminals of a four-way connecting strip which may conveniently be bolted to the chassis using one of the holes through which

the transformer holding bolts are passed. The connections from the power unit which normally go to the transformer secondary are taken to the second set of terminals. Two lengths of mains flex are then taken from the connecting strip out through the cabinet for connection to the transformer via another connecting strip which must be securely screwed to our piece of board. With normal precautions there is now no danger of short circuits, open circuit or electric shocks. Having found and marked the angle and noted the orientation of the windings all this temporary wiring can be dismantled. The piece of paper with the angle marked on it is now cut out and stuck with Sellotape in the required position on the chassis and the transformer is remounted in its new position.

RESULTS SO FAR

I was delighted and relieved to find that this new transformer position more than fulfilled the requirements of hum-free reproduction on Gram. With volume far above normal listening level (and I do like to hear a symphony orchestra!) and bass boost which would only be acceptable in the jungle, there was no audible mains hum at all. A photograph shows the finished job. Keen eyed readers will notice that the transformer is held in position by a nylon strap and two nuts and bolts. Personally I find this adequate but some experimenters will no doubt prefer to make up suitable metal fixing brackets.

What have we got as a result of this work? Very acceptable reproduction, but we still have that terrible bass! How much have we spent? The cost of a G800 plus the components for making the pre-amplifier and its power unit are quite reasonable I believe. There are still other "budget improvements" required improving the bass, fitting an inexpensive tuning meter (which I believe is almost an essential) and the much-disregarded and extremely important matter of achieving and maintaining good tracking on gramophone records. I will deal with these matters in a subsequent article.

CQ! CQ! CQ! CQ!

ISSUES WANTED

- .. November 1973, December 1973 and January 1974 issues of P.W.—C. R. D. Croney, "Hastings Lodge", St. Matthias Road, Hastings CH. CH., Barbados, West Indies.
- .. January 1975 issue of P.W. with Part 1 of Model Control by Radio.—G. Greenshields, Eliock House, Sanquhar, Dumfriesshire, Scotland.
- .. P.W.'s for August 1972, March 1974, November and December 1974, January 1975.—Nigel E. Bacon, 51 Dares Walk, Hinckley, Leicestershire.
- .. February and April 1973, November 1974.—S. Reid, 6 Culloden Crescent, Arbroath, Angus, DD11 1JX.
- .. October 1973 P.W. containing Datacards 1 and 2.—Charles Burnham, 5 Berwyn Close, Marchwiell, Wrexham, Clwyd, Wales.
- .. August 1974 P.W. and January 1972 to June 1974 Television. Also August 1974 to October 1974 Television.—M. A. Hickman, 53 Larkhill Lane, Liverpool, L13 9BL.
- .. October 1974 issue of P.W.—E. O. Bennett, 35 Stephen Hill Road, Crosspool, Sheffield, S10 5NQ.

Practical Wireless, October 1975

AIDS to IMPROVED RECEPTION

PART 1

C. HEATH

ANYONE wanting to carry out serious listening on the short wave bands, amateur or broadcast, generally ends up possessing a 'communications' receiver. So the natural question to ask is 'what has the comm. receiver got that the ordinary set hasn't?' The best way to answer this question is to relate the deficiencies of the latter and it is hoped that this short series of add-on projects will go some way towards overcoming these deficiencies. However, it must be clearly understood that a good comm. receiver is a complex bit of equipment with each stage designed to carry out its particular function as efficiently as possible while working with its associated stages. Add-on units can only be a compromise at best but they will give the listener some idea of what he can expect from a real comm. receiver.

A basic superheterodyne receiver, Fig. 1, will have

a mixer stage, one or more intermediate frequency (IF) stages, an AM detector or demodulator and one or more audio amplifying stages, usually feeding a loudspeaker. Because the mixer can produce the same IF from two differing signal input frequencies the unwanted (second channel) station can interfere with the wanted one. Similarly, stations can appear on the dial, due to second channel effect, that ought not to be there, making a cheap receiver seem a better performer than it really is! A tuned amplifying stage ahead of the mixer will go a long way to eliminating second channel problems.

The IF stages provide most of the gain in a receiver but at the same time they should reduce the bandwidth of the IF channel to the minimum necessary to pass the signal without, in the case of speech, detracting from its intelligibility. For high quality AM signals, including music, this bandwidth


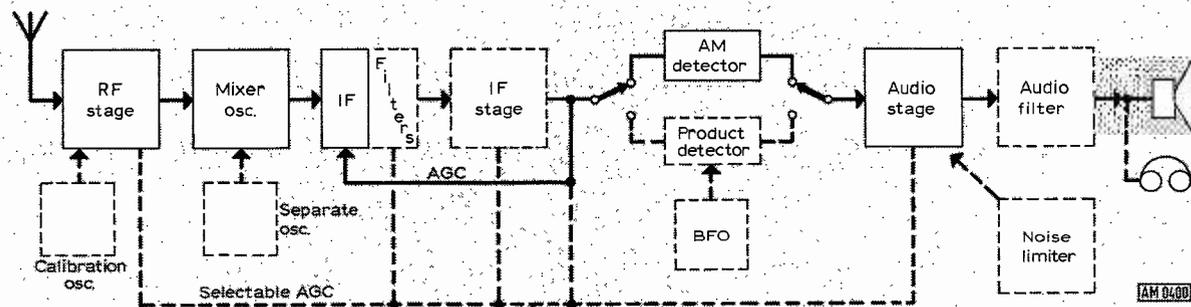


Fig. 1: above, shows the stages of a basic superhet receiver (solid lines) with the extra facilities to be expected in a communications receiver (dotted lines). Fig. 2: left, compares the IF response curves of the two receivers.

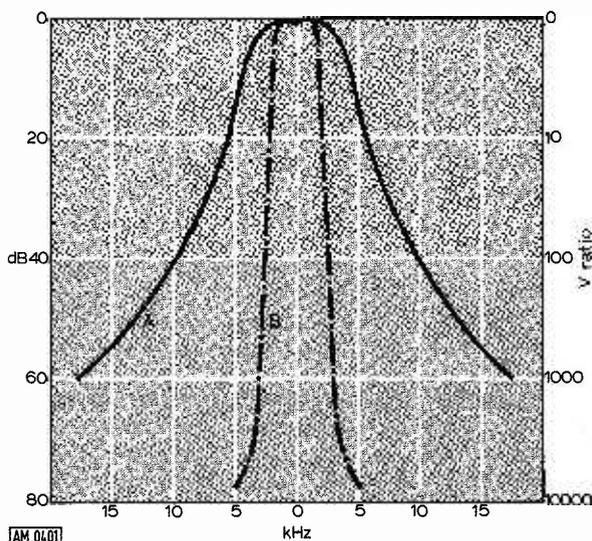

may be 9 or 10kHz but, at the other extreme, 50kHz can suffice for CW (Morse) signals! So a choice of bandwidths is essential, generally using switched crystal or mechanical filters.

The simple receiver with one or two IF stages using ceramic filters will have a bandwidth of 4 or 5kHz but its response, moving away either side of the centre frequency, will be excessive and quite unacceptable for any other reception mode. A good filter will have 'skirts' which fall away very rapidly indeed outside the required passband, Fig. 2. In an expensive comm. receiver there may be separate switched filters for upper and lower sideband on SSB, AM and another for CW.

A simple superhet will probably have a diode to demodulate the AM signal, followed by a filter to remove any remaining IF component; four components at most! In a comm. receiver a beat frequency oscillator (BFO) is used to enable the

demodulator stage to resolve SSB and provide a beat note on CW. The diode detector can be used for these two modes as well as AM but the relative levels of signal from the IF stage and the BFO are quite critical for proper resolution of SSB so that in a comm. receiver a separate product detector (PD) circuit is employed for SSB and CW only. The BFO may take on the more sophisticated name of 'carrier insertion oscillator' (CIO). The simple BFO added to a receiver will not be all that effective on SSB since the signal levels are seldom taken into account, and the stability of the BFO will leave a lot to be desired.


While a simple audio stage and speaker will suffice for AM on an ordinary set the comm. receiver's audio stages will have a frequency response carefully matched to that part of the speech frequencies which convey the most information, usually 300Hz to 3kHz. There may also be a very narrow audio filter for use on CW, with a centre frequency around 1.5kHz. Other features on a comm. receiver will include an excellent dial easily resettable to a particular frequency plus electrical or mechanical adjustment of the dial to permit correct calibration against an internal crystal controlled frequency standard on 100kHz or even 25kHz.

The AGC circuits will have separate characteristics for AM, SSB and CW, automatically switched in by the mode switch. There will be a tuning or 'S' meter indicating relative signal strength and, finally, there will be a headphone socket! A small point but a very important one. A lot of money may have been spent on a comm. receiver in order to get the best signal-to-noise ratio (electrical) only for the audio to be fed to a speaker located in a situation where the signal-to-noise ratio (domestic) is frequently less than unity!

AERIAL MATCHING UNIT

THE AMU is most helpful when relatively short aeriels are used in the HF and medium wave bands. An improvement of several S-points is possible, compared with the same aerial used untuned. The coil is 70 turns of 26SWG enamelled copper wire on a 40mm diameter former, space wound in the 3, 4 and 6 turn sections. Try various tappings and adjust VC1 for best results. A crocodile clip or wafer switch connected to the taps allows the number of turns to be changed quite easily.

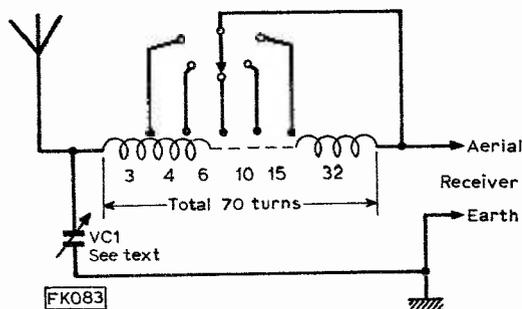The unit can be built in a plastic box, with terminals or sockets for external connections, but a metal box is preferable. Fit a simple dial, marked from 1 to 10, and number the tap positions. Once




the correct positions have been found for a particular band the numbers can be recorded for rapid reference.

Variable capacitor VC1 can be 250pF or 500pF or the two sections of a standard 208+176pF gang connected in parallel.

INPUT ATTENUATOR


WHERE strong signals cause overloading, cross-modulation or cause the receiver to perform inadequately on CW or SSB, an input attenuator provides a possible solution. A 470Ω carbon linear potentiometer is suitable for 75Ω to 600Ω input impedance receivers. It gives as much as 40dB attenuation at around 15MHz and greater values at lower frequencies. Attenuation is less on HF bands where RF leakage reduces the efficiency.

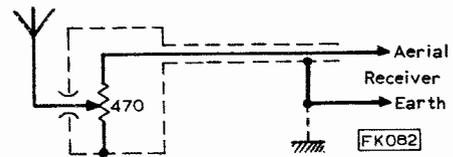If the connecting lead is short and kept clear of the aerial proper, the attenuator may not need screening. The attenuator can be fitted inside the receiver or in a separate metal box—with a coaxial lead to the receiver, the preferred arrangement.



TUNING METER

A TUNING METER helps accurate tuning, shows if changes to aerial or earth systems increase signal strength and helps in alignment where optimum adjustment of circuits will usually agree with the maximum meter indication. The BC107 NPN transistor is used for receivers using PNP transistors and positive earth line. Increasing signal strength moves the AGC line positive, reducing receiver gain, thereby increasing the meter reading. The OC71 PNP transistor stage is for receivers with a negative earth line and NPN transistors.

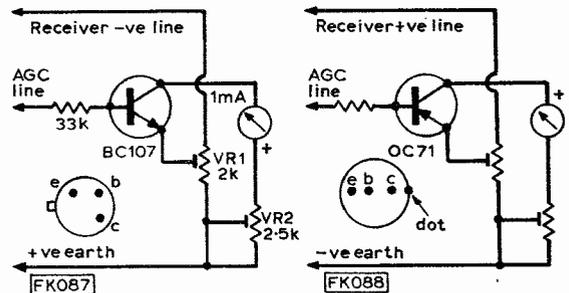


Pre-set potentiometer VR1 is set so that the meter is reading zero with no signal, preferably with aerial and earth shorted together. The sensitivity control VR2 is necessary for receivers with varying degrees of AGC action. The meter and components can be fitted inside the receiver or in a separate box,

which is more usual, to avoid the problems of cutting a large meter hole in the panel. Meters calibrated in 'S' units are available but remember that the indication is purely a relative one, the sensitivity varying with the sensitivity of the receiver at any particular frequency.

FREQUENCY MARKER

THE marker provides a stable signal at 1MHz intervals and the harmonics may be used to 30MHz or higher. Receivers can be calibrated at 1MHz points enabling bands to be located. One frequency on each waveband must be identified by reference to known stations and points can then be counted off, upwards and downwards, from this. Standard frequency transmissions on 5 and 10MHz furnish ideal identification points and allow precise adjustment of the marker frequency by means of the 50pF trimmer.

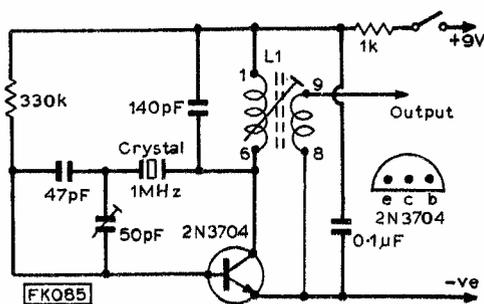


The signal produced is an unmodulated carrier which will register on a tuning indicator or S-meter or heard if a BFO is fitted. Coil L1 is a Denco Yellow Range 2 coil and its core is adjusted for lowest battery current consistent with reliable starting when switching on. The output lead is placed near the receiver aerial lead or it can be connected to the receiver aerial socket through a small capacitor, say 47pF.

The unit can be built into a receiver or in a separate plastic or metal box. A PP3 9V battery will be quite adequate for the low, intermittent drain.

HF BANDS AMPLIFIER

SOME receivers give poor results above about 14MHz so using the amplifier shown here can improve reception by several S-points. It tunes from about 13 to 24MHz. Coil L1 is wound with 20SWG copper wire on a 40mm diameter former. It has 13 turns in all, tapped at 2 turns up for the base connection and 6 turns up for the aerial. Choke RFC must be clear of L1 and at right angles to it.

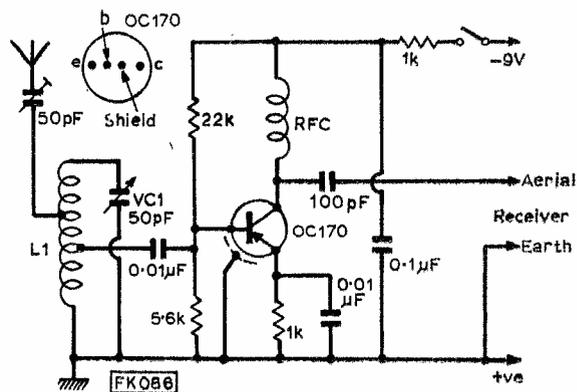
The amplifier is built in a small metal box, with reasonably short connections. The output lead should be as short as possible, preferably coaxial cable, if very short. Capacitor VC1 peaks up signals. If the receiver has good AGC action, switch the AGC off when setting VC1 for a particular band, or watch the tuning indicator for maximum signal unless signals are very weak.



Do not omit to connect the shield of the transistor to earth or instability may result. The series aerial trimmer should be adjusted so that a reasonably sharp peak is obtained when tuning VC1 on a signal.

BEAT FREQUENCY OSCILLATOR

A COMMUNICATIONS receiver has a BFO so that CW (Morse) and SSB (single sideband) transmissions can be resolved. The coil is wound with 40SWG enamelled copper wire, on a 7mm former with an adjustable core. Winding 1-2 has 200 turns, occupying about 9mm. Winding 3-4, wound in the same direction has 40 turns, just clear of the larger winding and taking up about 3mm. This BFO is for receiver IF's of around 465kHz to 470kHz. If oscillation is not obtained, check that the phase of the windings is as shown.

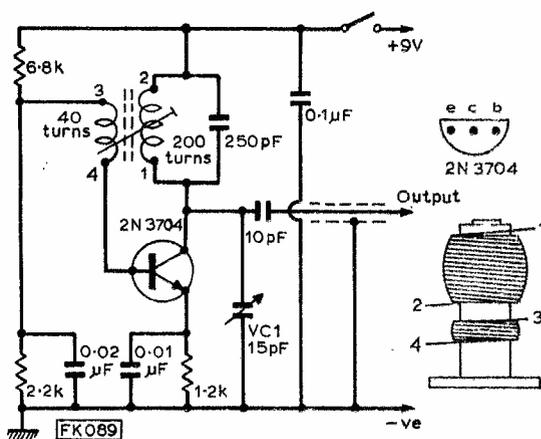

The output lead, preferably coaxial cable, is placed near or connected to the last IFT at the demodulator diode. A few tests will show the best degree of coupling. Rotate the coil core until a strong whistle is heard on all AM signals tuned in, when variable capacitor VC1 is rotated either way from the half open position. VC1 is then adjusted for best results with CW or SSB, but the BFO must be switched off for AM.

If the BFO is built into a receiver it should be completely screened to prevent the signal from affecting the AGC circuits.

continued on page 492

PRODUCTION LINES

colin riches

SINCLAIR'S LATEST



Sinclair announces a major British technological breakthrough for its new mains/battery Scientific Programmable Calculator.

At £29.95 including carrying case, mains adaptor and VAT, this latest model sets a new price level for programmable calculators. This price has been achieved because the machine is based on a single chip which is designed by and exclusive to Sinclair. It is the first programmable calculator to be operated on a single integrated circuit.

According to Roger Helmer, Sinclair Marketing Manager, the Scientific Programmable has been developed particularly with scientists, students, engineers and statisticians in mind. He comments "This calculator is especially designed to dramatically lighten the load for those who have repetitive calculations to perform, for example the analysis of experimental results."

"This ability to perform calculations repetitively makes it an enormously powerful tool for solving equations and evaluating integrals by iterative methods and an enormous variety of other mathematical applications."

Programmes, of up to 24 steps, which are entered directly through the keyboard are stored ready to operate on any numbers which are subsequently entered.

Number entry can be in scientific notation or fully-floating decimal point. All results—appearing in large green digits on the fluorescent display—are in scientific notation with a 5 digit mantissa and 2 digit exponent, both signable.

Sine, cosine, arcTangent, (all in radians), \log^{10} , $\text{antilog}^{10}(10^x)$ scientific functions are all directly available and arcSine, arcCosine, tangent, degree conversion and \log_e are readily derivable.

In addition to the four standard arithmetic functions $+$, $-$, \times , \div , the unit also gives x^2 , $1/x$, square root and sign change. It has a memory with three separate memory operations, store, recall and exchange and the post-fixed operators (reverse Polish logic) are ideal for full-flow chain calculation.

The Scientific Programmable is housed in a matt black case 153 x 76 x 25mm and features simple two-level keyboard operation with all facilities including programming available from just 19 click-action keys. Power is from a PP3 battery or from the mains via an adaptor.

Sinclair Radionics Limited, London Road, St Ives, Huntingdon, Cambs PE17 4HJ. Tel: (0480) 64646. Telex: 32250.

MARANTZ AMPLIFIER

Pyser Limited, the sole UK distributors of Marantz equipment tell us that the 1040 amplifier will shortly be available at £132 plus VAT.

It has a power output of 20W RMS per channel into 8Ω and there is a remote speaker switching facility with 'ambiance' to give 'realism' when using four speakers. There is tape monitoring circuitry for two decks, loudness compensation, mode switch and an HF filter.


In America, Marantz have found that large numbers of the 1040 are purchased by students on limited budgets but their Executive Director states that he is confident that in Britain the 1040 will be bought by music lovers from all walks of life who want a medium-priced amplifier.

There's a moral somewhere—perhaps it would pay us all to become students in the U.S.!

RESISTANCE METER

The Chinaglia OH470 multi-range resistance meter uses a $40\mu\text{A}$ moving-coil movement with core magnet and sprung jewel mounts. A tough ABS case combined with a full view scale and simple range switching make for an easy-to-use instrument suited to a wide variety of environments.

Six measuring ranges are provided, giving the ability to identify resistance from 0.1Ω up to above $50\text{M}\Omega$ to within 2.5% accuracy. Internally housed batteries make the instrument independent of external power sources and suitable test leads designed to co-operate with specially designed sprung sockets on the instrument simplify low value measurements. Ranges are: $0-200\Omega$; $0-10\text{k}\Omega$; $0-100\text{k}\Omega$; $0-1\text{M}\Omega$; $0-10\text{M}\Omega$; $0-100\text{M}\Omega$. *Alberto Coniglio, 19 Mulberry Walk, London SW3 6DZ 01-352 1897.*

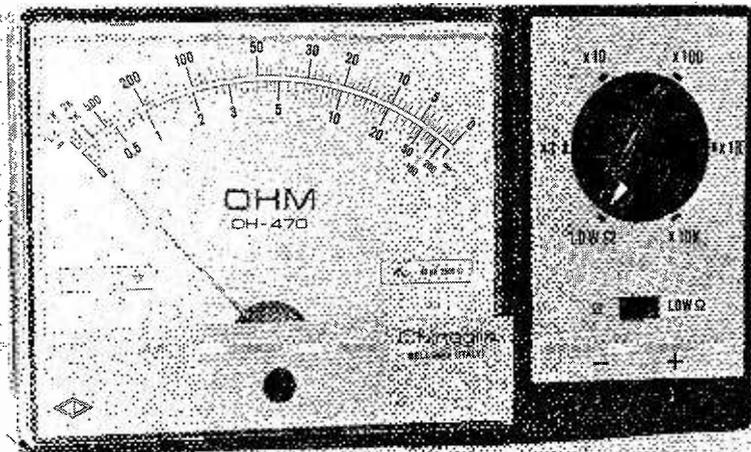

Chinaglia OH470

ORGAN KIT

The Heathkit/Thomas TO-1160 electronic organ has two 44-note overhanging manuals with tilted keys and a 13-note radial arc pedal rack. Other features include a colour-glow key system and a quick-play organ course. The built-in amplifier has an output of 25W RMS and plays through a built-in 300mm (12in.) speaker.

Fingertip controls include a variable pedal volume, variable manual balance-switch tabs for vibrato and a new light vibrato for true orchestral effects. There is also an accessory panel under the keyboards with line in and out facilities from a cassette recorder and a headphone jack, which when in use cuts out the main speaker.


Voicing stops on the upper manual are: flute 16', 8' and 4'; Trumpet 8'; Oboe and Violin 8'. The lower manual provides Horn 8'; Diapason 8', Melodia 8' and Cello 8'. The pedal rack has a Flute 16'-8' combination.

The cabinet is fully finished and overall dimensions are 1120 x 1100 x 640mm, or if you haven't the faintest idea what that is, 44 x 43½ x 25in.

Along with the TO-1160, Heathkit announce the TOA-60-1 rhythm section which complements the organ. Basic spec. is as follows: the choice of pre-programmed rhythm patterns of Waltz, Fox Trot, Rock, Soul, Polka, Samba, Bossa Nova, Rhumba with a variable volume and tempo control. Push-buttons also select the Drums (choice of Snare/Tom-Tom and Cymbals).

The TOA-60-1 also features a Fancy Foot control which gives alternating bass pedal notes that fit into the rhythm pattern chosen, when a foot pedal is held down, and Syncopated or Alternating Bass selections are available. The Rhythm Section also adds Piano, Guitar, Banjo or Harpsichord accompaniment, which again has the variable volume control

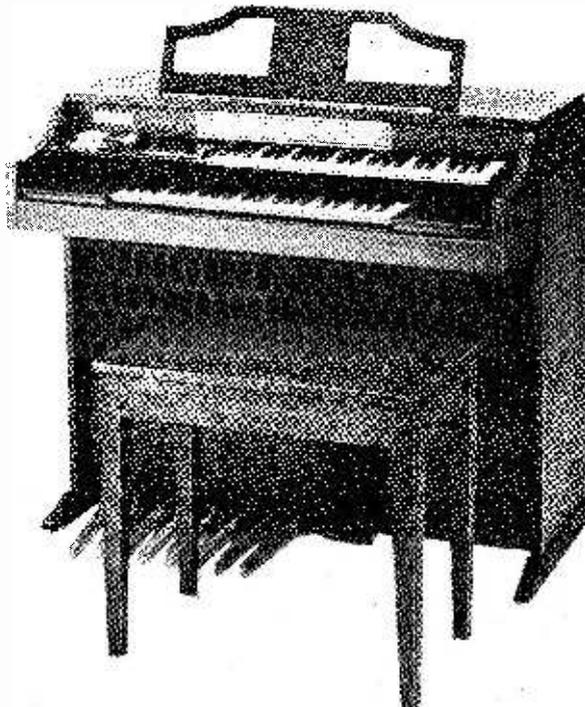List prices on these models, including VAT and delivery



within the U.K. are: Kit TO-1160, £600 and Kit TOA-60-1, £160, though Heathkit will be running an introductory offer of £660 for both kits when purchased together. This saving of £100 is quite attractive and the firm hopes it will appeal to people as the addition of the TOA-60-1 Rhythm Section really makes the organ.

WOLSEY ADASET

From Wolsey Electronics comes the new Adaset range of Mercury 40 and Mercury 80 amplifiers, both variations of the Mercury Standard ultra broad band amplifier. The new models have been designed with the do-it-yourself enthusiast very much in mind, and form the perfect answer to simple TV and stereo radio distribution installations.

Quite simply they are the ideal amplifiers for small installations with four (Mercury 40) or eight (Mercury 80) coaxial output sockets suitably padded to provide a slightly improved signal level to each receiver over that provided by the aerial. Each output can be used for either VHF or UHF television or stereo FM radio—providing of course the appropriate aerials are installed and adequate

signals are available in the area.

Technical Specifications:

Amplifier: Frequency coverage: 40–860MHz; Gain (typical): Mercury 40: 8dB Mercury 80: 2dB; Output (maximum peak): Mercury 40: 25mV Mercury 80: 12.5mV; Noise Figure: 6 to 10dB.

Integral Power Unit: Voltage Requirement: 240V ac 50Hz; Power: 4W.

Dimensions: Length: 200mm. Width: 111mm; Height: 67mm; Weight: 0.85 kg.

Recommended Retail Prices: Mercury 40: £24.60. Mercury 80: £29.10 (both plus VAT).

Wolsey Electronics, a division of A.B. Electronic Components Limited is located at *Cymmer Road, Porth, Mid Glamorgan (Telephone Porth 2711)*.

AERIAL AMPLIFIER

A quality FM aerial is not necessarily the passport to good stereo reception. All too often listeners on the "fringes" of reception areas are plagued with the interference which accompanies weak signal strength. The Wolsey "Clearsound" amplifier is designed to overcome this problem by boosting the received signal in the downlead cable near the aerial.

Constructed for mast head or fascia board mounting, Clearsound is an ultra low noise, high signal handling wide band VHF/FM amplifier, which is currently available in a well screened metal case. The Clearsound is powered via the coaxial signal cable in the conventional manner with the power unit being situated at some convenient position near the tuner.


Clearsound specifications:

Amplifier: Frequency coverage: 87.5 to 108MHz; Gain (minimum): 20dB; Output (maximum peak): 40mV 32dB.

Power Unit (Separate): Power consumption: 6.1W.

Dimensions: Amp: 60mm diameter; 86mm high; Power unit: 96mm long; 87mm wide; 60mm high; Combined weight: 0.78kg

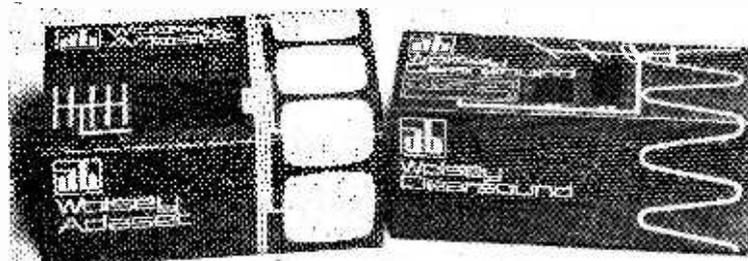Recommended Retail Price £16.45 plus VAT (this includes Power unit)



VARICAP ABSORPTION WAVEMETER

H.S. WOOD G8SX T. Eng. (CEI) MITE


An absorption wavemeter is a very useful device for checking output frequencies of various stages in a transmitter, or oscillator stages in a receiver, but suffers from the disadvantage that it has to be held near the circuit under test and be tuned at the same time. If harmonics or spurious frequencies are present these have to be separately tuned and noted.

Having had experience with a wobulator for receiver alignment it was decided to see if the same principle could be applied to an absorption wavemeter and the following design was evolved. The advantages are that no tuning is required and that a wide band of frequencies is visible at the same time. An oscilloscope is essential but it need not be very elaborate.

CIRCUIT

Basically the unit is a simple tuned circuit, Fig. 1, feeding a diode detector D2, with the tuning carried out by a varicap diode D1. The voltage to the varicap diode is taken, via an operational amplifier IC1, from the oscilloscope time base which should be operating at about 50Hz. The detector diode output is fed to the "Y" amplifier on the oscilloscope and any signal which is detected by the wavemeter appears as a response curve on the screen. If there is more than one frequency present within the tuning range then all these frequencies will be displayed on the screen.

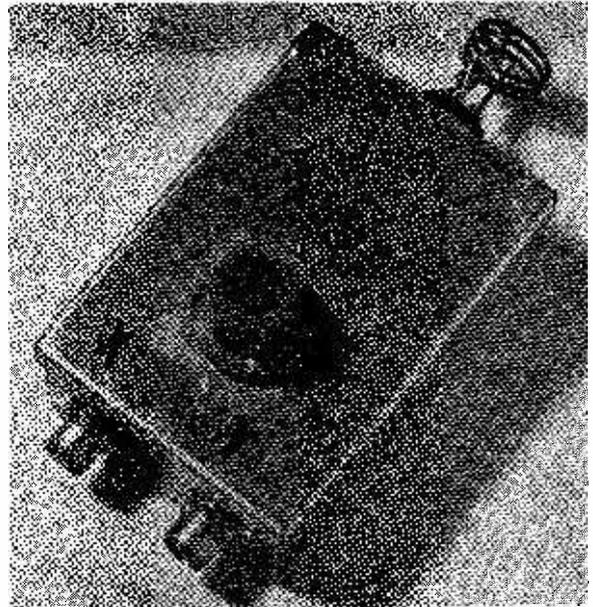Power for the 741 IC can be obtained from two 9V batteries in series but, in the writer's case, there



was 50V DC on the timebase output of the oscilloscope and, as the current requirement of the operational amplifier is very small, this voltage was reduced by a series resistor and smoothed by a 100 μ F capacitor thus making the batteries unnecessary.

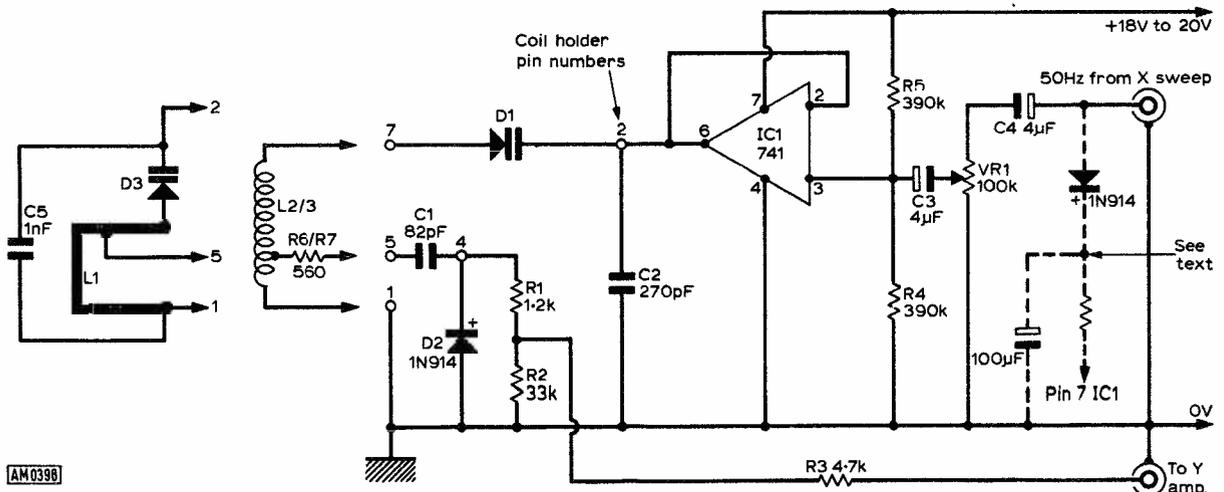


Fig. 1. Circuit of the Wavemeter, showing the two styles of coil used. The part of the circuit shown dotted is explained in the text.

CONSTRUCTION

The detector and varicap diode were built around ceramic 9 pin valveholder because some plugs were available to fit this and so the coils were built on these. Actually any low-loss plug and socket will do depending on the frequency of operation required.

The IC was fitted on a piece of Veroboard and the whole unit mounted in an aluminium box with the coil socket protruding at one end. Coaxial sockets were fitted, one for detected output and the other for sweep input. If batteries are used for power it might be necessary to add a switch and provide room inside the box for the batteries.

VARICAP DIODE

The sweep bandwidth and frequency of operation are very dependent on the type of varicap diode used and as the writer wanted to cover at least up to 144MHz the stray capacities had to be kept down. The varicap diode used is listed as a VHF type BB121A but it has a fairly high minimum capacity with good capacity swing. The results were good enough for the immediate requirements but there is room for improvement and it is intended to try some of the UHF type varicaps as these should have smaller minimum capacity and larger capacity swing.


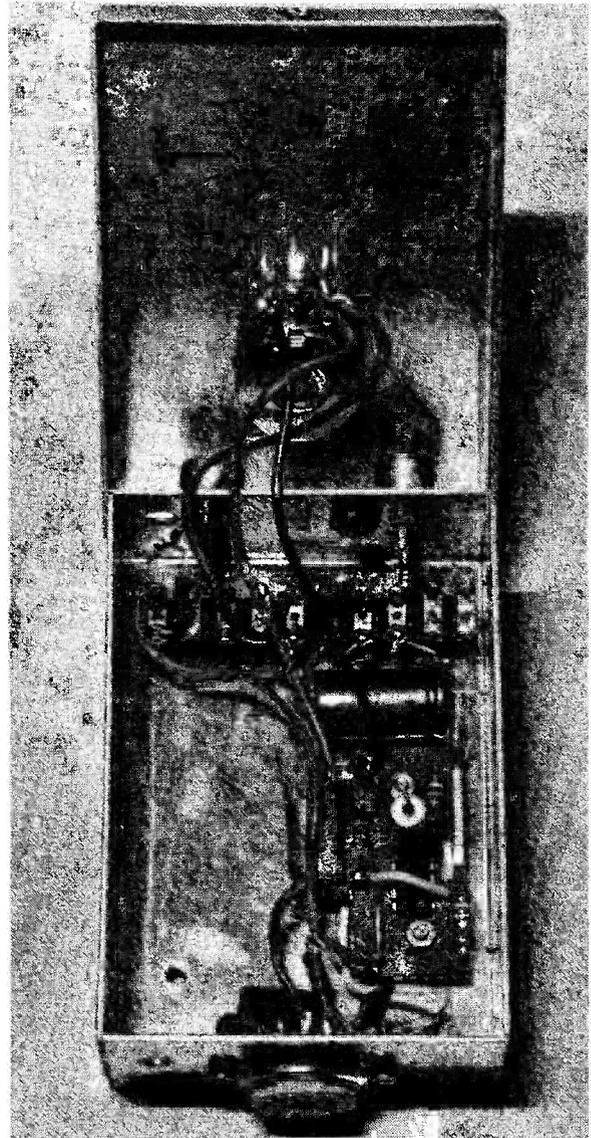
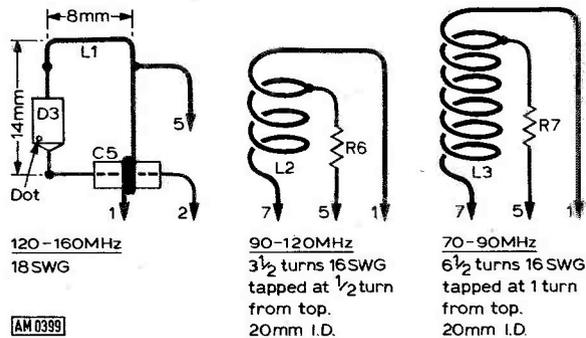


Fig. 2: Constructional information for the three coils required to cover 70 to 160 MHz approximately. Other frequencies may be covered with those indicated in Fig. 1. The terminal strip carries the optional components shown dotted in Fig. 1.

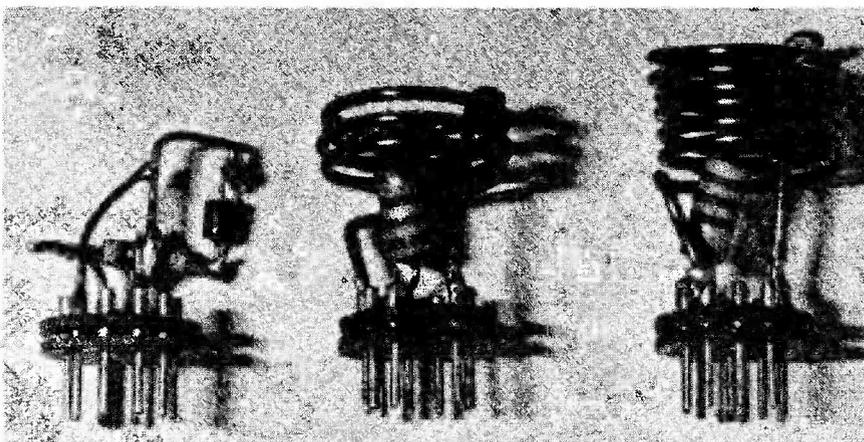

Photograph of the three coils wound for the prototype wavemeter. Details are shown in Fig. 2. Adjustments to coverage of L2 and L3 can be made by altering the spacing of the turns.

★ components list

Resistors	
R1 1.2k Ω	R5 390k Ω
R2 33k Ω	R6 560 Ω
R3 4.7k Ω	R7 560 Ω
R4 390k Ω	VR1 100k Ω
Capacitors	
C1 82pF (or 100pF) silver mica	C4/5 4 μ F 24V
C2 270pF silver mica	C5 1nF feedthrough
Semiconductors	
IC1 741	
D1/3 BB121A (or similar)	
D2 1N914	
Miscellaneous	
Holder for 741. Valveholder B9A with three plugs. Coaxial sockets (2). Knob. Terminal strip. Aluminium box 102 x 70 x 40mm (4 x 2 $\frac{3}{4}$ x 1 $\frac{1}{2}$ in.)	

The highest frequency range was achieved by using two varicap diodes, one built into the box D1 for use with the low frequency coils, the other, D3, built into the high frequency coil as shown in Fig. 2.

The sweep width is about 40MHz at 144MHz with correspondingly reduced sweep at lower frequencies.

COILS

The diode detector is tapped into the tuned circuit as shown, Fig. 2, and if this is done it is quite easy to construct coils to give the frequencies required. In the writer's case, with the exception of the highest frequency coil, existing coils for a grid dip meter were found to be one range lower in frequency than in the grid dip meter and it was not necessary to construct new coils.

OPERATION

The unit is connected to the oscilloscope and the sweep control is adjusted to a point where a vertical line on the screen, caused by overload of the IC disappears off the end of the trace. With this setting a maximum sweep is being obtained and if the coil of the wavemeter is held near a source of RF, of suitable frequency, a trace will be seen.


The oscilloscope should be used on its most sensitive range and the signal level should be controlled by moving the wavemeter away from the source of RF. The sweep width control needs no adjustment other than the initial setting to give maximum sweep. Calibration is best done by holding the wavemeter near a calibrated grid dip meter. It is only necessary to note the frequencies at each end of the trace for each coil because the output of the grid dip meter can be seen on the screen at the same time as the circuit under test and the frequency can be read off the dial of the grid dip meter.

It has been found to be a tremendous advantage to be able to see all the output frequencies of a unit at the same time. The three frequencies of a mixer VFO, for example, can be watched while the circuit is adjusted to increase the wanted output and reduce the unwanted output. PW

AIDS TO IMPROVED RECEPTION—continued from page 487.

PRODUCT DETECTOR

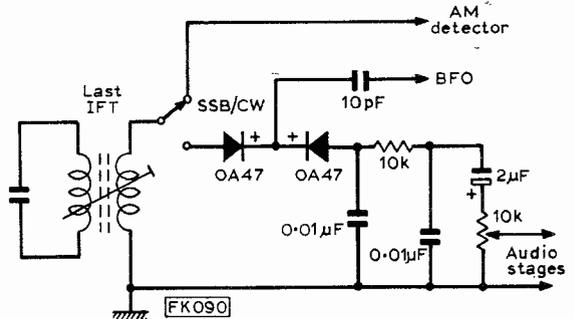THE product detector is easily added to a receiver and is intended to provide improved reception of SSB signals, as well as CW, when used in conjunction with a BFO. If the mode selector switch AM/SSB-CW is a double-pole one it can automatically switch on the BFO in the SSB/CW position.



The diodes must be germanium ones. The values of the components in the filter following the diodes are not very critical, those shown being for IF's around 465kHz.

The ratio of BFO signal to the signal from the IF stage must be right for best reception of SSB telephony so the RF or IF gain control should be adjusted carefully. In the absence of such controls an aerial attenuator can be used.

TO BE CONTINUED


Mail Order Protection Scheme

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements; placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

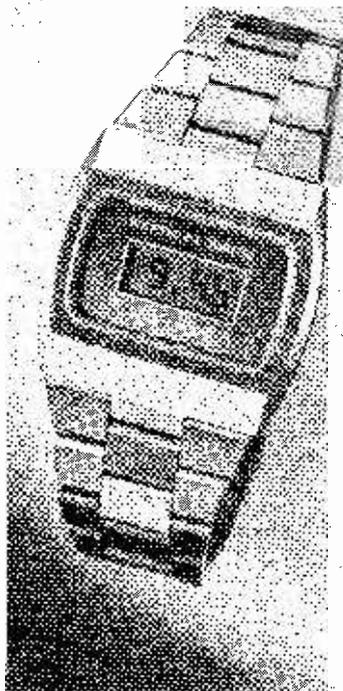'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.



J.B.Dance

ELECTRONIC Wrist WATCHES

TRANSISTOR DRIVEN WATCHES

The delicate contacts employed in the LIP watch were a great disadvantage, since they required periodic replacement. The work of Marius Lovet of France led to the development of contactless watches in which the switching was carried out by means of a transistor. One watch of this type is known as the "Dynatron".

The balance wheel of a Dynatron watch carries small permanent magnets which move near two coils: a feedback coil and a power coil. When the balance wheel magnets move past the feedback coil, they induce a signal in it which is used to make a transistor conduct. A current passes through the transistor to the power coil which pulls the magnet on the balance wheel so as to keep the wheel moving.

The Junghans 600·12 self-starting wrist watch employs a transistor driven balance wheel of this type.

MOST of the wrist watches being manufactured at the present time employ the same basic type of mechanical oscillator as that developed by Christiaan Huygens of Holland in the 17th Century. However, during the past few years extremely accurate types of electronic wrist watches have been developed. Although electronic watches are expensive at the moment, they will bring about great changes in the watch industry. Some of these watches employ no moving parts and show the time in the form of digits.

Electronic watches do not have a spring which must be wound each day, but they do employ a miniature power cell which must be replaced about once per year. This minor disadvantage is largely outweighed by the fact that electronic watches require no regular cleaning or other maintenance. In addition, most electronic watches are almost unaffected by magnetic fields.

FIRST ELECTRIC WATCH

In March 1952 the LIP Company of France released the first watch which employed a small electric cell as a source of power. The watch employed a conventional balance wheel, but was rather more accurate than conventional watches, since the amplitude of swing of the balance wheel remained almost constant throughout the life of the power cell.

In the LIP watch, a jewelled cam on the pivot of the balance wheel pushed fine wire against a contact; this resulted in a current flowing through a small electromagnet which attracted a magnet fitted to the rim of the balance wheel so as to keep the latter moving. The average current taken from the 1.55V cell was 5 μ A.

This watch was "electric" rather than "electronic", since the only electronic component used was a diode for spark suppression.

TUNING FORK WATCHES

Wrist watches employing electronically driven tuning forks have been available since the Bulova Company announced their first "Accutron" model on October 25th, 1960. It was the first watch to employ a timing mechanism which did not involve


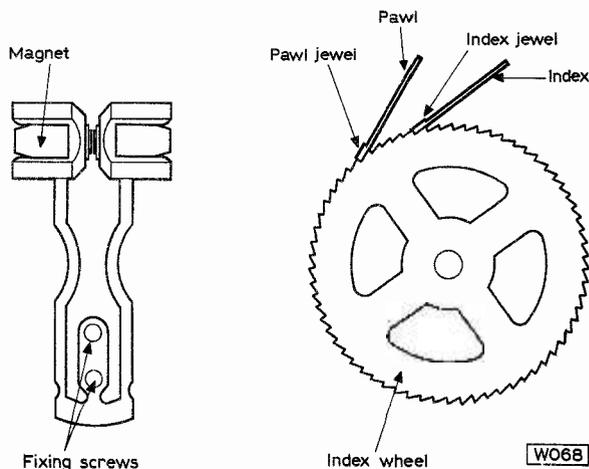


Fig. 1a (left) The tuning fork of a typical "Accutron" watch. Fig. 1b (right) The ratchet and pawl mechanisms which convert vibrations of the tuning fork into rotary motion.

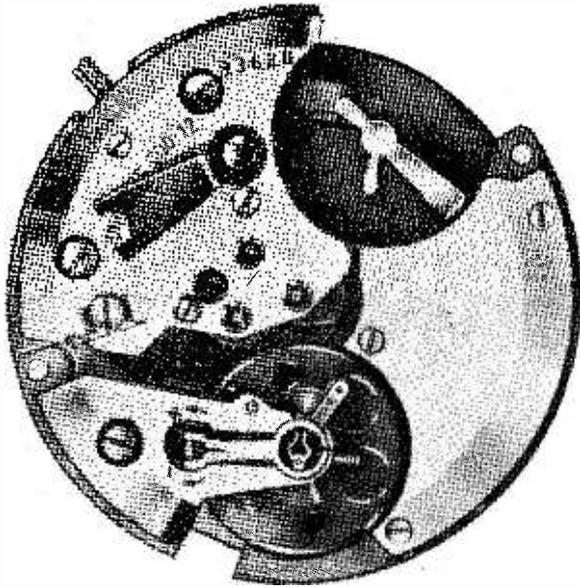

The mechanism of the Junghans "Dato-chron" movement. A contactless self-starting balance wheel is used which runs for at least a year on the 1.35V cell shown.

a balance wheel and hair spring. In addition, it was the first watch to be provided with a written guarantee of accuracy, namely one minute per month.

A tuning fork of a typical "Accutron" watch is shown in Fig. 1a; it oscillates at 360Hz. A strong conical magnet and a cup of magnetic materials are fitted to each side of the tuning fork. A coil of about 8,000 turns of insulated wire is fitted over each magnet so that it is close to the magnet but not touching it. A simple transistor oscillator circuit provides the power which keeps the tuning fork vibrating.

The vibrations of the tuning fork are converted into rotary motion by means of the ratchet and pawl mechanism shown in Fig. 1b. The index pawl is attached to one arm of the tuning fork; the tiny jewel at the end of this lever causes the index wheel to advance one tooth for each complete vibration of the tuning fork. During the return of the index jewel, the index wheel is held in position by a pawl jewel.

The index wheel is only 2.4mm in diameter, but has 300 teeth. This wheel drives a gear train which turns the hands of the watch.

A series of "Accutron" models for ladies was introduced in 1970. The smaller tuning fork operates at 480Hz, but the current consumption is similar to that in the models for men (about 8μA).

BALANCED TUNING FORK

A group of Swiss watch manufacturers, Ebauches S.A., have designed a balanced tuning fork movement known as the "Mosaba". This has the advantage that its accuracy is unaffected by its position relative to the vertical gravitational field.

The Mosaba movements operate at 300Hz and are used in such watches as the Longines "Ultronic" range, the Baume and Mercier "Tronosonic" watches and the Omega "300" range.

All of these watches have an accuracy of about one minute per month; they emit a low hum instead

of the ticking noise emitted by a normal balance wheel watch.

THE MEGASONIC


A new type of tuning fork watch known as the Megasonic 720 is being introduced by the Omega Company. It has an accuracy which is much better than that of any other watch employing a mechanical oscillator, namely ± 10 seconds per month. The tuning fork is driven by an integrated circuit oscillator; it operates at 720Hz and is said to be less sensitive to shock than the larger movements operating at lower frequencies.

QUARTZ CONTROLLED WATCHES

As long ago as 1880 the piezo-electric effect was discovered by the brothers Pierre and Jacques Curie. They showed that when mechanical forces are applied to suitable crystals in certain directions, electrical charges are formed on the faces of the crystals. Shortly afterwards Lippman found that an electric field will produce a mechanical deformation in the same crystals. Such crystals can therefore form resonators where the stored energy oscillates between the mechanical deformation of the crystal and the electric field.

In 1921 Cady used the piezo-electric effect in quartz to stabilise the frequency of an electronic oscillator. Since then it has been widely used for this purpose, for example, for stabilising the frequency of a radio transmitter. Quartz controlled oscillators have been used for stabilising the oscillators of very accurate clocks, but the first quartz controlled wrist watches did not become available until April 1970. The accuracy is usually about one minute per year.

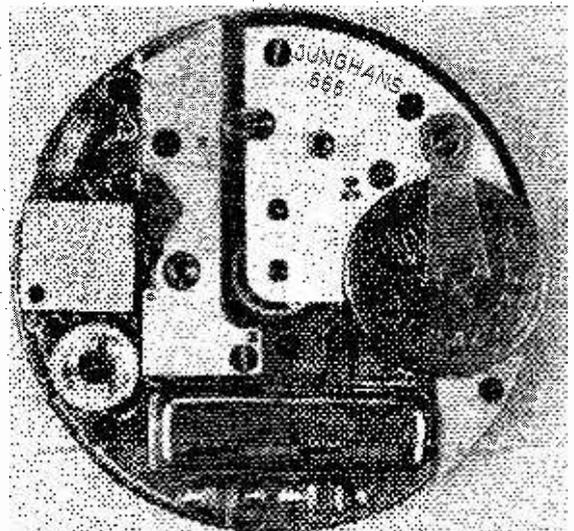Quartz oscillators operate at very high frequencies (kilohertz to megahertz). In a watch the high frequency from the quartz oscillator must be divided down to produce a low frequency suitable for driving a motor or showing the time as digits. It is only in the last few years that miniature integrated circuits



The interior of the Junghans "Astroquartz" showing the power cell on the right and the quartz crystal case at the bottom.

Practical Wireless, October 1975

have been developed which will divide the high frequency signal whilst consuming very little power. In general these circuits employ complementary metal oxide silicon (CMOS) designs which are ideal for miniature low power applications.

CONTROLLED BALANCE WHEEL

A watch developed by the Golya Company of Switzerland employs an electronically driven balance wheel having four magnets, but the exact frequency of oscillation of this balance wheel is controlled by a quartz crystal oscillator. It is known as the "μ-Quartz" watch.

The 32,768Hz ($=2^{15}$ Hz) pulses from the quartz oscillator are divided in frequency by a CMOS integrated circuit containing some 450 components.

The hair spring used in this watch is deliberately designed so that the frequency of the balance wheel is dependent on its amplitude of oscillation. The circuit is arranged so that the strength of the pulse given to the balance wheel depends on the phase of its motion relative to the frequency divided signal from the quartz oscillator. The frequency of the balance wheel is thus stabilised at a value determined by the signals from the quartz controlled oscillator circuit.

As in all quartz controlled watches, the timing is regulated by means of a trimmer capacitor which adjusts the exact frequency of the quartz oscillator circuit.

ASTROQUARTZ

The Junghans "Astroquartz" watch employs a quartz crystal in the shape of a tuning fork which oscillates at 32,768Hz. The crystal is driven by an integrated circuit which also divides the frequency to produce an output of one pulse per second. These pulses drive an electromagnetic transducer which is connected to the second hand.



The Bulova "Accuquartz" watch (right) by the side of an earlier model which employs the "Beta 21" movement.

The size of the integrated circuit employed in this watch is only 2.1×1.6mm. The total current consumption is about 14μA from the 1.3V 150mA-hour cell.

CYBERNETIC WATCH

The Longines "Ultra-quartz" watch is particularly interesting, since it is probably the only quartz controlled watch which does not employ an integrated circuit; it first became available on 21st August 1971.

The quartz crystal resonates at 9350Hz, but the watch also employs a mechanical vibrator operating at 170Hz. Signals from the quartz controlled oscillator circuit are used to correct the frequency of the mechanical vibrator 170 times per second.

The correction is carried out by a relatively simple circuit employing 14 transistors, 19 resistors and 7 capacitors. Logical deductions made by this circuit are fed to the vibrator as correction signals. This comparison circuit or "brain" has resulted in the "Ultra-quartz" being called a "cybernetic" watch.

The vibrator movement is converted into a rotary motion by means of a pawl system similar to that used in the tuning fork watches.

STEPPING MOTOR

The Girard-Perregaux Company introduced its series 350 watch in 1972. It employs a 32,768Hz quartz controlled oscillator, the pulses from which are divided in frequency by a factor of 65,536 by means of a CMOS integrated circuit containing 312 transistors.

The output from the integrated circuit consists of a short pulse of one polarity followed one second later by a pulse of the opposite polarity. These pulses drive a miniature stepping motor which causes the second hand of the watch to jump forward. The minute and the hour hands are driven by a conventional gear train.



The tuning fork movement and the quartz crystal of the Bulova "Accuquartz" under examination.

QUARTZ TUNING FORK WATCH

The current Bulova "Accuquartz" watch is interesting because it contains a quartz oscillator operating at 32,768Hz which is used to control the frequency of a $341\frac{1}{2}$ Hz tuning fork movement. This movement operates the normal watch gearing as in the Bulova "Accutron" models. The centre second hand therefore appears to revolve continuously instead of jumping once or twice per second as in some quartz watches.

The accuracy is quoted as one to two seconds per week. Prices range from £115 to £675.

THE MEGAQUARTZ 2400


The Omega Division of SSIH (Société Suisse pour l'Industrie Horlogère) in collaboration with Batelle Institute has designed a watch with an accuracy of about one second per month; this is the most accurate wrist watch which has been put into production.

The Megaquartz 2400 is available in an 18ct yellow gold case and bracelet at around £2,050. A stainless steel version will soon be coming onto the market at a price of about £440.


The quartz crystal in the Megaquartz operates at a frequency of 2,359,296Hz—far higher than that of any other watch. A CMOS integrated circuit manufactured by the Intersil Company is used as an analogue divider to reduce the frequency to 1Hz. It employs about 400 transistors on a silicon chip 4mm² in area.

DIGITAL WATCHES

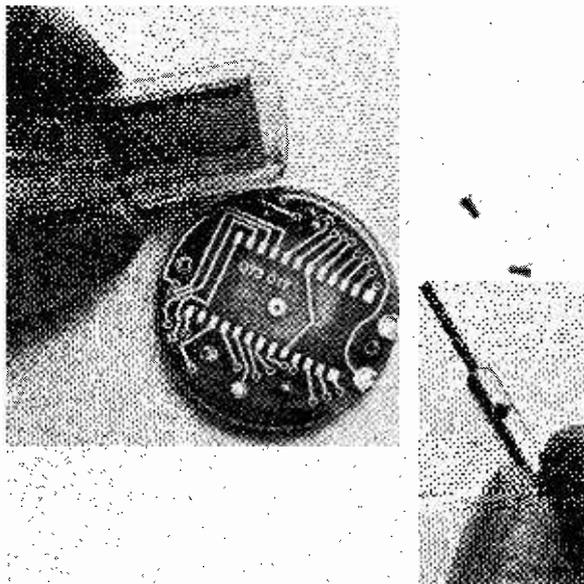Quartz controlled watches which provide a digital display have recently appeared on the market. They employ no moving parts and have an accuracy of about one minute per year. Two forms of display have been used, namely electroluminescent diodes and liquid crystals.



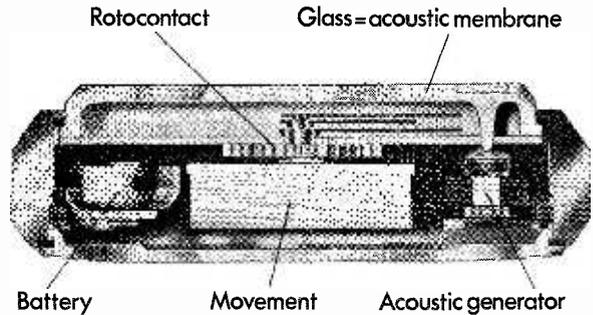Removing the liquid crystal display unit is very easy in the new Nepro watch (also seen in our heading photograph).



The interior of a Nepro watch in which an electronic mechanism is used to sound an alarm. The glass of the watch vibrates when the alarm is being sounded.

ELECTROLUMINESCENT DISPLAYS

Digital displays using electroluminescent diodes emit red light and have a very long life. Their main disadvantage is that the current required by the display is so great that the time cannot be continuously displayed. A button must be pressed whenever one wishes to see the time.

The Hamilton "Pulsar" watch (not available in Europe) and the Omega "Time Computer" employ a 32,768Hz quartz oscillator. This frequency is divided by an integrated circuit and the resulting signal is used to drive the display. When a button is pressed, the hours and minutes are displayed for 1.25 seconds, but if the button is held down, the seconds are displayed for as long as it is depressed.

LIQUID CRYSTAL DISPLAYS


Liquid crystal displays do not emit light, but merely reflect a different proportion of the incident light from different parts of the display. Such displays can therefore operate at very low currents (typically 1μA at 10 to 20V). They can therefore display the time continuously, but the display cannot be seen in the dark.

A liquid crystal display can be formed by applying an electric field across certain parts of a "nematic" material. The field is applied by suitably segmented transparent electrodes so that it is in the shape of the digits to be indicated. As the crystals come into alignment, they reflect back the incident light. In the Longines watch a mirror is placed behind the display so that light is reflected back at those places where no field is applied.

The liquid crystal display will disappear above a certain critical temperature (55°C in a typical case), but returns on cooling. There is still some doubt about the life of liquid crystal displays, but most manufacturers offer a guarantee of some years. When failure occurs, the clarity of the display gradually deteriorates.

A number of watches provide a liquid crystal display showing the hours and minutes in digits with a colon flashing once per second in between the hours and minutes digits. However, the Longines watch provides a continuous readout of the day of the month, the hours, the minutes and seconds.

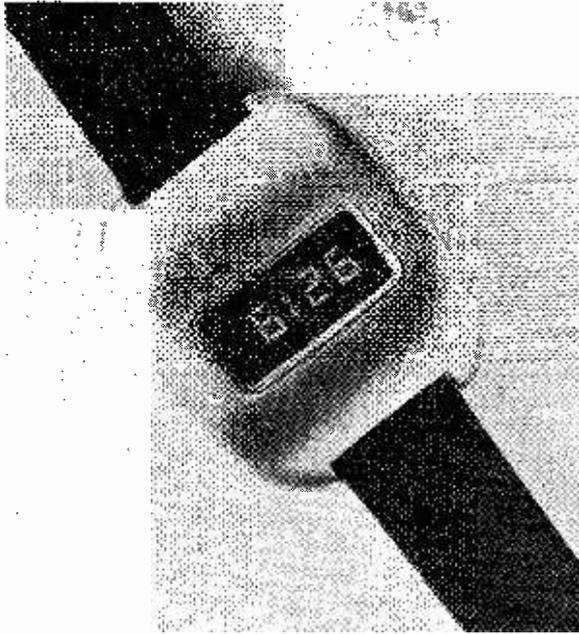One of the latest quartz controlled watches with a liquid crystal display is the type CX15 introduced by the Nepro Company of Switzerland at the end of 1974. At the present time about 5,000 of these



The Avia liquid crystal digital watch. The colon flashes once per second. Liquid crystal displays operate from a supply of about 15V and therefore a DC to DC converter is incorporated in this watch.

watches are being produced each month. Except for the integrated circuit, all of the components in this watch are of Swiss origin.

The crystal oscillator operates at 32.768kHz. The circuit is driven by a 3V source without any transformer. Particular attention has been paid to ease of servicing in the design of the Nepro watch. For example, it is only necessary to remove two screws in order to replace the whole liquid crystal display system.

Nepro intend to offer other models soon, including those which display the date and the number of seconds, models for ladies and other watches which include a facility for illuminating the display. Mr. Palo Spadini, chairman of Nepro, hopes to form a pool of Swiss manufacturers so that the modules used in the watches can be standardised and the cost of parts reduced.

ALARM WATCHES

The watches discussed previously employ electronic circuits to improve the accuracy or to provide a digital display. The Nepro Company of Switzerland have used electronic alarms in wrist watches which will sound at any time of the day. They can be heard in a busy street.

CONCLUSION

The prices of integrated circuits have been falling rapidly during the past few years, whilst labour costs have been rising. If this trend continues, it seems certain that a much greater proportion of the watches manufactured will be electronic ones containing only a few modules. PW

Practical Wireless, October 1975

TELE-TENNIS BALL SPEED CONTROL

—continued from page 462

★ components list

Resistors (all $\frac{1}{4}$ or $\frac{1}{2}$ W $\pm 5\%$)

R1 4.7k Ω	R7 4.7k Ω
R2 15k Ω	R8 4.7k Ω
R3 15k Ω	R9 4.7k Ω
R4 4.7k Ω	R10 330 Ω
R5 2.7k Ω	R11 4.7k Ω
R6 2.7k Ω	R12 330 Ω

VR1 10k Ω	} vertical skeleton preset
VR2 10k Ω	
VR3 1M Ω	

Capacitors

C1 1000pF
C2 1000pF
C3-C9 0.1 μ F (7 off)

Integrated Circuits

IC1 SN7403N
IC2 SN7400N
IC3 SN7400N
IC4 NE555
IC5 NE555
IC6 SN7403N
IC7 SN7400N
IC8 SN7400N

Note that the redundant 7400 from Board A (IC8) is used for IC14

Miscellaneous

RLA DIL single pole make reed relay (RS) (see text)

Printed circuit board.

A ready drilled, roller tinned, cut to size p.c.b. is available from:

System Printed Circuits Ltd.,
3 Redcliffe Way,
Brundall Gardens, Brundall, Norwich
priced at £1.20 (inc. p. & p. and VAT).

A complete set of parts is available at £6 inclusive.

relay contacts and set the new preset to the new speed—not too fast however or the ball will pass through the bases.

NB: If the reed relay cannot be obtained or if a spare 12V relay is available, simply wire in a transistor driver and connect the base resistor to pin 6 IC7 and the relay between the collector and unregulated 12V supply. PW

AVAILABLE NOW!

REPRINT OF PW's

TELE-TENNIS SERIES

July-November 74


Send 75p + 7p (post & packing) to: Chief Cashier
(PW Tele-Tennis), IPC Magazines, Tower House,
Southampton St., London, WC2E 9QX.

SAXON ENTERTAINMENT LTD.

NEW PROFESSIONAL MODULES TO SAVE YOU £££

THE NEW POWER AMPLIFIERS

Three brilliant new power modules employing the same circuitry, using 10 transistors, three diodes and one zener diode with electronic over temperature cutout as well as normal thermal protection, load line short circuit and incorrect load protection, integrally mounted output capacitor. Fused supply and output terminals. May be solder or screw connected. The input impedance is high enough to accept all types of mixer having an output of 250 mV.

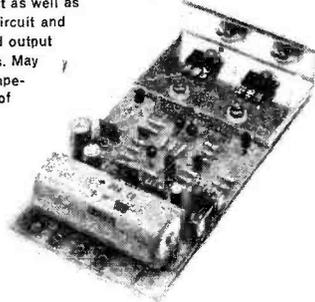

New features—new performance standards

- ★ New 90°C overtemperature cutout (electronic not mechanical).
- ★ New integral output capacitor, no external components required for normal operation.
- ★ Short circuit load line type protection with twin summing amplifiers.
- ★ Inherently open circuit proof.
- ★ Input sensitivity -10 dBm (240 mV into 100k) ie suitable for most mixers. Response 20Hz-40KHz ±1dB.
- ★ Typical distortion 0.4% (Noise -80 dB (as graph in catalogue)).
- ★ Compact: 15cm x 8 cm x 3 mm
- ★ Suitable for all public address, discotheque, and group applications.
- ★ Fused supply and output terminals.
- ★ Single supply line (split supply not required).

SA608
60 w.r.m.s. into 8Ω;
30 w.r.m.s. into 15Ω
Texas 15A output transistors.

£11-50

CONSTRUCTIONALLY & ELECTRONICALLY BETTER : MULTIPLE TESTED : GUARANTEED

SA1208

120 w.r.m.s. into 8Ω
60 w.r.m.s. into 15Ω
Glass fibre printed circuit board.
Texas 15A output transistors

£16-00

SA308

30 w.r.m.s. into 8Ω
15 w.r.m.s. into 15Ω
basic circuit identical to SA 1208
10A 'Plastic Power' output transistors

£9-00


THE NEW POWER SUPPLIES

- ★ One piece, ready to wire assembly with integral glassfibre pcb.
- ★ Grain oriented laminated transformers for compactness.
- ★ Facilities for preamp supply.
- ★ Fully fused.
- ★ Size of all models 10 x 8 x 13cm.

PM1201	95 volts for one SA1208	£11-00
PM1202	95 volts for two SA1208	£14-00
PM601	65 volts for one or two SA 608	£9-00
PM301	45 volts for one or two SA 308	£7-50

MODULAR PRE-AMPS Mono & Stereo

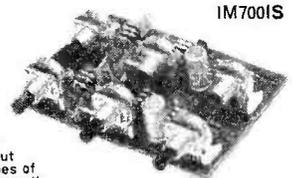Up to twenty IM7001 input modules may be used with the IM7002 mixer module. Each input module has various types of equalisation and monitor path outlets.



★ Equalisation to suit ceramic AND magnetic cartridges, low and high imp. mic. all musical instruments. ★ Mono and stereo. ★ Mono module may be matrixed into stereo. ★ Low noise circuitry with carbon film resistors. ★ 20 Hz-50 kHz ± 1dB. ★ Wide range bass and treble controls—zero noise with vol. at min. ★ 18 volt supply. ★ Outputs for monitoring and echo send. * May be used in conjunction with the discotheque mixers and Minotaur amplifiers.

IM7001M (mono) **£5-50** IM7001S (stereo) **£9-00**

IM7002 Mixer module with output suitable for most amplifiers PLUS up to 1 Watt of monitoring power. ★ Accepts up to twenty IM7001 input modules. ★ Mono or stereo. ★ Up to 3V output—will feed loads down to 600 ohms. ★ Up to 1 watt into 8Ω for monitoring (will feed higher impedance). ★ Accepts echo and other effects return signals.


IM7002M (mono) **£5-50** IM7002S (stereo) **£9-00**

SAXON SUPERFECT

(illustrated)

All these features in ONE UNIT:
No other commercially available module to our knowledge, offers all these facilities in one complete unit.

- ★ Sequential display with variable speed.
- ★ Frequency dependent channels—individually fused.
- ★ Continuously variable function control gives uninterrupted light display in absence of signal.
- ★ Electronic override on each channel.
- ★ RCA 8 Amp. triacs handling 1000 watts per channel.
- ★ Timer circuitry to reduce 'flicker'.
- ★ Individually controlled bass middle and treble plus master audio control for ease of adjustment.

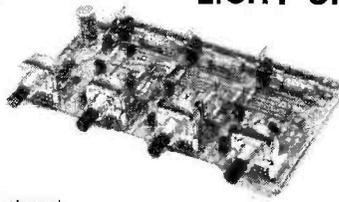

LIGHT UNIT

£19-75

SAXON SOUND-LITE

- Our ever popular 3000 watt unit is now available in module form at only
- ★ Individual control of bass middle and treble plus master control for ease of adjustment.
 - ★ 1000 watts per channel—individually fused.
 - ★ Negligible load on amplifier.
 - ★ RCA 8 AMP triacs for reliability.

£13-50

THE ULTIMATE IN MIXER MODULE

- ★ Inputs for two decks (ceramic cartridge) plus tape; overall bass and treble controls
- ★ Hi/lo imp. mic input with separate volume bass and treble controls.
- ★ Continuously variable autofade depth plus preset threshold control.
- ★ Low noise (-80dB) virtual earth mixing circuitry.
- ★ Up to 0.5W from low distortion push pull monitor amp.
- ★ Response 20Hz-50kHz ± 1dB.
- ★ Low power consumption (20mA at 18 volts).
- ★ Compact—mono version 40cm x 6cm x 3cm. stereo version 40cm x 10cm x 3cm.
- ★ Output -10dBm (240mV) to suit all Saxon amplifiers and most other makes.

MONO VERSION

£18-50

STEREO VERSION

£27-50

SAXON MONO & STEREO DISCOTHEQUE MIXER WITH AUTOFADE



SAXON ENTERTAINMENTS LTD.

WHITE HORSE ROAD
CROYDON, SURREY CRO 2HS

SYSTEM 7000

PROFESSIONAL STANDARD COMPLETE UNITS

A total range project to satisfy the most discerning

- ★ STAINLESS STEEL ESCUTCHEONS*
- ★ TOTALLY COMPATIBLE WITH ALL SAXON MODULES
- ★ TOUGH EASILY READ FACIA
- ★ PLUG ISOLATED TERMINALS THROUGHOUT.




- ★ Extremely compact (27cm x 16cm x 10cm).
- ★ Fully protected against all incorrect loads and short circuits.
- *Except minotaur (anodised aluminium).

MINOTAUR 100

- ★ 100 W.r.m.s. into 8Ω.
- ★ Two mixed inputs, wide range bass & treble controls.
- ★ May be operated as a slave amplifier.

£47.50

SYSTEM 7000 DISCO CONTROL UNIT

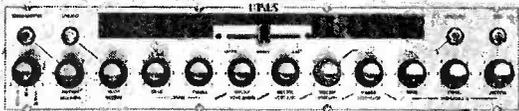

- ★ Mono or stereo.
- ★ 2 Deck and one tape inputs, individually controlled plus L/R deck fader (ineffective at central).
- ★ Wide range bass and treble controls plus separate MIC volume bass and treble controls. Overall master control.
- ★ Continuously variable autofade depth and threshold.
- ★ Five position monitoring switch with two mute positions—ample headphone power.
- ★ Complete, cased with all terminations by plug/socket etc.
- ★ Noise —80 dB Response 20Hz-50 kHz ± 1dB.


Mono £28.50

Stereo £45.00

SYSTEM 7000 MODULAR MIXING—UP TO 20 CHANNELS

Complete versions of the IM7001 and IM7002 modules shown in our advertisement make a professional quality versatile mixer to your requirements using these modules mono and stereo inputs may be combined.

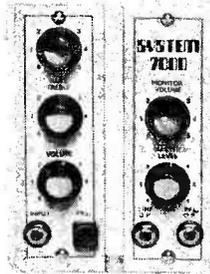- ★ The mixing modules split mono signals.
- ★ Each input module has own monitor switch.
- ★ Stainless steel panel on 15cm x 5cm matrix (approx.).
- ★ Input equalisation for all types of signal inc. magnetic cartridge.
- ★ Complete system may comprise twenty channels, mono or stereo with ample monitoring power.
- ★ May be patched in with disco mixers or minotaur amplifier.



Mono Input module £8.50

Stereo Input Module £12.00

Mono Mixer Module £8.50

Stereo Mixer Module £12.00

Power Supply Unit for up to 20 Modules £7.50

SYSTEM 7000 LIGHTING CONTROL UNIT

- ★ 1000 watts per channel. Sound light and SEQUENTIAL and OVERRIDE.
- ★ Individual control of bass middle and treble.
- ★ Master control for easy adjustment.
- ★ Plug/socket terminations throughout.
- ★ Slider control for function, allows sound/light, sequencing or combination of both.
- ★ Stainless steel front panel to match disc control unit.
- ★ Compact (17 cm x 10 cm x 10 cm approx.).
- ★ Electronic override eliminates clicks.
- ★ High sensitivity, negligible input power.

£35.00



ALL SAXON MODULES AND UNITS ARE GUARANTEED FOR TWO YEARS FROM DATE OF PURCHASE.

TO ORDER TELEPHONE 01 684 6385 NOW. FOR INFORMATION RING 01 684 0098 WE ACCEPT TELEPHONE ORDERS FOR COD AND ACCESS/BARCLAYCARD ACCOUNT HOLDERS.

IF ORDERING BY POST PLEASE SEND CHEQUE/CROSSED POSTAL ORDERS MADE PAYABLE TO SAXON ENTERTAINMENTS, OR ENCLOSE YOUR ACCESS/BARCLAYCARD NUMBER.

TRADE ENQUIRIES:

To NORMAN ROSE ELECTRICAL LTD AT ANY BRANCH.
LONDON TEL: (01) 837 9111 BIRMINGHAM (021) 236 4710
MANCHESTER (061) 273 1498 BRADFORD (0274) 24008

ALL PRICES INCLUDE POST & PACKING BUT V.A.T. AT 8% MUST BE ADDED TO VALUE OF ORDER.

Shop Hours Monday to Saturday 9.00 a.m.—5.00 p.m.
Telephone as shown above.

TRANSFORMERS

ALL EX-STOCK

MAINS ISOLATING
PRI 120/240v SEC 120/240v
CENTRE TAPPED AND
SCREENED

Ref. No.	VA (Watts)	£	p & p
07*	20	2.80	38
149	60	4.37	45
150	100	4.89	45
151	200	8.13	53
152	250	9.83	73
153	350	11.88	73
154	500	13.65	91
155	750	20.51	BRS
156	1000	29.15	BRS
157	1500	33.23	BRS
158	2000	37.07	BRS

* 115 or 240V sec. only.

12 and or 24 Volt
PRIMARY 240-250 VOLTS

Ref. No.	Amps	£	p & p
111	0.5	1.35	23
213	1.0	0.5	1.74
71	2	1	2.29
18	4	2	2.86
70	6	3	4.12
108	8	4	4.56
72	10	5	5.14
116	12	6	5.52
17	16	8	7.28
115	20	10	10.39
187	30	15	13.59
226	60	30	16.83

30 VOLT RANGE

SECONDARY TAPS

0-12-15-20-25-30

Ref. No.	Amps	£	p & p
112	0.5	1.81	30
79	1.0	2.40	38
3	2.0	3.49	38
20	3.0	4.33	45
21	4.0	5.13	53
51	5.0	6.41	53
117	6.0	7.16	60
88	8.0	9.87	67
89	10.0	9.90	73

50 VOLT RANGE

SECONDARY TAPS

0-19-25-33-40-50

Ref. No.	Amps	£	p & p
102	0.5	2.58	30
103	1.0	3.38	38
104	2.0	4.68	45
105	3.0	5.81	53
106	4.0	7.60	67
107	6.0	12.10	67
118	8.0	12.98	85
119	10.0	16.99	BRS

60 VOLT RANGE

SECONDARY TAPS

0-24-30-40-48-60

Ref. No.	Amps	£	p & p
124	0.5	2.33	38
126	1.0	3.41	38
127	2.0	5.08	45
125	3.0	7.52	60
123	4.0	8.75	67
40	5.0	9.75	73
120	6.0	11.30	85
121	8.0	15.00	BRS
122	10.0	17.52	BRS
189	12.0	19.98	BRS

AUTO TRANSFORMERS

Ref VA Auto Taps

Ref No.	VA (Watts)	£	p & p
113	20	1.67	30
64	75	2.90	38
4	150	4.12	45
66	300	5.82	53
67	500	8.82	67
84	1000	13.68	91
93	1500	18.11	BRS
95	2000	24.20	BRS
73	3000	35.09	BRS

CASED AUTO TRANSFORMERS

240V mains lead input and USA 2 pin outlets 20VA £3.23 p & p 38p 113W
500 VA £10.45 p & p 80p 67W
1000 VA £17.51 BRS 84W

HIGH VOLTAGE

Mains Isolating

PRI	SEC	VA	Ref.	£	p & p
200/220 OR 400/440		60	243	4.37	63
		350	247	10.41	95
		1000	250	27.06	BRS
		2000	252	41.07	BRS

SCREENED MINIATURES

Ref mA	Volts	£	p & p
238	200	3-0-3	1.54
212	1A, 1A	0-6, 0-6	1.84
13	100	9-0-9	1.41
235	330, 330	0-9, 0-9	1.56
207	500, 500	0-8-9, 0-8-9	1.92
208	1A, 1A	0-8-9, 0-8-9	3.30
236	200, 200	0-15, 0-15	1.43
214	300, 300	0-20, 0-20	1.93
221	700(DC)	20-12-0-12-20	2.17
500	VA, 1A	0-15-20, 0-15-20	3.46
203	500, 500	0-15-27, 0-15-27	3.00
204	1A, 1A	0-15-27, 0-15-27	3.85
5113	500	12, 15, 20, 24, 30	1.88

BRIDGE RECTIFIERS

VA	Ref.	£	p & p
50v	2A	30p	
100v	2A	35p	
200v	1A	40p	
400v	4A	60p	
600v	2A	45p	
500v 10A	PM7A6	£2.35	

P & P 15p

METERS

Model	£	p & p
AVO 8 Mk 5	£50.80	
AVO 72	£19.75	
U4313*	£11.80	
U4315*	£13.85	

* (USSR) Inc. Steel Carry Case

P & P 95p.

MAINS KEYNECTORS

£3.25, P & P 25p.

MAINS TIMER

Delay 1-30 minutes (Adjustable)

£5.95, P & P 25p.

PLUS

POWER UNITS
A125 6-9v at 200mA in moulded case forming a 2 pin 5A plug
£2.45 P & P 25p.
CC12-08 Output Switched 3.4-5.6-7.5-9-12v at 500mA
£4.08 P & P 30p.

CARBON FILM RESISTORS

1W 10 ohm-1 Mohm

90p per 100, inc. P & P.

CAPACITORS

MINIATURE CERAMICS

22p-0.047mid 30p per doz.

PAPER (Metal cased)

0.01-0.025-0.05-0.1mfd

85p per doz. P & P 15p

PLEASE ADD VAT AFTER P. & P.

ELECTROSLIP & SEMICONDUCTOR STOCKIST

SEND STAMP FOR CAT.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CPW 10, READING RG7 4PF CPW10

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name


Address

POST CODE



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

CARBON SLIDE POTENTIOMETERS

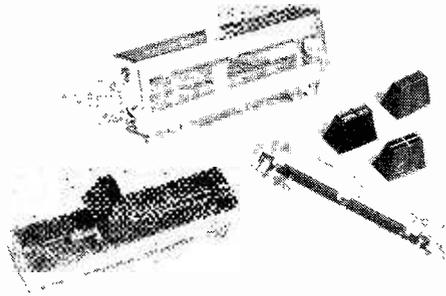

60mm Single Track including Black Knob 60p (inc. V.A.T.), 60mm Twin Track including Black Knob 70p (inc. V.A.T.), 60mm Quad Slide Potentiometers—Prices upon application. 1K, 5K, 10K, 25K, 50K, 100K, 500K ohms Log, Lin, Antilog. Metal Case. 3-2db Matched Track. 15mV Nominal Noise (B.S. 2122). Life Exceeds 20,000 cycles. Fixing Holes 2 x M3 on 80mm Centres.

Designed, Manufactured and Supplied by:—

RIVLIN INSTRUMENTS LTD

DOMAN ROAD, CAMBERLEY, SURREY GU15 3DJ

Send cash with order to above address. Postage and packing 20p per order. Trade enquiries invited.

PA100



£14.25

CARR. FREE

50 W RMS into 8 Ω with PP50/2 or 100W into 16 Ω with 2XPA50 Bridged and PP50/3

ZENTAC STUDIO QUALITY MODULES

Noise 70db
2% T.H.D.
± 38V D.C. max.
S/C, O/C, thermal prot.
20 HZ-20K22 B/width.
Continuously rated. 500mu into 10K. 5 easy connections plus two for Bridge/Normal operation. Complete with heat sink and full instructions. Ratings ± .5db.

PA50



£11.00

CARR. FREE
100W RMS into 4 Ω with PP50/3 or 75W into 4 Ω with PP50/2
2XPA 100 Bridged give 150W into 8 Ω with PP50/4 or 200W with PP50/6.

RP3



£8.50

CARR. FREE
REGULATED MODULE giving 3A at 24V falling to 2A at 6V. Current LIMIT AND VOLTAGE CONTINUOUSLY VARIABLE. S/C and THERMAL PROTECTION. Ripple at 3A—1mV. Needs 30V 4A D.C. supply PP30/4. Complete with controls and instructions.

POWER SUPPLIES

PP50/2 £9.00
PP50/3 £10.50
PP50/4 £12.00
PP50/6 £18.00
PP30/4 £7.00
50p Carriage

ALL PRICES FULLY INC

ZENTAC

265 PENTONVILLE ROAD
KING'S CROSS, LONDON
N1 01-837 2382

MAIL ORDER ONLY



Silica fibres . . . not coax

Concerning an item, 'Optical Coax' by Ginsberg (*Hotlines*, August 1975), I would like to correct a number of errors and enclose some information which should clarify the nature of my research work which was described in the third paragraph. First, coaxial cable will not be replaced by plastic fibres but by plastic-coated glass or silica fibres. The plastic coating is for protecting the fragile fibre and ease of handling. A typical optical fibre has a cladding (outside) diameter of about 50 microns and a core diameter of approximately 30 to 40 microns, for a multimode fibre. A single mode fibre has a similar size cladding but a very small core diameter, typically 3 microns. The plastic-coated fibre used in experiments at UCL, which has been kindly provided by STL, has an outside diameter of 1mm.

The statement in the third paragraph is incorrect. We do not 'tap' off signals but place signals on a guided optical carrier by means of clip-on acoustic (piezoelectric) transducers, not sensors. The prototype transducers were mounted in the jaws of clothes pegs for ease of attachment to the plastic-coated fibre. The transducers phase modulate the optical carrier by modulating, essentially, the refractive index of the glass. Each modulator is driven at a different sub-carrier frequency. It may easily be shown that a system of cascaded phase modulators forms a linear modulation system such that each channel may be recovered without crosstalk. Basically, this optical fibre communications system is a spatial frequency division multiplex system (FDM).

Signals from many data sources

may be put on the optical carrier anywhere along the length of the fibre and delivered to one destination. It should be noted that this optical data highway system is rather novel, since all the proposed optical fibre communication systems use intensity modulation of a laser or LED whilst this system uses phase modulation.

I am concerned that a correction be published, especially since such statements may be given further currency in other scientific journals.—S. A. Kingsley B.Sc.(Eng.) (Dept. of Electronic and Electrical Eng., University College, London).

Easybuild organ

During keyboard construction of this project, it has been found necessary to carry out a further test other than those listed in Mr. Hughes' articles. I append detailed notes and trust that you will publish them in an early issue in order that other constructors may have the benefit and advantage of my experience:

Following assembly of the key-switches and busbars it should be noted that at no time during depression of the keys should contacts 'b' and 'c' be connected to the earth busbar.

In my case it was found possible for contacts 'd' and 'a' to make connection with contacts 'c' and 'b', prior to release of the earth busbar. This, of course, means that the signal busbars would be shorted to earth during playing.

By carefully bending the key-switch contact wires, this type of defect can be eliminated, whilst still maintaining an acceptable "keying" position.

Reference is made particularly to Part 3 of the instructions, published in the May 1975 issue.—Peter R. Smith (Stockport).

Scientific error?

I have read with interest the letter by R. T. Russell (September 1975 "Letters"), regarding the apparent malfunction of the Sinclair Scientific Calculator.

The malfunction was caused by the entry $1,E,1+1,E-9,9,+$ which gives 2.0000 01, i.e. 20.

The cause of this anomaly is due to the number being entered incorrectly.

The Sinclair manual states on

page 10 that for fractional numbers the entry must be made with a leading zero, that is, $0,1,E,-9,8,+$.

Using this, the original problem is correct, and now looks like the following:— $1,E,1,+0,1,E,-9,8,+$, which gives 1.0000 01, i.e. $10+1^{-99}=10$.

I hope this will clear up any problems other readers have had in this area.—H. C. Pike (Berks).

Improve your mind!

I would like to take this opportunity to inform your readers of an RAE course to be held on Thursday evenings between 6.30 and 9 p.m., at Birkenhead Technical College, Borough Road, Wirral. The lecturer will be Mr. L. Roberts G3EGX, 38 Croxteth Avenue, Wellasey, Wirral.


Applications should be made early in September or via the lecturer.—A. Seed G3FOO (Wirral).

GOING BACK—

continued from page 478

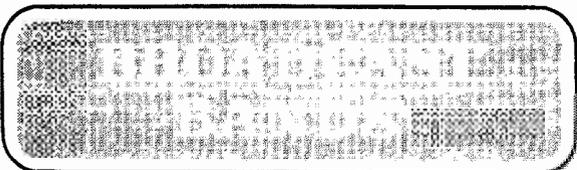- (2) Move the Fultograph instrument further away from the wireless set. This is likely to be required especially when a portable set is being used because of the possibility of interaction with the frame aerial.
- (3) It should never be necessary, but in extreme cases a certain cure can be made by using a separate HT battery for the Fultograph. This battery may then also be used for grid bias as well.

The Fultograph system for home use never really managed to get off the ground. It was a messy business, at the receiving end, making up the solution, cutting and soaking the paper, etc. Besides, television was being earnestly talked about at that time and rapid development of this medium doomed the Fultograph. In conclusion, I must thank once again all those readers who very kindly lent me notes, drawings and illustrations for this article. I have replied to some and I will gradually get round to answering all the many letters I have received on the subject of the Fultograph. Thank you all, and keep the letters coming in as we hope to publish extracts from some of them in future "Going Back" articles.



SHORT WAVE BROADCASTS

by *Derek Bell*

HURRAY for Radio Canada International! They very kindly sent me samples of the new programme schedules along with a sample of the new pennant. RCI also announce a change in policy in that the armed services transmissions are now separated from those of the Canadian overseas services for the purposes of QSL cards. In future armed services broadcast reports should go to "the department in question" although no address is given. I do not know if this will result in a separate QSL.

The first dip into the post bag this month brings forth **William Maybury** of Coatbridge in Bonny Scotland. This seventeen-year-old, using a twenty-foot length of copper wire hanging out of the window with "an ancient three band valved job" tied to the end, pulled in Pekin, much to his evident delight, and following this column's advice, QSLed them. (*Suggest it was Pekin via Tirana, Albania!—Ed.*)

Welcome to another new friend in **Dr. H. S. Broadribb** from St. Leonards-on-Sea. The good doctor seems to qualify for our "oldest living SW radio" stakes since he runs a 1948 Bush EBS4. While having some hard words about out-of-band Italian amateurs (passed to Eric Dowdeswell!) Dr. Broadribb asks for the address of Radio Budapest. This is Brody Sandor utca 5/7 1800 Budapest, Hungary. Radio Hanoi have been in touch and sent word to the Broadribb QTH that their schedule is 0100, 1000, all on 10040 and 12025, 1300 and 1600 GMT, plus a service on 10040 and 15120 at 1800, but it seems that the 15120 was heard at St. Leonards on 15005! Another example of out of band operation.

Many thanks go to all who helped **Dave Evered** of Cardiff with his Eddystone problems. In a second letter Dave says he received several letters of advice and assistance and is now able to use the set to such good effect that he has pulled in 32 QSL cards since April. He also enjoyed the strains of the Radio Australia "Pacific Islands Service" on 9770 at 1800. One final word from Dave is that he has reported four times to Moscow and seven to Cairo without reply. "How long DO they take?" he cries! Well Dave, Moscow was reported in July as taking between 37 and 77 days (by the WDXC QSL column) while Cairo was credited with 108 days!

The calibration station he calls the "Turin Clock", on exactly 5000, has turned up again in a report from **Harold Emblam** who says it was at fair strength from 1545 to 1600 frequently during July, heard at Mirfield, Yorks, on an Eddystone 730/4. Although the Latin American DX is on the way out as winter draws on the last gasp may well be worth going for. With this in mind **Raymond Robinson** reports that RTV Dominicana, recently featured in this column, is now on 9505 in English at 2145 to 2200. This was heard in Luton on Raymond's VEF 204.

The close relative of the 204, the VEF 206, is in use at **James Farrar's** QTH in Crook, Co. Durham, sprouting a ten-foot vertical aerial. James passes on the tip that Radio Austria is following up QSL reports with a free booklet listing the times, frequencies, and wavelengths of broadcasts to Europe. The address to write to is:—Austrian Radio Technical Dept., P.O. Box 200, A-1043, Vienna, Austria. James notes the rarely reported Radio Bangladesh on 15620 at 1225 to 1230 in English.

Steven Witt, residing in London wonders why this column does not give more space to logs rather than information on preselectors, bandspread or suchlike electronic wizardry. Well Steven, many readers are newcomers and need the help, plus the fact that this year has not so far been exceptional for DX. Thus the same stations get reported by several readers, and if reproduced would tend to be repetitious. The inhabitants of your shack are listed as a modified Chapman communications set with the PW audio processor, ATU and a 40-foot inverted-L aerial. If I can help readers to achieve this standard then the reports that plop on my doormat will be more varied. As it is, I am amazed that so much is reported with simple equipment.

Jolyon Jenkins from Knebworth, in Herts, is an avid QSL collector and would like to increase his score but is uncertain how to go about it. The requirements for a report are as follows, time of broadcast, frequency, date, receiver type, aerial type, SINPO rating of signal, and ten minutes worth of programme content written out. Do not forget your name and address and I always advise people to add a polite letter. Many stations need International Reply coupons in order to cover return postage but more often than not this only applies to the smaller stations or those that exist on donations, such as religious broadcasters.

I hear that Radio Finland is to continue its English language transmissions. Readers will remember that this column recently carried a reader's letter appealing for support to save them. It seems that letters from the fans of Radio Finland have won the day. That seems to be all for this month so I will wish you 73s and all the best to you and yours.

AMTRON KITS

- UK 302** Radio Control Transmitter 4 channel £17·50p
- UK 105/C** FM Microtransmitter £8·07p
- UK 325** R/C 'Gxc2' Channel Splitting Unit 1000 cc 2000Hz £8·34p
- UK 330** 'Gxc2' Channel Splitter Unit 1500 cc 2500 Hz £8·34p
- UK 220** Signal injector £3·53p
- UK 345/A** Superhet R/C Receiver £8·81p
- UK 555** R/C 27mHz Field Strength Meter £9·65p
- UK 780** Electronic Metal Detector £11·65p
- UK 875** Capacitive Discharge Electronic Ignition Unit Neg. Earth £17·33p
- UK 230** AM/FM Antenna Amplifier £4·16p
- UK 285** DHF/UHF Antenna Amplifier £8·87p

★ NEW ★ NEW ★ NEW ★ NEW ★

I.C. INSERTION TOOL

Just pick the I.C. up with the tool, which brings into line the pins and insert direct into the P.C.B. or D.I.L. sockets. So simple but a very great time saver.

£1·45

★ NEW ★ NEW ★ NEW ★ NEW ★

I.C. EXTRACTION TOOL

45p EACH

MULLARD BY164

Bridge Rectifier

In Line Pins
120 Piv. 1·4 amp. **45p each**

MINIATURE GLASS ENCAPSULATED REED SWITCHES

Glass Body 20mm long
Normally Open Contacts

5 for £1·00. 50 for £8·50
100 for £16·00

DISPLAYS

Type EP27
common anode
4 for £5·00

MAINS NEON INDICATORS RED OR AMBER

Round—Panel Mounting—Press Fitting—Tag End Connections
1/2" dia. x 1 1/2" long

4 for £1. 25 for £5
50 for £9. 100 for £17

LM 3900
NATIONAL SEMI-CONDUCTOR
14 pin DIL quad amp
69p

ALL PRICES INCLUDE

V.A.T.

Please allow 20p to cover P. and P.

723

FAIRCHILD

14 Pin DIL
var. voltage
Regulator

65p

LM 380

NATIONAL SEMI-CONDUCTOR

14 Pin DIL
2 watt
Audio Amp

£1·20

741

FAIRCHILD

8 Pin DIL
Op-amp

33p

LM 1303

NATIONAL SEMI-CONDUCTOR

14 Pin DIL
Stereo
Pre-Amp

£1·65

MC 1310P

MOTOROLA

14 Pin DIL
Coiless
Stereo
Decoder

£2·30

ZN 414

FERRANTI

Radio
Chip

£1·25

NE 555v.

SIGNETICS

8 Pin DIL
Timer

70p

MM 5314

NATIONAL SEMI-CONDUCTOR

24 Pin DIL
Clock Chip

£4·35

2N 3055

R.C.A.

70p

TIP 3055

TEXAS

50p

LM 380/8

NATIONAL SEMI-CONDUCTOR

8 pin DIL
1 watt
Audio Amp

£1·05p

SMOOTHING CAPACITORS CAN TYPE

1250 µF 25V. **40p**
Size: 1" x 1 1/2"

1500 µF 160V. **£1·50**
Size: 2" x 4"

4700 µF 63V. **£1·10**
Size: 1 1/2" x 4"

6800 µF 40V. **90p**
Size: 1 1/2" x 4"

10,000 µF 40V. **£1·50**
Size: 2" x 3 1/2"

10,000 µF 63V. **£1·75**
Size: 2" x 4 1/2"

15,000 µF 16V. **60p**
Size: 1 1/2" x 4"

SEMICONDUCTORS AND INTEGRATED CIRCUITS (TTL—CMOS)

We have in stock a very wide range of the above. All brand new and full spec. Devices at competitive prices.

WHY NOT PHONE US FOR YOUR REQUIREMENTS?

MACK'S ELECTRONICS

283 EDGWARE ROAD
LONDON W2 1BB

TEL. 01-262 8614


HOURS OF BUSINESS—9.30 a.m.—6 p.m., MON. TO SAT.

LISTEN TO

CODAR®

THE WORLD!

★ **CR70A**

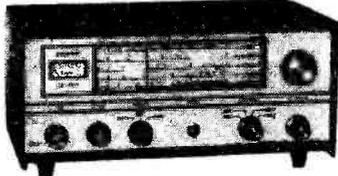

COMMUNICATION RECEIVER

★ **MADE TO ORDER!**
£39.00! (carr. free)
+ VAT **£9.75**

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.
It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q", Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder.
Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

* Special discounts for Educational Authorities and Senior Citizens.



"Free Gift!! Claim your Codar ball-point pen free with your next order!!"

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX
WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE.



★ **MADE TO ORDER!**

★ **P.R.40** ★



£11.00! (carr. free)
+ VAT **£2.75**

R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes.
It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio.
Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee . . .



★ **MULTIBAND-6** ★

SHORT WAVE RECEIVER KIT

£16.56! (carr. free)
+ VAT **£4.14**

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspeed, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual. fully detailed step by step.
Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST (STAMP APPRECIATED)

CODAR®

NEW! AVAILABLE SOON!!
THE MINI-CLIPPER STARTER KIT. ALL SOLID STATE SHORT WAVE RECEIVER. ALSO SUPER HI-"Q" A.T.U.

Tel: LANCING 61901

BN15 - 8TZ

PLEASE ADD APPROPRIATE V.A.T.

P&P and Ins. Extra



PERSONAL CALLERS ARE WELCOME!

all items subject to manufacturers increase and availability



High Quality Construction Kits, stocked at all branches. Send for catalogue!

AMPLIFIERS P&P 95p	Ins. £1
Sansui AU2200	£50.96
Garrard AU4400	£78.00
Sinclair 4000	£50.00
Pioneer SA5300	£45.60

RECORD DECKS P&P 85p	Ins. 50p
Garrard SP25 Mk. IV	£16.80
Garrard SP25 Mk. IV/G800	£27.50
Plinth & Cover	
BSR MP60	£12.75
Connoisseur BD1 Kit	£13.25
BD2 Chassis/SAU2	£34.15
SAU2 Pick-up Arm	£14.25
SCU1 Cartridge	£5.95
Pioneer PL12D	£46.59
Sansui SR212P	£44.80

SPEAKERS P&P 45p	
EMI 13" x 8", 8 ohm plain	£2.50
with co-axial tweeter	
8 ohm only	£2.75
with Tweeter & Crossover	
15 ohm only	£4.25
Type 350 8 ohm, 20 watt	£8.25
13" x 8" Bass unit, 15 watt	£5.45
8" x 8 ohm, 10 watt	£2.95
8" x 8 ohm, 10 watt	£4.50
8" x 5" C. Mag, 5 watt 3, 8 or 15 ohm	£1.70
8" x 5" Dualcone 8 ohm, 10 watt	£2.95
Elac 6 1/2" 8 ohm Dualcone	£2.45
8" x 8 ohm Dualcone	£2.70
Baker Group 25 12", 8 or 15 ohm	£12.00
Adastra 10" 10 watt, 8 or 15 ohm	£3.75

WHARFEDALE SPEAKER BARGAINS	
P&P 85p Ins. £1	
Denton 1 (pair)	£25.35

Denton 2 (pair)	£32.00
Denton 3 (pair)	£34.20
Linton 3 (pair)	£47.60
Linton 2 (kits)	£20.95
Glendale 3 (kits)	£35.95

KIT FORM CABINETS	
Teak Veneer P&P 85p Ins. 50p	
12" x 8" x 4 1/2" (8 x 5 or 7 x 4 cutout)	£3.75
14" x 12" x 7 1/2" (10", 8 x 5, 8", 6 1/2" and 3 1/2")	£5.25
18" x 11" x 7 1/2" (8" x 3 1/2" or 13 x 8)	£6.55
22" x 14" x 7 1/2" (12" x 3 1/2" or 13 x 6)	£7.95

TWEETERS & CROSSOVERS	
P&P 25p	
Cone Tweeter 8 or 15 ohm, 10 watt	£2.95
Cone Tweeter 8 ohm, 3 watt	£1.55
Horn Tweeter 8 ohm, 20 watt	£6.50
Dome Tweeter 8 ohm, 30 watt	£5.75
Crossovers CN23 (3 ohm) CN28 (8 ohm), CN126 (16 ohm)	£1.40

CARTRIDGES & STYLII			
P&P 25p	Cart.	D.D.	Stylin
Acos GP91/25C or 35C (ster. comp)	£1.10	£1.25	
GP93/1 or 95/1			
ster. cryst	£1.35	£1.25	
GP94/1 or 96/1			
ster. ceram.	£1.75	£1.25	
GP101 cryst. comp.	£0.80		
GP104 ster. ceram.	£1.95	£1.25	
BSR X5M or H5X			
cryst. comp.	£1.95	£1.25	
SX6M or SX6H			
cryst. ster.	£2.10	£1.25	

SC5M ster. ceram.	£2.85	£1.25
Sonotone 9TAHC or 9TAHC G (Diam)	£1.95	£1.25
3509 ster. ceram.	£1.95	£1.25
Audio Technica AT55	£1.95	
Empire 999 REX	£3.95	
Goldingr 6850	£3.10	£1.95
G800	£4.25	£1.95
G800H	£4.25	£1.95
G800E	£7.25	£3.95
Shure M44G	£4.95	£3.95
M55E	£3.25	£4.95
M75ED Type 2	£11.75	£8.25
M75EJ Type 2	£9.75	£6.25
V15 Type 3	£32.25	

MICROPHONES P&P 25p	
CM70 Planet stick metal, switch	£1.70
DM160 Dynamic omni-dir. ball metal	£4.95
UD130 50K 600 ohm, uni-dir, ball metal	£6.75
TW209	£5.90
CONDENSER MIKE 600 ohm, uni-dir.	£9.50
Cassette STICK MIKE with R Control on/off switch (2.5 & 3.5 mm) J/Plv)	£1.85
Cassette STICK MIKE with R/Control (Phillips Type)	£2.00

BATTERY ELIMINATORS	
P&P 25p	
240v input 6, 7.5 or 9 volt output	£3.10
12v d.c. Input (specify output 6, 7.5 or 9 d.c.) at 300mA	£2.45

CASSETTES P&P25p				
Type	Low noise	Phillips	Memorex	Ampex
C45	35p	55p	65p	45p
C60	45p	75p	75p	55p
C90	45p	75p	£1.10	75p
C120	55p	£1.10	£1.55	99p

CASSETTE CASES	£0.12
Cassette Head Cleaner	£0.45
BIB Stereo Test Cassette	£2.15
AMPEX Head Cleaner Demag	£1.65

TAPES P&P 25p			
Std.	LP	DP	Cases
55p	65p	£1.00	20p
65p	85p	£1.35	25p
80p	£1.10	£1.85	30p

BIB ACCESSORIES P&P 25p	
Compact Tape Head Cleaning Kit Ref. J	£0.55
Tape Editing Kit Ref. 23	£1.45
Record Tape Splicer Ref. 20	£1.25
Cassette Tape, editing Ref. 24	£1.60
Cassette Salvage Kit Ref. 29	£0.55
Hi-Fi Stereo Hints & Tips Book Ref. 56	£0.32
Stylus Balance Ref. 32A	£1.30
Spirit Lever Ref. 46	£0.60
Hi-Fi Stereo Test Cassette	£2.60
Groove-Kleen Record Cleaner	£2.00

PLEASE BRING THIS ADVERTISEMENT TO OBTAIN THE BENEFIT OF THESE SPECIAL PRICES

ALL MERCHANDISE FULLY GUARANTEED

NEWMART ELECTRONICS

Mail Order Dept
Belmont St, Monton,
Eccles, Manchester.
Tel: 061-789 5268

Manchester
30-32 Shudehill. tel 061-832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738



MEDIUM WAVE DX

by **CHARLES MOLLOY**

RAMADAN, which starts on the 7th September this year is a four-week period during which broadcasts from the Middle East should be conspicuous on the medium waves. Many outlets which would normally sign-off during the evening will remain on the air all night giving the medium wave DXer the opportunity to log a number of rarities. Look for Kuwait on 539kHz and 1345kHz; Riyadh, Saudi Arabia on 587kHz; Tabriz, Iran on 647kHz; Bagdad 760kHz; Thourah, Iraq on 908kHz; Izmir, Turkey on 926kHz; Radio Sanaa, Yemen on 1000kHz; Radio Pakistan, Hyderabad 1010kHz; Dubai on 1250kHz and 1480kHz; Oman on 1259kHz; Kabul, Afghanistan on 1280kHz; Sharjah on 1575kHz. Broadcasts from Algeria can be heard on 251kHz on the long waves and on 529kHz, 548kHz, 890kHz, 980kHz; from Morocco on 209kHz (long waves) and 593kHz, 611kHz, 827kHz, 1232kHz; from Libya on 1124kHz and 1250kHz and from Tunisia on 629kHz and 960kHz.

Roy Patrick (Mackworth, Derby) has been digging out some interesting DX on the medium waves between the hours of 0200 and 0300 GMT, using a Trio 9R59D communications receiver. Trans World Radio in Bonaire (Netherland Antilles) was heard on 800kHz (this station broadcasts in English); Amman in Jordan also on 800kHz; CJON St John's in Newfoundland on 930kHz; WINS in New York City on 1010kHz and Radio Tupi in Sao Paulo, Brasil on 1040kHz. A fine log which covers three continents.

Fifteen-year-old **Stephen Boyle** of Auchterarder in Perthshire is a newcomer to the medium waves. Using a Philips receiver and the metal core of his mother's washing line as an aerial (a dangerous practice with a mains receiver) he logged Radio Sweden on 1178kHz (in English at 2345), Radio Montecarlo on 1466kHz and an unidentified broadcast 'Paris Calling Africa'. Stephen is hoping to obtain an ex WD CR100 communications receiver. The CR100 can often be obtained privately for quite a modest sum. In spite of its age it is a really outstanding performer on the medium waves. **Dr H. S. Brodribb** (St Leonards-on-Sea) reports that he has acquired a CR100 which he intends to recalibrate. Together with **Roger Barker** (Wolverhampton), **D. Sullivan** (Chiswick) and **James Woodruff** (Cannes, France) he asks for information about the FET Pre-amplifier which is used with the Practical Wireless Medium Wave Loop antenna. An article covering the amplifier and the loop appeared in the April 1973 issue of Practical Wireless. Although this issue is out of print copies may be obtainable by advertising in the CQ column.

Alfred Johnson (Barnet) has been active on the band between the hours of 0200 and 0300 GMT during the month of June. His log includes an interesting group of broadcasters in Newfoundland, mainly at the low frequency end of the band; VOXM in St John's on 590kHz, CBNA St Anthony on 600kHz, CKCM Grand Falls on 620kHz, CBN St John's on 640kHz, CJCJ Grand Falls on 680kHz plus the most regular of all North Americans, CJON St John's on 930kHz. Other North Americans reported are WNBC on 660kHz, WABC on 770kHz, WCBS on 880kHz, WINS 1010kHz all in New York City, WHDH on 850kHz and WBZ on 1030kHz, both in Boston and the Canadians CBH Halifax Nova Scotia on 860kHz, CHER Sydney N.S. on 950kHz and CBA Moncton, New Brunswick on 1070kHz. During the month of September North American DX starts to come in after midnight GMT.

AMATEUR BANDS

by **Eric Dowdeswell G4AR**

LET'S start off this month with a note on a new group that has been formed in Edinburgh, the Pioneer Radio Club. First meeting is on 9 September, a Tuesday, and subsequent meetings will also be on Tuesdays at the Church Hall, Ravenscroft Street, Gilmerton, Edinburgh. First guest speaker will be George Burt better known on the air as GM30XX (with whom I have had the pleasure of many a snappy QSO on CW!). So switch off those rigs on the 9th and get along to support this new project. Further info from my informant, Mr. A. Sinclair, 32 Burdiehouse Street, Edinburgh EH17 8HB, or ring him at (031) 664 6570.

Ian Fay (Mansfield) reports for the first time on his doings from 15 to 80m using a Trio 9R59DS, Codar PR40 preselector and an ATU, the last two items having 'markedly increased results over the last few weeks'. **Stephen Budd** A8713 (Worthing) did not leave 20m judging by his log but remained

content with several new countries including Sabah 9M6, Mount Athos SV1GA/A, and EA9ES/EA9 obviously on holiday in the sunny Spanish Sahara!

Mike Green A8088 (Northwich) stuck to set-up consisting of a QP166 front end feeding a CR100 as tunable IF plus PW audio processor plus half wave dipoles and covered all bands from 10 to 160m. I think we had better shorten the description of his gear to the 'Green Mk1!' If **Peter Walton** A9002 ever gets on the air he will be in dead trouble with a QTH like Llanfairpwllgwyngyll! In Gwynedd, incidentally. His location in lat and long might be easier! I'm glad to see he logged at least one station using CW on his Eddystone 358X and 85ft long wire. I know it is so easy to copy SSB but give the low end of the bands a go now and again, chaps.

Steve Cottis A8961 (Harrogate) has been very busy, completing his Heathkit SW717G, joining the RSGB and going on holiday. He comments on the number of stations on 80m who seem to forget to mention call signs. I'd like to think that these are mainly non-amateur services who share the band with the amateurs. Another busy bee is **Mark Hill** A9008 (Birmingham) who, very wisely, has a plan of campaign which includes an audio processing unit, a ground plane for 2m and a set for 70cm based on a Microwave Modules module! Oh, yes, he did send a log! It is a very sensible idea to make



out a rough plan of 'things-to-do' especially as we approach the winter season. Work on aeri-als should be done now while the weather is fine leaving constructional work for later.

An interesting letter from professional yachtsman **Bob Salmon** (Wembury, Devon) who normally uses commercial gear on the marine frequencies but is now keen on an amateur MM licence. He mentions DJ9ZT/MM who has a daily schedule with DK0SS and DLOMX at 1400 daily on 14100 SSB. **Alan Doherty** (Portrush) is BRS34968 and very impressed with the improved results obtained by using a new Codar PR40 preselector in front of his FR50B and 132ft dipole. **D. Harley** (Chesterfield) at 15 has already outgrown his HAC set and looks forward to you-know-who at Yuletide! Don't worry too much OM about the arms of your dipole wandering from the straight lines shown in the textbook! Why not use 300 ohm feeder and an ATU and use it on all the bands?

Graham Nicholls G4DLB (Banbury) has not deserted the page in spite of getting his full ticket! He's full of praise for the excellent conditions he's been experiencing on 2m with an OZ causing cross-modulation of signals on his receiver! Graham has been busy working round Europe with his 15W from a Pye Vanguard. On 70cm he has worked a string of PA0's and Germans with 6W to a QQV03-25 and 15 elements at just 10½ft! **Godfrey Manning** G8JBH (Edgware) has also been having fun on 2m with 18W input and a five element yagi in the loft.

Michael Bennett (Datchet) found HK0AA on San Andres on 20m SSB while **Andrew Swiffin** (Cheadle) went about it the hard way copying HK0COK on 40m SSB. Our SSTV 'king' **Paul Barker** (Sunderland) managed two new countries on that mode, namely OZ and VU2. His first pictures on 40m came from OE9IM. **David Coupe** BRS35997 (Thornton Stainton, Middlesbrough) has also been extolling the virtues of 2m but 'A's 'O's and RAE's have been taking up all the time! He recommends any readers in the Middlesbrough area to pay a visit to the Middlesbrough PO ARC (G8BAY and G8GPO) any Thursday evening at 200 Marton Road, next to the main telephone exchange. More details from Graham Gaunt G8CDP QTHR. **Steve Blake** A8597 is yet another who preferred 2m to the HF bands, in Aylesbury.

C. Ashby (High Wycombe) dusted off his FET receiver and 30ft vertical only to hear a very strange call sign, 7SL4BP, on 20m. This military radio club is at Falun in Sweden.

Nothing further yet on our proposed competition for readers of this page. Some 'administration problems' have arisen which need to be sorted out.

Log extracts

I. Fay:— 80m VU2GDG ZB2BK 20m FP8DH HP9XJS HR6FWA KG4AN KZ5TC 15m CE3EG ZP5AR

M. Green:— 20m CR4DF FY7AN HR6SWA VP2AB

P. Walton:— 20m TU6DMF 9M8VLC 9V1RD

M. Hill:— 20m A2CBW JW5NM 2m F1ALS F1QV (both via Oscar 7)

G. Nichols: 2m **DJ6LN** DC0BI OZ1ABF OZ4BE SM4AXY 70cm DC8CF DK7LP **PA0VV**. All stations worked.

A. Doherty:— 80m C31FO 20m KH6AHO KM6EA YJ8AN

M. Bennett:— 80m YS3FU 20m PJ3DO HK0AA FL8CH

A. Swiffin:— 80m ZS6HVM 8P6CJ 40m FL8OM HK0COK VK2AVA VU2GDG YS1SC 20m VE8MD VQ9GP VQ9P ZD7SD

D. Coupe:— 2m DK1KO ON5CW OZ5TG PA0SWH SM6BHZ

J. Hinton:— 80m M1BS 20m VK6CT 15m HM4VBK PZ5WU ZP5JN

S. Blake:— 2m DL2VB GD3FLH/P OZ1OF PI50ARU SM6AEK

P. Barker:— SSTV 40m OE9IM 20m DJ2IV F3RT HB9IT OD5JW OE9IM OZ3WP VU2AIK 20m SSB A6XR JW5NM LA4C (Dx-pedition?)

S. Budd:— 20m AP2SA EA5ES/EA9 FB8ZG Amsterdam Is. FP0XX HB0AWQ JT1AI JW5DQ KH6GKD/KB6 KS6FF PV0AKL Fernando de Noronha SUI1MA SV1GA/A Mt. Athos VK9XI Christmas Is. 3B8DO 5T5GS 5W1AR

All stations are SSB except those in bold which are CW.

BROADCAST BANDS

Short Wave reports by the 15th of the month to Derek Bell c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/ alphabetical order by the end of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey, KT21 2TW.

TELEVISION—OCTOBER

●VIDEOCASSETTE RECORDERS

A two part examination of the Philips N1500 VCR machine, describing its mechanical arrangements and control systems and the signal coding techniques used.

●SWITCH-MODE TV POWER SUPPLIES

Several switch-mode power supply circuits used in TV sets at present on the market are described, and advice is given on servicing.

●BASIC TRANSISTOR LINE OUTPUT STAGE OPERATION

Since this circuit is the heart of any TV set, it is worth knowing just what goes on in this department. The article illustrates exactly what happens during the various stages of the scan cycle.

●SERVICING FEATURES

Colour chassis used in the Korting 90° series of models. A guide to common faults.


Decca monochrome dual-standard chassis used in the DR1 series.

PLUS ALL THE REGULAR FEATURES

ON SALE SEPTEMBER 15

NEW EDU-KIT MAJOR

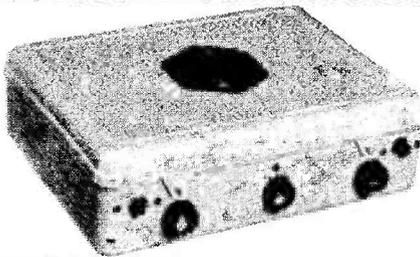Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder



Total Building Costs


£10-30 PP Ina. 85p
(Overseas Seamail P & P £8-40)

Components Include: 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3 1/2" Loudspeaker ● Ear-piece ● Mica Baseboard ● 3 12-way connectors ● 2 Volume controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6 1/2 yards of wire ● 1 Yard of sleeving etc. ● Parts Price List and Plans 55p free with parts.

- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator.
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier.

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

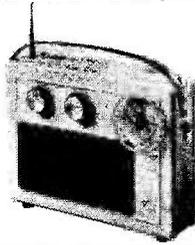


Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans free with parts.

Total Building Costs **£8-70** PP & Ina. 58p
(Overseas Seamail P & P £8-40)

NEW Everyday Series

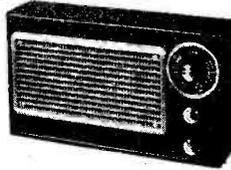Build this exciting New series of designs E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans free with parts.



Total Building Costs **£4-25** PP & Ina. 50p
(Overseas Seamail P & P £2-30)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

Total Building Costs **£4-98** PP & Ina. 50p
(Overseas Seamail P & P £2-30)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans free with parts.

Total Building Costs **£5-60** PP & Ina. 50p
(Overseas Seamail P & P £2-50)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL 7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.




Total building costs **£8-73** PP & Ina. 65p
(Overseas Seamail P & P £3-50)

ROAMER TEN Mk 2

WITH VHF INCLUDING AIRCRAFT


Now with free earpiece and switched socket. 10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeaker. 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

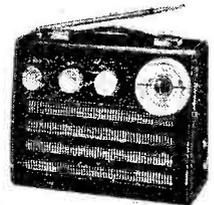

(Total building costs Overseas Seamail P & P £3-50) **£11-87** PP & Ina. 65p

POCKET FIVE

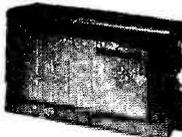NOW WITH 3" LOUD-SPEAKER 3 Tunable wavebands. M.W. L.W. and Trawler Band, 2 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/4" approx. Plans and Parts Price List free with parts.



Total Building Costs **£3-70** PP & Ina. 38p
(Overseas Seamail P & P £2-30)

TRANSONA FIVE NOW WITH 3" LOUDSPEAKER


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List free with parts.

Total Building Costs **£4-00** P.F. & Ina. 38p
(Overseas Seamail P & P £2-30)

TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1 SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

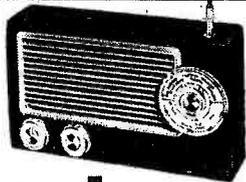Total building costs **£5-98** PP & Ina. 50p
(Overseas Seamail P & P £2-50)



ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1 SW2 Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Total building costs **£5-48** PP & Ina. 50p
(Overseas Seamail P & P £2-50)

"EDU-KIT"



Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct

Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

Total building costs **£6-87** PP & Ina. 50p
(Overseas Seamail P & P £3-40)

"ALL PRICES NOW INCLUSIVE VAT"

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelle's" shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 ISA
Tel.: 0234 52867. Reg. No. 788372.

I enclose £..... for

Name.....

Address

(Dept. PW.10)

Have you seen
this years most important
component catalogue yet?

**HENRY'S 1975
CATALOGUE
IS NOW AVAILABLE**



Don't buy another electronic component until you've considered the Henry's 1975 issue! It's packed with more items than ever before—over 5000 in all, making the Henry's range of electronic components the largest in the UK for the home constructor. There are literally dozens of new lines and new ranges to get excited about! And many components are selling at reduced prices. Get your copy soon, and start reading these 200 pages of vital statistics about electronic components. If you don't, you'll miss out on a lot of kits, projects and test gear, apart from all the other products.

ONLY 50p

+20p p & p

Complete with
FREE 50p
Discount Voucher!

FREE to Educational
Establishments when ordered
on official headed notepaper.

Get your copy NOW - send remittance of 70p (cheque or P.O.).

MIDLANDS:

New Electronics Store Open.
94/96 Upper Parliament Street,
Nottingham. Tel: (0602) 40403

HENRY'S

**ELECTRONIC FOOTBALL
& TENNIS**

WITH THE FABULOUS
VIDEO SPORT
ON YOUR OWN TV

Play three exciting electronic ball games. FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. M's operated.



OUR INCREDIBLE PRICE **£29.50/VAT**
DEMONSTRATIONS NOW IN ALL CENTRES!

AM/FM MODULES LP1179 LP1171
Combined AM/FM tuner modules, together with a small number of R.C.'s Ferrite aerials, make up a sensitive FM/MW/LW tuner. 6v. Supply, supplied with data and circuit sheets.
LP1171 COMBINED IF STRIP £4.60
LP1179, FM FRONT END AND AM GANG £4.60.
£8.62 THE PAIR.
Sultalia Ferrite aerial 87p.



UHF TV TUNERS

825 line receiver UHF transistorised tuners UK operation.
Brand new. (Post/packing 25p each).
TYPE A var. tun. slow motion drive **£3.50.**
TYPE C variable tuning **£2.90.**
TYPE B 4-button push button (ad.) **£4.60.**
TYPE D 6-button UHF/VHF tuner **£5.20.**

**ALL HENRY'S PRICES
INCLUSIVE OF VAT**

**Build the Texan & FM Tuner
TEXAN 20 +20 W STEREO AMP**

Features glass fibre PC board, Gardners low field transformer, 6-IC's 10-transistors plus diodes etc. Designed by Texas Instruments engineers for Henry's and P.W. 1974. Overall size 15 1/2" x 23" x 6 1/2" mains operated. Free teak sleeve with every kit.

£29.95 (CARRIAGE 50p).
(also built and tested £39.95)

HENELEC STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in teak sleeves 8" x 22" x 6 1/2". Complete kit with teak sleeve.

£26.25 (Carriage 50p).
(also built and tested £31.20).

**JOIN THE LARGE BAND OF
CONSTRUCTORS!**

**SPECIAL OFFER
GARRARD CT4 STEREO CASSETTE
TRANSPORT MECHANISM**

Features
● Stereo Heads
● Built in Motor Stabiliser
● Auto Stop-Eject
● Pause Control
● 12V DC Operation
Robust, precision engineered mechanism based on the "STARR" patented design, ideal for use in Car stereo cassette players, hi-fi stereo cassette recorders, industrial and many other applications. Suitable for the 'PW' Ascot Stereo Cassette Deck.
£13.50 inc. VAT p & p 35p



FREE:
**SEND NOW FOR OUR FREE LIST
NO. 36 FOR OUR COMPLETE RANGE
OF OVER 10,000 SEMICONDUCTOR
DEVICES AT NEW LOW PRICES.**

Electronic Centres
505, 406 Electronic Components & Equipment 01 402 8381
354 PA Disco Lighting High Power Sound 01-402 8554
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Prices correct at time of preparation. Subject to change without notice. E & O E

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday-Saturday

ALL BELOW—ADD 25% VAT
TV plugs, metal type, 6 for 50p.
TV sockets, metal type, 5 for 50p.
TV line connectors (back-to-back socket), 4 for 50p.
Mixed electrolytics, large bag, £1.
OC200 transistors, 6 for 50p.
BSY95A transistors, 6 for 50p.
PNP audio type TO5 transistors, 12 for 25p.
IF cans 1/2" square, suitable for rewind, 6 for 30p.
DIN SPEAKER SOCKETS (2-pin) 4 for 30p.
HIGH QUALITY SPEAKERS, 8 1/2 x 6 1/2 elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W. £1.50 each, or 2 for £2.75 (qty. discount available).

ALL BELOW—ADD 8% VAT
Black plastic knobs, 1/2in dia., 1/2in spindle, 4 for 50p.
Ring magnets, 7mm outside dia., 20 for 50p.
Large box of P.C. Boards, containing transistors, I.C.'s, trim pots, resistors, capacitors, etc. (not unknown computer rubbish), £3 per box.
1/2in polythene chassis mounting fuseholders, 6 for 30p.
LES Lamps, 24V 2W, 10 for 40p.
3 Switch Push Button Units (3 x 2 pole, 2 way), min. push-push switches, 1/2in dia. buttons, mounted on one unit, 40p.
Perspex coil formers, 1 1/2in x 1/2in dia., 5 for 25p.
Turret tags, 1/2in dia., 25p pack.
Rotary switches, min. 4 pole 2-way, 2 for 50p.
Telephone type earpiece insert, 50p.
Reeds (for reed relays) single-pole make, 5 for 30p.
Multiturn tubular ceramic trimmers, 1-18uF, 6 for 50p (as featured in Rad. Comm. Jan. p. 25).
I.C.'s, some coded, 14DIL type, untested, mixed, 20 for 25p.
Miniature slider switches, 2 pole, 2-way, 5 for 50p.

ALL BELOW—ADD 8% VAT
VARIABLE STABILISED PSU, solid-state 240V a.c. input, output 0-24V d.c. at 500mA, +32V d.c. at approx. 50mA. Voltage controlled by external 5kR pot. Size: 7 1/2 x 2 1/2in (less 5kR pot). 15 each.
THREE-TURN WIRE-WOUND POTS, 5kR, for above, 75p each.
MAINS TRANSFORMERS
All 240V input, voltages quoted approx. RMS. (Please quote type no. only when ordering.)
TYPE 10/2, 10-0-10V at 2A, £1.50 each.
TYPE 18/2, 18V at 2A, £1.65 each.
TYPE 28/4, 28V at 4A + 125V at 500mA, £4.
TYPE 63/1, 6-3V at 1A, 85p each or 2 for £1.60.
TYPE 129, 400V at 20mA + 200V at 10mA + 6-3V at 500mA, £1.25.
TYPE 72/03, 400V at 10mA + 200V at 5mA + 6-3V at 400mA, £1.25.
TYPE 70462, 250-0-250V at 80mA + 6-3V at 2A, £1.75.
RADIOSPARES 500W AUTO TRANSFORMERS, 100-110-130-200-220-240-250V tapped input and output, step-up or step-down facility, ex-new equip. £6.
CURLY LEADS, 4 core telephone type, 2 for 50p.
TRANSISTOR HEATSINKS, to take 2 x TO18 transistors, screw in clamps, block size 1 x 1 1/2 x 1/2in, with holes for mounting, 3 for 50p.
LARGE DIE CAST BOXES (brand new I.T.T.) 10 1/2 x 2 1/2in, £2 each.
25-WAY ISEP PLUGS AND SOCKETS, 40p set (1 plug + 1 socket).
Rotary switches 9-way 4-pole (separate wafers, plastic) 1/2in spindle, 40p each.
Heatsinks (Approx. 3in x 4in 2in high), 12 fins (drilled for 1 x TO3 transistor) brand new, 45p each.
PC board withdrawal handles, mixed cols., 8 for 50p.
Scrap, 20SWG, 60/40 alloy, approx. 9yds, 25p.
TO3 transistor insulator sets, 10 for 50p.

TERMS OF BUSINESS: CASH WITH ORDER (minimum order £1) POST FREE (UK ONLY), PLEASE ADD VAT AS SHOWN
Export enquiries welcome. Callers welcome, Tues. to Sat.
Please enclose S.A.E. with ALL enquiries.

**Train for
television**

Course commences January 5th 1976

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept. PW1) 34a Hereford Rd., London W2 5AJ

IC OF THE MONTH

Number 54

MOTOROLA MC14440 CMOS CLOCK

A CMOS watch/clock integrated circuit which is capable of directly driving a four digit, seven segment liquid crystal display has recently been introduced by Motorola. Designated the MC14440, the new device comes in a 40-pin package and has a really low current consumption: $4\mu\text{A}$ when operating and only $0.1\mu\text{A}$ in the quiescent state.

The MC14440 is compatible with the recently announced Motorola liquid crystal displays type MLC500 or MLC400. To build a complete clock or watch with the new IC requires the LCD display, three switches, an MTQ32A 32.768kHz crystal, three diodes, five resistors, three capacitors and a 1.58V battery. The complete circuit is shown in Fig. 1.

CIRCUIT OPERATION

Under normal conditions, the LCD display will show the time in hours and minutes, the colon in between the hours and minutes digits flashing on and off twice per second. When the seconds/date demand switch (S3) is closed, seconds are displayed on the two right hand digits, the colon stays on and the other two digits are blanked. When S3 is returned to its normal position, the date will be displayed on the two central digits of the display for a couple of seconds, the outer digits and the colon being blanked.

SETTING THE TIME

When the hours display is indicating 12 the minute/date set switch (S1) acts as a minute set switch, the digits advancing at 1Hz. With the hours indicating anything other than 12 S1 acts as a date set switch, the digits again advancing at 1Hz. A separate switch (S2) is used for setting the hours to the required figures.

During the setting of the minutes digits, the second digits are set to zero and S1 acts as a clock start control, enabling the clock to be started with reference to a precision time standard.

An optional display test switch can be incorporated if required.

POWER SUPPLIES

The frequency of the on-chip oscillator is controlled by the 32.768kHz crystal, the exact fre-

quency being set by the 6.35pF trimmer. Outputs from the oscillator (HF and $\overline{\text{HF}}$) are provided which can be used to drive a simple diode/capacitor voltage tripler which produces an output of 3.8V, sufficient to drive the IC and the LCD display.

AVAILABILITY

At the time of writing, the MC14440 is not stocked by the Motorola distributors but the devices are expected to enter the country soon. Prices are £8.08 for the plastic package. For ordering details contact any of the Motorola distributors.

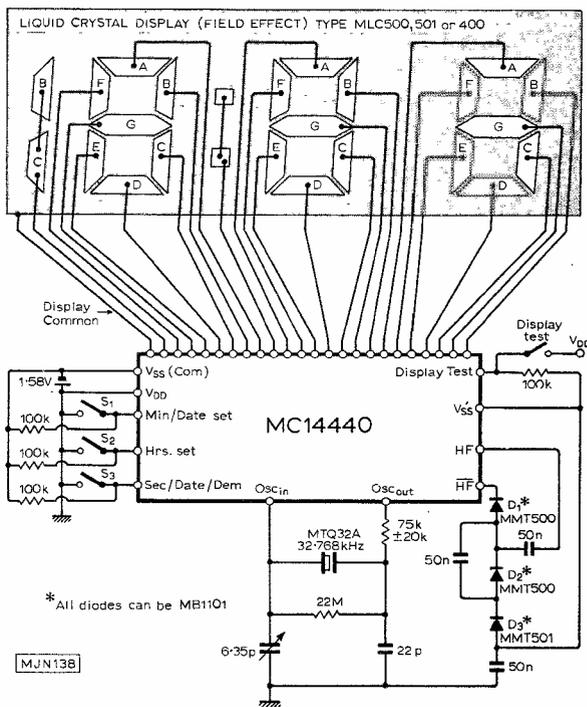


Fig. 1: Complete circuit using the MC14440 in a watch, with the new liquid crystal display type MLC500, 501 or 400.

FANE 'SPECIALIST' RANGE LOUDSPEAKERS



Illust.
12"
'DISCO 60'

OF OUTSTANDING QUALITY FOR THE DISCRIMINATING PROFESSIONAL

Features include **ROBUST CAST ALUMINIUM CHASSIS** and **2" EXTRA HIGH POWER VOICE COILS**. All models available in impedances of 8 ohm or 15 ohm. Guarantee: 2 years. Recommended Prices inc. VAT

12" 'DISCO 60' 60 watts R.M.S.

Linen Cone Surround. Fitted extra large Tweeter Cone. Frequency Range 50-15,000 Hz

Rec. Retail Price
£24.75

12" 'GUITAR 60L' 60 watts R.M.S.

Plastiflex Cone Surround. Aluminium Centre Dome. Frequency Range 50-9,000 Hz. DESIGNED FOR LEAD GUITAR

Rec. Retail Price
£23.50

12" 'GUITAR 60B' 60 watts R.M.S.

Linen Cone Surround. Frequency Range 45-9,000 Hz. Rec. Retail Price

£23.95

FOR USE IN MULTIPLES FOR BASS GUITAR

12" 'PA 60' 60 watts R.M.S.

Plastiflex Cone Surround. Fitted Tweeter Cone. Frequency Range 50-15,000 Hz. Rec. Retail Price

£23.50

FOR GENERAL PURPOSE PUBLIC ADDRESS

15" 'BASS 70' 70 watts R.M.S.

Linen Cone Surround. Frequency Range 40-7,000 Hz. Can be used singly but ideally TWO UNITS IN A SINGLE CABINET.

Rec. Retail Price
£33.75

RECOMMENDED FOR ALL BASS INSTRUMENTS

MODEL D40 50 WATT DISCO KIT

Consisting of 12" 13,000 Gauss BASS UNIT, HPXI HIGH POWER Cross-over and PH50 TWEETER. All purpose. Full range. Imp. 8-15 ohms.

£21.50

AND for those who can afford the very best there is our range of

'CRESCENDO'

MODELS

12" UNITS


from **£46.95**

Rec. Retail

15" UNITS

from **£60.95**

Rec. Retail

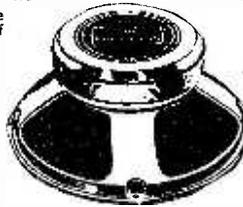

HIGH FREQUENCY HORN UNITS

MODEL 910 Mk II

Rating 50 watts with recommended filter. Rec. Price:

£16.95

MODEL 912 with even higher sensitivity

Rec. Price
£19.50

MODEL 920 Mk II (as illust) significantly increased sensitivity. Rating with recommended filter 100 watts

Rec. Price
£47.50

HPXI HIGH POWER CROSS-OVER UNIT Suitable for above Horn Units Rec. Price £2.50



Prices shown correct at 19 Aug, 1975

Distributors (Wholesale & Retail Trade): **LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.** Manufacturers enquiries to: **FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS.**

'POP' RANGE

FAST SELLING and RELIABLE UNITS

POP 15 12" 15w **£7.70**

POP 33 12" 33w **£10.99**

POP 50T 12" 50w **£14.95**

POP 55 12" 60w **£19.99**

POP 60 15" 60w **£22.95**

POP 70 15" 70w **£24.50**

POP 100 18" 100w **£38.95**

Available in impedances of either 8Ω or 15Ω

Please send S.A.E. for leaflets on any of above ranges

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the **Grad. Brit. I.E.R. Exam.**; the **RADIO AMATEUR'S LICENCE**; **P.M.G. Certificates**; the **R.T.E.B. Servicing Certificates**; etc. Also courses in **Television**; **Transistors**; **Radar**; **Computers**; **Servo-mechanisms**; **Mathematics and Practical Transistor Radio** course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. **Fullest details will be gladly sent without any obligation.**

To: **British National Radio & Electronics School, Dept W.C. 105 P.O. Box 156, Jersey, C.I.**

Please send **FREE BROCHURE** to

NAME Block

ADDRESS Caps.

..... Please

.....

BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL



4½in x 3½in **METER.** 30µA, 50µA or 100µA, **£3.85. P. & P. 13p.**

TAPE RECORDER LEVEL METER

500µA, 80p P. & P. 10p.



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, **£7.40. P. & P. 13p.**

42 x 42mm METERS 1mA, 10mA, 100mA, 500mA, **£2.76, 11p P. & P.**

60 x 45mm METERS 50µA, 100µA, 500µA and 1mA **VU METER £2.92, 11p P. & P.**

EDGEWISE METERS, 90mm x 34mm, 1mA £3.40, 13p P. & P.

MULTI-METER

Model ITI-2 20,000 ohm/volt, **£6.90. P.&P. 16½p.**



3WATT STEREO AMPLIFIER 1½W PER CHANNEL **£4.30. P. & P. 12½p.**

All above prices include V.A.T. **LARGE S.A.E. for List No. 12.** Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

ELECTROVALUE

Present

STABILIZED PRICE POLICY QUALITY COMPONENTS, KEEN PRICES AND DEPENDABLE SERVICE

112 page catalogue · attractive discounts · free postage & packing (U.K.)

A 100 OF THE BEST out of our latest catalogue

2N1307	47p	AF200U	40p	BD135	37p
2N2646	51p	AF239	60p	BD136	39p
2N3053	30p	B1906	36p	BDY20	83p
2N3054	60p	BA138	31p	BF194	15p
2N3055	70p	BB103	24p	BFR39	23p
2N3702	11p	BB104	48p	BFR79	23p
2N3703	10p	BB105	34p	BFX29	33p
2N3704	11p	BB107	18p	BFX84	27p
2N3705	10p	BC107B	18p	BFY51	23p
2N3794	18p	BC108B	15p	BRY39	50p
2N3819	28p	BC109B	18p	BY154	51p
2N4082	11p	BC109C	18p	C106B1	42p
2N4443	93p	BC109C	18p	C106D1	47p
2N5052	42p	BC147A	12p	C1408	78p
2N5163	20p	BC147B	13p	MJ481	£1.20
2N5459	35p	BC148B	12p	MJ481	£1.35
40361	48p	BC149C	14p	MJ2955	80p
40382	44p	BC1585	15p	MJE371	89p
40602	48p	BC159A	15p	MJE521	81p
40636	£1.36	BC167B	13p	MJE2955	£1.12
40669	£1.10	BC168B	12p	MJE3055	68p
AC128	17p	BC169B	12p	OA91	8p
AC151R	36p	BC169C	13p	SD4	8p
AC153	27p	BC179B	28p	TIP31A	70p
AC153K	37p	BC182L	12p	TIP32A	80p
AC176	24p	BC184L	11p	TIP41A	80p
AC176K	38p	BC212L	12p	TIP42A	£1.00
AC187K	31p	BC214L	14p	W02	30p
AC188K	28p	BC257A	14p	ZTX300	14p
AD133	£1.82	BC259B	14p	ZTX304	23p
AD136	£1.11	BCY58	78p	ZTX500	14p
AD149	52p	BD130	40p	ZTX504	45p
AD161	42p	BD131	78p		
AD162	40p	BD132	52p		

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6.3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	11p	8p	8p
1.0	—	—	—	—	11p	8p	8p	8p
2.2	—	—	—	—	11p	8p	8p	8p
4.7	—	—	—	11p	8p	8p	8p	8p
10	—	11	—	—	8p	8p	8p	8p
22	—	—	8p	8p	8p	8p	8p	10p
47	8p	—	8p	8p	8p	8p	10p	10p
100	8p	8p	8p	8p	8p	10p	12p	19p
220	8p	8p	8p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	—	—	26p	37p	41p	—	—
4,700	—	—	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/3	4.7-470K	1-3	1-1	0-9 nett
C	1/2	4.7-10M	1-3	1-1	0-9 nett
C	3/4	4.7-10M	1-5	1-2	0-97 nett
C	1	4.7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0.22-0.47Ω	18	14	11 nett
WW	1	0.56-3.9Ω	12	10	8 nett
WW	3	1-10K	9	8	6 nett
WW	7	1-10K	11	10	8 nett

Codes:

C=carbon film, high stability, low noise.
MO=metal oxide, Electrofil TR5 ultra low noise.
WW=wire wound, Plessey.

Values: All E12 except C 1/2W, C 1/2W and MO 1/2W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades.

E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:
5% except WW 10% ±0.05Ω below 10Ω and 1/2W MO 2%

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

all in the E.V. CATALOGUE 7 (issue 3)

112 pages of up-dated information and prices. More valuable than ever now that our price stabilizing has been introduced, includes a 25p refund voucher for spending on orders for £5 or more list value. So before you even look at a screwdriver, make sure you have your E.V. Catalogue No. 7 issue 3 to hand. Price, post paid

30p

PRICE STABILIZATION

Instead of changing prices from day to day with all the difficulties that brings, EV prices are held for 3 monthly periods and then reviewed to see if changes are necessary for the next 3 months following. So far, to date, we have made no changes since Jan 1st this year.

DISCOUNTS

apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

FREE POSTAGE & PACKING

In U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under, there is an additional handling charge of 10p.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to makers specifications. No rejects, seconds or sub-standard merchandise.

VAT

—add 25% to total value of order except for items marked ● which carry only 8% VAT. Every effort is made to ensure correctness of information at time of preparing and putting this advertisement to press.

CAPACITORS

DALY ELECTROLYTIC in cans, plastic sleeved

1000mF25V 34p	2200/100 £1.81
5000/100 £3.58	1000/50 50p
5000/25V 75p	2000/50 70p
2000/25 45p	5000/50 £1.44
1000/100 £1.00	

POLYESTER TYPE C.280, Radial leads for P.C.B. mounting. Working voltage 250V d.c.

0.01	0.015	0.022	0.033	0.047	ea. 3p
0.068	0.1	0.15			ea. 4p
0.22 5p	0.33 7p	0.47 8p	0.68 11p	1.0 14p	1.5 21p
2.2 24p					

SILVERED MICA. Working voltage 500V d.c. Tolerance 1% or 0.5p

Values in P.Fs—2.2 to 250 in 26, stages	ea. 6p
270-820 in 9 stages, ea. 7p	
1000, 1500, 1800 9p; 2200 10p; 2700, 3600, 4700, 5000 16p;	
6800, 8200, 10,000 25p	

TANTALUM BEAD

Values in P.Fs—2.2 to 250 in 26, stages	ea. 16p
0.1, 0.22, 0.47, 1.0 mF/35V, 1.5/20V	ea. 16p
2.2/16V, 2.2/35V, 4.7/16V, 10/6-3V	ea. 21p
4.7/35V, 10/16V, 22/6-3V	ea. 11p
10/25V, 22/16V, 47/6-3V, 100/3V, 6.8/25V, 15/25V	ea. 23p

POLYCARBON

Type B-32540 Values in µF:	
0.0047; 0.0088; 0.01; 0.015; 0.022	ea. 4p
0.018; 0.027; 0.033; 0.039; 0.047; 0.068; 0.1;	ea. 5p
0.056; 0.082; 0.12; 0.15	ea. 6p
0.18; 0.22 7p; 0.27, 0.33 9p; 0.39, 0.47 11p; 0.56, 0.68	16p

CERAMIC PLATE

Working voltage 60V d.c.
In 26 values from 22p to 6800pF, ea. 2p

POTENTIOMETERS

ROTARY, CARBON TRACK.

Double wipers for good contact and long working life
P.20 SINGLE linear 100 ohms to 4.7 meg ohms, each 14p
P.20 SINGLE log. 4.7 Kohms to 2.2 megohms, each 14p
J.P.20 DUAL GANG lin. 4.7 Kohms to 2.2 megohms, each 48p
J.P.20 DUAL GANG log. 4.7 Kohms to 2.2 megohms, each 48p
J.P.20 DUAL GANG antilog 10K, 22K, 47K, 1 megohm only, each 48p
J.P.20 DUAL GANG antilog 10K only 14p extra.
2A DP mains switch for any of above
Decades of 10, 22 and 47 only available in ranges above.
Skeleton Carbon Presets, Type PR, horizontal or vertical 6p each.

SLIDER

Linear or log mono 4.7K to 1 meg. in all popular values each 30p

STEREO, matched tracks, lin. or log in all popular values from 4.7K to 1 meg. 80p
Escutcheon plates, mono, black or grey, each 10p
Control knobs. blk/wht/red/yel/grn/blue/dk.grey/lt.grey, each 7p

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL. £1.20
Suitable BCD decoder driver 7447 £1.18
3015G showing + or - & 1 & dec. pt. £1.20

LEDS (Light Emitting Diodes)

Photo Cells, cadmium sulphide each 40p

ANTEX Soldering Irons

C240	£2.25	Spare bits	32p
CCN240	£2.65	Spare bits	42p

ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-5.30 daily; Sat. 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PW 7 S.A.E. with enquiries requiring answers.

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 25% Telephone 6743

0B2	50	6BA6	-91	6K8G	-58	12J7GT	-70	85C5	-85	DF96	-65
0Z4	55	6B08	-90	12K1	2.84	12K5	1.17	35D5	-90	DK40	82
LA3	65	6BE6	-41	6.6GC	-68	12K7GT	-59	35L6GT	-88	DK92	1.15
LA5GT	59	6BE9	-75	6L7	-59	12K8	-85	35W4	-80	DK96	7.0
LA7GT	70	6B36	-64	6L18	-64	12Q7GT	-83	35Z3	-88	DL06	6.4
LB3GT	59	6BK7A	-85	6L19	2.34	128C7	-59	35Z4GT	-82	DM70	8.0
LB5GT	80	6BQ7A	-64	6LD20	-88	128G7	-58	35Z5GT	-80	DY71	1.76
LI4	80	6B87	1.29	6Q7G	-50	128T7	-50	42	1.00	DY87/6	-41
LI5GT	70	6B88	1.00	6Q7M	-60	128T7	-70	58	1.00	DY87	-47
1R5	50	6BS7	1.64	6Q7GT	-60	128T7	-70	58	1.00	E80CC	2.57
1R4	39	6B8W	1.00	6Q7M	-64	128R7	-75	50C5	-70	E80F	2.50
1U4	70	6B8W	-65	6R7G	-70	14H7	-64	50CD6G	-88	E80CC	1.20
1U5	88	6BZ6	-57	6R7M	-88	1487	-1.10	50E2C	1.48	E80CC	1.20
9D21	90	6C4	-47	6SA7	-55	19A95	-65	50EH5	-88	E180F	1.17
2K5	75	6C6G	-59	6S7GT	-50	19G8	7.00	50L6GT	1.00	E180CC	3.00
2X2	70	6C8	-47	6S7G	-52	20D1	-80	85A2	-75	E1148	6.2
3A4	70	6C9	2.00	6S7H	-55	20F2	-88	85A3	-75	E1A50	-4.0
3D6	-47	6CD6G	1.60	6S7J	-64	20L1	1.39	90A3	2.93	E1A76	1.40
3Q4	85	6C8A	-88	6S7K	-52	20P3	84	90C1	-88	E1ADC0	4.5
3Q5GT	70	6CL6	-76	6S7L	-53	20P4	1.17	90C2	2.81	E1AC91	6.5
3S4	-47	6CL8A	-94	6V6G	-80	20P5	1.50	160B2	1.00	E1A42	8.8
3V4	82	6CM7	-88	6V6GT	-53	25A5G	-70	215S9	-59	E1AF80	1.80
4CB6	75	6C05	-88	6X4	-47	25L6G	-70	807	1.17	E1B34	-4.0
6C68	75	6CW4	1.17	6X5GT	-53	25Y5G	-80	5702	1.20	E1B91	2.3
6R4GY	-94	6D3	-75	7B6	-88	25Z4G	-50	5763	1.78	E1BC41	8.8
6U4G	-50	6D37	-88	7B7	-82	25Z5	-75	6057	1.00	E1B81	4.5
6V4G	-59	6D76A	-88	7H7	-88	25Z6G	-60	6060	1.00	E1BF80	4.8
6Y3GT	-55	6E9W	-88	7Y4	-88	25D7	2.00	6067	1.00	E1BF83	5.0
E23	-88	6E5	1.17	7Z4	-94	30A5	-76	7193	-62	E1BF89	-4.0
E24G	-55	6F1	-80	9D7	-76	30C15	-82	9008	-59	E1B21	2.84
E24GT	-55	6F6G	-80	10C2	-76	30C17	-70	9006	-59	E1C86	8.0
6/30L2	80	6F13	-90	10D7	-88	30C18	1.10	ACPEP	1.17	E1C88	9.5
6A8G	1.48	6F14	-88	10E1	-88	30P3	-78	ACZPEN	-88	E1C92	5.5
6AC7	80	6F15	-76	10F9	-76	30FL1	1.10	DD	1.17	E1C33	2.50
6AG5	-85	6F18	-64	10F18	-64	30FL2	1.10	ACSPEN	-80	E1C35	2.00
6AH6	80	6F23	-82	10LD11	-88	30FL3	1.05	ACTH1	-88	E1C40	1.20
6AJ5	-76	6F24	1.00	10P13	-88	30FL3	-64	AL60	1.00	E1C81	-4.0
6AK5	-47	6F25	1.17	10P14	2.34	30FL4	-82	ATZ4	-50	E1C82	3.9
6AK8	70	6F28	-78	12A6	-75	30L5	-82	ATP1	-50	E1C83	3.9
6AM8A	70	6F32	-70	12AC6	-90	30L17	-76	AZ1	-50	E1C84	-4.1
6AN8	-68	6G6G	-60	12AD6	-90	30P4MR	-70	AZ21	-85	E1C85	4.7
6AQ5	-53	6GH8A	-88	12AE6	-90	1.05	AZ1	-50	E1C86	1.00	
6AR5	-80	6GK5	-76	12AT6	-47	30P12	-80	BL6	2.34	E1C88	5.5
6AS7	1.17	6GU7	-88	12AU6	-53	30P19	-80	CL33	1.55	E1C189	8.0
6AT6	-58	6HGT	-29	12AV6	-59	30P4	-88	CT1C	1.00	E1C397	1.41
6AU8	-40	6HGT	-78	12BA6	-59	30P11	1.00	CY31	-70	E1C80	-5.0
6AV6	-53	6J6	-85	12BE8	-59	30P13	1.20	DAF91	-60	E1C82	-5.0
6AW8A	-90	6J7G	-85	12BH7	-59	30P14	1.29	DAF96	-60	E1C86	8.8
6AX4	-88	6JUS8A	-88	12BY7	-85	30P15	-94	DC90	-70	E1C804	2.68
6B8G	-35	6K7G	-85	12E1	2.51	35A3	-76	DF91	-35	E1C821	2.84

ECH35	1.60	EY84	-92	PCF801	-65	TP2620	1.00	W799	1.17	AD161	-59	BYZ19	-83
ECH42	95	EY87/6	-40	PCF802	-82	UABC80	-47	X65	1.46	AD182	-59	BYZ13	-83
ECH51	-40	EY88	-60	PCF806	-60	UAB47	-75	X66	1.46	AF114	-83	FSY11A	-89
ECH58	-58	EY91	-60	PCH200	-50	UC41	-70	X101	2.34	AF115	-20	FSY41A	-89
ECL84	-50	EZ40	-55	UBC81	-60	UC81	-60	Z759	5.85	AF117	-25	OA9	-16
ECL80	-50	EZ41	-55	PCL82	-45	UBF80	-47			AF121	-29	OA10	-55
ECL82	-45	EZ80	-85	PCL83	-55	UBF80	-47			AF124	-83	OA47	-13
ECL83	-82	EZ81	-85	PCL84	-50	UBL21	2.34			AF125	-22	OA70	-20
ECL84	-70	GY501	-82	PCL86	-55	UC92	-60	1N4744	-18	AF126	-23	OA73	-90
ECL86	-70	GZ32	-69	PCL805	-70	UC84	-90	2N404	-23	AF180	-62	OA79	-19
ECL86	-47	GZ33	1.46	PEN45	1.00	UC85	-53	2N966	-88	AF186	-71	OA81	-19
EP22	1.25	GZ34	-80	PEN45DD	UCF80	-80	2N1766	-84	BA115	-18	OA85	-12	
EP40	-48	GZ37	1.20	PEN46	1.00	UCI42	2.84	2N2147	1.10	BA116	-23	OA89	-16
EP41	-82	HAB080	-80	PEN46	-60	UCI43	-87	2N2297	-89	BA129	-16	OA91	-13
EP42	-90			PEN453DD	UC8H1	-47	2N2369	-18	BA130	-20	OA95	-12	
EP73	1.78	HL23DD	-80	PEN45	2.00	ULC82	-45	2N3053	-42	BA153	-20	OA200	-19
EP80	-30			PENDD	ULC83	-64	2N3121	3.22	BC107	-17	OA202	-13	
EP83	1.45	HL1ADD	4020	1.00	UF41	-82	2N3703	-25	BC108	-16	OC44	-13	
EP85	-40			1.00	PF1200	-82	UF42	-82	2N3709	-26	OC109	-16	
EP86	-50	HL2ADD	PL33	-50	UF80	-41	AA119	-20	BC113	-83	OC46	-20	
EP89	35			1.00	PL36	-70	UF85	-52	AA120	-20	BC115	-20	
EP91	-50	HVR309	1.76	PL81	-53	UF89	-47	AA129	-20	BC116	-33	OC71	-14
EP92	-60	HVR2	1.17	PL81A	-60	UL41	-75	AA123	-33	BC118	-29	OC72	-14
EP97	-44	HVR2A		PL82	-43	UL84	-49	AC107	-20	BC119	-59	OC74	-89
EP98	-96			1.17	PL83	-47	UM90	-80	AC113	-33	BC121	-64	
EP183	-40	KT41	1.17	PL84	-50	UY41	-50	AC126	-18	BCY33	-20	OC76	-20
EP184	-40	KT68	2.93	PL84	-50	UY41	-50	AC127	-22	BCY34	-29	OC77	-25
EP804	1.75	KT81	2.10	PL84/500	UY85	-50	AC127	-22	BCY38	-29	OC78	-20	
EH90	-53	KTW61	1.76	PL508	1.10	U19	5.00	AC154	-33	BCY39	-33	OC81	-14
EL32	-60	KTW82	1.76	PL608	1.10	U19	5.00	AC154	-33	BCY39	-33	OC81	-14
EL34	1.00	KTW63	1.17	PL609	1.66	U25	-70	AC156	-26	BF159	-33	OC81D	-14
EL35	3.00	MHLD6		PL59/2	-60	U26	-66	AC157	-33	BF165	-26	OC82	-14
EL37	3.00			PY81	-40	U33	1.75	AC166	-22	BF173	-49	OC82D	-14
EL41	-80	P61	6.0	PY82	-40	U35	1.75	AC166	-22	BF180	-39	OC83	-26
EL41	-70	PAB080	-45	PY83	-45	U81	-80	AC168	-49	BF181	-52	OC84	-81
EL43	-36	PC88	-70	PY88	-47	U191	-59	AC176	-71	BF185	-52	OC123	-29
EL86	-60	PC95	-70	PY900A	U251	-94	AC177	-36	BF194	-20	OC139	-29	
EL980	1.80	PC97	-55	PY900	1.11	U201	-65	AC177	-36	BF250	-29	OC159	-29
EL506	1.20	PC90	-47	PY800	-47	U403	-90	ACY18	-26	BFY61	-25	OC172	-43
EM30	-53	PC85	-50	PY801	-47	U404	-75	ACY19	-25	BFY52	-26	OC200	-59
EM34	-64	PC88	-65	PZ30	-50	U801	-80	ACY20	-23	BY102	-23	OC201	-59
EM38	-47	PC89	-65	QVQ08/10	U4020	-75	ACY21	-25	BY114	-33	OC202	-55	
EM45	1.20	PC189	-60	Q75/20	2.10	VP23	-65	ACY22	-23	BY126	-20	OC203	-39
EM87	1.10	PC190	-47	Q875/20	2.10	VP41	-88	ACY28	-23	BY127	-23	OC204	-39
EY61	5.0	PCF84	-70	Q895/10	1.00	UY15	-85	AD140	-47	BY210	-33	OC205	-55
EY81	5.0	PCF201	1.06	Q895/10	1.00	VU111	-80	AD149	-64	BYZ11	-33	OC206	1.17
EY83	-70	PCF201	1.06	TH233	1.00	W107	-75						

VALVES ALSO REQUIRED FOR CASH, LOOSE OR BOXED, BUT MUST BE NEW. OFFER MADE BY RETURN. PLEASE NOTE: EXPORT ORDERS—MINIMUM ACCEPTED +\$3.00
All goods are unused and subject to the standard 90 day guarantee. Cash or cheque with order only
Despatch charges:—Orders below £10 in value, add 25p for post and packing. Orders over £10 post and packing free of charge. Same day despatch. Any parcel insured against damage in transit for only 5p per parcel extra. Terms of business free on request. Many others in stock too numerous to mention. Please enclose S.A.E. for reply to any correspondence.

Mail Order Protection Scheme

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

NICKEL CADMIUM RECHARGEABLE CELLS

(1.25V PER CELL)
500M/AH—£1.43; 1.2AH—£1.92; 1.8AH—£2.50; 3.5AH—£3.12; 4AH—£5.50; 7AH—£5.93; 10AH—£8.66.
These cells can be supplied in sealed packs with or without built in mains charging unit at various voltages, i.e. 6V 4AH, 12V 7AH. S.A.E. for prices giving D.C. voltage and current required and if built in charger required.

TRANSFORMERS

240V A.C. Primary: Sec. 0-6V 1A—£2.00; Sec. 0-0-6V 1A—£2.06; Sec. 0-0-9V 1A—£2.33; Sec. 12-0-12V 1A—£2.32.

RELAYS

6V D.C.—£1.12; 12V D.C.—£1.38; 3V D.C.—£1.38.

INVERTORS

8W 6V, 8W 12V, 5 amp 12 way terminal strips, 28 way tag mounting strip, condensers, B.A. bolts, nuts, washers, solder tags. Resistors 3w carbon—20p doz; sw—4p each. Transistors, OP/AMP 741, Rectifier bridges, Zeners, Thyristors.


Prices include V.A.T. Post and Packing 30p for orders under £5. S.A.E. for lists to:—

Nixon's Electronics G3CLP, H.F.P. (CHESTERFIELD) LTD.,
536 Sheffield Road, Chesterfield, Derbyshire.

CLEARANCE BARGAINS

Special Offer metallised Polyester Capacitors by Erie, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed, 100 for £2.00.

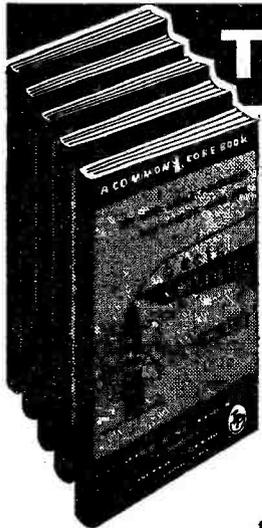Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene, tremendously good selection. 300 for £1-70



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR
100%
GUARANTEE**

Should you be, in any way dissatisfied with the **MANUALS** your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

- I didn't know this subject could be so easily presented. *J. K., Earlsfield*
Pleased to say how understandable your books are—I now have a sound knowledge of the subject. *A.K., Hull*
Invaluable for my training as a Technician. *W.J., Stockport*
They have an easy approach to learning that a mathematical idiot like myself can easily understand. *K.L.Y., Ashton-u-Lyme*
Thank you for the excellent publication; the best in form and type I have ever come across. *T.L.O., Shanklin*
I find the Basic Manuals the best in their class and a real help in my work in prototype electronics. *C.L.P., Cardiff*

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £8.00
BASIC ELECTRONICS 6 parts £9.50
BASIC TELEVISION 3 parts £5.00

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS
FULL POSTAL.....
ADDRESS

POST NOW FOR THIS OFFER!


SPARKRITE MK 2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

"Sparkrite MK 2" is a high performance, high quality, capacitive discharge, electronic ignition system. Sparkrite completely eliminates the problems of the contact breaker. Misfire due to contact breaker bounce is electronically eliminated, contact breaker burn is eliminated, the condition of the contacts is not relevant to the performance of the ignition, and the system is no longer dependent on the dwell period for recharging. Sparkrite will give you: Up to 20% better fuel consumption, instant all weather starting, cleaner plugs—they last up to five times longer without attention, faster acceleration, higher top speed, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance. The Kit comprises everything needed: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions. WE SAY IT IS THE BEST SYSTEM AT ANY PRICE

Voted best of 8 ignition systems tested by a leading Motoring Magazine

Press: D.I.Y. assembly kit £10.99 including VAT post and packing. Ready built unit £13.99 including VAT post and packing. (Both to fit all vehicles with coil/distributor ignition up to 8 cylinders.) Switch for instant changeover from "Sparkrite" ignition to conventional ignition £2.79 including VAT post and packing. R.P.M. limiting control £2.42 including VAT post and packing. (Fitted in case on ready built unit. Dashboard mounting on kit.) We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request. CALL IN AND SEE US FOR A DEMONSTRATION

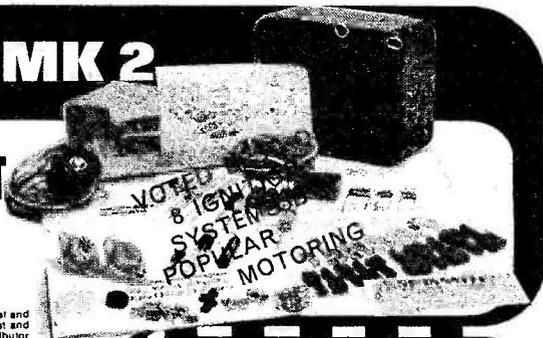

ORDER NOW

To Electronics Design Associates Dept.
92 Beth Street, Walsall, WS1 3DE, Phone 33652.
From Name
Address

Quantity Please Supply
Sparkrite Mk. 2 D.I.Y. Assembly kits at £10.99
Sparkrite Mk. 2 Ready Built Negative earth at £13.99
Sparkrite Mk. 2 Ready Built Positive earth at £13.99
Ignition changeover switches at £2.79
R.P.M. Limit systems in the above units at £2.42
Fluorescent light assembly kits at £3.46
Fluorescent light built units at £4.18
Diffusers for the above at 39p
of number aluminium boxes at
of number aluminium boxes at
of number aluminium boxes at

I enclose cheque/P.O. for £..... Cheque No.....
(Send S.A.E. if brochure only required).

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

Prices include lids, screws and VAT (at 8%). 18p should be added to the total order value for postage and packing.

No. 7	5 1/2"	by 2 1/2"	by 1 1/2"	high	47p
No. 8	4"	by 4"	by 1 1/2"	high	46p
No. 9	4"	by 2 1/2"	by 1 1/2"	high	46p
No. 10	5 1/2"	by 4"	by 1 1/2"	high	46p
No. 11	4"	by 2 1/2"	by 2"	high	46p
No. 12	3"	by 2"	by 1 1/2"	high	38p
No. 13	6"	by 4"	by 2"	high	58p
No. 14	7"	by 5"	by 2 1/2"	high	75p
No. 15	8"	by 6"	by 3"	high	83p
No. 16	10"	by 7"	by 3"	high	£1.14

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12V SW fluorescent light. Everything needed is supplied: white enamelled drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, and caps, cable, the fluorescent tube, nuts, bolts, washers and simple assembly and operating instructions. When complete the light has many uses: workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping, and boating, as an inspection lamp and many more. Prices: Assembly kit £3.46 inc. VAT post and packing. Ready built £4.18 inc. VAT post and packing. Diffuser 59p inc. VAT post and packing.

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER

STEREO AND MONO

Plays 15", 10" or 7" records
Auto or Manual. A high
quality unit backed by BSR
reliability with 12 months'
guarantee. AC 200/250v.
Size 13 1/2 x 11in.
Above motor board 8 1/2in.
Below motor board 2 1/2in.
With STEREO/MONO CARTRIDGE



£9.25 Post 45p.

PORTABLE PLAYER CABINET

Modern design. Size 16" x 15" x 7" resin
covered. Large front grille. Hinged lid. Chrome
fittings. Motor board out for Garrard deck.
Few only, in red and black.

£5.25 Post 45p.

SOLID MAHOGANY PLINTH


With P.V.C. Cover. Cut out for most
B.S.R. or Garrard decks.
Size 12 1/2 x 14 1/2 x 7 1/2 in.

£7.50 Post 45p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with
separate pick-up arm fitted
LP/78 turnover mono
compatible cartridge.

£5.25 Post 45p

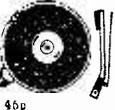


R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/comp. cartridge. Base-
plate. Size 11in x 8in. Turntable. Size 7in diameter. A/C
mains. 220/250V motor has a separate winding 14 volt to
power a small amplifier.
3 speeds plays all size
records.

£6.95 Post 45p

COMPLETE STEREO SYSTEM


Two full size loudspeakers 13 1/2 x 10 x 8in. Player
unit clips to loudspeakers making it extremely compact.
Overall size only 13 1/2 x 10 x 8in. 3 watts per
channel, plays all records 33
rpm 45 rpm.
Separate vol-
ume & tone
controls 240v
AC mains

Attractive
Teak finish
Weight 13lbs.

Bargain Price
£29
85p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES

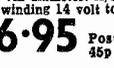Single pole two-way surface mounting
with fixing screws. Will replace existing
wall switch to give light for return home,
garage, automatic anti-burglar lights etc. Variable knob
Turn on or off at 10 or intermediate settings.
Fully insulated. Makers last list price £4.50. Brand new and
fully guaranteed. OUR PRICE **£2.50** Post 35p.



CASSETTE RECORDER MOTOR ONLY. 6 Volt.

Will replace many types. Ideal for models. £1.25.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in sides
6 x 4in 45p; 8 x 6in 55p; 10 x 7in 65p; 12 x 8in 85p;
14 x 9in 95p; 16 x 8in 95p; 12 x 3in 50p; 16 x 10in £1.

ALUMINIUM PANELS 18 s.w.g. 6 x 4in 12p; 8 x 6in 19p;
14 x 8in 29p; 10 x 7in 24p; 12 x 6in 25p; 12 x 8in 34p;
16 x 6in 34p; 14 x 8in 40p; 12 x 12in 47p; 16 x 10in 60p.

1 1/2inch DIAMETER WAVECHANGE SWITCHES 45p. EA.
3 p. 2-way, or 2 p. 6-way, or 3 p. 4-way.
1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way.

TOGGLE SWITCHES, sp. 20p; dp. 25p; dp. dt. 30p.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape P.U., Guitar, etc. Can be used with
Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size
1 1/2" x 1 1/2" x 1". Response 25 c.p.s. to 25 Kc/s, 28 db gain.
For use with valve or transistor equipment. **£1.45** Post
Full instructions supplied. Details S.A.E. 20p

NEW TUBULAR ELECTROLYTICS CAN TYPES

2/250V	14p	250/25V	14p	16+16+16/275v45p
4/350V	14p	500/25V	20p	50+50/300V
9/350V	18p	100+100/275v	65p	32+32/450V
16/350V	22p	150+200/275v	70p	100+50+50/350v95p
32/500V	30p	8+8/450V	25p	32+32+32/350
25/25V	10p	8+16/450V	25p	900MFD/350V
60/50V	10p	16+16/450V	40p	4700/63V
100/25V	10p	32+32/350V	95p	

LOW VOLTAGE ELECTROLYTICS.

22, 25, 50, 68, 150, 470, 500, 880, 1500, 2200, 3300, mfd
all 6 volt 10p. ea.
22, 25, 68, 100, 150, 200, 220, 330, 470, 680, 1000, 1500,
2200, mfd all 10 volt 10p ea.
220, 330, 1000, 4700, mfd all 4v. 10p ea.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
1000mF 12V 15p; 25V 20p; 50V 30p.
5000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
200mF 5V 25p; 250mF 5V 25p; 50V 47p; 4700/30V 95p.
2500mF 50V 82p; 3000mF 25V 47p; 50V 85p.
5000mF 6V 25p; 12V 42p 25V 75p; 35V 85p; 50V 95p.
500V-0-001 to 0-05 4p; 0-1 10p; 0-25 12p; 0-47 25p.
CERAMIC 1pF to 0-01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V-0-1 7p; 0-5 18p; 1mF or 2mF 150V 15p.
MICRO SWITCH single pole changeover 20p
MICRO SWITCH 2 pole 25p
TWIN GANG. "0-0" 205pF+176pF, £1.10.
Slow motion drive 365pF+865pF with 25pF+25pF, 50p;
500pF standard twin gang 75p. 120 FF twin gang 50p.

ELAC 9 x 5in. HI-FI SPEAKER. TYPE 69RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE 10 WATT. 8 OHM. CERAMIC MAGNET. £3.45

NEON PANEL INDICATORS. 250V AC/DC Amber. 30p

RESISTORS 1/2 w., 1 w., 20%, 1p; 2 w. 5p. 10 Ohm to 10M-
HIGH STABILITY. 1/2 w. 2% 10 ohms to 6 meg., 10p.
DITO 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-BOUND RESISTORS 1/2 w. 5p. 10 Ohm to 15 watt,
10 ohms to 100K. 10p each; 2w 0.5 ohm to 8.2 ohms 10p.
TAPE OSCILLATOR COIL. Valve type. 35p.
FERRITE ROD 8" x 1/2" 20p; 6" x 1/2" 20p; 3" x 1/2" 10p.

MAINS TRANSFORMERS ALL POST 40p each

250-0-250V 80MA. 6.3-3.2A £2.95.
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £4.60
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1a. or 5 v. 2 a. £5.30
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 6.3 v. 2 a. 27-00
MINIATURE 200 v. 20 mA., 6.3 v. 1 a. 2 1/2" x 2 1/2" x 2in. 95p
MIDGET 220 v. 45 mA., 6.3 v. 2 a. 2 1/2" x 2 1/2" x 2in. £1.20
WIRE-BOUND 250 v. 6.3 v. 3 amp. £1.45; 1 amp. 95p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs
at 2 amp., 3, 4, 5, 6, 9, 10, 12, 15, 18, 24 and 30 v. £4.60
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4.60
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £7.00
3 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8.70
5 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11.25
5, 8, 10, 16 v. ± A £2.6-0-6 v. 500 mA 90p. 9 v. 1 amp. 95p.
12 v. 300 mA 75p. 12 v. 500 mA 85p. 12 v. 750 mA 95p.
40 v. 2 amp. tapped 10 v. or 30 v. £2.50. 20V 3 amp. £2.
40V 3 a. £2.50. 220-0-220 4 a. 28
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v.
150w. £4.60; 500w. £8.70; 750w. £17.50; 1000w. £21.00.
CHARGER TRANSFORMERS. Input 200/250v.
for 6 or 12v., 1 amp. £1.50; 2 amp. £1.90; 4 amp. £3.
BATTERY CHARGERS. Ready built with leads and clips
4 amp. £4; 5 amp. £4.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS:
6 or 12v. outputs. 1 amp. 40p; 2 amp. 55p; 4 amp. 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240v. Secondary 0-240v. 3 amps. 720
watts. Insulated terminals. Varnish impregnated. Fully
enclosed in steel case with fixing feet.
Famous make. (Value £19) OUR PRICE **£13.50** Carr.
Suitable for outside use. 85p

R.C.S. 3 WAY CROSSOVER

Complete with 12 ft. twin lead fitted with din speaker plug.
Ready assembled with leads for speakers, bass, mid and
tweeter. Crossover frequencies—950 cps and **£2.20**
3,000 cps.

VOLUME CONTROLS 80 Ohm Coax 5p yd.

5 K. ohms to 2 Meg. LOG or
LIN. L/S 30p. D.P. 35p.
STEREO L/S 55p. D.P. 75p.
Edge 5K. S.F. Transistor 25p

BRITISH AERIALITE
AERAXIAL-AIR SPACED
40 yd. £2; 60 yd. £3.
FRINGE LOW LOSS 10p yd
Ideal 625 and colour. yd

Wirewound controls 1in. diam. 3 watts. 10 ohms to 100K
British made with long spindles 1in. dia 80p ea.

DUAL CONCENTRIC POT 500k LOG + 500k LIN D.P.
Inner spindle 3in; outer spindle 2 1/2in. 75p.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With tweeter. £5-25
And crossover. 10
watt. State 8 or 8
or 15 ohm. As illustrated. Post 85p

With flared tweeter cone and ceramic
magnet. 10 watt.
Bass res. 45-60 cps.
Flux 10,000 gauss.
State 3 or 8 or 15 ohm. Post 35p

Bookshelf Cabinet £6.60

Fluted wood front 16x10x7in. Teak Veneer Post 45p

GOODMANS 6 1/2 in. HI-FI SPEAKER £4.60

8 ohm, 10 watt. Large ceramic magnet
Special Rubber cone surround.
Frequency response 30-15,000
cps. Ideal T.A. Columns,
Hi-Fi Enclosure Systems, etc.
Suitable cabinet 12 x 8 x 6 £24.80.
Suitable Tweeter £2.30.



ELAC CONE TWEETER £2.25

The moving coil diaphragm gives a good
radiation pattern to the higher frequencies
and a smooth extension of total response
from 1,000 cps to 18,000 cps. Size 8 1/2
x 3 1/2 x 2in. deep. Rating 10 watt, 8 ohm.
Crossover £1.90
Post 20p



GOODMANS 8 in. WOOFER £4.35

8 ohm 12 watt. Deep cone.
Heavy ceramic magnet. Bass
resonance 35 cps. Frequency
response 30-8,000 cps.
Ideal bass unit for £4.35
Hi-Fi systems



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in. £1.25; 6in. £1.60; 8 x 5in. £1.60; 8in. £1.75; 10 x 6in. £1.90; 10in. £2.20.

SPECIAL OFFER. LOUDSPEAKERS! All Brand New.
8 ohm, 2 1/2in; 2 1/2in; 3in; 3in; 8 ohm, 2 1/2in; 3in; 3in;
5in. 15 ohm, 3in; 5in; 6 x 4in; 5in x 3in; 7 x 4in; 8 x 5in.
25 ohm, 2 1/2in; 3in; 5 x 3in; 5in. 35 ohm; 5in; 5in;
80 ohm, 2 1/2in; 2 1/2in. 120 ohm, 3in. **£1.25 EACH**

LOUDSPEAKER VOLUME CONTROL 15 ohm 10 watt with 1in long threaded bush for wood panel mounting 75p.

RICHARD ALLEN TWIN CONE LOUDSPEAKERS. 8in.
diameter. 4W £2.50, 10in. diameter 5W £2.95; Post 85p.
18in. diameter, 6W, £3.50; 3 or 8 or 15 ohm models.
SPEAKER COVERING MATERIALS. Samples Large S.A.E.
Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £2.60.
De Luxe Horn Tweeters 2-18 Kc/s, 15W, 8 ohm £4.00.
TWO-WAY 2000 c.p.s. CROSSOVERS 3 or 15 ohm £1.80.
3-WAY CROSSOVER 850 cps and 3000 cps (25 watt) £2.20.

GOODMANS CONE TWEETER £3.60

18,000 cps. 25 watts. 8 ohm. Price **£3.60**.

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5v d.c. operation over 250 hrs. continuous on SP2 battery.
Fully adjustable swing and speed. Ideal displays teaching
electro magnetism or for metronome: strobe etc. 95p. Post 20p

R.C.S. VALVE AMPLIFIER

2 Stage Triode Pentode valve. 3 watts 3 ohm output. Volume
on/off and tone controls AC mains. Complete and tested.
With Loudspeaker. **£4.50** Post 35p.

WEYRAD COILS

P60/LAC-60p.	RA2W 85p.	Twin Gang £1.10.
P60/CC-40p.	OPTI 65p.	Printed Circuit 85p.
P60/CC-40p.	LFD4. 65p.	

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p
OUTLET BOXES, SURFACE MOUNTING 25p.
BALANCED TWIN RIBBON FEEDER 300 ohms, 7p yd.
JACK SOCKET Std. open-circuit 15p, closed circuit 25p;
Chrome Lead Socket 45p. Phone Plugs 10p. Phone Socket 5p
JACK PLUGS Std. Chrome 20p; 3-6mm Chrome 15p. DIN
SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS
Lead 3-pin 15p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p.
VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

FM/VHF AERIAL FEEDER CABLE

300 ohm suitable for stereo 7p per yard.

BRITISH FM/VHF TUNING HEAT

88 to 108 Mc/s British made. 2 Transistors
ready aligned—requires 10.7
Mc/s I.F. Complete with tuning caps.
Connections supplied but some
technical experience required.
SUITABLE I.F. STRIP £4.95.
Our Price **£3.95**
Post 20p.

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 30p. CALLERS WELCOME

RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p. Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

£6-75 THE PAIR. Post 45p.
(Available separately.
Woofer 24-25; Tweeter
Post 45p 41-90).
Comprising a fine example of a Woofer
10 1/2 x 6 1/2 in. with a massive Ceramic
Magnet. 44oz. Gauss 13,000 lines.
Aluminium Cone centre to improve
middle and top response. Also the E.M.I.
Tweeter 8 1/2 in. square has a special
lightweight paper cone and magnet flux
10,000 lines. Crossover condenser and
full instructions supplied.
Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 25 to 13,000 cps
Bass Resonance 45 cps



£14-50
Post 75p

SUITABLE ENCLOSURE 20 x 13 x 12 in.
MODERN DESIGN. TEAK WOOD FINISH.

ELAC 8in. or 10 x 6in. HI-FI SPEAKER



Dual cone plasticised roll sur-
round. Large ceramic magnet.
50-16,000 cps. Bass resonance
55 cps. 8 ohm impedance.
8in. 10 watts **£4-35**

TEAK VENEER HI-FI SPEAKER CABINETS Fluted Wood Fronts

MODEL "A". 20 x 13 x 12 in.
For 12in. dia. **£14-50** Post
10in. speaker. 75p



MODEL "B". 16 x 10 x 7 in.
For 8 x 8 in. or **£7-60** Post
8in. speaker. 45p

LOUDSPEAKER CABINET
WADDING 18in. wide, 20p ft.

BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft.
HI-FI CABINET **£21-50**. Carr. 22 each. Few only.
Size 30 x 20 x 12 in. Teak Finished Fluted Front.

TEAKWOOD LOUDSPEAKER FRONT GRILLS
Modernise your cabinets with the Grooved look. Sizes—
18 1/2" x 10 1/2"—75p. 10 1/2" x 7 1/2"—45p.

BARGAIN 4 CHANNEL
TRANSISTOR MONO
MIXER. Add musical
highlights and sound effects
to recordings. Will mix
Microphone, records, tape
and tuner with separate
controls into single output.
9 volt battery
operated. **£5-20**



STEREO VERSION OF ABOVE **£6-85**.

R.C.S. STEREO FM TUNER BRITISH MADE



This completely cased mains powered Hi-Fi
Tuner with brushed aluminium fascia is British
made using the latest circuitry. Bargain **£30**
Post 45p.

BARGAIN 8 WATT AMPLIFIER. 4 Transistor
Full-Full Range but volume, treble and
bass controls. 15 volt battery operated. **£4-50**

WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and
drying applications in the home, garage, greenhouse,
factory (available in manufacturing quantities). Approx.
size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V. a.c.
850 watts approx. Printed circuit element enclosed in
asbestos fitted with connecting wires. Completely flexible
providing safe Black heat. British-made for use in photo-
copiers and print drying equipment.
Ideal for home handmen and experimenters. Suitable
for Heating Pads, Food Warmers, Convector Heaters, etc.
Must be clamped between two sheets of metal or asbestos,
etc., to make efficient clothes dryers, towel rails—ideal for
airing cupboards. Ideal for anti-frost device for the garage
—prevents frozen radiators or acting as oil sump heater.
Use in the greenhouse for seed raising and plant protection.
Invaluable aid for bird houses, incubators, etc., etc. Can
be used in series for lower heat. Or in parallel for higher
heat applications.

ONLY 40p EACH (FOUR FOR £1-50)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £11-50



Post 40p
30-14,500 c/s. 12in. double
cone, woofer and tweeter cone
together with a BAKER
ceramic magnet assembly
having a flux density of
14,000 gauss and a total flux
of 145,000 Maxwells. Bass
resonance 40 c/s Rated 20
watts. NOTE: 3 or 8 or
15 ohms must be stated.

Module kit, 30-17,000 c/s
with tweeter, crossover, baffle
and instructions. **£14-50**

Please state 3 or 8 or 15 ohms. Post 45p

"BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to
long periods of electronic power.
As used by leading groups and discos

Useful response 30-13,000 cps.
Bass Resonance 55 cps.

GROUP "25" **£8-95**
12in. 25 watt
3, 8 or 15 ohms.

GROUP "35" **£10-50**
12in. 35 watt
3, 8 or 15 ohms.

GROUP "50" **£19-50**
15in. 50 watt
8 or 15 ohms.

GROUP 50/12in. **£14-50**
50 watt 8 or 15 ohms

Post 50p
Group + PA Cabinets in stock
Send for Leaflet.

MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised.
Ideal for Groups, Disco and P.A.
4 inputs speech and music. 4 way
mixing. Output 8/15 ohm. a.c. Mains.
Separate treble and bass controls.
Guaranteed. Details SAE.
De Luxe Model in wood case **£69**.



£59 Carr.
£1-00

NEW MODEL—MAJOR 50 WATT £49-95

4 inputs 2-way mixing. 2 outputs separate treble
and bass controls. Ideal disco or P.A. amp.

DE LUXE 100 WATT VALVE AMPLIFIER CHASSIS

4 input 10 wide range controls. For Mixers, Discos, Organs
Guitars, etc. 4, 8 & 15 ohm loudspeakers matching **£82-00**.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of
tape reels. A.C. mains 200/250V.
Leaflet S.A.E. **£4-35** Post
80p



QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 1 1/2 thick wood cabinet. Size
18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23lbs. This
cabinet features a wide mesh Silver Grill
covering a separate compartment for mount-
ing Tweeters or Mid-Range Horn. The fully
sealed bass compartment is cut out for
8 1/2 inch Woofer. **£8-50** Carr. 85p.
Rosewood Version **£9-50** Carr. 85p.
Baffle could be cut to take larger speaker.



SPECIAL OFFERS

100 Ohm 20 watt Rheostat 2 1/2 in diam. Ceramic Former.
Screw Terminals 3 in. diam. spindle. **95p**. Post 25p.
AC mains relay 3 pole change over **75p**.

E.M.I. GRAM MOTOR

120v. or 240v. A.C. 2,400 rpm. 2-pole
70mA. Size 2 1/2 x 2 1/2 in.

£1-25
Post 30p.

E.M.I. TAPE MOTOR

4 pole, 240 v. 135 mA. Size 3 1/2 x 2 1/2 x 2 1/2 in.
1200 rpm. Spindle 1/4 in diameter.
120v version **£1**.

£2-00
Post 80p

BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

REGENT

12in. 15 watts

An inexpensive unit for the
beginner in high fidelity and
for general purposes. May be
used to improve any Radio,
Amplifier, Hi-Fi or Television
receiver.
Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models.

£9-50 Post
40p

DE-LUXE Mk II

12in 15 watts

Especially designed to provide
full range reproduction at an
economical cost. Suitable for
use with any high fidelity
system. Built-in concentric
tweeter cone.
Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£12-50 Post
40p

SUPERB

12in. 20 watts

A high quality loudspeaker,
its remarkable low cone
resonance ensures clear
reproduction of the deepest
bass. Fitted with a special
copper drive and concentric
tweeter cone resulting in full
range reproduction with
remarkable efficiency in the
upper register.
Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£17-00 Post
50p

AUDITORIUM

12in. 25 watts

A full range reproducer for
high power, Electric Guitars,
public address, multi-speaker
systems, electric organs.
Ideal for Hi-Fi and Dis-
cotheques.
Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£14-50 Post
50p

AUDITORIUM

15in. 35 watts

A high wattage loudspeaker
of exceptional quality with a
level response to above
8,000 cps. Ideal for Public
Address, Discotheques, Elec-
tronic instruments and the
home Hi-Fi.
Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£19-50 Post
80p

Hi-Fi Enclosure Manual containing plans, designs, cross-
over data and cubic tables. 60p. Post 3p.

CUSTOMERS FREE CAR PARK

OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-2-30

SPECIALISTS 337 WHITEHORSE ROAD . CROYDON

(Exports Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

SINCLAIR
IC20
AMPLIFIERS
SEND SAE FOR FREE DATA BOOKLET

IC20 10+10W stereo amp. kit with free booklet and printed circuit £8.58
PZ20 power supply kit for above £5.91
VP20 volume, tone control and preamp kit £6.56

SINCLAIR CALCULATORS

This month's snip. Get the Sinclair Cambridge Memory Calculator at the same price as the normal Cambridge. Only £11.20**

CALCULATORS

Cambridge £11.20
Cam. Memory £11.20
Scientific £14.10
Oxford 100 £10.37
Oxford 200 £15.90
Oxford 300 £22.98

MAINS UNITS

For Oxford Series £3.69
For Cambridge, Cam. Mem. and Scientific £3.95

FERRANTI ZN414

IC radio chip with data £1.69. Also available kit of extra parts to complete a radio £3.38. Send sae for free leaflet.

SINCLAIR PROJECT 80

AFU £8.31 FM Tuner £14.91
Z40 £6.55 Stereo decoder for above £9.69
Z50 £8.31 Transformer for PZ8 £5.16
Q16 £8.87 Stereo 80 £14.91
PZ5 £6.21 Project 805 £38.22
PZ6 £9.69 Project 805SQ £46.65
PZ8 £9.45 Project 80 Quadrasonic decoder £20.97

BATTERY ELIMINATOR BARGAINS

6-WAY SPECIAL

The most versatile battery eliminator ever offered. Switched output of 3, 4½, 6, 7½, 9 and 12V at 500 mA £5.45.

3-WAY MODEL

Switched outputs of 6, 7½ and 9V at 250mA with unique 4 way multi jack plug and socket output connector £3.55.

RADIO MODELS

50mA output with poppet battery connectors for transistor radios etc. 6V £3.86, 9V £3.86, Double 4½+4½V £4.43, 6+6V £4.43, 9+9V £4.43.

TAPE RECORDER MAINS UNITS

7½V output complete with 5 pin DIN plug to run cassette tape recorders from the AC mains £4.61.

HEAVY DUTY MODELS

500mA, British made to very high standards. Our best buy suggestion. 6V £4.90, 7½V £4.90, 9V £4.90.

SINCLAIR IC12

6W IC power amp and preamp with 44 page booklet and printed circuit £4.10

SWANLEY IC TOMORROW

Similar to above, 10W into 15 ohms, but no printed circuit £2.12.

SEND SAE FOR FREE LEAFLET ON BOTH

S-DECS AND T-DECS

S-DeC £2.34
T-DeC N/A
1/2-DeC A-N/A
1/2-DeC B-N/A
IC carriers:—
16 diff: plain N/A
With socket £2.21
10 TO5: plain £1.09. With socket £2.08

SWANLEY ELECTRONICS
PO BOX 68, SWANLEY,
KENT BR8 8TQ.

Prices include post and VAT.
Official credit orders from schools etc welcome.
No VAT charged on overseas orders.
All prices are special offers.

ALL FREE
6p/sq in
PCB's
Brochure on New KITS
Whether professional, student, teacher or amateur, the field of electronics has opened up a new world for you

CROFTON don't just sell kits, we offer you a technical back up service to ensure your success
The following is a selection of some of the more popular kits

- ★ Mullard CCTV Camera
- ★ PE. CCTV Camera
- ★ PE Rondo Quadrasonic Four Channel Sound (Designer Approved)
- ★ Electronic Ignition
- ★ Electronic Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE: PCB's for most published projects available to order

CROFTON ELECTRONICS LTD
Dept B 124 Colne Road, Twickenham, Middx O1 898 1569

H.A.C. SHORT-WAVE KITS
WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1975 "DX" RECEIVER
Complete kit—Price £5.50 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valve."
This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.
Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX NO. 16, EAST GRINSTEAD,
SUSSEX RH19 3SN

Everest Instruments Ltd.
34, Shakespeare St., Nottingham.
Tel. (0602) 45466

All prices quoted include p. & p., & VAT, min. order £1. CWO only.

Transformers

All 240v 50hz primaries	10 x 6 EMI	7.38
	8 ohm 20 watt	
	13 x 8 EMI	6.75
	8 ohm 20 watt	
	13 x 8 EMI	7.84
	8 ohm 25 watt	

Semiconductors

Diodes		
IN4001	6p	
IN4002	7½p	
IN4003	8½p	
IN4004	9½p	
IN4006	12p	
IN4007	13p	
OA70	8p	
OA81	7½p	
OA90	6p	
OA91	6p	
OA202	7½p	
BA154	8½p	
BA156	13p	
IN914	4p	
400mw zeners		
3v to 33v		10p
Silicone bridge rectifiers		
2a 50v rms		46p
2a 100v rms		47p
Thyristors		
1a 100v piv		30p
1a 400v piv		45p
3a 400v piv		57p
P.C. Board		
Single sided fibre glass	9.70 sq ft	
Double sided fibre glass	1.00 sq ft	
Cut in multiples of 6"		
i.e. 6 x 6, 6 x 12, 12 x 12, 12 x 18, etc.		
Circuit etchant 250ml	0.55	
1 lb ferric chloride	0.50	
250ml plastic bottles	0.16	
Speakers	£ p	
3" Goodman tweeter		
8 ohm 51 CD4	1.47	
3" Audax tweeter		
8 ohm 15 watt	1.60	
5" Audax bass		
8 ohm 10 watt	3.23	
6½" Audax 8 ohm 15 watt	2.95	
8 ohm 10 watt	3.59	
8 x 5 EMI d/cone 8 ohm 10 watt	3.67	
8" Celestion d/cone 8 ohm 10 watt	2.78	
7 segment led numeral display		
16p D.I.L.		115p
D.I.L. sockets		
8 pin		15p
14 pin		15p
16 pin		16p
Electrolytics. Tubular with axial leads except where stated.		
Mfd.	Volts	Pence
47	4	7
330	4	7
68	6.3	7
470	6.3	9
1000	6	11
25	10	7
47	10	7
220	10	7
330	10	9
15	16	7
33	16	7
68	16	7
220	16	9
220	16	9
16	20	11
1000	16	20
10	25	7
22	25	7
47	25	7
100	25	7
150	25	9
200	25	11
1250	25	24
5000	25	55
10000	25	32
2500	30	40
40	6.8	7
16	40	7
100	40	9
1000	50	35
1	63	7
4.7	63	7
10	63	7
32	63	7
800	63	32
2500	63	80
4700	63	140



GIRO NO. 331 7056. Access accepted.
C.W.O. only. P. & P. 15p on orders below £5
Discount: £10-10% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

PLEASE ADD AN EXTRA 15% VAT EXCEPT ON TEST METERS, AND VEROBOARD SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 ½W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
25E12 ½W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3½p. 0.068µF, 0.1µF, 4½p. 0.15µF, 5p. 0.22µF, 6p. 0.33µF, 8p. 0.47µF, 10p. 0.68µF, 13p. 1µF, 16p. 1.5µF, 24p. 2.2µF, 27p.

MULLARD POLYESTER CAPACITORS C295 SERIES
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 3p. 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3½p. 0.047µF, 0.068µF, 0.1µF, 4½p. 0.15µF, 7p. 0.22µF, 9p. 0.33µF, 13p. 0.47µF, 15p.
160V: 0.01µF, 0.15µF, 0.022µF 3½p. 0.047µF, 0.068µF, 4p. 0.1µF, 4½p. 0.15µF, 5½p. 0.22µF, 6p. 0.33µF, 7p. 0.47µF, 9p. 0.68µF, 13p. 1µF, 15p.

MINIATURE CERAMIC CAPACITORS
50V: (GF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8. (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2½p. each. 0.1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%
(GF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 4½p.

RESISTORS
CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%
W—Type Range 1—99 100—499 500—999 1000+ Size mm

CF 22-1M	1	0.80	0.65	0.60	2.4x7.5
CF 22-2M2	1	0.80	0.65	0.60	3.9x10.5
CF 22-1M	1	0.80	0.65	0.60	5.5x16
MF 10-2M7	2	1.7	1.4	1.2	3x7
MF 10-2M2	2	1.6	1.3	1.1	4.2x10.8
MF 10-10M	3	1.98	1.81	1.65	6.6x13
MF 10-10M	4	3.52	3.08	2.75	8.6x15

(Price in pence each).

VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0.25W Vertical or horizontal 7p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 7p each.



B. H. COMPONENT FACTORS LTD.

(P.W.) LEIGHTON ELECTRONICS CENTRE,
59 NORTH ST., LEIGHTON BUZZARD, BEDS.
Tel.: LEIGHTON BUZZARD 2316 (STD. Code 05253)
CATALOGUE No. 4

Miniature Mullard Electrolytics

1.0µF 63V	7p	100µF 25V	7p
1.5µF 63V	7p	150µF 16V	17p
2.2µF 63V	7p	150µF 63V	17p
3.3µF 63V	7p	150µF 63V	17p
4.0µF 40V	7p	220µF 6-4V	7p
4.7µF 63V	7p	220µF 10V	7p
6.8µF 63V	7p	220µF 16V	8p
10µF 25V	7p	220µF 63V	25p
10µF 63V	7p	330µF 16V	14p
15µF 16V	7p	330µF 63V	28p
15µF 63V	7p	470µF 6-4	8p
16µF 40V	7p	470µF 40V	25p
22µF 25V	7p	680µF 16V	17p
22µF 63V	7p	680µF 40V	28p
32µF 10V	7p	680µF 16V	25p
33µF 63V	7p	1000µF 25V	28p
33µF 40V	7p	1500µF 6-4V	17p
47µF 10V	7p	1500µF 16V	28p
47µF 25V	7p	2200µF 10V	28p
47µF 63V	8p	3300µF 6-4V	28p
68µF 16V	7p		
68µF 63V	14p		
100µF 10V	7p		

VEROBOARD 0.1 0.15

2½ x 5"	36p	36p
2½ x 3½"	33p	25p
3½ x 5"	42p	46p
3½ x 3½"	36p	36p
2½ x 5" (Plain)	10p	9p
2½ x 3½" (Plain)	19p	19p
5 x 3½" (Plain)	29p	29p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 50	22p	22p

TRANSISTORS

AC127	21p	BC212L	13p
AC128	22p	BC213L	13p
BC107	12p	BC214L	18p
BC108	12p	OC44	19p
BC109	13p	OC71	13p
BC148	13p	OC81	17p
BC149	13p	OC170	22p
BC182L	13p	2N2926	13p
BC183L	13p	2N3702	14p
BC184L	14p		

POTENTIOMETERS
Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17½p Dual Gang 48p. Log single with switch 28p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001 6½p	DIN 2 Pin	12p
IN4002 7½p	3 Pin	13p
IN4003 9p	5 Pin 180°	16p
IN4004 9p	Std. Jack	20p
IN4005 12p	2.5mm jack	13p
IN4006 14p	Phone	7p

PLUGS

IN514 7p	DIN 2 Pin	10p
IN516 7p	3 Pin	10p
BA100 10p	5 Pin 180°	12p
OA5 42p	Std. Jack	18p
OA47 9p	2.5mm jack	13p
OA200 8p	Phone	7p

SOCKETS

ELECTROLYTIC CAPACITORS. Tubular & Large Can (µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p. 50/50, 8p. 100/50, 200/25, 10p. 250/50, 10p. 500/10, 8p. 500/25, 17p. 500/50, 25p. 1000/10, 17p. 1000/25, 25p. 1000/50, 40p. 2000/10, 20p. 1000/100, £1.10. 2000/25, 35p. 2000/100, £1.20. 2500/25, 38p. 2500/50, 68p. 5000/25, 69p. 5000/50, £1.20.

Hi-VOLT: 4/350, 20p. 8/350, 23p. 100/100 27p. 16/350, 35p. 100/100, 27p. 00.250, 40p.

METALLISED PAPER CAPACITORS
250V: 0.05µF, 0.1µF, 6p. 0.25, 6p. 0.5µF, 7½p. 1µF, 9p. 500V: 0.025, 0.05, 6p. 0.1, 6p. 0.25, 7½p. 0.5, 9p. 1000V: 0.01, 12p. 0.022, 13p. 0.047, 0.1, 19p. 0.22, 28p. 0.47, 36p.

PLEASE NOTE OUR NEW ADDRESS
Our new Electronics Centre is now open in Leighton Buzzard and all callers are welcome. As well as our normal stock of over 2000 product lines, we have a large range of surplus equipment, Bargains, Calculators, etc. **OPEN 6 DAYS 9 to 5** (shut 12.30 to 1.30).

NEW KIT
5E12 ½W Metal Film, 5 each value 10Ω-1M, total of 305 £3.75 net.

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator 20,000Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—5Ω—1MΩ in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465 KHz (A.M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8.64 net p & p 50p.

MULTIMETER U4341
27 Ranges plus Transistor Tester, 16,700Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 6 ranges.
Idc—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2KΩ—2MΩ in 4 ranges.
Accuracy—dc—2½%, ac—4% of F.S.D.
Hf—10—350 in 4 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.88 net p & p 50p.

MULTIMETER U4324
34 Ranges. High sensitivity. 20,000Ω/Volt. Overload protected.
Vdc—0.6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25Ω—5MΩ in 5 ranges.
Accuracy—dc and R—2½% of F.S.D. ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £10.64 net p & p 50p.

MULTIMETER U4313
33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy. mVdc—75mV
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—0.6—1500mA in 6 ranges.
Iac—0.6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1½%, ac—2½%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net p & p 50p.



HAVE YOU GOT YOURS
CATALOGUE NO. 4
NEW CONVENIENT SIZE, AND FULLY ILLUSTRATED.
CONTAINS MANY HARD TO GET ITEMS

PAYS FOR ITSELF WITH DISCOUNT VOUCHERS WORTH 20p

- ★ DISCOUNTS
- ★ ALL NEW STOCK
- ★ SATISFACTION GUARANTEE
- ★ DEPENDABLE SERVICE

SEND NOW!
YOUR SINGLE SOURCE FOR THE EASY-BUILD ORGAN

We are the only manufacturers supplying the easy-build organ complete. Full after sales advice given.

Studio Electronics LTD

PO BOX 18 HARLOW CM18 6SH ESSEX
Tel: HARLOW (STD 0279) 416771
New catalogue now available on receipt of S.A.E.


it is new! it's News!

Pocket size medium wave signal generator. Can align, trim and tune I.F.'s and M.W. bands. Variable frequency. Can also be used as SIGNAL INJECTOR. Price £ 3.50 by post parcel. Send bank draft with order.

Pen sized, fully transistorised handy signal injector. Covers 1000 Hz. with harmonics upto 30 MHz. Helps trouble-shoot any tube or transistor audio, I.F. and R.F. circuitry. Price £ 3.00


WHOLESALE ENQUIRIES WELCOME
CENTRAL IMPORTS & EXPORTS
68, MOUNT PLEASANT, WEMBLEY MOOX (U.K.)

SUPERSOUND 13 HI-FI MONO AMPLIFIER

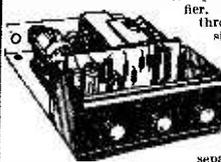

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz \pm 3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, excite/cheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE \pounds 15.00. P. & P. 65p.

DE LUXE STEREO AMPLIFIER

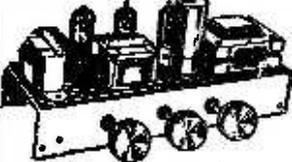

A.C. mains 200/240 v. V or 110 v heavy duty fully insulated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x E280 5v rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts into 8 ohm speakers). Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Supplied built & tested to a high standard. \pounds 18.50. P.&P. 80p.

Valve line up: 2 x ECL86 Triode Pentodes, 1 x E280 5v rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts into 8 ohm speakers). Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Supplied built & tested to a high standard. \pounds 18.50. P.&P. 80p.

ALL-PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v, and 8v, and 12v, at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested. PRICE \pounds 6.35 P. & P. 55p.

YNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 04 in. wide. Our price \pounds 1.30 yd. length. P. & P. 30p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully insulated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. PRICE \pounds 5.00 P. & P. 60p BARGAIN PRICE

FEW ONLY! High grade mains transformer with grain orientated lamination. Primary 200/240 Secondary 15.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2 1/2" x 2 1/2" x 2" d overall. \pounds 1.40 plus 30p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price \pounds 2.75 P. & P. 60p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240V. Sec. 9-0-9 at 500 mA. \pounds 1.35. P. & P. 30p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. \pounds 1.50. P. & P. 30p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. \pounds 2.20. P. & P. 40p.

3 VOLT RELAY 100 mA single pole normally closed. 2 for \pounds 1.50 P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-15v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price \pounds 1.35p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 7p.

Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents, \pounds 1.00; Transistor Equivalents, \pounds 1.20; Transistor Characteristics, \pounds 1.40; POST FREE All three together, \pounds 3.20

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias \pounds 1.70. Post Free 8 pole 3 way 2 bank low loss Yaxley type switches 1 1/2" sections. Standard spindle. 2 switches 75p + 15p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday.

All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). PRICE \pounds 27.50 Post and Packing \pounds 1.00.

STEREO-DECODER SIZE 9" x 3 1/2" ready built. Pre-aligned and tested. Sens. 20-600 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. \pounds 6.25 plus 15p. P. & P. Stereo beacon light if required 45p extra.



SPECIAL BARGAIN OFFER! Limited number of BSR C129/123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY \pounds 11.00 + p. & p. 60p.

LATEST Hi Sensitivity Uni-directional slim-line condenser microphone as used by many professionals. Very low acoustic feedback. Available hi impedance or low impedance. State which required. \pounds 18.25 plus 25p P. & P.

LATEST ACOS GPN118C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. \pounds 1.75. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal Mounting brackets and turnover stylus. 70mV per channel output. ONLY \pounds 2.06 + p. & p. 15p.

SONOTONE STARC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY \pounds 2.02 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. \pounds 3.18. P. & P. 16p.

LATEST CRYSTAL T/O STEREO COMPATIBLE CARTRIDGE for LP/EP/Stereo/78. \pounds 1.98 P. & P. 15p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. ONLY \pounds 1.75. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE \pounds 26.50. P. & P. 75p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE \pounds 27.75. P. & P. 75p.

HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which). **OUR PRICE \pounds 11.25** each Carr. \pounds 1.25. Cabinet Available Separately \pounds 8.25, Carr. \pounds 1.10. Also available in 8 Ohms with EMT 13" x 8" bass speaker with parasitic tweeter \pounds 10.00, Carr. \pounds 1.25.

LOUDSPEAKER BARGAINS


5in. 3 ohm \pounds 1.45. P. & P. 15p. 7 x 4in. 3 ohm \pounds 1.69. P. & P. 25p. 10 x 6in. 3 or 15 ohm \pounds 2.50. P. & P. 35p. E.M.I. 8 x 5in. 3 ohm with high flux magnet \pounds 2.06. P. & P. 25p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm \pounds 4.12. P. & P. 35p. E.M.I. 13 x 5in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network \pounds 5.50. P. & P. 35p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 16 ohms, \pounds 2.00 + 25p. P. & P.

BRAND NEW Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly \pounds 9.50. Guitar models: 30w \pounds 8.95, 35w \pounds 10.50, P. & P. 75p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKERS Size 12 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only \pounds 7.68 each. P. & P. 50p.

NOW ALSO AVAILABLE: 8", 10 watts, r.m.s. 20 watt peak 40Hz-20,000Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cars. \pounds 5.18 + 40p P. and P.

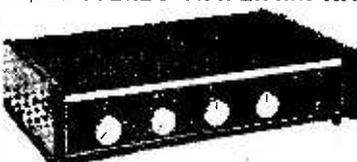HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 55v. at 1.0 amp. Overall size 12" w x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or sent 25p plus large S.A.E.

AMPLIFIER KIT \pounds 15.00 P. & P. 50p (Magnetic input components 33p extra)

POWER PACK KIT \pounds 5.25 P. & P. 55p
CABINET \pounds 5.25 P. & P. 55p (Post Free if all units purchased at same time)

Full after sales service
Also available ready built and tested \pounds 32.50. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc. and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only \pounds 7.75. P. & P. 70p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. \pounds 5.50 P. & P. 70p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided, giving good lift and cut. Valve line-up: 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + SAE (Free with parts) All parts sold separately, ONLY \pounds 12.00 (P. & P. \pounds 1.00). Also available ready built and tested \pounds 18.50 P. & P. \pounds 1.00.

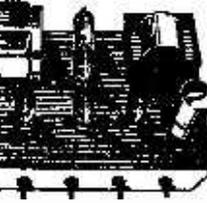

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo $\frac{1}{4}$ inch jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE \pounds 4.05. P. & P. 25p.

Prices include VAT at Current Rate

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station.
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

YOU DESERVE A BIGGER SALARY

"I earn more thanks to ICS"

Thousands of people have said it. Now it's your turn. ICS point the way to the better future you know you deserve.

Personal Tuition

Whether you need a basic grounding or tuition to complete your technical qualifications, ICS offer expert guidance from fully qualified tutors. You take the road to a better life at your own pace, in your own home, with the backing of the world's most experienced home study school.

Guaranteed success

ICS offer all examination students guaranteed tuition until successful. Plus expert advice on exam techniques. Make sure of your future with ICS. Choose the right course now.

City and Guilds Certificate

Make sure you get your Certificate with ICS:

Telecommunications Technicians
Radio TV and Electronics Technicians
Electrical Installations Technicians
Electrical Installation Work

Radio Amateurs

Also MPT Radio Communications Certificate

Technical Training

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:

Electronic Engineering & Maintenance
Computer Engineering & Programming
Radio TV & Audio Engineering & Servicing
Electrical Engineering, Installations & Contracting
Self Build Practical Radio Kits

Colour TV Servicing

Technicians trained in TV servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

QUALIFY FOR A NEW CAREER

Home study courses also available for leading professional examinations and diploma courses for over 200 business and technical subjects including:

Accountancy	Engineering	Motor
Administration	Farming	Personnel
Advertising	Heating	Purchasing
Air Conditioning	Management	Sales
Building	Marketing	Storekeeping
Catering	Mechanical	Work Study

G.C.E. 60 subjects at 'O' and 'A' levels.

POST OR PHONE TODAY FOR FREE BOOKLET

I am interested in

Name

Address

ICS

To: International Correspondence Schools,
Dept. S30, Intertext House, LONDON SW8 4UJ
or telephone: 01-622 9911 (all hours)

Accredited by CACC.

- ★ ELECTRONIC PIANO KIT
- ★ SYNTHESISER KIT
- ★ ELECTRONIC ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard. £145-29. ★ Console organ with 5 octave keyboard. £250-93. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board. £470-65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board. £680. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board. £960. ★ W/W Sound Synthesiser Kit. £149. ★ W/W Touch Sensitive Electronic Piano. £110.

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc. Lesley type speaker units from £50. Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

Elvins Electronic Musical Instruments

12 Brett Road, Hackney, London E8 1JP (Tel. 01-986 8455);
8 Putney Bridge Road, London SW18 1HU (Tel. 01-870 4949);
40a/42a Dalston Lane, Dalston Junction, London E8 (Tel 01-249 5624).

Business hours: Open 10 a.m. to 7 p.m. Monday to Saturday. Closed all day Thursday. Open 10 a.m. to 1 p.m. Sunday.

J. BIRKETT Radio Component Suppliers

25 The Strait, Lincoln, LN2 1JF

Telephone: 20767

5 WATT ZENER DIODES 3.5, 4.25, 9, 11, 12, 15, 18, 20, 22, 24, 30 Volts. All at 30p each.

TAPE RECORDER MECHANICAL COUNTERS @ 20p.

MINIATURE TUNING CAPACITORS. With Slow Motion

Drive. 250 + 250pf @ 38p, 500 + 500 + 17 + 17pf @ 38p.

12 SUB-MINIATURE PRE-SET POTENTIOMETERS 3 x 300

ohm, 3 x 2.5K, 3 x 5K, 3 x 47K for 35p.

1 WATT I.C. AUDIO AMPLIFIER Type TAA 611B with circuits

@ 70p.

60 ASSORTED WIRE WOUND RESISTORS 1 to 10 Watt @ 57p.

200 TUBULAR CERAMICS Assorted @ 57p.

50 IN 4000 SERIES Manufacturers Fall Outs @ 57p.

50 ASSORTED RADIO and TV KNOBS for 75p.

50 AC 128 TRANSISTORS Untested @ 57p.

200 ASSORTED TUBULAR CERAMIC CAPACITORS @ 57p.

20 P CHANNEL MOS FET's with circuits @ 75p.

100 ASSORTED SILVER MICA CAPACITORS @ 57p.

SILICON PHOTO TRANSISTORS 33p, PHOTO DARLINGTON TRANSISTORS @ 45p.

25 METAL TO 18 TRANSISTORS like BC 107-8-9 Untested @ 57p.

COMPRESSION TRIMMERS 10pf, 30pf, 50pf, 1000pf. All at 6p each.

LARGE PACKET OF MICA WASHERS for TO 3, TIP Series,

BD Series, Bushes, ecc. @ 33p.

200 POLYSTYRENE CAPACITORS Assorted @ 57p.

10 MINIATURE 10 Amp SILICON BRIDGES Untested for £1.25.

75 MULLARD C280 CAPACITORS Assorted for 80p.

5 WATT AUDIO I.C. Type SN 76013ND with data @ £1.

MULLARD LOCKFIT TRANSISTORS BC 147, BC 148, BC 149,

BC 157, BC 158, BC 159, BF 194, BF 195, BF 196, BF 197. All at 6 for 57p

50 ASSORTED POTENTIOMETERS for £1.

BF 180 or BF 181 TRANSISTORS 5 for £1.

18 VOLT 1 amp MAINS TRANSFORMER 240 Volt Prim. @ 85p.

200 ASSORTED DISC CERAMIC CAPACITORS @ 57p.

BF 224 RF AMPLIFIER TRANSISTORS 6 for 50p.


6 TUNING VARACTOR DIODES with data @ 35p.

25 ASSORTED TRANSISTOR I.F. TRANSFORMERS @ 40p.

FERRANTI ZTX 107 (BC 107) TRANSISTORS 8 for 57p.

TRANSISTOR T.V. TUNER BRAND NEW @ £1-10.

All V.A.T. Paid and Post Free Over £1.

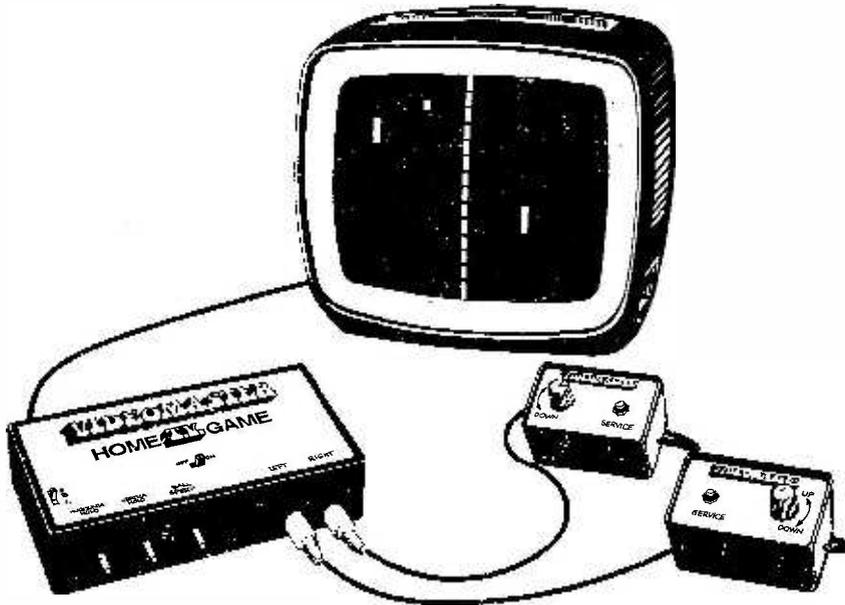

Videomaster urge all good electronics enthusiasts to play the game

The best thing about the Videomaster Home T.V. Game Mk. III is that the sheer pleasure of building it is immediately followed by the excitement of playing three fascinating games.

The famous Videomaster is now available for you to make. It plugs into any standard UHF 625 line TV set, and it shouldn't take you longer than a few hours to build.

In detail . . . The Videomaster Mk. III has eleven integrated circuits . . . four transistors . . . eleven diodes . . . is easy to build . . . with no alignment necessary because with ready-built and tested transistorized UHF modulator, is complete with all parts . . . including fully drilled and prepared p.c.b. . . handsome plastic box . . . control leads . . . complete step by step assembly instructions . . . Runs on a PP7 9 volt battery . . . and has logic and analogue "state of the art" circuitry all with National Semiconductors CMOS devices . . . with full specification.

The cost? Only **£19.95** (+VAT)

POST TODAY TO:

Videomaster Ltd

119/120 Chancery Lane, London WC2A 1QU

Please send me (insert no.) Videomaster Mk. III kits at £21.55 ea. inc. VAT. P & P

I enclose my cheque/money order for £.

Tick if VHF Modulator required -£1 extra

NAME

ADDRESS



PW 1

ALLOW 14 DAYS FOR DELIVERY

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 14p per word (minimum 12 words), box number 35p extra. Semi-displayed setting £12.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue. (01-634 4451).

Receivers and Components

VALVES, RADIO-TV-TRANSMITTING-INDUSTRIAL 1950 to 1975. 2200 types stocked. Many obsolete. SAE for quotation. List 20p Postal Export Service. We purchase new and boxed valves. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 2023.

UNTESTED PACKS: Capacitors, 50 disc ceramics, 30p; 20 polyesters, 40p; 25 electrolytics, 54p. 100 Resistors, 99p. Semiconductors, 200 mixed 54p; 8 branded AC128, 54p; 40 2W zeners, 54p; 50 400mV zeners, 54p. BC107 & 8, 11p each; BC109, 12p; 2N3055, 40p; 2N3819e, 25p; DL704 seven segment LED displays, 95p or 4+ 90p each. Driver IC for DL704 (7448), 90p each; 1lb bag of ferric chloride, 80p; 3lb of computer panels, £1.65; 10 assorted potentiometers, 54p; 1,000 or 2,000µF 30V electrolytics, 52p each; 10µF 65V elec., 5p each. For price list send SAE or 10p. ALL prices include VAT at present rate. Please add 20p P&P on all orders under £5.
TAMAR ELECTRONICS
PO Box 17, Plymouth, PL1 1YJ

UNBELIEVABLE SPEAKER BARGAINS! 8Ω Acoustic Suspension, teak/splained foam front, 6 watt £5.30; 12 watt £6.50; 16 watt (8in woofer, 3in tweeter) £7.90. (Lists 20p.) Satisfaction guaranteed (10% p&p). Gregg Electronics, 105 Grange Road, London SE25.

BETA DEVICES MANUFACTURERS BRANDED PRODUCTS

TRANSISTORS	DIODES & RECT.	BRIDGE RECT.
AC187/8 PR 0-40	IN914 0-04	1A 100V W01 0-20
BC107/8/9 0-09	IN4148 0-04	1A 200V W02 0-22
BC109C 0-11	BY127 0-14	1A 600V W06 0-30
BC147/8/9 0-10	IN4001/2 0-05	2EA 200V £2.00
BCY70/71/720-18	IN4008/8/5 0-08	ZENERS
BFX88 0-20	IN4006/7 0-08	BZY88c 3-3-
BFX60 0-18	IN5401 0-11	33v 5% 0-09
BFX15/2 0-12		1 watt 68- 0-15
2N1132 0-25	555 Timer 0-50	200v 5% 0-15
2N1711 0-25	556 Dual Tr 1-50	L.E.D.
2N2646 0-30	TBA800 1-50	909-RED 0-17
2N2905A 0-21	TBA810 1-60	LED CLIP 0-02
2N3055 0-14		OP. AMP. 10's
OC28 0-45	D.I.L. SOCKETS	709C T099 0-30
OC35 0-35	14 Pin 0-12	709C D.I.L. 0-30
TIP29A 0-49	16 Pin 0-14	741C T099 0-30
TIP31A 0-61		741C D.I.L. 0-30
TIP41A 0-74		723C D.I.L. 0-30
TIP42A 0-90		747C D.I.L. 0-30
		748C D.I.L. 0-30
	ADD 17% V.A.T.	
7400N 0-16	74 SERIES TTL	74121N 0-50
7404N 0-18	7447N 1-00	74123N 1-28
7410N 0-18	7474N 0-87	74141N 1-18
	ALUMINIUM ELECTROLYTIC CAPACITORS	
10µF 22µF 47µF 100µF 220µF 470µF 1,000µF		
18v 0-07 0-07 0-07 0-10 0-13 0-14 0-22		
25v 0-07 0-07 0-08 0-10 0-13 0-16 0-26		

ALUMINIUM ELECTROLYTIC CAPACITORS
10µF 22µF 47µF 100µF 220µF 470µF 1,000µF
18v 0-07 0-07 0-07 0-10 0-13 0-14 0-22
25v 0-07 0-07 0-08 0-10 0-13 0-16 0-26

£W.O. PLUS P.P. 15p TO BETA DEVICES,
4, Highbridge Street,
Waltham Abbey, Essex.

COMMUNICATIONS RECEIVER models. Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11.50. SAE details. PR College Electronics, Millend, Stonehouse, Glos.

MYLAR FILM. 100V: 0.001, 0.002, 0.005µF, 2p; Electrolytic: 0.47/50V, 1/50V, 2.2/50V, 4.7/50V, 10/50V, 5p; Polyester, 250V: 0.01-0.047µF, 3p; Polystyrene: 10pF-8200pF, 5p; Tantalum Bead, 11p; Zeners, 10p; Resistors, ¼W 1.5p, 1W, 2p; 6BA ¼ in screws, nuts, tags, 3 for 1p. Inclusive prices. P&P 10p. Full list, SAE, D. Coulam, Thimbleby, Horncastle, Lincs.

Precision Polycarbonate Capacitors

All High Stability - Extremely Low Leakage		440V AC RANGE		63V DC RANGE	
Value (µF)	Dimensions (mm) each	Price	Value (µF)	Price	Radial leads
0.1µF	L 19.7	51p	0.01µF	60p	42p
0.15µF	27 12.7	59p	0.1µF	60p	42p
0.22µF	33 16	64p	0.22µF	67p	50p
0.25µF	33 16	67p	0.33µF	67p	50p
0.33µF	33 16	75p	0.47µF	67p	50p
0.47µF	33 19	80p	0.68µF	74p	50p
0.5µF	33 19	87p	1.0µF	82p	50p
0.68µF	50-8 19	95p	1.5µF	89p	71p
1.0µF	50-8 19	110p	2.2µF	96p	75p
1.5µF	50-8 25.4	121p	3.3µF	115p	82p
2.0µF	50-8 25.4	144p	4.7µF	122p	113p
INTEGRATED CIRCUITS					
NE555 Pinor 8 Pin 81p					
741C 8 Pin DIL 32p					
ZNA14 1.15 122µF					

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 15V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 6V or 8V; 100.0µF at 2V. ALL at 10p each, 10 for 85p, 50 for 84p.

TRANSISTORS: BC184/183L 11p BFX50 20p
BC107/8/9 9p BC184/184L 12p BFX61 20p
BC114 15p BC212/212L 14p BFX62 20p
BC147/8/9 10p BC547/558A 13p AF178 20p
BC153/7/8 12p BFX194 12p OC71 12p
BC182/182L 11p BFX197 12p 2N3055 20p

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 80p; 1N4148 6p, 14 for 45p, 14 for 50p; 24 for £1.00. 1N4148 5p, 6 for 27p, 12 for 45p; 1N4001 5p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p. **LOW PRICE ZENER DIODES**—400mV, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 5 for 85p, 10 for 65p. **SPECIAL OFFER:** 100 Zeners (may be mixed) for 26.00.

RESISTORS—High stability, low noise carbon film 5%, ¼W at 40°C, ¼W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 5p for 10 of any one value, 70p for 100 of any one value. **SPECIAL PACK:** 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 65p.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wirewound D027: 100 P.I.V. 7p (4 for 20p); 400 P.I.V. 9p (4 for 30p).

BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 17p POST AND PACKING ON ALL ORDERS BELOW £1. ALL EXPORT ORDERS ADD COST OF SRA/AIRMAIL.

PLEASE ADD 25% V.A.T. TO ORDERS.
Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.
MARCO TRADING (Dept. W10),
The Old School, Edinstown, Mr. Wren, Shropshire.
Tel: Whittall 464/465 (STD 094 872)
(Proprs. Mintcoast Trading Ltd.)

COMPONENTS GALORE, pack of 500 assorted Radio, TV and Electronic components, a real bargain at a realistic price. Send only £1.50 c.w.o. This applies only to United Kingdom and Ireland. Overseas prices by arrangement. Caledonian Components, PO Box 3, Glenrothes, Fife, Scotland.

STEREO JACK PLUGS (Standard) 55p for 5 (including P&P). S. F. Downe, 5 Powderham Road, Exeter.

TAPE HEADS

Send stamp for lists.

R.D.I. Ltd.

Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

For valve and transistorized recorders from £2 ea.

NICKEL CADMIUM Cylindrical Accumulators. Sealed. High power/weight ratio. All sizes: 1.2V, 1.2Ah (SP11 size approx.), weight 50gm, £1.94 each. Heavy duty (U2 size approx.), 150gm, 4Ah, 1.2V, £4.15 each. Others include 450mAh, 1.2V (HP7 size approx.), £1.56 each; 2.5Ah, 1.2V, £3.43 each. Ultra heavy duty, 6Ah, 1.2V (60 amps for 5 mins.), £5.71 each. Special 9V transistor radio battery (PP3 size approx.), £3.80 each. Current limiting chargers from £8.00. Further information and sales from Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands. 021 354 9764.

5lb parcels surplus electronic components resistors, capacitors, switches, pots etc. £1.20 p & p 60p.
Wirewound resistors 2W and upwards mixed values 100 for £1, p & p 30p.
Lights bulbs mixed voltage & wattage eg. 2.5v, 6v, 12v etc. from 0.5 watt upwards, including panel lights and vehicle bulbs 30 for £1, p & p 30p.
R. A. Stobbs, 933 Manchester Rd., Cowlesley, Huddersfield, Yorks HD4 5TA.

BRAND NEW COMPONENTS BY RETURN: Electrolytics—16V, 25V, 50V—0.47, 1.0, 2.2, 4.7, 10 mfd.—5p, 22, 47—5½p. (50V—6p) 100—7p. (50V—8p), 220—8p. (50V—10p), 500—11p. (50V—16p), 1000/25V—18p. Subminiature bead-type tantalums —0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V—11p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—3p. 0.04, 0.05—3½p. Mullard tubular polyester 400V E6 series 0.001-0.022—3½p. 0.033-0.1—4½p. Mullard miniature C333 ceramics 63V E12 series 2%, 1.8 pf.-47 pf.—3p. 56 pf.-330 pf.—3½p. Polystyrene 63V E12 series 10 pf.-1000 pf.—5p. 1200 pf.-10,000 pf.—4p. Miniature Highstab. carbon film resistors ½W E12 series 5% 1Ω-10MΩ. (10% over 1MΩ) 1-2p. Postage 10p. Prices VAT Inclusive. The C.R. Supply Co., 127, Chesterfield Road, Sheffield S8.

BARGAIN RELPAK TESTED SEMICONDUCTORS
R6.7.2N2926—Mixed 75p R7.5.BC107NPN 75p
50 Mixed CF Resistors ½ W Packs
R9.100-820 ohms 75p ZN 414 £1.38
R10.1K-82K 75p IN4001 6p IN4002 7p
R11.10K-82K 75p IN4006 15p IN4148 6p
R12.100K-820K 75p TTL-74001/2/3/4 17p
75p Technical enquiries pro rata
Export enquiries welcomed. Deduct 8% VAT. Mail Order only. Satisfaction guaranteed or money back. P & P & VAT included.
RELTRAN LIMITED (Dept PW)
P.O. Box 18, Camberley, Surrey

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc. Sample pack 65p incl. postage or send stamp for list. Redhawk Sales Ltd., 10 Maple Lodge Close, Rickmansworth, Herts. Mail Order Only.

Service Sheets

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS) ALL AT 50p EACH

" PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS "

Otherwise cannot be attended to

(Uncrossed P.O.s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA 71 BEAUFORT PARK LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

NO OVERSEAS MAIL PLEASE

SERVICE SHEETS for Radio, TV, Tape Recorders, Stereo, etc., with free fault-finding guide, 50p and SAE, Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

For Sale

MICROPHONES: AKG D202EI, £45.00; AKG D190C or E, £20.00; AKG D224, £60.00; Sennheiser MD211N, £45.00. All brand new and boxed. Please add 25% for VAT. All other AKG and Sennheiser mikes, SAE for quote. J. J. Francis (Wood Green), Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

COPPER CLAD LAMINATE

FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.5p/sq. inch. Single sided 1/16" glass-epoxy—2.0p/sq. inch. Any rectangular sizes cut to your requirements. Please send cash with order.

Price includes postage and packing. From: **SIMTECH ENGINEERING LTD**, Dedham Road, Ardleigh, Colchester, Essex, CO7 7QA. Telephone 0206 230133

DISCOLIGHTS. Best! Cheapest! Reliable! Bumper catalogue: Aarvak, 98A(P) West Green Road, N15 5NS. 01-800 8656.

Ladders

LADDERS, timber and aluminium. Tel: Telford 586644 for brochure.

Practical Wireless, October 1975

Wanted

TOP PRICES PAID for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C), 367 Kensington Street, Bradford 8, Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners with GCE (or equivalent) in Maths, and English.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on January 5th.

Prospectus from: London Electronics College, Department B10, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

Situations Vacant

MEN!
£90 p.w.
can be yours

Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 D.W. as a starter and can reach over £90 D.W.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators Training Centre

Y28, Oxford Hse., 9-15 Oxford St. W1. Tel: 01-734 2874

Books and Publications

UFO CHARTS: Wave Prediction 56p; Daily Flight Pattern 50p; TV Detection 66p; Propulsion Theory 57p; "Anti-Gravity" 57p; Map 52p; Circuits: Transistor Optical Detector 68p; Radiation/Optical 46p; Crystal Radiation Counter 85p; Sighting Recorder 55p; 22-Range Multimeter Digital 95p. R & E, Highlands, Needham Market, Suffolk.

Technical Books — Radio & Electronics

World's Radio & TV Stations (International Edit.)	£0.68
Audio Amplifiers	£0.70
Boys Book of Crystal Sets & Simple Circuits	£0.33
Television Timebase Circuits	£1.15
Radio TV and Industrial Tube & Valve Equip	£0.68
How to get the best out of your Tape Recorder	£1.67
Practical Electronic Science Projects	£0.85
Jack Darr's Service Clinic	£1.55
Transistor Circuits for Modern Test Equipment	£0.68
Rad & Electr Colour Codes and Data Chart	£0.20
Handbk of Transistor Equip and Substitutes	£0.48
Hi-Fi & Disco Amplifier Design Handbk	£0.87
Radio Servicing Problems	£0.75
Electronic Circuits for the Amat Photographer	£0.68
Handbook of Simple Transistor Circuits	£0.40
TV Fault Finding	£1.10
Sound and Loudspeaker Manual	£0.60
Practical Stereo & Quadrophony Handbook	£0.85
Radio Amateur Operator's Handbook	£0.85
Coil Design & Construction Manual	£0.58
Radio TV & Electronics Data Book	£0.68
79 Electronic Novelty Circuits	£0.80
Receiving Pal Colour Television	£5.35
Radio Technicians Bench Manual	£3.30
Servicing Transistor Radio Receivers	£0.90
1st Book of Hi-Fi Loudspeaker Enclosures	£0.68
2nd Book of Hi-Fi Loudspeaker Enclosures	£0.68
Manual of Electronic Circuits for the Home	£0.60
Modern Crystal Set Circuits for Beginners	£0.40
Electronic Novelties for the Motorist	£0.58
2nd Book of Transistor Equip & Substitutes	£1.07
Handbook of Electronic Musical Novelties	£0.58
Transistorised Novelties for Hi-Fi Enthusiast	£0.40
Fault Location Exercises in Rad. & TV Vol.1	£0.95
Fault Location Exercises in Rad. & TV Vol.2	£1.55
Colour TV Picture Faults	£2.70
Practical Transistor Novelty Circuits	£0.48
Boys Book of Practical Radio & Electronics	£0.68
Radio Receiver Construction using ICs & Transis.	£0.68
ICs & Transistor Gadgets Construction Handbk	£0.68
Integrated Circuits Equip & Substitutes Hbk.	£0.85
Audio Technicians Bench Manual	£3.30
Improving your Hi-Fi	£3.30
Guide to Printed Circuits	£2.80
Towers International Transistor Selector	£3.30
WORLD RADIO TV HANDBOOK 1975	£3.80

All prices include Postage & Packing

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

Aerials

STOCKISTS of Jaybeam Stereobeams, Antiference Mush Killers, Rotars, coax cable, masts and fittings. Send stamp for full lists competitive prices. Alan Turner Services, 26 Chapel Garth, Skipsea, Driffield.

NEW HIGH GAIN 4 ELEMENT VHF/FM RADIO AERIAL

Stereo or mono!

Increase volume, quality and sensitivity of any VHF/FM

Radio or Hi-Fi stereo or mono with this genuine aerial. It's a necessity if you want the best out of your equipment, whether a small radio or expensive stereo. Don't put up with poor reception any longer. Send now, hear for yourself. Ideal for the do-it-yourself enthusiast. Supplied with clamp, instructions and advice. Use inside or out FREE with order maps and channel reference of all Radio and TV Transmitters! Money Back Refund. Send Direct to Dept. NS10 219 Mansfield Rd., Nottingham.

ONLY
£4.49
inc VAT
+65p P&P
Best Cable 12 pzd

IMPERIAL TRADING (AERIALS) LTD.
The quality Aerial Specialists.

GENUINE FULL SIZE
18 element TV aerial
 as used by leading
 TV companies

ITV
 BBC1
 £28/W
 & Colour

Guaranteed
 Perfect Pictures.
 Save EEs. We supply
 this genuine U.H.F. aerial
 for only £2.55. can be fitted
 outside or inside. Quality made
 technically advanced design. Precision
 grid reflector eliminates ghosting.

FOR ONLY
£2.55

Complete with clamp, instructions, advice.
 Money Back Refund. Wall/Caravan Bracket
 25p. Best Cable 12p per yard. Plug 10p &
 FREE with order maps & channel reference of
 Radio & TV Transmitters. Send direct to
 Dept. PW.10 219 Mansfield Rd. Nottingham

IMPERIAL TRADING LTD.
 1000

Miscellaneous

PCB MANUFACTURER'S OFFER. IPC approved full spec., fully drilled ready to assemble PCBs for: "PW" Easy-build Organ, £5.70 (2 PCBs); Tricolour, £1.37; Tele-Tennis (6 PCBs), £5.70; Add-on Sound Effects, £1.10; Telephone Exchange, £1.10; Ferret Metal Locator, 78p; Derby, 85p; Audio/Mixer, 40p; Tone & Rumble, 65p; "PE" CCTV, £2 (2 PCBs); Orion with printed layout on PCB, £1.20; Power Slaves, £1.60 (3 PCBs); Scorpio 2, 70p; Gas Detectors, £1.20; Pulse Generator, £1.10. CWO. Prices totally inclusive. Many others available. SAE for lists. Production space for PCB production, Electroplating, Screen Printing, Tinning, plus all Graphic/Art & Photographic and Design facilities and supplies. Estimates by return or Phone WKF Electronics, Welbeck Street, Whitwell, Worksop, Notts. S80 4TW. Tel: Whitwell 695 (Derbys.). Callers to 1-3 Station Road.

ALUMINIUM PROJECT BOXES

Box No.	Length"	Width"	Height"	Price
7	5½	2½	1½	47p
8	4	4	1½	48p
9	4	2½	1½	48p
10	5½	4	1½	49p
11	4	2½	2	46p
12	3	2	1	38p
13	6	4	2	58p
14	7	5½	2½	75p
15	8	6	3	83p
16	10	7	3	£1.14

Prices include VAT (at 8%) but 18p should be added to the total order value for postage and packing.
9 WATT 12 VOLT FLUORESCENT LIGHT KIT
 Complete Kit including all components, heatsink, channel, tube, etc.
ONLY £3.49 inc. VAT p & p
 Ready Built £4.10 inc. VAT, p & p
 Diffuser 59p extra inc. VAT, p & p
 Send Cheque or P.O. with your order direct to —
ELECTRONICS DESIGN ASSOCIATES
 (Dept. PW9), 82 Bath Street, Walsall WS1 3DE
 Phone: Walsall 33652

TRIACS (plastic) 10A/400V 67p (3 + 64p), Diac 19p, NE555V 55p (3 + 50p), 2N6027 PUT 30p, Ferrite Rods 1¼ in X ¾ in dia. 10p, Plastic Lightdimmer Frontplate 20p, with ¾ in dia hole 22p. P&P 15p. Add VAT. T.K. Electronics, 106 Studley Grange Road, London W7 2LX.

TEXAN AMPLIFIER 20 + 20 Watt
 Complete Kit £32.00 (Tax extra)

Pack 1. Res. 80p. Pack 2/3. Capacitors £3.65.
 Pack 5. Switches £1.50. Pack 6. Pots. Pack 7. Semi Cond. £8.25. Pack 9 P.C.B. £3.00. Pack 10. Chassis £3.00 Case £3.50.
 Toroidal Transf. £8.00 P.P. + Tax extra £2.
 (Toroidal Transf. for 28W £6.10 + tax & post £2)

TELERADIO ELECTRONICS
 325 Fore St., Edmonton, London N9

FORESIGHT ELECTRONICS

62 HIGH ST., CROYDON MAIL ORDER ONLY. C.W.O. Allow 14 days

P.W. DIGI-CLOCK KIT

Complete inc. super steel case, Filter Lens, and all Electronic Components for the incredible price of

£16.50

inc. V.A.T. and p.p.

P.W. EASIBUILD ORGAN

Set of two P.C.Bs £6.80

Set of all semiconductors plus both P.C.Bs £34.90

inc. V.A.T. and p.p.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples: width, depth, height, 8in x 5in x 3in, £1.55; 10in x 6in x 3in, £2.20; 10in x 8in x 3in, £2.75; 12in x 10in x 3in, £3.60; 8in x 4in x 4in, £1.80; 10in x 6in x 4in, £2.70; 12in x 8in x 4in, £3.60; 7in x 7in x 5in, £2.65; 8in x 10in x 6in, £3.60; 12in x 8in x 7in, £4; 12in x 12in x 7in, £4.40. Plus 8% VAT & 50p postage. Over 200 models to choose from. Prompt despatch. Free literature (stamp would be appreciated), Bazelli, Dept. No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

Smiths motaysyn position indicator and transmitter, with or without modification will work as an aerial or wind direction monitor, £1.70p. No. 7 Moving Coil hand mike, 75p. Vero board 0.1 matrix 3/32" sq. 22p. LED Red or Green with clips 15p. Ex-aircraft m/c meter, 1mA FSD. Scaled 0-110% (with coloured sectors) 3" dia. £2.75p. Min. order 25p. Prices include P & P. SAE for list.

Eldon Electronics, 16, Raven Road, Timperley, Cheshire.

E. WENMOUTH, Radio & Television, 50 South Street, Exeter. Tel: 76058. Due to popular demand we have pleasure in announcing that our stocks of radio, amateur and DIY spares are now being increased to meet your requirements.

THE SCIENTIFIC WIRE CO

Copper - Nickel Chrome - Eureka - Manganin Wires.
 Enamelled - Silk - Cotton - Tinned Coverings.
 No minimum charges or quantities.
 Trade and Export enquiries welcome.
 S.A.E. Brings List.
 P.O. BOX 30, LONDON, E4 9BW

BEGINNERS. Our two, large (33in x 23in) data sheets give the information you need on radio transmission, reception and components. Plus circuits, and crystal clear, full size plans for simple long, medium and short wave receivers. No soldering. Components easy to obtain. Send 65p + 10p P&P to: Tekna Data Sheets PW (Radio and Electronics), 11 Lawn Avenue, Doncaster, South Yorks DN1 2JE. Mail order UK only.

DIGITAL CLOCK CHIP, AY-5-1224, with data & circuit diagram, £3.66 + VAT, Jumbo LED digits (16mm high) economy type DL-747, only £2.04 each + VAT, post free.—Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

TREASURE TRACER
MK III Metal Locator



- Varioap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit
- Send stamped, addressed envelope for leaflet

Our price **£10.90** Built & tested **£15.25**
 Plus 6% VAT (5% VAT) Post 60p + £1.20 VAT (5%)

MINIKITS ELECTRONICS,
 18 CLEVELAND ROAD,
 LONDON, E18 3AN (Mail order only)

LOW-COST I.C. MOUNTING for any size DIL package. 100 pin sockets, 50p. 7 and 8 hole plastic supports, 5p/pair. Quantity rates. SAE details and sample. Trial pack, 50p, (P&P 10p/order.) PKG Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

FELSTEAD ELECTRONICS (PW93)

Longley Lane, Gatley, Cheshire, Ches. SK8 4EE

Our new complete list with illus. Stylus chart & best values in Cartridges, Cassettes, Tape, Audio Leads, Microphones, Meters & Multimeters, Phones, Plugs, Sockets & many useful accessories for Radio, Recording & Hi-Fi—YOURS FREE FOR S.A.E. USUAL TRUSTWORTHY SERVICE.

Most items available to callers in Manchester At **TRIONIX, 177 School Lane, Kingsway Corner, 19.**

GLASS FIBRE P.C.B.'s. Send master and 30p per board plus 7p per square inch tinned or plus 9p per square inch drilled and tinned. Proto Design, 4 Highcliff Way, Wickford, Essex. Previously Electro Circuits, Wickford.

175cc.P.C.B. INK !!

£ 1-50 post & vat free
Mawson Associates
 64, Brookbank Road,
 London SE13.

Synthesiser
"Sounds Supreme"

by **Dewtron** (25% VAT extra.)

Famous kits. e.g. waa-waa complete kit £4.50; Fuzz kit £6.50 P&P 25p under £10. Ring Modulator modules £11. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

12 VOLT 21" 13 Watt Fluorescent Lighting
(by Thorn/AE) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT
SALOP ELECTRONICS 23 Wyle Cop,
Shrewsbury, Shropshire Tel. 53206

RANDOM NUMBER SELECTOR
Minicomp 6L: New! Electronic Dice, range 1-6. Jumbo. 0.6in LED display. 4 ICs. Kit £14.75; built and tested £16.90.
Minicomp 10L: Two ranges 1-6 and 0-9. Kit £17.75, built and tested £19.90.
Minicomp 100: Four ranges 1-6, 0-36 (Roulette), 0-59 (Pools) and 0-99. Nixie display, 6 ICs. Built and tested £29.50.
Terms: CWO, Mail Order only. Prices inclusive. 1 year guarantee.

MICROELECTRONICS
51 Mexfield Road, London SW15 2RG

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ Pocket-sized **MAXI-VOLT** Big 1/2 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £2.45 for your Maxi-Volt now!

★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £7.95 for yours now!

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £3.50 now! (all prices include V.A.T., packing & postage.)

Send remittance to:

BOFFIN PROJECTS,
4 CUNLIFF ROAD,
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)
Or for more details, send 20p for lists

GADGETS GALORE!!

★ **READY BUILT & TESTED** ★

Signal Injector £2.25 Signal Tracer £3.25
Logic Probe £4.45 Noise Generator £8.95
Metronome £3.95 Continuity Tester £3.95
Now available from our new shop!

Prices include U.K. Postage and Batteries
Please call or write (SAE list) to:

G.K. SERVICES, (G2)
38 High St., St. Mary Cray, Orpington
BR5 3NJ

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4 1/2 p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

JAYBEE FOR KITS

AMTRON, JOSTYKIT, ETC.

Send S.A.E. for full information

JAYBEE ELECTRONICS, Sarum Farm Est.
SARUM ROAD, WINCHESTER, HANTS
Telephone 0962-61806

FANTASTIC NEW MICROTEST 80

MEASURES ONLY

90 x 70 x 18 mm
ELECTRONIC ZERO Ω

Amazing Value at **£11.95**
8 fields of measurement
and 40 ranges

PRINTED CIRCUIT BOARD IS
REMOVABLE WITHOUT SOLDERING

Volts D.C. 6 ranges: 100mV - 2V, -10V, -50V, -200V, -1000V. (20kΩ/V) ±2% precision on DC and AC

Volts A.C. 5 ranges: 1.5V, -10V, -50V, -250V, -1000V. (4kΩ/V)

Amp. D.C. 6 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A

Amp. A.C. 5 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A

Ohms 4 ranges: Low Ω - Ω x 1 - Ω x 10 - Ω x 100 from 1/10 Ω until 5 Mega Ω

V Output 5 ranges: 1.5V, -10V, -50V, -250V, -1000V.

Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB

Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF



SUPERTESTER 680R ICE

20,000 Ohm per Volt sensitivity • Fully screened against external magnetic fields • Scale width and small case dimensions (128 x 95 x 32mm) • Accuracy and stability (1% in D.C., ±2% in A.C.) of indicated reading • Simplicity and ease of use and readability • Full ranges of accessories • 1000 times overload • Printed circuit board is removable without de-soldering • More ranges than any other meter. Ask for free catalogue

£18.50

Accessories (extra) available to convert Microtest 80 & Supertester 680R into following: LIGHT METER GAUSS METER ELECTRONIC VOLTMETER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100K Multiplier, SIGNAL INJECTOR—Send for details.

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0-99-9A - 9 Ranges.

A-AC 0-3-3A - 5 Ranges.

V-DC 0-6-1200 V - 9 Ranges.

V-AC 3-900 V - 8 Ranges.

Freq.: In the range of 45 to 20kHz.

Resistance: 500 Ohm to 5MΩ

5 Ranges. Decibel: -10 to +22dB

Accuracy: ±2.5% DC, ±4% AC.

Dimensions: 167 x 98 x 63 mm.

Only **£9.25**

ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including ★ 170V-21mA ★ All d.c. operation ★ Uniform, continuous line characters of equal height ★ Memory with simple solid state drive circuits ★ Readability in high ambient light... 200 footlamberts brightness ★ Long life with no loss of brightness ★ Character height 2 1/2 in.

Price only **99p** each plus 16p P/P.
Bases for above 60p each.

JUST ARRIVED !!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA, Pulse duration 100μs. Character height 0.51, overall size 1-4.

Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853st

1-25 £1. 25 + 90p 100 + 80p
1000+ price on application
8% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

BUILD YOUR OWN

You are invited to send S.A.E. for lists of our very extensive range of high quality amplifier, pre-amps, F.M. tuners, instruments. Radiocontrol ignition units and many other kits.

TELERADIO ELECTRONICS,
325 FORE STREET, EDMONTON,
LONDON N9

ELECTRONICS HOBBY SHOP

Transistors I.C.s, Diodes, C.Mos, Resistors, Pots, Capacitors and many more items

ARIES

ELECTRONICS

33 Rutland Road,
Maidenhead
(Near Tech College)

Please send
for lists
or phone:

Maidenhead 37431

DIGITAL CLOCK KITS

MHI—A modular approach to digital clock building. An MHI kit uses an MHI clock kit plus an MHI display kit. Any of the clock kits will interface with any of the display kits or with any other common-anode LED display. Each clock kit contains basic components plus a PCB—all you have to supply is a few resistors, transistors, etc.

MHI-5376. This kit has full car/boat clock facilities, quartz time source, brightness control, etc. Display is switchable with ignition for power saving.
KIT: MM5378, socket, CA3081, 2Mhs XTAL and trimmers, PCB. **£15.10**

MHI-5024. The MHI-5024 kit will act as a 6 or 4 digit stop watch chip with readouts down to 1 sec. Clock will count up or down and can (with additional components) also act as a calculator.
Kit: MK5024, socket, CA3081, PCB **£14.00**

MHI-5314. Six digit basic clock, 12/24 hour, MM5314 chip. **£8.60**

MHI-5025. Six digit alarm clock, Snooze, MK5025 chip. **£9.35**

MHI-7001. Six digit Time/Date/Alarm/Timer, can be used as electronic time-switch in addition to other functions. **£10.00**

MHI-D707. Four or six digit display kit. 0.3" digits
4 Dig—**£6.95**
6 Dig—**£9.50**

Supplied with PCB. 6 Dig—**£12.00**
MHI-D727. Four or six digits, 0.5" high digits.
4 Dig—**£8.50**
6 Dig—**£12.00**

Supplied with 6 digit PCB.. 4 Dig—**£9.80**
MHI-D747. Four or six digits, 0.6" high digits.
4 Dig—**£9.80**

Supplied with PCB for 6 digits. 6 Dig—**£14.70**

TERMS: CWO. Access. Barclaycard (simply quote your number and sign). Credit facilities to Accredited account holders.

BYWOOD

68 Ebbens Road, Herts HP3 9RDA. VAT: All prices exclude VAT (8%) P/P: 15p.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER. CALLERS SATURDAYS ONLY

OUR NEW LOW PRICES MEANS YOU PAY LESS VAT.

TRANSISTORS (less 10% for 25+ of one type)			
AC125	13p	BC148	7p
AC126	11p	BC149	9p
AC127	11p	BC154	8p
AC128	11p	BC157	13p
AC141	20p	BC158	13p
AC142	15p	BC159	13p
AC176	11p	BC167	12p
AC187	12p	BC168	12p
AC188	11p	BC169	12p
ACV17	35p	BC170	11p
ACV19	25p	BC171	11p
ACV20	24p	BC172	11p
ACV21	20p	BC177	16p
ACV22	16p	BC178	16p
AD140	48p	BC179	16p
AD149	45p	BC182	10p
AD181	34p	BC183	10p
AD182	34p	BC184	11p
AF114	13p	BC184L	11p
AF115	13p	BC212	12p
AF116	13p	BC212L	12p
AF117	13p	BC213	10p
AF118	40p	BC214	10p
AF121	33p	BCY42	28p
AF125	30p	BCY43	25p
AF126	30p	BCY58	18p
AF127	30p	BCY59	18p
AF139	33p	BCY70	15p
AF181	45p	BCY71	15p
AF185	48p	BCY72	15p
AF239	38p	BD124	75p
BC107	9p	BD131	40p
BC108	9p	BD132	40p
BC108B	12p	BD137	45p
BC108C	12p	BD145	52p
BC109	9p	BDY60	75p
BC109C	12p	BDY61	65p
BC147	7p	BF115	22p
		BF127	26p
		BF178	23p
		BF179	33p
		BF180	33p
		BF184	22p
		BF185	22p
		BF194	10p
		BF195	10p
		BF196	10p
		BF197	12p
		BF252	32p
		BF256	36p
		BF595	18p
		BFX86	21p
		BFX88	22p
		BFY50	15p
		BFY51	15p
		BFY52	17p
		BSX20	16p
		BU105	62p
		BU106	62p
		NJE371	78p
		MJE520	62p
		MPP103	30p
		MPP104	30p
		MPP105	30p
		OC23	144p
		OC28	40p
		OC28	40p
		OC35	48p
		OC36	32p
		OC37	32p
		OC42	15p
		OC44	12p
		OC45	12p
		OC70	11p
		OC71	11p
		OC72	11p
		OC73	11p
		OC81	12p
		OC82	12p
		OC83	28p
		OC140	10p
		OC201	70p
		OC202	80p
		TIC44	30p
		TIP29	43p
		TIP29A	45p
		TIP30	48p
		TIP30A	54p
		TIP31	54p
		TIP32	64p
		TIP33	95p
		TIP34	130p
		TIP41A	68p
		TIP42A	74p
		TIS43	28p
		TIS44	28p
		ZTX107	10p
		ZTX108	8p
		ZTX109	12p
		ZTX130	12p
		ZTX131	14p
		ZTX302	18p
		ZTX302A	22p
		ZTX311	10p
		ZTX341	19p
		ZTX500	15p
		ZTX501	15p
		ZTX502	18p
		ZTX504	42p
		ZTX531	23p
		ZTX550	18p
		IS44	5p
		IS920	7p
		IS921	7p
		IS922	8p
		IS923	10p
		2N696	15p
		2N697	13p
		2N698	13p
		2N706	11p
		2N708	16p
		2N918	40p
		2N930	18p
		2N1131	20p
		2N1132	20p
		2N1301	20p
		2N1302	17p
		2N1303	20p
		2N1304	24p
		2N1305	24p
		2N1306	24p
		2N1307	24p
		2N1308	24p
		2N1309	24p
		2N1310	24p
		2N1990	45p
		2N2160	62p
		2N2162	23p
		2N2217	20p
		2N2221	20p
		2N2222	20p
		2N2303	25p
		2N2369	14p
		2N2483	30p
		2N2646	38p
		2N2904	20p
		2N2905	15p
		3N148	85p
		3N141	85p
		2N926G10P	40p
		40362	40p
		2N926R	8p
		40873	58p

TTL 74c			
Less 5% for 15+ mixed			
DIGITAL IC. Less 10% for 25+			
7400	14p	7430	15p
7401	14p	7432	25p
7402	15p	7433	36p
7403	15p	7437	27p
7404	15p	7438	27p
7405	18p	7440	15p
7406	38p	7441	65p
7407	38p	7442	65p
7408	15p	7443	120p
7409	15p	7444	105p
7410	15p	7445	85p
7411	20p	7446	105p
7412	20p	7447	100p
7413	35p	7448	70p
7414	60p	7450	15p
7416	35p	7451	15p
7417	35p	7453	15p
7420	15p	7454	15p
7422	24p	7460	15p
7423	27p	7470	30p
7425	27p	4772	26p
7426	27p	7473	32p
7428	38p	7474	32p
		7475	32p
		7476	32p
		7480	44p
		7481	99p
		7482	27p
		7483	83p
		7484	90p
		7485	125p
		7489	275p
		7490	40p
		7491	80p
		7492	48p
		7493	59p
		7495	63p
		7496	72p
		74121	32p
		74122	45p
		74123	63p
		74141	65p
		74151	69p
		74190	160p
		74191	160p

DIODES				
BY100 18p				
BY127 11p				
OA5 38p				
OA9 38p				
OA10 38p				
OA47 8p				
OA70 8p				
OA79 8p				
OA81 8p				
OA85 10p				
OA90 6p				
OA91 6p				
OA100 10p				
OA200 6p				
OA10 38p				
IN914 6p				
1N4001/2 5p				
1N4003 5p				
1N4004/5 6p				
1N4006/7 6p				
1N4148 6p				
1S320 6p				
1S921 6p				
Price £2.75, p & p 10p				
709C	14 pin	25p	LM304H	17p
741C	26p	LM305	17p	
747C	70p	LM380	95p	
748C	28p	LM381	160p	
AY-1-0212	5-8p	LH390	65p	
AY-1-5051	1-15p	LM300	55p	
AY-5-1224	36p	MC724P	55p	
AY-5-3500	610p	MC1303L	148p	
AY-5-3507	610p	MC1304P	360p	
AY-5-4007	735p	MC1310P	220p	
CA3018	72p	MC1710CG	55p	
CA3020	145p	MFC4000B	54p	
CA3035	135p	MFC4000B	54p	
CA3036	90p	MLM309K	158p	
CA3046	55p	NE555	48p	
CA3048	22p	NE555DB	99p	
CA3075	150p	NE555	34p	
CA3081	150p	NE561	315p	
CA3089E	195p	NE561	249p	
CA3090A	250p	SL405D	150p	
CA3123E	140p	SL414A	160p	
LM300H	17p	SN7623	160p	
LM301	42p	SN7623	160p	

LINEAR IC'S			
SN76115	200p	BRIDGE RECTIFIERS (plastic case)	1A 50V 38p
TAD100	130p	1A 50V 20p	1A 100V 42p
TBA800	95p	1A100V	24p
TBA810	150p	1A200V	26p
ZN414	95p	1A400V	27p
		1A600V	29p
		2A50V	30p
		2A100V	38p
		2A200V	44p
		3A 600V	99p
		2A400V	54p
		2A600V	54p
		4A100V	53p
		4A400V	60p
		4A800V	60p
		6A100V	64p
		6A400V	60p
		6A1000	54p
		BY124	44p
		BY164	44p

OPTO ELECTRONICS			
LED TIL 209 (red) with socket	15p	ALUM. BOXES with lid	50p
LED Larger 0.2" diam. Red	15p	2 1/2 x 3 1/2"	50p
LED Larger Green, Yellow, Amber	19p	4 x 4 1/2"	50p
7 Seg Display		4 x 2 1/2 x 1 1/2"	50p
MINITRON 3015F	100p	4 1/2 x 1 1/2"	58p
MAN 3640	170p	4 1/2 x 2 1/2"	50p
LIT 707	125p	3 1/2 x 1 1/2"	44p
LIT 747	195p	6 x 4 1/2"	78p
		7 x 5 1/2"	84p
		8 x 6 1/2"	106p
		10 x 7 1/2"	122p
		10 x 4 1/2 x 3"	110p
		12 x 5 1/2 x 3"	120p

FUSES AND HOLDERS			
20mm 150mA-5A	3p	1" Mains, 2A, 3A, 5A, 7A, 10A,	
1 1/2" 500mA-15A	3p	13A,	5p
Anti-surge 20mm		HOLDERS	
100, 250, 500, 800mA,		Panel Single	6p
1A, 1.6, 2, 2.5, 3.15,		20mm Chassis	16p
5A,		1 1/2" Chassis	22p

ALL DEVICES BRAND NEW AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 20p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE.

VAT Applicable to U.K. Customers only. All prices are exclusive of VAT. Please add 8% to devices marked * To the rest add 25%.
Send 15p postage for our comprehensive catalogue

POLYESTER CAPACITORS: Axial lead type (Values are in µF)			
400V: 0-001, 0-0012, 0-0015, 0-0018, 0-0022, 0-0033 3p; 0-0047, 0-0068, 0-01, 0-015, 0-022 4p; 0-033, 0-047, 0-068, 0-1, 0-15, 0-22, 7p; 0-33, 15p; 0-47, 17p; 180V: 0-1, 0-15, 4p; 0-22 5p; 0-33 6p; 0-47 8p; 0-68 13p; 1-0 15p.			
250V: 0-01, 0-015, 0-022, 0-033 3p; 0-047, 0-068, 0-1 4p; 0-15 6p; 0-22, 0-33 7p; 0-47 9p; 0-68 10p; 1-0 14p; 1-5 22p; 2-2 24p.			

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF)			
63V: 0-47, 1-0, 1-5, 2-2, 3-3, 4, 4-7, 6-8, 10, 15, 20, 22, 47, 68, 6p; 100, 12p; 40V 100, 6p; 50V: 1000, 42p; 30V: 3500, 41p; 25V: 10, 68, 150, 6p; 220, 11p; 470, 13p; 680, 18p; 1000, 24p; 2200, 34p; 3000, 39p; 4700, 47p; 16V: 4, 10, 125, 250, 6p; 16V: 1000, 1500, 18p; 10V: 4, 10, 5p; 640, 10p; 1000, 14p; 2200, 18p.			

POTENTIOMETERS (AB) Carbon			
Track, 0-25W Log & 0-5W Linear values			
1KΩ-2MΩ single gang	14p		
5KΩ-2MΩ single gang D/P switch	32p		
2KΩ-2MΩ dual gang stereo	45p		

SLIDER POTENTIOMETERS			
0-25W log and linear values			
10KΩ-500KΩ single gang	35p		
50KΩ-500KΩ Dual gang	50p		
50KΩ Lin 150mm WS 150	250p		

PRESET POTENTIOMETERS			
1/4W 50Ω-1MΩ Vertical only	5p		
0-25W 10Ω-2-2MΩ Horizontal	6p		
0-25W 1KΩ-2-2MΩ Vertical	6p		

QUALITY RESISTORS. ERIE MAKE			
Carbon, Miniature, High Stability, Low Noise			
POWER Tol. RANGE Val. 1-99 100+			
0-25W 5% 2-2Ω-4-7M E24	1p	0-8p	
0-5W 5% 2-2Ω-4-7M E12	1p	0-8p	
1W 5% 2			

TTLs		7482 70p		OP. AMPS		VOLTAGE REGULATORS (PLASTIC)		Transistors	
7400	13p	7483	80p	301A	Ext. Comp. 8 pin DIL	723	1 amp + Ve - Ve	AC126/7	11p
7401	14p	7484	95p	709	Ext. Comp. 8/14 pin DIL	14 pin DIL	5v 7805 140p 7905 250p	AC128	11p
7402	14p	7485	120p	710	Diff. Comp. 14 pin DIL	12v	7812 140p 7912 250p	AC141/2	18p
7403	16p	7486	30p	741	Int. Comp. 8/14 pin DIL	15v	7815 140p 7915 250p	AC176	11p
7404	16p	7489	270p	747	Dual 741 14 pin DIL	18v	7818 140p 7918 250p	AC187	12p
7405	16p	7490	40p	748	Ext. Comp. 8 pin DIL	24v	7824 140p 7924 250p	AC188	11p
7406	38p	7491	75p	776	Programmable Op. Amp.			AD149	43p
7407	36p	7492	45p	TO5				AD161	36p
7408	14p	7493	40p	CA3130SCOSMOS Op. Amp. 8 pin				AD162	36p
7409	20p	7494	75p	DIL				AF114/5	13p
7410	14p	7495	65p	LM3900 Quad. Op. Amp. 14 pin				AF116/7	13p
7412	23p	7496	78p	DIL				AF139	33p
7413	32p	74107	30p	MC1458 Dual Op. Amp. 8 pin DIL				AF239	38p
7414	60p	74121	30p	NE536T FET Op. Amp. TO5				BC107/8	9p
7416	33p	74122	48p	LINEAR I.Cs.				BC109	10p
7420	14p	74123	68p	CA3046 Transistor Array 14DIL				BC147/8	7p
7422	18p	74141	65p	CA3048 4 Low Noise Amp. 14 DIL				BC149C	8p
7423	34p	74151	72p	CA3089 FM IF System				BC157	10p
7425	30p	74153	85p	CA3090 FM Stereo Decoder				BC158	8p
7427	37p	74154	150p	ICL8038BC Fun. Gen. 14 pin DIL				BC159	9p
7430	14p	74155	76p	ICL8038CC Fun. Gen. 14 pin DIL				BC169C	12p
7432	25p	74156	76p	LM380 2W Audio Amp. 14 DIL				BC177	18p
7437	25p	74160	99p	LM381 Stereo Preamp. 14 DIL				BC178	17p
7440	14p	74161	99p	MC1310 SQ Quad. Dec. 14 DIL				BC179	18p
7441	65p	74162	99p	MC1312				BC182/3	10p
7442	60p	74163	99p	MC1314				BC184	11p
7447	75p	74164	120p	MC1315				BC187	30p
7448	70p	74166	126p	MFC4000 1/4 Audio Amp. PCB				BC212	11p
7450	15p	74175	85p	MFC6040 Electronic Attenuator				BC213	10p
7451	16p	74180	100p	NE555 Timer 8 pin DIL				BC214	14p
7453	16p	74181	2.98p	NE556 Dual 555 14 pin DIL				BCY70	18p
7454	16p	74182	82p	NE561 PLL with AM Demod.				BD123	100p
7460	15p	74185	135p	NE562 PLL with VCO 16 DIL				BD124	65p
7470	27p	74190	144p	NE563 PLL FM/IF Demod.				BD131	36p
7472	25p	74191	144p	NE565 PLL 14 pin DIL				BD132	40p
7473	30p	74192	120p	NE566 PLL Fun. Gen. 8 pin DIL				BF115	22p
7474	30p	74193	120p	NE567 PLL Tone Dec. 8 pin DIL				BF167	23p
7475	45p	74194	108p	2567 Dual 567 14 pin DIL				BF173	25p
7476	30p	74195	75p	TBA800 5W Audio Amp.				BF181/2	33p
7480	50p	74198	198p	TBA810 7W Audio Amp.				BF184/5	22p
7481	95p	74199	180p	TBA820 2W Audio Amp.				BF194	10p
C-MOS I.Cs		4028AE140p		ZN414 TRF Radio Receiver				BF195	9p
4000AE	19p	4029AE196p		Basic data sheets at 10p each + SAE.				BF196	14p
4001AE	19p	4046AE202p		CLOCK I.Cs.				BF197	15p
4002AE	19p	4047AE137p		AY 5-1224 14 pin DIL	400p	VAT		BF257	32p
4009AE	67p	4049AE 63p		MM 5314 24 pin DIL	430p	@		BFR39/40	30p
4011AE	21p	4054AE196p		MM 5316 40 pin DIL	900p	8%		BFR79/80	30p
4013AE	63p	4055AE196p		Data sheets 30p each plus sae				BFX29/30	30p
4016AE	63p	4056AE135p		LOW PROFILE DIL SOCKETS BY				BFX84	26p
4017AE	163p	4060AE229p		TEXAS 8 pin 13p, 14 pin 14p, 16 pin				BFX85/6	25p
4018AE	229p	4071AE 26p		15p, 24 pin 70p				BFX87	20p
4022AE	169p	4081AE 26p						BFX88	24p
4023AE	21p	4510AE160p						BFY50	16p
4024AE	116p	4511AE250p						BFY51/2	16p
4027AE	91p	4528AE120p							

Minimum order £2. P & P 20p. MAIL ORDER ONLY
Please add VAT as shown Govt., Colleges, etc, orders welcome

TECHNOMATIC LTD. 54 SANDHURST ROAD, LONDON, NW9
Tel. 01-204 4333

INDEX TO ADVERTISERS	
Ambit International	cover iv
Aries Electronics	525
A.S.P. Ltd.	444
Astro Electronics Ltd.	476
Audio Equipment	438
Bamber, B.	508
Barrie Electronics	499
Bentley Acoustics Ltd.	512
Beta Devices	522
B.H. Component Factors Ltd.	518
Bib Hi-Fi Ltd.	528
Bi-Pak Ltd.	452-453
Bi-Pre-Pak Ltd.	467
Birkett, J.	520
Boffin Projects	525
British Institute of Engineering Technology	448, 472, 500
British National Radio & Electronics School	436, 510
J. Bull (Electrical) Ltd.	464
Bywood Electronics	525
C. Caranna	523
Central Imports & Exports	518
Chromasonic Electronics	cover iii
C.J.L.	442
Codar	504
Colomar (Electronics) Ltd.	516
Crescent Radio Ltd.	437
Crofton Electronics	517
C.T. Electronics	cover ii
D.E.W. Ltd.	524
Doram	443
Dziudas, M.	510
Eldom Electronics	524
Electroni-Kit	444
Electronic Brokers	525
Electronic Design Associates	513-524
Electronic Mail Order Ltd.	436
Electrospares	442
Electrovalue Ltd.	511
Elliott Blunt Assocs.	436
Elvins	520
Everest Instruments Ltd.	517
Felstead Electronics	524
Foresight Electronics	524
G.K. Services	525
Goldring	448
Greenbank Electronics	450
Greenweld Electronics	472
H.A.C. Short-Wave Supplies	517
Harversons	519
Heath (Gloucester) Ltd.	463
Henry's Radio Ltd.	508
H.F.P.	512
I.L.P. Electronics Ltd.	445
Imperial Trading	523 & 524
Intertext - I.C.S.	520
Jaybee Electronics	525
Kensington Supplies	523
Lasky's Ltd.	439-440-441
Lektrokit	516
Lewis Radio	449
Linear Products	510
London Computer Operators Training Centre	523
London Electronic College	523
Lowe Electronics	450
Macks Electronics	503
Maplin Electronic Supplies	471
Marco Trading	522
Mawson Associates	524
Microelectronics	525
Marshall, A. & Son	472
Minikits Electronics	524
Newmart Electronics	504
Partridge Electronics Ltd.	476
Pembridge College of Electronics	508
R.D.I. Ltd.	522
Radio Book Services	523
Radio Component Specialists	514-515
Radio Exchange Ltd.	507
Reltran Ltd.	522
Rivlin Instruments Ltd.	500
R.S.C. (Hi-Fi) Centres Ltd.	434-435
R.S.T. Valve Mail Order Co.	451
R. & T.V. Components Ltd.	446-447
Salop Electronics	525
Sales Team	521
Saxon Entertainments Ltd.	498-499
Scientific Wire Company, The	524
Selray Book Co.	513
S.I.G.A. Electronics Ltd.	449
Simtech Engineering Ltd.	523
Sintel	516
Stobbs, R. A.	522
Studio Electronics	518
Surplectronics	468
Swanley Electronics	517
Tamar Electronics	522
Technomatic Ltd.	527
Teleradio Electronics	524 & 525
Toner Electronics	444
Trampus Electronics Ltd.	449
Vero Electronics	450
Watford Electronics	526
West London Direct Supplies	450
Wilmslow Audio	468
Xeroza Radio	512
Z. & I. Aero Services	528
Zentac	500

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

FULLY GUARANTEED															
OA2	0.45	6AJ5	0.65	6CB6	0.50	6SG7	0.50	ECH8	0.50	EL84	0.35	PCC88	0.55	U81	0.80
OA3	0.55	6AK5	0.70	6CD6GA	1.60	6SJ7	0.90	ECH83	0.50	EL86	0.50	PCC189	0.65	U81	0.75
OB2	0.45	6AK6	0.40	6CG7	0.70	6SL7GT	0.85	ECH84	0.50	EL90	0.50	PCF80	0.40	U281	0.60
OC3	0.45	6AL5	0.60	6CL6	0.75	6SNTGT	0.85	ECH200	0.70	EL93	0.70	PCF82	0.40	U282	0.60
OD3	0.45	6AM6	0.60	6CL8A	0.90	6SQ7	0.90	ECL80	0.40	EL90A	0.70	PCF86	0.65	U301	0.55
1A3	0.55	6AQ5	0.50	6CS7	0.85	6SR7	0.60	ECL82	0.42	EL804	0.80	PCF200	0.90	U403	0.75
1A7	0.60	6AR5	0.70	6CU5	1.00	6SS7	0.40	ECL83	0.75	EL803	2.00	PCF201	0.85	U404	0.75
1A4D	1.20	6AS6	0.80	6CX8	1.00	6U8A	0.35	ECL84	0.60	EL822	2.10	PCF801	0.55	U801	0.80
183GT	0.55	6AS11	1.00	6CY5	0.75	6V6GT	0.60	ECL85	0.65	ELL80	2.00	PCF802	0.55	UABC80	0.50
1R4	0.50	6AT8	0.60	6CY7	1.00	6X4	0.45	ECL86	0.55	EM80	0.55	PCF806	0.80	UAF442	0.70
1R5	0.55	6AT8A	0.90	6DK6	0.80	6X5GT	0.85	ECL800	4.00	EM81	0.80	PCH200	0.75	UBC81	0.50
1S4	0.40	6AU4GT	0.60	6DQ6B	1.00	6X8	0.80	EF9	0.90	EM83	0.50	PCL81	0.55	UBC80	0.50
1S5	0.40		0.75	6DT6A	0.80	12AB5	0.80	EF37A	0.90	EM84	0.40	PCL82	0.40	UBF80	0.50
1T4	0.40	6AU5GT	1.50	6DT8	0.80	12AC6	0.80	EF41	0.75	EM85	1.00	PCL83	0.70	UBF89	0.50
1U4	0.70	6AU8	0.40	6EA8	0.75	12AD6	0.80	EF42	0.80	EM87	1.00	PCL84	0.50	UBL21	0.75
1U5	0.80	6AV5GT	1.00	6ES5	0.85	12AE9	0.75	EF50	0.40	EY81	0.45	PCL85	0.60	UC92	0.50
1V2	0.70	6AV8	0.50	6EW6	0.60	12AL5	0.50	EF55	1.50	EY81	0.45	PCL86	0.60	UC94	0.75
1X2B7	0.75	6AW8A	0.75	6F1	0.85	12AQ5	0.55	EF59	0.50	EY87	0.50	PCL200	0.75	UC95	0.50
2D21	0.55	6AX6GT	1.00	6F6GB	0.80	12AT6	0.45	EF83	1.25	EY88	0.50	PCL205	0.60	UC96	0.75
2X2	0.75	6BA4	1.20	6F11	0.65	12A77	0.45	EF85	0.45	EZ41	0.75	PC500	0.50	UCB21	0.70
3A3	0.80	6B8	0.60	6F13	0.75	12AU6	0.50	EF86	0.40	EZ80	0.30	PFL200	1.50	UCH42	0.80
3A4	0.80	6B8C	0.80	6F15	0.70	12AU7	0.38	EF89	0.35	EZ81	0.35	PL33	0.40	UCH81	0.50
3A5	1.00	6B8E	0.45	6F18	0.60	35Z5GT	0.60	EF91	0.60	EZ90	0.45	PL36	0.60	UCH11	0.70
3A8GT	0.85	6BF5	1.00	6F23	0.90	12AV7	0.90	EF92	0.60	GLU50	0.40	PL81	0.55	UCL33	0.70
3B4	0.90	6BF6	0.75	6F24	0.80	12AX7	0.38	EF93	0.38	GZ30	0.65	PL82	0.50	UCL33	0.70
3D6	0.40	6BH6	0.75	6F25	1.00	12B4A	0.80	EF94	0.40	GZ33	2.00	PL84	0.50	UFF1	0.70
3Q4	0.75	6BJ8	0.75	6F28	0.75	12BA6	0.50	EF95	0.40	GZ34	0.75	PL84	0.50	UFF1	0.70
3Q5	0.60	6GB8	1.40	6GH8A	0.75	12BE8	0.60	EF96	0.35	HB81	0.50	PL95	0.70	UF41	0.75
3S4	0.50	6AS7	1.40	6K4F	0.60	12BH7	0.60	EF97	0.70	HLA	0.75	PL504	0.90	UF42	0.75
3V4	0.80	6BN6	0.80	6GK6	0.85	12BL9	0.70	EF98	0.80	KT33C	1.20	PL508	0.90	UF80	0.40
5R4G	1.00	6BN8	0.85	6J5GT	0.55	12BY7A	0.70	EF183	0.35	KT44	0.40	PL508	0.90	UF85	0.50
5U4G	0.55	6BQ7	0.65	6J6	0.35	12CU6	0.90	EF184	0.40	KT66	2.95	PL509	1.30	UF85	0.50
5U8	0.75	6BR7	1.20	6J7	0.65	12E1	3.75	EF800	2.00	KT88	3.25	PT4	1.00	UF89	0.50
5V4G	0.85	6BR8	1.00	6JS6B	1.30	12FSGT	0.55	EFL200	1.25	KTW61	1.50	Y31	0.50	UL41	0.70
5W4GT	0.85	6BK7B	0.60	6K4F	0.60	12F8	0.70	EH90	0.60	PC86	0.65	Y33	0.65	UL84	0.70
5X4G	0.80	6BU8A	0.85	6K5GT	0.70	56T0	0.40	EH91	0.45	PC88	0.65	Y81	0.45	UM80	0.50
5Y3GT	0.65	6BW6	1.00	6K6GT	0.80	12J5GT	0.40	EH92	0.40	PC92	0.65	Y82	0.45	UM81	0.75
5Z4G	0.85	6BW7	1.00	6K8GT	0.55	12J7GT	0.70	EH93	0.40	PC95	0.70	Y83	0.50	UM84	0.60
9/30L2	0.90	6BX7GT	1.20	6L6GT	0.80	12K7GT	0.60	EL36	0.60	PC96	0.50	Y88	0.50	UY11	0.60
6AB4	0.50	6BZ6	0.55	6L18	0.60	12K8	0.70	EL41	0.80	PC97	0.55	Y90A	1.10	UY11	0.60
6AC7	0.60	6BZ7	0.70	6LD20	0.60	12Q7GT	0.55	EL42	1.20	PC98	0.55	Y90B	0.50	UY41	0.55
6AG5	0.35	6C4	0.60	6Q7	0.60	12S7GT	0.55	EL81	0.80	PC94	0.45	Y801	0.35	UY42	0.55
6AG7	0.60	6CSGT	0.80	6S4A	0.85	12SF7	0.65	EL82	0.60	PCC85	0.45	U25	1.00	UY82	0.60
6AH6	0.70	6C85A	1.75	6SA7	0.55	12SG7	0.55	EL83	0.60	PCC88	0.65	U26	0.85	UY85	0.45

FULLY GUARANTEED



VALVES

35A3	0.70	6146B	4.00	EB41	1.00	6146B	4.00	EB41	1.00
35B5	0.70	6360	1.40	EBC33	0.70	6360	1.40	EBC33	0.70
35C5	0.70	6870	3.50	EBC41	0.75	6870	3.50	EBC41	0.75
35D5	0.80	6938	3.50	EBC51	0.40	6938	3.50	EBC51	0.40
35L5GT	0.90	7360	4.00	EBF80	0.45	7360	4.00	EBF80	0.45
35W4	0.60	7551	2.50	EBF83	0.50	7551	2.50	EBF83	0.50
35X4	0.60	7586	3.00	EBF89	0.40	7586	3.00	EBF89	0.40
35Z3	0.80	7587	3.00	EBL1	1.00	7587	3.00	EBL1	1.00
35Z4GT	0.70	7591A	1.20	EBL21	1.00	7591A	1.20	EBL21	1.00
35Z5GT	0.80	7895	3.00	EBL31	3.00	7895	3.00	EBL31	3.00
50B5	0.85	8055	1.50	ECS6	0.75	8055	1.50	ECS6	0.75
50C5	0.70	9002	0.55	ECS8	0.75	9002	0.55	ECS8	0.75
50CD6G	1.20	9003	0.70	EC91	2.60	9003	0.70	EC91	2.60
50EH5	0.85	DK92	1.00	ECC34	0.80	DK92	1.00	ECC34	0.80
50L6GT	1.00	DK96	0.75	ECC40	0.80	DK96	0.75	ECC40	0.80
607	0.65	DL66	1.25	ECC81	0.45	DL66	1.25	ECC81	0.45
608	1.50	DL91	0.40	ECC82	0.38	DL91	0.40	ECC82	0.38
609	1.00	DL92	0.50	ECC83	0.38	DL92	0.50	ECC83	0.38
610	0.50	DL93	0.60	ECC84	0.35	DL93	0.60	ECC84	0.35
611	1.20	DL94	0.80	ECC85	0.45	DL94	0.80	ECC85	0.45
612	1.50	DL95	0.75	ECC86	1.25	DL95	0.75	ECC86	1.25
613	0.55	DL96	0.85	ECC88	0.50	DL96	0.85	ECC88	0.50
614	1.00	DM70	0.70	ECC199	0.80	DM70	0.70	ECC199	0.80
615	0.80	DM160	1.20	ECC807	1.00	DM160	1.20	ECC807	1.00
616	1.50	DY51	0.65	ECC80	0.45	DY51	0.65	ECC80	0.45
617	0.80	DY55	0.42	ECC82	0.45	DY55	0.42	ECC82	0.45
618	2.50	DY802	0.47	ECCF6	0.75	DY802	0.47	ECCF6	0.75
619	4.00	EAC280	0.48	EFC801	0.75	EAC280	0.48	EFC801	0.75
620	0.75	EAC291	0.35	EFC802	0.75	EAC291	0.35	EFC802	0.75
621	0.75	EAF42	0.70	ECH21	1.00	EAF42	0.70	ECH21	1.00
622	3.75	EAF801	0.65	ECH42	0.85	EAF801	0.65	ECH42	0.85

OUR 1975 CATALOGUE/PRICE LIST IS AVAILABLE AND WILL BE POSTED ON RECEIPT OF A P.O. for £0.20.

ALL PRICES ARE EXCLUSIVE OF V.A.T. WHEN REMITTING CASH WITH ORDER PLEASE ALLOW £0.15 IN £ FOR HANDLING AND POSTAGE SUBJECT TO A MINIMUM CHARGE OF £0.20.

ERSIN

Multicore

5 CORE SOLDER

for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser

A coil of Ersin Multicore Savbit Solder in a dispenser 7 1/2 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm).

Size 12 £1.72

ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32

Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44

For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

NEW BIB WIRE STRIPPER & CUTTER

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B. 80p

NEW SOLDER WICK

Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited, Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 15p P&P. Prices and special offers subject to change without notice.

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at a mutilated condition or in any unauthorised cover by way of Trade or mixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

CHROMASONIC electronics

Dept 3 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C-MOS

74 TTL

LINEAR I.C.'s

	1-24	25-99	100up
CD4000AE	23p	19p	15p
CD4001AE	23p	19p	15p
CD4002AE	23p	19p	15p
CD4006AE	£1.59	£1.33	£1.06
CD4007AE	23p	19p	15p
CD4008AE	£1.75	£1.46	£1.17
CD4009AE	Use	CD4049	
CD4010AE	Use	CD4050	
CD4011AE	23p	19p	15p
CD4012AE	23p	19p	15p
CD4013AE	69p	58p	46p
CD4014AE	£1.75	£1.46	£1.17
CD4015AE	£1.75	£1.46	£1.17
CD4016AE	69p	58p	46p
CD4017AE	£1.75	£1.46	£1.17
CD4018AE	£2.51	£2.09	£1.67
CD4019AE	80p	66p	53p
CD4020AE	£1.97	£1.64	£1.31
CD4021AE	£1.75	£1.46	£1.17
CD4022AE	£1.83	£1.53	£1.22
CD4023AE	23p	19p	15p
CD4024AE	£1.26	£1.05	84p
CD4025AE	23p	19p	15p
CD4026AE	£2.79	£2.33	£1.86
CD4027AE	98p	82p	65p
CD4028AE	£1.53	£1.28	£1.02
CD4029AE	£1.12	£1.76	£1.41
CD4030AE	71p	59p	47p
CD4035AE	£1.75	£1.46	£1.17
CD4040AE	£2.01	£1.68	£1.34
CD4042AE	£1.49	£1.24	99p
CD4049AE	69p	58p	46p
CD4050AE	69p	58p	46p
CD4051AE	£2.78	£2.32	£1.85
CD4052AE	£2.78	£2.32	£1.85
CD4056AE	£2.12	£1.76	£1.41
CD4060AE	£2.51	£2.09	£1.67
CD4066AE	£1.13	94p	75p
CD4068AE	28p	24p	19p
CD4069AE	28p	24p	19p
CD4070AE	28p	24p	19p
CD4071AE	28p	24p	19p
CD4077AE	71p	59p	47p
CD4081AE	28p	24p	19p
CD4082AE	28p	24p	19p
CD4085AE	£1.28	£1.06	85p
CD4086AE	£1.28	£1.06	85p
CD4093AE	£1.56	£1.20	£1.04
CD4099AE	£2.95	£2.46	£1.96

	1-24	25-99	100+
7400	14p	12p	10p
7401	14p	12p	10p
7402	14p	12p	10p
7403	15p	12p	10p
7404	16p	13p	11p
7408	16p	13p	11p
7409	16p	13p	11p
7410	16p	13p	11p
7413	29p	24p	20p
7417	27p	22p	20p
7420	16p	13p	11p
7421	27p	22p	18p
7423	16p	13p	11p
7427	27p	22p	18p
7430	16p	13p	11p
7432	27p	22p	18p
7437	27p	22p	18p
7441	75p	62p	50p
7442	65p	55p	43p
7445	85p	71p	57p
7447	95p	83p	67p
7447A	95p	83p	67p
7448	85p	71p	57p
7470	30p	25p	20p
7472	25p	21p	17p
7473	30p	25p	20p
7474	32p	26p	21p
7475	47p	39p	31p
7476	32p	26p	21p
7482	75p	62p	50p
7485	£1.30	£1.09	87p
7486	32p	26p	21p
7489	£3.56	£2.80	£2.10
7490	49p	40p	32p
7491	65p	55p	45p
7492	57p	46p	36p
7493	49p	40p	32p
7495	67p	55p	45p
74100	£1.08	89p	72p
74107	35p	28p	22p
74121	34p	28p	22p
74122	47p	39p	31p
74141	78p	63p	51p
74145	68p	58p	48p
74154	£1.75	£1.48	86p
74174	£1.00	83p	67p
74180	£1.06	88p	71p
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p
74193	£1.35	£1.14	90p
74196	£1.64	£1.34	99p

555 (8 pin dip) V	55p	7824UC (TO-220)	£1.84	MC1303L	£1.84	SN76003N	£3.30
555 (TO-99) T	81p		£1.72	MC1306P	80p	SN76013N	£1.98
556 (14 pin dip)	£1.29	ICL8038	£3.52	MC1310P	£2.39	SN76023N	£1.98
703 (RF/IF Amp)	59p	AY-1-0212	£6.93	MC1312	£2.42	SN76227N (MC1327)	£1.89
709 (8 pin dip)	38p	AY-1-5051	£1.44	MC1314	£4.13	SN76532N	£1.88
709 (TO-99)	45p	AY-5-1224	£3.95	MC1315	£4.62	SN76544N	£1.81
709 (14 pin dip)	39p	AY-5-3500	£6.59	MC1327	£1.12	SN76550-2 (TAA550)	89p
710 (8 pin dip)	39p	AY-5-4007	£7.94	MC1330P	83p	SN76552-2	81p
710 (TO-99)	45p	BHA0002	£3.01	MC1350	64p	SN76660N (TBA120)	75p
710 (14 pin dip)	44p	CA2111	£1.19	MC1351	88p	SN76666N (CA3065)	£1.12
711 (TO-99)	51p	CA3045	£1.69	MC1352	88p	TAA263	£1.50
711 (14 pin dip)	44p	CA3046	88p	MC1357	£1.52	TAA300	£2.16
720 (A.M. Radio)	£1.76	CA3053	59p	MC1358 (CA3065)	£1.16	TAA310A	£1.87
723 (TO-99)	£1.09	CA3065	£1.60	MC1375	£1.48	TAA320	£1.44
723 (14 pin dip)	74p	CA3075	£1.64	MC1455 (555T)	62p	TAA350	£2.43
741 (8 pin dip)	36p	CA3078	£1.26	MC1456CG	£1.88	TAA370	£3.40
741 (TO-99)	43p	CA3080	59p	MC1458CP1	84p	TAA550	75p
741 (14 pin dip)	36p	CA3081	£1.86	MC1468G	£2.18	TAA570	£2.74
747 (14 pin dip)	£1.04	CA3082	£1.86	MC1495L	£4.24	TAA700	£5.03
748 (8 pin dip)	42p	CA3089E (TDA1200)	£2.43	MC1496G	96p	TBA1205	£1.25
748 (TO-99)	51p	CA3097E	£1.67	MC3302P	£1.50	TBA231	£1.02
748 (14 pin dip)	49p	CA3123E	£1.76	MC3401P	74p	TBA281 (723)	£2.59
753 (F.M. 1st. I.F.)	£1.08	CA3401E (LM3900)	68p	MFC4000B	87p	TBA500Q	£3.16
75491	88p	CA3600E	£1.44	MFC4060A	79p	TBA520Q	£3.85
75492	£1.10	CA3700T	£5.34	MFC6030A	99p	TBA530Q	£3.27
Regulators 100mA	80p	LO05TI (TO-3)	£1.46	MFC6040	96p	TBA540Q	£3.72
78105WC (TO-92)	60p	L036TI (TO-3)	£1.46	MFC6070	£1.66	TGA550Q	£5.29
78115WC (TO-92)	60p	L037TI (TO-3)	£1.46	MMS314	£4.80	TBA560CQ	£5.29
Regulators 100mA	80p	LM301T (TO-99)	65p	MMS316	£9.99	TBA625A	£1.03
78105AVC	90p	LM301S (8 pin dip)	65p	MVR12V (TO-3)	£1.45	TBA625B	£1.03
78112AVC	90p	LM301A T (TO-99)	67p	MVR15V (TO-3)	£1.45	TBA625C	£1.03
78115AVC	90p	LM301A S (8 pin dip)	59p	NE540L	£1.45	TBA651	£1.87
Regulators 500mA	59p	LM301A T (TO-99)	67p	NE546A	£1.25	TBA720Q	£2.79
78M05HC	£1.35	LM301A S (8 pin dip)	59p	NE558B	£5.06	TBA750Q	£2.79
78M12HC	£1.35	LM307 T (TO-99)	59p	NE561B	£5.06	TBA800	£1.11
78M15HC	£1.35	LM307 S (8 pin dip)	57p	NE562B	£5.06	TBA810S	£1.24
78M18HC	£1.35	LM308 T (TO-99)	£1.96	NE563	£2.96	TBA810AS	£1.24
78M24HC	£1.35	LM308 S (8 pin dip)	98p	NE565N	£2.63	TBA820	86p
Regulators 1A	£2.09	LM308A T (TO-99)	£7.92	NE566V	£1.87	TBA920Q	£4.71
7805KC (TO-3)	£2.09	LM308A S (8 pin dip)	£6.90	NE567	£2.63	TCA720Q	£5.24
7812KC (TO-3)	£2.09	LM309K	£2.34	SL414A	£2.09	TCA760	£2.16
7815KC (TO-3)	£2.09	LM339	£2.25	SL415A	£2.75	TCA800Q	£7.24
7818KC (TO-3)	£2.09	LM337N	£2.85	SL437D	£7.50	TCA830S	£1.04
7824KC (TO-3)	£2.09	LM371	£2.08	SL440	£2.84	TCA940	£2.25
Regulators 1A	£1.72	LM372N	£1.99	SL610C	£2.03	TDA1054	£1.50
7805UC (TO-220)	£1.72	LM373N	£2.99	SL612C	£2.03	TDA1200	£2.43
7812UC (TO-220)	£1.72	LM377N	£2.71	SL613C	£4.31	TDA1405	80p
7815UC (TO-220)	£1.72	LM380	£1.25	SL620C	£3.06	TDA1412	80p
7818UC (TO-220)	£1.72	LM381	£1.85	SL621C	£3.06	TDA1415	80p
		LM382	£1.66	SL622C	£7.62	TDA2010	£3.00
		LM382	£1.66	SL623C	£5.57	TDA2020	£3.75
		LM703	£1.03	SL624C	£1.87	ULN2111A	£1.92
		LM1820	£1.03	SL630C	£3.75	ZN4121	£1.26
		LM2111	£1.12	SL640C	£3.75		
		LM3900	69p	SL641C	£3.75		
				SL645C	£3.75		
				SL650C	£9.85		
				SN75491N	88p		
				SN75492N	£1.10		
				SN76001N (TAA611)	£1.82		

SIEMENS LCD's

LINE-O-LIGHT

LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing. Ref AN4132R 13mm character height. Can be directly driven by National Semiconductors Alarm Clock chip MM5316. £13.99



NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20pin dual-in-line package. Ideal for solid state analogue meters or dials. Type 101 RED £2.26



PHOTO-DARLINGTON


SPECIAL PURCHASE

SEVEN SEGMENT DISPLAYS

2N5777
V_{ceo}: V_{ceo} 25v, V_{ebo} 8v
V_{ceo}: V_{ceo} 25v, V_{ebo} 8v
I_{fe} 2500; I_c 250 mA **35p.**

enables
LIT707 90p; LIT747 £1.99
0.3" 0.6"

litronix
Xeilon
Monsanto

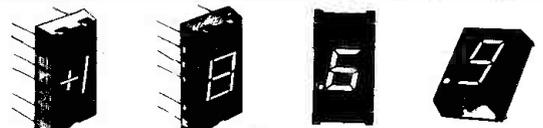

I.C. SOCKETS
Dual-in-line IOS
Pins 8 14 16 24 28 36 40 8 10
Price 13p 15p 15p 26p 30p 39p 44p 31p 35p

NEW
Litronix Double Digit Displays
0.5"; Common Anode + 2 R/H
D.P.'s
DL721 gives ± 1.9
DL727 gives 0.0 to 9.9
Suitable for Clocks; Instruments;
T.V. Channel Indicator
Our Price £4.75 each

L.E.D.'s
Free snap-on plastic retainer

	0.125" dia. lens (TIL209)	0.16" dia. lens	0.2" dia. lens (MLED 650)
Red	16p 15p 13p	27p 24p 22p	18p 16p 14p
Green	27p 24p 22p	33p 30p 27p	30p 27p 25p
Orange	27p 24p 22p	33p 30p 27p	30p 27p 25p
Yellow	34p 31p 29p	35p 32p 29p	35p 33p 30p

NOTICE
Postage & Packing Charges
With the recent increase in postal charges and a continuing increase in packaging cost we have been forced to review our policy.
Henceforward:
1. Orders valued at £5 or more will be post free.
2. All U.K. 'small package' orders will go first class mail.
3. Minimum postage & packing charge will increase to 20p.


	COMMON ANODE R/H Dec. Pt.	COMMON ANODE L/H Dec. Pt.	COMMON ANODE I Dec. Pt.	COMMON CATHODE R/H Dec. Pt.	Our Price
0.3"	RED DL707P	DL707	DL701	DL704	£1.82
	GREEN MAN51	MAN52	MAN53	MAN54	£1.82
	RED MAN71	MAN72	MAN73	MAN74	£1.82
	YELLOW MAN81	MAN82	MAN83	MAN84	£1.82
	ORANGE MAN3610	MAN3620	MAN3630	MAN3640	£1.82
0.4"	GREEN XAN51	XAN52	-	XAN54	£1.49
	RED XAN71	XAN72	-	XAN74	£1.49
	YELLOW XAN81	XAN82	-	XAN84	£1.49
0.6"	GREEN MAN4510	MAN4520	MAN4530	MAN4540	£2.32
	RED MAN4710	MAN4720	MAN4730	MAN4740	£2.32
	YELLOW MAN4810	MAN4820	MAN4830	MAN4840	£2.32
	ORANGE MAN4610	MAN4620	MAN4630	MAN4640	£2.32
	C.A. L/H Dec. Pt.	C.A. L/H Dec. Pt.	C.C. L/H Dec. Pt.	C.C. L/H Dec. Pt.	
	RED DL747	DL746	DL750	DL749	£2.42

VAT INCLUDED

Items marked with a • Include 8% VAT
Items unmarked include VAT at 25%

Illustrated below are some of the products that TOKO make for wireless manufacture. These and other TOKO products are available from Ambit, together with many linear and discrete semiconductor devices specializing in radio and audio applications. Full catalogue 40p.

wireless tecknowledgedgy from TOKO

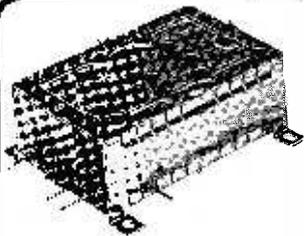

Varicap FM tunerhead:

The EF5603 represents the top of the range in TOKO FM tuner modules. With 5 double varicap tuned circuits, and dg MOSFET RF stage, the performance is really excellent. (12v supply) 1-24 £9.05 each



Coils for VHF RX/TX's

S18 are fully molded coils, complete with cores. A wide range of custom types with up to two taps is available - standard types for VHF are available ES. 1-24 18p each




Ceramic IF filters

Similar to Murata and Verritron types, these ceramic filters are the easiest way to achieve FM IF selectivity. Two per set are required. 1-24 40p each



6 pole linear phase filter

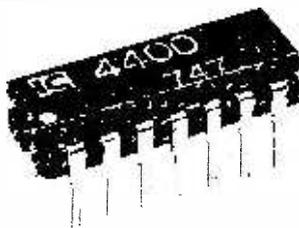Centered on 10.7MHz, this linear phase filter offers all the necessary selectivity for the construction of a Hi Fi FM stereo tuner. 1-24 £2.25 each



ICs for IF, decoder

The popular 1310, and 3089 types for FM MPX. 1310/4400 1-24 2.20 each 3089/4402 1-24 1.94 each



19 & 38 kHz notch filter

BLR3107 filters will remove the interference that causes annoyance when listening to or recording from MPX transmissions on FM. 1-24 £1.60ea




7BA Low cost RF choke

Miniature chokes 1uH to 1mH. Useful for all low power decoupling applications in RF circuits, logic circuits, filter circuits etc. Stock values 1, 4.7 and multiples through to 1mH. Custom orders 1000 min. for other values 1-24 15p ea



10K coils for HF/VHF

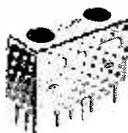The ideal coil for all FM and TV IF applications. Excellent stability - available from a very broad 'shelf stock' range, and also to exact custom specs., where a min. of 1000 pcs applies. With or without an internal capacitor. 1-24 30p ea



CFT ceramic series AM IF filters

Low cost filters for use with IC or discrete circuits. Each unit includes an input/output matching transformer. For 455 and 470 kHz BW 6kHz. CFT 1-24 50p each, or slightly larger with higher Q: CFU050 (470 kHz only) 1-24 55p each.



MFH mechanical 455kHz IF filters

Bandwidth 4 or 7 kHz, for IC and discrete IF strips. Includes input/output IFT for matching 5k/800 ohms. 1-24 £1.45 each



7P min MF/HF coils

Only 7mm square base area makes the 7P ideal for all miniature receiver circuits. Available as IFs and osc. for AM/FM. (AM IFTs are available ES.) 1-24 30p each



10E coils for AM/FM

The 10E is available in the broadest-range of stock types of all TOKO coils, covering applications in MF/HF radio and FM IFTs. Base area 10mm square. 1-24 27p each

Please address all enquiries and orders for 1000 pcs or less to the distributor, AMBIT international.

AMBIT international
37 High Street
Brentwood
Essex, CM14 4RH
tel 216029 tlx 995194

Please note TOKO UK have moved to larger premises at:

Ward Royal Parade
Alma Road
Windsor, Berks. SL4 3HR
tel 54057 tlx 848095

Terms: Min CWO £1.00, VAT extra
Post 20p per order (CWO)
Min invoice £7.50 pp 50p.

PRACTICAL WIRELESS

SIMPLE HOME PROJECTS

8 PAGE SUPPLEMENT No.1

OCTOBER 1975

CONTENTS

IC TUNER	1
MEMO REMINDER	3
RAIN WARNING BLEEPER	4
SIMPLE SIGNAL INJECTOR	5
SIGNAL BOOSTER	6
DOOR ALARM	7

ALL these projects are fairly easy to build. The layout of components is not critical except, perhaps, the IC Tuner where the design should be followed and wiring kept as short as possible. As the tuner uses a ferrite rod aerial it is important to rotate the unit as a whole for best reception from a particular station. A metal case must **NOT** be used with this project or the signal strength will be severely reduced.

If a metal case is used for any of the other designs care must be taken to see that short-circuits do not occur to the wiring. For this reason a plastic tube is recommended for the Signal Injector, where space is at a premium.

Much of the wiring can be done using the existing leads on resistors, capacitors and other components. Otherwise, use 22SWG tinned copper wire or thin insulated bell wire.


Take special care when soldering transistors. See that the leadouts are scraped clean and use a minimum of heat to make the joints.

In general, a particular transistor may be replaced with another of similar characteristics provided it is of the same type, that is, PNP for PNP. The following are some of those in the same PNP group:—OC42, OC71, AC128 and NKT251 while in the NPN group are:—BC107, BC108, BC109, BSY95A, 2N3704, 2N3904 and ZTX300. If a change is made to the type of transistor used in any of these circuits then a check must be made of the lead-out connections of the replacement transistor.

If a change of polarity is made to one of these circuits it will still work provided the transistor type is changed, as already noted, and that the polarity of any polarised (electrolytic) capacitor is reversed.

Note that there is no alternative for the ZN414 IC used in the Tuner project. The Tuner could be used on the long wave band by adding the appropriate coil on a ferrite rod and a simple changeover switch. Alternatively the input circuit of the Signal Booster may be employed, with an external aerial.

IC TUNER for audio amplifiers

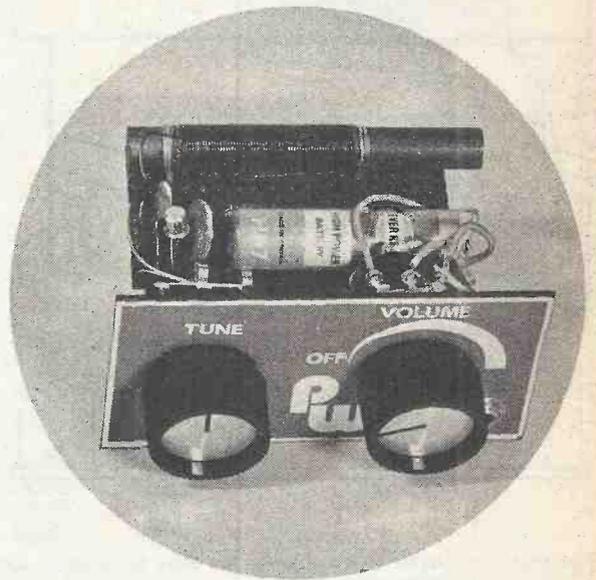


A single silicon integrated circuit provides several functions not normally available in TRF receivers.

Use this medium wave tuner with an audio amplifier or tape recorder to obtain excellent reception of local stations or to record radio programmes. It is self-contained, does not need an external aerial and only requires a screened lead equipped with a plug to suit your amplifier or recorder. It can also be used for local stations or personal listening of records by plugging in a high impedance headset or earpiece.


The ZN414 silicon "radio chip" provides RF amplification, automatic gain control and detection. The input signal is taken from the ferrite rod winding L1, and the audio output is taken to the level control VR1. This circuit has very few other components and it will be found to give excellent results provided one or two important points are

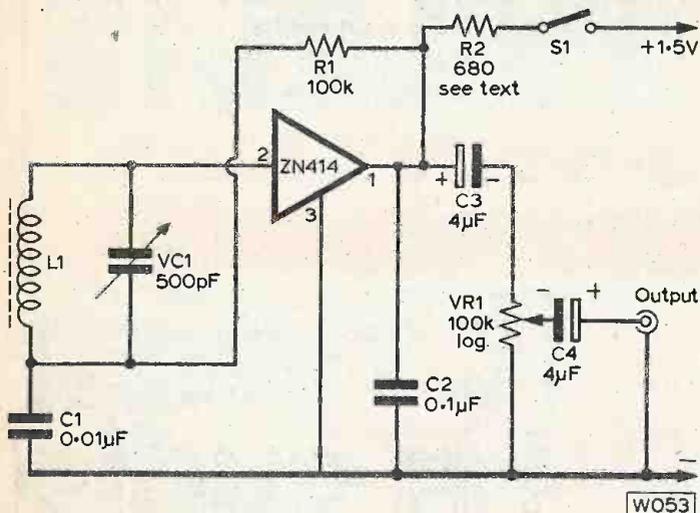not overlooked. Strong local signals can overload the ZN414, causing distortion. This can be avoided by turning the tuner so that pick-up by the ferrite rod aerial is reduced. In addition, the output is generally more than adequate, so that the associated audio equipment may be overloaded; avoided by setting the level control well back.



W053

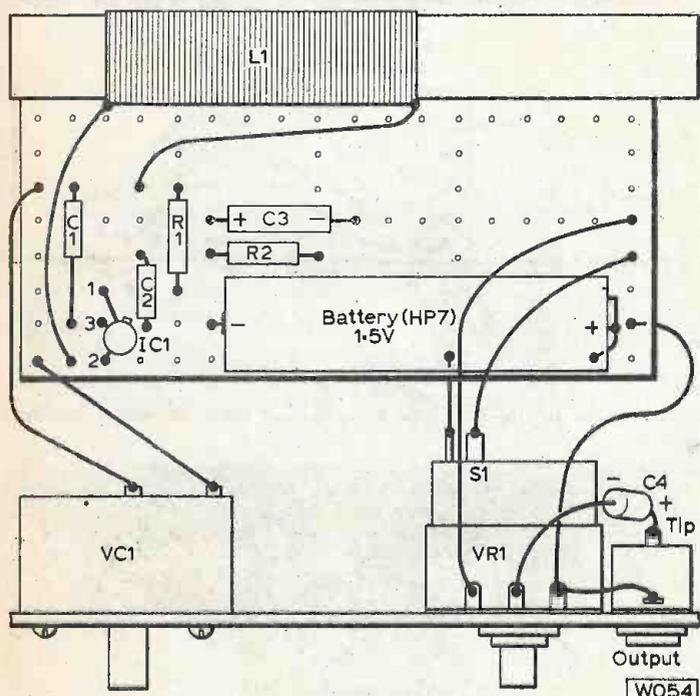The tuner circuit using the ZN414 IC. Under no circumstances must the supply voltage exceed 1.5V.



W054

Plan view of the layout of components. The board is connected to VC1 and S1 by heavy copper wires.

In terms of circuit adjustment, there is no alignment or similar procedure and the unit can be expected to work well immediately. For best possible results in all circumstances, and to compensate for variations in layout, it can be worthwhile to look at R2. This can be 470, 560, 680 or 820Ω but if the value is lower than optimum, whistles will accompany some stations. On the other hand, an unnecessarily high value reduces sensitivity. Initially, fit the value shown.


Components are fitted as shown. Note the cuts or drilling away of the foil conductors. The IC has its leads arranged as shown. Bring lead 3 between leads 1 and 2, avoiding any short circuit. The IC will then fit the holes as indicated which helps separate input and output circuits.

The aerial is sixty turns of 24SWG enamelled wire, close


Bits and Pieces

- R1 100kΩ 1W 5%
- R2 680Ω 1W 5%
- VR1 100kΩ log. potentiometer, with switch
- C1 0.01μF disc ceramic
- C2 0.1μF disc ceramic
- C3/4 4μF 6V
- IC ZN414

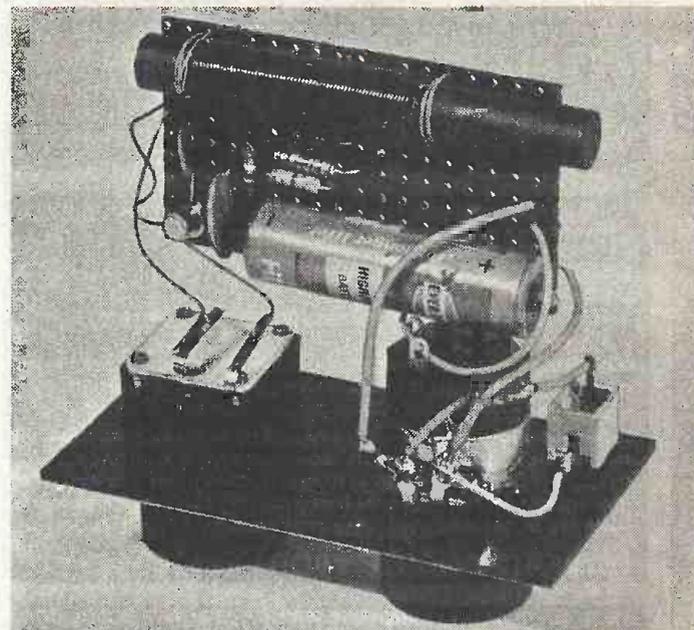VC1 Jackson Dialmin 500pF Veroboard 70 x 38mm (0.15in. matrix), 3.5mm jack socket. Knobs. HP7 cell. Ferrite rod, 9mm dia. 75mm long, 24SWG enamelled copper wire. Small panel, plastic or metal.



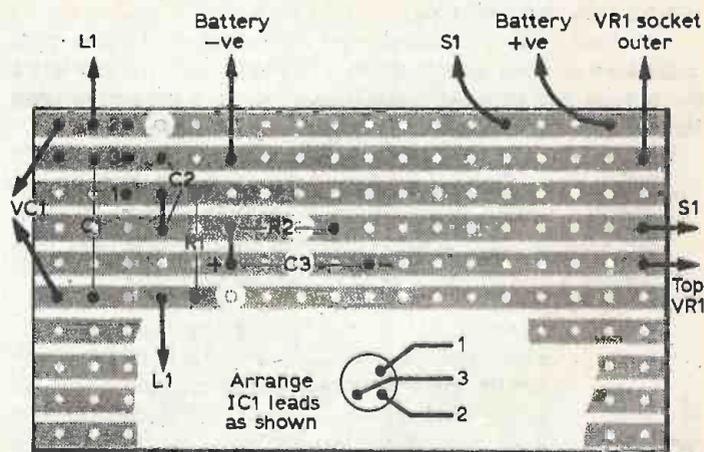General view of the tuner showing the rod aerial fixed to the board with fine thread.



70 x 38 mm (0.15in. matrix)

W055

Diagram showing breaks required on the veroboard before components are soldered in place.


wound on a 9mm diameter ferrite rod, 75mm long. The ends of the winding are secured with glued thread, which also holds the rod to the board. As battery drain is very small, wires are left projecting from the board and the battery is soldered to these. The outer case is negative. More than a single 1.5V cell *must not be used*. Clips could be fitted to take a battery, if preferred. The box or case must be of insulating material, with minimum internal dimensions approximately 75 x 65 x 40mm.

MEMO reminder



A slowly flashing lamp increases the battery life in this Memo Reminder.

This device is a flat plastic box provided with a note pad, normally left with the pad uppermost. When a message has to be left, if only "Back in five minutes", this is written on the pad and the device turned over. In this position, a lamp at the end of the case flashes on and off at about one second intervals, thereby drawing attention to the pad. This side of the case carries the message "I have left a note, please turn over." When the box is reversed to read the message, the flashing bulb is switched off.

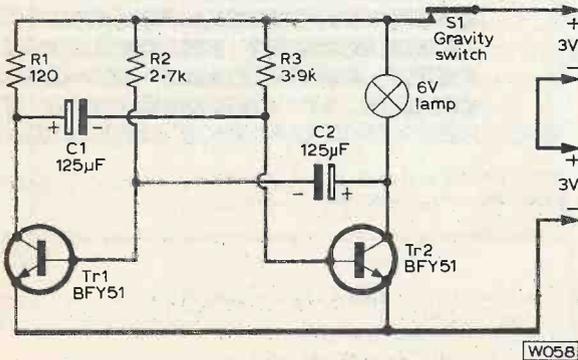


The simple multivibrator circuit is activated by the gravity switch S1. The operating current of the lamp should be as low as possible.



The circuit uses a two-transistor flip-flop oscillator, collector current of Tr2 passing through the lamp, which is a 6V bulb as used for cycle dynamo back lights and other purposes. The device will operate from 4.5 or 6V but here two 3V batteries are used for the supply.

Gravity switch S1 is operated by turning the case over


and it is made as shown from a piece of metal rod about 40mm long (sawn off a volume control shaft) and pivoted on a bolt, fixed with lock nuts to a bracket. When the box is in the flashing position this rod rests on a second bolt, completing the circuit. When the box is turned over to read the note the rod rests on the insulated top of the case. The contact bolt and swinging rod should be bright and

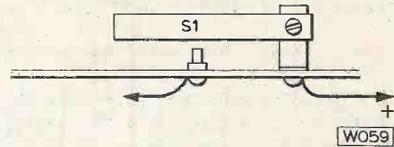

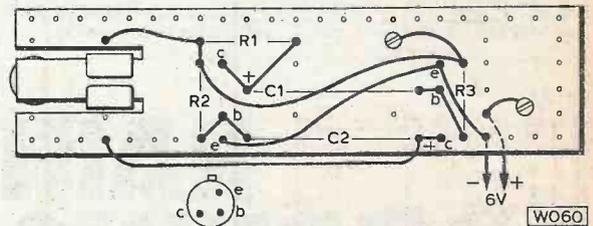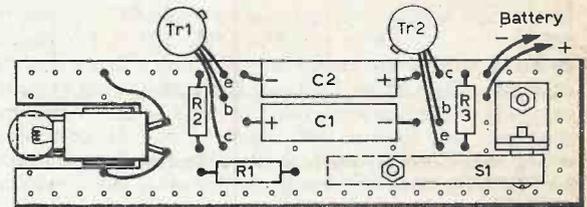Details of the gravity switch and bracket.



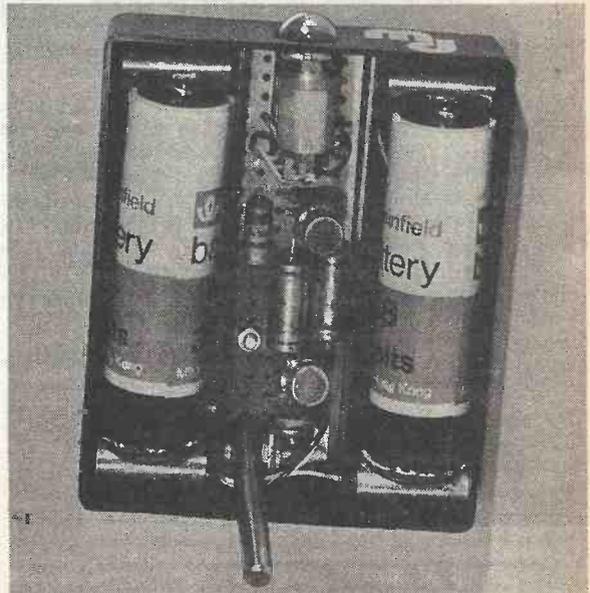Layout of the components on a piece of plain veroboard and associated wiring.



Inside the Memo Reminder showing the board in the centre and the gravity switch at the bottom, lifted up from its normal position to show the fixed contact.

Bits and Pieces


R1 120Ω ¼W 10%
 R2 2.7kΩ ¼W 10%
 R3 3.9kΩ ¼W 10%
 C1/2 125μF 10V
 Tr1/2 BFY51

Bulb and holder. Board. Plastic box and lid.
 Note pad to suit box.
 Batteries, 2 x 3V (U8) but see text.

clean and if the rod pivots freely it will be quite reliable.

The circuit is assembled on 0.15in perforated board about 90 x 22mm. The bulbholder is the type which has a clip that slips on the insulated board cut to accommodate it as shown. The holder may be slid along to place the bulb inside or outside the box. The box actually used (available from shops selling fishing tackle) is about 95 x 80 x 25mm and divided into three sections. This allows the circuit board to occupy the central section, with a U8 3V battery each side. Clips of tin, bent to a U shape, are cut to go at each end of the batteries, with the leads soldered on. The clips can be packed with foam rubber or otherwise arranged to keep pressure on the batteries. An additional lead passing from one battery to the other joins positive to negative.

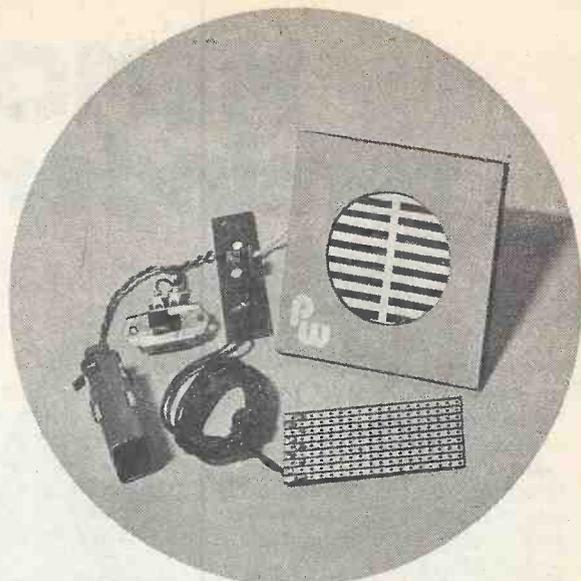A small scribbling pad to suit the box is held with elastic bands, which will also keep the lid on and finish the device. A pencil can also be attached. A box with a transparent lid allows the "turn over" instruction to be fixed inside.




The speaker, circuit board, switch and battery can be fitted into any convenient sized box, leaving the pad to be placed outside in the open.

somewhat on the pad resistance. In these circumstances the current is about 10 to 25mA. A switch allows the device to be turned off, as there are times when it will not be needed or when note has already been taken of the warning.

RAIN WARNING BLEEPER


One small spot of rain on the sense pad of this bleeper will start this audio warning that drying clothes may need to be brought in! It can also be operated by rising water, if the pad is hung at the level the water should reach.

The circuit has two transistors, with feedback via capacitor C1, but Tr1 cannot operate as long as the pad is dry. In these conditions battery current is zero, so a battery will last for a very long time. When the pad conducts Tr1 and Tr2 form an audio oscillatory circuit, the pitch depending

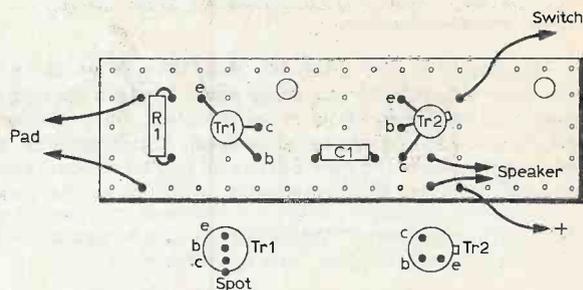

WO62

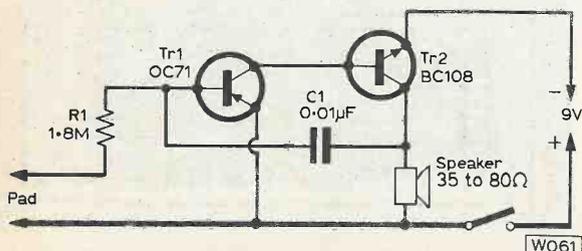Position of the components and foil side of the veroboard showing breaks required to be made before assembly.




The circuit of the Rain Warning Bleeper could hardly be simpler. Altering the values of R1 and/or C1 will change the tone.

Bits and Pieces

R1 1.8MΩ ¼W 10%
 C1 0.01μF disc ceramic
 Tr1 OC71
 Tr2 BC108

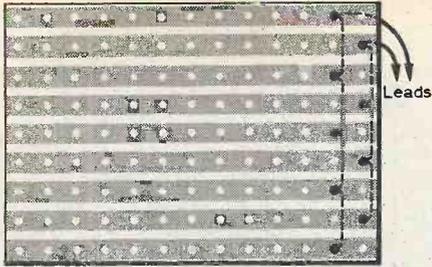On-off switch
 9V battery (PP3)
 Speaker, small size, approximate impedance 35 to 80Ω.
 Veroboard for oscillator and pad. Flex.
 Battery clips. Suitable box. see text.



W063


The size of the piece of veroboard used for the rain-detecting pad is not important but ensure alternate rails are connected as shown here.

First use a cutter or drill to break the foil sections where shown. The transistors and other components can then be inserted and soldered in place. Provide positive and negative flexible leads for the 9V battery, via the on-off switch, and for the speaker. A long, twin flexible lead is also required for the pad. The board is mounted by two bolts or screws in a case able to take the board, battery, speaker and switch.

The pad should have a minimum area of at least 30cm² with alternate foils connected together by wires on the insulated side of the board. The board is placed outside the house, foil side upwards. A touch with a moistened finger anywhere on the board should start the alarm.


capacitors, but C3 is a 150V tubular capacitor, to give isolation from any voltage likely to be encountered. The clip, on a flexible lead, provides an earth return, but this need not always be used.

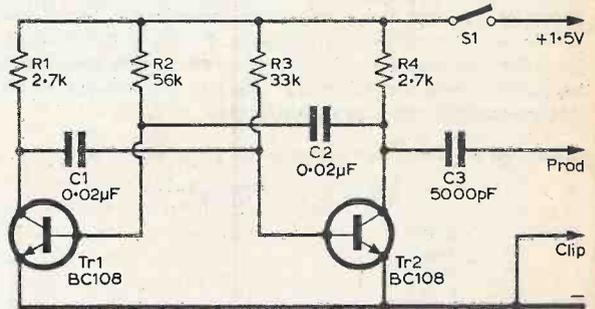Dimensions of the insulated case are not critical but anything smaller than about 65mm long and 35mm diameter may cause difficulty in fitting all the components. A slot is cut or filed in the lid and switch S1 fixed with two bolts




W056

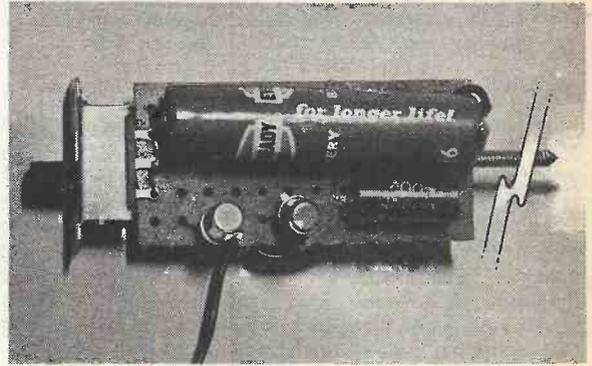The Signal Injector also uses a multivibrator circuit the output of which is very rich in harmonics.



The board is fixed to one set of contacts on the switch by wire passing through holes in the board. The other set of contacts is used for the on-off switch.

simple SIGNAL INJECTOR


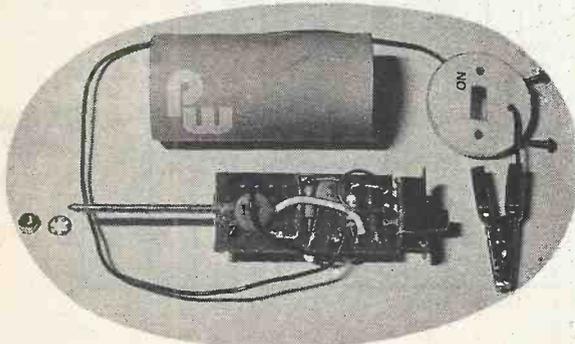


The finished Signal Injector ready to be fitted into its case, preferably a plastic one.

With this miniature signal generator a rapid check can be made of audio stages or the audio section of a radio receiver. Though an audible tone is produced, harmonics extend to much higher frequencies as is usual with circuits of this type, so that some tests can also be made for the intermediate frequency (IF) and other sections of a receiver.

Tests with the injector should only be made with battery operated receivers, as some types of mains equipment have a "live" chassis or dangerous voltages around.

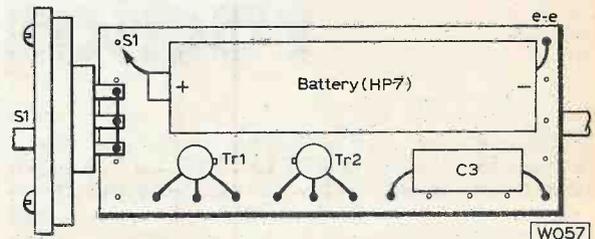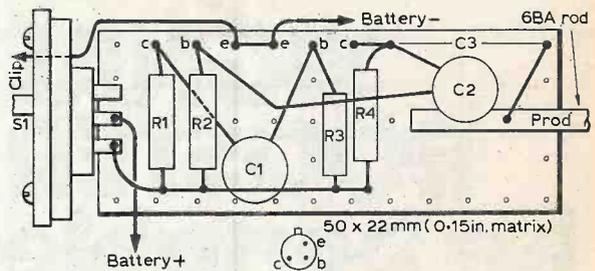In order to accommodate the components in a small cylindrical case, C1 and C2 are low voltage disc ceramic



W057

Having got the size of the board right the parts can be fitted as shown here. The battery wires are soldered to the battery contacts. A battery holder would take up too much space.

The small piece of insulated board can be attached to one set of unused tags on S1, with twisted wire, for support. At the other end the prod passes through a hole in the bottom of the container. The prod is 6BA threaded rod, secured with adhesive and a tight binding of thread, also smeared with adhesive, passing round it and through holes in the board. The tip of the prod is filed to a sharp point.

As battery drain is under 1mA, leads are soldered directly to the battery, outer case negative. If components are kept towards the middle, and close to the board, the whole will slip easily into the case. A lead with clip runs from the negative line. A nut on the rod outside holds this securely. Check that the metal cases of the transistors do not touch each other or anything else.

Bits and Pieces

- R1: 2.7k Ω
- R2: 56k Ω
- R3: 33k Ω
- R4: 2.7k Ω
- All resistors 1/4W 10%
- C1/2: 0.02 μ F disc ceramic
- C3: 5000pF 150V tubular
- Tr1/2: BC108


Battery, 1.5V (HP16). S1: Miniature slide switch, DPST or DPDT, Veroboard, Crocodile clip, 6BA threaded rod. Plastic tube and cap, see text.

When testing a circuit, work backwards, step by step, from the output stage. When the point at which a fault arises is passed, signals cease. The output of the injector is only sufficient to be just audible when taken directly to a speaker of 15 Ω or higher impedance. However, when the output stage and other amplifying stages are present, volume is greatly increased. The clip is generally taken to the equipment's "earth" line. In addition to locating a non-working stage, or break at a component, or in a winding the probe can also show if cracks exist in the foil conductors in AF sections of equipment. Remember to work step by step, taking in only one joint, foil conductor, coupling capacitor or other component at a time.


SIGNAL BOOSTER for portable radios

Many popular portable receivers cannot give enough volume from the weaker or more distant stations, especially during daylight hours. The unit described here is able to provide a considerable increase in signal strength and may even allow satisfactory reception of signals which are scarcely audible without its aid.

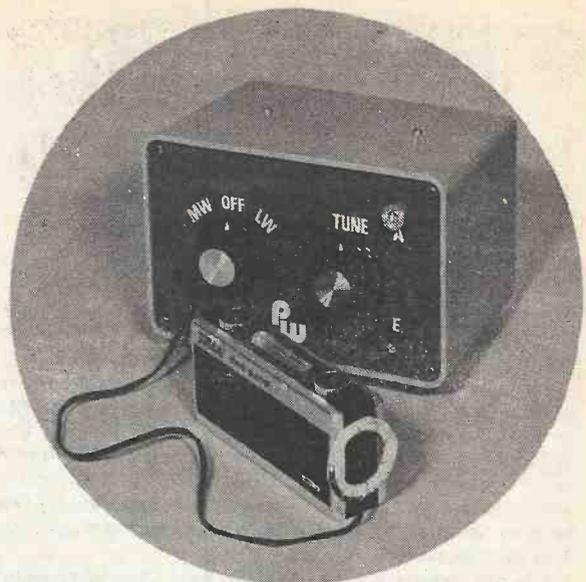Signals for the unit are obtained from an external aerial which may be an internal or external wire up to about



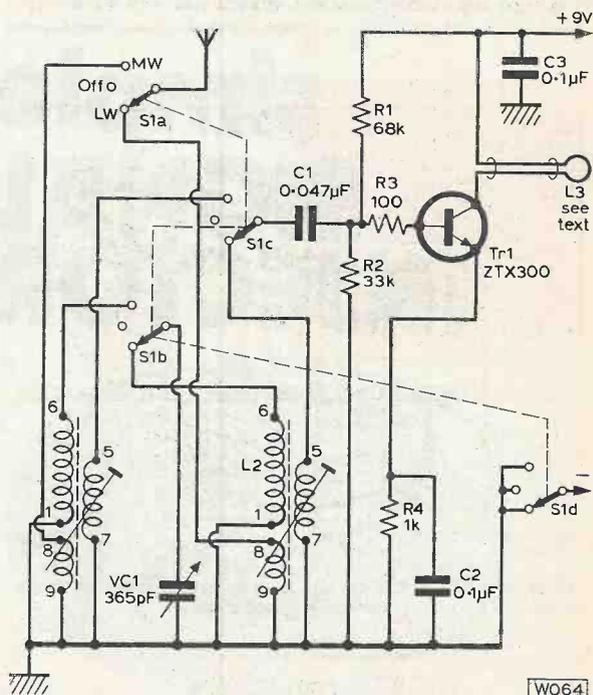Here the output coil of the Signal Booster is placed close to the internal aerial of the transistor radio.




Circuit of the Booster which uses a single transistor and an external aerial. An earth connection will often help to increase the signal even further.

5m long. A telescopic aerial may prove satisfactory if nothing else is available, but the wire aerial will give much better results.

Switch S1a selects the aerial coupling winding of the long wave coil L1 or the medium wave coil L2. Switches S1b and S1c similarly select the appropriate tuned and base coupling windings. Variable capacitor VC1 will peak the signal over the range selected. S1d is the on-off switch.

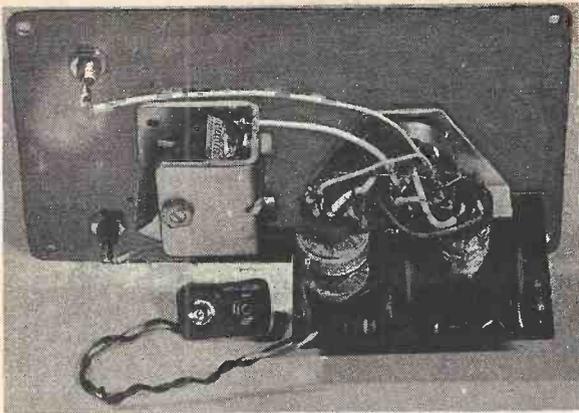
Coil L3 is a home-made 10 turn loop, about 25mm in diameter, wound with any fine insulated copper wire and



Rear view of the Booster showing circuit board fitted to the front panel via a metal bracket held under the wavechange switch.

bound with plastic tape. The coil is connected to a length of twin flexible lead or coaxial cable about 300mm long. The coil allows the coupling of the amplified signals to the ferrite rod aerial inside the receiver. Closest coupling occurs when the loop is slid on to the rod itself but it may be sufficient to place the coil outside the set with its turns parallel with the turns on the rod aerial.

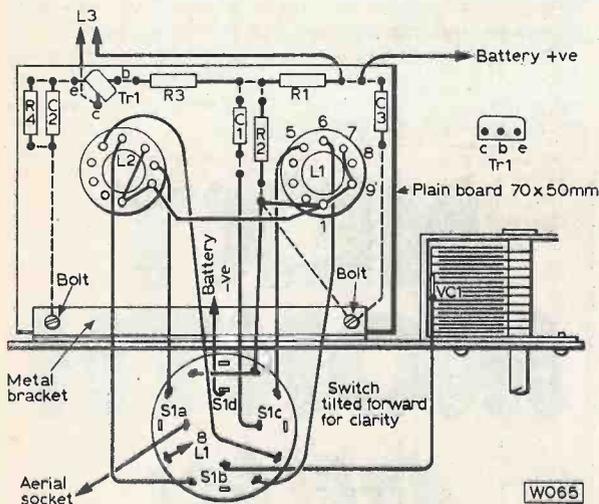A 150 x 100 x 100mm metal or plastic box with metal panel was used but the size is unimportant. The component



The parts should be laid out as shown here. The switch is, in fact, mounted on the vertical part of the metal bracket.

Bits and Pieces

- R1 68k Ω
- R2 33k Ω
- R3 100 Ω
- R4 1k Ω
- All resistors $\frac{1}{2}$ W 5%
- C1 0.047 μ F
- C2/3 0.1 μ F
- VC1 365pF variable
- Tr1 ZTX300
- S1 4-pole 3-way rotary wafer switch. Knobs. L1 Denco BLUE Range 1T. L2 Denco BLUE Range 2T. Case 150 x 100 x 100mm. Sockets. Battery 9V (PP3) and clips. Plain board. Wire for L3, see text. Twin flex.

board is bolted to a metal bracket fixed under the bush and out of the switch. When soldering to the pins on the coils scrape the pins clean and use a minimum of heat or the plastic former will soften. The aerial socket is insulated from the panel but the earth socket is connected to the panel.

The coupling of L3 to the receiver is a matter of trial and error and when it is correct there will be a marked increase in signal strength and VC1 will have a definite tuning point. Make sure that the unit is switched to the range required.

simple electronic DOOR ALARM


This unit replaces a door bell or buzzer and it runs economically from its own 9V battery. It is an easy and useful constructional project for a complete beginner. The circuit has numbered points which refer to the numbered tags of the tag-board. This should help anyone not familiar with electronic circuits to follow the theoretical circuit in conjunction with the actual wiring up of components.

Transistors Tr2 and Tr3 form a multivibrator and the audio tone produced is fed to the amplifier Tr1, by the coupling capacitor C1, which amplifies the tone for driving the loudspeaker.

The bell-push operates as an on-off switch so that no current is drawn until the push is operated. Pre-set potentiometer VR1 is a "pitch" setting control which allows the tone or frequency to be adjusted, but if two units are used for front and back doors the tones can be set at different frequencies. The push which has been operated can then be identified by the tone heard.

Bits and Pieces

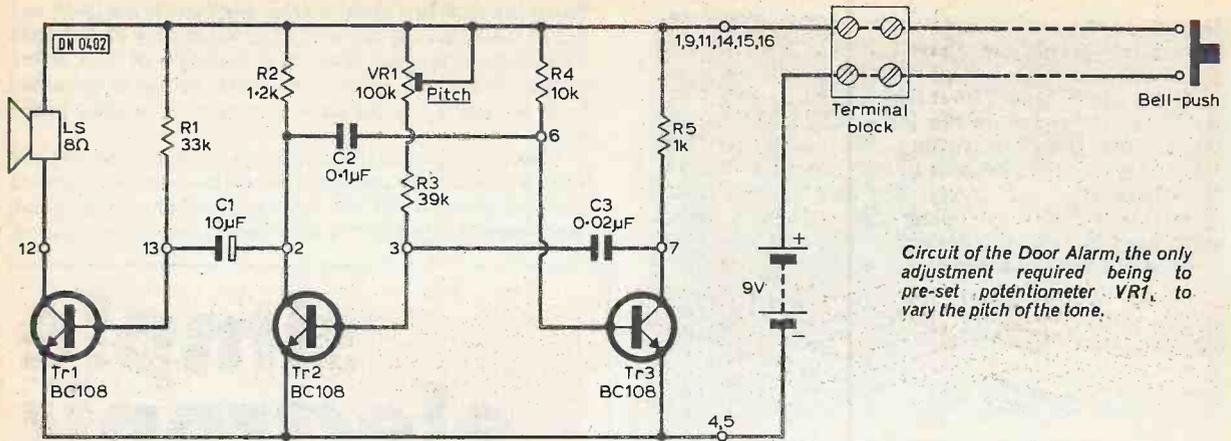- R1 33k Ω
- R2 1.2k Ω
- R3 39k Ω
- R4 10k Ω
- R5 1k Ω
- All resistors 10% $\frac{1}{2}$ W
- VR1 100k Ω miniature pre-set
- C1 10 μ F 10V
- C2 0.1 μ F
- C3 0.02 μ F
- Tr1 BC108
- Tr2 BC108
- Tr3 BC108
- PP6 9V battery and clips. Tagboard. Small speaker, approx. 8 Ω . Material for case. Bell-push. Bell-wire.



Circuit of the Door Alarm, the only adjustment required being to pre-set potentiometer VR1, to vary the pitch of the tone.


The wooden case used is intended to hang high up on a wall out of the way, and the front slopes downwards slightly. The case is 140mm square, 70mm deep at the top, sloping to 40mm at the bottom. All these parts can be of 4mm or similar plywood, but the dimensions are in no way critical. Cut a hole to suit the diameter of the speaker cone. The parts of the case are held together with glue, and panel pins if required. Strips or blocks of wood can be glued in to strengthen the corners. The case can be varnished or painted any colour to suit the decor. Glue fabric over the speaker opening and fix the speaker to the wall with a small metal tab.

Solder transistors, resistors and capacitors to the tagboard as shown. Transistor leads need not be cut down at all. If the soldering iron has reached its proper temperature, and is removed as soon as the joint is correctly made,

no damage to the transistors or other parts is likely from overheating.

One outer tag and the slider tag of VR1 are soldered to tags 9 and 11 to support this component. In most places bare wires can be arranged so that they are clear of each other. Elsewhere, insulated sleeving is put on connections, or insulated wire is used. When the board is finished, fix it as shown, with woodscrews. Spare nuts or other spacers are put on the screws to raise the board a little, to clear the edge of the speaker. See that the screws do not project through the front of the case. Alternatively, use 6BA screws through the tagboard and front of the case.

Only low-voltage bell wire need be used to the bell-push. A 2-way block allows these connections to be made without soldering. Cut a clip from scrap metal and screw it to the case to hold the PP6 9V battery.

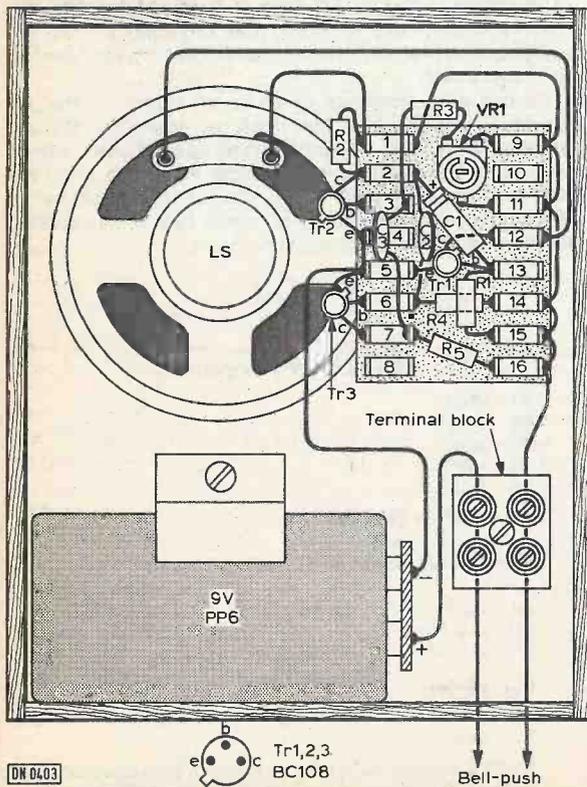

DN 0403

Physical layout of the alarm, the tag numbers on the board corresponding to those shown in the circuit diagram.

NEXT MONTH
another
8-PAGE
SUPPLEMENT
SIMPLEHOME
PROJECTS - 2