

PRACTICAL WIRELESS

JULY
1976

35p

A VERSATILE TRANSISTOR TESTER Part 1

Also:
VERTICAL
AERIALS
for 144 MHz
&
PREAMPLIFIER
for the PW
DISCO SYSTEM





TRAMPUS ELECTRONICS LTD

58-60 GROVE RD.,
WINDSOR, BERKS.
SL4 1HS.
TEL. 54525.

ADD 8% VAT TO PRICES MARKED *
ADD 12% VAT TO ALL OTHER PRICES
OR AS CURRENT VAT LEGISLATION
SEND C.W.O. (EXCEPT GOV'T DEPT)
POST & PACKING 20P FOR THE UK
ENGLAND & ACCESS BY POST,
OR £5 MIN ON TELEPHONE ORDERS.
CATALOGUE LIST FREE SEND SAE.
MONEY BACK IF NOT SATISFIED.

YOU WON'T BELIEVE OUR PRICES


FAST FAST SERVICE

NORMALLY 24 HOURS
ON EX STOCK ITEMS.

QUALITY PRODUCT

FULL SPEC. DEVICES,
NO REMARKS, REJECTS,
OR FLOORSWEEPINGS.

ADD VAT
TO PRICES

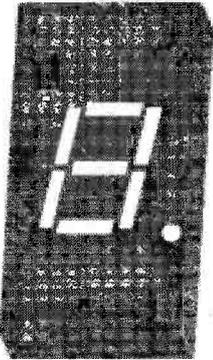

OPTO ELECTRONICS

ALL FULL SPECIFICATION LED
DL707 LITRONIX COM ANODE &
DL704 LITRONIX COM CATHODE
0,3" 0-9 & DEC POINT 89pea *
DL747 JUMBO DISPLAY 0,8"
LED 0-9 DP.COM ANODE £1.75 *
3015F FILAMENT DISPLAY £1.25*
DISCO ETC STROBE TUBE £5.ea*

RED LEDS 1/2"

209 STYLE OR 0,2" NO CLIP 11p*
TIL209 OR 0,2" RED. & CLIP 13p*
GREEN LED LARGE OR SMALL 22p*
ORANGE LARGE OR SMALL 22p*
ORP12 57p* 2N5777 33p*
TEC12 IC PHOTO DETECTOR 81p*

CMOS LOGIC

NEW MOTOROLA

CD4000	15p*	CD4028	73p*
CD4001	16p*	CD4046	£1 *
CD4002	16p*	CD4047	73p*
CD4009	45p*	CD4049	45p*
CD4011	17p*	CD4054	94p*
CD4013	45p*	CD4055	£1 *
CD4016	45p*	CD4060	90p*
CD4017	82p*	CD4071	17p*
CD4018	82p*	CD4081	17p*
CD4022	77p*	CD4510	£1.19*
CD4023	16p*	CD4511	£1.90*
CD4024	63p*	CD4528	£1.10*
CD4027	45p*	CD4558	£2.35*

DIGITAL CLOCKS

MM5314 £3.39*
MM5316 ALARM, £5*MM5311 £9.00*
AY51224 4DIGIT £3.49*PCB £1.*
LED DISPLAY PCB 4DIGIT 75p*

vero

36PINS 28p*FACE CUTTER49p*
COPPERCLAD 0,1 PITCH VERO
2 1/2"x5" 32p* 2 1/2"x3 1/2" 29p*
3 1/2"x5" 37p* 3 1/2"x3 1/2" 32p*
3 1/2"x17" £1.70*
3 1/2"x17" PLAIN 0,1" £1.06*
DIL BREADBOARD 6x4" £2*

DALO pen

DALO ETCH RESIST PEN 69p*
FEC ETCH PAK 500gm 89p*
6x4" COPPER BOARD 50p*
PCB KIT 3 ITEMS £2*

CASSETTE MECHANISM

FEW AVAILABLE TOP LOAD £15

TELEPHONE 54525

IC's LOW PRICES

703 RF/IF	26p	MC1303	£1.47
709 TO99	22p*	MC1310	£2.09
709 DIL 14	28p*	MC1312 SQ	£1.50
710 DIL 14	31p*	MC1318	£2.50
723 Regal 1r	45p*	MC1330	75p
741 DIL 8	20p*	MC1339	£1.49
741 DIL 14	31p*	MC1350/1/2	75p
741 TO99	31p*	MC1466 1W	£3
747 2x741	67p*	MFC4000 1W	59p
748 DIL 8	27p*	NE536 FETOPA	£2*
7805 5V	£1.39*	NE540	£1.10*
7812 12V	£1.39*	NE550 2vR	£1 *
7815 15V	£1.39*	NE555 TIMER	41p*
7900 Series	£3 *	NE556 2x"	84p*
78013 6W AF	75p	NE560. PLL	£4.00
CA3046	59p	NE561 PLL	£4.00
CA3048	£2.20	NE562 PLL	£4.00
CA3054	£2	NE563	£2.25
ICL8038	£2.69*	NE565	£2.50
LM300	£1.50*	NE566	£1.55
LM301 OPA	41p*	NE567	£2.20
LM304 0-40V	£3*	SN72741 741	20p*
LM308 H1 Bo	95p*	SN76660 IF	75p
LM309K 5V	£1.75*	SN76611 IF	£1
LM372 IF	£2.00	TAD100 1/2"	£2
LM377 2x2W	£3	TBA800	89p
LM380	60745 89p	TBA810 7WAF	80p
LM381	£1.50*	TBA820	£1.49
LM3900 40PA	63p*	2N414 RX	99p

TRANSISTORS

PRICE EACH:-		MATCHING	20p*
AC127 & 128	10p*	2N3055 SET	6p
AC176	15p*	TIP29 & 30	43p*
AC187 & 188	18p*	TIP31 & 32	54p*
AD149	45p*	TIP41	63p*
AD161 & 162	33p*	TIP42	67p*
BC107	8p*	TIP2955	99p*
BC107B	12p*	TIP3055	67p*
BC108	7p*	TIS43 UJCT	26p*
BC108B	12p*	ZTX107/8/9	11p
BC109	8p*	ZTX300 x304	20p
BC109C	12p*	ZTX500 x504	42p
BC147/8/9	9p	2N706 & 708	11p*
BC157/8/9	12p	2N2646 UJT	36p*
BC167/8/9	12p	2N2904 & 5	20p*
BC177/8/9	18p	2N2936b/ovg	9p
BC182/3/4A&L10p		2N3053	16p*
BC212/3/4A&L10p		2N3054	42p*
BCY70/1/2	16p*	2N3055 115W	37p*
BD131 & 132	39p*	2N3055 RCA	60p*
BFR88 250V	35p	2N3702/3/4/5	8p
BFY50	14p*	2N3706/7/8/9	8p
BFY51	14p*	2N3710 & 11	8p
BFT52 & 53	14p*	2N3819E FET	12p
BSX19/20/21	16p*	2N3820 FET	40p
MJ2955 TO3	75p*	2N3823E FET	16p
MJE2955	89p*	2N3904/5/6	15p
MJE3055	64p*	2N4289 mini	31p
MPU131 PUT	49p	2N5457 FET	45p

2N3055 37p

BC109 8p

BFY51 14p

FET3819 14p

741 8pin 20p

NE555 42p

7400N 9p



7400 series TTL IC's

7400N	9p*	7450/3/4	12p*	7491	60p*	74155	65p*
7401	10p*	7460	12p*	7492	43p*	74157	90p*
7402/3	11p*	7470	26p*	7493	38p*	74160/1	95p*
7404	13p*	7472	22p*	7495	58p*	74162/3	95p*
7405/6/7	25p*	7473/	26p*	7496	88p*	74164	£1.20
7406/8/10	9p*	7474	25p*	7498	£1 *	74165	£1.20
7411/12	20p*	7475	44p*	74107	30p*	74175	95p*
7413	26p*	7476	28p*	74120	£1 *	74180	£1 *
7417	27p*	7480	40p*	74121	26p*	74181	£2 *
7420/27	26p*	7481	95p*	74122	42p*	74185	£3 *
7430/32	16p*	7482	72p*	74123	58p*	74190	£1.40*
7440	12p*	7483	80p*	74141	64p*	74193	£1.10*
7441	64p*	7485	£1.20*	74143	£2 *	74195	75p*
7442	59p*	7486	33p*	74147	£2 *	74196	£1 *
7445	75p*	7489	£2.70*	74151	65p*	74197	£1 *
7447	67p*	7490	37p*	74194	£1.30*	74198/9	£2 *



CAPACITORS

CERAMIC 22pf to 0.1 uf 50V 5p.
ELECTROLYTIC, IN 10, 25 & 50V.
2UF/10V, 10, 50, & 100uf 25V
& 10V 7p ea, 50VOLT 10p ea.
1000 uf 25V 18p, 200/500uf 9p.

POTENTIOMETERS

LN OR LOG 2.2K to 1 MEG. 16p
PRESETS 6p. RESISTORS 1p ea 1W

AUDIBLE WARNING BLEEPER

12VOLT 35mA, SPARKLESS £1*

TGS GAS DETECTORS £2 ea†

LOGIC PROBE FOR TTL etc £5*

TRANSISTOR TESTER

TTC TESTS ALPHA, BETA Ico
NPN/PNP & DIODES NOW £13*

C1000 MULTIMETER £3.49*
BENCH POWER SUPPLY P1076
3-12V 1A ONLY £3.99 *
ALL ANTEX SOLDERING IRONS

HEATSINKS TO5/18 7p.*TO3 15p*

TV4 PLASTIC POWER 16p*

TO3 EXTRUDED 1" FINNED 39p*

DIN PLUGS ALL 12p. SOCKETS 9p.

ALL CASES AB5/AB7 50p* AB13 69p*

AB13 69p* AB9 59p* AB12 40p*

TRANSFORMERS 100mA 6,9 or 12V 89p*

1/2A/1A 6/12 or 12/24 £2 ea *

LOW NOISE NOT REJECTS.
C60 33p ea TEN FOR £2.70
C90 42p ea TEN FOR £3.65

DIODES

OAB1 & OA91 GERMANIUM 5p.
1N4001 1A50V & 1N4002 5p*
1N4004 6p* 1N4007 9p*
1N4148 & 1N914 SILICON 4p.
ZENERs BZY88 400mV 9p.
ZENERs 11W 17P, Z11000e11
BRIDGE RECTIFIER 1A50 18p
1A400V 25p, 4A100V 45p

SCR's TRIACS

SCR's TAG1/400 1A400V 40p*
1A50V 25p/1A 600V 65p*
C106D 4A400V SCR ONLY 47p*
TRIAC SC146D 10A 400V £1.
10A 400V Int.Diac £1.25*
16A 400V DISCO TRIAC £1.75*
16A 400V Int.Diac £2.*
DIACS: BR100 25p*

BULK OFFERS PER 100off each.

1N4001 £2.50* 1N4004 £3.50*
AC128 £10 * AC176 £12 *
BC107 £6.80* BC108 £6.80*
BC109 £7.00* 2N3055 £27 *
NE555 £37 * 741C(8)£18 *

BARGAIN PAKS

£1 ea. Full spec.

PAK A 10 RED LEDS our choice £1*
PAK B 5 741C OP AMP 8 PIN £1*
PAK C 4 2N3955 £1*, D 12 BC109£1*
PAK E 10 BC182 £1, F 11 2N3704 £1
PAK G 8 BFY51 £1*, H 9 2N3819e1*
PAK J 9 2N3053 £1*, K 40 1N914 £1
NEW PAK M 4 PLASTIC 3055 90W £1*

Oil sockets

TOP QUALITY NYLON
SOCKETS, HALF PRICE
8, 14, or 16 PIN 12p*

SOLDERCON PINS:
100 65p*1000 £3.50

SLIDER CLEARANCE WHILE
STOCKS LAST ALL 10p ea.



PRACTICAL WIRELESS

VOL. 52 NO. 3

ISSUE 833

JULY 1976

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metall

TECHNICAL EDITOR

Terry Carter

PRODUCTION & NEWS EDITOR

Colin Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Karen O'Neil

Jill Austin

ADVERTS MANAGER

01-261 6275

Roy Smith

CLASSIFIED ADVERTS

01-261 5762

Colin R. Brown

Advertisement correspondence and enquiries to the Advertisement Manager, Roy Smith, Practical Wireless, Kings Reach Tower, Stamford Street, London, SE1 9LS

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4444

BINDERS

Binders £2.10 and indexes 45p (inc. VAT) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

216 LEADER ARTICLE—One flew over the Citizen's Band

217 NEWS . . . NEWS . . . NEWS . . .

222 TELEVISION—contents of our 'sister' magazine

225 HOTLINES on recent developments

226 R.S.G.B. EXHIBITION

231 LETTERS—our readers comment

232 PRODUCTION LINES—*Colin Riches*

235 NEXT MONTH IN PRACTICAL WIRELESS

246 NEW BOOKS—read all about it!

252 NOTES ON PUBLISHED ARTICLES

254 P.W. READERS' PCB SERVICE

257 ON THE AIR—Amateur Bands—*Eric Dowdeswell, G4AR*
Broadcast Bands SW—*Derek Bell*
Broadcast Bands MW—*Charles Molloy*

● CONSTRUCTIONAL

218 VERTICAL AERIALS FOR 144 MHz—*F. C. Judd, G2BCX*

229 PREAMPLIFIER FOR THE P.W. DISCO SYSTEM—*C. Toms*

236 A VERSATILE TRANSISTOR TESTER, Part 1—*I. Hickman*

247 DIGITAL FREQUENCY METER, Part 2—*T. J. Johnston*

● OTHER FEATURES

230 TECHNICROSS No. 14—Puzzle

234 GOING BACK—Wireless of Yesteryear—*Colin Riches*

244 IC OF THE MONTH—LM1808 IF amplifier/FM detector/
audio package

253 STRAY SIGNALS—Point Contact

Get to the Point Quickly with ANTEX Model X25

prices include Vat & p extra as shown in brackets

Point 1

Near-perfect insulation. Breakdown voltage 1500 A.C. Leakage current 3.5 uA.

Point 2

Top efficiency in heat transfer. Element slides inside the soldering bit.

25 watts but equivalent in heat capacity to 60 watts.

Point 3

High grade phenolic handle (own moulding!) Stainless steel shaft. - 3 core 0.4mm

Flexible lead.

Point 4

Iron-coated bits that do not stick to the shaft but slide on and off easily. 3 tip sizes 2.4, 3.2 and 4.7mm.

Point 5

Price with standard (3.2mm.) bit £3.20 (P+P 0.22)

Spare elements £1.52 each
Spare bits £0.50 each incl. V.A.T

Point 6

A well balanced tool - length 22cm. weight 50gr.



STAND ST.3

High grade insulation material, chromium plated steel spring. Suitable for all our models. Replaceable springs, space for spare bits. Complete £1.37 (P+P 0.24)



From electrical, radio or car accessory shops or from Antex Ltd., Freepost (no stamp required) Plymouth. PL1 1BR Telephone 0752 63777/8

Please send the following: Name _____

ANTEX colour catalogue. Address _____

I enclose cheque/P.O./Cash (Giro No. 258 1000) _____

PW/7/76

RSC 100 WATT DISCO SYSTEM



DISCOMAJOR Mk. 2 POWER DISCO CONSOLE with integral Power Amp. Twin Jack output sockets. TWIN BSR turntables. Cartridges with Diamond Styl. Separate volume controls each t/table. Full Headphone Monitoring Facilities. PAIR OF 60 WATT SPEAKERS: Black Vynide covered cabinets approx. size 18" x 18" x 8". PAIR OF HI-FI HEADPHONES and MATCHING 'MIKE': STEREO VERSION £299.95
PACKAGE PRICE (including VAT) Carr. £4.
OR DEPOSIT £31.99 and 12 mthly. payments £12.48 (Total £181.75) **£159.95**

FANE DISCO 600 SPEAKER UNITS. Fabulous 'Specialist' range Speaker in heavy Vynide covered cab. Fitted protective corner pieces. **£45 ea.**
A pair can be supplied in lieu of RSC Speakers with the above system for £25 extra.

MOBILE DISCO CONSOLE

MIC. JACK. PHONE JACK. MONITOR VOL. CONTROL. MONITOR SELECTOR DECK (1) Vol. Control. DECK (2) Vol. control. Mic. Vol. Control. Treble Control. Bass Control. ON/OFF Switch. Neon Indicator. Twin Turntables **£59.95**
Carr. £3




ALL RSC PRICES INCLUDE V.A.T.

40W DISCO SYSTEM Inc. Mobile Disco Console with O/P Stage £79.95 & Pr. 12" Spkrs. **£99.95**

POWER (SLAVE) AMPLIFIER 100 WATT

Suitable for use with above or other DISCO-Consoles. Also for increasing output of lower-powered Amplifiers. Terms: Dep. £9.00 and 8 mthly payments of £5.22 (Total £50.76) carr. £1 **£45.00**

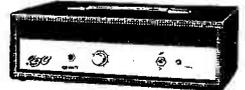

Imp. 8-15 Ω

TITAN GROUP/DISCO SPKRS

GUARANTEED FOR 5 YEARS

	Rec. Price	RSC Price
T12/35 12" 35w	£14.63	£10.95
T12/60A 12" 60w	£21.00	£14.95
T12/100 12" 100w	£36.00	£23.95
T15/60 15" 60w	£27.00	£17.99
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£39.50	£28.95
T18/100 18" 100w	£44.00	£29.95

SPECIAL OFFER

FOR ONE MONTH ONLY
FANE CRESCENDO
12 BASS 12" Super Bass Guitar Speaker
Our Price **£33.95**
Carr. Free
Rec. Ret. Price **£49.30**

TERMS MODEL	MONTHLY PAYMENTS DEPOSIT	TOTAL
Model T12/35 (Pair)	£4.90 & 8 at	£26.62 £26.62
Model T12/60A (Pair)	£6.90 & 8 at	£28.87 £28.87
Model T12/100 (Each)	£4.99 & 8 at	£28.08 £28.08
Model T15/60 (Each)	£3.99 & 8 at	£21.99 £21.99
Model T15/70 (Each)	£4.95 & 8 at	£28.37 £28.37
Model T15/100 (Each)	£6.00 & 8 at	£28.87 £28.87
Model T18/100 (Each)	£6.95 & 8 at	£28.81 £28.81

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and interleaved where necessary. Primaries 200-250v. 50/s. Screened ALL PRICES INCLUDE VAT

MIDGET CLAMPED TYPE	PRICE
250v. 60mA 6.3v. 2a.	£1.75
250-0-250v. 60mA 6.3v. 2a.	£1.85
FULLY SHROUDED UPRIGHT MOUNTING	
250-0-250v. 60mA 6.3v. 2a. 0.5-6.3v. 2a.	£2.60
250-0-250v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	£4.35
300-0-300v. 130mA 6.3v. 4a. C.T. 6.3v. 1a. for Mullard 610 Amplifier	£5.20
250-0-250v. 70mA 6.3v. 2a. 0.5-6.3v. 2a.	£4.35
350-0-350v. 150mA 6.3v. 4a. 0.5-6.3v. 2a.	£5.20
425-0-425v. 200mA 6.3v. 4a. C.T. 5v. 2a.	£6.95
425-0-425v. 200mA 6.3v. 4a. 0.5-6.3v. 4a. 5v. 3a.	£10.00
450-0-450v. 250mA 6.3v. 4a. C.T. 5v. 2a.	£10.45
TOP SHROUDED DROP-THROUGH TYPE	
250-0-250v. 70mA 6.3v. 2a. 0.5-6.3v. 2a.	£2.60
250-0-250v. 100mA 6.3v. 2a. 0.5-6.3v. 2a.	£2.90
250-0-250v. 100mA 6.3v. 2a. 6.3v. 1a.	£3.20
350-0-350v. 80mA 6.3v. 2a. 0.5-6.3v. 2a.	£4.35
250-0-250v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	£4.35
300-0-300v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	£4.35
300-0-300v. 130mA 6.3v. 4a. 0.5-6.3v. 1a.	£5.20
suitable for Mullard 610 Amp.	£5.20
350-0-350v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	£4.35
350-0-350v. 150mA 6.3v. 4a. 0.5-6.3v. 3a.	£5.20
FILAMENT OR TRANSISTOR POWER PACK	
Type: 12v. 1a. £1.10. 6.3v. 1.5a. £1.08. 6.3v. 2a. £1.10. 6.3v. 3a. £1.70. 6.3v. 6a. £2.80. 12v. 3a. or 24v. 1.5a. £2.80. 0-9-18v. 1ja. £2.26. 0-12-25-42v. 2a. £2.10	
CELEBRATOR TRANSFORMERS	
0-9-18v. 1ja. £2.08. 2ja. £2.26. 3ja. £2.32. 5a. £2.84. 6a. £3.19. 8a. £3.48.	

AUTO (STEP UP/STEP DOWN) TRANSFORMERS 0-10/120v. 200-230-250v. 50-50w. £2.90 150 watts £5.20, 250 watts £6.37, 500 watts £9.84.

OUTPUT TRANSFORMERS Standard Pentode 5000 to 8 ohm, or 7000 ohm to 3 ohm £1.12. Push Pull 8 watts EL84 to 8 ohm or 15 ohm £1.68; Push Pull 10-12 watts 6v, 6 to 3 ohm or 15 ohm £2.61; Push Pull 10-12 watts to match 6v. 6 to 3, 5, 8 or 15 ohm £2.72; Push Pull EL84 to 3 or 15 ohm 10-12 watts £2.61; Push Pull Ultra Linear for Mullard 510 etc. £4.36; Push Pull 15-18 watts, sectionally wound 6L6 KT86 etc. from 3 or 15 ohm. £3-71p. Push Pull 20 watt high quality sectionally wound EL84 6L6 KT86 etc. to 3 or 15 ohm, fully shrouded. £6.37p.

SELENIUM RECTIFIERS F.W. (Bridged) All 6/12 v. D.C. output. Max. A.C. input 12v. 1a. 45p, 2a. 57p, 3a. 85p, 4a. 95p, 5a. £1.15.
L.F. CHOKES 150mA, 7-10H, 250 Ω £1.28; 200mA, 10H, 200 Ω £1.10; 60mA, 10H, 400 Ω 41p.

RSC 200 WATT DISCO SYSTEM

STEREO 100 plus 100 WATT OUTPUT

AT A FANTASTIC LOW PRICE!



Consisting of (1) Twin T/table Console with Stereo Pre-Amp and P.U. Cartridges. (2) 100 + 100 watt Power Amplifier. (3) & (4) Pair 100 Watt Loud-speakers including Twin 12" Units

Rec. Mic. UD150 Cardioid £9.95 extra with system only

SYSTEMS UP TO 300 WATTS OUTPUT AT UNBEATABLE PRICES Send for Catalogue

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £119.95

Twin McDonald MP60 type turntables. Sonotone or Acos cartridges with Carr. diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amp. £2.50 p/ler, complete with lid. Or Dep. £18.95 and 18 fortnightly pymts £6.78 (Total £185.99)

STEREO VERSION £155 or DEPOSIT £25 and 18 fortnightly pymts £8.80 (Total £174.40). Carr. £3

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 16 Ohms covered in Vynide & Vynair TYPE C132 40-50 WATTS £28.95

Incorporating two exceptionally efficient 13" x 8" speaker units. Dep. £4.95 and 8 monthly payments £8.50 (Total £88.95) Carr. 65p

TYPE C4/80 80 WATTS. Fitted four 12" highly sensitive high flux speakers with high power voice coils. Approx. size 54" x 14" x 11". Deposit £8.00 and 12 mthly. pymts. £4.00. (Total £49.95) Carr. 85p.

£199.95 Carr. £7.50

Terms: Dep. £40.00 and 12 monthly payments £15.00 (Total £267.20)

- ★ ILLUMINATED P.U. ARMS
- ★ FULL SIZE B.S.R. Turntables
- ★ SEPARATE MAINS SWITCHES for L. & R. Turntables
- ★ NEON MAINS INDICATORS for all three switches
- ★ INPUTS (Each with its own SLIDER Control) for Mic & Tape
- ★ MASTER BASS, TREBLE and VOLUME CONTROLS
- ★ FADE IN/FADE OUT SLIDER MIXER Controls for each T/table

TDI DISCO CONSOLE

Incorporating twin BSR MP60 type turntables and Sonotone or Acos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MOTORING FACILITIES plus Treble and Bass Controls. Separate input for 'mixe' with vol. control. Black Vynide covered Cabinet with lid. Or DEP. £14.95 and 18 fortnightly pymts. £5.47 (Total £118.41) Carr. £1.50

£99.95

TD2S STEREO VERSION OF ABOVE

Terms DEPOSIT £20 and 18 fortnightly payments £8.71 (Total £140.75) Carr. £2.00

£125.00

FANE DUO DISCO 60C SPKR UNITS

Can be supplied with 200W system in lieu of RSC spkrs. for £56 extra. Twin Fabulous specialist range Spkrs in heavy Vynide covered cabinets with protective corner pieces and handles. Rating 120 watt R.M.S. each. List Price £150 Pair.

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

<p>'POP' 100 18" 100 Watt 14,000 gauss 8/15Ω £39.95 Dep. £8.95 and 8 mthly payments £4.38 (Total £48.99)</p>	<p>'POP' 60 15" 60 Watt 14,000 gauss 8/15Ω £23.95 Dep. £5.95 and 8 mthly payments £2.68 (Total £28.96)</p>	<p>'POP' 50/2 12" 50 Watt 12,000 gauss 8/15Ω £14.99 Dual Cone. Terms for pairs Dep. £8.98 & 8 mthly pymts £3.97. Total £28.94 PAIR SUITABLE FOR ALL PURPOSES</p>
---	---	---

'POP' 25/T 12" 25W

Dual cone. 15 ohm Imp. (Not for Bass Guitar use). £9.95
Terms for Pairs: Deposit £4.90 and 8 mthly payments of £2.87 (Total £28.86). Carr. free.

HIGH POWER TWEETER PH50

Response 3KHz-20KHz with 2 mid. Non elect. filter available 55p. £6.65
50 Watt 8Ω

TITAN T2H HIGH FREQUENCY UNITS

Incorporating a pair of Highly Sensitive Horns with substantially flat response to over 16 kHz. Rating 70/100 watts. Imp 8 or 15 Ω. Or Dep. £8.95 & 8 monthly payments £4.38 (Total £48.99). Carr. 55p

HIGH QUALITY L'SPEAKER UNITS

ALL 2-TONE VYNIDE & VYNAIR FINISH L12/2 70/100W Fitted pair of 12" 35 watt high flux speakers. Imp. £39.95
8-15 ohms. Music rating 100w. Carr. £1.50. Terms: Dep. £5.11 & 8 monthly payments of £5.11. (Total £45.99).
L12/50 12" 50 WATT 13,000 lines 15 ohms. Terms: Dep. £4.95 and 8 mthly pymts. £3.37 (Total £31.91) Carr. 75p.

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

SUPER MINTREL 10 W GUITAR AMP.

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphones and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed, Tremolo Intensity. £29.99
Terms: DEPOSIT £7.75 and 8 monthly payments £8.80 (Total £34.15) Carr. free

RSC PHANTOM 50 COMBO AMP. £59.95

Rating 50 watts. 3 inputs, 2 vol. controls—Bass, Treble Presence. Carr. £1.50 Suitable for Lead or Rhythm Guitar, mic., Radio, Tape etc. Inc. High Flux 12" 50W Speaker. Dep. £7.95 & 8 monthly payments £7.48 (Total £67.79).

PHANTOM 50/GP all purpose version of above. £69.95

Extra high sensitivity. Can be used with Bass Guitar. Or Dep. £8.95 & 8 monthly payments £8.70 (Total £78.55) Carr. £1.75

FAL PHASE 50-4 AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protection against serious o/p overloading. O/p for spkrs. 8 to 16 ohms. 200-250v. A.C. mains. Output 50 watts R.M.S. cont. £48.60
Deposit £8.60

& 8 mthly. payments £5.75. Total £54.00 Carr. Free.

FAL PHASE 100-4 £67.95

Facilities as above. Output 100 watt MUSIC, 70W RMS

FAL PHASE 50-4 WITH L12/2 70 W TWIN SPEAKER UNIT

Vynide covered. Fitted with protective corner pieces. Carr. £2.50. £88.00
Or Dep. £10.00 & 12 monthly payments £7.87 (Total £108.04) or with L125 100W TWIN SPKR UNIT

£94.50

Suitable for all purposes inc. Bass Guitar. Carr. £2.50
Terms. Dep. £14.50 & 18 fortnightly payments £5.15 (Total £107.80)

FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES



I.S.E. JINGLE MACHINES JINGLE 8+

Employing Standard 8 Track Cartridge £37.95
Or Dep. £4.85 & 8 monthly pymts £4.85 (Total £48.65)

ECHO CHAMBERS £51.95

Excellent quality units

HEAVY DUTY CABINETS

Black Vynide covered. Fitted Protective Corner Pieces. Cut for various Speaker Combinations. 18" x 18" x 8" £10.95
24" x 24" x 12" £19.95
30" x 24" x 12" £28.95
each unit. 30" x 28" x 12" £28.95
Sizes approx.:



LIQUID WHEEL from PROJECTORS £29.95

'SOUND TO LITE' SYSTEM

PULSAR special price complete kit £106.95

Dep. £14.95 and 18 fortnightly pymts. £5.98. (Total £121.99). Super 8L Unit. 1000 watt per channel. Manual override buttons. 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd. and 10 yd. leads, fitted plugs. Units sold sep.

FAL SOUND-TO-LITE UNIT £21.60

3-WAY SPOT BANK £16.20

Excluding Bulbs Each Carr. £1.50
COMPLETE SYSTEM Incl. 2 Spotbanks and bulbs. £55

New Branches at YORK CARLISLE, DEWSBURY LIVERPOOL, PRESTON

OPEN ALL DAY SATURDAYS (5 Day Week)
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-235 1279 (Closed Wed.).
CARLISLE 8 English Street. (Closed Thurs.). Tel. 38744
COVENTRY 17 Shelton Sq., The Precinct. Tel. 25983
DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361
DARLINGTON 19 Northgate (Cl. Wed.). Tel. 68043
DEWSBURY 9/11 Kingsway (Closed Thurs.). Tel. 468058
DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 33069



All items subject to availability. Prices correct at 7.5.76 E. & O.E.
EDINBURGH 101 Lothian Rd. (Cl. Wed.). Tel. 229 8501
GLASGOW 326 Argyle St. (Cl. Tues.). Tel. 248 4158
HULL 7 Whitfriargate (Closed Thurs.). Tel. 20505
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252
LIVERPOOL 35 Dawson's Way, St. John's Shopping Centre Tel: 708 9380 (Cl. Wed.).
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 793 1625
MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 238 2774
MIDDLESBROUGH 103 Linthorpe Rd. Tel. 210585 (Closed Wed.).

Barclaycard and Access accepted
MAIL ORDERS & EXPORT ENQUIRIES TO: AUDIO HOUSE, HENNINGER LANE, LEEDS, 18. Tel: Pudsey (09735) 77631.
MAIL ORDERS MUST BE SENT TO SHOPS
TERMS C.W.O. or G.O.D. No G.O.D. under £1.
POSTAGE 40p PER ORDER OR AS QUOTED.
TRADE SUPPLIED. LARGE S.A.E. REQUIRED FOR FREE CATALOGUE.
NEWCASTLE UPON TYNE 24 Newgate Shopping Centre, 59 Grainger St. (Closed Wed.). Tel. 21469
NOTTINGHAM 10/19A Market Street. (Closed Thurs.). Tel. 46088
PRESTON 21 George Street Shopping Prec. Tel. 61678
SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.). (Closed Thurs.). Tel. 20716
STOCKPORT 2 Little Underbank (Closed Thurs.). Tel. 480-0777
SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573
YORK 5 CHURCH ST. (Closed Wed.). Tel. 34355



VHF-UHF MANUAL

Third Edition

by D. S. Evans, PhD, AIM, G3RPE,
and G. R. Jessop, CEng, MIERE, G6JP

**Everything about vhf/uhf radio techniques
— in a single book**

Since 1969 the RSGB *VHF/UHF Manual* has been a best seller around the world as the standard textbook on techniques and equipment for amateur radio transmission and reception at frequencies over 30MHz. (You will find a copy in many a professional radio technician's bookcase, as well).

Now we are proud to announce the latest and best-ever edition.

Over 400 large-format (180 × 245mm) pages packed with ideas, information and constructional details of tried and tested equipment, each specialist topic contributed by an acknowledged expert in the field.

There are chapters on receivers, transmitters, space communications, filters, aerials, microwaves and much more. Simple amateur television is covered and a data section provides valuable facts and figures to help the constructor.

Many of the designs make use of integrated circuits, and the microwave chapter gives details of equipment for use up to 24GHz.

It is the most comprehensive and up-to-date review of vhf and uhf techniques available today. If you are seriously interested in operation at these frequencies it is a book you must have.

Price £4.95 plus 68p p & p, hardbound

Obtainable direct from the publishers.

RADIO SOCIETY OF GREAT BRITAIN

Publications (Sales), 35 Doughty Street, London WC1N 2AE

ELECTROTIME

SPECIALISTS IN ELECTRONIC TIMEKEEPING

ELECTRONIC DIGITAL ALARM CLOCK MODEL EC 3



- ★ LARGE 4 DIGIT DISPLAY
- ★ AM/PM INDICATOR
- ★ FLASHING SECONDS INDICATOR
- ★ 5 MINUTE REPEATING SNOOZE ALARM
- ★ 24 HOUR ALARM
- ★ BRIGHTNESS CONTROL
- ★ ATTRACTIVE WHITE CASE

COMPLETE BUILT CLOCK PRICE **£14** inc. VAT

THE "MISTRAL" I DIGITAL CLOCK



- ★ PLEASANT GREEN DISPLAY
- ★ 12/24 HOUR READOUT
- ★ FULLY ELECTRONIC
- ★ PULSATING COLON
- ★ PUSH BUTTON SETTING
- ★ BUILDING TIME 1 HOUR

COMPLETE KIT PRICE **£11.07** inc. VAT

BUILT CLOCK PRICE **£14.95**

LCD MODEL TLC4

CONTINUOUS
READOUT
UTILISING
LIQUID CRYSTAL
DISPLAY.

WITH BACKLIGHT
FOR NIGHT
READING

FEATURES—

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE



RHODIUM **£39.95**

GOLD **£41.50** inc. VAT

LED MODEL TLE5

FEATURES—

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE
- ★ DAY OF WEEK



£29.50 inc. VAT

GOLD OR
RHODIUM PLATED

We are proud to announce the opening of our new Showroom in which you will find one of the Largest Ranges of Digital Electronic Clocks and Watches available in the UK so why not call in and see us? One year's guarantee with all models Electronic accuracy to within seconds per week

ELECTROTIME, DEPT. 3/7, 11, SHEPLEY'S YARD,
SHOPPING PRECINCT, TOWN CENTRE,
CHESTERFIELD, DERBYSHIRE. TEL (0246) 35804

PLEASE SUPPLY
I ENCLOSE CHEQUE/POSTAL ORDER

NAME

ADDRESS




Stirling Sound Products

FROM BI-PRE-PAK

UNIT 1 PRE-AMP/CONTROL

SUPERB VALUE AT

£7.80

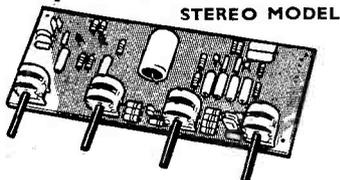


UNIT 1, latest addition in the Stirling Sound range of realistically priced constructional modules is going to assure many more constructors of obtaining quality where price has prevented it before. UNIT 1 offers full stereo facilities, is guaranteed and easy to connect up.

MADE IN OUR OWN FACTORY IN ESSEX AND SOLD DIRECT

- Input sensitivity—50 mV, adjustable
- Output—200 mV for 50 mV in
- Bass control— ± 15 dB at 30 Hz
- Treble control— ± 15 dB at 10 kHz
- Balance control; volume control; $\frac{1}{4}$ " spindles bushed
- Operating voltage—10 to 16V

MORE POWER—LESS VAT

SS.140 MK3

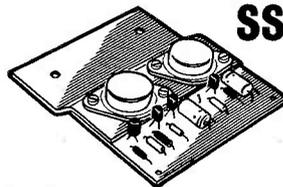

POWER AMP.
Built for hard work

40 WATTS
R.M.S.

INTO 4 Ω

£3.95*

+ 8% V.A.T.

Resulting from research and development, the Mk. 3 version of this most popular power amp. now includes built-in output capacitor with improved stability under severest working conditions. Greatly used for P.A., disco and similar work, SS.140 offers fantastic value for the price.

Build and save with Stirling Sound

BASIC MODULES FOR BUILDING UP TO A STEREO TUNER-AMP DATA WITH EACH MODULE

● TUNING

SS.201 X Geared variable tuning 88-108 MHz. AFC facility **£5.00**

SS.202 I.F. amp A meter and/or A.F.C. can be connected (size 3" x 2") **£2.65**

SS.203 Stereo decoder
For use with Stirling Sound modules, or with any other good mono F.M. tuning section. A L.E.D. beacon can be added to indicate when a stereo signal is tuned in (Red, 18p) (3" x 2"). **£3.85**

● POWER AMPS

SS.103 Simple I.C. module, 3 W output **£1.75**

SS.103-3 Stereo version of above **£3.75**

SS.105 5 watt amplifier to run from 12V. (3 $\frac{1}{4}$ " x 2" x $\frac{3}{4}$ ") **£2.25**

SS.110 Mk. 3 Similar to SS.105 but more powerful giving 10W into 4 ohms, using 24 volts **£2.75**

SS.120 Mk. 3 20 watt module when used with 34 volts into 4 Ω **£3.25**

SS.125 De-luxe hi-fi amp with only 0.04% distortion at all levels. 50V operation. 25 W R.M.S. out **£5.00**

● CONTROL


SS.100 Active tone control, stereo ± 15 dB cut and boost with suitable network **£1.60**

SS.101 Pre-amp for ceramic p.u., radio & tape with passive tone control details **£1.60**


SS.102 Stereo pre-amp with R.I.A.A. equalisation, mag., p.u., tape and radio in. **£2.25**

● POWER STABILISER


SS.300 Add this to your unstabilised supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench etc. Money saving and very reliable **£3.25***

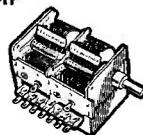

SS.201

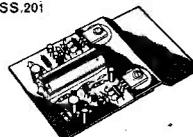

SS.125

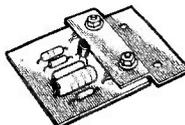


SS.105



SS.203

Stirling Sound

POWER PACKS

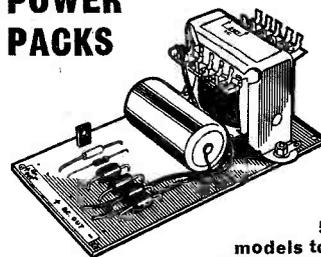

5 models to choose from

Not only do these excellent power packs stand up unflinchingly to hard work, inclusion of a take off point at around 13-15V adds to their usefulness and once again price value is outstanding.

Made to serve for years

SS.312 12V/1A **£3.75***

SS.318 18V/1A **£4.15***

SS.324 24V/1A **£4.60***

SS.334 34V/2A **£5.20***

SS.345 45V/3A **£6.25***

Add 50p for p/p any model.

Direct from the makers and obtainable only from Bi-Pre-Pak Ltd. Stirling Sound products are designed by professional experts and made in our own factory. They are distributed exclusively through Bi-Pre-Pak Ltd.

TERMS OF BUSINESS:

VAT at 12 $\frac{1}{2}$ % must be added to total value of order except for items marked * or (8%) when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 30p for UK orders unless marked otherwise. Minimum mail order acceptable—£1 Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

NEW SHOWROOM

We have extended and added exciting new stocks at our West Road premises. All welcome

Order your Stirling Sound products from

BI-PRE-PAK LTD

Co Reg No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344

TO STIRLING SOUND (BI-PRE-PAK LTD) 220/222 WEST ROAD WESTCLIFF-ON-SEA, ESSEX SSO 9DF

Please send

..... for which I enclose £

Inc. V.A.T.

NAME

ADDRESS

.....PW7C

CHEQUES/MONEY ORDERS PAYABLE TO BI-PRE-PAK LTD

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All mail order and callers (OPEN 9-6 MON-SAT.) to this address please
—callers only to 21 Dettford Broadway, SEB (Tel. 01-692 2009), and 38 Lower
Addiscombe Road, Croydon (Tel. 01-688 2950).

PC ETCHING KIT Mk II

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO Quick Dri Etch resist pen, abrasive cleaner, 2 miniature drill bits, etching dish and instructions. £3-65

7lb BARGAIN PARCELS
Hundreds of new components—pots, resistors, capacitors, switches, PC Boards with transistors, diodes and zeners, loads of odd and ends. NOW REDUCED TO £2-90

TRANSISTOR PACKS
200 asstd. mainly out of spec. transistors, mostly unmarked—NPN PNP plastic, TO5 TO18 RF AF Small signal and TO3 power devices. About 75% useable devices. Only £1-60. 100 unmarked BC108, untested £2-10. 10 out of spec. 2N3055 £1.

COMPUTER PANELS
Large quantity always available: 3lb asstd. £1-75; 7lb £2-85; 5lb £1-60. Pack with about 500 components inc. at least 50 transistors £1-00; Pack with 12 High quality panels, inc. IC's, power transistors, multitrans trim pots, hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2-75. 7400 IC pack—20 74 series IC's on panels £1-20.

PE Gas Ignitor Kit, as featured in July 75 edition. Still only £3-00.

FERRIC CHLORIDE
Anhydrous technical quality in 1lb double sealed packs. 1lb 85p; 3lbs £1-90; 10lbs £4-80; 100lbs £36-00.

VEROBOARD
100sq ins asstd. sizes and pitches, about 8 pieces (All 0-1" if requested) £1-30.

DEVELOPMENT PACKS
50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF, total 210 caps. £2-70.
CR25 carbon film 1/3rd watt resistors, 5%, 10 of each value 10 ohms to 1M Total 610 resistors £6-00. Electrolytics, wire ended 25V working 10 each of: 1, 2, 2, 4, 7, 10, 22, 47, 100µF, 70 capacitors for £3-20. 400mV zeners 5% 10 each 3V to 30V. 260 in all. Only £14-00.

JULY OFFERS

All full spec. marked components.

7400 10 for £1-20; 74121 4 for £1-20; 555 timer 1-9 40p; 10-24 38p; 25-99 36p; 100+ 34p. 741 Op-amp 1-9 25p; 10-24 22p; 25-99 20p; 100+ 18p.

2N3819 5 for £1-20. Neon with built in resistor for mains operation, plastic sleeve, flying leads. 5 for 40p.

ODDS AND ENDS

Edge Connectors: gold plated 0-1" 40 way single sided 60p; 78 way double sided £1-50. Heat shrink sleeving, 1m length 0-125" dia 10p. Spiral binding 3m x 3-2mm 20p. 100mfd 10V Tantalum Caps, 10 for 50p. 33k or 1-8k 1% resistors, 20 for 50p. 100k 1% resistor blocks, 12 way 2A or 5A 20p; 10+ 18p; 25+ 16p. Insulation tape—Red, Black, Blue, Yellow, Green, White or Brown. 5yds x 0-75" 10p per reel, 104-9p; 25+ 8p. 1 1/2" Quick blow fuses 1, 1k, 2, 3, 5, 10 or 15A. 30p per doz of one value, 10 doz mixed £2-50. 2000mfd 10V capacitors vert mntg, long leads 14 for £1-00. 20 ohm GPO balanced armature telephone insert 30p. 250V 2A bridge rect 50p; 50V 1A 30p. Crystal Mic insert 1 1/2" Dia, 32p. 22V 2W zener BX70 12p.

SEE PRACTICAL ELECTRONICS FOR INDIVIDUAL COMPONENT PRICES
All prices quoted V.A.T. AT THE NEW RATE and UK/EPG postage.
Most orders despatched on day of receipt. SAE with enquiries or for List please.
Send 10p for Multimeter catalogue—free on request on orders over £3. Official Orders accepted from Schools, etc. Export/Wholesale enquiries welcome.
Surplus components always wanted.

MULTIMETER MODEL LT22



Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styling meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2.5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50 A -25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300-3k-30k) db's 4 ranges -20db to +42db. Size 130 x 90 x 42mm. £9-00.

VEROBXES & CASES
Case type 110 205 x 140 x 40mm £2-90
1411, 205 x 140 x 75mm £3-25
1412, 205 x 140 x 110mm £4-20

Plastic Boxes—Professional quality, two tone grey polystyrene boxes with threaded inserts for mounting PC boards.

Type 2518, 120 x 65 x 40mm £1-52;
2520, 150 x 80 x 50mm £1-75; 2522, 188 x 110 x 60mm £2-40; Sloping front type: 220 x 174 x 100/52mm £4-20.

INTERCOM UNIT
Chassis 230 x 155mm with Celestion 3 ohm 110mm speaker, small buzzer, 3 pole 4 way switch, line matching transformer, 10 way terminal block, 100k pot, etc. £1-25.

HEAT SINK
Large finned matt black aluminium heat sink 230 x 200 x 35mm with 4 silicon power transistors, 51m, to 2N3716, and 16 1 ohm 5W resistors. £3-00.

BULK OFFERS
CR25 1rd Watt Resistors 5% carbon film 1 ohm to 10M 85p/100 of one value. 1N4148 1000 off £12. 1N4002 1000 off £23. BC107-8-9 All £7-50/100 2N3055 £30/100. 33pF ceramic plate 2% £5/1000. Send SAE for Wholesale list.

COMPONENT PACKS
400 asstd. carbon resistors £1-35
250 Hi-St. 1, 2, 5%, 1-1W £1-25
100 Wirewounds 2-15W £1-90
200 Miniature resistors, 1, 1/2 and 1W, mostly carbon film £1-20
200 poly, mica, ceramic caps £1-10
100 Polyester, 0.1-2-24µF £1-00
200 miniature electrolytics, but many unmarked so only £1-00
15 Useful switches, micro, toggle, rocker and rotary. £2-00.
35 Crystals, mostly HC11U, at least 30 diff. freqs. 4-8MHz £1-30.

TRANSFORMERS
All have mains primaries: 6-0-6V 100mA 90p; 9-0-9V 100mA 97p; 12-0-12V 50mA PC mntg 85p; 12-0-12V 100mA £1-00; 24-0-24V 500mA £2-05; Multitapped transformer to give 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24 or 30V, or 12-0-12, or 15-0-15V 1A version. £3-15; 2A version £4-45; 30-0-30V 1A £3-15; 6-0-6V 1 1/2A £1-95; 12-0-12V 1A £2-15; 25V 1 1/2A £2-00; 29V 50mA 75p; Type LGC: 17V @ 2-4A, 15-7V @ 1-5A, 12-5V @ 1A Only £1-50. Type JBS: 110V Primary, 31V 300mA Sec. Use 2 (Series pri) to get 31V @ 600 mA, or 62V @ 300mA. Price for 2 £1-65. Type SMS: 12V 130mA, 5-0-5V 120mA, 11-0-11V 10mA £1-20. Few only, 16V 20A £5-50.

RELAYS
Miniature Plug-in types: 1255 ohm 4c/o 40p; 700 ohm 4c/o 50p. PO 3000 type 650 ohm with 6 heavy duty c/o contacts (Ex-equip) 75p; 10 for £4-00. 6" easily removable reeds in 3580 ohm coil 50p; Plug in relay, BTG Base 17mm dia x 42mm long 10k coil 1c/o contact 40p. Omron MK3P plug in relay. 230V AC coil, 3 sets 10A/c/o contacts. £1-20.


WIREWOUND POTS
30k 5W; 200k 4W; 10k 3W; 1k 3W, 500 3W; 90k 3W; 58k 3W; 80p 3W; 100k 3W. All 25p each, any 10 £2-00.

QUALITY STEREO SOUND

SOLENT AUDIO SYSTEM

ALMOST 1/2 PRICE OFFER!

£5-95
down

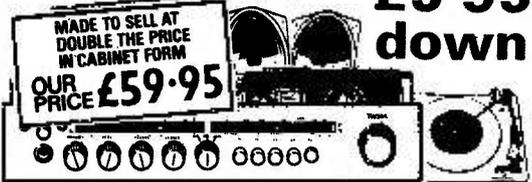

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) AFC Switching, Tape record and playback facilities. Dimensions 18 1/2" x 9" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £59-95. Credit Sale £5-95 deposit 9 monthly payments of £7-00 (Total Credit price £68-95). P. & P. £3-00. Send £8-95 today.

Chassis only available for cash at £45-00.

Full 12 months Guarantee.

CALLERS WELCOME.

Access and Barclaycard telephone orders accepted

Stereo headphones supplied with every complete order.



PW/7/76 100 CHASE SIDE SOUTHGATE
LONDON N14 5PL Telephones: 01-382-1644

A hobby that pays big salaries.

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full test details will be gladly sent without any obligation.

BRITISH NATIONAL RADIO & ELECTRONICS
SCHOOL, Dept WC76
P.O. Box 156, Jersey, Channel Islands.

NAME _____
ADDRESS _____
(Block caps please)

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

12p for 1 Valve.
Each additional Valve add 2p in UK


DM70	0-69	EF80	0-68	PC84	0-84	PL504	1-40	30C15/	
DY86/7	0-70	EF83	1-10	PC85	1-02	PL508	1-73	PCF800	1-22
DY802	0-52	EF85	0-70	PC88	0-88	PL509	2-23	30C17	1-29
EABCB80	1-16	EF86	1-73	PC89	0-97	PL502	2-23	30C18	
EB91	0-97	EF89	1-78	PCL189	1-22	PY33	0-73	PCF805	1-29
EBC81	0-38	EF91	1-35	PCF80	0-84	PY81/800	0-72	30F5/PP818	
EBF80	0-63	EF92	1-51	PCF82	1-37	PY82	0-70		1-35
EBF85	0-66	EF95	1-63	PCF86	0-97	PY86/7	70P	30FL1/	
EBF89	0-50	EF188	0-88	PCF200	1-50	PY88	0-84	PCF800	0-98
EC86	0-82	EF184	0-83	PCF201	1-50	PY90A	1-80	30FL2	1-03
EC88	0-86	EF190	1-22	PCF801	0-97	PY90	0-86	30FL12	1-44
EC89	0-94	EL34	1-40	PCF802	1-02	PY91	0-72	30FL14	1-20
EC97	0-89	EL36	0-50	PCF803	0-97	U26	1-22	30LL/PC84	
EC981	0-70	EL84	0-70	PCL82	1-78	U191	1-12		0-63
EC982	0-70	EL86	1-40	PCL83	1-84	U193	0-56	30LL15/	
EC983	0-70	EL95	1-02	PCF83	0-97	UABC80	1-01	PCF805	1-35
EC984	0-63	EM81	1-24	PCL84	0-88	UBC81	0-80	30LL17	1-12
EC985	1-02	EY61	0-85	PCL85	0-72	UBF89	0-45	30FLMR	1-33
EC986	1-22	EY88	0-85	PCL86	0-72	UC48	0-66	30P1Z	
EC989	0-77	EY86/87	0-70	PCL86	0-97	UC81	1-73	PC801	1-22
EC990	0-63	EY88	0-81	PCL805/800-97		UCL82	1-02	30P19/	
EC992	0-90	EZ80	0-84	PD500	2-28	UCL83	1-02	PC802	1-06
EC996	0-76	EZ81	0-70	PL200	1-23	UL84	1-23	30P1L/	
EC998	1-73	EY501	1-73	PL1	1-23	UY85	0-73	PCL801	1-35
EC999	0-66	EY88	0-85	PL1A	1-23	6/30LZ/		PC1800	1-47
EC999A	1-00	EC83	0-78	PL51A	1-40	EC804	1-20	30FL14/	
EC999B	1-02	PC88	1-40	PL62	0-43	6P28/EF812		30FL14/	
EC999C	0-69	PC88	1-40	PL63	1-78	PCL88	1-16	30FL15	1-44
EC999D	0-83	PC97	0-70	PL84	1-02	30C1/PCF80			
EC999E	0-82	PC900	0-84	PL500	1-40		0-84		

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

A21	1-00	EF37A	1-50	N78	5-00
AZ21	1-00	EF39	1-25	OA2	0-45
CB131	1-40	EF80	0-85	OB2	0-45
CL33	1-80	EF86	0-45	PC86	0-65
CT31	1-00	EF86	0-65	PC88	0-65
DAF91	0-40	EF89	0-85	PC97	0-55
DAF98	0-80	EF91	0-40	PC900	0-55
DC900	1-85	EF92	0-50	PC84	0-45
DF91	0-40	EF95	0-45	PC88	0-68
DF96	0-60	EF98	0-80	PC89	0-60
DK91	0-50	EF183	0-60	PCL189	0-55
DK92	1-00	EF184	0-65	PCF80	0-40
DK96	0-75	EL32	0-60	PCF82	0-42
DL92	0-50	EL33	3-00	PCF86	0-65
DL94	0-48	EL34	0-70	PCF801	0-60
DL96	0-55	EL36	0-60	PCF802	0-55
DY86	0-45	EL37	3-40	PCF805	0-90
DY87	0-45	EL41	0-90	PCF806	0-90
DY802	0-47	EL42	0-85	PCF808	1-00
EABCB80	0-38	EL84	0-85	PCL82	0-45
EA472	0-70	EL95	0-60	PCL83	0-70
EB91	0-30	EM80	0-55	PCL84	0-50
EBC38	1-00	EM81	0-60	PCL85	0-60
EBC41	0-75	EM84	0-40	PCL86	0-50
EB981	0-40	EM87	1-00	PCL805/86	
EBF80	0-40	EY81	0-45	PD500	1-50
EBF83	0-45	EY86	0-65	PEN45	0-85
EBF89	0-38	EY88	0-60	PL86	0-62
EBL31	2-00	EZ40	0-60	PL81	0-55
EC981	0-45	EZ41	0-75	PL81	0-55
EC982	0-38	EZ80	0-80	PL82	0-50
EC983	0-38	EZ81	0-81	PL83	0-50
EC984	0-35	EY001	0-90	PL84	0-50
EC985	0-45	EZ80	0-60	PCF80	0-55
EC988	0-50	GZ22	0-45	PL504	0-35
EC989	0-50	GZ24	0-75	PL508	0-80
EC942	0-85	HN309	1-50	PL509	1-55
EC981	0-35	KT61	3-00	PL502	2-00
EC983	0-50	KT66	3-40	PX25	8-50
EC980	0-60	KT81(7C5)2-00		YF33	0-63
EC982	0-42	KT91	1-75	YF81	0-65
EC983	0-45	KT93	3-45	YF82	0-45
EC986	0-55	KTW61	1-50	YF83	0-80
ECLL800	3-50	MU14	1-00	YF88	0-83

PY500	1-10	GJ5M	0-85
PY81/800	0-50	GJ6G	0-45
PY801	0-55	GJ8	0-35
ST41	0-55	GJ7G	0-80
SP91	0-85	GJ7M	0-80
T41	1-50	GK6GT	0-50
U14	0-75	GK7G	0-85
U26	1-00	GK7M	0-45
U26	0-85	GK8G	0-45
U191	0-75	GK8M	0-70
UABC80	0-40	GK26	1-00
UAF42	0-75	GL6G	1-25
UBC41	0-40	GL6CC	0-80
UBC81	0-50	GQ7G	0-40
UBF80	0-50	GQ7M	0-60
UBF89	0-50	68L7GT	0-55
UC086	0-50	68N7GT	0-55
UC48	0-50	68Q7GT	0-50
UC81	0-80	GUBG	1-40
UC92	0-40	6V6G	0-80
UCL83	0-70	6V6GT	0-80
UF41	0-75	6X4	0-45
UF89	0-50	6X5G	0-45
UL41	0-85	6X5GT	0-55
UL84	0-50	7B6	0-80
UBC41	0-55	7B7	0-80
UY86	0-45	7C5	2-00
VR105/30	0-40	7C6	1-00
VR160/30	0-45	7H7	0-80
1R5	0-50	7R7	1-80
1R5	0-40	7R7	2-25
1T4	0-40	7Y4	0-80
884	0-55	12A7	0-45
8A5	0-45	12A7	0-45
6A87G	1-00	12A7	0-45
6A76	0-60	30PFL1	1-00
6A76	0-60	30PFL2	1-00
6A76	0-60	30PFL14	1-00
6A76	0-60	30PFL15	0-95
6A76	0-60	30PFL17	0-95
6A76	0-60	30PFL19	0-95
6A76	0-60	30PFL249	0-95

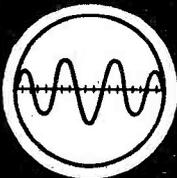

TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

PRE AMPLIFIERS



VAO8

Designed for use with TUAC power amplifier modules. Extensive research has gone into various wide range tone control circuits to produce superb sound quality. Thousands are already in use in high quality professional amplification systems.

VAO8 Vol. Treb, Mid and Bass controls. HI. IMP. FET. I/P suitable Mid. Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 1kHz Bass +20 -10dB at 40Hz.

£8.50


VAO6 Vol, Treb, and Bass controls. Sensitivity 8mV. Treb +28 -15dB at 12kHz, Bass ±18dB at 40 Hz.

£7.50

SVAO8 STEREO PRE AMP VqI, Treb, Mid and Bass controls, I/P suitable, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 4kHz. Bass +20 -10dB at 40Hz Plus Full Balance Control. Full I/C operation supply voltage ± 15VDC.

£15.00

MONO DISCO MIXER WITH AUTO FADE

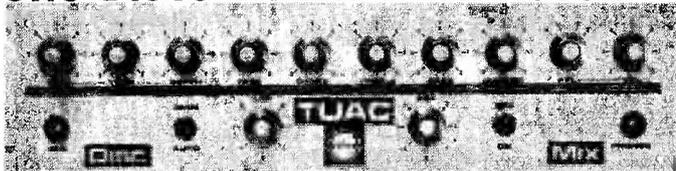

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth, auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol on/Off Sw. Max output 3V RMS.


Specification: Deck Inputs—50mV into 1MΩ; Deck tone controls—Treble total range 36dB at 15kHz—Bass total range 36dB at 50Hz. Mic input—200 ohms upwards 2mV into 22kΩ. Mic tone control—Total range 40dB at 15kHz. Tape input—100mV into 200 ohms. Power requirements 20-50 volts D.C. at 50mA. (R.I.A.A. Comp mag inputs available 75p.)

£39.75

PANEL SIZE
18 x 4 1/2 in.
DEPTH 3 in.

★ TUAC AMPLIFIER MODULES ★ POWER AND QUALITY ★

- 125 watts RMS continuous sine wave output

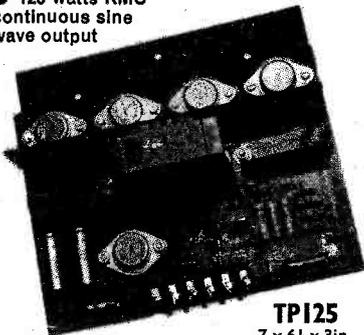


TP125
7 x 6 1/2 x 3 in

£23.25

- 4 R.C.A. 150 watt 15 amp output transistors

- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 6 connections

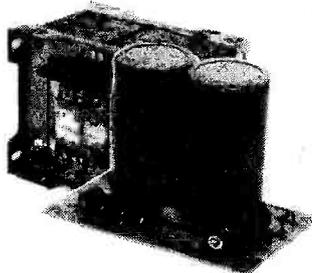Power supplies vacuum impregnated. Transformers with supply board incorporating pre-amp supply.



PS 250 for supplying 2 TP125s

£28.00

PS 60/60 for supplying 2 TL60s

£25.50

PS 125 ± 45 volts for TP125

£16.75

PS 100 ± 43 volts for TL100

£15.50

PS 60 ± 38 volts for TL60


£14.50

PS 30 ± 25 volts for TL30

£9.75

PSU 2 for supplying disco mixer

£6.50

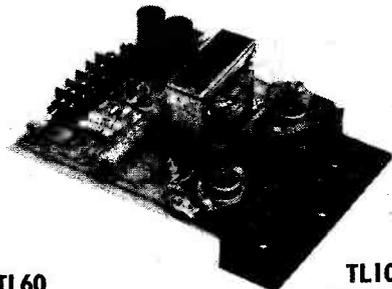

TL60

5 x 5 x 3 in

- 60 watts RMS continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

£16.75

TL100

5 x 5 x 3 in

- 100 watts RMS continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors

£18.75

Specification on all power modules. All output power ratings ± 0.5dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10kΩ; Frequency response 20Hz-20kHz ±2dB; Hum and noise better than -70dB.

STOCKISTS—CALLERS ONLY

Geo. Matthews, 85/87 Hurst Street, Birmingham (Tel. 021-622 1941)
Arthur Sallis Ltd., 28 Gardner St. (Tel. Brighton 65806)

Bristol Disco Centre, 26 The Promenade, Gloucester Road (Tel. Bristol 41666)

Socodi, 9 The Friars (Tel. Canterbury 60948)

Cookies, Disco Centre, 132 West St. (Tel. Crewe 4739)

H.B. Electronics, 54 Montagu Street (Tel. Kettering 83922)

Leighton Electronics Centre, 59 North Street (Tel. Leighton Buzzard 2316)


Al Music Centre, 88 Oxford Street, Manchester (Tel. 061-236 0340)

Damon Electronics, 89 Carrington Street (Tel. Nottingham 53880)

Electra Centre, 58 Lancaster Road (Tel. Preston 58488)

Mitchell Electronics, 64 Winchester Street (Tel. Salisbury 23689)

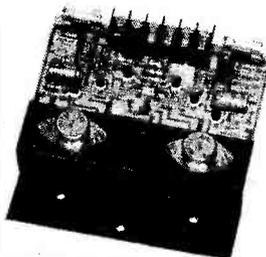Mitchell Electronics for Southampton area



SIZE 5" x 5" x 1 1/2"

TL30 New from TUAC TL30 D.C. coupled power amplifier module.

- OUTPUT POWER 30 WATTS RMS CONTINUOUS SINE WAVE
- OUTPUT IMPEDANCE 8-15 OHMS
- T.H.D. AT FULL POWER 0.5%
- SIGNAL TO NOISE RATIO -85dB
- INPUT SENSITIVITY 60mV INTO 50K OHMS
- FREQUENCY RESPONSE 25Hz-50kHz
- 8 TRANSISTORS
- 4 DIODES
- ONLY SIX CONNECTIONS

£12.50

Send large stamped addressed envelope with all enquiries or send £1 (refundable against purchase) for fully illustrated 20 page catalogue.

FUZZ LIGHTS




RED GREEN
BLUE AMBER

240 volt a.c. Long Life Candle Bulb, Revolving Reflector, adds a new dimension to disco lighting effects.


£19.50

TUAC

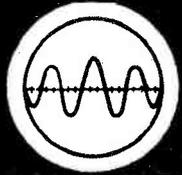MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
PERSONAL SHOPPERS MON. TUES. THURS. FRI and SAT
9am-6pm WED 9am-1pm



TUAC STEREO DISCO MIXER

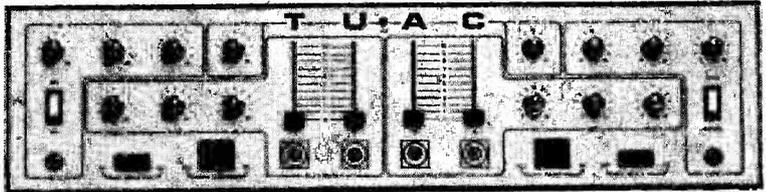

INPUTS. Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume treble, and bass controls for each pair of sliders. Sensitivity mag., 3mV (R.I.A.A. comp.). Flat 50mV at 1kHz. Bass controls $\pm 18\text{dB}$ at 60Hz. Treble controls $\pm 18\text{dB}$ at 15kHz.

OUTPUTS. Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary Master and Balance controls. Band width 15Hz-25kHz $\pm 1\text{dB}$.


P.F.L. Output 250mV into 8 ohms. Rotary Volume Control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

MISCELLANEOUS FACILITIES. Two illuminated deck on/off switches. Mains illuminated on/off switch. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.

£115

Size: 25in long x 6in high x 3in deep

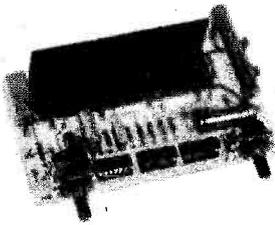4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER—4LSMI



- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections

Patents applied for **£18.75**

Model 501 500w per channel as above without sound triggering **£12.25**

3 CHANNEL LIGHT MODULATOR

- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections




SILMB

£18


(Single Channel Version 1500 Watts **£9.50**)

NEW FROM TUAC FRONT PANELS FOR LIGHTING EFFECT MODULES

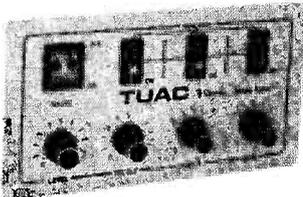
complete with switches, neons and knobs as illustrated



For 3SDM1 **£6.50**

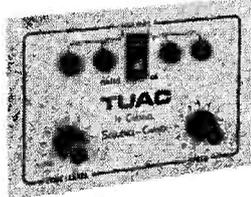

For 4LSM1 **£5.50**

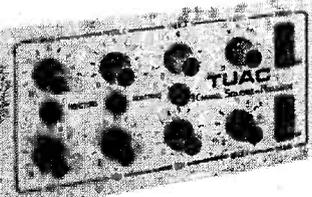

For 3SDM1 combined with 4LSM1 **£7.50**

ADD SEQUENCE CHASING AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel
- 9 easy connections

SEQUENCE DIMMER MODULE—3SDM1 £13

Manufactured and assembled in Gt. Britain fully guaranteed

HOW TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD (PW7)

or quote Access/Barclay Card No. and post to TUAC LTD (PW7)

163 Mitcham Road, London, SW17 9PG

We accept phone orders from Access/Barclay Card Holders

Phone: 01-672 3137/9080

ALL PRICES INCLUDE V.A.T. POSTAGE AND PACKING FREE

Suppliers to H.M. Govt. Depts. **TRADE AND EXPORT ENQUIRIES TEL. 01-672 9080**

74 TTL

1-24	25-99	100+	
7400	14p*	12p*	10p*
7401	14p*	12p*	10p*
7402	14p*	12p*	10p*
7403	15p*	12p*	10p*
7404	16p*	13p*	11p*
7405	16p*	13p*	11p*
7406	16p*	13p*	11p*
7407	16p*	13p*	11p*
7408	16p*	13p*	11p*
7409	16p*	13p*	11p*
7410	16p*	13p*	11p*
7411	22p*	22p*	20p*
7412	22p*	22p*	20p*
7413	22p*	22p*	20p*
7500	22p*	22p*	20p*

LIGHT EMITTING DIODES

0.125" dia. lens (TTL 209)	0.16" dia. lens	0.2" dia. lens (MLED 650)
Red 1+ 10+ 100+ 16p* 15p* 13p*	1+ 10+ 100+ 20p* 18p* 16p*	1+ 10+ 100+ 17p* 16p* 15p*
Green 26p* 24p* 22p*	26p* 24p* 22p*	26p* 24p* 22p*
Amber 26p* 24p* 22p*	26p* 24p* 22p*	26p* 24p* 22p*
Yellow 26p* 24p* 22p*	26p* 24p* 22p*	26p* 24p* 22p*

I.C. SOCKETS

Pin Sockets, pins in strips of 100. Just snap off what you need. 65p per strip

Dual in line *

8 pin 13p.	24 pin 26p.	TOS
14 pin 15p.	28 pin 30p.	8 pin 31p.
16 pin 15p.	36 pin 39p.	10 pin 35p.



The AY-51224 tick-tock

Another marvel from G.J.L. A 16 pin 12-24 hr. Clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p (inc. VAT) (Leaflet alone 20p.) Full Kit (excluding case) available towards end of 1975. Phone Clive for details.



LINE-O-LIGHT

NEW LED Linear Curators each device contains 10 light emitting diodes in a 20-pin dual-in-line package. Ideal for solid state analogue meters or dials Red and Green £3.19*. Check on Yellow some in stock now



DISPLAYS

Can/M/A Dec. p. 1
Can/M/A Dec. p. 2
Can/M/A Dec. p. 3
Can/M/A Dec. p. 4
Can/M/A Dec. p. 5

all £1.82* each (Red only)
all £1.49* Each (Red, green, yellow, Orange)
all £2.32* Each (Red, Green, Yellow, Orange)
all £2.42* Each (Red only) C/C as C/A
0.6 Xciton Red £1.79; green and yellow £2.42

PHOTO-DARLINGTON

Vceo 25v 2N5777
Vcbo 25v
Vbeo 8v
I1 250 mA
Pd 200 mW
Hfe 2500


Low cost Red GaAsP Motorola MLED 500 in a T092 package

35p*



MULLARD MODULES

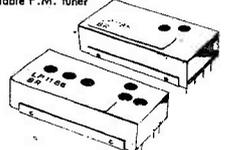Still make the simplest, highly reliable F.M. tuner



LP186 Varactor front end £7.74
LP185 i.F. Strip £6.25
LP1400 Multiplex decoder £8.12

OPTO-ISOLATORS

111 4N25 or TL1116
6 pin Industry standard package
2.5KV Isolation £1.21*


TRANSFORMERS

Secondaries	Transformers	1A	2A	4A
6-0-6 100mA 99p*	0-9-17V -	£2.49*	£3.57*	£4.55*
9-0-9 100mA 99p*	0-12-15-20-24-30V -	£3.47*	£4.65*	-
12-0-12 100mA 99p*	0-24-30-40-48-60V -	£5.18*	£7.02*	-
20-0-20 1A £3.45*	0-19-25-33-40-50V £3.47*	£4.65*	£7.24*	-
24-0-24 0.5A £2.95*				
28-0-28 1A £3.95*				

P & P on transformers 20% of price, min. 25p.

3 1/2 DECADE DVM I.C.

3 1/2 DECADE DVM I.C.

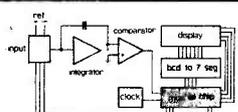

This state-of-the-art MOS LSI chip contains all the logic necessary for a 3 decade, dual slope integrating, automatic polarity detecting DVM. Supplied with free data and circuit booklet. AY-5-3507

OUR PRICE ONLY £6.59*
(Data and Circuit Booklets alone 20p.)

Short Form Catalogue

for your free copy send a S.A.E.

Latest prices, latest devices, lots of new items, lots of data, all for 35p.

VAT INC

Items followed by * inc. VAT at 8% all others include 12 1/2%
Overseas customers deduct 2/3 from * items - 1/3 from others
Postage and Packing 25p Orders for over £6, post free. Except transformers

'THE MEN FROM THE BOYS!'

The current 11 year Sunspot Minima is causing poor Short Wave Communication. Despite this, G4DJY established 2 way communication with no less than 68 North Americans in the recent A.R.R.L. 2 day contest. Peter used the PARTRIDGE SYSTEM 'A' (£32.40 del.), the fast selling 7' 6" WORLD RECORD aerial system for modern receivers and low power transceivers. Delivery by mail, ex stock.

TRANSMITTING AMATEURS

————— If a PARTRIDGE SYSTEM 'A' can work FOUR CONTINENTS using 'FLEA POWER' in poor Sunspot conditions, then surely it must be false economy these days to use expensive QRO to overcome the defects of an aerial.

Send stamp for full details of this and other PARTRIDGE SYSTEMS and accessories.

PARTRIDGE SUPER PACKAGE

Send stamp for details and expert advice.

COMPLETE RADIO STATION FOR ANY LOCATION. Comprising: Trio QR666 Gen. Cov. RX, Headphones VFA., System "A" all connecting cables, del. (our Risk) ASSEMBLED IN SECONDS! SAVE £11.06. SECURICOR DELIVERY (OUR RISK).

£189.00

PHONE 0843 62535 (OR 62839 AFTER OFFICE HOURS)
JUST TELEPHONE YOUR CARD NUMBER

BOX 5



OVERCOME YOUR PROBLEM— GIVE US A RING!

G3CED G3VFA



J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln, LN2 1JF

Telephone: 20767

1000uf 40v.w. ELECTROLYTICS size 1 1/2 x 1 1/2 @ 3 for 35p.
 60 ASSORTED WIRE WOUND RESISTORS 1 to 10 Watt @ 57p.
 20 SILICON NPN PHOTO TRANSISTORS Untested for £1.
 GERMANIUM TRANSISTORS AC 138 @ 10p, AC 141K, AC 142K, AC 153K, AC 176K, AC 187K, AC 188K. All at 20p each.
 POSTAGE STAMP TRIMMERS 10pf, 30pf, 50pf, 150pf, 750pf, 1000pf @ 6p each.
 20 ASSORTED TUNING VARACTOR DIODES Untested @ 45p.
 400 PIV 1 Amp SHORT LEAD DIODES IN 4004 12 for 40p.
 SN 7511 VIDEO AMPLIFIER I.C. @ 30p each.
 10 MINIATURE 10 Amp SILICON BRIDGES Untested @ £1.25.
 ITT PMT2R FILM CAPACITORS 1.5uf 100v.w. @ 6 for 30p.
 50 ASSORTED TRANSISTOR ELECTROLYTICS @ 57p.
 VHF DUAL GATE MOS FET LIKE 40673 @ 33p, 4 for £1.10.
 PLASTIC THYRISTORS 50 PIV 6 Amp @ 15p, 40 PIV 6 Amp @ 40p.
 F.M. I.C.'s like TAA 570 Untested with data @ 5 for 57p.
 50 AC 128 TRANSISTORS Branded but untested @ 57p.
 BD 187 4 Amp 1/2 POWER TRANSISTOR 40p, 4 for £1.35.
 BATTERY CHARGER AMMETERS 2, 3, 4, 6 Amp. All at 66p each.
 100 ASSORTED 1/2 and 1/3 Watt RESISTORS 17 different values @ 57p.
 500 YD REEL OF PVC 1/4 STRAND -0048 CABLE @ £3.
 50 ASSORTED RADIO and TV KNOBS @ 75p.
 300 to 500 ASSORTED POLYESTER CAPACITORS @ £1.
 OCTAL PLUG-IN MODULES with 2 300 PIV 1 Amp Diodes @ 12p.
 SUB-MINIATURE DISC CERAMICS 50v.w. 5.6pf, 6.8pf, 22pf, 33pf, 100pf, 150pf, 270pf, 1000pf, 2200pf, 4700pf, .01uf. All at 20p doz.
 POWER TRANSISTORS MP 8112 NPN @ 15p, MP 8512 PNP @ 15p.
 HIGH SPEED 40 kHz STACKED SOLAR CELLS .5 volt 250uA. 6 in a row @ 45p.
 VHF POWER TRANSISTORS Unmarked Good 2N 3866 @ 40p each. 3 for £1.
 FERRANTI ZTX 108 TRANSISTORS 6 for 57p.
 20 ASSORTED BRANDED 250m-W ZENERS @ 75p.
 TV POWER TRANSISTORS R2008 @ 75p, R2010B @ £1.25.
 SILICON SOLAR CELLS .5 volt 15mA @ 35p, .5 volt 50mA @ 50p, .5 volt 100mA @ 60p, .5 volt 200mA @ £1.
 10 SILICON 10 Amp SUB-MINIATURE BRIDGE RECTIFIERS Untested for £1.25.
 NPN to 35 POWER DARLINGTON TRANSISTORS @ 20p each.
 Please add 20p post and packing on orders under £2

SOUTHERN VALVE COMPANY

P.O. Box 144, BARNET, Herts.

New, 90 day guaranteed valves of many popular makes. Postage 9p 1st, 7p additional valves, max 50p.
 Telephone: 01-440 8641.

ALL NEW & BOXED VALVES (Incl. tax)

AZ31	65p	EZ40/1	50p	PD500	28.25	UL84	44p
DY86/7	36p	EZ80	35p	PFL200	78p	UY85	35p
DY802	48p	EZ81	30p	PL36	68p	UY25	75p
EB91	18p	G7601	80p	PL81	50p	UY26	82p
ECC81	35p	GZ20	45p	PL81A	54p	UY81	70p
ECC82	34p	PC85	65p	PL82	38p	6/80L2	70p
ECC88	84p	PC88	68p	PL83	45p	8/W7	68p
ECC85	40p	PC97	40p	PL84	48p	6F28	70p
ECC88	47p	PC900	48p	PL500		6F28	68p
EOH42	72p	PC84	40p	PL504	75p	6V6	47p
EOH81	36p	PC85	65p	PL508	83p	10F1	68p
EOH83	32p	PC88	62p	PL809	£1.80	30L1	80p
EOH84	62p	PC89	62p	PL819	£2.80	30P4	85p
ECL80	52p	PCF189	58p	PL802	£2.00	30C1	40p
ECL82	47p	PCF80	40p	PY83	52p	30C15	78p
ECL83	68p	PCF82	50p	PY81/3	41p	30C17	78p
ECL86	48p	PCF86	58p	PY88	41p	30C18	£1.21
EF80	30p	PCF200	95p	PY800	41p	30F8	75p
EF85	37p	PCF801	50p	PY801	41p	30FL1	
EF86	52p	PCF82	65p	PY802	41p	30FL2	97p
EF89	35p	PCF805	£1.21	PY500A	£1.00	30L1	40p
EF188	37p	PCF806	54p	UBF89	40p	30L15	78p
EF194	37p	PCF808	£1.12	UC85	46p	30L17	78p
EH90	66p	PCF200	77p	UCH42	72p	30P12	75p
EL84	53p	PCL82	37p	UCH81	42p	30P19	70p
EL41	69p	PCL83	50p	UCL82	42p	30PL1	£1.35
EL84	35p	PCL84	47p	UCL83	50p	30PL13	75p
EL90/1	47p	PCL85	62p	UF41	68p	30PL14	85p
EM84	47p	PCL805	62p	UF89	42p	30PL15	85p
EY51	47p	PCL86	50p	UL41	72p	30P4MR	90p
EY86/7	38p	PCL200	£1.15				

We offer return of post service. Post free over £10.00.
 Most other types available.

Items in stock at time of going to press but subject to possible market fluctuations if unavoidable.

TRADE. Representative will call West Country & S. Wales, also Suffolk, Norfolk, Hunts, etc.

Enquiries s.a.e. DISCOUNT PRICES, CWO only.

One valve post 9p, each extra valve 7p (maximum 50p) LISTS s.a.e. please. VAT @ 12 1/2% incl.

ENGINEERS

FREE



YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE



CUT OUT THIS COUPON

Tick or state subject of interest.
 Post to address below.

- | | | |
|--|--|---|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Radio, Servicing & Repairs | <input type="checkbox"/> Painting & Decorating |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT) | <input type="checkbox"/> Radio Amateur's Exam. | <input type="checkbox"/> MECHANICAL |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> A.M.S.E. (Mech.) |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> Motor Mechanics | <input type="checkbox"/> General Mech. Eng. |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> C. & G. Motor V. Mechanics | <input type="checkbox"/> Inst. Engineers & Technicians |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> General Auto Engineering | <input type="checkbox"/> Maintenance Engineering |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Welding |
| <input type="checkbox"/> RADIO & TELECOMMUNICATIONS | <input type="checkbox"/> Heating, Ventilating & Air Conditioning | <input type="checkbox"/> MANAGEMENT & PRODUCTION |
| <input type="checkbox"/> Colour TV Servicing | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> Computer Programming |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> DRAUGHTSMANSHIP & DESIGN |
| <input type="checkbox"/> Radio & TV Engineering Course | <input type="checkbox"/> Plumbing Technology | <input type="checkbox"/> General |
| | <input type="checkbox"/> General Building | <input type="checkbox"/> Draughtsmanship |
| | | <input type="checkbox"/> A.M.I.E.D. |
| | | <input type="checkbox"/> Electrical |
| | | <input type="checkbox"/> Draughtsmanship |



G.C.E.

—58 'O' & 'A' Level Subjects
 —over 10,000 Group Passes!

Aldermaston College

Dept. TPW 19, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

Postcode

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

SINCLAIR IC20
IC20 10W + 10W stereo IC amplifier kit with free booklet and printed circuit £4.95.
PZ20 Power supply kit for the above £3.95.
VP20 Volume, tone-control and preamp kit £7.50.
SP20 10W 4 ohm speaker for IC20 £2.70.
CS20 11 x 6 x 3ins attractive case for IC20 £2.95*.

Send sae for free leaflet.

JC12 AMPLIFIER
6W IC audio amp with free data and printed circuit £1.95*



DELUXE KIT FOR JC12

Includes extra parts for the pcb and vol, bass and treble controls for mono version £2.06. Stereo model with balance control £4.46.

JC12 POWER KIT
Supplies 25V 1Amp £3.25.

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono £1.40. Stereo £2.90. Type 2 for ceramic or crystal pickups. Mono 78p. Stereo £1.56.

LOUDSPEAKERS FOR JC12
8in x 5in 8 Ohms 5W £2.28.

SEND SAE FOR FREE LEAFLET ON KITS.

FERRANTI ZM414

IC radio chip with data £1.34. Printed circuit and extra parts for radio £3.25. Case 80p extra. Send sae for free leaflet.

SINCLAIR PROJECT 80

FM tuner £13.25. Q16 £9.50. PZ5 £3.95. PZ6 £8.70. PZ8 £9.10. Trans for PZ8 £5.60. Z40 £5.75. Z60 no longer available, but we stock a similar 30W equivalent amp £10.30. Stereo 80 £11.95.
Project 80S £18.95. Quad decoder £14.95

PRINTED CIRCUIT KIT £3.95*

Make your own printed circuits. Contains etching dish, 200 sq. ins. of copper clad board, 1 lb ferric chloride, etch resist pen, small drill bit, laminate cutter and instructions.

MAINS TRANSFORMERS

6-0-6V 100mA 86p. 9-0-9V 100mA 86p. 18V 1A £1.65*. 0, 12, 15, 20, 24, 30V 1A £2.95*. 12-0-12V 1A £1.95*. 0, 12, 15, 20, 24, 30V 2A £4.20*. 20V 2.5A £2.00. 6 and 9V trans are DC rated, others are AC volts.

SINCLAIR BLACK WATCH

Fully assembled with black strap £20.95*. With bracelet £22.95*.



SINCLAIR CALCULATORS*

Cambridge £4.95. Cambridge % £7.35. Scientific £8.95. Cambridge Scientific £11.45. Oxford 100 £4.95. Oxford 300 £13.50. Programmable Scientific £25.95. Mains adaptors—for programmable and Oxfords £3.19; for Camb. and scientific £3.15.

CBN CALCULATORS*

778MD 7 digit/1/2% memory £5.95. 796MD 8 digit/1/2% memory £6.45. 897D 8 digit/1/4% function memory £7.60. SR7919D 8 digit/memory/trig/10p/pi/powers/scientific notation £13.20. SR1800 10 digit scientific £23.25. SR4148R 14 digit rechargeable scientific with charger £29.95. Mains adaptor for other machines £2.95.

CASIO CALCULATORS*

Pocket 6S 8 digits/1/2% const £6.95. Memory 8R 8 digit/1/2% memory/const £8.95. Pocket Mini P-310 8 digits/1/2% memory/const/miniature fits into your shirt pocket £8.95. FX20 8 digit/memory/trig/10p/pi/powers/scientific notation £18.95. Mains adaptors for all models £3.95.

NOVUS CALCULATORS*

750 6 digit £5.45. 835 8 digit/1/2% const/sq. root/4 function memory £7.60. 4525 10 digit programmable scientific calculator £45.90. 4510 £21.20. 4515 £37.65. 4520 £22.65. Mains adaptor £4.20.

24 HR DIGITAL CLOCK KIT*

Includes pcb, mains power supply, attractive case. 0.5in jumbo green display, clock chip, and all other parts. Displays hours and minutes separately by a pulsating colon. Kit £10.95. Built £12.50. Send sae for free leaflet. Built with alarm £13.95.

S-DECS AND T-DECS*

S-DeC £2.24

T-DeC £4.05

U-DeC A £4.45

U-DeC B £7.85

N-DeC £10.45

IC carriers:—

16 dil: plain £1.07

with socket £2.21

10 TO5: plain 99p, with socket £1.95.

SST1 60p. SSU1 60p. SSM1 80p.



BATTERY ELIMINATOR BARGAINS

35 WAY SUPER

New switched model. 3 to 30V in 1V steps. Fully stabilized. 1A output. Kit £7.95. Assembled £10.95. 2 Amp model. Kit £9.95. Built £12.95.



6-WAY SPECIAL

Switched output of 3/4, 6/7 1/2, 9/12V at 500mA with 4-way multi-jack plug and free matching socket £5.20.

6-WAY DOUBLE RADIO MODEL £5.20

Similar to above, but with press-stud battery connectors. 3 + 3/4 + 4 1/2 + 6 1/2 + 7 1/2 + 9/12 + 12V at 250mA. Also gives 15/18/24V single.

3-WAY MODEL

Switched output of 6 1/2/9V at 250mA with 4-way multi-jack plug and free matching socket £2.95*.

RADIO MODELS

50m with press-stud battery connectors for radios etc. 9V £3.25. 6V £3.45. 9 + 9V £4.45. 6+6V £4.45. 4 1/2 + 4 1/2V £4.45. Also 9V 300mA £3.95.

CASSETTE MAINS UNITS

7 1/2V output to run cassette recorders from the mains. Complete with 5 pin DIN plug. 50mA model £3.45. 300mA model £3.95.

CAR CONVERTORS

Input 12V DC. Output 6 1/2/9V DC 1A regulated £3.95*.

BATTERY ELIMINATOR KITS

Send sae for free leaflet on range. 100mA radio type with press stud battery terminals. 4 1/2V £1.80. 6V £1.80. 9V £1.80. 50mA double radio type with press stud terminals. 4 1/2 + 4 1/2V £2.50. 6 + 6V £2.50. 9V + 9V £2.50. 100mA cassette type with 5 pin DIN plug. 7 1/2V £1.80. Stabilized 8-way type with voltage stabilizer to give low hum. 3/4/6 1/2/9/12/15/18V 50mA £2.95. Heavy duty 12-way types 4 1/2/6 1/2/11/13/14/17/21/28/34/42V. 1Amp £3.95. 2 Amp £5.95.

SWANLEY ELECTRONICS

Dept. PW, PO Box 68, Swanley, Kent

Post 30p on orders under £2, otherwise free. Prices include VAT. (Overseas customers deduct 7% on items marked *, otherwise 10%). Official orders from schools, government labs, etc. welcome.

Greenbank Electronics (Established 1970)

DIGITAL CLOCK MODULES, KITS

'E' LED DISPLAYS
DL-704E 0.3" 70p
DL-707E 0.3" 70p
DL-728E 2 x 0.5" £1.80
DL-727E 2 x 0.5" £1.80

DL-750E 0.6" £1.50
DL-747E 0.6" £1.50
PHOSPHOR DISPLAYS
5LT01 4 x 0.5" £5.80

CLOCK CHIPS
AY-5-1224A £3.50
MK 50253 £5.30
AY-5-1202 £4.76

OP-AMPS
CA 3130 (COS/MOS) 75p
741 Minidip 25p
IC SOCKET PINS
100 50p
1000 £4.00

CMOS WITH DISCOUNTS! (Any mix: disc. 10% 25+, 25% 100+)

CA 3130	0.75	4030/14057	0.45	4059/	—	3.60	4098/14528	0.85	14532/4532	1.60
4000/14000	0.15	4031/	1.80	4060/	—	0.90	4099/	1.50	14534/	6.00
4001/14001	0.15	4032/14032	0.85	4061/	—	16.40	4700/	1.50	14536/	2.85
4002/14002	0.15	4033/	1.10	4062/	—	7.30	7083/	4.25	14537/	15.25
4006/14006	0.95	4034/14034	1.55	4063/	—	0.90	14501/	0.15	14539/	1.05
4007/14007	0.15	4035/14035	0.95	4066/14066	0.55	14502/4502	1.00	14541/	1.80	
4008/14008	0.75	4036/	1.80	4067/	—	2.95	14505/	3.30	14543/	1.50
4009/14009	0.45	4037/	0.75	4068/14068	0.15	14506/	1.35	14549/	2.95	
4010/14010	0.45	4038/14038	0.85	4069/14069	0.15	14508/4508	2.35	14552/	8.05	
4011/14011	0.15	4039/	2.85	4070/14070	0.15	14510/4510	1.10	14553/	3.50	
4012/14012	0.15	4040/14040	0.85	4071/14071	0.15	14511/4511	1.25	14554/	1.20	
4013/14013	0.45	4041/	0.65	4072/14072	0.15	14512/	1.05	14555/4555	0.70	
4014/14014	0.80	4042/14042	0.65	4073/14073	0.15	14514/4514	2.55	14556/4556	0.70	
4015/14015	0.80	4043/14043	0.80	4075/14075	0.15	14515/4515	2.55	14557/	3.20	
4016/14016	0.45	4044/14044	0.75	4076/14076	1.25	14516/4516	1.10	14558/	0.90	
4017/14017	0.80	4045/	1.15	4077/14077	0.15	14517/	5.40	14559/	2.95	
4018/	—	4046/14046	1.10	4078/14078	0.15	14518/4518	1.00	14560/	2.95	
4019/14019	0.45	4047/	0.70	4081/14081	0.15	14520/4520	1.00	14560/	1.55	
4020/14020	0.90	4048/	0.45	4082/14082	0.15	14521/	2.00	14561/	0.45	
4021/14021	0.80	4049/14049	0.45	4085/	—	0.55	14522/	1.50	14562/	5.25
4022/14022	0.75	4050/14050	0.45	4086/	—	0.55	14524/	N/S	14566/	1.20
4023/14023	0.15	4051/14051	0.75	4089/	—	0.65	14526/	1.50	14572/	0.35
4024/14024	0.60	4052/14052	0.75	4093/14093	0.65	14527/4527	1.20	14580/4018	6.00	
4025/14025	0.15	4053/14053	0.75	4094/	—	1.50	14528/4098	0.85	14581/40181	3.05
4026/	—	4054/	0.95	4095/	—	0.85	14529/	1.30	14582/40182	1.15
4027/14027	0.45	4055/	1.05	4096/	—	0.85	14530/	0.65	14583/	0.71
4028/14028	0.70	4056/	1.05	4097/	—	2.95	14531/	1.25	14585/	1.45
4029/	—	4057/	20.35							

Terms: C.W.O. Add VAT to all prices at 8%. Post etc., U.K. 10p per order. Orders processed same day. Official govt., 'varsity, poly etc. orders welcomed.

GREENBANK ELECTRONICS (Dept. W7P)

94 New Chester Road, New Ferry, Wirral, Merseyside, L62 5AG, England. Tel:—051-645 3391

RECHARGEABLE BATTERIES

CAN SAVE YOU A FORTUNE!
Bush & Meissner's two purpose-built battery chargers for economy minded enthusiasts:

The "KESTREL-DOWN" Charger £10.69 & £11.77 for Alkaline rechargeable batteries, no-load voltage of 1.5volts per cell, for the following sizes ALKALINE (All prices include VAT)

Equivalent	Type	Capacity	PRICE
U2 size	SA-13D	2Ah	£2.37
U7 size (pencil)	SA-15AA	0.3Ah	£0.78p

NICKEL-CADMIUM (All prices include VAT)
The "DAIMON" Charger £9.98

for Nickel-Cadmium batteries, no-load voltage of 1.25 volts per cell, for the following sizes

Type	Capacity	PRICE
NCC400	4Ah	£4.74
NCC200	2Ah	£3.20
NCC50	0.5Ah	£1.65

Battery containers extra 44p to 83p each

Charger designed to give optimum results with a specific type of cell. Never be without power, day or night.

*Note, under no circumstances must Alkaline batteries be used with the Daimon charger.

S.A.E. brings full details

Bush & Meissner

Importers & Distributors
Dept. L5260
275 West End Lane,
London
NW6 1QS
01-794-9611



SAXON ENTERTAINMENTS LTD

**NOW ALSO AT WALLINGFORD
WITH SALES & SERVICE 6 DAYS A WEEK**

(BETWEEN READING)
and OXFORD

**FLINT HOUSE HIGH ST
WALLINGFORD OXON OX10 0DE
Phone (0491) 35529**

A423 Henley M4 to London & M40

A 329

FLINT HOUSE

Reading M4 to Wales
A413 Didcot

POWER AMPS AT LOWER* PRICES MODULE RANGE FROM 30 TO 110W R.M.S.



SA.1208 (120w r.m.s./8Ω/95V) £19.50
SA.1204* (120w r.m.s./4Ω/75V) £13.50
SA.608 (60w r.m.s./8Ω 65V) £12.50
SA604* (60w r.m.s./4Ω/50V) £10.50
SA.308 (30w r.m.s./8Ω/50V) £9.50

- Only 4 connections
- Distortion typically 0.4%
- Single supply rail
- Input—240mV
- Size—6" x 3" x 1"
- Individually tested & grntd.

POWER SUPPLIES FOR

- 1 x SA.1208—PM.1201/8 £11.60
- 2 x SA.1208—PM.1202/8 £15.30
- 1 x SA.1204—PM.1201/1 £11.60
- 2 x SA.1204—PM.1202/4 £15.30
- 1 or 2 x SA.608—PM.601/8 £10.50
- 1 or 2 x SA.308—PM.301/8 £8.80

SAXON EQUIPMENT IS DESIGNED AND MADE IN OUR OWN CROYDON FACTORY

SYSTEM 7000 CONTROL UNIT



- Ready to plug in—no soldering at all
- Stainless steel front panel
- Inputs for 2 ceramic cartridges/tape/microphone
- Individual deck controls AND left/right fader
- Low noise (−80dB) 20Hz −50kHz ± 1dB
- ½ watt headphone monitor
- CONTROLS—Master, Monitor, Volume, Selector X-fade, etc.

READY BUILT
MONO £34.50
STEREO £49.50

MODULAR PCB with all electronics
Mono £18.50
Stereo £27.50
Front panel £3.50


SAXON CENTAUR 100W RMS

STEREO SOUND-LIGHT MOBILE DISCO
Today's most challenging value—with sound-light converter, synchronous motor twin turntables, and features that give you professional levels of operation, it still costs under £200 (V.A.T. extra). With full-range heavy duty speakers which pack to make a single complete transportable unit. ABSOLUTELY COMPLETE INC. HEADPHONES, CONDENSER MIC. & CONNECTING CABLES.

- 4-channel sound/light converter, variable speed
- X-fade and P.F.L.
- Tape & mic. inputs
- Strong wood cabinets, Vynidex covered

£199.00

Delivered U.K.

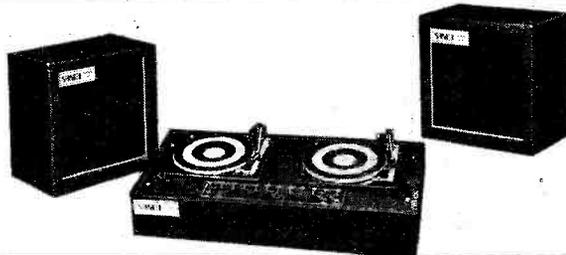


MINOTAUR 100

100 WATT RMS TOTAL
RANGE AMPLIFIER

Compatible with all Saxon System 7000 units, this is a superb amplifier readily adaptable to a wide range of applications

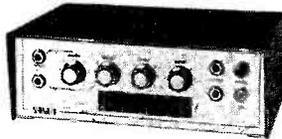- 100W r.m.s. into 8 Ω.
- Two mixed inputs, wide range bass and treble controls
- May be operated as a slave amplifier
- Extremely compact (27cm x 16cm x 10cm)



- Fully protected against all incorrect loads and short circuits
- Plug isolated terminals
- Silver anodised fascia

£49.50

SYSTEM 7000 LIGHTING CONTROL

- Full control of 3kW of lights (1kW/channel)
- Audio control plus sequence plus override
- Variable speed sequence
- Stainless steel two tone panel—matches mixer
- Operates from any amplifier
- Attractive Bondene case—free standing or panel mounting
- Inc. case and plug—ready to use

£38.00



SUPERFECT MODULE
On P.C.B. panel mounting £27.75

SOUNDLITE 3KW
CONVERTER
Use with any amp. £15.50

SYSTEM 7000 MODULAR MIXING

- Inputs for all sources inc. mag. cartridge
- Wide range bass and treble controls
- ½W monitor power outlet
- Echo send/return facility
- Feeds most amplifiers
- With front panels, ready to use
- Individual monitor buttons

INPUT		MIXER	
Mono	£8.50	Mono	£8.50
Stereo	£12.00	Stereo	£12.00

PCB Modules only		PCB Modules only	
Mono	£5.50	Mono	£5.50
Stereo	£9.00	Stereo	£9.00



SAXON STROBES & LIQUID WHEEL

SUPERSTROBE AT NEW LOW PRICE
 ■ 1 flash/2 secs.—up to 20/sec.
 ■ Compact black Bondene case
 ■ Ideal for mobile disco or smaller club
 NOW ONLY £17.50

PRO-STROBE
 ■ Giant 80 watt tube
 ■ Discharge energy up to 6 Joules
 ■ External trigger—audio up to 240w
 NOW ONLY £29.50

150 WATT LIQUID WHEEL PROJECTOR
 ■ Complete with wheel and 150 watt tungsten lamp
 ■ Wide range of extra effects may be attached. Spare wheels £4.90
 £29.20



Loudspeakers 12"/50W high grade chassis units: 14000 gauss: presence dome: £14.50

Cabinets Attractive range of speaker and other cabinets at our showrooms. Enquiries welcomed.

ACCESSORIES Mics: Headphones: Special Lamps.

PRICES include carriage and packing. VAT must be added to all orders at 8%. C.O.D. 65p extra. S.A.E. with all enquiries please.

Send or phone your ACCESS or BARCLAYCARD No. for prompt attention. After 4.0 p.m. leave your message on our answer-phone.

Orders by post—Please make cheques or crossed P.O.'s payable to
SAXON ENTERTAINMENTS LTD.
 327-333 WHITEHORSE ROAD, CROYDON, SURREY CR0 2HS
 Telephone: 01-684 0098 /6385
 Shop Hours 9am-5pm (Lunch 12.30-1.30); Sat. 9.30am-5pm. Prices and specifications subject to alteration without notice. Mail Order desk 10am-4pm Mon-Fri.

TRADE ENQUIRIES
 NORMAN ROSE (ELECTRICAL) LTD.
 London 01-837 9111
 Birmingham 021-236 4710
 Manchester 061-273 1498
 Bradford, Yorks. 0274 26104

Sparkrite mk2

Capacitive discharge
electronic ignition

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept., iP/W/7
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY NEEDED	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		Cheque No.
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		Send SAE if brochure only required.

Random FLASHER UNIT
Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random **£18.95**

TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH
14 1/2 inches **UNIT**
B.C. Fitting **£9.55**
EACH
E.S. Fitting **£10.35**
EACH

Sound to Light MASTER UNIT 600 WATTS PER CHANNEL
£30.95
INCLUDING CHANNEL
OUTPUT PLUGS AND
MAINS INLET SOCKET.

TYPE A SPOT
(less lamp)
B.C. Fitting **£1.95** EACH
E.S. Fitting **£2.12** EACH

TYPE B 3 BANK UNIT
(Less Lamps)
B.C. Fitting **£6.90** EACH
E.S. Fitting **£7.26** EACH

TWIN BANK 12 LIGHT UNIT
Length 31 1/2
(less lamps)
B.C. Fitting **£15.60** EACH
E.S. Fitting **£17.00** EACH

100 WATT SPOT LAMPS
RED, YELLOW, GREEN
BLUE
CLEAR **£1.18** each
Minimum 3 lamps
£3.54
B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. and POST & PACKING
(These prices apply to the United Kingdom only)

ALBEN ENGINEERING CO. LTD.
DEPT P W THE CRESCENT, WORSTHORNE,
BURNLEY, LANCS. Tel Burnley 20940

Send 20p for illustrated leaflet & price list.

poly-planar
20-Watt Full Range Speaker

Completely replaces the
conventional cone speaker
Super-thin construction
permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input Impedance:
8 ohms. Operating temperature range: -20°F to +175°F. Size
(WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£8.50 each Stereo pair £16.50
INCLUSIVE OF VAT AND POSTAGE

web europa
P.O. Box 9, Ruthin Clwyd

PRACTICAL WIRELESS T.V. SOUND TUNER
(Nov. 75 article by A. C. Ainslie)

IF Sub-Assembly (G8) **£6.80**. P & P 55p.
Mullard ELC1043 Varicap UHF Tuner **£4.20**. P & P 30p.
3-way Station Control Unit **£1.20**. P & P 25p.
6-way Station Control Unit (Special Offer) **£1.00**.
Resistors, Caps, Semiconds etc. **£5.22**. P & P 55p.
Printed Circuit Board **£1.00**. P & P 25p.
Mains Transformer **£2.50**. P & P 50p.

Add 12 1/2% VAT to price of goods. P & P all items 65p.
Copy of original article supplied on request

Callers welcome at shop premises.

MANOR SUPPLIES
172 WEST END LANE, LONDON NW6
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

15-240 Watts!

HY5 Pre-amplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4-7kΩ at 1kHz.


OUTPUTS: Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble ± 12dB at 10kHz; Bass ± at 100Hz.

DISTORTION: 0-1% at 1kHz. Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up. SUPPLY VOLTAGE ± 16-50V.

Price £4.75 + £1.19 VAT P&P free.

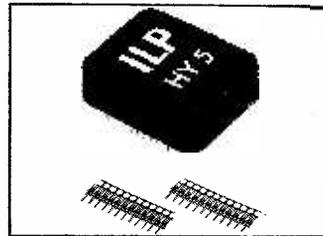

HY30 15 Watts into 8Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8Ω; **DISTORTION** 0-1% at 1-5W.

INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

SUPPLY VOLTAGE ± 18V.

Price £4.75 + £1.19 VAT P&P free.

**Available
June '76**

HY50 25 Watts into 8Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


SPECIFICATIONS: INPUT SENSITIVITY 500mV

OUTPUT POWER 25W RMS into 8Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0-04% at 25W

at 1kHz **SIGNAL/NOISE RATIO** 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

SUPPLY VOLTAGE ±25V **SIZE** 105 50 25mm

Price £6.20+£1.55 VAT P&P free.

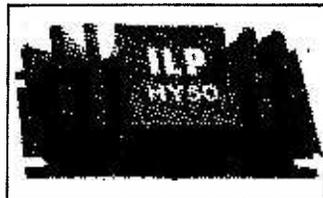

HY120 60 Watts into 8Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS

INPUT SENSITIVITY 500mV.


OUTPUT POWER 60W RMS into 8Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0-04% at 60W

at 1kHz **SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB

SUPPLY VOLTAGE ±35V

SIZE 114 50 85mm

Price £14.40+£1.16 VAT P&P free.

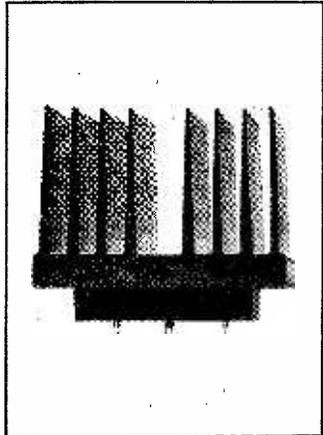

HY200 120 Watts into 8Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0-05% at


100W at 1kHz.

SIGNAL/NOISE RATIO 96 dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

±45V

SIZE 114 100 85mm

Price £21.20+£1.70 VAT P&P free.

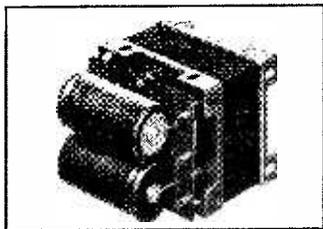

HY400 240 Watts into 4Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4Ω! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS

OUTPUT POWER 240W RMS into 4Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0-1% at

240W at 1kHz

SIGNAL NOISE RATIO 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

±45V

INPUT SENSITIVITY 500mV **SIZE** 114 x 100 x 85mm

Price £29.25+£2.34 VAT P&P free.

POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus £1.19 VAT. P/P free.

PSU50 suitable for two HY50's £6.20 plus £1.55 VAT. P/P free.


PSU70 suitable for two HY120's £12.50 plus £1.00 VAT. P/P free.

PSU90 suitable for one HY200 £11.50 plus £0.92 VAT. P/P free.

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel. (0227) 63218

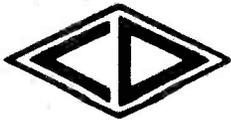Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name and Address _____
Signature _____



CHINAGLIA

INTRODUCING THE

DOLOMITI

20kΩ/V a.c. and d.c.

A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED


Accuracy: D.C. ranges, ± 2.0%, A.C. & Ω ranges ± 2.5%.

39 ranges: d.c.V, 0-150mV, 500mV, 1.5V, 5V, 15V, 50V, 150V, 500V, 1.5kV; d.c.I. 0-50μA, 500μA, 5mA, 50mA, 0.5A, 5A; a.c.V, 5V, 15V, 50V, 150V, 500V, 1.5kV; a.c.I, 5mA, 50mA, 0.5A, 5A; dB -10 to +65 in 6 ranges; Ω 0-0.5kΩ, 5kΩ, 50kΩ, 500kΩ, 5MΩ, 50MΩ; pf 50kpf, 500kpf.

Automatic overload protection and high current range fusing.

Scale mirror and fine pointer for accuracy of reading. Single knob main range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 650g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

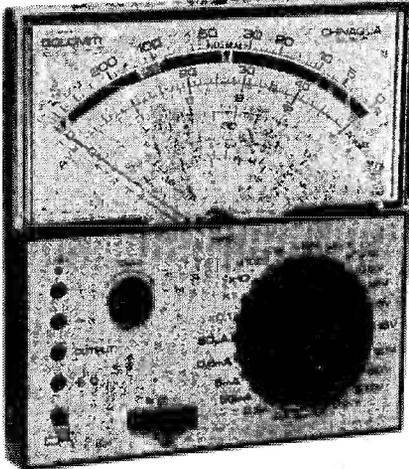Meter £33.15 incl. VAT (80p P. & P.) 30kV Probe £10.80 incl. VAT



For details of this and the many other exciting instruments in the Chinaglia range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

ALCON

 Instruments Ltd.

91 MULBERRY WALK . LONDON SW3 6DZ TEL: 01-352 1897

Get a great deal from

Marshall's

A Marshall (London) Ltd Dept: PW

42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2 Telex: 21492

& 85 West Regent St, Glasgow G2 2QD Tel: 041-332 4133

& 1 Straits Parade Fishponds Bristol BS16 2LX Tel: 0272-654201/2

& 27 Rue Danton Issy Les Moulineaux Paris 92

Catalogue price 30p

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linears

CA3020A	£1.80	CD4049	45p	NE555V	70p	SN7446	84p	SN74153	68p
CA3028A	79p	CD4050	45p	NE556	£1.30	SN7447	80p	SN74154	£1.20
CA3035	£1.37	CD4510	£1.25	NE560	£4.48	SN7448	90p	SN74157	76p
CA3046	70p	CD4511	£1.94	NE565	£4.48	SN7450	16p	SN74161	88p
CA3048	£2.17	CD4516	£1.25	SL414	£2.35	SN7451	16p	SN74162	88p
CA3052	£1.62	CD4518	£1.87	SL610C	£2.35	SN7453	16p	SN74163	88p
CA3089E	£1.96	CD4520	£1.87	SL611C	£2.35	SN7454	16p	SN74164	£1.60
CA3090Q	£4.23	LM301A	48p	SL620C	£2.35	SN7460	16p	SN74165	£1.60
CA3130	88p	LM308	£1.17	SL620C	£3.50	SN7470	29p	SN74167	£3.30
CD4000	18p	LM309K	£1.88	SL621C	£3.50	SN7472	21p	SN74174	99p
CD4001	18p	LM380	98p	SL623C	£5.75	SN7473	31p	SN74175	70p
CD4002	18p	LM381	£2.07	SL640C	£4.00	SN7474	30p	SN74176	£1.14
CD4006	99p	LM702C	75p	SN7400	16p	SN7475	45p	SN74180	£1.10
CD4007	18p	LM709	38p	SN7401	16p	SN7476	30p	SN74181	£1.95
CD4008	82p	T099	38p	SN7402	16p	SN7480	42p	SN74190	£1.86
CD4009	52p	8D1L	45p	SN7403	16p	SN7481	£1.00	SN74191	£1.86
CD4010	52p	14D1L	38p	SN7404	19p	SN7482	65p	SN74192	£1.15
CD4011	18p	LM710	47p	SN7405	19p	SN7483	82p	SN74193	£1.15
CD4012	18p	LM723C	66p	SN7406	36p	SN7484	95p	SN74196	£1.80
CD4013	45p	LM741C	40p	SN7407	36p	SN7485	£1.00	SN74197	£1.58
CD4014	85p	T099	40p	SN7408	19p	SN7486	29p	SN74198	£1.80
CD4015	89p	8D1L	40p	SN7409	18p	SN7490	42p	SN74199	£1.80
CD4016	45p	14D1L	38p	SN7410	16p	SN7491	75p	SN76003N	£2.92
CD4017	88p	LM747	£1.05	SN7411	20p	SN7492	45p	SN76013N	£1.95
CD4018	18p	LM748	44p	SN7412	22p	SN7493	45p	SN76023N	£1.80
CD4019	52p	8D1L	44p	SN7413	28p	SN7494	75p	SN76033N	£2.92
CD4020	98p	14D1L	41p	SN7416	28p	SN7495	68p	TAA263	£1.03
CD4021	88p	LM3900	61p	SN7417	28p	SN7496	68p	TAA300	£1.84
CD4022	85p	LM7805	£1.88	SN7420	16p	SN74100	£1.10	TAA350A	£1.96
CD4023	18p	LM7812	£1.99	SN7423	23p	SN74107	30p	TAA550	32p
CD4024	72p	LM7815	£1.99	SN7425	23p	SN74118	85p	TAA611C	£2.18
CD4025	18p	LM7824	£1.99	SN7427	23p	SN74119	£1.75	TAA621	£2.18
CD4027	42p	MC1303L	£1.50	SN7430	15p	SN74121	75p	TAA661B	£1.03
CD4028	83p	MC1310P	£2.50	SN7432	22p	SN74122	42p	TBA641B	£2.25
CD4029	£1.06	MC1330P	90p	SN7437	28p	SN74123	65p	TBA651	£1.69
CD4030	52p	MC1351P	80p	SN7438	28p	SN74141	75p	TBA800	89p
CD4031	£1.98	MC14553	£4.07	SN7440	16p	SN74145	72p	TBA810	98p
CD4037	88p	MC1468L	£3.90	SN7441	68p	SN74150	£1.20	TBA820	80p
CD4041	70p	MC1469R	£2.75	SN7442	65p	SN74151	68p		

POPULAR SEMICONDUCTORS

2N696	22p	2N3906	19p	AF139	65p	BF115	29p	MPSA56	31p
2N697	16p	2N4058	18p	AF239	65p	BF117	55p	OC28	£1.48
2N699	59p	2N4062	15p	AF279	70p	BF154	20p	OC42	50p
2N706	14p	2N4921	83p	AF280	79p	BF159	27p	TIP29A	49p
2N708	17p	2N4923	£1.00	AL102	£1.00	BF180	35p	TIP31A	62p
2N916	28p	2N5245	29p	BC107	14p	BF181	34p	TIP32A	74p
2N918	32p	2N5294	48p	BC109	15p	BF184	30p	TIP34A	£1.31
2N1302	18p	2N5296	48p	BC147B	10p	BF194	12p	TIP35A	£2.90
2N1308	47p	2N5458	26p	BC149B	11p	BF196	13p	TIP36A	£3.70
2N1711	37p	2N5459	29p	BC157A	16p	BF197	15p	TIP41A	79p
2N2102	60p	2N5627	45p	BC159A	16p	BF198	18p	TIP42A	90p
2N2148	94p	3N140	£1.00	BC168B	15p	BF244	21p	TIP295S	98p
2N2218A	47p	3N141	81p	BC169B	15p	BF258	53p	TIP305S	80p
2N2219A	52p	3N200	£2.49	BC182	12p	BF259	55p	TIS43	28p
2N2220	25p	40361	40p	BC182L	12p	BF398	25p	ZTX300	13p
2N2221	19p	40362	44p	BC183	12p	BF399	24p	ZTX301	13p
2N2222	20p	40406	44p	BC183L	12p	BF399	24p	ZTX501	13p
2N2223	20p	40407	35p	BC184	13p	BF429	32p	ZTX502	18p
2N2646	55p	40408	50p	BC184L	13p	BF434	30p	IN914	£1.35
2N2905	47p	40409	52p	BC212	16p	BF435	30p	IN4007	70p
2N2906	33p	40410	52p	BC213L	15p	BF438	30p	IN4148	7p
2N2907	39p	40411	52p	BC214L	18p	BF450	30p	IN5404	22p
2N2926G	12p	40594	84p	BC227B	18p	BFV51	28p	IN5408	30p
2N3053	25p	40595	84p	BC239C	16p	BFV52	30p	AA119	8p
2N3054	60p	40636	£1.10	BC257A	16p	BFY39	48p	BA145	18p
2N3055	65p	40673	73p	BC259B	17p	ME4102	11p	BA155	12p
2N3391	28p	AC126	20p	BC301	34p	MJ480	95p	BB103B	23p
2N3393	13p	AC127	40p	BC307B	20p	MJ481	£1.20	BB104B	45p
2N3397	18p	AD128	35p	BC309C	20p	MJ490	£1.93	BY126	27p
2N3442	£1.40	AC132	40p	BC328	23p	MJE3055	£1.45	BYZ11	31p
2N3638	15p	AC153	35p	BC328	23p	MJE395	£1.00	BYZ12	51p
2N3702	12p	AC176	41p	BCY70	17p	MJE370	65p	OA47	6p
2N3703	13p	AC188K	40p	BCY72	18p	MJE371	75p	OA90	6p
2N3706	15p	AD143	68p	BD121	£1.00	MJE520	60p	OA91	6p
2N3708	14p	AD161	69p	BD124	67p	MJE521	70p	OA200	80p
2N3716	£1.80	AD162	69p	BD131	40p	MJE2955	£1.20	BY164	57p
2N3771	£2.20	AF106	40p	BD132	22p	MJE3055	75p	STZdrac	£1.00
2N3773	£2.65	AF109	40p	BD136	22p	MJE3113	40p	AO669	£1.00
2N3789	£2.06	AF115	35p	BD137	24p	MPSA05	25p	TIC44	29p
2N3819	37p	AF116	35p	BD138	26p	MPSA06	31p	CI06D	65p
2N3904	19p	AF118	35p	BD139	71p	MPSA05	21p	ORP12	60p

London, Glasgow, Paris and now **BRISTOL**
It's our service that makes us grow

Prices correct at June, 1976, but all exclusive of VAT. P.&P. 30p



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohms	£8-64
Baker Group 35, 3, 8 or 15 ohms	£10-25
Baker Group 50/12 8 or 15 ohms	£14-09
Baker Group 50/15 8 or 15 ohms	£18-62
Baker Deluxe 12" 8 or 15 ohms	£12-30
Baker Major 3, 8 or 15 ohms	£10-69
Baker Superb 8 or 15 ohms	£10-31
Baker Regent 12" 8 or 15 ohms	£9-09
Baker Auditorium 12" 8 or 15 ohms	£14-65
Baker Auditorium 15" 8 or 15 ohms	£19-41
Celestion G12M 8 or 15 ohms	£12-95
Celestion G12H 8 or 15 ohms	£15-95
Celestion G12/50 8 or 15 ohms	£16-50
Celestion G12/50TC 8 or 15 ohms	£18-00
Celestion G15C 8 or 15 ohms	£20-95
Celestion G18C 8 or 15 ohms	£24-50
Celestion HF1900 8 or 15 ohms	£8-58
Celestion HF2000 8 ohms	£8-55
Celestion MH1000 8 or 15 ohms	£13-50
Celestion CO3K	£4-46
Decca London Ribbon horn	£28-80
Decca London CO/1000/8 Xover	£6-75
Decca DK30 ribbon horn	£17-25
Decca CO/1/8 Xover (DK30)	£4-50
EMI 14 x 9 Bass 8 ohms 14A/770	£11-92
EMI 8 x 5, 10 watt, d/cone, roll surr.	£3-56
EMI 8" d/cone, roll surr. 8 ohms	£3-93
EMI 8" roll surr. bass	£5-73
EMI 5" mid range	£3-15
Elac 59RM109 (15) 59RM114 (8)	£3-38
Elac 6 1/2" d/cone, roll surr. 8 ohms	£3-83
Elac 10" 10RM239 8 ohms	£1-57
Eagle Crossover 3000hz 3, 8 or 15 ohm	£5-91
Eagle FR4	£8-86
Eagle FR65	£11-08
Eagle FR8	£14-06
Eagle FR10	£3-96
Eagle HT15	£6-13
Eagle HT21	£4-00
Eagle MHT10	£8-10
Eagle FF28 multcell. horn	£5-25
Fane Pop 15, 8 or 16 ohm	£27-95
Fane Pop 33T, 8 or 16 ohm	£37-95
Fane Pop 50, 8 or 16 ohm	£39-95
Fane Pop 55, 8 or 16 ohm	£49-95
Fane Pop 60, 8 or 16 ohm	£39-95
Fane Pop 70, 8 or 16 ohm	£49-95
Fane Pop 100, 8 or 16 ohm	£59-95
Fane Crescendo 12A, 8 or 16 ohms	£27-95
Fane Crescendo 12BL, 8 or 16 ohms	£37-95
Fane Crescendo 15/100A, 8 or 16 ohms	£39-95
Fane Crescendo 15/125, 8 or 16 ohms	£49-95
Fane Crescendo 18, 8 or 16 ohms	£59-95
Fane 910 Mk II horn	£27-95
Fane 920 Mk II horn	£15-75
Fane HPX1 crossover 200 watt	£38-95
Fane 13 x 8, 15 watt dual cone	£2-50
Fane 801T 8" d/c, roll surr.	£8-96
Goodmans Axent 100	£7-60
Goodmans Auditorium 200 8 ohm	£13-46
Goodmans Axent 402 8 or 15 ohm	£19-80
Goodmans Twinaxiom 8, 9 or 15 ohm	£9-50
Goodmans Twinaxiom 10, 8 or 15 ohm	£9-76
Goodmans 8P 8 or 15 ohm	£5-95
Goodmans 10P 8 or 15 ohm	£6-25
Goodmans 12P 8 or 15 ohm	£14-95
Goodmans 12PG 8 or 15 ohm	£16-50
Goodmans 12PD 8 or 15 ohm	£16-95
Goodmans 12AX 8 or 15 ohm	£39-00
Goodmans 15AX 8 or 15 ohm	£45-00

SPEAKERS

Goodmans 15P 8 or 15 ohm	£22-50
Goodmans 18P 8 or 15 ohm	£39-00
Goodmans Hifax 750P	£18-00
Goodmans 5" midrange 8 ohm	£4-05
Gauss 12" 200 watt	£84-00
Gauss 15" 200 watt	£96-00
Gauss 18" 200 watt	£129-00
Jordan Watts Module 4, 8 or 15 ohm	£15-38
Kef T27	£5-18
Kef T15	£6-25
Kef B110	£6-75
Kef B200	£7-85
Kef B139	£15-08
Kef DN8	£2-08
Kef DN12	£2-38
Kef DN13 SP1015 or SP1017	£4-05
Lowther PM6	£30-60
Lowther PM6 Mk 1	£32-85
Lowther PM7	£48-60
Peerless KO10DT 4 or 8 ohms	£7-25
Peerless DT10HFC 8 ohms	£8-28
Peerless KO40MRF 8 ohms	£9-28
Peerless MT225HFC 8 ohms	£2-95
Richard Allan CA12 12" bass	£19-80
Richard Allan HP8B	£11-93
Richard Allan LP8B	£8-33
Richard Allan DT20	£6-08
Richard Allan CN8280	£16-20
Richard Allan CN820	£3-15
Richard Allan Super disco 60W 12"	£16-95
Richard Allan CG15 15" bass	£27-45
Richard Allan Super Disco 10" 50 watt	£13-25
Richard Allan Super Disco 8" 50 watt	£12-95
Radford MD9	£10-50
Radford MD6 dome mid range	£12-50
Radford TD 3	£7-25
Radford Crossover network	£13-00
BD25 Mk II	£22-00
STC 4001G	£5-90
Tannoy 10" HPD	£67-50
Tannoy 12" HPD	£73-75
Tannoy 15" HPD	£88-15
Wharfedale Super 10 RS/DD 8 ohms	£13-50
Castle 8 RS/DD	£9-28

SPEAKER KITS

Baker Major Module 3, 8 or 15 ohms	each	£13-28
Goodmans DIN 20 4 or 8 ohms	each	£13-28
Goodmans Mezzo Twin Kit	pair	£42-47
Helme XLK 20	pair	£13-50
Helme XLK 30	pair	£17-10
Helme XLK 35	pair	£21-60
Helme XLK 40	pair	£31-50
Helme XLK 50	pair	£50-40
KEF kit I	pair	£44-10
KEF kit III	each	£39-38
Peerless 20-2	each	£15-70
Peerless 30-2	each	£21-85
Peerless 20-3	each	£23-90
Peerless 60-4	each	£36-45
Peerless 1080	pair	£50-40
Peerless 1070	each	£41-40
Peerless 1120	each	£45-00

SPEAKER KITS

Richard Allan Twin assembly	each	£13-48
Richard Allan Triple 8	each	£20-25
Richard Allan Triple 12	each	£25-16
Richard Allan Super Triple	each	£29-25
Richard Allan RA8 Kit	pair	£37-80
Richard Allan RA82 Kit	pair	£59-40
Richard Allan RA82L Kit	pair	£65-70
Fane Mode One Mk2	each	£18-35
Wharfedale Linton II kit	pair	£20-81
Wharfedale Glendale 3XP kit	pair	£47-70
Wharfedale Dovedale III kit	pair	£59-40

HI-FI

ON DEMONSTRATION in our showrooms

Akai, Armstrong, Bowers and Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc. Ask for our Hi-Fi Discount Price List.

THIS MONTHS SPECIALS! Pioneer PL12D £43-00, Pioneer PL15R £53-00, Pioneer SX434 £98-95, Rotel RX202 £80-00, Videotone Minimax II £39-00.

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

All Prices include VAT
(Prices correct at 7.5.76)

Send stamp for Free 32 page booklet
'Choosing a Speaker'.

All units guaranteed New and Perfect.
Carriage and Insurance: Speakers 50p each, 12" and up 75p each. Kits 80p each (£1.60 per pair). Tweeters and crossovers 30p each.

WILMSLOW AUDIO

Dept. PW

Loudspeakers, Mail Order and Export:
Swan Works, Bank Square, Wilmslow.
Hi-Fi, Radio & TV: Swift of Wilmslow
5 Swan Street, Wilmslow, Cheshire.

PA, Hi-Fi & Accessories: Wilmslow
Audio, 10 Swan Street, Wilmslow,
Cheshire.

Telephone:

Loudspeakers, Mail Order and Export
Wilmslow 29599

Hi-Fi, Radio, etc., Wilmslow 26213

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, HiFi Answers Monitor (Rogers), HiFi News No Compromise (Frisby), HiFi News State of the Art, Wireless World Transmission Line (Bailey), Practical HiFi and Audio Monitor (Giles), Practical HiFi and Audio Triangle (Giles), Popular HiFi (Colloms), etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi Answers Monitor, Free on Request.

P.A. Amplifiers, microphones etc. by Shure, Linear, Eagle, Beyer, AKG etc.

FREE with orders over £10—"HiFi Loudspeaker Enclosures" Book


A.S.P. LTD

(DEPT. PW5), SIMMONDS ROAD, WINCHEAP
CANTERBURY, KENT Tel: (0227) 52436

TRANSFORMERS VAT 8%

CASED TRANSFORMERS

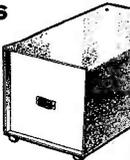Housed in smart resin coated steel cases with 3 core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets and are available with 110 volt or 240 volt output (please state). Auto types are fitted with 2-pin flat style sockets up to 600VA, 3-pin sockets from 750 to 3000VA. See Auto Isolation Sections for prices. Plugs extra.



SAFETY ISOLATING See catalogue for full range. Prim. 120/240V. Sec. 120/240V. Centre Tap with screen.

VA (Watts)	REF	PRICE CASED	PLUGS 2 Pin+Earth	PRICE OPEN	POST
60	149	9.45	0.98	5.02	0.72
200	151	12.87	0.85	9.07	0.97
250	152	14.47	0.98	10.81	1.18

AUTO TRANSFORMERS

See catalogue for full range.

VA (Watts)	REF	PRICE CASED	PLUGS 2 & 3 pin	PRICE OPEN	POST
1500	93	24.37	0.95	20.13	O/A

MINIATURE & EQUIPMENT

Primary 240V with screen. See catalogue for full range.

VOLTS	MILLIAMPS	REF	PRICE	POST		
3-0-3	2	200	2.85	1.75	0.34	
0-6	0-6	500	500	2.84	1.75	0.34
0-8	0-6	1000	1000	2.12	2.32	0.46
0-9	—	100	13	1.75	0.34	
0-9	0-9	330	330	2.55	1.75	0.34

12 & 24 VOLTS

Primary 200-240 Volts. See catalogue for full range.

AMPS	24V	REF	PRICE	POST
12V	1	71	2.64	0.61
4	2	18	3.17	0.62
6	3	70	4.82	0.72
8	4	108	5.65	0.85

30 VOLTS

Primary 200/240V
Secondary 12, 15, 20, 24, 30V

AMPS	REF	PRICE	POST
0.5	112	2.17	0.61
1	79	2.74	0.66
2	3	4.32	0.72
3	20	5.05	0.85
4	21	5.98	0.85
5	51	7.05	0.95
6	117	7.88	0.97
8	88	10.31	1.18
10	89	10.87	1.18

50 VOLTS

Primary 200/240V
Secondary 19, 25, 33, 40, 50V

AMPS	REF	PRICE	POST
0.5	102	2.33	0.61
1	103	3.67	0.76
2	104	5.57	0.85
3	105	6.39	0.85
4	106	8.35	1.08
6	107	13.56	1.18
8	118	14.59	1.18
10	119	18.56	1.86

60 VOLTS

Primary 200/240V
Secondary 24, 30, 48, 60V

AMPS	REF	PRICE	POST
0.5	124	2.72	0.72
1	126	4.08	0.72
2	127	5.63	0.85
3	125	8.30	0.97
4	123	9.55	1.18
5	40	10.73	1.18
6	120	18.00	1.36
8	121	16.48	O/A
10	122	21.99	O/A
12	189	19.24	O/A

BRIDGE RECTIFIERS

One Amp	Price	Four amp	Price
50P.I.V.	0.25	100P.I.V.	0.80
100P.I.V.	0.30	200P.I.V.	0.85
200P.I.V.	0.35	400P.I.V.	0.85
600P.I.V.	0.40	600P.I.V.	0.80

Two Amp	Price	Six Amp	Price
50P.I.V.	0.40	50P.I.V.	0.70
100P.I.V.	0.45	100P.I.V.	0.75
200P.I.V.	0.50	200P.I.V.	0.90
400P.I.V.	0.55	400P.I.V.	0.95

Add 12½% VAT on all prices.
Post 10p.

SPECIAL OFFER
2 KVA ISOLATORS
Fully impregnated & screened
2 Primary windings 110V each
2 Secondary windings 115V each
(2 matching transformers) £29.50 plus carriage
VAT 8%.

NEW! 2" and 4" PANEL METERS VAT 8%

2"	4"
Size: 60mm wide x 45mm high x 40mm deep.	Size: 110mm wide x 82mm high x 43mm deep
Movement Ohms	Movement Ohms
0-5 micro A	0-50 micro A
0-100 micro A	580
0-500 micro A	170
0-1 mA	170
0-5 mA	170
0-10 mA	6
0-50 mA	0.5
0-100 mA	0.5
0-500 mA	0.5
0-1 Amp	0.5
0-2 Amp	0.5
0-25 Volt	15K
0-50 Volt	50K
0-300 Volt	300K
"S" meter	170


FOR MULTI-METERS, INSTRUMENTS, RESISTORS, NEONS, TOOLS, POWER SUPPLIES, etc. Send for Catalogue.

Vu meters are complete with detectors. Modern wide view. Price 2" £3.30 Post 10p. Price 4" £4.10 Post 20p. VAT 12½%. Lamps 95p per set. Plus 8% VAT.

NEW CATALOGUE 25p

NEW CATALOGUE 25p

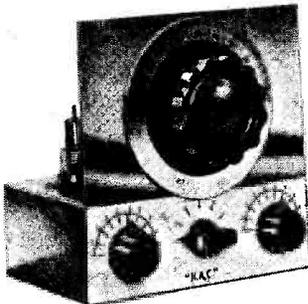H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1976 "DX" RECEIVER
Complete kit—Price £8.00 (incl. p. & p. & V.A.T.). Customer writes: "I think the performance is astonishing for such an inexpensive and foolproof kit. I would wholeheartedly recommend this kit to anyone, however inexperienced, as an antidote to TV-titis, and as an entry into a fascinating hobby".

This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX NO. 16, EAST GRINSTEAD, SUSSEX RH19 3SN

4-STATION INTERCOM



£17.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 75p.

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £31.24 per pair P. & P. 75p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £12.95

+ VAT £1.04

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £13.95 + VAT £1.12 P. & P. 70p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW5)
188 KENSINGTON HIGH STREET, LONDON, W8

ALARM CLOCK MODULES

Require only switches and transformer for operation. 12 hour, 4 digit 0.5" readout plus either clock-radio type or tone-type alarm outputs.

MA1001F or MA1002F—
Clock-radio £7.97

MA1001H or MA1002H
Tone Alarm £7.97

Suitable Vero case
6" x 3¼" x 2¼" £2.95

+ 25p post & pack.

Send SAE for data and catalogue.

BYWOOD

68 Ebbens Road, VAT: All prices
Hemel Hempstead, exclude VAT (8%)
Herts HP3 9RA P/P: 15p
TEL: 0442 62757

ELECTROVALUE

the good components service

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

CATALOGUE 8-ISSUE 2

With the first printing sold out, Issue No. 2 is up-dated on prices, etc. 144 pages. New Items. Opto-electronics. Diagrams of components, applications, I.C. circuits, etc. Post free 40p, including voucher for 40p for spending on order over £5 list value.

DISCOUNTS

On all C.W.O. mail orders, except for some items marked NETT.
5% on orders list value **10%** on orders list value
 £10 or more £15 or more

FREE POST & PACKING

On all C.W.O. mail orders in U.K. over £2 list value. If under, add 15p handling charge.

PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months—Next price review due July 1st 1976.

QUALITY GUARANTEE

On everything in our Catalogue—No manufacturer's rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Dept. 711, 28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 284475. Shop hours 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours Daily 9-5.30 pm; 9-1pm Sats.

FND500 Jumbo 0.5" CC Red LED display £1-02

ADVANCED CLOCK KIT

Complete kit including attractive slim case for 6 digit alarm clock with bleep alarm, snooze, high brightness driving of Jumbo LED displays, automatic intensity control—with optional add-ons of touch switch snooze control and crystal control/battery back-up. **£28-80**

P.E. CAR CLOCK with Journey Timer

6 digit clock for use in any car with 12V battery, with an independent journey timer incorporated. Bright Jumbo LED display comes on with ignition—automatic intensity control. Complete kit of all parts needed including case, PCB's and all components. Full instructions. **£39-50**

Easy to Build **E.E. DIGITAL CLOCK** (Jan. Issue). Kit of all components, including case etc., for this attractive clock with 12mm green display. Full instructions. **£15-70**

50 Hz Xtal Timebase Kit for clocks (incl. advanced kit above). **£6-28**

CMOS ICs	CD4029 0-99	CD4059 4-77	CD4510 1-18	Displays
RCA MOT	CD4030 0-48	CD4080 0-87	CD4511 1-36	FND500 1-02
ON	CD4031 0-82	CD4081 18-92	CD4514 2-72	MAN3M 0-48
CD4000 0-18	CD4032 0-82	CD4082 7-77	CD4515 2-72	TIL321 1-30
CD4001 0-18	CD4033 1-21	CD4083 0-95	CD4516 1-18	TIL322 1-20
CD4002 0-18	CD4034 1-65	CD4086 0-61	CD4518 1-08	XAN652 1-75
CD4005 1-02	CD4035 1-02	CD4087 3-12	CD4520 1-08	XAN654 1-75
CD4007 0-18	CD4036 2-23	CD4088 0-20	CD4527 1-37	5LT01 5-80
CD4008 0-83	CD4037 0-83	CD4089 0-20	CD4532 1-25	
CD4009 0-48	CD4038 0-83	CD4090 0-20	CD4555 0-78	Flat Cable
CD4010 0-48	CD4039 2-23	CD4071 0-20	CD4556 0-78	20WAY 1M
CD4011 0-18	CD4040 0-92	CD4072 0-20	MC14528 1-01	1-00
CD4012 0-18	CD4041 0-73	CD4073 0-20	MC14534 6-04	10M for 8-50
CD4013 0-48	CD4042 0-73	CD4075 0-20	MC14553 4-07	10WAY 1M
CD4014 0-87	CD4043 0-87	CD4076 1-34	MC14566 1-21	10M for 0-60
CD4015 0-87	CD4044 0-81	CD4077 0-48	MCM14552	10M for 4-90
CD4016 0-48	CD4052 1-22	CD4074 0-20		
CD4017 0-87	CD4046 1-16	CD4081 0-20	Clock Chips	
CD4018 0-87	CD4047 0-78	CD4082 0-20	MK30253 5-60	
CD4019 0-48	CD4048 0-48	CD4085 0-62	MM5314 4-44	
CD4020 0-97	CD4049 0-48	CD4086 0-62	AY51224 3-56	
CD4021 0-87	CD4050 0-48	CD4089 1-34	AY51202 2-89	
CD4022 0-83	CD4051 0-81	CD4093 0-69	MY50250 5-00	
CD4023 0-18	CD4052 0-81	CD4094 1-82		
CD4024 0-67	CD4053 0-81	CD4095 0-91	CMOS	
CD4025 0-18	CD4054 1-01	CD4096 0-91	751410J 2-64	
CD4026 1-50	CD4055 1-14	CD4097 3-12	751411D 2-94	
CD4027 0-48	CD4056 1-14	CD4099 1-59	751412K 4-00	
CD4028 0-78	CD4057 21-56	CD4502 1-07	uA78L12WC	

ADD VAT at 8% (Higher rate does not apply to any of above).
 25p P & P on all orders—Despatch is by 1st Class Post.
 Price list and data sent FREE with an order, or on request (an SAE helps).
 Official orders welcomed (written or phoned)—Univs, Polys, Govt, Cos, etc.
 Export orders: no VAT, add 35p (Europe) £1 (overseas) for Airmail p & p.
 (No Export outside Europe for databooks and transformers).

SINTEL, 53n Aston Street, Oxford. Tel: 0865 49791



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become somebody who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 44 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

**To: ALDERMASTON COLLEGE
 DEPT. CPW 19, READING RG7 4PF** CPW19

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name

Address

POST CODE

Verocases
 751410J 2-64
 751411D 2-94
 751412K 4-00
 uA78L12WC 0-80

IC Socket Pins
 100 0-50
 1000 4-00
 3000 10-50

CMOS
 751410J 2-64
 751411D 2-94
 751412K 4-00
 uA78L12WC 0-80

Books
 No VAT or P & P
 MCMOS 2-77

BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY


'SPECIALIST'

RANGE

5 Models for
5 purposes

Illust.
Model
DISCO
60

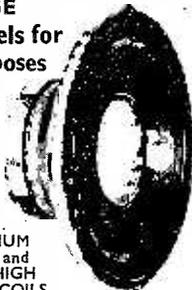All have
ROBUST
CAST
ALUMINIUM
CHASSIS and
EXTRA HIGH
POWER COILS.



**OUTSTANDING
QUALITY**

FOR THE DISCRIMINATING
PROFESSIONAL MUSICIAN

Available in 8 or 15Ω Imp.
2 Year full Guarantee

*12" DISCO 60 Rec. Price
Linen cone surround
Extra Large TWEETER **£25.95**

12" GUITAR 60L **£24.75**

12" GUITAR 60B
For use in multiples
for Bass Guitar **£24.95**

12" PA60 **£24.75**
General Purpose
All above 60w R.M.S.

15" BASS 70 70W
For all Bass Instruments **£37.75**

*Single unit in handsome
Vynide & Vynair
covered Cabinet **£45.00**
Twin units in cabinet **£75.00**

FANE CRESCENDO COLOSSUS

18" DIAM.

4" POLE


Total Flux 366,000
For front or rear
mounting

200w R.M.S.

Rec price inc. VAT

£99.95

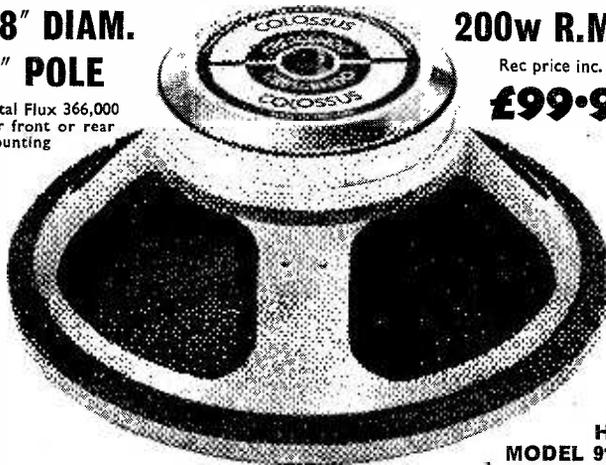Weight 31½ lb
Bass Resonance 23 Hz
Range 22 Hz-3.2 kHz



ELITE RANGE

CRESCENDO 12A
" 12L
" 12 BASS
ALL 100 Watt R.M.S.
CRESCENDO 15
" 15 BASS
" 18A
" 18 BASS
" COLOSSUS

Rec. Prices from
£49.30 inc.
VAT

HIGH FREQUENCY HORN UNITS

MODEL 910 Mk II

Rating 50
watts with
recommended
filter. Rec. Price
£17.75



MODEL 920 Mk II

significantly increased
sensitivity. Rating with
recommended filter 100 watts
(as illust) Rec. Price **£49.95**

HPXI HIGH POWER CROSS-OVER UNIT
Suitable for above Horn Units Rec. Price **£2.70**

Prices shown correct at May 7, 1976

And don't forget our fast selling
and reliable 'Budget Speakers'

'POP' RANGE

'POP' 15 12" 15w **£6.99**

'POP' 33T 12" 33w **£11.98** 'POP' 60 15" 60w **£23.95**

'POP' 50/2 12" 50w **£14.99** 'POP' 70 15" 70w **£25.95**

'POP' 55/2 12" 60w **£20.95** 'POP' 100 18" 100w **£39.95**

Above are Rec. Prices inc. V.A.T. Guarantee is for 2 years.

Please send SAE
with all enquiries

Distributors (Wholesale & Retail Trade)

LINEAR PRODUCTS LTD.,
Electron Works, Armley, Leeds.

Manufacturers enquiries to: **FANE ACOUSTICS LTD.,**
286 Bradford Road, Batley, Yorks.

PRECISION PETITE LTD.

119A HIGH STREET, TEDDINGTON, MIDDX. TEL. 01-977 0878

Now with the

• NEW MK. II DRILL •

10,000 r.p.m., 120 cmg.

**"MORE
POWER—
MORE
TORQUE"**


12v. - 14v. DC

DRILL ONLY £8.00
(P.P. 35p)

STAND £3.76
(P.P. 35p)
Incl. VAT

(Together 50p P.P.)

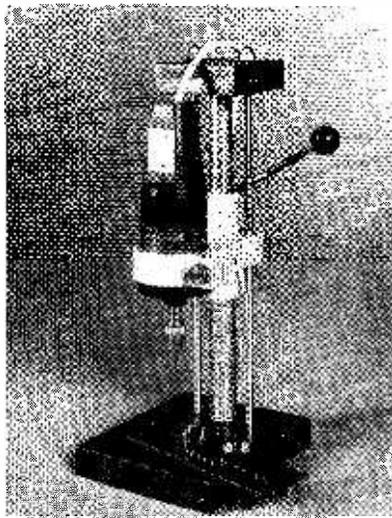SAE for illustrated
leaflet and order form



You
can
rely
on a
CROFTON
KIT



Please send SAE
for our price list and catalogue

CROFTON don't just sell kits, we offer you a technical
back up service to ensure your success

The following is a selection of some of the more popular kits -

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ 'Mistral' Digital Clock Kit **£12.50**
incl. VAT. p. & p. 50p. Made up
£18.00 incl. VAT. p. & p. 50p
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

CROFTON ELECTRONICS LTD
Dept. B, 35 Grosvenor Road, Twickenham,
Middx. Tele. 01-891 1923

SUPERSONIC 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. **PRICE £13.75. P. & P. 85p.**

DE LUXE STEREO AMPLIFIER

A.C. mains 200-240 v. U.I. a 10 g heavy duty fully isolated mains transformer with full wave rectifier 110 a 110 a giving adequate smoothing with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. **£18.40. P.&P. 95p.**

ALL-PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v, and 9v, and 12v, at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested. **PRICE £5.75 P. & P. 85p.**

VYNAIR & REXINE SPEAKERS & CABINET FABRICS approx. 54 in. wide. Our price £1.50 yd. length. P. & P. 35p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AO mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. **£5.00 P. & P. 85p BARGAIN PRICE**

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-40V. Secondary combinations 0-5-10-15-20-25-30-35-40-50V. half wave at 1 amp, on 10-0, 20-0-20, 30-0-30V. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.90 P. & P. 75p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240V. Sec. 9-0-9 at 600 mA. £1.50. P. & P. 35p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.65. P. & P. 35p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.35. P. & P. 70p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300V. Frequency response 10Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price £1.60. P. & P. 15p.

STEREO-DECODER
SIZE 2" x 3" x 1 1/2" ready built. Pre-aligned and tested. Sens. 20-560 mV for 9-18V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (included of hints and tips) supplied. **£5.68 plus 20p. P. & P.** Stereo beacon light if required 40p extra.

QUALITY RECORD PLAYER AMPLIFIER MK. II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. **PRICE £9.50. P. & P. 20p.**
ALSO AVAILABLE mounted on board with output transformer and speaker. **PRICE £7.30. P. & P. £1.**

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.
All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSON SURPLUS CO. LTD.
(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station.
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed. A/C Mains 200/240V (not available in kit form). **SPECIAL OFFER £22.50 + £1.20 p. & p.**

LATEST ACOUS GP91/180 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.60 P. & P. 18p.

CERAMIC STEREO CARTRIDGE. Universal Mounting brackets and turnover stylus. 70mV per channel output. **ONLY £1.90 + 18p P. & P.**

MONOTONE STEREO COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. **ONLY £2.36 P. & P. 10p.** Also available fitted with twin Diamond T/O stylus for Stereo LP. **£2.86. P. & P. 18p.**

LATEST CRYSTAL T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. £1.80 P. & P. 18p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. **Only £1.58. P. & P. 18p.**


SPECIAL OFFER

Solid State Stereo Amplifier Chassis. Brand New, £7.50. Send S.A.E. for full details.

SPECIAL OFFERS

Mullard LP1169 R.F.-I.F. Double Tuned Amplifier Module for nominal 40V K.F. Size approx. 2 1/2" x 1 1/2" x 7/8" Volt + earth. Brand new pre-aligned. Full specification and connection details supplied. **£2.25. P. & P. 12p**

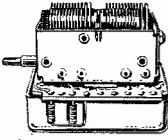Pre VHF/FM Tuner Head covering 88-108 MHz. 10.7 MHz I.F. output. 7.8 Volt + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-gear 4 PM gang and 323PI + 323PI A.M. Tuning gang only **£3.15 + P. & P. 35p.**



PRECISION MADE
Push Button Switch bank. 8 Buttons giving 16 S/C C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" x 2 1/2" x 1 1/2". Supplied complete with chrome finished switch buttons. 2 for **£1.50 + 10p P. & P.**


HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high x 16 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. **AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which).**
OUR PRICE £12.00 each Carr. £1.60.
Cabinet Available Separately £7.25, Carr. £1.20.
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £10.25, Carr. £1.60.

LOUDSPEAKER BARGAINS
5in. 3 ohm £1.45, P. & P. 30p. 7 x 4in. 3 ohm £1.60, P. & P. 45p. 10 x 6in. 3 or 16 ohm £2.50, P. & P. 70p. E.M.I. 6 x 5in. 3 ohm with high flux magnet £2.06, P. & P. 50p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. **£2.00 + 25p. P. & P.**

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details.
Only **£7.25** each + P. & P. (one 60p, two 80p).
Now also available 8" - 8 ohm 10 watts, r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cars **£4.90 + p. & p.** (one 35p, two 65p).

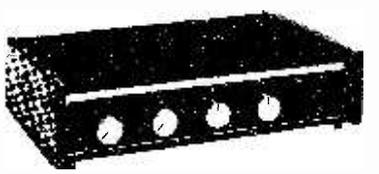HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—Instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v, at 1.0 amp. Overall Size 12" w x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.


AMPLIFIER KIT **£13.50 P. & P. 55p** (Magnetic input components 35p extra)

POWER PACK KIT **£4.85 P. & P. 85p**
CABINET **£4.85 P. & P. 75p**

SPECIAL OFFER—only £22.50 if all 3 items ordered at one time including P. & p.

Full after sales service
Also available ready built and tested **£29.25. P. & P. £1.**

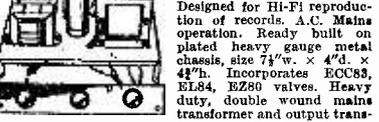Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record deck), etc. and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, 3Z80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£7.80. P. & P. 85p.**

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc **£7.00 P. & P. 85p.**

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + S.A.E. (Free with parts) All parts sold separately. **ONLY £11.25 P. & P. £1.25.** Also available ready built and tested **£15.20 P. & P. £1.20.**

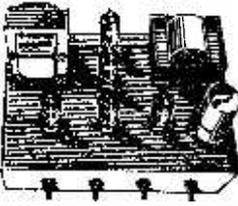

SPECIAL OFFER Limited number of the latest BSR C141RI Auto/Manual changer de-luxe. Lightweight tubular arm, cueing lever bias compensator **£12.60 + £1.10 p. & p.**

Prices include VAT at Current Rate

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

SEMI-CONDUCTORS

TRANSISTORS

BRAND NEW FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC117K	*0.18	AF175	*0.51	BC159C	*0.10	BC440	*0.31	BF117	*0.46	BFY53	*0.13	OC75	*0.16	2N705	*0.08	2N2646	*0.34	2N3703	*0.09		
AC126	*0.14	AF179	*0.51	BC170	*0.10	BC450	*0.37	BF119	*0.71	BFY59	*0.16	OC76	*0.16	2N706A	*0.09	2N2646	*0.34	2N3704	*0.09		
AC127	*0.11	AF181	*0.51	BC171	*0.09	BD115	*0.63	BF152	*0.56	BSX30	*0.16	OC77	*0.26	2N708	*0.11	2N2650	*0.18	2N3705	*0.08		
AC128	*0.11	AF186	*0.51	BC172	*0.09	BD116	*0.81	BF153	*0.48	BSY25	*0.16	OC81	*0.16	2N718	*0.15	2N2650A	*0.18	2N3706	*0.08		
AC128K	*0.26	AF239	*0.38	BC173	*0.09	BD123	*0.87	BF154	*0.46	BSY26	*0.16	OC81D	*0.16	2M918	*0.18	2N2905A	*0.18	2N3707	*0.08		
AC141	*0.19	AL102	*0.75	BC174	*0.15	BD124	*0.79	BF155	*0.71	BSY27	*0.16	OC82	*0.16	2N1131	*0.18	2N2905A	*0.18	2N3708	*0.08		
AC142	*0.18	AL103	*0.75	BC175	*0.22	BD131	*0.38	BF156	*0.49	BSY28	*0.16	OC82D	*0.16	2N1132	*0.18	2N2906A	*0.14	2N3709	*0.08		
AC142K	*0.26	BC107	*0.08	BC176	*0.18	BD132	*0.40	BF157	*0.31	BSY29	*0.16	OC83	*0.20	2N1302	*0.15	2N2907	*0.15	2N3710	*0.09		
AC153K	*0.24	BC109	*0.08	BC178	*0.16	BD133	*0.67	BF158	*0.56	BSY30	*0.19	OC83	*0.20	2N1303	*0.15	2N2907A	*0.16	2N3711	*0.09		
AC176	*0.11	BC113	*0.10	BC179	*0.16	BD135	*0.41	BF159	*0.61	BSY31	*0.19	OC84	*0.20	2N1304	*0.18	2N2923	*0.15	2N3719	*0.14		
AC176K	*0.26	BC114	*0.16	BC180	*0.25	BD136	*0.41	BF173	*0.15	BSY41	*0.29	OC170	*0.26	2N1305	*0.18	2N2924	*0.15	2N3850	*0.40		
AC180	*0.20	BC115	*0.16	BC181	*0.25	BD137	*0.46	BF176	*0.36	BSY95A	*0.13	OC171	*0.26	2N1306	*0.21	2N2925	*0.15	2N3823	*0.16		
AC180K	*0.30	BC116	*0.16	BC182L	*0.09	BD138	*0.51	BF179	*0.31	BU105	*0.90	OC200	*0.26	2N1307	*0.21	2N2926G	*0.09	2N3903	*0.12		
AC181	*0.20	BC117	*0.19	BC183	*0.09	BD140	*0.61	BF180	*0.31	MJE255	*0.88	OC201	*0.29	2N1308	*0.24	2N2926R	*0.07	2N3904	*0.12		
AC181K	*0.30	BC118	*0.09	BC183L	*0.09	BD145	*0.81	BF181	*0.31	MJE255S	*0.88	OC202	*0.29	2N1309	*0.24	2N2926R	*0.07	2N3905	*0.14		
AC187	*0.17	BC119	*0.31	BC184	*0.09	BD155	*0.61	BF182	*0.31	MJE3055	*0.57	OC203	*0.26	2N1615	*0.16	2N2926B	*0.07	2N4287	*0.18		
AC187K	*0.23	BC120	*0.31	BC184L	*0.09	BD176	*0.61	BF195	*0.15	MJE3055S	*0.57	OC204	*0.26	2N2147	*0.73	2N3053	*0.15	2N4288	*0.18		
AC188	*0.19	BC137	*0.16	BC186	*0.29	BD177	*0.67	BF197	*0.12	MJE3440	*0.51	OC205	*0.38	2N2148	*0.58	2N3054	*0.40	2N4289	*0.18		
AC188K	*0.23	BC139	*0.41	BC187	*0.29	BD178	*0.67	BF198	*0.12	MPF104	*0.28	ORP12/	*0.44	2N2218	*0.18	2N3055	*0.40	2N4290	*0.18		
AD140	*0.49	BC140	*0.31	BC207	*0.11	BD179	*0.67	BF199	*0.12	MPF105	*0.56	ORP12	*0.44	2N2219	*0.18	2N3403	*0.21	2N4291	*0.18		
AD142	*0.55	BC141	*0.31	BC208	*0.11	BD180	*0.71	BF257	*0.28	OC19	*0.36	ORP60	*0.41	2N2219A	*0.18	2N3403	*0.21	2N4292	*0.18		
AD143	*0.49	BC142	*0.31	BC209	*0.12	BD185	*0.67	BF258	*0.36	OC20	*0.36	ORP61	*0.41	2N2220	*0.22	2N3405	*0.43	2N5172	*1.12		
AD149	*0.45	BC143	*0.31	BC212	*0.10	BD186	*0.67	BF259	*0.46	OC22	*0.47	TIP29	*0.40	2N2221	*0.18	2N3614	*0.69	2N5457	*0.28		
AD150	*0.63	BC145	*0.46	BC212L	*0.10	BD187	*0.71	BF262	*0.56	OC23	*0.49	TIP30	*0.45	2N2222	*0.18	2N3615	*0.78	2N5458	*0.28		
AD161	*0.36	BC147	*0.08	BC213	*0.10	BD188	*0.71	BF263	*0.58	OC24	*0.57	TIP31A	*0.52	2N2368	*0.18	2N3616	*0.76	2N5459	*0.28		
AD162	*0.36	BC148	*0.09	BC213L	*0.10	BD189	*0.71	BF270	*0.56	OC25	*0.39	TIP32A	*0.66	2N2369	*0.12	2N3646	*0.09	40361	*0.30		
AD161 & AD162(WP)		BC149	*0.09	BC214	*0.10	BD190	*0.77	BF271	*0.31	OC26	*0.31	TIP41A	*0.65	2N2369A	*0.12	2N3702	*0.09	40362	*0.35		
		BC150	*0.19	BC214L	*0.16	BD195	*0.67	BF272	*0.81	OC28	*0.60	TIP42A	*0.72								
		BC151	*0.20	BC225	*0.28	BD196	*0.87	BF273	*0.36	OC29	*0.60	TIS43	*0.25								
		BC152	*0.28	BC226	*0.36	BD197	*0.92	BF274	*0.36	OC35	*0.45	UT46	*0.20								
		BC153	*0.28	BC251	*0.10	BD198	*0.92	BFX29	*0.25	OC36	*0.51	ZTX107	*0.07								
		BC154	*0.29	BC301	*0.28	BD199	*0.98	BFX24	*0.19	OC41	*0.25	ZTX108	*0.07								
		BC157	*0.11	BC302	*0.25	BD200	*0.98	BFX25	*0.25	OC42	*0.25	ZTX300	*0.07								
		BC158	*0.11	BC303	*0.31	BD205	*0.81	BFX26	*0.22	OC44	*0.16	ZTX300	*0.07								
		BC159	*0.11	BC304	*0.37	BD206	*0.81	BFX27	*0.22	OC45	*0.13	ZTX500	*0.09								
		BC160	*0.48	BC327	*0.12	BD207	*0.98	BFX28	*0.22	OC70	*0.10	2N696	*0.10								
		BC161	*0.51	BC328	*0.12	BD208	*0.98	BFY50	*0.13	OC71	*0.10	2N697	*0.11								
		BC167	*0.10	BC337	*0.12	BD120	*1.02	BFY51	*0.13	OC72	*0.15	2N698	*0.20								
		BC168	*0.10	BC338	*0.12	BF115	*0.15	BFY52	*0.13	OC74	*0.15	2N699	*0.36								

VAT CHAT

Please add 8% to prices marked *
Remainder add 12 1/2%. Do not add V.A.T. to prices marked †.

SUPER UNTESTED PAKS

Pak No.	Description	Price
U 1	120 Glass Sub-min. General purpose Germ. diodes	*0.60
U 4	30 Germanium transistors like OC31, AC128	*0.60
U 5	60 200mA Sub-min. silicon diodes	*0.60
U11	20 PNP Sil. planar trans. TO-5 like 2N1132, 2N2904	*0.60
U15	20 NPN Sil. planar trans. TO-5 like 2N696, 2N697	*0.60
U19	20 Silicon NPN transistors like BC108	*0.60
U25	30 Fast switching silicon diodes like 1N914 Micro-Min.	*0.60
U29	10 1 Amp SCR's TO-5 can. up to 600 CRS/25-600	*£1.20
U32	25 Zener diodes 400mW DO-7 case 3-18 volts mixed	*0.60
U38	20 Silicon planar NPN transistors TO-5 BFY50/51/52	*0.60
U45	7 3A SCR's up to 600V	*£1.20
U46	20 Unijunction transistors similar to TIS43	*0.60
U48	9 NPN Sil. Power transistors like 2N3055	*£1.20

Code No's mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
BA100	*0.10	OA11	*0.14	OA51	*0.37	OA95	*0.37
BA116	*0.21	BY100	*0.16	OA47	*0.07	OA85	*0.07
BA126	*0.22	BY126	*0.15	OA70	*0.07	OA200	*0.07
BA143	*0.15	BY127	*0.16	OA79	*0.07	OA202	*0.07
BA154	*0.12	BY128	*0.16	OA81	*0.07	1N914	*0.06
BA156	*0.14	BY164	*0.51	OA85	*0.09	1N916	*0.06
BA173	*0.15	BYX3830	*0.43	OA90	*0.07	1N4148	*0.06

THYRISTORS

PIV	0.6A	0.8A	1A	3A	5A	5A	7A	10A	16A	30A
TO18	TO92	TO5	TO66	TO66	TO64	TO48	TO48	TO48	TO48	TO48
10	*0.13	*0.15	—	—	—	—	—	—	—	—
20	*0.15	*0.13	—	—	—	—	—	—	—	—
30	*0.19	*0.22	—	—	—	—	—	—	—	—
50	*0.22	*0.28	*0.20	*0.25	*0.36	*0.35	*0.48	*0.51	*0.54	*1.18
100	*0.25	*0.30	*0.25	*0.25	*0.48	*0.48	*0.51	*0.57	*0.58	*1.43
150	*0.31	*0.38	—	—	—	—	—	—	—	—
200	*0.38	*0.44	*0.25	*0.30	*0.50	*0.50	*0.57	*0.62	*0.62	*1.63
400	—	—	*0.30	*0.39	*0.55	*0.57	*0.62	*0.71	*0.77	*1.79
600	—	—	*0.39	*0.48	*0.69	*0.69	*0.78	*0.89	*0.90	—
800	—	—	*0.58	*0.65	*0.81	*0.81	*0.92	*1.22	*1.39	*4.07

SILICON RECTIFIERS

PIV	300mA (DO 7)	750mA (SO 16)	1 Amp Plastic (SO 10)	1.5 Amp (SO 10)	3 Amp (SO 10)	10 Amp (SO 10)	30 Amp (TO 48)	
50	*0.05	*0.06	IN4001	*0.05	*0.07	0.14	*0.13*	*0.56*
100	*0.05	*0.07	IN4002	*0.06	*0.09	0.16	*0.21*	*0.69*
200	*0.06	*0.09	IN4003	*0.07	*0.12	0.20	*0.23*	*0.93*
400	*0.07	*0.14	IN4004	*0.08	*0.14	0.28	*0.35*	*1.25*
600	*0.08	*0.16	IN4005	*0.09	*0.18	0.33	*0.45*	*1.78*
800	*0.11	*0.18	IN4006	*0.10	*0.18	0.35	*0.51*	*1.94*
1000	*0.13	*0.22	IN4007	*0.11	*0.23	0.44	*0.60*	*2.31*
1200	—	*0.32	—	—	*0.28	0.54	*0.69*	*2.88*

SIL.G.P. DIODES

300mW 400 PIV (min) SUB-MIN FULLY TESTED
Ideal for Organ builders
30 for 50p. 100 for £1.50. 500 for £5. 1,000 for £9.

TRIACS

2 Amp	Case TO5	100V	200V	400V
8 Amp	TO66	*0.51	*0.61	*0.77
10 Amp	TO48	*0.77	*0.92	*1.12

GP300

115 WATT SILICON TO3 METAL CASE
Vcbo 100V. Vceo 60V. IC 15A. Hfe, 20-100 suitable replacement for 2N3055, BDY11 or BDY20
1-24 *50p 25-39 *48p 100+ *48p

GP Switching Trans

TO18 SIM. TO 2N706/8 BSY27/28/95A
All usable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2906, BCY70. 20 for *50p. 50 for *£1. 100 for *£1.80. 500 for *£8. 1,000 for *£14.
When ordering please state NPN or PNP

WORLD SCOOP!!

JUMBO SEMICONDUCTOR PAK
Transistors-Germ. and Silicon.
Rectifiers-Diodes. Triacs-Thyristors-I.C.'s and Zeners. ALL NEW AND CODED.
Approx. 100 pieces only *1.85p.

ZENER DIODES

FULL RANGE IN STOCK, 2-33 Volts
400mW 5p 1.5W 17p 10W *50p

HANDBOOKS

TRANSISTOR DATA BOOK
DTE 1 227 Pages. packed with information on European Transistors. Full specification including outlines. Price £2.85 each

TRANSISTOR EQUIVALENT BOOK
BPE 75 256 Pages of cross references and equivalents for European, American and Japanese Transistors. This is the most comprehensive equivalents book on the market today and has an introduction in 13 languages. Price £2.68 each

DIODE EQUIVALENT BOOK
DE 74 144 Pages of cross references and equivalents for European, American and Japanese diodes, Zeners, Thyristors, Triacs, Diacs and L.E.D.'s. Price £1.98 each

THE WORLD'S BROADCASTING STATIONS
WBS 75 An up to the minute guide for those interested in DX-ing. Contains all the world's broadcasters on SW, MW and LW, as well as European FM

COMPONENTS

ALUMINIUM BOXES

No.	Length	Width	Height	Price
BA1	5 1/2"	2 1/2"	1 1/2"	*0.45
BA2	4"	4"	1 1/2"	*0.45
BA3	4"	2 1/2"	1 1/2"	*0.45
BA4	5 1/2"	4"	1 1/2"	*0.54
BA5	3"	2 1/2"	1 1/2"	*0.45
BAG	3"	2 1/2"	1 1/2"	*0.39
BA7	7"	5"	2 1/2"	*0.79
BA8	8"	6"	3"	*£1.02
BA9	6"	4"	2"	*0.65

(Each complete with 1/2" deep lid and screws). PLEASE ADD 20p POSTAGE AND PACKING FOR EACH BOX.

COMPONENTS

CARBON RESISTOR PAKS
These Paks contain a range of Carbon Resistors, assorted into the following groups:

R1	50 Mixed	100 ohms-820	ohms
R2	50 Mixed	1K ohms-8.2K	ohms
R3	50 Mixed	10K ohms-82K	ohms
R4	50 Mixed	100K ohms-820K	ohms
R5	30 Mixed	100 ohms-820	ohms
R6	30 Mixed	1K ohms-8.2K	ohms
R7	30 Mixed	10K ohms-82K	ohms
R8	30 Mixed	100K ohms-820K	ohms

THESE ARE UNREPEATABLE PRICES

REPANCO CHOKES & COILS

RF Chokes	CH1	2.5mH	0.27
	CH3	7.5mH	0.29
	CH5	1.5mH	0.26
	CH2	5.0mH	0.28
	CH4	10mH	0.31

COILS	DRX1	Crystal set	0.29
Dual range	DRR2		0.42

CARBON POTENTIOMETERS

Log and Lin	4-7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M	
VC1	Single Less Switch	0.20
VC2	Single D.P. Switch	0.40
VC3	Tandem Less Switch	0.60
VC4	1K Less Switch	0.20
VC5	100K Log anti-Log	0.60

HORIZONTAL CARBON PRESETS

0-1 Watt	0.09 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M.	

REPANCO TRANSFORMERS

240V Primary. Secondary voltages available from selected tapings 4V, 7V, 8V, 10V, 40V, 50V and 25V-0-25V.			
Type	Amps	Price	p & p
MT/50/1	1	£3.00	0.45
MT/50/1	1	£4.00	0.48
MT/50/2	2	£5.00	0.60

COIL FORMERS & CORES

NORMAN 1/4" Cores & Formers	0.07
3/4" Cores & Formers	0.09

VEROBOARDS

VBI containing approx. 50 sq. ins. various sizes all 0-1 matrix	*0.60
VB2 containing approx. 50 sq. ins. various sizes all 0-15 matrix	*0.60

CABLES

CABLES	Per Metre
CP1 Single lapped screen	*0.08
CP2 Twin Common Screen	*0.11
CP3 Stereo Screened	*0.12
CP4 Four Core Common Screen	*0.21
CP5 Four Core Individually screened	*0.28
CP6 Microphone Fully Braided Cable	*0.11
CP7 Three Core Mains Cable	*0.11
CP8 Twin Oval Mains Cable	*0.08
CP9 Speaker Cable	*0.06
CP10 Low Loss Co-Axial	*0.14

C280

CAPACITOR PAK
Containing 75 of the C280 range of capacitors assorted in values ranging from 0.1uF to 2.2uF. Complete with identification chart.

FANTASTIC VALUE ONLY £1.20

Add 8% VAT to all prices marked *.
Remainder add 25%.

PLEASE NOTE THE ABOVE DIRECTIONS

VAT

COMPONENT PAKS

Pak No.	Qty.	Description	Price
C1	200	Resistors, mixed values approx. count by weight.	0.60
C2	150	Capacitors, mixed values approx. count by weight	0.60
C4	75	1/8th width Resistors, mixed preferred values	0.60
C5	5	Pieces assorted Ferrite Rods	0.60
C7	1	Pak Wire 50 metres assorted colours	*0.60
C8	10	Reed Switches	*0.60
C9	3	Micro Switches	*0.60
C10	15	Assorted Pots & Pre-Sets	0.60
C12	30	Paper Condensers preferred types, mixed values	0.60
C13	20	Electrolytics Trans. types	0.60
C14	1	Pack assorted Hardware: Nuts, Bolts, Grommets, etc.	*0.60
C16	20	Assorted Tag Strips and Panels	0.60
C19	2	Relays 6-24V Operating	0.60
C20		Sheets Copper Laminate approx. 200 sq. ins.	*0.60

Please add 20p post and packing on all component packs, plus a further 10p on pack nos. C1, C2, C19 and C20.

AVDEL BOND

SOLVE THOSE STICKY PROBLEMS

CYANOACRYLATE C2 ADHESIVE

The wonder bond which works in seconds bond plastic, rubber, transistors, components permanently, immediately!

OUR PRICE ONLY 69p for 2gm phial

AUDIO LEADS

S221	5 pin DIN plug to 4 phono plugs length 1.5m	£1.08
S222	5 pin DIN plug to 5 pin DIN socket length 1.5m	68p
S237	5 pin DIN plug to 5 pin DIN plug mirror image length 1.5m	£1.20
S238	2 pin DIN plug to 2 pin DIN socket length 5m	68p
S270	2 pin DIN plug to 2 pin DIN socket length 10m	80p
S271	5 pin DIN plug to 2 phono plugs connected to pins 3 & 5 length 1.5m	70p
S275	5 pin DIN plug to 2 phono sockets connected to pins 3 & 5 length 23cm	68p
S318	5 pin DIN socket to 2 phono plugs connected to pins 3 & 5 length 23cm	68p
S404	Coiled stereo headphones extending cord extends to 7m	£1.49
S217	3 pin DIN plug to 3 pin DIN plug length 1.5m	80p
S219	5 pin DIN plug to 5 pin DIN plug length 1.5m	80p
S474	3.5mm Jack to 3.5mm Jack length 1.5m	68p
S600	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m	80p
S700	5 pin DIN plug to 3.5 Jack connected to pins 1 & 4 length 1.5m	80p

SWITCHES

DF/DT Toggle	0.28
SP/ST Toggle	0.22



Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.00.

BIB ACCESSORIES

REF 'D'	2 Hi-Fi Cable & Flex Tidy	*34p
REF 'I'	Tape Head Cleaning Kit	72p
REF 'P'	Hi-Fi Cleaner	*30p
Model 9	Wire Stripper	*£1.00
REF 33	1/2" Tape Editing Kit	*£1.80
REF 24	1/4" Cassette Ed'ng Kit	*£1.84
REF 29A	Salvage Cassette	*44p
REF 32A	Stylus Balance	£1.28
REF 33	Splicing Tape	*38p
REF 36A	Record & Stylus Cleaning Kit	*32p
REF 41	8 Track Cartridge Head Cleaner	88p
Model 42	Groov-Kleen	*£1.84
REF 42/5	Roller & Brush for REF 42 & 2000	*24p
REF 43	Record Care Kit	*£2.76
REF 45	Auto Changer Groov-Kleen	*98p
REF 46	Spirit Level	*72p
REF 48	Record Dust-Off	*26p
REF 52A	Cassette Tray	54p
REF 53	Hi-Fi Stereo Test Cassette	*£2.40
REF 56	Hi-Fi Hints & Tips Book	*48p
Model 60	Groov-Kleen	*£1.72
REF 60/5	Replacement Brush Velvet Pad and Base Sticker for Model 60	*24p
REF 62	Cassette Head Cleaner (Liquid)	*48p
REF 71	Record 'Dust Off' (Displays of ten)	*66p
REF 71A	Record 'Dust Off' (Bubble Pack)	*70p
REF 75	Indexa Record	*£1.50
REF 76	Stylus Cleaner	*36p
REF 78	Cassette Fast Hand Winder	*98p
REF 83	Cassette Title & Container Labels (20 & 10)	*36p

DYNAMIC MIKES

TYPE B1223. 200 ohms impedance. Complete with stand, on/off switch and 2.5mm and 3.5mm plugs. Suitable for cassette tape recorders. PRICE £1.67

ANTEX Equipment

SOLDERING IRONS	
X25. 25 watt	*£2.95
Model G. 18 watt	*£3.25
CCN 240. 15 watt	*£3.25
SK1. Soldering Kit	*£4.60

BITS

102 for model CN240 3/32"	*42p
104 for model CN240 1/8"	*46p
06 for model CN240 3/32"	*46p
1100 for model CCN240 3/32"	*46p
1101 for model CCN240 3/32"	*46p
1102 for model CCN240 3/32"	*46p
1020 for model G240 3/32"	*46p
1021 for model G240 3/16"	*46p
1022 for model X25 3/16"	*46p
50 for model X25 3/32"	*46p
51 for model X25 3/16"	*46p
52 for model X25 3/16"	*46p

ELEMENTS

Model ECN 240	*£1.25
Model EG 240	*£1.60
Model ECN 240	*£1.60
Model EX25	*£1.40

SOLDERING IRON STAND

ST3 Suitable for all models	*£1.25
Antex heat shunt	*12p

PLUGS & SOCKETS

PLUGS	Price
PS1 D.I.N. 2 Pin (Speaker)	0.10
PS2 D.I.N. 3 Pin	0.10
PS3 D.I.N. 4 Pin	0.14
PS4 D.I.N. 5 Pin 180°	0.15
PS5 D.I.N. 5 Pin 240°	0.15
PS6 D.I.N. 6 Pin	0.16
PS7 D.I.N. 7 Pin	0.17
PS8 Jack 2.5mm Screened	0.17
PS9 Jack 3.5mm Plastic	0.11
PS10 Jack 3.5mm Screened	0.17
PS11 Jack 4" Plastic	0.14
PS12 Jack 4" Screened	0.16
PS13 Jack Stereo Screened	0.33
PS14 Phono	0.09
PS15 Car Aerial	0.14
PS16 Co-Axial	0.14

INLINE SOCKETS

PS21 D.I.N. 2 Pin (Speaker)	0.13
PS22 D.I.N. 3 Pin	0.19
PS23 D.I.N. 5 Pin 180°	0.19
PS24 D.I.N. 5 Pin 240°	0.19
PS25 Jack 2.5mm Plastic	0.15
PS26 Jack 3.5mm Plastic	0.15
PS27 Jack 4" Plastic	0.28
PS28 Jack 4" Screened	0.32
PS29 Jack Stereo Plastic	0.28
PS30 Jack Stereo Screened	0.35
PS31 Phono Screened	0.17
PS32 Car Aerial	0.20
PS33 Co-Axial	0.20

SOCKETS

PS35 D.I.N. 2 Pin (Speaker)	0.07
PS36 D.I.N. 3 Pin	0.09
PS37 D.I.N. 5 Pin 180°	0.09
PS38 D.I.N. 5 Pin 240°	0.10
PS39 Jack 2.5mm Switched	0.11
PS40 Jack 3.5mm Switched	0.11
PS41 Jack 4" Switched	0.19
PS42 Jack Stereo Switched	0.28
PS43 Phono Single	0.07
PS44 Phono Double	0.09
PS46 Co-Axial Surface	0.09
PS47 Co-Axial Flush	0.19

INSTRUMENT CASES

In 2 sections, Vinyl covered top in Black or Blue, sides and bezel No. Length Width Height Price

BV1	8" x 5 1/2" x 2"	*£1.25
BV2	11" x 6" x 3"	*£1.62
BV3	6" x 4 1/2" x 1 1/2"	0.92
BV4	6" x 5 1/2" x 2 1/2"	*£1.39

20p P & P Per Box. Please state colour.

RECORD CASES

7 in. E.P. 18 1/2" x 7" x 8"	(50 records)	*£2.48
12 in. L.P. 13 1/2" x 7 1/2" x 12 1/2"	(50 records)	*£3.30

CASSETTE CASES

Holds 15. 10" x 3 1/2" x 5". Lock and handle	*£1.50
--	--------

8-TRACK CARTRIDGE CASES

Holds 14. 13" x 5" x 6". Lock and handle	*£2.20
Holds 24. 12 1/2" x 8" x 5 1/2". Lock and handle	*£3.20

BI-PAK

P.O. BOX 6, WARE, HERTS

One flew over the Citizen's band

THERE is a decidedly bad odour in the air. It is interpreted by some semi-knowing nostrils as "Citizen's Band" (CB) and it is growing markedly stronger in the UK. However, a little thought reveals that this evil aroma emanates not from the idea of a Citizen's Band, but from the approach being made in implementing it.

Let us be realistic; there will be a Citizen's Band in the UK. The problems include when, where and how? Which frequencies are to be involved, what power allowed, the cost, types of emission, what equipment? Interference considerations also give cause for concern. This has reached very serious proportions in both Germany and the USA.

What about overcrowding? If one takes a crude rule of thumb by comparing the USA with the UK, somewhat alarming figures result. In America there are approximately 10,000,000 (ten million) CB users and some 250,000 to 270,000 fully licensed Amateurs or Hams. Thus the ratio of CB users to Amateurs is 40:1. If that same ratio were projected for the UK, it would mean 800,000 CB users all packed into a 0.25MHz bandwidth. The situation would become a radio frequency madhouse—unless we act and plan now.

Other problems are even more serious and could affect British workers, people not even interested in CB.

Think; when a CB opens in the UK there will be a huge demand for low-priced walkie talkie type equipment. Imagine the sheer volume of sets required. Now think of all the individual components needed to manufacture those sets. Good, this means more work for Britain in producing the goods, more work more jobs, right?

Wrong! The Japanese for one have already proved themselves masters in the areas of marketing this type of equipment and the design and manufacture of it in large volume. Thus a CB in the UK could offer big business to overseas manufacturers, no increase in employment for Britain, but a big increase in our import bills.

Before you say it couldn't happen, consider the colour television tube dumping allegations made against the Japanese. If these do not convince you, go talk to the ex-workers who *used* to work in the Thorn factory which *used* to produce colour TV tubes, or people who *used* to work at the Pilkington factory which *used* to produce colour TV tubes.

Citizen's Band will come. Will we learn from the mistakes of other countries or will we, through lack of sensible preparation, blunder in and make exactly the same mistakes all over again?

The Government has lent weight to compulsory membership of a Trades Union so a principle has been established—we have a precedent as the legal profession would say. Why not compulsory membership of the Radio Society of Great Britain (RSGB) before any kind of licence is issued?

Why the RSGB? Because here, Government would have a fully organised, fully qualified, tailor made watch-dog and one which genuinely has the interests of both ether and Amateur at heart. It is the only organisation which is so admirably equipped to handle the situation.

Making would-be CB operators become members would at least ensure that they were under the guidance and influence of a responsible and experienced organisation. The Society could steer these operatives along the lines of sensible band useage and behaviour, perhaps through its literature, and by encouraging them to attend meetings of their local Amateur radio clubs where expert advice on virtually any radio/electrical/electronic subject or topic can invariably be found.

Let a proper committee be set up now which includes the RSGB. Priorities should be (a) the frequencies involved and (b) the minimal specifications for equipment.

There should also be very stiff penalties for pirate stations but, more importantly, there should be even stiffer penalties for any person or shop which sells CB transmission equipment to another party which does not produce a valid licence at the time of purchase (try getting a road fund disc without the necessary documentation).

Further, all equipment should, by law, have a unique letter/number combination so that it, like a car registration number and log book, can enable the owner/vendor to be found.

This leader article is not aimed at popularising the RSGB nor at "knocking" Government departments. It is aimed at putting a critical spotlight on a situation which could fester into bedlam, and it has made positive suggestions. Bureaucracy has no excuse, it is now well aware of the dangers.

Citizen's Band is coming. Let us make sound preparations now and let the Government of the day and its relative departments recognise that they have a clear duty to plan the event properly. Isn't that why we voted these people into Parliament—or have I got democracy all wrong?

LIONEL E. HOWES—*Editor*

Bi-Pak Competition

MR. M. S. BLUNT, 3 Woodbury Street, Tooting London SW17 9RP, accepts the 1st prize of a 22in colour television from Mr. Roger Powell of Bi-Pak Semiconductors.

Other winners in the competition held in Bi-Pak's adverts were: 2nd Prize (Legionaire Stereo Amplifier, Deck and E.M.I. Speakers): Mr. William J. B. Atrill, 97 Sandringham Road, Barking, Essex, IG11 9AF. 3rd Prize (Black and White Portable TV): Mr. I. A. Barton, 31 Linton Road, Loose, Maidstone, Kent, ME15 0AG. 4th Prize (Electronic Calculator): Mr. R. Attwood, Dept. Electrical Engineering, Imperial College, London, S.W.7.

Forty-nine consolation prizes of Electronic Slide Rules have also been sent and Bi-Pak Semiconductors wish to thank all participants. If you were unlucky this time, perhaps it will be your turn next year! Watch for the date.

A full list of winners is available on request from: *Bi-Pak Semiconductors, P.O. Box 6, Ware.*

Xciton lightin'

CHROMASONIC ELECTRONICS have signed their first franchise agreement for the supply of Xciton Opto-Electronic products. In addition to the items already stocked Chromasonic can now supply Xciton 0.3 in. and 0.6 in. High Brightness LED displays in red, green and yellow. *Chromasonic Electronics, 56 Fortis Road, London, N10 3NH.*

Practical Wireless, July 1976


Official recommendation for DECS

THE DEC solderless breadboards and Super Solder Boards have now been officially recommended for teaching electronics in Britain's 5,000 schools.

Designed and manufactured by P.B. Electronics (Scotland) Limited, the system facilitates the easy design, testing and production of prototype and custom PCBs without the use of chemicals.

Response to the official recommendation has been almost immediate. P.B. Electronics is currently marketing a complete CSE electronics educational system comprising all five text books, six S-DECS, six Super Solder Boards plus discrete components for only £25.

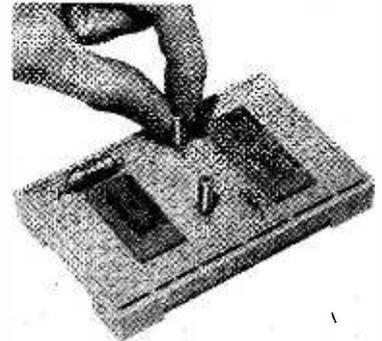Peter Brownlie, managing director of P.B. Electronics said, "With 5,000 schools in the UK as potential buyers the growth for DECS and SSBs in this area is obvious but it doesn't stop there. We are currently discussing similar accep-



tance and recommendation in other countries. The ultimate growth for these products in the education markets alone is enormous."

Officially recommended for the CSE electronics course by the National Centre for Schools Technology, it is virtually certain that DEC/SSB approval will include it in the GCE electronics course slated for next year. Further information on DECS, etc., can be obtained from *P.B. Electronics (Scotland) Limited, (Dept. P.W.), 57 High Street, Saffron Walden, Essex (s.a.e. appreciated).*

Barclay Electronics

DUE to an error in the Barclay Electronics advert on page 255 of this issue, calculator prices were quoted wrongly. The Casio FX20 should be priced at £15.65 and the Rockwell 63R should be priced at £25.60. Further information may be obtained from *Barclay Electronics (Dept. PW) 1115 Finchley Road, Temple Fortune, London, N.W.1.*

Goldring move

GOLDRING announce the move of their Sales and Technical Service Department to new premises at: *Anglian Lane, Bury St. Edmunds, Suffolk, IP32 6SS. Tel. (0284) 64011 (8 lines). Tlx. 817110.*

All correspondence concerning Sales and Service of Goldring/Lenco Record Playing Equipment must now be made to the above address.

BBC Radio Bristol

SINCE Friday, 19 March, Radio Bristol's mf service on 1546kHz (194 metres) has been transmitted from a new site at Mangotsfield and the old transmitter at Clevedon has closed down.


The vhf service is not affected by this change.

Welsh Convention

THE 1976 Welsh Amateur Radio Convention will be held on Sunday, 26th September, 1976, at its usual venue, Oakdale Community College, Blackwood in Gwent, South Wales.

Last year's attendance clearly established the Convention as the major amateur radio event in Wales. This year's programme will enable visitors to attend both the technical lectures and film/slide shows. Further gen from: *R. B. Davies, GW3KYA, 16 Vancouver Drive, Penmain, Blackwood, Gwent, NP2 0UQ.*

VERTICAL AERIALS

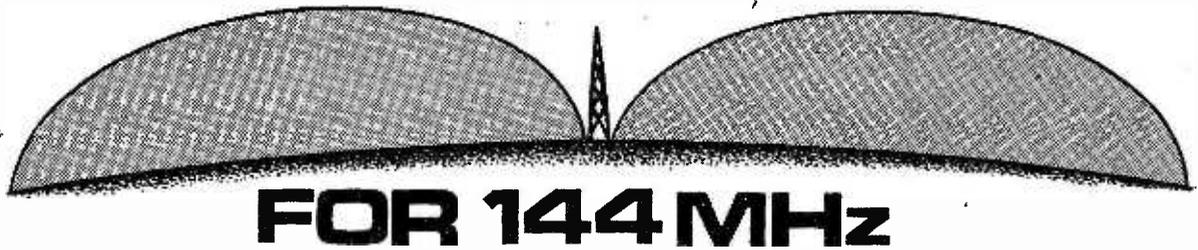


FOR 144 MHz

F. C. JUDD G2BCX

MOBILE and repeater station operation on the 2 metre (144-146MHz) and 70 centimetre (430-440MHz) bands has brought about increasing use of vertically polarised transmitting aerials with omnidirectional radiation at low angles. Such aerials range from simple quarter-wavelength pull-out rods used on hand-held portable transceivers to multiple half-wave element colinear systems which provide a worthwhile gain over a single half-wave dipole. Probably the most popular aerial in use is the so-called "5/8 wavelength" vertical and for fixed station operation this usually consists of the aerial mounted above a system of metal radials which form an "artificial earth" or "ground plane". This aerial is also used extensively for mobile operation in which case it is mounted on the roof, or some part of the car body, which acts as the ground plane.

Much the same reasoning applies to the $\frac{1}{2}\lambda$ aerial. It has a relatively low impedance feed point at its centre and when operated vertically at ground level, the radiation is also at a low angle, assuming perfectly conducting earth. The problem of high attenuation of the radiated signal, due to surrounding structures and ground losses, still remains. However, if this aerial is elevated to several wavelengths above ground it behaves as a "free space" aerial. Ground losses are eliminated, attenuation due to nearby buildings, etc., is reduced and, again, the higher the aerial the greater the working range.

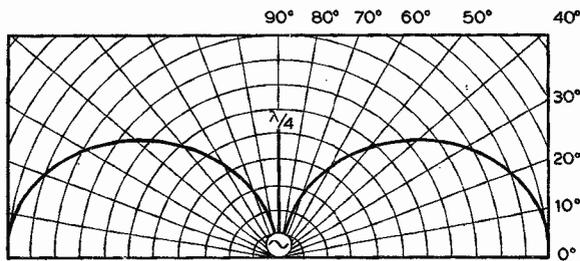These two useful basic aerials are capable of providing the all-important low-angle radiation equally in all directions. The simple quarter-wave ground plane can, however, be modified to provide increased radiation whilst the effectively "free space" dipole can be used in a configuration popularly known as a "colinear" aerial to provide a worthwhile degree of gain over a single element.




W201

Fig. 1: Theoretical radiation pattern in the vertical plane for a quarter-wave vertical aerial near to earth.

The quarter-wave vertical

A vertical aerial, a quarter-wavelength long, has a relatively low impedance feed point at the end nearest earth. Such an aerial radiates equally well in all horizontal directions and, assuming a perfectly conducting earth, the vertical radiation angle is quite low, as in Fig. 1. However, at VHF such an aerial would be at a considerable disadvantage because at ground level and even with perfectly conducting earth beneath it, the radiated signal would be quickly absorbed by surrounding structures, buildings and walls, etc. In any case real earth is far from being a perfect conductor so a considerable loss in radiated power would also occur. The only answer is to provide an artificial earth of high conductivity material beneath the aerial, to reduce otherwise high ground losses. This still permits the aerial to radiate at a low vertical angle when the whole system can be elevated. Attenuation by surrounding structures is largely overcome and the horizon raised and the useful working distance increased.

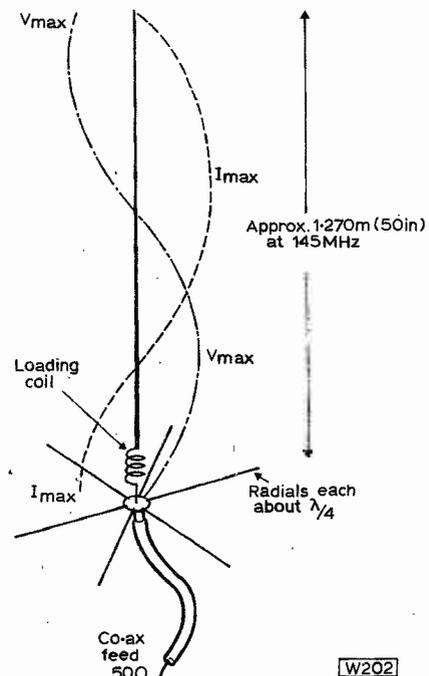

W202

Fig. 2: Basic configuration of a vertical aerial five-eighths of wavelength long.

The " $\frac{5}{8}\lambda$ " ground plane

Called a " $\frac{5}{8}\lambda$ wavelength" aerial because this is approximately its physical length, electrically it is $\frac{3}{4}\lambda$ but as the current and voltage distribution along the aerial shows, Fig. 2, the first section is electrically a $\frac{1}{4}\lambda$ because of the loading coil. The aerial requires a ground plane for efficient operation and the feed point impedance is about 50Ω . Construction is not difficult and both the aerial and its radial section can be made from thin copper or aluminium tubing, or stiff wire such as welding rod, or even from wire coathangers straightened out. The rib frame of an old umbrella also makes a very efficient folding ground plane as will be shown later! The loading coil consists of 4 turns of 16 SWG wire 19mm (0.75in) diameter on a paxolin or PTFE former. The top portion of the aerial is made adjustable to achieve resonance. An outline of the construction is given in Fig. 3.

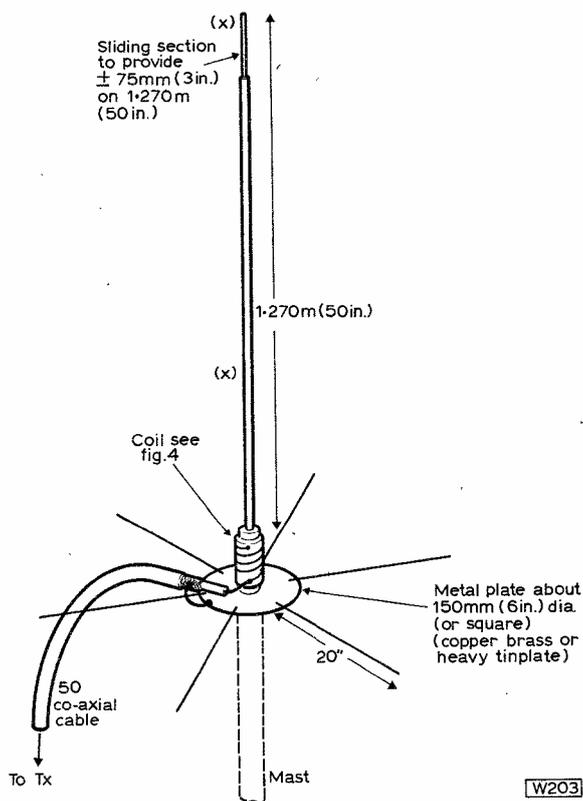


Fig. 3: A practical method of constructing the aerial of Fig. 2.

There should be absolutely no need to trim the 50Ω feed line, however long this might be as with the radiator properly adjusted for resonance the standing wave ratio (SWR) should be not more than 1 to 1.1 or 1.2. With 10W going into the aerial it should be possible to light fully a 6W fluorescent tube (240V) as used for cabinet lights, etc., at the voltage points marked "X" in Fig. 3.

A method of constructing the loading coil is given in Fig. 4. The radials should be not less than about 510mm (20in) long and whilst four are essential, six should be used for preference. The base mounting plate may be copper, brass or tinfoil, thick enough

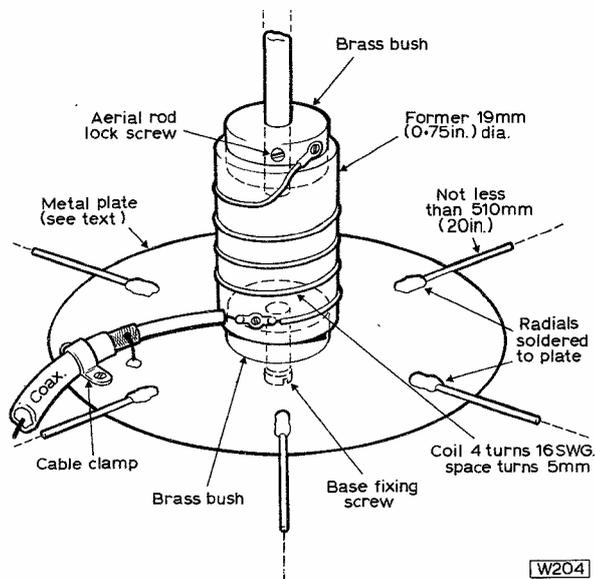


Fig. 4: Details of the loading coil and radial assembly.


to support the radials which are bolted or soldered to it. Do not bend the radials down to achieve low SWR. If this cannot be obtained by adjusting the radiator to resonance, as described, there may be another reason such as wrong feeder impedance or a mismatch at the transmitter end, etc. Adjustment for resonance can be carried out with the aerial at a low height but clear of other conductors. If it is to be used outdoors make sure that water cannot enter the open end of the coaxial feeder where it joins the coil and where the screening braid ends. Seal with Sealastic or similar non-conducting sealer. The coil can be covered with PVC tape and the whole aerial, including the taped coil, may be given a coat of polyurethane varnish for protection against the weather.

This aerial is also suitable for mobile operation using the car body as the ground plane. Centre rooftop mounting is best and the loading coil is insulated from the car metal work as with the ground plane version. The coaxial feed is the same except that the screening braid is connected to the car metalwork as close to the loading coil as possible.

Colinear aerial


This aerial is also omnidirectional, can be made to provide a useful degree of gain over a dipole and is not too difficult to construct. There is now a number of commercially made colinears available for 2 metre operation but the claims made for gain should be viewed with some suspicion. Specifications often quote "10db gain" which is meaningless unless a reference level is given but which may be related, as are other seemingly high gain figures, to that obtained from a quarter-wave aerial, the efficiency of which is much lower than that of a dipole. The standard 0dB reference aerial for gain measurements is the dipole in free space.

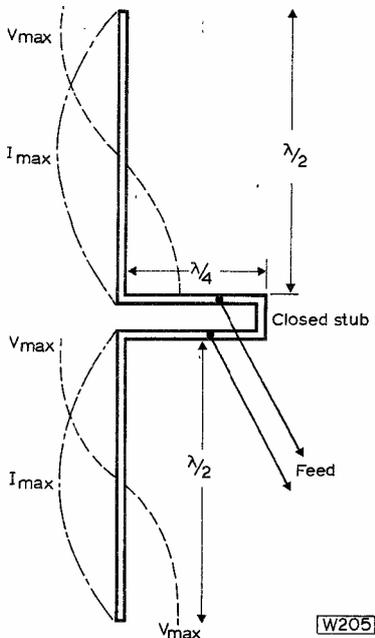A simple colinear array consists of two (half-wave) dipoles made to radiate 'in phase' so the total radiated power is about 1.5 times that of a single dipole, i.e., the power gain is about 2dB, Fig. 5. More elements can be used to achieve higher



W205

Fig. 5: above, simple colinear vertical aerial with voltage and current distribution shown. Fig. 6: below, is the radiation pattern of the aerial in the vertical plane.

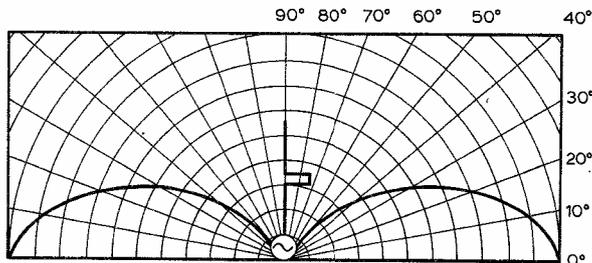

W206


gain and with the conventional close-spaced element system this will be about 3.2dB from a three-element system and about 4.3dB from a four-element system. More than four elements are rarely used as the increase in gain is not worthwhile. Gain could be increased by spacing the elements wider apart. For example, with a spacing of about 0.4λ a gain of more than 3dB can be obtained with only two elements, but then it becomes very difficult to achieve a suitable feed match and phasing with 50Ω or 75Ω cable. (Note: gain figures quoted in this article are with reference to that of a dipole as 0dB.) The close spaced element system is better from the constructional and feed point of view.

The vertical angle of radiation from a two element colinear is shown in Fig. 6 but like all VHF vertical aeriels it needs to be high, the higher the better.

Construction


The whole aerial must be well insulated from the mast or other support, because the ends of the elements are at high RF potential which means that insulation between elements must also be good. The elements and matching stubs can be made from large diameter copper wire but this would require extra insulating support. Copper, brass or aluminium tubing is better and more or less self-supporting.

Insulating material may be PVC wastepipe which is very strong and best for heavy tubular elements. Paxolin or PTFE tubing can be used for light-weight elements or a "plumbing" job with copper water pipe for the elements and stubs using appropriate fittings to join them together. The writer has built quite a number of colinears using all the materials mentioned but successful construction depends largely on the ingenious use of readily available materials.

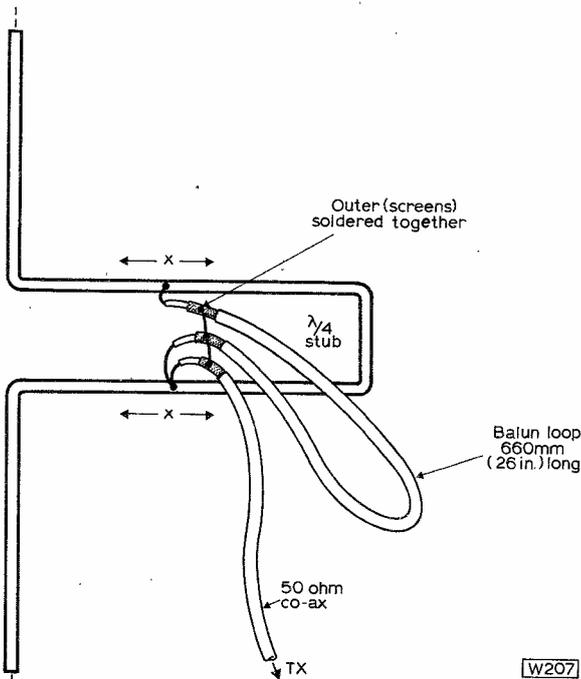

W207

Fig. 7: above, A balun being used to match the unbalanced coaxial feeder to the balanced stub on the aerial. Fig. 8: below, the colinear may be expanded to three or four half wave elements as shown here.

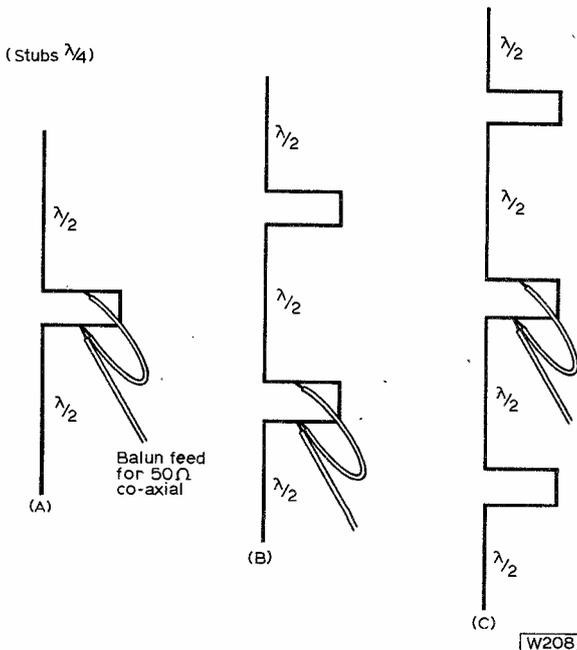

W208

Feeding and matching

The radiating elements are "in phase", connected by means of quarter-wave stubs and the whole system can be fed at a suitable point on one of the stubs. Coaxial cable provides an unbalanced feed but by using a balun as shown in Fig. 7 an impedance step-up of about 4 to 1 can be obtained to about 200 ohms, as well as a balanced connection. Providing the elements are resonant and the stubs properly constructed, good matching and low SWR can be obtained by finding the right tapping points along the stub for the feeder/balun connection. The configurations for two, three and four element colinears are shown in Fig. 8.

Practical colinears

One colinear used by the writer is shown in Fig. 9 and is a "plumbing" job as the elements and stub are made from copper water pipe joined with appropriate fittings. Note that a blow-lamp is needed to soft-solder the fittings. The aerial is self-supporting and can be mounted on the top of a metal mast as shown by means of a "T" junction let into the lower leg of the stub and coupled to a section of PVC waste pipe. Suitable couplers for this can be obtained from builders merchants.

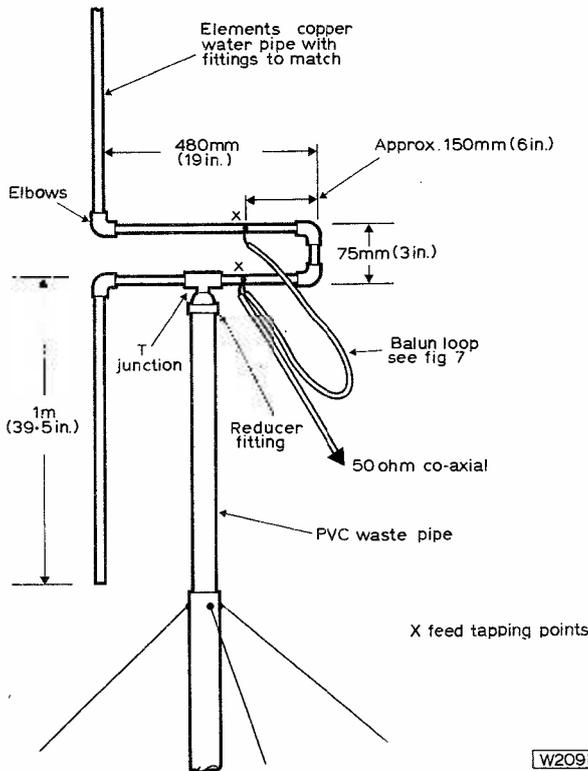


Fig. 9: Use of copper water pipe and fittings in constructing a colinear aerial.

All dimensions are given in Fig. 9 and details for the balun feed will be found in Fig. 7. Adjust the tapping points (X) for maximum radiation (field strength meter, power meter, neon or fluorescent tube at voltage points, etc.) and low SWR which

Practical Wireless, July 1976

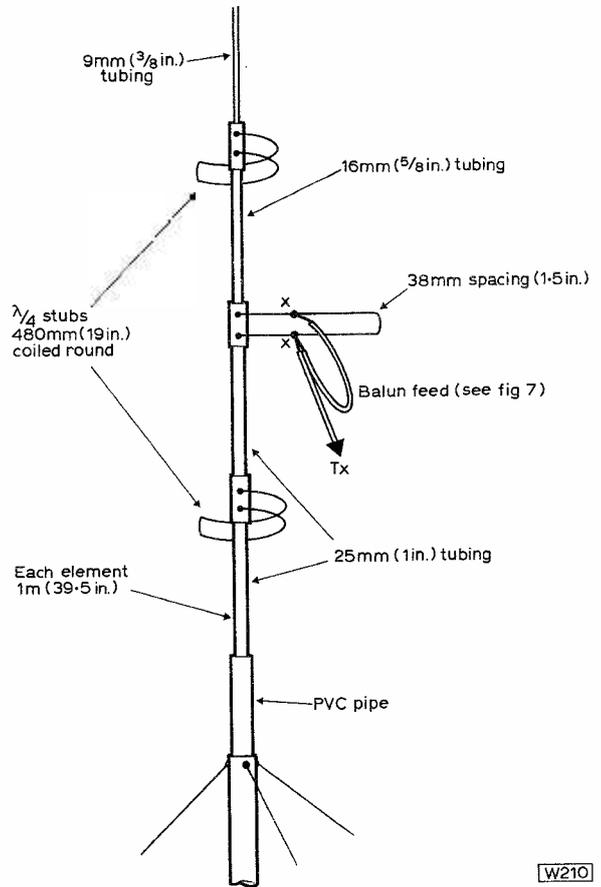


Fig. 10: A four element colinear can be built as shown here, with shorted stubs between elements.

should not be greater than 1 to 1.2. Adjustment can also be made on a steady signal by adjusting for maximum signal meter reading.

The colinear shown in Fig. 10 is a four-element version, also in use, made from copper tubing, sections of waste pipe and stiff wire for the stubs. The feeder line may require some support to prevent drag on the stub and the upper and lower stubs can be coiled up to about 150mm (6 in) diameter to reduce windage. All the elements are 1m (39.5 in) long. Again the only adjustment is for maximum radiation and low SWR by finding the correct tapping points (X) for the balun feed.

The umbrella ground plane

As mentioned earlier, an old umbrella frame, shorn of its cover, makes an excellent 2 metre ground plane. The ribs will need to be soldered together (old coaxial outer braid), as electrical contact between them is rather poor. Using the $5_8\lambda$ radiator and loading coil as described in Figs. 3 and 4, the umbrella ground plane makes a useful portable aerial particularly if the radiator is made detachable when the ground plane can be folded up. For portable use, all that is required is a light sectional mast. The arrangement used by the writer is shown in Fig. 11 and with a 4m (12ft) mast in clear surroundings quite long distances have been covered including continental DX with tropospheric lift.

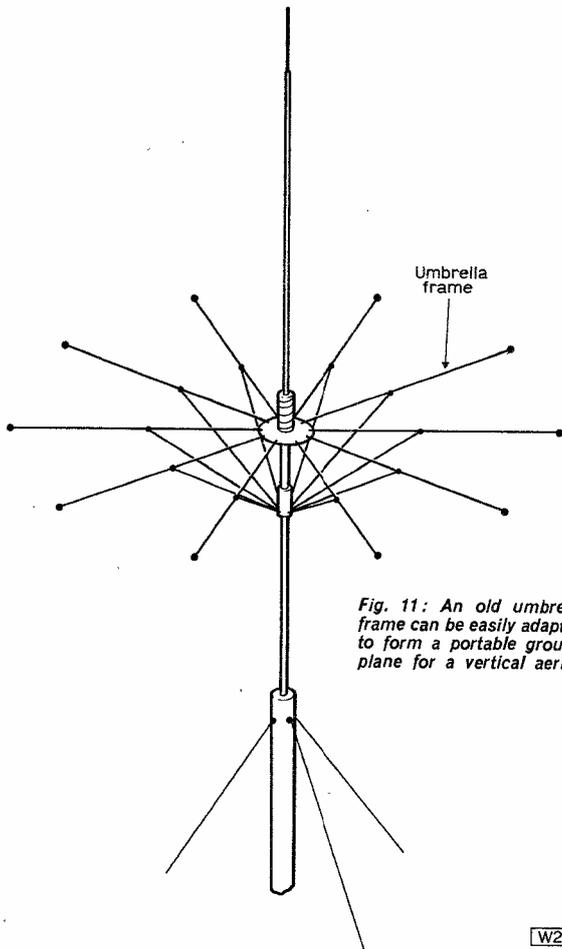


Fig. 11: An old umbrella frame can be easily adapted to form a portable ground plane for a vertical aerial.

W211

Conclusion

The aerials described can be adapted for the 70cm band with proportional dimensions but, as with all aerials at UHF/VHF, siting is important. They should be well clear of other metal structures such as water pipes, guttering, metal roofs, etc. and mounted as high as possible. When using a new aerial don't rely on the report of the first contact made as one may get an S9+ or an S1 depending upon the path over which the signal travels. Make lots of contacts and plot the signal reports on a map with distance circles from your QTH drawn in. The signal path can introduce some peculiar effects on transmission and reception and even a small change in operating conditions can bring an S9+ signal down to zero, or vice versa.

Please mention

PRACTICAL WIRELESS

when replying to
advertisements

TELEVISION

IN THE JULY ISSUE

OPTOCOUPLED AUDIO EXTRACTOR

Taking an audio signal from a mains-powered TV set for hi-fi or recording purposes presents safety problems due to the set's live chassis. There is a new, simple method: using an optoelectronic coupler to provide the required isolation. Full constructional details of a simple unit using one of these devices will be given.

THORN 1500 CHASSIS

Probably more of these sets than any others have been produced during the eight year and still continuing production run. John Law provides a detailed guide to stock faults.

PATCHING PCBs

Printed board burn-ups due to component overheating are a common problem. The most reliable repair method consists of inserting a new board patch. E. Trundle describes how to go about this.

MORE ABOUT TV ICs

Since we last surveyed the TV IC scene three years ago many new devices have come into use and a number of interesting ones using some novel techniques are about to appear. So it's time to review the position again.

TELEFUNKEN 711 CHASSIS

The solid-state 110' colour chassis has been available in the UK for several years; stock faults are now known and standard servicing procedures have become established. These will be described along with the workings of some of the less usual circuits. Part 1 deals with the power supplies.

SOLID-STATE FIELD OSCILLATORS

Most solid-state chassis use a silicon controlled switch (SCS) or its discrete component counterpart the complementary relaxation oscillator to initiate discharge of the field charging capacitor. The operation of these circuits will be thoroughly explored.

PLUS ALL THE REGULAR FEATURES

TO.....
(Name of Newsagent)

Please reserve/deliver the JULY issue of TELEVISION (40p), and continue every month until further notice.

NAME

ADDRESS

DORAM


A PROFESSIONAL DEAL FOR AMATEURS

*ORDERS BY RETURN OF POST *NO QUIBBLE REPLACEMENT PART SERVICE
*QUALITY BRANDED PRODUCTS *FREE UPDATE INFORMATION SERVICE


TOOLS

The handy EXPO 12V d.c. drill is supplied complete with drill kit containing 4 small drills, two spare collets, two cutters, wire brush, soft buffer, grindstone and 9 various milling and reaming tools.

Drill & kit £9.50 + s
Kit only £4.75 + s

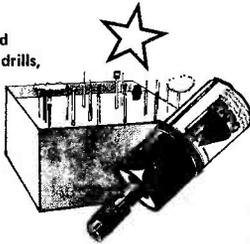

ORYX 50W SOLDERING IRON

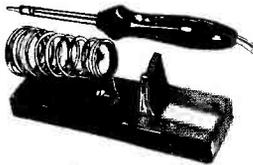

Temperature can be altered between 200-400°C.

Iron 240V £6.90 + s
Stand £2.80 + s

ISO-TIP CORDLESS IRON

Mains and 12V d.c. versions available
£11.50 + s



DE-SOLDER TOOLS

Three high-section models available

SR2 £6.20 + s
SR3 £5.20 + s
SR3AS £4.80 + s
Spare nozzle 60p ea. + s
Please state type



NICKEL-CADMIUM RECHARGEABLE CELLS

	Sim. to dry cell	nom. capacity	charge cur. (mA)	
HP7	0.5Ah	50	£1.10 s	
—	1.2Ah	100	£1.24 s	
HP11	2.0Ah	200	£1.80 s	
HP2	4.0Ah	400	£2.70 s	

- * High performance
- * For 2 & 4 stroke engines
- * Improved start/running
- * 'Crisper' throttle response
- * Reduce battery drain

Neg. earth or pos. earth

£15.00 + s


Please state type required



ELECTRONIC IGNITION UNIT

BATTERY ELIMINATOR

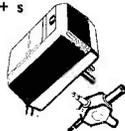Switched output 6, 7.5 or 9V at 250mA.
D.C. pos. or neg. earth
£3.15 + s



SEMI-CONDUCTOR DEVICES

RECTIFIERS


IN 4001 - 5p ea.)
IN 4002 - 6p ea.) + s
IN 4003 - 6p ea.)



1-0A bridge (400V) - 32p + H
1-6A " (200V) - 48p + H
1-6A " (800V) - 70p + H
2-0A " (200V) - 72p + H
2-0A " (600V) - 90p + H

MULLARD MODULES

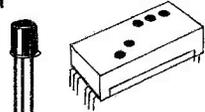LP 1173 - £6.10 + H
LP 1184/2 - £6.58 + H
LP 1185 - £4.50 + H
LP 1186 - £6.32 + H
LP 1400 - £5.15 + H



TRANSISTORS

BC 107 - 12p s
BC 108 - 11p s
BC 109 - 12p s
BFY 50 - 20p s
BFY 51 - 19p s
BFY 52 - 20p s
2N 3055 - 80p s
2N 2646 - 94p s
TIP 2955 £1.14 s
TIP 3055 - 61p s
BC 237B - 11p H
BC 238C - 10p H
BC 239C - 12p H
ZTX 107 - 10p H
ZTX 108 - 9p H
ZTX 109 - 12p H
ZTX 300 - 13p H
ZTX 500 - 14p H
MJE 340 - 62p H
TIP 31A - 36p H
TIP 32A - 40p H
2N 3819 - 32p H
3N 141 - 65p s
CS 715 - 18p H
(Similar to 2N 3819)
BF 180 - 40p s
BRY39 - 72p s

I.C.'s
T05 Reg - £1.10 s
MVR 5 - £1.55 s
MVR 12 - £1.55 s
MVR 15 - £1.55 s
LM 309K - £2.10 s
7805 - £1.55 s
7812 - £1.55 s
7815 - £1.55 s
7824 - £1.55 s
±15V D.I.L. - £2.82 s
TBA 231 - £1.75 H
TBA 800 - £1.20 H
TBA 810S - £1.31 H
TBA 820 - £1.00 H
ZN 414 - £1.30 H
ZN 424 - £1.25 H
741 Op-amp - 36p s
747 Op-amp (Dual 741) - 95p s
748 Op-amp - 48p s
555 TIMER - 56p s
556 (dual 555) - £1.10 H
HA 1156 - £1.60 H
(similar to MC1310P)
ORP12 - 72p s
8A Triac - £1.18 s
ZN 1034E - £4.70 s

'INTERNATIONAL 25'
Build yourself a BIG SOUND amp at a budget price



As featured in 'ETI' Oct. 75 edition

FEATURES

- * Triple Op-amp pre-amplifier
- * Power 'Darlington's'
- * Modern styling
- * 25W per channel into 8 ohms.

Complete kit with assembly instructions

Overseas orders £34.50
S.A.E. for full spec.

£29-95 + £3.74 VAT


BRY39 (z)

Hi-fi hints and tips

Towers international transistor selector £2.95 ea.
Electronic components (Newnes) £1.80 ea.
P.C.B. assembly (Newnes) £1.80 ea.
Electronic diagrams (Newnes) £1.80 ea.

'SAMOS' CASES

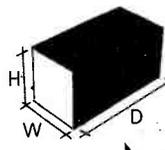Low-cost blue cover and white base PVC steel cases



S1 50W x 50H x 100D £1.03 + s
S2 100W x 50H x 100D £1.17 + s
S3 150W x 50H x 100D £1.31 + s
S4 50W x 75H x 125D £1.47 + s
S5 100W x 75H x 125D £1.68 + s
S6 150W x 75H x 125D £1.97 + s
S7 200W x 75H x 125D £2.19 + s

SPECIAL OFFER!

If 60p catalogue ordered simultaneously with order for SAMOS cases - case price less 25%

CONDITIONS OF SALE

All prices are ex-VAT
If affixed with s add 8%
If affixed with H add 12 1/2%
Z = Zenc. rated
Package by posting free for orders over £3.00
Overseas orders add 25%
Cash with order. Cheques/Postal Orders to Doram Electronics Limited, P.O. Box TR8, Leeds, LS12 2UF
Small order handling charge of 40p for orders under £3.00

NEW RADIO MODULE RANGE



144 MHz Converters

28-30 MHz £15.25 + H
2-4 MHz £15.25 + H

70cm - 432 MHz Converters

144-146 MHz £18.25 + H
28-30 MHz £18.25 + H

144 MHz Dual Output Pre-Amp £9.25 + H

ALL AVAILABLE EX-STOCK

432 MHz Varactor Tripler £17.65 + H

M252AA Rhythm Generator £7.99 + H

DIGITAL : CLOCKS : KITS : CALCULATORS

"ALPHA": 4 GREEN .5" HIGH DIGITS

	Alarm	Std.
Alpha Module (excl. case) Kit	13-00	10-00
Alpha Module (excl. case) Built	14-00	11-00
Alpha complete: Perspex Case Kit	15-50	12-50
Alpha Clock: Perspex Case Built	21-50	17-50

ALARM

- Tilt Snooze ● AM/PM ● Mains failure Ind. ●
- Auto-Control Brightness by Photocell ●

"DELTA": 4 RED .5" HIGH LEDs

	Alarm	Std.
Delta Module (excl. case) Kit	11-50	9-00
Delta Module (excl. case) Built	12-00	9-50
Delta complete: Perspex Case .. Kit	15-00	12-00
Delta Clock: Perspex Case Built	21-00	17-00
Delta complete: Teak Case Kit	15-70	12-70
Delta Clock: Teak Case Built	21-70	17-70

Perspex Case Colours: Black, White, Red, Green, Blue, Orange
 Built Modules and Clocks: state 12 or 24 hour (Delta 12hr only).
 Complete Clocks: 2 Year Guarantee

"NOVUS" CALCULATORS

650 Mathbox £5-40 ● 850 Mathbox £6-75
 4510 Mathematician .. £16-20 ● 6020 Statistician .. £21-60

Module kits

f
r
o
m

£9:00

INCLUDING VAT, P. AND P.
 SATISFACTION GUARANTEED

- Modern 2 Part Case
- Drilled P.C.B.
- 4 Digit Display 0.5 inch high
- All components included
- Even Mains lead included
- Full instructions
- Assembly Drawing
- Circuit Diagram

●●●●●●●●
 You supply only mains plug
 and standard tools — Easy!




C.W.O. PULSE ELECTRONICS (PW13), 202 Shefford Road, Clifton, Shefford, Beds. SAE complete range
 TELEPHONE: HITCHIN (0482) 814477

G SPRING MADNESS M I L W A R D B A R G A I N B A G S

- Echo-chambers. Variable time delay. Variable number of repeats
 Uses cartridge tape (not loop) giving very long life. More versa-
 tile than other units costing several times the price! £37-50
- F.M. Tuners. 8-transistor chassis with stereo-decoder and L.E.D.
 Indicator. Requires only 6 volts. 20ma. £12-90
- Stereo Amps. 3-watt, 8ohm. With knobs and Escutcheon £2-75
- 10-watt Amps. 12 volt D.C. 3/8/15ohm output £4-40
- Cartridges. Acos GP 104. Ceramic/Diamond £1-50
- Cartridges. Acos GP 101. Crystal/Sapphire/Compatible £0-50
- Speakers. 2" — 8-ohm £0-35
- Speakers. Car Stereo. 8-ohm, 5-watt. In cabinets £2-50
- Dynamic Tape Mikes with remote-control facility £0-90
- Crystal Tape Recorder Mikes £0-60
- Crystal Mike inserts with bracket £0-20
- Indicators. 12-volt L.E.D. In Chrome Bezel £0-35
- "Bargain Bags" 4lbs Caps/Resistors/Transistors/Diodes £4-00

ALL ABOVE ITEMS PLUS 12½% VAT

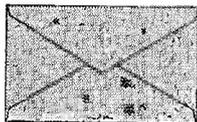

PRICES IN THIS ADVERTISEMENT RELATE
 TO EXISTING STOCK ONLY. SEND
 STAMPED ADDRESSED ENVELOPE PLUS
 10p IN STAMPS. FOR FULL DETAILS OF
 ALL THESE ITEMS PLUS OUR COMPLETE
 STOCK LIST.

- Fluorescent 12-volt Camping Lights. 21" 13-watt £4-90
- 12" 8-watt £3-90
- "Disco type 3-Channel flashing light units. Built-in mike. No
 connection needed to amp £17-50
- Multimeters. AC 0-1000V, DC 0-1000V., 0-100 ma. 0-150kohm £3-50
- Multimeters A.C. 0/1000 volts. 5 Ranges. £1-00
- D.C. 0/1000 volts. 7 Ranges. £1-00
- D.C. current 0/10 ua to 0/500ma. 4 ranges. £14-50
- Resistance 0/130 ohms. 0/100 megohms. 8 Ranges. £3-50
- Decibels — 20 to +62 db. £1-40
- Panel Meters. 0/30 ua. 4½" x 3½". Illuminating kit available. £3-50
- Soldering irons. 15-watt. Pencil Bit. £1-40
- Servisol Switch Cleaner (with Snorkel) £0-50
- Copper-clad Fibre Glass Board. Single-sided. Square foot £1-00
- Double-sided £1-25
- "Fotolak" Light sensitive spray for printed circuit making £1-30
- Developer for same £0-30
- Ferric Chloride for etching £0-40

ALL ABOVE ITEMS PLUS 8% VAT

G. F. MILWARD, 369 Alum Rock Road,
 Tel. 021-327 2339 Birmingham B8 3DR.


POSTAGE: Below £10 50p
 Above £10 Free

New Release!

PLAIN P.A.K. STRIP

(Patents applied for)

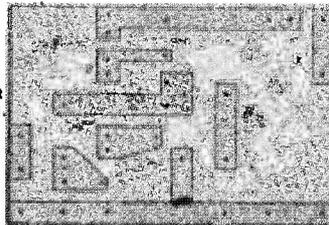Make your own p/c boards
 without etching



6" x 4" sheet
 only 39p incl.
 VAT and
 postage

Use with
 types A and B
 as previously
 advertised

PLAIN P.A.K. STRIP is a very thin copper-coated P/C
 board with a self-adhesive backing. Cut any shape you want
 with scissors and just stick down. Butt solders perfectly.
 Use on plain drilled matrix board and you can prick holes in
 it with a pin.

TIP OF THE MONTH. How to turn a plastic box into
 a screened box—line it with PLAIN P.A.K. STRIP.

PRINT-A-KIT ELECTRONIC SUPPLIES

408 SHARROW VALE ROAD, SHEFFIELD S11 82P

HOTLINES

ON RECENT DEVELOPMENTS

SOLAR CELL COSTS

Japanese interest and capability in electronics is now well known. A quick look at what these Easterners are up to proves very interesting. Toshiba, for example, has issued a statement which is truly staggering; they intend to cut the cost of solar cells by 99 (ninety nine) per cent! The company has discovered a new method of producing the silicon cells. Instead of making each one separately, the silicon material is pulled in a long strip from a melt. Aply described as the Sunshine Project it appears to be showing great promise as a method of fabrication. To date, ribbons of solar cell have been pulled which are about 300 μm thick and some 30mm wide. The longest "pull" so far is 800mm.

ELECTRONIC ENGRAVING

Elsewhere in Japan the mighty Matsushita has been concentrating its efforts in another direction; electronic engraving. One application is in identity cards or credit cards, etc. The image is picked up by a vidicon camera and then fed into a memory. This can then be held and/or fed to an engraving head. This takes the form of a stylus which cuts into the "card". The latter is a black (or dark) surfaced plastic which has a lighter colour immediately beneath it. The stylus pricks into the surface of the card exposing the lighter areas. The greater the signal from the memory the further the stylus bites into the plastic and so the whiter that part of the image becomes. Some 32 degrees of tone are possible and the engraver operates at a resolution of 5 lines/millimetres.

Securitywise it appears very useful since the photograph cannot be removed nor another inserted in its place. Also, since the plastic isn't laminated, it isn't possible for would-be baddies to erase magnetic stripes by heating the cards until the temperature is above the curie point of the material. Already two chains of petrol stations are using the system.

32" COLOUR TELLY

Our last port of call in Japan is the Sony Corporation which just launched a 32in. colour television set. Neck of the tube is 36.5mm in diameter and it has a deflection angle of 114°. Perhaps big is beautiful?

SPECIAL TUBE

Speaking of displays reminds me of the new high-resolution crt unit which has a spot diameter of one fifth of a millimetre. Resolution is 193,354 separate picture elements on its 8 x 10cm screen face and it is aimed at rather specialised markets such as nuclear and X-ray scanning, etc.

SUN POWER

Earlier I talked about Toshiba making solar cells in ribbon form. In the United States an American company has opted for a different idea. It intends to market a hand-held unit which will collect and convert solar energy. One market option is to use the units to power calculators and portable radio receivers. A special technique is employed which enables the company to claim that it's units only need 30% the number of silicon cells required by more conventional approaches. Not available here and no further information as yet, but it looks promising.

GOT IT TAPED!

Know what happens when you speed up a tape recorder? The voice goes higher and higher as the speed increases and, of course, more words per minute are transmitted. One enterprising company has launched what it calls a "Pitch Control microcomputer". Using this device enables the speed of speech to be altered without altering it's pitch. Using a digital technique it samples the speech from a tape running at normal speed but it does this sampling at a rate of 16kHz. The

tape speed is controlled by the user who can slow it down or speed it up. But as it slows (or speeds up) so the sampling rate slows or increases accordingly in step with the tape.

In many analog methods of attempting to do this a problem is encountered; the splice noises and other pops are noticeable. In this digital approach a special intelligent splicing algorithm is employed. The voice input is sampled and digitized, and this data is then stored in a RAM (random access memory). The data entering the memory is, of course, always a function of the tape speed but when it comes out of the RAM it always does so at the basic centre frequency of 16kHz which thus ensures that the pitch remains unchanged.

C.B. FOR U.K.?

Shortwave listeners and others who have tuned into the American 27MHz Citizens Band will know that it makes for hours of fascinating listening although sometimes it can be baffling. A storm is brewing in the US over this band and it will be interesting to see just how it is all resolved. To operate on the Citizens Band in the US is comparatively simple and it has an avid collection of users. It has been estimated that in the US alone there are some 10 million Citizen Band enthusiasts—all transmitting at one time or another. Now this does tend to make the band just a tiny bit crowded and, as some tyros point out, ten million Citizen Band users are packed into 250kHz while only 250,000 Hams are allowed to use some 42MHz of r.f. space all the way up to 450MHz. The problem is compounded because many feel that expansion around 27MHz is not the answer and are eagerly looking to other frequencies. Trouble is that there just isn't any area in the r.f.

CONTINUED ON NEXT PAGE

The logo for Ginsberg, featuring the name in a stylized, cursive script with a horizontal line underneath.

HOTLINES

ON RECENT DEVELOPMENTS

spectrum from 27MHz right up to 1GHz that is free and the only way a slice would be available would be by taking it away from other users. Would it be too dramatic a thing to suggest that Hams should be very vigilant indeed—it could be their pieces of the ether which are taken or, even worse, shared with 10 million CB users—and that's only in the US!

A 'HOLY' BUSINESS

Just to keep a sense of proportion when you think of small things, how about an American company which "drills" a 0.001in. hole in a metal cap. The hole is then electro-polished to smooth out irregularities around its diameter. Then, it is electroplated with gold to prevent corrosion closing it up. The plating reduces

the size of the hole to something like 0.00001in. in diameter. The object of the exercise is to test hermetically sealed packages for leakage and with the hole and pressures involved, the leakage rate is something of the order of 10^{-8} atmosphere cubic centimeters/second. I understand that the method works very well on the whole.

MINI RELAY

For the builder of miniature things, a tiny relay from the US will doubtless be of interest. Measuring only 0.64in² by 0.4in deep, its contacts are capable of switching 2A at 28V d.c. Contact resistance is given as less than 50 milliohms and the 2 pole double throw unit I saw was rated to keep going for over 100,000 operations.

CHIP 'C's'

The last item is really a kind of rehash. Chip capacitors called Vee Cals were launched and were novel in that along their sides they had a series of adjustment points. By rubbing a pencil and forming a conducting bridge between two of these points, the capacitance of the otherwise "fixed" capacitor could be altered. The company has now altered the range of values and also brought out the adjustment points so that they lie on the top face of the chip thus permitting easier adjustment. Nominal capacitance values range from 1 to 55pF and the capacitors measure only 0.12 x 0.1 x 0.03in.

LAST MONTH

In the item 1k CQ's the final paragraph should have been included under "Creditable".

Ginsberg

RSGB RADIO COMMUNICATION EXHIBITION Alexandra Palace July 30/31st and August 1st 1976

Alexandra Palace is situated in the Muswell Hill area of North London—easily reached along the North Circular road (A) and easily accessible from A1, A10, A11, A41, M1, M3, M4 etc. London transport bus services 29, 41, 102, 123, 134, 212, 221 and 244 are within easy walking distance and bus No. W9 connects with the London Underground service at Wood Green on the Piccadilly line and Finsbury Park, served by both Piccadilly and Victoria lines. The buildings and mast are easily seen from the east and south of London and form a visible landmark.

Talk-in Talk-in facilities will be provided on 2-80-160 metres.

Family interest There are many facilities provided free which members of the family not interested in the exhibition may use:—18-hole pitch and putt golf course, boating lake, park trail, ski slope, children's playground, open-air roller skating rink (bring your own skates), rose garden (open through exhibition).

Catering Buffets and bars provided—open all exhibition hours.

Open Friday 1000 hours to 2000 hours—official opening 1200
Saturday 1000 hours to 2000 hours
Sunday 1000 hours to 1600 hours

Charges Parking free
Entrance to exhibition: Adults 40p
Children 20p

Opening ceremony will be performed by Lord Wallace of Coslany, next years RSGB President, at 1200 hours on Friday 30th July.

Coaches Adequate free parking.

BBC Ceefax demonstrations.

Disabled Facilities exist for wheel chairs.

Caravans will be permitted on the race-course car park, but are not to be used for living in.

Creche will be provided for children, supervised by full qualified staff.

Raffle A portable TV to be won every day!

Additional attraction It is hoped that a local radio station will be broadcasting direct from the exhibition.

International Night There will be a reception at 6pm on Friday evening for our overseas visitors, for which 75p will be charged.

RADIO SOCIETY OF GREAT BRITAIN


Mail Order Protection Scheme

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as—

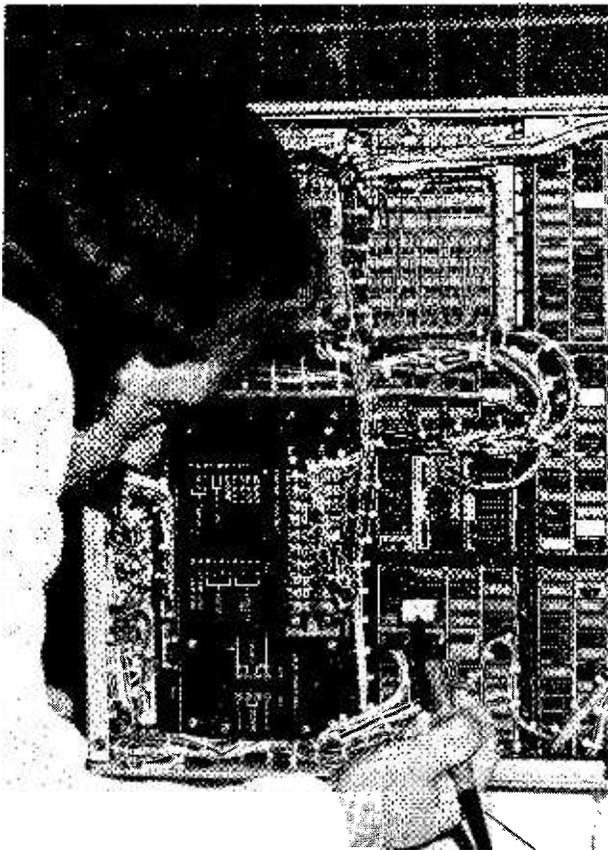'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.




This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

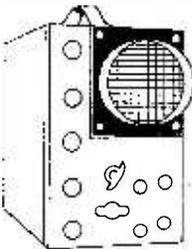All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A certificate is given at the end of every course.




1 Build an oscilloscope.

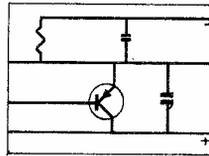As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2 Read, draw and understand circuit diagrams.

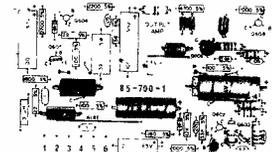In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

PLUS

FREE GIFT!



ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

Brochure without obligation to:
**BRITISH NATIONAL RADIO
 & ELECTRONICS SCHOOL, Dept WH76**
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

(Block caps please)

preamplifier

for the PW DISCO SYSTEM

C.TOMS

FOLLOWING the publication of the PW Stereo Disco System in the December 1975 and January/February 1976 issues of PW some correspondence was received commenting on the lack of bass when using some of the recommended ceramic pick-up cartridges. It was therefore decided to design a simple stereo equalisation preamplifier to cater for two turntables.

Since the amplifier response is linear, within the usual audio limits, and most disc recordings follow the standard Radio Industries Association of America (RIAA) curve, it follows that if a pick-up cartridge is used which has an output that is pro-

response that takes into consideration the disc recording characteristic, the deficiencies of the pick-up cartridge used, and the amplifier loading. Resistor R1 and capacitor C1 provide correction but since the value of these components will vary with the make of cartridge a table is given for the more popular types of cartridge in use. Where no information is available experiments with values of R1 and C1 should provide satisfactory results.

As well as correcting the loss incurred by the matching procedure the preamplifiers will provide some extra gain for the low output type of cartridge, such as the Sonotone 9TAHC.

★ components list

Resistors

R1-4	1MΩ*	R13-16	15kΩ
R5-8	470kΩ	R17-20	15kΩ
R9-12	68kΩ	R21-24	270Ω

All $\frac{1}{2}$ W 5% carbon film. * see text and table.

Capacitors

C1-4	47pF* miniature ceramic (plaquette)
C5-8	10 μ F 30V minimum WV
C9-12	10 μ F 30V
C13-16	10 μ F 30V

Miscellaneous

Tr 1-4, BC184 or similar low-noise NPN. Printed circuit board (Readers PCB Service, see ads). Screened connecting wire.

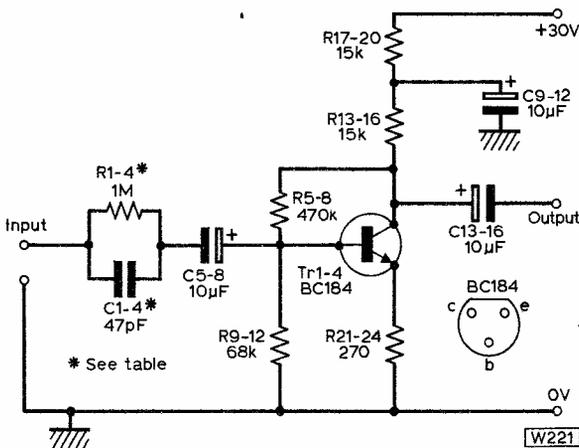


Fig. 1: The circuit of one of the four preamplifiers required for the two turntable stereo system.

portional to the velocity of the recording then the result will be attenuated low frequencies and accentuated high frequencies.

In the case of magnetic pick-up cartridges the RIAA correction is usually incorporated in the preamplifier circuitry. In the case of the PW Disco System any such correction would be most undesirable as it would affect all the mixer inputs. The use of a magnetic pick-up cartridge would also bring hum problems.

THE CIRCUIT


The matching unit comprises four separate preamplifiers, one of which is shown in Fig. 1, and calls for an equalising circuit which has a frequency

The component list above is for all four preamplifiers. If any other form of BC184 is used check leadout connections against those shown.

CONSTRUCTION

The printed circuit board is shown full size in Fig. 2 together with the layout of the components on the board. The prototype board is mounted on the rear right of the Disco control panel, next to the pick-up inputs. The turntable screened leads

CARTRIDGE	R1-4	C1-4
Sonotone 9TAHC	1MΩ	47pF
Coloring CS96	100kΩ	150pF
Aeos ceramic	680kΩ	100pF
BSR ceramic	1.2mΩ	None

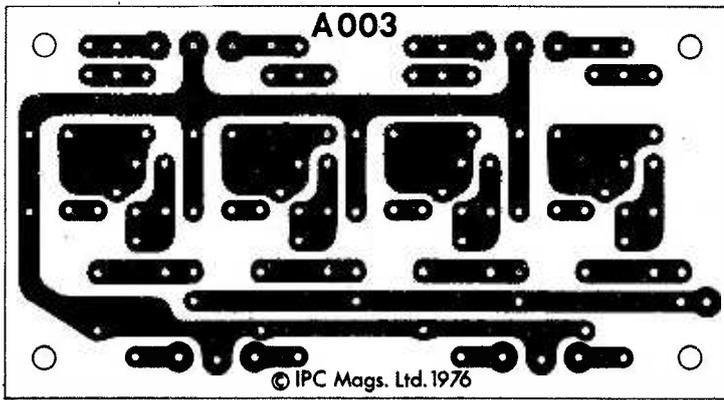

are disconnected from the mixer inputs and connected to the corresponding inputs on the matching unit. The screen of each pick-up lead is connected to the respective centre pin of each input, as indicated on the PCB.

The output of each preamplifier is connected to the respective mixer input in a similar manner, using short lengths of screened lead ensuring that the screens of these are connected to BOTH the matching unit and the mixer's copper plane. This also provides the negative side of the supply voltage. The supply for the unit is obtained from the 30V positive stabilised supply which feeds the main preamplifier board in the Disco.


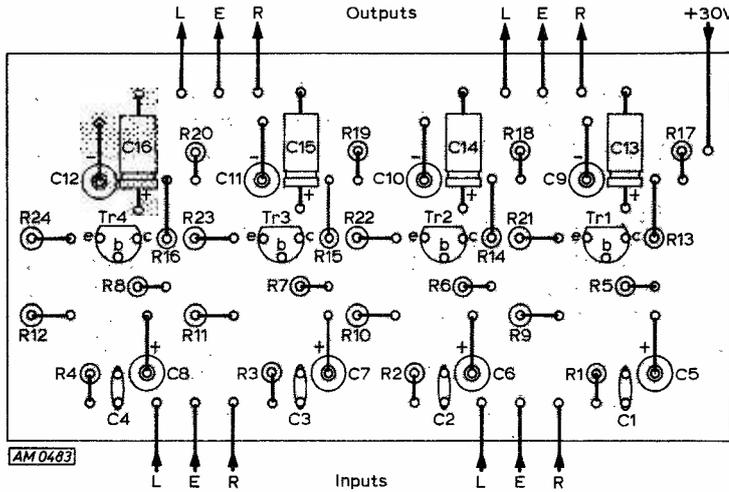


Fig. 2: The PCB is shown here full size for the four preamplifiers, together with the component layout.

MONO OPERATION

The matching unit may also be used for a mono pick-up but it must be appreciated that a stereo cartridge connected for mono will require slightly different values for the resistor R1 and capacitor C1, which will have to be found by trial and error. On mono only two of the matching amplifiers need be wired up on the printed circuit board. Pw

TECHNICROSS No. 14

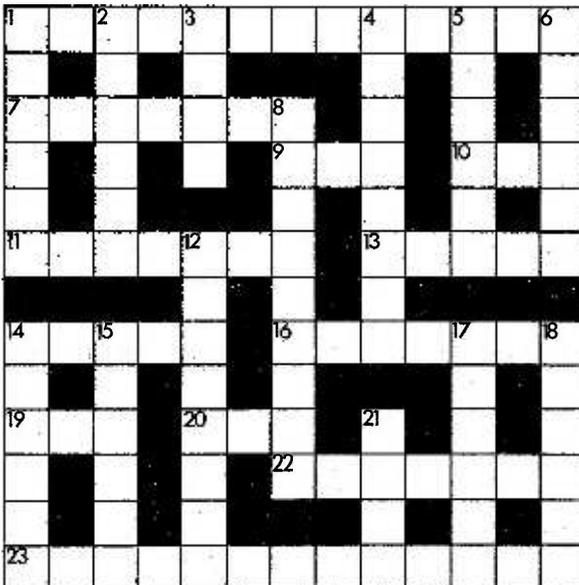

ACROSS

- 1 Signal success with this cleaner type? (3-4, 6)
- 7 Lace used in 14 Down? (7)
- 9 Oscillator badly installed? (3)
- 10 Little senior citizen starts O.A. Peru (3)
- 11 Onions and rice but no ham in it (7)
- 13 Soothe media about one subject (5)
- 14 His receiver is in the loft (5)
- 16 He arranges aerial exhibitions (7)
- 19 Army power unit on 2 Down? (3)
- 20 Drop of spirit around tone-nut? (3)
- 22 A case of over-charging? (7)
- 23 Hear them as substitutes for letters (8, 5)

DOWN

- 1 Undistorted in real modulation? (6)
- 2 Radio sisters at the spa? (6)
- 3 Power unit with split infusion (4)
- 4 There's no interfering with this! (8)
- 5 Do tire of adapting such valves ... (6)
- 6 ... and smoothing over such voltage problems? (6)
- 8 Thousands of burn-outs! (9)
- 12 It's opened up at full power (8)
- 14 Addiction to the relay system? (4-2)
- 15 It gets woolly reception from Spain (6)
- 17 Linked with the 007 programme? (6)
- 18 Fiddlers in the radio business? (6)
- 21 C.I.D.'s distortion is a record? (4)

FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH

Dear Sir,



letters

Unjust comment?

I have just bought a Sinclair Oxford 300 calculator, and consider your comments in the "Special Product Report" on this calculator, completely unjustified.

First, I would not describe the case as "dull" but rather plain; it is functional rather than "flashy", and the on/off switch is, contrary to your opinion, perfectly acceptable. I find it exceptionally good for hand-held operation, and no worse than most, for desk-top use.

I would therefore like to congratulate Sinclair for producing an extremely able calculator at a very modest price, and in my opinion stands up very well when compared with more expensive models.—Sean Kelly (Nottingham)

Speedy valve

After fruitless weeks searching my local dealers in Eastbourne for a 6BR7 valve, and obtaining comments like "No sir, never heard of that before", or "you won't get one of those these days", I wrote to RST Valve Co.

I posted the order on the 15th March and got my valve on the 17th March. As you can imagine I was amazed at this type of service. Thank you RST and PW.
Brian Ward (Eastbourne)

Save it!

When using the PW Tuner Cassette in a tape machine with a remote control facility, it is possible to save on batteries by simply plugging in the micro-

phone and moving the mic. switch to OFF. This switch is usually wired as a pause control, and turns off the power to the motor only, leaving the electronics supplied with power. This is for setting-up purposes, such as obtaining a correct recording level.

An alternative to this, if the microphone has no ON/OFF switch, or to obviate the need for carrying the microphone, is to insert a suitably wired spare plug in the 'remote' or possibly the 'mic' socket depending upon the type of connection used. The problem of dents in the pinch wheel, is eliminated by a small stiff strip in the tuner cassette, which occupies the same position as the tape would in a normal cassette. This prevents the capstan coming into contact with the wheel whilst not running.—Peter Rostgaard (Broxbourn)

Good work, Robin!

The Geography teacher at Codsall Comprehensive School wanted to build the PW Music Box electronic organ for his children and, knowing my enthusiasm for electronics, asked me to help him, although I am at another school. We only worked for about an hour a week but managed to finish it and to tune it with the aid of a piano. Another teacher, Mr. Simkin has a commercial version of the organ but prefers ours to his own! The Headmaster Mr. Bates, and teachers Messrs Price, Mincher and Mansell were all impressed with a demonstration so all I can say is that it is a very good design.

I hope that you can publish my letter.—Robin Bayley (Kingswood School, Allrighton, near Wolverhampton)

What? No rumba

The Rhythm Generator project featured in May '76 PW undoubtedly created great interest among constructors who are musically inclined and tribute must be paid to the skill of SGS-ATES in designing the M252 device which is the basis of the project. Musical readers may at

the same time share my curiosity why given a capability of 15 rhythms, SGS-ATES elected to include the rarely used Jazz Waltz and Shuffle at the expense of the much more common Rumba.

This is perhaps even more puzzling when one observes that the companion device M253 (which provides for 12 rhythms) actually includes the Rumba but excludes not only the Jazz Waltz, Mambo and Bajon—but also the ubiquitous Foxtrot.

Unless there is an electronic explanation—and I can think of none—one is tempted to conclude that SGS-ATES know a great deal more about IC technology than they do about contemporary dance rhythms! D G Daverson (Brentwood)

Wake-up PW

I understand from your company that you have cancelled your subscription service. Could this possibly be true? If so, this must surely mean one more nail in the proverbial coffin of yet another well established, and, I gather, profitable magazine.

I know many people, including myself, who took PW by subscription, who will now think twice about taking PW on a regular basis, especially as recent price increases have pushed the price out of all proportion. True, it's a good magazine, but when you have to go out of your way to obtain a copy, its logical that you'll only do it if there is something published that really captures the imagination.

This action possibly affects your foreign readers even more so than your UK readers. They have no way of obtaining a copy, except by subscription.


How many readers can you afford to lose by such moves? Another point that I would like to grouse about is the subject of back editions of PW. Many times since taking PW, I have been told of an interesting project that was published in months gone by. I would gladly pay the cover price plus a little extra to get my hands on that particular issue. But can I?—not on your life!

So come on PW, wake-up, and lets have a bit of good old-fashioned service for your faithful readers.—T. McCahill (Barrow-in-Furness).

PRODUCTION LINES

colin riches

ANTEX ALARMS

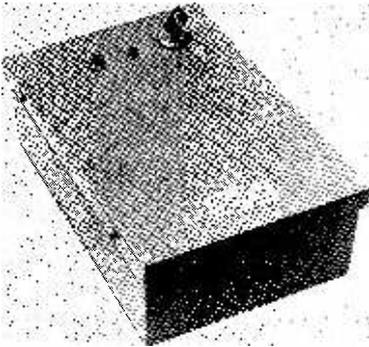

Antex (the soldering iron people) have launched what is believed to be the first D.I.Y. burglar alarm kit which complies with the BS 4737 Standards.

The picture shows the control box of the battery-operated version (model A1 B). The kit comprises the control box with instructions, 6in. (15cm) alarm bell, heat sensor, exit/entry switch, 6 magnetic contacts, 30 metres twin and 15 metres 4-core cable, 100 cable clips, screws, rawlplugs, terminal block. Price is £50 plus 25% VAT and batteries.

A mains/battery version is also available for £74.

The control box is a strong steel box of pleasing appearance. It houses the electronic circuit necessary to ensure reliable operation and to reduce the chances of false alarms to a minimum. Magnetically operated switches are fitted to doors and windows where an intruder is likely to attempt gaining access to the property. These switches are connected to the control box by "double pole wire". The control box is fitted with a key-operated ON/OFF switch. When the key switch is set to the ON position, any of the door or window switches being opened will cause the alarm to sound. Closing the door or window again will not stop the alarm sounding. Cutting either or both of the double pole wires or shorting them together will also cause the alarm to sound. The only way to stop the bell ringing under any of these conditions is to turn the ON/OFF key switch on the control box to the OFF position.

Further information from *Antex Electronics Limited (Dept. P.W.), Mayflower House, Plymouth, Devon. Telephone: 0752 67377/8.*


TRIMMING POTS

Lemo (UK) have announced a range of minilinear and exponential trimming potentiometers: the Siegert cermet TPO C range. Measuring 4 by 5 by 2.6mm, they are ideal for p.c.b. and hybrid circuit work. Values offered are from 470Ω to 1MΩ (exponential), or 100Ω to 1MΩ (linear), at a power rating of 150mW at 70°C.

The exponential effect is achieved by joining two tracks of differing characteristics, at a point between 125° and 165° of function angle. Total angle of travel is about 260°. Resistance tolerance is ± 30%. Siegert say that the potentiometers comply with DIN 41 450 when used as trimmer resistors.

Applications suggested for these micro potentiometers include car and pocket radios, paging devices, com-

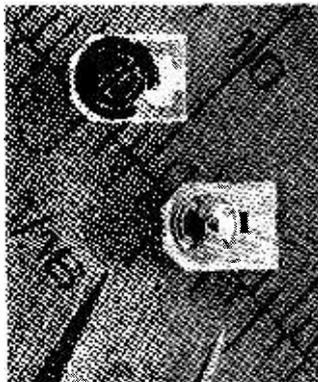puters, hearing aids, calculators, electronic watches and defence circuitry. Further gen from: *Lemo (UK) Ltd., (Dept. P.W.) 6 South Street, Worthing, Sussex BN11 3AE. Telephone: 0903 204651.*



CABLE METER



Electronic Services & Products Limited announce a new instrument for accurately determining the length of coaxial cables and the location of open faults.

Its circuit incorporates ICs; it is completely portable and its small size makes it an ideal piece of test equipment for Service Engineers, TV Service Departments and Engineers concerned with the location of open faults.

Measurement is made by connecting the cable to the instrument and reading the length directly in metres off a linear scale. Lengths of coax from less than 10cm up to 100metres of either 50Ω or 75Ω cable can be accurately measured simply by selecting one of the four ranges.

Power is provided by a 9V PP3 battery or similar type and a LED battery monitor is incorporated which does not light when the battery voltage drops below a certain value thus preventing a false reading being made.

Price of the instrument is £45.00 inclusive of batteries. For further details contact: *E & L (Dept. P.W.) Cross Lane, Braunston, Nr. Daventry, Northants. Telephone Rugby 890672.*

TRANSFORMERS GALORE

S. G. Wright Ltd. of Burnley inform us that as transformer suppliers their boast is that they have a transformer for almost every application required in P.W. projects. In fact, they have their own winding equipment and will wind to readers' specs. at very keen prices.

If you send them a stamped, addressed envelope, they will be pleased to forward a free copy of their catalogue/price list. *S. G. Wright's Ltd., (Dept. P.W.) Bishop House Works, Rylands Street, Burnley, Lancs. Tel: 26934.*

TAPE-SLIDE SYNCHRONISER

Square M Electronix inform us that they market a "Mark III" tape-slide synchroniser for £20 plus 90p for postage and packing.


It is designed for use with automatic slide projectors and reel-to-reel or cassette stereo tape recorders. The 1kHz pulse signal duration is pre-timed to make it suitable for use with any automatic projector. Connecting leads are suitably terminated to suit standard DIN configurations.

In order to achieve the maximum economic use of a cassette tape, the recording of the pulse is on the left-hand channel and the commentary or music on the right-hand channel. This facility enables the use of cassettes in both directions (side 1 and side 2). This selection of tracks offers greater flexibility with commercially available cassette recorders. At the same time, however, the possibility of the recorded 1kHz pulse interaction between channels is minimised. Due to the track allocation for cassettes, the LH channels are well separated when the recording is made on side 1 and side 2.

Although the selection of tracks is not compatible with the Philips system, which restricts the cassette to unidirectional use requiring a special record-replay tapehead, the Square-M Electronix method offers bi-directional use of either cassette or reel-to-reel recording and reproduction facilities of any commercial unit.

By special request, the wiring of the pulse record and replay DIN socket can be made in accordance with CET'S, USPEC 2 or IEC proposals for international pulse standardisation.

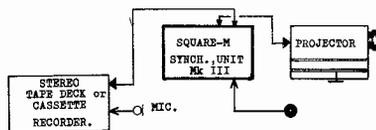Further information on this very interesting piece of equipment may be obtained by sending a stamped, addressed envelope to Square M Electronix (Dept. P.W.) 34 Rippleside, Portishead, Bristol, BS20 9NB. Telephone: 0272 844595.




The diagram above shows how the synchroniser is connected to an automatic projector and stereo recorder. The photograph shows the unit together with a typical recorder and projector.

PYE PORTABLE

Pye Ltd. have launched a new portable receiver called the 1650. It has a power output in excess of 1 watt, has four wavebands, long, medium, VHF and a 49 metres shortwave band. There is also a push-button wave change together with a slider volume control.

An internal ferrite rod aerial is provided for long and medium wavebands, while for shortwave or VHF listening there is an external hinged telescopic aerial.

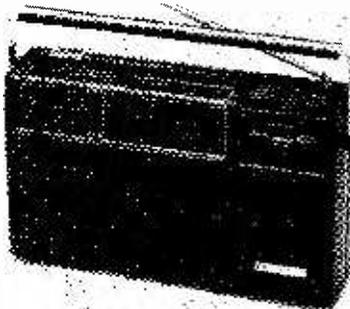
The 1650 can be mains or battery operated, each set being supplied with a detachable mains lead. Should battery operation be preferred the power source is four standard 1.5



volt batteries. There is a separate on/off switch which allows controls to be pre-set and a two position tone control—high and low. Should the use of an earphone be required there is an earpiece socket suitable for 3mm plug.

Housed in a scratch resistant black Abstrene cabinet with silver carrying handle, the 1650 is equally suitable in the home or in a 'knock about' situation. It measures 267mm x 153mm x 60mm, and the recommended retail price is £37.50.

BURGESS SOLDERING IRON

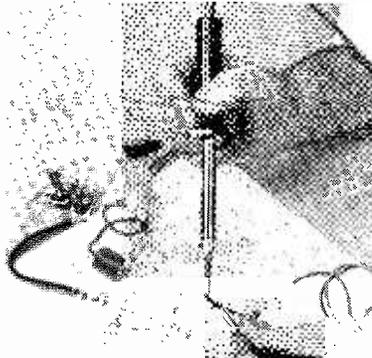


Burgess Power Tools Limited have introduced a new Soldering Iron and a complete soldering kit. Both are available through tool stores and DIY shops.

The Model 25 Powerline 25 watt Electric Soldering Iron is balanced to allow it to be laid on the bench or worktable without the soldering tip resting on the working surface. It has a long-life copper/cobalt tip which is easily exchangeable, 6ft. (1.9m) of cable, and is guaranteed for twelve months. Recommended retail price is £3.25 plus 8% VAT.

The Powerline soldering iron is also contained in the Model 25K kit which also includes a supply of resin-cored solder, a heat dissipator, a locating and positioning probe, tweezers, and an interchangeable 2.30mm (3/32in) cobalt/copper tip for intricate work. This kit is also guaranteed for twelve months and full working instructions are included with both models. The cost of the Model 25K is £4.50 (r.r.p.) + 8% VAT. Burgess Power Tools Limited, (Dept. PW), Sapcote, Leics. LE9 6JW. Tel: 045.527.2292.



GOING BACK...

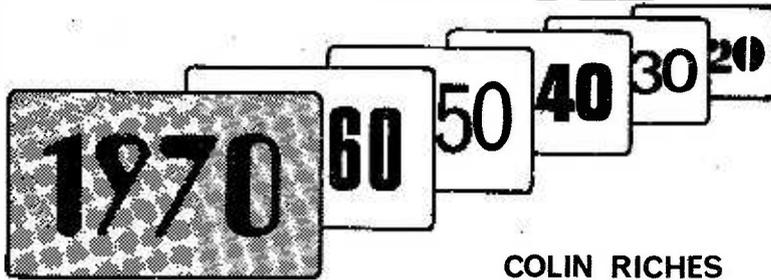

Dynatron info.

THIS month, I wonder if readers could help me a little. I am searching for information on the Dynatron company together with photographs of some of their earlier receivers. I hope to compile a "Going Back" on this firm some time in the future and any help would be mightily appreciated!

Vintage meeting

REMEMBER from time to time we mention Tudor Rees' vintage wireless emporium? Well, if any readers are interested, Tudor is holding a meeting on July 4th at 64 Broad Street, Staple Hill, Bristol BS16 5NL. Anyone interested in vintage radio is cordially invited to attend and take along a piece of vintage gear or a component to show around and have a general chin-wag about the "good old days". I'm afraid it's rather short notice but Tudor's on the phone if anyone wants to get in touch (Bristol 565472). Should be well-worth attending! Whilst on the point, Tudor tells me that his 1976 full catalogue is ready. Apart from equipment for sale, the catalogue includes some photographs of early gear, period adverts (my favourite) and technical tips. Price is 50p post paid or for our colleagues across the pond, \$2 airmail, post paid.

Sir William Preece

SIR William Preece, F.R.S. was without doubt one of the country's most outstanding engineers at the end of the Victorian era. He influenced the course of Victorian telecommuni-

COLIN RICHES

cations development in the United Kingdom more than any other man. As Preece grew to manhood (he was born three years before Victoria came to the throne) electricity began to be utilised for signalling and silver plating. With the discovery of more about the qualities of electricity, physicists had to amend their hypotheses. That process of revising theories was bound up in the Victorian way of life. It is therefore rather apt that a record of Preece's life should be published in the year that marks Alexander Graham Bell's invention of the telephone.

The record comes in the form of a book entitled "*Sir William Preece, F.R.S., Victorian Engineer Extraordinary*". Author is E. C. Baker and there is an introduction written by Professor J. H. H. Merriman of the Post Office.

Preece said once of Marconi, at a Royal Institution lecture in 1897, "He has not discovered any



Sir William Preece, F.R.S.

new rays. His receiver is based on Branly's coherer. Columbus did not invent the egg, but he showed how to make it stand on its end. Marconi has produced from known means a new electric eye more delicate than any known electrical instrument, and a new system of telegraphy that will reach into places hitherto inaccessible..."

This book has been written with great charm and erudition. It is a volume which will be welcomed by all those interested, or engaged in, all fields of telecommunication. As today's prices go, you get very good value for £6.50 with this book. Publishers are: Hutchinson & Co. Ltd., 3 Fitzroy Square, London, W.1.

Vintage CC

BOOKS FOR DISPOSAL

Would sell or swap the following for an SX28 or AR88, condition unimportant so long as it's complete. Wireless Telegraphy and Telephony by W. H. Eccles (c1915). Newnes Everyman's Wireless Book by F. J. Camm (c1937). Newnes Chronicle Wireless Constructors Encyclopaedia by F. J. Camm (c1938). The Book of Practical Radio by J. Scott-Taggart (c1933). The Elementary Principles of Wireless Telegraphy by R. D. Bangay (c1918). Admiralty Handbook of Wireless Telegraphy (c1925) and R.S.G.B. Handbook and Supplement 2nd. Edition (c1941).—R. W. Sharp, 77 Cloche Way, Upper Stratton, Swindon, Wiltshire.

WANTED

Valves VY2 and VCL11 for pre-war German Peoples Set. I have crystal sets for exchange. H. H. Journeaux, 7 Blair Avenue, Parkstone, Poole, Dorset. Tel. Parkstone 748072.

... Any gen on Admiralty Pattern M361 receiver, serial number 5708. It has 4 valves—two HF stages, either SG or HF pentodes. Detector is an SP2 with a PM22A as output. Tuning ranges: 235-100kHz, 510-215kHz, 1080-460kHz, 2250-1000kHz, 4500-2000kHz. When tuned to the last range, a 6th range can be obtained by moving a plug on each of the 3 coils from a socket marked "out" to "in", when the range changes to 8500-3500kHz.—Dr. H. S. Brodribb, 8 Brittany Road. St. Leonards-on-Sea, TN38 0RA.

write your own
messages on
the tv screen!

pw 'Easybuild'


VIDEO-WRITER

IN NEXT MONTH'S
**PRACTICAL
WIRELESS**

The Video-Writer resembles a typewriter but it displays the text directly on the screen of a domestic TV set or a video monitor.

A page of text, which is alphanumeric with a wide range of punctuation, comprises 16 lines of 32 characters. Hold one page in memory while composing the second!

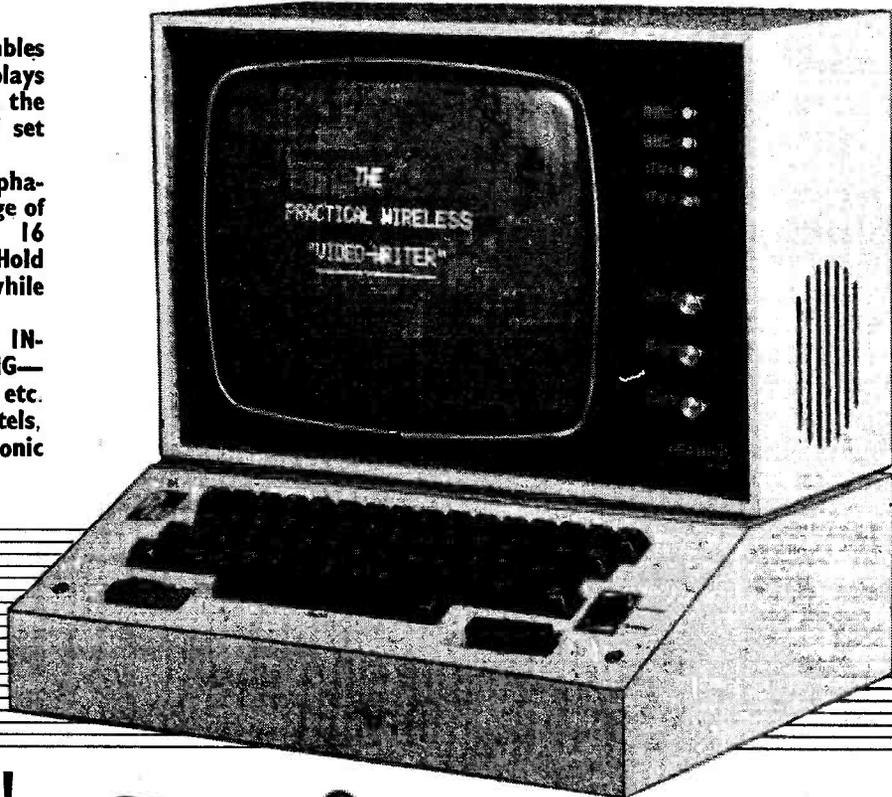USE IT for DISPLAYING INFORMATION—ADVERTISING—SCORING for darts, bowls etc.—silent PAGING in hotels, clubs, libraries — electronic SCRABBLE.



BOAT OWNERS!
DON'T BE A SLAVE TO
YOUR ECHO SOUNDER
FIT THIS SIMPLE



**AUDIO
DEPTH
ALARM**



&


**Cassette
POWER SUPPLY
for Cars**

ON SALE IN JULY

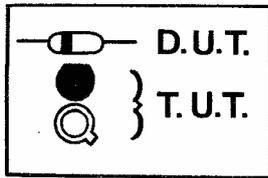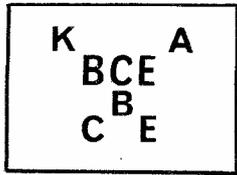

A VERSATILE TRANSISTOR TESTER


Ian HICKMAN

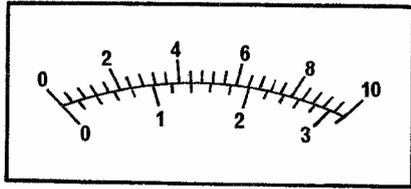

Parameters

- h_{FE} Direct Current Gain.
- h_{fe} Dynamic Current Gain.
- I_{CES} Collector Current Flowing With Base Short Circuit To Emitter.
- I_{CEO} Collector Current Flowing With Base Open Circuit.
- r_{dON} Drain/Source Slope Resistance At Zero Gate Voltage.
- V_G Gate Voltage Of FET's.
- I_{DSS} Drain Saturation Of FET's.

VERY useful adjunct to any electronic laboratory, home or professional, is a versatile transistor tester, especially if it will also test diodes, zeners, FET's, light-emitting diodes etc. In the nature of things, a transistor tester comes in for intermittent use, rather than the longer periods of use typical for signal generators, level meters and test instruments generally. Thus, if power transistors are excluded, a transistor tester can be conveniently designed to run from internal batteries. The freedom from a mains lead greatly enhances

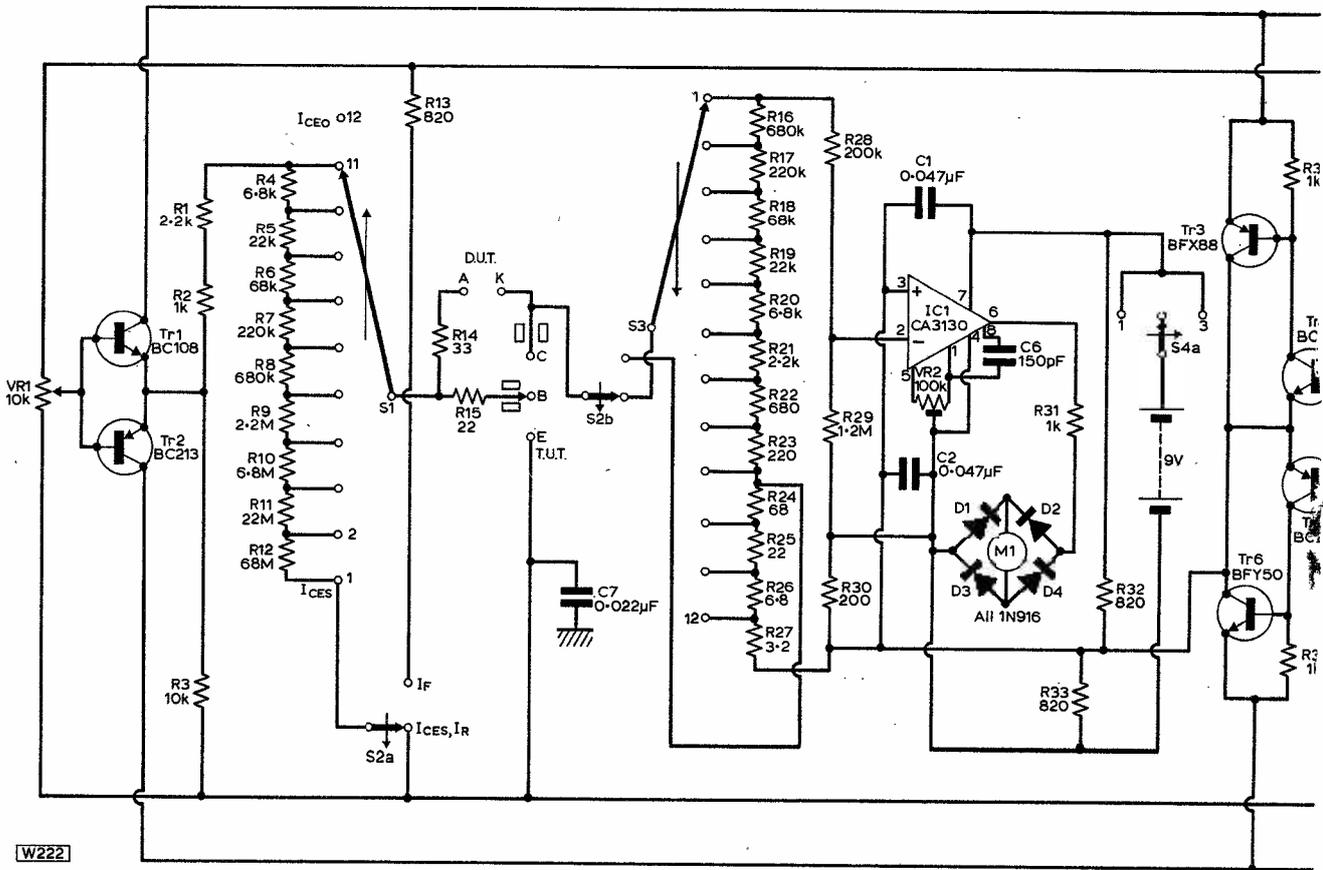


W222

Parameters

- Direct Current Gain.
- Dynamic Current Gain.
- Collector Current Flowing With Base Short Circuit To Emitter.
- Collector Current Flowing With Base Open Circuit.
- Drain/Source Slope Resistance At Zero Gate Voltage.
- Gate Voltage Of FET's.
- Drain Saturation Of FET's.

A VERY useful adjunct to any electronic laboratory, home or professional, is a versatile transistor tester, especially if it will also test diodes, zeners, FETs, light-emitting diodes etc. In the nature of things, a transistor tester comes in for intermittent use, rather than the longer periods of use typical for signal generators, level meters and test instruments generally. Thus, if power transistors are excluded, a transistor tester can be conveniently designed to run from internal batteries. The freedom from a mains lead greatly enhances


the instrument's utility and the maximum current of 30mA does, in fact, allow transistors to be tested satisfactorily, explained later. At the other end of the instrument allows transistors to be tested at collector currents down to a few nanoamperes whilst leakage currents of a few nanoamperes are indicated on the 500µA FSD meter. When an earlier version of this transistor tester was designed, the provision of direct

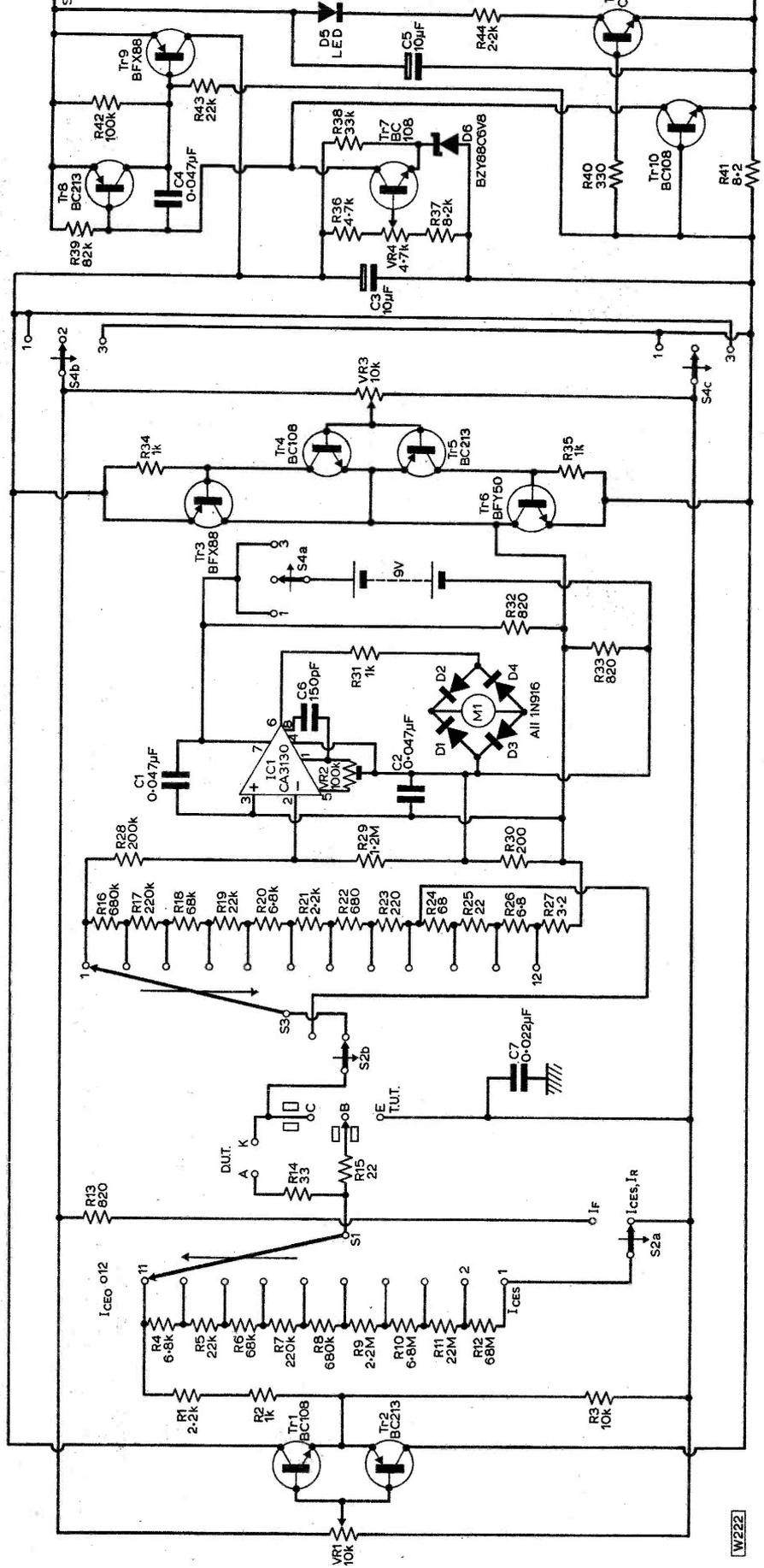

W222

Part 1

TRANSISTOR TESTER

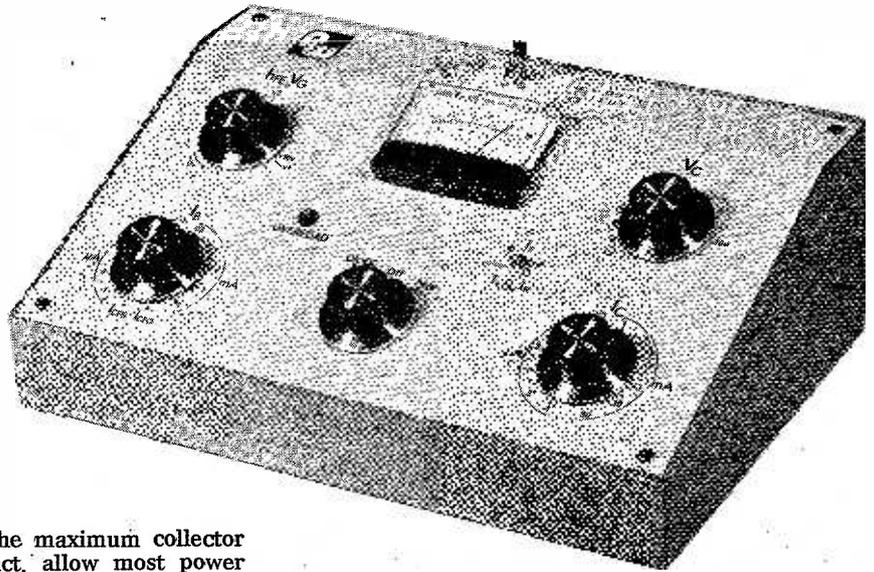

the instrument's utility and the maximum collector current of 30mA does, in fact, allow most power transistors to be tested satisfactorily, as will be explained later. At the other end of the range, the instrument allows transistors to be tested for h_{FE} at collector currents down to a micro-amp or less, whilst leakage currents of a few nanoamps are indicated on the 500 μ A FSD meter.

When an earlier version of this transistor tester was designed, the provision of direct reading scales

for h_{FE} at given collector currents was considered and rejected, as it was felt that defined values of base current in conjunction with a meter scaled in collector current were more convenient (the method of use is dealt with later) and the arrangement has been retained in the present design. However, the design still permits the measurement of h_{FE} at a given collector current if required. Also rejected was the inclusion of facilities for measuring h_{fe} since circuits depending on a transistor having a particular value of this parameter should be avoided wherever possible.

The result is a notably simple design, without the plethora of switching usually employed to cope with measurements on both NPN and PNP types, and which also tests J FETS, MOS FETS (enhancement and depletion types), diodes and zeners etc.

CIRCUIT DETAILS

As mentioned above, to measure the h_{FE} of a transistor the instrument injects a defined base current and displays the collector current. Referring to Fig. 1., assume that the NPN/PNP selector switch S4 has been set to NPN and an NPN transistor has been connected to the correct "transistor under test" TUT terminals. In this position, transistors Tr2, Tr5 and Tr6 are not used and the emitter of Tr1 is at a voltage with respect to the lower end of R3, determined by the setting of VR1. When the latter is set to the scale indication denoting $h_{FE} \times 1$, this is 10.5V. The odd 0.5V is a compromise allowance for the V_{be} of the transistor under test, be it silicon or germanium, and hence there is 10.0V across the base current resistor chain. The resistance in circuit, selected by the BASE CURRENT switch S1, may be set at 3.2K ($R1+R2$) in position 11 to 100M Ω in position 2. Thus the base current can be set in 10 steps from 3.16mA down to 0.1 μ A. At the lower currents, the V_{be} of Tr1 tends to fall some-

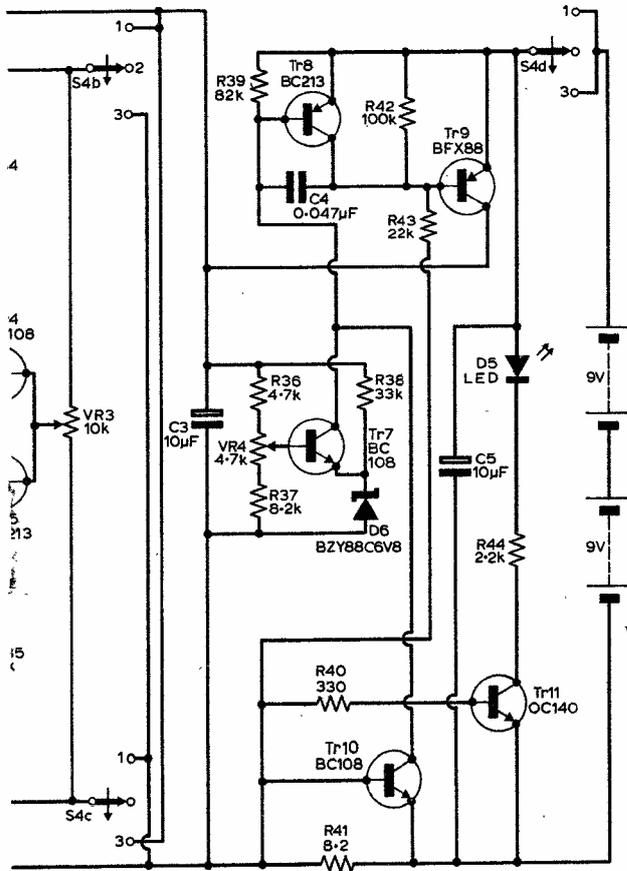


Fig. 1. Circuit diagram including inter-component wiring on the P.C.B. For clarity most of the functions performed by switches and variable resistors have not been shown. Note, suitable cut-outs for the meter scale and the D.U.T./T.U.T. panel are incorporated in the heading.

★ components list

Resistors

R1	2.2kΩ 1%	R25	22Ω 1%
R2	1kΩ 1%	R26	6.8Ω 1%
R3	10kΩ	R27A*	6.8Ω 1%
R4	6.8kΩ 1%	R27B*	6.8Ω 1%
R5	22kΩ 1%	R27C*	47Ω 1%
R6	68kΩ 1%	R28	200kΩ
R7	220kΩ 1%	R29	1.2MΩ
R8	680kΩ 1%	R30	200Ω
R9	2.2MΩ 1%	R31	1kΩ
R10	6.8MΩ	R32	820Ω
R11	22MΩ	R33	820Ω
R12	68MΩ	R34	1kΩ
R13	820Ω	R35	1kΩ
R14	33Ω	R36	4.7kΩ
R15	22Ω	R37	8.2kΩ
R16	680kΩ 1%	R38	33kΩ
R17	220kΩ 1%	R39	82kΩ
R18	68kΩ 1%	R40	330Ω
R19	22kΩ 1%	R41	8.2Ω
R20	6.8kΩ 1%	R42	100kΩ
R21	2.2kΩ 1%	R43	22kΩ
R22	680Ω 1%	R44	2.2kΩ
R23	220Ω 1%		
R24	68Ω 1%		

* These three in parallel equal 3.2Ω

All resistors are 5% 1W carbon film unless otherwise stated. TR5 Metal Oxide resistors in 2% tolerance range are usually nearer 1% and could be used instead of 1% as specified without appreciable loss of accuracy.

Variable resistors

VR1	10kΩ Panel Mounting
VR2	100kΩ Skeleton Vertical
VR3	10kΩ Panel Mounting
VR4	4.7kΩ Skeleton Vertical

Semiconductors

Tr1	BC108
Tr2	BC213
Tr3	BFX88
Tr4	BC108
Tr5	BC213
Tr6	BFY50
Tr7	BC108
Tr8	BC213
Tr9	BFX88
Tr10	BC108
Tr11	OC140

IC1 CA3130

D1	1N916
D2	1N916
D3	1N916
D4	1N916
D5	Any LED
D6	BZY88C6V8

Switches

S1	1 Pole, 12 Way, Rotary.
S2	2 Pole, 2 Way, Biased Toggle, Miniature
S3	1 Pole, 12 Way, Rotary.
S4	4 Pole, 3 Way, Rotary.

Miscellaneous

Meter, 500μA FSD Watford Electronics, type T23. Batteries, 2 off type PP7, 1 off type PP3, Connectors to suit. Case, 10½" x 7½" x 3½", Watford Electronics type W.E.1. Knobs, 4 off to suit switches and variable resistors. P.C.B., Readers PCB Services Ltd., see advert. Ferrite beads, 2 off 3/16" x 1/4" dia. Veroboard 2" x 1" approx., 0.15" Matrox.

what, resulting in more than 10V being applied across the S1 resistor chain. By drawing a 1mA standing current, R3 reduces this effect.

Alternatively, the base of the TUT can be earthed (via S2a and position 1 of S1) to measure the short circuit collector current I_{CES} or left open circuit (position 12 of S1) to measure the open circuit collector current I_{CEO} .

The base stopper resistor R15 and the anti-parasitic ferrite beads on the base and collector leads ensure that when the TUT is a very high frequency type it does not oscillate.

The collector current passes through a current shunt selected by the COLLECTOR CURRENT RANGE switch S3. The voltage drop across the shunt is always 100mV at full scale, thus a 3.2Ω shunt is used for the 30mA range (position 1 of S3) and 1MΩ (total) for the 100nA range (position 12 of S3). As resistors are only readily available down to 4.7Ω, the p.c. layout allows for three resistors in parallel, see Fig. 5. Two resistors of 6.8Ω and one of 47Ω provide the right value.

Note that the meter is so scaled that 1mA (FSD) on the 0-1mA range corresponds to 3.15mA on the "0.3mA" range, which is actually calibrated up to 3.2mA. This is important as will appear in the section on using the instrument.

The drop across the selected part of the collector current shunt, applied to the operational amplifier IC1 via the remaining shunts plus R28, is equivalent to a voltage source applied through a 1.2MΩ total. Since R29 is also 1.2MΩ the amplifier produces 100mV at the junction of R29 and R30 at FSD. Thus R30 defines the current through the meter. After passing through the current shunt the collector current is absorbed by the augmented emitter follower Tr4 and Tr3. This stage sets the collector voltage of the TUT, as determined by the setting of the COLLECTOR VOLTAGE control VR3.

When testing a PNP transistor, S4b and S4c invert the polarity applied to the TUT and also to VR1 and VR3. Thus the base current and collector voltage are now provided by Tr2, Tr5 and Tr6, but the scale calibration of the h_{FE} MULTIPLIER control VR1 and COLLECTOR VOLTAGE control VR3 still apply. The direction of collector current flow through the current shunt is reversed but this is of no consequence as the meter is in a bridge rectifier circuit. This arrangement results in less wiring and a neater layout compared to reversing the meter with extra poles on S4 and also simplifies testing of diodes for both forward and reverse current.

The meter amplifier is powered by a single 9V battery type PP3 and a stabiliser is not provided. The offset voltage of IC1 is adjusted by VR2 and, after initial setting to give zero reading on the meter, no further adjustment is required over a long period. An offset of either polarity will, of course, cause the meter to read due to the bridge rectifier action. To ensure meter protection the maximum overload current is limited to about four times full scale by R31 and the $r_{d(on)}$ of the output stage of IC1.

The TUT circuit is powered by 2 PP7 batteries, via a current limited stabiliser. This is so arranged that a 12V output can be obtained with only a few hundred millivolts drop across the regulator transistor Tr9, permitting the batteries to be used almost down to 1V per cell. On an intermittent use basis, the batteries would therefore provide many hours' use at 30mA drain and, of course, even longer

board blank by placing it over the board with a piece of carbon paper in between and then going over the p.c. tracks firmly with an HB pencil. Provided the copper has been well cleaned beforehand, the carbon paper will mark the copper clearly enough to be easily visible in an oblique light. For cleaning the copper, a piece of well-used "Scotch" green kitchen scouring cloth, used wet, is ideal. (When new it is a little **too** scratchy!) The tracks should next be marked in with a suitable ferric chloride resist using one of the fibre pens available for this purpose. The author used a brushing cellulose as sold for touching-up car paintwork. The p.c. pads were all marked in first, by applying a blob of the paint with a fine brush. Practice on an odd piece of copper clad board soon shows the right amount to apply; the paint will then spread out into a neat circle. Finally the shaded areas were filled in, using a paint brush. These areas not only reduce the supply rail impedance, they save a fair amount of ferric chloride!

After etching, which takes about half an hour, wash the board well. If cellulose paint has been used, it can be removed with "Polystrippa" paint


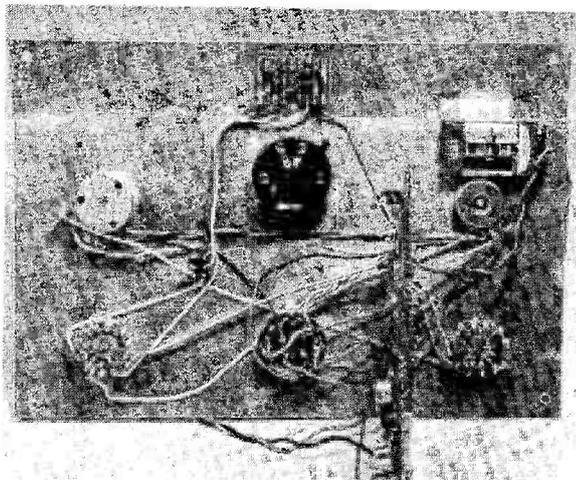


Fig. 4. Printed wiring pattern designed for minimum etch. This pattern is full size and may be traced directly onto single sided clad board.

Photo of reverse of front panel, with P.C.B. removed, showing main component positions.

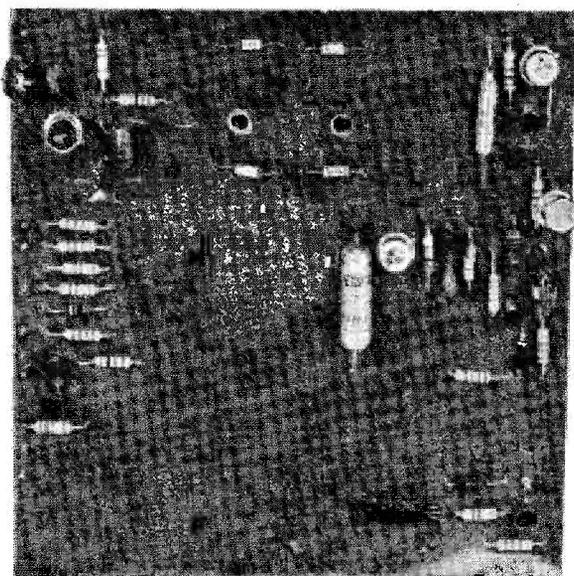




stripper. Wash the board well again and dry. It is best to drill the board and assemble all the components and pins straight away. The track side of the board can then be lightly varnished to prevent the copper tarnishing—a purely aesthetic point this. If available, "Letracote" spray is suitable, hair spray might even do at a pinch!

Having completed the p.c. board, assemble the controls, the meter and the test socket to the drilled front panel. Wire up as per the circuit diagram, noting that in Fig. 1 the arrows on the switch wipers indicate clockwise direction of rotation viewed from the front. The holder for the 9V PP3 battery powering the meter circuit is simply a strip of tinplate cut to size and stuck to the front panel with Araldite. Assemble the p.c. board to the meter and connect the pins to the front panel controls and battery leads as appropriate.

Part 2, to be published in our August issue, will describe the calibration and operation of the equipment.

Photo of the author's board. (Compare with Fig. 5.). Note the short component leads.

Fig. 5. Component side of the board with component locations identified. The track pattern is shown to eliminate the possibility of wrong insertion.

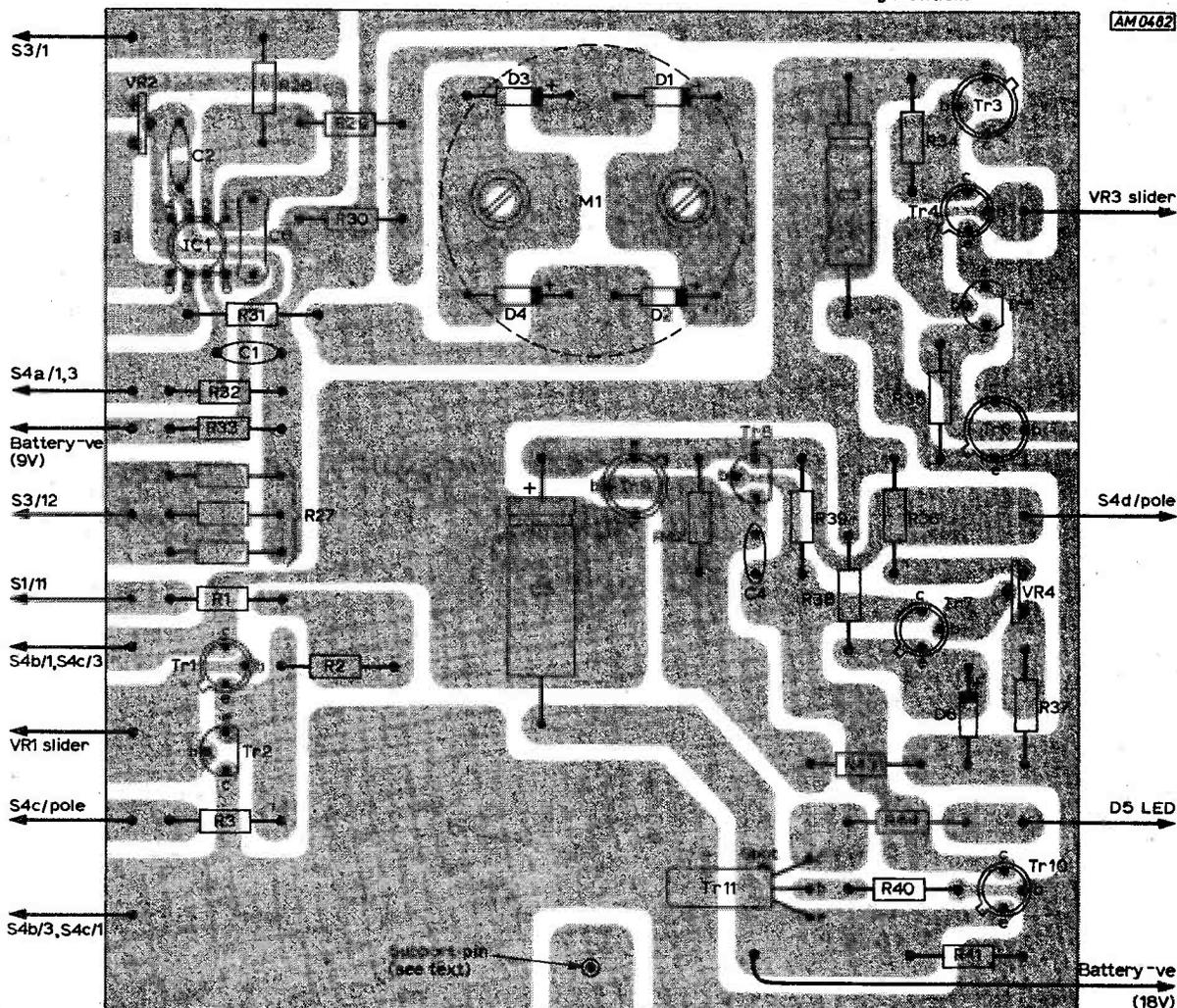


The Black Watch kit

£14.95!

* **Practical**—easily built by anyone in an evening's straightforward assembly.

* **Complete**—right down to strap and batteries.

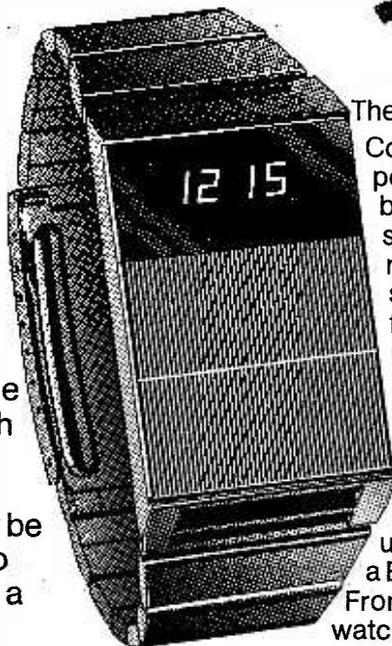* **Guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day—but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.






The Black Watch by Sinclair is unique. Controlled by a quartz crystal, and powered by two hearing aid batteries, it uses bright red LEDs to show hours and minutes, and minutes and seconds. And it's styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.

The Black Watch kit is unique, too. It's rational—Sinclair have reduced the separate components to just four—and it's simple: anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.

Touch and tell

Press here for hours and minutes... here for minutes and seconds.

Batteries easily replaced at home.

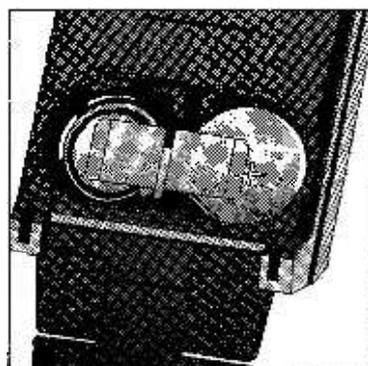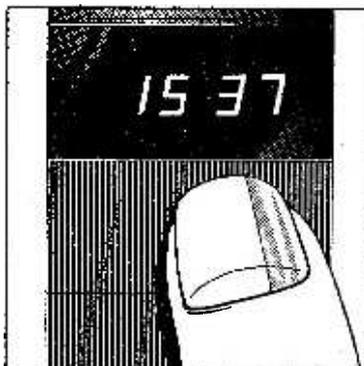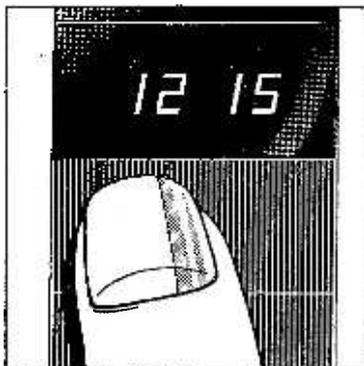

The specialist features of the Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra—see order form.)

Large, bright, red display—easily read at night. Touch-and-see case—no unprofessional buttons.

Runs on two hearing-aid batteries (supplied). Easily re-set using special button—no expensive jeweller's service.

The Black Watch—using the unique Sinclair-designed state-of-the-art IC.

The chip...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology—integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate *all* circuitry for a digital watch on a single chip.

...and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.

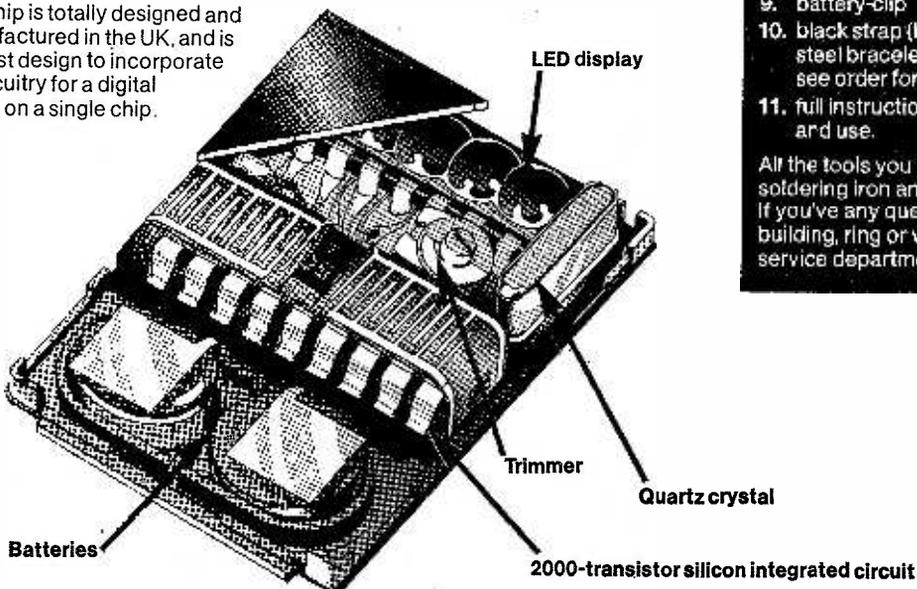

Complete kit £14.95!

The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra—see order form)
11. full instructions for building and use.

All the tools you need are a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to Sinclair service department for help.

Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit in original condition within 10 days and we'll refund your money without question. All parts are tested and checked before despatch—and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it—today!

Price in kit form: £14.95 (inc. black strap, VAT, p & p).

Price in built form: £24.95 (inc. black strap, VAT, p&p).

sinclair

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ.
Tel: St Ives (0480) 64646.

Reg. no: 699483 England, VAT Reg. no: 213 8170 88.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch kit(s) at £14.95 (inc. black strap, VAT, p&p).

* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.

..... (qty) Sinclair Black Watch(es) built at £24.95 (inc. black strap, VAT, p&p).

* Please debit my *Barclaycard/Access/American Express account number

..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p).

Name (please print) _____


Address _____

Signature _____

PW/7

FREEPOST—no stamp required.

* Delete as required

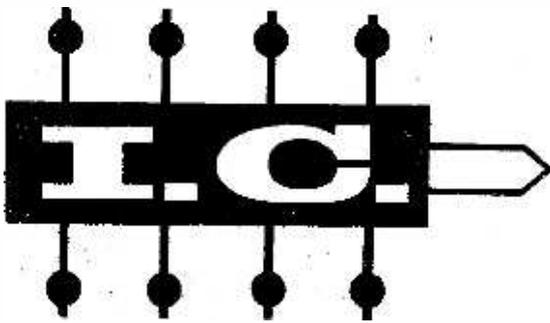

OF THE MONTH

by BRIAN DANCE

Number 59 LM1808 IF AMPLIFIER/FM DET/AUDIO PACKAGE

THE AVAILABILITY of modern integrated circuits specifically designed for radio applications has enormously simplified the design of modern receivers. Nevertheless, we are still some way from the time at which a radio receiver can be made by connecting an IC to a tuning control, a volume control and a loudspeaker without the use of any other components. However, the recent release of the National Semiconductor LM1808 device has moved us a step nearer to this ideal, since it contains an IF amplifier/limiter, FM detector, electronic volume control and a 2W audio power amplifier in a single package.

Although the LM1808 has been primarily developed as a television sound system the IF amplifier circuit is very similar to that of the LM3065 device (equivalent to the RCA CA3065 and the Fairchild 3065) which is intended for television sound IF use. These devices are rather similar to the 3075 types intended for FM IF radio applications. The LM1808 has a better volume control circuit than the 3065.

In addition, the LM1808 contains an audio power amplifier similar to the well-known LM380N. This power amplifier can be used with simpler circuitry than is possible with many other types and it is fully protected against shorting of the output and against thermal overloads.

CIRCUIT

The LM1808 is a dual-in-line device with 18 pins; this unusual number of connections makes it rather difficult to obtain a ready made socket for the device. The connections are shown in Fig. 1 together with the internal circuitry in block form.

A typical circuit for the use of the LM1808 is shown in Fig. 2. The IF input is fed to pin 13 via C5. Pin 12 is the other input of the differential amplifier; it is necessary to keep pins 12 and 13 at almost the same steady potential by means of a resistor R2. The input impedance is about 17k Ω , whilst an input of about 200 μ V is required to cause limiting of the input amplifier. The output of the amplifier is fed to the demodulator circuit, the tuned circuit connected to pins 9 and 10 forming part of the demodulator. The Toko tuned circuit type KACS-K-586HM has been found very suitable for use as a 10.7MHz tuned circuit in this application; it is available from Ambit International, 25 High St.,

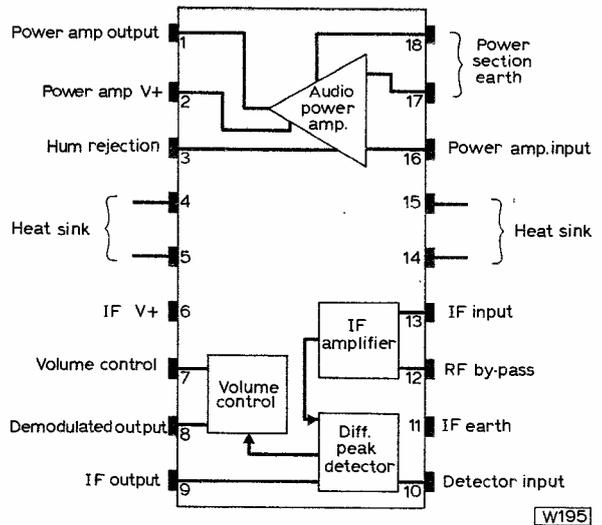


Fig. 1: Top view of the pin connections for the LM1808 with the internal stages shown in block form.

Brentwood, Essex, CM14 4RH. The Toko type 94AES 30465N should also be suitable.

The detector output is fed to the volume control circuit. Variation of VR1 of Fig. 2 will provide a linear variation of the output over a very wide range, typically 75dB. When pin 7 is earthed, the residual feed-through signal at pin 1 does not exceed 15mV RMS. The connection to pin 7 controls the volume by its steady DC potential; no signal voltages are present across VR1. A long unscreened lead can therefore normally be used to connect VR1 to the LM1808, since any hum or noise picked up by this lead can be bypassed and will not appear at the output. The rejection of amplitude modulated signals, including car ignition noise, is over 40dB for inputs of 1mV to 100mV RMS.

POWER STAGE

The audio output from pin 8 is fed via C7 to the input of the power amplifier at pin 16 where the input impedance is typically 200k Ω . C6 is an optional capacitor which will provide about 38dB rejection of any hum on the power supply line; a smaller value of this capacitor will also provide a useful amount of hum rejection.

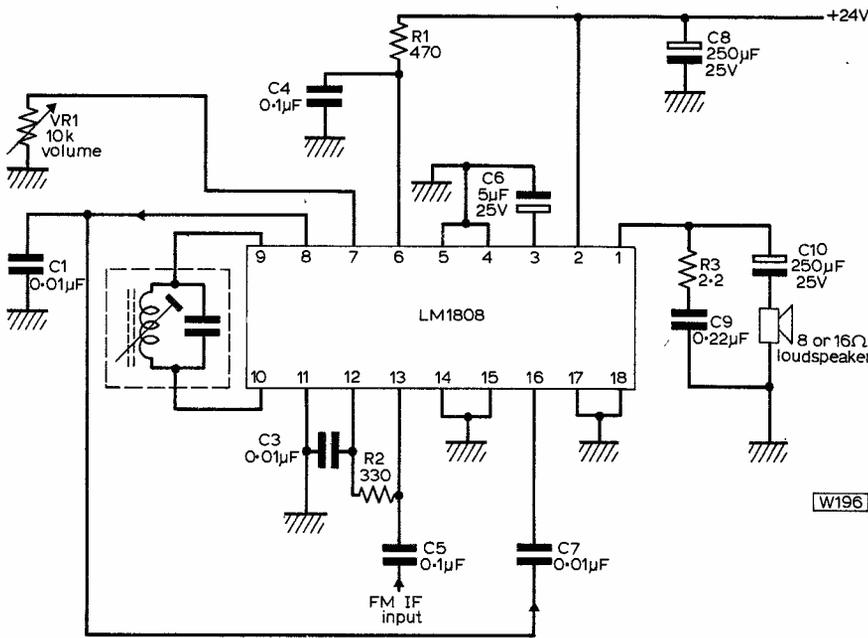


Fig. 2: Typical circuit providing IF amplifier, FM detector and audio output stage. The circuit across pins 9 and 10 is tuned to 10.7MHz. The volume control VR1 may be some distance from the associated circuitry.

The components R3 and C9 across the loudspeaker are used to prevent a 5 to 10MHz oscillation from occurring; this oscillation can appear during the negative swing into a load which takes a fairly high current if these two components are omitted. The distortion at the output is of the order of 1.2 per cent at 2W output power. The voltage gain of the output stage is fixed at 50 times (34dB); this enables the simplest possible circuits to be used.

POWER SUPPLY

The power supply voltage is connected directly to the power amplifier at pin 2; if the capacitor C8 is further than about 8cm from pin 2, an additional 0.1µF capacitor should be connected from pin 2 to earth to provide good decoupling at radio frequencies. The power supply to the IF section of the IC flows through R1 to pin 6; the internal regulator circuit in the LM1808 adjusts the pin 6 voltage to between 10.5 and 12.5V.

A 24V supply is shown in Fig. 2 (as suggested in the device data sheet), but a somewhat lower supply voltage may be used if R1 is reduced to keep the current to pin 6 to a suitable value. However, the supply voltage must be considerably greater than the maximum value of the stabilised voltage at pin 6 or the stabiliser circuit will not be able to function correctly. The absolute maximum permissible supply voltage is 30V. The current to pin 6 is 7 to 15mA, whilst the quiescent current to pin 1 is 2 to 20mA; obviously this latter current increases greatly when the device delivers power into a load.

The input to the circuit of Fig. 2 may be conveniently obtained by using a commercially manufactured front-end unit and feeding the output through a 10.7MHz ceramic filter to a Fairchild µA753 amplifier, as described in *Practical Wireless*, October 1974. The output from the µA753 can be fed directly to C5 of Fig. 2 or through a second ceramic filter to C5. However, any 10.7MHz input which is at a level greater than about 200µV may be fed to C5.

In conclusion, it may be mentioned that the writer has also used the LM1808 to amplify the signal from an ultrasonic transducer; the power amplifier in the LM1808 was used to close a large relay when the ultrasonic waves fell on the transducer. However, this is another story!

This device is now available from: D.T.V. Group Ltd., 126 Hamilton Road, West Norwood, London, S.E.27. at £1.86 inc VAT, post and packing.

PW




EQUIPMENT WANTED

- ..active filter unit Sinclair Project 60—R. W. Sheppard, 48 Grindstone Crescent, Knaphill, Woking, Surrey.
- ..a TAA960 integrated circuit (Mullard).—G. Singh, 250 St. Pauls Road, Highbury Corner, London, N.1.
- ..stereo tuner (250mV output) for use with PW (Jan/Feb 1973) 10W + 10W amplifier.—F. Southworth, 58 Sheephill Lane, New Longton, Preston, PR4 4YN.
- ..Perdio transistor receivers 'Caralux' or 'Town & Country' for spares.—W. Pearce, 32 Wathen Road, Dorking, Surrey.
- ..FL50B transmitter in good condition. All offers acknowledged.—R. J. Wallace, 26 Broadheath Drive, Chislehurst, Kent.

ISSUES FOR DISPOSAL

- ..Oct 1968, Aug 1968, May and June 1967, Jan 1968 to Mar 1969 inclusive, Television. Would like to swap for Television July and Aug 1974 and Wireless World Sept and Oct 1971.—E. T. Robins, 1 Old Kingston Road, Worcester Park, Surrey, KT4 7QH.
- ..volumes PW/TV issues (bound) to be disposed of in 1 lot. SAE for details.—N. Stevens, 48 Eversley Avenue, Barnehurst, Kent.
- ..Practical Electronics Aug 1970 to Jan 1975.—M. V. Pedersen, 19 Belgrave Street, Brighton, BN2 2NS.

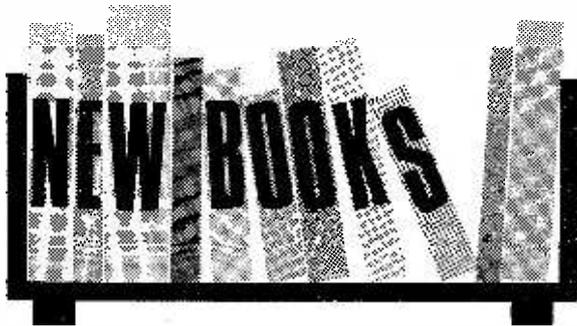

AUDIO ON WHEELS

By Vivian Capel
Published by Newnes-Butterworths,
Borough Green, Sevenoaks, Kent, TN15 8PH
199 pages 22.5cms × 14cms
Price £6

A fair amount to pay for a book of this size, but worth every penny or 'P'. Audio on Wheels covers all aspects of 'in-car entertainment', detailing how to choose and install mobile audio equipment. Basic principles of radio and tape recording are given and the book also explains how to set-up complete systems. Many types of radio, cassette and cartridge players are discussed—including of course, stereo and 4-channel systems.

The book caters for the radio engineer, motor mechanic and DIY man. For readers with little or no knowledge of audio, Part 1 outlines the basic principles of receivers and sound recording. Part 2 deals with practical applications and covers such things as: power supplies, speakers, car aerials, car radios, stereo and multi speaker systems, cassette players, cartridge players, motor control circuits, disc systems, installation, interference suppression, mobile public address, setting up a workshop and repairs and maintenance.

FOUNDATIONS OF WIRELESS AND ELECTRONICS (9th Edition)

by M. G. Scroggie
Published by Newnes Technical Books, Butterworths,
Borough Green, Sevenoaks, Kent, TN15 8PH
521 pages 21.5cms × 13.5cms
Price £3.75

SINCE this book was first published in 1936, over ¼ million copies have been sold. This new edition, like the previous ones, covers the whole basic theory starting with a sound exposition of the elementary principles needed in all branches of radio and electronics. No previous technical knowledge is assumed and the author has only used maths where he deems it absolutely essential. The first chapters are not greatly changed from previous editions but those that follow, on applications, were almost completely re-written in the 8th edition to take in more on semiconductors. In this 9th edition, more attention has been given to ICs and printed circuits and information on ceramic filters, SSB radio and photoelectric devices is included.

Without a doubt, this book is really excellent value and the following contents list gives some idea of what you get for your money: General View of a System, Electricity and Circuits, Capacitance, Inductance, Alternating Currents, Capacitance in AC Circuits, The Triode at Work, Transistor Equivalent Circuits, The Working Point, Oscillation, Radio Senders, Inductance in AC Circuits, The Tuned Circuit, Diodes, Triodes, Transmission Lines, Radiation and Aerials, Detection, Low Frequency Amplification, Selectivity and Tuning, The Superhet Receiver, HF Amplification, CRTs, TV and Radar, Electronic Waveform Generators and Switches, Computers, Power Supplies, Appendix.

ELECTRONIC COMPONENTS (A Newnes Constructors Guide)

by M. A. Colwell
Published by Butterworth & Co. (Publishers) Ltd.,
88 Kingsway, London WC2B 6AB.
104 pages 21.5cms × 13.5cms
Price £1.80

USEFUL hints that one acquires through experience of handling components are provided and the book sets out to tell the reader—in somewhat verbose terms—what components look like, what they do and where they could be employed.

PRINTED CIRCUIT ASSEMBLY (A Newnes Constructors Guide)

By M. J. Hughes & M. A. Colwell
Published by Butterworth & Co. (Publishers) Ltd.,
88 Kingsway, London WC2B 6AB.
88 pages 21.5cms × 13.5cms
Price £1.80

CHAPTERS are headed, "How and Why PCB's are Used," "Board Materials and their Characteristics", "Planning a Printed Circuit Layout", "Processing Techniques", "Component Assembly", "Manufacturing Techniques" and "Alternative Proprietary Boards".

The book guides the reader through the stages of translating circuit diagrams into PCB layouts. Image transference, etching, milling, and trimming methods are described.

TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR (3rd Revised Edition)

by Alan Douglas and S. Astley
Published by Pitman Publishing Limited,
39 Parker Street, London WC2B 5PB.
119 pages 14.5cms × 22.5cms
Price £4.25

THE construction of inexpensive compact electronic organs is now well within the capabilities of the home constructor as our readers will know. ICs are used in some of the designs in this book but readily-available transistors are employed in the majority of circuits.

A point of interest is that a design for a Leslie-type rotating curtain speaker is included—a useful design and one for which we on P.W. often have enquiries. Once again, this is an expensive book but one which will appeal to the home-constructor organ enthusiast for it contains some useful little circuits for experimentation.

ELECTRONICS AND THE PHOTOGRAPHER


by T. D. Towers, MBE, MA, B.Sc., C.Eng., MIERE
Published by Focal Press Limited,
31 Fitzroy Square, London, W.1.
316 pages 22.5cms × 14.5cms
Price £6.50

This book describes in detail the electronic content of photographic equipment. It sets out to serve all those interested in electronics or camera mechanisms. Using a minimum of technical jargon, the text sets out precisely all the areas of photography where electricity is used. Its explanation of electronic fundamentals forms the basis from which non-technical readers can approach subsequent chapters. The discussion is extended to include separate exposure meters and their calculators. In the area of lighting, the author covers the functioning of electronic flash-guns and 'computerised' flash units. Photographic processing is covered and the book describes automatic timing, darkroom equipment, print exposure and process control systems (B & W and colour). The author finishes the book by looking into the "future", and covers automatic focusing, and micro-circuit technology which can compress the works of a camera 'computer' into a pin-head sized chip of silicon.

DIGITAL FREQUENCY METER

PART 2

T. J. JOHNSON

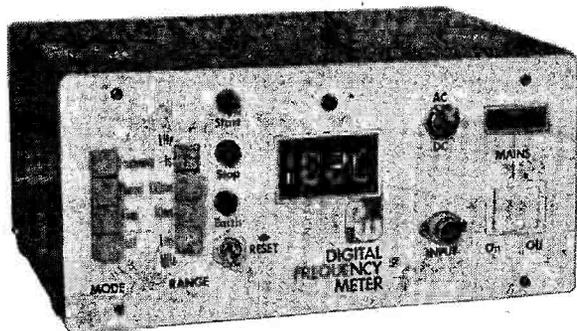


THE function of S5 is not so obvious and can be explained as follows: When S5b is in the position shown, the store pulse is allowed to pass through. When the switch is put in the opposite position, the condition presented to the inverters is logic '1', the store pulse thus effectively cut off. This means the actual condition presented to the stores is again '1'. The stores thus follow the data at their inputs. This is useful when in the time mode, since the counting may actually be seen. The second part of the switch S5a applies a logic '0' to the reset lines, thus preventing the counters from being reset, and forming a useful hold facility. The second function of the switch is to produce a low-to-high transition which is used to reset the counter

when first switched on and when in the time mode. This is achieved by placing the switch in one position and then the other, fairly rapidly.

COUNTER/STORE/DECODER/ DISPLAY

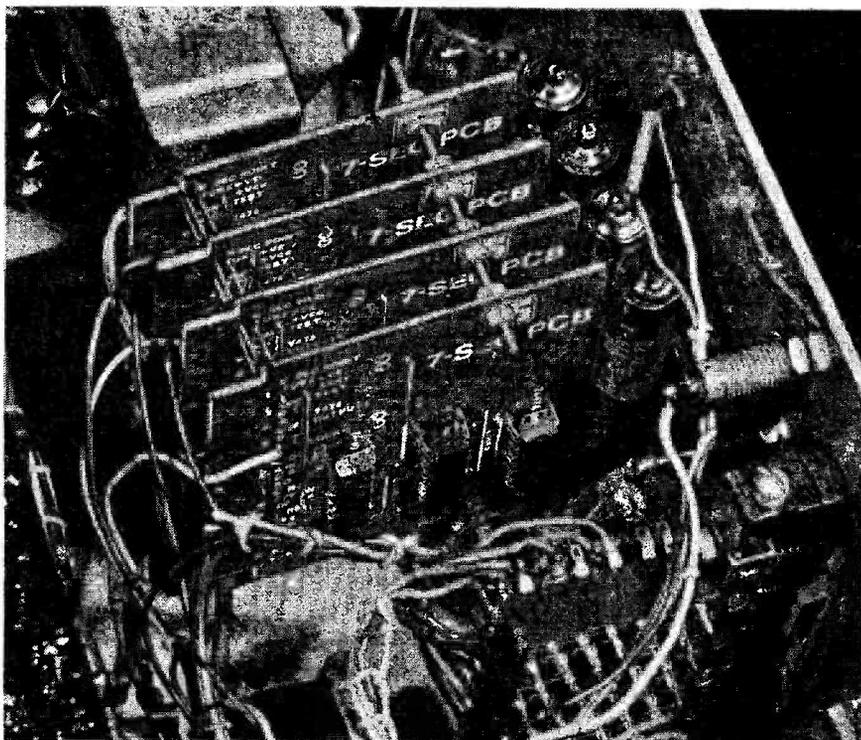The four counters IC11 to IC14, Fig. 8, receive the incoming signal from the Gate, IC10. The reset terminals of each IC are connected together and



Detailed photograph of the Doram PCB's, specifically designed for use with the 7-segment filament tubes. All boards are identical except for connections to the 'decimal point' contact on boards 3 and 4.

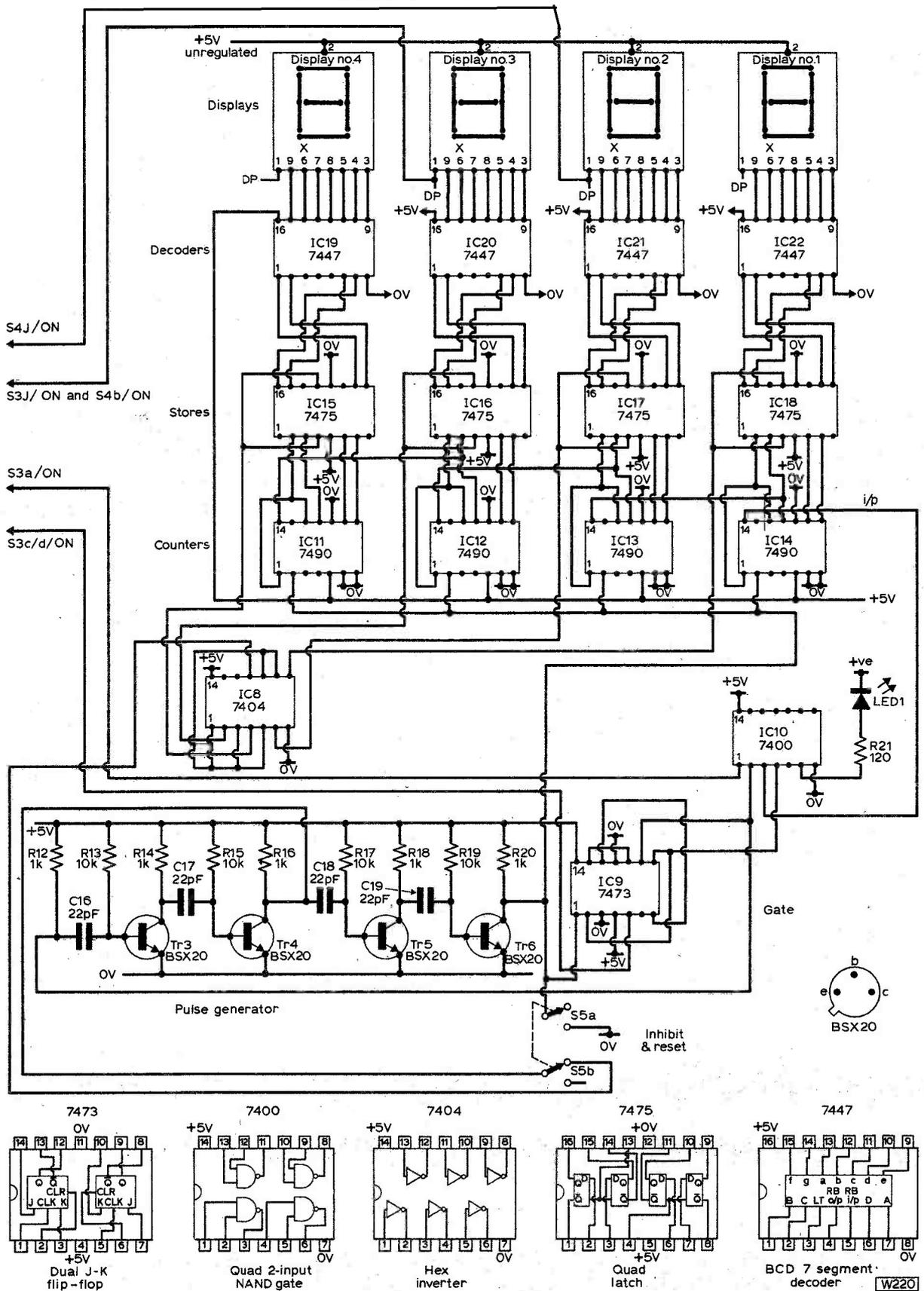


Fig. 8: Diagram of the remainder of the circuit. This should be used in conjunction with Fig. 7 part 1. IC's 11 to 22 are all housed on the filament tube PCB's.

taken to the collector of Tr6. Four four-bit latches are used as the store, these are IC's 15 to 18. The store command signal comes from Tr4 in the pulse generator, via S5b and the inverters in IC8. The inverters are required to present a pulse of correct positive going shape to enable the stores. One inverter per IC is used, so as not to load the pulse generator too greatly.

Four decoders IC19 to IC22 type 7447's are used in the present design, since the displays chosen require these types. Alternatively, the 74141 IC may be used to drive cold cathode tubes although since a vast amount of modification is required to the circuit and PCB's this was not considered a viable proposition. (There is no reason however, why the type of display could not be changed. For example LED's may be used with no change in the circuit. However, an alternative method of mounting the LED's must be found.) The displays used in this design, are the Doram 7 segment indicators. These are incandescent types, working off a supply of 5V, and are ideally suited to the present application.

CONTROL LOGIC

As was explained earlier the signal needs to be applied to the counter for a certain gate time, this is achieved by using the gate IC10. It is possible to apply the gate times direct to the gate, but unreliable operation would result. Instead the gate is controlled by a signal from FF2 IC9, this has the


advantage of isolating the signal and the gate times (this may also be referred to, as the Clock pulse).

It is obvious that if the counters are not reset after each count, the frequency being measured will add to itself each time and cause an incorrect count. There are various methods of achieving this reset condition, and luckily the counters require a positive going pulse at either of their reset terminals. One method is to use a free running multivibrator to produce such a pulse, at the same time it may be used to display the count for a certain time, thus having a certain display time. Also in this design, a complication is added with the inclusion of the 7475 stores in order to achieve a stable display.


We now have to produce two separate pulses, one to reset the counters, and the other to enable the stores. The second pulse is needed to allow data at the 'D' inputs to be transferred to the 'Q' outputs of IC15 to IC18, this is accomplished when the Clock is high (7475 operation condition). It follows then, that if the clock inputs are low then no further data can arrive at the decoders to be displayed, thus for a steady signal the numbers displayed would be the same.

PULSE GENERATOR

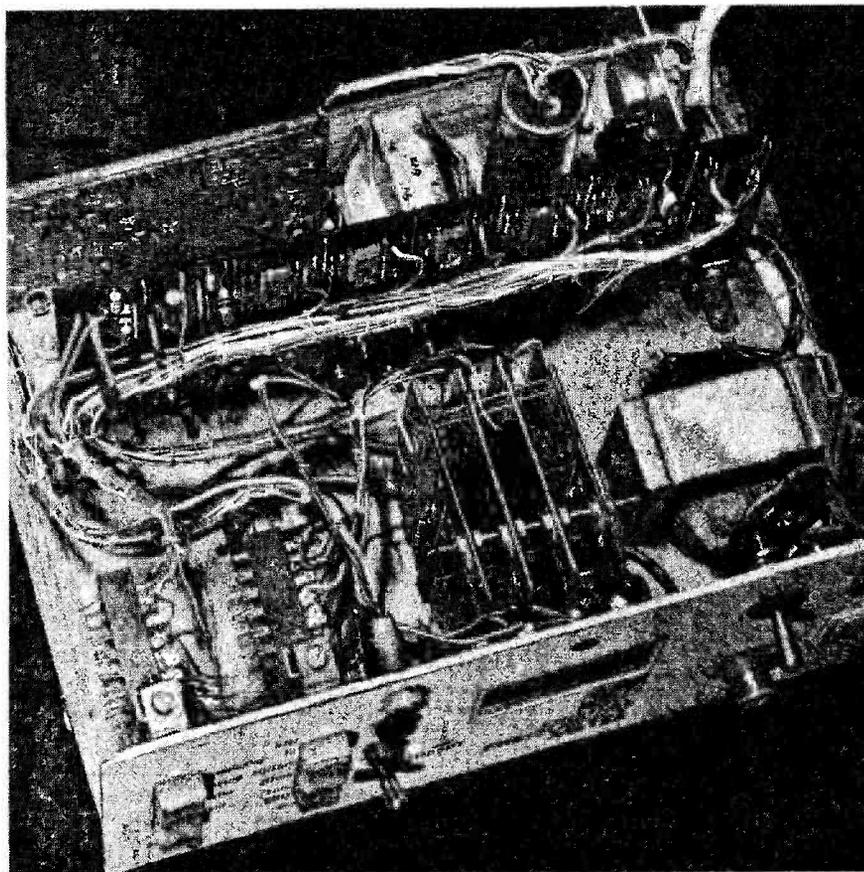
The important point to notice, is that the stores must be enabled before the counters are reset, since if the counters are reset first, the stores will pass this data to the decoders, and the resultant display would



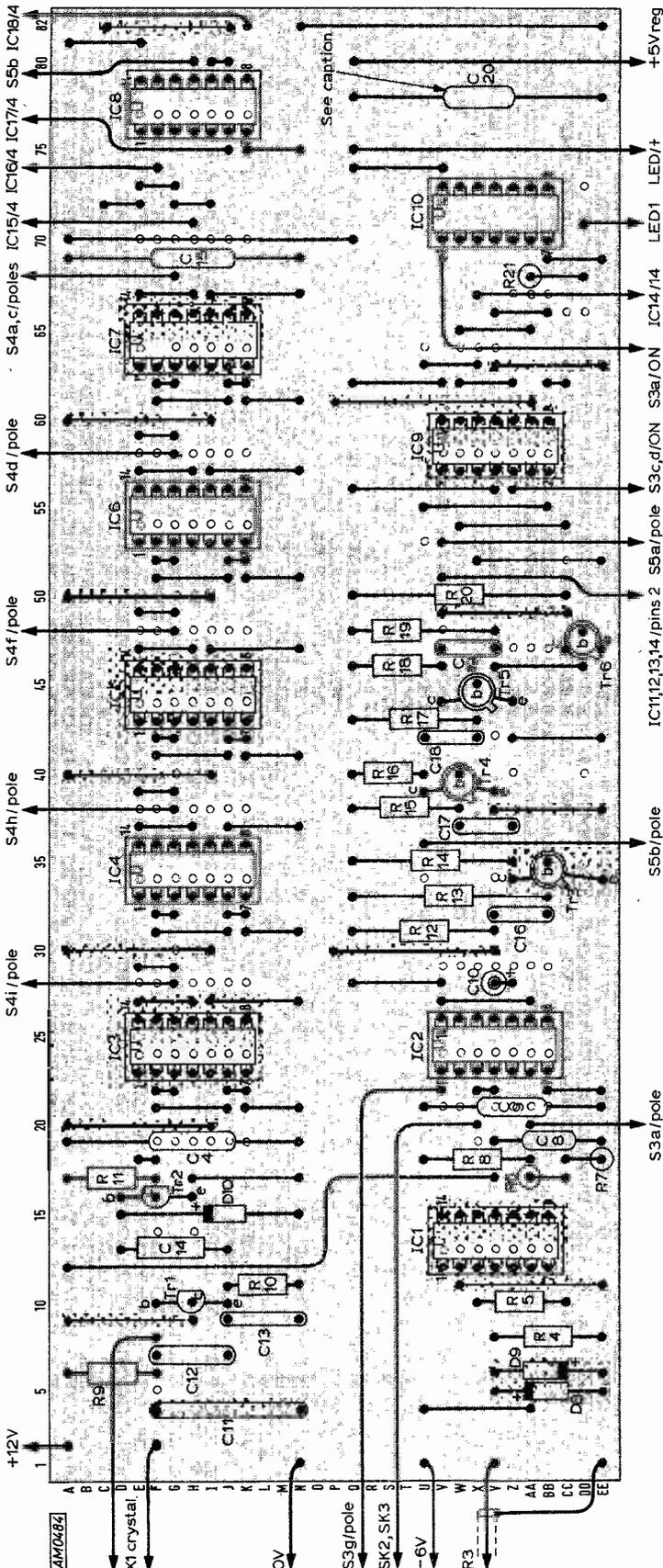Overall plan view photograph of the DFM. Note the general component layout and inter-board wiring.



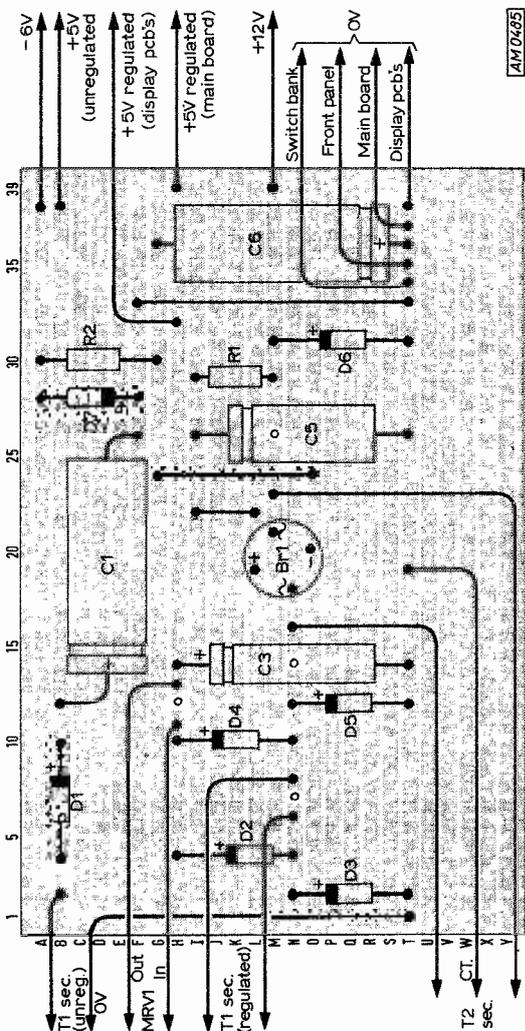▲ Fig. 11: Main veroboard shown actual size, containing IC's for crystal clock, dividers, timer, pulse generator, gate and inverter. The width of this board should be 80mm and not 95mm as printed in the component list. Additional decoupling may be required for the regulated supply at IC10, in which case connect a 10nF capacitor (C20) across the 5V supply.



▲ Fig. 12: Power supply veroboard on 0.1in matrix showing layout of rectifiers and smoothing components.

a problem, if the layouts shown in Figs. 11 and 12 are followed. Construction of the display boards are simplified by the use of ready made PCB's. The display boards should be joined together using

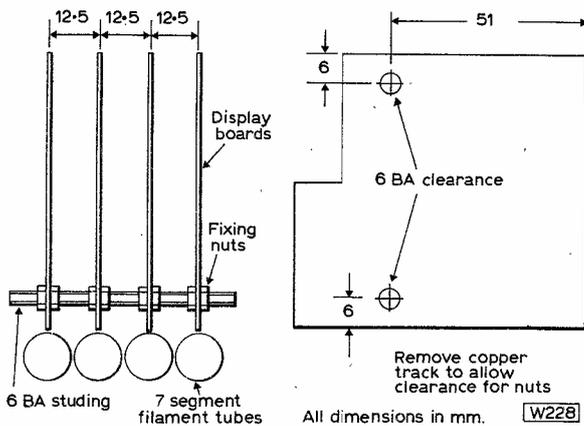


Fig. 13: Connect all four display boards together with a length of 6BA studding. Don't forget to remove any copper track that might short to the studding.

lengths of 6BA studding, as shown in Fig. 13.

The mounting bracket for the regulator and fuse holder is made from aluminium, and shown in Fig. 14.

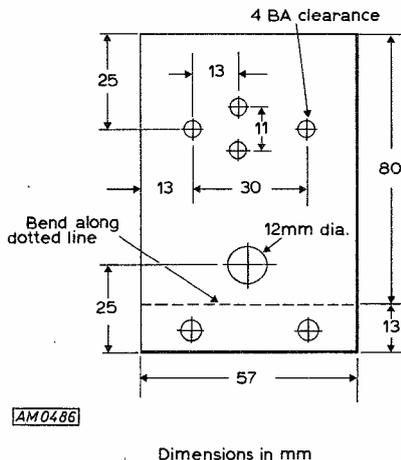


Fig. 14: Aluminium bracket for mounting the voltage regulator MVR1 and fuse holder. The fuse was omitted in Fig. 6 and should be connected between mains live and S1.

TESTING

It is preferable that the power supply be tested first, since the remaining circuits require to be set up using the power supply. Testing of the power supply should present no problems, since all that is required, is to ensure the correct voltages are obtained.

The display boards should be tested in turn by connecting each to the power supply, and connecting the reset line to 0V. The store line shouldn't be connected, and a 1Hz square wave of approx 5V should be applied to the input. The display should advance one digit per second. This should be done

to each display, any faults being cleared before construction commences.

It may at this point be worth trying to find the board with the highest operating frequency, and using this in the first position. This may be done by applying a continually higher frequency to all the boards (all the boards must be connected in series) and noting when the display ceases. Using this method the fastest display board can be used thus extending the operating frequency of the counter. This is because the first board must operate at the maximum frequency of 30MHz. Thus the first board divides by 10 presenting a frequency of 3MHz to the second, well within the capability of the IC's.

The input stage is the next to be tested and involves applying a variety of frequencies and amplitudes to ensure that IC1 converts the waveform into a good square wave. The effectiveness of the input protection may also be tested, but be careful!

The crystal clock and dividers can now be tested, it is advisable to check each divider IC before inserting it into the circuit since a 'dud' can upset the entire clock generator. It will be noticed that no adjustment is provided for the crystal oscillator, since the crystal itself is very accurate. The timer control is tested to ensure that only a single pulse is generated when the input is earthed. It is recommended that a micro-switch be used to eliminate the contact bounce associated with normal press type switches. The remainder of the circuit, ie the control logic can only be tested when the other units are fully connected.

After construction is completed a final check should be made in the case of any shorts etc, and power applied. If all is well, the instrument can then be tested to ensure correct operation, after which the counter is ready for use.

FAULT FINDING

With a complicated circuit such as this, the possibility of a 'dud' IC is not uncommon, it is therefore important that the IC be eliminated as faulty, as far as possible. The removal of an IC from a circuit board, can, more often than not, cause other damage. The use of IC sockets can eliminate this, but due to the expense, were not used in the prototype.

KINDLY NOTE!

Rhythm Generator, June 1976

It has been brought to our attention that pins one and two of IC5 (PCB3, Fig. 11) were connected together. This is incorrect, pin one should be bent clear and not soldered.

stray signals

by **POINT CONTACT**

A fit of nostalgia was sparked off by a find whilst browsing through secondhand books one Sunday afternoon in a market town in rural Hampshire. Rural Hampshire being peopled by honest folk, there are racks of books outside the shop under a covered forecourt, even a notice saying "OAP's Take One Free". There I came across a copy, in excellent condition, of "A Manual of Modern Radio", by J. Scott-Taggart. As Point Contact is not yet quite old enough to benefit from that notice, I duly put the price marked inside the front cover—30p—through the slot by the door and that evening walked through the covers of the book into a long-lost Arcadia, full of differential reaction condensers (reduces the effect of hand capacity), basket weave coils and of course egg-shaped insulators.

But don't get the idea that Point Contact is a boring old man who lives entirely in the past. As a practising chartered engineer I am also involved with the latest techniques of information transmission, both line and wireless (sorry, radio!). And like any good engineer, I like to know what is going on in other fields of engineering. Some of the developments are fascinating—take Optical Computing, for instance, I had always assumed that if a photograph was taken out of

focus, the fine detail was irretrievably lost; certainly putting the negative in the enlarger equally out of focus in the other direction won't help! Nevertheless, the way the blurring on the negative takes place is uniquely determined by the lens and the degree of out-of-focus. Imagine the blurred negative from an out of focus picture of a point of light on a black background. If we could process the information on the negative through a system with a transfer function equivalent to the inverse of the "point spreading function" of the out of focus lens, the negative could be made to yield a print showing the original point.

Exactly this has in fact been done, using holographic techniques, for real photographs full of detail. A minor snag is that certain "spatial frequencies" (number of lines-per-mm on the negative) depending on the original lens and degree of out of focus are missing from the "sharpened" picture. On normal subjects this is not noticeable any more than a narrow bandstop filter causing a 'hole' in the audio spectrum, on ordinary programme material like a full orchestra. There are numerous other applications of the technique, which is called "optical computing" because the holographic system is in fact processing vast amounts of information in parallel in real time.

Of course, not everyone is interested in science and technology; take Mrs. Point Contact for example—although I was surprised to find that even she can (usually) tell the difference between a resistor and a capacitor. And the little Point Contacts don't really show any interest in electronics at all, perhaps because they have been threatened with dire consequences if they grunch anything in my "laboratory". I am fortunate enough to have a corner of the spare bedroom for my work bench; well,



Clearing up when we have visitors.

most of the spare room, actually, so a certain amount of clearing up is called for when we have visitors. How much depends on the visitor.

In the 20's, for most people, components were very expensive, but ready-made sets just prohibitive. Later on, as volume production of all-mains sets got under way, prices came down considerably and just before the war I bought a Cossor 365 Superheterodyne Receiver for the princely sum of £7.19.6. Of course, in real terms, that was equivalent to the present day price of a good television set, and as a receiver it had a remarkably good performance. "Excellent bass radiation and good crisp treble" was the verdict of the Wireless & Electrical Trader. In practice this meant 6dB per octave top cut from about middle C upwards, aided beyond a Kc or two by heavy RF filtering at the detector and 'High Q' IF transformers. Nevertheless, it did have a tuned RF stage and Long, Medium and Short Wavebands and with a long aerial and a following wind would pick up plenty of American and the odd Australian station. Years later, when servicing it, I found out the hard way that whilst the top cap of the RF pentode was grid 1, that on the pentode in the IF stage was anode!



Threatened with dire consequences.



EDITORIAL ANNOUNCEMENT

NEW!

PRACTICAL WIRELESS

PCB SERVICE FOR READERS

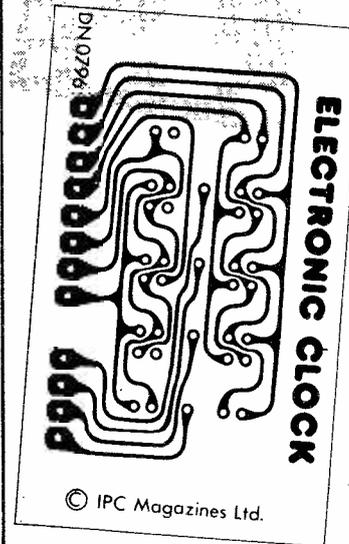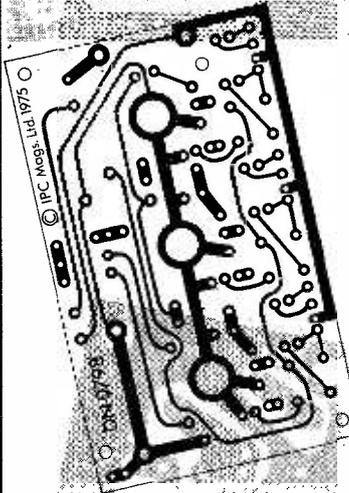All boards, except SRBP, are glassfibre, drilled and roller-tinned



To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es

Issue	Project	Ref	Price P/P		
Mar 75	Electronic Organ (set of two)	AM0315 AM0318	7.56 + 25	<input type="checkbox"/>	
Sep 75	Electronic Clock (set of three)	DN0795 DN0796 DN0797		2.40 + 15	<input type="checkbox"/>
Dec 75	Radio-Pickup Link	DN0792	0.98 + 12		<input type="checkbox"/>
Dec 75	Random Number Selector	DN0793A	0.98 + 12		<input type="checkbox"/>
Dec 75	Sound-To-Light Display	DN0798	1.15 + 12	<input type="checkbox"/>	
Dec 75	12V PA System	DN2/JM	0.98 + 12	<input type="checkbox"/>	
Dec 75	Disco System, Amplifier (2 required)	each AM0421	3.40 + 18	<input type="checkbox"/>	
Dec 75	Disco System, Light Modulator	AM0423	2.70 + 18	<input type="checkbox"/>	
Jan 76	Music Box	SRBP DN1/JM	2.25 + 18	<input type="checkbox"/>	
		glassfibre DN1/JM	3.00 + 18	<input type="checkbox"/>	
Jan 76	Emergency Light Unit	AM0419	3.50 + 18	<input type="checkbox"/>	
Mar 76	CMOS Crystal Calibrator	AM0438	1.19 + 12	<input type="checkbox"/>	
Apr 76	DF Receiver (set of two)	DN4/JM DN5/JM	1.92 + 15	<input type="checkbox"/>	
Apr 76	Wobulator	AM0443		1.08 + 12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33 + 15	<input type="checkbox"/>	
Jul 76	Transistor Tester	A002	2.08 + 15	<input type="checkbox"/>	
Jul 76	Disco Preamplifier	A003	0.65 + 12	<input type="checkbox"/>	

Post and packing is for one board or set of boards. Prices include VAT
Remittances with overseas orders must be sufficient to cover despatch
by sea or air mail as required. ACCESS welcome. Send card number only.

I enclose Postal Order/Cheque No..... for £..... made payable to READERS PCB SERVICES LTD.

NAME.....

ADDRESS

..... Post Code

Any correspondence concerning this service must be addressed to READERS PCB SERVICES and not to the Editorial offices.

barclay

ELECTRONICS

TECHNOLOGICAL
PRECISION PRODUCTS

DECIMO

VATMAN—SCIENTIFIC

Large green display, 8-digits, 2 exponents, 4 trig log functions 10⁻⁹⁹.

Radian degrees. Exchange, Memory, π , Reciprocal, X² etc. Single Function keyboard. 20 hr battery life. **£25.50**



MINI-VATMAN—Similar to above but slimmer. Green display 8-digits. % key. **£8.84**

MINI-VATMAN M—As above but with % and full-function memory. **£10.70**

VATMAN—8 digit. % key. Green display. **£8.84**



SUPER-VATMAN—Similar to above but with full-function memory, X² Reciprocal, π , $\sqrt{\quad}$. **£11.58**

SINCLAIR

NEW SCIENTIFIC

Only 1" x 2" x 1/4". Yet has 8-digits or 5 + 2 exponents. Using the NEW chip, it has full algebraic logic and many more functions. Algebraic logic is constant on all four arithmetic functions.

FUNCTIONS:
C & CE key ● sin ● cos ● tan ● arcsin ● arccos and tan ● reciprocal ● E to the X ● natural log ● antilog ● memory+ ● memory- ● memory exchange ● memory cancel ● EE exponent ● change notation ● PLUS a degree radian switch. **ONLY £13.58**

OXFORD 300—Larger version of above. **£16.25**

CAMBRIDGE—**£7.45**

CAMBRIDGE MEMORY—**£9.99**

OXFORD 150—**£8.32**



CBM

4148R—10-digits, 2 exponents. Full log and trig functions. X², Reciprocal, π , X root of Y, Polar rect-angular co-ordinates. 2-store memory. Rechargeable. Mean and Standard deviation. **(R) £30.22**

Including recharger.

4190R—10 digit, 2 exp. 90 pre prog. scientific, statistical and metric conversions. **(R) £41.61**

SR1800—Similar to the 4148R. Green display. Battery operated. **£22.68**


796D—8-digits, % and store. **£6.27**

997R—Rechargeable % and full memory. **(R) £11.58**

Including recharger.

7919D—Full trig and logs, 8-digit or 5 + 2 exponents. Reciprocal, π , $\sqrt{\quad}$ memory. **£12.88**

ADD 8% VAT TO ALL PRICES + 55p p&p

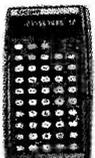


ROCKWELL

63R

8-digit, 2 exponent. 10⁹⁹ Memory. 2-level parenthesis. All trig and log functions. Degree radian. Factorial. Reciprocal. π , $\sqrt{\quad}$ etc. Rechargeable. **(R) £23.95**

Including recharger.

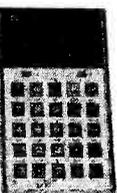

61R—Green display. 8-digits. All trig and log functions. **£20.42**

44RD. 9-digits or 5 digit & 2 Exp. Green display. Store. Otherwise similar to 63R less factorial. **£17.55**

64RD. 12-digit or 8-digit + 2 Exp. Additional to 44RD. Polar Rec co-ordinates. Degree Rad or Grad. **£22.20**

8R—Special purchase. 8-digits. % key. Only **£8.11**

20R—Special purchase. 8-digits. % key. Full-function memory. **£10.15**

24RD—Green display. 8-digit. **£12.75**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. $\sqrt{\quad}$. Click-buttons. Rechargeable. Including recharger **(R) £20.35**

NOVUS

4320—8-digit, 2 exponent. 10⁻⁹⁹ RPN Logic. Full trig and log functions. 4 Roll stack. Memory. Memory exchange. $\sqrt{\quad}$. Rechargeable. **(R) £21.20**

Including recharger

4325—Rechargeable. Programmable version of 4320. **(R) £42.50**

Including recharger

4510—8-digits, 3 level stack. All trig and log functions. $\sqrt{\quad}$, π . Reciprocal. Memory etc. **£13.80**

4515—100-step programmable version. **(R) £35.10**

6020—Financier. **£16.65**

6025—Rechargeable. Financier 100-step programmable. **(R) £42.50**

Including recharger

6030—Statistician. **£16.50**

6035—100-step programmable Statistician. Rechargeable. **(R) £42.50**

Including recharger



TEXAS

SR50A—10-digit, 2 exponent. Rechargeable. All trig and log functions. Hyperbolic. X to the root of Y. Radian and degree. Factorial. Memory etc. **(R) £31.75**

Including recharger

SR51A—As above but with 3 independent memories. Linear regression. Mean. Variance. Standard deviation. Permutation. Random number generation + 20 basic conversions and their inverse. Rechargeable. **(R) £46.26**

Including recharger

NEW SR52. Card Programmable. 20 Memories, 224 Prog Steps **£231.48**

PLUS FREE Manual on any one of the following: 1. Statistics. 2. Electrical Engineering. 3. Mathematics. 4. Finance.

NEW SR55 100 step prog. 10 digit, 2 Exp. 10 Inde. memories all log, trig & statistical functions. **(R) £74.25**

T1200—8-digit. % key. **£8.29**



Digital Wrist Watches

T'EXELAR



WITH STRAP Inc. batteries. 3 Functions. Shows hours mins. & secs. Single button operation. Limited supplies at this low, low price. **ONLY £13.75. Gold finish £14.75**

THE SUPERB 10-FUNCTION PULSTRONIC



Shows date and month in correct order! Single button control. Display visible in pitch dark. Hrs, Mins, Secs. Date + Month in Letters, Day of Week in Letters. Self-adjusting calendar. Auto hold and fade-out. A.M. setting indicator. P.M. setting indicator. Undoubtedly one of the most sophisticated watches available at this unbeatable price! Styled in finest solid Stainless-steel satin finished with polished bevelled edges. Complete with adjustable matching stainless-steel bracelet AND a FREE presentation box. **LIMITED SUPPLIES AT Inc. batteries, ONLY £34.62**

DECIMO DIGITAL CLOCK/RADIO

£32.95 OUR PRICE Incl. VAT plus £1 p&p

LARGE DIGITAL READOUT



This is the most unique clock/radio in the country today having a soft 1 1/2" high orange-glow digital readout which is completely silent and non-pulsating. In a beautiful teak style cabinet with up-to-date VHF/MW radio. You can awake to soft music or alarm—and if you want up to 10 minutes more—just press the 'Drowse' button. Automatic 80 minute 'sleep' button in case you drop off while the radio's on.

ORDER FORM

PHONE CALLS AND PERSONAL CALLERS WELCOME MONS to THURS BETWEEN 2 & 5 p.m. 01-458 4755. SUNDAYS 10 a.m. to 1 p.m. To: BARCLAY ELECTRONICS Dept. 7PW, 1115 FINCHLEY ROAD, TEMPLE FORTUNE, LONDON N.W.11

Please send me.....
with/without optional mains adaptor. I enclose cheque/money order total value £.....including 55p to cover P&P
NAME.....
ADDRESS.....

barclay
ELECTRONICS

DESIGNED BY TEXAS



**Texan Amplifier
as featured by
PRACTICAL WIRELESS
SOLE U.K. DISTRIBUTORS - HENRY'S**

Build it yourself for only

£32 KIT PRICE INC. VAT + £1.00 p&p.
Build and tested £42.00 inc. VAT + £1.00 p&p.

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

Look at the Texas specification

Incorporating fully integrated stereo preamp and power amp. with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardener's low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall. 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

★ Can be built Stage by stage
★ Ask for leaflet 5.
★ Everything necessary supplied.
★ Full after sales service and guarantees.

TEXAN FM TUNER KIT **£23.50**
inc. VAT + 50p p&p

Build and tested £28.50 inc. VAT + 50p p&p.
Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

THE NATURAL FOLLOW-ON

**Henry's latest
ELECTRONICS
CATALOGUE**

- * over 5000 items - many new
- * free 50p voucher inside every copy
- * virtually everything needed by amateurs and professionals

- * over 200 pages
- * easy-to-use, complete alphabetical index
- * section index
- * everything at competitive prices

ONLY **50p**

FREE to Educational Establishments when ordered on official headed notepaper

+ 20p carr./pack.

TRANSISTOR & VALVE DISCOUNT PRICE LIST
over 2000 types
SEND FOR YOUR FREE COPY

All mail to: **Henry's Radio**
303 Edgware Rd, London W2

LONDON W2: 404/6 Edgware Road. Tel: 01-402 8381

LONDON W1: 231 Tottenham Ct Rd. (lower floor) Tel: 01-636 6681

* NOTTINGHAM: 94/96 Upper Parliament St. Tel: (0602) 40403

* READING, BERKS: 130/131 Friar Street. Tel: (0734) 583230

* HARROW: 190/4 Station Road. Tel: 01-863 7788

* CROYDON: 110 North End. Tel: 01-681 3310

* **NEW STORES**

Please Note: Mail Order Customers
HENRY'S WILL CREDIT ANY
VAT DOWN VAT OVERPAYMENTS

TRANSFORMERS

MAINS SAFETY ISOLATING Primary 240V. Sec. 120V or 240V.
Please state which type you require.
All types are screened and Centre tapped to earth.

V.A. (watts)	OPEN TYPE £	P. & P. p	CASED TYPE £	SOCKETS 5 amp / 15 amp	CARRIAGE	PLUGS FOR CASED TYPE complete set
50	3-98	62				
100	4-53	70				
200	7-26	80				
250	8-80	1-10				
350	10-59	1-18				
500	12-18	1-34	23-25	1	—	O.A. 1-20
750	19-85	O.A.	30-80	1	—	O.A. 1-20
1000	26-00	O.A.	37-77	2	—	O.A. 2-40
1500	29-65	O.A.	44-30	3	—	O.A. 3-60
2000	35-00	O.A.	51-85	1	1	O.A. 2-70
3000	55-00	O.A.	75-35	1	1	O.A. 5-10

CASED TYPES These are of extremely high quality to British Standard Specification, with resettable fused primary winding, and are fitted with covered outlet sockets. Housed in steel cases with carrying handles and 3ft of 3 core cable.

12V or 24V Primary 240V Please state which voltage				MINIATURE TRANSFORMERS Primary voltage 240V			
AMPS	PRICE	P & P	Sec. volts	mA	PRICE	P & P	P & P
12V	24V	£	p	3-0-3	200	1-37	25
1	5	1-30	26	0-6 x 2	1A	1-80	45
2	1	1-58	45	0-9 x 2	330	1-34	26
4	2	2-05	45	0-9 x 2	500	1-83	45
6	3	3-76	62	0-9 x 2	1A	2-60	52
8	4	4-30	85	0-15 x 2	200	1-30	25
10	5	4-67	95	0-20 x 2	300	1-72	52
12	6	4-93	98	0-20 x 2	1A	3-08	72
16	8	6-35	1-20	0-15-27 x 2	1A	3-86	72
20	10	9-27	1-20				

QUANTITY DISCOUNTS
1 to 24 off Basic Price
25 to 49 off 2 1/2% off Price
50 to 99 off 5% off Price
100 to 249 off 10% off Price
250 to 499 off 15% off
500 to 999 off 20% off
1,000 to 1,999 off 25% off
2,000 and over 30% off

We manufacture Power Transformers to customers own special requirements, please send details of any Transformer you may require custom built. All queries must be accompanied by S.A.E.

PLEASE ADD 8% V.A.T. TO TOTAL PRICE

S. G. Wright's Ltd., Bishop House Works, Rylands St., BURNLEY, Lancs. BB10 1RG Tel. 26934

CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT
ALL PRICES INCLUDE P&P AND V.A.T.

ANTEX SOLDERING IRONS (with slide on & off bits)			WIRE STRIPPER & CUTTER £0.85
15W 'C' miniature irons	£2.70		HAND DRILLS Leytout precision, compact, 5/16" chuck £3.99
3/32" 1/8" 3/16" bits—each	£0.45		AERIALS Extend 15-120cm £1.50
'C' Elements	£1.30		CASSETTE 'Head Demagnetisers' Shaped pole—saves time £3.65
18W 'G' miniature irons	£3.15		EARPHONES Stethoscope £1.25
3/32" 1/8" 3/16" bits—each	£0.45		Crystal earphone, lead & plug £0.65
'G' Elements	£1.65		Headphone, 2,000 Ω £3.20
15W 'CCN' Low leakage irons	£3.15		INTERCOMS 2-station £6.35
3/32" 1/8" 3/16" bits—each	£0.45		MICROPHONES Dynamic £2.15
'CCN' Elements	£1.65		PRINTED CIRCUIT KITS - All items for producing p.c.'s £3.99
25W 'X25' Low leakage irons	£2.70		SIGNAL INJECTOR - Audio through video signals, self contained £4.25
3/32" 1/8" 3/16" bits—each	£0.47		STEREO HEADPHONES 8Ω £4.65
'X25' Elements	£1.45		SPEAKERS - 75mm dia. 8Ω £1.00
'SK1'; 'SK2' Soldering Kits	£4.50		
ST3 Stands—for all models	£1.40		
SOLDER in Bib dispenser	£0.45		

DIGITAL CLOCK KITS
using N.S.C. Module 12/24 hr. £14-70
12/24 hr. Alarm £15-70

STEREO HEADPHONES:—8 OHMS
with Stereo/Mono switch £10-35
without switch £8-25

TELEPHONE AMPLIFIER:— £10-95

STEREO 4 CHANNEL MIXER:— £12-25
2 L.H. Channel 2 R.H. Channel

REGULATED POWER SUPPLY:— £18-25
O/P 6, 7, 5, 9, 12, Volts D.C. Max. 1 amp

PRINTED CIRCUIT KIT:— £2-65
Contains everything to produce printed circuits

RESISTORS:—
1/2 watt 5% 1p each, 555 Timer—38p; BC 107/8/9—9p. each

C.W.O. VAT included 25p P & P. Send 20p for lists or enquiries.

CLEVELAND SUPPLIES (PW)
P.O. BOX 20, REDCAR, CLEVELAND.



AMATEUR BANDS

by Eric Dowdeswell G4AR

I HAVE had an interesting letter from **J. Watson** of Bolton in which he says he has written to the RSGB to propose that they run a course for beginners, in **Radiocommunication**, which would complement the **Guide to Amateur Radio** and the **Radio Amateur's Examination Manual**. Personally speaking I would have thought that the **Guide** would have been enough but, as **JW** says, once into ones fifties and things get a bit more difficult! **JW** would like to learn just enough to pass the **RAE** but in the event one could hardly avoid learning quite a lot more. Not much point in just acquiring a lot of isolated facts even though that could be enough to pass the examination which, in all conscience, could hardly be simpler! **JW** did try a night school class at a technical college but found the hour or so a week a waste of time and very protracted. Unfortunately, **JW** still awaits a reply to his suggestion, written on March 4th.

Paul Turner (Bishops Stortford) found 15m a good and improving band during the month, as did several other correspondents. Only to be expected with the summer coming on, I suppose. Paul's main problem is the seemingly eternal **QRM** from the timebases of local colour TV sets but with the rise in the usable frequencies as we get further into the year this trouble ought to tend to diminish, being worse on the **LF** bands. Paul also noted an improvement in the 20m band especially in the afternoons when central and south African stations were prominent.

Steve Cottis G15294/A8961 (Harrogate) queried a station signing /P/4U which would appear to be an amateur with one of the **UN** forces, such as those on the **Golan Heights**, although the **4U** prefix is generally used by stations in Geneva, under the aegis of the **ITU**. Steve also noted **4J6A** operating in a contest which turned out to be a **UG6** station! To forestall any enquiries Steve's "call" G15294 is an identification issued on joining the **International Short Wave League**. I am glad to know that Steve has now made an audio oscillator so as to get on with the task of learning Morse. Don't try to do it all by yourself Steve, try and find an experienced op to assist or you will get into some bad habits!

Neil Whiteside (Hitchin) sent in a brief log for 20m but has in fact been mainly listening on the 2m

band but reports that nothing has happened there recently to be worthy of mention. On 70cms Neil has a Microwave Modules converter fed from two 6-element yagis with matching harness. He is looking forward to the operation of the 70cms Bedford repeater **GB3BD** which has been carrying out **QRP** tests apparently. **Paul Flatman** (Ipswich) decided to fix his **HRO** after all and as he says "when it is working properly it is really pulling them in" on an "old bit of bent wire" as he puts it. Paul is another to comment on the up and coming 15m band. On 40m he caught **YV40W/P/7** on **SSB**. Could this be a new country in the offing? **QTH** said to be **Margarita Island**.

Another **Paul**, of the **Barker** clan (Sunderland) always sends in two log sheets, one for **SSB** and the other for **SSTV** in which mode he got **PY4AP** for a new country. Paul is wondering if an article on **SSTV** would be of interest in the magazine. I think it would so he is being duly encouraged by me! I am sure a lot of people would take up **SSTV** if they could only get some practical advice to put them on the right track. As well as studying for the **RAE** **Robin Bayley** (Nr. Wolverhampton) has managed to complete a converter for 2m and to put in some listening time in the **HF** bands with his ex-**RAF** **R1475** and long wire aerial.

L. Thompson (Reading) mentions the very much improved results obtained when his 350ft long wire at 35ft up had to be bent back to form a vee when the old elm at the far end had to come down. "Could this be some sort of beam"? he asks. It is, more or less, but if he feeds it with open feeder at the apex and uses an **ATU** he will have a very effective beam indeed and usable on all the **HF** bands. Seems it has around 200ft per side now. I know a lot of licensed chaps who'd be glad to get that sort of aerial up in their gardens!

Alan Doherty (Portrush, Co. Antrim) didn't find the bands particularly good and apologises for the poor log covering 20, 40 and 80m **SSB**. Don't know if his move to the spare bedroom, out of everybody's way, has got anything to do with it! Still has his **PR40/FR400SDX** set-up and 120ft of wire. Being only 100 yards from the sea he bemoans the fate of some of his aerials due to the Atlantic gales, but adds "I wouldn't change it for the world". He also comments on the lack of activity by yours truly on the bands. My head is duly bowed in shame! However I do have a rig which I am endeavouring to get on to the 80m band as soon as possible. It was a commercial rig with four switched crystal channels but by the time I have finished with it it ought to qualify for the appellation "home-brew"!

Stan Hunt (Wigan) **BRS36555** finally dragged himself away from his studies to write to us for the first time. Thank you Stan but don't let amateur



radio deter you until you have passed everything you have to pass. There will be plenty of time later. He has a Trio 9R59DS with a dipole for 40m which is also very effective on 15m. This is in the loft but he hopes to get a 14AVQ vertical up on a pole in the garden very shortly. Stan surprised me by asking how he can send cards through the Bureau. Presuming you mean the RSGB Bureau, Stan. I should have thought you would have been supplied with all the relevant info on this when you "joined up"! Briefly, all outgoing cards are sent to Arthur Milne G2MI, long time manager of the Society's QSL Bureau but incoming cards are received by means of SAE's, from your own Sub-Manager whose QTH you can find by reading Rad-Com or contacting RSGB HQ.

From **Bernard Hughes** in Worcester comes a nice log courtesy of his FR500SDX plus 20m dipole and 66ft of wire on other bands. Having a few days off work he took the chance to look at 20m in the afternoons and was pleasantly surprised to find plenty of VK's coming through. **Martin Chapple** (Leamington Spa) A9090 gets best results on all bands when he connects half his 20m dipole with his 100ft wire. If you look at the total length of all the wire in use OM you will probably find a multiple of 66ft somewhere! Like 132ft?. A half wave on 80m and excellent on all the higher frequency bands. Martin also queries the lack of G4AR on the air but I hope my notes above will explain all.

M. P. Bennett BRS 36644 just sent a log but, looking at the excellence of the entries, obviously had no time to write a letter! Back to **Steve Cottis** who was very impressed with the course on short wave propagation obtainable from Radio Nederland, PO Box 222, Hilversum, Holland, free of charge. Meant for the broadcast band boys but very useful still when they advance to the amateur bands! 9K2DT was so pleased with his report from Steve that he not only returned the IRC's but put seven stamps on the envelope including a set of five featuring birds. Feathered ones, naturally, which incidentally, is my second hobby when I have the

time! Wonder if 9K2DT should read 9J2DT?

Phew! Who said everyone is on holiday now and that I wouldn't get any reports! Seem to be more than ever! Following on from my remarks on **Tim Charles** A8927 last month he was kind enough to telephone me to say he is now G4EZA and, as we both remarked together, that's not too bad on CW! Tim was one of the few who regularly sent in logs of stations heard on CW, and now he's lost to us, boo-hoo! SOS—will **Paul Cowburn** who wrote me a long letter please let me have his QTH? I have an envelope here with an answer and some goodies but no address to which to send it. Unfortunately I can't find a previous letter from you, Paul.

Log extracts

P. Turner:— 15m ZS6U 9G1JX CX5BF 2m ON5UN PA0YZ (via aurora)

S. Cottis:— 80m A2CJP CT3AB JH0BQU VP2KF YB0ABV ZB2CJ 20m CR9AJ JR1UHM (Guam Is) KG6JBX HL9TX TU2GA VS6DO VR8A 7P8AC 15m CT3BK JA4JUJ UK0AAC

N. Whiteside:— 20m CP5DT HP1XMU KV4AB VP5MA

P. Flatman:— 40m YV4OW/P/7 20m HR3JRR VQ9DF (Mahé Is) YB0ABV ZS4BP 5N2NAS 9V1NR 15m EL2FW JA3MPT PZ9AB VS6DO ZD8RD ZP5WU

P. Barker:— SSTV 20m CT1JI HA5KFZ I0FZW K4QPR OE1HNW PY4AP 9K2DO 20m AD7ZJD/AG6 (Guam Is) CT7BC KG6JBX TJ1AF

R. Bayley:— 80m FP8DH 40m EA6DA VP8AA 20m A2CGO KH6PP

A. Doherty:— 80m PY7HS ZE6JL 40m 5T5AR 6W8DY 20m AL7CSX(KL7) FG0GE TG9HW VP2LCG YJ8DE

S. Hunt:— 80m ZB2CJ 20m FG7AN HR6SWA (Swan Is) VE8NS 8P6CG 15m 5T5ZR 9J2GJ

B. Hughes:— 20m DU1DBT KG6JBX TJ1AF YB0ACG 3D6BD 5R8BL 9M6MA

M. Chapple:— 80m EA8CR ZL3FA 40m VK2AVA 20m VP8HZ 9X5SP

M. Bennett:— 80m AP2AD 20m A35AM (JA1XFB) HM2JM KG6AA TR8JCV VK2PA/LH (Lord Howe Is) 8R7X 15m FY0PHI TI2WX

P. Cowburn:— 80m HK0COP KZ5HP ZL1JC 3B4AJ 40m CE3BGL VK5PV 20m HI8AB KV4IJ VP2KF 5N2NAS



SHORT WAVE BROADCASTS

by **Derek Bell**

OR what to do with an egg insulator! **John Curtis** of Beaminster in Dorset, after reading the recent comments in this column on the problems of securing aerials to trees, passes along a tip first used by him in the '20s. This involves fastening a length of stout rope to the tree sufficient to clear the tree branches, on the end of which is fastened a pulley wheel with the aerial wire running through it. From the pulley wheel the aerial runs to a bucket

or similar container filled with something heavy to keep the aerial wire taut.



Pulley wheels can be expensive, so why not substitute an egg insulator? This, as its name suggests, is in the shape of an egg and is made of a ceramic substance for good insulation. Through it are two holes at right angles to each other so one hole can take the securing line while the other has the wire running free through it. This then runs down to the ground and is held taught by a suitable weight. The cost is mainly for the eggs, one for the tree end and one for the building end. This one is secured to an appropriate point by another lashing with the aerial running through or tied off to it, if you prefer the lead-in away from the house wall.

David Birch of Trowbridge has another sort of aerial, this is a Yagi coupled to a Wien Multi-Five set and was enough to pull the following goodies:

Radio Australia on 9570 at 0745



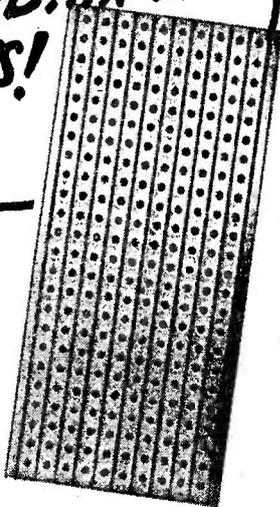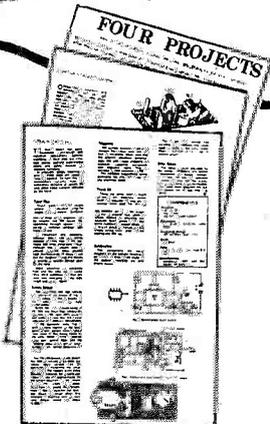FREE! A PIECE OF VERO BOARD... PLUS 4 PROJECTS!



As you know, I'm fairly well in with the Managing Director of Home Radio Components Ltd. He was deep in thought when I called on him the other day. "Cooking up something new?" I said. "Yes" he replied "I'm thinking of giving a piece of Veroboard to everybody who buys one of our catalogues, but I'm wondering if the idea is a bit gimmicky." "Certainly not" I assured him "Several electronic magazines have done it before and I'm sure lots of customers appreciate it". Encouraged, he went on "I thought that if I offered 4 projects for which the board could be used it would make it even more useful and interesting". That set the ball rolling, and with the co-operation of Vero Electronics Ltd. and of Mr. Fred Bennett, Editor of 'Practical Electronics' he is now able to make this unique offer . . . to every purchaser of a Home Radio

Components Catalogue will be sent a piece of Veroboard and four projects for using it. The offer lasts for one month from the publication date of this journal. If you have not already got a current Home Radio Components Catalogue here is a wonderful opportunity to correct the omission (no constructor should be without one) and at the same time to win a useful piece of material and four interesting projects—a Touch Switch, a Thermometer, a Waa Waa Unit and a Light Operated Switch. The catalogue costs only 99p (including 34p for packing and postage) and it includes vouchers to the value of 30 pence if used as directed. This is too good to miss—send the coupon below with your cheque or P.O. for 99 pence. Why delay? Do it today!

Today's finest Components Catalogue
65p plus 34p POST & PACKING

The price of 99p applies only to customers in the U.K. and to BFPO Addresses

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. PW,
 234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No. London 912966)



POST THIS COUPON
 with cheque
 or p.o. for
99p




HOME RADIO (Components) LTD, Dept. PW, 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

uni-lectronics

A COMPLETE RANGE OF DISCO MIXERS POWER AMPS & ELECTRONIC MODULES

DISTRIBUTED BY MAIL ONLY. WRITE TO:—
PARBOLD ELECTRONICS, 17 CHORLEY ROAD, HILLDALE, PARBOLD, WN8 7AN LANCS.
ALL PRICES INCLUDE VAT POST AND PACKING

PA 110 (AS ILLUSTRATED) 110W 4Ω WITH 45-0-45V DC 3 AMP P.S.U. ALL YOU NEED IS AMP CARD AND TRANSFORMER ! HI-POWER, HI-FIDELITY AND LOW NOISE !! KIT: £19.50. BUILT: £24.50. TRANSFORMER £9.90.

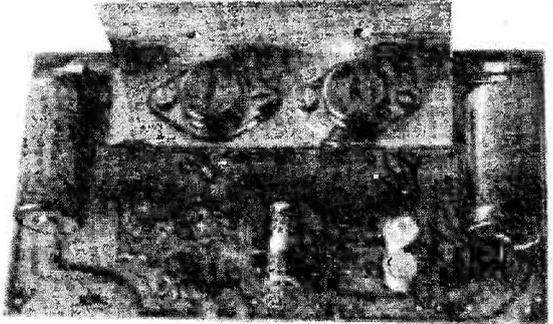

PA 50. 50W 4Ω WITH 45V 2A DC PSU 150 WATT OUTPUT TRANSISTORS AND 5 DIODE PROTECTION CIRCUIT. FUSES AND CAPS ON PSU. BUILT: £7.95. PSU CARD BUILT: £5.95. TRANSFORMER: £4.95.


IC 2/4 INPUT MICROCHIP PRE-AMP TO SUIT EITHER AMP UNIT. FACTORY SET AT 14 MV 50kΩ LINEAR ADJUSTABLE TO 3MV 47kΩ RIAA MAG. EQUALISED OR ANY MAGNETIC CRYSTAL OR CERAMIC DEVICE HIGH OR LOW IMP! UP TO 2.5V OUTPUT AVAILABLE! BUILT: £12.95. CADMIUM PLATED CHASSIS KIT WITH KNOBS, SCREWS, ETC. £9.95. (SCREEN PRINTED AND DRILLED). PACKAGE DEAL PA110 £64.95, PA50 £49.95 INC. CHASSIS & CAB.

CHUNKY 3/4" THICK METAL CORNERED WOODEN CAB WITH HEAVY DUTY FEET AND HANDLES. REALLY PRO. FINISH: £8.95. MONO DISCO PREAMP KIT £49, BUILT: £69, STEREO DISCOMIX KIT £79, BUILT: £119. FUZZ LIGHTS, RED, BLUE, AMBER: £19.50.

TEAK CABS: 7" x 4" £3.90, 8" x 5" £4.90, 8" £5.90, 10" £7.90, 12" £8.90, 12" + TW £9.90.

BLACK CABS: 1 x 12" £12.90, 2 x 12" £16.90, 1 x 15" £19.90, 15" BIN £36.90, 4 x 12" TALL £24.90.

INVERTORS

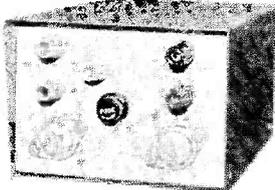

240v-50Hz from your 12v car battery
 25 watt-£4.75 300 watt (12v)-£33.08
 40 watt-£8.27 400 watt (24v)-£39.95
 75 watt-£12.03 500 watt (24v)-£48.18
 150 watt-£21.27 1 Kw (50v)-£127.90
 300 watt (24v)-£26.45 1.5 Kw (110v)-£140.80

All above invertors are in kit form but may be purchased built up in metal case and ready for use. Price list sent on receipt of s.a.e. Prices include p. and p.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24.50 plus £1.70p.p.

FLUORESCENT LIGHT INVERTER KIT

8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for factories, hotels, &c.
 12"-4 watt £3.90 + 35p p. & p. Built up £4.90 + 35p p. & p.
 21"-13 watt £4.20 + 52p p. & p. Built up £5.80 + 52p p. & p.

TRANSFORMERS AND COILS

Both high volume and small order capacity available.
 Special offer. Miniature mains transformer 12-0-12v-6v. A. 85p + 10p p. & p.

ORION STEREO AMPLIFIER



20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response ± 1dB 20 Hz to 20kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.


Complete kit of parts including slim line bookend case, silk screened front panel and knobs £47.30 inc. VAT and p. & p.

The bookend case, I.C's and semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information.

INSTRUMENT CASES

Bookend Amplifier and attractive styled Instrument Cases available. Send S. and A. envelope for Price List.

ASTROIGNITION

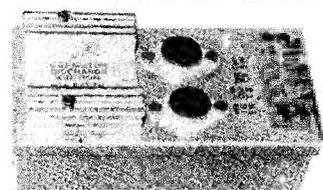

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10.45 inc. VAT Ready built with only two connections to alter £13.75 inc. VAT. Thousands have used this system both home and abroad. Consider these advantages—more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth.

TRADE and EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS

ASTRO ELECTRONICS
 Springbank Road, West Park
 CHESTERFIELD. 31475



Radio Kuwait on 11940 at 1745
HCJB Quito on 9760 at 0800

a sure sign that summer is on its way when Kuwait is heard after tea. Can anyone tell us if the pop show is still going on this slot?

A Joystick package is used by **Lawrence Bennet**, tagged on the front of his Trio 9R59DS. There have been varying claims made for this system and it seems that there is some justification for them since Lawrence logged the following:

AIR Delhi on 3255 at 1730
Radio Chad on 4904 at 1910
Ghana National service on 4915 at 1915
Ghana Commercial service on 4980 at 1920
Radio Mauritania on 4850 at 1930
Benin 'Voix de Revolution' on 4870 at 2015
Radio Togo on 5047 at 2055

Recently in this column there appeared a comment by **Ian Walker** on the fact that Radio Peace and Progress was popping up at an odd spot on the dial of his rig. This and other remarks on this station so moved **Alan Potter** of Bristol that he provided a long screed on the mathematics of intermediate frequencies to prove that this signal was a spurious one. In words of one syllable and numbers under ten, that my poor enfeebled brain can cope with, Alan proved that many receivers have an IF of 450-470kHz and thus the indicated freq was, in fact, spurious. Were it to be put through the mathematical mill it would show one of Radio P&Ps true frequencies. Working the proper way round Alan shows that if one takes the true freq, it is possible to calculate the probable freqs that spurii will inhabit.

Radio Pakistan, Alan tells us, are asking listeners in the UK to report to them on the quality of the evening signal on 7375 and 9465 between 1915 and 2145, so if you care to co-operate the address is: 82a Satellite Town, Rawalpindi, Pakistan. For the benefit of Radio Pakistan I have a report that 7375 is usually a good signal while 9465 is drowned in QRM.


I also have in front of me the scheds for "Peace and Progress" up to October of this year. This, although sent to the UK, only deals with the Asian portion of our globe and is in Chinese and English, is shown in "metres" only and the air time is from 0800 to 1600 with gaps into which the Chinese broadcasts are inserted.

The Principality of Wales comes next in station news with **John Higginbotham's** letter passing on the tip that dear old Radio Nederland is starting to include propagation predictions in its "DX Jukebox" show. This seems to me to be one of the best ways of getting up-to-date information and I would like to see more propagation spots in DX shows. While on the subject of Radio Nederland it is with sadness that I pass on the news that they announced during March, the death of Eddy Startz at the age of seventy-seven. Many long-time DXers will remember Eddy who created the Happy Station shows and who was associated with them for over forty years. While he had retired it was not in Eddy's make-up to sit back and vegetate, and only four or so years

ago he was travelling the world lecturing and writing his memoirs. I suggest that any gathering of DXers should lift a glass to Eddy's memory.

From **Les Waldron**, in Stoke-on-Trent, comes a plea for information on a set that he rescued from a junk yard and thinks is an ex-Service rig. The set has four bands from 1.4 to 20MHz and has on the back a plate stating "Vancouver Radio Labs Inc". So, if you can help, contact Les at 60 Cathanne Road, Chell Heath, Stoke-on-Trent.

Our final word this month is once more on aerials. **J. Watson** from Bolton enquires about an aerial for a loft that he saw ages ago. The thing about this set-up was that it was in the form of a square. This form of aerial is perhaps not very common but one advantage is that the sides can be formed to the length desired. Maximum directivity is generally at right angles to the line of a wire thus by forming a square one can achieve equal input from all points of the compass. A download of low impedance coax from the centre of the wire can be fed out through the eaves and down the wall and back in through the shack window. The wire of course should be suspended from the roof joists with insulators. With that I will declare the innings closed and wish you best 73s.

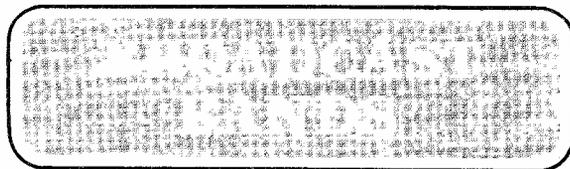

MEDIUM WAVE DX

by **CHARLES MOLLOY**

READER **J. M. Kracinski** reports from Newcastle-on-Tyne with an interesting log of DX from south east Europe and the Middle East. He uses a Philips 10RL59D transistor portable with internal aerial and in spite of the limitations of this type of receiver for DXing he picked-up Bucharest on 603kHz (after Lyons had signed off) the BBC Eastern Mediterranean Relay in Cyprus on 638kHz and 1322kHz; Belgrade on 683kHz; Baghdad on 760kHz; the Voice of America relay at Kavalla in Greece on 791kHz; Dyakabir, Turkey on 1061kHz and Sofia, Bulgaria on 1223kHz. He also asks about a Middle East station on 200kHz on the long waves, behind Radio 2. This is Ankara in Turkey which has been on this channel since early last year when it moved from 181kHz.

The internal aerial in a transistor portable is directional. Maximum pick-up is at right angles to the ferrite rod or slab and there are two nulls, directions of minimum pick-up, along the length of the rod. These nulls enable the DXer to reduce or even eliminate interference simply by rotating the receiver. A ferrite rod aerial could be connected to a communications receiver but DXers have developed the medium wave loop, which is based on the frame aerial used in the early days of radio. The directional properties of a loop together with the sensitivity and selectivity of a communications receiver provide the DXer with a powerful tool with which to explore the medium waves.

A medium wave loop has similar properties to a ferrite rod aerial; it is directional and tunable, but on account of its greater size its pick-up is much



greater. The type of loop in use by many DXers consists of a main winding of seven turns of plastic-covered wire of about 22SWG wound in the shape of a square of 40in. side. A one turn coupling winding is wound parallel to and centrally on the main winding. The two windings are supported by a frame made out of two pieces of lin. square wood which are joined at right angles to make a shape like the letter X. The turns are supported by four paxolin spacers fitted to the ends of the arms. These spacers have saw cuts $\frac{1}{4}$ in. apart along one edge to keep the windings in place.

The main winding is connected across a 500pF variable capacitor which is mounted at the centre of the loop and is used to tune the loop. The coupling winding goes to a small terminal block mounted on the loop from which a length of twin feeder (or twin lighting flex) is taken to the aerial and earth terminals of the receiver. The loop is mounted on a stand in such a way that it can be rotated around its vertical axis. When using a loop, tune-in a station on the receiver, peak-up the signal with the loop tuning control and then rotate the loop for minimum interference.

J. Watson (Bolton) and **M. J. Watson** (Enfield) are constructing loops. So is **F. T. Shortridge** of Llandudno who remarks that he had better results on the medium waves in the 1930s when using a "straight" set than he has now with his AR88. Interference (QRM) was a lot less in the '30s hence the need for a loop! Some DXers claim that a loop gives a "cleaner" signal than a longwire. The reduction in overloading and cross modulation would no doubt give this impression. An improvement in signal-to-noise ratio is nearly always obtained with a loop while, in summer, atmospheric caused by thunderstorms in the southern hemisphere can be considerably reduced when the DXer is listening towards the west or the east.

Glyn Morgan (Tredegar, Gwent) who has been using an Astrad VEF17 portable temporarily for his DXing has at last succeeded in repairing his HA230 communications receiver. The middle wafer of the wavechange switch had developed a "short" on the rotary section. The coil unit had to be stripped, the wafer removed and the carbon scraped away and filled-in with Araldite! A truly remarkable repair by a determined DXer. Glyn used to be a service engineer before an illness deprived him of the full use of his hands and forced him into early retirement. Since the repair he has logged the BBC Eastern Relay on Masirah Island, Oman on 1421kHz and Algiers on 1421kHz (with Saarbrücken, which is on the same channel, off the air). Glyn uses a 40ft long wire fastened to a tree in the garden but a loop is now under construction!

News of another repair comes from **Harold Emblem** of Mirfield in Yorkshire. His Eddystone 730 developed a high noise level and poor sensitivity which was cured when the frequency changer valve, which had worked loose, was pressed fully into its holder. It is always worth while keeping a spare of each type of valve in the receiver so that one can

be replaced should a fault develop. With his receiver back in service again Harold pulled in All-India Radio at Lucknow on 760kHz and Radio Pakistan in Hyderabad on 1010kHz, both stations being heard after 0130 GMT.

Broadcasting in Spain is complex. Radio Nacional Espana, which is state owned, operates a number of high power regional outlets, many of which can be heard easily by the listener in the UK. Local radio, too, is well established. Chains of low power commercial stations operate across the country under the callsign prefixes EAJ, EAK, ECS and EFE each belonging to a different network. Over a hundred are on 1106kHz, 1133kHz, 1385kHz, 1394kHz, 1412kHz, 1430kHz, 1475kHz, 1520kHz and 1570kHz. Picking out these stations can be a real challenge to the DXer as well as being a source of interest. Listen at midnight when many sign off, usually with a full identification. These locals are good verifiers if an International Reply Coupon is enclosed with the report. Many will send the listener a QSL card, pennant or picture postcard of the locality. Listen on 1133kHz for Radio Juventud Murcia (EFJ19) and La Voz de Malaga (EFJ56); on 1385kHz for Radio Centro Madrid (ECS11); on 1394kHz for Radio Popular Vigo (EAK33) and RP Santander (EAK78); on 1412kHz for Radio Tarrasa (EAJ25) and on 1570kHz for La Voz de Alicante (EFE8). A full list of Spanish locals is contained in the World Radio TV Handbook 1976, obtainable now for £4.50 from Argus Books Ltd, Station Road, King's Langley, Herts.

BROADCAST BANDS

Short Wave reports by the 15th of the month to Derek Bell c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any Amateur band/s in band/alphabetical order by the 25th of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashtead, Surrey, KT21 2TW.

SUBSCRIPTIONS

"PRACTICAL WIRELESS" - "TELEVISION"

We are still receiving letters requesting subscriptions to *Practical Wireless* and *Television* magazines. For those readers who are not aware, we regret that our magazines can no longer be supplied on direct subscription by IPC Limited due to escalating costs.

This action is very much regretted, but it should not mean that any reader is deprived of his/her regular copies of *Practical Wireless* or *Television*. Readers should order direct from their local newsagents. Any readers outside the UK who have difficulty in locating a supplier should write to the Editor, PRACTICAL WIRELESS, FLEETWAY HOUSE, FARRINGDON STREET, LONDON EC4A 4AD, ENGLAND.

T.T.L. 74 I.C.'s. Prices include Postage and V.A.T. plus BIG QUANTITY DISCOUNTS

7400 12p	7413 30p	7432 25p	7454 15p	7480 35p	74121 25p	74139 100p	74156 70p	74174 100p	74189 350p
7401 12p	7414 60p	7437 25p	7460 15p	7491 75p	74122 40p	74141 60p	74157 70p	74175 75p	74190 140p
7402 12p	7416 30p	7438 25p	7470 30p	7492 45p	74123 60p	74142 270p	74160 90p	74176 100p	74191 140p
7403 12p	7417 30p	7440 15p	7472 25p	7493 40p	74125 30p	74143 270p	74161 90p	74177 100p	74192 120p
7404 12p	7420 15p	7441 65p	7473 30p	7495 60p	74126 50p	74144 270p	74162 90p	74178 140p	74193 120p
7405 12p	7422 20p	7442 65p	7474 30p	7496 70p	74130 130p	74145 75p	74163 90p	74179 140p	74194 160p
7406 12p	7423 25p	7445 80p	7475 30p	74100 95p	74131 100p	74147 230p	74164 125p	74180 100p	74195 160p
7407 35p	7425 25p	7446 85p	7476 30p	74104 40p	74132 65p	74148 160p	74165 125p	74181 280p	74196 100p
7408 15p	7426 25p	7447 75p	7483 85p	74105 40p	74135 100p	74150 120p	74166 125p	74182 75p	74197 100p
7409 15p	7427 25p	7448 70p	7485 100p	74107 30p	74136 80p	74151 85p	74167 325p	74184 150p	74198 185p
7410 13p	7428 40p	7451 15p	7486 30p	74109 80p	74137 100p	74153 55p	74170 200p	74185 150p	74199 185p
7411 20p	7430 15p	7453 15p	7489 250p	74120 90p	74138 125p	74155 70p	74173 150p	74188 350p	

SPECIAL OFFER ALL 22 I.C.'s FOR P.W. DIGITAL FREQUENCY COUNTER FOR £7.50

POPULAR BRANDED TRANSISTORS

BC147 — BC148 — BC149 — BC157 — BC158 — BC159 — BF194 — BF195 — BF196 — BF197
7p each. 100 for £6.00. Type numbers may be mixed for quantity discount.

Bulk Purchase I.T.T. IN4148 10 for 30p, 100 for £1.50

1 Amp Diodes IN4001, IN4002, IN4003 4p each, 30 for £1.00
IN4004, IN4005, IN4006 6p each, 30 for £1.50

Zener Diodes BZY88, 400MW 3V to 33V 7p each, 100 for £6.00

NEW LOW PRICE
741 OP Amps
ANY QUANTITY 20p each
555 TIMERS
ANY QUANTITY 35p each

TRANSISTORS, etc.

AC128 12p	MTCHN PR 80p	AF117 18p	BC148 7p	BC182L 12p	BC212L 12p	BCY72 16p	BF190 30p	BFX85 25p	2N3702 12p
AC176 12p	AF114 18p	BC107 9p	BC149 7p	BC183 10p	BC547 12p	BD124 70p	BF182 30p	BFX87 25p	2N3704 12p
AD149 45p	AF115 18p	BC108 9p	BC157 7p	BC183L 11p	BC548 12p	BD131 35p	BF183 30p	BRV39 35p	1N914 3p
AD161 35p	AF116 18p	BC109 9p	BC159 7p	BC184 11p	BC549 12p	BD132 35p	BF200 30p	BRV56 35p	BY100 15p
AD182 35p		BC109 9p	BC169 12p	BC184L 12p	BCY70 16p	BD135 50p	BF244 18p	BSX20 16p	BY126 16p
		BC147 7p	BC182 11p	BC212 11p	BCY71 16p	BD137 40p	BFX84 25p	2N3055 50p	BY127 12p

PLEASE NOTE THAT ALL PRICES INCLUDE POSTAGE AND V.A.T. AT 8 OR 12½% AS APPROPRIATE

**MAIL ORDER ONLY
XEROZA RADIO**

1, EAST STREET, BISHOPS TAWTON, BARNSTAPLE, DEVON

SUMMER SALE DEDUCT 10% FROM THE PRICES SHOWN HERE. OFFER CLOSES JULY 31st 1976 min. CWO £1.

LINEAR ICs

CA3089E 1.94	7805KC 1.75*
KB4402 1.94	7805UC 1.55*
TDA1200 1.94	78L12 0.45*
HA1137W 2.20	78M12 1.20*
CA3090AQ 3.75	TDA1412 0.95*
MC1310P 2.20	7812 1.55*
KB4400 2.20	7815 1.55*
CA3053 0.40	78M20 1.20*
CA3089E 1.50	78M24 1.20*
LM1496 1.02	uA723 0.80*
	NE550 0.80*
MC1350P 0.70	LS8038 3.10*
SN7666ON 0.75	NE555 0.70*
TBA120AS 1.00	NE560 2.50
TBA651 1.81	NE561 2.50
uA720PC 1.40	NE562 2.50
uA753 0.99	NE566 2.55*
TDA440 1.75	NE565 2.50
	NE567 2.50*
LM380 1.00	NE567 2.50*
LM381N 1.81	MVAM2 1.05
LM3900 0.68*	BA102 0.30
MC3401 0.68*	BA121 0.30
uA741 0.40*	MV104 0.45
TBA810AS 1.09	MEM615 0.38
TCA940E 1.80	MEM616 0.50
TDA2020 2.99	11C90 14.00*

DISCRETE

ZTX107n 0.14	BD515n 0.27
ZTX108n 0.14	BD516p 0.30
ZTX109n 0.14	BD165n 0.50
ZTX212p 0.16	BD166p 0.54
ZTX213p 0.16	BD535n 0.52
ZTX214p 0.16	BD536p 0.53
ZTX413n 0.18	BD609n 0.70
ZTX551p 0.18	BD610p 1.20
ZTX451n 0.18	BD377n 0.29
BF224n 0.22	BD378p 0.32
BD515n 0.27	1N4001 0.06
BD516p 0.30	1N4004 0.10
BD165n 0.50	1N4148 0.07
BD166p 0.54	OA91 0.08
BD535n 0.52	DL704 0.95*
BD536p 0.53	SLA1 1.25*
BD609n 0.70	
BD610p 1.20	

Modules, tuners


5600	Varicap Mosfet with 4 tuned RF ccts.	11.00
EC3302	Varicap FET/Bipolar min. tunerhead.	5.50
9001	Frequency meter, scale 88 - 108.	2.50
9002	Strength meter, scale 0 - 10.	2.50
9007	Tuning meter, scale 3 - 0 - 3	2.50
7700	'Off-air' UHF TV sound receiver Varicap tuned, with interstation muting, and sound detection at 38 MHz (Built). inc. P.S.U.	26.00
8011	6 station electronic station selector for any positively tuned varicap tuner system, incorporating a muting output, AFC lock and scan tuning. Built.	14.99
7252	Top quality tunerset VHF to audio Varicap tuned with 3 meter outputs.	24.00
7253	Tunerset with built-in stereo decoder. Varicap tuned.	24.00
8319	Dual Mosfet tunerhead as used in 7252.	12.00
2020k	TDA2020 stereo amplifier kit.	7.85
2020HS	Heatsink for one TDA2020 (only with IC).	0.75
8001k	55kHz low pass filter (birdy filter) for stereo radio (between detector and decoder).	1.75
Suffix 'k' indicates kit, otherwise supplied built and tested.		
NEW MODULES (EDGE TERMINATED)		
5619	6 stage, dual mosfet UHF tunerhead.	£12.50
7020k	10uV FM IF system with muting, agc, main tuning voltage AFC system.	£4.50
92310k	Comprehensive 1310 decoder, with notch filters and 6x gain.	£5.35

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 12½%, but where items are marked * only add 8%. In stock orders despatched within 48 hours.

ambit INTERNATIONAL
25 High Street, Brentwood, Essex. Tel: (0277) 216029, Telex: 995194.

RTVC

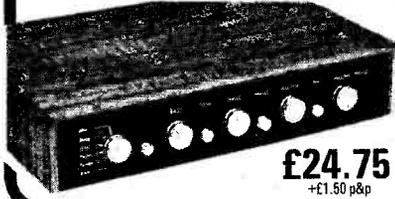
Now the VISCOUNT IV 30 x 30 Stereo Amp IN KIT FORM



£24.75
+£1.50 p&p

For the experienced constructor the Viscount IV amplifier comes complete with teak finished cabinet, front trim panel, knobs and all necessary metalwork. The specification for the NEW 30 x 30 is similar to the complete system offered below, but of course with the bigger output.

STEREO

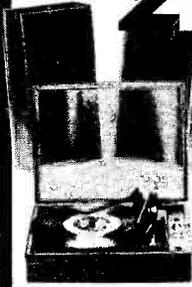

COMPLETE ONLY
£23.00 + p&p £4.00

INCORPORATING A GARRARD DECK
Garrard 3 speed Deck automatic, manual facilities together with stereo cartridge and cueing device.

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in Simi Teak, and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes - 3 speed deck, automatic manual facilities together with stereo cartridge and cueing device.

Two speakers with cabinets. Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions. Specifications - For the technically minded.

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs.

Overall Dimensions. Speakers approx 12" x 9" x 5". Complete deck and cover in closed position approx 15 1/2" x 12" x 6". Extras if required. Optional Diamond Stylus **£1.50**. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.25**

BSR DECKS WITH PLINTHS AT FANTASTIC REDUCTIONS



MP 60 Type (illustrated) £14.40
Less Cartridge p&p £2.00
C141 (not illustrated) £10.80
Auto, with Cue p&p £1.50
Fitted Stereo Cartridge
All plinths finished in matching Teak veneer.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 1/2" tweeter and matching crossover. Easily put together with just a few basic tools.

Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£19.80 pair complete Complete with crossover Components and circuit diagram.



EASYBUILD THE NEW 'COMPACT' SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitered and professionally finished, and fix together with masking tape till glue dries.

The cabinet measures 12" x 9" x 5" deep approx. finished in simulated teak, incorporating a quality 8" speaker, maximum power handling 7 watts, impedance 8 ohms nominal, magnet size 2 3/8" approx., with 1 1/2" parasitic tweeter.

£7.50
PAIR INCLUSIVE
+ p&p £1.70



EMI 350 KIT

£6.55 + £1.20 p & p.
Complete with crossover Components and circuit diagram

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

VISCOUNT IV STEREO AMP

COMPLETE 20 x 20 SYSTEMS

SYSTEM 1b £65.00

The new 20 + 20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion at 10 watts better than 0.2%. Six switched inputs: 1. Magnetic PU. - 3 millivolts at 47 K ohms (R.I.A.A.), 2. Crystal/ceramic PU. - 50 millivolts at 50 K ohms (R.I.A.A.), 3, 4, 6. Tape Tuner/Aux. - 140 millivolts at 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts at 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 kHz at full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ±15 dB at 50 Hz; Treble ±12 dB at 10 KHz. Power requirements: 250V A.C. mains at 60 watts.

Approx size: 15 1/2" x 3" x 10". **MP60 type deck** with magnetic cartridge, de luxe plinth and cover. **Two Duo Type II B matched speakers** - Enclosure size 18 1/2" x 13 1/2" x 7 1/4" approx. in veneer teak. Drive unit 10" with 2 1/2" tweeter. 12 watts handling 24 watts peak.

Complete System with these speakers
£65.00
+ £6.50 p&p.

SYSTEM 2 £80.00

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS, 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System with these speakers **£80.00** + £7.60 p & p.

PRICES: SYSTEM 1a
Viscount IV amplifier £24.75 + £1.90 p & p.
2 Duo Type II B speakers £27.00 + £8.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £19.80 + £3.30 p & p.
Total if purchased separately: £71.55
Available complete for only: **£65.00** + £6.50 p & p.

PRICES: SYSTEM 2
Viscount IV amplifier £24.75 + £1.90 p & p.
2 Duo Type III speakers £41.40 + £7.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £19.80 + £3.30 p & p.
Total if purchased separately: £86.95
Available complete for only: **£80.00** + £7.60 p & p.



20x20 SYSTEM

Scotland P & P Surcharge + £1.75 System 1a £1.75 System 2 £3.50

Note: 30 x 30 kit available only as a separate item.

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT



IF YOU CAN SOLDER CORRECTLY ON A PRINTED CIRCUIT BOARD YOU CAN BUILD THIS KIT CORRECTLY

NOW YOU CAN BUILD YOUR OWN PUSH BUTTON CAR RADIO!

This construction kit comprises a fully built and aligned R.F.I.F. module: Printed circuit board, with ready mounted integrated circuit output stage and all other components. The push button tuning mechanism is fully built and tested ready to mate with the printed circuit board. (once it is assembled).
NOTE: No test equipment is required for alignment, but remember you must have the ability to solder on a printed circuit board.


TECHNICAL SPECIFICATION

(1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide, 2" high and 4 3/4" deep approx. Speaker including baffle and fixing strip £1.80+45p. p&p. Car Aerial Recommended—fully retractable £7.40 +£1.05 p&p. £1.45+40p. p&p.

STEREO CASSETTE TAPE DECK KIT

Kit comprises of ready built cassette tape transport mechanism. Featuring pause control, solenoid assisted auto-stop, 3 digit tape counter, belt-driven balanced fly wheel, DC motor with electronic speed control, ready built and mounted record/replay PC board, and two VU meters, power supply, PC board, mains transformer. Input and output sockets and two level controls. Specification power source 240 AC 50Hz. Output more than 0.5v input mike -65dB. 10KΩ. DIN -47dB. 100KΩ. Track system 2 channel stereo record play-back. Tape speed, 4.8CM/SEC. Frequency response 50-12000 Hz signal to noise ratio -42dB. Recording system AC Bias. Erasing system AC erase. Bias frequency 57KHz. Size of mechanism 8" x 5" x 3 1/2" approx. unit easy to mount into your cabinet 3" required to clear base of mechanism approx.

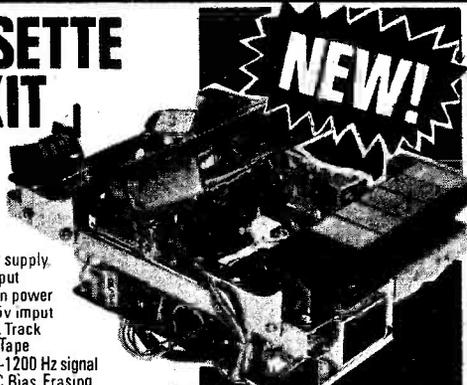* This is an advanced kit not suitable for those without electrical knowledge and those unable to solder.



£29.25
+ p&p £1.50
or send SAE for complete details.

NEW PRODUCT DISCO 35 MONO AMPLIFIER


An ideal general purpose 35 watt mono amplifier with full mixing facilities. Suitable for DISCO, PUBLIC ADDRESS & GUITAR/MUSICAL INSTRUMENTS. Unit housed in an attractively styled teak veneered cabinet. 4 Inputs: DISC 1 & DISC 2 (BOTH FOR CERAMIC CARTRIDGES), tape and microphone. CONTROLS: All level mixing controls are fitted with integral switches, push button type. DISC 1 & DISC 2: Volume combined treble filter. TAPE: Volume combined bass booster switch. MASTER: Volume control combined on/off. MIC: Volume combined bass booster switch. INDEPENDENT BASS AND TREBLE CONTROLS.

TECHNICAL SPECIFICATION

Power output: 35RMS into 4 ohms. Speaker: (Suitable for 4 to 15 ohms speakers). Sensitivities: DISC 1 & DISC 2: 30 mv (into 120k RIAA). Treble Filter Switch: 12 db@ 10 KHz. Tape: 100 mv (into 120k Flat). Bass Booster Switch=18 db@ 60 Hz. Mic: 2 mv (equilised for dynamic). Bass Booster Switch=20 db@ 60 Hz. Bass Control: ±15 db@ 60 Hz. Treble Control: ±12 db@ 10 KHz. £25.00 +£1.40 p&p

8 TRACK HOME CARTRIDGE PLAYER

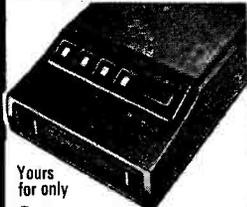Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV.



Yours for only **£12.60** +£1.70 p & p.

SPECIAL OFFER

As above but complete with build yourself Unisound Amplifier Kit (see opposite Panel) + 2 'Compact' easy to build speaker kits (see opposite page) **£24.50** + p & p £2.00

BUILD YOUR OWN STEREO AMPLIFIER




For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£8.00 £1.05 p & p.

Also available with the 'Compact' (see opposite page) easy build speaker kit £14.50 + £2 p & p

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

PORTABLE DISCO CONSOLE

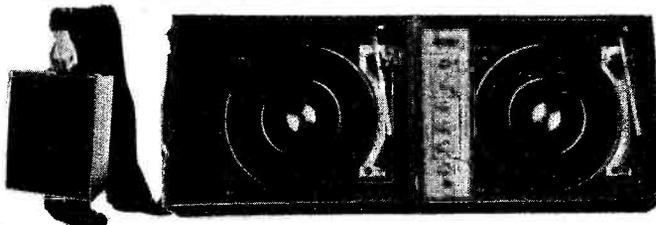

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV.
Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation.
Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter).
Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17 1/4" x 13 1/4" x 8 1/4" (app.)
Unit Open — 35 1/4" x 13 1/4" x 4 1/4" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edge, diamond spun control knobs with matching control panel.

Yours for only **£49.00** +£6.50 p & p.

All prices include VAT at current rates

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelopes. Goods not despatched outside U.K.

All items subject to availability. Prices correct at 1st May 1976, and subject to change without notice.

Minimum order on ACCESS/BARCLAYCARD—£11.



DO NOT SEND CARD
Just write your order giving your credit card number



21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

NO HIDDEN EXTRAS—Prices include VAT and P & P. EXCEPT WHERE CARRIAGE WILL BE ACCORDING TO WEIGHT & DISTANCE—BRS. Widerange of Audio accessories, semiconductors, Panel Meters & Multi-Meters

CALLERS WELCOME (MON.-FRI.) OR SEND STAMP FOR LISTS.

MAINS ISOLATING

Sec. 120/240V CENTRE TAP WITH SCREEN Ref. VA (Watts) £

07*	20	3-97
149	60	5-84
153	100	6-67
151	200	10-43
152	250	12-67
153	350	14-99
154	500	17-21
155	750	23-69†
156	1000	33-01†
157	1500	37-68†
158	2000	42-03†
159	3000	66-40†

*115V or 240V Sec. only.

12 and or 24 Volt PRIMARY 240-250 VOLTS

Ref. VA Amps £

111	12v	0-5	1-97
023	1-0	0-5	2-24
71	2	1	2-80
68	3	1	4-60
18	4	2	3-98
85	5	3	4-91
108	6	4	5-56
108	8	4	6-41
116	12	6	7-42
17	16	8	9-13
115	20	10	13-52
187	30	15	16-86
226	60	30	19-08†

HIGH VOLTAGE Mains Isolating

Sec. 100/120 or 200/240 P & P VA Ref. £

60	243	5-77
350	247	13-33
1000	250	28-41†
2000	252	47-65†

AUTO TRANSFORMERS

Ref. VA (Watts) £

113	20	0-115-120-240	2-44
64	75	0-115-200-220-240	4-07
4	150	0-115-200-220-240	5-45
66	300	"	7-51
67	500	"	11-46
84	1000	"	17-25
93	1500	"	20-54†
95	2000	"	27-44†
73	3000	"	39-46†

CASED AUTO TRANSFORMERS

240V mains feed input & USA 2 pin outlets. Ref. VA £

44	33	Ref 113V
150VA	47-80	Ref 4W
500VA	£13-37	Ref 67W
1000VA	£19-85†	Ref 84W
2000VA	£31-01†	Ref 95W

ON SITE TOOL ISOLATORS

240 to 110V · 500VA to 2KVA (to BS3535) Send for details

50 VOLT RANGE

Prim. 200-240V Sec. 0-19-25-33-40-50V Ref. No. Amps £

102	0-5	3-46
103	1-0	4-61
104	2-0	6-61
105	3-0	7-63
106	4-0	9-83
107	6-0	15-08
118	8-0	16-46
119	10-0	19-17†

SCREENED MINIATURES

Ref. mA Volts £

238	200	3-0-3	1-98
212	1A, 1A	0-6-0-6	2-71
13	100	0-9-0	1-96
235	330, 330	0-9-0-9	2-04
207	500, 500	0-8-9-0-8-9	2-73
208	1A, 1A	0-8-9-0-8-9	3-94
236	200, 200	0-15-0-15	1-94
214	300, 300	0-20-0-20	2-82
221	700 (DC)	20-12-0-12-20	4-28
206	1A, 1A	0-15-20-0-15-20	4-70
203	500, 500	0-15-27-0-15-27	4-18
204	1A, 1A	0-15-27-0-15-27	5-14
5112	500	12, 15, 20, 24, 30	2-68

BRIDGE RECTIFIERS

Ref. VA £

50V	2A	0-55
100V	2A	0-61
100V	6A	0-95
200V	1A	0-85
200V	2A	0-67
400V	2A	0-72
400V	4A	0-89
600V	2A	0-78
1000V	2A	0-89
500V	10A(P17A6)	2-70

TEST METERS

Ref. £

AVO 8 MK5	£67-17
AVO 72	£26-78
AVO 1M5	£23-40
AVO T169	£27-26

AVO Cases and Accessories.

POWER UNIT

CC12-05 Output Switched 3-4-5-6-7-5-9-12V at 500mA. £5-03.

SWITCHES

SPST TOGGLE 3 FOR 0-97 DPDT TOGGLE 3 FOR 1-18 DPDT SLIDE 6 FOR 0-97 Ref. £

ANTEX SOLDERING IRONS	15W £3-40 18W £3-19 25W £2-92
SOLDERING IRON KIT	£4-48 STAND FOR ABOVE £1-49

MAGNETIC TO CERAMIC CARTRIDGE CONVERTER

OPERATING VOLTAGE 20-45V ONLY £3-17.

COMPONENT PAKS

- 200 Mixed value resistors (count by weight)
 - 150 Mixed value capacitors (count by weight)
 - 30 Mixed value precision resistors ½ 2%
 - 15 Assorted pots & pre-sets
 - 10 Reed switches
 - 3 Micro Switches
 - 20 Assorted tag strips
- PLEASE STATE PAK REQUIRED 87p PER PAK.

AUDIO KIT 25W

- 2+25W Amplifiers
- 1+Pre-Amp
- 1+Power supply
- 1+Transformer
- 1+Front Panel
- 1+Kit of parts to include on/off switch, neon ind. Stereo headphone socket. Plus instructions book £32-07.

TEAK AUDIO KIT 25W

- Teak veneered cabinet
- 162+113+32+, aluminium chassis, heat sink and front panel, brackets plus back panel and sockets etc. £11-00

NEW STEREO 30

- Complete Stereo Chassis inc. 7+7w RMS, 5amp, Pre-amp, Power Supply, Front Panel, Knobs (only needs Mains Trans.).
- Stereo 30 £18-67. Mains Trans £3-15. Teak veneered cab. £4-51.

STEREO FM TUNER

- fitting with Phase-lock Loop
- 4 Pre-selected stations supply 20-35V, 90mA Max. £22-71

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ TELEPHONE: 01-488 3316/7/8 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

B. BAMBER ELECTRONICS

Dept PE, 5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

FREE WELLER 25W (SP25) SOLDERING IRON (worth £3-24 inc. VAT) with all orders over £20 Limited period only. Send now.

HEAVY DUTY RELAYS, 24V d.c. operated (will work on 18V) 3 heavy duty make contacts (around 10A rating) & 4 change over contacts + 1 break contact. New, complete with mounting bracket (ideal for switching HT on Lines). Many uses for this high quality unit. £1-50 each.

Good Quality Pressure Gauges, 2 1/2 in dia. flange mounting, 3 models avail. 0-60 lb/sq in., 0-100 lb/sq in., 0-200 lb/sq in., state which £1-25 each.

2N3855 type Transistors, O.K. but unmarked, 5 for £1.

ALU-SOL ALUMINIUM SOLDER (made by Mull-core). Solders aluminium, 10 itself or copper, brass, steel, nickel or tinplate. 16 w.e.g. with multicore flux, with instructions. Approx. 1 metre coil 30p each. Large reel (approx. 12 metres) £2-75.

MIXED COMPONENT PAKS, containing resistors, capacitors, switches, pots, etc. All new (random sample bag, revealed approx. 700 items), £2 per pack, while stocks last.

TUNED COILS, 2 section coils, around 1MHz, with a black smart tuning knob, which moves an internal core to vary the inductance. many uses, easily rewound, 3 for 50p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.) approx. 3/4 x 1 1/2 in., 3 for 50p.

PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108 MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 9 1/2 x 1 1/2 in., 2 for 35p.

Multiturn Pots, 10 turns, 1/4 in spindle (ax-equip), following values available, 2kohm, 5kohm, 20kohm, £1 each.

Lead suppressors (10kohm) for mobile plug leads, 4 for 50p.

1MA Meters, 2 in square, plastic fronts (these have a paper scale stuck over the original marked 0-1mA which is easily peeled off and an internal 18K resistor which is easily removed), £1-75 each or 2 for £3.

R/S Midget 3 pole 4 way, rotary switches, 40p each.

HIGH QUALITY SPEAKERS, 8 1/2 in x 6 in elliptical, only 2in deep. Inverse magnet, 4 ohms, rated up available @ 125p each or 2 for £2-75 (qty discount available @ 125p VAT)

TV PLUGS AND SOCKETS TV Plugs (metal type), 5 for 50p. TV Sockets (metal type), 4 for 50p. TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 12 1/2% VAT.

PLUGS AND SOCKETS N-Type Plugs 50 ohm, 60p each, 3 for £1-50. N-Type Sockets (4-hole chassis mounting, 50 ohms (6 small coax lead type), 50p each. P1239 Plugs (P7FE), brand new, packed with reducers, 65p or 5 for £3.

S0239 Sockets (P7FE), brand new (4-hole fixing type), 50p each or 5 for £2-25.

25-way ISEP Plugs and Sockets, 40p set (1 plug + 1skt).

Plugs and sockets sold separately at 25p each Bulk/Innord Free Skts, 3 pin, for mains input on test equipment, etc., 25p each.

Mobile Converters, 24V DC input 13-8V at approx 3-4A DC output, fully stabilised, £3-50 each (ideal for running 12V car radio from 24V lorry battery).

Pkts. of 2BA Nuts (the self-locking ones with the nylon insert) 100 for 50p.

We now stock Spiralax Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

I.F. Cans, 1in square, suitable for rewind, 6 for 30p + 12 1/2% VAT.

Miniature earphones with min. jack plug, 2 for 50p + 12 1/2% VAT.

TWIN I.F. CANS, approx. 1in x 1/2 in x 1in high, around 3-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.

Dubilier Electrolytics, 50uF, 450V, 2 for 50p.

Dubilier Electrolytics, 100uF, 275V, 2 for 50p.

Plessey Electrolytics, 470uF, 63V, 3 for 50p.

TCC Electrolytics, 1000uF, 50V, 3 for 60p.

Plessey Electrolytics, 1000uF, 180V, 40p each (3 for £1).

Dubilier Electrolytics, 5000uF, 35V, 50p each.

Dubilier Electrolytics, 5000uF, 50V, 60p each.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

Dubilier Electrolytics, 5000uF, 70V, 65p each.

ITT Electrolytics, 880uF, 25V, high grade, screw terminals, with mounting clips, 50p each.

Plessey Electrolytics, 10,000uF at 63V, 75p each.

Plessey Cathodray Capacitors, 0-0-40 at 12-5kV DC, Screw terminals, £1-50 each.

PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

SPECIAL OFFER! MAINS TRANSFORMER, TYPE 14/4, 14V at 4A, £2-50.

TO3 transistor insulator sets, 10 for 50p.

MINIATURE 2 PIN PLUGS AND SOCKETS (fit into 3in hole, pins enclosed, with covers for chassis mounting, or can be used for in-line connectors). Bargain pack of 3 plugs + 3 sockets + covers, 50p.

PROGRAMMERS (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable, ideal for switching diode lights, displays, etc. or industrial machine programming. (Need slow motion motor to drive cams, not supplied)

9 switch version £1-50, or 16 switch version £2.

HEAVY DUTY HEAT-SINK BLOCKS, undrilled, base area 2 1/2 in x 2 in, with 6 fins, total height 2 1/2 in 50p each.

RUBBER MAGNETS 1/2 in square, with mounting hole, 20 for 30p.

SPERRY 7-SEGMENT P.G.D. DISPLAYS, digit height 0.3in, red, with decimal points, 150V to 200V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new. At THE BARGAIN PRICE OF 50p PER DIGIT, TYPE 332 (two digits in one mount) £1 each, Type 333 (three digits in one mount) £1 50p. (Sorry, no single digit available.) Data Supplied.

BSX20 (VHF Osc/Mult), 3 for 50p.

BC108 (metal can), 4 for 50p.

PBC 108 (plastic BC108), 5 for 50p.

OC200 Transistors, 6 for 50p.

BFY51 Transistors, 4 for 60p.

BCY72 Transistors, 4 for 50p.

HEAVY DUTY TRANSISTORS, 12 for 25p.

BF125 (UHF amp/lexer), 3 for 50p.

BA121 Varicap Diodes, 4 for 50p.

1N914 diodes, 10 for 25p.

1 1/2 in polythene chassis mounting fuseholders, 6 for 30p.

Mulard Tubular ceramic trimmers, 1-16pF, 6 for 50p.

I.C.s, some coded, 14 DIL type, untested, mixed, 20 for 25p.

DIACBAT BOXES (approx size in inches)

4.3 x 2.3 x 1.2 85p

4.8 x 2.3 x 1.5 95p

4.8 x 3.6 x 1 1-00

4.8 x 3.8 x 2 1-25

6.8 x 4.8 x 2 1-75

4.8 x 3.8 x 3 2-85

6.8 x 4.8 x 4 2-75

8.6 x 5.8 x 2 2-25

10.6 x 6.8 x 2 2-85

Please add 8% VAT

WELLER SOLDERING IRONS EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.

EXPERT SOLDER GUN, £8-80 + VAT, (54p)

EXPERT SOLDER GUN KIT (spare bits case, etc.), £9-80 + VAT (78p)

SPARE BITS, PAIR, 25p + VAT (2p)

MARKSMAN SOLDERING IRONS

SP15D 15W £3 + VAT (24p)

SP25D 25W £3 + VAT (24p)

SP25K 25W + bits, etc. kit £3-85 + VAT (31p)

SP40D 40W £3-44 + VAT (28p)

BENCH STAND with spring for Marksmen Irons, £2-22 + VAT (18p)

SPARE BITS

MT8 for 15W, 44p + VAT (4p)

MT4 for 25W, 34p + VAT (3p)

MT10 for 40W, 42p + VAT (3p)

TCPI TEMPERATURE CONTROLLED IRON, Temperature controlled iron & PSU, £20 + VAT (£1-60)

SPARE TIPS

Type C single flat tip, Type K double flat fine tip, Type P - very fine, £1 each + VAT (8p).

ALL SPARES AVAILABLE

MULTICORE SOLDER

Size 5 Savbit 18 w.s.g. in alloy dispenser, 32p + VAT (3p)

Size C15AV18 Savbit 18a.w.g., 56p + VAT (4p)

Size 12 SAVBIT 18a.w.g. on plastic reel £1-80 + VAT (15p)

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE WITH ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS SATURDAYS ONLY 9.30-10.00, 1.30-5.00.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £2-50 plus 45p post and VAT. Made up model £1-25 extra.

PERMEABILITY TUNERS

M.W. two stage ideal for use with ZN414 or similar circuit. Price 15p each + post and VAT 15p.

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1-50. VAT + postage 60p.



NUNICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XN11. Price £1-25 each, 20p Post and VAT.

DC HIGH CURRENT PANEL METERS

3 1/2" wound wide angle 240 movement meters, flush mounting fitted with external shunts, made by Crompton Parkinson, brand new, still in maker's cartons. These are a real bargain at £5-50 each. Reasonable quantities available in the following ranges 0-15 amps, 0-20 amps, 0-30 amps, 0-40 amps, Post and VAT 80p each.



WINDSCREEN WIPER CONTROL

Very speed of your wiper to suit conditions. All parts and instructions to make. £2-75 plus 80p post and VAT.



SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w) Unit in box all ready to work. £7-95 plus 90p VAT and postage.



SPIT MOTOR

200-250V Induction motor, driving a Carter gearbox with a 1 1/2" output drive shaft running at 5 revs p.m for roasting chickens, also for driving mills—winemills, coloured disc lighting effects, etc. £2-50 plus 50p post and VAT.



OVEN THERMOSTAT

Made by the famous Diamond H Company, this has a sensor joined by a capillary to a variable control and when fitted with a knob is ideal for many ovens or processes, 50p each + post and VAT 15p.



MAINS TRANSFORMERS

All standard 230-250 volt primaries	£ p
1v.....	1 amp (special) 1-78
2-4v.....	5 amp 8-85
6-3v.....	2 amp 1-25
6-3v.....	3 amp 1-75
9v.....	1 amp 8-95
9v.....	2-5 amp 2-50
12v.....	1 1/2 amp 1-50
12v.....	1 amp 1-00
6-3v-0-6v.....	2 amp 5-50
18v.....	1 amp 1-50
24v.....	2 amp 2-25
24v.....	3 amp 3-60
12-0-12v.....	50mA 1-20
6-0-6v.....	50mA 1-20
3-0-3v.....	3 amp 1-50
25-0-25v.....	2 amp 5-50
25v.....	1 1/2 amp 1-95
40v tapped 10 20 30.....	250 watts 3-50
60v 2 amp & 6-3v.....	1 amp 4-50
60v 5 amp & 5v.....	1 amp 7-50
27v.....	8 amp 4-50
30v.....	37 amp 22-00
60v tapped 7v & 70v.....	2 amp 5-50
230v-60mA & 6-3v.....	1-5 amp 1-75
275-0-275v at 90mA & 604v 3 amp.....	2-25
EHT Transformer 5000v 25mA.....	(intermittent) 5-60
Charge Transformers	
6v and 12v.....	2 amp 1-50
6v and 12v.....	3 amp 2-25
6v and 12v.....	5 amp 3-50

Add 30p per £1 to cover postage and VAT


LIGHT PIPE

A mains operated travelling light array 24ft. long it uses 130 miniature bulbs which flash in sequences to make bands of light move along the tube.—The tube can be draped around a particular item or set and cannot fail to attract attention—complete kit consists of—24ft. of translucent tubing—140 miniature bulbs—8 yards multicore cable—motorised switch—taps for quick connections and full wiring instructions, £15-00 for the complete kit. Post and V.A.T. paid.



HONEYWELL PROGRAMMER

This is a drum timing device, the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control. Boiler firing. Dispensing and Vending machines. Display lighting animated and signs. Signalling, etc. Price from makers probably over £20 each. Special snip price £9-96. £1-00 Post and VAT. Don't miss this terrific bargain.

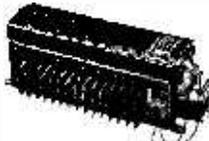

BREAK-DOWN UNIT

Contains hundreds of useful parts some of which are as follows—68 silicon diodes equivalent OA91, 68 resistors, mostly 1/2 watt 5% covering a wide range of values 4 x .1 mfd 400v condensers, 15 x .01 mfd 100v condensers, 2 RF chokes 8 x B9 valve holders, 1 x 4H choke, 1 x 115v transformer, 1 boxed unit containing 4 delay lines also tag panels, trimmer condensers, suppressors, etc., on a useful chassis sized approx 9" x 5" x 7". Only 75p (the 66 diodes would cost at least 10 times this time) This is a snip not to be missed. Post and VAT 75p.



THIS MONTH'S SNIP

POWER SUPPLY MADE BY BUSH RADIO

A PP3/PP9 battery illuminator in casing with input and output leads. Original price over £6-00. Offered at this month's snip £2-68. Post and VAT paid.

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14-00 including VAT and postage.



HIGH POWERED TRANSFORMER


Rated at 250 Watts, upright mounting varnish impregnated. Its primary is for 230/240 volts 50 cycles, it has four secondaries each 10v very high current windings. Just a few of the circuits it can power are: 10-0-10v at up to 12 amps; 20-0-20v at up to 6 amps; single 10v at 25 amps; single 20v at 12 1/2 amps; single 30v at 9 amps; single 40v at 6-5 amps. This can be used for charging or for amplifiers, etc., there being an earth screen between primary and secondaries. A transformer like this today would cost at least £15 from the makers; however, we are making a special offer at £3-50 + 25p post £1 + 8p each. Grab some while you can, our stock may not last long.

TWIN OUTPUT POWER PACKS

These have two separately R.C. smoothed outputs so can operate two battery radios on a stereo amp without cross modulation (they will of course operate one radio-tape-cassette-calculator in fact any battery appliance and will save their cost in a few months' service). Full wave rectification, double insulated mains transformer—total enclosed in a hard P.V.C. case—three core mains lead—terminal output—when ordering please state output voltage 41v, 6v, 7 1/2v, 9v, 12v or 24v. Price £3-95. Post and VAT included.

ONLY £1-50 FOR SEVEN ELECTRIC MOTORS

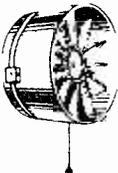7 powerful batt. motors as used in racing cars and power models. Output and types vary for use in hundreds of projects—Toots, toys, models, etc. All brand new reversible and for 1 1/2-12v batts. Wiring diag. inc. VAT + Post 40p. FREE plan for min. power station.



EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector and fixing brackets. £4-75 including post & VAT.



Monthly list available free; send long stamped envelope.

TERMS: Where order is under £5 please add 30p surcharge to offset packing expenses.

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.), 103 TAMWORTH ROAD,
CROYDON CRO IXX

ITS FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—its an interesting list and its free—just send S.A.E. Below are a few of the Bargains still available from previous lists.

Stereo timing lights generally need a 50 mA bulb. We have these in plastic encapsulations suitable for panel mounting with output leads. Price 40p + 10p. Available in 6v or 12v.

12v. Blower. Complete unit ready to install into car or caravan, etc., size approx 3" diameter by 3" long—made for services so good quality, quiet in operation—low current consumption. Price £2-00 + 16p. Post 40p + 4p.

30 amp D.P. Changeover Switch. These are very heavy duty in solid cast iron boxes sprayed silver and intended for switching from mains to emergency supply or from one transformer or generator to another for maintenance. Hand-operated by lever on the side. Price £9-75 + 22p each, plus carriage £1-50 + 12p. £1-50. Note. These are ex-equipment. Ditto but 60 amp £3-75 + 30p. Carriage £2-00 + 16p.

More Disco Switches. These are similar to the Honeywells, which are regularly stocked, except that they are by a Swiss maker and not new but in good working order, covered by our normal ex-equipment guarantee. Two models available, 2 switch driven by mains-operated motor with gear box giving 20 rpm. Price £2 + 16p. Post 30p + 3p. Other is 12 changeover switch model driven by motor in plastic enclosure of 15 rpm. Price £3-50 + 25p. Post 40p + 4p.

Panel Meter 0-1 mA, full vision flush mounting. Each. Regular price over £3. Our price £2 each plus 10p. Post 15p.

Camping Lights. Two new 12v camping lights have arrived this week. All made up ready to join to your car battery. 2 models—2 1/2" 13w. Price £3-75 + 30p. Post 85p + 7p. And 1 1/2" 8w. Price £2-50 + 24p. Post 75p + 6p.

Tuner Cassette as described in March "Practical Wireless". Please note we can supply the ferrite slab and the ZN 414 IC. Price for these two items £2-25 including post and VAT. Copy of the circuit supplied on request.

Burglar Alarms. More and more burglars seem to be thriving on the properties of people who cannot be bothered to install burglar alarms. We can offer the intruder alarm as described in "Everyday Electronics" September issue. This is a good circuit and not too expensive. Price is £3-83 + 81p. Post 40p + 10p.

Thermally protected motor. American made 1" stack. This revs. at 2400 RPM, suitable for fan or similar application. Special feature is the trip which cuts off the mains should the motor overheat. Price £1-60 + 15p. Post 25p + 2p.

Amplifier in case with speaker, marketed by British Relay. This is in good quality cabinet with back and elliptical speaker. The amplifier is the Newmarket PC 4 module, together with your own control, £4 + £1. Post 40p + 10p.

Teak veneered double cabinet. We believe that this was made from one of the Leak systems. It is 25" x 4 1/2" high x 8" deep made of thick board with sound/vent holes and should be ideal to house amplifier and tuner, or amplifier and one speaker. Very high quality cabinet which would cost £4 or £5 to make today. Price £2 + 60p + 80p + 20p.

Disco Dimmers made by Ultra Electronics, this is a variable controller which can be fitted behind a panel or into a standard switch box and it will control by 1250 watts along your similar non-inductive load. Very special price only £3 + 24p + 30p + 3p.

Disco Black Light Lamp 175 watts—230/240v pear-shaped back out glass which obscures all visible radiation but emits long wave ultra violet (black light). This lamp provides a convenient way of fluorescing a discotheque, club, dance hall, party, etc., and being a direct plug in replacement of a tungsten lamp it is very convenient for temporary usage anywhere. Price £6-50 + 60p. Post 60p + 4p.

Some more Relay bargains. Miniature plug-in type with perspex dust cover 700 ohm 12v DC working. 4 sets of gold-plated changeover contacts 1/2 amps. Normally an expensive relay. Our price £1 + 8p.


Mains Relays 230/240v. AC operated with 10 amp changeover contacts, open type, one screw fixing 3 sets changeover contacts £1 + 8p each.

Three Changeover perspex covers—plug-in types £1-25 + 10p each for same 30p + 2p each. Available with following coil voltages 12v AC. 50v AC 230/240 AC. Also still available the most versatile type 800 relay which, having a double wound coil, is suitable for working off 6, 12 or 24v. DC or mains through series resistor. This has multiple contacts and the price is 40p + 3p each.

Sound Transducer balanced armature type, 800 ohm imp. In capsule, size diameter 1 1/2" by 1 1/2" thick. Useful in digital equipment or for auto monitoring or as a microphone or speaker, good quantities available. Basic price 50p + 4p less our usual quality discounts.

Special Instrument offer is a Russian made Galvo, very sensitive precision instrument, full scale deflection 7-0-7A. This is a bench mounting instrument of extremely high sensitivity (3/2A per division) size approx. 6 1/2" x 2 1/2" x 2". Price £9-50 each + 75p. Post 50p + 4p.

Dolby™ Noise Reducer Kit

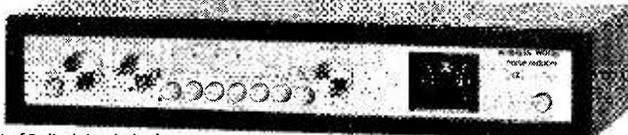

PRICE: £34.40 + VAT

'Wireless World'
May, June, July '75

Trademark of Dolby Laboratories Inc.

The latest addition to our exclusive range of matching high fidelity units.

The Dolby Noise Reduction System is designed to reduce background noise on open reel or cassette tape recorders. Used in the signal path to and from the tape recorder, the unit will encode (Dolbyse) signals during recording, and, during playback, may be used to decode either your own encoded material, or commercially available Dolby encoded cassettes.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

Typical performance

Noise reduction better than 9dB weighted

Clipping level: 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level (typically 0.05% over most of band, rising to a maximum of 0.12%)

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output

Dynamic Range > 90dB

30mV sensitivity

Calibration tapes are available for open-reel use and for cassette (specify which) PRICE £1.80 + VAT*

S-2020TA STEREO TUNER/AMPLIFIER KIT

PRICE: £48.95 + VAT

SOLID MAHOGANY CABINET

A high-quality push-button FM Varicap Stereo Tuner with Intersteram mute combined with 20W r.m.s. per channel Stereo Amplifier.



THD < 0.1% @ 20W
Tuner S/N 30dB @ 1.8µV (mono)
Toroidal Transformer

Please add VAT at 12½% unless marked thus * when 8% applies
We guarantee full after sales technical and servicing facilities on all our kits

Please send SAE for complete lists and specifications
Portwood Industrial Estate, Church Gresley,
Burton-on-Trent, Staffs DE11 9PT
Tel. Burton-on-Trent (0283) 215432. Telex 377106

INTEGREX LTD.

Access
Barclaycard

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% Telephone 6743

QB2	-40	6BA6	-80	6KT7	-85	12E1	8-50	95A3	-80	DF91	-80	PCF88	-65	PZ30	-50	U301	-55	AC168	-44	BF185	-47
OZ4	-55	6RC8	-90	6KR8	-90	12J7GT	-70	35C5	-85	DF96	-80	PCF89	-50	QQV03/10	U403	90	AC175	-54	BF190	-28	
LA3	-60	6BB6	-40	6L1	2-50	12K5	1-50	35D5	-90	DK40	-70	PCCL89	-80	U404	75	AC177	-32	BF761	-23		
1A5GT	-65	6BB6	-70	6L6GC	-70	12K7GT	-50	35L6GT	-80	DK92	1-00	PCF82	-50	Q875/20	U801	-80	AC178	-30	BFY52	-23	
1A7GT	-60	6BJ6	-65	6L7	-60	12K8	-75	35W4	-55	DK96	-70	PCF82	-50	U400	75	AC179	-23	BY100	-21		
1B9GT	-65	6BK7A	-85	6L18	-80	12Q7GT	-50	36Z3	-80	DL96	-65	PCF84	-70	Q895/10	VP23	-65	AC179	-23	BY114	-21	
1H9GT	-59	6BQ7A	-80	6L19	2-00	12R7	-50	36Z4CT	-70	DM70	-80	PCF200/1-00	U400	75	VP41	-90	AC180	-21	BY127	-21	
1L4	-25	6BR7	-100	6LD90	-80	12R8GT	-55	35Z5GT	-80	DM71	1-75	PCF201/1-00	U400	75	VP41	-90	AC181	-23	BY127	-21	
1N6GT	-75	6BR8	1-25	6N7GT	-70	12S7H	-50	42	-1-50	DY87/6	-40	PCF801	-55	QV160/15	U111	1-00	AC182	-13	BY210	-30	
LR5	-50	6BS7	1-70	6Q7G	-60	12S7	-60	43	-1-25	DY802	-45	PCF801	-55	U1120	1-00	AC182	-13	BY211	-30		
LS4	-40	6BW6	1-00	6Q7GT	-60	12S8Q	-60	50B5	1-00	E80CC	2-50	PCF802	-55	U120A	AD140	-42	AC183	-18	BY212	-30	
LU4	-70	6BW7	-85	6Q7(M)	-65	12S8T	-75	90C5	-75	E80CC	2-50	PCF806	-60	R19	75	AD149	-58	BY213	-30		
LV6	-85	6BZ6	-80	6R7G	-70	12H7	-75	60CD6G	-70	E80F	2-50	PCF806	-60	TP2630/1-00	W107	-75	AD162	-53	FBY41A	-26	
2D21	-55	6C4	-40	6S4T	-55	14S7	-1-10	1-20	E80D	2-50	E80F	2-50	PCF806	-60	UABC80-45	W729	1-20	AD114	-30	OA9	-14
2GK5	-75	6C5G	-60	6S7GT	-75	19A05	-65	60H5E	-75	E82C	1-00	PCF806	-60	UAF42	-70	X41	1-00	AD115	-13	OA47	-12
2X2	-70	6C6	-45	6S8T	-60	19G6	6-50	60L6GT	-70	E82E	1-00	PCF806	-60	UBC41	-60	X66	1-60	AD117	-23	OA70	-13
3A4	-55	6C9	2-00	6S8T	-55	20D1	-70	1-00	E182CC	EF89	-35	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
3D6	-40	6C8A	-60	6S17	-60	20F2	-85	85A2	-75	EF91	-50	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
3Q4	-80	6C8DG	1-80	6S7GT	-65	20L1	1-20	85A3	-75	EF188CC	2-50	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
3Q5GT	-70	6C8GA	-90	6S7GT	-60	20P1	1-00	90A9	3-00	EF92	-50	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
3S4	-45	6C8B	-90	6V6G	-80	20P3	1-00	90C1	-85	E1148	-60	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
3V4	-80	6C8LA	-95	6V8GT	-55	20P5	1-00	90CG	2-80	EA50	-40	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
4CB6	-75	6CM7	1-00	6X4	-45	20P5	1-50	150B2	1-00	EA76	1-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5C08	-75	6C05	-90	6X5GT	-60	25A6G	-70	21S8G	-60	EABC80	-60	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5R4GY	1-00	6G04	1-17	7B6	-80	25L6G	-80	807	1-10	EAC91	-55	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5U4G	-60	6D3	-75	7B7	-80	25Y6G	-80	5702	1-20	EAF42	-75	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5V4G	-60	6D7	-90	7H7	-80	25Z4G	-50	5783	1-65	EAP01	-55	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5Y3GT	-55	6D7GA	-85	7Y7	2-00	25Z6G	-75	8067	1-00	EB34	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5Z3	1-00	6E76A	-85	7Y4	-80	25Z6G	-80	8060	1-00	EB91	-20	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5Z4G	-55	6E5	1-00	7Z4	-80	28D7	2-00	6067	1-00	EB41	-75	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
5Z4GT	-55	6F1	-80	9D7	-70	30A5	-75	7193	-60	EB81	-45	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6/30L2	-80	6F6G	-80	10C2	-70	30C15	1-00	90E2	-55	EBF80	-40	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6R3GT	1-40	6F13	-80	10DE7	-80	30C17	1-00	9006	-45	EBF83	-45	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AC7	-55	6F14	-90	10E7	-75	30C15	1-00	AC9N	1-20	EBF83	-45	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AG5	-55	6F15	-75	10F9	-65	30F25	-75	AC9EN	1-20	EBF83	-45	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AH6	-70	6F18	-80	10F13	-65	30FL1	1-10	-80	EC86	-90	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18	
6AJ5	-75	6F23	-80	10LD11	-75	30FL2	1-10	AL60	1-20	EC88	-90	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AK5	-45	6F24	-80	10P13	-80	30FL3	-70	ARP3	-60	EC92	-55	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AK6	-70	6F25	1-00	10P14	2-50	30FL4	1-10	ATP4	-60	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AK5A	-70	6F25	-75	12A6	-85	30L15	-80	AZ1	-60	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AN5	-70	6F32	-70	12AC6	-80	30PL13	1-20	DAF91	-35	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AQ5	-50	6G6G	-80	12AD6	-80	30P4MR	-75	AZ41	-50	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AR5	-80	6G8A	-80	12AE6	-80	30P4MR	-75	B36	-75	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AS7	1-00	6GK5	-75	12AT6	-45	30P12	-80	BL63	2-00	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AT6	-50	6G77	-80	12AU6	-60	30P19/	-75	CL33	1-75	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AU6	-40	6H9GT	-80	12AV6	-80	30P4	-90	CT1C	1-00	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AV6	-50	6J5GT	-50	12BA6	-50	30PL1	-95	CT31	-70	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AW8A	-90	6J6	-35	12BB6	-55	30PL13	1-20	DAF91	-35	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6AX4	-75	6J7G	-85	12BH7	-55	30PL14	1-30	DAF96	-60	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18
6BR6	-35	6J8A	-90	12B77	-85	30PL15	0-90	DD90	-60	EC93	-30	PCF806	-60	UBC81	-60	Z759	5-85	AD121	-35	OA73	-18

VALVES ALSO REQUIRED TO PURCHASE. LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.

All goods are unused, tested, and guaranteed. Despatch charges:—25p on all orders below £10 in value. Orders over £10 post free. Orders despatched same day as received. Any parcel insured against damage in transit for 5p per parcel extra. Terms of business available on request. Many others in stock too numerous to list. Please enclose S.A.E. for reply to any correspondence.

RETURN OF POST MAIL-ORDER SERVICE

JUST RELEASED

R.C.S. 100 watt VALVE AMPLIFIER



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A. where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier.
Suitable carrying cabinet £14. Price **£85** carr. £2.50

ANOTHER R.S.C. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.

Price **£3.25** Post 40p



8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts.

£3.95

10in round **£4.95.**

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in.
For 12 in. dia. or **£11.25** Post 10in. speaker.

MODEL "B". 16 x 10 x 9in.
For 13 x 8in. or **£6.95** Post 8 in. speaker

MODEL "C". 20 x 20 x 12in.
Reflex cabinet will accept 1-12in. bass unit, 1-5in. mid range, 1-3in. tweeter. Teak finish. Grooved front
£21.50 Carr. £3

LOUDSPEAKER CABINET
WADDING 18in. wide, 25p ft.



GOODMANS CONE TWEETER

3 1/2in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3.25**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and turner with separate controls into single output. volt **£5.20** battery operated.

STEREO VERSION OF ABOVE **£6.85.**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply **£3.95**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. **£3.95** Post 40p

WAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in many quantities). Approx. size 10 1/2 x 8 1/2 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboard. Ideal for anti-frost device for the garage—preventing frozen radiators or setting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR **£1.50**)
ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £10.35



Post 60p
30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£13**

Please state 3 or 8 or 15 ohms. Post 50p

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic Power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25"

12in 30 watt
3, 8 or 15 ohms.

£8.95

Post 50p

GROUP "35"

12in 40 watt
3, 8 or 15 ohms.

£10.50

Post 50p

GROUP "50/12"

12in 60 watt professional model. 8 ohms or 15 ohms.

£14.50

Post 80p

GROUP "50/15"

12in 75 watt
8 or 15 ohms.

£19.50

post 90p

MAJOR 50 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All Purpose transistorised.

Ideal for Groups, Disco and P.A. 4 inputs speech and music. 2-way mixing. Output 8/15 ohm A.C. mains. Separate treble and bass controls. Guaranteed. Details S.A.E.

£49 Carr. £1.00



Latest 100 watt Model as illustrated **£68**

100 WATT DISCO AMPLIFIER CHASSIS

MADE BY JENNINGS MUSICAL INSTRUMENTS


4 speaker outputs, vol., treble, bass controls

£52

CAN BE USED AS 100WATT SLAVE

QUALITY LOUDSPEAKER ENCLOSURE

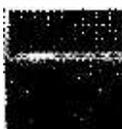Teak veneered 3/4in thick wood cabinet. Size 18in x 18 1/2in x 8 1/2in. Weight 28lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6in Woofer. £7.50. Carr. 85p. Rosewood Version £8.50. Carr. 85p. Baffle could be cut for larger speaker.



P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watt each. As featured in December Practical Wireless. Price **£12.50** Cabinet extra £3.

8 inch PHILIPS LOUDSPEAKER

4 ohm. 4 watt. ceramic magnet **£1.95**

MAINS TRANSFORMERS

6 VOLT 1/2 AMP. £1.00 3 AMP. £1.40
12 VOLT 300 MA. £1.00 750 MA. £1.30
18 VOLT 1/2 AMP. £1.00 2 AMP. £2.00
20 VOLT 1/2 AMP. £1.75 1 AMP. £2.00 3AMP. £3.20

E.M.I. TAPE MOTOR

4 pole, 240 v. Size 3 1/2 x 2 1/2in. 1200 rpm. Spindle 1/4in. diameter. 120v version 75p. **£1.85** Post 45p



E.M.I. GRAM MOTOR

240V a.c. 2,400 rpm 2-pole. Size 2 1/2 x 2 1/2in. **£1.25** Post 35p

BAKER DISCO SPEAKERS HIGH QUALITY—BRITISH MADE

2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners Black finish. Other cabinets in stock.

50 WATT R.M.S. £43

70 WATT R.M.S. £46

100 WATT R.M.S. £55



1 x 15" + 1 x 12" 100 WATT CABINET
Size 36" x 24" x 15" **£63.50.**

Ideal for Disco or PA work. High quality.

SUPERB HI-FI

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cones resulting in full range reproduction with remarkable efficiency in the upper register.
Bass Resonance 85cps
Flux Density 16,500 gauss
Useful response 30-17,000cps
8 or 15 ohms models.

£15.50 Post 80p



AUDITORIUM

12in. 35 watts

A full range reproducer for high power, Electric Guitars, Public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-18,000cps
8 or 15 ohms models.

£15.50 Post 80p



AUDITORIUM

15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£19.50 Post 90p



Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 65p

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Open 9—6 Wed. 9—1 Sat. 9—5 (Closed for lunch 1.15—2.30)
Cash price includes VAT Access & Barclay cards welcome. Rail Selhurst. Tel. 01-684 1665

Minimum post 30p. Components Lists 10p. *Practical Wireless, July 1976*


ANNOUNCEMENT

RHYTHM GENERATOR™

SWING, WALTZ, ROCK, TANGO, CHA CHA, MARCH, MAMBA, FOX TROT, SHUFFLE.

ALL COMPONENT PARTS ARE AVAILABLE SEPARATELY S.A.E. FOR LISTS, OR FOR PRICING.

Tel. 0246-31475

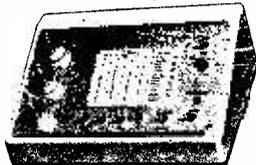

FULL KIT: £39.90 + £1.00 (Includes V.A.T.)

KIT INCLUDES NEW UPDATED P.C.B.'s

With Printed layout for easy assembly, all components "nice" switches and knobs, case, in fact everything you need to complete this very exciting Project.

P.C.B.'s ARE AVAILABLE SEPARATELY.

Set of NEW UPDATED P.C.B.'s with a printed layout, made in first class quality fibre-glass, by a well known national company.

Price on application to:

ASTRO-W.K.F. Inc.
1 QUEEN STREET NORTH
WHITTINGTON MOOR,
CHESTERFIELD,
DERBYSHIRE
Tel: 0246-31475



SPECIAL OFFER

CRESCENT RADIO LTD.

164-166 HIGH ROAD, LONDON N22 6EJ
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ Phone 888-4474

CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.
ME6 = 0 to 50 micro amp Full Scale
ME7 = 0 to 100 micro amp Full Scale
ME8 = 0 to 500 micro amp Full Scale
ME9 = 0 to 1 m/a Full Scale
ME10 = 0 to 5 m/a Full Scale
ME11 = 0 to 10 m/a Full Scale
ME12 = 0 to 50 m/a Full Scale
ME13 = 0 to 100 m/a Full Scale
ME14 = 0 to 500 m/a Full Scale
ME15 = 0 to 1 amp Full Scale
ME16 = 0 to 50 volts
ME17 = 0 to 300 volts
A.C. Full Scale
ME18 = "S" Meter
ME19 = "VU" Meter



OUR PRICE £3.00 + 8%

WAFFER SWITCHES

1 Pole 12 Way
2 Pole 2 Way
2 Pole 3 Way
2 Pole 4 Way
2 Pole 6 Way
3 Pole 4 Way
4 Pole 3 Way




30p each + 8%

CRESCENT BUBBLE LIGHT SHOW

This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—150W convection cooled. At 30ft the projected image is 18ft.
Motor—1 rev. per 2 min.
Liquid Wheel—8in. diameter multi colour.
Our Price £28 + 8%

BARGAIN PROJECT BOX.

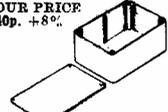A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied). An ideal box to give a small project a professional finish SIZE (Internal) 81mm x 110mm x 28mm
OUR PRICE 40p. + 8%



ANTEX SOLDERING IRONS & SPARES

X25 25 watt £2.99
X25 Spare Element £1.47
X25 Spare Bits No. 50, 51, 52 44p each
C240/2 15 watt £2.99
C240/2 Spare Element £1.20
C240/2 Spare Bits No. 2, 3, 6 32p each
ST3, Soldering Iron Stand suitable for all models £1.10
Plus 8% VAT

POWER SUPPLY UNITS + 8%



PFL switched 3, 4, 6, 7, 9 and 12 volts at 500 m/a, with on/off switch and pilot light. Size: 180mm x 56mm x 75mm.
ONLY £4.50

CABLELESS SOLDERING IRON WAHL. "ISO-TIP", 8%

★ Completely Portable
★ Heats in 5 seconds
★ Solders up to 150 joints or more per charge
★ Recharges automatically in its own stand
★ No AC leakage or induced current to damage delicate components.
★ Heats to 700 deg. F
★ Fine Tip for delicate and general purpose soldering
★ Only 8" long and weighs just 6 ozs.
OUR PRICE £9.75 + 8% (spare bits are available)

FERRIC CHLORIDE

Anderson ferric chloride in double sealed one pound poly packs. Our Price 55p + P.P. + V.A.T @ 8% per lb.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel Base, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 75p P. & P. + 8%



BARGAIN TRANSFORMERS 12-0-12 volt 500m/a

240 volt primary transformer bargain. approx size 60mm x 40mm x 50mm fixing centres 75mm
Our Price £1.20 + 8%

ABS PLASTIC BOXES + 8%

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.
1005 = 105mm x 73mm x 45mm = 55p
1006 = 150mm x 75mm x 47mm = 78p
1007 = 184mm x 124mm x 60mm = £1.28
1021 = 106mm x 74mm x 46mm (slipping front) = 55p

GOODMANS CROSSOVER

Bargain Price Crossovers manufactured by Goodmans for the "Havant" Loudspeaker System. 3 way, 8 ohm. £1 each + 12 1/2% VAT.

LOW NOISE LOW PRICE CASSETTES + 8%

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C90 = 35p C90 = 45p C120 = 60p
10% Discount on ten or more cassettes of one type

LOUDSPEAKERS + 12 1/2%

2 1/2" 8 ohm 60p
2 1/2" 40 ohm 60p
2 1/2" 80 ohm 60p
5" 8 ohm ceramic £1.25



10-INCH 8 OHM DUAL CONE
Manufactured by "ELAC" to a very high standard these loudspeakers are a real bargain.
SPEC:—Size = 10" Dual Cone.
Power = 10 Watts
Frequency = 40-12000Hz
+ 12 1/2% Our Price = £3.75p each

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED
VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

Dept. No. 777V, Intertext House, LONDON SW8 4UJ or telephone 622 9911

Subject of Interest.....
Name.....
Address.....

Tel:.....

ALL PRICES INCLUDE V.A.T.



PERSONAL CALLERS ARE WELCOME!

all items subject to manufacturers increase and availability



High Quality Construction Kits, stocked at all branches Send for catalogue!

AMPLIFIERS P&P 95p Ins. £1
 Sansul AU2200 £53.75
 AU4400 £87.75
 Pioneer SA5300 £56.70

RECORD DECKS P&P 85p Ins. 50p
 Garrard SP25 Mk. IV £20.70
 Garrard SP25 Mk. IV/G800 £33.20
 Plinth & Cover
 BSR MP80 £15.30
 Connosseur BD1 Kit £14.90
 BD2 Chassis/SAU2 £38.40
 SAU2 Pick-up Arm £16.03
 SCU1 Cartridge £6.70
 Pioneer PL12D £49.50
 Plinth-cover for Garrard or BSR £4.77

SPEAKERS P&P 45p
 EMI 13" x 8", 3, 8 ohm plain 8" x 5" C. Mag. 5 watt 8 or 15 ohm £2.35
 8" x 5" Dualcone 8 ohm, 10 watt £3.70
 Etac 6 1/2" 8 ohm Dualcone £2.75
 8" 8 ohm Dualcone £3.05
 Baker Group 25 12", 8 or 15 ohm £13.50
 Goodmans 8" x 5" 8 ohm £11.90
 Global 8 ohm 5 watt (pair) £8.95
 Richard Allan 12" 50 watt 8 or 15 ohm £12.95
 Richard Allan 12" Dualcone £13.95

WHARFEDALE SPEAKER BARGAINS
 P&P 85p Ins. 50p
 Chevin (pair) £28.80
 Danton 2 (pair) £38.25
 Linton 3 (pair) £53.55
 Linton 2 (kits) £23.56

KIT FORM CABINETS
 Teak Veneer P&P 85p Ins. 50p
 12" x 8" x 4 1/2" (8 x 5 or 7 x 4 cutout) £3.34
 12" x 12" x 7 1/2" (10" 8 x 5, 8", 6 1/2" and 3 1/2") £4.75
 18" x 11" x 7 1/2" (8" x 3 1/2" or 13 x 8) £5.94
 22" x 14" x 7 1/2" (12" x 3 1/2" or 13 x 8) £7.18

TWEETERS & CROSSOVERS
 P&P 25p
 Cone Tweeter 8 or 15 ohm, 10 watt £3.30
 Cone Tweeter 8 ohm, 3 watt £1.75
 Horn Tweeter 8 ohm, 20 watt £7.85
 Dome Tweeter 8 ohm, 30 watt £6.40
 Crossovers CN23 (3 ohm) CN28 (8 ohm), CN126 (16 ohm) £1.57

CARTRIDGES & STYLII
 P&P 25p Cart. D.D. StylII
 Acos GP91/25C or 35C (4 for comp) £1.60 £1.20
 GP93/1 or 95/1 ster. cryst £2.00 £1.20
 GP94/1 or 96/1 ster. cryst £2.00 £1.20
 GP101 ster. comp. £1.00 —
 GP104 ster. ceram. £2.15 £1.20
 BSR X6M or H6X cryst. comp. £1.65 £1.20
 SX6M or SX6H cryst. ster. £2.25 £1.20

SC5M ster. ceram. £2.75 £1.20
 Sonotone 9TAHC or 9TAHC G (1 pair) £2.25 £1.20
 3509 ster. ceram. £2.25 £1.20
 Audio Technica AT55 £2.25 —
 Empire 999 REX £4.95 —
 Goldring G850 £3.50 £1.75
 G800 £5.25 £1.75
 G800H £5.25 £1.75
 G800E £9.00 £3.50
 Shure Cartr & StylII
 M44G £5.56 £4.45
 M65E £7.03 £5.56
 M75ED Type 2 £63.21 £9.30
 M75EJ Type 2 £10.96 £7.03

MICROPHONES P&P 25p
 CM70 Planet stick metal, switch crystal £2.12
 DM160 Dynamic omnl-dir. ball metal £5.56
 UD130 50K 600 ohm, uni-dir. ball metal £6.60
 CONDENSER MIKE 600 ohm, uni-dir. £9.56
 Cassette STICK MIKE with R Control on/off switch (2-5 & 3-5 mm) J/Ply £1.56
 Cassette STICK MIKE with R/Control (Phillips Type) £1.93
 UD 147 £10.40

BATTERY ELIMINATORS
 P&P 25p
 240v Input 8, 7-5 or 8 volt output £2.55
 12v d.c. Input (specify output 6, 7-5 or 9 d.c.) at 300mA £4.20

CASSETTES P&P 25p

Type	Low noise	Phillips	Memor
C80	37p	59p	81p
C90	48p	81p	£1.18
C120	59p	£1.18	£1.67

CASSETTE CASES £0.13
 Cassette Head Cleaner £0.48
 Bib Stereo Test Cassette £2.32
 AMPEX Head Cleaner Demag £1.99

TAPES P&P 25p

5"	Std.	LP	DP	Cases
5"	59p	70p	£1.08	32p
5 1/2"	70p	82p	—	38p
7"	92p	£1.19	£1.99	43p

SINCLAIR PROJECT 80 P&P 25p
 Stereo Pre-amp £14.50
 Z80 25 watt Amp. £8.15
 P25 Power Supply for 240 £6.13
 P28 Power Supply for 240 £9.50
 P28 Power Supply for 260 £9.75
 FM Tuner £14.50
 C10 Speaker £8.40
 IC20 stereo amp. kit £8.40
 PZ20 Power kit £5.90

Send 25p for complete catalogue.


PLEASE BRING THIS ADVERTISEMENT TO OBTAIN THE BENEFIT OF THESE SPECIAL PRICES

ALL MERCHANDISE FULLY GUARANTEED

NEWMART ELECTRONICS

Mail Order Dept PW7
 Belmont St, Monton,
 Eccles, Manchester.
 Tel: 061-789 5268

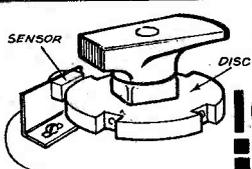Manchester
 30-32 Shudehill. tel 061-832 7710
 Leeds
 4 New Market St tel 0532 42708
 Liverpool
 15 Whitechapel tel 051-236 0738



Capacitor Discharge IGNITION
 ■ MAXIMUM PERFORMANCE
 ■ MAXIMUM ECONOMY
 ■ EASY COLD START

SYSTEM I
 Professional photoelectric ignition using L.E.D. light source and reflective disc. This machined aluminium disc gives a timing accuracy far superior to other methods and is simple to fit. Unit housed in diecast box 4 1/2" x 3 3/4" x 2 1/4" Price £18.80 (Kit £16.80) State car/model/manufacturer across cam lobes.

SYSTEM II
 Contact breaker model as above less sensor. Price £12.80 (Kit £10.80) M/C Twin unit Price £15.00. S.A.E. for descriptive leaflet - ALL UNITS IN STOCK. Mail orders to CDI Electronic Systems Ltd, 275 Vale Road, Ash Vale, Aldershot, Hants. Demonstration/Callers to Hillside Motors, 292 Carshalton Road, Carshalton, Surrey, telephone 01-642 9973.

VALVE BARGAINS

Any 5-64p, 10-£1.10, 50-£5. Your choice from the following list:
 ECH84, ECC82, ECL80, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14, 6F28
 Colour Valves 30p each PL508, PL509, PY500/A.

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set fitting, with Co-ax Plugs and Sockets.
 B11—For Stereo and Standard VHF Radio.
 B12—For the older VHF Television, please state BBC1 and ITV Channels.
 B45—For mon. or colour this covers the complete UHF band.
 All Boosters are complete with Battery and take only minutes to fit. Price £3.60 each.

POLYESTER CAPACITORS 250v/w

Price 25p per pack of five: 01uF, .022uF, .047uF, .1uF, .22uF, .47uF.
 Prices include V.A.T. P. & P. under £1.15p, £1 to £3.20p above £3.30p. Overseas at cost. Money back guarantee on all orders.

ELECTRONIC MAILORDER LTD.,
 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCs. Tel. Rams. 3036

100s TRANSFORMERS in stock. Send SAE and enquiry for quote. NEW TRANSFORMERS 25-0-25 1 amp £1.40 pp 30p/24 volt 2.5 amp £2.95 pp 60p/6-3y 600 MA + 6-3 volt 6 amp + 230-0-230 260MA screened C core construction £4.32 pp £1.20. Unregulated but smoothed and rectified power supplies in aluminium box 6" x 9" x 2 1/2" and 240v set 0-6-3 1A 21v CT 21v CT 30v CT 1A £3.95 each pp 70p. OC35-20p Inc pp/Trilacs full spec 2N5574 15A-400V £1.30 inc pp. 5 lb POTENTIOMETER PARCEL approx 25 various types all new approx 70 pots in all £2.18p pp 80p (once only offer don't miss it). MULLARD PL81 valves new boxed 75p each inc pp. CROUZET MOTORS 50v, 110v, 230v from 1-30rpm £2.75 each pp 20p. State volts and speed required. FERRITE ROD AERIALS 5 mixed sizes £1.00 pp 20p. FERRIC CHLORIDE 11b bag 54p pp 30p. Our new 20lb bargain parcel (Fantastic bargain) this may be the last one £5.00 inc. pp (No rubbish). So hurry and order now. HEAT RESIST SLEEVING various sizes 10 meters for £1.00 pp 20p. COMPUTER TAPE on spools 1" £1.30 each pp 70p. New G.P.O. RELAY UNITS contain 20 PO type 3000 relays all modern gear not rubbish. £5.40 each pp £1.60. CAPACITORS RESISTORS over 600 items all new components £0.70p pp 30p. COLVERN W/W pots various values in stock 32p each pp 20p. SWITCHES biased DP/CO 48p inc pp 5p/Pole biased 38p inc pp. Chassis new with 2 output transformers, caps, resistors, pots all low tolerance £1.00 each pp 70p. SPEAKERS Goodmans 8" x 4" elliptical 4 watts £1.20 each pp 30p. METERS Taylor edgewise 50 uA FSD £1.00 each pp 20p/TAYLOR edgewise small 50 uA-0-50 uA movement no numerals 1" x 2 1/2" £1.00 pp 20p. VIDEO TAPE once used 1" only £3.50 each pp 70p. PYE 625 B/W 25" monitors tested working £35.00 each. Few only left, delivery by arrangement. RADYNE 10kw C90 Induction heater. New oscillator valve unused since purchased £1,300.00 (SAE details). COUNTERS resettable 6 digit 120v only £3.75 pp 75p. 10lb mixed bag nuts, bolts odds/ends £1.00 pp 50p. 24V RELAYS 2 P/CO 60p, 3 P/CO 75p, 4 P/CO 95p pp 20p. ULTRASONIC GENERATORS by Elliot 1-25kva output 250vac these are new units and are offered at a fraction of original cost, and are brand new units price £150.00 each + V.A.T. + delivery. GRUNDIG DICTATING MACHINES new units untested but damaged at £5.40 each pp £1.00 its worth it just for the parts. GEARED MOTOR UNITS new 12 volts operates 3 micro switches. Final drive approx 4 rpm. Very powerful all in a neat flip top box £2.16 ea. pp 70p. PAPER CAPS 2uF 600V DC 30p pp 20p. PCB etch resist ink 6oz £1.30 pp 20p. 10 various PCB Panels £1.50 pp 40p. THYRISTORS BT119 Gold bonded 10A 400V 95p inc pp. CAPACITORS 15uF 63v reversible. 18p pp 12p. PLASTIC STRIP CONNECTORS 5 amp 10 for £1.00 pp 20p. LA7 POT CORES on panel (easy to dismantle) 60p inc pp. FANS 230V 3 1/2" blade. Small motor £1.40 ea pp 30p. RESISTANCE WIRE STABLOHM 43/38 swg/21-550 per to 2-5 oz reel £1.75 pp 30p. Other various sizes in stock in small quantities. VEROBOARO 1 1/8" x 4 1/2" £1.88 inc pp. FLUORESCENT QUICK START BALLAST UNITS inc P/F correction capacitor leads, tubes, ends etc. Just fit 4' 40 watt tube to make it work only £1.75 ea. pp £1.00. THYRISTORS PLASTIC type C106B1 60p inc pp. (SAE) for quantity discounts. (UK only). All overseas enquiries (SAE) for prices plus postal charges.

INDUSTRIAL RF SERVICES

692, 4284 51 Deptford Broadway London SE8 4PH.

We buy and sell all types of surplus and new electronic equipment/components and machines.

FULL SPEC. LED'S

Packs of 5—Inc clips & data

	-125" lens	-16" lens	-2" lens
RED	£0.75	£0.75	£0.75
GREEN	£1.20	£1.20	£1.20
YELLOW	£1.20	£1.20	£1.20
ORANGE	£1.20	£1.20	£1.20

ECONOMY QUALITY LED'S

MIXED BAGS ALL COLOURS OF ALL SIZES—
IDEAL FOR EXPERIMENTS

50—£5
100—£9

FULL SPEC LED

SEVEN SEGMENT DISPLAYS

0.8" COMMON ANODE
L.H. DECIMAL
RED, GREEN, YELLOW
£1.85 ea Inc data



ECONOMY QUALITY

0.8" COMMON ANODE—L.H. Dec. REL1 73p ea.

PLASTIC BOXES— COLOUR GREY



ABS—Ribbed inside on 5mm centres for 1.6mm PCB. Brass Corner Inserts for securing top with 3mm screws. 62mm x 112mm x 31mm 1-9 55p ea; 10+ 49p; 120mm x 65mm x 40mm 1-9 66p ea; 10+ 62p ea; 150mm x 80mm x 50mm 1-9 75p ea; 10+ 71p ea.

POLYSTYRENE—PLAIN INSIDE—TOP SECURED BY SELF TAPPING SCREWS
61mm x 112mm x 31mm 1-9 85p ea, 10+ 32p ea.

SPECIAL OFFER

SAMPLE PACK—4 BOXES—1 ea size £2.10
P. & P. 25p per £1—minimum 25p.

NEON INDICATORS

150mm lead out wires

TYPES

AA AH AG



Fit 5mm hole and include spire clip for fixing
RED, AMBER, CLEAR, OPAL —19p ea
GREEN —28p ea

TYPE MP

Fits 6.4mm hole—nut fixing
RED, AMBER, CLEAR, OPAL —22p ea

LAMPOLDER DH



Takes either LES (with adaptor provided) or MIDGET FLANGE BULBS.


Fits 13mm hole—nut fixing
RED, BLUE, GREEN, AMBER, CLEAR, OPAL,
ORANGE 25p ea (bulbs not provided)

QUOTATIONS FOR LARGER QUANTITIES ON REQUEST. ALL PRICES INCLUDE VAT AT 8%. ORDERS UNDER £10 please add 20p P.P. ORDERS FOR BOXES P.P. 25p per £1—Min. 25p to Max. £1.50 TERMS C.W.O.

MICHAEL WILLIAMS ELECTRONICS

47 Vicarage Avenue,
Cheadle Hulme, Cheshire SK8 7JP

INTER-LOCKING PLASTIC STORAGE DRAWERS

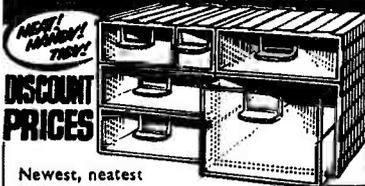

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

AS SUPPLIED TO POST OFFICE,
INDUSTRY & GOVERNMENT DEPTS.

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins) £2.40 DOZEN.
DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins) £4.20 DOZEN.
TREBLE (3D) £4.20 for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £5.90 for 8.
EXTRA LARGE SIZE (6D1) £5.40 for 8.
PLUS QUANTITY DISCOUNTS!

Orders over £20, less 5%.
Orders over £60, less 7½%.
PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

FLAIRLINE SUPPLIES

(Dept PW7)

124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

GREENWAY

Radial Lead Polyesters I.T.W. *10% 100V D.C. .001 3p; .0022 3p; .0047 3p; .0063 3p; .01 3p; .015 .035p; .022 .035p; .033 .04p; .047 .04p; .063 .07p; .082 .08p; .15 .09p; .22 .065p; .33 .075p; .47 .095p. *Radial Polycarbonate 630V D.C. .33 .25p; .47 .25p; .68 .30p; 1mf; 400V .35p. *Axial Lead Polyesters 10% 200V D.C. I.T.W. .01 15p; .022 .15p; .047 .17p; 1mf; 20p. *Dipped Tantalum Capacitors (Bead type) values: 1; .15; .22; .33; .47; 1; 1.5; 2.2; 3.3; 35V 10p each. 4.7; 6.8; 10mf; 25V 11p. 4.7-10mf 10V 10p; 15; 22 16V 12p; 33 10V 12p; 47 6V; 68 3V; 100 3V 14p. Ceramic Capacitors 5mm Radial 250V 50-1800pf & *Polystyrene 63V-160V 100p-15000pf. Axial prices: 5-390 .035 each; 470-1000 .04; 1200-1800 .045; 2200-4700 .05; 4701-10,000 .06; 10,000-18,000 .07p. *Electrolytic Capacitors (axial) 1000-40V 25p; 470-16V 15p; 220-25V 12p; 100-25V 6p; 47-25V 5p; 47-10V 5p; 22-40V 5p; 10-25V 5p; 4.7 63V 5p; 2.2-63V 5p; 1mf 63V 5p. *(radial) 2200 (Tag) 40V .50p each; 1000-16V 25p; 470-25V 19p; 220-25V 12p; 100-25V 6p; 47-16V 5p; 33-16V 5p; 10-16V 4p; 5mf 16V 4p; 4.7 16V 4p. *Carbon Film Resistors ¼ Watt RD1 3 ½% (70%) .015p each—90p per 10 15-100 (M2-10M 10%). Special pack 20 popular values quarter watt—5 of each 90p. Semiconductor BC107/8/9 .09p; *BC147/8/9 10p; *BC157/8/9 9p; BCY70/1/2 17p; BFY51 19p; SCR C106D/2PM-400V 50p each; TIP29A .47p; TIP31A .57p; TIP32A .67p; TIP3055 .48p; BU208 £2.00; Integrated Circuits 741 8 Pin D11 25p; 723 (TO9) 57p; LM309K (TO3) 1.48p; NE555V 60p; NE556V 1.12p; *I/C Sockets (Gold) 8/14/16 15p; (Tin) 8/14/16 14p. Zener Diodes 400 MW 9p; 1 Watt 17p (standard voltages); Diodes 1N4148 .05p; BAX16 .05p; Rectifiers 1A 1N4001 5p; 1N4002 .06p; 1N4003 .07p; 1N4004 .08p; 3 Amp 3A05 (50V) 10p; 3A10 (100V) 11p. Terminals C.W.O. V.A.T. (*) add 12½% others 8%. P & P 25p on all orders under £3. SPECIAL OFFER: *A.C. Capacitors 16mf 500A C. £1.50 plus .42 p & p; Mains Toroidal Transformer 20V 500M.A. £1.90 plus .42 p & p.

GREENWAY ELECTRONIC COMPONENTS (EAST GRINSTEAD) LTD.

62 Maypole Road, Ashurst Wood
East Grinstead, Sussex RH19 3RB
Service: Tel Forest Row 3782 (STD 034-282)

Wire Wound Resistors. Our selection of mixed values. 30 for £1.40. 100 for £3.50.

Audio Amplifier Module. Mullard LP1173. Output nominal 10 watt. Supply voltage +24vt. With data and circuit. £2.30.

Varicap Control Selector. 4 way 25K. £1.50. 6 way 14.5K. £2.00.

Mains Droppers. 10 mixed values £1.00.

Edgewise Level Meters. 200µA. Size ½" overall 50p.

15 Assorted Switches. Micro, push button, etc. £1.90.

Tag Strips. 3 way to 7 way. 50 for £1.15.

Chrome Plastic Knobs. 3 Types 4 off each with spring clip. £1.25.

Ferguson Stereogram Chassis. Model 3357. All transistor. Med/LW. FM. 3 watts per channel S/M. With connection data. Less tuning scale. £18.00. P/P free.

Ferguson Stereogram Chassis. MW. LW. FM. With tuning scale (5+5 watts sine wave) 15 ohms £26.25. P/P free.

Copper Clad Laminate. 8" x 7"—3 boards £1.00 + 8%.

Ferric Chloride. 1lb 65p + 8%.

Crystals HC6U. (MHz) 12700; 12891.6; 9455.55; 9530.55; 9087.5; 9456.25; 52-01667; 52-02500; 37-7625; 51-56667; 52-03333; 9090.62; 9531.94; 9533.33, 50p each.

Transfilter. 455KC. A.M. 5 for £1.00.

Electrolytics. 32/32/32µF, 325v. 2" x 1½" 35p; 80µF 150V 1½" x 1" 20p; 2000µF 30v, 2½" x 1" 25p; 2000µF 35v 3" x 1" 30p; 470µF 100v 3" x 1½" 25p; 2000/2000µF 25v 2" x 1½" 35p; 700µF 200v 3½" x 1½" 30p; 16/16µF 275v 1½" x 1" 20p; 4500/900/900µF 30v 2½" x 1½" 50p; 2500µF 40v 3" x 1½" 40p; 470µF 25v 1½" x 1½" 15p; 4000µF 25v 3" x 1½" 40p; 32µF 450v 1½" x 1" 30p; 8µF 16µF 450v 1½" x 1½" 30p; 1000µF 12v 1½" x 1½" 15p 5000µF 50v 2" x 1½" 50p; 150/200/200µF 300v 3" x 1½" 50p; 16/16/16µF 350v 2" x 1" 30p; 50/50µF 500v 3½" x 1½" 50p; 400µF 40v 1½" x 1½" 20p.

Try our parcel of small capacitors 20 mixed values £1.50 + post.

Miniature Presets—Selection of various values 10 for 65p.

Coil Formers. 50 mixed. £1.25.

Slider Volume Controls. 1K Lin; 100K Log; 1 Meg Log; 25K Lin; 25K Log; 10K/100K Log; 100K/100K Log; 50K Log, 35p each.

U.H.F. 625. Transistor push button tuner (NSF Telefunken), as used on Decca MS2400. Brand new and boxed. Circuit diagram supplied. £3.00.

Thorn T.V. 1F. Chassis 950 Series (less valves) £1.60.

Aluminium Chassis. 7½" x 5½" x 2½" 65p. 10" x 7½" x 2½" 75p. 11" x 7½" x 2½" 85p. + 8%.

Thorn TA/28. Slide synchroniser for 4 track reel to reel recorders. 6 pin DIN socket models. £4.50.

Please add 10% P/P. Unless stated free P/P. VAT 12½% to be added to total order unless stated 8%. No goods despatched outside U.K.

BSR Single Play Decks with Cue-Fitted stereo cartridge. P146 £11.00. P153 £12.00.

SURPLECTRONICS

216 LEAGRAVE ROAD,
LUTON, LU3 1JD, BEDS.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 14p per word (minimum 12 words), box number 35p extra. Semi-displayed setting £12.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the GMG Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Room 2337, King's Reach Tower, Stamford Street, London SE1 9LS, for insertion in the next available issue. (01-261 5846).

Receivers and Components

TRIACS (Plastic) TAG250 400V/10A 67p (3+64p); Diacs 19p, 8-pin di ICs 741 24p, 555 44p, Mini Mains Transformers 100mA 6.0-6V 85p, 12-0-12V 95p, 2N3055 36p, 300W Dimmer Kit £1.95. P&P 15p. Add 8% VAT. T. K. Electronics, 106 Studley Grange Road, London W7 2LX.

VALVES

Radio-TV Industrial Transmitting 2200 Types, 1930 to 1975, many obsolete. List 20p. S.A.E. for quotation. Postal export service. We wish to purchase all types of new and stocked valves. Wholesaler's, Dealer's, etc., stocks purchased.

COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. West Wittering 2023

BRAND NEW COMPONENTS BY RETURN. Electrolytics 16V, 25V, 50V-0.47-1.0, 2.2, 4.7, 10mfd.-5p, 22, 47-52p (50V-6p); 100-7p. (50V-8p), 220-8p. (50V-10p), 500-11p. (50V-16p), 1000-25V-18p. Subminiature bead-type tantalums, 0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/25V-11p, 10/25V, 22/16V, 47/6V, 100/3p-12p. Mylar Film 100V, 0.001, 0.002, 0.005-3p, 0.01, 0.02-3.2p, 0.04, 0.05-4p. Mullard C280 series miniature polyester vertical mounting E6 series 0.01-0.1-4p, 0.15, 0.22-5p, 0.33, 0.47-8p, 1.0-15p, 1.5-20p, 2.2-24p. Mullard miniature ceramics 63V, 2%, E12 series 1.8 pf.-47 pf.-3p, 56 pf.-330 pf.-3.2p. Plate ceramics 50V E12 series 22 pf.-1000 pf. E6 series 1500 pf.-47000 pf.-2p. Polystyrene 63V E12 series 10 pf.-1000 pf.-3p, 1200 pf.-10000 pf.-4p. Miniature Highstab carbon film resistors 3W E12 series 5% (10% over 1M Ω) 1 Ω -10M Ω -1p. 1N4148-3p, 1N4002-5p, 1N4006-7p, 1N4007-8p. Postage 10p. Prices VAT inclusive. The C. R. Supply Co., 127, Chesterfield Rd., Sheffield S8.

VINTAGE RADIO

1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet. Full 1976 catalogue, 50p post paid.

TUDOR REES (Vintage Services), 64, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 565472.

500 COMPONENTS. Resistors, capacitors, diodes, transistors, pots, coils, etc. Identified, formed leads, fall-out, and surplus. Good value at £1.60. All inclusive (U.K. postal rates only). CWO please to L. Pensney, PW Bankhead Farm, South Queensferry, West Lothian.

COMMUNICATIONS RECEIVER modules. Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11.50. SAE details. PR Gollidge Electronics, Millend, Stonehouse, Glos.

Precision Polycarbonate Capacitors

All High Stability—extremely Low Leakage			Very DO RANGE		
440V AC RATED Value (μ F)	Dimen- sions (mm) each: L D	Price	Value(μ F) $\pm 1\%$	$\pm 2\%$	$\pm 3\%$
0.1 μ F	27 12.7	68p	0.01-0.2	£1.28	75p 50p
0.16 μ F	27 12.7	89p	0.22-0.47	£1.32	77p 51p
0.22 μ F	33 16	85p	1.0 μ F	£1.74	£1.56 67p
0.25 μ F	33 18	88p	2.2 μ F	£1.98	£1.88 75p
0.33 μ F	33 18	99p	3.3 μ F	£2.48	£1.60 99p
0.47 μ F	33 19	£1.10	4.7 μ F	£2.82	£1.88 £1.23
0.5 μ F	33 19	£1.16	6.8 μ F	£3.48	£2.82 £1.47
0.68 μ F	50.8 19	£1.25	10 μ F	£4.98	£3.32 £2.01
1.0 μ F	50.8 19	£1.37	15 μ F	£7.14	£4.76 £3.66
1.5 μ F	60.8 25.4	£1.94	22 μ F	£9.66	£6.44 £3.99
2.0 μ F	50.8 25.4	£1.95			

TANTALUM BEAD CAPACITORS—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8 μ F at 16V/25V or 35V; 10.0 μ F at 16V/20V or 25V; 22.0 μ F at 8V/10V or 16V; 33.0 μ F at 6V or 10V; 47.0 μ F at 3V or 6V; 100.0 μ F at 3V. All at 12p* each, 10 for £1.10*, 50 for £5*, 100 for £8*.

TRANSISTORS & I.C.'s
 BC107/8/9 8p *BC212/212L 90p 2N3055 50p
 *BC114 12p *BC213/213L 11p OC71/2 30p
 *BC147/8/9 10p *BC214/214L 11p OC71/2 30p
 *BC165 12p *BF194/5 12p NE555 Timer 61p
 *BC164/7/8/9 12p BFE501/1/2 20p 741C 8 pin DIL 32p
 BC182/182L 11p AP178 40p ZN414 £1.15
 *BC183/183L 11p AP224 35p SN76018ND
 *BC184/184L 12p SN709/4 11p

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 6p, 8 for 45p, 14 for 90p; 1844 5p, 11 for 50p, 26 for £1.00, 1N4148 6p, 6 for 27p, 12 for 46p; 1N4001 5p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p.
LOW PRICE ZENER DIODES—400mW, T $\pm 5\%$ at 5mA. 3V; 3V8; 3V6; 4V7; 5V1; 5V6; 6V2; 6V8; 7V6; 8V2; 8V1; 10V; 11V; 12V; 13V; 13.6V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each, 6 for 35p, 10 for 65p, 50 for £3.12. SPECIAL OFFER: 100 Zeners (may be mixed) for £6.00.

RESISTORS—High stability, low noise carbon film 5% 1W at 40°C, 1W at 70°C. E12 series only—from 2.2 Ω to 2.2M Ω . ALL at 1p each. 8p* for 10 of any one value, 70p* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2 Ω to 2.2M Ω (730 resistors) 85p.

SILOCON PLASTIC RECTIFIERS—1.5 amp, wire-ended D02T: 100 P.I.V. 7p (4 for 36p); 400 P.I.V. 8p (4 for 36p).

BRIDGE RECTIFIERS—24 amp: 200V 45p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: All at 5p each; 50: 100; 220; 470; 680 ohm; 1k; 2k2; 4k7; 6k8; 10k; 15k; 22k; 47k; 100k; 320k; 680k; 1M; 2M; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with *

which are 124%.
 Send S.A.E. for additional stock lists.
 Wholesale price lists available to bona fide companies.
MARCO TRADING (Dept. P4),
 The Old School, Egham, Surrey, Wokingham.
 Tel: Whithal 464/485 (STD 04 878)
 (Propra. Minicost Trading Ltd.)

ORCHARD ELECTRONICS

I.C.s. TTL, C/Mos. Linear. Capacitors, Resistors (E12), Sil/Rectifiers, Diodes, LED, Thyristors, Zeners, Voltage Reg. DIL, Sockets, Bridge Rectifiers, Potentiometers, Presets, Triacs, Diacs, Plugs, Sockets, Cable, Verco. Carefully selected range, excellent despatch service. Same day turnaround. S.A.E. List. Orchard Electronics, Flint House, High Street, Wallingford, Oxon. Tel: 0491-35529.

U.K. Agents Required

ELECTRONIC CALCULATOR
 Manufacturers & Exporter
PACIFIC TRADING COMPANY
 77A Waterloo Road, Kowloon
 P.O. Box 8173, Hong Kong
 Telex: 84672 VRHGT HX
 (C&F UK less than £3.00, mail order not accepted. Invite Enquiries only).



Books and Publications

FREE T.V. CIRCUIT DIAGRAMS
 All main British T.V. sets (plus many foreign) comprehensively covered in our easy-to-follow T.V. Repair Manuals—4 mono and 3 colour. Just send model no., if colour (mfrs. chassis type helps) with £4 and receive the manual covering your set—plus your sets circuit diagram on request free. Set of 7 only £25.
 British T.V. Circuit Diagram Manuals—the main mono (over 37 series) for £9.50 and virtually every colour for £16.
 Full details of these and other publications from
T.V. TECHNIC
 78 Church St., Larkhall, Lanarks ML9 1HE
 Tel. (0698) 823334.

Technical Books—Radio & Electronics

World's Radio & TV Stations (International Ed.)	£0-70
WORLD RADIO TV HANDBOOK 1976	£5-00
Incorporating How to Listen to the World	£5-00
Boys Book of Crystal Sets	£0-35
Resistor Selection Handbook	£0-68
Audio Hi Fi Construction Projects	£0-95
How to get the best out of your Tape Recorder	£1-70
Practical Electronic Science Projects	£0-85
Jack Darr's Service Clinic	£1-80
Transistor Circuits for Modern Test Equipment	£0-85
Modern Tape Recording Handbook	£0-85
1st Book of Transistor Equip. and Substitutes	£0-80
Hi Fi, PA & Disco Amplifier Design Handbook	£0-87
Radio Servicing Problems	£0-75
Electronic Circuits for the Amat. Photographer	£0-70
32 Projects using IC 741 or Equivs	£0-85
TV Fault Finding	£1-15
Trans. Circuits for Rad. Control Models	£0-50
Practical Stereo & Quadrophony Handbook	£0-85
Radio Amateur Operator's Handbook	£0-85
Coil Design & Construction Manual	£0-60
Radio TV & Electronics Data Book	£0-70
70 Electronic Novelty Circuits	£0-85
The Complete Car Radio Manual	£0-85
Radio Technicians Bench Manual	£3-40
Servicing Transistor Radio Receivers	£0-95
1st Book of Hi Fi Loudspeaker Enclosures	£0-70
2nd Book of Hi Fi Loudspeaker Enclosures	£0-70
Manual of Electronic Circuits for the Home	£0-60
Modern Crystal Set Circuits for Beginners	£0-45
Electronic Novelties for the Motorist	£0-60
2nd Book of Transistor Equip. & Substitutes	£1-10
Handbook of Electronic Musical Novelties	£0-60
Transistorised Novelties for Hi Fi Enthusiast	£0-45
Failure Location Exercises in Rad. & TV Vol. 1	£1-00
Failure Location Exercises in Rad. & TV Vol. 2	£1-00
Colour TV Picture Faults	£2-80
Practical Transistor Novelty Circuits	£0-50
Boys Book of Practical Radio & Electronics	£0-70
Radio Receiver Construction using ICs & Transis.	£0-70
ICs & Transistor Gadgets Construction Handbook	£0-70
Integrated Circuits Equip. & Substitutes Handbook	£0-85
Audio Technicians Bench Manual	£3-40
Radio Antenna Handbook for Long Dist. Receptn.	£0-90
Guide to Printed Circuits	£3-40
Diode Characteristics Equip. & Substitutes	£1-10
Electronic Gadgets & Games	£0-90
PRICES INCL. POST & PACKING. Send S.A.E. for Lists	

RADIO BOOK SERVICE

40 Elwill Way, Beckenham BR3 2RZ

MORSE IMPROVEMENT
C90 Cassettes
 1-12 wpm with simple exercises.
 12-24 wpm Computer produced professional level operator material including international symbols.
 Price: complete with instruction and exercise booklets £4 including postage. Overseas £1 extra.
 Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation. Price £3 including postage. Overseas £1 extra.
MHEL Electronics
 12 Longshore way, Milton
 Portsmouth, (UK) PO4 8LS

**START YOUR OWN BUSINESS
REWINDING ELECTRIC MOTORS**

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc. A goldmine of information and knowledge.

Only £3-65 plus 25p P&P.

Magnum Publications Dept PWS
Brinkway Trading Estate, Brinkway,
Stockport SK3 9BZ.

Overseas Distributors wanted.

Educational

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians, Telecomm Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kite. Get the qualifications you need to succeed.

Free details from:

**INTERNATIONAL
CORRESPONDENCE SCHOOLS,**
Dept. 778V, Intertex House, London SW8 4UJ.
Or Phone 01-622 9911 (All Hours)

BE A SUCCESSFUL TV ENGINEER.
Join our full-time Two-Year College Diploma Course, specially designed to cover the examinations of the City and Guild Radio, Television and Electronics Technician's Certificate. Full theoretical and practical instruction on all types of modern receivers including the latest colour sets. Enrolments are now under way for September 1976. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English. September includes a specialised Colour TV and FM Stereo servicing course, plus a 2nd year Technicians' Course. Contact us for free prospectus. **THE PEMBRIDGE COLLEGE OF ELECTRONICS,** Dept. PW, 34a Hereford Rd., London W2 5AJ. Tel: 01-229 9117.

TAPETALK

THE CLEVER WAY TO LEARN

TWO C60 Cassettes entitled
INTRODUCING ELECTRONICS
£5.44 plus 55p VAT/P. & P.
TAPETALK, P.O. Box 99 (PW)
Milton Keynes MK3 5BR
Tel.: Milton Keynes (0908) 77710

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

For Sale

DISCOLIGHTS. Best! Cheapest! Reliable! Bumper catalogue: Aarvak Electronics, 12a(P) Bruce Grove, N17 6RA. 01-808 8923.

**COPPER CLAD LAMINATE
FOR
PRINTED CIRCUITS**

Single sided 1/16" paper base—1.5p/sq. inch.
Single sided 1/16" glass-epoxy—2.0p/sq. inch.
Any rectangular sizes cut to your requirements.
Please send cash with order.
Price includes postage and packing.
From: **SIMTECH ENGINEERING LTD**
Dedham Road, Ardleigh, Colchester,
Essex, C07 7QA
Telephone 0206 230133

AKG D190C Mikes. New & boxed £24.00. 'E' model £26.00 inc. VAT & postage. J. J. Francis (Wood Green) Ltd Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

COLOUR T.V.

Decca CTV 19 Colour T.V.'s complete but not working. Special price to clear £30. Must be collected.

TELEMEC LTD.

4, Waterloo Terrace, Bridgnorth,
Salop. Phone 3079 or 2585.

Tape Recorders

TAPETALK

THE NATURAL WAY TO LEARN

Two C60 cassettes entitled
INTRODUCING TRANSISTORS
£5.44 plus 55p VAT/P. & P.

TAPETALK, P.O. Box 99 (PW)
Milton Keynes MK3 5BR
Tel.: Milton Keynes (0908) 77710

Service Sheets

SERVICE SHEETS—COLOUR TV SERVICE MANUALS

LARGE SELECTION COVERING MOST MAKES—S.A.E. WITH ENQUIRIES PLEASE TO:

BELL'S TELEVISION SERVICES

190 KINGS ROAD, HARROGATE, N. YORKSHIRE TEL. (CODE 0423) 55885

We also have a large stock of Books & Magazines on Radio, TV, etc. Free lists on request

**LARGE SUPPLIER
OF
SERVICE SHEETS**

(T.V., RADIO, TAPE RECORDERS,
RECORD PLAYERS, TRANSISTORS,
STEREOGRAMS, RADIOGRAMS,
CAR RADIOS)

ALL AT 50p EACH
Please state if Circuit will do if Service Sheet not in stock.

**"PLEASE ENCLOSE LARGE S.A.E
WITH ALL ENQUIRIES & ORDERS"**

Otherwise cannot be attended to

(Uncrossed P.O.s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11 6RX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882
Large Stocks of Colour Manuals
NO OVERSEAS MAIL PLEASE

SERVICE SHEETS for Radio, TV, Tape Recorders, Stereo, etc., with free fault-finding guide, 50p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

SERVICE SHEETS—COLOUR TV MANUALS

Service Sheets for Black and White TV, Radios, Record Players and Tape Recorders 50p. Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers.
B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA etc.
Please send a Stamped Addressed Envelope for a prompt reply.

G. T. TECHNICAL INFORMATION SERVICE
10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA
MAIL ORDER ONLY

BELL'S TELEVISION SERVICES for service sheets, manuals & books on radio/TV etc. Service sheets 50p plus SAE. Service sheet catalogue 25p. Back issues of magazines from April 74 onwards cover price plus 12p post. Free booklists on request. SAE with enquiries please to B.T.S., 190 Kings Road, Harrogate, Yorkshire. Telephone Harrogate (code 0423) 55885.

Wanted

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

**TOP PRICES PAID for NEW VALVES
and TRANSISTORS**

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C).
367 Kensington Street, Bradford 8,
Yorkshire.

Electrical

STYL & CARTRIDGES. For the best at keenest prices send SAE for free illustrated list to Felstead Electronics (PW), Longley Lane, Gatley, Ches. SK8 4EE.

Miscellaneous

H. M. ELECTRONICS

275a FULWOOD ROAD, BROOMHILL,
SHEFFIELD S10, 3BD.

BEC CABINETS (illus'd)



METAL CASES
DRY TRANSFER LETTERING

Send 15p for leaflets (Refundable)
Trade enquiries invited

DO-IT-YOURSELF loudspeakers for hi-fi are our speciality. Full range of components and accessories including chassis speakers, crossovers, sound absorbent, grille fabrics etc. always available. We stock the fabulous value Helme speaker kits complete with full and easy instructions, also Peerless and Wharfedale kits. Just about the lowest prices anywhere! Send 8½p stamp for bargain list to: Audioscan, Dept. PW776, 4 Princes Square, Harrogate, North Yorkshire.

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs. Prompt service. Send 15p for catalogue.

Ramar Constructor Services,
Masons Road, Stratford on Avon,
Warwicks. Tel: 8789

LOW-COST I.C. MOUNTING for any size DIL package. 100 Soldercon sockets 60p. 7 and 8 hole plastic supports 5p/pair. Quantity rates. SAE details and sample. Trial pack 60p. (P & P 10p/order). P.K.G. Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

GORSE'S MAIN STOCKISTS FOR GRUNDIG

Satellit 2000, 21 Wave Band Radio, TK645 and TK745 Stereo Tape Recorders, Radios, Radio/Cassette Recorders, Cassette Recorders, Microphones, etc., etc.

Please write, phone or call for full details and prices.
42-44 CHURCH ST., 77 THE MALL
BLACKBURN, BURNLEY
Tel: 51682 Tel: 35229

HELME
DO-IT-YOURSELF
HI-FI STEREO
SPEAKER KITS
The best value around!
Send for details
HELME AUDIO
PRODUCTS LTD.
Drpt. PW
SUMMERBRIDGE
HARROGATE YORKS
Tel. Darley 279 (Std Code 0423-72)

1LB PACKS of assorted copper laminates for 60p plus p/p 30p. Cash with order to Crossley & Bradley, 248 Slater Lane, Leyland, Lancs.

LOOKING FOR BARGAINS

Light Dimmer 500W module with knob £1.99*
LM380 2W Audio Amplifier 14 pin DIL 79p
LM555CN Timer 8 pin DIL 42p*
723 Voltage Regulator 2-37 Volt 44p*
CA3088E FM IF system 16 pin DIL £1.89
CA3090A Q Stereo Decoder 16 pin QIL £4.22
Please add 12½% VAT (*8%) and 15p postage or send SAE for catalogue to:-

FRASER-MANNING LTD.
26 HERVEY STREET, IPSWICH, SUFFOLK

ALUMINIUM SHEET AND BOXES cut and folded to your design. Sheet: 22, 20, 18 S.W.G. 0.5p/sq inch; 16, 14 S.W.G. 1p/sq inch. Boxes: 22, 20, 18 S.W.G. 1p/sq inch; 16 S.W.G. 1½p/sq inch; 14 S.W.G. 2p/sq inch. Maximum length of any side: 2ft. Maximum depth of box: 1 ft. Please add 8% VAT. P&P 25p per item. SAE for special quotes (UK only). Trade enquiries welcomed. Simtec Electronics (UK) Ltd., Unit 37, Faircharm Trading Estate, St. Mary's Mills, Leicester. Tel: (0533) 824380.

Synthesiser "Sounds Supreme"

by **Dewtron** (25% VAT extra.)

Famous kits, e.g. waa-waa complete kit £4.50; Fuzz kit £6.50 P&P 25p under £10. Ring Modulator modules £11. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

RECHARGEABLE NICAD BATTERIES. Pencil, AA—£0.94p. Sub. 'C'—£1.16. 'C'—£1.92. 'D'—£2.59. PP3—£4.48. Chargers, £4.48, £4.48, £4.98, £4.98, £3.98 respectively. Others. All prices include VAT. Add 10% Post and Package. SAE for price list plus 25p for information booklet. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands. 021 354 9764.

the TEXAN HiFi Amp

28 watt version available ex stock
at **£35 incl. tax**

You are invited to send S.A.E. for lists of our very extensive range of high quality amplifier, pre-amps, F.M. tuners, Instruments, Radiocontrol, Ignition units and many other kits. Please state requirements.

TELERADIO ELECTRONICS,
325 FORE STREET, EDMONTON,
LONDON N9

SUPERB INSTRUMENT CASES by Bazell, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples: width, depth, height, 8in x 5in x 3in, £1.55; 10in x 6in x 3in, £2.20; 10in x 8in x 3in, £2.75; 12in x 10in x 3in, £3.60; 8in x 4in x 4in, £1.80; 10in x 6in x 4in, £2.70; 12in x 8in x 4in, £3.60; 7in x 7in x 5in, £2.65; 8in x 10in x 6in, £3.60; 12in x 8in x 7in, £4; 12in x 12in x 7in, £4.40. Plus 71p. Carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated), Bazelli, Dept. No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

12 VOLT FLUORESCENTS

35% OFF
RRP

MADE BY THORN LIGHTING. Ideal for Caravan, Boat, Tent, Emergency Lighting etc. All lamps guaranteed for 12 months.

21 ins
13 watt
£4.90



12 ins
8 watt
£4.00

All lamps have On/Off Switch, Wrong Polarity Protection Device and Diffuser.

C60 CASSETTES 32p All Cassettes in Plastic Case with Index and Screwed Assembly.
C90 CASSETTES 45p

All prices include VAT. Add Postage 5p in £1.

Quantity Discounts. **SALOP ELECTRONICS**
10 Units 5%
50 Units 7%
100 Units 10%
23 WYLE COP
SHREWSBURY
Tel. 53206

THE SCIENTIFIC WIRE CO

Copper - Nickel Chrome - Eureka - Manganin Wires.

Enamelled - Silk - Cotton - Tinned Coverings.

No minimum charges or quantities.
Trade and Export enquiries welcome.

S.A.E. Brings List.
P.O. BOX 30, LONDON, E4 9BW

GLASS FIBRE PCBs. Send 1:1 master and 7p per square inch tinned or 10p per square inch drilled and tinned. Plus 40p per board. Send for quotation on double sided boards. Discount for quantity. Proto Design, 4 Highcliffe Way, Wickford, Essex SS11 8LA.

DOWN WITH QRM!

Get rid of CW and heterodyne QRM. FAST with a TUNABLE AUDIO NOTCH FILTER. Winkle out the rare DX. Goes between RX and speaker. EASY TO MAKE. All parts, case, instructions, money back assurance, ONLY £5.30 inc. post.

CAMBRIDGE KITS

45 (L), Old School Lane, Milton, Cambridge

BUILD THE TREASURE TRACER MK III Metal Locator

- Var/Cap tuning
- Britain's best selling metal locator kit; 4,000 sold
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete **£12.50** Built & tested **£17.50**
K.I.I. Post 35p + £1.03 VAT 8%. Post 85p + £1.40 VAT 8%

MINIKITS ELECTRONICS,
8a CLEVELAND ROAD,
LONDON, E15 2AN (Mail order only)

RADIO. Learn from the beginning. 16 vintage circuit diagrams, receivers and transmitters with notes. £1. Allister, 58 Wavell Road, Maidenhead, Berks, SL6 5AD.

ENAMELLED COPPER WIRE

S.W.G.	1 lb reel	½ lb reel
10 to 19	2.40	1.35
20 to 29	2.45	1.40
30 to 34	2.60	1.50
35 to 40	2.85	1.60

All the above prices are inclusive of postage and packing in U.K.

COPPER SUPPLIES

102 Parrswood Road, Wichington,
Manchester 20 Tel: 061-445 8753

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 37774

ALL DEVICES BRAND NEW AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHQ/INT. P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 25p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. (SEND 25p FOR OUR CATALOGUE).

VAT Applicable to U.K. Customers only. All prices are exclusive of VAT. Please add 8% to devices marked * To the rest add 12 1/2%.

Callers welcome to our retail shop at 33, Cardiff Road, behind Watford Football Ground, Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F).
40V: 0-001, 0-0015, 0-0022, 0-0033 5p; 0-0047, 0-0068, 0-01, 0-015, 0-018, 0-022 6p;
0-033, 0-039, 0-047, 0-068 8p; 0-1, 0-15, 0-22, 10p; 0-33, 0-47, 18p; 0-68 24p.
160V: 0-15 4p; 0-22 5p; 0-33 6p; 0-47 10p; 0-68 15p; 1-0 18p; 1-5 20p; 2-2 24p; 4-7 28p
DUBILIER: 1000V: 0-01, 14p; 0-022, 15p; 0-047, 16p; 0-1, 19p; 0-47 43p.

POLYESTER RADIAL LEAD (Values in μ F): 250V: 0-01, 0-015, 0-022, 0-027 5p; 0-033, 0-047, 0-068, 0-1 6p; 0-15 7p; 0-22, 0-33 9p; 0-47 10p; 0-68 14p; 1-0 19p; 1-5 24p; 2-2 28p.
FEED THROUGH CAPACITORS: 1000pF/350V 8p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F).
100V: 100 μ F, 40p; 100V: 20, 6p; 50V: 0-47, 1-0, 1-5, 2-2, 2-5, 3-3, 4-7, 6-8, 8, 10, 15, 22, 27, 33, 50, 10p; 50V: 1-0, 6p; 50, 10p; 220, 15p; 470, 23p; 1000, 42p;
40V: 33, 6p; 2200 40p; 35V: 1000, 38p; 25V: 8, 10, 22, 40, 6p; 80, 100, 160 9p; 220 13p;
470 17p; 640, 21p; 1000, 27p; 2200, 34p; 3300, 39p; 4700, 47p; 16V: 10, 40, 47, 68, 10p;
125, 220, 6p; 470, 11p; 1000, 15p; 4700, 44p; 10V: 4, 10p, 6p; 640, 10p; 1000, 14p;
125, 220, 2200, 28p; 470, 11p; 1000, 15p; 180, 17p; 4700, 46p; 10V: 4, 10p, 6p; 640, 10p; 1000, 14p;
220, 18p; 2200, 28p; TAG-END TYPE: 70V: 2500, 98p; 4700, 111p; 50V: 2000, 72p; 25V: 4700, 48p.

TANTALUM BEAD CAPACITORS
35V: 0-1 μ F, 0-22, 0-33, 0-47, 0-68, 1-0, 2-2 μ F, 3-3, 4-7, 8-8, 25V: 1-5, 10, 16V: 10 μ F, 22, 10V: 15 μ F, 33, 6V: 47 μ F, 3V: 100 μ F.
Price: 11p each.

MYLAR FILM CAPACITORS
100V: 0-001, 0-002, 0-005, 0-01 μ F 4p
0-015, 0-02, 0-04, 0-05, 0-056 μ F 5p
0-1 μ F, 0-15, 0-2, 0-5V: 0-47 μ F 6p

SLIDER POTENTIOMETERS
0-25W log and linear values 60mm 43p
5K Ω -500K Ω single gang 5p
10K Ω -500K Ω Dual gang 5p
50K Ω Lin 150mm WS 150 £3.90

DIAGNOSTIC VARIABLE CAPS.
Electronic Dial Drive 4103
1000/300pF 86p 6-1/36:1 488p
500/50pF 95p 0-1-36:5pF 240p
DILEMMON 00 2 36:5pF 240p
4332/2K 2 speed 00 208/176 240p
Drive unit complete with knobs and coupling 322p
Drum 54mm 30p
6:1 Ball Drive 1" 3x319pF 312p
4511/D4F 97p 00-3x25pF 323p

CERAMIC TRIMMER CAPACITORS
2-7pF, 4-15pF, 6-25pF, 8-30pF, 17p each
MINIATURE 3-10pF, 3-30pF, 10-40pF 25p
60p
COMPRESSION 18p
3-40pF 18p
20-250pF 27p
100-500pF 32p
125pF 32p

SILVER MICA (45P)
3-3, 4-7, 6-8, 12, 18, 22, 33, 50, 75, 82, 85, 360, 120, 150, 260, 330, 860, 7p each
2200pF 11p

DENCO COILS
Dual P.D.P. R/W
1-5 B.Y.R. 69p
6-7 B.Y.R. 60p
1-5 Green 74p
Rng. 1-5 B.Y.R. W 78p
BnA Valve Base 19p
RFC 5 choke 76p
IFT 13/14/15/16/17 70p
IFT18/465 or 1-6m 80p
TOC 1 75p
MW 5F.R. 72p
MW/LW 5FR 94p

ALUM. BOXES
with lid 22x53x1 46p
44x11 46p
42x23x1 46p
44x51x1 58p
42x23x2 46p
32x21 46p
with slow 75x52 84p
88x63 106p
10x7x3 122p
10x4x3 110p
12x5x3 120p
12x6x3 180p

EARPHONES
Magnetic 2-5mm plug 15p
3-5mm plug 15p
Crystal 3-5mm plug 30p

SLOPING FRONT ALUM BOX* WE1 £1-75
PANEL METER* £3-05
DIAL ETCH RESIST Pen & spare tip. 74p

COPPER CLAD BOARDS*
SRBP 3" x 9" 48p
Fibre Glass 6" x 6" 64p
12" x 6" 115p

SPEAKERS
0.3W 3" 23p
2 1/2" 3" 56p
64 0-3W 2" 60p
16 0 7 x 4" 5W 170p

VEROBOARD* Pitch
0-1 0-15 0-15
(copper clad) (plain)
2 1/2 x 3 3/4 32p 24p 15p
2 1/2 x 5 35p 35p 20p
3 1/2 x 3 3/4 35p 35p 20p
3 1/2 x 5 40p 41p 25p
3 1/2 x 7 105p 75p 60p
4 1/2 x 7 145p 115p 75p
4 1/2 x 7 185p 110p

Pkt of 36 pins 22p
Spot face cutter 52p
Pin insertion tool 72p

TRANSISTORS		BD145*		OC28*		OC35*		OC36*		OC41*		OC42*		OC43*		OC44*		OC45*		OC46*		OC47*		OC48*		OC49*		OC50*		OC51*		OC52*		OC53*		OC54*		OC55*		OC56*		OC57*		OC58*		OC59*		OC60*		OC61*		OC62*		OC63*		OC64*		OC65*		OC66*		OC67*		OC68*		OC69*		OC70*		OC71*		OC72*		OC73*		OC74*		OC75*		OC76*		OC77*		OC78*		OC79*		OC80*		OC81*		OC82*		OC83*		OC84*		OC85*		OC86*		OC87*		OC88*		OC89*		OC90*		OC91*		OC92*		OC93*		OC94*		OC95*		OC96*		OC97*		OC98*		OC99*		OC100*			
AC125*	28	BC148	7	BD145*	55	OC28*	58	OC35*	54	OC36*	58	OC41*	58	OC42*	58	OC43*	58	OC44*	58	OC45*	58	OC46*	58	OC47*	58	OC48*	58	OC49*	58	OC50*	58	OC51*	58	OC52*	58	OC53*	58	OC54*	58	OC55*	58	OC56*	58	OC57*	58	OC58*	58	OC59*	58	OC60*	58	OC61*	58	OC62*	58	OC63*	58	OC64*	58	OC65*	58	OC66*	58	OC67*	58	OC68*	58	OC69*	58	OC70*	58	OC71*	58	OC72*	58	OC73*	58	OC74*	58	OC75*	58	OC76*	58	OC77*	58	OC78*	58	OC79*	58	OC80*	58	OC81*	58	OC82*	58	OC83*	58	OC84*	58	OC85*	58	OC86*	58	OC87*	58	OC88*	58	OC89*	58	OC90*	58	OC91*	58	OC92*	58	OC93*	58	OC94*	58	OC95*	58	OC96*	58	OC97*	58	OC98*	58	OC99*	58	OC100*	58

CMOS*		4028AE 94p		LINEAR IC'S		CA3130 88p		NE567*		150p																																																																																																																																																																																																																									
4001AE 16p	4028AE 94p	709C 14 pin	29p	ICL8038CC*270p	170p	SL403D	176p	4002AE 16p	4030AE 45p	710	43p	LM300H	170p	SL403A	38p	LM301A	38p	SL414A	176p	4003AE 16p	4032AE 111p	741C	22p	LM309	90p	SN76013	280p	4004AE 89p	4034AE134p	747C	70p	LM390	90p	SN76013	280p	4005AE 85p	4036AE 144p	748C	70p	LM391	160p	SN76013	280p	4006AE 89p	4038AE 177p	749C	70p	LM392	160p	SN76013	280p	4007AE 16p	4040AE 88p	749C	70p	LM393	160p	SN76013	280p	4008AE 89p	4042AE 87p	749C	70p	LM394	160p	SN76013	280p	4009AE 85p	4044AE 75p	749C	70p	LM395	160p	SN76013	280p	4010AE 16p	4046AE 110p	749C	70p	LM396	160p	SN76013	280p	4011AE 16p	4048AE 87p	749C	70p	LM397	160p	SN76013	280p	4012AE 16p	4050AE 110p	749C	70p	LM398	160p	SN76013	280p	4013AE 16p	4052AE 87p	749C	70p	LM399	160p	SN76013	280p	4014AE 16p	4054AE 110p	749C	70p	LM399	160p	SN76013	280p	4015AE 81p	4056AE 106p	749C	70p	LM399	160p	SN76013	280p	4016AE 16p	4058AE 87p	749C	70p	LM399	160p	SN76013	280p	4017AE 76p	4060AE 144p	749C	70p	LM399	160p	SN76013	280p	4018AE 76p	4062AE 110p	749C	70p	LM399	160p	SN76013	280p	4019AE 44p	4064AE 106p	749C	70p	LM399	160p	SN76013	280p	4020AE 90p	4066AE 106p	749C	70p	LM399	160p	SN76013	280p	4021AE 81p	4068AE 110p	749C	70p	LM399	160p	SN76013	280p	4022AE 76p	4070AE 16p	749C	70p	LM399	160p	SN76013	280p	4023AE 16p	4072AE 87p	749C	70p	LM399	160p	SN76013	280p	4024AE 64p	4074AE 87p	749C	70p	LM399	160p	SN76013	280p	4025AE 17p	4076AE 87p	749C	70p	LM399	160p	SN76013	280p	4026AE 13p	4078AE 87p	749C	70p	LM399	160p	SN76013	280p	4027AE 13p	4080AE 87p	749C	70p	LM399	160p	SN76013	280p	4028AE 13p	4082AE 87p	749C	70p	LM399	160p	SN76013	280p

TTL 74* Less 5% for 15 + mxid
Less 10% for 25 + mxid

DIGITAL ICs		7400		7401		7402		7403		7404		7405		7406		7407		7408		7409		7410		7411		7412		7413		7414		7415		7416		7417		7418		7419		7420		7421		7422		7423		7424		7425		7426		7427		7428		7429		7430		7431		7432		7433		7434		7435		7436		7437		7438		7439		7440		7441		7442		7443		7444		7445		7446		7447		7448		7449		7450		7451		7452		7453		7454		7455		7456		7457		7458		7459		7460		7461		7462	
7400	13p	7401	13p	7402	14p	7403	15p	7404	18p	7405	18p	7406	18p	7407	38p	7408	15p	7409	15p	7410	13p	7411	20p	7412	20p	7413	35p	7414	35p	7415	35p	7416	35p	7417	35p	7418	35p	7419	35p	7420	22p	7421	22p	7422	22p	7423	22p	7424	22p	7425	27p	7426	27p	7427	27p	7428	38p	7429	38p	7430	15p	7431	15p	7432	25p	7433	25p	7434	25p	7435	25p	7436	25p	7437	27p	7438	27p	7439	27p	7440	27p	7441	65p	7442	65p	7443	120p	7444	105p	7445	105p	7446	105p	7447	80p	7448	70p	7449	70p	7450	70p	7451	70p	7452	70p	7453	15p	7454	15p	7455	15p	7456	15p	7457	15p	7458	15p	7459	15p	7460	15p	7461	15p	7462	26p		

DIODES		AEY11		BA100		BY126		BY127		IN916		OA9		OA10		OA17		OA70		OA71		OA81		OA85		OA86		OA87		OA88		OA89		OA90		OA91		OA92		OA93		OA94		OA95		OA96		OA97		OA98		OA99		OA100	
AEY11	70p	BA100	10p	BY126	12p	BY127	12p	IN916	12p	OA9	9p	OA10	40p	OA17	9p	OA70	10p	OA71	10p	OA81	8p	OA85	10p	OA86	10p	OA87	10p	OA88	10p	OA89	10p	OA90	10p	OA91	10p	OA92	10p	OA93	10p	OA94	10p	OA95	10p	OA96	10p	OA97	10p	OA98	10p	OA99	10p	OA100	10p		

BRIDGE RECTIFIERS		1A50V		1A100V		1A200V		1A400V		1A600V		1A800V		1A1000V		1A1500V		1A2000V		1A2500V		1A3000V		1A3500V		1A4000V		1A4500V		1A5000V		1A5500V		1A6000V		1A6500V		1A7000V		1A7500V		1A8000V		1A8500V		1A9000V		1A9500V	
1A50V	20p	1A100V	42p	1A200V	47p	1A400V	26p	1A600V	27p	1A800V	28p	1A1000V	29p	1A1500V	30p	1A2000V	31p	1A2500V	32p	1A3000V	33p	1A3500V	34p	1A4000V	35p	1A4500V	36p	1A5000V	37p	1A5500V	38p	1A6000V																	

TRANS-SISTOR
Insulation Kit. Mica & Bushes 6p*

SWITCH*
Blased Toggle DPDT 99p

Connectors*
Snap on PP3 6p
Snap on PP9 9p

JACK PLUGS
Screened chrome
Plastic body

SOCKETS
Open metal
Moulded with break contacts

KNOBBS* fits 1/8" shaft with grub screw, except K2 (push fit) & K8 (for sliders)
K1 Black or White pointer type
K2 Slim silvered aluminium
K4 Black serrated. Metal top with line indicator 33mm diam.
K4A As above but 25mm diam.
K5 Black fluted metal top and skirt calibrated 0-10, 37mm diam.
K6 Pink as K5, pointer on skirt
K7 Black, knurled, tapered. Metal top & skirt. Calif. 0-10, 30mm
K8 Black or silvered for slider pot

PANEL METERS* Full scale
59x46 x 35mm req. 1 1/2" hole
0-50µA 0-100mA
0-100µA 0-500mA
0-500µA 0-1 Amp
0-1mA 0-50V DC
0-5mA 0-300V DC
0-10mA "15"
0-50mA "VU"
Price £3-85 each.
108 x 82-5 x 38mm req. 60mm panel hole
0-50µA; 0-100µA; 0-500µA £4-40

TRANSFORMERS (Mains Prim. 220-240V)
6-0-6V 100mA 90p
9-0-9V 100mA 90p
12-0-12V 100mA 90p
15-0-15V 100mA 120p
0-12-0-12V 150mA 160p
0-6-0-6V 280mA 170p
0-12-0-12V 0-5A 160p+
24-0-24V 0-5A 180p+
9-0-9V 1A* 180p+
12-0-12V 1A* 180p+
15-0-15V 1A* 180p+
18-0-18V 1A* 230p+
30-24-20-15-12-0 1A*
Multi tappings 285p+
30-24-20-15-12-0
2A* multi tappings 435p+
(Please add 48p p&p charge to all prices marked +, above our normal postal charge.)

DIN
2 1/2 in Loudspeaker
3, 4, 5 (180° & 240°)

CO-AXIAL (TV)

PHONO
assorted colours
Metal screened

BANANA 4mm 2mm

LAMP HOLDERS AND LAMPS*
LES HOLDER Dome shaped, Red, Blue, Green, Yellow, White
LES BULBS 6v and 12v
MES HOLDERS Chrome cover, Red or Amber, Jewelled top
MES BULBS 3-5V 6V 12V
NEONS Mains Sealed with Resistor. Sq. Top, Red or Grn. Round Top Red Neon when leads, 95V AC (No resistor) 9p

SWITCHES*
TOGGLE: 2A, 250V
SPST
DPDT
SUB-MIN TOGGLE
SP changerover
SPST on/off
DPDT 6 tag
DPDT Centre off

SLIDE 250V:
1A DP
1A DP C/O
1A DP
PUSH BUTTON
SPRING loaded
SPST on/off
DPDT C/over
DPDT 6 tag

SWITCHES* PUSH BUTTON:
Miniature Non Locking
Push to Make
Push to Break
ROCKER (white): 10A 250V
SP changerover centre off
ROCKER: (black) on/off 10A 250V
ROCKER: Illuminated (white)
Lights when on. 3A 240V
ROTARY: (ADJUSTABLE STOP) 1 pole/
2-12 way, 2p/2-6W, 3p/2-4W, 4p/2-3W 30p
ROTARY: Mains 250V AC, 4 Amp 28p

ENGINEERS
FREE
YOURSELF FOR A BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 44 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!
Tick or state subject of interest. Post to the address below.

POST NOW

Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit) Electronic Engineering Computer Electronics Computer Transistor Technology CITY AND GUILDS Installations and Wiring CITY AND GUILDS Electrical Technicians CITY AND GUILDS Telecommunications Radio Amateurs' Exam etc. etc.

Electrical Engineering Colour TV Servicing C&G Radio, TV & Electronic Mechanics General Radio and TV Engineering Radio Servicing, Maintenance and Repair Mathematics

EPW 17

To ALDERMASTON COLLEGE Dept. EPW-17, Reading RG7 4PF
Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate London, EC2Y 5EJ Tel: 01-628 2721

NAME (Block Capitals Please) _____
ADDRESS _____
POST CODE _____
Other subjects _____ Age _____
Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

INDEX TO ADVERTISERS

Alben Engineering	206
Alcon Instruments	208
Ambit International	263
Antex	194
A.S.P. Ltd	210
Astro Electronics	260, 271
Bamber, B.	266
Barclay Electronics	255
Barrie Electronics	266
Bell's Television Services	275
Bentley Acoustic Corporation Ltd.	268
B.H. Component Factors Ltd.	228
Bi-Pak Ltd.	214-215
Bi-Pre-Pak Ltd.	197
Birkett, J.	203
Boffin Projects	277
British Institute of Engineering Technology	203, 211, 279
British National Radio & Electronics School	198, 227
J. Bull (Electrical) Ltd.	267
Bush & Meissner	204
Bywood Electronics	210
C.D.I. Ltd.	272
Cambridge Kits	276
Caranna, C.	275
Chromasonic Electronics	202
C.J.L. Ltd.	256
Cleveland Supplies	256
Colomor (Electronics) Ltd.	270
Copper Supplies	276
Cox Radio (Sussex) Ltd.	274
Crescent Radio Ltd.	271
Crofton Electronics	212
D.E.W. Ltd.	276
Doram Electronics	213
Electronics Design Associates	206
Electronic Mail Order Ltd.	272
Electro-Time	196

Electrovalue Ltd.	211
Flairline Supplies	273
Fraser-Manning Ltd.	276
G.T. Technical Information Service	275
Gorse's	276
Greenbank Electronics	204
Greenwell Electronics	198
Greenway Electronics	273
H.A.C. Short-Wave Supplies	210
H.M. Electronics	276
Harversons Surplus	213
Helme Audio	276
Henry's (Radio) Ltd.	256
Home Radio	259
I.L.P. Electronics Ltd.	207
Intertext I.C.S.	271, 275
Integrex Ltd.	268
Kensington Supplies	275
Kenyon Components	280
Lewis Radio	198
Linear Products	212
Lynx Electronics	277
Mhel Electronics	274
Magnum Publications	275
Manor Supplies	206
Maplin Electronic Supplies	cover iv
Marco Trading	274
Marshall, A. & Sons	208
Milward, G. F.	224
Minikits Electronics	276
Newmart Electronics	272
Oliver, P.G.	277
Orchard Electronics	274
Pacific Trading Co.	274
Partridge Electronics Ltd.	202
Pulse Electronics	224

Precision Petite	212
Print-A-Kit	224
Radio Component Specialists	269
Radio Book Service	274
Radio Exchange Ltd.	cover iii
Ramar Construction Services	276
Radio Society of G.B.	196
R.S.C. (Hi-Fi)	194, 195
R.S.T. Valve Mail Order Co.	199
Radio & T.V. Components Ltd.	264-265
R.F. Service	272
Salop Electronics	276
Saxon Entertainments Ltd.	205
Scientific Wire Company, The	276
Simtech Engineering Ltd.	275
Sinclair Radionics Ltd.	242-243
Sintel	211
Southern Valve Co.	203
Surplronics	273
Swanley Electronics	204
Tape Talk	275
Technomatic Ltd.	228
T.V. Technic	274
Telemac Ltd.	275
Teleradio Electronics	276
Time-Micro Electronics	270
Trampus Electronics	cover ii
Tuac Ltd.	200-201
Tudor Rees (Vintage Services)	274
Unilec Electronics	260
Watford Electronics	278, 279
Web Europa	206
West London Direct Supplies	210
Michael Williams Electronics	273
Wilmslow Audio	209
Wrights, S. G.	256
Xeroza Radio	263
Z. & I. Aero Services	280

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

MULTIMETERS—MADE IN USSR



AC/DC MULTIMETER TYPE U4324
33 ranges covering
D.C. current
60µA to 3A;
AC current
300µA—3A;
DC voltage: 0.6—1200V
AC voltage: 3—900V
Resistance: 500Ω—500kΩ
Level: —10 to +12db
Sensitivity: 20,000 o.p.v. DC, 4,000 o.p.v. A.C.

Instrument is powered by re-chargeable nickel cadmium batteries.
PRICE £10.85*



AC/DC MULTIMETER TYPE U4315
42 ranges covering:
D.C. current
50µA—2.5A; A.C. current: 500µA—2.5A; AC/DC voltage: 1—1000V; Resistance 300Ω—500kΩ; Capacity up to 0.5µF; Transmission level: —15 to +2db;
PRICE £11.25*

TRANSISTORS FOR T.V. APPLICATIONS

R2008B	0.95	BU133	1.55
R2010B	1.65	BU208	2.00
BU126	1.55		

LINEAR I.C. AMPLIFIERS

TAA263—3 stage low level amplifier. Bandwidth DC to 600kHz. Supply voltage 6-8V. Output power 10mW 150Ω load. Typical gain 77dB. TO72 case. **£0.65**
TAA293—Med. freq. amplifier up to 600kHz. Supply voltage 6V. Output power 10mW into 150Ω. Typical gain 89dB. TO74 case. **£0.65**
TAA320—MOST stage followed by a bi-polar transistor. Gate-to-source voltage 9-14V. Drain current 1µA. Power dissipation 200mW. TO18 case. **£0.60**

HIGH GAIN DARLINGTON PAIRS

Plastic 3-lead case encapsulated DARLINGTON pair. Typical current gain 30,000. Max. collector voltage V_{CS} 40V. Max. collector current: 400mA. I_{CS} = 10nA. BC516-PNP **£0.80**. BC517-NPN **£0.80**

Full description of the above, as well as other instruments, is available in our illustrated 126-page catalogue, which also includes price list of comprehensive range of transmitting and receiving valves, semiconductors and passive components. Please send 20p for your copy.

HANDLING AND POSTAGE CHARGES. When ordering through our Mail Order Service please add £1.00 for each instrument and 20p in £ for other items (subject to a minimum charge of 20p).

VALUE ADDED TAX: Prices are exclusive of VAT. Items marked with asterisk are at present rated at 8% and others at 25%. This percentage must be added to the total value of the order including handling charges.

MAINS TRANSFORMERS

PRI. 240v sec. 27/0/27v at 800 m/a, **£2.35**. P.P. 50p.
PRI. 110/240v sec. 50v at 10 amps, **£10.00**. P.P. £1.50.
PRI. 110/240v sec. 20/21/22v at 8 amp, **£9.00**. P.P. £1.50.
PRI. 110/240v sec. 23/24/25v at 10 amp, **£7.00**. P.P. £1.50.
PRI. 110/240v sec. 24/40v at 1½ amp, **£1.90**. P.P. 60p.
PRI. 240v sec. 20/40/60v at 2 amp, **£3.00**. P.P. 70p.
PRI. 240v sec. 20v at 2½ amp, **£2.00**. P.P. 65p.
PRI. 240v sec. 18v at 1.5 amp and 12v at 1 amp, **£2.25**. P.P. 50p.
PRI. 240v sec. 18v at 1 amp, **£1.10**. P.P. 35p.

MINI UNISELECTORS

12 volt 11 way, 4 bank (3 non-bridging, 1 homing) **£2.50**. P.P. 35p.
24 volt 11 way, 6 bank (5 non-bridging, 1 bridging) **£2.00**. P.P. 35p.

EDGE CONNECTOR

54 way .1 vero size etc.
Can easily be cut to any length 55p. P.P. 10p.
Side Guides for above connectors 16p each.

MINIATURE METERS

500 micro-amp (level-stereo beacon, etc.), scaled half black/half red. Size 1 x 1 in, 65p. P.P. 15p.

AM/FM TUNING METER

125-0-125 ua Edgewise 1½ x ½ **£1.10**

SIGNAL STRENGTH METER

250 ua Illuminated edgewise 1½ x ½ **£1.10**

OUTPUT METER

500ua 1½ x 1½ clear plastic panel type **£1.30**

SMITHS GEARED MOTORS

240v AC 3 revs per mln./4 revs. per min. } **£1.50**
- 2 revs per hr./6 revs per hr. } p.p. 25p

S-DECS AND T-DECS

S-DEC **£1.90**. T-DEC **£3.60**. } P.P. 25p.
U-DEC A **£4.20**. U-DEC B **£6.90**.

CIRCUIT BOARD

P.C.B. 1/16 1 oz. COPPER

FORMICA

Dim. 8.4 x 7.7 in 3 pcs., **80p.**
Dim. 9.4 x 8.1 in 3 pcs., **90p.**
Dim. 10.1 x 7.9 in 3 pcs., **£1.00.**
Dim. 13.1 x 9.4 in 3 pcs., **£1.20.**
Dim. 17.0 x 9.0 in 2 pcs., **£1.20.** } P.P. 35p

BARGAIN PACK

10 pcs. 10.1 x 7.9 in. Plus free ½ lb etching Xtals, **£3.10**. P.P. 45p.

FIBRE GLASS P.C.B.

Dim. 6 x 6 in, **50p** each.
Dim. 12 x 6 in, **75p** each. } P.P. 15p
Dim. 12 x 12 in, **£2.00** ea.
Equals less than 1p sq.in.

RESIST COATED P.C.B. FIBRE GLASS

6 x 6 in, **65p** ea.
12 x 6 in, **£1.20** ea.
12 x 12 in, **£2.00** ea.
Post & Packing 15p per sheet.

FERRIC CHLORIDE ETCHING XTALS

1 lb makes 1 litre pack, **70p**. P.P. 35p.
5 lb makes 5 litre pack, **£2.65**. P.P. 65p.

PRINTED CIRCUIT KIT

The no frills all value kit. Containing 4 pcs 8 x 7 Formica laminate, 1 pcc 6 x 6 Fibre glass laminate, 1 lb Etching Crystals, 50 c.c. Resist ink, with instructions. **£2.40**. P.P. 65p.

BLUE P.C.B. INK

Etch resist use with any pen. Much cheaper than ready loaded pens.
50 c.c. 55p. P.P. 10p.

ETCH RESIST PEN

55p p.p. 5p

FIBRE GLASS BARGAIN PACK

200 sq. in. single & double sided pieces, **£1.25**. P.P. 25p.

SIEMENS MINIATURE RELAYS

6v 4c/o with base, **65p** ea.
24v 2c/o with base, **50p** ea.

MAINS RELAY 240v

3 c/o 10 amp contacts. **£1** with base.

MINIATURE RELAYS

(1½ x 1½ x 2½) 24v, 4 c/o 40p

RIBBON CABLE

8 way, 8 colours. Bonded flat side by side.
10 Metres, **£1.90**.
100 Metres, **£12.50**.

OVERLOAD CUT-OUTS

Panel mounting 800 M/A. 1.8 amp. 10 amp. **55p** ea.

HIGH CAPACITY ELECTROLYTICS

250mfd/63 volt, **20p**. P.P. 8p.
1000mfd/100 volt, **70p**. P.P. 25p.
2200mfd/100 volt, **90p**. P.P. 25p.
4700mfd/25 volt, **65p**. P.P. 20p.
6800mfd/16 volt, **50p**. P.P. 15p.
10,000mfd/25 volt, **75p**. P.P. 25p.
47,000mfd/40 volt, **£2.00**. P.P. 50p.
100,000mfd/10 volt, **£1.50**. P.P. 50p.
160,000mfd/10 volt, **£2.00**. P.P. 50p.

3 GANG TUNING CAPACITOR

8.5pf to 320pf, **80p**. P.P. 20p.
10.7 M.H.Z. canned I.F.s Size 1½ x ½ in, **65p**. P.P. 10p.

KINNIE COMPONENTS 10 NELMES WAY, HORNCHURCH
ESSEX RM11 2OZ
HORNCHURCH 45167

MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT


Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotoh (Asia) Ltd., South Africa—Central News Agency Ltd. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, re-sold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

RADIO EXCHANGE LTD.

**REDUCTIONS ON ALL KITS
FOLLOWING VAT CHANGES**

NEW EDU-KIT MAJOR

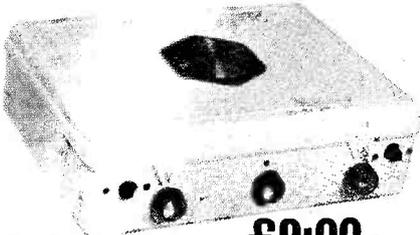Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder



Total Building Costs £9.00 INC. VAT
P & P - Ins. 65p. (Overseas Seamail P & P £3.50)

- ★ 4 Transistor Earpiece Radio
- ★ Signal Tracer
- ★ Signal Injector
- ★ Transistor Tester NPN-PNP
- ★ 4 Transistor Push Pull Amplifier
- ★ 5 Transistor Push Pull Amplifier
- ★ 7 Transistor Loudspeaker Radio MW/LW
- ★ 5 Transistor Short Wave Radio
- ★ Electronic Metronome
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Regenerative Radio
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier

Components include: 24 Resistors ★ 21 Capacitors ★ 10 Transistors
★ 3 1/2 Loudspeakers ★ Earpiece ★ Mica Baseboard ★ 3 12-way connectors
★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs
★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 6 1/2 yards of wire
★ 1 Yard of sleeving, etc. Complete kit of parts including construction plans.

VHF AIR CONVERTER KIT


Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Use a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.



All Parts including Case and Plans. **£3.95** P & P and Ins. 40p. INC. VAT

NEW Everyday Series

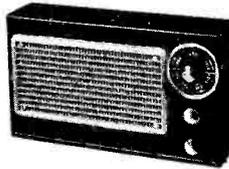Build this exciting new series of designs.



E.V. 5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. All parts including Case and Plans.

Total Building Costs **£4.30** INC. VAT P & P + Ins. 50p

E.V. 6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. All parts including case and plans.

Total Building Costs **£4.95** INC. VAT P & P + Ins. 55p

E.V. 7. Case and looks as above, 7 Transistors and 3 diodes. Six waveband, MW/LW, Trawler Band SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. All parts including Case and Plans

Total Building Costs **£6.35** INC. VAT P & P + Ins. 55p

TRANSONA FIVE




NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List free with parts.

Total Building Costs **£4.05** P & P + Ins. 50p

EDU-KIT

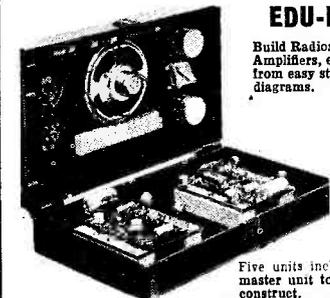Build Radios, Amplifiers, etc. from easy stage diagrams.



Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine-tune 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All Parts including Case and Plans **£6.30** INC. VAT P & P + Ins. 55p

POCKET FIVE

NOW WITH 3" LOUDSPEAKER
8 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx.




Total Building Costs **£3.60** INC. VAT P & P + Ins. 50p.

ELECTRONIC CONSTRUCTION KITS

ECK 2 Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker, Gain Control. Superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. (Loc) Stations, etc. Operates from a 9 Volt PPT Battery (not supplied with kit).

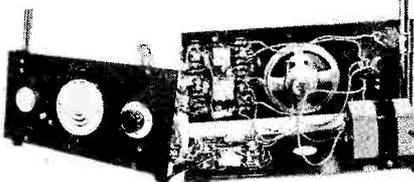Complete kit of parts including construction plans **£7.15** INC. VAT P & P and Ins. 55p.



ECK 4 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5" x 3" Loudspeaker.

Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 8" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor. Resistors, Capacitors, etc. Operates from a 9 Volt PPT Battery (not supplied with kit). Complete kit of parts including construction plans. **£6.55** INC. VAT P & P and Ins. 55p.



EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage - No Battery necessary.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage.
- ★ 4 Transistor Medium Wave Loudspeaker Radio.
- ★ Electronic Noise Generator
- ★ Electronic Metronome.
- ★ 4 Transistor Push/Pull Amplifier.

All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.55 INC. VAT P & P + Ins. 55p

JIFFY TESTER

Easy to build and operate. Fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Complete with earpiece, jack plug and socket resistors, capacitors, components, etc. Complete kit of parts including construction plans.



£2.85 P & P + Ins. 30p INC. VAT

**TO RADIO EXCHANGE LTD.,
61A HIGH STREET, BEDFORD MK40 1SA
Tel: 0234 52367.**

ALL PRICES INCLUDE VAT Reg. No. 788372

- ★ Callers side entrance "Lavelis" Shop.
- ★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.


I enclose £.....
for.....
Name.....
Address.....

PW776

Make it with MAPLIN!


ELECTRONIC COMPONENTS
WIDE RANGE • HIGH QUALITY • FAST SERVICE

The 4600 SYNTHESISER

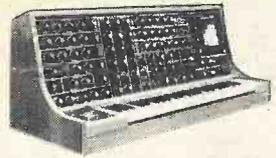

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or send SAE for specification.

ELECTRONIC ORGAN

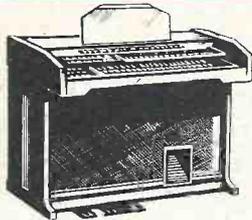


BUILD IT YOURSELF ... IN STAGES

Get started with a 49 note instrument - features tremulant and reverberation. Ideal to learn on. Leaflet MES 51. Price 15p gives full details to build this complete instrument.

Extend the range of MES 51 by adding another keyboard and several new tone colours. Leaflet MES 52. Price 15p also shows how to use 61 note keyboards.

Fully controllable attack and decay controls (normally found only on the most expensive organs), up to seven footages on each keyboard, up to 70 controls including drawbars, and a 13 note pedalboard, make up the additions described in the step-by-step 32 page instruction leaflet MES 53. Price 35p.

GRAPHIC EQUALIZER

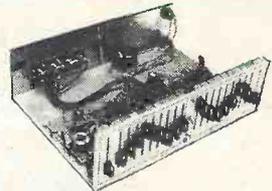

A really superior high quality stereo graphic equalizer featuring 9 octaves per channel. We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

DIGITAL CLOCK KITS

ONLY **£8.60** INC. VAT
E/P/P



This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied. Simple to connect

to alarm and your battery/mains radio. Smart case available shortly. Data sheet available separately. Please send SAE.

- Bright 4 Digit 0.5" Display
- Flashing Colon (1Hz)
- Switch for Display Seconds
- Alarm Set Indicator
- P.M. Indicator
- Power Failure Indicator
- Sleep Timer
- Snooze Timer
- Time can be set accurately to within one second
- Leading Zero Blanking

SIMPLE ALARM KIT - £9.38 ALARM CLOCK KIT - £10.99.
ALARM CLOCK & RADIO CONTROLLER KIT - £11.51.
SMART PLASTIC CASE with fully punched chassis - £1.99.

Please send SAE for our Clock data sheet.



100 W PER CHANNEL STEREO DISCO

- Automatic voice operated fader
- Belt drive turntables
- Monitor facilities (Headphones and VU meters)
- Sound operated light show - plus many other advantages.

Send for our leaflet MES 41, giving full details for construction. Price 20p. Soon you'll be the Deejay everyone wants at their party!

Get our FABULOUS NEW 1977/78 CATALOGUE

PUBLICATION DATE OCT. 28, 1976 ON APPROVAL

All new . Completely re-written . Hundreds of new lines.
Lots of exciting new projects to build - PRICE 50p.
SEND NO MONEY NOW. Overseas send 8 International reply coupons.

JOIN OUR MAILING LIST NOW!
Published every two months our Newsletter gives full details of our latest guaranteed prices. Send just 30p and we'll send you the next six news letters as they are published.

- SAVE ££'S ON SPECIAL OFFERS!
- DETAILS OF NEW PROJECTS AND NEW LINES

Please rush me a copy of your brand new 1977/78 catalogue the instant it is printed (October 28th, 1976). Only if I am completely satisfied that it is worth every penny will I send 50p within 14 days of receipt. If I am not satisfied I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____

PW

ADDRESS _____



MAPLIN ELECTRONIC SUPPLIES
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.
Shop: 284 London Road, Westcliff-on-Sea, Essex
(Closed on Monday). Tel: Southend (0702) 44101

If you do not wish to cut magazine, write your request for catalogue on separate sheet.
1975/76 GREEN COVER CATALOGUE STILL AVAILABLE PRICE 40p