

FEB
1978

practical WIRELESS

45p

ECONOMY TIMING STROBE

THE IGNITION SYSTEM



Fig. B.3
When the groove in the crankshaft is
with the small projection on the
and 4 pistons

ALSO:
ACTIVE TONE CONTROL
PLUS ALL THE USUAL FEATURES

the engine is now started...
rear flange of the crankshaft pulley...
the small projection on the timing...
piston is exactly at T.D.C. (see Fig. B.3...
Set the contact breaker points to 014...
(5) Screw the distributor into its housing, and engage...
dog lugs with the drive shaft teeth (both...
which are offset) by slowly rotating the rotor...
clamp plate to the distributor housing, and do not...
tighten them. Failure to leave these bolts slack will...
cause misalignment of the distributor resulting in...
excessive wear of the drive gears.
(6) Position the distributor so that the vacuum...
diaphragm to the rear.
the points are fully closed. Then the vacuum...
in a clockwise direction. Until the...
commence to open. Secure the...
pinch-bolt and nut, give the...
allow fully tighten the...
that the rotor arm is...
for the cylinder wh...
tion stroke
IMPORTANT:
an electrical...
actual pos...
following...
W...
trib...

tion B.7
The igni...
ments of...
INFORM...
After...
distrib...
ins...
order...
contact...
its pivot...
polish the...
subolt. After...
and apply a...
of the pivot. The...
should be between...
(ms) measured at the...
07 and...
of...
fact...
ap...
Se...
D...
the dr...
the un...
Extra...
plate

...VING AND REPLACING THE...
DISTRIBUTOR...
...tor can be removed and re...
with the ignition timing, pro...
bolt is not disturbed. ...
the replacement of ...
cover and turn it ...
... position po...
... lead from the terminal on...
the suction advance pipe at...
... the distributor clamp...
... and withdraw the

...os. 1
... Issue 2 27

T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD Etc

7400 14p	7413 30p	7432 25p	7454 15p	7490 35p	74121 30p	74139 100p	74156 70p	74174 100p	74189 350p
7401 14p	7414 60p	7437 25p	7460 15p	7491 75p	74122 60p	74141 60p	74157 70p	74175 75p	74190 140p
7402 14p	7416 30p	7438 25p	7470 30p	7492 25p	74123 60p	74142 270p	74160 90p	74176 100p	74191 140p
7403 14p	7417 30p	7440 15p	7472 25p	7493 40p	74125 50p	74143 270p	74161 90p	74177 100p	74192 120p
7404 14p	7420 15p	7441 65p	7473 30p	7495 60p	74126 50p	74144 270p	74162 90p	74178 140p	74193 120p
7405 14p	7422 20p	7442 65p	7474 30p	7496 70p	74130 130p	74145 75p	74163 90p	74179 140p	74194 100p
7406 40p	7423 25p	7445 80p	7475 30p	74100 95p	74131 100p	74147 230p	74164 125p	74180 100p	74195 100p
7407 40p	7425 25p	7446 85p	7476 30p	74104 40p	74132 65p	74148 160p	74165 125p	74181 200p	74196 100p
7408 20p	7427 25p	7447 75p	7477 30p	74105 30p	74135 100p	74150 120p	74166 125p	74182 75p	74197 100p
7409 20p	7428 40p	7448 70p	7483 85p	74107 30p	74136 80p	74151 65p	74167 125p	74183 150p	74198 185p
7410 15p	7429 15p	7449 15p	7485 100p	74109 50p	74137 100p	74152 70p	74168 125p	74184 150p	74199 185p
7411 20p	7430 15p	7451 15p	7486 30p	74118 90p	74138 125p	74153 70p	74169 125p	74185 150p	
7412 20p		7453 15p	7489 250p	74120 90p					

SEMICONDUCTORS by MULLARD, TEXAS, MOTOROLA, SIEMENS, I.T.T., R.C.A.

AA113 10p	BA138 16p	BC168B 14p	BC548C 14p	BF123 45p	BF336 35p	BY164 50p	OC140 150p	TIP35A 230p	2N1305 30p
AAZ17 30p	BA148 16p	BC168C 15p	BC548C 13p	BF125 45p	BF337 35p	BYX94 8p	OC171 40p	TIP35C 280p	2N1306 38p
AC121 30p	BA154 12p	BC169C 15p	BC549C 14p	BF127 50p	BF363 60p	C1120 30p	OC200 80p	TIP36A 350p	2N1308 50p
AC126 19p	BA157 15p	BC171 12p	BC557 13p	BF186 30p	BF594 30p	C1164 20p	ORP12 70p	TIP41A 70p	2N1711 22p
AC127 19p	BA173 15p	BC178C 12p	BCY34 80p	BF187 25p	BFV58 20p	E100 42p	R1039 150p	TIP41C 80p	2N2219A 25p
AC127/01 25p	BA216 16p	BC178A 16p	BCY70 15p	BF173 25p	BFV59 30p	E300 47p	TIP29 45p	TIP41C 80p	2N2483 30p
AC128 18p	BA316 16p	BC182 16p	BCY71 15p	BF179 35p	BFX81 130p	E430 125p	TIP29A 47p	TIP42B 85p	2N2906 18p
AC151 25p	BAX13 5p	BC182L 12p	BCY72 15p	BF179C 40p	BFX84 25p	MJE340 45p	TIP30 55p	TIP295 70p	2N307 20p
AC153K 40p	BAX16 5p	BC183 10p	BD121 85p	BF180 30p	BFX85 30p	MPSA06 25p	TIP30A 58p	TIP305 55p	2N3053 20p
AC176 20p	BB105A 35p	BC183L 12p	BD123 100p	BF181 35p	BFX87 25p	OA10 40p	TIP30B 58p	TIS90 25p	2N3054 50p
AC177 35p	BC110 45p	BC184 12p	BD124 85p	BF182 30p	BFX88 25p	OA47 15p	TIP30B 58p	TIS91 25p	2N3055 60p
AC179 30p	BC107 10p	BC184L 12p	BD131 36p	BF183 30p	BFY50 20p	OA90 6p	TIP30B 58p	TIS91 25p	2N3055 60p
AD149 80p	BC108 10p	BC186 24p	BD132 39p	BF186 25p	BFY52 20p	OA91 6p	TIP30B 58p	TIS91 25p	2N3055 60p
AD161 40p	BC108C 15p	BC205 14p	BD133 45p	BF194 10p	BFY90 125p	OA202 6p	TIP30B 58p	TIS91 25p	2N3055 60p
AD162 40p	BC109 10p	BC212 11p	BD135 40p	BF195 10p	BR101 35p	OC23 200p	TIP30B 58p	TIS91 25p	2N3055 60p
AD161/2MP 90p	BC109C 14p	BC212L 12p	BD136 40p	BF196 10p	BRV39 35p	OC25 100p	TIP30B 58p	TIS91 25p	2N3055 60p
AF114 22p	BC113 12p	BC213L 12p	BD137 38p	BF197 10p	BRV39 35p	OC28 75p	TIP30B 58p	TIS91 25p	2N3055 60p
AF115 22p	BC117 18p	BC214 13p	BD139 40p	BF198 25p	BRV39 35p	OC35 75p	TIP30B 58p	TIS91 25p	2N3055 60p
AF116 22p	BC125 20p	BC214L 14p	BD139 40p	BF199 25p	BRV39 35p	OC42 35p	TIP30B 58p	TIS91 25p	2N3055 60p
AF117 22p	BC126 15p	BC258 13p	BD140 40p	BF200 30p	BRV39 35p	OC43 35p	TIP30B 58p	TIS91 25p	2N3055 60p
AF118 50p	BC146 12p	BC294 35p	BD181 80p	BF224 20p	BRV39 35p	OC45 35p	TIP30B 58p	TIS91 25p	2N3055 60p
AF125 25p	BC147 10p	BC303 55p	BD182 80p	BF225 20p	BRV39 35p	OC71 25p	TIP30B 58p	TIS91 25p	2N3055 60p
AF139 35p	BC148 10p	BC317 15p	BD207 70p	BF241 16p	BU105 150p	OC72 30p	TIP30B 58p	TIS91 25p	2N3055 60p
AF239 45p	BC157 10p	BC323 60p	BD233 60p	BF244B 35p	BU153 75p	OC75 30p	TIP30B 58p	TIS91 25p	2N3055 60p
AS126 40p	BC159 10p	BC328 13p	BD263 85p	BF257 28p	BU100 20p	OC81 30p	TIP30B 58p	TIS91 25p	2N3055 60p
BA114 9p	BC158 10p	BC338 12p	BDY10 100p	BF258 26p	BY100 20p	OC81D 25p	TIP30B 58p	TIS91 25p	2N3055 60p
BA121 9p	BC159 10p	BC547 12p	BDY62/01 90p	BF259 30p	BY126 15p	OC83 50p	TIP30B 58p	TIS91 25p	2N3055 60p
	BC167A 12p	BC547B 12p	BF120 50p	BF274 15p	BY127 15p	TIP35 225p	TIP35 225p	TIP35 225p	2N3055 60p
		BC548 12p	BF121 45p	BF324 30p	BY133 22p	OC84 50p			

555 TIMERS 100 for £30

ROTARY SWITCHES BY LORLIN

1P 12W	40p
2P 6W	40p
3P 4W	40p
4P 3W	40p
BZY88	
400M.W. Zeners	
OV7	10p
2V4	10p
2V7	10p
3V0	10p
3V3	10p
3V6	10p
3V9	10p
4V7	10p
5V1	10p
5V6	10p
6V2	10p
6V8	10p
7V5	10p
8V2	10p
9V1	10p
10V	10p
11V	10p
12V	10p
13V	10p
15V	10p
18V	10p
20V	10p
22V	10p
27V	10p
30V	10p
33V	10p
100 Mixed Zeners 850p	

DIL SOCKETS

8 Pin	13p
14 Pin	14p
16 Pin	15p

741 Op AMPS 100 for £20

ELECTROLYTIC CAPACITORS

µF/V		
47/25	5p	330/35 16p
1/16	5p	470/10 12p
1/25	5p	470/25 12p
1/50	5p	470/35 18p
2-2/25	5p	470/50 22p
2-2/35	5p	680/25 25p
3-3/25	5p	1000/16 25p
4-7/10	5p	1000/35 30p
4-7/16	5p	1000/63 50p
4-7/25	5p	2200/10 28p
4-7/50	5p	2000/35 50p
6-8/25	5p	2200/16 35p
10/10	5p	2200/63 75p
10/16	5p	2200/100 120p
10/25	5p	3300/16 40p
10/35	5p	3300/25 42p
10/50	5p	3300/63 80p
22/6V3	5p	3300/63 80p
22/10	5p	4700/25 45p
22/16	5p	4700/40 50p
22/25	5p	4700/63 20p
22/35	5p	
22/50	6p	
33/6V3	5p	
33/16	6p	
33/25	6p	
33/40	6p	
33/50	7p	
47/10	6p	
47/16	6p	
47/25	6p	
47/35	6p	
47/50	7p	
100/10	6p	
100/16	6p	
100/25	6p	
100/50	8p	
100/63	10p	
125/15	6p	
125/16	6p	
220/16	10p	
220/25	12p	
220/50	20p	
330/25	15p	

POLYMER CAPACITORS

µF	
0.001	5p
0.002	5p
0.003	5p
0.004	5p
0.005	5p
0.006	5p
0.007	5p
0.008	5p
0.01	5p
0.02	5p
0.03	5p
0.04	5p
0.05	5p
0.1	6p
0.2	7p
0.3	8p
0.4	8p
0.5	12p
1.0	20p
2.2	25p
4.7	35p
6.8	40p

RESISTORS CARBON FILM 5%

25 W	2p
2-2 Ω-4-7M	2p
5 W	
2-2 Ω-4-7M	2.5p
1 W	
2-2 Ω 10 MEG	3-5p

POTENTIOMETERS

1K Lin	30p
5K Lin	30p
10K Lin	30p
25K Lin	30p
50K Lin	30p
100K Lin	30p
250K Lin	30p
500K Lin	30p
1 Meg Lin	30p
2 Meg Lin	30p
5K Log	30p
10K Log	30p
25K Log	30p
50K Log	30p
100K Log	30p
250K Log	30p
500K Log	30p
1 Meg Log	30p
2 Meg Log	30p

SPECIAL OFFERS

BC147	
BC148	
BC149	
BC157	100 ASSORTED FOR £7.50p
BC158	
BC159	
BF194	
BF195	
BF196	
BF197	

CMOS

4000	20p	4023	20p	4055	140p
4001	20p	4024	100p	4056	145p
4002	20p	4025	20p	4060	130p
4005	120p	4026	200p	4066	55p
4007	20p	4027	85p	4069	30p
4009	70p	4028	155p	4071	30p
4011	20p	4029	130p		
4012	20p	4030	60p	4072	30p
4013	55p	4032	150p	4081	20p
4015	90p	4043	220p	4082	30p
4016	55p	4046	150p	4083	145p
4017	110p	4047	115p	4511	200p
4018	250p	4049	70p	4518	140p
4020	140p	4050	50p	4518	110p
4022	180p	4054	130p	4528	130p

BRIDGE RECTIFIERS

1A 50V	25p	V/REG.	
1A 100V	30p	7805	140p
1A 200V	30p	7812	140p
1A 400V	35p	7815	140p
1A 600V	40p	7815	140p
2A 50V	35p	7818	140p
2A 100V	50p	7818	140p
2A 200V	55p	7824	150p

SPECIAL SCOOP OFFERS

LEDS -125
OR 2 RED ONLY
100 for £9.00
1000 for £60.00
SPECIAL QUOTATION FOR LARGER QUANTITIES

SKELETON PRE-SET POTENTIOMETERS	LEDS -125 15p GREEN -125 25p YELLOW -125 25p RED -2 15p GREEN -2 25p YELLOW -2 25p DL747 0-6" Display 200p
---------------------------------	--

ENAMELLED COPPER WIRE 50GR REEL

CA3076	200p	SN76013N	125p
CA3085	85p	SN76013ND	125p
CA3088	190p	SN76023N	180p
CA3089	210p	SN76023ND	125p
CA3090AQ	400p	SN76227N	160p
CA3130	100p	SN76228N	180p
LM300TOS	170p	SN76568N	100p
LM301AN	65p	TA A300	150p
LM307N	65p	TA A350	190p
LM308TOS	130p	TA A550	50p
LM308DIL			

FEBRUARY 1978 · VOLUME 53 · NUMBER 10

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

News and Views

- 730 **EDITORIAL**—A time of change
- 731 **NEWS . . . NEWS . . . NEWS**
- 739 **PW READER'S PCB SERVICE**—Prices and details of the PCBs available
- 746 **TELEVISION**—Details of the February issue
- 749 **HOTLINES**—Recent developments in electronics *Ginsberg*
- 755 **KINDLY NOTE**—Jubilee organ, September–November 1977. Gas/Smoke Sensor Alarms, April 1977
- 758 **PRODUCTION LINES**—Information on the latest products *Bill Tull*
- 759, 778 **NEW BOOKS**—Comments on the latest books in the electronics field
- 763 **PRACTICAL WIRELESS**—Pre-view of our next issue
- 773 **ON THE AIR**—Amateur Bands *Eric Dowdeswell G4AR*
 SW Broadcast Bands *Charles Molloy G8BUS*
 MW Broadcast Bands *Charles Molloy G8BUS*
 VHF Bands *Ron Ham BRS15744*

For our Constructors

- 732 **MULTIVIB "MUSICO"** *R. H. Longden*
 A novelty music-box design
- 738 **IC OF THE MONTH**
 The Thomson CSF ESM 1601 Proximity Detector
- 745 **AUDIO DUMMY LOAD** *F. G. Rayer*
 An Amplifier test aid, offering a selection of impedances
- 750 **HEATSINK THERMOMETER** *Ian Hickman*
 A simple unit for checking transistor temperatures
- 752 **ECONOMY TIMING STROBE** *B. Harvey*
 Tune up your car and save petrol
- 756 **S-DECNOLOGY Project No. 12** *David Gibson*
 A continuity tester
- 760 **OSCILLOSCOPE VIEWING HOODS** *Maurice Allenden*
 A novel solution to stray light problems
- 762 **EXPERIMENTER'S CORNER**
 Simple Low-Z Preamp. Basic 9V Stabiliser

General Interest

- 740 **THE 5-METRE STORY—1** *Ron Ham*
 Memories of the days when amateurs were licensed to operate on the 60MHz band
- 764 **SO YOU WANT TO PASS THE RAE?—6**
 Dealing this month with drawings, valves and semiconductors
John Thornton-Lawrence GW3JGA and Ken McCoy GW8CMY
- 770 **THE FORCEFUL MR. FLEMING**
 A look at a problem posed by readers of our RAE Series
 Medium Wave Tuner/Amplifier, trailed last month, has been delayed. We hope to feature it in a forthcoming issue

COPYRIGHT

© IPC Magazines Limited 1978. Copyright in all drawings, photographs and articles published in 'Practical Wireless' is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by 'Practical Wireless' to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Sparkrite Mk2

Capacitive discharge electronic ignition kit

VOTED BEST OF 8 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE OCT 74



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

IMPROVE PERFORMANCE & ECONOMY NOW

Note—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. £3.35 inc. V.A.T. p & p. E.D.A. 82 BATH STREET, WALSALL, WS1 3DE.

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept., PW2
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQD.	
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		

I enclose cheque/PO's for £

Cheque No.

Send SAE if brochure only required.

Random FLASHER UNIT

Wired ready for use
Complete with three
100 watt coloured lamps
that flash independently
at random.

£18.95

TWIN BANK 6 LIGHT UNIT
(less lamps) LENGTH 14 1/2 inches

BC Fitting **£9.55** EACH
E.S. Fitting **£10.35** EACH

Sound to Light MASTER UNIT 600 WATTS PER CHANNEL

£30.95

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET.

TYPE A SPOT
(less lamp)

BC Fitting **£1.95** EACH
E.S. Fitting **£2.12** EACH

TYPE B 3 BANK UNIT
(Less Lamps)

BC Fitting **£6.90** EACH
E.S. Fitting **£7.26** EACH

TWIN BANK 12 LIGHT UNIT
Length 31 3/4

(less lamps)
BC Fitting **£15.60** EACH
E.S. Fitting **£17.00** EACH

100 WATT SPOT LAMPS
RED, YELLOW, GREEN
BLUE CLEAR **£1.50** each
Maximum 3 lamps **£4.50**

B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. and POST & PACKING
(These prices apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list.

ALBEN ENGINEERING CO. LTD.
DEPT. P W THE CRESCENT, WORSTHORNE,
BURNLEY, LANCS. Tel Burnley 20940

THE IDEAL ANYTIME PRESENT

S · R · B

MINIATURE SOLDERING IRON
for HOBBY or TRADE

MAIL ORDER PRICES:
(including VAT and P and P)

Irons £3.70 each

Bits 41p. each

(Bit type 20 fitted as standard).

Stands £3.90 each

Solder 28p & 56p.

18 watts of power at 240 v. straight to the bit

BIT SIZES:
19 (1.5 mm) 20 (3.0 mm)
21 (4.5 mm) 22 (6.0 mm)

Trade Enquiries Welcome

From your Local Dealer or Direct from the Manufacturers:

S. & R. BREWSTER Ltd.
86-88 UNION ST · PLYMOUTH Tel 0752.65011

AS ADVERTISED ON TV

JANUARY SALE - MANY ITEMS HALF PRICE

ALL PRICES GROUP/DISCO EQUIP. REDUCED - SALE ENDS 31st JAN.

LIGHTING by FAL. OPTIKENETRIKS & PULSAR - GROUP EQUIPMENT by CARLSBRO, FAL, TITAN Etc.

RSC 100 WATT DISCO SYSTEM



Consisting of
(1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES
(2) & (3) PAIR 50 WATT LOUD-SPEAKERS including 12" UNITS

Or Dep £16.49 & 18 f'tnly pymts. £6.75 (Total £137.99) Carr. £3.50. (£109.95)

★ DISCOMAJOR POWER DISCO CONSOLE with integral Power Amplifier.
★ TWIN FULL SIZE BSR turntables with cueing device.
★ CARTRIDGES with Diamond Styli.
★ 3 SEPARATE VOLUME CONTROLS for each turntable and Mic. CONSOLE COMPLETE WITH LID. FULL HEADPHONE MONITORING FACILITIES
Terms: Deposit £30.00 and 18 fortnightly pyts. £9.80 (Total £206.40) Carr. £4.75. (£159.95)

Also available 200 WATT SYSTEM (£189.95)

TD1 DISCO CONSOLE Incorporating twin BSR type turntables & Sonotone or Acos Cartridges with diamond styli. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate Input for 'mike' with vol. control. Black Vynide covered Cabinet with lid.
Carr. £3.50. (£109.95)

TD2S STEREO VERSION OF ABOVE (£119.95) Carr. £3

ALL RSC PRICES INCLUDE VAT INTEREST REFUNDED on Credit Purchases settled in 3 mths

TITAN 100W BASS BINS £89.95

High quality 15" high flux Bass Unit and J104 Horn Tweeter in folded horn enclosure providing amazing level of sound output. Terms Dep. £14.95 and 18 fortnightly payments. £5.58 (Total £115.39) Carr. £3.50. Value £145.



FANE HIGH POWER SPEAKERS

POP 33T 12" 33w (£10.95)
POP 50/2 12" 50w (£13.99)
POP 75 12" 70w (£18.99)
POP 60 15" 60w (£15.95) POP 100 18" 100w (£39.95)

SALE PRICES

shown in BRACKETS Terms apply to normal prices

TITAN GROUP/DISCO SPEAKERS GUARANTEED

Carr. £1.20, under £18, over this add 6p per £1. 5 YEARS

Value	RSC Price
T12/45 12" 45w	£15.00 (£11.95)
T12/60A 12" 60w	£21.00 (£13.95)
T12/100 12" 100w	£36.00 (£25.95)
T15/60 15" 60w	£26.00 (£16.99)
T15/70 15" 70w	£28.00 (£19.95)
T15/100 15" 100w	£41.00 (£29.95)
T18/100 18" 100w	£47.00 (£36.95)

CABINETS FOR ABOVE Heavy duty, finished in black Vynide with Vynair fronts, protective corner pieces Vynair sizes and cut-outs. TE1 1 x 12" £11.95 (£10.95) Carr. £1. TE2 2 x 12" (£15.95). Low Deposit Terms on orders over £20.




TITAN TA/100C COMBO

100w R.M.S. Amp. incorporating a fabulous Fane Crescendo 12" 100 watt spkr for really superlative results with Lead Guitar (£99.95) Val. £149 Carr. £6 Or Dep £17.95 & 18 f'tnly payts £6.69 (Total £138.37)

DISCO MAJOR/100 TWIN TURNTABLE POWER CONSOLE (£119.95)

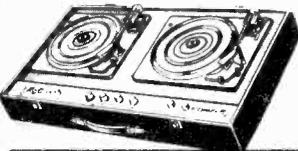Twin Full size BSR turntables. Sonotone or Acos Cartridges with Diamond Styli. Facilities as TD1 Console but with built-in 100 watt Power Amplifier complete with lid. Terms: Deposit £19.95 and 18 fortnightly payments £7.70 (Total £158.55) Carr. £3.50



DISCOMAJOR/200 (£139.95) Carr. £4.00


200 watt version of above. Terms: Dep. £29.95 and 18 fortnightly payments £8.60 (Total £184.75)



RSC PHANTOM 50 COMBO AMP. (£55.50)

Rating 50 watts. 3 inputs, 2 vol controls—Bass, Treble Presence. Suitable for Lead or Rhythm Guitar, mic., Radio, Tape, etc. Inc. High Flux 12" 50w Speaker. Dep. £10.95 & 8 monthly payments £8.71 (Total £80.63) Carr. £2.

100W POWER (SLAVE) AMPLIFIER

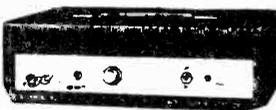


Suitable for use with DISCO-Consoles. Also for increasing output of lower-powered Amplifier. Dep. £9.00 and 8 mthly pyts of £6.05 (Total £57.40) Carr. £1.50 (£44.50)

100+100W MODEL (£57.75) Carr. £1.50

TITAN TA/50A 50W AMPLIFIER

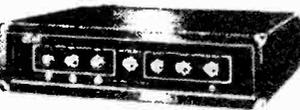Solid state. 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. with corner protectives. Value £60. Terms: Dep. £9 & 8 monthly payments £6.05. (Total £57.40) Carr. £1. (£36.95)



TITAN TA/100A 100W AMPLIFIER


TWIN CHANNEL—4 INPUTS (NORMAL OR BRIGHT) A De-luxe professional unit with many facilities. R.M.S. Rating. Matching 2 x 12" 120w Cabinet speaker £49.95 with above only. Carr. £1.50 (£59.95)



TITAN 'ADD-ON' HIGH FREQUENCY HORN UNITS



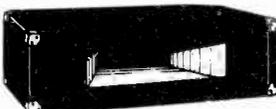MODEL TS2H
Inc. Pair of highly sensitive Horns. Range 3-15 kHz Imp 16Ω. Use with 8 or 15Ω 2 x 12" or 1 x 15" or 18" Drive Unit for increased sound clarity and projection. Rating 100 watts. Either model (£17.95) Carr. 95p
Terms: Dep £6.95 & 8 mthly pyts £3.12 (Total £31.91)



MODEL TIH
With single super efficient Horn. Range 3-15 kHz. Imp 8Ω. Use with max 8Ω 2 x 12" or single 15" or 18" 8Ω Drive Units. Maximum amplifier power output to be 100 watts. Comparable with units at twice the cost.

FANE HIGH FREQUENCY HORNS 'J' SERIES

MODEL J44 Imp 8Ω
Size approx. 3 1/4" x 3 1/4" x 3"
Rating 30-50 watts Range 3-15 kHz
Carr. 60p. (£3.99)

MODEL J73 Imp 8Ω
Size approx 7 1/4" x 3" x 6 1/4"
Rating 50 watts Range 2-20 kHz
Carr. 75p (£5.95)

FAL DISCO LIGHTING SYSTEMS from (£55.95)

Incl 2 Spotbanks and bulbs



MODEL J104 Imp 8Ω
Size approx 10 1/4" x 3 1/4" x 7 1/4"
Rating 50-70 watts Range 2-15 kHz
Carr. 75p (£7.75)

'CROSSOVERS' HFXIR & HFXIR (£2.25)

NEW BRANCHES AT HANLEY AND WOLVERHAMPTON

OPEN ALL DAY SATURDAYS (5 Day Week)
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)
CARLISLE 8 English Street (Closed Thurs.). Tel. 38744
COVENTRY 17 Shelton Sq., The Precinct. Tel. 25983
DERBY 97 St. Peter's Street (Closed Wed.). Tel. 41361
DARLINGTON 19 Northgate (Cl. Wed.). Tel. 68043
DUNSBURY 9/11 Kingsway (Closed Tues.). Tel. 468058
DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069
EDINBURGH 101 Lothian Rd. (Cl. Wed.). Tel. 229 9501
GLASGOW 326 Argyle St. (Cl'd Tues.). Tel. 248 4158



HANLEY Stoke-on-Trent, 44 Piccadilly

HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LEEDS 16 County (Mecca) Arcade, Briggate. (Closed Wed.). Tel. 449609.
LIVERPOOL TEMPORARILY INOPERATIVE due to serious fire.
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629
MANCHESTER 30A Oldham Street (Closed Wed.). Tel. 236 2778

Barclaycard & Access PHONE ORDERS quoting CARD NUMBER accepted MAIL ORDERS & EXPORT ENQUIRIES TO—AUDIO HOUSE, HENCOXNER LAKE, LEEDS, 18. Tel: 0632 577881.

MAIL ORDERS MUST NOT BE SENT TO SHOPS TERMS C.W.O. or C.O.D. under £3. POSTAGE 60p PER ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.

MIDDLESBROUGH 103 Linthorpe Rd. Tel. 247096 (Closed Wed.)
NEWCASTLE UPON TYNE 59 Grainger St. (Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street
PRESTON 41 Friargate Walk, St. Georges Shoppes Prec. Tel. 48068
SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.)
STOCKPORT (Closed Thurs.). Tel. 20716
8 Little Underbank (Closed Thurs.). Tel. 480-0777
SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573
WOLVERHAMPTON 6, Wulfrun Way. (Cl'd Thurs.). Tel. 26612

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!

★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKET DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 10000pF. Total 210, £3.35

K002 Extended range, 22pF to 0.1µF. 330 values £4.90

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75

K004 Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for £3.75

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF, E12 series 5% 160V. Total 370 for £12.30

K006 Tantalum bead capacitors. 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2, 3, 4, 7, 6, 8, all 35V; 10/25 15/18 22/16 33/10 47/6 100/3. Total 170 totals for £14.20

K007 Electrolytic capacitors 25V working, small physical size. 10 each of these popular values: 1, 2, 2, 4, 7, 10, 22, 47, 100µF. Total 70 for £3.50

K008 Extended range, as above, also including 220, 470 and 1000µF. Total 100 for £5.90

K009 Extended range, total 850 resistors from 1R to 10M £8.30

K010 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 27V to 36V, E24 series. Total 280 for £15.30

K011 As above but 5 of each value £3.70

71b BARGAIN PARCEL
Hundreds of new components—pots, switches, resistors, capacitors, PC Boards with semiconductors, loads of odds and ends. Amazing value at only £3.45.

PC ETCHING KIT MK III
Now contains 200 sq. ins. copper clad board, 1lb. Ferric chloride, DAPL etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.15

FERRIC CHLORIDE
Anhydrous technical quality in 1lb double sealed packs. 1lb £1.00; 3lb £2.18; 10lb £5.60; 100lb £39.00

MOTORS
240V ac 60 rpm. High torque, drive to 6mm shaft 20mm long. Size 70mm dia x 55mm £2.20.

LED DIGIT DRIVER
ITT type 7105. 16 pin DIL package. Supplied with data sheet. 8 for £1.

VERO OFFCUTS
Pack A, All 0.1" Pack B, All 0.15"
Pack C, Mixed Pack D, All 0.1" Plain
Each pack contains 7 or 8 pieces with a total area of 100 sq. in. Each pack is £1.40. Also available by weight. 1lb £3.45, 10lb £31.

17 x 3 1/2" Strips: 0.1" £2.20; 10 for £15
0.15" £1.96
0.1" Plain £1.83

Our retail shops at 21 Deptford Broadway, London, SE8 (01-692 2009) and 38 Lower Addiscombe Road, Croydon (01-888 2950) stock some of the advertised goods for personal callers only. Ring them for details.

All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

SIRENS

Work off 4 x HP7 batteries, emit very loud noise. Overall size 110 x 75 x 60mm. Use as Burglar Alarm in car, house, workshop, etc. ONLY £1.95.

VEROCASES

Plastic top and bottom, ally panels front and back.

Type	
1410 205 x 140 x 40mm	£3.70
1411 205 x 140 x 75mm	£4.17
1412 205 x 140 x 110mm	£5.20
1237 154 x 85 x 40mm	£2.83
1238 154 x 85 x 60mm	£3.05
1239 154 x 85 x 80mm	£3.75

VERO PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.

Type	
2518 120 x 65 x 40mm	£2.24
2520 150 x 80 x 50mm	£2.68
2522 188 x 110 x 60mm	£3.72

Sloping front version.

Type	
2523 220 x 174 x 100/52mm	£6.90
1798 171 x 121 x 75/37.5mm	£4.65

Gen. purpose plastic potting box 71 x 49 x 24. In black or white 40p. Hand Controller box, shaped for ease of use in the hand, 94 x 81 x 23mm 64p.

RELAYS AND SOLENOIDS

12V DC enclosed, 2 10A c/o contacts £1. Open construction relay with 2 10A c/o contacts, coil rated 24V ac, but works well on 6V DC 80p.
240V ac enclosed, 11 pin plug in base. 3 10A c/o contacts, £1.20.
240V ac open, 2 15A c/o contacts £1.50.
6V miniature low profile for PC mounting, 0.1" pitch. 2 pole c/o 137R coil—RS price £2.71—our price £1.90.
Solenoid, rated 48V DC, but work on 24V. 10mm push or pull action. Single hole fixing. Size 27 x 18 x 15mm. Made by Varley. Only 40p.

WIRE AND FLEX

Flex pack—5m of 5 diff. colours, thick or thin. 25m for 30p. 25 way (14/0076) cable with braided overall screen and PVC sheath. 40p/m.

EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third their original list price!
18 way 41p; 21 way 47p; 32 way 72p; 40 way 90p; 43 way 97p; 49 way 111p.

SOLAR CELLS

As used on space labs, etc., these tiny cells give 50µA @ 0.5V in sunlight. Ideal for powering small C-MOS projects, etc. Can be banked together for greater power output. Size 18 x 6.5mm. 3 for £1; 10 for £3; 25 for £7; 100 for £25.

POWER PACK

Wood grained metal case 90 x 80 x 75mm containing mains transformer giving 6V @ 200mA, 2 co.-ax. sockets, PC board with 1 1/2 fuseholder R's c/s, etc. Only £1.

S-DECS & T-DECS

S-DEC Breadboard	£2.25
T-DEC Breadboard	£3.95

1977/78 CATALOGUE NOW AVAILABLE — MUCH BIGGER AND BETTER, WITH 50p DISCOUNT VOUCHERS ONLY 30p, Plus 15p POST.

COMPONENT PACKS

400 asstd. carbon resistors	£1.50
100 Wirewounds 2-15W	£1.50
200 Miniature resistors, 1, 1, and 1W	£1.30
200 poly, mica, ceramic caps	£1.20
100 polyester, .01-2.2uF	£1.00
200 PC resistors	75p

TEXAS 741

8 Pin DIL—Full Spec.

100 off £19.50

25 off £5.50

WIRELESS TIME :



approx. 3/4 full size digits shown here

National's MA1012 LED digital clock module is a complete clock & alarm unit, operating from 50 or 60 Hz mains, and offering all the features you would expect: Hours-minutes display in bright 0.5" leds with optional seconds, sleep and snooze alarms, fast and slow setting, AM/PM indicator, switched alarm outputs - but best of all no RFL. Thus the MA1012 is suitable for use in any radio/tuner applications, and requires just 1.75 x 3.75 x 0.7" total. (Ex. transformer). £9.45 per module, isolating mains transformer £1.50 each. (*8% vat) Two modules, and two transformers for £20.00 (+8% vat)

In the latest Ambit catalogue: more TOKO coils, chokes, filters etc., data on the short wave coil sets, a revised price list, micro-microphone inserts, special offer lines etc.

DETECKNOWLEDGEY

Metal locator principles and practise, including some of the facts and information manufacturers of £100+ detectors would rather you didn't know. £1.00 each.

The Bionic Ferret 4000 - a VCO metal locator based on the PW seekit, including all parts, plasticwork, ready wound coil etc. Inc. free copy of detecknowledgey. £34.26 in pp and VAT at 8%.

Special announcement. The Bionic Radiometer metal locator is at last to be released. A full VLF discriminator, with simultaneous display of ferrous, non-ferrous and foil objects. With a little practise, you can actually find objects obscured by junk. Outperforms units costing £150+. Digital control. Demo available at Brentwood, on sale soon for less than £75.SAE info:

COMPONENTS

Herewith the list of first quality parts and modules for wireless, inc. Europe's largest range of signal coils and inductors. 1/2m in stock!

CA3089E	FM IF 1.94	BC413	lo noise 0.18	MFL 2.4 kHz sbb mech.
KB4402	FM IF 1.94	40238	shld RF 0.25*	filter for sbb gen/IF 455kHz
HA1137FM	FM IF 2.20	BF224	6ghz RF 0.22	with matching transfs. 9.95
TBA120	FM IF 0.75	BF274	7ghz RF 0.18	MFH series 4/5/7kHz band-
TBA120S	FM IF 1.00	ZT X212	50v/.3w 0.17	width @ 455kHz 1.95
sn76660n	FM IF 0.75	ZT X213	30v/.3w 0.16	MFK series 7/9kHz bw 1.65
ua720	AM rad 1.40	ZT X214	30v/.3w 0.17	Modules/tunerheads etc.
CA3123E	AM rad 1.40	ZT X451	60v/1w 0.18	EC3302 3cct v/cap fm 7.50
HA1197	AM rad 1.40	ZT X551	60v/1w 0.18	EF5600 5cct v/cap fm 12.95
TBA651	AM rad 1.81	BD515	45v/10w 0.27	EF5800 6cct v/cap fm 15.25
MC1350	agc gain 1.00	BD516	45v/10w 0.30	EF5801(5800+osc op) 17.45
ua753	fm gain 1.80	BD535	60v/50w 0.52	8319 4 v/c, mso mixer 11.45
LM1496	Bal mix 1.25	BD536	60v/50w 0.53	7252 complete fm mono
MC1310P	mpx dec2.20	BD609	80v/90w 0.70	tunerset. afc, agc, mute 26.50
KB4400	as above 2.20	BD610	80v/90w 1.20	7253 complete fm stereo
ca3090aq	mpx dec4.35	BF256	1ghz fet 0.34	tunerset. afc, agc, mute 26.50
HA1196	mpx dec2.40	E176	p ch swt 0.38	7020 10.7MHz fm if 6.95
LM380	2w AF 1.00	MEM614	(40822) 0.38*	7030 linear phase fm if 10.95
LM381	preamp 1.81	MEM616	(40673) 0.67*	93090 ca3090aq dec 8.36
tda2020	15w AF 2.99	MEM680	lo noise 0.75*	92310 1310 decoder 6.95
tc940E	10w AF 1.80	BA102	vhf varic 0.30	91196 ha1196 decoder 12.99
tb810as	7w AF 1.08	BA121	vhf varic 0.30	91197 mw/lw v/cap tun11.35
LM301an	op amp 0.39*	BB104	dual var. 0.45	7122 3 v/c mw (OR lw) tuner
ua741	op amp 0.34*	BB105	uhf varic 0.40	KIT 15v tuning 9.00
LM3900	op amp 0.68*	mvam2	dual AM 1.48	810k 7w af kit comp. £3
7805uc	5v/1amp1.55*	mvam115	15v/AM 1.05	940k 10w af kit 3.95
tda1142	12v/1/2 A 0.95*	mvam125	25v/AM 0.90	tda2020k pr. tda2020 ics,
78M20	20v/1/2 A 1.20*	LLC238	7mm 0.33	pcb, heatsinks for pa 9.35
78M24	24v/1/2 A 1.20*	LLC4827	7mm 0.33	All mpx decoders feature
ua723cn	variable 0.80*	LLC4828	7mm 0.33	TOKO pilot tone filters.
NE550a	as above 0.80*	CF510	7 ceramic 0.50	Tuners: complete
taa550b	32v ref 0.50*	BLR3107N	mpx 1.90	Larsholt signalmaster Mk 8
ic18038cc	sig gen 4.50*	BBR3132	6pole ft 2.25	Best fm tuner kit under £100
NE555v	timer 0.70*			Looks as good as it sounds.
NE566v	vco 2.50*			Full instructions 86.95
NE567v	tone dc 2.50*			Audiomaster amp. Matching
NE560B	hf pll 3.50*			25+25w rms amp. 79.00
NE561B	hf pll 3.50*			<i>carriage on above £3 extra ea.</i>
NE565K	lf pll 2.50*			Misc.
MC1312	quad 1.50*			FX1115 beads 100.25
11C90	650mhz 14.00*			MW/LW ferrite rod ant 0.90
ZTX107	50v/.3w 0.14			min. foil trimmers (see pl)
ZTX108	30v/.3w 0.14			221 100k pots for tuning.45
ZTX109	30v/.3w 0.14			RFchokes: 1uH to 120mH

VAT is extra at 12 1/2%, except where otherwise shown (*8%). PP now 25p per order. Catalogue 45p (inc). Pse send A5 or larger SAE with enquiries. Price lists free with an SAE. Full range of components etc available to callers at our new easy-to-get-to premises.

ambit INTERNATIONAL

Number 2, Gresham Road, Brentwood, Essex. CM14 4HN
telephone (0277) 216029

Our new premises are only 200 yards from Brentwood station - with parking facilities outside the door !!

RST VALVE MAIL ORDER CO.

CLIMAX HOUSE, FALLS BROOK ROAD, LONDON SW16 6ED

SPECIAL EXPRESS MAIL ORDER SERVICE

SEMICONDUCTORS

AA119 0-20	AS226 0-45	BC159 0-13*	BCY72 0-17	BF194 0-12*	BZ561 0-20	OA70 0-30	OC82 0-75	ZS271 0-22*	2N697 0-16	2N3055 0-65
AA30 0-13	AS27 0-50	BC167 0-13*	BCZ11 1-50	BF195 0-11*	Series	OA79 0-30	OC83 0-55	ZS278 0-56*	2N698 0-30	2N3440 0-60
AA53 0-25	AS215 1-25	BC170 0-18*	BD115 0-60	BF196 0-13*	BZ788 0-13	OA81 0-30	OC84 0-60	ZTX107 0-11*	2N705 0-80	2N3441 0-80
AAZ15 0-31	AS217 1-25	BC172 0-13*	BD121 1-50	BF197 0-14*	Series	OA85 0-30	OC122 1-50	ZTX108 0-10*	2N706 0-12	2N3442 1-20
AAZ17 0-25	AS220 0-75	BC173 0-15*	BD131 0-51	BF224 0-30*	CRS/105 0-45	OA90 0-08	OC123 1-55	ZTX109 0-12*	2N708 0-21	2N3525 0-80
AC107 0-75	AS221 1-50	BC177 0-19*	BD132 0-54	BF244 0-35*	CRS/140 0-60	OA91 0-08	OC139 2-25	ZTX300 0-12*	2N930 0-26	2N3614 1-20
AC125 0-30	AU110 1-70*	BC178 0-18*	BD133 0-35*	BF257 0-37	CRS/305 0-45	OA95 0-08	OC140 1-95	ZTX301 0-13*	2N1131 0-26	2N3702 0-15*
AC126 0-25	AU113 1-70*	BC179 0-20	BD136 0-38*	BF258 0-42	CRS/340 0-75	OA200 0-10	OC141 2-25	ZTX302 0-17*	2N1132 0-26	2N3703 0-15*
AC127 0-25	AU117 1-70*	BC182 0-11*	BD137 0-37*	BF259 0-45	CRS/360 0-90	OC202 0-01	OC170 0-75	ZTX303 0-17*	2N1302 0-37	2N3704 0-15*
AC128 0-25	BA145 0-15*	BC183 0-11*	BD138 0-40*	BF336 0-50*	GEX46 1-50	OC210 0-75	OC171 0-25	ZTX304 0-19*	2N1303 0-37	2N3705 0-15*
AC141 0-20	BA148 0-15*	BC184 0-11*	BD139 0-43*	BF337 0-53*	GEX541 1-75	OC211 1-50	OC200 1-50	ZTX311 0-12*	2N1304 0-45	2N3706 0-14*
AC141K 0-30	BA154 0-10	BC192 0-14*	BD140 0-47*	BF338 0-55*	GJ3M 0-75	OC201 1-50	OC201 1-50	ZTX314 0-20*	2N1305 0-45	2N3707 0-18*
AC142 0-20	BA155 0-10*	BC213 0-14*	BD144 2-00	BF521 2-27	GJM5078A 1-50	OC202 1-25	OC202 1-25	ZTX500 0-13*	2N1306 0-50	2N3708 0-14*
AC142K 0-25	BA156 0-13	BC214 0-17*	BD181 1-38	BF528 1-38	KS100A 0-50	OC203 1-25	OC203 1-25	ZTX501 0-16*	2N1307 0-50	2N3710 0-14*
AC176 0-25	BA162 0-05	BC237 0-17*	BD182 1-48	BF591 0-25*	MJE370 0-85	OC204 1-75	OC204 1-75	ZTX502 0-16*	2N1308 0-60	2N3711 0-15*
AC187 0-25	BAX13 0-07	BC238 0-12*	BD237 0-80	BF598 0-28*	MJE371 0-81	OC205 1-75	OC206 1-75	ZTX503 0-17*	2N1309 0-60	2N3712 0-15*
AC188 0-25	BAX16 0-07	BC301 0-45	BD238 0-85	BF599 0-28*	MJE520 0-65	OC206 1-75	OC207 1-25	ZTX504 0-20*	2N1693 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC207 1-25	OC207 1-25	ZTX505 0-20*	2N1693 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC208 2-00	OC208 2-00	ZTX506 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC209 2-00	OC209 2-00	ZTX507 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC210 2-00	OC210 2-00	ZTX508 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC211 2-00	OC211 2-00	ZTX509 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC212 2-00	OC212 2-00	ZTX510 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC213 2-00	OC213 2-00	ZTX511 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC214 2-00	OC214 2-00	ZTX512 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC215 2-00	OC215 2-00	ZTX513 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC216 2-00	OC216 2-00	ZTX514 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC217 2-00	OC217 2-00	ZTX515 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC218 2-00	OC218 2-00	ZTX516 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC219 2-00	OC219 2-00	ZTX517 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC220 2-00	OC220 2-00	ZTX518 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC221 2-00	OC221 2-00	ZTX519 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC222 2-00	OC222 2-00	ZTX520 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC223 2-00	OC223 2-00	ZTX521 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC224 2-00	OC224 2-00	ZTX522 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC225 2-00	OC225 2-00	ZTX523 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC226 2-00	OC226 2-00	ZTX524 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC227 2-00	OC227 2-00	ZTX525 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC228 2-00	OC228 2-00	ZTX526 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC229 2-00	OC229 2-00	ZTX527 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC230 2-00	OC230 2-00	ZTX528 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC231 2-00	OC231 2-00	ZTX529 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC232 2-00	OC232 2-00	ZTX530 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC233 2-00	OC233 2-00	ZTX531 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC234 2-00	OC234 2-00	ZTX532 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC235 2-00	OC235 2-00	ZTX533 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC236 2-00	OC236 2-00	ZTX534 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC237 2-00	OC237 2-00	ZTX535 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC238 2-00	OC238 2-00	ZTX536 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC239 2-00	OC239 2-00	ZTX537 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC240 2-00	OC240 2-00	ZTX538 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC241 2-00	OC241 2-00	ZTX539 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC242 2-00	OC242 2-00	ZTX540 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC243 2-00	OC243 2-00	ZTX541 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC244 2-00	OC244 2-00	ZTX542 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC245 2-00	OC245 2-00	ZTX543 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC246 2-00	OC246 2-00	ZTX544 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC247 2-00	OC247 2-00	ZTX545 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC248 2-00	OC248 2-00	ZTX546 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC249 2-00	OC249 2-00	ZTX547 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC250 2-00	OC250 2-00	ZTX548 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC251 2-00	OC251 2-00	ZTX549 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC252 2-00	OC252 2-00	ZTX550 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC253 2-00	OC253 2-00	ZTX551 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC254 2-00	OC254 2-00	ZTX552 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC255 2-00	OC255 2-00	ZTX553 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC256 2-00	OC256 2-00	ZTX554 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC257 2-00	OC257 2-00	ZTX555 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC258 2-00	OC258 2-00	ZTX556 0-16*	2N1893 0-33	2N3717 0-15*
AC189 0-25	BAX16 0-07	BC301 0-45	BD239 0-85	BF599 0-28*	MJE521 0-75	OC259 2-00	OC259 2-00	ZTX557 0-16*	2N1893 0-33	

The most economical, compact and convenient breadboards on the market!

They are the PROTO-BOARD* PB-6 and PB-100 solderless breadboard kits.

Buy them, and you are only minutes away from the first circuit.

Contacts are made from non-corrosive nickel-silver alloy, and are reliable for more than 10,000 insertions.

Contact resistance is a mere 0.4 m Ω , insertion force is typically 3ozs per lead, and interterminal capacitance is typically less than 5 pF.



The kits are a must for experimental and development work in digital, audio, RF, video and beyond.

Resistors, capacitors, transistors, DIP's, LED's, transformers, pots, jumpers and any other component with leads between 0.015" and 0.032" will fit the contacts.


You can run circuits well beyond the recommended ambient operating temperature (100°C) if you wish, because the plastic used in the PROTO-BOARD is rated to over 200°C.

The kits come complete with instruction manual, assembly hardware, binding posts, non-scratch feet and the appropriate number of preassembled sockets and bus strips.

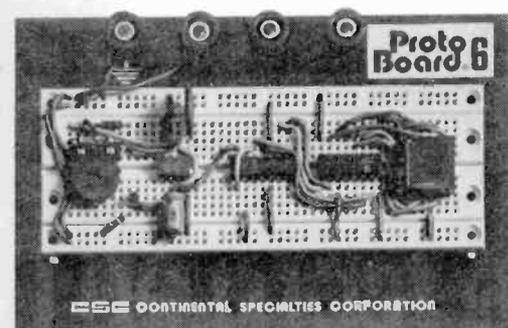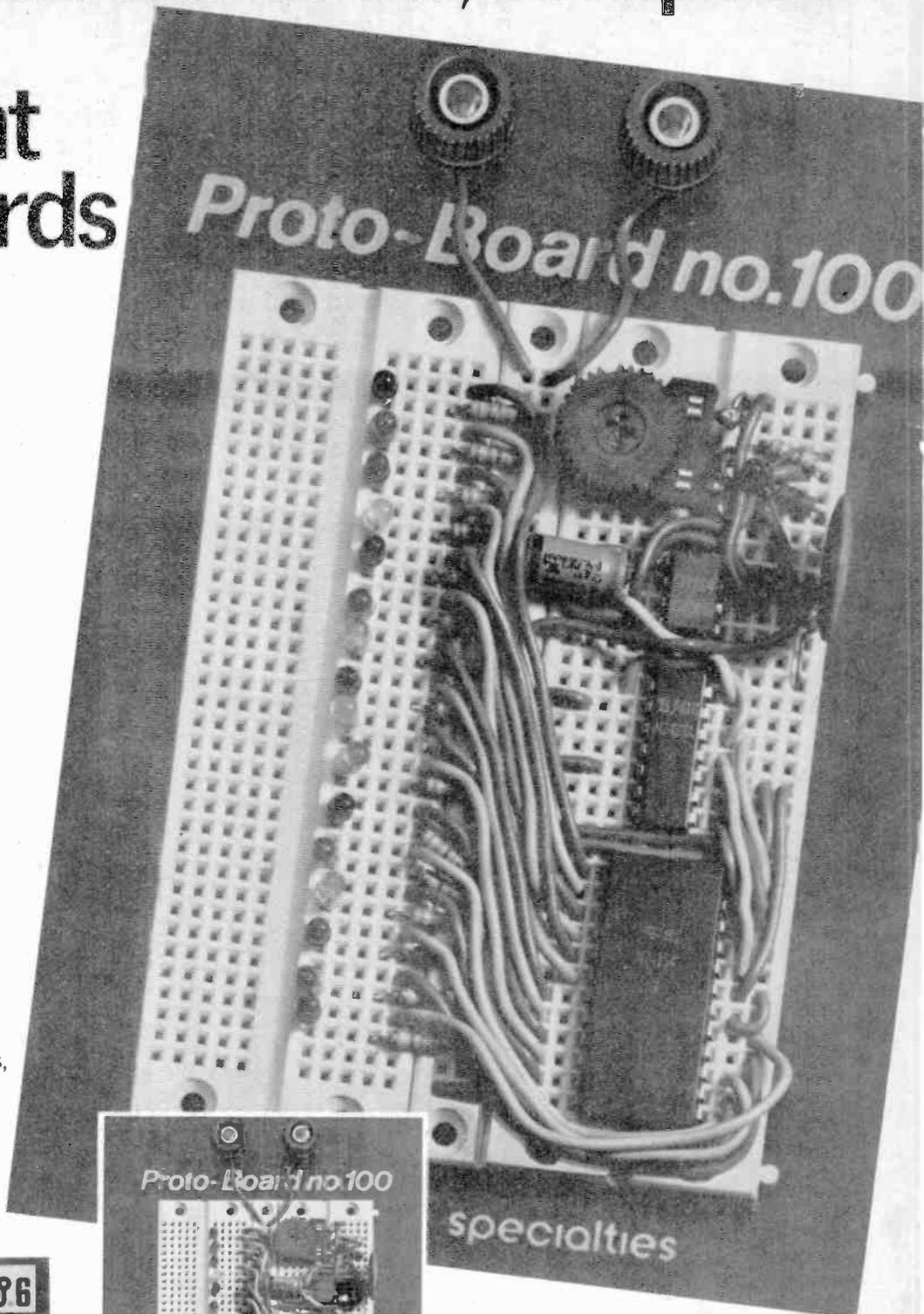The sooner you order, the sooner you'll have that first circuit operating.



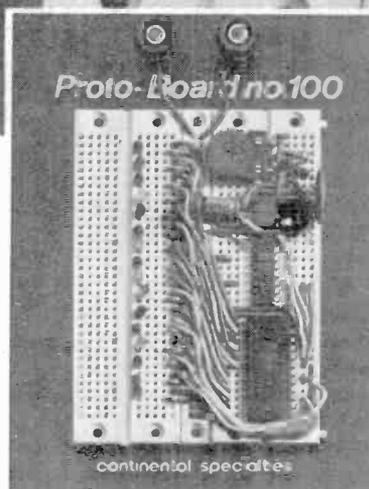THE PB-6 630 SOLDERLESS CONTACTS. TAKES UP TO SIX 14-PIN DIP'S, OR EQUIVALENT IN LARGER AND SMALLER IC'S. FOUR 5-WAY BINDING POSTS. 6" x 4". ONLY COSTS £10.47.



THE PB-100 760 SOLDERLESS CONTACTS. TAKES UP TO TEN 14-PIN DIP'S, OR EQUIVALENT IN LARGER AND SMALLER IC'S. TWO 5-WAY BINDING POSTS. 6" x 4.5". ONLY COSTS £13.50.


Ring us (01-890 0782) with your Access, Barclaycard or American Express number and your order will be in the post that night. Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days. Otherwise ask for our complete catalogue. Our prices include VAT (8%) and postage. All prices and specifications correct at the time of going to press.

CONTINENTAL SPECIALTIES CORPORATION



TRANSISTORS:	BC117 19p	BC184 13p	BD136 38p	BF273 14p	OC72 45p	7447A 50p	14 Pin DIL:	ZENER DIODES:	PRECISION POLY-CARBONATE CAPACITORS
AC107 30p	BC184L 14p	BD137 40p	BF336 37p	OC75 45p	7450 29p	1+ 22p	400mW + - 5% 3V-33V	All High Stability—extremely Low Leakage	
AC117 32p	BC184LB 15p	BD138 40p	BF337 35p	OC77 48p	7453 29p	10+ 21p	10p each: 10/95p		
AC126 32p	BC185 23p	BD139 40p	BF458 48p	ORP1D 50p	7460 29p	50+ 18p	3V3-200V		
AC127 32p	BC186 20p	BD140 58p	BF459 52p	ORP1E £1.10	7470 38p	100+ 16p	18p each: 10/£1.75		
AC128 28p	BC187 19p	BD141 58p	BF459 52p	F2008B £1.95	7473 36p				
AC128K 32p	BC187 19p	BD142 58p	BF459 52p	F2010B £1.95	7474 36p				
AC141 22p	BC187 19p	BD143 58p	BF459 52p	TIP29 54p	7475 36p				
AC141K 44p	BC187 19p	BD143 58p	BF459 52p	TIP31A 55p	7476 36p				
AC142 26p	BC187 19p	BD143 58p	BF459 52p	TIP32A 57p	7482 36p				
AC142K 44p	BC187 19p	BD143 58p	BF459 52p	TIP33 96p	7490 68p				
AC153K 38p	BC187 19p	BD143 58p	BF459 52p	TIP34 96p	7493 68p				
AC154 20p	BC187 19p	BD143 58p	BF459 52p	TIP41A 76p	7493 68p				
AC176 25p	BC187 19p	BD143 58p	BF459 52p	TIP42A 79p	7496 90p				
AC178 44p	BC187 19p	BD143 58p	BF459 52p	TIP3055 £1.15	7421 43p				
AC179 14p	BC187 19p	BD143 58p	BF459 52p	TIS43 38p	7422 52p				
AC187 32p	BC187 19p	BD143 58p	BF459 52p	TIS90 25p	7411 41p				
AC187K 42p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7414 41p				
AC188 32p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AC188K 42p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AC193K 41p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AC194K 41p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AC197 54p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AD140 84p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AD142 81p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AD143 83p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AD149 68p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AD161 58p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AD162 58p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF114 32p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF115 32p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF116 32p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF117 32p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF118 60p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF121 53p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF124 36p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF125 36p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF126 36p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF127 36p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF129 45p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF137 39p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF178 64p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF179 74p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF180 75p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF181 75p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF186 36p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF239 45p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AF299 80p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AS Y67 £1.30	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AU110 £1.75	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
AU113 £1.45	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC107 12p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC107A 14p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC107B 14p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC108 12p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC108A 14p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC108B 14p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC108C 14p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC109 12p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC109A 14p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC109B 14p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC109C 15p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC113 15p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC114 15p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC115 15p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				
BC116 19p	BC187 19p	BD143 58p	BF459 52p	TIS91 26p	7415 41p				

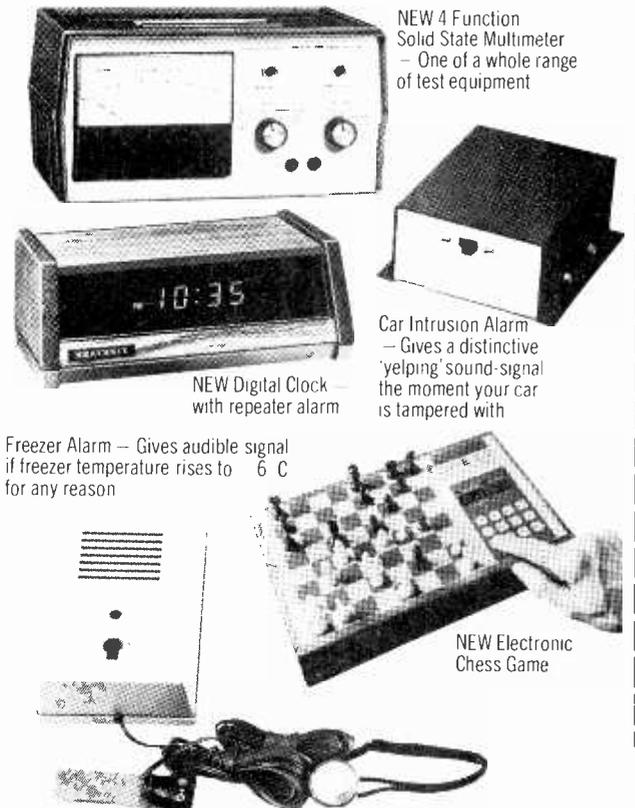Over 200 kits in the free Heathkit Catalogue



NEW 4 Function Solid State Multimeter — One of a whole range of test equipment

Car Intrusion Alarm — Gives a distinctive 'yelping' sound-signal the moment your car is tampered with

NEW Digital Clock with repeater alarm

Freezer Alarm — Gives audible signal if freezer temperature rises to 6°C for any reason

NEW Electronic Chess Game

Right now, there's a brand new edition of the Heathkit Catalogue — packed with hundreds of practical and fascinating items which you can build yourself.


Send for your copy now!

To Heath (Gloucester) Ltd.
Department PW-28
Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit Catalogue. I enclose 1p in stamps to cover postage only.

Name _____
Address _____

When you receive your catalogue you'll get details of this free offer worth approximately £4.75.

Soldering iron offer FREE

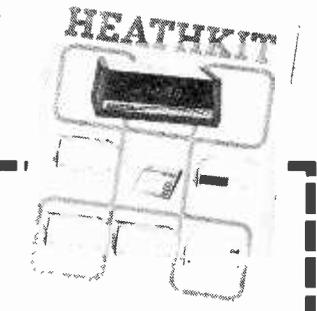

HEATH
Schlumberger
The world's biggest producers of electronic kits.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (Gloucester 29451).

TTLS by TEXAS		741's		4001		20p		NE531V		MEMORY I.C.s		MPSA56		2N2907/A		DIODES			
7400	14p	7497	290p	74LS00	30p	4006	95p	CA3130	108p	709	40p	MPSU05	72p	2N2926RB	9p	BY127	12p	OA202	10p
7401	14p	74100	140p	74LS02	30p	4007	20p	CA3140	108p	733	150p	MPSU06	78p	2N2926OG	11p	OA47	9p	IN916	7p
7402	16p	74104	75p	74LS04	30p	4008	115p	LM318N	175p	741	25p	MPSU55	90p	2N3053	22p	OA81	15p	IN4001/2	6p
7403	16p	74105	75p	74LS10	32p	4010	60p	LM301A	40p	747	75p	MPSU56	98p	2N3054	65p	OA85	15p	IN4003/4	7p
7404	24p	74107	36p	74LS13	55p	4011	20p	LM324N	130p	748	40p	OC28	90p	2N3055	65p	OA90	9p	IN4005/7	8p
7405	25p	74109	60p	74LS20	32p	4012	20p	LM348N	140p	776	216p	OC35/6	70p	2N3442	151p	OA91	9p	IN4148	4p
7406	40p	74110	60p	74LS22	34p	4013	55p	MC1458P	75p	3900	70p	OC71	32p	2N3643	54p	OA95	9p	IN5401/3	15p
7407	40p	74111	75p	74LS30	30p	4014	115p					R2008B	225p	2N3644	54p	OA200	9p	IN5404/7	20p
7408	22p	74116	216p	74LS33	30p	4015	90p					R2010B	225p	2N3702/3	14p				
7409	22p	74118	160p	74LS47	150p	4016	50p	LINEAR I.C.s				TIP29A	50p	2N2704/5	14p				
7410	18p	74119	225p	74LS55	45p	4017	400p	AY-1-0212	65p	NE543K	225p	TIP29C	62p	2N3706/7	14p	BRIDGE RECTIFIERS			
7411	26p	74120	130p	74LS73	60p	4018	110p	AY-1-1313	775p	NE555	35p	TIP32A	62p	2N3708/9	14p	1A 50V	25p	4A 400V	96p
7412	25p	74121	32p	74LS75	60p	4019	52p	AY-1-5050	255p	NE556	97p	TIP33A	62p	2N3713	320p	1A 100V	27p	4A 50V	96p
7413	40p	74122	50p	74LS77	60p	4020	120p	AY-3-8500	775p	NE561B	450p	TIP34A	62p	2N3717	320p	1A 400V	31p	6A 100V	108p
7414	85p	74123	75p	74LS75	75p	4021	120p	AY-5-1315	75p	NE562B	450p	TIP31A	56p	2N3819	27p	2A 50V	40p	6A 400V	120p
7416	40p	74125	70p	74LS85	144p	4022	100p	AY-5-1317A	75p	NE565	140p	TIP31C	66p	2N3820	50p	2A 100V	45p	10A 400V	270p
7417	40p	74126	65p	74LS86	65p	4023	22p	CA3028A	112p	NE566	200p	TIP32A	63p	2N3823	70p	3A 200V	70p	25A 400V	432p
7420	18p	74128	82p	74LS90	80p	4024	80p	CA3048	85p	NE567	180p	TIP33A	97p	2N3866	97p	4A 100V	80p	VM18	
7421	45p	74132	81p	74LS93	80p	4025	22p	CA3048	250p	RC4151N	432p	TIP33C	120p	2N3905/6	22p	4A 100V	90p	1A100V	48p
7428	28p	74136	81p	74LS107	55p	4026	178p	CA3053	75p	SG3402N	275p	TIP33C	120p	2N3905/6	22p				
7423	36p	74141	85p	74LS107	55p	4026	178p	CA3053	75p	SN7210N	54p	TIP33A	120p	2N3905/6	22p				
7425	33p	74142	300p	74LS115	120p	4027	65p	CA3065	200p	SN76033N	275p	TIP33A	120p	2N3905/6	22p	TRIACS Plastic			
7426	43p	74145	95p	74LS138	140p	4029	120p	CA3068E	250p	SN26008	280p	TIP33A	120p	2N3905/6	22p	3A 400V	85p	15A 400V	200p
7427	40p	74147	205p	74LS139	150p	4030	55p	CA3090A	425p	SN76013N	175p	TIP33A	120p	2N3905/6	22p	2A 400V	107p	15A 500V	225p
7428	40p	74148	160p	74LS151	110p	4033	250p	ICL8038CC	400p	SN76013ND	160p	TIP33A	120p	2N3905/6	22p	6A 500V	120p	40430	T066
7430	18p	74150	130p	74LS153	110p	4034	250p	LM339N	175p	SN76013ND	160p	TIP33A	120p	2N3905/6	22p	10A 100V	140p		
7432	37p	74151	81p	74LS153	110p	4034	250p	LM339N	175p	SN76013ND	160p	TIP33A	120p	2N3905/6	22p	10A 500V	160p	40669	T0220
7433	43p	74153	81p	74LS157	130p	4035	100p	LM337N	112p	SN76023ND	160p	TIP33A	120p	2N3905/6	22p				
7437	37p	74154	160p	74LS160	180p	4042	100p	LM3800	220p	SP8515	710p	TIP33A	120p	2N3905/6	22p				
7438	37p	74155	97p	74LS161	180p	4043	100p	LM389N	160p	TCA940	200p	TIP33A	120p	2N3905/6	22p				
7440	18p	74156	97p	74LS162	180p	4044	100p	LM3911N	120p	TAA961A	310p	TIP33A	120p	2N3905/6	22p				
7441	85p	74157	97p	74LS163	180p	4046	140p	M252AA	850p	TBA120	97p	TIP33A	120p	2N3905/6	22p				
7442	75p	74159	250p	74LS164	120p	4047	100p	MC1310P	190p	TBA541B	300p	TIP33A	120p	2N3905/6	22p				
7443	120p	74160	100p	74LS164	120p	4047	100p	MC1310P	190p	TBA541B	300p	TIP33A	120p	2N3905/6	22p				
7444	120p	74161	100p	74LS164	120p	4047	100p	MC1310P	190p	TBA541B	300p	TIP33A	120p	2N3905/6	22p				
7445	108p	74162	100p	74LS175	160p	4050	57p	MC1496L	120p	TBA810	125p	TIP33A	120p	2N3905/6	22p				
7446	108p	74163	100p	74LS175	160p	4050	57p	MC1496L	120p	TBA810	125p	TIP33A	120p	2N3905/6	22p				
7447	75p	74164	120p	74LS181	375p	4055	140p	MC3340P	160p	TAA820	100p	TIP33A	120p	2N3905/6	22p				
7448	85p	74165	150p	74LS181	375p	4055	140p	MC3360P	180p	TAA820A	310p	TIP33A	120p	2N3905/6	22p				
7450	18p	74166	160p	74LS190	250p	4056	135p	MC3401	70p	TAA2020	360p	TIP33A	120p	2N3905/6	22p				
7451	18p	74167	320p	74LS191	200p	4060	130p	MFC4000B	120p	ZN414	40p	TIP33A	120p	2N3905/6	22p				
7453	18p	74170	260p	74C00	25p	4067	425p	NE540L	225p	ZN425E	420p	TIP33A	120p	2N3905/6	22p				
7454	18p	74172	750p	74C02	25p	4068	24p					TIP33A	120p	2N3905/6	22p				
7460	18p	74173	190p	74C04	27p	4069	27p					TIP33A	120p	2N3905/6	22p				
7470	38p	74174	120p	74C08	27p	4070	65p					TIP33A	120p	2N3905/6	22p				
7472	32p	74175	87p	74C10	27p	4071	27p					TIP33A	120p	2N3905/6	22p				
7473	36p	74176	130p	74C14	90p	4072	27p					TIP33A	120p	2N3905/6	22p				
7474	37p	74177	120p	74C42	110p	4073	30p					TIP33A	120p	2N3905/6	22p				
7475	43p	74180	120p	74C48	230p	4076	170p					TIP33A	120p	2N3905/6	22p				
7476	37p	74181	324p	74C73	75p	4081	21p					TIP33A	120p	2N3905/6	22p				
7480	54p	74182	60p	74C74	70p	4082	24p					TIP33A	120p	2N3905/6	22p				
7481	108p	74183	250p	74C85	200p	4093	94p					TIP33A	120p	2N3905/6	22p				
7482	90p	74185	90p	74C86	65p	4098	115p					TIP33A	120p	2N3905/6	22p				
7483	99p	74186	990p	74C90	90p	14502	180p					TIP33A	120p	2N3905/6	22p				
7484	108p	74190	120p	74C93	90p	14503	90p					TIP33A	120p	2N3905/6	22p				
7485	120p	74191	120p	74C107	125p	14507	55p					TIP33A	120p	2N3905/6	22p				
7486	95p	74192	50p	74C160	125p	14508	300p					TIP33A	120p	2N3905/6	22p				
7489	340p	74193	100p	74C151	260p	14508	300p					TIP33A	120p	2N3905/6	22p				
7490	36p	74194	160p	74C157	250p	14510	130p					TIP33A	120p	2N3905/6	22p				
7491	90p	74195	110p	74C160	125p	14511	160p					TIP33A	120p	2N3905/6	22p				
7492	58p	74196	100p	74C161	155p	14512	110p					TIP33A	120p	2N3905/6	22p				
7493	36p	74197	130p	74C162	155p	14515	160p					TIP33A	120p	2N3905/6	22p				
7494	90p	74198	250p	74C163	155p	14518	110p					TIP33A	120p	2N3905/6	22p				
7495	75p	74199	250p	74C164	140p	14520	110p					TIP33A	120p	2N3905/6	22p				
7496	80p	74221	175p	CMOS	4000	20p	14560					TIP33A	120p	2N3905/6	22p				

FANE NEW "POP" RANGE SPEAKERS

Improved appearance — higher sensitivity

12" "POP" 40	45w	£14.95
12" "POP" 50H	50w	£16.99
12" "POP" 75	75w	£22.95
15" "POP" 65	70w	£25.95
15" "POP" 80	80w	£29.95
18" "POP" 100	100w	£49.95
18" "POP" 150	150w	£55.00

SPECIALIST RANGE

★ 12" DISCO/80	80w	Fitted large Tweeter Cone	£28.95
★ 12" DISCO/100	100w		£30.95
★ 12" GUITAR/80L	80w	For Lead Guitar	£26.95
★ 12" GUITAR/80B	80w	Prs rec for Bass Guitar	£27.95
★ 12" PA/80	80w	Duel Cone. For general purpose P.A.	£26.95
15" BASS/85	85w	For Bass Guitar	£39.95
15" BASS/100	100w		£42.00

HIGH FREQUENCY HORNS

J44 Range: 2-5KHz-15KHz Power: 50watt with HPX1R Imp: 8 ohms Size approx 3 1/2" x 3 1/2" x 3" **£7.95**

J73 Range: 2-5KHz-20KHz Power: 50w with HPX1R Imp: 8 ohms Size approx 7 1/2" x 3" x 6 1/2" Rec Price **£11.75**

920/2 Range: 1 KHz-18KHz Power: 100w with HPX1 Imp: 8 ohms Size approx 14" x 9" x 15" Rec Price **£59.95**

HIGH POWER "CROSS-OVERS"

HPX1R (3-5KHz) **£3.25**
 HPX2R (5KHz) **£3.25**

Impedance or total impedance of Bass Drivers not to exceed 8Ω. Otherwise use series Horns or attenuation provided with HPX1R and HPX2R.


FANE SPEAKERS—SUPPLIED TO MOST LEADING U.K. MANUFACTURERS OF GROUP & DISCO EQUIPMENT<

RADIO EXCHANGE LTD.

NEW ELECTRONIC MASTER KIT


WITH SPECIAL MULTI-BAND V.H.F. TUNER MODULE TO CONSTRUCT. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

PROJECTS: V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor MultiBand V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor MultiBand V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio. ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. MultiBand Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster. **£14.99 + P & P £1.10**

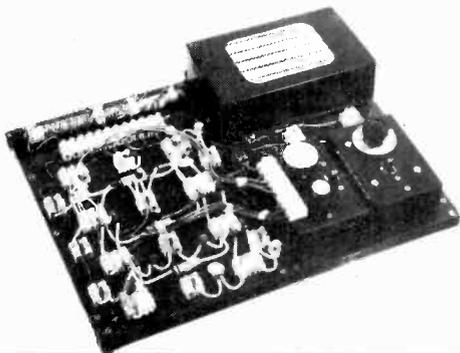

NEW ROAMER TEN MODEL R.K.3

MULTIBAND V.H.F. AND A.M. RECEIVER. 13 TRANSISTORS AND FIVE DIODES. QUALITY 5" x 3" LOUDSPEAKER.
 WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P.P.9—9 volt Battery.
 Complete kit of parts including carrying strap. **£13.99** Including Post and Packing Case Enclosure Kit (if required) £1.90 inc. P. & P.

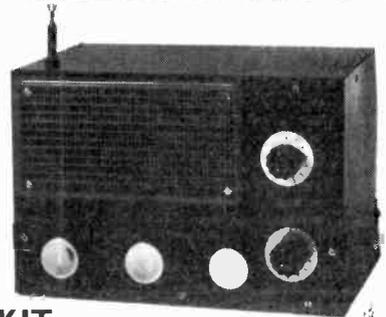

NEW MODEL R.K.1

MultiBand A.M. Receiver. M. W. L. W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.




£8.99 + P & P 90p

ELECTRONIC CONSTRUCTION KIT

E.C.K. 2 Self Contained Multi-Band V.H.F. Receiver Kit.


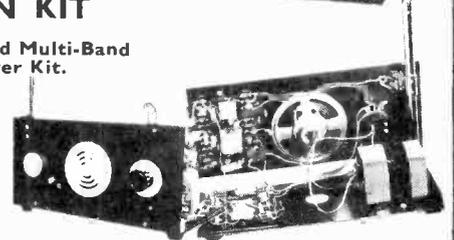
8 transistors and 3 diodes. Push pull output. 3in. loudspeaker, gain control, 7 section chrome plated telescopic aerial V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit)



Complete kit of parts **£7.95 + P & P and Ins. 90p**

NEW MODEL R.K.2

MW, LW and Air Band Receiver. Eight Transistors and Four Diodes. 3" Loudspeaker, Telescopic Aerial, Internal Ferrite Rod Aerial. Complete with Carrying Strap, and ready-drilled Panels and all components necessary for construction. A sensitive Receiver with the additional luxury of an Air Band section to pick up Aircraft from many miles away. Full Instruction Manual enables stage by stage construction. Uses P.P.9 Nine Volt Battery. **£9.99 + P & P £1.10**

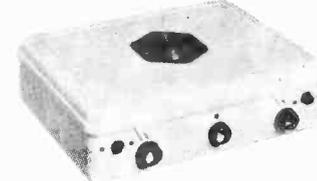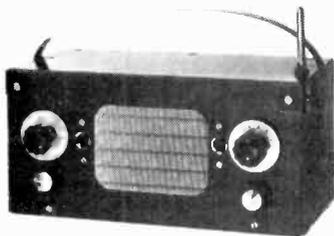

EDU-KIT MAJOR COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT

BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

Complete kit of parts including construction plans Total building costs

£9.99 + P & P and Ins. £1.10

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester
- NPN—PNP Amplifier
- 4 Transistor Push Pull Amplifier

- 24 Resistors
- Earpiece
- 2 Slider Switches
- 21 Capacitors
- Mica Baseboard
- Ferrite Rod
- 10 Transistors
- 3 12-way Connectors
- 1 Tuning Condenser
- 5" x 3" Loudspeaker
- 2 Volume Controls
- 3 Knobs
- Ready Wound Coils
- 6½ yards of wire
- 1 yard of sleeving, etc.

E.V.6.

Build this exciting new design. 6 Transistors and 2 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5½in. x 2½in. approx. All parts including Case and Plans.



Total Building Costs **£5.95 + P & P and ins. 90p**

ALL PRICES INCLUDE VAT

V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. All parts including case and plans

£4.95 + P & P and Ins. 60p



TO: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 1SA
 Tel.: 0234 52367 REG NO. 788372

● Callers side entrance "Lavells" Shop.
 ● Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

I enclose £..... for.....
 Name.....
 Address.....
 PW278

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% Telephone 6743

OA2	-85	3AM8A	-70	6F25	1.00	7R7	2.00	14H7	-75	50CD6G	
OB2	-60	6A38	-70	6P26	45	7X7	2.00	1487	1.00		
OC3	-50	6AQ5	-75	6F28	-85	7Y7	-80	1875	1.25	60EH5	-85
OZ4	-85	6AQ8	-60	6F32	1.00	7Z4	-80	19AQ5	-65	60LGT1-00	
1A3	-80	6AR5	1.05	6G6G	1.00	8D2	-50	19BG6G		66K11	1.00
1A6GT	-85	6AB7G	1.60	6G88A	-80	8D8	-58			72	1.00
1A7GT	-80	6AT6	-60	6GK5	-75	9BW6	-90	19G6	6.50	77	-45
1B3GT	-85	6AU6	-60	6GK6	2.00	9D7	-70	19H1	4.00	85A2	1.40
1C2	1.00	6AV6	-85	6G77	-90	9C4	-45	19Y3	-40	85A3	1.40
1D5	1.00	6AW8A	1.15	6HGT	-85	9C2	-70	20D1	-70	90C1	1.50
1G8GT	1.00	6AX4	-75	6J5GT	-85	10C14	-52	20D4	2.50	108CJ	-40
1H8GT	1.00	6B8G	-75	6J6	-35	10D1	-80	20F2	-85	150C2	-65
1L4	-85	6BA6	-52	6J7G	-60	10DE7	-1.00	20L1	1.80	2158G	-80
1LD6	-70	6BC8	-90	6J7M	-65	10F1	-67	20P1	1.00	956	-50
1LN8	-70	6BE8	-70	6J8A	-90	10F9	-85	20P3	1.00	807	1.10
1N8GT	-75	6B6G	-60	6K7G	-85	10F14	-65	20P5	-84	1825	2.60
1R5	-80	6BH6	1.10	6K8G	-50	10L11	-45	20F5	1.50	1821	1.00
1R6	-40	6BJ6	-75	6K8GT	-55	10L14	-75	25A6G	-70	6702	1.20
1R8	-35	6BK7A	-65	6L1	2.50	10LD12	-75	25L6G	-70	6763	2.75
1T4	-30	6BN8	1.00	6L7	1.50	10PE1	-70	25Y5	-80	6087	2.00
1U4	-70	6BQ5	-48	6L12	-50	10P13	-80	25Y5G	-60	6060	2.00
1U5	-85	6BQ7A	1.40	6L18	-60	10P14	2.50	25Z4G	-50	6097	2.00
2D21	-85	6B7	1.00	6L19	-60	12A6	1.00	25Z5	-75	6146	4.70
2GK5	-70	6BR8	1.25	6LD12	-48	12AC6	-80	25Z6G	-80	6483	2.00
2X2	-75	6BW6	3.50	6LD20	-80	12AD6	-80	25D7	2.00	7025	2.00
3A4	-55	6BW7	-65	6N7G	-70	12AP6	-80	30A5	-75	7193	-60
3B7	-55	6BX6	-40	6PL12	-80	12AT5	-45	30C1	-80	7475	1.20
3D6	-40	6BY7	-45	6P15	-48	12AT7	-52	30C15	1.00	9002	-55
3Q4	-80	6BZ8	1.50	6Q76	-75	12AU6	-50	30C17	-90	9006	-45
3Q5GT	-70	6C4	-50	6Q7GT	-70	12AU7	-52	30C18	2.25	A3042	6.00
3V4	-65	6C6	-45	6Q7M	-75	12AV6	-60	30F5	-70	AC2PEN	1.20
3B4	1.00	6C9	2.00	6R7G	-70	12AX7	-52	30L1	-39	AC2PEN	1.00
4CB6	-75	6C10	1.00	6R7A	-70	12B48	-80	30L15	-75	AC2PEN/	
4GK5	-75	6CB6A	-65	6RC7GT	-1.00	12B48	-80	30L17	-70	DD	1.00
5CG8	-75	6C12	-55	6RGT	-70	12B66	-85	30P4M	-98	AC6PEN	
5R4GY	1.00	6CD6G	4.00	6RH7	-70	12B67	-85	30P12	-74		
5T4	3.00	6CG8A	-90	6R7	-70	12E1	3.50	30P19	-90		
5U4G	1.00	6CL6	-75	6SK7	1.00	12J5GT	-40	30P4	-90	AC/P4	1.50
5V4G	1.00	6CL8A	-95	6K7GT	-70	12J7GT	-70	30P16	-50	ACTH1	1.00
5Y3GT	-65	6CM7	1.00			12K5	1.50	30P18	-50	AL60	1.50
5Z3	1.40	6C86	-65	6SQ7	-70	12K7GT	-80	30P11	1.25	ARP3	-60
5Z4G	-75	6C95	-90	6T4GT	1.00	12K8	-75	30P12	-62	ATP4	-60
5Z4GT	1.00	6D3	75	6U7G	-55	12Q1GT	-50	30P13	1.30	AZ1	-60
6J30L3	-80	6E7	-70			12S47	-75	30P14	1.50	AZ31	1.00
6A8G	1.40	6DT6A	-85	6V6G	-50	12RC7	-50	30P15	1.30	AZ41	-50
6AC7	-70	6E6W6	-85	6V6GT	1.00	12RG7	-55	35A3	1.00	B36	-75
6A05	-35	6E5	1.00	6X4	-85	12RH7	-50	35C5	-80	B719	-50
6AG7	-70	6F1	-80	6X5GT	-80	12R7	-80	35D5	-90	B729	-90
6A16	-70	6F6G	-70	6Y6G	-95	12SK7	-80	35L6GT	-80	B183	2.00
6AJ5	-70	6F12	-70	6Y7G	1.25	12SN7GT				CL33	-80
6AJ8	-55	6F14	-90	7A7	-80					CV6	-80
6AK5	-66	6F15	-85	7B6	1.00	12QGT	-80	35Z4GT	-70	CV63	-80
6AK6	1.50	6F16	-1.00	7B7	1.00	12QGTGT		35Z5GT	-80	CV988	-25
6AK8	-48	6F18	-80	7D5	2.00					CY1C	1.00
6AL5	-85	6F23	1.00	7E8	2.00	12SR7	-78	60B5	-95	CY31	1.00
6AM6	-70	6F24	-80	7E7	1.00	13D8	2.00	60C5	-70	D1	-60

D83	-50	EC53	1.00	EL32	1.00	KT86	3.00	PFL200	1.12	UL41	-90	AA199	-18	BF178	-44
DA632	-80	EC64	1.00	EL37	3.00	KT71	1.00	PL31	1.00	UL84	-85	AA213	-61	BF181	-47
DAF91	-85	EC68	-84	EL41	1.00	KT81	3.00	PL36	-80	UM80	1.00	AC107	-18	BF184	-47
DAF96	1.00	EC68	-84	EL81	1.00	KT88	6.75	PL81	-49	U9	1.00	AC113	-30	BF186	-47
DC90	-70	EC90	-55	EL83	1.00	KTW61	1.50	PL81A	-75	UL12	-45	AC126	-14	BFY60	-26
DD4	-80	EC92	1.00	EL84	-48	L63	-65	PL82	-50	UV41	-70	AC127	-80	BFY61	-23
DF33	-75	EC97	-75	EL86	-80	LN119	-70	PL83	-50	UY42	-70	AC128	-26	BFY62	-23
DF91	-80	EC99	1.00	EL90	-75	LN162	-55	PL84	-50	UY86	-70	AC132	-28	BY100	-81
DF92	-25	ECC33	2.00	EL95	-80	LN309	-75	PL85	1.00	UI0	1.00	AC134	-30	BT114	-21
DF96	1.00	ECC35	2.00	EL96	2.00	LN319	-75	PL85A	1.00	UI2/14	1.15	AC156	-23	BY126	-19
DH63	-75	ECC40	1.00	EL608	2.50	M8182	2.00	PL504/500		U18	1.05	U18	2.50	BY127	-21
DH76	-50	ECC81	-52	EL509	2.50	MHL4	1.00	PL508	1.80	U19	4.00	AC165	-30	BZ210	-80
DH77	-80	ECC82	-52	EM80	1.00	MHLD6	99	PL509	2.55	U25	1.00	AC166	-30	BZ211	-80
DH81	1.00	ECC83	-52	EM81	1.00	MKT4	1.20	PL519	2.80	U26	-90	AC168	-44	BZ212	-80
DE32	-60	ECC84	-50	EM83	1.00	MU14	1.15	PL802	8.20	U28	1.75	AC176	-64	BZ213	-80
DK40	1.00	ECC85	-50	EM84	1.00	MX40	1.00	PT4D	1.00	U35	1.75	AC177	-32	FBY11A	-96
DK91	-50	ECC86	2.00	EM85	1.20	N150	1.00	PY382	-50	U47	2.80	ACY18	-23	FBY41A	-26
DK92	1.00	ECC88	-72	EM87	1.45	N305	-98	PY80	-80	U81	-80	ACY19	-33	OA9	-14
DK96	1.00	ECC91	-35	EMM803		N709	-48	PY81	-60	U191	-50	ACY20	-30	OA7	-18
DL83	-70	ECC189	1.00	EM88	2.80	P61	-60	PY82	-40	U251	1.00	ACY21	-80	OA70	-18
DL82	1.00	ECC304	-80	EY81	-65	PABC90	-45	PY83	-60	U301	1.00	ACY22	-18	OA78	-18
DL92	-65	ECC807	2.80	EY81	1.50	PC86	-80	PY88	1.12	U408	-90	ACY28	-21	OA79	-11
DL94	1.00	ECCF80	-45	EY83	1.40	PC88	-80	PY800A1	56	U404	-75	AD140	-50	OA81	-11
DL96	1.00	ECCF82	-50	EY86/7	-45	PC88	-80	PY801	-60	U801	1.00	AD161	-53	OA85	-11
DM70	1.25	ECCF86	-80	EY88	1.00	PC85	1.00	PY801	-60	U4020	1.00	AD162	-53	OA89	-14
DM71	1.75	ECC85	2.00	EY91	-50	PC97	-75	PZ30	-50	VP4 (5)	2.00	AP114	-30	OA91	-11
DM74	1.15	ECC42	1.00	EY900	1.45	PC900	-65	QV03/10		VP23	-65	AP115	-80	OA95	-11
DW4	-70	ECC81	-55	EZ35	-50	PC84	-39	Q895/10	2.00	VF41	-90	AF17	-32	OC35	1.00
DY11	2.00	ECC88	1.00	EZ40	1.00	PC88	-47	Q8150/15		VF150	-75	AF124	-88	OC45	-18
EY87/8	-62	ECC84	-75	EZ41	1.00	PC88	-61	Q8150/15		VU111	1.00	AF180	-56	OC70	-14
EY802	-50	ECL80	-55	EZ80	-42	PC89	-49	Q8150/15		VU120	1.00	AF186	-94	OC71	-18
EY80C	4.75	ECL82	-60	EZ81	-45	PC89	-49	QV04/7	8.00	VU183	1.00	BA115	-16	OC72	-13
EY80F	6.00	ECL84	-90	EZ90	-95	PC89	-49	QV08/20		W107	1.00	BA116	-81	OC74	-86
EY83	5.50	ECL85	-80	EY801	1.25	PC89	-49	QV08/20		W229	1.20	BA129	-14	OC75	-13
EY83C	1.20	ECL86	-94	GZ30	75	PCF84	-70	R10	4.70	X41	1.00	BA130	-12	OC76	-18
EY8CC	4.50	ECL88	-94	GZ32	1.00	PCF86	-57	R19	5.00	X66	2.00	BA148	-20	OC77	-82
EY80C	5.00	ECL89	-94	GZ33	4.00	PCF200	1.35	UABC90	-45	Z759	6.50	BA163	-18	OC77	-82
EY82	1.00	ECL90	-94	GZ34	2.25	PCF201	1.00	UAF42	-70	Transistors		BC107	-14	OC78D	-13
EY83	1.00	ECL91	-94	GZ37	4.00	PCF801	-49	UBC41	-70	Diodes		BC108	-14	OC81	-13
EY84	1.00	ECL92	-94	HABC80	-80	PCF802	-80	UBC81	-55	1N4744	-16	BC109	-14	OC81D	-13
EY85	1.00	ECL93	-94	HL13C	-60	PCF805	2.25	UBF80	-50	2N404	-21	BC113	-30	OC82	-13
EY86	1.00	ECL94	-94	HL23DD	-68	PCF806	-70	UBF89	-39	2N966	-61	BC115	-13	OC82D	-13
EY87	1.00	ECL95	-94	HL41DD	1.00	PCH200		ULB21	-20	2N1766	-58	BC116	-30	OC83	-23
EY88	1.00	ECL96	-94	HL42DD	1.00	PCL82	-62	UC92	-90	2N2147	-99	BC118	-26	OC83	-23
EY89	1.00	ECL97	-94	HL43DD	1.00	PCL83	-75	UC92	-90	2N2297	-26	BCY10	-53	OC84	-23
EY90	1.00	ECL98	-94	HL44DD	1.00	PCL84	-75	UC95	-45	2N2369	-16	BCY12	-58	OC123	-86
EY91	1.00	ECL99	-94	HL45DD	1.00	PCF80	-80	UCF80	-80	2N3053	-58	BCY32	-23	OC139	-50
EY92	1.00	ECL100	-94	HL46DD	1.00	PCF805	2.25	UCH21	2.00	2N3121	-26	BCY34			

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 AND 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V	24V	£	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
71	2.0	1.0	3.41	0.78
18	4	2	4.03	0.96
70	6	3	5.35	0.96
108	8	4	6.98	1.14
72	10	5	7.67	1.14
116	12	6	8.99	1.32
17	16	8	10.39	1.32
115	20	10	13.18	2.08
187	30	15	17.05	2.08
226	60	30	26.82	0A

30 VOLT RANGE

Prim 220/240V Sec 0-12-15-20-24-30V
Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V 15-0-15V, 12-0-12

Ref	12V	15V	20V	24V	£	P & P
112	0.5	0.5	2.64	0.78	0.78	0.78
79	1.0	1.0	3.57	0.96	0.96	0.96
3	2.0	2.0	5.27	0.96	0.96	0.96
20	3.0	3.0	6.20	1.14	1.14	1.14
21	4.0	4.0	7.44	1.14	1.14	1.14
51	5.0	5.0	8.37	1.32	1.32	1.32
117	6.0	6.0	9.92	1.45	1.45	1.45
88	8.0	8.0	11.73	1.64	1.64	1.64
89	10.0	10.0	13.33	1.84	1.84	1.84

60 VOLT RANGE

Prim 220/240V Sec 0-24-30-40-46-60V
Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V or 24-0-24V or 30-0-30V

Ref	24V	30V	40V	£	P & P
124	0.5	0.5	0.96	0.96	0.96
126	1.0	1.0	5.58	0.96	0.96
127	2.0	2.0	7.60	1.14	1.14
125	3.0	3.0	10.54	1.32	1.32
123	4.0	4.0	12.23	1.84	1.84
40	5.0	5.0	13.95	1.64	1.64
120	6.0	6.0	15.66	1.84	1.84
121	8.0	8.0	20.15	0A	0A
122	10.0	10.0	24.03	0A	0A
189	12.0	12.0	27.13	0A	0A

50 VOLT RANGE

Prim 220/240V Sec 0-20-25-33-40-50V
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40, 50, 25-0-25 or 20-0-20

Ref	25V	30V	£	P & P
102	0.5	0.5	4.41	0.78
103	1.0	1.0	5.37	0.96
104	2.0	2.0	6.98	1.14
105	3.0	3.0	8.45	1.32
106	4.0	4.0	10.70	1.50
107	6.0	6.0	14.62	1.64
118	8.0	8.0	17.05	2.08
119	10.0	10.0	21.70	0A

MAINS ISOLATING (SCREENED) PRIM 120/240 SEC 120/240 CT

Ref	VA (Watts)	£	P & P
*07	20	4.40	0.79
149	60	6.20	0.96
150	100	7.13	1.14
151	200	11.16	1.50
152	250	12.79	1.84
153	350	16.28	1.84
154	500	19.15	2.15
155	750	29.06	0A
156	1000	37.20	0A
157	1500	45.60	0A
158	2000	54.80	0A
159	3000	79.05	0A

*This model 115 or 240v only

HIGH VOLTAGE MAINS ISOLATING PRIM 200/220V or 400/440V Sec 100/120V or 200/240V

Ref	100V	120V	£	P & P
60	243	5.89	1.32	1.32
350	247	14.11	1.84	1.84
1000	250	35.65	0A	0A
2000	252	54.25	0A	0A

AUTO TRANSFORMERS

Ref	VA (Watts)	£	P & P
113	15 0-115-210-240	2.48	0.71
64	75 0-115-210-240	3.95	0.96
4	150 0-115-200-220-240	5.35	0.96
67	500 0-115-200-220-240	10.99	1.64
84	1000 0-115-200-220-240	18.76	2.08
93	1500 0-115-200-220-240	23.36	0A
95	2000 0-115-200-220-240	34.82	0A
73	3000 0-115-200-220-240	48.00	0A

CASED AUTO TRANSFORMERS 240V cable in 115V USA flat pin outlet

VA	£	P & P	Ref
15	4.96	0.96	113W
150	8.48	1.14	4W
200	9.92	1.45	65W
250	10.49	1.45	69W
350	12.53	1.64	53W
500	15.73	1.64	67W
750	18.55	1.76	83W
1000	22.68	0A	94W
1500	26.02	0A	93W
2000	37.65	0A	95W

SCREENED MINIATURES

Ref	Volts	£	P&P
238	200 3-0-3	1.99	0.55
212	1A, 1A 0-6-0-6	2.85	0.78
13	100 9-0-9	2.14	0.38
235	330, 330 0-9-0-9	1.99	0.38
207	500, 500 0-8-9-, 0-8-9	2.59	0.71
208	1A, 1A 0-8-9, 0-8-9	3.53	0.96
236	200 0-15-0-15	1.99	0.38
214	300, 300 0-20-0-20	2.56	0.78
221	700 (DC) 20-12-0-12-20	3.41	0.78
206	1A, 1A 0-15-20-0-15-20	4.63	0.96
203	500, 500 0-15-27-0-15-27	3.99	0.96
204	1A, 1A 0-15-27-0-15-27	5.39	0.96
239	50 12-0-12	1.99	0.38
S112500	12-15-20-24-30	2.64	0.78

PLUS

HIGH QUALITY MODULES

10 Watts RMS AMPLIFIER	£3.66
25 Watts RMS AMPLIFIER	£4.57
35 Watts RMS AMPLIFIER	£6.95
125W RMS AMPLIFIER	*£15.95
PRE-AMP for 5-10W	£6.70
PRE-AMP for 25W	£13.88
POWER SUPPLIES 5-10W	£11.30
POWER SUPPLIES 25W	£13.75
TRANSFORMER 5-10W	£3.09
TRANSFORMER 25W	£4.79

P & P Modules 35p. Trans 96p.
VAT 12½% *VAT 8%

STEREO 30—Complete chassis in 7-7 W rms amp, pre-amp power supply, front panel knobs. (needs trans) £19.05. Trans £3.57. Teak cab £5.25 p & p £1.02 VAT 12½%

BLOB BOARD (Pack of 3)

2.5" x 5.1" 1" or 2.5" x 5.1" 1.5"	£0.75
3.75" x 5.1" 1" or 3.75" x 5.1" 1.5"	£1.14
10" x 6" 1" or 10" x 6" 1.5"	£3.78

IC Range £0.96. 4.75" x 7.5" £2.13
P & P 35p VAT 8%

ELECTRONIC CONSTRUCTION KIT
10 projects (Including electronic organ). No soldering needed £7.29. VAT 8% P & P 70p

COMPONENT PACKS

200 Mixed value resistors (count by weight)	150
150 Mixed value capacitors (count by weight)	30
30 Mixed value precision resistors ½W 2%	15
15 Assorted pots	10
10 Reed switches	15
15 Wire wound resistors—mixed wattage	1
1 Pack wire 50 metres assorted colours	25
25 pre-set assorted types and values	Please state pack required. 60p per pack
VAT 12½% P & P 40p	

Prices correct 27-11-77. Please add VAT after P & P.

TEST METERS

AVO 8 MK5	£71.00
AVO 71	£29.00
AVO 73	£39.00
AVO MM5	£24.00
AVO TT169 in circuit	£30.00
Transistor Tester	£30.00
Oscilloscope CL-5 10 meg 3 inch tube	£55.00
Carriage £4.00 8% VAT.	
Wee Megger £58.80	
U6315 Budget Meter 20K Ω/VDC, 2K1VAC 1000V AC/DC, 2-5A AC/DC, 500K rcs. In robust steel case—leads £14.95. VAT 8% P & P £1.15	
AVO cases and accessories	

BRIDGE RECTIFIERS

200V 2A	£0.45
400V 2A	£0.55
200V 4A	£0.65
400V 4A	£0.80
400V 6A	£1.05
500V 10A*	£2.35
VAT 12½% *VAT 8% P & P 15p.	

Audio Kit 25W + 25W
Complete with instructions £27.55
Teak cab & mounting hardware £9.20 P & P £1.73 VAT 12½%.

MUSIC CENTRE CHASSIS FM (STEREO)/MW/LW 15+15W Music Power Inc. Transformer Price £22.50 inc. VAT. P & P £1.50 VAT 8%

Battery Eliminator "Save on Batteries"
Stabilised 3-6-7 5-9V/400mA multiplug outlet £5.95
3300 fits into 13A socket 6-7 5-9V 300mA multiplug outlet £3.30
B12 3, 4, 5, 6, 7, 5, 9, 12V 500mA DC plug outlet £5.32
VAT 12½% P & P 55p

DECS SOLDERLESS BREAD-BOARDING

S Dec 70 contacts	£1.98
T Dec 208 contacts	£3.83
U Dec "A" for I.C.s etc	£3.99
U Dec "B" for I.C.s etc	£6.99
VAT 8% P & P 40p	

ANTEX SOLDERING IRONS

15W	£3.75
25W	£3.40
Stand	£1.40
VAT 8% P & P 46p	

MINI-MULTIMETER DC-1000V AC-1000V DC-100mA Res-150K Ω 1000 Ω/V Bargain £5.86 VAT 8% P & P 62p

STEREO FM TUNER PHASE-LOCK LOOP

4 Pre-selected stations, Varicap tuning, switched AFC, LED Beacon.
£20.45 VAT 12½% P & P 40p

TRANSFORMERS SPECIAL OFFER

BE1 Prim 0-120, 0-120V (120 or 240V) Sec 24V 10A	£5.50 P & P £1.66
BE2 Prim 0-100-110-200-220-240V Sec 0-110V 0-20-24V	2A £2.25 P & P 95p. VAT 8%
BE3 100V line to 4 ½ 7/10W £2.05 P & P 66p	
BE4 Prim 120 or 240V 9-0-9 1A	£1.88 P & P 0.38
BE5 15W matching trans. sec 15Ω	£1.50 P & P 30p. Ref. 30 240-240 isolator 200VA £4.20 P & P 30p. Ref. 62 240-240 isolator 250VA £5.20 P & P 96p.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

CRESCENT BARGAINS in Multimeters

A special bulk purchase of Eagle multimeters enables us to offer four from their range at never-to-be-repeated prices.

Order now direct from Crescent at up to 15% off Eagle's own recommended retail price



KEW 7 pocket multimeter.
Handy pocket-size (3½" x 2½" x 1") 1000 opv meter with 'off' damping. Includes all basic ranges:
DC volts: 0 to 10, 50, 250, 1000.
AC volts: 0 to 10, 50, 250, 1000.
DC amps: 0 to 100 mA.
Resistance: 0 to 150K ohms.
Decibels: -10 to -22dB. £5.95 inc. VAT with leads and battery.

CI095 20,000 opv multimeter with hinged 4-position scale for easy-reading bench use. Anti-parallax mirror, 3-colour scale, overload protection. Ranges: DC volts: 5, 25, 50, 250, 500, 2,500 (20,000 opv). AC volts: 10, 50, 100, 500, 1,000 (10,000 opv). DC amps: 50µA, 2.5mA, 250mA. Resistance: 50K ohms, 5 megohms. Decibels: -20 to +22dB. £14.95 inc. VAT.

EP20KN 20,000 opv multimeter with 'off' damping and anti-parallax mirror. Ranges: DC volts: 25, 5, 25, 125, 500, 1,000 (20,000 opv). AC volts: 10, 50, 250, 1,000 (10,000 opv). DC amps: 50µA, 2.5mA, 250mA. Resistance: 60K ohms, 600K ohms, 6 megohms. Decibels: -20 to +22dB. £16.95 inc. VAT.

NEW EMI200 100,100 opv multimeter complete with real leather carrying case, shoulder strap and probes. A really comprehensive range of features includes: 3-colour scale, anti-parallax mirror, taut band movement, electronic protection, reversible polarity, up to 15 amps AC capacity. Ranges: DC volts: 0.15, 0.5, 1.5, 5, 15, 50, 150, 500, 1,500 (100,000 opv). AC volts: 1.5, 5, 15, 50, 150, 250, 500, 1,500 (30,000 opv). DC amps: 10µA, 15µA, 500µA, 15mA, 500mA, 1.5A, 15A. AC amps: 15A. Resistance: 0-20K ohms, 200K ohms, 2 megohms, 20 megohms, 200 megohms. (Mid-scale): 100 ohms, 1K ohm, 10K ohms, 100K ohms, 1 megohm. Accuracy: DC -2%, AC -3%. Size (in case): 8½" x 7" x 3". £42.95 inc. VAT.



Call at Crescent Radio 164-166 High Road, London N.22 (01-888 3206) or 13 South Mall, Edmonton, London N.9 (01-803 1685), or buy direct from our Mail Order Department: 1 St. Michael's Terrace, Wood Green, London N.22 (01-888 4474).

Make cheques or P.O.'s payable to Crescent Radio Ltd., and add 50p for carriage and packing (UK only). Full money-back guarantee. Access and Barclay cards accepted.



Wilmslow Audio

THE firm for speakers!

SEND 10P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.


ATC • AUDAX • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMANS • HELME • I.M.F. • ISOPHON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • TANNOY • VIDEOTONE • WHARFEDALE

WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street

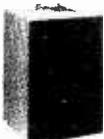TEL: WILMSLOW 29599 FOR SPEAKERS
WILMSLOW 26213 FOR HIFI



EASY BUILD SPEAKER DIY KITS

Specifically designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms, 30 watts peak, each unit. + p & p £5.50 Cabinet size 20" x 11" x 9" (approx.).

£2800
STEREO PAIR
+ p & p £5.50

SPEAKERS AVAILABLE WITHOUT CABINETS.
It's the units which we supply with the enclosures illustrated. Size 13" x 8" (approx.) woofer, (EMI), 2 1/2" app. £1700 per tweeter, and matching crossover components. stereo pair Power handling 15 watts rms, 30 watts peak. + p & p £3.40

COMPACT FOR TOP VALUE These infinite baffle enclosures come to you ready mitted and professionally finished. Each cabinet measures approx. per stereo pair 12" x 9" x 5" deep, and is in wood simulate. Complete with two 8" (approx.) speakers for £850 maximum power handling of 7 watts. 8Ω. + p & p £2.20

SPEAKERS Two models - Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/2" (approx.). Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11" app. Duo IIb **£17 PER PAIR** Duo III **£52 PER PAIR** + p & p £6.50

DECCA 20 WATTS STEREO SPEAKER stereo pair This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters complete with crossover networks. 8Ω. £4.00 p & p **£2000**

PERSONAL SHOPPERS

STEREO CASSETTE record/replay fully built P.C. board **£275**

AM. FM. TUNER P.C.B. with Mullard L.P. 1186, 1185, 1181 modules. **£950**

100K Multiturn Varicap tuning pots, 6 for **£100**

PAIR STEREO 8 WATT SPEAKERS 8" bass units with 3 1/2" approx. tweeters **£1295**

Size 16 1/2" x 11" x 8 1/2".

Plinth & cover BSR or Garrard teak finish **£600**

DECCA OC1000 Stereo Cassette P.C.B. complete with switch oscillator coils and tape-heads **£295**

AM. FM. Stereo Multiplex Car Radio/cassette player in dash fixing Negative earth 5 watts output **£3600**

I.C. Stereo 8 Track to Cassette adaptor converts, any 8 track player to cassette player. **£1895**



20 x 20 WATT STEREO AMPLIFIER £2990

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary Rear panel features two mains outlets. DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak. £2.50

30 x 30 WATT AMPLIFIER KIT £2900

Viscount IV amplifier. 60 + 60 peak. p & p £2.50
NOW AVAILABLE fully built and tested. **£3500**
Output 30 + 30 watts rms, 60 + 60 peak. p & p £2.50

FREE To cash or cheque personal shoppers
A 4 channel Stereo Adaptor to all buyers of the Viscount 20 x 20 **£290** Available separately **£395**
Amplifier at + £1.00 p & p.

ADD-ON STEREO CASSETTE TAPE DECK KIT

Designed for the experienced D.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record/replay electronics with twin V.U. meters and level control for mating with mechanism. Specifications: Sensitivity - Mic. 0.85 mV a 20K OHMS; Din. 40mV a 400K OHMS; Output - 300mV RMS per channel a 1KHz from 2K OHMS source; Cross Talk - -30db; Tape Counter - 3 Digit. Resettable; Frequency Response - 40Hz - 8KHz ± 6db; Deck Motor - 9 Volt DC with electronic speed regulations; Key Functions - Record, Rewind, Mains Transformer **£1995**
Fast Forward, Play, Stop & Eject. £2.50 + £1 p & p £2.50
Opt. extras: Pair of Dynamic microphones £3.95 + £1.00 p & p.

RTVC All enquiries send stamped addressed envelope
323 EGGWARE ROAD, LONDON W2
21c HIGH STREET, ACTON W3 6NG
ALL PRICES INCLUDE VAT AT 12 1/2%
All items subject to availability. Price correct and subject to change without notice



45 WATT MONO DISCO AMP

£3500 p & p £2.50
Size approx. 13 1/2" x 5 1/2" x 6 1/2"



45 watts rms, 90 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"



Brushed aluminium fascia and rotary controls. Five vertical slide controls - master volume, tape level, mic level, deck level. PLUS INTER-DECK FAOER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading 100 watt peak p & p £4.00
in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. 100 watt **£65**

CHASSIS RECORD PLAYER DECKS



Type ILS1
cuing device and stereo ceramic head, p & p £2.50
BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. p & p £2.50
Home 8 Track cartridge player. This unit will match with the Viscount IV 9" x 8" x 3 1/2". p & p £2.50 **£1650**


BSR BDS 95 TYPE illus. £2495

Belt drive turntable unit. 2 speed, semi automatic p & p £2.55
BSR MP60 TYPE Single **£195**
play record deck p & p £2.55
less cartridge.
Cartridges to suit above
Acos. magnetic stereo **£4.95**
Ceramic stereo **£1.95**
BSR automatic record player deck **£29**

BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. p & p £2.50
Home 8 Track cartridge player. This unit will match with the Viscount IV 9" x 8" x 3 1/2". p & p £2.50 **£1650**

Tourist IV CAR RADIO KIT

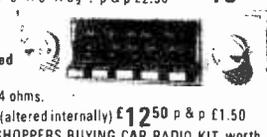For the experienced constructor only
Output 4 watts into 4 ohms.
12 volts pos or neg (altered internally) **£1250** p & p £1.50
FREE TO PERSONAL SHOPPERS BUYING CAR RADIO KIT worth ELECTROMATE Rear window heater, modern line element, £3.00



Personal Shoppers EGGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday. ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK

Start the New Year well by buying this famous Component Catalogue!



- The finest components catalogue yet published.
- Over 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1.40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.
HOME RADIO (Components) LTD.,
Dept. PW., 234-240 London Road,
Mitcham, Surrey CR4 3HD

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD., Dept. PW., 234-240 (Regn. No London Road, Mitcham, Surrey CR4 3HD London 912966)

TRAMPUS ELECTRONICS LTD

A SEMICONDUCTOR POWERHOUSE. TRAMPUS ELECTRONICS LTD., 58-60 GROVE ROAD, WINDSOR, BERKS. ENGL. TELEPHONE WINDSOR (07535) 54525
CALLERS WELCOME MON-SAT 9AM-5PM

Fast service, on Ex Stock product, normally 24 hour turn around. Quality devices to manufacturers specifications. Barclaycard & Access by post or telephone £5 minimum. Send C.W.O. Add 20p post & packing plus 8% VAT to items marked *. 12 1/2% VAT to unmarked items. No minimum order charge for cheque or postal orders. Government depts., schools, N.M.A. £5 min. order. FREE CATALOGUE SALE LIST. Send SAE. Money back if not satisfied. (Prices may change).

IC's	All price each	FULL SPEC PAKS	£1	TIS43 or 2N2646	50p*
555 DIL8 Timer	34p*	Pak A: 10 x Red LED	£1*	2N2904 & 2905	30p*
723 Regulator	69p*	Pak B: 4 x 741 DIL 8	£1*	2N2926 YG	15p
741 DIL 8 pin	26p*	Pak C: 3 x 2N3055	£1*	2N3053	24p*
741 DIL14/TO99	36p*	Pak H: 6 x 2N3819e	£1	2N3055 115W	45p*
747 DUAL 741	89p*	Pak K: 40 x IN914	£1*	2N3442/472 120V	£1.50*
748 DIL 14 pin	28p*	Pak N: 25 x OA81/91	£1	2N3702/3/4/5/6	10p
748 DIL 8 pin	49p*	Pak T: 4 x LM301	£1*	2N3819e & 23e	18p
7805 plastic or TO3	£1*	Pak W: 20x EL'trolytics	£1*	2N3820 FET	33p
7812 or 15	£1.50*	More paks in lists.		2N5457 low noise	50p
78013 or 78023	£1.49	CAPACITORS:		INS Bush sets	10p
8038 Sig Gen	£5*	Ceramic	5p	Matching	Add 20p
AYC1924 Clock	£2.25*	Electrolytic 1vf-200vf	2p	DIODES OA81/91	3p
LM301 DIL 14	29p*	Heatsinks: TO18/TO5	5p*	IN14 & 4148 sil	4p*
LM301 DIL 8	58p*	TO3 small 29p* Big	69p*	IN4001 5p*	4004 7p*
LM 309K TO3 5V	£1*	DIL SOCKETS		Bridge 1A 50V	25p*
LM382 (LM381)	£2	Low Profile 8 pin	12p*	BZY88 400mW	50p*
LM3901/60745	89p*	14 or 16 pin	15p*	Zeners 3-30V	10p*
LM3130/CA3130	95p*	VERO All 0-1" stocked		SCR & TRIACS	
LM3900	75p*	2 1/2" x 3 1/2" 42p* 3 1/2" x 5" 56p*		Disco Triac 10A 400V £1*	
MC1310 MPX DR	75p	3 1/2" x 1 1/2" £2.50 2 1/2" x 5" 50p*		Disco SCR C106 4A 400V	49p*
NE555 Timer	34p*	DIL Board 6" x 4" £2.44		SCR 1A 400V 50p	
NE556 2 x 555	£1*	POTS. 25p PRESETS 9p		DIAC-ST2 25p BR100 40p	
TBA810 or 820	£1	RESISTORS 2p		Silicon Grease (min) 25p	
		LEDS 1/4" & 2" dia.		CMOS: Range In lists.	
		Red no clip	11p*	4001 or 2	23p*
		.2" or 209 & clip	15p*	4009/10	59p*
		Colour LEDES All	19p*	4011 20p*	4049/89 23p*
		New Bezel LED cover		TTL 7400N SERIES	
		DISPLAYS (Red Led)	10p*	7400 14p*	7485/86 10p*
		0-3" DL704/2	59p*	7401 16p*	7490 49p*
		0-3" DL707/2	59p*	7404/5 20p*	7491/2 50p*
		0-6" DL747/2 No DP	£1*	7408/10 17p*	7493/5 50p*
		TGS308 Gas D	£5*	7413 39p*	74107 20p*
		390pI Tuning Cap	£1	7417/20 25p*	74121 33p*
		Sleeper RS type	£1.48*	7430 15p*	74123 39p*
		Dalo PCB Pen	69p*	7440 15p*	74141 80p*
		SRBP 6" x 4"	60p*	7441 79p*	74157 50p*
		1kg Ferric Tub	£1*	7445 49p*	74193 50p*
		PCB etch kit	£2*	7447 84p*	QUOTE
		VV Meters	£1.50*	7470/72 25p*	THIS
		TUNER SALE		7473/74 35p*	AD FOR
		MW/LW & FM with		7475 40p*	SPECIAL
		MPX Decoder & Push		7476 39p*	PRICES
		buttons only		7480/2/5 10p*	WORN
		Stereo TW Amp.	£2.60		

15-240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input Impedance 4-7k Ω at 1kHz.


OUTPUTS: Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0-1% at 1kHz. Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up. SUPPLY VOLTAGE \pm 16-50V.

Price \pounds 5.22 + 65p VAT P&P free.

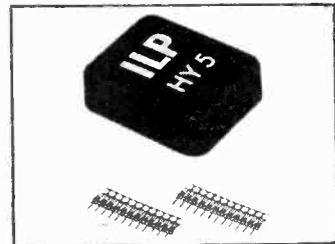

HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω . DISTORTION 0-1% at 1.5W.

INPUT SENSITIVITY 500mV. FREQUENCY RESPONSE 10Hz-16kHz—3dB.

SUPPLY VOLTAGE \pm 18V.

Price \pounds 5.22 + 65p VAT P&P free.



HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


SPECIFICATIONS: INPUT SENSITIVITY 500mV

OUTPUT POWER 25W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0-04% at 25W at 1kHz

SIGNAL/NOISE RATIO 75dB FREQUENCY RESPONSE 10Hz-45kHz—3dB.

SUPPLY VOLTAGE \pm 25V. SIZE 105 50 25mm

Price \pounds 6.82 + 85p VAT P&P free.

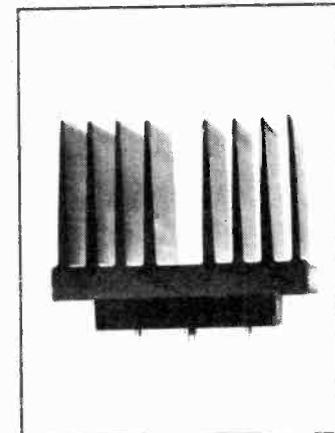

HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS

INPUT SENSITIVITY 500mV.

OUTPUT POWER 60W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0-04% at 60W at 1kHz

SIGNAL/NOISE RATIO 90dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE \pm 25V

SIZE 114 50 85mm

Price \pounds 15.84 + \pounds 1.27 VAT P&P free.

HY200 120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0-05% at 100W at 1kHz.

SIGNAL/NOISE RATIO 96dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE \pm 45V

SIZE 114 50 85mm

Price \pounds 23.32 + \pounds 1.87 VAT P&P free.

HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial


SPECIFICATIONS

OUTPUT POWER 240W RMS into 4 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0-1% at 240W at 1kHz.

SIGNAL NOISE RATIO 94dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE \pm 45V

INPUT SENSITIVITY 500mV SIZE 114 100 85mm

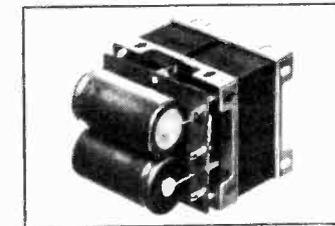Price \pounds 32.17 + \pounds 2.57 VAT P&P free.



POWER SUPPLIES

PSU36 suitable for two HY30's \pounds 5.22 plus 65p VAT. P/P free.

PSU50 suitable for two HY50's \pounds 6.82 plus 85p VAT. P/P free.

PSU70 suitable for two HY120's \pounds 13.75 plus \pounds 1.10 VAT. P/P free.

PSU90 suitable for one HY200 \pounds 12.65 plus \pounds 1.01 VAT. P/P free.

PSU180 \pounds 23.10 + \pounds 1.85 VAT.

B1 \pounds 0.48 + \pounds 0.06 VAT.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON, CANTERBURY, KENT, CT4 7AD.

I.L.P. ELECTRONICS LTD.,
CROSSLAND HOUSE, NACKINGTON,
CANTERBURY, KENT, CT4 7AD.

Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name and Address _____
Signature _____



ELECTRONICS (London) Ltd

NASCOM I

Microcomputer for the Hobbyist

HARDWARE FEATURES:

- * SUPPLIED IN KIT FORM FOR SELF-ASSEMBLY.
- * FULL DOCUMENTATION SUPPLIED.
- * INCLUDES PRINTED CIRCUIT BOARD.
- * FULL KEYBOARD INCLUDED.
- * INTERFACES TO KEYBOARD, CASSETTE RECORDER & T.V.
- * 2K x 8 RAM.
- * 1K x 8 EPROM MONITOR PROGRAM.
- * POWERFUL Z80 CPU.
- * 16 LINE x 48 CHARACTER DISPLAY INTERFACE TO STANDARD, UNMODIFIED T.V. SET.
- * ON BOARD EXPANSION TO 2K x 8 EPROM.
- * ON BOARD EXPANSION FACILITY FOR ADDITIONAL 16 LINES I/O.
- * TOTAL EXPANSION TO 64K x 8 MEMORY.
- * TOTAL EXPANSION TO 256 INPUT PORTS AND 256 OUTPUT PORTS.

SOFTWARE FEATURES:

- * 1K x 8 'NASBUG' PROGRAM IN EPROM.
- * PROVIDES 8 BASIC OPERATOR COMMANDS INCLUDING SINGLE STEP.
- * EXPANDABLE SOFTWARE SYSTEM VIA ADDITIONAL USER PROGRAMS IN RAM OR EPROM.

Cost £197.50 PLUS 8% VAT

Phone or write for details to:


**92 BROAD STREET, CHESHAM, BUCKS.
TELEPHONE: (02405) 75154.**



I.C.E. MULTIMETERS

**TWICE the information
in HALF the size**

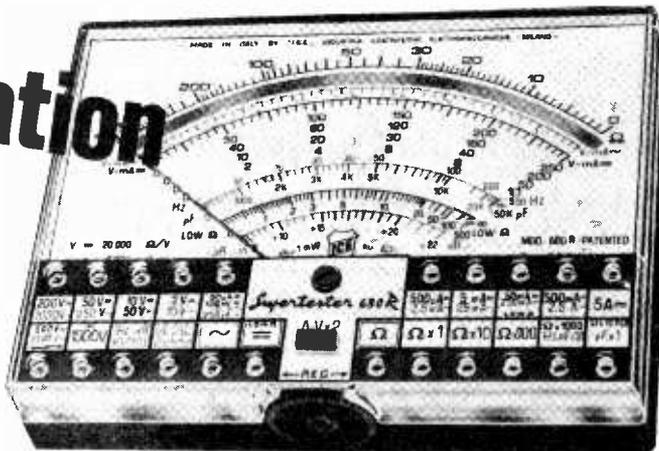The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.



Supertester 680R (illustrated)

- * 20k Ω /V, $\pm 1\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 80 Ranges - 10 Functions
- * 140 x 105 x 55mm

£25.25 + VAT

(For Mail Order add 80p P&P)

Supertester 680G

- * 20k Ω /V, $\pm 2\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 48 Ranges - 10 Functions
- * 109 x 113 x 37mm

£19.95 + VAT

(For Mail Order add 80p P&P)

Microtest 80

- * 20k Ω /V, $\pm 2\%$ fsd on d.c.
- 4k Ω /V, $\pm 2\%$ fsd on a.c.
- * 40 Ranges - 8 Functions
- * Complete with case - only 93 x 95 x 23mm

£14.95 + VAT

(For Mail Order add 80p P&P)

All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.



Electronic Brokers Ltd.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Plessey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14.00 including VAT and postage.




ROOM THERMOSTAT

Famous Satchwell, elegant design, intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0-30°C. Special snip this month £3.00 post and VAT paid.



SOUND TO LIGHT UNIT

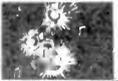Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £7.95 plus 95p VAT & Postage.



MICRO SWITCH BARGAINS

Rated at 5 amps 250 volts. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 for £1.00, VAT and post paid.



RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set. £3.95 VAT and postage inc.



MULTISPEED MOTORS

Six speeds are available 500, 850 and 1,100 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 1/4" diameter and approximately 1" long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2" dia. x 5" long. Price £2.00 including Post & VAT.



RECTANGULAR HOT PLATE

Aluminium panel with ridged top and angled underneath to strengthen it. This is approx. 10" x 4 1/2" of flat plate. Beneath plate is 100w element and sensor switch which will maintain the surface of the plate just too hot to touch. With leads and tages. This is ideal if you are making up a food warmer or for an airing cupboard, etc. Price £1.03.



HUMIDITY SWITCH

American made by Ranco, their type No. J11. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive microswitch adjustable by a screw, quite sensitive—breathing on it for instance will switch it on. Micro 3 amp at 250v AC. Overall size of the device approx. 3 1/2" long, 1" wide and 1 1/2" deep. 75p.



MAINS RELAY

With triple 10 amp changeover contacts—operating coil wound for 230 volts AC, chassis mounting, one screw fixing, ex unused equipment 80p each, post and VAT paid.



PP3/PP9 REPLACEMENT MAINS UNIT

Japanese made in plastic container with leads size 2" x 1 1/2" x 1 1/2", this is ideal to power a calculator or radio, it has a full wave rectified and smoothed output of 9 volts suitable for a loading of up to 100mA. £2.53.



MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of many of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.50. Postage 50p.

DRILL CONTROLLER

CONTROL DRILL SPEEDS

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45 including post & VAT. Made up model £1.00 extra.

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output £1.50 including Post & VAT. Model 1172 1W, power output £1.85 including Post & VAT. Model EP9000 4 watt power output £2.90 including Post & VAT. EP 9001 twin channel or stereo pre-amp. £2.90 including Post & VAT.



SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1.90—crystal earphone 55p including VAT and postage.



BREAKDOWN PARCEL



Four unused, made for computer units containing most useful components, and these components unlike those from most computer panels, have free ends of usable length. The transistors for instance have leads over 1" long—the diodes have approx. 1/2" leads.

List of the major components is as follows:—17 assorted transistors—38 assorted diodes—60 assorted resistors and condensers—4 gold plated plugs in units which can serve as multipin plugs or as hook up boards for experimental or quickly changed circuits (note we can supply the socket boards which were made to receive these units). The price of this four units parcel is £1 including VAT and post (considerably less than value of the transistors or diodes alone) DON'T MISS THIS SPLENDID OFFER.

FLUORESCENT TUBE INVERTOR

For camping—car repairing—emergency lighting from a 12v battery you can't beat fluorescent lighting, it will offer plenty of well distributed light and is economical. We offer inverter for 21" 13 watt miniature tube for only £3.75 with tube and tube holders as well.



THIS MONTH'S SNIP



is a miniature sealed relay 12v dc operated with two sets of changeover contacts. The unique feature of this relay is its heavy lead out wires, these provide adequate support and therefore the relay needs no fixing; on the other hand there is a fixing bolt protruding through one side so if you wish you can fix the relay and use its very strong lead outs to secure circuit components—an expensive relay; but we are offering it for only 87p each. Don't miss this exceptional bargain!


EXTRACTOR FAN

Ex computers—made by Woods of Colchester, ideal for fixing through panel—reasonably quiet running—very powerful 2500 rpm. Choice of two sizes 5" or 6 1/2" dia. £4.41 and £6.



SPIT MOTOR WITH CARTER G/BOX

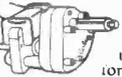Probably one of the best spit motors made. Originally intended to be used in very high priced cookers, however this can be put to plenty of other uses, for instance your garden barbecue or to drive a tumbler for stone polishing; in fact there are no ends to its uses. Normal mains operation. £4.32 including POST & VAT.



LATCHING RELAY



by Guardian Electric, mains operated it is in fact two relays mounted on a metal base plate. The relays being mounted in such a way to ensure that when one closes the other opens and vice versa thus when closed relay A would remain locked until manually released or electrically released by energising relay B. Each relay has 2 sets of 10 amp changeover contacts. Should be ideal for burglar alarms and similar applications £2.11.

TERMS:

Cash with order—prices includes VAT and carriage unless stated but orders under £6 must add 50p to offset packing etc. BULK ENQUIRIES WELCOMED. Phone 01-688 1833

J. BULL (ELECTRICAL) LTD
(Dept. PW), 103 TAMWORTH RD.
CROYDON CR9 1SG

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

FM Tuner and decoder, two very well made (Japan) units, nice clear dial, excellent reproduction £9.95 the pair £1.25 VAT.

12 Volt Heavy Duty Relay, plug in type has three pairs of 10 amp changeover contacts. A transparent dust cover, price £1 + 8p, suitable 11 pin base 27p + 2p. 4 Changeover Mains Relay, upright mounting with perspex type dust cover, the really interesting feature is 4 sets of 10 amps changeover contacts price £1.62 + 12p.

12 Volt Pump. Designed we believe as a bilge pump, this is 12 volt AC/DC motor coupled by a long enclosed shaft to a submersible pump. Suitable for water or most any fluids. Price £1.70. Post 80p.

Just arrived. Fruit machines, working order very impressive choice of several but very heavy so you must collect. £50.

High Load 24 Hour Clock Switch, made by the famous AEG Company for normal mains but with clockwork reserve has load capacity of 80 amps at 240v 50hz. Therefore suitable for dealing with large loads of say shop lighting, water heating, storage heaters etc. Has triggers for on and off once per 24 hours but extra triggers will be available. Price £1.50 per pair Size of clock approximately 8" x 5" x 5", totally encased but has lift up flap for ease of altering switching times. Price, new and unused £10.65 or used but guaranteed o.k. £6.50.

Enclosed 24 Hour Clock, with contacts for breaking 10-12 amps at 240 volts. This one has two sets of on/off per 24 hours, price £7.00.

Smiths 24 hr. Timers—Heart only, with over-ride similar to those used in the auto set etc. £4.75 + 38p.

Light Dimmer, our timer module with small mods makes an excellent light dimmer. Contains a 4 amp 400v SCR so it should be suitable for loads approaching 1kW. Price of module with variable resistor and instructions £2.25.

Push Pull Solenoids, mains operated solenoids which will push as well as or instead of pull. Very heavy duty estimate this at 20lbs push or pull 1 1/2" x 3 1/2" x 4" made Magnetic Devices Co. £7.50.

Flashing Lights, chasing lights, random flashes, strobe effects etc. etc. can easily be achieved using our disco switches and with Christmas just around the corner you can do something special for your home or business. These switches are offered at approximately one-fifth of their proper price are ex-equipment but guaranteed perfect and supplied with an adaptor suitable for mains working. To get some idea of the loading number, each switch is 10 amp which is approx 2kW so the 6 switch model could handle over 12kW's.

For the light pipe or Catherine Wheel effect we suggest 12 switch model, interconnecting the switches to give fastest speed. 6 switch model £5. 9 switch model £9.75. 12 switch model £6.20. Also add 50p post per switch. If you want the light pipe diagram please request this.

Always in Stock. Turntables with pick-up lift, ideal for disco's at £11.95, post £2.25. We are also expecting some professional belt drive type at £25. Call or ring us for more information.

Reed Switches, standard 60 watt glass type. Normal open contacts glass lengths 2" diameter 3/16" 10 for £1 + 8p, 100 for £8 + 64p, 1000 for £65 + £5.20.

Flat Reed Switches, for stacking, greater quantity in confined space. Price 50p each. 4p.

Single Ended Types for jobs where it is not easy to bring a lead to each end 75p each. All these switches are normally open but can be biased to a normally closed position by fitting a magnet adjacent. The reed switch would then be opened by a magnet of opposite polarity being brought up to it.

Ceramic Magnets suitable for operating reed switches, central fixing hole. 10 for £1.

Music Centre Transformer 12-0-12 at 1 amp and 9 volt at 1/2 amp. Normal primary, upright mounting, impregnated and varnished for quiet operation. Price £2.95. Post 54p.

"W" Shaped Fluorescent Tubes for porch light, box signs or where you want light evenly spaced over a confined area of approx. 10" x 10", 30 watts, made by Philips price £1.60. Post 54p.

Plinth for BSR Record Player still available at the record price of 95p + 12p. This is excellent value but unfortunately being a bulky and delicate item the postage has to be £1.50 + 12p so this is obviously only a bargain for callers.

Our Smokey Cover can be used with the above plinths, four small locating pins are fitted to the motor board. Size approx 12 1/2" x 14 1/2". Price £2.50 + 32p Post £2.00 + 16p.

Extension Speakers 8 ohm 4-5 watts handling power. We have 5 or 6 different models in stock, cheapest being the Partytime at £3.95 each, again only really a bargain for callers as postage is £1.50 per speaker.

T.V. Monitor, an item for callers, believed to be in good working order, switchable thro' 405-525 & 625. 21" tube line systems, normal controls, volume, brightness, contrast, width etc. Price £16-20, 12" model £18, suitable for conversion into special purpose scope, etc.

Auto transformers for working American tools and equipment, completely enclosed in sheet metal case with American type flat output socket made for computer so obviously first class, 500 watts With carrying handle, offered at about half price only £15 + 80p, carriage £2 + 16p. These may be a bit soiled but are fully guaranteed. Similar but 1000 watt £29.50 or £6.48. Post £1.62.

AUDIO MODULES - ALL REDUCED! TRANSISTOR PRICES SLASHED! MANY PAKS 33% OFF

BI-PAK GREAT SPACE

WE NEED THE SPACE

SPECIAL OFFER!

THYRISTORS

No. THY1A/50	1 Amp.	50 volt	T05	18p
No. THY1A/400	1 Amp.	400 volt	T05	32p
No. THY3A/50	3 Amp.	50 volt	T064	25p
No. THY3A/200	3 Amp.	200 volt	T064	32p
No. THY3A/400	3 Amp.	400 volt	T064	40p
No. THY5A/50	5 Amp.	50 volt	T066	25p
No. THY5A/400	5 Amp.	400 volt	T066	40p
No. THY5A/600	5 Amp.	600 volt	T066	50p
No. C106/4	6 Amp.	400 volt	T0220	42p

TRIAC

S84	8 Amp.	400 Volt	T0220 Plastic (Non Isolated Tab)	80p
-----	--------	----------	----------------------------------	-----

DIACS

BR100				15p
D32				15p

SWITCHES

No. 16178	5 x Mains Slide Switches	40p*
No. S17	5 x Miniature Slide Switches	40p*
No. S18	4 x Standard Slide Switches	40p*
No. S19	4 x Miniature Push to Make single hole mounting	40p*
No. S20	3 x Miniature Push to Break single hole mounting	40p*
No. S21	Push button Switch Pak 4 x Assorted types multi bank and singles Latching and non-Latching	£1.00*

CAPACITOR PAKS

16201	18 Electrolytics	4.7µF - 10µF	
16202	18 Electrolytics	10µF - 100µF	
16203	18 Electrolytics	100µF - 680µF	
All 3 at SPECIAL PRICE of £1.20*			
16160	24 Ceramic Caps	22pF - 82pF	
16161	24 Ceramic Caps	100pF - 390pF	
16162	24 Ceramic Caps	470pF - 3300	
16163	21 Ceramic Caps	4700pF - 0.047µF	
All 4 at SPECIAL PRICE of £1.60			

RESISTOR PAKS

Order No.				
16213	60½W.	100 ohm - 820 ohm		
16214	60½W.	1K - 8.2K		
16215	60½W.	10K - 82K		
16216	60½W.	100K - 820K		
All 4 at SPECIAL PRICE of £1.60*				
16217	40½W.	100 ohm - 820 ohm		
16218	40½W.	1W - 8.2K		
16219	40½W.	1K - 8.2K		
16220	40½W.	100K - 820K		
All 4 at SPECIAL PRICE of £1.60*				

TRANSISTOR FALL-OUT PACK, GERM, SILICON, POWER, NPN, PNP. ALL MIXED. YOURS TO SORT AND TEST. Approx. 500 Pieces. Order No. S23 £1.25 per pack.

VOLTAGE REGULATORS

Positive			
No. MVR7805	µA7805	T0220	85p
No. MVR7812	µA7812	T0220	85p
No. MVR7815	µA7815	T0220	85p
No. MVR7818	µA7818	T0220	85p
No. MVR7824	µA7824	T0220	85p
Negative			
No. MVR7905	µA7905	T0220	£1.10
No. MVR7912	µA7912	T0220	£1.10
No. MVR7915	µA7915	T0220	£1.10
No. MVR7918	µA7918	T0220	£1.10
No. MVR7924	µA7924	T0220	£1.10
µA723C T099	38p	72723 14 pin Dil	38p
LM309K T03			£1.20

MICROPHONES

DYNAMIC DUAL IMPEDANCE UNI DIRECTIONAL CARDIOID MICROPHONE
Impedance 600 ohms and 50K. Response 50-14,000 Hz. Sensitivity 54db at 50K.
Size 1½" Dia x 6½" Long
Order No. 1328 £7.50*

DYNAMIC CASSETTE MIC

Fitted with On/Off switch, 1 metre of tough lead with floating 2.5 and 3.5 mm plugs.
Impedance 200 ohms Sensitivity 90db
Frequency 90-10,000 Hz.
Size 20mm Dia. x 120mm Long
Order No. 1326 £1.15*

LOGIC PROBE

A pocket size instrument capable of detecting T.T.L., D.T.L. Flip Flop and other pulse circuits. It is easy to use and operates from the 5V. D.C. supply of the circuit under test. The logic levels are indicated by 2 red LED's one for High and the other for Low. There is also a green LED for the Pulse Mode of the unit.
No. S59 Our Special Price £18.95.

TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	*9p	TIP32A	34p	2N1613	15p
AC126	14p	BC178	12p	BF195	*9p	TIP32B	35p	2N1711	15p
AC127	16p	BC179	12p	BF196	*12p	TIP32C	36p	2N1893	28p
AC128	16p	BC182	*9p	BF197	*12p	TIP41A	34p	2N2218	15p
AC128K	24p	BC182L	*9p	BF200	25p	TIP41B	35p	2N2218A	18p
AC176	16p	BC183	*9p	BFX29	22p	TIP41C	36p	2N2219	15p
AC176K	24p	BC183L	*9p	BFX84	18p	TIP42A	36p	2N2219A	18p
AC187	16p	BC184	*9p	BFY50	12p	TIP42B	37p	2N2221	15p
AC187K	26p	8C184L	*9p	BFY51	12p	TIP42C	38p	2N2221A	16p
AC188	16p	BC212	*10p	BFY52	12p	TIP2955	65p	2N2222	15p
AC188K	26p	8C212L	*10p	MPSA05	*22p	TIP3055	42p	2N2222A	16p
AD161/1		BC213	*10p	MPSA06	*22p	ZTX107	*6p	2N2369	10p
162 MP	80p	BC213L	*10p	MPSA06	*22p	ZTX108	*6p	2N2904	14p
AF139	30p	BC214	*10p	MPSA55	*22p	ZTX109	*7p	2N2904A	15p
AF239	30p	BC214L	*10p	MPSA56	*22p	ZTX300	*7p	2N2905	14p
BC107	6p	BC251	*10p	OC44	12p	ZTX301	*7p	2N2905A	15p
BC108	6p	BCY70	12p	OC45	12p	ZTX302	*9p	2N2906	12p
BC109	6p	BCY71	12p	OC71	9p	ZTX500	*8p	2N2906A	14p
BC118	*10p	BCY72	12p	OC72	12p	ZTX501	*10p	2N2907	12p
BC147	*8p	BD115	40p	OC75	10p	ZTX502	*12p	2N2907A	13p
BC148	*8p	BD131	*35p	OC81	14p	2N696	10p	2N2926G	*8p
BC149	*8p	BD132	*37p	TIP29A	35p	2N697	10p	2N2926Y	*7p
BC154	*16p	BF115	17p	TIP29B	35p	2N706	7p	2N3053	12p
BC157	*9p	BF167	19p	TIP29C	36p	2N706A	8p	2N3055	35p
BC158	*9p	BF173	20p	TIP29C	36p	2N708	8p	2N3702	*7p
BC159	*9p	BF180	25p	TIP30A	38p	2N1302	12p	2N3703	*7p
BC169C	*10p	BF181	25p	TIP30B	37p	2N1303	15p	2N3704	*6p
BC170	6p	BF182	25p	TIP30C	38p	2N1304	15p	2N3903	*11p
BC171	*6p	BF183	25p	TIP31A	32p	2N1307	18p	2N3904	*11p
BC172	*6p	BF184	25p	TIP31B	33p	2N1308	22p	2N3905	*11p
BC173	7p	BF185	25p	TIP31C	34p	2N1309	22p	2N3906	*11p

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	8AX16/		BYZ16	30p	OA85	7p
AAZ13	4p	OA202	5p	BYZ17	28p	OA90	6p
BA100	6p			BYZ18	28p	OA91	7p
BA115	5p	BY100	15p	BYZ19	28p	OA95	7p
BA144	5p	BY127	*10p	OA47	5p	IN34	5p
BA148	10p	BY210	32p	OA70	5p	IN60	6p
BA173	10p	BY211	32p	OA79	7p	IN914	4p
BAX13/		BYZ12	32p	OA81	7p	IN4148	4p
OA200	5p	8YZ13	30p				

LINEAR I.C.'s

TBA800	12 pin QIL	*75p	UA711C T099	25p	UA748 T099	28p
TBA810	12 pin QIL	*£1.00	UA703 T099 (Plastic)	20p	72558 (Dual 748) T099	45p
TBA820	14 pin QIL	*80p	741P 8 pin DIL	18p	MC1310P 14 pin DIL	*£1.25
LM380	14 pin DIL	*80p	72741 14 pin DIL	20p	76115 14 pin DIL	*£1.25
LM381	14 pin DIL	*£1.35	UA741C T099	20p	NE555 8 pin DIL	32p
72709	14 pin DIL	28p	72747 14 pin DIL	55p	NE556 14 pin DIL	60p
UA709 T099		28p	748P 8 pin DIL	28p	SL414A 10 pin	*£1.80

NEW CONSIGNMENT ZN 414 RADIO CHIP 75p*

OPTOELECTRONICS

Displays		2nd QUALITY LED PAKS			
No 1510	707 LED Display	70p each	No. 1507	10 x LED's Assorted	75p
No 1511	747 LED Display	£1.50 each	LED CLIPS		
No. 553	DL33 Triple 7 Segment LED Display Character height 11 Common Cathode 12 pin DIL	30p each	No 1508/125	.125	5 for 12p
LED's			No 1508/2	.2	5 for 15p
No. S51	Red TIL209 (5 x .125")	50p	SPECIAL REDUCTIONS		
No. S52	Red FLV117 (5 x .2")	50p	No 1514	NORP 12	45p each
No. 1502	Green .125"	18p each	No S76	OC7P1	5 for £1.00
No. 1505	Green .2"	18p each	No S83 5,	NIXIE Tubes ITT 5870 ST	£2.00
No 1503	Yellow .125"	18p each	(including Data)		
No. 1506	Yellow .2"	18p each	No S77	Neon Indicator Lamps 230V A.C State Colour (Red, Amber and Green)	25p each
No. S82	Clear .2" (illuminating red)	12p			

D.I.Y. PRINTED CIRCUIT KIT

Contains 6 pieces of copper laminate board, box of etchant powder, measure, tweezers, marker pen, high quality pump drill, Stanley knife and blades and 6 in metal rule.
Full easy to follow instructions.
Order No. S64 Sale Price £5.50

P.C.B. BOARDS

S61	8 pieces 8" x 3½" (approx.) single sided paper	50p
S62	4 pieces 8" x 3½" (approx.) single sided fibreglass	50p
S63	3 pieces 7" x 3½" (approx.) double sided fibreglass	50p

ETCH RESIST PENS

Order No. 1609 50p each

SOLDER

5m of 18 sw Multi-core Solder.
Order No. S60 50p

I.C. INSERTION EXTRACTION TOOL

Order No. 2015 30p

MAMMOTH I.C. PAK

Approx 200 Pieces Assorted fall-out integrated circuits, including Logic, 74 series Linear, Audio and D.T.L. Many coded devices, but some unmarked - you to identify
Order No 16223 £1.00

POWER SUPPLY STABILIZER BOARD

Unused ex-equipment stabilizer board. Input 30V D.C. Output 20V Complete with circuit diagram.
Order No. S81 £1.25

P.O. RELAYS

S85 - 2 Off Post Office relays 40p

BATTERY HOLDERS

to take 6 x HP7's
Order No. 202 10p each

EX. G.P.O. MICROSWITCHES

Order No. S51 4 for 50p

CABLE CLIPS

S84 - 50 2.5mm round single pin fixing 30p

SEMICONDUCTOR PAKS

Code No's shown below are given as a guide to the type of device. The devices themselves are normally unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40p
No. 16131	150 Germ. Point contact diodes like OA70/81	40p
No. 16132	100 200mA Sil. diodes like OA200	40p
No. 16133	150 75mA Sil. Fast switching diode like IN4148	40p
No. 16134	50 750mA Sil. top hat Rects. like OA70	40p
No. 16135	20 3 amp Sil. stud Rect.	40p
No. 16136	50 400mW Zeners D.O.7 case	40p
No. 16137	30 PNP Plastic trans. like BC107/8	40p*
No. 16138	30 PNP Plastic trans. like BC177/8	40p*
No. 16139	25 NPN trans. like 2N697/2N1711 T039	40p
No. 16140	25 PNP trans. like 2N2905 T039	40p
No. 16141	30 PNP trans. like 2N706 T01B	40p*
No. 16143	30 PNP Plastic trans. like 2N3906	40p*
No. 16144	30 PNP Plastic trans like 2N3905	40p*
No. 16145	30 PNP Germ. trans. like OC71	40p
No. 16147	10 NPN to 3 Power trans. like 2N3055	80p

I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.00
No. S67	10 x 14 pin DIL Sockets	£1.00
No. S68	9 x 16 pin DIL Sockets	£1.00
No. S69	4 x 24 pin DIL Sockets	£1.00
No. S70	3 x 28 pin DIL Sockets	£1.00

TRANSISTOR SOCKETS

No. S71	15 x T018 Sockets	£1.00
No. S72	10 x T05 Sockets	£1.00

MOUNTING PADS

No. S73 50 Mixed Transistor Pads T018 and T05 40p

TRANSISTOR HEATSINK PAK

20 Assorted types, T01, T05, T018, T092
Our Mix
Order No. S75 60p

TRANSISTOR INSULATING KITS

Mica washers and bushes assorted types i.e. T0220, T066, T03 etc. Approx. 100 pieces. (Approx. 40 sets)
Order No. S74 50p

DARLINGTON POWER TRANSISTORS

70 watt 8 amp NPN and PNP in plastic case 199 High Voltage (Typ 80V). High gain. 10 pieces 5 NPN and 5 PNP Data Sheet supplied.
Order No. S78 £1.00 per Pak

MATCHED PAIRS OF PNP GERMANIUM MED. POWER TRANS

2 amp		750mW	
VCE	VCB	HFE	
NKT301	40	60	30-100 35p per pair
NKT302	40	60	50-150 35p per pair
NKT303	20	30	30-100 25p per pair
NKT304</			

SAVING SALE BI-PAK

YOU MAKE THE SAVING!

OPT FOR OPTOELECTRONICS! PRINTED CIRCUIT KITS, BOARDS & PENS.

SILICON RECTIFIERS - 1/2 AMP. G.E.

No. S48	40 x 50V	60p
No. S49	30 x 200V	60p
No. S50	20 x 700V	60p

G.E. HIGH VOLTAGE SILICON RECTIFIERS

GR559	10mA 14KV (14,000)	20p each
GA432	1 AMP. 2 KV (2,000)	20p each
FD2.5	2.5 KV Voltage Doubler	20p each

POTENTIOMETERS

Slider 40mm TRAVEL			
Order No.			
16191	6 x 470 Ohm LIN Single	40p*	
S24	6 x 1 K LIN Single	40p*	
S25	6 x 5 K LIN Single	40p*	
16192	6 x 10 K LIN Single	40p*	
S26	6 x 10 K LOG Single	40p*	
16193	6 x 22 K LIN Single	40p*	
16195	6 x 47 K LOG Single	40p*	
16194	6 x 47 K LIN Single	40p*	
S27	6 x 100 K LIN Single	40p*	
S28	6 x 100 K LOG Single	40p*	
S29	6 x 500 K LOG Single	40p*	

Slider 60mm TRAVEL			
Order No.			
S30	6 x 2.5 K LOG Single	40p*	
S31	6 x 10 K LIN Single	40p*	
S32	6 x 50 K LIN Single	40p*	
S33	6 x 250 K LOG Single	40p*	
S34	4 x 5 K LOG Dual	40p*	
S35	4 x 10 K LIN Dual	40p*	
S36	4 x 100 K LOG Dual	40p*	
S37	4 x 1.3 MEG LOG Dual	40p*	

S38 MIXED SLIDER POTS - VARIOUS VALUES AND SIZES - OUR MIX ONLY £1.00*
S39 6 x CHROME SLIDER KNOBS 40p*

WIREWOUND

A range of wirewound single gang pots. with linear tracks of 1 watt rating.

Order No.	Value	Order No.	Value
1891	10 ohms	1894	100 ohms
1893	47 ohms	1895	220 ohms
1896	470 ohms	1898	2K2
1897	1K	1899	4K7

NOW 35p* each

16173	15 Rotary Potentiometers. Assorted values and types.	40p*
16186	25 Pre-sets Assorted Values and types	40p*

SALE PRICE 40p

MULTI-TURN PRE-SETS

S40 3 x 100 K LIN ONLY 50p*

AUDIO PLUG AND SOCKET PAKS

Order No.		
S1	5 x 3.5 mm Plastic Jack Plugs	40p*
S2	5 x 2.5 mm Plastic Jack Plugs	40p*
S3	4 x Std. Plastic Jack Plugs	30p*
S4	2 x Stereo Jack Plugs	30p*
S5	5 x 5 Pin 180° DIN Plugs	50p*
S6	8 x 2 Pin Loudspeaker Plugs	50p*
S7	6 x Phono Plugs Plastic	50p*
S8	5 x 3.5 mm Chassis Sockets (Switched)	25p*
S9	5 x 2.5 mm Chassis Sockets (Switched)	25p*
S10	4 x Metal Std. Chassis Switched Jack Sockets	50p*
S11	2 x Stereo Jack Sockets with instruction leaflet for H/Phone connection.	50p*
S12	5 x 5 Pin 180° DIN Chassis Sockets	40p*
S13	8 x 2 Pin DIN Chassis Sockets	50p*
S14	6 x Single Phono Sockets	40p*

AUDIO LEADS

Order No.		
117	A.C. Mains connecting lead for cassette recorders and radios Telefunken type	45p*
118	5 pin DIN headphone plug to stereo socket	78p*
119	2 x 2 pin plug to inline stereo socket for headphones	60p*
123	20 ft. of coiled guitar lead	£1.15*
124	3 pin to 3 pin DIN plug	50p*
125	Audio lead 5 pin plug to 5 pin DIN plug	50p*
126	Audio lead 5 pin DIN plug to tinned open ends	50p*
127	Audio lead 5 pin DIN plug to 4 phono plugs	90p*
129	Audio lead 5 pin plug to 5 pin DIN plug - Mirror Image	70p*
130	5 metre lead 2 pin DIN plug to 2 pin DIN inline socket	45p*
132	10 metre lead 2 pin DIN plug	65p*

HEAVY GAUGE BLACK PLASTIC BOX

With aluminium lid and fixing screws. Size 6 1/2" x 3 1/2" x 2" Order No. S16 Only 75p

74 SERIES TTL ICs

TYPE		QUANTITY		TYPE		QUANTITY		
1	Ep	1	Ep	1	Ep	1	Ep	
7400	0.09	0.08	7448	0.70	0.68	74122	0.45	0.42
7401	0.11	0.10	7450	0.12	0.10	74123	0.65	0.62
7402	0.11	0.10	7451	0.12	0.10	74141	0.68	0.65
7403	0.11	0.10	7453	0.12	0.10	74145	0.75	0.72
7404	0.11	0.10	7454	0.12	0.10	74150	1.10	1.05
7405	0.11	0.10	7460	0.12	0.10	74151	0.85	0.80
7406	0.28	0.25	7470	0.24	0.23	74153	0.70	0.68
7407	0.28	0.25	7472	0.20	0.19	74154	1.20	1.10
7408	0.12	0.11	7473	0.26	0.22	74155	0.70	0.68
7409	0.12	0.11	7474	0.24	0.23	74156	0.70	0.68
7410	0.09	0.03	7475	0.44	0.40	74157	0.70	0.68
7411	0.22	0.20	7476	0.26	0.25	74160	0.95	0.85
7412	0.22	0.20	7480	0.45	0.42	74161	0.95	0.85
7413	0.26	0.25	7481	0.90	0.88	74162	0.95	0.85
7416	0.28	0.25	7482	0.75	0.73	74163	0.95	0.85
7417	0.26	0.25	7483	0.88	0.82	74164	1.20	1.10
7420	0.11	0.10	7484	0.85	0.80	74165	1.20	1.10
7422	0.19	0.18	7485	1.10	1.00	74166	1.20	1.10
7423	0.21	0.20	7486	0.28	0.26	74174	1.10	1.00
7425	0.25	0.23	7489	2.70	2.50	74175	0.85	0.82
7426	0.25	0.23	7490	0.38	0.32	74176	1.10	1.00
7427	0.25	0.23	7491	0.65	0.62	74177	1.10	1.00
7428	0.36	0.34	7492	0.43	0.35	74180	1.10	1.00
7430	0.12	0.10	7493	0.38	0.35	74181	1.90	1.80
7432	0.20	0.19	7494	0.70	0.68	74182	0.80	0.74
7433	0.38	0.36	7495	0.60	0.58	74184	1.50	1.40
7437	0.26	0.25	7496	0.70	0.68	74190	1.40	1.30
7438	0.26	0.25	74100	0.95	0.90	74191	1.40	1.30
7440	0.12	0.10	74104	0.40	0.35	74192	1.10	1.00
7441	0.60	0.57	74105	0.30	0.25	74193	1.05	1.00
7442	0.80	0.70	74107	0.30	0.25	74194	1.05	1.00
7443	0.95	0.90	74110	0.48	0.45	74195	0.80	0.75
7444	0.95	0.90	74111	0.75	0.72	74196	0.90	0.85
7445	0.80	0.75	74118	0.85	0.82	74197	0.90	0.85
7446	0.80	0.75	74119	1.30	1.20	74198	1.90	1.80
7447	0.70	0.68	74121	0.28	0.26	74199	1.80	1.70

Devices may be mixed to qualify for quantity price. Data is available for the above series of ICs in booklet form price 35p.

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.14	CD4018	£0.85	CD4035	£1.40	CD4056	£1.15
CD4001	£0.16	CD4019	£0.45	CD4037	£0.78	CD4069	£0.32
CD4002	£0.16	CD4020	£0.95	CD4040	£0.78	CD4070	£0.32
CD4006	£0.80	CD4021	£0.85	CD4041	£0.68	CD4071	£0.20
CD4007	£0.17	CD4022	£0.80	CD4042	£0.68	CD4072	£0.20
CD4008	£0.80	CD4023	£0.18	CD4043	£0.78	CD4081	£0.20
CD4009	£0.50	CD4024	£0.64	CD4044	£0.78	CD4082	£0.20
CD4010	£0.50	CD4025	£0.18	CD4045	£1.15	CD4510	£1.10
CD4011	£0.18	CD4026	£1.85	CD4046	£0.95	CD4511	£1.25
CD4012	£0.17	CD4027	£0.48	CD4047	£0.75	CD4516	£1.10
CD4013	£0.42	CD4028	£0.80	CD4049	£0.46	CD4518	£1.10
CD4015	£0.80	CD4029	£0.95	CD4050	£0.46	CD4520	£1.10
CD4016	£0.42	CD4030	£0.46	CD4054	£0.95		
CD4017	£0.80	CD4031	£1.80	CD4055	£1.60		

AUDIO MODULE SALE

Type	Description	Normal Price	Sale Price
AL30A	10W RMS Power Amp	£3.65*	£2.95*
AL60	25W RMS Power Amp	£4.35*	£3.55*
AL80	35W RMS Power Amp	£6.95*	£5.95
AL250	125 W RMS Power Amp	£16.95*	£14.45
SPM80	35V Power Supply	£2.75*	£3.10*
PS12	20-30V Power Supply for AL30A	£1.30*	£1.15*
PA12	Stereo Pre-Amp for AL30A	£6.20*	£5.95*
PA100	Stereo Pre-Amp for AL60/AL80	£12.75*	£12.45*
S450	Stereo F.M. Tuner	£20.45*	£18.65*
MPA30	Magnetic-Ceramic Pre-Amp	£2.65*	£2.55*
Stereo 30	Complete Audio Chassis 7W - 7W RMS	£16.25*	£14.95*

LOOK & LISTEN GE 100 NINE CHANNEL MONO-GRAPHIC EQUALIZER MODULE

The GE100 has nine 1 octave adjustments using integrated circuit active filters. Boost and Cut limits are ± 12db, Max. Voltage handling 2 V RMS, T.H.D., 0.5%, input impedance 100 K, output impedance less than 10 K. Frequency response 20 Hz-20 KHz (3db). The nine gain controls are centred at 50, 100, 200, 400, 800, 1600, 3200, 6400 and 12,800 Hz. The suggested gain controls are 10 K LIN sliders. (Not supplied with the module). See Paks S31 and 16192.

ONLY £19.50

SG30 Power supply board for GE100 15-0-15 Volt £4.50

SEND SAE FOR TECHNICAL DATA ON ANY OF THE AUDIO MODULES.

SPECIAL OFFER! COMPONENT PAKS

Order No.	Quantity	Value
16164	200 approx. Resistors mixed values. (Count by weight)	40p*
16165	150 approx. Capacitors mixed values. (Count by weight)	40p*
16167	80 1/2W Resistors mixed values	40p*
16168	5 pieces Assorted Ferrite rods	40p*
16169	2 pieces Tuning gangs MW/LW	40p*
16170	50 metres Single strand wire assorted wire	40p
16171	10 Reed switches	40p*
16172	3 Micro switches	40p*
16176	20 Assorted electrolytics Trans types	40p*
16177	1 pack Assorted hardware nuts/bolts etc.	40p
16179	20 Assorted tag strips and panels	40p
16180	15 Assorted control knobs	40p*
16184	15 Assorted Fuses 100mA - 5 amp	40p*
16188	60 1/2W resistors mixed values	40p*
16187	30 metres stranded wire assorted colours	40p

1/2 PRICE BARGAIN!

£4 worth (Min. Value)

of Electronic Project Books, Technical, Semiconductor Data and Equivs - Books of Assorted Titles. **OUR CLEARANCE PRICE £2 per bundle**

Order No. S80

SUPER SOUND SAVING METROSOUND LOW NOISE CASSETTES



Order No. S53 10 for £2.50*

BIB GROOVE CLEAN

Model 60. Chrome Finish Plastic

Order No. 829 £1.40*

HOT OFFER

ANTEX SOLDERING IRONS

Order No. 1931 X25 25 watt. LOW LEAKAGE

Usually £3.40 SALE PRICE £2.95

PLUS FREE Heatshunt

1948 Model C 15 watt General purpose

Usually £3.40 SALE PRICE £2.95

PLUS FREE Heatshunt

1939 ST3 Soldering Iron Stand suitable for either Iron. £1.20

NEW Siren Alarm Module

American Police screamer powered from a 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down, and other security purposes.

Order No. S15 £3.50

AVDEL BOND

Cyanocrylate adhesive bonds - plastic, rubber, transistors, components in seconds.

Order No. 143 55p per 2 gm. phial

ORDERING

Please word your orders exactly as printed, not forgetting to include our part number.

VAT

Add 12 1/2% to prices marked*
Add 8% to others excepting those marked †. These are zero.

BI-PAK



EDITOR

Geoffrey C. Arnold

ASSISTANT EDITOR

Dick Ganderton, C. Eng., MIERE

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Ted Parratt, BA

NEWS & PRODUCTION EDITOR

Alan Martin

TECHNICAL SUB-EDITOR

Peter Preston

TECHNICAL ARTIST

Rob Mackie

SECRETARIAL

Sylvia Barrett
Lynda Goddard

EDITORIAL OFFICES

Westover House, West Quay Road,
POOLE, Dorset BH15 1JG
Telephone: Poole 71191

ADVERTISING MANAGER

01-261 5000

Roy Smith

CLASSIFIED ADVERTISING

01-261 5762

Colin R. Brown

ADVERTISING OFFICES

King's Reach Tower, Stamford Street,
London SE1 9LS

BINDERS

Binders, for either the old or the new format, are £2.85 and Indexes are 45p (Inc VAT) and can be obtained from the Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF. Remittances with overseas orders for binders should include 60p to cover despatch and postage.

BACK NUMBERS

We are very glad to announce the re-establishment of a PW Back Numbers Service for our readers. In future back numbers dated from June 1977 only will be available from our Post Sales Department for 65p, which includes postage and packing. Cheques and Postal Orders should be made payable to IPC Magazines Ltd.

Send your orders to:- Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

A Time of Change

THOSE among our readers who notice such things will have realised that there are quite a number of new names among the staff of *PRACTICAL WIRELESS*, as listed on this page. When it was announced earlier this year that some of the Practical group of magazines were to move to Poole, there were several staff members who, for various personal reasons, felt unable to make the move away from London.

To those we have left behind, we say a farewell, and thank them for all that they have done for the magazine in the past. Some were comparative newcomers, others had been familiar names for many years. Some will, we hope, continue to make a contribution to *PW*, and so for them the break will not be complete.

We bid a welcome to our new staff, who bring with them in-depth knowledge of several fields which are, we know, of great interest to you, our readers. We plan to make use of this knowledge for your future interest and enlightenment.

With all these changes, including a new occupant for the editor's chair, you will probably be wondering what the future pattern of the magazine will be. Well, there will undoubtedly be some changes, but we hope not to frighten away our established readers! As our title would imply, we shall continue to give regular attention to wireless or radio—call it what you will—in its various applications, but will not neglect the ever-popular fields of hi-fi, disco equipment, musical instruments, nor the requirements of the electronics hobbyist. We hope you'll like the mix!

Geoffrey C. Arnold

PLEASE NOTE

We do not operate a Technical Query Service except on matters concerning constructional articles published in *PW*. We do not supply service sheets or information on commercial radios, TV's or electronic equipment.

All queries must be accompanied by a stamped self-addressed envelope otherwise a reply cannot be guaranteed.

Mini Monitor

Shown for the first time at Video-Tradex, the Sinclair picture monitors MON 1A and MON 1A/S are derived from the well-proven Microvision.

Special interfacing provides for standard level international signals. The model at the exhibition operates on the CCIR format but, as with the Microvision receiver, Sinclair will be able to adapt the device to 525-lines 60 fields.

Model MON 1A is cased, uses integral, rechargeable NiCad batteries and is supplied with a power unit. In addition to its normal function, it could well find application as a view-finder.

The MON 1A/S is supplied less case and cells, but is otherwise likened to the MON 1A. It is principally aimed at OEMs and systems engineers.

Both monitors in their CCIR form accept a standard, composite input of 0.7 volts video/0.3 volts sync, which is terminated by 75 ohms.

Connection is via a BNC socket.

Each unit is unconditionally guaranteed by the manufacturer for 1 year from date of purchase; should any unit fail within this time, the Company will repair or replace it free of charge. For details of price apply to:

Sinclair Radionics Ltd., London Road, St. Ives, Huntingdon, Cambridgeshire.



More Chips!

Texas Instruments have recently announced details of several new devices. The TL505 is an analog-to-digital converter IC, and is designed for use with microprocessors similar to the Texas TMS1000 series. Both the TL505 and the TMS1000 are designed to operate from a single 7 to 15 volt supply, making them ideal for battery operation. Other features are three-digit (0.1%) accuracy, on-chip reference voltage, auto-zero, and high impedance MOS inputs. Unfortunately, prices are only quoted for 100 piece batches—in this case £2.29 each chip.

Also announced, and in roughly the same operating area, is a 5 volt regulator, with, it is claimed, greatly improved accuracy. Designated TL7805AC it is credited with an output current capability of 1.5 amps, with internal current limiting and thermal shutdown, thus providing reasonable immunity to overload. This device is priced at £1.12 each item, per batch of 100.

Finally, two new series of BIFET op. amps have emerged. These are the TL061 series, comprising three low-power op. amps, and the TL071 series with four low-noise audio op. amps. These are monolithic IC op. amps using high impedance junction field-effect transistors and bipolar transistors in a single chip. The TL061 device features a 3.5V per second

slew rate, and the TL071 is quoted with a harmonic distortion of 0.01% typically, and a low noise level of 18 nanovolt per root Hertz. Both series feature a very high input impedance, and wide unity gain bandwidths, allowing significantly higher gain at higher frequencies than the 741 series. Both the TL061 and the TL071 are available in 8 pin plastic and ceramic dual-in-line packages. No prices are to hand for these, but details may be obtained, as with the rest of the devices reviewed, from:

Texas Instruments, Linear Circuits Department, Manton Lane, Bedford.

Video Recording at South London Tech.

A short course of nine special lectures on monochrome and colour video recording techniques, systems and applications of magnetic tape and cassette recorders for closed circuit television and broadcasting will be held in the Lecture Hall on consecutive Tuesday evenings from 6.30 to 8.30pm, commencing 17 January 1978. Slides will be shown and demonstrations will be given.

This course is intended for radio and television technicians and engineers, and for video recording enthusiasts. A basic knowledge of radio and television will be assumed. The course will be conducted by specialists

from industrial organisations. The course fee is £6 and early enrolment is advised.

For details apply to:

A. A. Rowlands, South London Technical College, Knights Hill, London SE27 2JR. Tel: 01 670 4488.

Get in quick


Have you got the latest Technomatic catalogue? If you haven't, read on.

The catalogue contains their latest price list, also a special offer list for the new year.

Technomatic specialise in the semiconductor field, supplying only first grade, current date code, quality devices, produced by major manufacturers. They are concentrating their efforts on providing a comprehensive service for all your semiconductor requirements. We are assured the components offered are not surplus, but are their regular stock items and are fully guaranteed.

The special offer list is normally valid until 21 January 1978, however, if you mention *Practical Wireless* with your order, Technomatic have kindly agreed to extend the closing date until 10 February 1978.

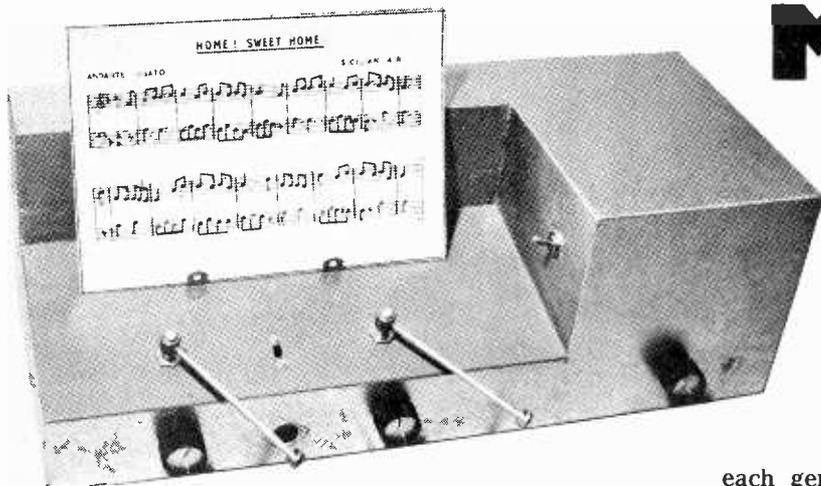The catalogue and special offer lists are available, free of charge, if you send a SAE (6in x 9in) from *Technomatic Ltd., 54, Sandhurst Road, London NW9 9LR. Tel: 01-204 4333.*



MULTIVIB 'MUSICO'

R.H. LONGDEN

The Theremin was a novel electronic instrument in which radio frequencies were combined to produce an audible beat. It had infinitely-variable pitch, obtained by hand capacitance, but would not meet present-day radiation suppression requirements. A similar result however is even more readily obtained by using a variable frequency multivibrator.

Most musical instruments can be divided into two classes. In one, the pitch is found by the skill of the performer: in the other, the note is pre-tuned and is selected by the performer from the available range. The Multivib "Musico" can be used in either way: as an instrument in which the frequency is selected by the movement of projecting arms or tillers, or with a plug-in keyboard, tuned for two octaves.

Two note generators are used, so that separate left and right-hand tones are available. The whole instrument, especially with the two tiller controls, is extremely straightforward and has an IC audio amplifier which further simplifies building. It is operated from a dry battery. Separate bass (left hand) and treble (right hand) output controls are fitted, in addition to a volume control. There is also a jack outlet, either to permit the use of a bigger speaker, or to allow personal practice with a headset.

Note Generator

As each generator is variable, only two are required, and the circuit, Fig. 1 is duplicated for the second unit. The frequency is controlled by the resistance connected to point 3, which is in series with R2. The output from C3 goes to the level control so that

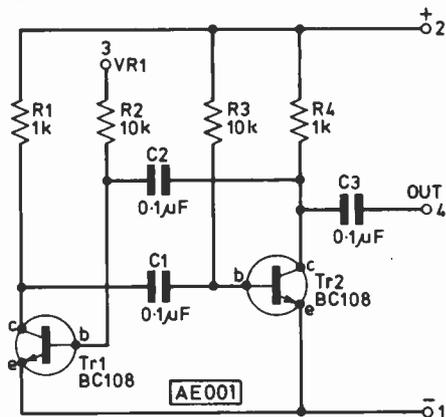


Fig. 1: The Tone Generator circuit diagram.

each generator is able to cover the same range of frequencies; with the two tillers in use, both may be operated at any point within the range available. Therefore both could be on bass or treble frequencies, if desired. This is particularly useful for sound effects.

When the keyboard is added, one generator is tuned for the octave below Middle C, the other running upwards from here, in order to obtain consecutive notation. The left hand is then confined to notes below Middle C, the right hand playing Middle C and higher notes.

Tag-Boards

Each board is made as in Fig. 2. Other forms of wiring could be employed, but this is a method needing no preparation, and taking very little time. Low voltage disc ceramic capacitors are used, and the components are not critical.

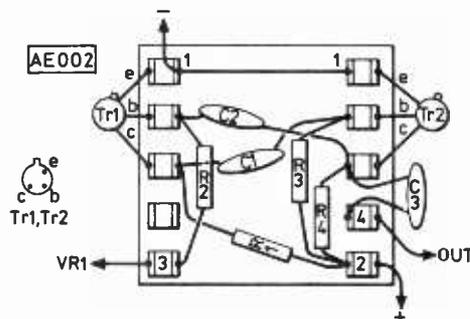


Fig. 2: Wiring the Tone Generator board.

The complete circuit

The full circuit (excluding the change-over switch and keyboard socket) is shown in Fig. 3. Each board has its own output control VR2, and VR2B, coupled to the common volume control VR3 by resistors R5 and R5B. VR2 and VR2B allow adjustment of the relative power of bass or treble.

The AF amplifier is available as a circuit board for the TBA800, having input, output, and battery connecting foils. Details of the amplifier are given later. It requires relatively few components and can provide a good audio output without heavy drain on the battery. A 16 ohm speaker can be used with some reduction in audio power. A jack breaks the speaker circuit, the audio signal then being available through tip and sleeve of the plug. Capacitor C4 is necessary to maintain stable operation. None of the component values in Fig. 3 was found to be critical.

It was not found necessary to screen the amplifier input or any other circuits. As all the potentiometers are mounted on wood, it is essential to connect the mounting bush and metal case of VR3 by wire to its negative tag. If a metal enclosure were used, this would not, of course, be necessary.

fillets to strengthen the whole. Allow for overlap where necessary, though the actual finished dimensions are not important.

The lower part of the case allows a simple music stand to be provided. This consists of two strips pivoted on brackets, so that they can be folded down

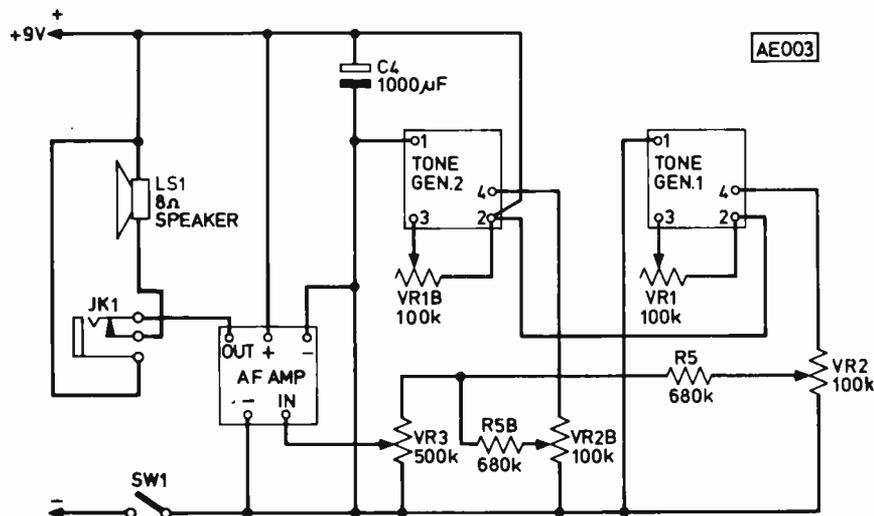


Fig. 3: Complete circuit diagram of the "Musico."


Case

The case (Fig. 4) has a low section for the pitch controls, and a higher part to accommodate the speaker and battery. It would be feasible to construct the equipment in a shallow, inverted box, if the speaker were separate or mounted flat. Assembly of the case is with panel pins and adhesive, with wooden

out of the way, or raised to support the music.

The battery fits in the higher part of the case, in a box glued in position, with a metal strip which can be moved aside to remove the battery.

Fig. 4: Constructional details of the "Musico" case.

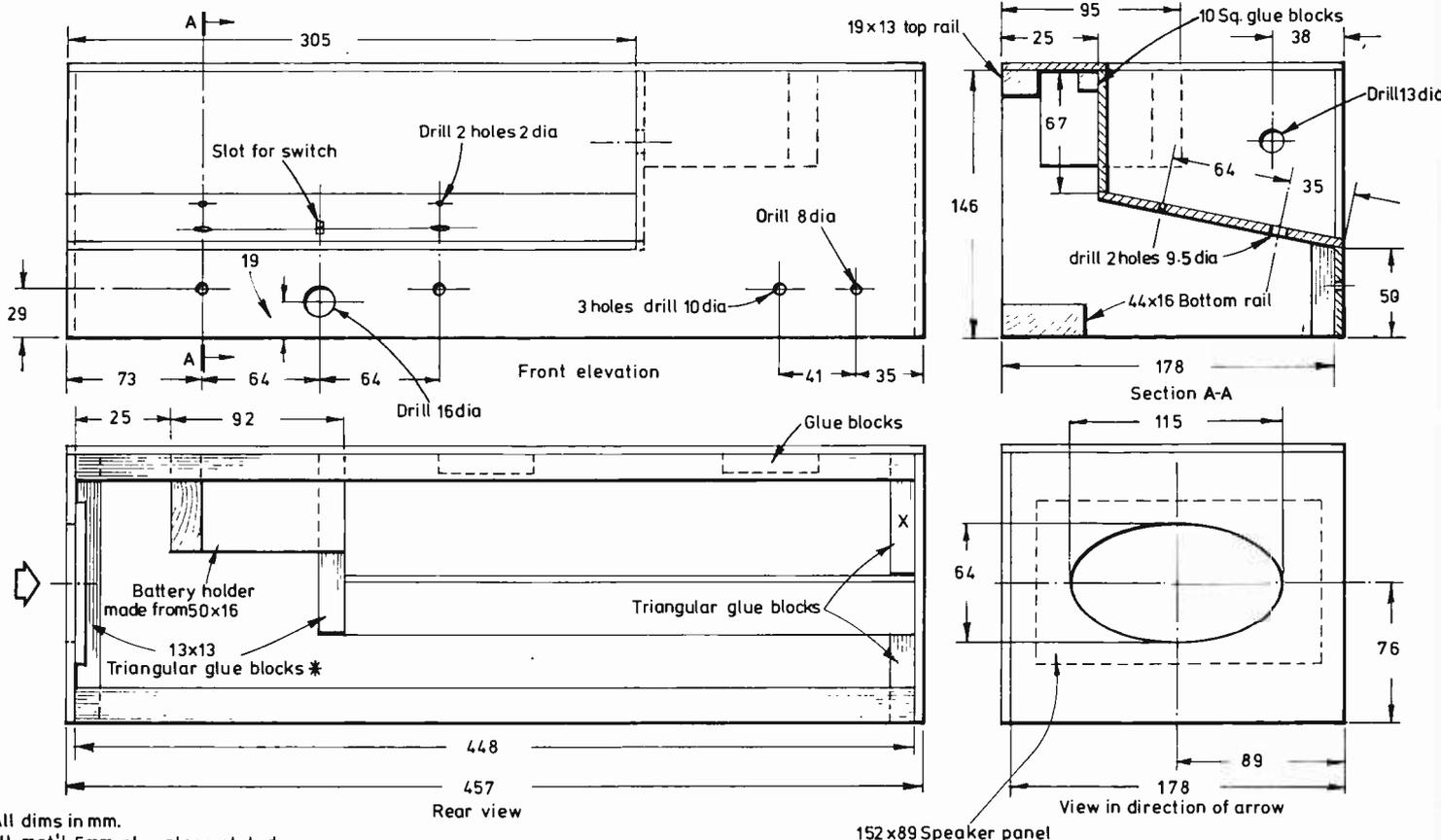

All dims in mm.

All mat'l 5mm ply unless stated.

* Triangular glue blocks attached to front panel, except X.

RW002

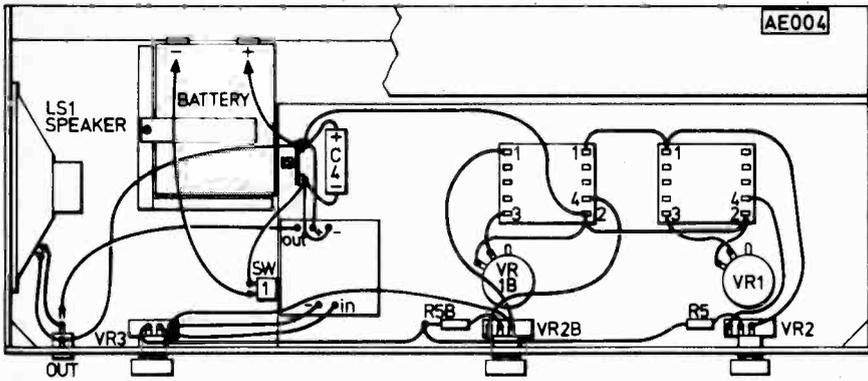


Fig. 5: Wiring diagram of the complete unit.

Underside wiring

The wiring is shown in Fig. 5. It is convenient to use red wire for positive and black for negative circuits. The boards are held clear of the wood by spare nuts or washers on the screws which hold them in place. A tag strip supports C4 and provides connecting points for positive and negative circuits. If these are wired as shown, loops which could cause instability will be avoided. VR3 could quite well have an on-off switch, if preferred.

Amplifier

For ease of building, it has been assumed that a ready-made printed circuit board, with IC, would be used, and a circuit for this item is shown in Fig. 6. It was found necessary to use quite a large decoupling capacitor (positive to negative) to avoid motor-boating and other troubles at some frequencies. If alternative audio amplifiers are used, they should have a fairly high input resistance and sufficient gain to avoid the need for a pre-amplifier.

The TBA800 can give a little over 1 watt with a 9V supply, and does not require a heat sink for this power. Higher outputs are possible with increased voltage, but a heat sink will then be needed.

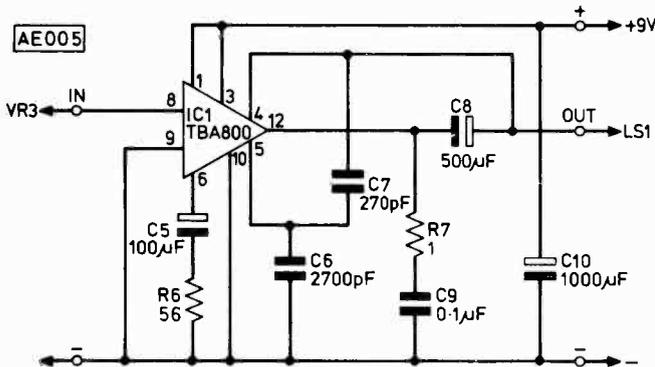


Fig. 6: Circuit diagram of the amplifier.

Tillers

The tillers were made by sawing a 6.3mm ($\frac{1}{4}$ in) brass coupler in two, thus obtaining collars which can be fitted to the potentiometer spindles. Each projecting arm was about 100mm (4in) long, with a small knob fitted at the end. They were made from Meccano rods, threaded 4BA at one end, with a collar the other end. Threading would not be needed with 4BA rods. This method of making the tillers is easy, but alternatives of wood, metal or plastic could be used.

Playing

Check that both oscillators work by adjusting VR2 and VR2B. Fit the tillers so that both notes are the same, with the knobs directly forward; a rise in pitch is obtained by moving the knobs to the right, and a fall in pitch to the left. It should be easy to find the positions which result in the notes being in unison

★ components

Tone Generator

Resistors

R1	1k Ω	R4	10k Ω
R2	10k Ω	R5	680k Ω
R3	10k Ω	All 5% $\frac{1}{4}$ W	
VR1	100k Ω lin	VR2	100k Ω log

Capacitors

C1, C2, C3 0.1 μ F 18V ceramic

Transistors

Tr1, Tr2 BC108

Miscellaneous

Tagboard 4-way

Note—All the above are duplicated for the second generator.

Amplifier, etc.

Resistors

R6	56 Ω	R7	1 Ω
VR3	500k Ω log		

Capacitors

C4	1000 μ F 10V elect.	C8	500 μ F 10V elect
C5	100 μ F 10V elect	C9	0.1 μ F
C6	2700pF	C10	1000 μ F 10V elect
C7	270pF		

Integrated Circuit

IC1 TBA800

Miscellaneous

LS1 5 x 3in elliptical, 8 Ω

SW1 SPST

JK1 Switched jack

Printed circuit board for TBA800 (obtainable from J. R. Hartley, 78b High Street, Bridgnorth, Salop.)

Knobs. Battery Clips. Materials for case and tillers (see text)

Keyboard

Resistors

VR4-VR29 100k Ω min. horizontal pre-sets (26 off)


Miscellaneous

Materials for case and keyboard

and octaves. The manipulation to best advantage needs some practice.

Warbling and similar odd background effects are readily produced, the general effect being similar to that heard from a musical saw. Vibrato effects are achieved by fluttering one or both tillers slightly with the fingers. There is separate volume control of rising or falling tones.

between VR1 and VR1B. In one position, this connects VR1 and VR1B as before; in the other position the keyboard resistors are connected instead. All the keys are connected together and return to point 2 on the oscillator boards. When any key is depressed, it touches a screw underneath it. Pre-set potentiometers VR4 to VR29 are divided into two sections, wired for left and right hands. A 3-way plug allows

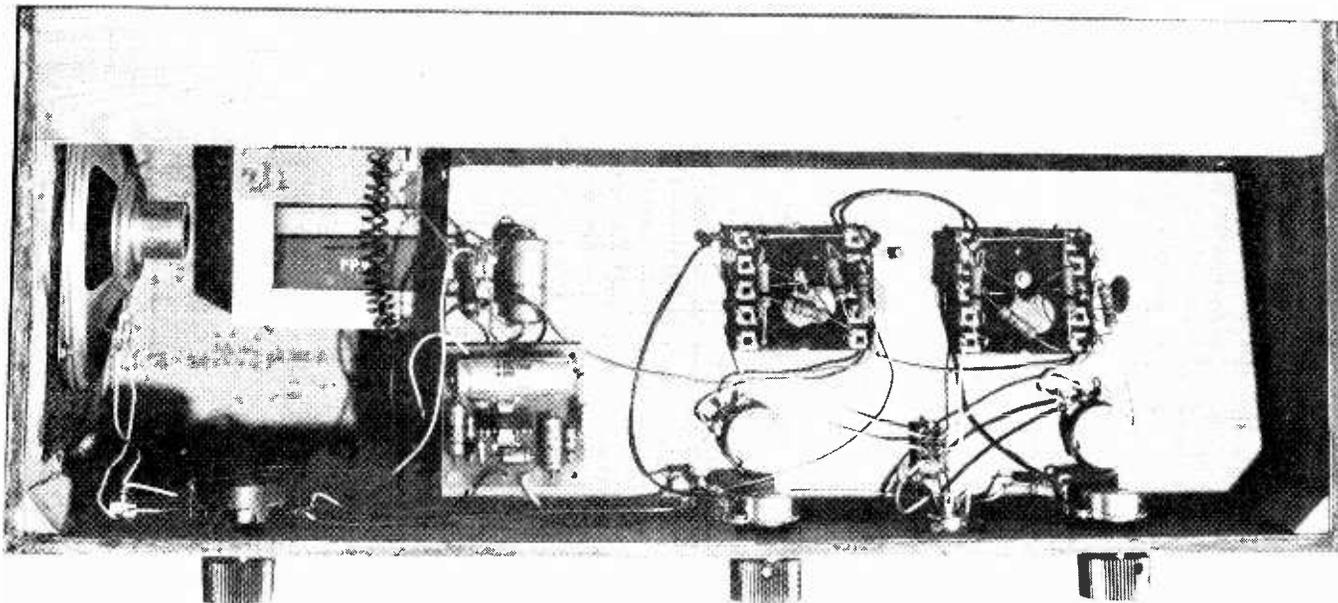

Plug-in Keyboard

It will be seen that if a pre-set resistor for each required frequency is substituted for VR1 and VR1B, the notes would be obtained by switching the appropriate resistance values into circuit. A simple means of doing this is to use the well-known type of stylus keyboard, where the circuit is completed by touching a metal point on a conductive area representing the note. The keyboard shown in Fig. 7 is not of this type, but has metal keys or switches which are pressed to complete the contact, as this is easier to manipulate rapidly.

A 2-pole 2-way slide switch is fitted on the board

the keyboard to be disconnected for carrying or when it is not needed.

It was decided to use Meccano strips for the keys, as these are of a convenient width and strength, and do not need drilling. Metal strips could of course be cut for this purpose. They are 114mm (4½in) long for the sharps and flats, and 140mm (5½in) long for the naturals. They could each have a wooden finger piece screwed on, but this was not done with the keyboard shown, and would have to be completed before fitting the keys. Finger contact with the metal has no effect on the pitch because all keys are joined electrically. The construction of the keyboard should be clear from Fig. 8.

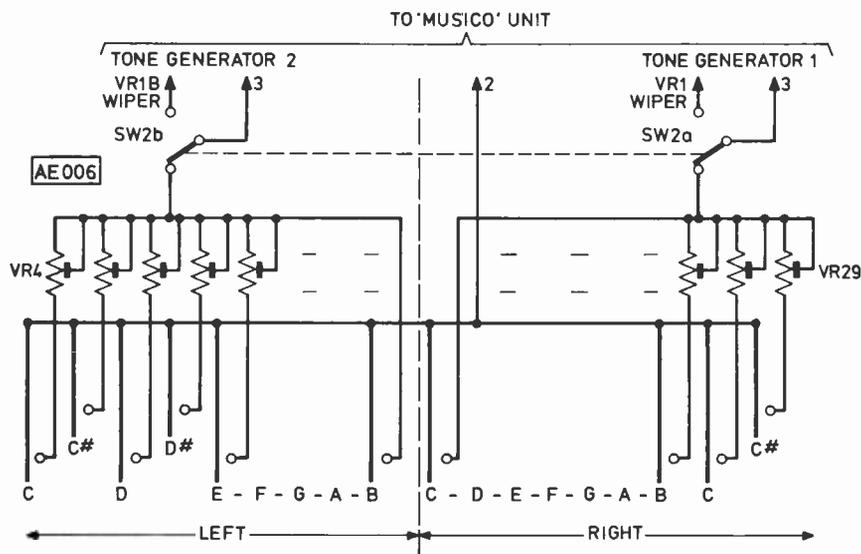


Fig. 7: Circuit diagram of the add-on keyboard.

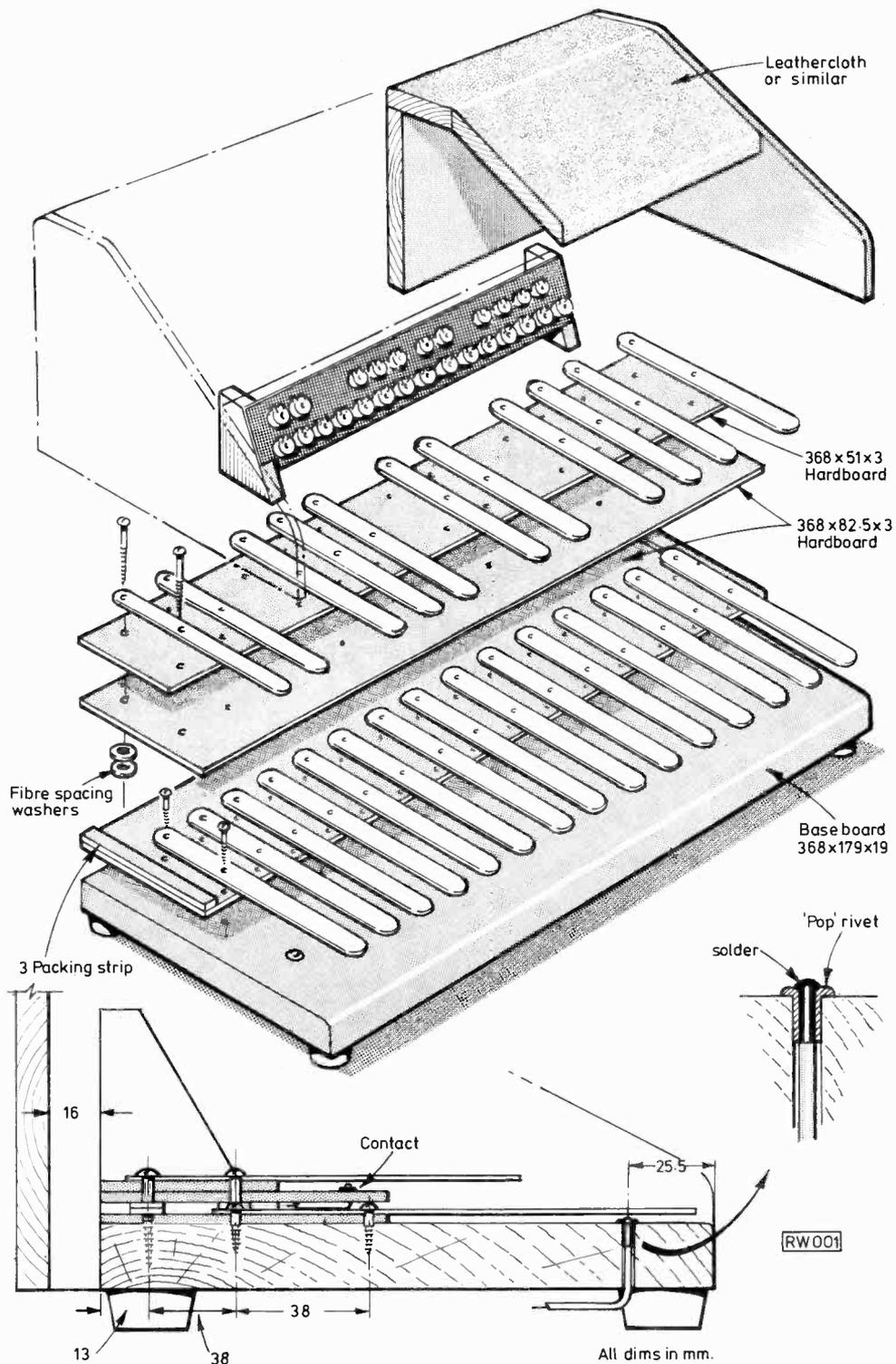



Fig. 8: An exploded view of the keyboard unit, showing constructional details and dimensions.

Pre-set Assembly

The pre-set potentiometers were fitted to a piece of 0.1in matrix perforated board 197 x 45mm (7³/₄ x 1³/₄in). The board is supported on two triangular pieces of wood, so that the pots are easily reached when soldering the leads. They are in two rows, the higher of these being set in pairs and threes to match

the sharp and flat keys, for ease of identification.

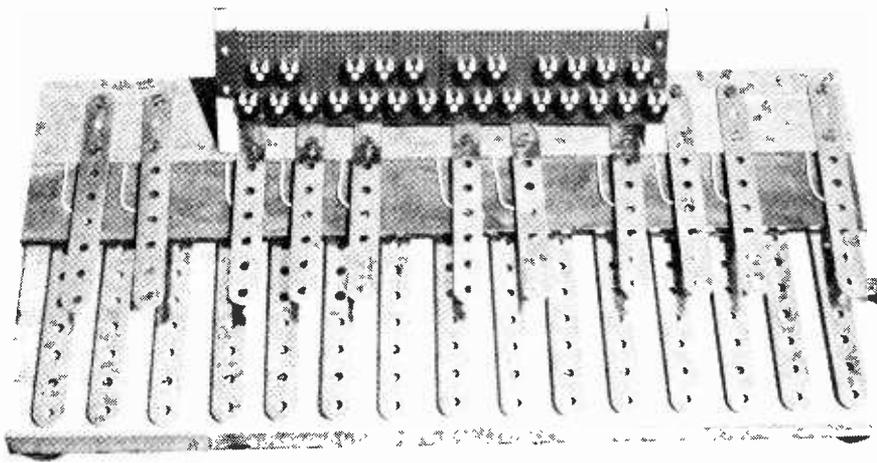All the potentiometers are wired into two groups (Fig. 7) for left and right hands. The wires from the keys are then brought up the back one by one, cut to length, and soldered to the correct potentiometer. A 3-core lead is prepared and used for left-hand, right-hand, and common key return circuits.



An internal view of the keyboard, showing the keys and the mounting board for the pre-set potentiometers.

The assembled keyboard unit.

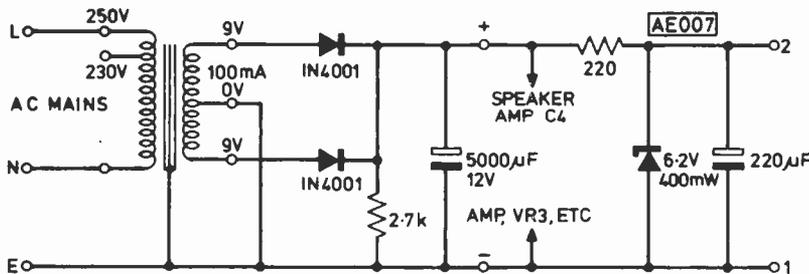
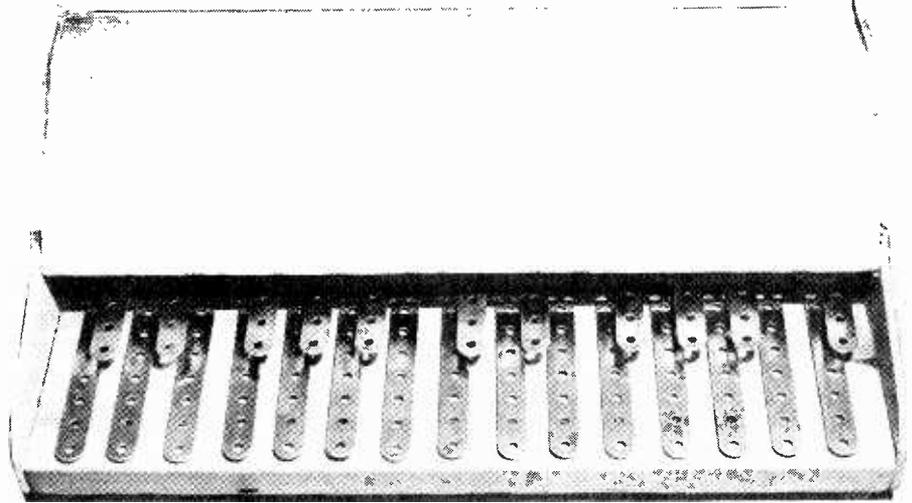


Fig. 9: Circuit diagram of a suitable mains power supply.

Tuning

The potentiometers should be connected so that the resistance in circuit increases, key by key, from right to left. Some rough adjustment can be given to the pots by clipping a meter to the board to measure resistance and depressing each key in turn. The resistance should increase note by note, and could be about 10k ohms for upper C, 25k for middle C, and 60k for lower C (exact values depend on other components). Such an adjustment will give some sort of progressive scale, with which to begin tuning.

A piano or other musical instrument should be available, so that each potentiometer can be adjusted to bring the note into tune. A good musician's ear is by no means necessary for this, as the adjustment is only to bring the pitch to that of a known note.

A tool with a fairly large handle, or fixed crossbar, permits quite critical adjustment. It would also be possible to use combinations of fixed and variable resistors for the notes, or pre-sets of lower values for the higher notes.

With the tillers only in use, no tuning is of course


required, frequency depending on the operator's ear. "Microtonal" music or similar sound effects are also then possible.

Mains Power Pack

Frequency does not depend too critically on battery voltage, but changes in tone from this source can be largely avoided by adding a Zener diode to stabilise the supply to the oscillators. A simple mains pack can be added, either assembled in a box to replace the battery, or fixed in the space available in the instrument.

The mains power pack circuit and connections for the diode are shown in Fig. 9. A 3-core mains lead should be used to provide earthing, and the plug fitted with a 2A fuse. In the interests of safety, mains connections should be made on insulated blocks, or should be enclosed so that they cannot be touched.

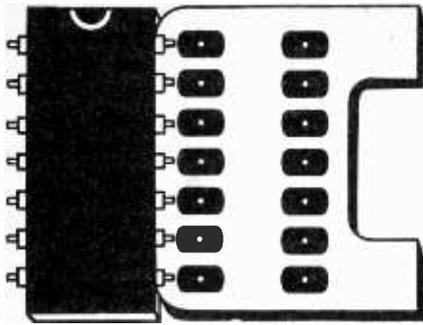The series resistor, diode and capacitor are supported by the adjacent tag board. A battery may still be used with the diode added.



OF THE MONTH 66

Brian DANCE M.Sc

THOMSON-CSF PROXIMITY DETECTOR

Proximity detectors are circuits which detect the presence of a piece of metal when it is brought close to a certain part of the circuit—often a coil. When the metal is brought into close proximity with the coil, the output voltage from the circuit changes. Proximity detectors may be used to measure the rate of rotation of a shaft, the rate of pulsing of the output being proportional to the speed of rotation of the shaft. They may, for example, be employed in a car rev counter, in which case a piece of metal connected to the cam shaft produces a pulse each time it passes the coil of the proximity detector. Alternatively, a proximity detector fitted to the propeller shaft or to one of the wheels of a vehicle can be used as an electronic speedometer. Another application in motor vehicles is the generation of the timing pulses for an electronic ignition system.

However, the use of proximity detectors is by no means confined to motor vehicle applications. They are very useful on industrial production lines for counting objects which may vary in size from a small piece of metal to a road vehicle. Indeed, they can be used in almost any application in which a piece of metal moves or in which the movement of any object can be converted into the movement of a small piece of metal.

The ESM 1601

The ESM 1601 is a new monolithic device manufactured by Thomson-CSF which can be connected to a small tuned circuit. The coil of this circuit is wound on a special ferrite cup core and when a piece of metal is brought up to the open face of this cup core, a large change in the output voltage occurs. The metal need not actually touch the cup core; the circuit operates when the metal is a few mm from the face of the core.

The ESM 1601 is encapsulated in a small TO72 metal transistor type package, the leadout of which is shown. The device requires only a very simple circuit as in Fig. 1. Although the IC will not be damaged if the power supply is accidentally connected with the wrong polarity, it is important to note that the use of the load resistor R1 is essential and that the device will normally be destroyed if the power supply is directly applied to the package.

Operation

The natural resonant frequency of the tuned circuit L1/C1 should be within the range 500kHz to 6MHz; it is, of course, equal to $\frac{1}{2\pi\sqrt{L_1C_1}}$. The values shown have been chosen to provide a natural resonant frequency of about 3.9MHz. The ferrite cup core used for L1 is shown in Fig. 2, but more details about it will be given shortly.


When no metal is near the coil, the circuit oscillates at the frequency of the tuned circuit. The output voltage is "low" when oscillation is taking place, the output being typically +1.55V at 25°C. The minimum output voltage during oscillation is 1.2V at 125°C and the maximum 2V at -40°C.

If a piece of metal is moved close to the face of the ferrite cup core (as shown in Fig. 2), Foucault or eddy currents flow in the metal. Power is absorbed from the tuned circuit since the currents generate a small amount of heat in the metal through which they flow. When the amount of power absorbed causes the amplitude of the oscillation to fall below a certain critical level, the output voltage rises suddenly to a value of between +5.7V and +6.9V. The rise and fall times of the output voltage are typically 8μs and 5μs with maximum values of 25μs and 15μs respectively. The circuit returns to its former state with the output voltage "low" when the metal is removed from the coil face.

Cup core and coil

The miniature ferrite cup core recommended for use with the ESM 1601 is only 9mm in diameter and 3mm in depth; it is manufactured by Thomson-CSF under the type number 9 x 5H32 and has a small hole at its centre for mounting purposes. The manufacturers recommend that the coil should consist of 50 turns of stranded (*Litzendraht*) wire comprising 5 strands which each have a diameter of 0.06mm. Unfortunately the writer did not have any of this wire available and it is unlikely that many readers will be able to obtain it easily.

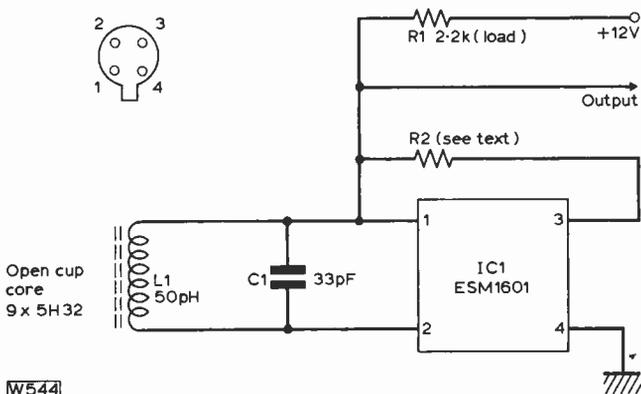However, it was found easy to make a coil using 50 turns of single silk covered enamelled copper wire of diameter 0.15mm (38 SWG). A small resistor was



W544

Fig. 1: Circuit of the ESM 1601 Proximity Detector.

selected which had a body diameter approximately the same as the internal diameter of the coil to be wound. About 20 turns of the wire were wound on the resistor, the width of the coil being suitable for fitting into the cup core. The 20 turns were fixed in position by applying a solution of polystyrene in amyl acetate before another 10 turns were added. These were fixed with the same cement before another 10 turns were added followed by further cement and the final 10 turns to make the total of 50 turns. Before the polystyrene cement had completely set, the coil was gently pushed off the resistor into the recommended ferrite cup core. A reasonably neat coil can be made in this way.

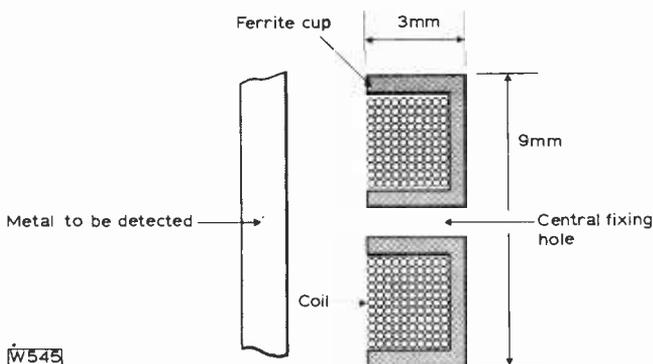


Fig. 2: Rough sketch of the ferrite cup core.

Value of R2

The value of the resistor R2 controls the amount of feedback; if R2 is small the circuit is more likely to oscillate than if it is large. The data sheet suggests that R2 can have a value of 47 kilohms when the recommended stranded wire is used for the coil L1. However, it was found that no oscillation occurred with the single wire coil when R2 had this value, but the circuit worked well when the value of R2 was reduced to about 8.2 kilohms. The additional losses in the coil using single wire necessitate the use of more feedback to maintain oscillation and this extra feedback is obtained by reducing the value of R2.

Load resistor

The value of the load resistor must limit the current to the device to the maximum permissible value of 20mA, but must not be so high that the current is less than 0.6mA. In addition, the maximum power dissipation (325mW at 25°C) must not be exceeded. The value shown is suitable for almost all applications, but is not at all critical. The minimum supply voltage is 8V.

In many applications, the output voltage may be used to deflect a small meter, but it can also be used to feed complex logic circuits. The maximum switching speed is 10kHz.

The ESM 1601 is available at 98p (including VAT) plus 20p for packing and postage from Phoenix Electronics Ltd., 46 Osborne Rd., Southsea, Hants PO5 3LT. Phoenix also supply the recommended cup core 9 x 5H32 price 75p including VAT.

READERS PCB SERVICE

To:- READERS PCB SERVICES LTD,
PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es.....

Issue	Project	Ref	Price P/P	
Dec 75	Sound-To-Light Display	DN0798	1.15+12	<input type="checkbox"/>
Dec 75	Disco System, Amp. (2 req'd) each	AM0421	4.40+22	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	3.50+22	<input type="checkbox"/>
Mar 76	CMOS Crystal Callibrator	AM0438	1.19+12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33+15	<input type="checkbox"/>
June 76	Dig. Freq. Meter (set of 5) A015 and 4x A004		3.17+15	<input type="checkbox"/>
July 76	Disco Preamplifier	A003	0.65+12	<input type="checkbox"/>
Aug 76	Cassette Player Power Supply	A001	0.65+12	<input type="checkbox"/>
Oct 76	Digital Car Clock (set)	A011/012/013	2.58+12	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0.80+12	<input type="checkbox"/>
Oct 76	Video-Writer (set)	D002/3/4/6 A007	21.44+50	<input type="checkbox"/>
Oct 76	Hazard Flasher	D005	0.76+12	<input type="checkbox"/>
Nov 76	Low Level Battery Indicator	A016	0.40+12	<input type="checkbox"/>
Nov 76	Electronic Thermostat	A017	1.30+12	<input type="checkbox"/>
Nov 76	Cirtest Probe	A018	0.48+12	<input type="checkbox"/>
Nov 76	Burglar Alarm	A019	0.50+12	<input type="checkbox"/>
Dec 76	Chromachase	A021	5.70+22	<input type="checkbox"/>
Jan 77	Oscilloscope Callibrator	A023	1.25+12	<input type="checkbox"/>
Jan 77	Icelert	A020	1.45+12	<input type="checkbox"/>
Feb 77	Transistor Checker	A026	1.18+12	<input type="checkbox"/>
Apr 77	Tug 'o' War (set)	A029/030	2.88+12	<input type="checkbox"/>
Apr 77	Gas/Smoke Sensor Alarm	A028	0.65+12	<input type="checkbox"/>
May 77	2-Way Intercom	D019	1.28+12	<input type="checkbox"/>
May 77	Protected Battery Charger	A027	2.38+12	<input type="checkbox"/>
May 77	Seekit Metal Locator	A031	3.38+12	<input type="checkbox"/>
June 77	Reverberation Amplifier	A032	2.38+12	<input type="checkbox"/>
June 77	Versatile AF Generator	A033	2.38+12	<input type="checkbox"/>
June 77	Tele-Games	D029	3.22+18	<input type="checkbox"/>
July 77	20W IC Amplifier	A034	1.38+12	<input type="checkbox"/>
July 77	Radio 2 Tuner	A035	1.68+12	<input type="checkbox"/>
July 77	Digital Clock Timer	A036	3.28+12	<input type="checkbox"/>
Aug 77	Shoot (Telegames)	D035	1.55+15	<input type="checkbox"/>
Aug 77	Atomic Time Receiver	D036	2.65+15	<input type="checkbox"/>
Aug 77	Morse Code Tutor Cards (SRBP)	A037	4.75+15	<input type="checkbox"/>
Sept 77	Jubilee Electronic Organ	A038	19.00+75	<input type="checkbox"/>
Sept 77	Electronic Car Voltage Regulator	D037	1.25+12	<input type="checkbox"/>
Oct 77	Audio Level Indicator	D039	0.98+12	<input type="checkbox"/>
Oct 77	Sine-Square Wave Generator	D040	2.35+15	<input type="checkbox"/>
Nov 77	Laboratory Power Supply	A039	3.50+12	<input type="checkbox"/>
Jan 78	Proportional Power Controller	DN9JM	0.78+12	<input type="checkbox"/>

Post and packing is for one board or set of boards. Prices include VAT. Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

I enclose Postal Order/Cheque ACCESS welcome.

No..... Send card number only.

for £..... made payable to READERS PCB SERVICES LTD

NAME

ADDRESS

..... Post Code.....

Any correspondence concerning this service must be addressed to READERS PCB SERVICES and not to the Editorial offices.

THE 5 METRE STORY part 1

Ron HAM BRS 15744

The object of this article is to pay tribute to the many radio enthusiasts, both licensed amateurs and SWLs, who pioneered the five metre band from 1930 until September 1 1939 when the amateur radio licences in the UK were withdrawn. Many of those 5m operators are still active today, and will, no doubt, add their personal "tit bits" to this story through the letters page of this journal.

To prepare this article, the author has gathered information from the *T & R Bulletin* (then, monthly journal of the RSGB), and other contemporary documents, and by personal contact with people who were "there at the time".

"Ultra High Frequency"

When the words "Ultra High Frequency" (UHF) are used today we automatically think of radio wavelengths shorter than one metre, but, in those pre-1940 days, UHF meant the 56 and 112Mc/s bands. In fact, Chapter 12 of the first edition of the *Amateur Radio Handbook*, published by the RSGB in 1939, is entitled *Ultra High Frequencies* and is devoted to the 5 and 2 $\frac{1}{2}$ m bands. In the circumstances we'll continue to use 'Mc/s'!

To really appreciate this story the reader must clear his mind of today's technology and accept the fact that the 5m band, 46 years ago, was an unexplored part of the radio frequency spectrum. Try to think as those early pioneers did. Is it really possible to work DX on such a band? Could a circuit oscillate around 56 million times per second? What about propagation, and what effect would the earth's atmosphere have on such a high frequency radio signal?

Try Anything

The past seventy years have shown us that as radio advanced from using wavelengths of 3000 metres to micro-wavelengths of three centimetres and less, radio amateurs have been prominent among the leading experimenters. Anything that was thought to be impossible, you can be sure that somewhere an individual radio enthusiast had tried it out, had a little success, and reported his progress to others.

Soon, a group of them would be trying to master the problem, with the technical press just itching to report their activities through the columns of their magazines.

Apart from the experimental aspect, 56Mc/s operation had certain advantages over the HF bands, mainly because it was very suitable for short distance working (across town), thus avoiding the congestion of the lower frequencies, and also because the aerials were smaller and required much less space. Converts to 'five' were delighted to find a band almost free of atmospherics, except for local thunder storms, although they soon found out that interference came from the ignition systems of the ever growing number of motor vehicles, and it was unfortunate for a 5m enthusiast who lived near a busy cross-road! We often forget that in the early thirties, the aeroplane, motor car, photography etc were growing side by side with radio communication, and each had its own band of enthusiasts.

When the author asked one 5m experimenter if he had any pictures of his early activity, he replied, "We could not afford photography as well as radio in those days". This remark was not surprising when one refers to the adverts in those early radio magazines e.g. in 1930:—a 0-100 mA meter £2.2.6, a quartz crystal £1, an output transformer £1.2.6, a tuning capacitor 15s, valves around 30s, a 10k Ω wire-wound pot 7s 6d and 'grid leaks' at more than 2s each!

Transmitting Licences

During his researches, the author was puzzled by a paragraph in the *T & R Bulletin* (p 411) March 1937 headed 'Special 56Mc/s Permits', and it read as follows:— "Members holding 56Mc/s permits are reminded that they may apply for permission to operate portable 56Mc/s stations from Good Friday until the end of September without additional fee. An assurance however must be given that frequency stabilised apparatus will be used. Applications must reach Headquarters not later than March 20."

Did this really mean that one could only operate portable in the summer months? Surely the authorities were aware of the fact that radio enthusiasts wanted to operate at any time and almost

anywhere if need be! The author telephoned Miss Constance Hall G8LY who, as well as being a 5m pioneer herself, is a mine of information on amateur radio matters. Fortunately, Constance had preserved her pre-war licence documents and instantly made them available for this article. On October 5 1937 Constance received a letter from the GPO authorising her to use a transmitter in the 5m band.

Like many of the other 5m enthusiasts Constance wanted to operate from a portable location, so, via the RSGB, she duly applied for permission to do so, but oh!, what restrictions! In a letter dated 15 April 1939, Constance was authorised to install and use an experimental wireless station, in the open air, on Saturdays and Sundays until the end of September 1939, but limited to a 10 mile radius of her home.

Only a Few

According to L. A. Moxon G6XN, writing in November 1930, there were less than a dozen active amateurs working on 5Mc/s in this country and very few in other parts of the world. One of these amateurs was G2DT who, in 1929, was the first 5m station in the UK to receive signals from a distance of over 100 miles.

Many SWLs played an important role in the development of the 5m band and one of these was Ted Williams (later G2XC) who, in 1932 joined the RSGB as a listening member. He was invited by the Society's Town Representative, Leonard Newnham G6NZ, to visit him. Len was firing everyone with enthusiasm for the 5m band and he transmitted every

Sunday morning using a self-excited rig, while the listening stations all had super-regenerative portable receivers.

Ted built himself such a receiver and took it along to Len's station in Southsea to make sure that it was working "in the band". He returned to his own location, perched in the back seat of a friend's car, with earphones on, and using an odd length of wire as an aerial. He heard G6NZ's transmissions for a few hundred yards and then nothing until the car reached the top of Portsdown Hill (near Portsmouth) about 4½ miles from G6NZ, and then nothing again when the car went down the other side of the hill.

Line of Sight

A few Sundays later Ted drove along the length of the ridge of the hill so that he could plot G6NZ's signal strength at various points. No one believed then that reception over anything other than "line-of-sight" was possible. Ted's outing was typical of the contribution made by the listeners, many of whom held transmitting licences. The important thing at this point was that the amateur concerned had built a working "UHF" receiver and was prepared to go almost anywhere to use it.

At the Crystal Palace

In May 1933 G6HP, G6NF and G6QB humped a variety of radio equipment to the top of the North Tower of Crystal Palace for the famous 56Mc/s tests. Their transmitter used two B12's in the usual push-pull oscillator circuit while the modulator used two 211-E's in parallel. The microphone was fed directly into the grid through a high-ratio modulation transformer with no further amplification. Their transmitter power was about 10 watts, and the aerial a 2½m length of copper petrol piping hanging from a stand-off insulator on the end of a pole which poked out, fishing-rod fashion, from the gallery of the tower.

The two receivers, both super-regens, were fed from independent LT and HT supplies so that they could be used together from opposite sides of the tower. This proved to be very useful and some interesting results were obtained. All the gear was tested out on the Saturday night and then, early next morning, the three operators re-climbed the 400 stairs and began working soon after 0900. Their first QSO was with G5VY of Tottenham, and then they called various receiving stations, some mobile and some fixed. G5IS heard them well on Inkpen Beacon but he was caught in a local thunderstorm and was unable to effect a two-way QSO.

Their signals were also received 130 miles away by Douglas Walters G5CV who was flying in an aircraft at 10 000ft "somewhere north of the Wash". Doug's report of R9+ was on top of the racket from a totally unsilenced and unscreened aero-engine. G5CV was a reporter for the *Daily Herald* newspaper and the aeroplane was chartered by the Editor for the occasion, another example of the enthusiasm toward wireless experiments in those days!

Kite Aerial

Their most amazing report came from G6PL at Hollin Bank, Yorks. G2NH heard them while he was using a kite aerial at South Harting, Sussex, during

n. 4.10.37.



Tel.: NATIONAL 6821
Extension No. 366

Your Reference
P.O. Reference WZ/A.3455

By GEORGE LEE,
L. B. S. C. W. O. B. E. M. C. M. I. E. E.
Inspector-Chief.

ENGINEER-IN-CHIEF'S OFFICE (Radio Branch)
GENERAL POST OFFICE,
ARMOUR HOUSE,
LONDON, E.C.1.

5 October, 1937.

Miss C. R. Hall,
North Waltham Rectory,
Winchester,
Hants.

Dear Madam,

Experiments in Wireless Telephony.

With reference to your letter of the 19th September, you are hereby authorised to send messages on waves within the frequencies and by the systems specified hereunder:-

Frequencies (in Kilocycles per second)	Approximate equivalent wavelengths (in metres)	Systems
28010 to 29990	10.71 to 10.00	(Continuous wave, modulated continuous wave and telephony)
56020 to 59980	5.36 to 5.00	(Continuous wave, modulated continuous wave and telephony)

at the experimental wireless station G8LY and Condition 2 of the licence dated 4th June 1937, is hereby extended accordingly.

Yours faithfully,



for Engineer-in-Chief.



A facsimile of the GPO letter authorising Miss Constance Hall to operate a transmitter in the 5 metre band.

the afternoon, but in the morning, on Hindhead in Surrey, he said that their signal was audible "160ft away from a pair of Browns 'A' phones"! The reports rolled in from G2KB Dunstable, G6GZ Farnborough, G6LK Cranleigh, G5JZ Nutley, Kent, G2GG Newbury, G6OA Westcliff, BRS1011 Leigh-on-Sea, G6NA Guildford and BRS1117 at Reigate, Surrey.



Douglas Walters G5CV operating the 5metre receiver in the chartered Daily Herald aircraft.

This historic photograph is the property of the RSGB, and is reproduced by their kind permission.

NFD

During the 1938 National Field Day, 2CIL with his brother and 2DCT, installed their receiving equipment in a beacon tower near Horsham, Sussex. Their aerial was a Yagi made up on broomsticks, fed by open wire feeder. It could be used horizontally or vertically so that transmitter polarisation could be observed from the incoming signal. On the Saturday they were listening, by arrangement, to the signals from G8LY who had a sked with GW6AA/P on Snowdon. An hour or so later there was a thunderstorm overhead and the tower lightning conductor took a charge! The receiver and the listeners were installed in a room below the lead roof; the set crackled but stood the shock. When the hail had finished the crew had to venture on to the roof to loosen the guy lines which were bending the broomsticks like a bow! However they received an award from the RSGB for a remarkable log which contained more than 30 entries and an extensive report of the event.

DX!

During the summer of 1939 G5CM was visiting 2CIL and tuned George's receiver to about 56Mc/s, acting on information supplied by Barbara Dunn G6YL, and heard MCW signals from CS3VA situated on an airfield in Spain. It seems that this signal was acting like one of our present day beacons because it was as a regular automatic signal sending "VVV de CS3VA". Of course by 1939 a large number of amateurs in many countries were both interested and active on the 5m band.

5 METRES	
SCHOOL HOUSE, ALFOLD, SURREY	
WORKED 57 COUNTRIES.	TO RADIO <input type="checkbox"/> 5band
R.S.G.B.	W.B.E. (C4)
W.A.C.	2CIL
This confirms our QSO of	ENGLAND
29-6-1938	G5CM
at 1735 BST	XMITTER
on 56 Mc bd	59 3-valve - 4V6
Ux sigs were	Antenna: 50 Poles
RST 3.1.1	Input 10 Watts
or	Aerial 60 V.F. Ant.
W.A.A. R.M.M.	QRG 5.611.2 KCS
Remarks	Receiver 2 tube
<i>many thanks for report George checks perfectly.</i>	
TNX	Op. T. H. STREETER.
<small>QSL Direct via RSGB</small>	

A QSL Card from G5CM acknowledging the 5m report from 2CIL.

They took to the Air

On Sunday May 21 1933, Douglas Walters G5CV took off in a Puss Moth aircraft with two completely shielded 3-valve super-regen 56Mc/s receivers on board. One was his own and the other belonged to George Jessop G6JP (Present General Manager and past President of RSGB). Immediately the plane left the ground, Doug was getting a tremendous signal from G6JP and very soon, altitude now 3000ft, a colossal carrier was heard from G6QB operating from the North Tower at Crystal Palace, mentioned earlier. As the plane flew over London about a dozen 56Mc/s signals were heard including G5MG, G6CJ, G6UH, G2JU and G6VA. When flying 60 miles north-east of London, Doug and his colleagues in the plane heard G6QB at terrific strength and later, at 8000ft, they heard both sides of a QSO between G6CJ and G6QB. Owing to the shortage of fuel the plane turned back toward London when at 10 000ft and at 130 miles out they were still getting a strong signal from G6QB at Crystal Palace. Douglas was convinced that had they been able to carry on in a more northerly direction G6QB's signals would have been heard at 250 miles or more.

TO BE CONTINUED

MK14—the only low-cost keyboard-addressable microprocessor!



The new Science of Cambridge MK14 Standard Microprocessor kit

Just
£39.95
(+ £3.20 VAT, and p&p)

The MK14 National Semiconductor Scamp-based Microprocessor Kit gives you the power and performance of a professional keyboard-addressable unit—for less than half the normal price! For less than £44.00 you can have your own microprocessor. One with a specification that makes it perfect for the engineer who needs to keep up to date with digital systems, or for use in school science departments. It's ideal for hobbyists and amateur electronics enthusiasts, too.

But the MK14 isn't just a training aid. It's been designed for practical performance, so you can use it as a working component of, even the heart of, larger electronic systems and equipment.

MK14 Specification

- * Hexadecimal keyboard
- * 8-digit LED display
- * 512 x 8 Prom, containing monitor program and interface instructions
- * 256 bytes of RAM
- * 4MHz crystal
- * 5V Stabiliser
- * Single 6V power supply
- * Space available for extra RAM and RAM I/O

Free Manual

Every MK14 Microprocessor kit includes a free Operation Manual. It contains operational instructions and examples for training applications, and numerous programs including math routines, timing, general purpose sequencing, games, etc.

Designed for fast, easy assembly

Each 31-piece kit includes everything you need to make a full-scale working microprocessor, from 14 chips, a 4-part keyboard, display interface components, to PCB, switch and fixings.

The MK14 can be assembled by anyone with a fine-tip soldering iron and a few hours' spare time, using the step-by-step illustrated instructions provided.

Tomorrow's technology—today!

"It is not unreasonable to assume that within the next five years...there will be hardly any companies engaged in electronics that are not using microprocessors in one area or another."

Phil Pittman, Wireless World, Nov. 1977

The low-cost computing power of the microprocessor is already being used to replace other forms of digital, analogue, electro-mechanical, even purely mechanical forms of control systems.

The Science of Cambridge MK14 Standard Microprocessor Kit allows you to learn more about this exciting and rapidly advancing area of technology. It allows you to use your own microprocessor in practical applications of your own design. And it allows you to do it at a fraction of the price you'd have to pay elsewhere.

Getting your MK14 Kit is easy. Just fill in the coupon below, and post it to us today, with a cheque or PO made payable to Science of Cambridge. And, of course, it comes to you with a comprehensive guarantee. If for any reason, you're not completely satisfied with your MK14, return it to us within 14 days for a full cash refund.

Science of Cambridge Ltd,
6 Kings Parade,
Cambridge,
Cambs., CB2 1SN.
Telephone: Cambridge (0223) 311488

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN. pw

Please send me an MK14 Standard Microprocessor Kit. I enclose cheque/money order/PO for £43.55 (£39.95 + 8% VAT and 40p p&p).

Name _____

Address (please print) _____

Allow 21 days for delivery.

Science of Cambridge

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30kHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200/250V. PRICE £15.00. P. & P. £1.20.

HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram., etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1-5mv into 47k. Input 2-5mv into 47k. (suitable for use with mic. or guitar etc.). Input 3 100mv into 1 meg. suitable for gram. tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240v. Size approx. 12 1/2" w. \times 5" h. \times 7 1/4" d. Special introductory Price £28.00 + £2.50 carr. & pkg. Mullard LP1159 RF-IF Module 470 kHz £2.25 + P. & P. 20p. Full spec. and connection details supplied. Pye VHF/FM Tuner Head covering 88-108 MHz, 10.7 MHz I.F. output, 7.8 Volt earth. Supplied pre-aligned, with full circuit diagram with precision-ganged FM gang and 323Pf + 323Pf A.M. Tuning gang only £3.15 + P. & P. 35p.

STEREO DECODER

SIZE 2" \times 3" \times 4" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p. P. & P. Stereo beacon light if required 40p extra.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp. Stereo Beacon Lamp indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w. \times 4" h. \times 9 1/2" d approx. **LIMITED NUMBER ONLY at £28.00 + £1.50 P. & P.** Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" \times 2 1/2" \times 1". Supplied complete with chrome finished switch buttons. 2 for £1.80 + 20p P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. ONLY £13.50 P. & P. £1.40. Also available ready built and tested £18.00 P. & P. £1.40.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" \times 14 1/2" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.40 each + p. & p. (one 90p, two £1.10). Now available in either 8" round version or 4 1/2" \times 8 1/2" rectangular. 10 watts RMS 60Hz-20KHz £5.25 + P. & P. (one 65p, two 75p).

SPECIAL OFFER. 6 1/2" long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for Hi Fi. £3.95 + 75p P. & P.

2" PLASTIC CONE HF TWEETER 4 ohm, £3.50 per matched pair + 50p P. & P.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3db 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω ; Full power bandwidth; \pm 3db 12-15,000 Hz. Bass boost approx. to \pm 12db. Treble cut approx. to \pm 16db. Negative feedback 18db over main amp. Power requirements 35v. at 1.0 amp.

Overall Size 12" w. \times 8" d. \times 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £13.50 P. & P. 80p

(Magnetic input components 33p extra)

POWER PACK KIT £5.50 P. & P. 95p

CABINET £5.50 P. & P. 95p

SPECIAL OFFER—only £23.75 if all 3 items ordered at one time plus £1.25 p. & p.

Full after sales service

Also avail. ready built and tested £31.25. P. & P. £1.50.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" \times 2 1/2" \times 1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £9.00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at £1.50 + 40p P. & P. if required. Full connection details supplied.

HA34 3 Valve Audio Amp. 4 1/2" w. output ready built and tested £8.50 + £1.40 P. & P. Also HSL 'FOUR' amplifier kit. £8.00 + £1.40 P. & P.

All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSON SURPLUS CO. LTD.


(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19. Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

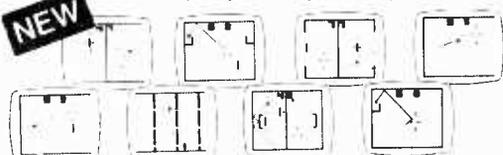Impress the neighbours with a game they haven't seen yet and proudly tell them you made it yourself



8 GAME T.V. PROJECT

BASED ON AY-3-8600

- ★ Basket-ball ★ Grid-Ball ★ Hockey ★ Tennis ★ Squash ★ Football
- + Two + One-Player Games ★ Horizontal and Vertical Bat Coverage
- ★ Automatic Ball Speed-Up ★ Players Colour Coded
- ★ Three Tone Sound-Effects ★ Sound from T.V.
- ★ Ball Colour Coded to indicate turn in Squash-Game
- ★ All Components supplied guaranteed including sound and vision modulator C.H. 36 UHF.
- ★ Power requirement 9v battery ★ Just add controls and case.
- Basic AY-3-8600 Paddle II Kit B + W only £15.00
- Colour only £20.90


JOY STICK CONTROLS

DESIGNED FOR T.V. GAMES
(AY-3-8550-AY-3-8600) Subminiature Size

UNBEATABLE LOW PRICE Two off £3.50

POPULAR AY-3-8500 PADDLE 1

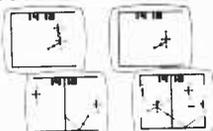- ★ Three Tone Sound Effects
- ★ All components supplied guaranteed just add controls, speaker and case
- ★ UHF varicap modulator (B+W)
- ★ Power requirement—9v battery
- ★ Stock clearance price down
- Black + White £10.50 £9.90
- Mini-Pack P.C.B. + chip B + W £8.90
- Colour CH36 £16.50 £15.90
- Colour £7.90



All Projects supplied with easy to follow assembly instructions. All prices include V.A.T. + Postage. Orders under £10.00 — Add 20p p. & p. Make all Cheques or Postal Orders payable to

TELECRAFT

Retail Shop and Demonstrations — 14 Station Road, New Barnet, Herts.
For further Details and Technical Help — Phone 01-446 7033
(French and German spoken) Quantity discount negotiable.
For extra speed phone your order on Barclay-or-Access Cards

SWL'S—YOU OWE YOUR RX A GOOD ANTENNA!

The World-famous JOYSTICK VFA (Variable Frequency Antenna) SYSTEMS continue to prove their worth in many amateur stations world-wide and in Government communication. Tunes continuously 0.5/30.00 MHz. and can be installed in any location. Comes in easily assembled form, carriage paid, 12 1/2% VAT included. Glowing testimonials from many users on our files.

SYSTEM 'A' £36.00
SYSTEM 'J' (improved 'Q') £42.60

PARTRIDGE SUPER PACKAGES

Complete Radio Stations for any Location
All Packages feature the World Record Joystick Aerial (System 'A') with 8' feeder, all necessary cables, matching communication headphones. Delivered Securior our risk. ASSEMBLED IN SECONDS! BIG CASH SAVINGS!

PACKAGE No. 1 As above with R.300RX £210.55
SAVE £17.28!

PACKAGE No. 2 is offered with the FRG7 RX £195.00
SAVE £12.21!

PACKAGE No. 3 Here is a lower-price high-quality package, featuring the all-solid state R.300 £184.50 FRG7 £162.00 SMC73 £128.81

RECEIVERS ONLY, inclusive delivery, etc.
R.300 £184.50 FRG7 £162.00 SMC73 £128.81

For further details, send 9p stamp. You can phone your Access or Barclaycard number, ring 0843 62535 (or 62839 after office hours).

Box 5, Partridge Electronics Ltd.

Partridge House, Prospect Road, Broadstairs CT10 1LD

G3CED (Callers by appointment) G3VFA

audio dummy load

F.G. RAYER G3OGR

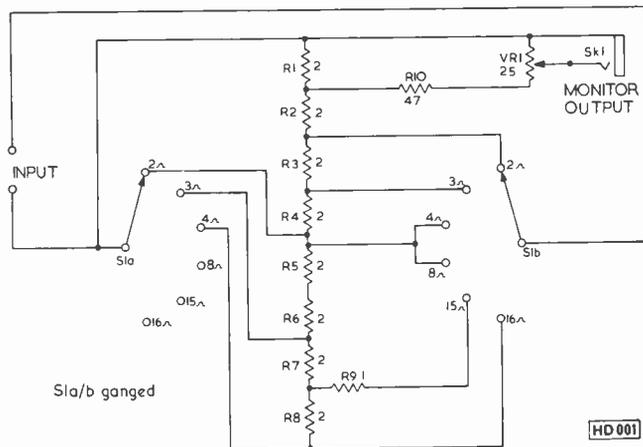


Fig. 1: Circuit diagram. Note that the power sinking capacity is different for various simulated loads—see table. The circuit doesn't include any reactive components; these may be more conducive to amplifier failure than a low value of load resistance.

When an amplifier is left working for a period to check temperature rise, or tested to find its output capability, the audio obtained from the speaker may be a great nuisance or even unendurable! This can be avoided by feeding the audio output into a dummy load. For other than moderately low power, it is convenient to make up the total load with a number of resistors which are individually of relatively low wattage. It is then easy to add a switch which will allow various output loads to be chosen. It is also convenient to add an attenuator and output socket so that a low-level output can be fed to a monitor speaker.

Resistor load

Fig. 1 is arranged to give best utilisation of eight 2Ω 6W resistors and one 1Ω resistor, with a 2-pole 6-way switch. For a 2Ω load, R1/R2 and R3/R4 are in parallel. For 3Ω, R1/R2/R3 and R4/R5/R6 are in parallel. For 4Ω, R1 to R4 are in parallel with R5 to R8. The 8Ω load is secured by R1 to R4 in series, while 15Ω is obtained with R1 to R7 plus R9, and 16Ω with R1 to R8.



Some of the resistors used were Bulgin 2Ω 6W, while others were the cheaper 2.2Ω 7W type, each with a 22Ω ½W resistor in parallel to obtain 2Ω. Suitable resistors are readily available. It would also be practical to make them from resistance wire, if low values of resistance can be measured accurately.

The wattage ratings quoted are for **continuous** operation. For relatively short periods of intermittent use they can be increased by about 20%. For **short** checks, just to find maximum power output, they can be increased by 50% or more.

Due to the way in which it is necessary to switch the resistors, the maximum **continuous** ratings with 6W resistors are as follows:-

2Ω	24W
3Ω	36W
4Ω	48W
8Ω	24W
15Ω	38W
16Ω	48W

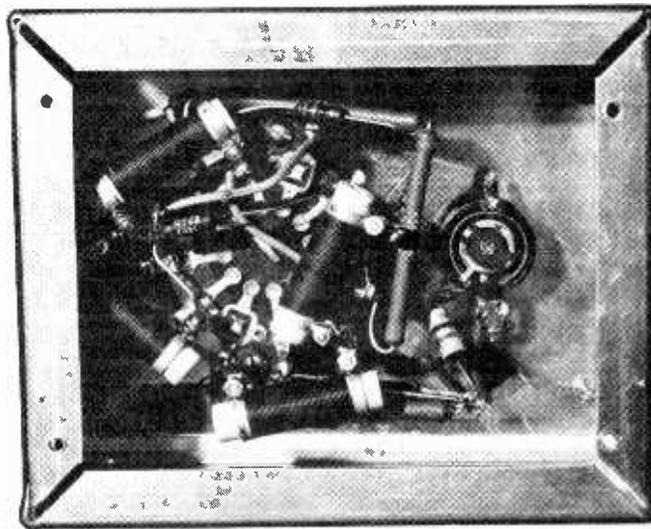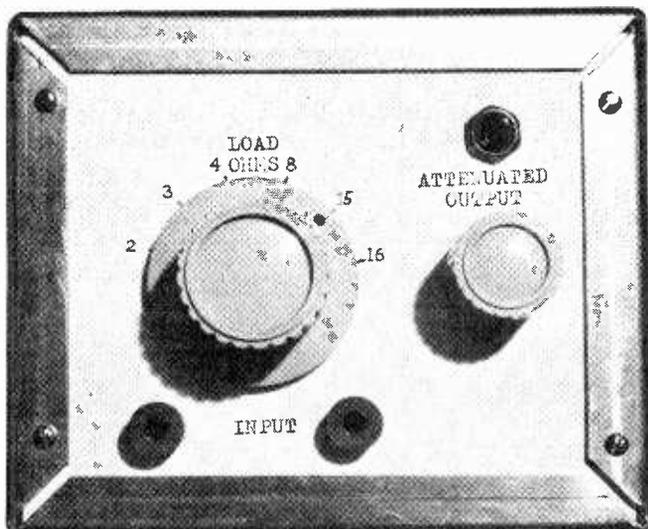
The 1Ω 2W resistor limits the power at 15Ω but it was not felt worthwhile to use larger resistors in some positions to secure a 48W rating throughout. R10 and VR1 allow sufficient audio to be fed, with negligible effect on the dummy load value, to a small monitor speaker or headphones.



KEEP YOUR COOL

WITH ANTEX SOLDERING IRONS...

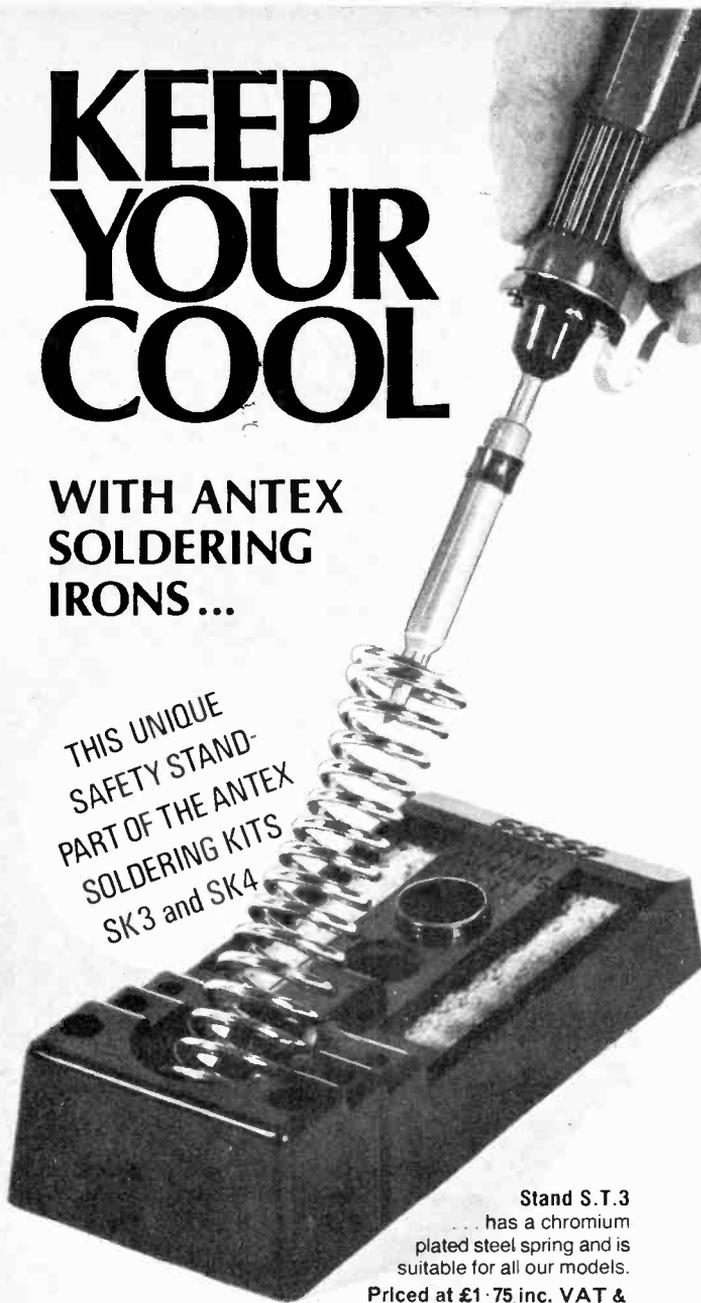THIS UNIQUE SAFETY STAND - PART OF THE ANTEX SOLDERING KITS SK3 and SK4



Stand S.T.3 ... has a chromium plated steel spring and is suitable for all our models. Priced at £1.75 inc. VAT & P&P.

With the new Antex soldering stand you have the assurance that with the iron tucked neatly into the strong angled spring coil you have maximum safety when preparing or waiting for the iron to heat. Moulded into this stand is provision for six alternative bits, and two small sponges for cleaning bits.

This sturdy plastic stand is a useful addition to any household or workshop. The SK3 and SK4 kits comprise of a full instruction card mounted with either the CX miniature soldering iron or the larger X25 general purpose iron. Included in both of these kits is the safety stand.

All the range of Antex soldering irons are made on the principle of putting the heating element inside a shaft, then the desired bit is eased over the shaft, giving maximum heat transference, this is why so often a small Antex iron can do the job of a larger conventional iron. The precision made slide on bits are slit to make them easily interchangeable.

Our comprehensive range is sure to meet your need.

Model CX-17 watts
... a miniature iron with the element enclosed first in a ceramic shaft, then in stainless steel. Virtually leak-free. Only 7½" long. Fitted with a ¼" bit £3.91 inc. VAT & P&P. Range of 5 other bits available from ¼" down to ⅛".

Model X25-25 watts
A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with ¼" bit and priced at £3.91 incl. VAT & P&P. Range of 4 other bits available. B.E.A.B.-APPROVED.

Model SK3 KIT
Contains both the model CX soldering iron and the stand S.T.3. Priced at £5.62 inc. VAT & P&P it makes an excellent present for the radio amateur model-maker or hobbyist.

Model SK4 KIT
With the model X25 general purpose iron and the ST3 stand and its B.E.A.B. safety label, this kit is a must for every toolkit in the home.

Model SK1 KIT
This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet, "How to solder." Price £6.18 inc. VAT & P&P.

Model MLX KIT
The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan, ready for soldering in the field. Price £4.59 inc. VAT & P&P.

Stocked by most of the well-known wholesalers and many retailers. Or direct from us if you are desperate.



Please send the following I enclose cheque/P.O./Giro No 258 1000

Name

Please send the ANTEX colour brochure Address

ANTEX LTD. FREEPOST, PLYMOUTH PL1 1BR TEL. 0752 67377
MAYFLOWER HOUSE, PLYMOUTH, DEVON PL1 1BR

P.W.12.77

MAYFLOWER HOUSE, PLYMOUTH, DEVON PL1 1BR

B. BAMBER ELECTRONICS

Dept. P.W. 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 10E
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

A RANGE OF DRAPER TOOLS FOR THE ELECTRONICS ENTHUSIAST

MAINS TESTER SCREWDRIVERS 100 to 500V. Standard size 50p. Large 70p.
RADIO PLIERS 5 1/2" £1.60. 6 1/2" £1.90.
DIAGONAL SIDE CUTTERS 6 1/2" £1.90.
SMALL SIDE CUTTERS LJ2. Standard £3.70. LJ7 (with wire holding device) £4.10.
MIDGET OPEN ENDED SPANNER SETS 0+1+2+3+4+5+6+7+8 BA sizes £2.85 set of 5. 4+4+5+5+5+5+6+7+8+9+10+11 MM sizes £3.50 set of 6.
MINIATURE FILE SETS. Set of 6 £1.90. Set of 10 £3.25 (Round, flat, etc.).
TAP AND DIE SETS (18 piece) contain 1 each of 0, 2, 4, 6, 8, BA SIZES in Dies, Plug Taps, Taper Taps + American type tap wrench, T type tap wrench, Die Holder. £11.60.
LARGE ELECTROLYTIC PACKS. Contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces, £3.00 per pack (+ 12 1/2% VAT).

A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES.

Aluminium Boxes with Lids.
AB10 5 1/2 x 4 x 1 1/2 60p
AB13 6 x 4 x 2 80p
AB14 7 x 5 x 2 1/2 £1.00
AB15 8 x 6 x 3 £1.30
AB16 10 x 7 x 3 £1.50
AB17 10 x 4 1/2 x 3 £1.30
AB25 6 x 4 x 3 £1.00

Vinyl Coated Instrument Cases

Light Blue tops and White lower sections. Very smart finish.
WB1 5 x 2 1/2 x 2 1/2 60p
WB2 6 x 4 1/2 x 1 1/2 £1.10
WB3 8 x 5 x 2 £1.60
WB4 9 x 5 1/2 x 2 1/2 £1.80
WB5 11 x 6 1/2 x 3 £2.00
WB6 11 x 7 1/2 x 3 1/2 £2.25
WB7 12 x 6 1/2 x 5 1/2 £2.60
WB853 8 x 5 1/2 x 3 1/2 £2.00

MAINS TRANSFORMERS. Type 60/2. Mains input 200-210-220-230-240-250V a.c., output 0-20-40-80V at 2A, in Metal and Plastic case, approx. 7 1/2 x 4 1/2 x 4, fully fused (ideal for PSU) £3.00 each.
MAINS TRANSFORMERS. Type 15/300 240V input. 15V at 300mA output. £1.50 each.
MAINS TRANSFORMERS. Type 45/100, 240, 220, 110, 20, 0V input. 45V at 100mA output. £1.50 each.

MAGNETIC DEVICES PROGRAMMERS. Contain 9 fully adjustable cams and 9 change over micro-switches (rated approx. 1A at 240VAC). Needs slow-motion motor to drive (not supplied). Ideal for disco lights, sequence switching, etc. ex equipment £1.50 each.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6.50 each. Brand New.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST

NEW FOR THE VHF CONSTRUCTOR. A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.

Type S (1/4 in. square, dummy type)
Type SA 20 to 30MHz (when 33pF fitted in parallel)
Type SB 35 to 50MHz (with link winding)
Type SC 70 to 100MHz (with link winding)
Type SD 135 to 175MHz (with link winding)
Type M (Min. 1/4 in. square types)
Type MA 19 to 28MHz (when 33pF fitted in parallel)
Type MB 22 to 32MHz (when 33pF fitted in parallel)
Type MC 25 to 35MHz (when 33pF fitted in parallel)
Type MD 38 to 50MHz (when 33pF fitted in parallel)
Type ME 45 to 60MHz (when 33pF fitted in parallel)
Type MF 100 to 200MHz (without slug) when 0 to 30pF variable fitted in parallel.
All the above coils available in packs of five only (same type) at 50p per pack of 5.

SEMICONDUCTORS

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 50p.
BCY72 Transistors, 4 for 50p.
PNP audio type T05 Transistors, 12 for 25p.
BF152 (UHF amplifier), 3 for 50p.
2N3819 Var. 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAY31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 50p.

741CG op amps by RCA. 4 for £1

RED LEDs (Min. type) 5 for 70p.

PLASTIC PROJECT BOXES with screw on lids (in black ABS) with brass inserts.
Type NB1 approx. 3 1/2 in. x 2 1/2 in. x 1 1/2 in. 40p each.
Type NB2 approx. 3 1/2 in. x 2 1/2 in. x 1 1/2 in. 50p each.
Type NB3 approx. 4 1/2 in. x 3 1/2 in. x 1 1/2 in. 60p each.

MULLARD 85A2 85V STABILISER VALVES (Brand New) 70p each or 2 for £1.20.

TO3 transistor insulator sets. 10 for 50p

PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108MHz and Channels 0-70. Clear numbers, rest blacked out, smart modern appearance. size approx. 8 1/2 in x 1 1/2 in., 2 for 35p.

PLUGS AND SOCKETS

N-Type Plugs 50 ohm, 60p each, 3 for £1.50.
PL259 Plugs (PTFE), brand new, packed with reducers. 65p each
SO239 Sockets (PTFE), brand new (4-hole fixing type). 50p each

SOLDER SUCKERS (Plunger type). Standard Model. £5. Skirted Model £5.50. Spare Nozzles 60p each.

NEW MARKSMAN RANGE OF SOLDERING IRONS.

S125D 25W 240V £3.80.
S140D 40W 240V £4.20.
S125DK 25W 240V + bits etc., KIT £4.90.

BENCH STAND with spring and sponge for Marksmen Irons £2.38.
Spare bits MT9 (for 15W) 50p, MT5 (for 25W) 45p, MT10 (for 40W) 50p.
ALL PRICES + 8% VAT.

TEMPERATURE CONTROLLED IRON.

Temperature controlled iron and PSU. £30 + VAT (£2.40)

SPARE TIPS

Type CC single flat. Type K double flat fine tip. Type P, very fine tip. £1 each + VAT (8p).
MOST SPARES AVAILABLE.

MULTICORE SOLDER

Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).
Size C15AV18 Savbit 18 s.w.g., 56p + VAT (4p).
1 Kg. (1.1lb) 60 x 40, 20 s.w.g. on plastic reel £3 + VAT (24p).

WELLER SOLDERING IRONS

EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN 8100D £9.90.
EXPERT SOLDER GUN KIT (spare bits, case, etc.) £12.90.
Spare bits 35p pair.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

ALU-SOL ALUMINIUM SOLDER (made by Multicore). Solders aluminium to itself or copper, brass, steel, nickel or tinplate. 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p each. Large reel £2.75.

VARICAP TUNERS Mullard type ELC1043/05. Brand New. £4.40 + 12 1/2% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Seatronc Manufacture. Approx. 100. £1.50 per pack + 12 1/2% VAT.

OSMOR REED RELAY COILS (for reed relays up to 1/4 in dia., not supplied) 12V. 500 ohm coil. 2 for 50p.

We now stock Spiralvax Tools for the electronic enthusiast. Screwdrivers, Nut spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

DuBilier Electrolytics, 500uF, 450V, 2 for 50p.
DuBilier Electrolytics, 100uF, 275V, 2 for 50p.
Plessey Electrolytics, 470uF, 63V, 3 for 50p.
TCC Electrolytics, 1000uF, 30V, 3 for 60p.
DuBilier Electrolytics, 5000uF, 35V, 50p each.
DuBilier Electrolytics, 5000uF, 50V, 60p each.
ITT Electrolytics, 6800uF, 25V, high grade, screw terminals, with mounting clips. 50p each.

PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS
TV Plugs (metal type), 4 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p.
Please add 12 1/2% VAT.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

1B3GT	0.65	6AK6	0.65	6CW4	3.75	12BA6	0.65	ECL80	0.60	EZ80	0.35	PCL805	0.75
1R4	0.50	6AK7	0.85	6CY5	1.00	12BE6	0.80	ECL81	0.60	GY501	0.85	PD510	3.35
1R5	0.50	6AL5	0.40	6CY7	1.00	12BH7A	0.75	ECL82	0.75	GZ30	0.65	PL36	0.75
1S4	0.40	6AM6	0.65	6DQ6B	1.45	12BY7A	0.80	ECL83	1.15	GZ32	0.65	PL81	0.65
1S5	0.40	6AM8	0.70	6DT6	0.80	35V4	0.70	ECL84	0.70	KT66	4.50	PL82	0.55
1T4	0.40	6AN5	2.50	6GH8A	0.80	50C5	1.00	ECL85	0.65	KT88	5.80	PL83	0.50
1U4	0.70	6AN6	0.85	6GK5	0.70	*75C1	0.80	ECL86	0.75	OA2	0.55	PL84	0.75
1U5	0.80	6AQ5	0.85	6J4	1.00	*85A2	0.85	EF80	0.40	OA3	0.75	PL95	0.70
1X2B	1.20	6AR5	0.70	6JS7	0.80	*90C1	1.20	EF85	0.48	OB2	0.60	PLS04	1.05
2CV4	4.50	6AS6	1.00	6J6	0.55	*807	1.00	EF86	0.55	OB3	0.75	PLS08	1.30
*2D21	0.80	6AS7G	1.10	6J7	0.80	*811A	3.20	EF92	0.75	OC2	1.40	PL802	2.80
*3.500Z	40.00	6AT6	0.75	6K6GT	0.85	*829B	6.30	EF97	0.70	OC3	0.75	PY81	0.70
*3E29	6.50	6AU6	0.50	6L6GT	0.80	*832A	6.00	EF98	0.90	OD3	0.75	PY82	0.55
3Q4	0.75	6AV6	0.60	6N7GT	0.85	*866A	3.00	EF183	0.70	PABC80	0.45	PY83	0.70
3S4	0.50	6AV8A	0.75	6Q7	0.90	*872A	6.00	EF184	0.70	PC86	0.70	PY88	0.70
5AQ5	0.75	6AX4GTB	1.00	6SA7	0.80	*5763	2.85	EFL200	1.00	PC88	0.70	PY500A	1.30
5ATB	0.80	6AX5GT	1.30	6SG7	0.80	DAF96	0.60	EH90	0.60	PC92	0.60	TT21	7.80
5T4	0.75	6BA6	0.45	6SK7	0.80	DF96	0.60	EL34	0.95	PC95	0.70	TT22	7.80
5U4G	0.60	6BE6	0.48	6SL7GT	0.70	DK92	1.00	EL36	0.95	PC96	0.50	U25	1.00
5U4GB	0.95	6BF5	0.85	6SN7GT	0.70	DL96	0.60	EL81	0.65	PC97	0.95	U26	1.00
5UB	0.75	6BF6	0.75	6SQ7	0.80	ECC84	0.60	EL82	0.60	PC900	1.00	UABC80	0.58
5V4G	0.60	6BH6	0.85	6VG7	0.65	ECC85	0.48	EL83	0.60	PCC84	0.50	UBF89	0.60
5X4G	0.80	6BJ6	1.20	6X4	0.60	ECC86	1.25	EL84	0.45	PC85	0.60	UBL21	0.85
5X8	0.90	6BN6	0.80	6XS7	0.60	ECC88	0.75	EL86	0.70	PCC88	0.65	UCC84	0.75
5Y3GT	0.65	6BQ7A	0.65	12AC6	0.80	ECC89	0.80	EL95	0.70	PC89	0.75	UCC85	0.55
5Z4GT	0.65	6BR8A	1.20	12AD6	0.80	ECC189	0.80	ELS04	0.80	PCF189	1.00	UCF80	0.75
6AB4	0.55	6B8B	0.85	12AE6	0.85	EF80	0.60	EM80	0.65	PCF80	0.65	UCH81	0.65
6AB7	0.60	6BV7	1.00	12AT6	0.60	ECF86	0.80	EM81	0.60	PCF82	0.45	UCL81	0.70
6AC7	0.80	6BZ6	0.65	12AT7	0.50	ECF200	0.90	EM84	0.60	PCF84	0.65	UCL82	0.75
6AF4A	0.70	6BZ7	0.70	12AU6	0.65	ECF201	0.90	EM87	1.00	PCF201	1.10	UCL83	0.80
6AG5	0.65	6C4	0.55	12AU7	0.47	ECH80	0.95	EY51	1.00	PCF806	1.00	UF85	0.50
6AG7	0.85	6CB6	0.55	12AV6	0.60	ECH82	0.95	EY81	0.60	PCL81	0.65	UL84	0.75
6AH6	0.85	6CS7	0.85	12AV7	1.00	ECH81	0.50	EY87	0.60	PCL82	0.75	UM80	0.60
6AJ5	0.65	6CUs	1.00	12AX7	0.47	ECH83	0.60	EY88	0.55	PCL84	0.75	UM81	0.75
6AK5	0.55	6CU6	1.00	12AY7	0.85	ECH200	0.80	EY500A	1.50	PCL86	0.75	UM84	0.45

AC/DC TAUT SUSPENSION MULTIMETERS TYPE U4315



Sensitivity D.C. 20,000 o.p.v.
Sensitivity A.C. 2,000 o.p.v.
D.C. Current 50µA-2.5A
A.C. Current 0.5mA-2.5A
D.C. Volts 75mV-1000V
A.C. Volts 1V-1000V
Resistance 300Ω-500kΩ
Capacity 0.5µF
Accuracy 2.5% D.C., 4% A.C.

Price complete with pressed steel carrying case and test leads. £14.95
Packing & postage + VAT 8% £1.35

VAT is not included. Please add 12 1/2% on all items except those marked with asterisk, on which VAT is 8%. Postage and packing charges are £0.10 per £ subject to a minimum of £0.30.

OUR NEW 1977/1978 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

HOTLINES

A REVIEW OF RECENT DEVELOPMENTS

In general, the author does not have any more information on products than appears in the article.

The ultimate deterrent?

Calling all motorists. Your salvation from radar speed traps is at hand—literally. An American company has produced a little 8lb receiver which tunes wideband from 8 to 18GHz and will give an alarm if it sniffs any radar radiation. It's intended for front line troops so that they will know when the enemy is watching them on radar. If it's for the military, then it should be good.

Unfortunately, the US Police Departments are also well up in electronics. They have just brought out a small radar which employs a microprocessor to help prevent its detection by "with-it" motorists.

This device will hold the microwave radar signal until the target vehicle is in sight. Then it fires. If the motorist has some form of radar detector, it will be too late to take any slowing down action because by the time he (the motorist) receives a warning, the police radar will already have measured the speed of the vehicle.

And it gets more complex, too. The new police radar also has to measure accurately the speed of the police vehicle—and to do this it has to emit a radar signal—which some motorist might detect! So; the police unit fires its radar emission in little blasts so quickly that it exceeds the integration time of most radar detectors. Pulse, frequency and period are all pseudo-random and it would be extremely difficult to find this complex "radio signature". Even if this were possible the police claim that they can alter all the elements by simply reprogramming the unit.

Seems to me it would be simpler just not to exceed the speed limit—or to stay at home with one of those German TVs and watch both pictures!

A weighty problem

Not having had my weight checked electronically before I was interested in the latest in bathroom scales which give ones weight digitally. The price is around £27 but then I found that the scales are really quite conventional in the weighing part, they just show the weight digitally.

The Americans have come up with something a little better. Certain electronic scales over there use strain gauges to sense the weight and the accuracy is to within one tenth of a pound. Another good idea is that the digital bit which shows you the weight, is a separate unit that can be wall-mounted where you can see it easily. Anyone who, like Ginsberg, has crouched in a precarious position, balanced on the edge of the bathroom scales, knees either side of ears, struggling to read a talcum-encrusted needle, will appreciate the usefulness of the newer approach. Trouble is, these new beasties will weigh heavily on your wallet; between £165 and £225 each! Ah well, back to the fifth lotus weighing position!

Split personality

Have you ever watched television and wondered what's on the other channel? Or perhaps, as an ardent button pusher you've "twitched" from one programme to another and back again? Relax—your worries are over. A German manufacturer has come up with the ultimate—two pictures at the same time—together—simultaneous—like! Just think, "Noddy meets Lady Chatterley", or "Ena Sharples versus the Six Million Dollar Man".

In practice it's not quite so easy to do! Basically, the manufacturer has managed to put a small picture (of the other channel) at the bottom of the screen which is filled with the channel picture that you are watching.

The difficulties become apparent when one considers that the tiny picture must somehow be 'shrunk' and that the single beam from the CRT's electron gun must produce both pictures simultaneously even though they are out of phase with each other. Again, both sweeps, horizontal and vertical, must be quite different to those required for the other picture because of the size difference.

The solution has been to use two memories. Video information is fed into the first memory and then fed out in the required timing sequences. While the first memory is being read out, the second memory is taking in fresh video data. The "memory" used


is a form of bucket-brigade device. Here, the signals are delayed by the time taken to pass them from one element in the chain to the next—rather like a chain of people would pass buckets of water to each other along a human chain. Here, the device is passing charges.

Unfortunately, the available BBDs which were conventional types proved useless; basically a MOS arrangement of transistors interspersed with capacitors. In practice, they didn't delay the signal long enough, even though several hundred transistors were employed. The solution was to manufacture a BBD device where the elements were arranged in a matrix with short line elements and low signal losses. In one of these chips, there are some 8,000 elements comprising 4,000 transistors and 4,000 capacitors—all in 12mm².

And all to let you look at two pictures at the same time! Perhaps the smaller picture could come from a CCTV camera pointing down your front path for security surveillance? Come to think of it, the current standard of TV programmes might make Ginsberg's front path more interesting viewing!

Puzzle corner

Computers and chess are often mentioned in the same breath. If you just happen to have an interest in both, then you'll be pleased to hear that the Computer Chess Newsletter has been started. This is aimed at providing information on chess programming for computers, records of games played with computers (and even between computers themselves) plus all sorts of news. If you are interested, why not drop the Editor a line? Write to Douglas Penrod at 1445 La Cima Road, Santa Barbara, California 93101, USA. You must send an IRC (international reply coupon—get one from the Post Office) and the equivalent of a dollar if you want a sample copy of the journal.

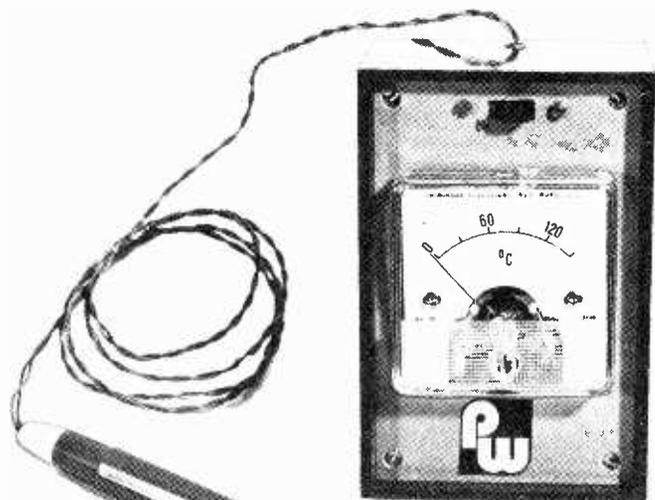

A HEATSINK THERMOMETER

I. HICKMAN

This simple thermometer was made up to check that power transistors on heatsinks were running at a safe temperature. Diode D1 is the temperature sensing element, Fig. 1, and is enclosed in a tiny copper heatsink which is held against the surface where temperature is to be measured. A constant current is passed through the diode by R1 from the stabilised voltage across D2. The voltage across D1 varies by approximately 2.1mV per degree Centigrade, resulting in a change of more than 300mV over the range, 0°C to 150°C.

This is measured by M1 the positive terminal of which is returned to the junction of R2 and R3. The potential at this point is set by VR2 such that it equals the voltage across the diode when the latter is at freezing point. Thus the meter reads zero at 0°C. VR1 is set so that the meter reads $\frac{2}{3}$ full scale at the temperature of boiling water, thus FSD corresponds to 150°C. A 5.6V zener was chosen for D2 as this offers nearly zero temperature coefficient and a low slope resistance. By supplying the zener from the high collector slope resistance of a transistor, excellent voltage stability is obtained even using the 9V battery down to a little over 6V. With intermittent use, the battery will last many months.

Construction

Fig. 2 shows how a small piece of 20SWG copper sheet is cut and shaped so that it can be bent up to virtually enclose D1. D1 should be of the "double slug" type of construction where the silicon wafer is sandwiched directly between metal slugs without any intermediate whisker. A fine copper wire, 42SWG

or thinner, is soldered to one end of the diode and the other end is soldered into the hole in the heatsink and the lead cut off flush. The diode should be hard up against the heatsink; the soldering process will not damage it. Another fine wire is soldered to the heatsink and the inside filled with Araldite, after arranging the wires in a small loop to minimise heat conduction. The wires are then passed up the inside of a length of 0.2in paxolin tube, to the end of which the diode/heatsink is Araldited.

Finally, the end of the heatsink is carefully filed flat to enable a good thermal contact to be achieved. The probe should be finished by mounting the paxolin tube in a suitable handle, which also contains the transition from the fine copper wires to a lightweight flex. The barrel of a felt tip pen makes a convenient handle.

The rest of the circuit, including the meter and battery, is mounted in a "Bargain Project Box" obtainable from Messrs. Crescent Radio Ltd. All the components except S1, D1 and the battery mount on a small PC board, Fig. 3, which fits over the meter terminal posts and is soldered to the meter's soldering tags.

★ components

Resistors

R1	3.3k Ω	VR1	4.7k Ω
R2	2.7k Ω	VR2	4.7k Ω
R3	470 Ω		min. skeleton
R4	47 Ω		vertical
R5	6.8k Ω		
All $\frac{1}{4}$ or $\frac{1}{2}$ W 5% carbon film			

Semiconductors

D1	1N916 (see text)
D2	BZY88 C5V6 (5.6V zener)
D3	1N916
Tr1	OC71 or similar

Miscellaneous

M1, meter 100 μ A FSD Type MR38P, S1, DP slide switch.
Copper for heatsink. Material for probe. Metal or plastic box approx 85 x 55 x 37mm (3 $\frac{1}{2}$ x 2 $\frac{1}{4}$ x 1 $\frac{1}{2}$ in.) PP3 battery.

GT121



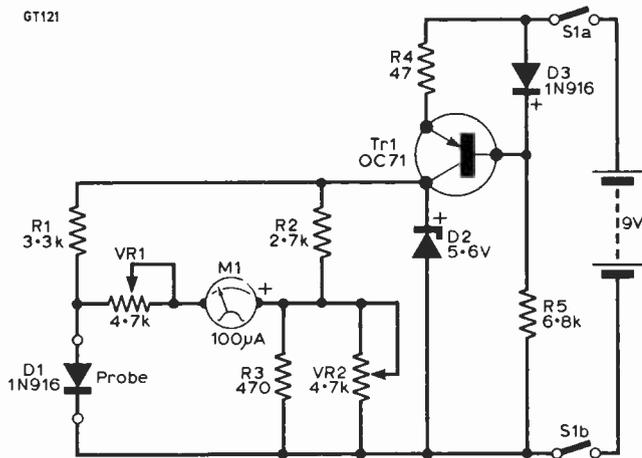


Fig. 1: Complete circuit diagram of the heatsink thermometer.

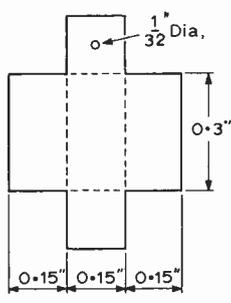


Material:- 20 SWG Copper
GT122

Fig. 2 (above): Temperature probe housing cutting details. Fig. 3 (right): A suggested PCB layout. All components are mounted on the copper side of the board.

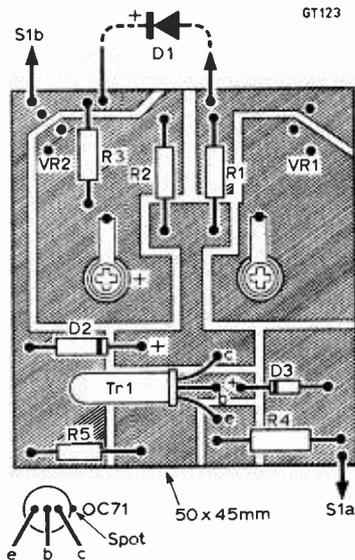


GT123

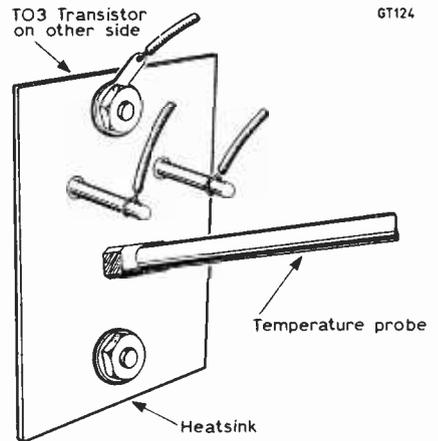

GT124

Fig. 4: The temperature probe should be applied to the heatsink, not the transistor case.

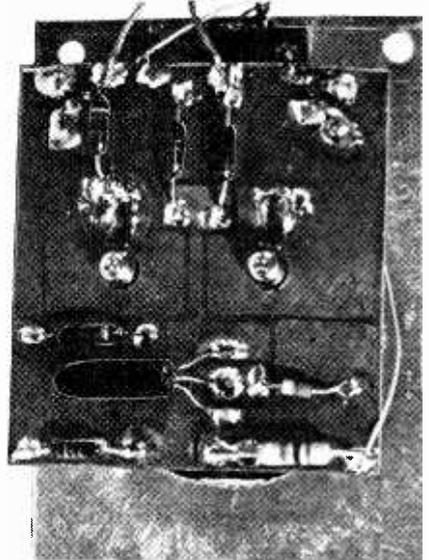

Calibration

Having finished construction and checked that 5.6V approx. appears across D2, set VR1 to mid-range and adjust VR2 for zero meter reading when the probe tip is immersed in a mixture of water and melting ice, well stirred. Next, dry the probe and place the tip on the outside surface of a kettle of boiling water, using plenty of heatsink compound. Adjust VR1 for a scale reading of 100°C. The probe will not quite have reached this temperature, but the difference should only be two or three degrees, as can readily be checked by immersing the probe tip. If you do, carefully remove all the heatsink compound first! The thermometer is now calibrated.

Use

The recommended method is to measure the temperature of the heatsink on the opposite side from

the power transistor, as in Fig. 4. To ensure that the power transistor is running at a safe temperature, it is necessary to deduce the junction temperature of the actual silicon chip inside. From the voltage across and the current through the transistor, calculate its dissipation P in watts. Next, to the thermal resistance from junction to case $R_{\theta_{j-c}}$ add that from case to heatsink $R_{\theta_{c-h}}$. These are quoted by the transistor manufacturer on the data sheet. There will usually be three values for $R_{\theta_{c-h}}$: (a) transistor mounted on heatsink direct (b) ditto, but with silicone grease and (c) insulated by a mica washer. Multiply the dissipation P by the total thermal resistance

$$R_{\theta_{j-h}} \text{ where } R_{\theta_{j-h}} = R_{\theta_{j-c}} + R_{\theta_{c-h}}$$

to find the temperature of the junction relative to the heatsink. Add this to the measured heatsink temperature and check that the resultant junction temperature is within the manufacturer's rating, e.g. 200°C for a 2N3055.

With today's very high cost of motoring, an increasing number of people are servicing their own cars. This can save a lot of money, but also lead to some difficulties. The efficiency of an engine depends on a large number of factors, one of which is the condition of the ignition system and how accurately it is set up.

Here lies one of the difficulties. The motorist can set the contact-breaker points gap fairly easily, whereas a garage will use an expensive dwell meter which measures the interval over which the points are closed. The ignition timing is a critical adjustment which has a great influence on fuel consumption, but is not so easily checked by the d-i-y motorist. True he can set the timing statically, using a bulb, but it is much better and more accurate to set the timing with the engine running. Here the professional uses a strobe timing light, but few motorists possess such an expensive piece of equipment:

A short while ago, the author wanted to fit an electronic ignition system to his car to improve its performance and fuel economy. The particular type being fitted used a magnetic sensing system to provide the timing, rather than the more usual mechanical contact-breaker. This meant that the timing method using a bulb could not be adopted. Instead a strobe timing light was necessary, and it was this which led to the development of the low-cost unit described here.

Circuit description

As can be seen from the circuit diagram, Fig. 1, a mains-driven power unit provides an output of some 200 to 300 volts d.c. This is connected across the xenon strobe tube, FT1, whose trigger electrode is connected to one of the sparking plugs. Each time a high voltage pulse from the distributor is applied to the plug, the strobe tube will fire, producing a flash of light. The power supply capacitor C1 will be discharged through the tube, and will recharge in the interval before the next trigger pulse.

The requirement for a mains power supply is the one disadvantage of this simple system. However, it does mean that the light output from the tube is greater than that obtained from some other low-cost designs. As the unit will not normally be used very often, it was not considered too great a drawback.

ECONOMY TIMING



Construction

The timing light is built in two parts: the strobe head itself, with the sparking-plug adaptor attached, and the power unit. The strobe head should be housed in a plastics box, for good insulation, and safety in handling. Constructional details are shown in Fig. 2. The strobe tube is mounted in a piece of

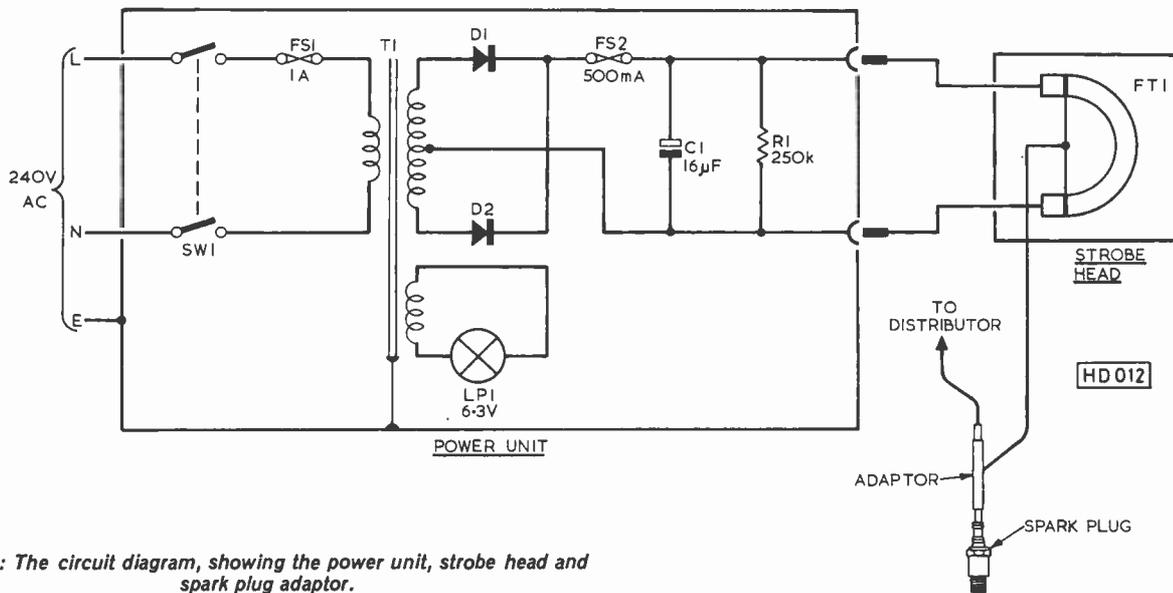


Fig. 1: The circuit diagram, showing the power unit, strobe head and spark plug adaptor.

STROBE

B. HARVEY



5mm (3/16in) thick Paxolin, and held in place by means of some flexible adhesive such as Evostik. The tube, being glass, is fairly fragile, and some care in handling is advisable. The aluminium reflector should be polished using Brasso, etc. to provide the maximum light output from the unit.

The connecting lead to the power unit should be in good quality heavy duty twin mains flexible, while that to the sparking-plug adaptor should be in car HT cable, obtainable from motor accessory shops. A length of one metre is normally adequate.

Sparking-Plug Adaptor

The sparking-plug adaptor is made from a piece of brass rod about 10mm ($\frac{3}{8}$ in) in diameter. One end is turned down in a lathe or electric drill until it will fit firmly into the plug lead cap. The size will depend on the type of plug lead used on your car. Usually, British cars use the plug with the adaptor screwed on the end, but many European cars use only the threaded portion, without the adaptor.

★ components

Resistor

R1 250k Ω 1W

Capacitor

C1 16 μ F 450V Electrolytic

Diodes

D1, D2 BY100 etc. (400V 1A)

Miscellaneous

T1 Pri: 240V

Sec 1: 200-0-200 to 300-0-300V

15mA (see text)

Sec 2: 6.3V 0.5A

FT1 Strobe tube (Tandy Cat. 272-1145 or similar)

FS1 1A

FS2 500mA

S1 D.P.S.T. mains switch

LP1 6.3V 0.3A lamp

Holders for lamp and fuses. Plastic box 101 × 54 × 41mm (Tandy Cat. 270-231 or similar). Metal box for power unit. Car HT cable (1m). Terminals or plug and socket for DC output connection. Paxolin, Perspex, aluminium sheet. Cable clamps, grommets, brass rod and plastic tubing for insulation.

The other end of the adaptor is drilled out to fit the top connector of the sparking plug. A slot is then sawn down the length of the hole and the sides sprung slightly inwards to give a firm fit.

Good insulation is essential on the sparking plug adaptor and on all connections inside the strobe head. Remember that the power supply is capable of giving a very dangerous shock, while the trigger lead will have anything up to 20,000 volts on it every time the plug fires.

Power supply

No constructional details are given for the power supply unit, because this can take more or less any form, and it may be that the constructor already has a suitable power pack available. The HT output should be capable of supplying 200-300 volts at not less than 15 milliamps.

For safety and robustness, the power unit should be housed in a metal case. The prototype used a die-cast box. It is advisable not to omit the pilot lamp, which provides a warning of the presence of the HT output.

Engine timing

What is usually referred to as the timing on a car engine, is the point at which the sparking plug fires in relation to the position of the piston in the cylinder. If the spark occurs too early then severe stress and even damage can occur in the valve gear, connecting rod, piston, crankshaft and bearings. If the spark occurs too late, some or all of the power developed by burning the fuel is allowed to dissipate itself to atmosphere via the exhaust pipe. This is not usually so dangerous to the engine as having the spark too far advanced, but is very wasteful.

The exact point at which the fuel air mixture in the cylinder is ignited is critical within close limits. A few degrees out either way causes the efficiency of the engine to drop.

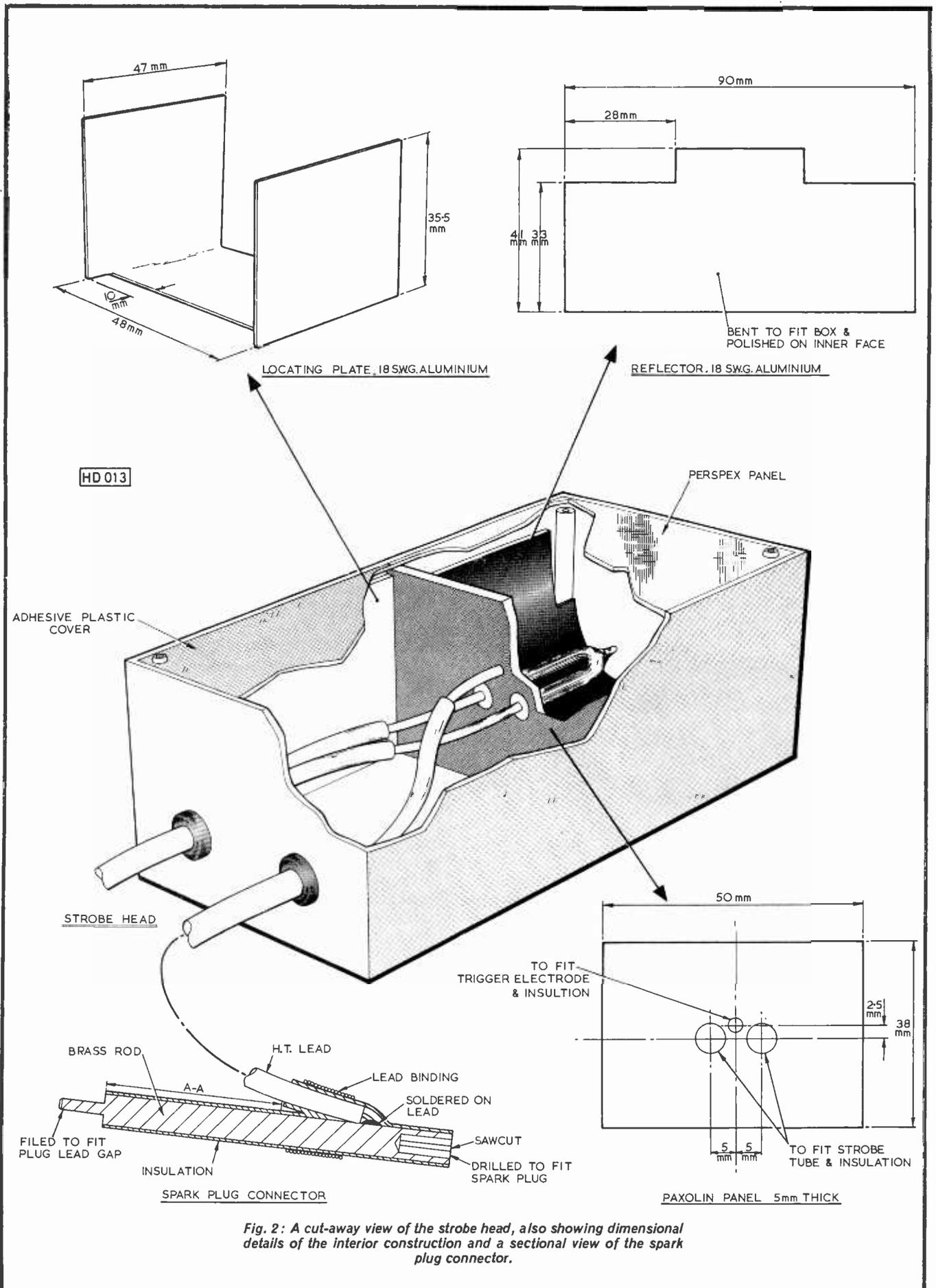


Fig. 2: A cut-away view of the strobe head, also showing dimensional details of the interior construction and a sectional view of the spark plug connector.

KINDLY NOTE!

In order to check the exact relationship between the timing of the spark and the position of the piston, some form of reference marks have to be used. On most car engines the end of the crankshaft protrudes through the front of the engine casing. On this shaft is mounted a pulley wheel which drives the cooling fan, the dynamo or alternator and sometimes the water pump via the fan belt. On the front face of the crankshaft pulley wheel, or sometimes on the edge, is a mark, indentation or raised portion that coincides with another mark on the body of the engine when one cylinder (usually No. 1, the front one) has its piston at the highest point it can reach, normally referred to as "top dead centre" (t.d.c.).

Therefore we have a simple indicator that shows when one of the pistons has reached top dead centre. If further marks are added corresponding to 5 degrees and 10 degrees before t.d.c. on our reference cylinder then the timing of the engine can be found. This will hold good for the other cylinders of the engine, as the firing of all cylinders is controlled by the distributor cam and cannot change.

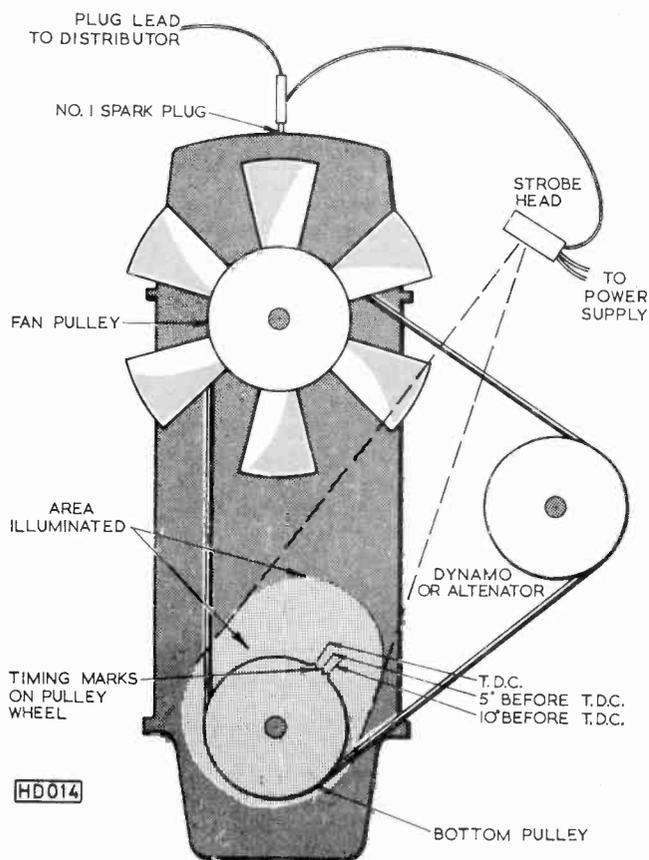


Fig. 3: A general view showing the strobe head illuminating the timing marks on the pulley wheel.

Using the Strobe

The strobe timing light should be connected to its power unit and the sparking plug adaptor connected in the lead to No. 1 cylinder plug. The engine should then be started up and allowed to stabilise its speed. If the power unit is now switched on, the strobe light will flash each time the spark occurs in No. 1 cylinder.


continued on page 757

Jubilee Organ Project

- i September 1977, p 353. Transistor ident. BFY71 should read BCY71.
- ii November 1977, Part 3. The circuit diagram of the accompaniment section, p 509, shows the base of Tr5 connected to the 12V positive rail. This connection should be broken, leaving the base connected to the free end of R44 (1 megohm) only.
The PCB as purchased from Readers' PCB Services is correct in this detail.
- iii The end of R45, shown connected to the 12V positive rail, should go to the junction between R40 and C17.
The PCB as purchased from Readers' PCB Services is correct in this detail.
- iv Collated components list, p 353 September 1977 contains the information "3-off 33nF"; this should read "3-off 3.3nF Polystyrene."

Gas/Smoke Sensor Alarms, April 1977

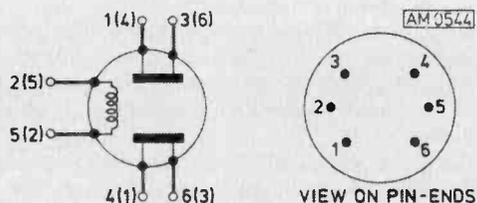We have received a number of queries from readers regarding the pin connections for the TGS812 Gas Sensor used in this design. These are as shown in the diagram below:



The TGS812 is a symmetrical device, and can be plugged into a standard 7-pin miniature (B7G) valve holder.

We regret that the pin numbers quoted in Fig. 1 of the article are incorrect. They should be amended as follows:


Pins 1, 2 and 3 to +5V (C1 positive)

Pins 4 and 6 to VR1

Pin 5 to negative supply rail (C1 negative)

S-DeCnology

DAVID GIBSON

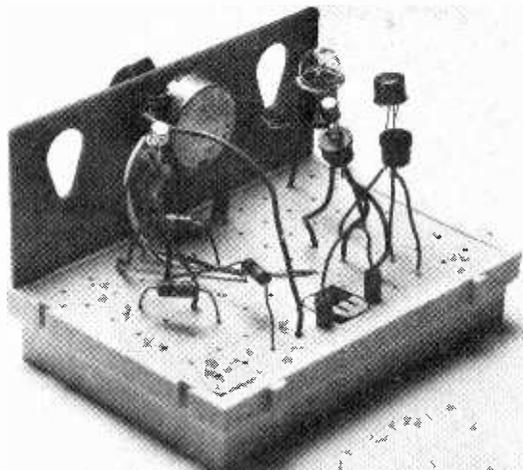

12



THIS MONTH



'The Might Light'

This month's S-DeC circuit, the last in the present series, should provide a gripping finish to any party. Two contestants are asked to hold a "probe" in each of their hands. An adjustment is made until a bulb just extinguishes. On the command "Go", each contestant must grip/squeeze his/her two probes as hard as possible. One contestant has the power (depending on the strength of grip) to make the bulb light—the greater the grip the brighter the bulb lights. Conversely, the other contestant can dim the bulb (greater squeeze equals dimmer light) and can keep the bulb turned off.

The circuit uses only eight components (plus a battery) and functions as follows. By gripping the upper pair of probes the "light" contestant puts the resistance of the body in parallel with the resistor R1. The less this body resistance is, the more Tr1 is biased "on" and the more it will drive transistors Tr2 and Tr3. As Tr1 draws more and more current, the voltage developed across VR1 becomes greater and so drives the Darlington pair (Tr2/Tr3) harder "on". As these Darlington-connected transistors draw more current, the bulb in their collector circuit will obviously glow brighter.

The "dark" contestant puts his body resistance across R3. The less resistance there is here, the more Tr1 will turn "off" i.e., the less current it will draw and so less driving voltage will appear across the potentiometer VR1. The resistor R2 was included as a safety measure since, if the "light" contestant probes were accidentally shorted together, then the base of Tr1 would be directly connected to the positive battery rail causing the circuit to draw heavy current.

The potentiometer offers a simple means of balancing the circuit prior to a contest. If both contestants hold the probes lightly, then VR1 is easily adjusted until the bulb just extinguishes. It is more exciting if the bulb is adjusted for a slight glow, as any variation in brightness can then be seen immediately by the onlookers and, of course, the judges!

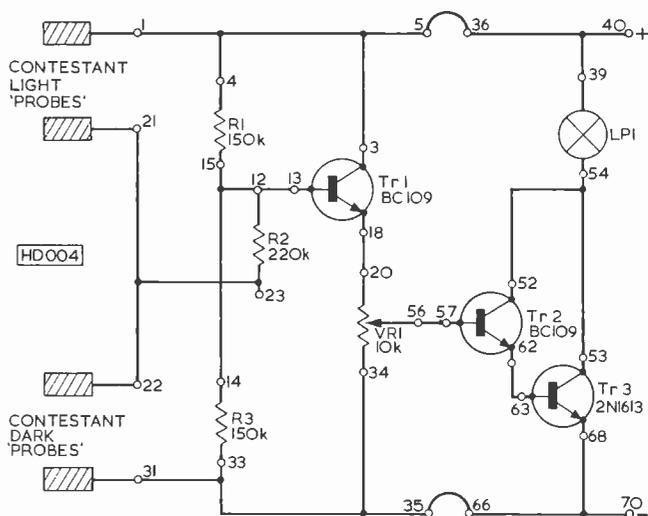


Fig. 1: The circuit diagram

Once you have assembled the circuit on your S-DeC (don't forget the shorting links between holes 5/36 and 35/66) you should apply the battery voltage, but leave the probes unconnected. It should be possible to swing the potentiometer to light the bulb from full brilliance to completely extinguished. The value of VR1 offers a wide range and can easily adjust for any values of human skin resistance.

The probes are best made from short lengths of metal pipe, about 125mm (5in) long and anything from 12mm (1/2in) to 25mm (1in) diameter. You can simply paint a band around the top part of each probe, using white and black paint for "light" and "dark" respectively. Don't paint the whole pipe or you will insulate the skin contact from the metal and the circuit will not function.

Games using the circuit are endless and limited only by the imagination. For example, teams could join hands and the leaders then hold the probes. The potentiometer is adjusted and on the command every-

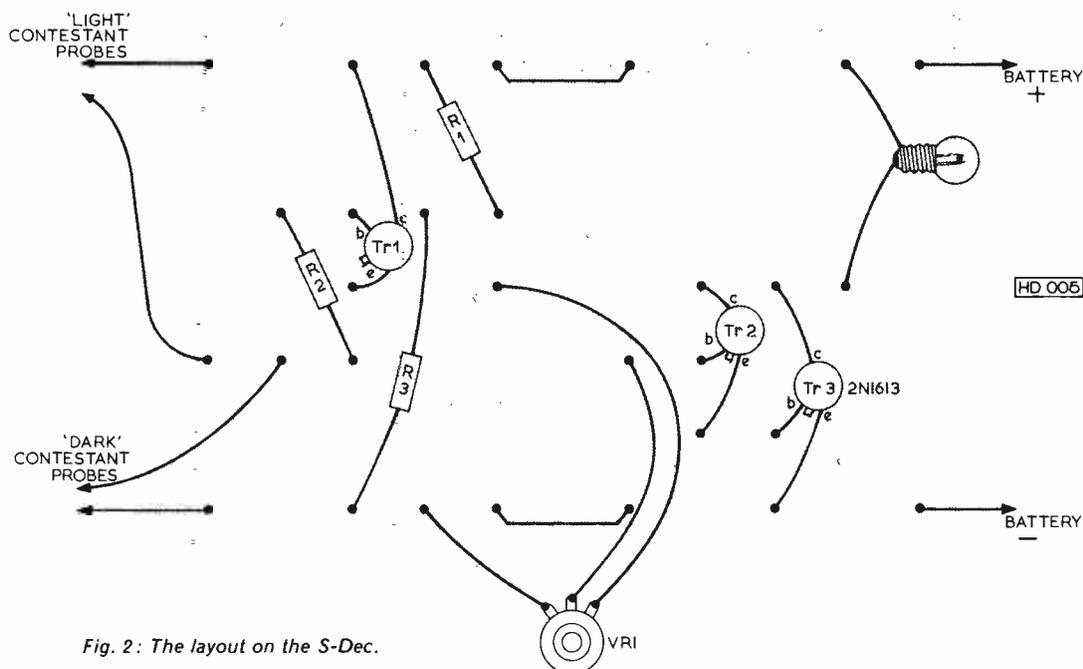


Fig. 2: The layout on the S-Dec.

you will need . . .

R1 150k Ω	Tr1 BC109
R2 220k Ω	Tr2 BC109
R3 150k Ω	Tr3 2N1613
VR1 10k Ω potentiometer	
LP1 6V 100mA bulb	
One S-Dec	
6V battery	
Four pieces metal pipe (see text)	

one must squeeze the wrist of their partners; a sort of "Squeeze-o-War".

Power demands

Battery voltage is not critical and the circuit will function with any voltage from 12V (maximum) down to 4.5V. It ceases to work below 4.5V. The lower voltages mean greater battery life although the bulb does not light quite so brightly at maximum brilliance. Since maximum brightness is not used anyway, it is sensible to use lower voltages. At 6V, the total circuit current measured was slightly under 90mA, and with VR1 adjusted to just extinguish LP1 the current was 24mA. These figures should be taken as a guide only, since the gains of individual transistors could alter this, although in the circuit shown the variations will not be enormous and VR1 can be adjusted for correct circuit operation no matter what.

This is the last S-DeCnology circuit in the series. However, a new series of one-IC circuits will start shortly. The principles of simple circuitry and ease of construction will be carried on, and the new series will use a DeC which can accept ICs plus discrete components.

ECONOMY TIMING STROBE—contd. from page 755

If the light flashes only very weakly, it is probably due to the power supply capacitor not recharging sufficiently between trigger pulses. This may be overcome by reducing the value of C1.

The strobe head can now be held in a position that allows it to illuminate the crankshaft pulley (Fig. 3), making sure that everything is safely out of the way of the blades of the fan, which are often difficult to see. Due to the stroboscopic effect of the light, the bottom pulley wheel will appear to be stationary. If the engine timing is correct, the two sets of marks on the pulley wheel and the engine body will line up. If they do not, the engine is either too far advanced or retarded. If the engine speed is then increased, a device called a centrifugal governor, housed in the distributor, will automatically advance the engine timing and show if the engine is advanced or retarded.

The precise method of making these checks will vary according to the particular engine. Most cars have the timing set for around 5 degrees before t.d.c. at 1,000 r.p.m. with the vacuum advance disconnected. If the exact procedure is not known then the information can be obtained from the car workshop manual. If it is found that the timing is incorrect then the usual method of adjustment is to rotate the body of the distributor, after first slackening the clamping bolt. Some distributors are provided with an adjusting mechanism which allows the timing to be adjusted over a few degrees by turning an external knurled nut. The letters "A" and "R" on the distributor body indicate which direction of movement advances or retards the timing.

The time required to carry out a timing check is very little, but it can save a considerable amount of money, and is well worth while.

PRODUCTION LINES


bill tull

NEW FROM SINCLAIR

A new concept—a "personal" digital multimeter, at a price competitive with low-cost analogue multimeters, has been launched by Sinclair Radionics.

Designated the PDM35, this 3½ digit meter measures just 155 × 75 × 30mm. The facilities incorporated were chosen as a result of an international market survey, and allow measurements in the range 1mV to 1000V DC, 1V to 500V AC, 1nA to 200mA DC and 1Ω to 20MΩ. The resistance ranges can also be used for semiconductor junction testing—matching V_{be} etc.

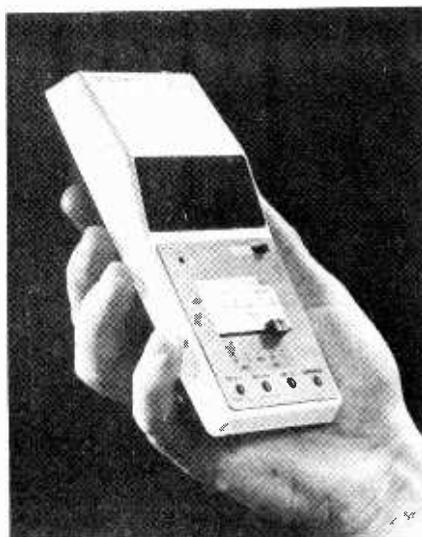Accuracy on resistance measurements is 1.5%, improving to 1% on



the other ranges. A red LED display is used, and auto-polarity is incorporated. Power is derived from an internal 9V PP3-size alkaline or zinc-carbon battery.

The PDM35 costs £29.95 plus VAT, including test leads, protective carrying pouch and operating manual.

Optional extras available are an AC mains adaptor, padded pouch for protection in the field, and a 30kV EHT probe.

Consumer research also influenced the design of Sinclair's new calculator, the "Enterprise". It led them to abandon liquid crystal displays,

increasingly popular with other manufacturers, as "Smudgy, slow and



unreliable'. Instead a new, bright 5.5mm red LED display was developed. Featuring the four standard functions, plus square root, percent and memory, the Enterprise measures 127 × 51 × 19mm (max.) and is powered by a PP3-type battery.

The price is £9.95 plus VAT, including instruction book and carrying case. An AC mains adaptor is available as an optional extra.

Further details on both these products from Sinclair Radionics Ltd., London Road, St. Ives, Huntingdon, Cambs PE17 4HJ.

Cassette deck

Watford Electronics are now supplying, ready built and tested, a stereo cassette deck, which, although not of the supreme highest quality, can boast a very respectable frequency response on Cr02 tape of 80 to 12000 Hz. Compris-



ing a high quality tape transport mechanism, and twin record/playback amplifiers, the TCD 68 is designed to be used in conjunction with an existing Hi-Fi set-up. Correct recording level is achieved by referring to two moving coil meters, while along with the usual cassette tape controls, switches are provided for Cr02/Normal tape, stereo/mono, and oscillator shift. Distortion is said to be around 2% maximum, while W/F is better than 0.25%. Price is £45.50 plus VAT, and if you can't get to the shop, then there's an extra £1.50 p & p.

Watford Electronics, 35 Cardiff Road, Watford, Herts. Tel: Watford 37774

A saw point!

Files and saws don't sound all that electronic do they? but like it or not they're still needed by the electronic enthusiast when filing out holes for potentiometers, and cutting bigger holes for displays etc. Just on the market is a brand new type of tool that combines the features of an awl for making and preparing holes in soft and hard woods and certain plastics, with the features of a rasp for working on metals, ceramic tiles, plastics and wood. Called the RASPAWL, price including VAT is 67p.

Looking very similar to the normal junior hacksaw, the DEEP sawfile



kit differs in that the frame has an extended depth of throat of 6in. This enables the saw to be successfully used on far more jobs than would normally be possible with a regular model. The kit, which is sold in a 'bubble pack' contains the saw frame, two Abrafile blades and a standard junior hacksaw blade. Price including VAT is 70p.

Abrasive Tools Ltd., Abrium Works, Colne Road, Twickenham, TW2 6QE. Tel: 01-894 1273

Transformers galore

Transformers off-the-shelf is the intention of Lascar Electronics and they have formed a new company to provide the service.

The initial range covers 3VA, 6VA, 12VA, 25VA and 50VA types and is available in chassis mounting or printed circuit board mounting formats. The secondary voltages have been carefully chosen to cover most popular applications, but are particularly suited to the construction of regulated power supplies. As an added safety measure, particularly where mains voltages are involved, all the transformers, bar one, are supplied with clip-on terminal insulators at no extra cost.

Providing a transformer can be wound on one of their standard bobbins, with the standard 120V/240V primary, they will wind the secondary, if possible, to your desired specification. Lascar call this their "Blue Riband" service and claim this system results in a drastic reduction in the time required to design, manufacture and deliver special purpose transformers (**Note minimum order 5 transformers**).

A range of transformer development kits is available and is claimed to be

the most convenient method of producing prototype or special transformers. The kits are available in 3VA, 6VA, 12VA, 25VA and 50VA sizes and both clamp-mounting and 0.1in printed circuit board mounting transformers can be constructed. A double-section bobbin with a 120V/240V primary already wound is provided. Bobbin shrouds, a mounting clamp, "E" and "I" lamination sections and terminal insulators make up the kit. The constructor can wind the secondary to his own specification on the empty half of the bobbin. Tapped or independent secondaries can be wound using a suitable insulated copper wire (not supplied). The transformer may then be assembled using the instructions provided, and can be finished off with a varnish dip if required.

A fully-priced brochure listing all their standard transformers and kit details is obtainable from:

Lascar Electronics, P.O. Box 12, Module House, Billericay, Essex CM12 9QA. Tel: 02774 3394.

£42 Per Watt.


If you feel like spoiling yourself for the new year, you might be interested in the "Globetrotter 800" from

Nordemende. According to Nordemende's marketing agents in Aldershot, Hants, this fully portable mains/battery receiver is the "latest thing" in quality portables. It covers 17 wavebands, dealing with FM, MW, LW, three SW ranges from 1.58 to 19 MHz, and 11 spread short-wave bands. The band-spreading is effected via a double superhet stage, a switchable BFO is included, and a product demodulator is active for SSB reception. Unusual features include a key for switching from LW ferrite rod to an external connection for DF "sonde" for radio navigation.

The power unit incorporates a charging unit for accumulator, automatic cut-off for batteries or accumulator when on mains operation, and a large meter is provided to indicate signal strength for fine tuning and a check on battery condition. The receiver, it is claimed, is fitted with a "large, good speaker", through which is provided 7W (music) power.

At £295, this receiver clearly provides wide coverage—at a price! This does include VAT.

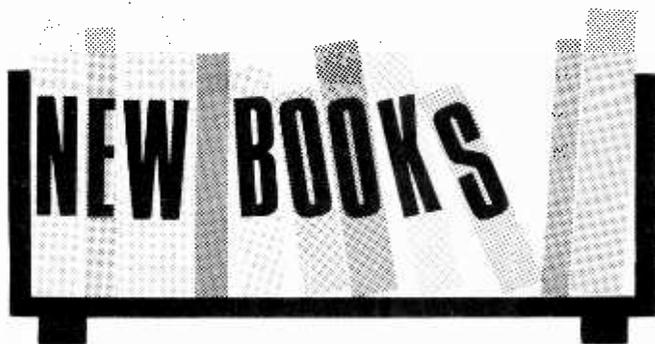Available from:
Vessco Vision and Radio Ltd., Vessco House, Unit 4, Blackwater Way, Ash Road, Aldershot, Hants.



HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS

by R.A. Penfold

Published by Bernard's Ltd., The Grampians, Shepherds Bush Road, London W6 7NF
118 pages £1.20

This very useful little book first describes a basic superhet using two transistors and an IC audio stage plus optional BFO. How the circuits work and how the set should be constructed and aligned is fully covered. The 'How to Build' bit of the title then just dies! The rest of the book contains circuits of alternative front-ends, audio and IF filters, Q-multiplier etc with a description of how they work and ways of connecting to the main receiver. The whole idea is to try all possible combinations and presumably end up with an 'advanced' receiver. However, by no stretch of the imagination could the result be termed 'advanced'. It would still be a basic, albeit effective, receiver.

Other than specifying a dial for the basic receiver no mention is made of tuning dials in general yet the overall performance of any SW set depends entirely upon the quality of the dial mechanism. Excessive backlash, wrong reduction ratio or bad parallax error can ruin an otherwise good receiver. Incidentally, the one facility to be found on any SW receiver worthy of the name is bandspread tuning yet our little book does not even mention the word, as far as I can recall!

The author has based the standard circuits on Denco coils since they are about the only ones available to the home constructor but this does mean that the LC ratio of the tuned circuits is pretty grim on the SW ranges. It must be remembered that the 365pF tuning capacitors are intended to cover the medium and long wave bands as well as the SW bands, accomplished by plugging in the appropriate set of coils. Hardly an advanced design!

On the production of the book itself, symbols such as 'mfd' and 'KHZ' should really not appear today. I would have liked the values of the components to be shown on the circuit diagram of the basic receiver especially as the circuit is necessarily divided up owing to the small page size. The component list is on yet another page. Strangely enough the remainder of the circuits do have the values of components on them! The first circuits show the symbols for the tuning coils and IFTs as if they were mains transformers! Nowhere are they shown as being adjustable by means of their cores.

In spite of these various drawbacks I would still recommend this book to the newcomer to receiver construction as it would give him the very important grounding in practical work that leads to a thorough understanding of receiver operation.

Eric Dowdeswell

OSCILLOSCOPE

Maurice ALLENDEN

VIEWING HOODS

The need for a cathode ray tube viewing hood became apparent when the author developed an interest in slow-scan television and the problem of daylight observation was encountered. Tubes made from thin card met with only limited success but eventually the local Garden Centre provided a solution.

The hoods shown in the photographs were all constructed from black plastic plant pots, which are available in a variety of sizes, both circular and rectangular. Those used in the prototype were of "STEWART" manufacture, 102mm (4in) square.

To provide a mount, the base (i.e. "closed" end) of a pot should be removed, leaving a 32mm (1.25in) rim which is then fixed around the C.R.T. face (Fig. 1). Once in position, it will accommodate a wide range of hoods, two of which are shown in the photographs. The short one would be for general use, whilst the long "radar" type is for viewing in high ambient light.




Construction

A number of pots will need to be purchased, the types and sizes being determined by the C.R.T. In the author's case, a 5FP7 tube of 127mm (5in) diameter was used, so the pot size selected was 102mm (4in) square. Black masking tape was then fixed to the oscilloscope graticule, leaving a square display area of 83mm (3.25in).

Referring to Fig. 1, carefully mark a line 32mm (1.25in) parallel to the open end of the pot—a yellow Chinagraph pencil is well suited for this purpose. Next, take a fine-toothed coping saw (or small hacksaw) and cut across each of the four corners in turn, until the blade goes through the thin plastic. Care is needed with this operation if damage to the pot is to be avoided. Gently saw from each corner until the cuts meet and the pot is divided. The rough edge may now be carefully smoothed and made parallel by means of a fine sanding block. The 32mm section is now fixed to the oscilloscope by making an accurate aperture in the front panel and then bonding with two spots of epoxy resin at each corner.



For existing panels, a small sub-frame of aluminium can be made and the hood mount secured to this. The sub-assembly is then fixed to the instrument with screws (Fig. 1).

Having produced the mount, make up some hoods from other plant pots, cutting and sanding the edges as before. Fig. 2 shows how the various pots are cut. For the larger hood "B," three pots are used. Cut carefully, then use polystyrene cement to butt-joint the sections together; a good, light-resisting design will result.

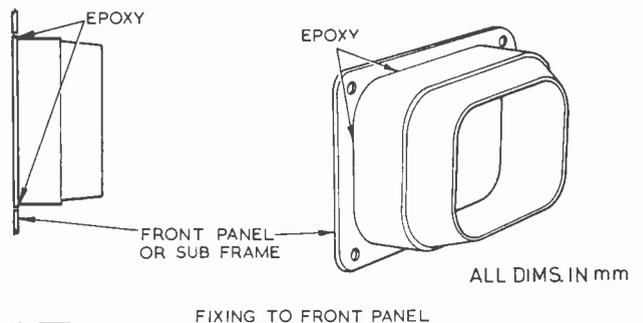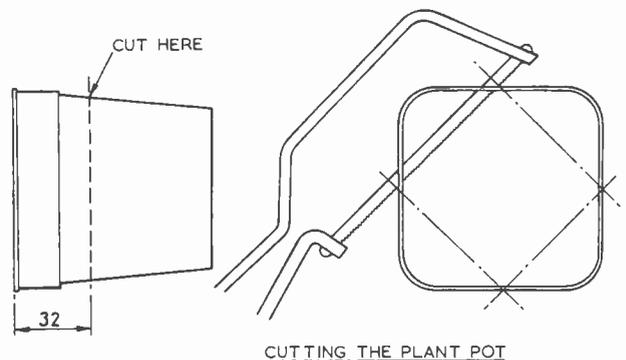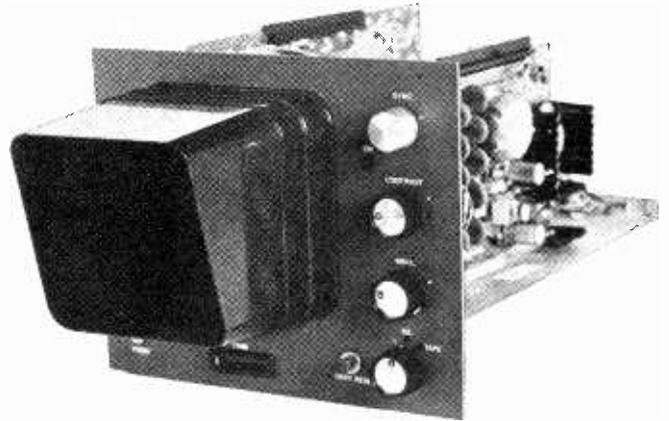

HDO16

Fig. 1: The mount for the various hoods is made from the rim of one plastic plant pot.

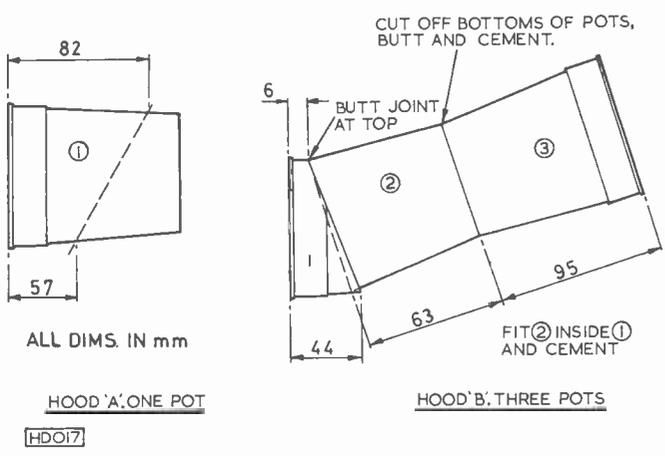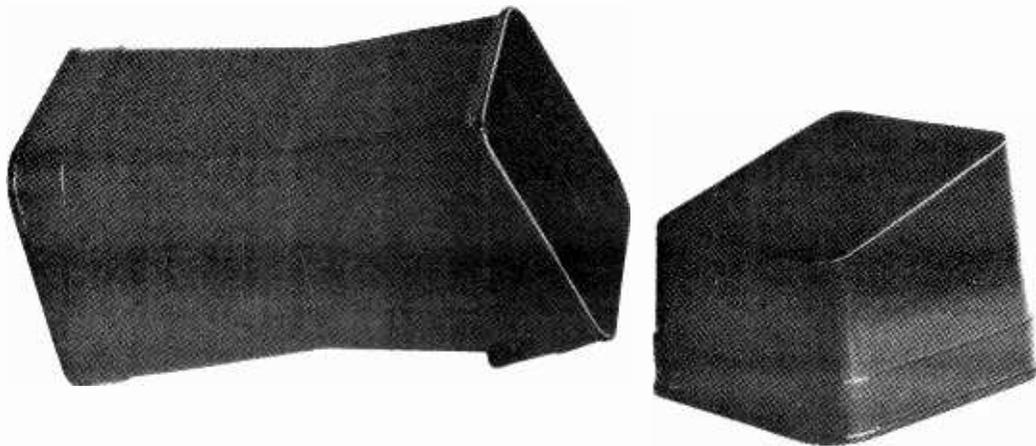

Finish

Further improvement can be achieved by spraying the inside with a matt black paint. If a cellulose-based paint is used it will tend to dissolve the surface of the plastic, giving an attractive matt-etched finish. The outside should be masked during this process for protection.


When fixed to the mounting, the hoods should be a nice, snug fit but if trouble is experienced, small pieces of PVC tape can be applied to the inside corners.


The hoods as described have given trouble-free service with the author's SSTV monitor for some time. With imagination, many purpose-built types of low cost and professional appearance can easily be made.

Acknowledgements


The author would like to thank Bob Weston for his assistance in preparing this article.

Fig. 2: Cutting details of the short hood, using one pot, and the long hood using three.

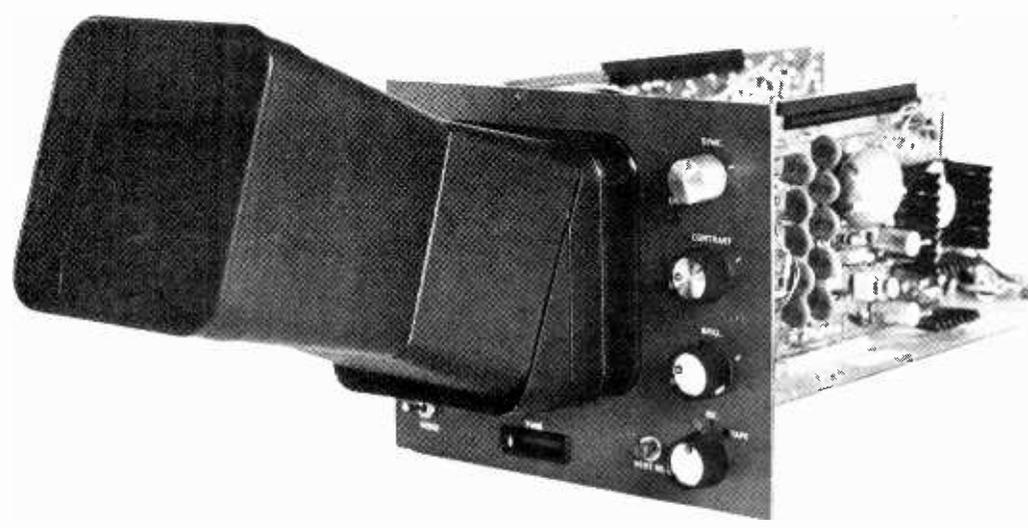

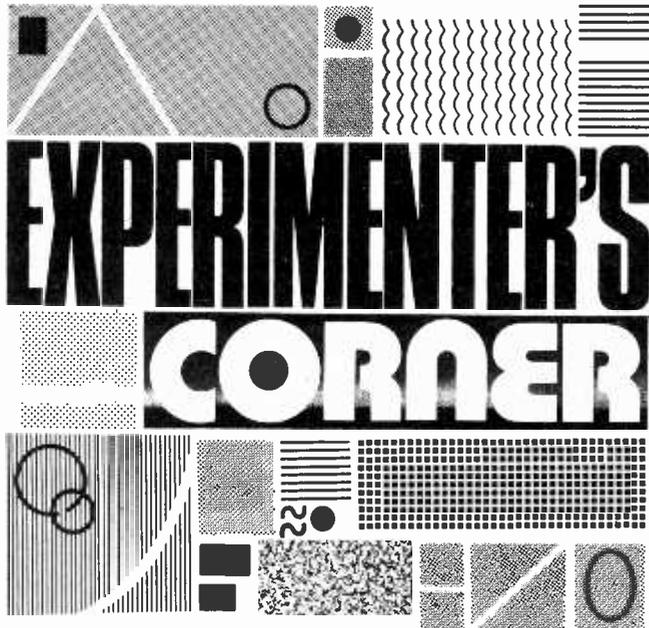


Simple Low-Z Preamp

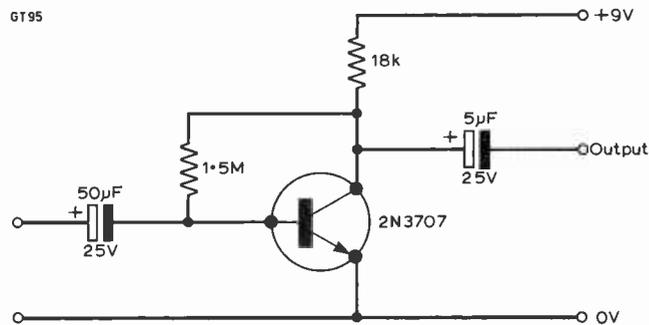

This general-purpose preamplifier is suitable for a wide range of applications where small signals are involved. Its advantages over more complex designs include ease of construction, cheapness of components, and compact dimensions. Employing a low-noise NPN transistor of the 2N3707 type, which is readily available, the amplifier presents a low to medium input impedance, and is therefore suited to moving-coil microphones, magnetic pick-ups, etc. In the circuit illustrated, the gain is fairly low, but a high-gain transistor may be used, such as the BC109, when very small signals are concerned. Supply is 9V in the circuit shown, but this may be varied from about 5V to 25V according to availability, with consequent shift in input impedance.

*D. L. Jones
Denbigh, N. Wales*

Basic 9V Stabiliser

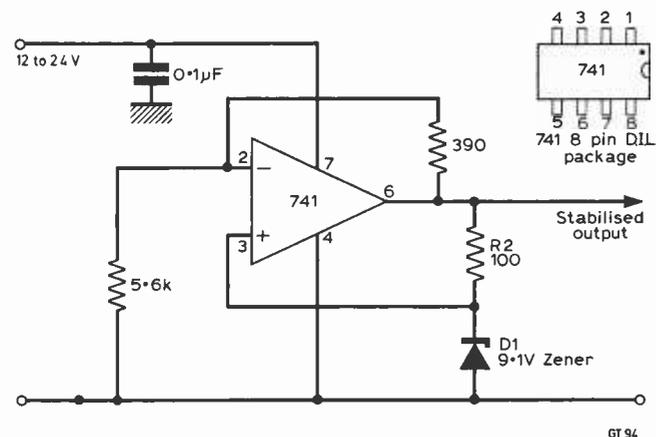

Matching supply voltage requirements of ancillary equipment to those of an established installation can sometimes be a problem. This stabiliser circuit is intended for situations where high power is not a fundamental factor, such as supplying a stereo decoder for use with a tuner unit operating on an 18V rail. It uses the versatile 741 operational amplifier, and may be used with any input voltage between about 12 and 24 to give approximately 9V stabilised (positive) output. Control is effected by means of a 9.1V Zener in the circuit shown, but any type operating within the range 4.7V to 12V will do, according to the output voltage required.

Devices for which the unit is suitable include decoders such as the MC1310, and the Mullard LP1186, or other VHF "front ends".

*R. N. Soar
Mexborough, S. Yorks*

NEXT MONTH IN...

practical WIRELESS

ON SALE FEB. 3RD.

* EXTRA INSIDE!

8~PAGE SUPPLEMENT

PW GUIDE TO AERIALS


~FROM LONG WAVES TO UHF~

Whether you are listening to an amateur in Australia or to your local radio station, the weakest link in the chain is your receiving aerial! Use our Free Guide to ensure that your radio equipment is getting what it deserves, the best in aerials.

ALSO:—

PW EUROPA

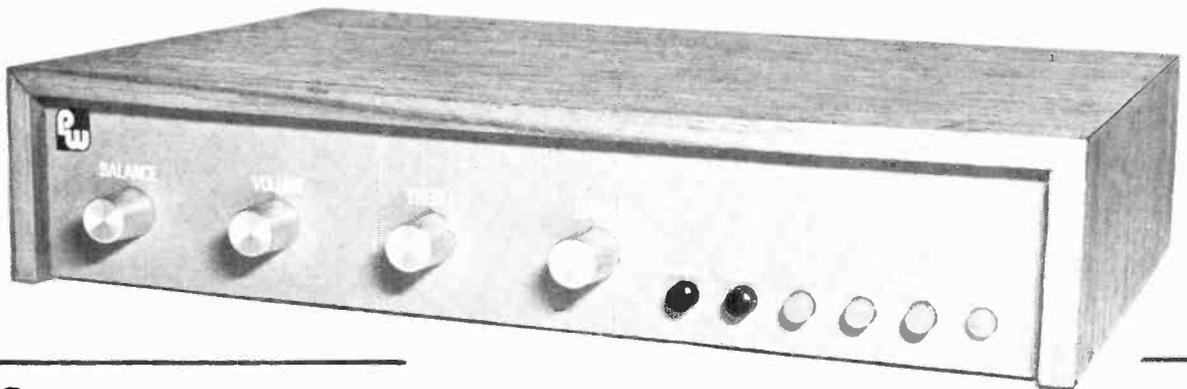The "Europa" stereo amplifier gives an output of 30 watts per channel into 4 ohms. Designed with ease of construction in mind, the Europa has almost all components mounted on a single p.c.b., and uses the case as heat-sink for the output transistors. Inputs are provided for magnetic, ceramic or crystal pick-ups, tape-head and timer.



PLUS:—

Starting next month!

U~DeCnology

Following on from the popular S-DeCnology series, David Gibson describes a number of circuits using a single i.c., each one built on another variety of plug-in solderless breadboard, the U-DeC.

Practical Wireless, February 1978

**DON'T
MISS THIS
ISSUE!**

So you want to pass the R.A.E. (Radio Amateurs' Examination)?

No. 6

John Thornton Lawrence GW3JGA & Ken Mc Coy GW8CMY

This month we are taking a break from calculations and theory to look at block and circuit diagrams and how to tackle these in the R.A.E. We will also be discussing valves and semiconductors and various applications for these in amateur radio equipment.

Block Diagrams

The purpose of a **block diagram** is to show, in the clearest possible way, the arrangement of a basic system or piece of equipment, and to show the signal flow through it. A block diagram can sometimes be so effective that no other explanation is necessary, Fig. 34.

In the block diagram of a piece of equipment, it is important that the path of the main signal is clearly shown and this will usually be from left to right. Any other less important signal entering or leaving the main signal flow should do so at right angles, e.g.

local oscillator and "S" meter, as shown in the super-het receiver block diagram in Fig. 35. Also see Fig. 6.3 in The Radio Amateurs Examination Manual.

However, if two equally important signal paths exist independently and these join to a common stage later on, then these can be drawn one above the other as shown in Fig. 36.

Block diagrams are concerned primarily with signal flow, signal processing, amplification, etc., no account is taken of how the processing is actually carried out, a valved radio receiver and a transistorised radio receiver may look identical in block diagram form although the detailed circuitry can be very different indeed.

When the block diagram is for a complete piece of equipment such as a receiver, then the power supply may also be included, but this is usually shown on its own away from the main operational part of the diagram as shown in Fig. 35.

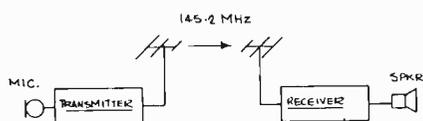


Fig. 34

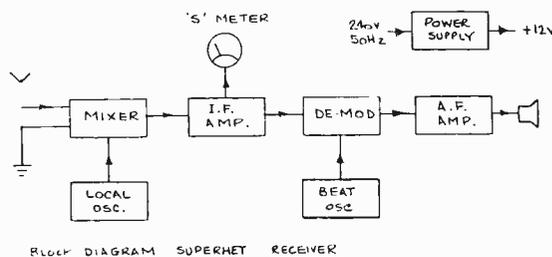


Fig. 35

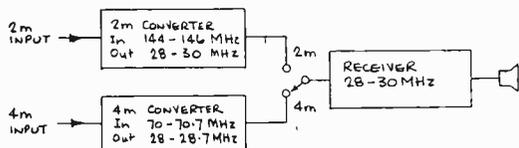


Fig. 36

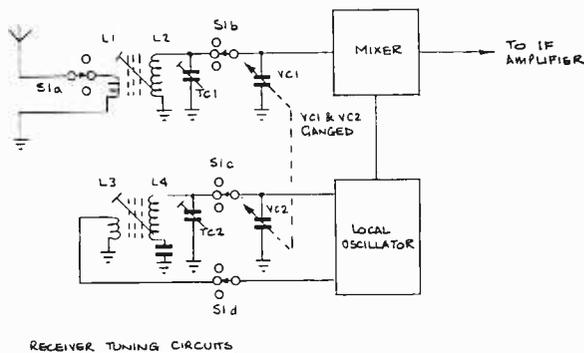


Fig. 37

Block diagrams are easy to draw using just a pencil and ruler, as these have been, but be sure to allow enough space for labelling the blocks. It is better and quicker to label the blocks directly on the diagram, but if this is not possible it will be necessary to give each item a letter, a, b, c, etc., and include a coded list adjacent to the diagram.

All diagrams should be drawn in pencil (H or HB) and if you have a good eraser (Staedler Noris—Plastic) then you can easily make any corrections or reposition something if you need to. Remember, in the exam, time is of the essence, speed and accuracy in drawing block and circuit diagrams only comes with practice, so plenty of practice in drawing a range of standard types of circuits is required, but more about these later.

Moving in a little closer now, you may be required to show a particular stage of the equipment in slightly more detail, but without going to the complete circuit diagram. The best way of doing this is to retain the basic block diagram approach but to show the important signal handling parts as actual components. The circuit in Fig. 37 shows the tuned circuits of a receiver, without being cluttered by biasing resistors, coupling and decoupling capacitors and so on.

Circuit Diagrams

Circuit diagrams are more difficult and more time-consuming to draw and so more care and attention to detail is required here.

The same rules that applied to the block diagram still apply, signal flow from left to right and other signals join and leave at right angles. In addition, we are now concerned with supply voltages and currents. Remember, we are thinking of conventional current (which flows from the positive supply through the circuit to the negative or zero) and this flow will be down the page from the top to the bottom as shown in Fig. 38.

If the diagram contains blocks of circuitry above or below the main central section then these may be considered as separate blocks each with their own supply lines. For example, in Fig. 35 the beat frequency oscillator may have its own positive supply line immediately above its circuit and the zero line below but with the direct current still flowing conventionally down the page.

For the purposes of the R.A.E. it would be convenient to stick to *nnp* transistors throughout as *nnp* transistor circuits have the positive line at the top and relate more readily to valve circuits and applications.

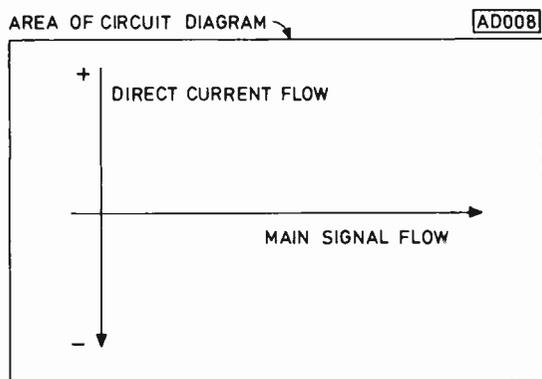


Fig. 38: In a circuit diagram, power supply paths run down the page, signal path across the page from left to right.

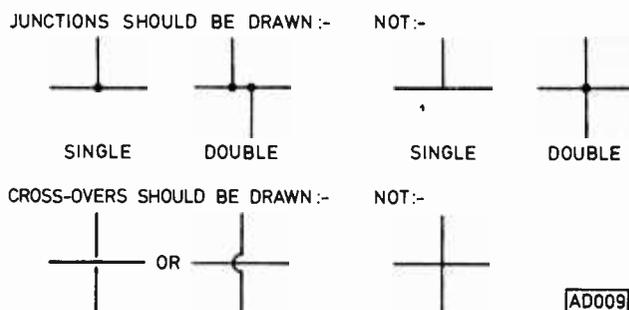


Fig. 39: The best method of drawing junctions is to some extent a matter of opinion.

There is nothing wrong with *pnp* transistors or negative supply lines but it does mean some upside-down thinking when describing these circuits and this is best avoided in the exam. Remember, "*nnp* Rules OK!"

The drawing of a circuit diagram is made easier by a moment or two of mental planning. Think of the parts of the circuit that are to be included, allow about 5 to 6cm spacing between valves or transistors, more where there are switches and coils, less where coupling is direct or very simple. Set an imaginary horizon line across the centre of the page and where convenient, keep the valves or transistors approximately on the line. Some circuits require the valves or transistors to be one above the other, space these so that they fit in conveniently. Provisionally, draw in a zero line and a positive supply line and see if you have enough room for everything vertically and horizontally. If you cannot manage to fit the diagram in horizontally then you can, if absolutely necessary, break the drawing and continue it on another sheet. However, this takes up valuable time, so avoid it if you possibly can.

In both the valve and transistor circuits, the direct current path through the resistors can easily be visualised as flowing down the page with the signal path crossing horizontally from left to right. See also Fig. 1. in the November 1977 issue of *PW*.

If the question requires you to insert typical component values then, to save time, this can be done alongside each component on the diagram. If there is not enough room, then the components must be numbered, R1, C1, etc. and a table of values given adjacent to the diagram. It is a good plan to number the components anyway, because, if you are required to describe the operation of the circuit, then the component can be referred to more readily, as for example, "C1" instead of "the input coupling capacitor"

There are various schools of thought on how junctions and crossovers should be drawn and although we are at variance with some of the excellent professional draughtspersons (including those at *PW*) we think that the methods of drawing junctions and crossovers given in Fig. 39. are less likely to be misdrawn or misunderstood when drawn by the examinee under examination conditions. For your own interest, have a look at circuit diagrams in various books and magazines and see how they do their junctions and crossovers.

The actual drawing of the circuit diagram should be done in pencil using a ruler and ideally a stencil. Radio component stencils are available at most big stationers or shops selling drawing instruments. A typical one made by UNO, is type BB4 at £3.85, but

this may reasonably be considered too expensive to buy just for use in the R.A.E. As an alternative, use a general purpose stencil which has circles, squares and triangles on it. Faber-Castell make a suitable one (Type 943) which is very useful and considerably less expensive.

All the diagrams in this section have been drawn using a ruler and the above-mentioned stencil.



Remember, drawing circuit diagrams takes time, so read the question very carefully before starting. The diagram should be as detailed as required by the question, but no more.

As a guide, the drawing times for the previous diagrams were as follows:—

- Fig. 34. 4 minutes
- Fig. 35. 10 minutes
- Fig. 36. 8 minutes
- Fig. 37. 20 minutes

When you have completed the drawing, check down the page to see that each vertical current path is complete all the way through component, valve or transistor and that the horizontal signal path is also complete whether it be direct or by coupling capacitor or transformer.

Someone said that one picture is worth a thousand words and this could be equally true for a correct and clearly drawn circuit diagram.

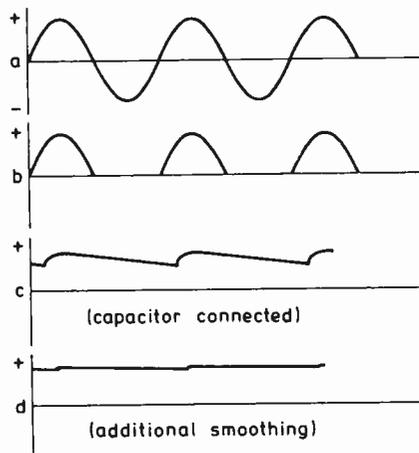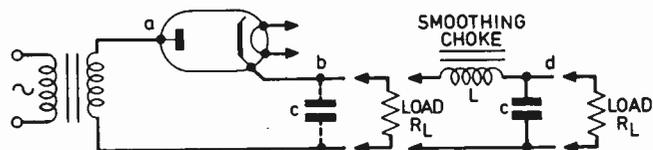

AD011


Fig. 41(a): A half-wave rectifier circuit, with voltage waveforms produced at various points.

VALVES AND SEMICONDUCTOR DEVICES

All the devices that we have discussed up to this point have been what might be called "passive" devices—that is they require no external power source to make them work. The devices which we will be considering next will be of the "active" type.

The Thermionic Diode

Although the thermionic diode has been almost totally superseded by the semiconductor diode in modern radio equipment, a description of its operation will help to show how valves work. Fig. 40 shows the construction of an indirectly-heated diode.


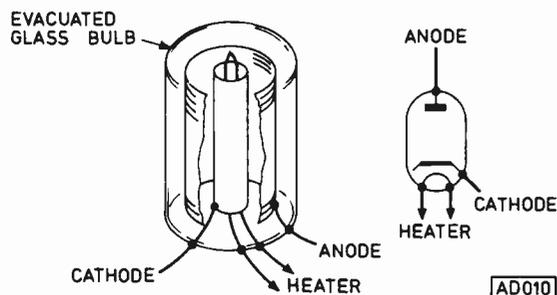


AD010

Fig. 40: Basic construction of an indirectly-heated thermionic diode.

The **cathode** structure consists of a narrow cylinder of nickel, coated with a layer of material which readily emits electrons when heated, in the centre of which is a heater.

The cathode is located in the centre of a hollow cylinder of nickel which forms the **anode**. The whole arrangement is contained inside a glass envelope from which all air is evacuated. Connections for the anode, cathode and heater are brought out through glass-to-metal seals.

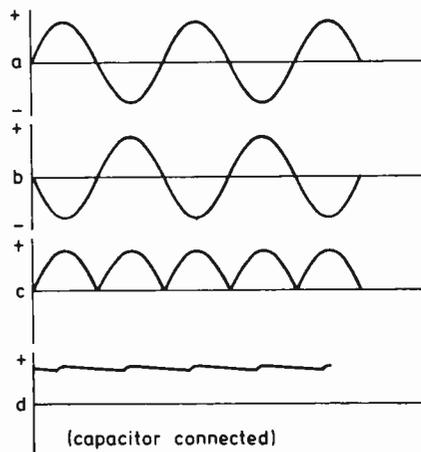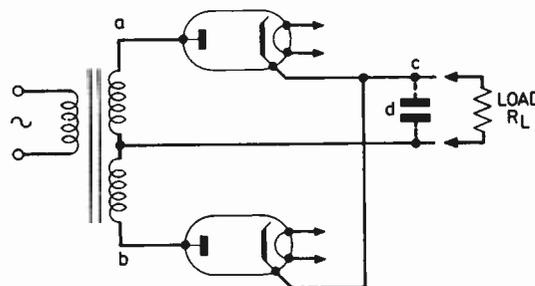

AD012

Fig. 41(b): A full-wave rectifier circuit, with waveforms. The ripple frequency is doubled compared with the half-wave case, easing smoothing problems.

When a current is passed through the heater and the cathode becomes heated, electrons, from atoms of the electron-emissive material, break free from the surface and form a "cloud" around the cathode. If a positive potential is applied to the anode then the electrons which are negatively charged, will tend to move in that direction causing a "current" to flow.

Alternatively, if a negative potential is applied to the anode, the electrons will be confined to the cathode region, since like charges repel. If, however,

an alternating potential is applied to the anode, then the diode will only pass current or "conduct" during the positive excursion of the anode.


The main application of a thermionic diode is in a **half-wave rectifier** circuit as shown in Fig. 41(a). Alternating voltage is fed to the anode and as the diode conducts only when the anode is more positive than the cathode, then current flows only during the positive half-cycles. This results in only the positive half-cycles of voltage appearing across the load.

By connecting a capacitor across the load, to act as a reservoir, the "chunks" of positive voltage can be smoothed to give an almost constant output. The capacitor is charged or recharged on each positive half-cycle and is discharged by a small amount in between each half-cycle by the current drawn by the load. The output voltage waveform is shown in Fig. 41(a).

By adding an extra diode and a further winding to the transformer, in which the voltage is of the opposite phase to the existing one, we can produce a **full-wave rectifier** circuit in which the two diodes conduct alternately on each half-cycle, as shown in Fig. 41(b). This has the effect of doubling the ripple frequency and reducing significantly the amplitude of the ripple across the smoothing capacitor. Further reduction of ripple can be obtained by adding a choke-capacitor filter.

The Thermionic Triode Valve

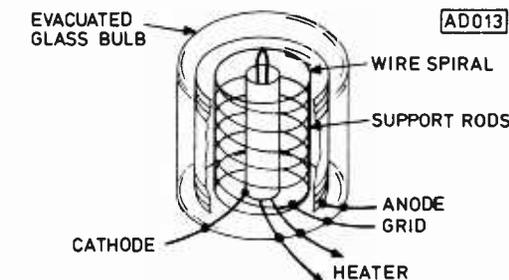The **thermionic triode** (three-electrode) valve is basically similar to the diode except that a "grid" is interposed between the cathode and the anode.



CONSTRUCTION OF TRIODE (BASE & PINS OMITTED)

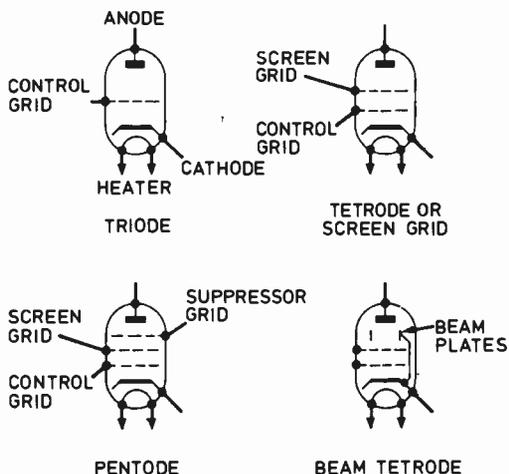


Fig. 42: Basic construction of a thermionic triode, plus circuit symbols for this and some more complex valves.

The **grid** consists of a spiral of wire (usually nickel) arranged around the cathode. The turns are welded to support rods for rigidity, as shown diagrammatically in Fig. 42.

If a positive potential is applied to the anode and the grid is connected to the cathode, electrons will leave the cathode, pass through the grid and accelerate towards the anode, causing the valve to "conduct".

If a negative potential is now applied to the grid, the grid structure will repel electrons and if the potential is great enough it will repel all the electrons emitted by the cathode, thus "cutting off" the flow altogether and making the valve non-conductive.

If however, the grid potential is held or biased a few volts negative, it is possible to control the conduction of the valve by small variations of the grid potential about this value.

There are a few simple relationships that we need to remember about the voltages and currents in the triode valve.

Mutual Conductance

The ratio of the change of anode current (for a fixed anode voltage) to a change of grid voltage is known as the **mutual conductance** or "slope" of the valve (symbol g_m). It is usually quoted in mA/V, sometimes millimhos or millisiemens.

$$g_m = \frac{\text{Change in anode current (mA)}}{\text{Change in grid voltage (V)}} = \frac{\Delta I_a}{\Delta V_g}$$

Amplification Factor

The ratio of the change of anode voltage to the change of grid voltage (for a constant anode current) is known as the **amplification factor** of the valve, (symbol μ or mu).

$$\mu = \frac{\text{Change in anode volts}}{\text{Change in grid volts}} = \frac{\Delta V_a}{\Delta V_g}$$

Impedance

The ratio of the change in anode voltage to a change in anode current (for a fixed grid voltage) is known as the **impedance** or a.c. **resistance** of the valve (symbol r_a).

$$r_a = \frac{\text{Change in anode volts}}{\text{Change in anode current}} = \frac{\Delta V_a}{\Delta I_a}$$

The relationship between mutual conductance, amplification factor and impedance is given by

$r_a = \frac{\mu}{g_m}$ and putting this in the form of a memory aid we have the triangle of Fig. 43. Note that if g_m is in milliamps/volt then μ must be multiplied by 1000.

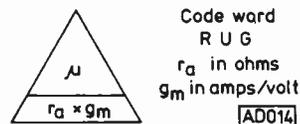


Fig. 43: The Impedance Triangle.

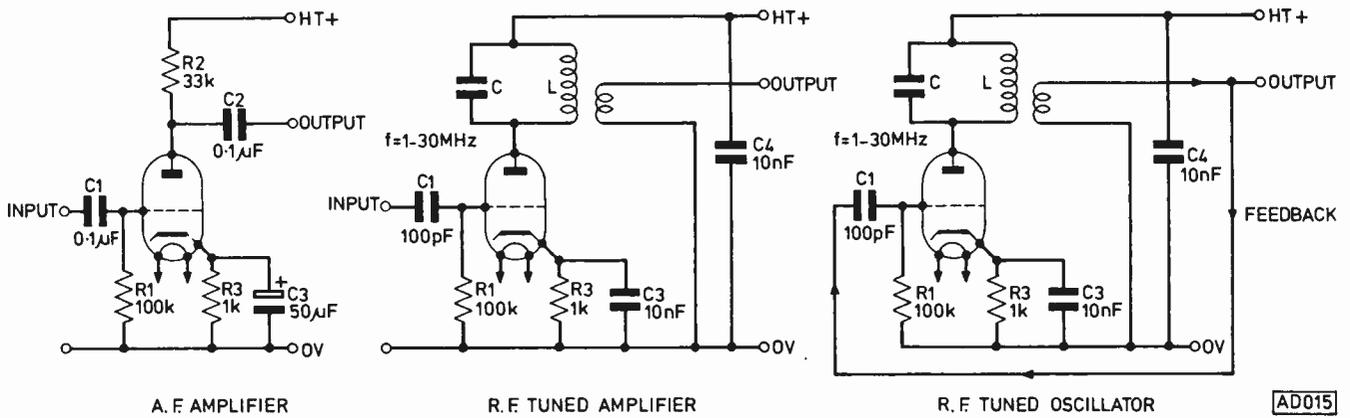


Fig. 44: Basic single-valve circuits for an A.F. Amplifier, a tuned R.F. Amplifier and an R.F. Oscillator.

Tetrodes and Pentodes

The **tetrode** (four-electrode) valve, has an additional grid, known as the **screen grid**, which is placed between the control grid and the anode. This grid, when maintained at a fixed positive potential, has the effect of increasing the amplification of the valve.

The **pentode** (five electrodes) has yet another grid interposed between the screen grid and the anode. This is known as the **suppressor grid**. It is normally connected to the cathode and its purpose is to suppress any secondary electrons which may be emitted from the anode and would otherwise be attracted to the screen grid causing excessive screen current and a reduction in efficiency.

A further improvement in the performance of tetrodes can be achieved by the use of **beam-forming plates**. These plates are arranged in conjunction with the grid structure to focus the electrons emanating from the cathode into a beam, thus reducing the screen-grid current and improving the overall efficiency of the valve. These valves are known as "beam tetrodes".

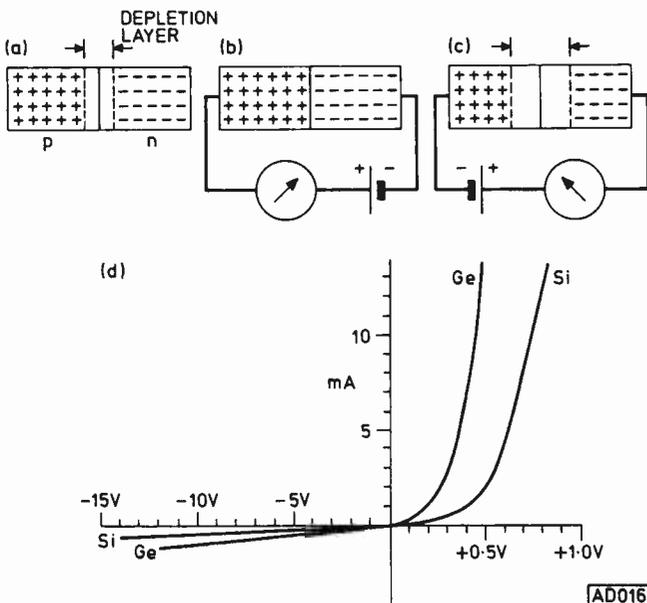


Fig. 45: The semiconductor junction diode (a) without external bias (b) forward biased and (c) reverse biased. In (d) is shown the current/voltage characteristic.

APPLICATIONS OF VALVES

Audio Amplifier

The triode valve in Fig. 44 is used as an **audio-frequency amplifier**. The negative bias voltage for the control grid is provided by including a resistor in the anode circuit. The current flowing in the anode circuit also flows through the cathode resistor resulting in the cathode being raised to a positive potential of a few volts. Since the grid is held at zero volts by R1 then, with respect to the cathode, the grid appears negative.

An audio frequency voltage applied to the grid will vary the electron flow to the anode (the anode current) and the variation of this current through R2 produces an audio frequency voltage across R2 and also at the output terminal. Capacitor C2 is included to pass this amplified audio frequency voltage but not the standing direct voltage on the anode.

The coupling capacitors C1 and C2 and the decoupling capacitor C3 are chosen to have a low reactance at audio frequencies and the values given are typical, as are the resistor values.

Tuned Amplifier

The DC conditions are similar to the AF amplifier but in this circuit the anode resistor is replaced by a parallel tuned circuit. The impedance of this tuned circuit is maximum at resonance and so the amplifier will have maximum amplification at the resonant frequency. The output could be taken from the anode or from a coupling winding as shown.

As in the previous circuits coupling and decoupling capacitors are chosen to have a low reactance at the operating frequency and the values shown are typical.

Valve Tuned Oscillator

By taking the output from the tuned amplifier and returning this to its input (and assuming that the polarity of the signal is correct) then the circuit becomes an oscillator.

Assume a small signal or disturbance occurs at the grid which produces an amplified signal at the output and this is in the same direction as the original signal.

When this is fed back to the grid the signal is amplified yet again and again until eventually the amplitude is limited by the valve being cut off or made fully conductive. The output signal is then an approximation of a sine wave at a frequency determined by the resonant frequency of L and C.

There are many types of oscillator circuits, all basically consisting of an amplifier with a frequency-selective or tuned circuit to define the frequency of oscillation. Look at some receiver circuit diagrams and find the oscillator tuned circuit and the transistor or valve providing the amplification to maintain the oscillation.

SEMICONDUCTOR DEVICES

Several of the reference books listed at the beginning of this series contain sections on the nature and behaviour of semiconductor materials and so we will omit these and pass on to describe briefly the semiconductor diode and transistor.

Semiconductor Diode

A semiconductor junction diode consists of a piece of *p*-type semiconductor and a piece of *n*-type semiconductor joined together as shown in Fig. 45(a).

The *p*-type material has an excess of holes and the *n*-type, an excess of electrons. At the junction, electrons and holes cross the junction and recombine leaving a region virtually depleted of all charge carriers, known as the **depletion layer**. Since the *p*-type has lost a few holes it acquires a slight negative charge and the converse is true for the *n*-type which acquires a slight positive charge. Thus there exists a small reverse bias across the junction.

In Fig. 45 we show the "forward biased" condition. The applied voltage has first to exceed this "built-in" reverse bias before current will flow. For silicon materials this is 0.6-0.7 volts and for germanium, 0.2-0.3 volts. Once this potential has been exceeded current flows readily in the "forward" direction.

The "reversed bias" condition is shown in Fig. 45c. Here the depletion layer has been increased in width, i.e. there is a large region where there are no free charge carriers and only a very small leakage current flows.

Increasing the voltage to a very high level will eventually cause the diode to break down. If the current is not limited in any way this will permanently damage or destroy the diode. The characteristic of a semiconductor diode is shown in Fig. 45(d).

Semiconductor diodes have many applications as rectifiers in power supplies, detectors, demodulators, switches etc.

SEMICONDUCTOR DIODE APPLICATIONS

Power Supplies

Because, unlike valves, semiconductor diodes do not require a heater and associated heater supply they are ideal for use in a bridge rectifier circuit which provides full-wave rectification from a single winding. The current flow through the bridge for each half-cycle is shown in Fig. 46.

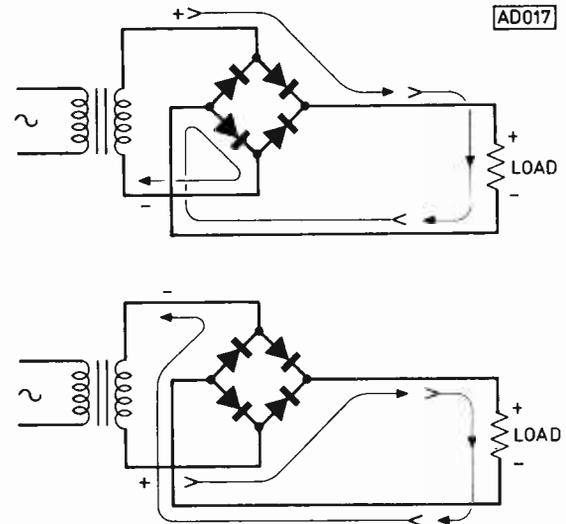


Fig. 46: Current flow around a bridge rectifier circuit.

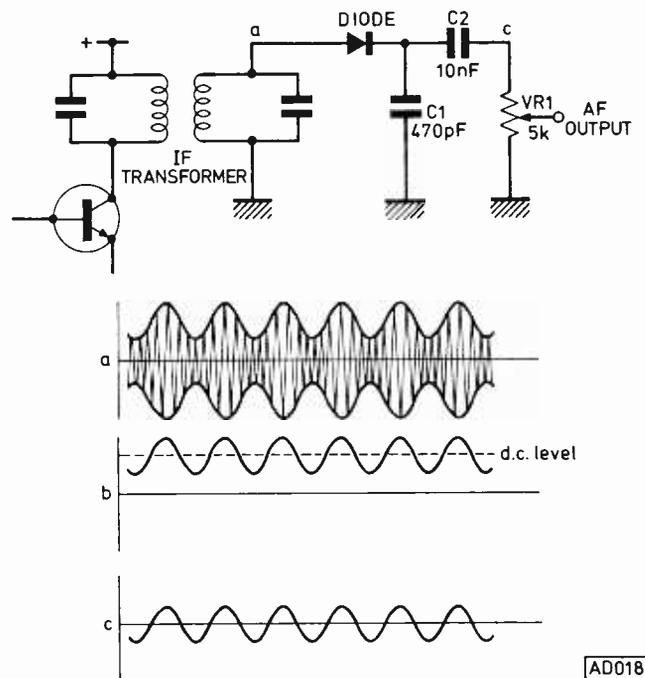


Fig. 47: A diode detector circuit with waveforms produced at various points.

Diode Detector

The circuit in Fig. 47 shows a simple amplitude modulation detector stage. An r.f. signal at the intermediate frequency, amplitude modulated with audio frequencies, is present at "a". At "b" the negative-going section of the r.f. and a.f. waveforms are removed and the a.f. appears varying about a DC level which is obtained by the "smoothing" action of C1 (similarly to DC power supplies). Capacitor C2 removes this DC level and passes the audio frequencies (now varying about zero level) to the load resistor VR1. From this point the a.f. goes through one or possibly several stages of amplification, to the loudspeaker.

Next month we cover transistors, transmitters and modulation.

THE FORCEFUL MR. FLEMING

"If the thumb and first two fingers of the left hand are held at right angles to each other, the first finger represents the direction of the field, the second shows the current, and the thumb points along the direction of the force". So runs Fleming's Left-Hand Rule. Don't feel dejected if you aren't a Russian gymnast and suffer with very stiff wrists (or happen to have a hand in plaster), the whole thing hinges on a bit of confusion regarding Part 4 of our series "Design Your Own", in which Fleming's Left-Hand Rule is quoted.

Several readers have noted that the Left-Hand Rule is traditionally associated with the electric motor principle, while the Right-Hand Rule covers the dynamo or generator principle. Most text books written before about 1970 will be found to follow this convention, indeed, even as late as 1968, Noakes ("Text-Book of Electricity and Magnetism", Macmillan, London) referred without question to "the Left-Hand motor rule and the Right-Hand dynamo rule". Similarly, Morley and Hughes in their perennial "Principles of Electricity" point out the difference, but without mention of alternative implications.

The definitive version is related to electron flow rather than to conventional current flow, and M. Nelkon in "Electricity" (Arnold, London, 1971), outlines on p.245 the background to the apparent divergence of views:

"Fleming's Right-Hand Rule . . . note that the current direction is that of conventional current, or the movement of positive charges, which is opposite to the movement of electrons or negative charges. Applying the rule to Fig. 1 the middle finger points from P to Q. Hence, this is the direction of the induced emf in the conductor. If a galvanometer is joined to P and Q, completing the circuit, conventional current flow is from Q round to P through the galvanometer. Electrons move through the galvanometer in the opposite direction, from P round to Q".

Diagrammatically, the two opposing concepts involved in this one principle may be summarised by Fig. 2. There is of course no reason why, if you are so inclined, you should not reject modern ideas about electron flow, stick to conventional current, and

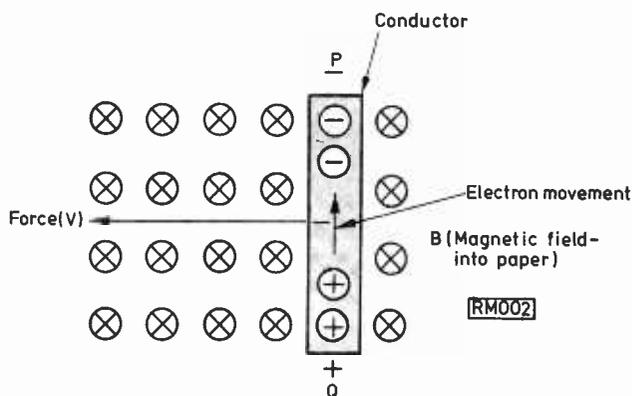


Fig. 1: The application of Fleming's Right-Hand Rule.

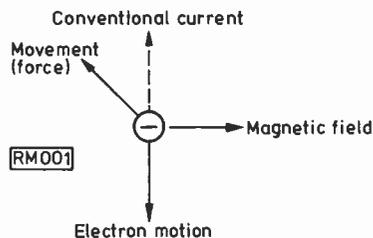


Fig. 2: If electron flow is used instead of conventional current, the opposite "Hand Rule" applies.


ignore the assumption that a motor is a generator "inside out" as it were. In other words, it's up to you how you respond on this one. At least one thing is certain—if the lights go out again all over Europe, it will only be the result of industrial action, and not the sudden unaccountable reversal of a universal principle of physics.

Ted Parratt, with acknowledgements to M. Nelkon, "Electricity".

The Sinclair PDM35.

A personal digital multimeter for only £29.95

(+8% VAT)

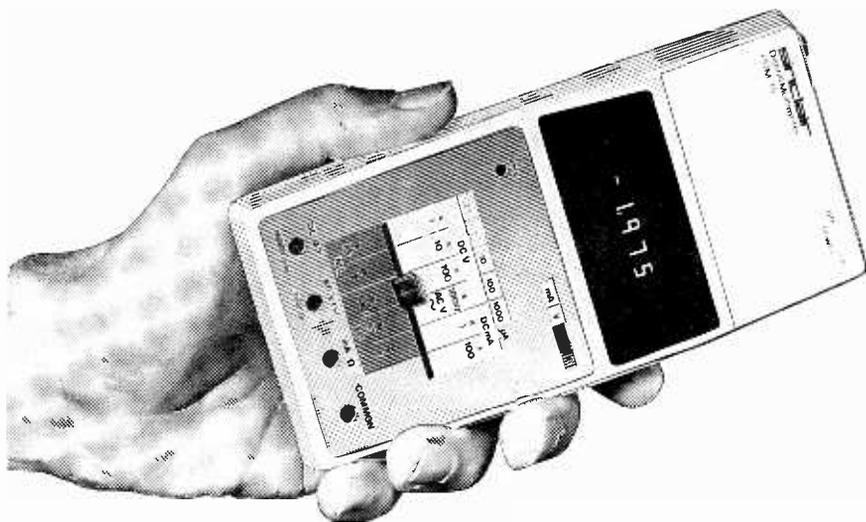

Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

What you get with a PDM35

3½ digit resolution.

Sharp, bright, easily read LED display, reading to ± 1.999.

Automatic polarity selection.

Resolution of 1 mV and 0.1 nA (0.0001 µA).

Direct reading of semiconductor forward voltages at 5 different currents.

Resistance measured up to 20 MΩ.

1% of reading accuracy.

Operation from replaceable battery or AC adaptor.

Industry standard 10 MΩ input impedance.

Compare it with an analogue meter!

The PDM 35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 MΩ is 50 times higher than a 20 kΩ/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

Technical specification

DC Volts (4 ranges)

Range: 1 mV to 1000 V.

Accuracy of reading: 1.0% ± 1 count.

Note: 10 MΩ input impedance.

AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading: 1.0% ± 2 counts.

DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading: 1.0% ± 1 count.

Note: Max. resolution 0.1 nA.

Resistance (5 ranges)

Range: 1 Ω to 20 MΩ.

Accuracy of reading: 1.5% ± 1 count.

Also provides 5 junction-test ranges.

Dimensions: 6 in x 3 in x 1½ in.

Weight: 6½ oz.

Power supply: 9 V battery or

Sinclair AC adaptor.

Sockets: Standard 4 mm for resilient plugs.

Options: AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts – from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/ PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

We'll mail your PDM35 by return!

Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ, England. Regd No: 699483.

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.

Please send me _____ (qty) PDM35(s)

@ £33.00 (inc £2.40 VAT and 65p P&P)

each: _____ £ _____

_____ (qty) De-luxe padded

carrying case(s) @ £3.00 (inc VAT

and P&P) each: _____ £ _____

_____ (qty) AC adaptor(s) for

240 V 50 Hz power @ £3.00

(inc VAT and P&P) each: _____ £ _____

I enclose cheque/PO made payable

to Sinclair Radionics Ltd for

(indicate total amount): _____ £ _____

I understand that if I am not completely

satisfied with my PDM35, I may return it

within ten days for a full cash refund.

Name: _____

Address: _____



sinclair
World leaders in fingertip electronics

PW/2



Handy size Reels & Dispensers

**OF THE WORLD'S FINEST CORED SOLDER TO DO
A PROFESSIONAL JOB AT HOME**

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.



SAVBIT handy solder dispenser

Contains 2.3 metres approx. of 1.22 mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.
Size 5 58p

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits.
PC115 69p
Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.
Size 19A 63p



handy size reels of SAVBIT, 40/60, 60/40 & ALU-SOL solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. mm	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£2.16
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2.46
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£2.16
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£2.16



BIB WIRE STRIPPER & CUTTER

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.

Pat. No. 1443913

Model 8B 97p

SOLDER-WICK



Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 Watt soldering iron. Quick and easy to use. Non-corrosive.

Size 18 97p

Sole U.K. Sales Concessionaires:

Bib Hi-Fi Accessories Limited,

Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ.

Prices shown are recommended retail, inc. V.A.T. From Electrical and Hardware Shops. In difficulty send direct, plus 20p P&P. Prices and specifications subject to change without notice.

Complete digital Clock Kits TEAK OR PERSPEX CASE



"DELTA"
6" x 2 1/2" x 3"

NON ALARM £12.50
ALARM £15.50

FEATURES

- 4 LED digits 1/2" high. Red.
- 12 hour display with AM/PM indication
- Mains frequency accuracy
- Easy to build: all components included
- Beautiful real wood case or Perspex: White, Black, Red, Blue, Green
- Flashes to indicate power cuts

NON-ALARM

Complete kit including case .. £12.50
Ready Built .. £14.50
Module kit excluding case .. £9.50
Ready Built .. £10.00

ALARM

Pulsed Alarm Tone. Automatic Brightness control.
9 minute Snooze. Simple Setting. Complete kit including case .. £15.50
Ready Built .. £17.00
Module kit excluding case .. £13.00
Ready Built .. £13.50

TIMER FACILITY: Stopwatch use up to 9min 59secs .. extra 50p.

EXCELLENT VALUE

- LCD gents watch, 5-function, Backlight. Chrome case. Black strap £15-95
- 4 Function Calculator .. £3-78

NOVUS

GUARANTEED

DISPLAYS: FND 500 1/2" LED £1.19 each: 6 for £6.48
NSB5430 1/2" red LED stick of 4 £4.32 SLT02 1/2" green phosphor stick of 4 £5.40

CLOCK CHIPS: 50253N Alarm 12/24hr. 4/6 digit £5.67

50382N Calendar clock £7.75 MM 5385N 12hr, 4 digit Alarm £4.32
6 Decade Up/Down Counters: 50395/6/7 £9.45

MICROPROCESSOR: Z80 C.P.U. £22.68

Z80CTC £15.70 1702A UV Erasable PROM £11.35
Z80 PIO £15.70 2102NA 1K Static RAM £2.70
UV PROM Eraser £103.00 + £5.00 p. & p. 4KX1 16-pin Dyn. RAM £7.05

RECHARGEABLE BATTERY SET Super Value £8.10

Includes: 4 A.A. (1.2v) Nickel Cadmium batteries (separately £1.08 each)
3/6/9v switched Universal Mains Adaptor with 4 plug connector for most calculators (separately £3.78) plus battery holder.


payment with order to:

BARON (P.W.)

SOUTHVIEW HOUSE, 6 GOWER ROAD,
ROYSTON, HERTS Tel. ROYSTON 43695



SAVE POUNDS

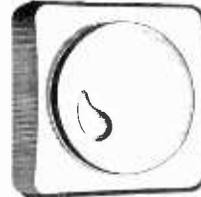

WITH THIS UNBEATABLE OFFER
from Britain's Largest Dimmer Makers

Complete Kit of Parts for our VCL500M, 500W Dimmer Switch, only £1.85, plus p & p 25p. (inc. Vat.) Full Instructions supplied.

BARGAIN COMPONENTS

ELECTROLYTIC CAPACITORS

470 MFD - 6.3V 15p. 1000 MFD - 16V 30p.
150 MFD - 6.3V 17p. 330 MFD - 63V 29p.
470 MFD - 10V 18p. 68 MFD - 6.3V 12p.

POLYESTER CAPACITORS

0.01 MFD - 400V 9p.

THYRISTORS

C106.01 70p. 41 RCS60 £4.50

B.L.12-WAY TERMINAL BLOCK

P.C.B. MOUNTING ... 39p.

POTENTIOMETERS

Pre-set 1MΩ Linear... 11p. Pre-set 4.7KΩ Linear... 12p.
Pre-set 220KΩ Linear... 11p. Pre-set 25KΩ Linear... 19p.
A.B.2 Gang 25 + 25KΩ... 82p. A.B.1 Gang 220KΩ ... 26p.

All prices include VAT. Postage & packing included on all orders over 50p. Under 50p. please add postage. For quick delivery please send cheque or P/O to: — Dept. PW1.

Fotherby, Willis Electronics Ltd.

GLADSTONE TERRACE, STANNINGLEY, LEEDS, LS28 6NE.
Telephone: Leeds (STD 0532) 563373 Telex: 557111

ON THE AIR

AMATEUR BANDS

by Eric Dowdeswell G4AR

It would seem that not all readers of this column appreciate the purpose of the "Log Extracts" item at the end of this blurb each month. I get some lengthy logs, obviously copied with a lot of care, which might contain just one entry that qualifies for Log Extracts. So, valuable listening time is being wasted! The idea is that as most listeners to the amateur bands keep a record of the number of different countries or zones heard, either from a sense of personal achievement or to get various certificates, they need to know of any activity from stations in countries or zones not normally or seldom heard. QSL information is most important and a rare station will usually have a "QSL Manager", frequently in the USA, and his callsign is all that is needed initially.

But, what is a "rare" station? Today, most such stations are "DX-peditions" organised by a group of amateurs to a seldom-heard country, and for a limited period. Unfortunately, like so many other ideas, the DX-pedition is frequently taken to extremes by "activating" remote reefs and islets, often under water for a lot of the time, that could not be considered "countries" by any stretch of the normal imagination. However, there are permanent stations in countries where amateur radio is viewed with a jaundiced eye by the authorities. Operation is intermittent and when a station does come on he could be considered as "rare".

The newcomer to amateur radio cannot, logically, expect to know what is rare and what is not until he has had some experience of the various bands and learned their characteristics. So choose your monthly selection of rare ones very carefully, half a dozen would be a lot!

First, an SOS! **David Birch** of Trowbridge, Wilts., are you there? I have mislaid your last letter and so your full address. If you will write to "G2DYM Aerials" you will hear something to your advantage! See their ad. in any issue of PW. **Les Weeks** of Manchester has been busy with his FRG-7 receiver, particularly on 10 and 15m bands. He comments that he has plenty of spare time "owing to muscular dystrophy, bronchitis and emphysema, but otherwise I'm OK"! Our hobby is probably about the best possible for such unfortunate folk. I do hope, Les, that you will soon be able to take your RAE and talk back to the stations that, so far, you have only logged.

A GM4 call in the New Year is the aim of **John Overton** in Glasgow and he has already decided that a Yaesu FR50B and FL50B set-up will do to start with! John is one of the few readers submitting some loggings on CW. Talking of CW, the award of the month for persistence must surely

go to **Jess Luxton G8GMI**, a member of the RAIBC, who has copied code for at least a couple of hours a day for the last four years and has now passed his test. I look forward to knowing your new call OM!

Bill Stewart of Dundee had had his FRG-7 for just a week when he wrote to me asking a string of questions on amateur matters! As with all newcomers I referred him to the RSGB's *Guide to Amateur Radio*, £1.38 by post, which contains all the answers, just about. Welcome to our world Bill. Another newcomer is **David Greenhalgh** who hails from Poynton in Cheshire. He has been SW DX-ing but now wants to move up to the amateur bands. Good lad, you are on the right track! However, being only 14 he doesn't have that much bread to spare for a suitable RX so if anyone has a spare set going cheap write to David at 24 Park Avenue, Poynton, Cheshire. Must get you active somehow, Dave!

Simon Robinson was also sans RX until he got hold of a version of the famous B40 at a rally. This plus a 100ft "invisible" aerial down the garden has got him going properly, at last. Simon, of Stocksfield, Northumberland, recently appeared on BBC TV's "Swop Shop" and later enjoyed a tour of the studios. He, too, is a hopeful for the RAE next year. **Dave Peck** BRS37621 remains the sole reader reporting on RTTY activity although I am sure that there must be others. He now has a brand-new Creed 7 printer which he celebrated by copying his first ZL in this mode.

From Worcester, **Bernard Hughes** submits a brief letter and log but since he is BRS25901 he is obviously an old hand at the game! Stations logged included 5W1AZ, HH5RB, HP1PS all of which I consider as "rare". He uses an FRG-7 plus dipoles and a 66ft wire. Regular **Brian Harrison** (Hastings) doesn't like turning his AR88 off in case he misses anything on the 10m band! Don't then, if you can afford to pay for the electricity! Or run the oscillator valve heater from a separate transformer that is permanently on, thus eliminating the annoying warm-up drift on this set. Catch of the Month for **Paul Pasquet** of Farnham, Surrey, was KC4USV/MM at the McMurdo Ice Station in the Antarctic, on 20m, on his new HQ170.

Log extracts

P. Pasquet:— 80m VP8OW 20m KC4USV/MM ZK1DR 3D6BP 15m VS6BB UV0EX (Sakahlin Is.) KG4SC 10m A6XB CX8BE FM0FC H18LAP HD1DX ZD8EW

B. Hughes:— 20m P29JS VU2LQA 5W1AZ 15m FM0FC HH5RB H18FEG HD1DX KZ5PM VP2MF VP2MUU 10m PY2CSS ZE6JC ZS6AYW

B. Harrison:— 20m CE0AE (Easter Is.) 15m DU2GL 10m A4XGB CW0A (Uruguay) EP2RL FG7AX FM7AV HD1DX (Ecuador) H18XDJ HP1PK HK0QA (San Andres) OA4M OY1A PZ1DP TA1ZB VP2MSA VP8LP VK6HK ZD7HH 3D6BE 5T5ZR

J. Overton:— 40m CW VK3AE ZL3GQ 20m PJ2FR TR8GB VP8PJ YN1KL FG7AR/FS7 FM7WV FP8DX

D. Peck:— 20m RTTY EA8IY JA4ONZ UA9PP VE1AA VK2SG VK4YS VK6IF YU3EM ZL2AQZ 4X4MR 7X4MD 9H1ET 20m KG6RT KL7BUY ZL3GS 6W8LZ

All loggings are SSB unless indicated otherwise.

BROADCAST BANDS

SHORT WAVE BROADCASTS

by Charles Molloy G8BUS

It was with regret that the writer listened to the final edition of DXers Calling from Radio Australia. On the air weekly without a break for the past 31 years, this programme finally came to an end on 20 October, though there will be a segment for DXers in Club Forum, which is broadcast at the same times one day earlier, Fridays at 2040 and Saturdays at 0240, 0840 and 1440. On a brighter note, Radio Nacional Espana now has a weekly programme for DXers in its European broadcasts. It can be heard on 7155, 9505 and 11840 kHz on Sundays towards the end of the English transmission. Listen around 2215 GMT.

Harold Emblem (Mirfield) sends news of the Voice of Turkey which is now on 7175 as well as 9515 with its nightly programme in English which starts at 2200. There is a DX programme in English on Monday to Friday at 2230. Harold logged the new channel at 2300 using his Eddystone 730/4. **G. A. Powell** (Lichfield) has been trying the short waves with an old Beethoven domestic set connected to a 40ft length of wire dangling from a 12th floor window (is this safe? A whip aerial on the window would probably give as good results). DX heard with this set-up between 2000 and 2330 included All India Radio and HCJB Ecuador both on the 25m band. The Voice of the Andes, HCJB, Quito Ecuador is operated by World Radio Missionary Fellowship and reports should go to Casilla 691, Quito, Ecuador. DX Party Line, from HCJB is now on the air on Mondays, Thursdays and Saturdays at 2000 on 11955 in the 25m band and 15300 in the 19m band.

"I have tried unsuccessfully to receive Latin American stations and I wonder if you can help me" writes **John Larkin** from Clonmel, Co. Tipperary. John uses a Philips 5-valve receiver with either an 80ft loft aerial or a TV aerial, and his log contains The Voice of Turkey on 9515 at 2225, Radio Havana Cuba on 17885 at 2025 and Radio Australia on 9520 at 0745. Listen for Latin America from 2100 in the evening on the 31m, 25m and 19m bands. On 31m look for Radio Aparacida Brasil on 9635, La Voz de Chile on 9680, Radio Rio Mar Brasil on 9695. On 25m listen for Radio Clarin, Dominican Republic on 11700, Radio Globo Brasil on 11805, Radio Brasil Centro on 11815, Cap Haitien in Haiti on 11835, Radio el Espectador Uruguay on 11835. When conditions are favourable many Latin Americans can be heard between 2100 and midnight on these bands.

It is on the Tropical Bands though, especially 60 metres (4750 to 5060kHz) that Latin America dominates the scene, for it is here that large numbers of low to medium power locals operate, and when there is a path of darkness to the UK they can easily be picked up here. Listen from 2300 onwards through the night for Radio Popular Ecuador on 4800, Radio Clarin, Dominican Republic on 4850 (in English Monday—Friday at 2330), Radio Universo Venezuela 4880, Radio Progreso Honduras 4920, Ecos del Torbes Venezuela 4980, Radio Sutatenza Colombia 5075.

Fred Ainslie's main interest is in the Tropical Bands since "there are no jammers or megawatters and West Africans and South Americans are regulars". Using a homebrew triple conversion receiver he reports hearing VLM4 Brisbane Australia on 4920kHz on several occasions just after dawn (must have been on the long route across the Pacific!), Radio Singapore on 5010 and 5050 (both channels carry the same programme which makes identification easy) and Burma on 4725 closing down in English at 1500. DX from Africa includes Lagos on 4990, Accra on


4915, Mauritania on 4845, Congo on 4765, ELWA Liberia on 4770, Dakar 4890, Benin 4870, Ivory Coast 4940, Togo 5047, all between 2100 and 2300.

"Any gen on Indonesian stations, are they still on the short waves?" asks Fred. Indeed they are. On the International Bands RRI is listed as broadcasting daily in English at 2330 on 9710 and 11970, though the writer has not managed to log it on either channel. On the Tropical Bands, though, there are plenty of Indonesian locals which can be heard in the UK during two time slots daily; from 1400 until sign-off at 1600 and again from sign-on at 2200 until fade-out after midnight. Search on 60m for Ujung Padang on 4719, Medan 4763 and Jakarta on 4774 during the afternoon at this time of year, and for Semarang on 3935 (75m band), Jakarta on 4805, Banda Aceh 4954 and Padang on 4985 in the late evening.

Tropical Band DXers will be interested in the Tropical Bands Survey, which is a 27-page booklet published annually in June, by the Danish Short Wave Club International. It contains a listing of all broadcasting stations in the range 2000 to 5900kHz, including transmission times where known. Stations are classified as Regularly Reported, Seldom Reported, Not Reported but known active, Possible Inactive, and there is information about Indonesian Provinces and Special Districts. Write to the DSWCI, Greve Strandvej 144, DK 2670 Greve Strand, Denmark enclosing 5 International Reply Coupons which are obtainable for 25p each at main post offices, for a copy of the Survey and details of club membership.

Ian McLean, Port Glasgow, has a Worldwide 9-band receiver purchased in Canada, which when connected to a 100ft long wire via a Codar PR40 Preselector pulled in Radio Jerusalem on 9090 at 2000, Cairo on 9495 at 2200, All India Radio on 9590 at 2202, Pakistan on 15110 at 1000, Radio Havana 17885 at 2110 and Radio Australia on 21570 at 0928. (The Address of Radio Australia is PO Box 428G, GPO Melbourne 3001, Australia). Ian has been trying to log Radio Afghanistan and NHK Japan. Try 15365 or 15195 at 1130 for Afghanistan in English in the International Service, or for the Home Service from 1530 until 1740 on 4775kHz in the 60m band.

Radio Japan can be heard in English between 0800 and 0830 on 15325kHz in the 19m band. On Sundays there is Tokyo Calling at 0810, followed by DX Corner at 0820. This transmission is also on the 16m band, though the frequency was not mentioned over the air and it could not be heard by the writer. Much louder reception was obtained, in Japanese at 0755 on 17795 and 17825 followed by the interval signal at 0800 and then talk in Chinese. According to a recent report in Sweden Calling DXers, Radio Japan intends to build relay bases in the Mediterranean and Caribbean area in order to improve reception in Europe and the Eastern United States.

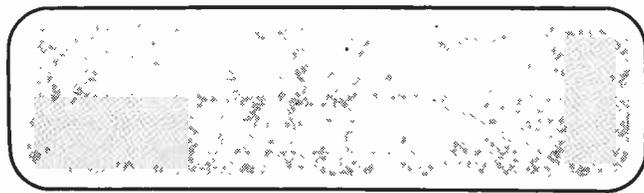

MEDIUM WAVE DX


by Charles Molloy G8BUS

A good log of Asiatic and American DX comes from Booterstown, Co. Dublin where **Mike McGovern** uses a Philips BX48A receiver along with a home-made pre-selector. Stations heard were Taipei in Taiwan, on 600kHz at 2100, Bangkok on 830 at 2300, Fukuoka Japan on 1410 at 2100, Iba in the Philippines 1470kHz at 1600 and Radio Nacional in Paraguay on 920 at 0130. Also KOMO in Seattle on 1000 at 0630, CHQM Vancouver on 1320 at 0530 and KFBK Sacramento on 1530 at 0430.

Although Mike has heard and verified 25 of the 50

LOOK! Here's how you master electronics.




...the practical way.

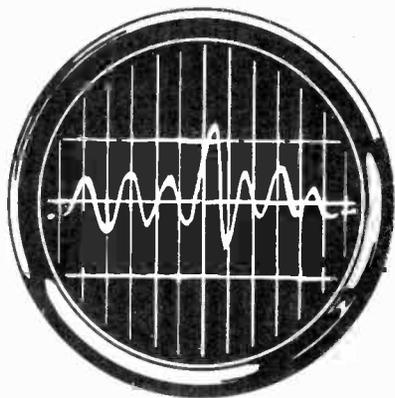

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

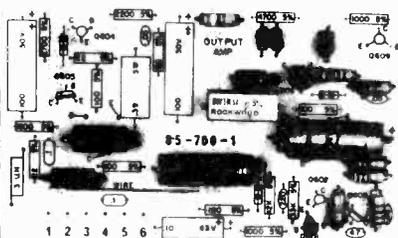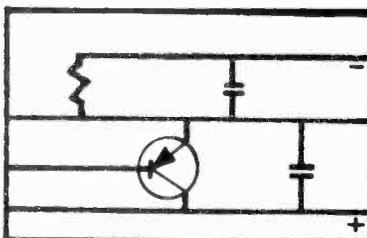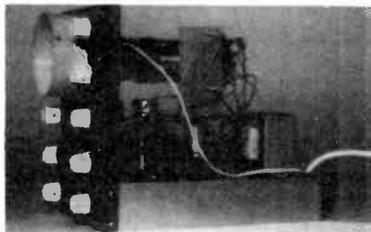All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



1 Build an oscilloscope.


As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3 Carry out over 40 experiments on basic circuits.

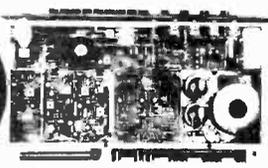We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v etc.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free!

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____


ADDRESS _____

WB 2

Block caps please

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for ALL subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE, P.M.G. Certificates; the R.T.E.B. Servicing Certificates, etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

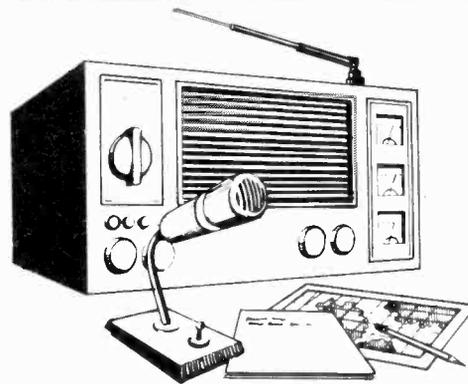

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

WL 2

MAIL ORDER DEPT:-

CRESCENT RADIO LTD

ST. MICHAELS TERRACE, WOOD GREEN,
LONDON, N22 4SJ

TELEPHONE: 888-4474

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000 WATT PER CHANNEL.
Three channel: Bass, Middle, Treble.
The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display.
Full instructions supplied or S.A.E. for details.
Fantastic Value at £20.00 + 8% VAT.

LOUDSPEAKER SELECTION + 12½% VAT

2½" 8, 40 and 75 ohm at £1.10
(Please state which impedance is required)
5" 8 ohm CERAMIC at £1.70
8" GOODMAN'S Audiom 8PA 8 ohm 15w at £5.25
10" 'ELAC' Dual Cone 8 ohm 10 watt at £4.75

EFFECTS PROJECTOR "150" (150 watt)
Ideal for disco work, this versatile machine takes a range of accessories and is of a sturdy metal construction. Comes complete with bulb and 6" Liquid Wheel. Ready to use.
A bargain at £34.00 + 8% VAT.

PIEZO ELECTRIC HORN UNITS 100 watt
New High Quality, High Power Tweeter. No Xover required. Freq. Response: 3.8KHz to 28KHz. Spec. Sheet sent on receipt of S.A.E.

OUR PRICE: £27.80 each + 8% VAT.

ACCESS AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED
ALL PRICES INCLUDE POSTAGE—PLEASE ADD V.A.T. AS SHOWN—S.A.E. WITH ALL ENQUIRIES PLEASE.

Personal callers welcome at: 164-166 HIGH ROAD, WOOD GREEN, N22. Phone: 888-3206
and 13 SOUTH MALL, EDMONTON N9 Phone: 803-1885

POWER SUPPLY UNITS + 8% VAT

PP1—Switched 3, 4½, 6, 7½, 9, 12v at 500mA with on/off switch and pilot light. Approx. size: 130 x 55 x 75mm. ONLY £6.00.
PP2—Switched 6, 7½, 9v at 300mA. This is a sealed, moulded unit fitted with a 3 pin 13A mains plug. Approx. size: 75 x 55 x 45mm. ONLY £4.00.
PP3—DC/DC Power supply for cars. Switched 6, 7½, 9v at 500mA from 12v DC input. Approx. size: 125 x 68 x 40mm. ONLY £6.25.
PP4—Stabilized Power supply. Switched 3, 6, 7½, 9v at 400mA with on/off switch and pilot light. Approx. size: 115 x 78 x 55mm. ONLY £7.00.
PP5—Heavy duty 12 volt power supply. 1.5A at 12 volt. Approx. size: 165 x 90 x 90mm. ONLY £8.00.

ALUMINIUM BOXES + 8% V.A.T.

AB7 = 5½" x 2½" x 1½" = 88p
AB8 = 4" x 4" x 1½" = 83p
AB9 = 4" x 2½" x 1½" = 88p
AB10 = 5½" x 4" x 1½" = £1.00
AB11 = 4" x 2½" x 2" = 88p
AB12 = 3" x 2½" x 1½" = 75p
AB13 = 6" x 4" x 2" = £1.00
AB14 = 7" x 5" x 2½" = £1.20
AB15 = 8" x 6" x 3" = £1.79
AB16 = 10" x 7" x 3" = £1.88
AB17 = 10" x 4½" x 3" = £1.68
AB18 = 12" x 5" x 3" = £1.86
AB19 = 12" x 8" x 3" = £2.34
(please note: all sizes are approx.)

BARGAIN TRANSFORMERS

240v primary, 12-0-12v 500mA secondary. Approx. size: 60 x 40 x 50mm. Fixing centres 75mm. PRICE: £1.80 + 8% VAT. Also available Mains transformer with 18v 500mA sec. Price and size same as above.

SECURITY SUPERMARKET

WE HAVE STOCKS OF EVERYTHING YOU NEED.
CALLERS WELCOME. OPEN 6 DAYS
EXPRESS POSTAL SERVICE
FREE CATALOGUE SEND S.A.E.

Complete Kit for House £54.00 inc. VAT plus postage
Control Unit 1006B £19.50 plus £1 p&p
(mains/Battery complete unit)

MAGNETIC CONTACTS	75p	TAMPER JUNCTION BOXES	24p
MATS LARGE 28" x 15"	1.20	VIBRATION DETECTORS	1.74
STAIR SIZE 6" x 24"	1.10	DOOR LOOPS COMPLETE	59p
WINDOW FOIL 33 M & S	2.45	BELLS & SIRENS FROM	6.00
KEY SWITCHES	1.95	BELL COVERS FROM	6.00

ELECTRONIC CAR ALARM ONLY £5.00.


Please add VAT 12½%, Post 70p min.



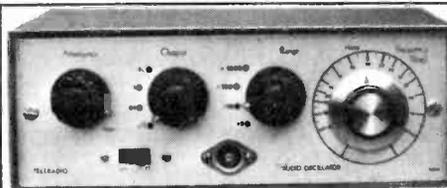A. D. E. (SECURITY) CO.,

217 WARBRECK MOOR
AINTREE, LIVERPOOL
TEL: 051-525-3440

STOP PRESS! Trade Price List Available
Applications on Official Stationery only



**HIGH QUALITY
Very Low
Distortion
Audio Signal
Generator**
AN IDEAL INSTRUMENT
FOR HI-FI TESTING

Based on a Linsley Hood design.

PRICES, assembled instrument, plastic case £23, metal case £26. (Kit, £19.50). Tax extra 8%, P.P. and Ins. £1.

Specification. Frequency range: 10 Hz-100kHz in 4 steps. Output: 10mV-1 volt in 3 steps. Sine- and Square-wave forms: Dist. below .02%. Attenuator: Powered by 9V battery.

Other instruments: Millivoltmeter, Frequency Meter, Reg. P.S. Units. THD Analyser. Also Hi-Fi Amp kits 10-100 F.M. Tuners, Kef Speaker Units.

S.A.E. for further information to:

TELERADIO ELECTRONICS (PW)
325, Fore Street, Edmonton, London, N.9. Telephone: 01-807-3719.

states of the USA he has not been successful with Alaska and he suggests the reason might be that the Great Circle path from his QTH to Alaska passes over the north magnetic pole which is in Bathurst Island. This of course is the reason why Alaska and parts of the Pacific are not logged in the UK. In the vicinity of the north magnetic pole absorption of medium wave signals is high and it is this factor rather than distance that prevents world wide reception on the medium waves. DXers in New Zealand and Australia are able to pick up medium wave stations in Europe and it is only the high level of QRM that inhibits reception in the reverse direction.

Another good log, this time from **Fred Ainslie** of Hartlepool, who uses a homebrew receiver and a 100ft long wire. He had modified the receiver so that the second IF is now 100kHz. This gives very good selectivity but has degraded the sound quality. Detuning slightly to either side of the carrier should improve the audio. Fred mentions the 1000kW transmitter in Calcutta on 1130kHz which he has heard regularly signing on at 2145 with the All India Radio theme tune followed by a programme in Chinese.

Highlights from a very comprehensive log include two Asiatics, Quetta Pakistan on 750kHz and Hyderabad India on 1010; four from the Caribbean, St. Vincent on 705, St. Lucia on 840, ZDK Antigua on 1100 and Martinique on 1310 and four Africans, Gambia on 648kHz, Dakar 764, Sierre Leone 1205 and Libreville, Gabon on 1554. All heard between 2300 and 0100 GMT.

David Brooks of Redruth in Cornwall asks for information about receiving far-off stations on the medium waves. First, there must be a path of darkness between transmitter and receiver. There is no DX to be heard during the day on the medium waves! The main obstacle to MW DXing in the UK is interference (QRM) as the band is overloaded with Europeans, many of whom stay on the air all night.

A communications receiver used with a loop aerial will go a long way to reducing QRM but a careful study of station schedules can also help. A number of Europeans do sign off at night, usually around 2300, but on Saturdays many are on extended schedule, so Saturday is actually the worst evening for DXing. On Sundays signing-on times are usually later than during the week and this applies to the BBC whose domestic services are up to one hour later in starting than on other days. Sunday therefore offers quite an advantage to the DXer who listens around sunrise.

A careful study of the European band plan, which incidentally will change next November, will pay big dividends. In Europe, stations are on channels separated by 9kHz (apart from near the band edges) while in other parts of the world the separation is 10kHz and the channels are also on multiples of 10kHz, i.e. the last digit is a zero. It follows from this that at intervals of 90kHz the channels of the two systems coincide and at these points DXing will be difficult. These are 620kHz, 800, 890, 980, 1070, 1160, 1250, 1340, 1430 and 1520kHz. There are other parts of the band where the separation between the closest European and possible DX channels is 4kHz. These frequencies occur in pairs such as 660kHz and 670kHz, 750 and 760, 840 and 850 and so on through the band. Baghdad is on 760kHz which lies between the European channels 755 and 764 and consequently it is logged frequently by DXers in the UK.


A few DX stations operate on what US DXers call a split channel—the last digit is a 5. St. Vincent on 705 logged by Fred Ainslie is an example of a “split” which lies between 701kHz and 710kHz, both heavily occupied by QRM. Studying the European band structure and searching for holes where DX may be found, plus a study of European schedules, will pay off in a big way for the MW DXer who lives in the UK. It may also help to explain to the newcomer to the hobby how quite exotic DX such as Japan, India and Latin America can be heard on occasion on the medium waves.

Derek Taylor (Preston) has been “doing a little experimenting” with loops recently. He fixed up two turns of wire the complete circumference of the room, which in practice is an 8 by 12ft loop. The turns should be vertical, not horizontal. The position of the fixed loop is roughly NE/SW and its effect on the signal strength of Latin American and Caribbean stations was remarkable. When listening to ZDK (1100kHz) on a 40in loop the station could just about be copied, but when the large loop was used a gain of some 10 to 15dB was obtained, while with Radio Margarita, Venezuela on 1020 an attenuator had to be switched in.

The rig in use is a Yaesu Musen FRG7 communications receiver. Derek says that although not very versatile and a little prone to QRM, his large fixed loop could make the difference between a station being unreadable and loud enough at least to get enough for a reception report. This type of aerial cannot be used with a transistor portable or other receiver that has its own internal aerial.

Two YENED (Greek Armed Forces) stations are mentioned in Derek Taylor's log. The 200kW transmitter in Athens on 980kHz can be picked up with a loop as the strong Arabic station (Algiers) that shares the channel, can easily be nulled-out. The other is Thessaloniki on 1178 which is usually swamped by Horby in Sweden and in this case a loop is of little help as the two stations are roughly on a reciprocal bearing from the UK. Horby though, signs off for half an hour from 2130 to 2200, between the end of its domestic and the start of its international service, providing a time slot when the Greek station can be heard loud and in the clear.

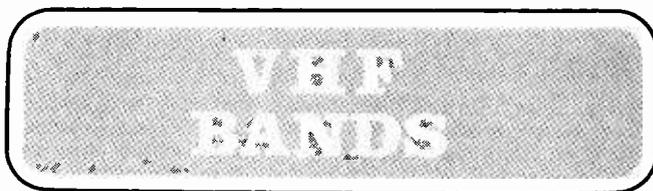Fourteen-year-old **Stephen Cook** has a Realistic DX160 communications receiver coming his way at Christmas and he would like to hear from fellow users. Write to Squirrels Leap, Bonville Chase, Altrincham, Cheshire, WA14 4QA. Postage will be returned.



by **Ron Ham BRS15744**

Congratulations to a frequent contributor, **Alan Baker**, formerly G8LGQ, who, having passed his morse test now sports the callsign, G4GNX. Alan plans to install HF gear both at his home in Newhaven and in his car, and will no doubt chalk up more super DX to add to his already spectacular VHF record. His first HF QSO was with an IT9 on 20m using the Mid-Sussex Amateur Radio Society's club station at Burgess Hill, and, a few days later, he made his first CW contact, from home, on 2m, with G6OX in Surrey and feeling happy with a key, his next QSO was, of course DX; a 559 on 2m with ON4VN.

It was Alan's regular reports that convinced me of the value of the repeater network for propagation studies, which prompted me to buy an FDK TM-56B, 12 channel plus 4 scan, FM monitor receiver, and its arrival coincided with the tropospheric opening which began on October 25th. The origin of this disturbance can be traced back to midnight on the 22nd when the atmospheric pressure gradually increased from 30.0in to 30.25in by midnight on the 24th, and then rose sharply to 30.4in at noon on the 25th where it remained for 24 hours and began to fall at midday on the 26th.

At 1016 on the 25th, a signal from the Bristol Channel repeater, R6, opened the squelch on my new toy, fed with a dipole 30ft AGL, and around the same time there were

539 signals on 70cm from GB3EM and GB3SUT. During the afternoon, G4GNX heard a Lancashire station operating through the Kent repeater, and, throughout the following day, I received strong signals from the repeaters in Birmingham, Bristol, Suffolk and Kent. Often the traffic through GB3BM was overpowering signals from our local repeater, GB3SN, in Hampshire; both on R5.

In the afternoon, Roy Bannister, G8LXR, Lancing, heard EI9Q working a 2m station in Crowborough and Andy Mepham, G4CBZ/P, worked a GW on 70cm using a vertical-colinear aerial on Ditchling Beacon, he also worked northern G stations on 2m using a 5/8 whip aerial mounted on his car.

For most of the day I received a watchable picture from Lichfield on Channel 8, strong signals from both the Emley Moor and Sutton Coldfield beacons on 70cm, and, around midday, a variety of continental broadcast stations were audible in Band II. At 1412 on the 29th, Alan Baker worked G8HPQ, Nr. Chesterfield, on 2m ssb, during another period of falling pressure, and in less favourable conditions, at 2155 on November 6th, he put out a chance CQ on 2m and contacted G8KHR in Newark.

The AP rose again to 30.2in from noon on the 8th to midnight on the 9th and by 0400 on the 10th it was falling, and, true to form, there was a brief tropospheric disturbance. For most of the morning I received strong signals from 10 continental broadcast stations between 88-100MHz, GW mobiles were opening my squelch via GB3BC and I heard a 59 signal from GU4EON via GB3SN. Around this time, Roy Bannister could hear both the Cambridge and Suffolk repeaters and French stations on S20, while G4GNX heard signals through the Bristol Channel and Kent repeaters and later had a 55 contact with G4DAZ in Bedfordshire.

Stan Heys, Peacehaven, a member of the St. Dunstan's Amateur Radio Society was, since 1972, an active SWL specialising in 80m, however, last August he obtained his licence and now operates on 2m under the call sign G8NOE. Stan has a Uniden 2030 giving him 10 watts of FM to a $\frac{1}{4}$ wave, loft-mounted ground plane, and so far he has worked about 100 stations and his best DX is St. Austell.

Cmdr. Henry Hatfield, Sevenoaks, and myself recorded several bursts of solar radio noise at 136MHz on October 22nd, 23rd, 25th and 28th, the result of which was no doubt responsible for the ionospheric disturbance reported by the BBC World Service on 27th and 28th. We both recorded further bursts on the 31st and November 2nd, 16th and 18th, noise storm conditions on the 6th and 17th, and high solar noise level on the 12th and 13th, which ties up nicely with the visual aurora reported at 2200 on the 14th and the ionospheric disturbance reported by the BBC World Service on the 16th.

On November 9, Henry gave a most interesting step-by-step survey, illustrated with slides, of the construction and workings of his spectrohelioscope, to a packed meeting of the Brighton and District Radio Society. Henry made many comparisons between the reception and bandwidth or radio signals and light waves but emphasised that his optical equipment works at 457 million megahertz. Members and guests present were fascinated by the pictures of the typical solar events which create the radio noise and cause radio blackouts and aurora which are frequently reported through this column and in other journals. On November 11th Henry saw two bright patches on the eastern solar limb and on the 13th he identified two new sunspots, and a fairly active area.

From October 23rd to 27th, Nigel Golds, BRS 36910, West Chilmington, Sx, heard 22 countries on 10m, from Israel to Argentina and from Italy to Ukraine. I have paid particular attention to the behaviour of signals from the International Beacon Project stations on 10m and at 1400 on October 31st I received a 539 signal from 3B8MS, Mauritius, and, a 559 from 5B4CY in Cyprus. Almost daily from November 3rd to 19th I heard 5B4CY around

0930 at strengths varying from 539 to 589, in fact, I could leave the receiver tuned to 28.220MHz and wait for its signal to appear. Most lunch times throughout this period, North American stations were as predominant on 10m as the Russian stations were in the early mornings.

Gordon Goodyer, BRS 37345, Petworth, Sx, using his Eddystone 750, a loft-mounted wire dipole and a homebrew, EF183 valve pre-selector did very well on 10m between 1030 and 1500 on the 13th. Gordon heard strong ssb signals from Ukraine to Rhodesia, Norway to North America, Spain to Argentina and much of South America. Between 0930 and 1030 on both the 13th and 15th I received 539 signals from the Bahrain beacon A9XC, 28.245MHz, and during the mornings of November 4, 5, 7, 8, 13, 14, 15 and 17, I heard signals, averaging 549, from ZE2JV a temporary propagation beacon for project TESSA (Transequatorial Scatter to Southern Africa).

Between 0830 and 2330, on November 14th and 18th I monitored the frequency (70.31MHz) of the Polish broadcast station at Gdansk and counted the number of times that its signal bounced off meteor trails (pings) during the Leonids meteor shower. The following rounded off daily figures show that the peak activity occurred on the 16th; total number of "pings" recorded daily were: 14th 7000, 15th 11000, 16th 14000, 17th 9000 and 18th 8000. I would be very interested to have more reports about this form of propagation.

Thanks again for your reports and for the interest you are taking in my column.

NEW BOOKS

MODERN ELECTRONICS MADE SIMPLE

George H. Olsen

Published by W. H. Allen

306 pages £1.75.

On the face of it, this book appears to offer more value, in terms of cash for paper, than book No. 1, but it is debatable whether this is a prerequisite for any technical summary, so alternative judgements must follow.

It is to be hoped, starting at the cover, that readers will not immediately conclude that every technical process is so easily capable of ultimate simplification: "Build Your Own Orbiting Laboratory" is hardly likely to follow hard on the heels of this publication, in spite of the assertion of its title.

To be fair though, its treatment of an immensely wide subject area is at once engaging and concise. There is plenty that is traditional, such as "slabs" on power supplies, Hartley and Colpitts oscillators, use of ICs and so on, and it does move into the more involved processes of synchronisation and principles of television.

The sections dealing with the integration process are lucid and interesting, but I was not so impressed with the somewhat behind-hand diagrams showing typical shadow mask construction. Precision-In-Line, slot aperture colour tubes have been around for long enough to warrant inclusion, especially since moving-coil pick-ups are mentioned, if only at the diagram stage. Overall then, only one or two reservations—at some points information is sketchy—but there is a clear attempt to attack the subject from a wide base, and this can itself introduce the perennial problem of dynamic selection.

A slightly disturbing sensation results from the perusal of page 299, however. Kits for some of the projects are apparently available from NESLO Electronics—palindromes are clearly grist to Mr. Olsen's mill!

Ted Parratt

FREE CATALOGUE/ORDER FORM SEND S.A.E.

500+ Top quality Transistors, I.C.'s, Resistors, Capacitors, Plugs/Sockets, Veroboard/cases, Indicators, Knobs, Switches, Wire and Books at prices you can afford.

741 ONLY 30p **555 ONLY 50p** **TIL209 ONLY 15p** **IN4001 ONLY 5p**

All prices include VAT. P&P FREE over £2.

Name _____
Address _____

Get an ACE up your sleeve!

ACE MAILTRONIX LTD
Dept. P.W. Tootal Street
Wakefield, W. Yorkshire WF1 5JR

V.H.F. TEST SET type 210 provides RF O/P over range 20 to 88Mc/s in 4 bands, approx 10 mill/v O/P C.W. or pulse mod at 5 freq around 30Kc. Also contains noise generator with 50 Ma meter, 2 Mc/s int calibrator, these units have int p.u. but this is not suitable for 50c/s (req 250v ht & 6.3v) supplied in case with Ae rods, cal chart circ & notes. £10.80.

SOLID STATE POWER SWT opto coupled control volts 5/15 dc, will handle 240v at 5 amp or 13 amp on heatsink okay for sound to light units £2.40.

ATTEN X Band var about 40Db w.g.16 new £4.50.

THERMISTORS bead type temp range 20 to 200' C new 65p.

CRYSTAL STANDARD 100Kc & 1 Mc/s in 10X case with circ £2.80.

RECEIVER UNIT small personal receiver covers 500Kc to 18Mc/s in 4 bands with 4 way plug in coil unit, 5 valve unit with BFO in metal case size 6½ × 3½ × 1½" fitted slow motion dial, these require ext phones & HT & LT supplies of 67.5 & 1.5v dc with circ & cal chart £10.80.

CRT VISOR with magnifier size 5 × 4 × 7" £3.

AERIAL DRIVE UNIT was used with radio compass aerial will turn small beam contains two 24v dc motors driving into differential gear with o/p shaft 1½ × ½" with threaded end, approx overhaul size 6½" dia 6" high less shaft with o/p to work 24v desyn £8.50.

CRYSTALS mixed 10X & 10XJ types in range 5 to 8.5Mc/s 20 for £2.20.

METER panel type 1 Ma fsd special scale 2" new £1.30.

V.H.F. power transis type 2N3375 7.5 watts at 100Mc/s 3 watts at 400Mc/s new £1.80.

CRYSTAL OVEN miniature type 55°C for 12/24v will take two Hc18 type plug in crystals new £1.20.

H. F. RECEIVER R4187 & CONTROL BOX aircraft remote controlled receiver covers 2.8 to 18Mc/s in 3 bands 24 crystal controlled channels, dual conversion Rx with 16 valves, I.F. filters, BFO, N.L. etc as O/P for phones, supplied with control box, copy of handbook & mods to enable Rx to tune 80, 40 & 20 meter bands, these require supplies of 200v ht & 19v DC. £18.30.

SIGNAL GEN type 6 special purpose unit provides 17 crystal controlled O/Ps over range 60 to 70Mc/s with provision for C.W. single & double freq A.M. & F.M. (were used for testing sonar-buoy receivers) as int carrier level meter, 4 stage o/p atten. Require ext p.u. 200v & 6.3 with circ & notes fuller disc on list £25.

U.H.F. RECEIVER single channel crystal controlled 225 to 400Mc/s double conversion, 19" rack mounting O/P 1 watt into 600 ohm fitted RF & AF gain controls uses Hc6/ju crystals in range 20/40Mc/s with circ for use on 230v mains £30.

HEATERS flat tubular 240v 150w approx size 6½ × 10" were used for film drying new £1.50.

ROTARY SWTS ceramic 6p 5w ¼" shaft new £1.20.

SWT UNIT precision attn with 1p 24w swt with 16 low value res in scr box new £2.

HELIPOTS 10 Tr 5K small type ¼" shaft new £1.75.

REMOTE CRYSTAL selector with provision for selecting 6 Tx & 6 Rx crystals contains 6c BC108, 6 tub trimmers, coils diodes etc new £1.80.

Above prices include carr/postage & VAT. SAE for list 18 or enquiry, goods ex equipment unless stated new. Shop open Tues to Sat.

A. H. SUPPLIES

122 HANDSWORTH RD., SHEFFIELD S9 4AE

Tel: 444278 (0742)

NEW
FROM CASIO,
OF COURSE.
**POCKET WATCH
CALCULATOR
TWO WAY
TIMER ALARM**

Ultra slim pocket calculator. LCD display. 6 Digit clock. Daily (10 second) Alarm, Timer, up to 12 hours, or Repeat Timer (for example, can be set to buzz every three hours.) Calculator Four key memory, percentage, square roots, etc. Battery life 2000 hours plus. Leatherette case.

AQ 810 An incredible **£19.95**

Casio 21QS-10B (ST. TM) 9.6mm £34.95

Western Time

LED 6+3 functions S/S finish Quality for £11.95

31QR-12B (ST) 8.5mm thick £29.95

Superb CASIO LCD watches. Seven functions, light, auto calendar, STOP-WATCH (ST) DUAL TIME ZONE (TM) All stainless steel, mineral glass, WATER RESISTANT to 100 feet. AVAILABLE JANUARY. Casio chronograph £59.95 and £64.95. ALARM watch (ST) £59.95. Send 15p for our illustrated catalogue. Lowest discount prices, widest range. Prices include VAT, P&P. Send cheque, P.O. or phone your credit card number to:-

TEMPUS Dept. P.W., 19/21 Fitzroy Street, Cambridge CB1 1EH Tel. 0223 312866

PRACTICAL WIRELESS T.V. SOUND TUNER
(Nov. 75 article by A. C. Ainslie) Copy of original article supplied on request

IF Sub-Assembly (G8) £6.80. P & P 75p.
Mullard ELC1043 V'cap UHF Tuner £4.50. P & P 35p.
3-way Station Control Unit £1.20. P & P 25p.
6-way Station Control Unit (Special Offer) £1.00.
Power Supply Prtd Circuit Board £1.00. P & P 30p.
Res, Caps, Semiconds, etc. for above £5.80.
Mains Transformer for above £2.50. P & P 30p.
Add 12½% VAT to price of goods. P & P all items 85p.
Callers welcome at shop premises.

MANOR SUPPLIES
172 WEST END LANE, LONDON NW6
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

THE DYNAMIC DUO



The C15/15 is a unique Power Amplifier providing Stereo 15 watts per channel or 30 watts Mono and can be used with any car radio/tape unit. It is simply wired in series with the existing speaker leads and in conjunction with our speakers S15 produces a system of incredible performance.

A novel feature is that the amplifier is automatically switched on or off by sensing the power line of the radio/tape unit hence alleviating the need for an on/off switch.

The amplifier is sealed into an integral heatsink and is terminated by screw connectors making installation a very easy process. The S15 has been specially designed for car use and produces performance equal to domestic speakers yet retaining high power handling and compact size.

C15/15
 15 Watts per channel into 4Ω
 Distortion 0.2% at 1KHz at 15 watts
 Frequency response 50Hz - 30KHz
 Input Impedance 8Ω nominal
 Input sensitivity 2 volts R.M.S. for 15 watts output
 Power line 10 - 18 volts
 Open and Short Circuit protection
 Thermal protection
 Size 4 × 4 × 1 inches

Data on S15
 6" Diameter
 5½" Air Suspension
 2" Active Tweeter
 20oz Ceramic magnet
 15 watts R.M.S. handling
 50 HZ - 15KHz frequency response
 4Ω Impedance

C15/15 Price £17.74 + £2.21 VAT P & P free

S15 Price pre pair £17.74 + £2.21 VAT P & P free

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.,
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218.

Please Supply
 Total Purchase Price
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number
 Name & Address
 Signature

TV GAMES IN FULL COLOUR

AY-3-8500 £6.30, AY-3-8505 £9.95.
Black and White TV games kits—
Standard model £11.95, Economy
model £6.95, Colour TV games
kits—Standard £19.45.
Economy £14.45. Colour Generator
kit adds colour to most black and white
games £7.50.
Rattle kit £4.95. Send sae for giant data



NEW COMPONENT SERVICE

Resistors 5% carbon E12 1Ω to 10M 1/4W 1/2p, 1W 3p
Presets pots subminiature 0-1M 100Ω to 4M7 9p
Potentiometers 1/4W 4K7 to 2M2 log or lin. Single
30p. Dual 95p. Polystyrene Capacitors E12 63V
22pf to 82000pf 3p. Ceramic Capacitors 50V E6
22pf to 47000pf 3p. Polyester Capacitors 250V E6
01 to 1mf 5p, 15, 22, 33mf 7p, 47mf 11p
Electrolytics 50V 47, 1, 2 mf 5p, 25V S, 10mf 5p,
16V 22, 33, 47mf 6p, 100mf 7p, 220, 330mf 9p, 470mf
11p, 1000mf 18p. Zener Diodes 400mW E24 3V3 to
33V 84p

MAINS TRANSFORMERS

6-0-6V 100mA 94p, 9-0-9V 75mA 94p, 0/12/15
20/24/30V 1A £3.85, 12-0-12V 50mA 94p, 0/12/15/
20/24/30V 2A £5.15, 6-3V 1 1/2A £1.99, 6-0-6V 1 1/2A
£2.75, 9-0-9V 1A £2.39, 12-0-12V 1A £2.69, 15-0-15V
1A £2.89, 30-0-30V 1A £3.59

PRINTED CIRCUIT MATERIALS

50 sq. inc. pcb 40p, 1lb. FeCl 1.05, Etch resist pens—
Economy type 45p, Dalo type 83p, Small drill bit 20p,
Laminate cutter 75p, Etching dish 68p.

S-DECS AND T-DECS*

S-Dec £2.23, T-Dec £3.98
u-DeCA £3.97, u-DeCB £6.67
IC carriers with sockets
16 dil £1.91, 10T05 £1.91



SINCLAIR CALCULATORS AND DVM*

Cambridge scientific programmable £13.95, Prog.
library £4.95, Cambridge scientific £8.45, Oxford
scientific £10.60, Mains adaptors £3.20, PDM 35
digital multimeter £26.95, Adaptor £3.20.

BATTERY ELIMINATOR BARGAINS

TV GAMES POWER UNIT
Stabilized 7-7V 100mA £3.25

3-WAY MODELS

With switched output and 4-way multijack
Type 1: 3/4/6V at 100mA £2.92,
Type 2: 6/7/9V 300mA £3.30.

100MA RADIO MODELS

With press-stud connectors, 9V £3.45, 6V £3.45,
9V+9V £5.15, 6V+6V £5.15, 4 1/2V+4 1/2V £5.15.

CASSETTE MAINS UNIT

7 1/2V with 5 pin din plug 150mA £3.65.

FULLY STABILIZED MODEL £6.40

Switched output of 3/6/7 1/2V 400mA stabilized.

CAR CONVERTERS 12V INPUT

Output 9V 300mA £1.80, Output 7 1/2V 300mA £1.80.

BATTERY ELIMINATOR KITS

Send sae for free leaflet on range.

100mA radio types with press stud battery terminals,
4 1/2V £2.10, 6V £2.10, 9V £2.10, 4 1/2V+4 1/2V £2.50, 6V+
6V £2.50, 9V+9V £2.50.

Cassette type 7 1/2V 100mA with din plug £2.10

Transistor stabilized 8-way type for low hum
3/4/6/7 1/2/9/12/15/18V, 100mA £3.20, 1 Amp £6.40

Heavy duty 13-way types 4 1/2/6/7 1/2/11-13/14/17/21
25/28/34/42V, 1 Amp £4.85, 2 Amp £7.95.

Car converter kit Input 12V DC, Output 6.7 1/2/9V
DC 1A transistor stabilized £1.95.

Stabilized power kits 3-18V 100mA £3.60, 3-30V 1A
£9.95, 3-60V 1A £10.95, 3-60V 2A £13.95.

BI-PAK AUDIO MODULES

S450 tuner £21.95, AL60 £4.86, PA100 £14.95, MK60
audio kit £36.45, Stereo 30 £17.95, SPM80 £3.75
BMT80 £5.95. Send sae for free data.

JC12, JC20, JC40 AMPLIFIERS

JC12 6W IC audio
amp with free data
and printed circuit £1.95.
Also new JC40 20W
model with pcb
£3.95. Sensational new JC20, 10W integrated circuit
amp with pcb £2.95. Send sae for free leaflet on all
3 models and associated power supply and preamp kits!



FERRANTI ZN414

IC radio chip £1.44, Extra parts and pcb for radio
£3.85, Case £1. Send sae for free data.

SWANLEY ELECTRONICS

DEPT. PW, PO BOX 68,
32 GOLDSSEL RD., SWANLEY, KENT

Post 30p. Prices include VAT. Official orders welcome.
Overseas customers deduct 7% on items marked *
and 11% on others.

"CASTLE ELECTRONICS"

MAIL ORDER

7, CASTLE STREET, HASTINGS, SUSSEX
Tel: (0424) 437875

R.C.A. 7163 L.D.R. 1" Dia, Dark Res 2-5M,
Light IK, 3 for £2.75.

Signal Switches 6 Pol C/O 40p, 4 Pol C/O 35p,
2 Pol C/O 30p incl. knob.

Stereo Slider Controls 10K Log, 250K Lin, 100K
Log, 3 1/2" long 40p each.

Ex G.P.O. New Stabilized Power Supplies 250
V.A.C. at 500M/A + - 2V £6.00.

H.F. Ammeters 0-2 Amp 2" Dia. £2.35.

Shure M91-ED Stereo Magnetic Cartridges £15.95.
Micro Switches 5 Amp 240V Contacts C/O
Button Opp 5 for £1.00.

Brand New EX-WD High Impedance Head-
phones £2.00 pair.

1 1/2lb Bags of New Electronic Components £1.95.
Stereo Jack Sockets 5 for 75p.

Thermometers 2" Dia. 70f-160f Chrome Front
Bezel, New £1.95.

Reed Switches 1-1/2" IN, 1-1/4" Dia 500 M/A 250V
Contacts 65p doz.

Photo Diodes 5 for £1.00.
Min High Power Electric Motors with Rev Sw
1 1/2" Long, 1 1/2" Dia. 6-12 VDC German manu-
facture £1.25.

Nical Cad Cells 5 x 1.2V (=6V) 225M/AH New
£1.75; Nical Cad Cells 5 x 1.2V (=6V) 50M/AH
New £1.00.

Low Noise Cassettes 10 x C60's £4.00, 10 x
C90's £5.00.

ALL PRICES INCLUDE VAT, POST AND PACKING.
Please send S.A.E. for further details on
items listed below.

Over 2,000 New Ex-WD Panel Meters in stock
from 75p-£3.50.

Amtron Electronic Kits, Complete Range in
stock (many obsolete kits at half price).

Complete range of Sanwa Multi-Meters in stock.
Panel Meters Alps 50ua-50 Amp, 10 MV-500V,
Full range. C-Scope Metal Detectors, complete
range in stock. VV ide range of surplus components.

VALVE BARGAINS

Any 5-64p, 10-£1.20, 50-£5.00. Your choice
from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802,
PCL82, PCL84, PCL85, PCL86, PCL805, PL504,
PY81/800, PY88, 30PL14, 6F28, PFL200.

Colour Valves—PL508, PL509, PL519, PY500/A.
All tested. 35p each.

Aerial Splitters—2 way, 75 OHMS, Inside Type,
£1.50.

AERIAL BOOSTERS

Aerial boosters can produce remarkable
improvements on the picture and sound, in
fringe or difficult areas.

B11—For TH stereo and standard VHF/FM radio.
B12—For the older VHF television—Please
state channel numbers.

B45—For Mono or colour this covers the complete
UHF Television band.

All boosters are complete with battery with
Co-ax plugs and sockets. Next to the set fitting.
£4.20

100—C280/1 CAPACITORS
Values from .01uF to 1.5uF, 250v/w. Price £1.50
(mixed packs).

100—ELECTROLYTICS
From 1uF to above 5000uF. Mixed voltages. Price
£2.00 (mixed packs).

All prices include VAT. P&P 30p per order
Please send uncrossed P.O. or cheques for
returning if we are out of stock of capacitor
bargain packs. Exports welcome at cost.

ELECTRONIC MAILORDER LTD.

62 BRIDGE STREET, RAMSBOTTOM,
BURY, LANCs.
TEL: RAMS (070 682) 3036

SEMICONDUCTOR OFFERS ALL FULL SPEC

BC212, BC182, BC237, BF197, BC159, All 8p each
RCA 2015 T03 POWER TRANSISTOR (SIM TO
2N3055) 35p, ACY18 18p, BF200 20p, MOTOROLA
MRD 3051 PHOTO TRANSISTORS 35p, N.CHANNEL
F.E.T.S. SIMILAR TO 2N3819 18p, MOSFET SIM. TO
404673 35p, 3N140 MOSFETS 50p, M203 DUAL
MATCHED PAIRS MOSFETS 13p, 2N4349 PER F.E.T.
40p, SL301 DUAL MATCHED PAIR SILICON
POWER TRANSISTORS FT 300MHz 30p, INTEL
1024 BIT MOS RAMS 95p, MULLARD BB113 TRIPLE
VARICAP DIODE 35p, MC1310 STEREO DECODER
I.C.s £1.20, TBA800 I.C. AMPS 90p, CD4051 CMOS
MC1303N ST. PREAMP I.C. £1.30, 741 8 PIN
D.I.L. 23p, MM531 C LOCK CHIPS £3.50, 400V 15
amp STUD S.C.R. 75p, 500V 600mA BRIDGE RECS.
(EX. EQUIP.) 25p, IN4002 100V 1A DIODES 4p,
14005 800V 1A DIODES 7p, 200 volt 5 amp SIL.
BRIDGES EX. EQUIP. 40p, CV7556 200V 150 amp
STUD RECS. £1.25, E.H.T. SIL. REC. 15kV 2.5 mA,
15mm x 5mm 85p, 7812 12v 1A PLASTIC V. REGS.
95p, MIN. NIXIES ITT 5870ST 13 x 6mm FIG SIZE 85p,
NIXIES ITT GN/9A 13 x 8mm 65p, 0-2" OR 1-25"
RED LEDS 12p each, MAN3A 3mm LED DISPLAYS
50p, MONSANTO 4640A 0-3" 7 SEG. C. CATH.
DISPLAYS 95p.

MICROPHONES—GRUNDIG ELECTRET INSERTS
WITH BUILT IN F.E.T. PREAMP £1.50, CRYSTAL
MIKE INSERTS 37mm 10p, ELECTRET CONDENSER
MIKES IKQ IMP. WITH STD JACK PLUG £2.85,
CASSETTE CONDENSER MIKES WITH 2.5 and 3.5
JACK PLUGS £2.85, STANDARD CASSETTE MIKES
200 OHM IMPED. WITH 2.5 and 3.5 JACK PLUGS
£1.50, P.A. MIKES MOBILE TYPE 50K D, THUMB
SWITCH £4.20.

MORSE KEYS—PLASTIC TYPE 95p, HI-SPEED TYPE
ALL METAL £2.25, HI-IMP. PHONES 2KΩ £1.65,
AERIAL COAX SWITCH 3 POSITION, 3 OUTPUTS,
0-30MHz, 150 watts MAX. USES 50239 SOCKETS
£4.95, LOW PASS IN-LINE FILTERS, 30MHz CUT
OFF, 50 OHM IMP. £3.30, S.W.R. METER, 50 OHMS
IMP. WITH POWER SCALE £10.50, XTAL MARKER
GEN. 300KHz STEPS SUPPLIED WITH
XTAL FOR THIS COVERAGE £7.90.

CRYSTALS—300KHz HCGU 40p, 4-43MHz C.T.V.
XTALS 45p, 0-1" EDGE CONNECTORS 64 WAY 65p,
32 WAY 40p.

RELAYS—MIN. SEALED RELAYS ALL 4 POLE
CHANGEOVER, 36Ω (6v DC) 45p, 185 Ω (12v DC)
55p, 700 Ω (24v DC) 55p, MIN. 220v AC SEALED
RELAY C/O 2 POLE COIL 50p, SEALED RELAY
3 POLE C/O 5 AMP CONTACTS 1 PIN BASE 80p,
12 VOLT 4 POLE N.O. REED RELAY 20p.

MOTORS—1-5 to 6v DC MODEL 20p, 115v AC
MIN. 3 R.P.M. WITH GEARBOX 30p, 240v AC
SYNCH. MOTOR 1/5TH R.P.M. 65p, 240v AC SYNCH
MOTOR 1/24th, R.P.M. 65p.

BOXES—BLACK A.B.S. PLASTIC WITH BRASS
INSERTS AND LID, 75 x 36 x 35mm 40p, 95 x 71 x
35mm 49p, 115 x 95 x 36mm 57p, GREEN PRINTING
BOXES WITH LUGS, 23 x 48 x 23mm 11p, 38 x 52 x
25mm 13p, 60 x 80 x 42mm 28p.

TRANSFORMERS—6-0-6v 100mA, 9-0-9v 75mA,
12-0-12v 50mA 75p each, 12-0-12v 100mA 95p, 12v
500mA 95p, 35v 2A AND 2-5v 2A TOROID £2.75 +
35p P & P, 18v 1 amp RECTIFIED £1.95 + 35p P & P,
25v 2 amp £1.75p + 35p P & P, 25-0-25-24-30v
2 amp £3.25 + 35p P & P, (2 amp VERSION £4.45 +
35p P & P), 30-0-30v 1A £3.00 + 35p P & P, 25-0-25v
2A £3.95 + 35p P & P, 100 volt LINE TRANS-
FORMER 15 watts MAX.—0-8-15Ω £1.80 + 35p P & P,
1:1 TRIAC XENON PULSE TRANSFORMER 30p,
6mh 3 amp CHOKES 30p.

SWITCHES—MIN. TIGGLE, SPST 12 x 6 x 9mm
54p, DPDT 12 x 11 x 9mm 60p, DPDT CENTRE OFF
12 x 11 x 9mm 75p, 4P 2W SLIDERS 20p 6P 3W
SLIDERS 30p DPDT C/O SLIDERS 20p, SPST 10 amp
ROCKERS 12p, R.S. SINGLE POLE C/O PUSH-
BUTTONS 45p, ROLLER MICRO SWITCHES 15p,
MIN. MICRO SWITCHES 13 x 10 x 4mm 20p, G.P.O. 4
KEYSWITCH ASSY, 3 SWITCHES 2 WAY, 4 WAY
MULTI-POLE 35p, MIN. PUSH TO MAKE OR PUSH
TO BREAK SWITCHES 16 x 6mm 15p, PLESSEY
WINKLER STUD SWITCHES 2 BANK, 1 POLE 30
WAY ADJ. STOP 75p, DE-SOLDERING TOOLS,
PLUNGER TYPE £4.95.

TAPE HEADS—JAP. CASSETTE MONO 90p,
CASSETTE STEREO £3.00, BSR MN1330 + TRACK
DUAL IMPEDANCE REC/PLAYBACK 50p, BSR
SRP90 + TRACK STEREO REC/PLAYBACK £1.95,
TD10 ASSEMBLES TWO HEADS + TRACK REC/
PLAYBACK STAGGERED STEREO WITH BUILT IN
ERASE PER HEAD £1.20, TAPE HEAD DEMAG 240v
AC £1.95.

BUZZERS—GPO TYPE 6-12v 30p, 6-12v HOOTERS
50p, MIN. SOLID STATE BUZZERS 6-9-12 OR 24v
15mA 75p, U.H.F. T.V. TRANSISTORISED PUSH
BUTTON TUNERS (NOT VARICAP) NEW AND
BOXED £2.50.

COMPUTER CAPS—20,000mFD 45p. (EX EQUIP)
40p.

POT CORES—ADJ. VINKOR 250-370 MICRO H
20p, 260 OR 500 MILLI HENRY CORES 10p each.

METERS—100-0-100uA LEVEL METERS 75p, STEREO
TUNING METERS 100uA PER MOVEMENT £2.75,
GRUNDIG BATT. LEVEL METER 1mA 40 x 40mm
£1.10, MIN. LEVEL METER 200uA 25 x 15mm 75p,
FERRANTI 1mA PANEL METER 55 x 70mm £2.95,
FERRANTI PANEL METER 100uA 55 x 70mm £3.50,
FERRANTI 600v AC METER £3.95.

BOARDS—G.P.O. BOARD WITH 64, BC 107 TYPE
TRANSISTORS, 2 REED, 1 MERCURY RELAY ETC.
£2.00 + 55p P & P, SINGLE STAGE STEREO PRE-
AMP BOARDS MAX I/P 700 M/V (HI-Z) GAIN 26 DB
40p, 465KHz I.F. PANELS, 6 I.F.T.'s, 30p, BOARD
WITH 14 12v N.O. REED RELAYS £2.40, BOARD
WITH 6v C/O REED RELAY £2.20.

AEROSOLS—SERVISOL SWITCH CLEANER +
LUBRICANT 8ozs 35p, FREEZER 6ozs 50p, GEAR
CLEANER + TAR REMOVER 14ozs 85p.

SOLENOIDS—240v AC 45p, 12v DC H DUTY 75p,
240v AC LARGE 25lbs PULL, 4" TRAVEL £3.25 +
50p P & P.

POSTAGE 30p UNLESS OTHERWISE SHOWN
(EXCESS POSTAGE REFUNDED WITH ORDER).
OVERSEAS POST AT COST. VAT INCLUDED IN
ALL PRICES.

ORDER ADDRESS
PROGRESSIVE RADIO

31 CHEAPSIDE
LIVERPOOL 2 051 236 0982

WHAT'S NEW?

ME, semiconductor teaching kit

the **most** MODERN, RAPID, ECONOMIC way to master space age electronics. Starting even from ZERO, by performing over.

100 EXPERIMENTS and creating more than 20 practical applications

You learn all about the most up to date electronic circuits: how to calculate, repair, and design them, while pursuing your favourite hobby. Start from scratch, or improve your present knowledge. Train and earn money in your spare time turn your pastime into valuable job opportunities. Compare our price: you receive the entire course, "mini laboratory" and components for LESS than the price of the components alone.



COMPLETE KIT: nothing else to buy*

you get:

- instruction manual : over 200 pages of detailed step-by-step instructions - starting from scratch, explains basic laws and physics of Electricity, semiconductor principles and operation electronic circuits : from diodes (including diac, zener) transistors, triacs to integrated circuits (C.MOS, operational amplifiers) etc...
- Over 200 Electronic components : aerospace technologie printed circuit experiment board, phototransistor, triac, thyristor I.C.S Transistors (including FET, MOSFET) LEDs + resistors, capacitors, speaker, milliammeter, potentiometers, variable capacitor, etc... etc... etc...
- measuring instruments (you assemble yourself from among components furnished in kit.)
- ELECTRONIC VOLTMETER, LOW FREQUENCY MEASURING AMPLIFIER, LOGIC INDICATORS, REGULATED POWER SUPPLY, MILLIAMMETER.


you perform:

- over 100 DIFFERENT EXPERIMENTS : from the most basic voltage measurements to radio transmitter circuits and including HI FI, Flip Flops, IC applications, triac use, etc... etc... etc...

you construct

- more than 20 complete functional systems : light modulator, high fidelity amplifier, radio control set, radio receiver and transmitter electronic gadgets and games and many, many more.

* Hand tools not furnished.

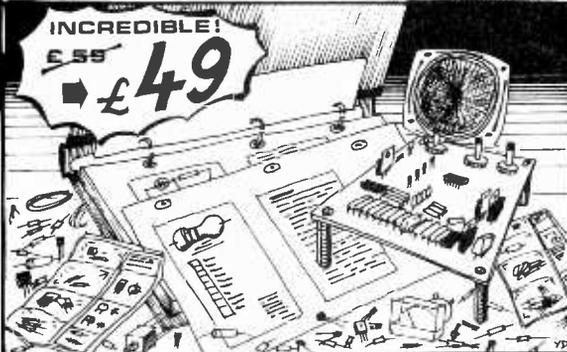

SAVE £10 - mail coupon today - SAVE £10

SAGA ENGLAND

PO BOX 401
KINGSHEAD LANE, KING'S LANE
CHIPPERFIELD, NR. KING'S LANGLEY,
HERTS. WD4 9PD

Please send me (QTY) IK2 teaching kit(s)

I enclose Cheque/Postal order for £

NAME

ADDRESS

SAGA FRANCE : 1 RUE PROSPER DELFAU
30160 BESSÈGES FRANCE. POST CODE



4 1/2 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £5-43. P. & P. 19p.

MICROPHONES FOR TAPE RECORDERS

- DM228R 200 ohm with 3.5 & 2.5mm Jack Plugs £1-42
 - DM229R 50K with 3.5 & 2.5mm Jack Plugs £1-60
 - DM18D 200 ohm with 5 & 3 pin DIN plug £1-75
- Postage on above microphones 11p.



CARDIOID DYNAMIC MICROPHONES

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £8-02. P. & P. 35p.

All above prices include V.A.T. Special prices for quantity quoted on request.

42 x 42mm METERS
1mA, £3-65, 11p P. & P.
60 x 45mm METERS
50µA, 100µA, 500µA and 1mA
VU METER £4-46, 13p P. & P.

6V BUZZERS 50mm diameter
30mm high. Very loud. 52p, post 9p



MULTI-METER

Model ITI-2
20,000 ohm/volt, £10-38.
P.&P. 33p.



TRANSFORMERS

Primary 240V
6-0-6V 100mA £0-75
9-0-9V 75mA £0-75
12-0-12V 50mA £0-85
12-0-12V 100mA £1-05

Post on above transformers 30p.
9-0-9V 1A £1-80
12-0-12V 1A £2-15
15-0-15V 1A £2-36
30-0-30V 1A £3-10
6-3V 1 1/2 A £1-80
6-0-6V 1 1/2 A £2-20

Post on above transformers 45p.

Send 40p for Fully Illustrated Catalogue.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

BULK BARGAINS

All devices listed are full spec and guaranteed.

AC127	£13	2N3054	£32	TRANSFORMERS, mains primary.
AC128	£13	2N3055	£34	6-0-6V 100mA* 10 for £6-20
AC176	£13	2N3583	£46	9-0-9V 75mA* 10 for £6-20
AC187	£17	2N3705*	£7	12-0-12V 50mA* 10 for £6-80
AC188	£17	2N3708*	£6	12-0-12V 100mA* 10 for £7-80
AD181	£18	2N3819*	£18	12-0-12V 1A 10 for £16-50
AD182	£60	2N4401*	£6	
AF279	£38	2N5401*	£22	VEROBOARD
BC107	£7	2SC536*	£5	0.1" copper clad offcuts, all good size
BC108C	£8	1N4002	£3-80	pieces, average
BC109	£8	1N4004	£5-90	4" x 3", 1 kilo (approx. 60 bits) £7-50
BC147	£6	1N4007	£6-80	5 kilos £32-50
BC149*	£6	1N4148	£2-30	
BC159*	£6	BYX94	£7-40	RESISTORS*
BC172*	£5	100V 3A stud	£10	Carbon film 1/4W miniature 5%
BC182*	£5	mntg	£19	All values in E12 series from 1R to 10M.
BC183*	£5	400V 10A stud	£28	(1M2-10M are 10%)
BC184*	£6	50V 1A bridge	£13	OR47 0-7W 80p/100, £6/1000 NO mixing
BC212*	£5	rect	£28	Sub-min presets, 2k horiz. £1/100, £7/1000
BC213*	£5	400V 1A bridge	£16	Thermistor VA1088 £3-50/100, £25/1000
BC214*	£5	rect	£16	Flex-7/0-2 and 14/0-2 on various size
BC252*	£9	400V 1A SCR	£28	reels. Assorted colours. 1000 metres mixed £30-00
BC328*	£11	LED 0.2" red	£9	5000 metres mixed £37-00
BC337*	£11	0-125" 741 8 DIL	£18	CAPACITORS*
BC347*	£6	555	£28	Tant bead 35V: 0-1 to 1-5µF £7/100;
BC348*	£5-50	7400	£9	2-2/35, 3-3/35 £8/100; 4-7/35 £9-50; 6-8/35,
BC351*	£18	7473	£15	10/35, 15/20, 22/16, 33/10, 47/6, 68/3, 100/3
BC548*	£5-50	7496	£48	Electrolytics: 1µF 25V £3/100;
BCX53*	£5	74107	£21	47µF 25V £4/100; others on list.
BCY70	£19	74121	£26	180V axial leads: 0-01, 0-015, 0-022, 0-068,
RCY71	£12	7417	£22	Min 50V ceramic plate. All values from
BCY72	£11	7421	£22	22pF to 1000pF 5% £2/100
BD112	£32	7430	£8	Polyester, 250V radial leads:
BF173	£13	7445	£48	0-015µF £1/100; £6/1000
BF181	£19	7493	£28	0-068µF £1-30/100; £15/1000
BF184*	£8	7405	£8	0-1, 0-15µF £1-80/100, £15/1000
BF195*	£6	74193	£54	400V axial leads: -0015, -002, -0022, -0033,
BF196*	£6	Zeners.		-0047, -0058 £1-30/100, £11/1000
BFY50	£11	400mW 5%. All values in E24 series from		-039, -047, -068µF £3-50/100, £28/1000
BFY52	£11	2V7 to 33V. £5-50/100. NO mixing, but if 10 values are ordered, deduct 10%		BATTERY CLIPS*
BSY95A	£18	1-3W 5%. All values from		PP3 type £4/100; PP9 type £7/100
MPSA66*	£16	3V3-100V in E24 series		EARPIECES*
MPSU52	£18	E24 series		magnetic type with 3mm plug £8/100
OC44	£12	£13/100, min 1 1/2" of 10 per value		crystal type with 3mm plug £20/100
ZTX212*	£6			FUSEHOLDERS*
ZTX341*	£8			1 1/2" chassis mounting £4/100
ZTX350*	£8			Minimum order charge £5+VAT. VAT must be added at appropriate rate. An asterisk after product indicates the higher rate, other items at standard rate. Add 25p postage to all orders. Mail order only—no callers. Send SAE for list.

JUNIPER ELECTRONICS

1 Southern Gardens, Totton, Southampton

A. P. ELECTRONICS

Manufacturer and Distributor of Electronic Components

3 MILDWAY ROAD, ROMFORD, ESSEX
RM7 7DA

Telephone: ROMFORD 28882

BONANZA

4 MILLION RESISTOR'S Brand new. A fabulous range of $\frac{1}{4}$ Watt, $\frac{1}{2}$ Watt, 1 Watt and 2 Watt. Carbon Film Resistor's. 1,000 mixed values. For the lowest price ever, VAT included **£3.50** only.

This is a bargain you cannot miss, only from A. P. ELECTRONICS. Count by weight. Post & Pack only **45p.**

$\frac{1}{2}$ A MILLION MINIATURE CERAMIC PLATE CAPS. 200 for only **£1.25.** Mixed values all brand new VAT included. Post & Pack **25p.** Count by weight.

$\frac{1}{4}$ OF A MILLION MULLARD C296 POLYESTER'S Many values, 75 for only **£1** VAT included. Post & Pack **30p.** Brand new. Count by weight.

MULLARD C280 75 mixed values for only **£1** VAT included. Post & Pack **20p.** Count by weight.

A FABULOUS PACK OF HARDWARE. Self tappers, nuts, bolts, washers, spacers, grommet's, etc. etc. **£1** VAT included. Post & Pack **40p.**

200 METRES of connecting PVC covered wire single and stranded mixed colours for only **£1.25** VAT included. Post & Pack **25p.**

50 ELECTROLYTICS CAPACITORS. Mixed values for only **£1** VAT included. Post & Pack **25p.**

50 WIREWOUND RESISTORS. From 2.5 Watt. Mixed values for only **£1** VAT included. Post & Pack **30p.** Count by weight.

OVERSEAS POST AT COST.

EX-STOCK. Transistor's, Diodes, I.Cs, C.MOSSs, Thyristors, Knobs, Pre-sets, Resistors, Capacitors, Tant's, Bridge-Rectifiers, Transformers.

Open all day from 9am till 5.30pm.

Open all day Saturday.

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, TV Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
Also MPT Radio Communications Certificate

Diploma Courses

Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV and Audio, Engineering and Servicing
Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept 276R Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number

VALVES

A0165	1-25	EL34	2-20	PL509	2-00
AR6	0-80	EL37	3-00	PL802	2-50
ARP3	0-80	EL41	0-80	PY33	0-60
ATP4	0-50	EL81	0-80	PY80	0-60
B12H	3-00	EL82	0-60	PY81/800	0-55
DAF96	0-80	EL84	0-35	PY82	0-45
DET22	12-85	EL86	0-50	PY83	0-50
DF86	0-60	EL90	0-50	PY88	0-50
DK86	0-80	EL91	1-60	PY500A	1-35
DL92	0-50	EL95	0-70	PY801	0-55
DL86	0-70	EL504	0-80	QQV03-10	2-00
DY86/87	0-45	EL821	3-00	QQV06-40A	2-00
DY802	0-45	EM31	0-75		
E88CC/01	1-30	EM80	0-55		
E180CC	1-30	EM81	0-60		
E182CC	3-50	EM84	0-40		
E810F	0-60	EM87	1-00		
EA50	0-45	EY51	0-45		
EA76	2-00	EY81	0-45		
EAB800	0-40	EY86/87	0-50		
EAF42	0-70	EY88	0-50		
EB91	0-30	EZ40	0-60		
EB33	0-60	EZ41	0-75		
EB41	0-75	EZ80	0-30		
EBF80	0-45	GZ32	0-65		
EBF83	0-45	GZ33	2-50		
EBF89	0-40	KT66	4-00		
EC52	0-40	KT88	5-00		
EC81	0-45	MH4	1-00		
EC82	0-40	ML6	1-00		
EC83	0-40	OA2	0-45		
ECC84	0-35	OB2	0-45		
ECC85	0-45	PAB80	0-40		
ECC86	1-25	PC86	0-65		
ECC88	0-55	PC88	0-65		
ECC89	0-80	PC92	0-65		
ECF80	0-45	PC84	0-45		
ECF82	0-45	PC85	0-50		
ECF81	0-75	PC89	0-55		
ECH42	0-85	PCC189	0-65		
ECF81	0-45	PCF82	0-40		
ECH84	0-60	PCF84	0-65		
ECL80	0-60	PCF86	0-65		
ECL82	0-40	PCF201	0-90		
ECL83	1-20	PCF801	0-55		
ECL86	0-55	PCF802	0-55		
EF36	0-75	PCF806	0-85		
EF39	1-00	PCF808	0-60		
EF40	0-70	PCF900	0-80		
EF41	0-75	PCL81	0-60		
EF80	0-35	PCL82	0-45		
EF83	1-50	PCL83	0-70		
EF85	0-45	PCL84	0-50		
EF86	0-45	PCL86	0-60		
EF89	0-35	PCL805/85	1-3		
EF91	0-65	PL1	0-60		
EF92	0-75	PFL200	0-70		
EF95	0-45	PL36	0-60		
EF183	0-40	PL81	0-55		
EF184	0-40	PL82	0-50		
EF804	2-00	PL83	0-50		
EFL200	0-75	PL84	0-50		
EH90	0-60	PL504	0-95		
EL32	0-60	PL508	0-95		

PLUMBICON TUBES

TYPE XQ. 1020R

Mullard—£150 each

3A4	0-60	6H6	0-45
3E29	5-50	6U4WA	1-75
3D6	0-40	6J5	0-75
3V4	0-50	6J5GT	0-55
5B/254M	5-50	6J7	0-70
5B/255M	5-50	6J7G	0-50
5B/258M	5-50	6K7	0-55
5R4Y	1-10	6K7G	0-35
5U4G	0-60	6K8GT	0-55
5V4G	0-65	6L6M	1-90
5Y3GT	0-65	6L6GT	0-60
5Z3	1-00	6L7	0-65
5Z4G	1-75	6SA7	0-55
5Z4GT	0-60	6S7	0-60
6A87	0-60	6S7J	0-60
6AC7	0-60	6S87GT	0-50
6AH6	0-75	6SK7	0-45
6AK5	0-45	6SL7GT	0-55
6AK8	0-40	6SN7GT	0-55
6AL5	0-30	6SQ7	0-65
6AL5W	0-65	6V6GT	0-60
6AM5	1-60	6X4	0-45
6AM6	0-65	6X5G	0-45
6AN8	0-85	6X5GT	0-55
6AB30	0-50	6Y6G	0-85
6AOSW	0-85	6Z4	0-65
6AS6	0-60	6-30L2	0-90
6AT6	0-65	7B7	0-60
6AU6	0-40	7Y4	0-80
6AV6	0-50	9D2	0-60
6AX4GT	0-80	9D6	0-75
6AX5GT	1-00	11E3	11-00
6B7	0-75	12A6	0-60
6BA6	0-40	12AL5	0-70
6BE6	0-45	12AT6	0-45
6B6G	1-00	12A7T	0-45
6B16	0-75	12A7U	0-40
6B07A	0-60	12AV6	0-80
6BR7	2-30	12AX7	0-40
6BV6	2-80	12BA6	0-50
6BW7	1-00	12BE6	0-60
6C4	0-40	12BH7	0-60
6C6	0-35	12C8	0-55
6CB6	0-50	12E1	4-25
6CH6	3-00	12J5GT	0-40
6CL6	0-75	12K7GT	0-60
6D6	0-50	12K8GT	0-70
6EA8	0-80	12Q7GT	0-50
6F8G	0-75	12SCT	0-55
6F12	0-65	12S7	0-55
6F17	1-00	12S7J	0-55
6F33	4-20	12Y4	0-40

POSTAGE: £1-£2.20p; £2-£3.30p; £3-£5.40p; £5-£10.60p; over £10 free, minimum order £1.

VIDECON TUBE TYPE P863B
English Electric—£20

1A57

1A57	1-00
19AQ5	0-75
19G3	10-00
19G6	6-00
19H5	17-00
20P3	0-60
20P4	1-10
251AGT	0-85
30C15	1-00
30C17	1-10
30C18	1-10
30F5	1-00
30FL12	1-20
30FL14	1-00
30L17	1-00
30P12	1-00
30PL1	1-00
30PL13	1-10
30PL14	1-10
35LGT	0-80
35W4	0-60
35ZAGT	0-70
50C5	0-70
50CD6G	1-20

1A57

TF 801D/1/S SIGNAL GENERATOR.
Range 10-485MHz in 5 ranges, R.F. output 0-1 V-I.V. Source C.M. 50Ω output impedance. Internal modulation at 1KHz at up to 90%.

TF 801B/2. Spec. as for 801D but minor circuit differences. Few only left.

TF 995A/1 or A/2 or A/2M or A5 SIGNAL GENERATORS. Very high class AM/FM 1-5MHz to 220MHz. Details spec. and price on application.

TF 995/3S with additional amplifier to give extra high output between 1-5 and 6 Mc/s.

1A57

TF 1400S DOUBLE PULSE GENERATOR WITH TM 6600S SECONDARY PULSE UNIT. Rep. freq. 10Hz to 100KHz, pulse with 0-1 to 100μ sec. delay —1-5 to +3000μ sec., rise time 30 sec.

TF 144H SIGNAL GENERATOR HIGH FREQUENCY SPECTRUM ANALYSER. MARCONI TYPE 1094A/S. Basic Freq. range 3 to 30 Mc/s and with LF unit from 100Hz to 2MHz. Measures relative amplitudes up to 60dB.

TF 934 DEVIATION METER. 250MHz.

TF1041 B VALVE MULTIMETER. DC voltage from 300mV to 1,000V AC voltage from 300mV to 300V at up to 1,000MHz.

TF1370 R.C. OSCILLATOR FOR SQUARE & SINE WAVE. Freq. —31-6V rms 10Hz-1MHz square wave 0-73 2pp. 10Hz-100KHz.

1A57

SIEMENS LEVEL OSCILLATOR TYPE BEL 3W51B. Frequency from 10KHz to 17MHz. Modulation is external output from +10dB to -60dB in 8 steps and in continuance with wobler step generator. Imp output 150, 145, 135, 75, 65 ohms.

LEVEL OSCILLATOR TYPE REL 3W2S. Frequency from 0-3 to 1200 Kc/s. Modl ext. output from +10dB to -60dB. Impedance output 75, 140, 600 ohms.

36-FOOT AERIAL MASTS consisting of 6 sections 6' 8" x 2 1/2" dia. Complete with all accessories to erect and instal.

AVO CT190 VALVE TESTERS LOW RESISTANCE HEADPHONES TYPE CLR £1-50. 40p postage VAT 12 1/2%.

AR88 D & LF SPARES. We hold the largest stock in UK. Write for list.

RF METERS. 0 to 6 amps 2 1/2" dia. USA. brand new £1-50 P&P 25p.

1A57

VAT TEST EQUIPMENT 8%

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when un-749 3934, trade and avoidable.

1A57

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc.: retail and export 743 0899.

RHODES & SCHWARZ

Z-g DIAGRAPH TYPE 2DU 30-420MHz 50Ω. Directly measures multiterminal networks, phase shift, phase angle with complementary POWER SIGNAL GENERATOR TYPE SMLM high freq. resolution, internal, external mod. up to 3v out.

FREQUENCY SYNTHESIZER TYPE XUA. 30Hz-30MHz with FREQUENCY INDICATOR TYPE FKM 15-30MHz 30-100MHz.

UHF SIGNAL GENERATOR TYPE SMLM from 30 to 303MHz.

UHF SIGNAL GENERATOR TYPE SLSL from 300 to 300-940MHz.

FREQUENCY INDICATOR TYPE FKM from 30 to 1,000MHz.

C.R. TUBES

DG7-5	15-00	3BF1	8-00
DG13-2	22-00	5FP7	10-00
MW13-35	85J	8-00	
	35-00	88L	8-00
VCR139A		VC1526	10-00

BARROW DRUM

(Trolley) WD Mk III on pneumatic wheels.

PANEL METERS

Voltmeters—Micro Ammeters. Milli Ammeters—Large Selection.

545A. Bandwidth DC to 30MHz (3dB down at 30MHz) ± 1dB, depending on plug-in unit. Specification and price on request.

570 CHARACTERISTIC CURVE TRACE

570A OSCILLOSCOPE wide band high voltage cathode ray oscilloscope designed for observing and photographically recording wave from having extremely short rise times.

DANA EXACT FUNCTION GENERATOR MODEL 121.

Frequency range 0-2Hz to 2MHz (7 ranges), voltage controlled to 10V sweep generator 1ms to 10 sec.

TEXSCAN ELECTRONIC SYSTEM ANALYZER MODEL 9990.

Frequency range 10MHz to 300MHz with market controls.

FURZELL SENSITIVE VALVE VOLTMETER TYPE V200A

full scale from 10mV to 1000V in 6 steps with output amplifier.

TRAINING SET for Radio Operators

with 10 key terminals and control frequency and volume.

TRANSMITTER RECEIVER.

Transmitter Type M9 receiver Type M17 with fixed frequency range 240MHz.

TEST SET FT2 for testing Transceivers A40

COLOMOR (ELECTRONICS LTD.)


120 Goldhawk Rd., London W.12

Tel. 01-743 0899

Open Monday to Friday

9-12.30, 1.30-5.30 p.m.

GREAT SOUND—GREAT VALUE!

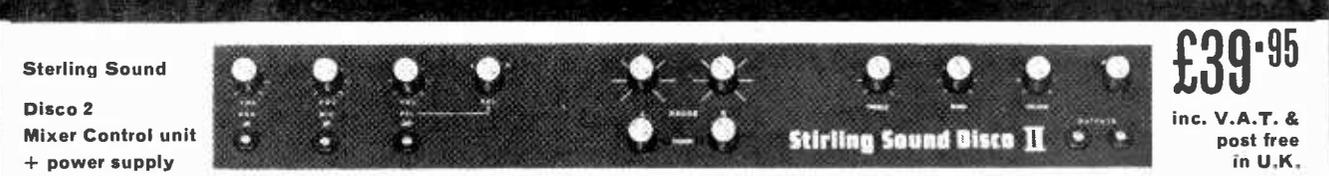

Sterling Sound Disco 2 Mixer Control unit + power supply

By designing and manufacturing in our own Essex factory, with strict material control and stage by stage checking and then selling direct to YOU, the customer, we can save you pounds, offer better service and guarantee satisfaction. Our latest modular assembly, Disco 2 has already been thoroughly field tested and is ready for immediate service under the toughest working conditions.

- **INPUTS**—Left deck, right deck, mic. and aux.
- **INPUT IMPEDANCE**—47K ohms
- **POWER SOURCE**—220-240V. A.C. Mains
- **CONTROLS**—Mains on-off, master volume, bass ±15db, treble ±15db, L and R mixing, L & R motor switches, selector switch for P.F.L. (Pre-Fade Listening), headphone volume, mic. vol., aux. vol., LED indicators on mains and decks on/off switches.
- **HEADPHONE AMPLIFIER**—Powerful 2 watts into 8 ohms; separate vol. control.
- **TERMINATIONS**—Five 1/4" jack sockets—2 input, 2 output, headphones.
- **SIZE**—23" x 3 1/2" x 2 1/4" max. depth to rear (plus separate power unit). Panel in matt black with controls sensibly grouped for easy handling.
- **PRICE**—Post free, with power unit and inc. V.A.T. **£39-95** Delivery ex-stock

SUITABLE STIRLING SOUND POWER AMPS. WITH HEAT SINKS AND POWER SUPPLY UNITS—140PH—£18. 160PH—£22. 1100PH—£26-75

Mail Orders to Dept. PW28
STIRLING SOUND, 37 VANGUARD WAY, SHOEBOURNESS, ESSEX (03708)

OTHER STIRLING SOUND DISCO/P.A. ITEMS

- **BASIC CONSTRUCTIONAL MODULES**
SS.104/2 Two channel mixer stage £3-75
SS.104/4 Four channel mixer stage £7-00
SS.DTM Output control stage. 30db variation on both treble and bass. Master vol. control. 3mV in for 2V out. 18V working voltage £6-75
- **STIRLING SOUND—LIGHT MODULES**
SSTL3/250 Three channels, each 250 watts output £9-25
SSTL3/1000 Three channels, each 1,000 watts £11-50
- **INTEGRATED POWER AMPLIFIERS**
Ready built in cases, tested and guaranteed —60 watts R.M.S. into 4 ohms
POWER AMP 60 with two channel mixer £48-00
POWER AMP 40—40 watts R.M.S. into 4 ohms with two channel mixer £43-00
POWER AMP. 100—100 watts R.M.S. into 4 ohms with 4 channel mixer £85-00
100 watt SLAVE AMP £50-00
- **READY BUILT ITEMS TESTED AND GUARANTEED**
SSTL3/250B Sound to light unit 3 channels, 250w. each £23-95
SSTL3/1000B Sound to light unit 3 channels, 1000w. each £25-95 £27-95

TO ORDER BY ACCESS OR BARCLAYCARD JUST WRITE OR PHONE IN YOUR NUMBER

ALL PRICES QUOTED INCLUDE V.A.T. AND GOODS SENT POST FREE IN U.K. with C.W.O. orders. Owing to length of time between preparing this ad and its appearance to the public, prices are subject to amendment without notice



5443 Shop & Showroom 220/224 West Rd., Westcliff-on-Sea (0372) 351048


MAINS INTERCOM



**NO BATTERIES
NO WIRES**
ONLY
£29.99
PER PAIR
+ VAT £3.75

The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1/2 mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom. between office and warehouse in surgery and in homes. P. & P. 99p.

4-STATION INTERCOM

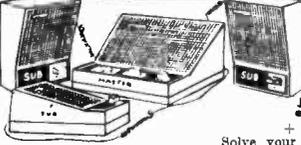

£19.95
+ V.A.T. £1.60

Solve your communication problems with this 4-Station Translator Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. A Battery and other accessories. P. & P. 99p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER




ONLY
£14.95
+ VAT £1.20

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume, conversation recording model at £19.95 + VAT £1.36. P. & P. 89p.

10-day price refund guarantee on all items.
WEST LONDON DIRECT SUPPLIES (PVT) LTD
169 KENSINGTON HIGH STREET, LONDON, W8
01-837 5548

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

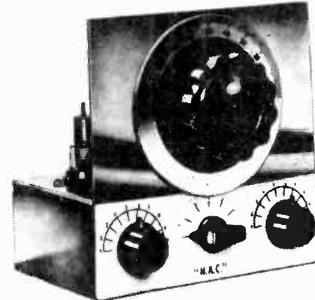

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Special offer AR8 valves—70p each.

1978 "DX" RECEIVER Mark III Complete kit—Price £9.00 (incl. p. & p. and V.A.T.). Customer who sent us five QSL cards, one from each continent writes: "Other countries of interest which I have heard are Korea, Japan, Sri Lanka, Liberia and many others. I was very surprised at the simplicity of the set, compared to its efficiency." This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.

SORRY, NO CATALOGUES WITHOUT S.A.E.
"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3Z

Please
mention
Practical
Wireless
when
replying
to
Advertisements

CHROMASONIC electronics

56 Fortis Green Road
Muswell Hill London N10 3HN
Telephone 01-883 3705

C-MOS


4000	18*	4049	58*	7442	52*
4001	18*	4050	58*	7445	70*
4002	18*	4051	86*	7447	59*
4006	1 09*	4052	86*	7448	65*
4007	19*	4060	1 16*	7451	16*
4009	62*	4066	22*	7470	27*
4010	62*	4070	22*	7472	22*
4011	18*	4071	22*	7473	27*
4012	21*	4081	22*	7474	27*
4013	53*	4082	22*	7475	40*
4014	1 00*	4510	1 24*	7476	30*
4015	97*	4511	1 54*	7485	76*
4016	58*			7486	27*
4017	97*			7489	2 32*
4018	97*			7490	38*
4019	58*			7492	41*
4020	1 08*	7400	16*	7493	42*
4021	87*	7401	16*	74107	27*
4022	88*	7402	16*	74121	27*
4023	19*	7403	16*	74123	49*
4024	78*	7404	17*	74141	41*
4025	19*	7408	19*	74145	95*
4026	1 76*	7410	16*	74151	49*
4027	58*	7413	27*	74154	85*
4028	87*	7420	16*	74174	72*
4029	1 18*	7427	28*	74192	86*
4040	1 08*	7430	16*	74193	86*
4042	83*	7441	56*	74196	97*

You can combine C-MOS & TTL for quantity discounts.
25 plus less 5%. 100 plus less 10%.

SEVEN SEGMENT DISPLAYS

LIGHT EMITTING DIODES

9-125" (inc. clip)	1+	10+	100+
TIL209 Red	15p	13p	11p
TIL212 Yellow (H.B.)	27p	22p	17p
TIL216 Red (H.B.)	27p	22p	17p
TIL232 Green (H.B.)	27p	22p	17p
TIL 220 Red	15p	13p	11p
TIL224 Yellow (H.B.)	30p	26p	20p
TIL228 Red (H.B.)	30p	26p	20p
TIL234 Green (H.B.)	30p	26p	20p
(H.B.)—High Brightness.			
LITRONIX All Red			
DL701 Com.A 0-30°+1	1 72*		
DL704 Com.C 0-30° R/H dec. pt.	1 72*		
DL721 Com.A 0-51° R/H Dou. dt.	3 04*		
DL746 Com.A 630°+1	2 43*		
DL747 Com.A 630° L/H dec. pt.	2 43*		
MONSANTO Green			
MAN51 Com.A 0-30° R/H dec. pt.	2 34*		
MAN52 Com.A 0-30° L/H dec. pt.	2 34*		
MAN53 Com.A 0-30°+1	2 34*		
MAN54 Com.C 0-30° R/H dec. pt.	2 34*		
Red			
MAN71 Com.A 0-30° R/H dec. pt.	1 52*		
MAN72 Com.A 0-30° L/H dec. pt.	1 52*		
MAN73 Com.A 0-30°+1	1 52*		
MAN74 Com.C 0-30° R/H dec. pt.	1 52*		
XCITON			
XAN362 C.A. R 0-30° L/H dec. pt.	1 81*		
XAN352 C.A. G 0-30° L/H dec. pt.	2 21*		
XAN82 C.A. Y 0-30° L/H dec. pt.	2 43*		

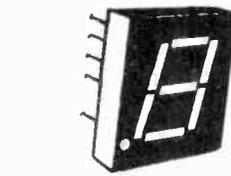

DL707 Com.A 0-30° L/H dec. pt.	1 72*
DL707R Com.A 0-30° R/H dec. pt.	1 72*
DL727 Com.A 0-51° R/H Dou. dt.	3 04*
DL750 Com.C 630° L/H dec. pt.	2 43*
Yellow	
MAN81 Com.A 0-30° R/H dec. pt.	2 34*
MAN82 Com.A 0-30° L/H dec. pt.	2 34*
MAN83 Com.A 0-30°+1	2 34*
MAN84 Com.C 0-30° R/H dec. pt.	2 34*
Orange	
MAN3610 Com.A 0-30° R/H dec. pt.	2 17*
MAN3620 Com.A 0-30° L/H dec. pt.	2 17*
MAN3630 Com.A 0-30°+1	2 17*
MAN3640 Com.C 0-30° R/H dec. pt.	2 17*

FREE OFFER

This Month's GIVEAWAYS
£1 00's Worth of Semicconductors
(2 x 7402, 1 x 741, 2 x 2N2926G,
3 x CIL108)
With every order £5.00 & over.
OUR NEW A4 I.C. BOOKLET
Supplied FREE with orders of any
I.C.'s worth £4.00 or more. Contains
Circuits, pin connections & Data.
(35p inc. P&P if sold alone).

LINEAR I.C.'s AUDIO I.C.'s

MC1352P		SN7653N2	1 55
TD A1352	1 20	SN7653N1	85
MC1327P		SN76660N	65
TD A1327	1 50	SN76666N	1 00
MC1330P	1 15	TA A263	2 50
MC1350P	1 00	TA A320A	75
MC1351P	1 00	TA A350A	2 70
MC1357P		TA A570	1 50
LM1211N	1 70	TBA1205	1 00
MC1375P	1 50	TBA231	1 00
MC1456CG	2 50	TBA520Q	2 00
MC1485L	4 90	TBA530Q	2 00
MC13302P	1 85	TBA540Q	2 00
MFC6030A	1 00	TBA550Q	2 00
NE540L	2 25	TBA651	2 25
NE548	2 15	TBA750Q	2 00
NE555	35*	TBA802	1 00
NE556	90*	TBA810S	1 10
NE560	4 40*	TBA820	1 10
NE561	4 40*	TBA900Q	2 00
NE562	4 40*	TC A730	4 69
NE565	1 40*	TC A740	4 89
NE566	1 65*	TC A940	1 75
NE567	1 85*	TC A2020	3 50
SL414A	1 90	UAA170	2 75*
SL145A	2 47*	UAA180	2 75*
SL440A	2 38*	UA A100	2 75*
SN75491N	95*	ZN414	1 10
SN75492N	1 15*	ZN417E	1 68
SN76001N	1 40	ZN423T	1 08*
SN76003N	2 45	ZN424E	1 35
SN76013N	1 60	ZN425E	3 78
SN76023N	1 60	ZN1034E	2 03
SN76033N	2 45	ZN1040E	8 43
SN76544N	1 55	ZN A116E	6 75*

I.C. SOCKETS

8 pin 10p*	16 pin 14p*	28 pin 30p*
14 pin 12p*	24 pin 26p*	40 pin 44p*
I.C. pins 100	54p*	1,000 £3.78*

LINEAR I.C.'s AUDIO I.C.'s LINEAR I.C.'s AUDIO I.C.'s

uA 748 (14 pin DIL)	60	CA3089/TDA1200	2 30	LM372N	1 75
uA748 (TO99)	65	CA3090Q	4 25	LM373N	2 99
uA753 (8 pin DIL)	1 95	CA3123E/LM1820	1 50	LM377N	1 95
AY-1-0212	6 50	CA3097E	1 75	LM380N-8	1 00
AY-1-9051	1 65	CA3130S	99	LM380N	99
AY-5-1224A	3 39*	CA3140S	99	LM381N	1 75
AY-5-3507	5 99*	CA3160S	1 60	LM382N	1 35
AY-5-4007	7 99*	CA3600E	1 75	LM3900N	85
CA3045	1 50	LM301AN (8 pin)	40	LM3905N	1 50*
CA3046	80	LM301AT (TO99)	50	LM3909N	70*
CA3053	85	LM308N (8 pin)	90	MC1303/LM1303N	1 10
CA3075	2 00	LM308T (8 pin)	1 40	MC1310P	1 80
CA5080	80	LM339N	1 00	MC1312P	2 15
CA3081	1 50	LM370N	2 75	MC1314P	3 50
CA3082	1 50	LM371	1 75	MC1315P	6 10

VAT INCLUSIVE PRICES

Items followed by a * include V.A.T. @ 8% all others include 12 5% ALWAYS PLEASED TO SEE PERSONAL CALLERS
TRADE AND EXPORT CUSTOMERS MOST WELCOME Overseas Customers deduct 2/27 from items marked with a * 1/9 from others



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

BRAND NEW COMPONENTS BY RETURN.

Electrolytic capacitors 10V, 25V, 50V.—0.47, 1.0, 2.2, 4.7 & 10mfd.—5p. 22, 47—5p. (50V—8p). 100—7p (50V—8p) 220—8p. (50V—10p) 470—11p. (50V—10p) 1000/10V—15p. 1000/25V—18p. 1000/50V—22p.

Subminiature bead tantalum electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 @ 35V, 4.7/25V—11p. 10/25V—13p. 22/10V, 47/6V, & 100/3V—15p.

Mullard miniature ceramic E12 series 2% 83V. 10pf. to 47pf.—3p. 56pf. to 330pf.—4p.

Vertical mounting ceramic plate 50V. E12 series 22pf-1000pf. E6 series 1500pf-47000pf.—2p.

Polystyrene E12 series 63V horizontal mounting. 10pf to 1000pf.—3p. 1200pf. to 10000pf.—4p.

Mullard polyester 250V vertical mounting E6 series. 0.1 to 0.1—4p. 0.15, 0.22—5p. 0.33, 0.47—8p. 0.68—11p. 1.0—13p. 1.5—20p. 2.2—22p.

Mylar (Polyester) Film 100V vertical mounting. 0.001, 0.002, 0.005—3p. 0.01, 0.02—4p. 0.04, 0.05—4p.

Miniature resistors Highstab E12 series 5%. Carbon Film 0.25W 10 to 10MΩ. (10% over 1MΩ)—1p. Metal Film 0.125W, 0.25W & 0.5W 10Ω to 2MΩ.—1p. Metal Film 1W. 27Ω to 10MΩ.—2p ea.

1N4148—3p. 1N4002—5p. 1N4006—7p. 1N4007—8p. BC107/3/9, BC147/8/9, BC157/8/9 & BF194 & 197—8p. Fuses 20mm. glass. 1½" glass & 1" ceramic. 21p. Post 10p. (Free over £4.00) Prices inclusive of VAT.

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8.

ELECTRONIC CENTRE (STOCKPORT) LTD., 45 Lower Hillgate, Stockport. Tel: 061-480 9791. Packs for DIY enthusiasts. Resistors 100 £1.00, mixed semiconductors large bag £1.20, capacitors various £1.10, thyristors 8A 100V 15 £1.00, rectifier bridges 3A 50V 6 £1.00, 741 OP Amps 5 £1.00. Many other items. SAE with enquiries please. C.W.O. under £2 add 20p.

VALVES

Radio - T.V. - Industrial - Transmitting We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves.

COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering, Sussex PO20 8BN West Wittering 2023 (STD Code 024366)

TEST METER PANELS, £2. Ex-GPO pliers and cutters, 75p each. Transistor Amplifiers, 75p each. P&P 50p per order. ARCHER, Box 139

SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.80 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

ORCHARD ELECTRONICS

I.C.s TTL, C/Mos. Linear. Capacitors. Resistors. (E12) SIL/Rectifiers. Diodes. LED. Thyristors. Zeners. Voltage Reg. DIL Sockets. Bridge Rectifiers. Potentiometers. Presets. Triacs. Diac. Plugs. Sockets. Cable. Vero. Carefully selected range, excellent despatch service Same day turn round. S.A.E. List. Suppliers to A.E.R.E. U.K.A.E.A. Governments Depts. Schools. Universities. Manufacturers. Accounts opened for trade and amateur. Join the professionals. Phone by 4 p.m. Goods out 1st class by 5 p.m. Try us and prove it!

ORCHARD ELECTRONICS
Flint House, High Street, Wallingford, Oxon. Telephone 0491-35529

GAMMA ENTERPRISES for transistors, resistors, capacitors, ICs, hardware, etc. Large SAE for catalogue. 18 Landale Road, Peterhead, Aberdeenshire AB4 6QP.

NOSTALGIA VINTAGE RADIO COLLECTING

1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet. Full 1977 catalogue, 70p post paid.

TUDOR REES (Vintage Services), 64, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 565472.

LED's. Mixed bags of 4 different sizes and 4 different colours. 50 at £5.25, 100 at £9.25 including VAT and post and packing. CWO. Michael Williams Electronics, 47 Vicarage Avenue, Cheadle Hulme, Cheshire, SK8 7JP.

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated Touch Plates. Easy to follow instructions. TSD300K—TOUCHSWITCH & DIMMER combined. ONE touch plate to switch light on or off. Brightness controlled by small knob—£5.20. TS300K—TOUCHSWITCH. TWO touch plates—£4.00. TS A300K—AUTOMATIC. ONE touch plate. Light turns off after preset delay—£4.00.

LD300K—LIGHT DIMMER KIT—£2.80.

400V TRIACS		BULK OFFERS		CMOS	
Plastic		BC148	£7/100*	4001	18p
3A	63p	555	£22/100	4007	18p
8.5A	78p	741	£18/100	4011	18p
12A	84p	8A/400V Triac	£71/100	4013	51p
15A	105p	DL727 dual 0.5" 7 seg.		4015	91p
20A	155p	LED Display	£62/50	4016	51p
6.5A with trigger	80p	555 36p (3 for £1)		4040	97p
Diac	21p	741 24p (5 for £1)		4049	51p

CLOCK 1KW APPLIANCE TIMER KIT Inc. AY-5-1230, 0.5".

LED display, triac, switches, box pcbs, etc. £16.25

AY-5-1230 CLOCK APPLIANCE TIMER IC £4.85

LM3911 THERMOMETER/TEMPERATURE CONTROL IC. £1.00

QUANTITY DISCOUNTS ON REQUEST

Add 8% (*12½%) VAT + 25p P&P. Mail Order Only to:

T.K. ELECTRONICS (PW)
106 Studley Grange Road, London W7 2LX

CRYSTAL CALIBRATOR!

Put yourself spot-onto any frequency in the LW, MW, SW, or VHF bands. Ingenious circuit gives cw. or int.AM. giving audible tone on harmonics of 1MHz, 100KHz, or 10KHz. Complete KIT only £12.72+8% VAT

or send 15p (not stamps) for details

ROCQUAINE ELECTRONICS

Aldebaran, Le Coudre, St. Pierre-du-Bois, GUERNSEY.

TIRRO ELECTRONICS the mail order division of Ritro Electronics UK offers a wide range of components for the amateur enthusiast. Large SAE or 20p brings list. Grenfell Place, Maidenhead, Berks. SL6 1HL.

BARGAIN SUPPLIES

Barrel kits for £1.99p. Guaranteed 50% or higher yield. 100% money back if not absolutely delighted. 50 pieces SN7400 series may include gates registers, flip flops, who knows? or 50 pieces linear, op-amps etc. 741, 709 555 you to sort, or 50 plastic transistors BC182/4/212 lots of 2N no's, or 6 LED readouts, factory returns—we've no time to test. 100% good devices, our 'A' type barrels all fully tested and guaranteed: £1.99p each. 35 TO3 power transistors, or 4 240/12-0-12 100mA transformer plus power supply P.C.B. brand new, or 200 500mA. 400V. PIV silicon diodes, or 200 capacitors all types all values, or 12 push to make switches red/yellow/green or 1 calculator keyboard 0-9 2 blanks. Please add 30p per line postage and packing all prices include VAT. **JONES SUPPLIES, 588, ASHTON RD. OLDHAM. LANCs. 061-652-9879.**

TRANSISTORS, Resistors, Caps, Pots, plugs 7 sockets, zeners, TTL, cable, boxes, all at very good prices. 65 Railway Road, Leigh, Lancs. Telephone Leigh 679575.

Books and Publications

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique. TV Publications (Ause PW), 76 Church Street, Larkhall, Lanarkshire.

THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens.

This book is a must for the keen home constructor. Latest technology DIY speaker designs. Contains full plans for infinite baffle and reflex designs for 10-100 watts, also unusual centre-bass system for those who want Hi-Fi to be "Heard and not seen". £1.95 (£2.20 post paid. \$5 Overseas).

VAN KAREN PUBLISHING
5 SWAN STREET
WILMSLOW
CHESHIRE

HOW TO START A BUSINESS. By popular demand a fully illustrated manual has now been produced, showing, in easy, step by step, stages, how to rewind ARMATURES & FIELD COILS as used in Vacuum Cleaners, Drills and Portable Tools. Chapters on taking data, materials required, test instruments required, rewind instructions, charts, etc. How to cost instruction manual £4.00 plus 30p P & P. CWO. COPPER SUPPLIES, 102 Parrswood Road, Withington, Manchester 20. Dept. PWA.

Radio Receivers

MULTIBAND RADIOS. 12 band . . . Marine, Aircraft, LP5B, HP5B, UHF (430/470), SW1/4, MW, LW, FM, RF gain. BFO. £150. GRUNDIG SATELITT £199. BFO Units, £16.50. SHARP MW/Aircraft, £13. Langtons, High Street, Rocester, Staffordshire. SAE lists.

Service Sheets

SERVICE SHEETS — COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p. Please send large Stamped Addressed Envelope. We can supply manuals for most makes of Colour Television Receivers by return of post.

B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON H.M.V. MARCONI AND MANY MORE

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court. S.A.E. for details. MAIL ORDER ONLY

G. T. TECHNICAL INFORMATION SERVICE

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV, etc., 75p plus SAE. Colour TV Service Manuals on request, SAE with enquiries to BTS, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and SAE. Catalogue 25p and SAE. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio TV, etc., 10,000 models. Catalogue, 24p, plus SAE with orders, enquiries, Telray, 154 Brook Street, Preston PR1 7HP.

LARGE SUPPLIER OF SERVICE SHEETS

All models at 75p plus s.a.e. except colour and Car Radios. Free TV fault finding chart or TV list.

C. CARANNA

71 Beaufort Park London NW11 6BX
01-458 4882

Aerials

G2DYM ANTI-TVI AERIALS

DO OVERCOME TVI PROBLEMS FOR BOTH THE SWL & TRANSMITTING AMATEUR. A 12½p SAE and 39p Stamps bring you full details, article on aerials and copies of genuine testimonials from satisfied customers with their names and full addresses.

LAMBDA, WHITEBALL, WELLINGTON, SOMERSET

For Sale

NEW ISSUES of "Practical Wireless" available from April 1974 edition up to date. Price 65p post free. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0243) 55885.

94 ISSUES OF PRACTICAL WIRELESS, May 63 to March 76. Offers Mr. S. Elson, Flat 253 Cannock Road, Chadsmoor, Staffs.

EDITIONS OF P.W. AND P.E. from Jan 1967-Dec 1977. 50p per copy, including postage; or £30 for the lot if collected. 214 Chorley New Road, Bolton. Tel (0204) 42545.

Wanted

WANTED. Valves, types PX4 and PX25, new or S/Hand; any quantity. Rees, 64 Broad Street, Staple Hill, Bristol. Tel: 0272 565472.

WANTED. New Valves, Transistors. Top prices, popular types. Kensington Supplies (C), 367 Kensington Street, Bradford 8, Yorkshire.

SURPLUS??? Turn it into cash. Phone 0491 35529 (Oxon).

WANTED NEW Valves, transistors, I.Cs, amplifiers, receivers, televisions (Anything Useful) any quantity. Stan Willetts, 37 High Street, West Bromwich. Tel: 021-553 0186.

CODAR PRESELECTORS, new or used. Write Glasson, 34 Minard Rd., London SE6.

"RADIO AND TELEVISION SERVICING" books wanted from 1964-65 edition up to date. £3.00 plus postage paid per copy by return of post. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

COURSES—Radio Amateurs Examination, City & Guilds. Pass this important examination and obtain your G8 licence, with an RRC Home Study Course. For details of this, and other courses (GCE, Professional examinations, etc.), write or phone: **THE RAPID RESULTS COLLEGE**, Dept. JX1, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service) or for a prospectus only ring 01-946 1102 (24hr recording service).

TELEVISION TRAINING

12 MONTHS' full-time course in Radio & TV for beginners. (GCE—or equivalent—in Maths. and English).

26 WEEKS' full-time course in Mono & Colour TV. (Basic electronics knowledge essential). **13 WEEKS'** full-time course in Colour TV. (Mono TV knowledge essential).

These courses incorporate a high percentage of practical training.

NEXT SESSION commences on
April 17th.

Prospectus from: London Electronics College, Department B2, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions.

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME

ADDRESS

Send to: Classified Advertisement Manager
PRACTICAL WIRELESS,
GMC, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5846

Rate
20p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

Electrical

LIST NO. 28 now ready—Styli illustrated equivalents also cartridges, leads, etc., free for long SAE. Felstead Electronics (PW), Longley Lane, Gatley, Cheshire SK8 4EE.

TIMESWITCHES. Cheap timeswitches. Sangamo 20 amp reconditioned guaranteed for one year. Only £3.70. Also electric eyes. Write:— J. Donohoe, 1 Upper Norfolk St., North Shields, Tyne & Wear.

Ladders

LADDERS. Varnished 20ft 9in extd., £28, carr. £2.40. Leaflets. Also aloft ext. up to 62ft 6in. Ladder Centre (WLS2), Halesfield (1) Telford. Tel: 586644. Callers welcome.

Miscellaneous

ARMATURE & COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied. All orders dispatched within 24 hrs.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.80
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices are inclusive of P. & P. in U.K.

COPPER SUPPLIES, 102 Parrswood Road, Withington, Manchester 20. Tel: 061-445 8753

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept No 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination. Cassette B: 12-24 w.p.m. for professional examination preparation. Morse by light system available. Morse Key and Buzzer Unit for sending practice.

Prices each Cassette (including booklets) £4; Morse Key and Buzzer £4. Prices include postage etc., Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept PW)
12 Longshore Way, Milton,
Portsmouth PO4 6LS

MONITOR RECEIVERS Marine or 2M amateur and other station accessories. SAE for details. MDH Radiotelephones, Munster House, Priory Road, Milford Haven, Dyfed. Tel. 06462 5534.

GOVERNMENT SURPLUS

Super Pack 40 Plus

1 12v reversible motor, 5 reed switches (open), 10 micro switches with leads, 5 D.P. Toggle switches, 4 magnetic Microphone/Speakers, 1 spring coil cable, 4 lengths 3 to 15ft multicore cable colour coded and spaded, 5 small magnets, 5 mini (1 x 1/2") electro magnets PLUS
Send £2.50 plus 50p P & P to **B. B. Supplies (Dept PW)**
125 High Street, Deal Kent. Tel. 03045 82573.
Trade please note new address and telephone number for enquiries.

OUTSTANDING 2200 Hi-Fi FM Tuner. Full coverage 88-102MHz. Varicap tuning. Latest silicon superhet design. Ideal for push button/manual tuning, only £9.95. Unique 3300 stereo class A Amplifier, power 32 watts peak, complete stereo Pre-Amplifier/2 Power Amplifiers, all inputs accepted. Only £10.95. 5500 Tuner Amplifier plus specification as above 2. Only £19.95. All equipment built, tested and guaranteed with full instructions. (P&P 50p.) **GREGG ELECTRONICS, 86-88 Parchmore Road, Thornton Heath, Surrey.**

SINTEL KITS, COMPONENTS, CMOS etc.

MOT. CMOS Databk 3-50 RCA CMOS Databk. 5-45
8800 Appl. Man. 12-95 280 Ass. Lang. Prog. Man.
NS TTL Databk. 2-10
Best of Byte Vol. 1 11-95 Z80-CPU Man. 5-60
All items CWO (Books-No VAT) 35p p&p.
Full range in our FREE **SINTEL, P.O. BOX 75F,**
CATALOGUE which **209 Cowley Road, Oxford**
will be sent by return. **Tel.: (0865) 49791.**

VERO Cases 19in x 12in x 4in Cat. No. ICD-2U-8, ideal for amplifiers. Test Gear. £6 each. 01-555 3755.

LOW COST ALUMINIUM BOXES with lids and screws. 3 x 2 x 1-42p, 4 x 3 x 1 1/2-49p, 4 x 3 x 2-56p, 6 x 4 x 2-62p, 6 x 4 x 3-72p, 8 x 6 x 2-97p, 8 x 6 x 3-£1.08. Prices include p&p. **Harrison Bros., P.O. Box 55, Milton Road, Westcliff-on-Sea, Essex SS0 7LQ.**

BUILD THE TREASURE TRACER MK III Metal Locator



- Varicaps tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield.
- Speaker and earphone operation
- 4,000 already sold
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete **£15.95** Built & tested **£20.95**
Post £1.20 + £1.57 VAT Post £1.20 + £1.77 VAT

MINIKITS ELECTRONICS,
10 CLEVELAND ROAD,
LONDON, E15 2AN (Mail order only)

NEED A HAND? Kits, projects built to your requirements by professional engineer. **K.E.S., 12 Woodside Court, Selbourne Road, Littlehampton, Sussex. Tel: 21858.**

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' Hardware. Printed circuit boards, top quality for individual designs. Prompt service. Send 25p for catalogue from:

RAMAR CONSTRUCTOR SERVICES
Masons Road, Stratford-on-Avon, Warwicks
Tel: 4879

IMMEDIATE BY RETURN DELIVERY. Large range of miniature synchronous motors, many speeds 1 rev per hour to 1 rev per 2 days. £1.10 to £2.50 each. 3 and 4 digit mechanical counters, 45p to 85p. 10 amp micro switches at 20p. SAE for list. **WALES (ELECTRICAL) LTD., Queen St., Newton Abbot.**

BURGLAR ALARM SYSTEMS! 12v siren £5-53, 240v siren £9-61, plastic coated and lettered bell box £5-25. Flush magnetic contact 60p, surface 65p. SAE for price list. **C.W.A.S., 11 Denbrook Walk, Bradford BD4 0QS. Bradford 682674.** All prices fully inclusive.

NO MORE DING-DONG

Now get MUSIC from your DOORBELL—or your CAR. New programmable Chime announces you or your surprised guests. 119 easy-to-change tunes or PROGRAM YOUR OWN. Just needs speaker and existing bell transformer or 12V. All parts, instructions and programs, postage, money back assurance, send £17.90 TODAY.

CAMBRIDGE KITS

45 (PB), Old School Lane, Milton, Cambridge

STABILISED P.S.U.s, large range of various voltages and currents, available cased or in chassis form. SAE for full particulars and prices. **A. BARTON, PW, Highbanks, Newport Road, Sandown, I.W.**

3 1/2 DIGIT DVM MODULE KIT. Autozero, autopolarity only £37.50. SAE details. **MLC, 116 College Road, Southwater, Horsham, Sussex.**

ENAMELLED COPPER WIRE

SWG	1 lb	8oz	4oz	2oz
14-19	2-40	1-20	.69	.50
20-29	2-45	1-60	.82	.59
30-34	2-80	1-70	.89	.64
35-40	2-85	1-90	1-04	.75

Inclusive of p&p and VAT.

SAE brings Catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY
PO Box 30, London E4 9BW
Reg. Office: 22 Coningsby Gardens,

H. M. ELECTRONICS

276a FULWOOD ROAD, BROOMHILL,
SHEFFIELD S10, 3BD.

REC. CABINETS (Illus'd)

METAL CASES
DRY TRANSFER LETTERING

Send 15p for leaflets (Refundable)
Trade enquiries invited



Sonic

HI-FI DISCOUNT CENTRES



DISCOUNT SPEAKERS

Imp 8 or 15Ω as app.
Guarantees:
TITAN 5 years
FANE 2 years
OTHERS 1 year
ALL PRICES INC. VAT
Prices correct at 27.10.77

HI-FI TYPES

	List/Value	Sonic Price
5" FANE 501 Mid or Full range	Sp. Price	£4.95
8" x 5" 15w Various makes	Sp. Price	£3.35
8" A.F. Model 80 Dual Cone	Sp. Price	£5.95
8" A.F. Model 83 Dual Cone	Sp. Price	£6.95
FANE 805	Sp. Price	£4.95
FANE 804	Sp. Price	£4.95
FANE 801 Dual Cone	Sp. Price	£7.95
FANE 8" 808T Dual Cone	Sp. Price	£3.95
FANE 8" 807TP	Sp. Price	£4.75
WH'FEADALE L'TON 3XP Kit Pr.	£60.70	£44.95
10" DENTON 2XP KIT Pr	£39.15	£27.95
10" GLENDALE 3XP KIT	£92.44	£29.95
8" FANE MODEL ONE KIT	Sp. Price Pair	£19.99
10" ELAC MODE 10RM	Sp. Price	£3.85
12" FANE 121/15LR 20w	Sp. Price	£7.95

GROUP/DISCO TYPES

12" FANE POP 15 15-20w	Sp. Price	£4.75
12" FANE POP 25T 25-30w	Sp. Price	£9.95
12" TITAN T12/45 45w	£15.80	£10.95
12" TITAN T12/60A 60w	£22.50	£12.95
12" TITAN T12/100A 100w	£36.00	£22.95
12" CELESTION G12M	£16.50	£12.99
12" CELESTION G12H 30w	£22.00	£15.95
12" CELESTION G12/50 50w	£25.75	£17.90
12" CELESTION G12/50TC	£28.00	£17.95
12" GOODMANS 12 PD	Sp. Price	£18.95
12" GOODMANS 12 PG	Sp. Price	£17.95
12" FANE 'SPECIALIST' P.A. 80	£26.95	£17.95
12" " DISCO 80	£28.95	£18.95
12" " DISCO 100	£30.95	£20.95
12" " GUITAR 80L	£26.95	£17.95
12" " GUITAR 80B	£27.95	£18.95
12" FANE CRESCENDO 12A 8Ω	£57.35	£39.99
12" FANE " 15Ω	£57.35	£39.95
12" FANE " 12L 8Ω	£59.95	£41.95
12" FANE " 15Ω	£59.95	£39.95
12" FANE " 12 BASS 8Ω	£56.70	£39.95
12" FANE " 15Ω	£56.70	£39.95
15" TITAN T15/60 60w	£26.00	£18.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£28.95
15" FANE 'SPECIALIST' BASS 85	£39.95	£29.95
15" " BASS 100	£42.00	£31.95
15" GOODMANS 15P	Sp. Price	£23.95
15" CELESTION G15C	£36.00	£28.95
15" FANE CRESCENDO 15/100A 8Ω	£72.95	£49.95
15" FANE " 15Ω	£72.95	£44.95
15" FANE CRESCENDO BASS	£76.00	£49.95
15" " 15/100LT	£74.69	£49.95
15" " 15/160 160w	£95.00	£65.95
15" " 15/125A	£95.00	£69.95
15" " COLOSSUS 200w	£108.00	£69.95
18" TITAN T18/100 100w	£47.00	£38.95
18" GOODMANS 18P	Sp. Price	£39.95
18" CELESTION G18C	£53.00	£39.95
18" FANE CRESCENDO 18A	£101.95	£69.95
18" FANE CRESCENDO BASS	£89.95	£59.95
18" " COLOSSUS 200w	£115.00	£69.95

HORN UNITS

CELESTION MH1000 25w	(Carr. 75p)	£17.00	£13.75
FANE 910 MK II 50w		£10.95	£10.99
" 920 100w		£59.95	£42.45
" J44 30-50w		£7.95	£4.95
" J73 50w		£11.75	£6.79
" J104 50-70w		£16.95	£9.75

HIGH POWER 'CROSS-OVERS'

FANE HPX1R or HPX2R Carr. 35p £3.25 £2.25

ADD-ON HIGH FREQUENCY UNITS

F.A.L. 'Add-on' Carr. £1	£51.84	£38.95
TITAN T1H 70w Carr. £1	£33.00	£23.95
TITAN T52H 100w Carr. £1	£33.00	£23.95
TITAN T2H Carr. £1	£39.00	£26.95

EXTRA SPECIAL MAIL ORDER OFFER

TITAN TA50A 50w AMPLIFIER

High sensitivity. Multi purpose three ind. controlled inputs. Controls: Bass, Treble & Presence. Robust, well styled compact cabinet Black Vynide covered. Attractive Black/Silver Fascia. 12 months Guarantee. Carr £1 **£39.95**

Also for personal shoppers only

AMPS, TTABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, CREDIT TERMS AVAILABLE orders £20 over

Phone orders accepted from Access & Barclay card holders.

Branches at
GLASGOW
403 SAUCHIEHALL STREET
Tel: 141 332 0700
24 NEWGATE SHOPPING CENTRE
NEWCASTLE

Tel: 0632 25168

Mail Orders & Export enquiries to NEWCASTLE Branch. Add 60p carr. on Hi-Fi spkrs. or kits. Otherwise add 95p (12" spkr.) £1-50 (15" £2-50 (18" £3-50)

Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive, instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11½in x 8½in and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems.

£7-10

plus 90p packing and surface post anywhere in the world.

Overseas customers should send for proforma invoice

Quantity discounts available on request. VAT zero rated.



Also available—a more elementary course assuming no prior knowledge except simple arithmetic.

Digital Computer Logic and Electronics

In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

£4-60

plus 90p P. & P.

Offer Order both courses for the bargain price **£11-10**, plus 90p P. & P.—a saving of £1-50.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

NEW from Cambridge Learning Enterprises:

FLOW CHARTS AND ALGORITHMS—use, design and layout; vital for computing, training, wall charts, etc.

£2-95
plus 45p P. & P.

Guarantee—If you are not entirely satisfied your money will be refunded.

Cambridge Learning Enterprises, Proprietors: Drayridge Ltd. Registered in England No. 1328762.

Reg. Office: Cambridge Learning Enterprises, Unit 7, FREEPOST Rivermill Lodge, St. Ives, Huntingdon, Cambs. PE17 4BR

*Please send me . . . set(s) of Design of Digital Systems at £8-00 each, P. & P. included

*or . . . set(s) of Digital Computer Logic and Electronics at £5-50 each, P. & P. included

*or . . . combined set(s) at £12-00 each, P. & P. included

*or . . . the Algorithm Writers Guide at £3-40 each, P. & P. included

Name

Address

*delete as applicable

No need to use a stamp—just print FREEPOST on the envelope.

PW2

Stirling Sound


OUR UNIQUE BARGAIN PLAN CLOSES JAN. 31ST

STIRLING POLICY means specs. and prices you can rely on—no hidden extras—nothing to misunderstand. Until Jan 31st, when ordering a power amp. and power supply unit together

DEDUCT	<i>If ordered</i>	DEDUCT	<i>If ordered</i>	DEDUCT
5%	<i>with</i>	A	<i>with</i>	A
	UNIT ONE	FURTHER	UNIT TWO	FURTHER
		£1-00		£1-18

AMPLIFIERS 3 to 100 WATTS R.M.S.

Ready assembled on P.C.B.s., tested and guaranteed. Easy to connect. With instructions. Output ratings ± 1dB.

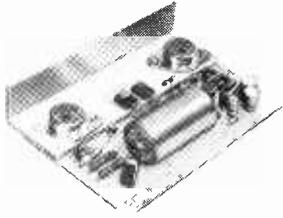
SS.103	I.C. amp. 3 watts R.M.S. using 20V/8Ω or 14V/4Ω. Input 100mV.	£2-85	
SS.103-3	Stereo version of above, 2 I.C.s	£5-00	
SS.105	5 watts R.M.S. into 3Ω using 13.5V. Sensitivity — 30mV. THD — 0-3%. 3½" x 2" x 1".	£3-95	
SS.110	10 watts R.M.S. into 4Ω using 24V. Sensitivity — 60mV. THD — 0-3%. 3½" x 2" x 1".	£4-85	
SS.120	20 watts R.M.S. into 4Ω using 34V. Sensitivity — 80mV. THD — 0-3%. 3½" x 2" x 1".	£5-15	
SS.125	25 watts R.M.S. into 8Ω using 50V. Sensitivity — 140mV. Distortion — Less than 0-05% into 8Ω S/N better than 70dB.	£7-25	
SS.140	40 watts R.M.S. into 4Ω using 45V. Sensitivity — 300mV. Distortion typically 0-1%. 5" x 3½" x 1½".	£6-50	
SS.160	64 watts R.M.S. into 4Ω using 50V. Sensitivity — 350mV. Distortion typically 0-1%. 5" x 3½" x 1½".	£8-50	
SS.1100	100 watts R.M.S. into 4Ω using 70V/2A. Input sensitivity — 500mV. Distortion at half-power, typically 0-1%. 5" x 3½" x 1½".	£10-50	
HS.160	Multi-finned heatsink for SS.140 or SS.160.	75p	
HS.1100	Ditto for SS.1100	£1-50	

THE CONTROL AND PRE-AMP MODULES

UNIT ONE
Combined stereo pre-amp & active tone control unit. Input sensitivity 50mV for 200mV out, 10/10V operation. Bass ± 15dB at 30Hz; Treble ± 15dB at 10KHz; Balance control; Volume control. For ceramic P.U. radio or tape inputs. WITH FREE CONTROL PANEL FASCIA **£9-00**

UNIT TWO
With control facilities similar to UNIT ONE but for magnetic cartridge input. R.I.A.A. corrected. Input sensitivity — 5mV for 200mV out (can be varied). WITH FREE CONTROL PANEL FASCIA **£12-43**

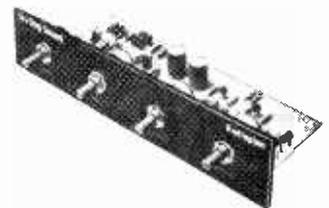CONTROL PANEL FASCIA available separately **50p**
SS.100 basic active stereo tone control module to provide ± 15dB on base at 30Hz and on treble at 10KHz. **£3-00**
SS.101 Stereo pre-amp suitable for ceramics, tape, radio, etc. **£2-75**



SS.102 Stereo pre-amp for mag. pick-ups. R.I.A.A. corrected **£4-45**
F.M. STEREO DECODER, phase lock loop type, with LED indicator showing when a stereo transmission is being received **£5-25**

POWER SUPPLY UNITS

Every Stirling Sound Power Unit is tested and guaranteed under working conditions before despatch. All units except SS.312 include a stabilised low voltage take-off point (13-15V) for pre-amp, tone control, radio tuner, etc. Outputs quoted minimal unloaded ratings.

SS.312	12V/1A	£6-60
SS.318	18V/1A	£6-95
SS.324	24V/1A	£7-65
SS.334	34V/2A	£8-75
SS.345	45V/2A	£10-75
SS.350	50V/2A	£11-75
SS.360	60V/2A	£12-75
SS.370	70V/2A	£14-75

SS.310/50 Stabilised power supply unit with variable output from 10V to 50V/2A. Short circuit protected **£17-75**

SS.300 Power stabilising unit variable from 10 to 50V/8A for adding to un-stabilised supply units **£5-50**



ALL GOODS POST FREE IN U.K. ALL PRICES INCLUDE V.A.T. Prices subject to alteration without notice. Order to Dept. PW28A.

STIRLING SOUND, 37 VANGUARD WAY, SHOEBOURNESS
ESSEX Phone (03708) 5543

Shop & Showroom 220/224 West Rd., Westcliff-on-Sea. Phone Southend (0702) 351048

ACCESS OR BARCLAYCARD CUSTOMERS—JUST TELL US YOUR NUMBER

STIRLING SOUND, 37 VANGUARD WAY, SHOEBOURNESS

Please send
(or as attached list) for which I enclose £.....

NAME

ADDRESS

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD HERTS. ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 37774

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS' ORDER. WITH ORDER: GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 25p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Bus Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F)
40V: 0-001, 0-0015, 0-0022, 0-0033 8p, 0-0047, 0-0068, 0-01, 0-015, 0-018 9p, 0-022, 0-033, 10p, 0-047, 0-068, 14p, 0-1, 1.5p, 0-15, 0-22, 0-25, 0-33, 0-47 35p, 0-68 45p.
50V: 0-001, 0-0015, 0-0022, 0-0033, 0-047 18p, 0-068, 1-0 22p, 2-2 32p, 4-7 38p.
DUBILIER: 1000V: 0-01, 0-015 16p; 0-022 18p; 0-047 18p; 0-1 34p; 0-47 43p; 1-0 85p.

POLYESTER RADIAL LEAD (Values in μ F): 250V: 0-01, 0-015 6p; 0-022, 0-027 7p; 0-033, 0-047, 0-068, 0-1 8p; 0-15 12p; 0-22, 0-33 14p; 0-47 16p; 0-68 20p; 1-0 24p; 1-5 27p 2-2 31p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F).
250V: 100 65p; 63V: 0-47, 1-0, 1-5, 2-2, 2-5, 3-3, 4-7, 6-8, 8-10, 10, 15, 22, 9p; 47, 32, 50, 12p; 63, 100, 27p; 50V: 1-0, 7p; 50, 100, 22p; 47, 50p; 1000, 62p; 2200, 68p; 40V: 22, 33, 5p; 10, 22, 9p; 100, 12p; 3300, 62p; 4700, 64p; 35V: 10, 33p; 70, 33p; 330, 47p; 1000, 48p; 10, 22, 9p; 6p; 8p; 100, 16p; 100, 8p; 220, 25p; 13p; 470, 64p; 25p; 1000, 27p; 1500, 30p; 2200, 34p; 3300, 47, 47p; 4700, 54p; 18V: 10, 40, 47, 68, 7p; 100, 125, 8p; 470, 16p; 1000, 150p; 2200, 34p; 3300, 47, 47p; 4700, 54p; 10V: 4, 10, 6p; 640, 10p; 1000, 14p.

TAG-ENT TYPE: 70V: 2000, 98p; 4700, 121p; 50V: 3000 75p; 40V: 2500, 65p; 25V: 4700, 48p; 2000, 37p; 40V: 2000-2000, 95p; 350V: 32+32, 185p.

TANTALUM BEAD CAPACITORS: 35V: 0-1 μ F, 0-22, 0-33, 0-47, 0-68, 1-0, 2-2Hf, 3-3, 4-7, 6-8, 25V: 1-5, 10, 20V: 1-5 μ F, 18p each; 10V: 22uF, 33, 60, 22uF, 47, 68, 3V: 100uF 20p each; 10V: 100uF 35p, 16V: 47, 100uF 45p

MYLAR FILM CAPACITORS: 100V: 0-001, 0-002, 0-005, 0-01 μ F 5p; 0-015, 0-02, 0-03, 0-04, 0-05, 0-056uF 8p; 0-1 μ F, 0-15, 0-2, 2-7p. 50V: 0-47uF 10p

CERAMIC CAPACITORS 50V: Range: 0-5pF to 10nF
15nF, 22nF, 33nF, 47nF, 4p, 100nF 3p

POLYSTYRENE CAPACITORS: 10pF to 1nF, 6p; 1-5nF to 47nF, 10p.

JACKSONS VARIABLE CAPS.
Dielectric 105p 0-2 385pF 275p
100/300pF 105p 0-2 365pF with 305p
500F 125p motor Drive 305p
DILEMIN 00 208/176 285p
3000F/500pF 185p " " with slow motor drive 305p
6:1 Ball Drive 4511/DAF 107p* C804-5pF; 10; 15; 25; 50p

SILVER MICA (25P)
3-3, 4-7, 6-8, 10, 12, 18, 22, 27, 33, 47, 50, 68, 75, 82, 85, 100, 120, 150, 200, 250, 300, 330, 360, 390, 600, 820pF 16p each
0-1-385pF (6p) 00-3x25pF 386p

CERAMIC TRIMMER CAPACITORS: 2-7pF: 4-15pF; 6-25pF; 8-30pF

MINIATURE TYPE: 2-5-6pF, 3-10pF; 3-30pF, 10-40pF 22p; 5-25pF, 65pF, 88pF 30p

COMPRESSION: 3-40pF, 10-80pF 22p; 15-200pF 33p; 100-500pF 12500pF 38p

AUDIBLE Warning Devices 12V 178p*

TRANSFORMERS* (Mainly Pri.M. 220-240V)
6-0-6V 100mA 90p 20-0-20 2A 320p+
9-0-9V 75mA 95p 6-0-6V 1.5A 345p+
12-0-12V 100mA 98p 0-18-0-18V 1.5A
0-12-0-12V 150mA 140p 0-15-0-15V 2A 240p+
0-4-5-0-4 5V 240p+
12-0-12V 0.5A 240p+
0-10-0-10 0.5A 240p+
15-0-15V 0.5A 240p+
24-0-24V 0.5A 280p+
2x 4-5V 0.5A 280p+
0-0-9V 1A 245p+
0-12-0-12V 1A 245p+
30-24-20-15-12-0 1A 240p
Multi tappings 36p+
30-24-20-15-12-0 2A, multi tap 445p+
15-0-15V 1A 245p+
18-0-18V 1A 275p+
30-0-30V 1A 295p+
(Please add 48p p&charge to all prices marked +, above our normal postal base.)

TRANSFORMERS* (Mainly Pri.M. 220-240V)
6-0-6V 100mA 90p 20-0-20 2A 320p+
9-0-9V 75mA 95p 6-0-6V 1.5A 345p+
12-0-12V 100mA 98p 0-18-0-18V 1.5A
0-12-0-12V 150mA 140p 0-15-0-15V 2A 240p+
0-4-5-0-4 5V 240p+
12-0-12V 0.5A 240p+
0-10-0-10 0.5A 240p+
15-0-15V 0.5A 240p+
24-0-24V 0.5A 280p+
2x 4-5V 0.5A 280p+
0-0-9V 1A 245p+
0-12-0-12V 1A 245p+
30-24-20-15-12-0 1A 240p
Multi tappings 36p+
30-24-20-15-12-0 2A, multi tap 445p+
15-0-15V 1A 245p+
18-0-18V 1A 275p+
30-0-30V 1A 295p+
(Please add 48p p&charge to all prices marked +, above our normal postal base.)

TRANSFORMERS* (Mainly Pri.M. 220-240V)
6-0-6V 100mA 90p 20-0-20 2A 320p+
9-0-9V 75mA 95p 6-0-6V 1.5A 345p+
12-0-12V 100mA 98p 0-18-0-18V 1.5A
0-12-0-12V 150mA 140p 0-15-0-15V 2A 240p+
0-4-5-0-4 5V 240p+
12-0-12V 0.5A 240p+
0-10-0-10 0.5A 240p+
15-0-15V 0.5A 240p+
24-0-24V 0.5A 280p+
2x 4-5V 0.5A 280p+
0-0-9V 1A 245p+
0-12-0-12V 1A 245p+
30-24-20-15-12-0 1A 240p
Multi tappings 36p+
30-24-20-15-12-0 2A, multi tap 445p+
15-0-15V 1A 245p+
18-0-18V 1A 275p+
30-0-30V 1A 295p+
(Please add 48p p&charge to all prices marked +, above our normal postal base.)

TRANSFORMERS* (Mainly Pri.M. 220-240V)
6-0-6V 100mA 90p 20-0-20 2A 320p+
9-0-9V 75mA 95p 6-0-6V 1.5A 345p+
12-0-12V 100mA 98p 0-18-0-18V 1.5A
0-12-0-12V 150mA 140p 0-15-0-15V 2A 240p+
0-4-5-0-4 5V 240p+
12-0-12V 0.5A 240p+
0-10-0-10 0.5A 240p+
15-0-15V 0.5A 240p+
24-0-24V 0.5A 280p+
2x 4-5V 0.5A 280p+
0-0-9V 1A 245p+
0-12-0-12V 1A 245p+
30-24-20-15-12-0 1A 240p
Multi tappings 36p+
30-24-20-15-12-0 2A, multi tap 445p+
15-0-15V 1A 245p+
18-0-18V 1A 275p+
30-0-30V 1A 295p+
(Please add 48p p&charge to all prices marked +, above our normal postal base.)

TRANSISTORS

AC107	P	BC170	P	BF179*	P	OC23*	P	TIS49	P	2N2218A
-------	---	-------	---	--------	---	-------	---	-------	---	---------

WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	*BRIDGE RECTIFIERS	SPEAKERS
AA119 15	(plastic case)	8Ω 0.3W
AAZ15 15	2" 2.5" 85	2" 2.5" 3" 58
AEY11 80	1A/50V 20	40Ω 2.5" 85
BA100 10	1A/200V 25	8Ω 5W 190
BY100 24	1A/400V 29	7" x 4" 160
BY126 14	1A/800V 34	
OA9 12	2A/50V 35	
OA27 12	2A/100V 44	
OA70 12	2A/200V 46	
OA81 12	2A/400V 53	
OA85 12	2A/600V 65	
OA90 15	4A/100V 72	
OA91 6	4A/200V 75	
OA95 6	4A/400V 79	
OA98 6	4A/800V 105	
OA200 9	4A/100V 120	
OA202 8	6A/100V 73	
IN814 4	6A/200V 78	
IN916 5	6A/400V 85	
IN4001/2 5	BY164 58	
IN4003 5	VM18 40	
IN4004/5 6		
IN4006/7 7		
IN4148 4		
IS44 20		
3A/100V 18		
3A/400V 20		
3A/800V 27		
3A/1000V 30		
6A/600V 50		
SCR's	ZENERS	LAMP HOLDERS AND LAMPS*
Thyristors	Rng: 3-3V-33V	LES HOLDER Dome shaped, Red, Blue, Green, Yellow, White
1A50V 38	400mW 9	1-3W 17
1A100V 42		
1A200V 47		
1A400V 52		
1A800V 70		
3A50V 38		
3A100V 43		
3A200V 80		
3A400V 110		
3A800V 120		
5A400V 129		
7A400V 125		
8A400V 150		
BT106 150		
CT106D 55		
TIC44 25		
TIC45 45		
2N4444 191		
	VARICAPS	LES BULBS 6v and 12v
	MVAM2 135	MES HOLDERS Chrome cover, Red or Amber, Jewelled top
	MVAM115 95	LES OR MES Batten Holders
	BB104 40	MES BULBS 3-5V 6V 12V
	BB105B 40	NEONS Mains, Sealed with Resistor, Sq. Top, Red or Grm. Round Top Red
	BB106 40	Neon Open with leads, 95V AC
	Noise Diode	FERRIC CHLORIDE*
	Z5J 105	1lb bag Anhydrous 65p + 30p p. & p.
	ALUM. BOXES with lid*	DALO ETCH RESIST
	2 1/2 x 3 1/2 88	PEN* + spare tip 75p
	4 x 4 x 1 1/2 88	COPPER CLAD BOARDS*
	4 x 2 1/2 x 1 1/2 60	Fibre Single-Double-SRBP
	4 x 5 1/2 x 1 1/2 78	Glass sided 8" x 10-5"
	4 x 2 1/2 x 2 64	6" x 6" 75p 90p 75p
	5 x 4 x 2 82	6" x 12" 130p 175p
	6 x 4 x 2 88	DIL SOCKETS*Low Profile (TEXAS)
	7 x 5 x 2 114	8 pin 10; 14 pin 12; 16 pin 13; 18 pin 20;
	8 x 6 x 3 148	22 pin 27; 24 pin 30; 28 pin 42; 40 pin 58
	10 x 7 x 3 172	SOLDERCON PINS*
	10 x 4 x 3 142	100 - 50; 1000 - 350;
	12 x 5 x 3 165	TERMINALS* - Screw type Insulated
	12 x 8 x 3 210	Red, Black, Yellow, Green, White 21

OPTO ELECTRONICS*

LEDS + Clip	7 Segment Displays
TIL209 Red 13	5-LT-01 Futaba 460
TIL211 Grn 23	TIL312 3" C.An 125
TIL212 Yellow 27	TIL313 3" C.Cth 125
0-2" Red 17	TIL321 5" C.An 140
0-2" Yellow, Grn, Amber 21	TIL322 5" C.Cth 140
OCF70 40	DL704 3" C.Cth 99
ORP12 63	DL707 3" C.Anod 99
2N5777 54	FND357 180
OPTO ISOLATORS	XAN351 3" Green 180
TIL111/2 105	XAN625 6" Green 250
TIL114 110	MINITRON 3015F 240
TIL117 164	DRIVERS
	75491 75; 75492 80

VOLTAGE REGULATORS*

723 DIL 45	Plastic Case
TBA625B 95	78L82AVC 1A 8V 51
TO3 Can Type	LM320-12 150
1A 5V 170	MC7805 1A 5V 130
1A 12V 180	MC7812 1A 12V 130
1A 15V 190	MC7815 1A 15V 135
1A 18V 210	MC7818 1A 18V 135
1A 20V 210	FT8N24 1A 24V 140
Variable Type	LM325N ± 15V 240
LM325N ± 15V 240	LM326N ± 12V 240
LM327N ± 5-12 260	LM317K 20W 1.5A 220
MVR5 180	LM317K 20W 1.5A 220
MVR12 180	1 + 1.2V to 37V 250

ROTARY: Make your own multiway Switch. Adjustable Stop Shifting Assembly, Accommodates up to 6 Wafers

Mains Switch DPST to fit Break Before Make Wafers, 1 pole/12 way, 2p/6 way, 3p/4 way, 4p/3 way, 6p/2 way	68
Spacer and Screen	34
ROTARY: (Adjustable Stop)	47
1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way	41
ROTARY: Mains 250V AC, 4 Amp	45

KNOBS* fit 3" shaft with grub screw except K2, K8, K12, K15, K16 (push fit).

K1 Black or White pointer type	9
K2 Slim Silvered Plastic	12
K4 Black serrated. Metal top with line indicator 33mm diam.	22
K4A As above but 25mm diam.	20
K5 Black fluted metal top and skirt calibrated 0-10, 37mm diam.	26
K6 PK2 as K5, pointer on skirt	26
K7 Black, knurled, tapered. Metal top & skirt. Callb. 0-10, 30mm	25
K8 Black or silvered for slider pot	10
K12 Aluminium plastic with line indicator 22mm	16
K15 Black plastic ribbed body, white indicator line, 15mm diam. tapered coloured Insert tops, Red, Blue, Yellow 19mm height.	16
K16 As above but 23mm diam	20

SWITCHES*

TOGGLE 2A 250V	58
SPST	28
DPST	34
DPDT	38
4 pole on off	54
SUB-MIN TOGGLE	
SP changeover	58
SPST on off	54
SPST biased	85
DPDT 6 tags	70
DPDT C/OFF	79
DPDT Biased	115
SLIDE 250V	
1A DP	14
1A DP CO	16
1A DP	13
4 pole 2-way	24
PUSH BUTTON Spring loaded	
SPST on off	60
SPDT C cover	65
DPDT 6 Tag	85
MINIATURE Non Locking	
Push to make	15
Push Break	25
ROCKER: (Black)	
on/off 10A 250V	23

SPECIAL OFFER



TV GAMES

"Olympic Kit" £20.80*
"Olympic" Colour Kit £28.50*

(p&p insured add 95p)
EconoGame Kit £8.99*

COLOUR ADAPTOR for existing Black and White Games £8.85*

"Sure Fire Rifle" Kit for "Olympic" Game £8.50*

"Sure Fire Rifle" Kit for other makes £9.25* (p&p insured add 48p)

"Joy Stick" £1.95*
IC AY-3-8500 £4.50*
IC AY-3-8550 £7.50*
IC AY-3-8600 £9.00*

RHYTHM GENERATOR

Build this PE (Jan. '78) Easy-build Low cost Rhythm Generator. We are the sole suppliers of the complete Kit including the case, pre drilled printed front panel and the printed Circuit Boards.
Complete Kit price incl. VAT £49.95 only (p&p £1).

(TV Games & Rhythm Gen. Demonstration on at our shop).

SAE FOR LEAFLET.

JACK PLUGS

Screened chrome body	Plastic	Open metal	Moulded with break
2.5mm 12p	8p	8p	8p
3.5mm 15p	10p	8p	8p
MONO 23p	15p	13p	20p
STEREO 31p	18p	15p	24p

SOCKETS

Din	Plugs	Socket	In line
2PIN Loudspeaker 3, 4 & 5 pin Audio	13p	8p	20p
CO-AXIAL (TV)	14p	14p	14p
PHONO assorted colours metal screened	10p	8p 1-way	12p 3-way
BANANA 4mm 2mm 1mm 3mm	10p	10p	8p
WANDER 3mm	8p	8p	8p

VEROBOARD* Pitch

0-1	0-15	0-15
2 1/2 x 3 1/2 (copper clad)	3p	29p
2 1/2 x 5" (plain)	43p	38p
3 1/2 x 3 1/2	43p	40p
3 1/2 x 5"	48p	53p
2 1/2 x 17"	134p	107p
3 1/2 x 17"	173p	143p
4 1/2 x 17"	222p	145p
Spot of 36 pins	—	29p
Spot face cutter	—	69p
Pin insertion tool	—	89p

VERO WIRING SPOOL* 365p
We are stockist of all Vero Products. Send SAE for our free list.

BLOB BOARDS*
We now stock the full range of Blob Boards.

INDEX TO ADVERTISERS

ACE Maitronix Ltd. 779	Electronic Mail Order 781	Partridge Electronics Ltd. 744
A.D. Security 776	Electrovalue 792	P.C. Radio (Colomor) 784
A.H. Supplies 779	Fotherby Willis Electronics 772	Progressive Radio 781
Alben Engineering 714	G3DYM Aerials & Projects 787	Radio Component Specialists cover iii
Ambit International 716	G.T. Information Service 787	Radio Exchange Ltd. 721
Antex 747	Greenwell Electronics 716	Ramar Constructor Services 788
A.P. Electronics 783	H.A.C. Short-Wave Supplies 785	R.S.C. (Hi-Fi) 715
Bamber B. 748	H.M. Electronics 788	R.S.T. Valve Mail Order Co. 717
Baron Electronics 772	Harversons Surplus 744	Radio & T.V. Components Ltd. 724
Barrie Electronics 723	Heathkit 719	Rocquaine Electronics 786
B.B. Supplies 786	Home Radio 724	Saga Ltd. 782
Bentley Acoustic Corp. 722	I.L.P. Electronics Ltd. 725, 780	Science of Cambridge 743
Bi-Pak Ltd. 728, 729	Intertext ICS 783	Scientific Wire Co., The 788
Bi-Pre-Pak Ltd. (Stirling Sound)... 784, 789	Jones Supplies 786	Selray Book 722
Birkett J. 720	Juniper Electronics 782	Sintel 788
Brewster S. R. 714	Linear Products 720	Sonic (Hi-Fi) 788
British National Radio & Electronics School 775, 776	Logic Leisure (Telecraft) 744	Southern Valve Co. 792
J. Bull (Electrical) Ltd. 727	London Electronic College 787	S.R.L. Minimeter 771
Cambridge Kits 788	Lynx Electronics 726	Swanley Electronics 781
Cambridge Learning 789	Manor Supplies 779	Technomatic Ltd. 720
Castle Electronics 781	Maplin Electronic Supplies cover iv	Teleradio 776
Caranna C. 787	Marco Trading 719	Tempus 779
Chromasonics 785	Marshall, A. & Son 792	T.K. Electronics 786
Continental Specialists 718	Mhel Electronics 788	Trampus 724
Copper Supplies 788	Minikits Electronics 788	Tudor Rees (Vintage Services) 786
Cox Radio (Sussex) Ltd. 786	Multico-e (Bib Hi-Fi) 772	Van Karen Publishing 786
Crescent Radio Ltd. 723, 776	Orchard Electronics 786	Watford Electronics 790, 791
C.R. Supply Co. 786		West London Direct Supplies 785
Dzubas 782		Wilmslow Audio 723
Electronic Brokers 726		Xeroza Radio cover ii
Electronics Design Associates 714		Z & I Aero Services 748

Get a great deal from Marshall's

A. MARSHALL (LONDON) LTD. DEPT. P.W.
LONDON—40-42 Cricklewood Broadway, NW2 3ET
 Tel. 01-452 0161. Telex 21492
 and at 325 Edgware Road, W2. Tel. 723 4242
GLASGOW—85 West Regent Street, G2 2QD
 Tel. 041-332 4133
BRISTOL—1 Straits Parade, Fishponds Road, BS16 2LX
 Tel. 0272 654201

CALL IN AND SEE US
 9-5.30 Mon-Fri.
 9-5.00 Saturday

EXPRESS MAIL ORDER
 Tel Orders on Credit Cards
 £10 minimum.



POPULAR SEMICONDUCTORS

2N706	28	2N5294	40	BC178	20	BF167	35	MJE520	45	LM380-8	90
2N708	28	2N5296	40	BC179	23	BF173	35	MJE521	45	LM380N	90
2N1131	30	2N5298	40	BC182	11	BF177	25	MPF102	30	LM381A	2.45
2N1132	37	2N5447	15	BC182L	14	BF178	25	MPF105	40	LM381N	1.00
2N1711	36	2N5448	15	BC183	12	BF179	25	MPSA05	25	LM382N	1.25
2N2102	60	2N5449	19	BC183L	14	BF180	30	MPSA06	25	LM384N	1.45
2N2218	33	2N5457	32	BC184	12	BF181	35	MPSA55	25	LM387N	1.05
2N2219	35	2N5458	33	BC184L	14	BF184	15	TIP29A	45	LM388N	90
2N2220	35	2N5459	29	BC212	14	BF195	15	TIP29C	69	LM389N	1.00
2N2221	25	2N5484	34	BC212L	17	BF196	15	TIP30A	49	LM702C	75
2N2222	25	2N8121	38	BC213	14	BF197	17	TIP30C	65	LM709C	65
2N2308	25	2N8122	41	BC213L	16	BF198	18	TIP31A	50	LM709N	45
2N2369	25	2N8123	43	BC214	16	BF200	35	TIP31C	60	LM710C	60
2N3053	28	2N8126	45	BC237	14	BF204J	20	TIP32A	55	LM710N	60
2N3054	60	AC126	45	BC238	12	BF244A	35	TIP32C	75	LM723C	85
2N3055	70	AC127	45	BC239	15	BF245A	40	TIP41A	70	LM723N	75
2N3441	85	AC128	45	BC257	17	BF257	37	TIP41C	90	LM741C	65
2N3442	135	AC151	40	BC258	18	BF258	45	TIP42A	80	LM741N	40
2N3702	13	AC152	50	BC259	19	BF259	48	TIP2955	50	LM747N	90
2N3704	15	AC153	55	BC307	15	BF336	38	TIP3055	55	LM748-8	55
2N3706	16	AC153K	55	BC308	15	BF337	45	TIS43	43	LM748N	55
2N3708	13	AC176	50	BC309	15	BF338	48	TIS50	35	LM1800	1.76
2N3771	1.95	AC176K	65	BC327	20	BF339	28	TIS61	25	LM1808	1.92
2N3772	2.00	AC187K	60	BC328	19	BF340	27	TIS62	45	LM1828	1.75
2N3773	2.90	AC189K	60	BC347	24	BF441	28	TIS68A	40	LM3301N	85
2N3819	36	AD161	1.00	BC548	12	BF379	28	TIS90	20	LM3302N	1.40
2N3820	38	AD162	1.00	BC549	14	BF380	27	TIS93	33	LM3401	70
2N3823	60	AF106	55	BC557	13	BF381	26	LM301A	67	LM3900	1.60
2N3904	21	AF109	75	BC558	12	BF399	39	LM301N	40	LM3905	1.60
2N4036	67	AF139	69	BC559	14	BF390	39	LM304	2.45	LM3909	90
2N4037	55	AF238	65	BCY58	25	BF384	35	LM307N	65	MC1310	1.91
2N4058	20	AF240	1.14	BCY70	25	BF345	30	LM308C	1.82	MC1458	91
2N4059	15	AF279	90	BFY71	28	BF386	30	LM308N	85	NE555	40
2N4060	20	AF280	85	BCY72	24	BF387	30	LM309K	1.85	SN7400	16
2N4124	17	BC107	15	BD115	80	BF388	30	LM317K	3.00	SN7402	16
2N4126	17	BC108	15	BD131	51	BFY50	25	LM318N	2.26	SN7404	26
2N4289	20	BC109	15	BD132	54	BFY51	25	LM323K	6.46	SN7410	25
2N4303	30	BC140	35	BDY35	27	BFY52	25	LM339N	1.40	SN7411	1.63
2N4904	1.70	BC141	40	BD136	38	BSX21	32	LM348N	1.50	SN7447	1.10
2N4919	65	BC147	12	BD137	38	BU104	1.65	LM360N	2.75	SN7448	1.10
2N4920	75	BC148	12	BD138	38	BU105	1.40	LM370N	2.50	SN7474	43
2N4921	50	BC149	14	BD139	40	BU126	1.90	LM371N	1.70	SN7480	61
2N4922	35	BC160	35	BD140	40	BU204	2.82	LM372N	1.70	SN7482	61
2N4923	70	BC181	35	BD433	50	BU205	2.20	LM373N	2.80	SN7483	61
2N5086	27	BC187	12	BD439	50	BU206	2.50	LM374N	3.10	SN7496	1.03
2N5192	75	BC188	12	BDY18N	1.70	MJE340	58	LM377N	1.75	SN74121	49
2N5194	72	BC189	12	BDY20	1.00	MJE370	58	LM378N	2.25	SN74141	63
2N5245	34	BC177	20	BDY56	1.90	MJE371	60	LM379S	3.95	76023N	1.45

Prices correct at 17 Nov. 1977, but please add VAT p&p 40p

OPTOELECTRONICS

Full range of Opto devices in our new catalogue



LEDs

3mm Red 19p, Gr 25p, Y 25p
 5mm Red 21p, Gr 26p, Y 26p
 TIL209 19p, ORP12 84p
 BPX 25 1.65

DISPLAYS

Single	Double	Display
DL704 2.00	3.00	0.31n Red
DL707 2.00	3.00	0.31n Red
DL747 2.50	3.40	0.51n Red
DL750 2.50	3.40	0.51n Red

TRIACS Plastic Pack 400V

6 amp	70	16 amp	1.10
8 amp	75	20 amp	1.78
12 amp	85	25 amp	2.00

DIACS

ST2	20p
BR100	48p

BRIDGES

Full range of Bridge Rectifiers and Diodes listed in new catalogue

THYRISTORS Plastic C106 116

4 amp 100V	0.35	8 amp 100V	0.43
4 amp 200V	0.40	8 amp 200V	0.49
4 amp 400V	0.49	8 amp 400V	0.62

WHY NOT PAY US A VISIT AT OUR NEW CENTRAL LONDON BRANCH AT 325 EDGWARE ROAD, W2, ABOUT 100 YARDS NORTH OF THE WESTWAY FLY-OVER. EXTENSIVE STOCK RANGE. MANY SPECIAL OFFERS TO PERSONAL SHOPPERS ONLY.

SPECIALIST CONSUMER

NEW CATALOGUE

- Stocking Distributors Officially Appointed
- NATIONAL ● VERO
 - TEXAS ● ANTEK
 - MULLARD ● ELECTROLUBE
 - SIEMENS ● SIFAM
 - SESCOEM ● ARROW HART
- MAKES COMPONENTS BUYING EASY**



ORDER NOW!

35p Post Paid or 25p To Callers
LARGE 32 PAGES packed with over 8500 **LINE ITEMS**

"What is a microprocessor?"

A complete teach yourself course with cassettes + brochure - £9.95 inclusive of VAT and p&p.

IT'S EASY WHEN YOU KNOW!

To avoid missing your copy of PRACTICAL WIRELESS—simply complete this order form and hand it to your newsagent.

ORDER FORM

To:

Address (name of newsagent)

Please reserve/deliver every month one copy of PRACTICAL WIRELESS until further notice.

My Name

Address

SOUTHERN VALVE CO. UPPER FLOOR, 8 POTTERS ROAD, BARNET, HERTS.

Telephone: 01 440/8641

MAIL ORDER ONLY

ALL NEW & BOXED "QUALITY" BRANDED VALVES GUARANTEED 3 MONTHS. BVA ETC. (TUNGSRAM ETC.). 6% ALLOWED IN LIEU OF GUARANTEE, ALTHOUGH DEDUCTED FROM OUR PRICES. Note: Prices are only correct at time of going to press. PLEASE VERIFY CURRENT PRICES. MIN. 75p!

Some leading makes available. VAT Invoices issued on request.

A731 90p	ECL83 75p	EY86/7 38p	PCF80 79p	PCL85 } 64p	PL508 £1.30	UCL82 55p
DY86/7 49p	ECL86 70p	EY500A 21.50	PCF82 50p	PCL 805 }	PL509 £2.50	UCL83 80p
DY802 50p	EF80 39p	EZ80 41p	PCF86 58p	PCL86 65p	PL519 £2.80	UF41 70p
EB91 24p	EF85 42p	EZ80 41p	PCF200	PCL86 65p	PL802 £2.75	UF89 45p
DY802 50p	EF86 52p	EZ81 40p	PCF801 50p	PCL200 80p	PL802 £2.75	UF99 45p
ECC81 45p	EF89 50p	GZ30 75p	PCF802 65p	PL812 40p	PL812 40p	UL94 90p
ECC83 45p	EF184 44p	PC86 72p	PCF805 POA	PL813 40p	PL813 40p	UL94 90p
ECC85 50p	EH90 56p	PC88 72p	PCF806 POA	PL814 70p	PL814 70p	UL94 90p
ECC88 50p	EL34 £1.20	PC97 72p	PCF806 75p	PL815 70p	PL815 70p	UL94 90p
ECH42 90p	EL41 90p	PC90 80p	PCF808 POA	PL816 70p	PL816 70p	UL94 90p
ECH81 54p	EL84 40p	PC84 35p	PCF808 POA	PL817 70p	PL817 70p	UL94 90p
ECH83 82p	EL90/1 47p	PC85 45p	PCH200	PL818 70p	PL818 70p	UL94 90p
ECH84 70p	EL509 £2.70	PC88 62p	PCL82 54p	PL819 70p	PL819 70p	UL94 90p
ECL80 55p	EM84 70p	PC89 50p	PCL83 70p	PL820 70p	PL820 70p	UL94 90p
ECL82 50p	EY51 64p	PCC189 55p	PCL84 49p	PL821 70p	PL821 70p	UL94 90p

One valve post 13p, each extra valve 6p. MAX 75p. LISTS & ENQUIRIES, SAE PLEASE! Large valves 14p each. ALL PRICES INCLUDE VAT @ 12½%.

We offer return of post service. CWO ONLY. NO C.O.D. Post free over £18. £5 to £18 -75p (max). Items in stock at time of going to press but subject to market fluctuations without notice. ENQUIRIES WELCOME FROM TRADE & RETAIL (same prices).

For Semi-Conductors including

- Small Signal Transistors
- Power Semi-conductors
- TTL, CMOS, I.Cs
- Linear I.Cs
- Signal and Power Diodes
- Zener Diodes
- Magneto Resistors
- Hall-effect devices
- Magnetic Proximity Switches
- Opto-electronic devices

Go to
ELECTROVALUE
 TO MAKE THE BEST OF

For passive components including

- Plastic Film Capacitors
- Electrolytics
- Semi-precision capacitors
- Transformers
- Pot Cores
- R.M. Cores
- Ring Cores, etc.

Go to
ELECTROVALUE
 THE PROJECTS YOU BUILD

The Open Door to Quality

It's the Electrovalve Catalogue No. 8 (4th edition black and white cover) with completely up-dated prices. 144 pages, well illustrated, 40p post free with 40p voucher usable on orders for £5 or more. Send for yours now and order in confidence.

GOODS SENT POST FREE IN U.K. FOR C.W.O. ORDERS. Keenly competitive prices plus ATTRACTIVE DISCOUNTS and only best quality goods.

ELECTROVALUE LTD

(Dept. PW.1) 28 St. Jude's Rd., Englefield Bay, Egham, Surrey TW20 0HB.
 Phone: Egham 3603. Telex: 264475.

North—680 Burnage Lane, Burnage, Manchester.
 Phone: (061) 432 5945.

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details.

Chassis only £94 Price £110 carr. £5

ANOTHER R.C.S. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM

This famous unit now available, 10 watts, 8 ohm.

Price £3.45 Post 40p



10" ELAC HI-FI SPEAKER

Large ceramic magnet. Response: 50-18,000 cps. Bass resonance 55 cps. 16 ohm impedance 10 watts. Post 40p

£4.50

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in. For 12in. dia. or 10in speaker. 14.50 Post £1.60 Illustrated.

MODEL "B" BOOKSHELF For 12 x 8in. or 8in. £8.50 Post £1 speaker

R.C.S. BOOKSHELF CABINET Size 16in. x 6in x 5in. approx. Response 50 to 14,000 cps. 6 watts rms. 8 ohms. £16 pair Post £1.30

LOUDSPEAKER CABINET WADDING 18in. wide, 20p ft.

GOODMANS CONE TWEETER

3 1/2in. diam. 18,000 C.P.S. 25 WATTS 8 Ω £3.25
8in. Audax 15 watts £4.95.
5in. EMI mid range £5.
10in. 30 watt GOODMANS woofer 4 ohm £10.85.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery £6.75 operated.

TWO CHANNEL STEREO VERSION OF ABOVE £8.50

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated or Mains Supply £2.95.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. £4.95 Post 40p

WAFER HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photo-copiers and print drying equipment.

Ideal for home handyman and experimenters. Suitable for Heating Pads, Food Warmers, Convecter Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides 6 x 4in. 70p; 8 x 6in. 80p; 10 x 7in. £1.15; 14 x 9in. £1.50. 16 x 6in. £1.45; 12 x 3in. 87p; 16 x 10in. £1.70. All boxes, many sizes in stock.

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in.



With MAGNETIC STEREO CARTRIDGE Cueing Device, Bias Compensator, Balanced Arm. All Post 75p GARRARD MINICHANGER. Plays All Records £9.95 BSR P128 with Ceramic Cartridge £19.50

BAKER MAJOR 12" £15.00



90-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 4 or 8 or 16 ohms must be stated.

Post £1

MODULE KIT

30-17,000 c/s with tweeter, crossover, baffle 18 x 12in. Please £19.00 slate 4 or 8 or 16 ohms.

Post £1.60

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25"

12in. 30 watt 4, 8 or 16 ohms.

£12.00

Post £1

GROUP "35"

12in. 40 watt 4, 8 or 16 ohms.

£14.00

Post £1

GROUP "50/12"

12in. 80 watt professional model. 4, 8 or 16 ohms. With aluminium presence dome.

£21.00

Post £1.60

GROUP "50/15"

15in. 75 watt 8 or 16 ohms.

£26.00

Post £1.60

Send for leaflets on Disco, P.A. and Group Gear

BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER



Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4-8-16 ohm. Slave output. A/C mains. Guaranteed. Details S.A.E. £75 Carr. £1.00

100 WATT DISCO AMPLIFIER

MADE BY JENNINGS MUSICAL INSTRUMENTS

4 Speaker outputs volume, treble, bass, controls

CAN BE USED AS 100 WATT SLAVE


£59

Carr. £1

B.S.R. SINGLE PLAYER DECK

3 speed. Plays all size records. Stereo Cartridge. Cueing device. Ideal Disco Deck.

£15.50 Post 75p

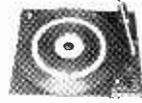

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Will control up to 500 watts AC mains. £3.25 Post 35p

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2.95 Post 35p

P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 800 to 1,000 watts each. As featured in Practical Wireless. Price £14.00 Cabinet extra £3.

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edson Screw Fitting 75p. Each.

MAINS TRANSFORMERS


6 VOLT 1 AMP. £1.00 3 AMP. £1.40
12 VOLT 300 MA. £1.00 750 MA. £1.30
30 VOLT 5 AMP. AND 34 VOLT 2 AMP. C.T. £3.45
20 VOLT 1 AMP. £2.00 2 AMP. £2.20 20-0-20 VOLT 1 AMP. £2.95
30 VOLT 1 AMP. £2.50 40 VOLT 2 AMP. £2.95
0-20-40-80 VOLT 1 AMP. £3.50 2 x 18 VOLT 8 AMP. £11.

GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at
2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £5.30
1A, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £5.30
2A, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £5.30
3A, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £11.00
5A, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £14.50

R.C.S. BOOKSHELF SPEAKERS

13 x 10 x 6in. 50 to 14,000 cps. 8 watts rms. 8 ohms

£16 pair Post £1.30

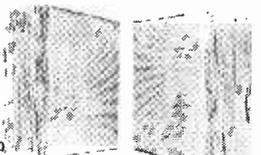

BAKER DISCO SPEAKERS

HIGH QUALITY—BRITISH MADE

2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners. Black vinyl covered. Other cabinets in stock. SAE for leaflet

60 WATT R.M.S.

£52

With one horn £60

With two horns £68

Carr. £3

80 WATT R.M.S.

£56

With one horn £64

With two horns £72

Carr. £3


100 WATT R.M.S.

£69

With one horn £78

With two horns £86

Carr. £5

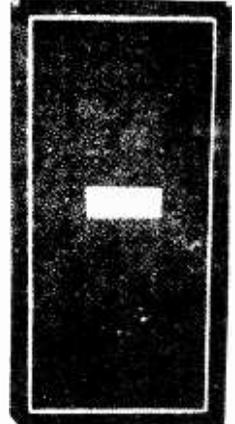

SINGLE 12inch CABS COMPLETE

30 WATT R.M.S.: £32. WITH HORN £40.

40 WATT R.M.S.: £34. WITH HORN £42.

60 WATT R.M.S.: £41. WITH HORN £49.

CARR £3 EA.

"SUPERB HI-FI"

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 15,500 gauss
Useful response 20-17,000cps
8 or 16 ohms models.

£22.00 Post £1.60



"AUDITORIUM"

12in. 35 watts

A full range reproducer for high power. Ideal for Hi-Fi and Discotheques, Electric Guitars, public address, multi-speaker systems, electric organs. Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-16,000cps
8 or 16 ohms models.

£21.00 Post £1.60



"AUDITORIUM"

15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic Instruments and the home Hi-Fi.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 16 ohms models.

£26.00 Post £1.60



Loudspeaker Cabinet Wadding 18in wide, 20p per ft.

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 68p.

E.M.I. 13 1/2 x 8in

SPEAKER SALE!

With tweeter. And crossover. £7.95

10W. State 3 or 8 ohm. Post 45p


15W model £10.50

8 ohms. Post 65p

GOODMANS 20W Woofer

Size 12 x 10in 4 ohms. £9.95

Rubber cone surround. Post 65p

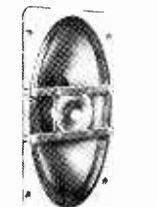

RADIO COMPONENT SPECIALISTS

Minimum post 30p.

Components List 20p.

Cash price includes VAT.

Access & Barclay cards welcome.

337 WHITEHORSE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)

Phone your order Tel. 01-684 1665

MAPLIN

in a modern world of electronics

THE 'DRUMSETTE' RHYTHM GENERATOR

Organists, pianists, guitarists . . . an automatic drum set to accompany you! Nine highly realistic instruments play fifteen different rhythms. Fifteen rhythm-select touch switches and a touch plate for stop/start without rhythm change gives absolute ease of operation. Build it yourself for under £35 including smart teak-effect cabinet. See it and hear it in our shop! Send for full construction details now: MES 49 price 25p



AUDIO MIXER

A superb stereo audio mixer. It can be equipped with up to 16 input modules of your choice and its performance matches that of the very best tape-recorders and hi-fi equipment. It meets the requirements of professional recording studios, FM radio stations, concert halls and theatres. Full construction details in our catalogue. A component schedule is available on request.



INTEGRATED CIRCUITS

Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applicator's circuits and projects to build. Post the coupon now!




10 CHANNEL STEREO GRAPHIC EQUALISER

A new design with no difficult coils to wind, but a specification that puts it in the top-flight hi-fi class. All this for less than £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 40p.



SYNTHESISER

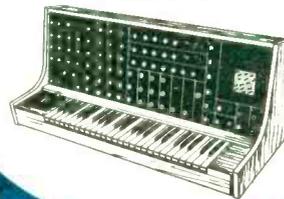The International 4600 Synthesiser. A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart teak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request, full construction details in our construction book £1.50



Who says the Maplin Catalogue's worth having?

"in our 'musts' for readers-to-collect list"—P.E.

"contains . . . just about everything the DIY electronics enthusiast requires"—P.W.

"probably the most comprehensive catalogue we have ever come across"—E.E.

"has been carefully prepared and is very well presented.—R.E.C.

"make the job of ordering components an easy, accurate and enjoyable pastime"—P.W.

"Only one word describes the publication—superb!" E.T.I.

OVER 60,000 COPIES SOLD DON'T MISS OUT!
SEND 60p NOW

MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3, RAYLEIGH, ESSEX SS6 8LR
Telephone: Southend (0702) 715155

Shop: 284 London Road,
Westcliff-on-Sea, Essex.

(Closed on Monday)
Telephone: Southend
(0702) 715157

Our bi-monthly newsletter keeps you up to date with latest guaranteed prices—our latest special offers—details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

POST THIS COUPON NOW
FOR YOUR COPY OF OUR
CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME

ADDRESS

.....

.....

.....



PW2