

RADIO... ELECTRONICS... INSTRUMENTS... AUDIO...

practical **WIRELESS**

50p

Australia 95c
New Zealand 95c
South Africa 90c
Malaysia \$2.75

AUG 1979

COMMUNICATIONS


**AUTOMATIC INTERCOM
SATELLITE COMMUNICATIONS
ULTRASONIC REMOTE CONTROL
LOWE SRX-30 RECEIVER REVIEWED
AERIAL DESIGN WITH SCALE MODELS**

**QUARTZ LCD
5 Function**

Hours, mins, secs., month, date, auto calendar, back-light, quality, metal, brass etc.

£6.65

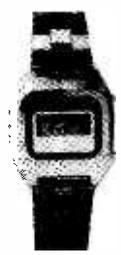Guaranteed same day despatch. Very slim, only 6mm thick.



M1

**SOLAR QUARTZ
LCD 5 Function**

Genuine solar panel with battery back-up. Hours, mins., secs., day. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.



M2

**QUARTZ LCD
11 Function** SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins., Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold! Guaranteed same day despatch.



M3

**QUARTZ LCD
ALARM 7 Function**

Hours, mins., secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

**MULTI ALARM
6 Digits 10 Functions**

- * Hours, mins., secs.
- * Months, date, day.
- * Basic alarm.
- * Memory date alarm.
- * Timer alarm with dual.
- * Time and 10 country zone.
- * Back-light.
- * 8mm thick.

£18.65



M5

**FRONT-BUTTON
Alarm Chrono
Dual Time**

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet.

£22.65

Guaranteed same day despatch



M6

**SOLAR QUARTZ LCD
Chronograph with Alarm
Dual Time Zone Facility**

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm, 9mm thick. Back-light. Fully adjustable bracelet.

£27.95



M7

**ALARM CHRONO
with 9 world time zones**

- * 6 digits, 5 flags.
- * 6 basic functions.
- * 8 further time zones.
- * Count-down alarm.
- * Stop-watch to 12 hours 59.9 secs.
- * In 1/10 sec. steps.
- * Split and timing modes.
- * Alarm.
- * 9 mm thick.
- * Back-light.
- * Fully adjustable bracelet.

£29.65



M8

**SOLAR QUARTZ LCD
Chronograph**

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£12.65

Guaranteed same day despatch.



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass. List Price £130.00

£105.00

METAC PRICE



M10

SEIKO MEMORY BANK

Calendar watch M354. Hours, mins., secs. Month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display month, year and all dates for any selected month over 80 year period. Memory bank function. Any desired dates up to 11 can be stored in advanced. 2 year battery life. Water resistant. List Price £130

£105

Metac Price



M11

**SEIKO-STYLE
Dual time-alarm
Chronograph**

Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

£35.00



M12

**HANIMEX
Electronic
LED Alarm Clock**



Features and Specification:
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

£9.65 Thousands sold! Mains operated.

Guaranteed same day despatch.

M13

**HANIMEX portable
LCD clock radio**



- * Time set & alarm controls.
- * Snooze & sleep controls.
- * Wake to music or alarm.
- * AM/PM indicator.
- * Battery operated. No plug required.
- * Receives all standard AM radio broadcasts.
- * Drawstring carrying case included.
- * Back-light.
- * Batteries supplied free.
- * Quartz crystal controlled.

£17.95

M14

**QUARTZ LCD
Ladies 5 Function**

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£9.95

Guaranteed same day despatch.



M15

**Price breakthrough
only
£18.95**



OUTSTANDING FEATURES

- * **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- * **CALENDAR FUNCTIONS** include the date and day in each time zone.
- * **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
- * On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- * **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch.

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100.
Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.

CALLERS WELCOME
Shops open 9.30 - 6.00.



Metac ELECTRONICS & TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, POOLE, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Subscriptions: INLAND and OVERSEAS £10.60 payable to IPC Services, Oakfield House, Perryment Road, Haywards Heath, Sussex. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Hire where the selling price is subject to V.A.T. and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

practical WIRELESS

AUGUST 1979
VOLUME 55
NUMBER 8
ISSUE 870

BRITAINS LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "*Practical Wireless*" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 75p each, including post and packing to addresses at home and overseas.

Binders are available (Price £2.85 to UK addresses or £3.45 overseas, including post and packing) each accommodating one volume of *PW*. Please state year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.**

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

NEWS & VIEWS

- 20 **Editorial** Communications
- 20 **PW Personality** Eric Dowdeswell
- 21 **News . . . News . . . News . . .**
- 29 **Special Product Report** Radat 3106 C Oscilloscope
- 33 **Kindly Note** Logical Noughts and Crosses, June 1979
- 37 **Production Lines** *Alan Martin*
Information on the latest products
- 50 **Special Introductory Offer** CSC Logic Probe Kit
- 60 **Radio Special Product Report** Lowe SRX-30 Communications Receiver
- 62 **RAE Reprint Announcement**
- 67 **Hotlines** *Ginsburg*
Recent developments in electronics

FOR OUR CONSTRUCTORS

- 34 **Telephone Bell Repeater** *B. Barnard*
An extension bell with no connection to the phone
- 44 **Automatic Intercom—1** *Keith Cummins*
Answer callers from your armchair
- 49 **VMOS Top Band Transmitter Follow-up** *J. R. Green*
Adding a p.t.t. facility to this project
- 55 **PW "Trent" Linear HF Amplifier—2**
A 150W broadband amplifier for 2–30MHz
- 65 **PW "Sandbanks" Follow-up—2** *P. J. Wales*

GENERAL INTEREST

- 23 **New PO Aerials for Satellites**
Describes the latest in communication satellite aerials
- 26 **Aerial Design with Scale Models** *Fred Judd*
How to check out a new aerial design without going up the mast
- 30 **IC of the Month** *Brian Dance*
The TDE 2608 Waveform Generator
- 38 **Ultrasonic Remote Control** *M. J. Darby*
Controlling Domestic Equipment without wires
- 41 **Changes in SW Broadcasting Band Listening—2** . *Jonathan Marks*
Looking at the international broadcasting scene
- 51 **BIFET Integrated Circuits** *D. F. Bowers*
- 68 **On the Air**
 - Amateur Bands *Eric Dowdeswell*
 - MW Broadcast Bands *Charles Molloy*
 - SW Broadcast Bands *Charles Molloy*
 - VHF Bands *Ron Ham*


Our cover photo this month shows Madley 1 earth station, and is reproduced by kind permission of the Post Office.

Our September issue will be published in early August
(for details see page 43)

The latest kit innovation!

from Sparkrite

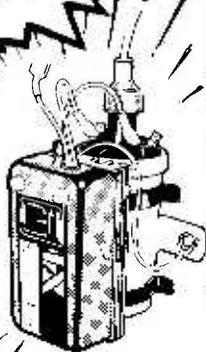Sparkrite - was featured by Shaw Taylor in "DRIVE IN"



the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete, it can be assembled in two or three hours and fitted in 1/3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in the respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminum extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing U.K. only.

Electronic Design Associates, 82 Bath Street, Walsall, WS1 3DE

Electronics Design Associates, Dept. PW8
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name
Address

Phone your order with Access or Barclaycard

Send SAE if brochure only required.

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X4 KIT	£16.65
TACHOPULSE SLAVE UNIT	£3.85

Please state polarity pos. or neg. earth
Access or Barclaycard No.

£
Cheque No.

VALVES

A1085	1.40	EF80	0.45	PC900	1.40	U25	1.15	5B/255M	8.45	6J7	0.80	18G3	6.75
AR8	0.70	EF83	1.70	PC884	0.75	U26	0.95	5B/250M	8.45	6J76	0.80	18G6	19.15
ARF3	0.70	EF85	2.25	PC889	0.65	U27	1.15	5B/250M	8.45	6K7	0.45	19H2	0.70
ATP4	0.60	EF86	1.00	PCC189	0.75	U191	0.85	5U46	1.05	6K7G	0.65	20D1	0.70
B12H	3.35	EF91	0.70	PCF60	0.90	U281	0.80	5V4G	0.75	6K8GT	2.15	20F2	1.15
CY31	0.60	EF92	1.00	PCF84	0.75	U801	0.60	5Y3GT	0.75	6L8M	1.05	20L1	0.45
DAF96	0.70	EF95	2.95	PCF86	0.75	UABC80	0.70	5Z3	1.15	6L9GT	0.75	20P1	0.60
DET22	21.95	EF183	1.40	PCF200	1.05	UAF42	0.85	5Z4G	0.45	6L18	0.70	20P4	1.15
DF95	0.70	EF184	0.80	PCF201	1.05	UBF80	0.85	5Z4GT	0.85	6L18	0.70	20P5	0.90
DK36	1.05	EF204	0.80	PCF801	0.75	UB11	1.15	6A6	0.85	6M7G	0.75	25L6GT	0.70
DH76	0.90	EF200	0.80	PCF805	2.05	URL21	1.15	6AR6	0.80	6SA7	0.85	25Z4G	1.15
DL92	0.60	EH90	0.80	PCF806	0.95	UCC84	0.70	6AK8	0.85	6S67	0.80	30C15	1.25
DY86/87	0.65	EL32	0.80	PCF808	2.05	UCC85	0.75	6AL5	0.45	6SJ7GT	0.70	30C18	1.15
DY802	0.65	EL37	0.80	PCH200	0.90	UCF80	0.90	6AL5W	0.75	6SK7	0.85	30C18	0.80
E551	0.45	EL38	0.80	PC81	0.70	UCF81	0.70	6AM5	1.80	6SL7GT	0.85	30F5	1.35
EE8 CC/01	1.50	EL41	0.90	PCL82	0.70	UCL82	0.85	6AM6	0.85	6S07	0.80	30F12	1.35
E180CC	1.50	EL41	1.20	PCL86	0.80	UF80	0.55	6AN8	0.95	6V6GT	0.70	30L14	2.05
E180E	0.75	EL82	0.70	PCL805/85	0.80	UF85	0.60	6AD5	0.95	6X4	0.65	30L15	1.15
E182CC	3.95	EL84	0.80					6AD5W	0.95	6X4	0.65	30L17	1.15
EA76	2.25	EL88	1.05					6AS6	0.80	6X5GT	1.10	30L17	1.15
EAC80	0.60	EL90	1.05	PD500	0.85	UL41	0.85	6AT6	0.85	6Y6G	0.70	30P12	1.15
EB91	0.45	EL91	1.80	PEL200	2.80	UN80	0.70	6A9B	0.45	6Z4	1.95	30P13	1.25
EB33	1.15	EL95	0.80	PL36	0.90	UM84	0.45	6A9C	0.50	6-30L2	0.90	30P13	1.25
EBF80	0.60	EL504	0.90	PL81	0.85	UY82	0.65	6AX4GT	0.90	7B7	0.80	30P14	1.15
EBF83	0.80	EL802	1.70	PL82	0.60	UY85	0.60	6AX5GT	1.15	7V4	0.70	35L6GT	0.80
EBF89	0.80	EL822	0.95					6B7	0.85	9D2	0.85	35A4GT	1.35
EC52	0.45	EM31	0.85	PL83	0.60	VR105/30	2.05	6B8	0.45	9D6	0.70	50C5	1.15
EC81	0.65	EM80	0.70	PL84	0.75	VR150/30	1.40	6B16	1.15	10F18	0.70	50C6G	0.90
EC82	0.60	EM81	0.70	PL504	1.60	Z66	1.05	6B7A	0.70	11E2	1.20	75C1	0.85
EC83	0.65	EM84	0.45	PL508	1.50	X61M	1.70	6BR7	2.60	12A6	0.55	76	0.85
EC84	0.50	EM87	1.15	PL509	0.75	Z80U	3.40	6BW9	3.10	12AT6	0.65	78	2.50
EC85	0.60	EM88	0.80	PL802	3.15	Z80UW	3.90	6C4	1.15	12AT7	0.80	8B2	12.40
EC86	1.40	EY81	0.55	PL803	3.15	Z80UW	3.90	6C6	0.45	12AV6	0.60	8B2	6.75
EC88	0.70	EY86/87	0.65	PL804	3.40	Z900T	1.70	6C6	0.65	12AV6	0.60	723A/8	20.25
EC88/89	0.90	EY88	0.65	PL805	3.70	IA3	0.70	6CH6	5.05	12AX7	0.60	803	1.15
EPF80	0.60	EZ80	0.55	PL806	0.70	IL4	0.40	6CL6	1.70	128A6	0.70	805	11.80
EPF82	0.55	EZ81	0.70	PL807	0.85	IR5	0.65	6CY5	1.00	128B6	0.70	807	12.40
EPF81	0.90	GY501	1.05	PL808	0.55	IS4	0.45	6E8	0.65	128M7	0.65	813	5.05
EPH34	1.15	GZ32	0.75	PL809	0.65	IS5	0.45	6E8A	0.85	12E1	0.45	832A	3.15
ECH35	1.70	GZ33	3.95	PL810	0.75	IT4	0.45	6F66B	0.75	12J5GT	0.70	866A	0.80
EDH42	0.95	GZ34	2.25	PL811	1.50	IU4	0.70	6F88	0.90	12K7GT	0.80	931A	0.55
EDH81	0.95	GZ37	2.80	PL812	0.90	IX2B	1.25	6F12	0.90	12K8GT	0.60	954	0.60
EDH82	1.15	KT68	0.65	PL813	1.15	IX2C	1.25	6F14	1.15	12L7GT	0.60	954	1.60
ECL80	0.70	KT88	1.45	PL814	1.15	IX2D	1.25	6F15	1.15	12M7	0.60	958	1.00
ECL82	0.65	MM4	1.15	PL815	1.15	IX2E	1.25	6F17	1.00	12SC7	0.80	958	1.15
ECL83	1.40	ML6	1.15	PL816	1.15	IX2F	1.25	6F24	4.75	12SH7	0.65	957	0.80
EDL85	0.75	OA2	0.65	PL817	1.15	IX2G	1.25	6F33	1.10	12SJ7	0.65	1625	1.15
EDL86	0.65	OB2	0.70	PL818	1.15	IX2H	1.25	6H6	1.95	12SQ7	0.45	1629	2.80
EF37A	1.70	PABC00	0.60	PL819	1.15	IX2I	1.25	6J4WA	0.85	12TA7	0.70	2051	7.35
EF39	3.30	PC85	0.80	PL820	1.15	IX2J	1.25	6J4WB	0.60	12TB7	0.60	5763	0.80
EF40	0.80	PC86	0.95	PL821	1.15	IX2K	1.25	6J4WC	0.85	14S7	0.85	5642	0.40
EF41	0.85	PC88	0.85	PL822	1.15	IX2L	1.25	6J4WD	0.85	19A05	11.25	5933	0.95

V.A.T. INCLUDED

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free, minimum order £1.
A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc.; retail 749 3934, trade and export 743 0899.

COLOMOR 907353/
(ELECTRONICS) LTD. London
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

Now, complete your system!




Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system 4/6 ch mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU E94.24.

The ultimate range of speakers

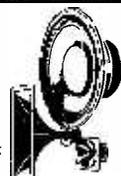We carry a good selection of high quality chassis for the DIY speaker constructor: 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from E13.77, or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only E6 18 each.



Projectors

Come and see our specially selected projectors from E42.12 (Squire Multi-facet 150) to E94.50 (Tutor 11E) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.



Turntables

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive ONLY E28.12.



Rapelights

Great effect at discos. 7 metres long. Multiway connectors. 4 channel. E43.20 (inc. pack of spare bulbs)

Bulgian Octal plugs and sockets

There's always hundreds of Bulgian Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 9A. Perfect for your Sound to Light System. P562 SOCKET E0.65. P561 PLUG E1.94.

Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES.

Multiway Cables
4 core (6A) 59p/metre
5 core (6A) 75p/metre
6 core (6A) 86p/metre

ALL SHOPS OPEN TUE-SAT
LATE NIGHT WED.
(UP TO 8 PM)

PERSONAL CALLERS ONLY

Roger Squire's

Disco Accessories

176 Junction Road, N19, 50yds Tufnell Park Tube Station. Tel: 01 272 7474

LONDON

BRISTOL 125 Church Road, Redfield (Near St. George's) 1 mile from end of M32. Tel: 0272 550550

MANCHESTER Tel: 061 831 7676

GLASGOW 1 Queen Margaret Road, Off Queen Margaret Drive, Kelvinside 20, just behind the BBC. Tel: 041 846 3303

LOOK!

Here's how you master electronics.

... the practical way.


This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

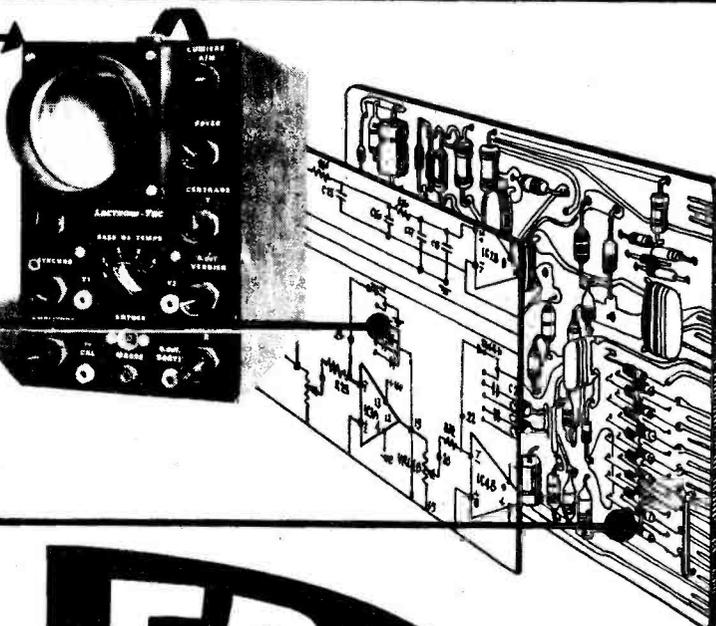1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also for later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

FREE

Post now, without obligation, to:-


BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands.

NAME _____


ADDRESS _____

Block caps please

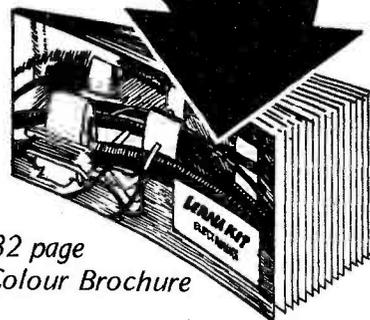

32 page
Colour Brochure

RSC 100 WATT DISCO SYSTEM

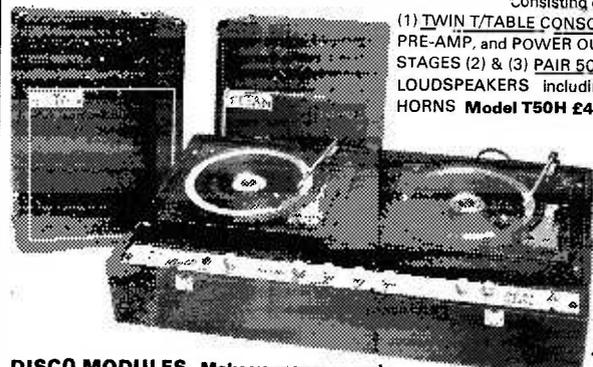


Consisting of
 (1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES (2) & (3) PAIR 50 WATT LOUDSPEAKERS including 12" UNITS and H.F. HORNS Model T50H £49.99 ea.

SAVE £40
£199.95
 Carr. etc £13

- * DISCOMAJOR POWER DISCO CONSOLE Mk.II with integral Power Amplifier **£149.98.**
- * TWIN FULL SIZE turntables with cueing device.
- * CARTRIDGES with Diamond Styl.
- * SEPARATE VOLUME CONTROLS for each turntable and Mic.
- CONSOLE COMPLETE WITH L.I.D. FULL HEADPHONE MONITORING FACILITIES.

TERMS FOR SYSTEM
 Dep. £29.95 and 38 weekly payments £5.33 (Total £232.49)

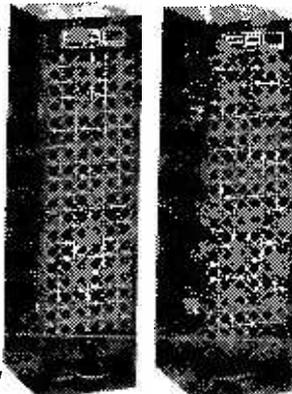DECOR LIGHT BOXES
 Standard Pair. List Price £58.32
 Total 6 lamps. Size 31" x 8 3/8" x 9" each half.



LIGHTING SYSTEM 'A'
 3 units complete with connecting leads
£89.95

or Deposit £9.95 and 38 weekly payments
£2.48 Total
£104.19 Carr. £3



List Price **£39.95**

AUTOMATIC RHYTHMLIGHT
 3-channel sound-to-light converter. Features separate channels for multicolour sequence light actuated from the bass, middle and treble frequencies of your sound system. Operates from L.S. outlet of amplifier. 750 watts capacity per channel. Total cost of above units normally

£98.27

MAIL ORDERS & EXPORT ENQUIRIES TO:—
 AUDIO HOUSE, HENCONNER LANE, LEEDS, 13.
 Tel. 0532 577631.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS

DISCO MODULES Make your own console
CONTROL UNIT (mains powered)



Vol. (left) Vol. (Right) Tape input and volume control. Bass, Treble, ON/OFF switch for each Table.

MONITOR UNIT With H/Phone Socket and Vol. Control Carr. Free.

FADER UNIT Carr. Free
100w OUTPUT UNIT
 Mains powered Carr. £1.50

TITAN GROUP/DISCO SPKRS

	Value	RSC Price
T12/45R 12" 45w	£18.00	£13.95
T12/60R 12" 60w	£22.50	£16.95
T12/100 12" 100w	£36.00	£25.95
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£51.00	£39.95

£25.00
 Carr. £1

£7.95

£7.95

£29.95



Rating RMS Imp 8-15 ohms

ALL RSC PRICES INCLUDE VAT



Barclaycard & Access
 PHONE ORDERS quoting CARD NUMBER accepted

- OPEN ALL DAY SATS (5 Day Week)**
- BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349
 - BIRMINGHAM** 30/31 Great Western Arcade. (Closed Wed.). Tel. 021-236 1279
 - CARLISLE** 8 English Street (Closed Thurs.). Tel. 38744
 - COVENTRY** 17 Shelton Sq., The Precinct. (Closed Thurs.). Tel. 25983
 - DERBY** 97 St. Peter's Street (Closed Wed.). Tel. 41361
 - DEWSBURY** 9/11 Kingsway (Closed Tues.). Tel. 468058
 - DONCASTER** 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069
 - EDINBURGH** 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
 - GLASGOW** 403 Sauchiehall Street Tel. 041-332 0700
 - HULL** 7 Whitefriargate (Closed Thurs.). Tel. 20505
 - LEICESTER** 32 High Street (Closed Thurs.). Tel. 56420
 - LONDON** 238 Edgware Road, W.2 (Closed Thurs.). Tel. 723 1629

Carr. £1-20, under £18, over this add 6p per £1.

ASTRA-PAK

92 GODSTONE ROAD
 WHYTELEAFE SURREY CR3 0EB

All prices include V.A.T. Add 25p for P & P (Extra for overseas). Discounts over £10 less 5%, over £20 less 10%, over £50 less 15%, over £100 less 20%. Send SAE for complete list of components.

7400 0.12 0.21	7484 0.90	74163 0.80 0.82	74368 0.52	20 pin 0.27
7401 0.12 0.21	7485 0.88 0.97	74164 0.89 1.20	74368 0.52	22 pin 0.29
7402 0.12 0.21	7486 1.28	74165 0.89	74390 1.90	24 pin 0.30
7403 0.12 0.21	7486 1.50	74166 0.99	74393 2.00	28 pin 0.44
7404 0.13 0.21	7489 2.00	74167 2.70		40 pin 0.55
7405 0.13 0.21	7490 0.35 0.95	74169 2.10	LINERS	
7406 0.28	7491 0.65	74170 1.88 1.94	CA3045 -14 0.45	CMOS
7407 0.28	7492 0.44 0.82	74172 4.00	CA3046 -14 0.70	4000 0.14 4067 3.50
7408 0.14 0.21	7493 0.40 0.95	74173 1.16 1.12	LM3800 -14 0.82	4001 0.15 4068 0.24
74508 0.40	7494 0.80	74174 0.89 1.12	LM3801 -14 1.20	4002 0.16 4069 0.17
7409 0.14 0.21	7495 0.54 1.05	74175 0.68 1.12	LM710N -14 0.32	4006 0.82 4070 0.17
7410 0.13 0.22	7496 0.80 1.30	74S175 3.25	LM711N -14 0.32	4007 0.16 4071 0.17
7411 0.18 0.21	7497 2.00	74176 0.80	MC1310P -14 1.50	4008 0.92 4072 0.17
7412 0.21 0.21	7497 2.00	74177 0.82	NE555N -8 0.30	4009 0.45 4073 0.17
7413 0.25 0.46	74100 0.94	74178 1.20	NE555N -14 0.65	4010 0.48 4075 0.17
7414 0.54 1.05	74104 0.40	74179 1.10	NE2501B -14 0.20	4011 0.15 4076 1.05
7415 0.21	74105 0.40	74180 0.90	SN72702N 0.50	4012 0.16 4077 0.46
7416 0.27	74107 0.28 0.40	74180 0.90	SN75110N 0.50	4013 0.42 4078 0.22
7417 0.27	74109 0.45 0.40	74181 1.75 3.38	SN76003N 1.95	4014 0.80 4081 0.17
7420 0.13 0.21	74110 0.46	74182 0.75	SN76013N 1.35	4015 0.77 4082 0.20
7421 0.28 0.21	74111 0.70	74182 2.30	SN76023N 1.35	4016 0.42 4083 0.17
7422 0.17 0.21	74112 0.40	74183 0.99	SN76033N 1.95	4017 0.77 4088 0.76
7423 0.25	74113 0.30 0.40	74184 1.20	TAA5508 0.35	4018 0.87 4089 1.65
7425 0.20	74114 0.40	74185 1.20	TAA681B 1.40	4019 0.42 4093 0.85
7426 0.25 0.28	74116 1.80	74186 7.20	TBA120S 0.84	4020 0.92 4094 1.80
7427 0.25 0.30	74118 0.82	74188 2.70	TBA61A 1.68	4021 0.82 4095 1.10
7428 0.34 0.34	74119 1.25	74189 3.60	TBA800 0.75	4022 0.82 4096 1.10
7430 0.13 0.21	74120 0.82	74190 1.05 0.96	TBA810S 1.04	4023 0.15 4097 3.50
7430 0.13 0.21	74121 0.25	74191 0.99 0.96	TCA2705Q 2.00	4024 0.66 4098 1.12
7430 0.13 0.21	74122 0.40	74192 0.99 1.50	TQA2020 1.20	4025 0.15 4099 1.90
7432 0.24 0.31	74123 0.50 0.59	74193 1.05 1.50	ZN414 3.00	4026 1.28 4404 1.00
7437 0.24 0.26	74124 1.25	74194 0.80 2.00	OP AMPS	4027 0.50 4412 0.30
7438 0.24 0.26	74125 0.40 0.46	74195 0.80 1.12	CA3130 -T099 1.00	4028 0.87 4421 0.30
7440 6.13 0.22	74126 0.45 0.46	74196 0.90 1.15	LM301A -8 0.30	4029 0.86 4445 1.50
7441 0.52	74128 0.62	74197 0.90 1.15	LM301A -T099 0.46	4030 0.48 4449 0.30
7442 0.55 0.70	74132 0.68 0.82	74198 1.48	LM348N -14 1.00	4031 2.34 4501 0.17
7443 0.90	74134 0.36	74199 1.48	LM709 -8 0.40	4033 1.25 4502 0.88
7444 0.80	74135 0.68	74201 1.50 1.05	LM709 -14 0.42	4034 2.00 4507 0.50
7445 0.70	74136 0.55 0.40	74247 1.50	LM709 -T099 0.50	4035 1.00 4508 2.25
7446 0.70	74137 0.94	74248 0.95	LM741 -8 0.22	4036 2.40 4510 1.06
7447A 0.80 0.94	74138 0.62	74249 0.95	LM741 -14 0.20	4037 0.99 4511 0.98
7448 0.80 0.94	74139 0.62	74251 1.00 0.95	LM741 -T099 0.45	4038 1.00 4512 0.92
7449 0.80 0.94	74140 0.58	74252 1.10	LM741 -14 0.70	4039 2.80 4514 2.85
7450 0.13	74142 2.00	74253 2.15	LM3900N -14 0.60	4040 0.88 4515 2.82
7451 0.13 0.21	74143 2.00	74257 1.12	NC1458P -8 0.42	4041 0.77 4516 1.02
7453 0.13	74144 2.00	74260 0.25	VOLTAGE REG	4042 0.72 4518 0.98
7454 0.13 0.21	74145 0.64 1.20	74261 3.25	LM300 -T099 1.00	4043 0.82 4519 0.50
7455 0.13 0.26	74147 1.30	74266 0.43	LM309K -T03 1.30	4044 0.82 4520 1.05
7460 0.13	74149 1.15	74273 2.15 1.80	W4723 -14 0.40	4045 1.40 4521 1.00
7470 0.28	74150 0.99	74279 0.55	7805 T0220 0.85	4046 1.32 4522 1.35
7472 0.22	74151 0.60 0.90	74283 1.70 1.05	7812 T0220 0.85	4047 0.96 4527 1.80
7473 0.26 0.36	74153 0.60 0.56	74284 6.85	7815 T0220 0.85	4048 0.60 4528 0.92
7474 0.26 0.36	74154 1.00 1.32	74289 3.92	7824 T0220 0.85	4049 0.42 4529 1.10
7357A 0.50	74155 0.63 0.98	74290 0.95	7905 T0220 1.10	4050 0.42 4536 3.56
7475 0.30 0.42	74159 0.82 0.88	74293 1.35 1.00	7912 T0220 1.10	4051 0.84 4553 4.20
7476 0.26 0.39	74157 0.63 0.60	74298 1.92 1.40	7915 T0220 1.10	4052 0.84 4555 4.80
7478 0.45	74158 0.58 0.62	74352 1.00	OIL SOCKETS	4053 1.04 4556 0.85
7480 0.45	74159 1.70	74353 1.05 0.8	11 4054 1.10 4558 1.25	4054 1.10 4558 1.25
7481 0.80	74160 0.80 1.30	74365 0.52 14 pin	12 4055 1.00 4566 1.40	4055 1.00 4566 1.40
7482 0.76	74161 0.80 0.80	74366 0.52 16 pin	13 4060 0.98 4583 0.76	4060 0.98 4583 0.76
7483 0.72 0.97	74162 0.80 1.30	74367 0.46 18 pin	14 4066 0.48 4585 1.03	4066 0.48 4585 1.03

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ainelle) Copy of original article supplied on request

- IF Sub-Assembly (G8) **£7.65.** P & P 75p.
- Mullard ELC1043 V'cap UHF Tuner **£6.19.** P & P 35p.
- 3-way Station Control Unit **£1.35.** P & P 25p.
- 6-way Station Control Unit (Special Offer) **£1.12.**
- Power Supply Prtd Circuit Board **£1.12.** P & P 30p.
- Res, Caps, Semiconds, etc. for above **£6.53.**
- Mains Transformer for above **£2.81.** P & P 30p.

(Price of goods includes 12 1/2% VAT) P & P all items 85p.
 Callers welcome at shop premises.
MANOR SUPPLIES
 172 WEST END LANE, LONDON NW6
 (Near W. Hampstead Tube Stn.) Tel. 01-794 8751


PHILIP H. BEARMAN

PLEASE ENQUIRE RE NEW COLOUR PRICES. (Colour CGE £3-50) 6 POTTERS Rd, NEW BARNET HERTS. SAE WITH ENQUIRIES PLEASE.

- Telephone enquiries welcomed. Tel: 01-449-1934/5.
 LARGE RANGE OF BVA & QUALITY VALVES. SAE LISTS.
 (Tel. Answering Machine: 449/1934 only.)
- NEW MONO TUBES, USUALLY 2 YEAR GUARANTEE.**
- A31/120; A31/300; A31/410W. **£18.50** incl VAT
 - A34/100; CME 1420 (M6529 FZP) **£19.50** incl VAT
 - A38/160; CME 1520, Thom. **£19.50** incl VAT
 - A44/120; CME 1713, Thom. **£19.50** incl VAT
 - Few AW47/91; CME 1903, A47.14W **£12.00** incl VAT
 - A47/11W; A47.26WR, Mullard, few only. **£15.00** incl VAT
 - A47/13W; CME 1906, Thom. (Limited Stocks) **£15.00** incl VAT
 - A50/120W; CME 2013, Vega. (Mullard Extra) **£18.00** incl VAT
 - A59/15W (AW59.91), Mullard. **£11.00** incl VAT
 - A61/120WR (CME2413) Vega (Mullard Extra) **£21.00** incl VAT
- VARIOUS OTHERS (Subject to availability) - NO 90° PORTABLE TYPES OR 310/340 PREFIX TYPES.
 CARRIAGE MAINLAND £2.25p EACH, ENQUIRIES SAE. (310, 340 SERIES).

Simply ahead!

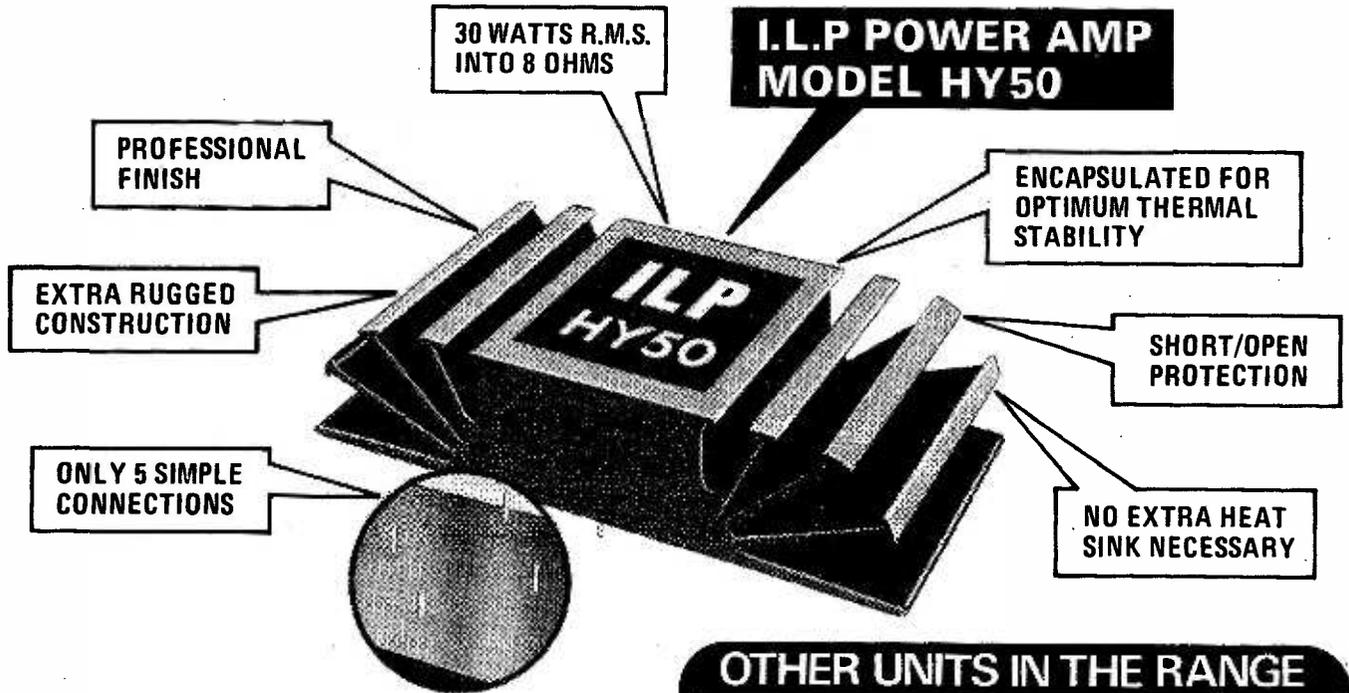**HIGH PERFORMANCE MODULAR UNITS
BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE**



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build or up-grade a hi-fi system, run a small high quality P.A. system, amplify a musical instrument (say for practise or small range use) or use it for lab work. Its useful 30 watts RMS output into 8 ohms, its rugged construction and freedom from heatsink worries make HY50 the ideal all-purpose quality power amp – and it is unconditionally guaranteed for five years. Tens of thousands are in use throughout the world.

... and a spec that means just what it says!

Encapsulated power amp with integral full-rated heatsink.

Input – 500mV
Output 30 watts RMS/8Ω
Load Impedance – 4 to 16Ω
Distortion – 0.04% from 100mW to 25 watts at 1KHz/8Ω
Supply Voltage – ±25V. Size 105 x 50 x 25mm
Inc. V.A.T. and postage in U.K.

£8.15

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensure world leadership for I.L.P. Now we have up-graded output ratings and down-graded prices to bring I.L.P. within easier reach of all who want the best.

New production techniques enable us to reduce prices by an average of 20%, making I.L.P. a better buy than ever. Prices subject to amendments if VAT rate is changed.

Guaranteed 7 days despatch on all products

USE OUR FREE POST SERVICE for sending your orders, requests for information sheets etc. Simply address envelope.

NO STAMPS REQUIRED.



FREEPOST 1
Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP
Phone(0227)54778 Telex965780

OTHER UNITS IN THE RANGE

All prices inc. V.A.T. & Postage in the U.K.



HY5 PRE-AMPLIFIER

Compatible with all I.L.P. power amps, and P.S.U.'s. In a single pack, needs external pots and switches. Multi-function equalization. 5 inputs. High overload margin. Active tone controls, 500 mV out. Distortion at 1 KHz – 0.01%.


Two connect easily for stereo. **£5.22**



THE POWER AMPS

With heatsinks, full load line and thermal protection. Distortion typically 0.05% at 1 KHz.

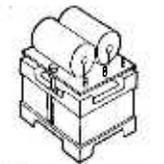HY120 60 Watts RMS/8Ω 114 x 50 x 85mm **£16.42**
HY200 120 Watts RMS/8Ω 114 x 50 x 85mm **£19.92**
HY400 240 Watts RMS/4Ω 114 x 100 x 85mm **£29.89**



THE POWER SUPPLY UNITS

(Split line outputs to suit I.L.P. power amps and HY5)

PSU60 for 1 or 2 x HY50 **£9.11**
PSU70 for 1 or 2 x HY120 **£14.70**
PSU90 for one HY200 **£14.70**
PSU180 for one HY400 or 2 x HY200 **£24.80**

Information sheets on application – Use our FREEPOST Service.

★ NOW-PRICES DOWN BY 20%

Please supply

Total Purchase Price

I Enclose Cheque Postal Orders

Please debit my Access/Barclaycard Account number

Name

Address

Signature

Reg. Bus. No. 1032630 Eng. FP1/7



MICROWAVE MODULES LTD

HAVE YOU BEEN CONVERTED?

In this special issue of "Practical Wireless" we are featuring details of our wide range of VHF and UHF frequency converters and preamplifiers, which are intended for use with existing receivers to provide coverage of various amateur bands, both VHF and UHF.

As space only permits a brief description of these units, we suggest that you contact us for any further details you may require, and to discuss any particular requirements you may have for similar converters etc.,

★ MMC28/144 ★

10 metre converter having an I.F. output on the 2 metre band. 10 metres is wide open to the entire world at the moment, so don't miss out on the REAL DX. GAIN: 15dB NOISE FIGURE: 1.8dB PRICE: £20.25 inc. VAT. DELIVERY FROM STOCK.

★ MMC144/28 ★

2 metre converter having an I.F. output on the 10 metre band. GAIN: 30dB NOISE FIGURE: 2.5dB PRICE: £20.25 inc. VAT. DELIVERY FROM STOCK THIS UNIT IS ALSO AVAILABLE FOR THE 136MHz SATELLITE BAND AND THE 156MHz MARINE BAND.

★ MMC432/28-S & MMC432/144-S ★

70 cm converter with dual range coverage of 432-436 MHz. Available with an I.F. output on 10 metres or 2 metres as required. GAIN: 30dB NOISE FIGURE: 3.0dB PRICE: £29.90 inc. VAT! DELIVERY FROM STOCK

★ MMA28 ★

Low noise 10 metre preamplifier for use with existing receivers to improved sensitivity. Two levels of gain are included, 30dB and 20dB. NOISE FIGURE: 1.8dB PRICE: £14.63 inc. VAT. DELIVERY FROM STOCK

MMC432/28-S PICTURED ABOVE



★ MMA144 ★

Low noise 2 metre preamplifier for use with existing receivers to improve sensitivity. Two independent outputs are included to feed two receivers, for example. GAIN: 18dB NOISE FIGURE: 2.5dB PRICE: £14.63 inc. VAT. DELIVERED FROM STOCK

Any further information on the above products and others from our extensive range may be obtained by contacting our sales department, who will be only too pleased to help.

ALL MICROWAVE MODULES PRODUCTS ARE FULLY GUARANTEED FOR 12 MONTHS

OTHER PRODUCTS AVAILABLE INCLUDE VHF and UHF Linear Amplifiers, VHF and UHF Linear Transverters, VHF and UHF Converters & Preamplifiers, 500 MHz Digital Frequency Meters

MICROWAVE MODULES
BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN,
Telephone: 051-523 4011 Telex 628608 MICRO G



Wilmslow Audio

THE firm for speakers!

SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNOY ● VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount Hi-Fi Etc. at 5 Swan Street and 10 Swan Street
Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

SINCLAIR PRODUCTS PFM200 £49.48, case £3.24, adaptor, £3.24, connector kit £10.58. Microvision TV UK model £89.95, mains adaptor £8.73. PDM36 £28.95, £3.19. DM350 £68.95, DM450 £97.95, DM235 £48.45, rechargeable batts £7.50, mains adaptor £3.70, case £8.45, enterprise prog calculator with £12.13, prog cambridge prog calculator £12.13, prog library £4.45, mains adaptor £3.20. **CSC** MAX100 freq meter £83.75. **CALSCOPE** oscilloscopes send see for data or see the Calscope advert in this magazine. Super 6 £174, Super 10 £238. **COMPUTER GAMES** Star chess £69, chess challenger 7 £95, checker challenger 4 £84, checker challenger 2 £44, Atari Video computer £158, cartridges £13.45. **COMPONENTS** IN4148 1.4p, IN4002 2.9p, 741 15p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4.5p, resistors 1/4W 5% £12, 10R to 10M 1p, 0.8p for 60+ of one value, 18V electrolytics, .5/1/2/5/10/22uf 5p, 100uf 5p, 100uf 10p, 1uF FcCl £1.13, dolo pen 79p, 40 sq in pcb 80p. **TV GAMES** AY-3-8500 + kit £8.95, rifle kit £4.95, AY-3-8610 + kit £15.70, stunt cycle chip + kit £16.70, AY-3-8603 chip £8.90. **TRANSFORMERS** 6-0-6V 100ma 74p, 1 1/2 £2.35, 6-3V 1 1/2 £1.89, 9-0-9V 75ma 74p, 1a £2.2a £2.80, 12-0-12V 100ma 90p, 1a £2.49.

IC AUDIO AMPS with pcb, JC12 6W £1.80, JC20 10W £2.95. **BATTERY ELIMINATORS** 3-way type 6/7/9v 300ma £2.95, 100ma radio type with press-studs 9V £3.35, 9V+9V £4.50, car converter 12v input, output 4 1/2/6/7/9v 800ma £2.50. **BATTERY ELIMINATOR KITS** 100ma radio types with press-studs 4+4v £1.40, 6v £1.40, 9v £1.40, 4+4+4+4v £1.80, 8+8v £1.80, 9+9v £1.80, stabilized 8-way types 3/4/6/7/9/12/15/18v 100ma £2.80, 1amp £6.40, stabilized power kits 2-18v 100ma £2.80, 2-30v 1A £6.85, 2-30v 2A £10.95, 12v car converter 6/7/9v 1A £1.35. **T-DEC AND CSC BREADBOARDS** d-acc £3.80, 1-dec £4.02, u-deca £4.40, u-decb £6.73, 16 dll adaptors £2.17, exp4b £2.48, exp300 £8.21, exp350 £3.40, exp325 £1.73. **BI-PAK AUDIO MODULES** #450 £23.51, AL60 £4.86, PA100 £16.95, aprm80 £4.47, brm80 £5.95, stereo 30 £20.12, AL30 £36.95, PA12 £7.80, PS12 £1.39, MA60 £38.44.

SWANLEY ELECTRONICS
Dept PW, 32 Goswell Rd., Swanley, Kent
Post 30p extra, prices include VAT.
Official and overseas orders welcome.
Lists 20p post free.

SOUTHERN VALVE CO. NEW BARNET, HERTS.

Telephone 01-440/8641 NO CALLERS PLEASE MINIMUM ORDER 80p

Some leading makes available. VAT includes issued on request. SVA valves do NOT carry any guarantee. Enquire prices. Some Mullard Moxide available at extra cost. NOTE: PLEASE VERIFY CURRENT PRICES. Correct only at time of going to press.

DY887	55p	EF86	55p	GY501	£1.40	PCF802*	82p	PL38	£1.10	PY500A	£1.80
DY802	55p	EF88	75p	PC88	80p	PCF806	£1.80	PL81A	70p	UBF89	55p
ECC81	60p	EF83	85p	PC89	80p	PCF806	75p	PC85	75p	UCB85	55p
ECC82	63p	EF184	55p	PC97	75p	PCF808	£1.80	PL84	50p	UCH81	50p
ECC83	63p	EH90	60p	PC900	65p	PCL82	65p	PL500	£1.20	UCL82	78p
ECC85	63p	EL34	£2.00	PCC84	35p	PCL83	£1.10	PL504	£1.20	UCL83	95p
ECH81	55p	EL84	52p	PCC85	53p	PCL84	70p	PL508	£1.78	UJF89	55p
ECH84	85p	EL509	£3.00	PCC89	50p	PCL805	65p	PL509	£3.05	ULJ41	95p
ECL80	52p	EM84	90p	PCC189	55p	PCL85	85p	PL513	£3.30	UL84	90p
ECL82	65p	EY86-7	48p	PCF80	80p	PCL86	85p	PL802*	£2.90	UY85	60p
ECL86	72p	EY500A	£1.60	PCF86	80p	PCL200	£1.45	PY88	90p	UZ5	60p
EF80*	42p	EZ80	43p	PCF200	£1.60	PD500	£3.70	PY800	70p	UZ6	60p
EF85	45p	EZ81	45p	PCF801	60p	PFL200	£1.35	PY801	70p		

Same day postal despatch. CWO ONLY, No C.O.D. or CREDIT Cards. MANY OTHERS AVAILABLE Post free over £25. £6 to £25-80p (max.)

Items in stock at time of going to press but subject to possible market fluctuations if unavoidable. STOP PRESS! One valve post 15p, each extra valve 6p. Large valves 2p each extra. STOCKISTS UHF WIDE BAND MAX 75p. LISTS AND ENQUIRIES, S.A.E. PLEASE! "MICRO" AERIAL ALL PRICES INCLUDE VAT @ 12 1/2%. E240/41, 66p each SIZE 1 1/2"x3" only £3.70p incl. ENQUIRIES WELCOMED FROM TRADE and RETAIL (same prices)

Catronics FOR BEST VALUE IN THE FINEST SHORTWAVE RECEIVERS

Lowie SRX30 as featured in this issue of P.W. Utilises a drift cancelling loop system to give performance plus. 500KHz - 30MHz coverage, USB/LSB/AM/CW, 240Vac/12Vdc supply. **£175**

Trio R300 with dual conversion on higher frequency band (above 18 MHz). 170KHz-30MHz coverage, USB/LSB/AM/CW, 120Vac/240Vac/12Vdc supply or internal batteries. **£185**

Both the above receivers are currently available from stock. Prices include VAT (12½%) but please add £3.50 for Securicor delivery.

CATRONICS FOR THE FINEST AMATEUR RADIO EQUIPMENT

Trio TR2300 2m FM portable transceiver PLL with all 80 FM channels **£195**
Trio TR3200 70cm FM handy transceiver fitted 3 channels **£186**
AR240 2m synthesised FM hand-held transceiver in 5KHz channels **£195**

USED AMATEUR EQUIPMENT

Catronics always have a good selection of reliable used and secondhand equipment - all with 3 months GUARANTEE, including TR2200G: £100-£120 and Liner 2: £100.

JAYBEAM AERIALS

Catronics stock the full range of amateur VHF & UHF aerials - S.A.E. for list and special prices.

MICROWAVE MODULES

Converters and transverters for 2m & 70cm - send S.A.E. for illustrated leaflet and price list.

All our prices include VAT (12½%)

Easy Terms available, Access and Barclaycard welcome.

**CATRONICS LTD., COMMUNICATIONS HOUSE,
(Dept. 988) 20 WALLINGTON SQUARE,
WALLINGTON, SURREY SM6 8RG.**

Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat. 1 p.m.)

BUILD YOUR OWN METAL DETECTOR TR/IB TR/VCO BFO . . .



Test equipment not required. Manuals for kits available at 25p each (refundable). UK prices post & VAT paid except where mentioned. Overseas: write for quote. Literature available: SAE please.

Shadow TR/IB (illustrated)

A true transmit receive/induction balance metal detector - uses the latest circuitry for maximum range and sensitivity. Speaker or phones. Pre-assembled search head with light-weight closed cell foam encapsulated coils for thermal insulation and water resistance. A very powerful machine!

Shadow TR/VCO

An advanced version of the above detector, use it as a sensitive TR/IB machine or switch to VCO mode when the depths achieved approach the maximum "in air" range. Low power requirement: runs on standard 9 volt batteries. The most sophisticated detector available as a kit.

Shadow TR/IB kit **£22.50 (£29.95 assembled)**
 Shadow TR/VCO kit **£27.50 (£36.95 assembled)**
 Padded stereo headphones suitable for 'Shadow' **£5.50**

Designing your own detector? Then we can supply the (hard to obtain) hardware "shell" including fully adjustable shaft with handle, search head moulding with hinge assembly, special clips to mount your own control housing (any box is suitable) completely non-metallic; suitable for any type of detector (TR-PI-VLF-BFO etc). Supplied undrilled as a kit with full instructions (as used on our Shadow range). **Detector Shell kit £8.50**

Low cost BFO detector 200mm (8") annular search head gives wide scan with easy pinpointing. Simple high efficiency circuit draws <3mA. Extra lightweight 300gms (10.5ozs) with battery. Very detailed construction manual; ideal as a first project. Absolutely everything supplied including pre-assembled search head, tuning coil and earpiece.

ALT3 detector (kit) - **£13.95**.
 Padded high Z headphones for ALT3: **£4.90**.

Order by post or phone (24 hours) - for quickest delivery quote credit card number. Callers by appointment only please!

ALTEK Dept. (P.W.) 1 Green Lane,
Walton-on-Thames, Surrey.
Phone (093 22) 44110

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
 Radio, TV Electronics Technicians
 Technical Communications
 Radio Servicing Theory
 Radio Amateurs
 Electrical Installation Work
 Also MPT Radio Communications Certificate

Diploma Courses

Colour TV Servicing
 Electronic Engineering and Maintenance
 Computer Engineering and Programming
 Radio, TV and Audio, Engineering and Servicing
 Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1990
 Dept K276 Intertext House, London
 SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 8 x 5in. £2-50. 5in. £1-50.
6 1/2in. £1-80. 8in. £2-60. 10in. £3. 12in. £4.
8 ohm. 2 1/2in. £1-50. 3in. £1-50. 5in. £1-50. 10in. £3. 12in. £4.
16 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 5in. £1-50. 8in. £2-60.
10in. £3. 12in. £4. 10 x 6in. £3-50.


THE "INSTANT" BULK TAPE ERASER
Suitable for cassettes, and all sizes of tape reels.
A.C. mains 200/249V.
Leaflet S.A.E. **£5-50** Post 50p



HEAD DEMAGNETISER PROBE £4-75

A.C. ELECTRIC MOTORS

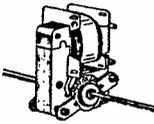2 Pole, 240V, .2 Amp. Spindle — 1.43 x 0.212in. £1-75. 2 pole, 240V, .15 Amp. Double spindle — 1.75 x 0.16in. Each £1-50. 2 Pole, 120V, .5 Amp. Spindle — 0.75 x 0.2in. Two in Series — 240V, 75p each. Brush Motor. From a Food Mixer 240V, 3 Amp. High Speed and Powerful. Spindle — 0.5 x 0.25in. £2-95 post 50p each.



BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p; 8 x 6in. £1-40; 10 x 7in. £1-55; 14 x 9in. £1-90; 16 x 6in. £1-85; 12 x 3in. £1-20; 16 x 10in. £2-20; 12 x 8in. £1-70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1-16.

ALUMINIUM ANGLE BRACKET 6 x 1/2 x 2 1/2in. 20p.

ALUMINIUM BOXES, MANY SIZES IN STOCK.
4 x 2 x 2in. 86p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1; 8 x 6 x 3in. £1-90; 12 x 5 x 3in. £2; 6 x 4 x 4in. £1-30. 10 x 7 x 3in. £2-20.

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in. With CERAMIC STEREO CARTRIDGE
Garrard 2025 Autochanger with ceramic cartridge. **£14-95**
Garrard Minichanger. Plays all size records. Ceramic cartridge. Stereo. **£8-95**
BSR. P182. Snake arm, flared Aluminium Turntable Stereo ceramic cartridge. Latest model. **£22-50**
BSR. Disco Single Player Cueing Device 1 lin. Turntable. Budget price **£19-50**
RSC Disco Deck 3 speed Stereo **£8 or £15 pair**



BAKER 50 WATT AMPLIFIER £59



Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet.

BAKER 150 Watt AMPLIFIER 4 inputs £79.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Post 35p **£3-25**

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. Post 35p **£2-95**

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi and all Disco Amplifiers. Cabinet extra £4. **£17**

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4. or 12 for £7-50.


MAINS TRANSFORMERS

6 VOLT 1/2 AMP. £1-00 3 AMP. £1-95 9 VOLT 3 AMP. £2-75
12 VOLT 300 MA. £1-00 750 MA. £1-30 20 VOLT 2 AMP. £2-50
30 VOLT 5 AMP. AND 34 VOLT 2 AMP. C.T. £3-45
20 VOLT 1 AMP. £2-00 20-0-20 VOLT 1 AMP. £2-95
30 VOLT 1 1/2 AMP. £2-75 40 VOLT 2 AMP. £2-95 30V 2 AMP. £3
0-20-40-60 VOLT 1 AMP. £3-50 2 x 18 VOLT 6 AMP. £9.
Low Voltage 0-8-12V. 3 AMP £3.
Low Voltage 12-0-12V. 2 AMP £3.

GENERAL PURPOSE LOW VOLTAGE. Voltages available at 2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V **£5-80**
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£5-80**
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8-50**
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11-00**
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£14-50**

R.C.S. TEAK COMPACT SPEAKERS

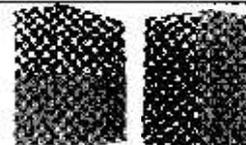13 x 10 x 6in.
50 to 14,000 cps.
10 watts. 4 or 8 ohms.
£16 pair Post £1-50



BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. Useful response 30-13,000 cps.

Bass resonance 55 cps.
GROUP "35" **£14-00**
12in. 40 watt
4, 8 or 16 ohms.

GROUP "50/12" **£21-00**
12in. 60 watt professional model. 4, 8 or 16 ohms.
Response 30 — 16,000 cps.
With aluminium presence dome.

GROUP "50/15" **£33-00**
15in. 75 watt
8 or 16 ohms.

Send for leaflets on Disco, P.A. and Group Gear.



E.M.I. 1 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. 10W. State 3 or 8 ohm. **£8-95** Post 45p

15W model **£10-50** Post 65p
8 ohms Bass unit only.

GOODMANS 20 Watt Woofer

Size 12 x 10in. 4 ohms. Rubber cone surround. **£8-95** Post 65p


GOODMANS TWIN AXIOM 8

8in. 8 ohm Hi-Fi Twin Cone Special unit **£9-95** Post 50p



R.C.S. MINI MODULE HI-FI KIT 15 x 8 1/2in 3-way Loudspeaker System, EMI 5in. Bass 5in. Middle 3in. Tweeter with 3-way Crossover and Ready Cut Baffle. Full assembly instructions supplied.

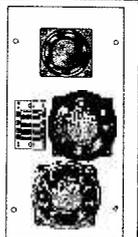Response = 60 to 20 000cps
12 watt RMS. 8 ohm.
£10.95 per kit. Two kits £20.
Postage 75p. One or two kits.



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Minimum post 30p. Components List 20p. Phone orders. Access & Barclay VISA only. Open 9—6 Sat. 9—5 (Closed all day Wednesday) Tel. 01-884 1665

P.W. JUMBO CLOCK

Kits of parts by the designers of the clock.

Kit A.

Comprising of printed circuit board. **Price £8.96.** V.A.T. and postage included.

Kit B.

Comprising of printed circuit board, case, perspex panel, pillars, transformer and l.e.d.s. **Price £22.72.** V.A.T. and postage included.

Kit C.

Comprising of full kit, excluding mains cable and wire. **Price £29.00.** V.A.T. and postage included.

Two colours of cases are available:— Gloss White & Simulated Black Leather Grain.

Please state colour with order e.g. Kit C/Black.

Full range of R.S. components available (48 hours service)

If you are experiencing difficulty in obtaining certain components for projects please do not hesitate to telephone us.

I.C.'s LM3900 & MC3302

£1.13 per pair Postage and package 20 pence.

V mos transistors. VN66AF

£1.30 each Postage and package 20 pence.

P.C.B'S FOR

PRACTICAL WIRELESS PROJECTS

Nov. 78.	Sarum Q Meter	R030	Price £3.30 & 20 pence p & p.
Nov. 78.	S.T.D. Charge Timer	AD212	Price £2.80 & 20 pence p & p.
Nov. 78.	Porch Light Timer	AD222	Price £0.60 & 12 pence p & p.
Nov. 78.	Battery Indicator	AD225	Price £0.60 & 12 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R034	Price £2.35 & 15 pence p & p.
Dec. 78.	Digital Door Chimes	R017	Price £3.78 & 25 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R032	Price £2.62 & 20 pence p & p.
Jan. 79.	Acoustic Delay Line	R018	Price £3.53 & 20 pence p & p.
Jan. 79.	Dorchester	R033	Price £10.80 & 30 pence p & p.
Jan. 79.	Sandbank Met. Det.	R035	Price £3.19 & 20 pence p & p.
Feb. 79.	Hythe Receiver	WR037	Price £5.94 & 20 pence p & p.
March 79.	Hythe Receiver	WR038	Price £2.70 & 20 pence p & p.
March 79.	Soudlite Converter	WK001	Price £5.98 & 20 pence p & p.
March 79.	Tone Burst Generator	R023	Price £1.60 & 15 pence p & p.
March 79.	Wide Band Noise Source	WR036	Price £0.70 & 12 pence p & p.
April 79.	PW 'Winton'	WR039	Price £15.42 & 30 pence p & p.
April 79.	FM Multitester	WR040	Price £2.70 & 15 pence p & p.
May 79.	Car Test Probe	WR042	Price £0.90 & 15 pence p & p.
May 79.	Follow up to PW Gillingham	WR044	Price £1.36 & 15 pence p & p.
May 79.	PW Imp	WR043	Price £1.42 & 15 pence p & p.
May 79.	Inline Crystal Calibrator	WR041	Price £1.58 & 15 pence p & p.
June 79.	Jumbo Clock		Price £8.66 & 30 pence p & p.
June 79.	Logical 0's+X's	WR046/7/8/9	
June 79.	Trent	WR050	Price £12.00 & 30 pence p & p.
July 79.	AAM/FM Frequency		Price £3.80 & 20 pence p & p.
	Readout	WR052	Price £3.42 & 20 pence p & p.
	V.MOS Top Band		
	Transmitter	WR056	Price £3.82 & 20 pence p & p.
	Sound Operated Switch	WK005/6	Price £3.50 & 20 pence p & p.
	Inexpensive A/F Voltmeter	WR055	Price £1.08 & 15 pence p & p.

Send

orders to:

C. BOWES & CO. LTD.,
4, Wood Street, Cheadle, Cheshire SK8 1AQ.
Tel. 061-428-4497.

Please state type number and enclose cheque or postal order.

Can YOUR Antenna do all this?

A SMALL SELECTION FROM OUR HUGE FILE OF TESTIMONIAL LETTERS ON THE JOYSTICK VARIABLE FREQUENCY ANTENNA (.5-30MHz).

G4DJY's COPY LOG shows 68 North Americans worked in the ARRL W/AE contest.

W6TYP worked WA6JPR over hundreds of miles on 40m. using the JOYSTICK VFA and MICROWATTS "equivalent to 1,000,000 MILES PER WATT"—A WORLD RECORD—we can supply conclusive evidence!

"I have used Rhombics, 4 x 1/2 waves in phase, centre fed dipoles, etc., but the success I have had with the V.F.A. has been AMAZING... only 20ft. high... in front of my mobile home, I NEVER RECEIVE LESS THAN R7 AND MOSTLY R9 ON CWDX WORKING—Bob Green, SUIKG/G3APH, W.B.E., W.A.C. Phone and CW.

W7OE, U.S.A. Government Electronics Engr. (ret'd.), claims "VFA 5ft. below ground, same as dipole, elevated 15ft., one "S" point UP on dipole."

IN USE BY AMATEUR TRANSMITTING AND SWL STATIONS WORLD-WIDE AND IN GOVERNMENT COMMUNICATION

JOYSTICK ANTENNAS

SYSTEM "A" £41.00
200 w. p.e.p.
OR for the SWL

SYSTEM "J" £47.95
500 w. p.e.p.
(Improved "Q" on receive)

"PACKAGE DEALS"

COMPLETE RADIO STATIONS FOR ANY LOCATION

All packages include the JOYSTICK VFA (System "A") 8ft feeder, all necessary cables, matching communication headphones. Delivery Securitor our risk. ASSEMBLED IN SECONDS. You SAVE £14.15 on each PACKAGE DEAL!

PACKAGE No. 1. Features R.300 Rx. **£222.00**
PACKAGE No. 2. Features FRG7 Rx. **£237.45**
PACKAGE No. 3. Features SRX30 Rx. **£212.45**
PACKAGE No. 4. Our "Rolls"—Rx. FRG7000. **£402.00**

RECEIVERS ONLY

R.300 £184.50 FRG7 £199.95
SRX 30 £174.95 FRG 7000 £364.50

All prices are correct at time of going to press and include VAT at 12½% and carriage.



Just telephone your card number
Phone 0843 62535 (ext.5)
(or 62839 after office hours)



or write for details, send 9p stamp



5, Patridge House, Prospect Road, Broadstairs, CT10-1LD. (Callers by appointment).

OUR 1979 CATALOGUE

including the first edition of

STOP PRESS

- ★ Latest low prices
- ★ Fascinating new items
- ★ Special offers — a bargain on their own
- ★ Lowest prices ever for TTL
- ★ Free 45p worth of vouchers



CHROMASONIC electronics

DEPT. 16, 56 FORTRIS GREEN ROAD
MUSWELL HILL, LONDON N10 3HN
TELEPHONE: 01-883 3705/2289



USE OUR "ORDER RING" LINES



VAT INCLUSIVE PRICES P&P 25p

CHORDGATE Ltd. SWINDON

Printed Circuit Boards. Add 27p post & packing for 1 to 3 boards. Larger quantities post & packing inclusive

Voltage Tripler P.C.B. contains 40.1 MFD 1000V, 2 pre-sets, 1 bridge rect., 4 IN4007, 9 resistors. 65p.

P.C.B. contains 2 TIP31 (or equiv.), MJE 340 and over 70 other resistors, diodes, zeners, transistors, bridge rect., and capacitors. 50p.

P.C.B. contains 2 x 741, 2N4921 and over 40 other components and multitrn 20k pot. 60p.

P.C.B. contains 2 IP 10W Wafer Switches, 2 x 7490 I/C, 2 x 74141 I/C, various Logic I/Cs, IN4148 and over 50 components. 60p.

P.C.B. with GEC, G424 Triac control IC, 2 SGS transistors, three 9 watt WW resistors and 12 other components. 70p.

P.C.B. with 8 x BC107, 8 x BCY70, 4 pre-set pot., and over 70 other components. 75p.

Parcel of 1 each of above, 6 P.C.B.'s. £3-30.

Post and packing inclusive.

Audio Amplifier Boards containing 2 x BFY50, IBFX29 and output pair of 2N5293 output transistors rated at 36 watts when heatsink mounted £1.75 or 2 for £3.00. Post and packing inclusive.

(Dept B.) 194 A DROVE ROAD, SWINDON, WILTS.

ALL OUR PRICES INCLUDE V.A.T.

CHORDGATE Ltd. SWINDON

ALL NEW AND FULL SPEC DEVICES

Add 27p post and packing. Orders over £2.50 post and packing inclusive.

Fairchild FND10 7 seg displays 0.5" red common cathode. 60p.

Pye Dynamics thick film. 1MHz. Clocking oscillator 5 volt supply. Drives one TTL load. 60p.

Min glass reed switch 20mm length. 10 for 60p.

Beehive trimmer 3-30PF. 10 for 50p.

Denco I.F.T.s. 470kHz interstage IFT13 60p. DET out IFT14 60p.

Tantalum bead 10MFD 6.3v. 10 for 60p.

PCB mounting HCU XTAL 368-640kHz. 75p. 10 for £5.00.

Honeywell plastic snap panel MTG P.B. DP/CO micro-switch. 15p. 10 for £1.25.

Latch and non-latch state type. Multi-turn 500.0HM trim pot PCB mounting. 20p. 10 for £1.50.

Stettner 3-15PF CER min trimmer. Vert mount. 15p. 10 for £1.00.

SILICON SEMICONDUCTORS

TIP31B 25p. Comp TIP32B 25p. 5 pairs £2.00, or 10 either type £2.00.

1N914 2.5p. 25 for 50p. Equiv. 1N4148. 2N5293 NPN 75v, 4A tab collector. 25p. 10 for £2.00.

BFY51. 15p. 10 for £1.20.

2N3707 NPN plastic G.P. 10 for 50p.

TIP34A NPN 60v 10A. 40p. 10 for £3.00.

BD525. 30p. Comp BD526. 30p. 60v 2A. Useful up to 50MHz. 5 pairs £2.50. 10 either type £2.50.

(Dept B) 194A DROVE ROAD, SWINDON, WILTS.

ALL OUR PRICES INCLUDE V.A.T.

RST VALVE MAIL ORDER CO.

CLIMAX HOUSE, FALLSBROOK ROAD, LONDON SW16 6ED

SPECIAL EXPRESS MAIL ORDER SERVICE

SEMICONDUCTORS

AA119 0-11	AAV30 0-29	AAZ13 0-19	AAZ15 0-37	AAZ17 0-29	AC107 0-86	AC125 0-22	AC126 0-22	AC127 0-22	AC128 0-22	AC141 0-27	AC141K 0-38	AC142 0-22	AC142K 0-32	AC176 0-22	AC187 0-22	AC188 0-22	AC189 0-22	AC197 0-92	AC198 0-86	AC199 0-81	AC200 0-76	AC201 0-81	AC202 0-81	AD139 0-82	AD149 0-76	AD161 0-49	AD162 0-49	AF106 0-49	AF114 0-81	AF115 0-81	AF116 0-81	AF117 0-81	AF139 0-43	AF186 1-30	AF239 0-49	AFZ11 2-97	AFZ12 2-97	ASV26 0-43	ASV27 0-43	ASZ15 1-35	ASZ16 1-35	ASZ17 1-35	ASZ20 1-62	ASZ21 2-16	AU110 1-84	AU113 1-84	AU114 1-84	AU115 1-84	BA145 0-15	BA149 0-15	BA154 0-10	BA155 0-11	BA156 0-10	BAW62 0-06	BAX13 0-07	BAX16 0-10	BAX18 0-10	BC107 0-13	BC108 0-13	BC109 0-14	BC113 0-13	BC114 0-14	BC115 0-15	BC116 0-15	BC117 0-15	BC118 0-11	BC125 0-18	BC126 0-23	BC135 0-18	BC136 0-18	BC137 0-17	BC138 0-17	BC146 0-09	BC149 0-10	BC157 0-10	BC158 0-09	BC159 0-11	BC167 0-14	BC170 0-11	BC171 0-11	BC172 0-11	BC173 0-11	BC177 0-16	BC178 0-15	BC179 0-17	BC182 0-14	BC183 0-11	BC184 0-12	BC212 0-14	BC213 0-14	BC214 0-17	BC237 0-10	BC238 0-14	BC301 0-27	BC303 0-26	BC307 0-11	BC308 0-11	BC327 0-23	BC328 0-21	BC329 0-21	BC337 0-21	BC338 0-19	BC340 0-18	BC341 0-18	BC342 0-18	BC343 0-18	BC344 0-18	BC345 0-18	BC346 0-18	BC347 0-18	BC348 0-18	BC349 0-18	BC350 0-18	BC351 0-18	BC352 0-18	BC353 0-18	BC354 0-18	BC355 0-18	BC356 0-18	BC357 0-18	BC358 0-18	BC359 0-18	BC360 0-18	BC361 0-18	BC362 0-18	BC363 0-18	BC364 0-18	BC365 0-18	BC366 0-18	BC367 0-18	BC368 0-18	BC369 0-18	BC370 0-18	BC371 0-18	BF194 0-10	BF195 0-10	BF196 0-11	BF197 0-14	BF200 0-23	BF224 0-23	BF244 0-30	BF257 0-26	BF258 0-26	BF259 0-35	BF336 0-32	BF337 0-32	BF338 0-33	BF341 4-28	BF342 2-41	BF343 0-23	BF344 0-23	BF345 0-23	BF999 0-23	BF1000 0-23
------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	-------------	------------	-------------	------------	------------	------------	------------	-------------

VALVES

AZ31

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200/250V. **PRICE £18.00, P. & P. £1.20.**

SONOTONE 9 TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. **ONLY £2.80 P. & P. 20p.** Also available fitted with twin. Diamond T/O stylus for Stereo LP. £3.00 P. & P. 20p.

LATEST CRYSTAL T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £2.20 P. & P. 20p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £2.20 P. & P. 20p.

STEREO MAGNETIC PRE-AMP sens. 3mV in for 100mV out to 35V neg earth. Equ. \pm 1db. From 20 Hz to 20 KHz. Input impedance 47k. Size 1 1/2" \times 2 1/2" \times 5 1/2". £3.00 + 20p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Size 1 1/2" \times 1 1/2" \times 1/2". Brand new complete with instructions. Price £2.20. P. & P. 30p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" \times 14 1/2" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.40 each + p. & p. (one 90p, two £1.10). Now available in 8" round version. 10 watts RMS 60Hz-20KHz £5.25. P. & P. (one 65p, two 75p).

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2" \times 2 1/2" \times 5 1/2". £3.00 + 20p P. & P.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" \times 4" \times 9 1/2" deep.

LIMITED NUMBER ONLY at £28.00 + £1.50 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT
A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 1/2 speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. **ONLY £18.00, P. & P. £1.40.** Also available ready built and tested **£22.00, P. & P. £1.40.**

STEREO DECODER
SIZE 2" \times 3" \times 1" ready built. Pre-aligned and tested for 9-15V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p. P. & P. Stereo beacon light if required 40p extra.

SPECIAL OFFER

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coil speakers, telescopic aerial and internal ferrite aerial. Earpiece socket for personal listening. Finished in attractive simulated leatherette. Size 7" H \times 9 1/2" W \times 4" D approx. Fully guaranteed. Bargain price of only £10.00 + £1.30 p. & p.

SPECIAL OFFER LIMITED NUMBER ONLY

GOODMANS speakers, 6 1/2" 8 ohm, long throw, ceramic magnet, full range rated 10 watts R.M.S., (when fitted in enclosure). £4.00 each + 80p p&p (p&p on two £1.20).

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £2.00 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω ; Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp.

Overall Size 12" w. \times 8" d. \times 2 1/2" h.
Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £14.50 P. & P. 80p (Magnetic input components 33p extra)

POWER PACK KIT £6.00 P. & P. 95p

CABINET £6.00 P. & P. 95p

SPECIAL OFFER—only £25.00 if all 3 items ordered at one time plus £1.25 p. & p.

Also avail. ready built and tested £31.25. P. & P. £1.50.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" \times 2 1/2" \times 1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10.00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500m/a can be supplied at £2.00 + 40p P & P if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

HARVERSON SURPLUS CO. LTD. (Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station. **Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.**

New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.

Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself—computers, oscilloscopes, transceivers etc. ... Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451). Registered in England, No. 606177.

Soldering Iron offer FREE



New Heathkit CI 1265 Digital Tach/Speedometer. Push-button digital readout. Displays engine speed/rpm. Accurate to 1 mph or rpm variations of 100.

To: Heath (Gloucester) Limited, Dept. PW879 Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.
Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name _____
Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.


When you receive your catalogue you will get details of this free offer.



HEATHKIT
HEATH Schlumberger

RADIO EXCHANGE LIMITED

NEW ELECTRONIC MASTER KIT

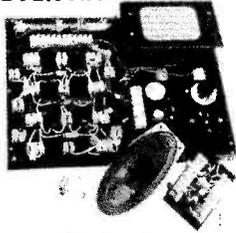

With special V.H.F. Tuner Module to construct. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws, etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

Projects:
 V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster.

£14.99 + P & P £1.10


V.H.F. AIR CONVERTER KIT



Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome-plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. Size 5½" x 1½" x 3½". All parts including case and plans.

£4.95 + P & P and Ins. 60p

ELECTRONIC CONSTRUCTION KIT E.C.K. 2

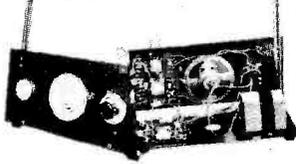


Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 2½ in. loudspeaker, gain control, 7 section chrome-plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P.7 battery (not supplied with kit).

Complete kit of parts

£7.95 + P & P and Ins. 90p


NEW MODEL R.K.1.

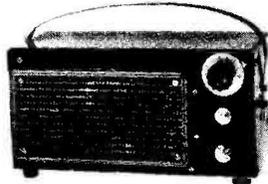

MultiBand A.M. Receiver. M.W.L.W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.

£8.99 + P & P 90p

EDU-KIT JUNIOR

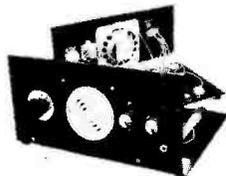


Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including Loudspeaker, Earpiece, M.W. Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.95 + P & P and Ins. 90p

NEW ROAMER TEN MODEL R.K.3.

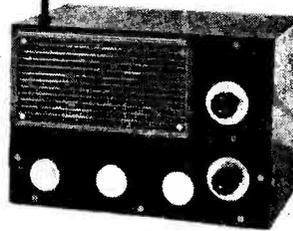

Multiband V.H.F. and A.M. Receiver. 13 Transistors and Six Diodes. Quality Loudspeaker

With Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with separate Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9-9 volt Battery.

Complete kit of parts including carrying strap. Building Instructions and operating Manuals.

£14.79 + P & P £1.10

E.V.6 PLUS ONE




Build this exciting new design. Now with 7 Transistors and 4 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and 2½ in. loudspeaker. Attractive case with speaker grille. Size 9 in. x 5½ in. x 2½ in. approx. All parts including Case and Plans.

Total Building Costs:

£6.95 + P & P and Ins. 90p

EDU-KIT MAJOR

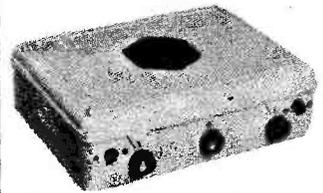

Completely solderless Electronic Construction Kit. Build fifteen projects including:—

- Signal Injector ● Transistor Tester NPN-PNP ● 7 Transistor Loudspeaker Radio MW/LW ● 5 Transistor Short Wave Radio.


Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 5" x 3" Loudspeaker ● Earpiece ● Mica Baseboard ● 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod 6½ yards of wire ● 1 yard of sleeving, etc. Complete kit of parts including construction plans.

Total building costs:

£9.99 + P & P and Ins. £1.10


RADIO CONSTRUCTION KIT Q7

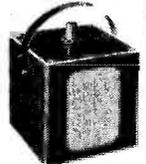

A compact small radio kit covering Medium Wave and Long Wave bands. Rugged Micanite construction and simple square design allows for easy carrying and positioning. Ideal for the Garage, Workroom, Kitchen, etc., has seven Transistors and four Diodes, quality Loudspeaker, ready wound Ferrite Rod Aerial and Carrying Strap. Size 4½" x 4½" x 4½". All parts and plans excluding 9v PP7 Battery.

£6.25 + P & P and Ins. 75p

POCKET FIVE

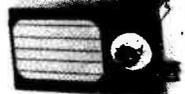

NOW WITH 2½" LOUSPEAKER 3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans.

Total Building Costs

£4.95 + P & P and Ins. 80p

To: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 ISA

Reg. No. 788372

- Callers side entrance "Lavelis" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

All prices include VAT

I enclose £.....for.....

Name

Address

PW879

Largest range of quality components in the U.K. — over 8,000 types stocked

Marshall's

Head Office and Mail Order to Dept. P.W.
A. Marshall (London) Ltd.,
Kingsgate House, Kingsgate Place,
London NW6 4TA. Tel: 01-624 0805.
Telex: 21492.

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 ALSO 325 Edgware Road, W2. Tel: 01-723 4242.
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133 AND Bristol: 108A Stoke's Croft, Bristol. Tel: 0272 426801/2.

TRANSISTORS

2N2219	0-38	2N6122	0-44	BC147	0-13	BD241C	0-65
2N2219A	0-39	2N6123	0-48	BC148	0-13	BD242A	0-65
2N2221	0-25	2N6126	0-48	BC149	0-15	BD242C	0-62
2N2255	0-27	3N200	2-85	BC180	0-38	BDX14	1-32
2N2399A	0-27	40067	0-57	BC181	0-13	BDX18	1-90
2N2646	1-70	40082	0-55	BC189	0-13	BFX30	0-34
2N2903	1-60	40405	0-73	BC177	0-22	BFY50	0-23
2N2904	0-31	40407	0-57	BC178	0-22	BFY51	0-35
2N2905	0-31	40408	0-82	BC179	0-22	BFY90	1-35
2N2905A	0-31	40409	0-82	BC182	0-12	BRY39	0-55
2N2908	0-25	40594	0-87	BC192L	0-12	BZ208	2-70
2N2907	0-25	40595	0-98	BC193	0-12	1300	0-37
2N2926	0-17	40836	1-37	BC183L	0-12	1310	0-64
2N3053	0-25	40873	0-80	BC184	0-12	MJ490	1-49
2N3054	0-22	AC125	0-48	BC184L	0-12	MJ491	2-10
2N3055	0-75	AC127	0-48	BC204	0-12	MJ2500	2-70
2N3439	0-85	AC128	0-48	BC205	0-17	MJ2501	2-75
2N3440	0-75	AC131	0-43	BC206	0-17	MJ2955	1-35
2N3441	0-82	AC152	0-54	BC207	0-17	MJ3001	2-15
2N3442	1-45	AC153	0-59	BC208	0-17	MJ3002	2-36
2N3863	0-29	AC133K	0-58	BC212	0-12	MJ4502	4-84
2N3702	0-14	AC178K	0-70	BC212L	0-12	MJ3340	0-34
2N3703	0-14	AC176	0-54	BC213	0-12	MJ3350	0-62
2N3704	0-14	AC187	0-59	BC213L	0-12	MJ2955	1-85
2N3705	0-14	AC187K	0-65	BC214	0-12	MJ3055	1-05
2N3706	0-14	AC188	0-54	BC214L	0-12	R2018	2-15
2N3707	0-14	AC189K	0-65	BC201	0-43	R2019	2-15
2N3708	0-12	AD161	1-00	BC302	0-37	TP259A	0-48
2N3709	0-12	AD162	1-00	BC303	0-54	TP29C	0-65
2N3771	2-15	AF230	1-30	BC304	0-60	TP30A	0-54
2N3772	2-20	AF231	1-30	BC305	0-22	TP30C	0-70
2N3773	3-15	AF239	1-70	BC517	0-22	TP31A	0-64
2N3819	0-36	AU113	1-70	BCY70	0-21	TP31C	0-72
2N3820	0-39	BC107	0-18	BCY71	0-26	TP32A	0-58
2N3804	0-18	BC108	0-18	BCY81	0-18	TP32C	0-82
2N3905	0-18	BC109	0-18	BD131	0-56	TP33A	0-66
2N3906	0-18	TS43	0-47	BD132	0-75	TP33C	1-18
TP35A	2-20	TL170	0-45	BD135	0-40	TP34A	0-87
TP35B	3-00	ZK107	0-17	BD136	0-40	TP34C	1-31
TP41A	0-76	ZK108	0-17	BD137	0-41		
TP41C	0-97	ZK109	0-17	BD138	0-43		
TP42A	0-86	ZK500	0-16	BD139	0-41		
TP42C	1-08	ZK501	0-17	BD140	0-43		
TP2955	2-25	ZK502	0-19	BD239A	0-44		
TP2955	2-52	BC140	0-30	BD239C	0-58		
2N5459	0-32	BC141	0-32	BD240A	0-49		
2N5460	0-85	BC142	0-32	BD240C	0-58		
2N6027	0-64	BC143	0-32	BD241A	0-48		

See catalogue
for full range

T.T.L

SN7400N	0-17	SN7414N	0-60	SN7442N	0-45	SN7475N	0-60	SN7494N	0-80	SN74145N	0-85
SN7401N	0-17	SN7415N	0-25	SN7445N	0-75	SN7476N	0-45	SN7495N	0-76	SN74148N	1-35
SN7402N	0-17	SN7417N	0-25	SN7446N	0-60	SN7478N	0-80	SN7496N	0-54	SN74150N	0-90
SN7403N	0-17	SN7420N	0-22	SN7447N	0-55	SN7479N	0-80	SN7497N	1-95	SN74151N	0-78
SN7404N	0-15	SN7423N	0-22	SN7448N	0-60	SN7482N	0-80	SN7480N	0-80	SN74153N	0-65
SN7405N	0-22	SN7425N	0-22	SN7449N	0-55	SN7483N	1-05	SN7481N	0-24	SN74154N	1-20
SN7406N	0-38	SN7426N	0-22	SN7451N	0-22	SN7484N	1-20	SN7482N	0-80	SN74155N	0-70
SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	SN74157N	0-78
SN7408N	0-22	SN7430N	0-22	SN7454N	0-20	SN7486N	0-38	SN74121N	0-28		
SN7409N	0-22	SN7432N	0-22	SN7458N	0-22	SN7489N	1-80	SN74122N	0-55		
SN7410N	0-20	SN7437N	0-24	SN7470N	0-38	SN7490N	0-38	SN74123N	0-55		
SN7411N	0-20	SN7438N	0-24	SN7472N	0-30	SN7491N	0-60	SN74124N	1-20		
SN7412N	0-20	SN7440N	0-18	SN7473N	0-36	SN7492N	0-38	SN74125N	0-45		
SN7413N	0-36	SN7441N	0-59	SN7474N	0-28	SN7493N	0-38	SN74141N	0-56		

CMOS

CD4000	0-20	CD4018B	1-05	CD4037	1-20	CD4071B	0-20	CD4096	1-30
CD4001B	0-20	CD4019B	0-52	CD4040	1-12	CD4072	0-27	CD4097	4-85
CD4002	0-18	CD4020B	1-15	CD4041B	0-88	CD4073B	0-20	CD4098	1-80
CD4006	1-25	CD4021	1-05	CD4042B	0-88	CD4075B	0-20	CD4503	0-58
CD4007	0-18	CD4022B	1-00	CD4043	1-05	CD4076B	0-99	CD4507	0-88
CD4008B	0-99	CD4023B	0-80	CD4044	0-00	CD4077	0-78	CD4510B	1-20
CD4009	0-58	CD4024B	0-76	CD4056	1-65	CD4078B	0-27	CD4511	1-75
CD4010	0-58	CD4025B	0-70	CD4059	6-00	CD4081B	0-20	CD4512	0-99
CD4011B	0-20	CD4027B	0-85	CD4068	1-15	CD4082	0-27	CD4514	2-54
CD4012	0-20	CD4028B	0-80	CD4069	0-00	CD4083	0-35	CD4515	2-54
CD4013B	0-52	CD4029B	1-10	CD4066	0-75	CD4085	0-89	CD4516	1-20
CD4014	1-00	CD4030	0-84	CD4067	4-85	CD4088	0-95	CD4518B	1-20
CD4015	0-75	CD4031B	2-25	CD4068	9-27	CD4093B	0-65	CD5415	0-84
CD4016	0-52	CD4034B	2-48	CD4069	0-20	CD4094	2-30	126B	12
CD4017B	1-05	CD4035B	1-30	CD4070B	0-55	CD4095	1-30	126C	12
								126D	12
								126E	400
								126F	0-80
								126G	0-80
								126H	0-80
								126I	800
								126J	1-07

LINEAR

CA3046	0-77	LM339N	0-80	LM747CN	0-78	LM78L12CH	0-85	NE565N	1-00	TAD100	2-80
CA3085E	2-80	LM340T-5	0-88	LM748-6	0-80	LM78L15CH	0-85	NE568N	1-75	TBA120	2-00
CA3130	1-06	LM340T-12	0-88	LM748-14	0-50	LM78L24CH	0-85	NE570N	1-00	TBA841B	3-00
CA3140	1-04	LM340T-15	0-88	LM1310N	2-10	LM7805KC	1-56	NE571N	4-95	TBA800	1-30
LM301AH	0-40	LM340T-24	0-88	LM1458N	0-45	LM7812KC	1-56	SN76003N	3-08	TB8410S	1-30
LM301-9	0-30	LM349N	0-95	LM1498N	0-97	LM7815KC	1-56	SN76013N	2-04	TCA2705	2-00
LM308N	0-55	LM317N	1-80	LM1500N	1-24	LM7824KC	1-56	SN76020N	1-72	TDA102	7-50
LM309KC	1-85	LM378N	2-40	LM1601N	2-25	LM7805CZ	0-30	SN76023N	2-05	TDA2020A	4-50
LM317K	3-38	LM3795	4-25	LM3900N	0-68	LM78L12CZ	0-30	SN760230D	1-72	TLO80CP	0-85
LM319N	2-45	LM390N	1-10	LM3905N	1-15	LM78L15CZ	0-30	SN76033N	3-08	TLO81CP	0-42
LM320T-5	1-86	LM381AN	2-78	LM3909N	0-78	LM7824CZ	0-30	SN76050N	1-58	TLO82CP	0-80
LM320T-12	1-86	LM723C-14	0-45	LM3911N	1-10	NE555P	0-33	SN76680N	0-87	TLO83CN	1-10
LM320T-15	1-86	LM741CH	0-60	LM3913N	P.O.A.	NE568N	0-65	SN76666N	0-99	TLO84CN	1-45
LM320T-24	1-86	LMK110-9	0-30	LM3950N	1-30	NE558N	1-96	SO41P	1-38	XR220CP	3-50
LM324	0-75	LM741C-14	0-60	LM7805CH	0-85	NE562N	4-50	SO42P	1-35	ZN414	1-85

See catalogue for full range

TRIACS

All prices are each	amps	volts	I +	100+	300+	Prices on request
206D	4	400	0-70	0-40		
226D	6	400	0-70	0-40		
226D	8	400	0-70	0-40		
236D	12	400	1-00	0-80		
246D	16	400	1-00	0-80		
253D	20	400	1-21	0-85		
263D	25	400	2-20	1-32		
4057B	15	400	2-20	1-85		
4086B	8	400	1-30	0-83		
4082B	6	450	1-25	0-84		
2N4444	5	800	1-95	1-47		

See catalogue for full range

THYRISTORS

	amps	volts			
106A	4	100	0-38		
106B	4	200	0-44		
106C	4	300	0-48		
106D	4	400	0-54		
118A	8	100	0-50		
118B	8	200	0-54		
118C	8	300	0-61		
118D	8	400	0-68		
126A	8	600	1-00		
126B	12	100	0-83		
126C	12	200	0-70		
126D	12	300	0-80		
126E	12	400	0-80		
126F	12	800	1-07		

100+ prices on request
See catalogue for full range

SIEMENS

LEOS - DPTD	RED 7 seg displays	Lefs	Red	Yell	Gm
HAT081	8mm CAN	1-58	Large	-19	-19
HAT091	8mm CCA	Ex	Bright	-44	-44
HAT093	1-58	Med	-30	-30	-30
HAT101	18mm CAN	Small	-14	-18	-18
HAT102	1-95	Small	-25	-28	-28
HAT103	18mm CCA	Ex bright	-13	TIL 211	-22
HAT183	1-95	TIL 209	-13	TIL 211	-22


Please add 40p for p. & p. to all orders.
Telephone orders £10.00 minimum.

NEW 1979 CATALOGUE
48 page catalogue, largest range, quality components from franchised suppliers available in UK. All VAT inclusive prices. Over 8,000 line items plus lots more. 50p post paid or 40p to callers at any of our branches.

COMPONENTS STOCKED
Transistors, diodes, I.C.s, capacitors, resistors, presets, microprocessors, memories, switches, test equipment, meters, cable, plugs, kits, etc.
See catalogue for full range.

STOCKISTS FOR:
VERO
ANTEX
ELECTROLUBE

Model TCSU1 Micro Soldering Station

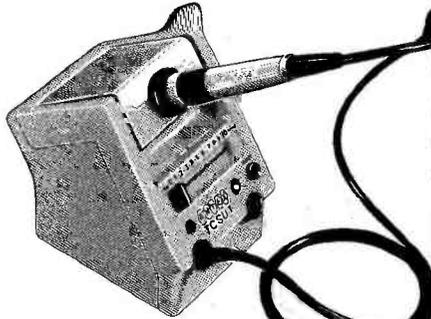

CTC 35 watt—



Accurate pin point temperature control between 65° and 400°C. Heating element and sensor built in tip of iron for fast response. Interchangeable slide-on bits from 4.7mm (3/16") down to 0.5mm. Zero voltage switching, no spikes. No magnetic field, no leakage. Supplied with miniature CTC (35-40 watt) iron or XTC (50 watt). TCSU1 soldering station with XTC or CTC iron **£38.88** including VAT (Nett to Industry). Postage extra.

Model CX - 17 watts



... a miniature iron with the element enclosed first in a ceramic shaft, then in a stainless steel. Virtually leak-free. Only 7 1/2" long. Fitted with a 3/32" bit. **£4.37** inclusive of VAT and P.&P. Range of 5 other bits available from 1/4" down to 3/64"

Model X25 - 25 watts



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at **£4.37** inclusive of VAT and P.&P. Range of 4 other bits available.

Model SK3 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at **£8.21** inclusive of VAT and P.&P. It makes an excellent present for the radio amateur, modelmaker or hobbyist.

Model SK4 Kit



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at **£6.21** inclusive of VAT and P.&P.

Model SK1 Kit

This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet, 'How to solder'. Priced at **£6.48** inclusive of VAT and P.&P.



Model MLX Kit

The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price **£4.83** inclusive of VAT and P.&P.



Now heat to any level

between 145° - 400°c

(with accuracy of 2%)



With the

Antex TCSU1 Soldering Station

All Antex soldering irons are made on the principle of putting the heating element inside a shaft, then the desired bit is eased over the shaft, giving maximum heat transference, this is why so often a small Antex iron can do the job of a larger conventional iron. The precision made slide on bits are slit to make them easily interchangeable.

The ANTEX multi purpose range of soldering equipment is fast becoming a must for every home. Built with precision for long life, each iron is fully tested and guaranteed.

ANTEX soldering irons are made in England to strict local and international standards of safety.

Stocked by many wholesalers and retailers or direct from us if you are desperate.



Mayflower House, Armada Way,
Plymouth, Devon.
Tel: 0752 67377/8
Telex: 45296

Please send me the Antex colour brochure I enclose cheque/P.O./ Giro No. 258 1000

Please send the following

Name

Address

Antex Ltd. Freepost, Plymouth PL1 1BR Tel 0752 67377 PWA

MAINS INTERCOM



**NO BATTERIES
NO WIRES
ONLY
£32.99
PER PAIR
+ VAT 12½%—£4.12**

The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1/2 mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom, between office and warehouse in surgery and in homes. P. & P. 99p.

4-STATION INTERCOM



**£27.95
+ VAT 8%—£2.24**

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. A Battery and other accessories. P. & P. 99p.

TELEPHONE AMPLIFIER



**£17.95
+ VAT 8%—£1.44
+ P. & P. 90p.**

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls; leaves user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £19.95 + VAT 8%—£1.60. P. & P. 90p.

DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boon for the invalid, the aged and busy housewife. Supplied complete d.i.y. kit with one internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock), mains power unit, cable (8-way) 50 ft. and wiring diagram. Price £54.95 + VAT 8%—£5.87 + P. & P. £1.25. Kit with two Telephones £64.95 + VAT 8%—£6.87 + P. & P. £1.50.

10-day price refund guarantee on all items.

**WEST LONDON DIRECT SUPPLIES (PWS)
169 KENSINGTON HIGH STREET, LONDON, W8
01-937 5548**

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V ac. 6.3V 1.5A £2.95; 3A £3.60; 6A CT £6.85; 12V 1.5A £3.35; 3A CT £6.85; 6A CT £6.80; 15V 0.5A £2.75; 18V 1.5A CT £6.85; 24V 1.5A £6.85; 3A CT £8.50; 5A CT £15.50; 8A CT £26.75; 12A CT £35.00; 40V 3A CT £12.25.

TWINEC TRANSFORMERS: Prim 240V ac. 6V 0.6A—6V 0.6A; 9V 0.4A—9V 0.4A; 12V 0.3A + 12V 0.3A; 20V 0.15A + 20V 0.15A; all at £3.65 each; 15V 0.75A + 15V 0.75A £5.65; 15V 1.5A + 15V 1.5A £7.75; 18V 1A + 18V 1A £6.85; 18V 1.5A + 18V 1.5A £8.50; 20V 1.5A + 20V 1.5A £8.50; 12V 4A + 12V 4A £10.50; 25V 2A + 25V 2A £11.50.

MIDGET RECTIFIER TRANSFORMERS: Prim 240V ac. 6.0-6V 1.5A or 9.0-9V 1A £3.00 each; 12V 0-12V 1A or 20V 0-20V 0.75A £3.75 each; 9.0-9V 0.3A or 12V 0-12V 0.25A or 20V 0-20V 0.15A £2.85 each.

LT TRANSFORMERS TAPPED 50%: Prim 240V ac. 0-10-12-14-16-18V 2A £6.50; 4A £8.25; 0-12-15-20-24-30V 2A £7.35; 4A £10.50; 0-20-30-60V 1A £8.25; 2A £10.50; 0-40-50-60-80-100-110V 1A £10.50.

MAINS TRANSFORMERS SPECIAL OFFER: Prim 240V ac. 250-0-250V 80Ma. 6.3V 1A £2.00; 250V 100Ma. 6.3V 2A £3.00; 9V 3A £2.50; 25V 0.3A £1.00.

LOUDSPEAKERS
2 1/2in 8Ω, 2 1/2in 8 or 25Ω, 2 1/2in 8Ω, 3in 35Ω, 3 1/2in 3.8, 16 or 80Ω, all at 1.25 each; 5 x 3in 4, 8, 15 or 25Ω, £1.50; 7 x 4in 4, 8, 16, 25 or 80Ω, £1.75; 8 x 5in 4, 8 or 25Ω, £3.00; 8in 8Ω, £2.50.

"INSTANT" BULK CASSETTE/TAPE ERASER
Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V ac. £8.00.

POWER SUPPLY, TWIN OUTPUT: Prim 240V ac. New, British manufacture, smoothed d.c. output 20V 1.5A plus stabilised output of 15V 100Ma, plus 12V ac 0.5A output, complete with diagram, £3.50.

EDGEWISE LEVEL METER FSD 200/µA
Size 19 x 18 x 20mm 800Ω £1.10.

CHARGING METERS 1 1/2 ins diameter
2A or 3A £1.25 each; 5A or 10A £1.50 each.

SYNCHRONOUS GEARED MOTORS, 240V ac.
Brand new, built in gear box, 1 or 20 RPH. £1.25 each.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS
P.P. sec tapped 3-8-15Ω, A-A 6K, 30W £15.25; A-A 3K, 50W £22.75; 100W (£1.21 KT95, each) £31.25.

E. E. C. MANUAL OF POWER AMPLIFIERS
Covers valve amplifiers 30W to 400W P.V.C. 00.

MULTIWAY SCREENED CABLE, PVC COVERED
36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; 4 way individually screened 25p per metre, fig 8 twin stereo do screened 15p, metre.

MAINS CABLE
4 way, 3A 30p metre; fig 8 for loudspeakers etc. £5.00 100 metres.

CONDENSERS
Electrolytic, 400/400V 75p; 2000/30V 30p; 1200/75 50p; 2200/40V 40p; 8-8/450V 40p; Paper tubular, W/E 4/160V, 6/160V, 2/160V, 0.1/2000V 25p each.

**CARRIAGE EXTRA ON ALL ORDERS
ALL PRICES INCLUDE V.A.T.**

Callers by appointment only. S.A.E. Enquiries, Lists.

**46, Kenilworth Road, Edgware, Middx.
HA8 8YG. Tel: 01-958 9314**

Sonic

HI-FI DISCOUNT CENTRES



DISCOUNT SPEAKERS

Imp 8 or 15 as app.
Guarantees:
**TITAN 5 years
FANE LIFETIME
OTHERS 1 year**
**ALL PRICES
INC. VAT**

Prices correct at 23.1.79

HI-FI TYPES

5" FANE 501 Mid or Full range	List/Value	Sonic Price
8" A.F. Model 80 Dual Cone	Sp. Price	£4.95
8" A.F. Model 83 Dual Cone	Sp. Price	£4.95
FANE 8" 80BT Dual Cone	Sp. Price	£6.95
WH/FEDALE L/TON 3xP Kit Pr.	Sp. Price	£3.95
DENTON 2xP KIT pair	£60.70	£36.95
GLENDALE 3xP KIT	£39.15	£21.95
A.F. FRI 8" SPKR KIT	£32.44	£19.95
8" FANE MODE ONE KIT	Sp. Price Pair	£14.95
10" ELAC Model 10RM 10-15w	Sp. Price Pair	£19.99
	Sp. Price	£2.50

CABINETS (TEAK VENEERED)

20" x 11 1/2" x 9 1/2" Suitable for Model 1 or FRI Kits and Models 80, 83 or 80BT Spkrs. Limited Number £6.95 ea.

GROUP/DISCO TYPES

12" TITAN T12/45R	£15.00	£12.95
12" TITAN T12/60R	£22.50	£14.80
12" TITAN T12/100A 100w	£36.00	£22.95
12" CELESTION G12M	£16.50	£11.95
12" CELESTION G12H 30w	£22.00	£14.95
12" CELESTION G12/50 50w	£22.75	£19.95
12" GOODMANS 12 PD	Sp. Price	£21.95
12" GOODMANS 12 PG	Sp. Price	£18.95
12" FANE 'SPECIALIST' P.A. 80	£29.95	£18.95
12" " " DISCO 80	£29.95	£19.95
12" " " DISCO 100	£31.95	£21.95
12" " " GUITAR 80L	£28.95	£18.95
12" " " GUITAR 100L	£31.95	£19.95
12" " " GUITAR 80B	£29.95	£19.95
12" FANE CRESCENDO 80	£44.95	£29.95
12" " " 80LT	£49.95	£34.95
12" " " 13A	£64.45	£41.95
12" " " 13L	£67.67	£39.95
12" " " 12 BASS	£63.95	£39.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£29.95
15" FANE 'SPECIALIST' BASS 85	£41.95	£29.95
15" " " BASS 100	£44.50	£31.95
15" GOODMANS 15P	Sp. Price	£23.95
15" FANE CRESCENDO/15	£82.66	£51.95
15" " " BASS	£8.95	£51.95
15" " " 15/100LT	£74.69	£51.95
15" " " 15/160 160w	£107.23	£72.95
15" " " COLOSSUS 200w	£121.31	£72.95
15" TITAN T15/100 100w	£31.00	£39.95
15" GOODMANS 15P	Sp. Price	£39.95
15" CELESTION G18C	£53.00	£41.95
15" FANE CRESCENDO 18A	£114.97	£72.95
15" " " BASS	£101.86	£59.95
15" " " COLOSSUS 200w	£129.81	£75.00

HORN UNITS

CELESTION MH1000 25w	(Carr. 85p)	£17.00	£13.75
FANE 910 MK II 50w		£17.75	£10.99
920 100w		£62.95	£44.50
J44 30-50w		£7.95	£4.95
J73 50w		£17.75	£7.95
J104 50-70w		£16.95	£10.95

HIGH POWER 'CROSS-OVERS'

FANE HPX1R or HPX2R Carr. 35p	£3.65	£2.25
-------------------------------	-------	-------

ADD-ON HIGH FREQUENCY UNITS

F.A.L. 'Add-on' Carr. £1	£41.95	£35.95
TITAN T1H 70w Carr. £1	£33.00	£23.95
TITAN TS2H 100w Carr. £1	£33.00	£23.95
TITAN T2H Carr. £1	£38.00	£26.95

SPECIAL OFFER! COLLARO RECORD DECKS

* 'S' Shaped Arm * Auto or Manual
* 12" Turntable * Ideal for Disco
£17.95 ea. or 2 for £30.
Carr. £1.50 ea


Also for personal shoppers only
**AMPS, TTABLES, JINGLE MACHINES,
DISCO CONSOLES, LIGHTING, CABINETS,
CREDIT TERMS AVAILABLE** orders £20 over

Phone orders accepted from Access & Barclay card holders.
**403 SAUCHIEHALL STREET
Tel: 041 332 0700
GLASGOW**

Mail Orders/Export enquiries to above. Add £1 carr. on Hi-Fi spkrs. or kits. Otherwise add £1.25 (12" Spkr). £1.50 (15") £2.50 (18")

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

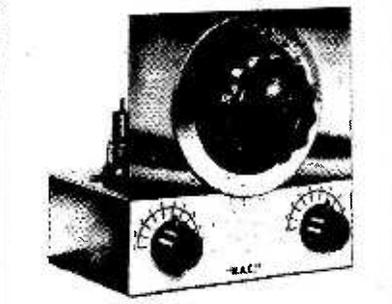

"H.A.C." well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories to suit the novice and the expert.
£10.50 INCLUSIVE—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.
NEW T TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £12.50 this receiver is outstanding value, and will give you hours of interest and entertainment.
Lastly the K and K plus (illustrated above) for the more advanced constructor. This receiver has recently been re-designed for even better reception. All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ

A. J. H. ELECTRONICS

(GBAGN)

Proprietor: A. J. HIBBERD
Tel. RUGBY daytime 76473, evening 71066

Terms of Business: Cash with order. Mail order only, or Callers by appointment. S.A.E. with enquiries. Handling Charge 40p. Minimum order £1.00. Official orders on a strict monthly basis. Prices now include VAT. FULL MONEY-BACK GUARANTEE ON ALL ITEMS.

STEREO CAR CASSETTE PLAYERS famous manufacturers warranty returns fully overhauled & in working order, output 5 watts per channel, controls—volume, balance, tone, fast forward & rewind, auto stop. Supplied less speakers & power lead, but we supply power plug & circuit. List over £50.00 our price ONLY £20.00. (negative earth only).

STEREO CAR CASSETTE PLAYER amplifier boards with two NIPON C1001H2 audio ICs 3 1/2 watts per channel, removed from new equipment by manufacturer size 120 x 45 mm supplied with circuit £2.50 each.

VARICAP FM TUNERS 88-108 MHz 10.7 MHz IF output contains 2 dual gate mosfets + 2 bipolar transistors small size 70 x 85 x 30 mm sorry no data, new unused £3.50.

MINIATURE NIXIE TUBE ITT 58535 side viewing with left & right hand decimal point character height 1 1/2 mm. 5 for £2.50, 10 for £4.50, 25 for £9.50 for £15.00, 100 for £25.00.

VIDEO CAMERA SCAN & FOCUS COILS transistor type for 1" vidicon tubes, no data new only £4.50.
MIXED BAG OF ELECTROLYTIC CAPACITORS 100 caps. of equal quantity of the following: 2.2/16v, 20/16v, 47/16v, 150/16v, 330/4v, 470/10v, 470/16v, 680/16v, price ONLY £1.50 per 100.

CAR RADIO RF/IF AMPLIFIER BOARD 470KHz IF amp plus mixer & stereo IC pre-amp ex-new car cassette/radios 80p inc. circuit.
CAR RADIO BOARD complete except for permeability tuner two types 7 or 8 transistor, output 5 watts M/LW only £1.00 or two for £1.75, 4 for £3.00 circuit supplied. Permeability tuner not correct one but should work OK 50p each (only supplied with above board).

COMPRESSION TRIMMER 9 x 14 mm PC type 10-80pf 8p each 10 for 60p.

MULLARD SEMI-AIRSPACED 7 mm 50p. TRIMMERS 1-5pf, 1-10pf, 1-15pf, 15p each. 10 mm dia. semi-airspaced 2-25pf 10p 10 for 40p, 4-60pf 15p each.

TETTER TRIMMER 1-10pf 9 mm dia. 25p each.
SLIDE SWITCH pre-set type 2pc. 10p each 10 for 50p.
512 BIT SHIF REGISTER IC, type MM5018B list over £3.00 our price only 60p 2 for £1.00 (not refect).


FERRITE CORES mixed bag of 100 50p.
DISC CERAMICS mixed bag of 100 values from 1pf to 220pf approx 18 values all made by ERIE largest size 1/2" dia. with long leads bargain e £1.50 per 100.

DOY BROKEN CAR RADIO BOARDS OK for spare parts of transistors, IFs, coils etc. approx 2 kilos in weight £2.50 + £1.00 post.
12v MOTORS as used in car cassette/cartridge players new 80p each.
AUDIO AMP ICs LM380 2 watt into 4 ohm, 80p each. ESM231 18 watts into 4 ohms 24 volt £1.80. TBA641A 2.4 watts into 4 ohms e 9 volts. £1.00, all with data.
IF AMP ICs CA3089E £2.00. TAD110 £1.50. T8A200A 80p.

**20 BARBY LANE, HILLMORTON, RUGBY,
WARWICKSHIRE CV22 50J**

Automatic Intercom

★ AS FEATURED IN
THIS ISSUE OF P.W.

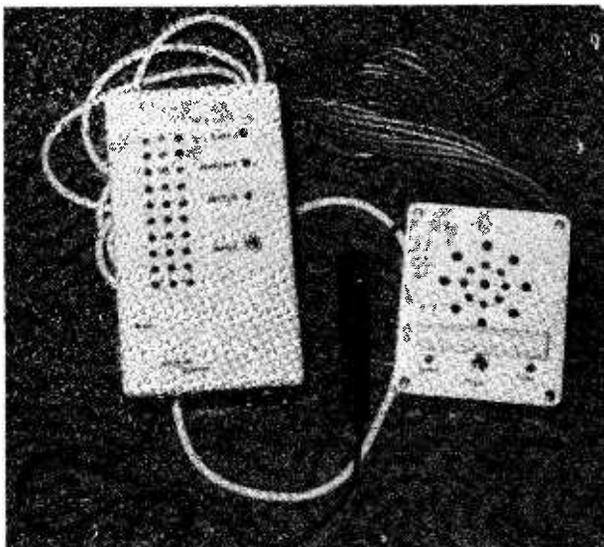

- INCREASE SECURITY!!
- ADD CONVENIENCE!!
- DETER UNWANTED CALLERS!!

We can supply a complete set of parts for this useful project — everything down to the last nut and bolt!! All parts as specified by the author, including PCB's and cases for **£29.95**, 4 core screened cable for interconnecting **27p/metre**.

THE NEW 1979 GREENWELD CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- PRICE 30p + 15p POST

Please adjust Prices to include VAT at NEW Rate.
(Not available at time of going to press)

All prices include VAT—Just add 25p post

GREENWELD

443B Millbrook Road Southampton SO1 0HX

Tel: (0703) 772501/783740

3W Amp Module

Ready built and tested, this handy amplifier will prove very useful around the workshop. Just requires 17V ac source (and 8R spkr) as bridge rect and smoothing cap are mounted on the PCB. The 4 transistor circuit provides enough sensitivity for most applications. Supplied complete with circuit diagram and wiring details. Only **£1.75**. Suitable transformer **£2.20**.

ENGINEERS

FREE

YOURSELF FOR A
BETTER JOB WITH **MORE PAY!**

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.



CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest.
Post to address below.

<input type="checkbox"/> ELECTRICAL & ELECTRONICS	<input type="checkbox"/> Radio, Servicing & Repairs	<input type="checkbox"/> Painting & Decorating
<input type="checkbox"/> Practical Radio & Electronics (with KIT)	<input type="checkbox"/> Radio Amateur's Exam.	MECHANICAL
<input type="checkbox"/> Electronic Engineering Certificate	AUTO & AERO	A.M.S.E. (Mech.) <input type="checkbox"/>
<input type="checkbox"/> General Elect. Eng. Certificate	<input type="checkbox"/> Motor Mechanics	General Mech. Eng. <input type="checkbox"/>
<input type="checkbox"/> C. & G. Elect. Installations	<input type="checkbox"/> C. & G. Motor V. Mechanics	Inst. Engineers & Technicians <input type="checkbox"/>
<input type="checkbox"/> Elect. Install. & Work	<input type="checkbox"/> General Auto Engineering	Maintenance Engineering <input type="checkbox"/>
<input type="checkbox"/> C. & G. Elect. Technicians	<input type="checkbox"/> A.M.I.M.I.	Welding <input type="checkbox"/>
	<input type="checkbox"/> Air Registration Board Certs.	MANAGEMENT & PRODUCTION
	<input type="checkbox"/> M.A.A./I.M.I. Dip.	Computer Programming <input type="checkbox"/>
<input type="checkbox"/> RADIO & TELECOMMUNICATIONS	CONSTRUCTIONAL	Inst. of Cost & Managements Accts. <input type="checkbox"/>
<input type="checkbox"/> Colour TV Servicing	Heating, Ventilating & Air Conditioning <input type="checkbox"/>	
<input type="checkbox"/> C. & G. Telecoms. Technician's Cert.	Architectural Draughtsmanship & Design <input type="checkbox"/>	DRAUGHTSMANSHIP & DESIGN
<input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert.	L.I.O.B. <input type="checkbox"/>	General Draughtsmanship <input type="checkbox"/>
<input type="checkbox"/> Radio & TV Engineering Course	<input type="checkbox"/> Carpentry & Joinery	A.M.I.E.D. <input type="checkbox"/>
	<input type="checkbox"/> Plumbing Technology	Electrical Draughtsmanship <input type="checkbox"/>
	<input type="checkbox"/> General Building	

POST NOW

G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College
Dept. TPW 24, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, London EC2Y 9DT. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

..... Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

SEMICONDUCTORS - COMPONENTS

CERAMIC PAK

Containing a range of first quality miniature ceramic capacitors
 16160 24 - 3 of each value - 22pf 27pf 33pf 39pf 47pf 68pf 82pf 87p
 16161 24 - 3 of each value - 100pf 120pf 150pf 180pf 220pf 270pf 330pf 390pf 470pf 560pf 680pf 820pf 1000pf 1500pf 2200pf 3300pf 4700pf 5600pf 6800pf 8200pf 01uf 015uf 022uf 033uf 047uf 87p

Type Price

AC107	£0.23
AC113	£0.22
AC115	£0.21
AC117	£0.21
AC117K	£0.21
AC121	£0.21
AC122	£0.18
AC125	£0.19
AC126	£0.19
AC127	£0.19
AC128	£0.17
AC128K	£0.28
AC132	£0.21
AC134	£0.21
AC137	£0.21
AC141	£0.23
AC141K	£0.32
AC142	£0.21
AC142K	£0.32
AC151	£0.21
AC153	£0.23
AC153K	£0.32
AC154	£0.21
AC155	£0.21
AC156	£0.21
AC157	£0.21
AC158	£0.21
AC166	£0.21
AC167	£0.21
AC168	£0.27
AC169	£0.21
AC171	£0.27
AC176	£0.19
AC176K	£0.28
AC178	£0.27
AC179	£0.27
AC180	£0.21
AC180K	£0.30
AC181	£0.21
AC181K	£0.30
AC187	£0.19
AC187K	£0.30
AC188	£0.19
AC188K	£0.30
AC197	£0.37
AC198	£0.37
AC199	£0.37
AC200	£0.37
AC201	£0.37
AC202	£0.37
AC203	£0.37
AC204	£0.37
AC205	£0.37
AC206	£0.37
AC207	£0.37
AC208	£0.37
AC209	£0.37
AC210	£0.37
AC211	£0.37
AC212	£0.37
AC213	£0.37
AC214	£0.37
AC215	£0.37
AC216	£0.37
AC217	£0.37
AC218	£0.37
AC219	£0.37
AC220	£0.37
AC221	£0.37
AC222	£0.37
AC223	£0.37
AC224	£0.37
AC225	£0.37
AC226	£0.37
AC227	£0.37
AC228	£0.37
AC229	£0.37
AC230	£0.37
AC231	£0.37
AC232	£0.37
AC233	£0.37
AC234	£0.37
AC235	£0.37
AC236	£0.37
AC237	£0.37
AC238	£0.37
AC239	£0.37
AC240	£0.37
AC241	£0.37
AC242	£0.37
AC243	£0.37
AC244	£0.37
AC245	£0.37
AC246	£0.37
AC247	£0.37
AC248	£0.37
AC249	£0.37
AC250	£0.37

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality mixed value miniature electrolytics.
 16201 Values from 47mFD - 10mFD 65p
 16202 Values from 10mFD - 100mFD 85p
 16203 Values from 100mFD - 680mFD 65p

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors assorted into the following groups.
 16213 80 mixed $\frac{1}{4}$ W 100 ohms - 820 ohms
 16214 60 mixed $\frac{1}{4}$ W 1K ohms - 82K ohms 67p
 16215 60 mixed $\frac{1}{4}$ W 10K ohms - 83K ohms 67p
 16216 60 mixed $\frac{1}{4}$ W 100K ohms - 820K ohms 67p
 16217 40 mixed $\frac{1}{4}$ W 100 ohms - 820 ohms 67p
 16218 40 mixed $\frac{1}{4}$ W 1K ohms - 82K ohms 67p
 16219 40 mixed $\frac{1}{4}$ W 10K ohms - 82K ohms 67p
 16220 40 mixed $\frac{1}{4}$ W 100K ohms - 820K ohms 67p
 16221 40 mixed $\frac{1}{4}$ W 1 Meg - 10 Meg ohms 67p
 16222 40 mixed $\frac{1}{4}$ W 1 Meg - 10 Meg ohms 67p

COMPONENT PAKS

16164 200 Resistor mixed value approx (Count by weight) 87p
 16165 150 Capacitors mixed value approx (Count by weight) 87p
 16166 50 Precision resistors. Mixed values 67p
 16167 80 $\frac{1}{4}$ W resistors mixed values 67p
 16168 5 Pieces assorted ferrite rods 67p
 16169 2 Turning gangs MW LW VHF 67p
 16170 1 Pak wire 50 metres assorted colours single strand 65p
 16171 10 Reed switches 67p
 16172 3 Micro switches 67p
 16173 15 Assorted pots 67p
 16174 5 Metal jack sockets 3 x 3.5 mm 2 x standard switch types 67p
 16175 30 Paper condensers - mixed values 67p
 16176 20 Electrolytics trans types 67p
 16177 1 Pak assorted hardware - Nuts, bolts, grommets etc 85p
 16178 5 Mains slide switches assorted 67p
 16179 20 Assorted tag strips and panels 85p
 16180 15 Assorted control knobs 67p
 16181 3 Rotary wave change switches 67p
 16182 2 Relays 5-24v operating 67p
 16183 1 Pak copper laminate approx 200 sq inches 65p
 16184 15 Assorted fuses 100 mA 5 amp 65p
 16185 50 Metres PVC sleeving assorted size and colours 65p

METAL FOIL CAPACITOR PAK

16204 Containing 50 metal foil capacitor like Mullard C280 series. Mixed values ranging from 01uf - 2.2uf. Complete with identification sheet. £1.35

SLIDER PAKS

16190 5 Slider potentiometers mixed values 67p
 16191 8 Slider potentiometers all 470 ohm 67p
 16192 6 Slider potentiometers all 10K ohm 67p
 16193 6 Slider potentiometers all 22K ohm 67p
 16194 6 Slider potentiometers all 47K ohm 67p
 16195 6 Slider potentiometers all 47K log 67p

TRANSISTORS

Brand New - Fully Guaranteed

Type Price

AD140	£0.84
AD145	£0.84
AD146	£0.81
AD149	£0.84
AD161	£0.37
AD162	£0.37
AD167/162	£0.75
AD170	£0.89
AD176	£0.89
AD178	£0.84
AD180	£0.84
AD181	£0.82
AD186	£0.54
AD187	£0.54
AD188	£0.54
AD189	£0.54
AD190	£0.54
AD191	£0.54
AD192	£0.54
AD193	£0.54
AD194	£0.54
AD195	£0.54
AD196	£0.54
AD197	£0.54
AD198	£0.54
AD199	£0.54
AD200	£0.54
AD201	£0.54
AD202	£0.54
AD203	£0.54
AD204	£0.54
AD205	£0.54
AD206	£0.54
AD207	£0.54
AD208	£0.54
AD209	£0.54
AD210	£0.54
AD211	£0.54
AD212	£0.54
AD213	£0.54
AD214	£0.54
AD215	£0.54
AD216	£0.54
AD217	£0.54
AD218	£0.54
AD219	£0.54
AD220	£0.54
AD221	£0.54
AD222	£0.54
AD223	£0.54
AD224	£0.54
AD225	£0.54
AD226	£0.54
AD227	£0.54
AD228	£0.54
AD229	£0.54
AD230	£0.54
AD231	£0.54
AD232	£0.54
AD233	£0.54
AD234	£0.54
AD235	£0.54
AD236	£0.54
AD237	£0.54
AD238	£0.54
AD239	£0.54
AD240	£0.54
AD241	£0.54
AD242	£0.54
AD243	£0.54
AD244	£0.54
AD245	£0.54
AD246	£0.54
AD247	£0.54
AD248	£0.54
AD249	£0.54
AD250	£0.54

Type Price

BC125	£0.19
BC126	£0.26
BC132	£0.20
BC134	£0.20
BC135	£0.17
BC136	£0.20
BC137	£0.20
BC139	£0.35
BC140	£0.32
BC141	£0.30
BC142	£0.24
BC143	£0.24
BC145	£0.52
BC147	£0.08
BC148	£0.08
BC149	£0.08
BC150	£0.23
BC151	£0.23
BC152	£0.23
BC153	£0.23
BC154	£0.23
BC155	£0.23
BC156	£0.23
BC157	£0.23
BC158	£0.23
BC159	£0.23
BC160	£0.28
BC161	£0.41
BC162	£0.14
BC163	£0.14
BC164	£0.14
BC165	£0.14
BC166	£0.14
BC167	£0.14
BC168	£0.14
BC169	£0.14
BC170	£0.10
BC171	£0.10
BC172	£0.10
BC173	£0.10
BC174	£0.10
BC175	£0.39
BC177	£0.17
BC178	£0.17
BC179	£0.17
BC180	£0.17
BC181	£0.17
BC182	£0.10
BC183	£0.10
BC184	£0.10
BC185	£0.10
BC186	£0.24
BC187	£0.24
BC188	£0.12
BC189	£0.12
BC190	£0.14
BC191	£0.14
BC192	£0.14
BC193	£0.14
BC194	£0.14
BC195	£0.14
BC196	£0.14
BC197	£0.14
BC198	£0.14
BC199	£0.14
BC200	£0.14
BC201	£0.14
BC202	£0.14
BC203	£0.14
BC204	£0.14
BC205	£0.14
BC206	£0.14
BC207	£0.14
BC208	£0.14
BC209	£0.14
BC210	£0.14
BC211	£0.14
BC212	£0.14
BC213	£0.14
BC214	£0.14
BC215	£0.14
BC216	£0.14
BC217	£0.14
BC218	£0.14
BC219	£0.14
BC220	£0.14
BC221	£0.14
BC222	£0.14
BC223	£0.14
BC224	£0.14
BC225	£0.14
BC226	£0.14
BC227	£0.14
BC228	£0.14
BC229	£0.14
BC230	£0.14
BC231	£0.14
BC232	£0.14
BC233	£0.14
BC234	£0.14
BC235	£0.14
BC236	£0.14
BC237	£0.14
BC238	£0.14
BC239	£0.14
BC240	£0.14
BC241	£0.14
BC242	£0.14
BC243	£0.14
BC244	£0.14
BC245	£0.14
BC246	£0.14
BC247	£0.14
BC248	£0.14
BC249	£0.14
BC250	£0.14

74 SERIES TTL IC'S

Type Price

7400	£0.10
7401	£0.12
7402	£0.12
7403	£0.12
7404	£0.12
7405	£0.12
7406	£0.24
7407	£0.24
7408	£0.14
7409	£0.14
7410	£0.12
7411	£0.18
7412	£0.16
7413	£0.26
7414	£0.54
7415	£0.43
7416	£0.43
7417	£0.25
7418	£0.25
7419	£0.25
7420	£0.12
7421	£0.22

Type Price

7422	£0.17
7423	£0.23
7424	£0.20
7425	£0.20
7426	£0.25
7427	£0.28
7428	£0.28
7429	£0.12
7430	£0.12
7431	£0.24
7432	£0.24
7433	£0.24
7434	£0.24
7435	£0.24
7436	£0.24
7437	£0.24
7438	£0.23
7439	£0.13
7440	£0.13
7441	£0.16
7442	£0.43
7443	£0.43
7444	£0.78
7445	£0.78
7446	£0.78
7447	£0.52

Type Price

7448	£0.60
7450	£0.12
7451	£0.20
7452	£0.12
7453	£0.12
7454	£0.12
7455	£0.12
7456	£0.12
7457	£0.12
7458	£0.12
7459	£0.12
7460	£0.12
7461	£0.12
7462	£0.12
7463	£0.12
7464	£0.12
7465	£0.12
7466	£0.12
7467	£0.12
7468	£0.12
7469	£0.12
7470	£0.12
7471	£0.12
7472	£0.12
7473	£0.12
7474	£0.12
7475	£0.12
7476	£0.12
7477	£0.12
7478	£0.12
7479	£0.12
7480	£0.12
7481	£0.12
7482	£0.12
7483	£0.12
7484	£0.12
7485	£0.12
7486	£0.12
7487	£0.12
7488	£0.12
7489	£0.12
7490	£0.12

Type Price

7489	£0.84
7490	£0.12
7491	£0.12
7492	£0.12
7493	£0.12
7494	£0.12
7495	£0.12
7496	£0.12
7497	£0.12
7498	£0.12
7499	£0.12
7500	£0.12
7501	£0.12
7502	£0.12
7503	£0.12
7504	£0.12
7505	£0.12
7506	£0.12
7507	£0.12
7508	£0.12
7509	£0.12
7510	£0.12

SEMICONDUCTORS POTS & IRONS


EXPERIMENTOR BREADBOARDS

FROM **CSC**
CONTINENTAL SPECIALS CORPORATION


No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


EXP.325. The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin IC's.
ONLY £1-60

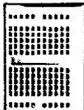


EXP.350. £3-50
270 contact points with two 20-point bus-bars.

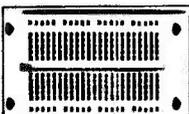

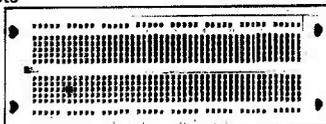EXP.300.
550 contacts with two 40-point bus-bars.
£5-75



EXP.650 for Micro-processors. **£3-60**

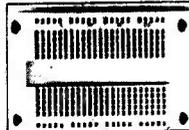

EXP.4B.
More bus-bars.
£2-30
All EXP.300 Breadboards mix and match with 600 series.



THYRISTORS

600ma	TO 18 Case	Price
10	THY600/10	£0-16
20	THY600/20	£0-17
30	THY600/30	£0-22
50	THY600/50	£0-24
100	THY600/100	£0-27
200	THY600/200	£0-41
400	THY600/400	£0-48

1 amp	TO 5 Case	Price
50	THY1A/50	£0-28
100	THY1A/100	£0-30
200	THY1A/200	£0-35
400	THY1A/400	£0-41
600	THY1A/600	£0-49
800	THY1A/800	£0-63

3 amp	TO 66 Case	Price
50	THY3A/50	£0-30
100	THY3A/100	£0-32
200	THY3A/200	£0-36
400	THY3A/400	£0-45
600	THY3A/600	£0-54
800	THY3A/800	£0-70

5 amp	TO 66 Case	Price
50	THY5A/50	£0-39
100	THY5A/100	£0-49
200	THY5A/200	£0-54
400	THY5A/400	£0-62
600	THY5A/600	£0-75
800	THY5A/800	£0-87

5 amp	TO 220 Case	Price
400	THY5A/400P	£0-81
600	THY5A/600P	£0-75
800	THY5A/800P	£0-87

7 amp	TO 48 Case	Price
50	THY7A/50	£0-52
100	THY7A/100	£0-55
200	THY7A/200	£0-62
400	THY7A/400	£0-67
600	THY7A/600	£0-84
800	THY7A/800	£0-99

10 amp	TO 48 Case	Price
50	THY10A/50	£0-55
100	THY10A/100	£0-62
200	THY10A/200	£0-67
400	THY10A/400	£0-77
600	THY10A/600	£1-07
800	THY10A/800	£1-32

16 amp	TO 48 Case	Price
50	THY16A/50	£0-58
100	THY16A/100	£0-63
200	THY16A/200	£0-67
400	THY16A/400	£0-83
600	THY16A/600	£0-97
800	THY16A/800	£1-50

30 amp	TO 94 Case	Price
50	THY30A/50	£1-27
100	THY30A/100	£1-54
200	THY30A/200	£1-76
400	THY30A/400	£1-93
600	THY30A/600	£3-78

No.	Price
BT101/500R	£0-86
BT102/500R	£0-86
BT106	£1-35
BT107	£1-00
BT108	£1-06
2N3228	£0-76
2N3535	£0-83
BTX30/50L	£0-36
BTX30/400L	£0-50
C106/4	£0-65

CARBON POTS (Linear Track)

Single gang with wire end terminations, 6mm x 50mm plastic shaft 10mm bushes supplied with shake proof washer and nut. Tolerance 20% of resistance.

1831 1k ohms	1837 100k ohms
1832 2k2 ohms	1838 220k ohms
1833 4k7 ohms	1839 470k ohms
1834 10k ohms	1840 1 Meg
1835 22k ohms	1841 2M2
1836 47k ohms	All at 29p each

CARBON POTS (Log Track)

1842 4k7 ohms	1847 220k ohms
1843 10k ohms	1848 470k ohms
1844 22k ohms	1849 1 Meg
1845 47k ohms	1850 2M2
1846 100k ohms	All at 29p each

Designed to fit 2.54mm pitch board. All tracks are linear law.

VC7	Price
1816 100 ohms	1824 47k ohms
1817 220 ohms	1825 100k ohms
1818 470 ohms	1826 220k ohms
1819 1k ohms	1827 470k ohms
1820 2k2 ohms	1828 1 Meg ohms
1821 4k7 ohms	1829 2M2 ohms
1822 10k ohms	1830 4M7 ohms
1823 22k ohms	All at 10p each

DUAL CARBON POTS (Log Law)

1860 4k7 ohms	1865 220k ohms
1861 10k ohms	1866 470k ohms
1862 22k ohms	1867 1 Meg
1863 47k ohms	1868 2M2
1864 100k ohms	All at 97p each

SINGLE GANG SWITCHED (Lin Law)

These potentiometers are fitted with double pole on-off switches. The switch is incorporated within the rotary action of the pot. Specification of pot is as VC1. Switch rating 1.5 amps at 250v AC.

1870 4k7 ohms	1875 220k ohms
1871 10k ohms	1876 470k ohms
1872 22k ohms	1877 1 Meg
1873 47k ohms	1878 2M2
1874 100k ohms	All at 73p each

DUAL GANG LOG-ANTI-LOG POT

1888 Track specification as dual gang pots VC3, but tracks mounted to log-anti-log action 100k ohms **£0-84**

POTENTIOMETERS

SPECIAL VOLUME CONTROLS

A miniature 16mm type replacement volume control incorporating single pole on-off switch. Resistance value 5k ohms. Tolerance ± 20% 1/8 watt rating.

1889 **£0-30** VC8

MINIATURE ROTARY VOLUME CONTROL

5k ohms log law with on-off switch 20mm grooved spindle. Tag connections 17mm dia. Supplied with fixing nut. Used mainly for replacement.

1890 **£0-61** VC9

WIRE WOUND POTS

A range of wire wound single gang pots with linear tracks of 1 watt rating, fitted with 10mm bush and supplied with shakeproof washer and nut.

1891 10 ohms	1896 470 ohms
1892 22 ohms	1897 1k ohms
1893 47 ohms	1898 2k2 ohms
1894 20 ohms	1899 4k7 ohms
1895 220 ohms	All at 90p each

SWITCHED POT (Log Track)

Specification as VC2 but track having (log) law.

1879 4k7 ohms	1884 220k ohms
1880 10k ohms	1885 470k ohms
1881 22k ohms	1886 1 Meg
1882 47k ohms	1887 2M2
1883 100k ohms	All at 73p each

PRE-SET POTS

Miniature type for transistor circuits. The wiper of the preset is provided with a slot for screw driver adjustment. The tags of the preset will fit printed wiring boards with a pitch of 2.54mm. All tracks are linear law.

1801 100 ohms	1809 47k ohms
1802 220 ohms	1810 100k ohms
1803 470 ohms	1811 220k ohms
1804 1k ohms	1812 470k ohms
1805 2k2 ohms	1813 1 M ohms
1806 4k7 ohms	1814 2M2 ohms
1807 10k ohms	1815 4M7 ohms
1808 22k ohms	All at 10p each

PRE-SET POTS

Miniature type for transistor circuits. Wiper adjustment is made by a screw driver slot.

VERTICAL MOUNTING

Miniature type for transistor circuits. Wiper adjustment is made by a screw driver slot.

SILICON RECTIFIERS

200mA	£0-07
IS920 50v	£0-07
IS921 100v	£0-08
IS922 150v	£0-09
IS923 200v	£0-10
IS924 300v	£0-11

1 Amp	Price
IN4001 50v	£0-05
IN4002 100v	£0-06
IN4003 200v	£0-07
IN4004 400v	£0-08
IN4005 600v	£0-09
IN4006 800v	£0-10
IN4007 1000v	£0-11

1.5 Amp	Price
ISO15 50v	£0-10
ISO16 100v	£0-11
ISO17 150v	£0-12
ISO18 200v	£0-13
ISO19 300v	£0-14
ISO20 400v	£0-15
ISO21 600v	£0-18
ISO22 800v	£0-22
ISO23 1000v	£0-27

3 Amp	Price
INS400 50v	£0-15
INS401 100v	£0-16
INS402 200v	£0-17
INS403 400v	£0-18
INS404 600v	£0-23
INS405 800v	£0-27
INS406 1000v	£0-32

10 Amp	Price
IS10/50 50v	£0-21
IS10/100 100v	£0-23
IS10/200 200v	£0-25
IS10/400 400v	£0-38
IS10/600 600v	£0-45
IS10/800 800v	£0-55
IS10/1000 1000v	£0-60
IS10/1200 1200v	£0-74

30 Amp	Price
IS30/50 50v	£0-60
IS30/100 100v	£0-74
IS30/200 200v	£1-00
IS30/400 400v	£1-35
IS30/600 600v	£1-90
IS30/800 800v	£2-09
IS30/1000 1000v	£2-49
IS30/1200 1200v	£3-11

70 Amp	Price
IS70/50 50v	£0-81
IS70/100 100v	£0-91
IS70/200 200v	£1-30
IS70/400 400v	£1-89
IS70/600 600v	£2-43
IS70/800 800v	£2-70
IS70/1000 1000v	£3-49
BYX38/300 6A 300v	£0-49
BYX38/600 6A 600v	£0-65
BYX38/300 Rev 6A 300v	£0-69
BYX38/600 Rev 6A 600v	£0-85

ANTEX IRONS

1943 15 watt high quality soldering iron totally enclosed element in a ceramic shaft fitted with 3/32" bit. **£4-10**

1947 Replacement element for 1943 iron. **£2-05**

1944 Iron coated bit 3/32" for 1943 iron. **£0-50**

1945 Iron coated bit 1/8" for 1943 iron. **£0-50**

1946 Iron coated bit 3/16" for 1943 iron. **£0-50**

1948 General purpose 18 watt iron fitted with iron coated bit. **£3-89**

1952 Replacement element for 1948 iron. **£2-05**

1949 Iron coated bit 3/32" for 1948 iron. **£0-50**

1950 Iron coated bit 1/8" for 1948 iron. **£0-50**

1951 Iron coated bit 3/16" for 1948 iron. **£0-50**

1931 Highly popular x25 25 watt quality soldering iron ceramic shafts to provide near perfect insulation break-

down voltage of 1500 volts AC and a leakage current of only 3-5uA and another shaft of stainless steel to ensure strength. **£3-89**

1935 Replacement element for 1931 iron. **£1-73**

1932 Iron coated bit 1/8" for 1931 iron. **£0-54**

1933 Iron coated bit 2/16" for 1931 iron. **£0-54**

1934 Iron coated bit 3/32" for 1931 iron. **£0-54**

1953 SK1 soldering kit - This kit contains 15 watt soldering iron fitted with a 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to solder'. In presentation display box. **£5-99**

1939 ST3 soldering iron stand. Stand made from high grade bakelite material, chromium plated strong steel spring, suitable for all models, includes accommodation for six spare bits and two sponges which serve to keep the soldering iron bits clean. **£1-62**

ZENER DIODES

400 mw (Bzy88) D007 Glass encapsulated range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

No. Z4 9p ea.


1w-1.5w Plastic and metal encapsulated. Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

No. Z13 16p ea.

10w Metal stud type S010 case. Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

No. Z10 38p ea.

PRINTED CIRCUIT BOARD TRANSFERS

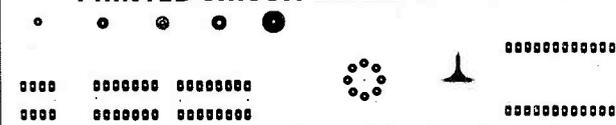


Draw your own boards with the new BI-Pak etch-resist transfers. Lay the symbols on the board, rub over with a soft pencil. The transfer will adhere to the board. Then complete the circuit with your BI-Pak etch-resist pen. Each pack contains 11 sheets of transfers, 1 of each as shown below. Illustrations approx 1/2 size.

Order No. TR400 £1-62 p&p 10

REGULATORS

Positive	£0-76
u.a. 7805 TO220	£0-76
u.a. 781	

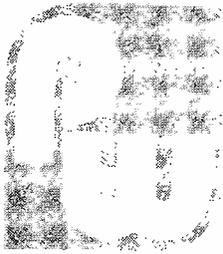

EDITOR

Geoffrey C. Arnold

ASSISTANT EDITOR

Dick Ganderton C. Eng., MIERE

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Peter Preston

NEWS & PRODUCTION EDITOR

Alan Martin

TECHNICAL SUB-EDITOR

Joe Bishop

TECHNICAL ARTIST

Rob Mackie

ASSISTANT ART EDITOR

Keith Woodruff

SECRETARIAL

Sylvia Barrett
Debbie Chapman

EDITORIAL OFFICES

Westover House,
West Quay Road,
POOLE, Dorset BH15 1JG
Telephone: Poole 71191

ADVERTISEMENT MANAGER

Telephone: 01-261 6636

Dennis Brough

CLASSIFIED ADVERTISEMENTS

Telephone: 01-261 5762

Colin R. Brown

MAKE UP & COPY DEPARTMENT

Telephone: 01-261 6570

Dave Kerindi

ADVERTISEMENT OFFICES

King's Reach Tower, Stamford St.,
London, SE1 9LS
TELEX: 915748 MAGDIV-G

Communications

OUR theme this month, communications, is a word with differing implications for different people. To a civil engineer, it means roads, railways, airports and docks. To a sociologist, it has to do with contact between individuals. In the field of radio and electronics, it means various ways of establishing that contact at a distance, traditionally by radio or wire, but also, more recently, by infra-red or by fibre-optic cable.

Whether "communications" can really be extended to cover contact between man and machine is arguable; perhaps it's a matter of scale. Where the machine in question is a computer operating in an interactive mode, such as that providing the Post Office Prestel service, it's difficult to call it anything else, though really, I suppose, the user is effectively communicating with the programmers who put the information into the computer originally. This month we have exercised literary licence to extend the use of the term to include "remote control" via ultrasonic links. It is, after all, simply a way of communicating your commands to a TV set, a garage door, or whatever.

Yet another variety of communication of great importance to us is that taking place between our contributors and editorial staff on the one hand, and the readers on the other, via the medium of the magazine. This is, of course, principally a one-way channel, though the feed-back which we get from you is very interesting to us, whether it's complimentary or otherwise!

We have recently been getting quite a few letters and telephone calls from readers having difficulty in getting their copies of *Practical Wireless* each month. First, let me say that we realise only too well the frustrations caused by the magazine being late on sale these past months. As I said a few issues back, I had hoped that we would have been appearing on the scheduled dates long before now, but no sooner do we get over one problem than another crops up. You may rest assured that we are not just sitting back, doing nothing about it—we are trying hard to get things to rights, and hope that the situation will soon improve.

To get back to the difficulty in finding a copy of *PW*, it does appear that there may be some problems in our distribution system, but it is impossible for us to investigate these without some detailed information, covering at least the following points:

1. Name and address of your newsagent or bookstall.
2. Do you have a regular order, or were you wanting to make a casual purchase?
3. When and where did you finally manage to purchase a copy of that particular issue?
4. Do you know of any other newsagents, etc., in the area, who get their copies of *Practical Wireless* earlier than your usual supplier?
5. Has your newsagent had difficulty in getting you a copy of *PW*, even if you place a firm order in advance?

If you are having these problems, I would be very grateful if you could spare the time to write and let us know, with any additional information which you feel might be useful. Please, won't you help us to help you?

Eric Dowdeswell—"On the Air" Contributor

Of "1918 vintage", Eric was introduced to the mysteries of radio at an early age by his father, and had become a licensed radio amateur by 1939. This, plus his work on mechanical TV projection systems, led him into war service in army wireless workshops around the Middle East, ending up in Istanbul.

There, he met and married a Greek girl, Christine, bringing her home when demob came in 1946. After a spell with Nagard, working on wideband amplifiers and oscilloscopes, Eric

decided to become a Flight Radio Officer, and spent 14 years with Sudan Airways in Khartoum. As ST2AR, he notched up over 200 certificates of achievement in working 273 countries on c.w. or s.s.b.

Returning to the UK in 1967, Eric became General Manager of the RSGB for a while, then joined the staff of *Practical Wireless*, remaining until the magazine moved to Poole in 1977, when domestic reasons forced him to stay in London.



Diary Date

The British Amateur Radio Teleprinter Group is holding its Annual Convention at the Harpenden Public Hall, Harpenden, Herts, on Saturday 21 July 1979, between 11.00 and 17.00hrs.

There will be trade stalls, bring and buy picture tape factory, demonstrations and lectures, including one by G3PLX, which is expected to attract particular attention.

The venue has been specially chosen for its ease of access from the motorway network and by rail, as well as for its car parking and refreshment facilities. Everyone, members and non-members of BARTG, is welcome.

Further details from: *J. P. G. Jones GW3IGG, Heywood, 40 Lower Quay Road, Hook, Haverfordwest, Dyfed SA62 4LR. Tel: Johnston (Dyfed) 890759.*

BAEC exhibition

The British Amateur Electronics Club will be holding their 14th Amateur Electronics Exhibition, in the Shelter at the centre of the Esplanade, Penarth, S. Glamorgan, between 21 and 28 July 1979. The exhibition will be open from 7.00pm each evening, except Sunday 22 July, and will also open during the afternoon on 21, 22 and 28 July.

The club will be displaying a large number of projects and electronic games built by members. All proceeds from the exhibition will be given to the Cancer Research Campaign.

Will members and prospective new members please note, the Hon Sec, John Margetts has moved from Bristol to Cheltenham. To contact, write to: *J. G. Margetts, Hon Sec, BAEC, 3 Bishopstone Close, Golden Valley, Cheltenham, Gloucester.*

RETRA is moving

RETRA, the Radio and Electrical and Television Retailers' Association moved to new offices in April.

From 23 April the Association's new address and telephone number will be: *RETRA House, 57-61 Newington Causeway, London SE1 6BZ. Tel: 01-403 1463.*

Practical Wireless, August 1979


Using your calculator

"Realisation of the educational potential of the electronic calculator has been surprisingly and disappointingly slow" according to the authors of a new paperback book published by Martin Books of Cambridge.

To help stimulate greater interest, electronics lecturer Robin Bradbeer, and maths teacher Michael Bawtree, have written "*The Sinclair Book of Students' Calculations*" for secondary education students and teachers to fully explain the application of calculators across a range of subjects.

The book's introduction gives valuable advice on how to choose between the many types of portable electronic calculator now available. This is followed by four chapters carefully graded in level from basic arithmetic and geometry to advanced problems in statistics, mechanics and higher mathematics. In each chapter the most effective use of the calculator is explained through informative examples.

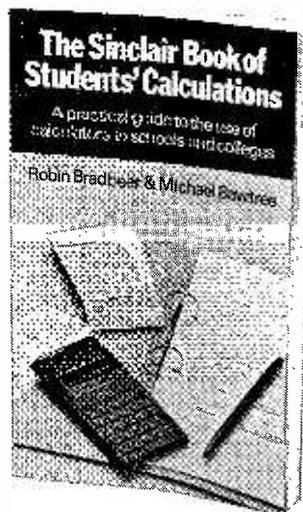The final chapter is an introduction to the exciting possibilities of the new generation of programmable calculators, based on the facilities of the new Enterprise programmable calculator from Sinclair, the British company which pioneered calculator miniaturisation in the early '70s.



The Sinclair Book of Students' Calculations is available from most branches of W. H. Smith, Boots, Foyles and leading bookshops throughout the UK, price £1.25, or direct from the publishers: *Martin Books, 8 Market Passage, Cambridge CB2 3PF, at £1.55 inclusive of postage and packing.*

Can you help?

The "Handicapped Aid Programme UK" is an organisation set up to help housebound handicapped people to enjoy the exciting hobby of Short-Wave listening.

The HAPUK would like to hear from anyone who could help, or perhaps has an old or redundant s.w. receiver (working or not) that they may like to give to the organisation, other spares are needed, such as, valves, headphones, variable capacitors, in fact any useful components.

I have two contacts with HAPUK, first the Chairman: *John Rose, 5 Hall Street, Wombwell, Barnsley S73 0JL, and the North Wales Area Representative: Les Crowther, 8 Plas Gwyn, Maes-y-Dre, Wrexham, Clwyd LL12 7DW. Tel: (0978) 262668.* Please help if you possibly can.

Sorry!

My apologies to Mr D. J. Pattle, whose address was printed incorrectly in Production Lines on page 51 of the April issue. The correct address is: *D. J. Pattle, Juniper, Hillbury Road, Alderholt, Fordingbridge, Hants. SP6 3BQ. Tel: Fordingbridge 52081.*

RAE courses

North Trafford College of Further Education, is offering another Radio Amateur's course this year, starting in September 1979.

Course ERA1 deals with RAE theory and will be held on Thursday evenings between 18.30 and 21.00hrs. Course ERA2 deals with the Morse code and will be held on Monday evenings between 18.30 and 21.00hrs and the lecturer will be J. T. Beaumont TEng., MITE, MASEE, G3NGD. Enrolment will be on 10, 11, and 12 September 1979, between 18.00 and 20.00hrs.

Further details from: *Course Co-ordinator, North Trafford College of Further Education, Talbot Road, Stretford, Manchester M32 0XH. Tel: 061-872 3731.*

Walsall Education Department is also offering an RAE evening course at: *The Broadway, North Centre, Queen Mary's Grammar School, Sutton Road, Walsall.*

For further details contact: *The Civic Centre. Tel: Walsall (0922) 21244 ext. 2319.*

Girls, Girls, Girls again

Following the introduction last year of the highly successful competition to find The Girl Technician Engineer of the Year, The Caroline Haslett Memorial Trust and The Institution of Electrical and Electronics Technician Engineers have decided to repeat the Award in 1979. This electrical and electronic engineering Award carries with it a prize of £250 and the closing date for nominations is 19 September 1979; the announcement of the winner will be made in November.

The engineering industry needs to attract more young people of the highest calibre and the aim to the Award is to focus attention on electrical and electronic engineering as a worthwhile career for women. By selecting the most outstanding girl Technician Engineer—who will have successfully undertaken the necessary technical

education and training, and have proved herself capable of holding a responsible job—it is the Award sponsors' express hope that she will, by her example, encourage more girls to enter the electrical and electronic engineering profession.

For further details and copies of the Award nomination form please apply to: *Mrs Eileen Sheldon, IETE, 2 Savoy Hill, London WC2R OBS. Tel: 01-836 3357.*

RAE Reprint

A reprint of the complete series—So You Want to Pass the RAE?—including details of the new examination format being introduced this year, is now available.

Order your copy by completing and returning the coupon on page 62.

Trio Technology

The new Trio TS 180S makes its debut—and what a beauty it is too. Covering the h.f. bands 160—10m this transceiver uses digital frequency control, designed around a dual-circuit phase-locked loop, comprising a 4-bit microcomputer and four memories, usable in transmit or receive modes.

Arrangements allow any of the memory frequencies to be tuned in 20Hz increments up or down, either step-by-step or by scanning, the original stored frequency being retained for instant recall. Its like having four v.f.o.s in addition to the "conventional" analogue v.f.o. with digital read-out. The memories permit split-frequency operation and three of the four provided can be retained by the use of battery back-up.

An innovative single-conversion p.i.l. system improves the spurious characteristics during transmission and reception, making i.f. shift and mono-dial

indication possible in any mode.

The dual i.f. filter, when inserted improves receiver S/N ratio and selectivity significantly increasing speech processor efficiency in the transmit (s.s.b.) mode.

Another interesting feature is the tunable noise-blanker. This detects signals mixed with 455kHz and the NB TUNE control selects the noise frequency.

The transmitter p.a. is, as you would expect, fully broadbanded and produces 200 watts p.e.p. output—160 watts c.w.—with a fractional reduction at 28MHz from the 13.8 volt supply.

We will be reviewing this transceiver in *PW* very shortly, so "watch this space".

For further information contact the importers, *Lowe Electronics, 119 Cavendish Road, Matlock, Derbyshire. Tel. (0629) 2430/2817.*

Free Brochures

The new, Erg six-page, four-colour d.i.l. switch brochure is now available.

It contains full technical specifications on all Erg d.i.l. switches and includes switching configuration diagrams for all types, plus prices.

Copies may be obtained from: *Erg Industrial Corporation Ltd., Luton Road, Dunstable, Beds LU5 4LJ. Tel: (0582) 622141.*

Winslow Component Systems Ltd. have recently produced a comprehensive brochure, describing all their accessories for use with the TO220 power semiconductor package.

Full details of over 30 products are given, including, dimensioned drawings, specifications and photographs. The products feature full fixing kits, insulating kits, heatsinks and sockets, in fact, almost every accessory the TO220 user is likely to need. Available from: *Winslow Component Systems Ltd., Southon House, Edenbridge, Kent. Tel: (0732) 864488.*

Special events

Yeovil Amateur Radio Club G3CMH, have arranged two special event stations to attend the following functions.

First, International Air Days, RNAS Yeovilton on Friday, 3 August and Saturday, 4 August 1979. Callsign GB3FAA applied for.


Second, Mid-Somerset Show at Shepton Mallet, on Saturday, 18 August and Sunday, 19 August 1979. Callsign GB2MSS applied for.

The club meets at 7.30pm every Thursday at Building 101, Houndstone Camp, Yeovil. For further information write to: *J. W. Howard G4EVI, 127 Goldcroft, Yeovil, Somerset BA21 4DD.*

Club News

Wisbech Radio Club would like to extend a welcome to anyone in the Wisbech Cambridgeshire area, whose interests include amateur radio. The club meets fortnightly at 19.30hrs and the next meetings will be on Monday 9 and 23 July 1979.

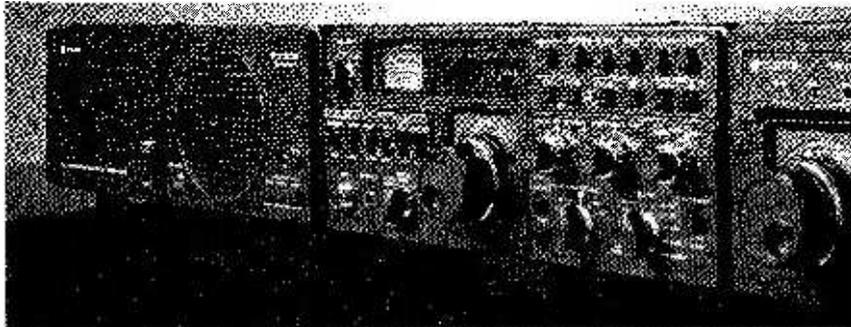Those interested may contact the Secretary, *D. Dunn G8RZN*, most evenings at the club's meeting place: *Five Bells, Parson Drove, Wisbech, Cambs.*



satellite communications

into the eighties

Earth Station Expansion and Development

The idea of using satellites for communications had its origins in an article by Arthur C. Clarke who, in 1945, foresaw the potential of satellites in providing worldwide television and speech communications. Since the very beginning, the British telecommunications industry and the British Post Office have been in the forefront of translating that idea into reality.

Today, a large proportion of the intercontinental telecommunications system involves the use of satellites positioned in geosynchronous orbit 36,000km above the Equator; in fact, a continental number dialled from the UK has about a 70% chance of being routed to its destination via satellite. It will be multiplexed with a very large number of similar calls and transmitted to the satellite on a microwave beam in the 6GHz band, the earthward path being in the 4GHz band. Submarine cables also support the system, of course, but cannot really offer the same traffic-handling capabilities, especially in respect of wide-band signals such as colour television, for instance.

Goonhilly


The British Post Office earth station at Goonhilly in Cornwall is well-known and has provided satellite links over the Atlantic and Indian Oceans for well over ten years. There are now four aerials at Goonhilly—Goonhilly 1, 2 and 3 operate to satellites poised over the Atlantic, where communications traffic between Europe and North America is far heavier than between other regions of the globe. Goonhilly 4 is currently being used for test transmissions to Europe's Orbital Test Satellite, OTS 2—forerunner to the European Communications Satellite, ECS. OTS 2 was launched on 11th May 1978 to prove the technology for digital satellite communications in the 11 and 14GHz frequency bands.

The aerials at Goonhilly are impressive structures indeed, reflector diameters in the case of Goonhilly 1, 2 and 3 being 25–30 metres or around 100ft. However, as the rapacious demands for international telecommunications facilities have been increasing so rapidly during recent years, a need for yet more aerials and associated ground terminal equipment has arisen. Also, as it seems that much of Europe's future telecomms. traffic is to be carried by the ECS, naturally the launch of this satellite will further increase this pressure. With this future expansion in mind, there are sites allocated for

another four aerials at Goonhilly. With ECS on the way, and the mighty Intelsat V series of satellites due for launch this year they, together with the new Madley earth station, will certainly be needed.

Goonhilly 4 and its associated equipment were formally handed over to the Post Office on September 5th, 1978. The prime contractor, Marconi Communication Systems Ltd., also equipped and commissioned Goonhilly 2 and 3 and remain the only British company to have supplied complete earth stations.

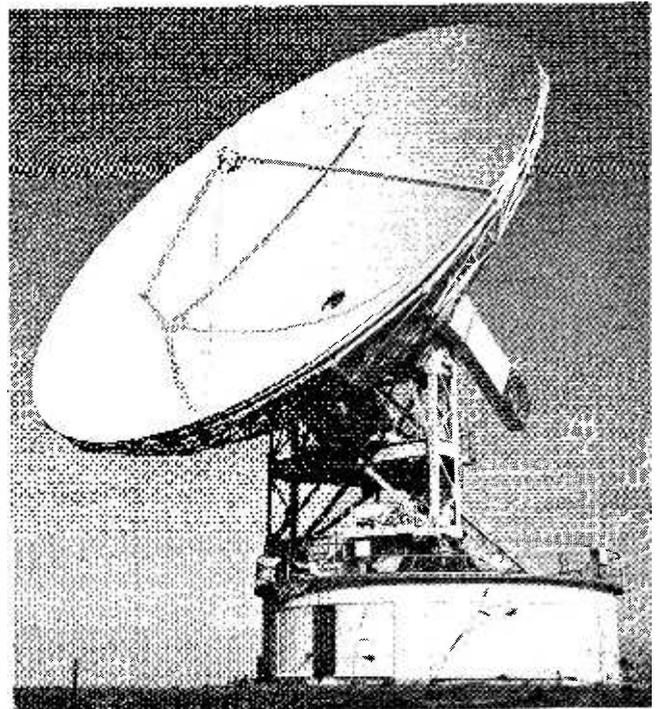The new aerial differs markedly from its older neighbours, principally in that it is smaller at 19 metres. Don't let that fool you into thinking that it is in any way inferior though; its propagation capabilities are just as formidable, but at far higher frequencies, receiving at 11GHz and transmitting at 14GHz. Dealing with such frequencies calls for mechanical accuracy of a very high



Goonhilly 4 (11/14GHz) is currently proving digital satcom. technology with the OTS2 satellite

order, as one might expect. The tolerance of the main reflector surface, for example, is 0.024 inches in a diameter of 62 feet! The aerial is cassegrain in type, the r.f. energy collected by the main reflector being focused not directly onto the "feedhorn" as in the conventional parabolic "dish", but onto a sub-reflector (a *pseudo-hyperboloid* for the geometrically-minded among you) which is supported from the main backing structure by a *tetrapod* (i.e. four legs). The signal is then reflected back along the aerial's axis, through a hole in the main reflector and thence to the waveguide system and down into the terminal equipment in the building below. The transmit signals follow the same route but in the reverse direction, naturally.

Like Goonhilly 3, the aerial is steered by a method known as the "monopulse tracking system". In fairly simple terms, guidance is achieved by sensing abnormal and undesired electromagnetic wave modes in the aerial-feed, which are extracted, analysed and then used to control the aerial's driving motors until a position is achieved at which the unwanted parameters are at a minimum—the aerial should then be pointed directly at the satellite. In the event of a failure of this system, or should the aerial be required to point at another satellite, manual or computer control of the aerial heading is also provided.


Madley

By 1970, it was clear that a second major earth station complex would be required in Britain. The growth of international communications of all types was, of course, a major factor in deciding to develop a second site—but just as important, perhaps, was the desire to avoid having all the eggs in one basket, particularly when they cost around £6m each! The requirement was for an electrically quiet area, free from radio interference and where the ground was capable of supporting aerials, buildings and ancillary plant (a single air-conditioning chiller compressor unit at Madley weighs around 40 tons, for example).

Eventually, it was a site at Madley, near the city of Hereford, that was selected as most closely matching the overall needs. Madley 1, which became operational at the end of 1978, now operates eastwards into the Indian Ocean Intelsat IVA satellite. This route was previously served by Goonhilly 1, which had been experiencing interference problems from French internal microwave systems and which, having been freed from this task by Madley 1, now assists with the busy Atlantic route. Calls to Africa, Australasia, the Middle East and the Indian sub-continent can all be routed via Madley.

The statistics of Madley 1 are impressive by any standards. The aerial itself, a 32 metre cassegrain type working in the 4/6GHz band, is somewhat larger than those at Goonhilly; but it is the sheer quantity of equipment that makes Madley 1 one of the largest earth stations in the Intelsat system. There are 14 chains of transmitting equipment producing up to seven microwave carrier signals with a standby facility on each, 10 air-cooled klystron power amplifiers with provision for another three to be installed later if required and, in all, 55 chains of receiving equipment—Madley 1 thus has the capability of simultaneous communication with around 40 countries.

The transmitters employed at Madley are of a new design using a 3kW klystron output stage. As the klystron is an essentially narrow-band device only one carrier can be handled by each one. Therefore, at Madley, the transmitter outputs are merged in a combining and selection matrix before being fed on up to the aerial. The use of single carrier klystron amplifiers (also used in Goonhilly 4's 14GHz transmitters, rated at 2kW) is a significant departure from the technology used in Goonhilly 1, 2 and

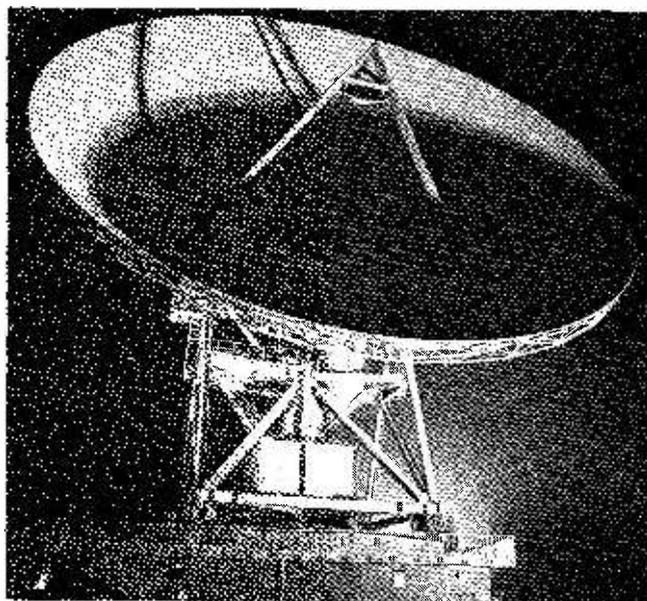

Madley 1 (4/6GHz) handles traffic via the Indian Ocean satellite

3 which use a single 10kW travelling-wave tube (t.w.t.) output stage. Being a wide-band device, several carriers previously combined at low power, can be amplified simultaneously.

Another important new feature of Madley 1, is the recently-developed "beam waveguide" aerial feed system, also used in Goonhilly 4. This is an arrangement of reflecting surfaces, somewhat in the form of a periscope, which interconnect the main reflector aperture and the equipment at ground level. Three concave surfaces and one plane surface are used; the idea is for polarisation errors occurring at one reflector surface to be cancelled out by errors of opposite characteristics at another. Signal losses are thus kept to a minimum and it becomes possible to locate all the radio equipment at ground level. The aerial itself can be lighter and less bulky while maintenance is, of course, much easier.

Aerial steering is by two systems, the previously described "monopulse" system and also by the "step-track" system. With the 'step-track' system, the 290 ton aerial makes small predetermined movements while the signal power received from the satellite is monitored. The aerial will continue to "step" in elevation and azimuth until the received signal is at a maximum. As it was uncertain whether the "step-track" method would be effective for small angles of elevation (6° in the case of Madley 1 working into the Indian Ocean satellite), it was decided to incorporate both systems into the new station.

The Future

The prospect, then, is one of continuing and rapid expansion. The Intelsat V series of satellites, to be launched this year, will double the system channel capacity to the equivalent of 12,000; the ECS will give Europe its own satellite system; a new global maritime satellite communications system is also on the way. The Space Shuttle will, in due course, make the launching and *servicing* of communication satellites that much easier and cheaper. Small wonder that Madley 2 is under way and due for completion this year, to be closely followed by Madley 3 at the end of 1980.

With satellite communications, the sky is apparently the only limit! ●

C.T. ELECTRONICS (ACTON) LTD.

Registered in England 1179820

267 & 270 ACTON LANE, LONDON W4 5DG. Telephone: 01-994 6275

9.30am-6.00pm
MON-SAT
CONTINUOUS

CMOS

4000UB	0.17	40278	0.44	40758	0.20
4001UB/B	0.17	40288	0.77	40768	1.17
4002UB/B	0.17	40298	1.03	40778	0.39
4006B	1.04	40328	0.89	40788	0.20
4007UB	0.18	40348	1.71	40818	0.20
4008B	0.87	40408	0.97	40828	0.20
4011UB/B	0.18	40438	0.88	40838	0.20
4013UB/B	0.43	40448	0.84	40838	0.80
4014B	0.83	4049UB	0.50	401618	1.19
4015B	0.83	4050B	0.43	401628	1.19
4016B	0.48	4051B	0.82	401638	1.19
4017B	0.79	4052B	0.82	401748	0.85
4018B	0.83	4053B	0.82	401758	0.86
4019B	0.83	4056B	0.55	401948	1.19
4020B	1.11	4066B	0.20	4510B	1.01
4021B	0.90	4069UB	0.20	4511B	1.25
4022B	0.82	4070B	0.46	4512B	0.91
4023UB/B	0.18	4071B	0.20	4516B	1.01
4024B	0.70	4072B	0.20	4518B	0.97
4025UB/B	0.20	4073B	0.20	4528B	0.80

TTL

7400	0.12	7451	0.20	74141	0.75
7401	0.12	7453	0.20	74150	1.00
7402	0.12	7454	0.20	74151	0.70
7403	0.12	7456	0.20	74153	0.70
7404	0.12	7470	0.20	74154	1.00
7405	0.16	7472	0.30	74155	0.70
7406	0.32	7473	0.30	74156	0.85
7407	0.32	7474	0.30	74157	0.75
7408	0.20	7475	0.45	74160	0.95
7409	0.20	7476	0.35	74161	0.50
7412	0.20	7480	0.50	74162	1.00
7413	0.30	7481	1.00	74163	1.00
7414	0.70	7482	0.90	74164	1.00
7415	0.30	7483	0.80	74165	1.00
7417	0.30	7484	1.10	74166	1.00
7419	0.50	7485	0.90	74167	2.50
7420	0.18	7486	0.30	74170	2.00
7421	0.20	7489	1.60	74174	0.95
7422	0.35	7490	0.35	74175	0.80
7423	0.32	7491	0.50	74176	0.80
7425	0.30	7492	0.45	74177	0.80
7426	0.30	7493	0.40	74180	0.80
7427	0.30	7494	0.90	74181	1.85
7428	0.40	7495	0.65	74182	0.95
7430	0.18	7496	0.65	74184	1.50
7432	0.26	7497	1.90	74185	1.50
7433	0.50	74100	1.40	74188	2.50
7437	0.50	74104	0.70	74190	1.00
7438	0.30	74105	1.70	74191	1.00
7440	0.18	74107	0.30	74192	1.00
7441	0.70	74109	0.55	74193	1.00
7442	1.50	74110	0.55	74194	1.00
7443	0.30	74118	0.95	74195	0.95
7445	1.00	74119	1.30	74196	0.95
7446	1.00	74121	0.28	74197	0.80
7447	0.75	74122	0.55	74198	1.60
7448	0.75	74123	0.55	74100	1.60
7449	1.00	74125	0.50		
7450	0.20	74132	0.70		

6" IMHOFF 19" Racks. Brand new. **£25.00 each** +8% VAT.

ALUMINIUM BOXES

Ins L	W	H	Retail price +8% VAT
AB7 [5 1/4]	2 1/2	1 1/2	0.70
AB8 [4]	4	1 1/2	0.70
AB9 [4]	2 1/2	1 1/2	0.70
AB10 [4]	5 1/4	1 1/2	0.70
AB11 [4]	2 1/2	2	0.85
AB12 [6]	2	1	0.70
AB13 [6]	4	2	1.00
AB14 [7]	5	2 1/2	1.20
AB15 [8]	6	3	1.55
AB16 [10]	7	3	1.75
AB17 [10]	4 1/2	3	1.45
AB18 [12]	5	3	1.75
AB19 [12]	8	3	2.40

SPECIAL OFFER
741 **15p**
8 pin D.I.L.

VEROBOARDS

0.15" Pitch Copper Clad	
2.5" x 5"	0.59
2.5" x 3.75"	0.50
3.75" x 5"	0.66
3.75" x 3.75"	0.59
3.75" x 17"	2.28
4.7" x 17.9"	2.99
2.5" x 1" (Sold in 5s)	0.70
0.15" Pitch Plain Board	
3.75" x 17.9"	1.49
3.75" x 2.5"	0.36
3.75" x 5"	0.56
0.15" Pitch Copper Clad	
2.5" x 5"	0.53
2.5" x 3.75"	0.44
3.75" x 17"	1.98
3.75" x 5"	0.74
0.15" Pitch Plain Board	
5" x 3.75"	0.47
2.5" x 5"	0.30
New V-Q DIP Board	1.11

Vero 19" sub rack units
1) Large DL27696, will accept card size 203(L) x (190-230)mm **£10** +8% VAT
2) Small 12401/C351 AIB will accept card size 203 x (95-115)mm **£6.00** +8% VAT

TRANSFORMERS, all 240V primary

6-0-6 500mA (63x35x48)	£1.40
0-11, 2A; 0-22, 1A (76x64x60)	£2.40
12V 130mA (36x45x40)	£0.75
17V 300mA (44x47x74)	£1.50
18V 2A (80x55x70)	£2.80
18V 2.5A (115x65x62)	£2.50
28V 200mA (53x45x37)	£1.00
32V 250mA (46x37x31)	£1.20
0-2-4-6-8-10-12, 0-1-1, 5A	£6.00

AUTO TRANSFORMERS

0-110-115-120-230-240-250V 150VA	£1.50
0-110-115-230-250V 2KW	£20.00

MAINS FILTERS

Potter 30A, 125V (184x51x70). Sealed	£3.00
Erie 8A, 250V (61x120x47). Diecast box	£5.00
Primar CRT M17/15GV, with scan coils and Wallis power supply. Rectangular screen (96x130)	£20.00

CINCH BARRIER STRIPS

5A 8-way (57x6)	£0.16
10A 6-way (66x8)	£0.24
10A 10-way (105x8)	£0.40
10A 12-way (124x8)	£0.48

CAM TIMERS by General Time

0-4.5min. with 22A 150VAC ms (70x70x60)	£4.00
0-60sec. with 10A 250VAC ms (84x84 fascia)	£4.00
1-17sec. with 10A 250VAC ms (80x80x50)	£4.00

LARGE PANEL METERS (Clear view)

SI fam 140-0-140microAmp (107x145). Calibrated 0-14 and 7-0-7. Boxed	£5.00
Anders 1mA f.s.d. (145x115). Calibrated 0-15KV, boxed	£5.00

We have at time of press over 2 million Electrolos & Welwyn Metal Oxide Resistors well below manufacturer's price. Phone for details.

This advertisement is a fraction of stock held by us. Phone for details:

No mail order accepted unless over £5.00. Hours of business 9.30am-6pm. Mon-Sat continuous. Carriage & packing charge extra. Government, colleges and export welcome.

We have considerable stock of PT10 & PT15 Presets. Special price for PT15 of the following value: 100Ω, 1k5, 2k2, 4k7, 10k, 22k, 47k, 100k. All the above values @£25/1.000. @12½% VAT. Retail prices all values 10p either PT10 size or PT15. Open or enclosed.

2200µF 100V computer grade electrolytic Mullard **£1.00** +VAT. 12½%.

PL259 Plugs with Reducers **50p each** retail. SO239 to suit Plug (259) Bulkhead Socket **45p each** +8% VAT.

BNC Plugs. Brand new. **30p** +8% VAT. Either 50Ω or 75Ω.

N Connectors available at a fraction of list price. Phone for details.

Seaelectro Plugs (miniature) Conhex for VHF & UHF applications

75p straight entry type 51-130-3187-91. **90p** right-angled gold plated type 055-014-3196.

All the above RF Connectors are held in depth and are brand new.

Cassette Monotape Heads ¼" **£1.00 each**. Brand new.

Cassette Erase Tape Heads ¼" **£1.00 each**. Brand new. +12½% VAT.

Potentiometers W. Wound 10-100v by A. B. or Colvern Ltd. ½ watt **40p**, 3 watt **60p**, 5 watt **80p**.

ROTARY SWITCHES available in 30 different types. Prices range from **45p-£1.20** +8%.

PREH Television Push-button Tuner Units. 4 and 6 button, brand new in original boxes. **75p each** +12½% VAT. Large quantity available.

SPECIAL OFFER 100k LIN Mono Slider Potentiometer by Noble (metal body) 63mm length, price **20p each** +12½% VAT. All boxed as original. **Discount on quantity.**

EDGE CONNECTORS

Single sided 0.1 pitch:	
24-way (fixing holes 73mm)—UCL	£0.70
40-way (fixing holes 118mm)—RS	£1.20
78-way (length 204mm)—UECL	£1.50
Single sided 0.15 pitch:	
15-way (fixing holes 73mm). Gold plated. EB	£0.60
18-way (fixing holes 85mm) inc. locating pin	£0.75
32-way (fixing holes 136mm). Gold plated. EB	£1.50
27-way (fixing holes 122mm)	£1.30

Double sided 0.1 pitch.
2 x 40-way (fixing holes 117mm). Gold plated **£2.00**
Double sided 0.15 pitch:
2 x 40-way (fixing holes 165mm). Gold plated **£2.00**

PUSHBUTTON SWITCHES by A.B. Electronics

4-way 2PCO. **£0.50**, 7-way, 5x2PCO, 2x4PCO **£0.80**

ILLUMINATED SWITCHES by Licon

Rectangular snap in (01-800 series). 10A contacts. Min. flange bulb holders
2PCO Latching **£1.50** SPCO Momentary **£1.00**
2PCO Momentary **£1.50** Indicator only **£0.50**
Price includes lenses but not bulbs.
Red, yellow, blue, green and white lenses available

KEYSWITCHES — HEAVY DUTY by Kraus & Naimer

2P (1PM-1PB) 12A 600VAC **£1.50** 49mm square
10P (4PM-6PB) 12A 600VAC **£3.00** fascia
By Baco:
8P (4PM-4PB) 10A 380VAC **£3.00**

LEVER SWITCHES GPO BP1000 Type

4PCO, 8PCO with knobs **£0.60**
All the above at 8% VAT

SPECIAL OFFER 2k 2 LIN single gang Potentiometer by Egen. ¼" shaft. ¾" bush plastic spindle. **Price 10p each** +12½% VAT. **Discount on quantity.**

Miniature Moulded Track Presets by Plessey Screwdriver operation. 0.25W dissipation PCB fixing. **15p each** +8%

Open Contact Presets. Most values in stock **15p each** +8% VAT.

Trimpots 100-500kΩ 10 turn and 20 turn **50p each** +8% VAT. By MEC, Paington. Bournes Mini Square, ¾" rectangular or 1½" rectangular German or W Wound.

Convergence Pots. Most television values **20p each** +12½% VAT.

A COMPLETE RANGE OF TRANSISTORS STOCKED

MOTORS (+8% VAT)

PAPST Motor HSZ 20-25-2-425 EEM. 42V 50C/S 10µf cap across size: < 6cm Diam 3.4cm. Shaft < 1.7cm Diam 4mm **£1.00 each**.

Smiths Motor 240V 50 C/S 3-hole fixing. Spaced 4.75cm 3rpm. Shaft 1.5cm 3mm diam. **£1.50 each**.

Cassette-deck Motor by Fujiya. 6V DC. < 3.25cm. Diam. 3.5cm. Shaft diam 2mm < 9mm. 3-hole fixing 4cm to centres. **£1.25 each**.

General Time Motors with clutch. 240V 1/5rpm. 2-hole fixing. 4.75cm, 3cm depth. Body diam 4.85cm. Shaft length 1cm, diam. 3mm. **£1.50 each**.

Crouzet Motors. Speeds 6rpm and 10rpm 2-hole fixing. 4.75cm, 3.9cm depth. Body diam. 4.5cm. Shaft < 0.9cm. Diam. 4mm. **£1.50 each**.

Miniature DC Motor 4-15v operation. High torque < 3.5cm. Body diam. 2cm. 2-hole front fixing, shaft diam 1.75mm. **£1.00 each**.

Plus large stocks General Time Motors in the following speeds: 1/180, 1/2 rph 12V DC, 1/5rpm 240V; 1rpm 240V.

Miniature Motor Clutches by General Time (USA) 24V operation. Body diam. 2.2cm. 6mm shaft centre **£1.30 each**.

Minimum £5.00 per order + Postage & VAT. Phone or write for Postage details. VAT at rate set on 12/7/79.

AERIAL DESIGN

using scale models

Fred JUDD G2BCX

Much of the initial development work on the "Slim Jim" and ZL series of 2 metre aerials recently described in *PW* (May 1977, April 1978, November 1978) was carried out with the aid of a u.h.f. scale-model aerial performance testing system. This was dealt with in *PW* in January 1978, but has since been much modified with the addition of a visual polar pattern display derived from a surplus 10in radar PPI unit as shown in Fig. 1. Because the above issue of *PW* is now out of print I will again, but briefly, deal with the method of employing ultra high frequency scale models as an aid to the design of aerials as well as performance measurement.

Similar aerials behave in exactly the same way, i.e., they will have the same gain and radiation pattern etc. whether operating at h.f. or u.h.f., so it is possible, for example, to scale down a typical beam aerial intended for operation at, say 28MHz to a small but easily handled model operated at around 500 to 700MHz. At frequencies much higher than this, matching the aerial to a feed cable and the transmitter becomes difficult.

Accurate matching is very important if gain is to be measured but is of little consequence if only radiation patterns are to be demonstrated. A mismatch between feed cable and aerial will not normally affect the radiation pattern, although wrong phasing between coupled radiating elements, such as in colinear arrays, will cause severe pattern distortion.

Transmitter

The first requirement is a "transmitter" which may in fact be a simple self-excited oscillator capable of delivering a few watts of power. Frequency stability is not greatly important as the model aerial to be tested is operated in "receive" mode, and the receiver itself need only be a tuned circuit with a diode rectifier, so as to obtain a rectified (d.c.) signal from the aerial. The distance between the transmitting aerial and the aerial being tested should not be less than about 10 wavelengths at the frequency used, e.g. at 600 MHz this would be about 5 metres (50cm per wavelength).

A circuit of a typical quarter-wavelength line oscillator suitable for a transmitter is shown in Fig. 2. The valve (V) may be any u.h.f. triode with appropriate power rating (on average the r.f. power output will be about 30 to 40 per cent of the d.c. power input). Tone modulation can be obtained by feeding an audio signal of a few volts to the grid via the 100kΩ resistor as shown, although this is only necessary if the model aerial system is to be used for demonstration so that signal variation can be made audible. The transmitting aerial may be a dipole but it is better with a plane reflector as shown in Fig. 3, which will increase the radiated power and confine it to one direction.

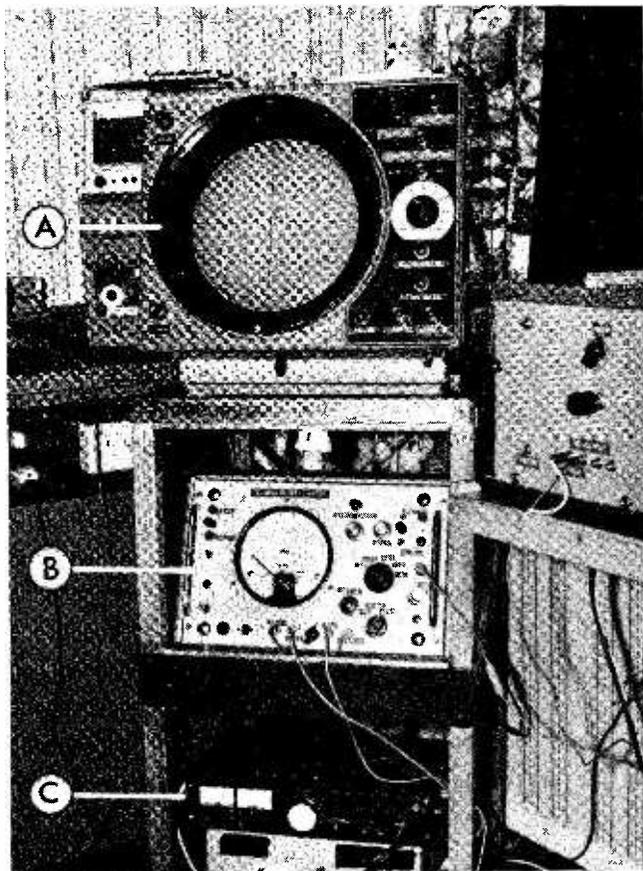


Fig. 1: The author's aerial test console, showing: (A) The PPI (polar pattern indicator) display (B) The linear reading decibel meter (C) Magnetic tape recorder. See text

Polar Pattern Indicator

It so happens that "PPI" stands equally for polar pattern indicator or for its original designation in radar, namely, plan position indicator. The display shown at (A) in the photograph Fig. 1 is in fact a converted marine radar unit. Rebuilt might be a better word, as all the original electronics was stripped out and replaced by solid-state circuitry to provide the special facilities required, as illustrated in the block diagram Fig. 4. The display c.r.t. is 10 inches in diameter and the tube is a long-persistence

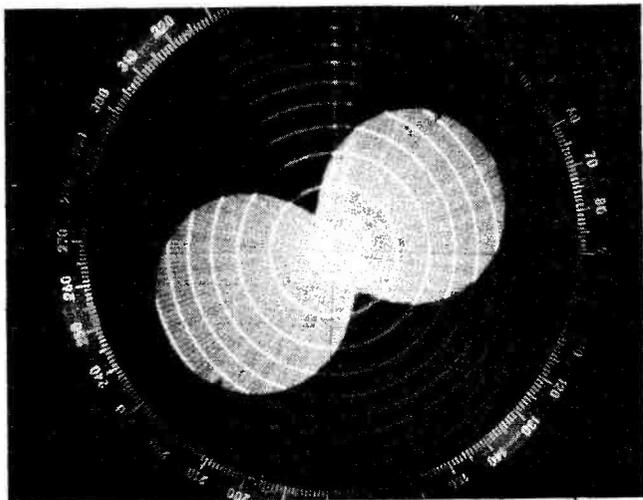


Fig. 6: Electronically generated reference dipole pattern with superimposed amplitude calibration markers

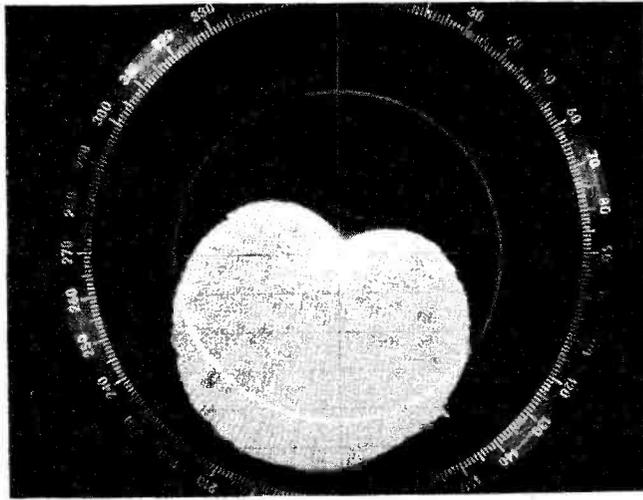


Fig. 8: Radiation pattern (cardioid) of a two-element ZL beam in vertical mode, with 3dB marker ring

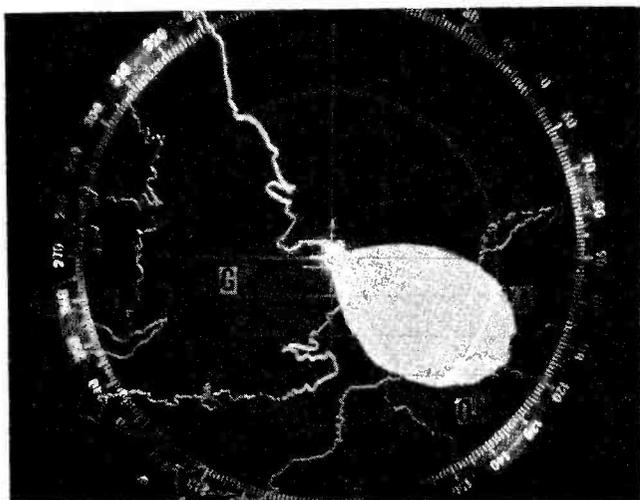


Fig. 7: Polar pattern of a two-element ZL beam in horizontal mode with map overlay. Display centre is based on the writer's QTH in Norfolk

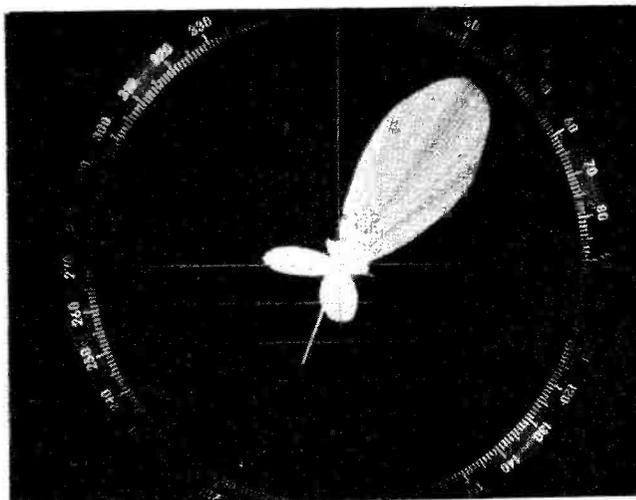


Fig. 9: Pattern from an experimental high-gain beam aerial, which shows that side lobes are too large and therefore the design is not acceptable

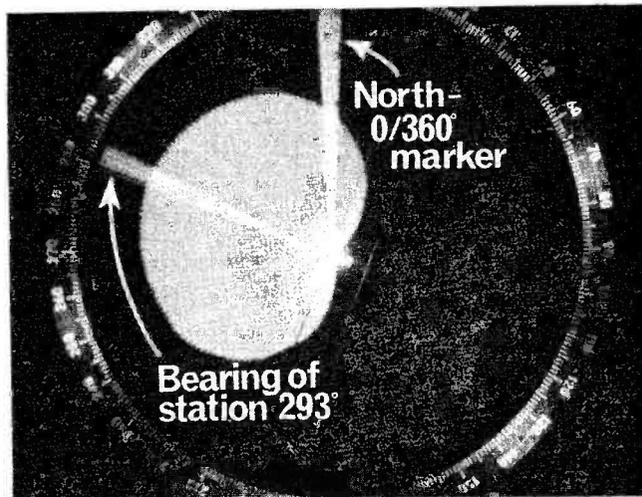


Fig. 10: The PPI display can be used for v.h.f. direction finding in conjunction with a continuously rotating aerial. See text regarding bearing markers


continued on page 33

SPECIAL PRODUCT REPORT



3106C

10 MHz OSCILLOSCOPE RADAT INDUSTRIES

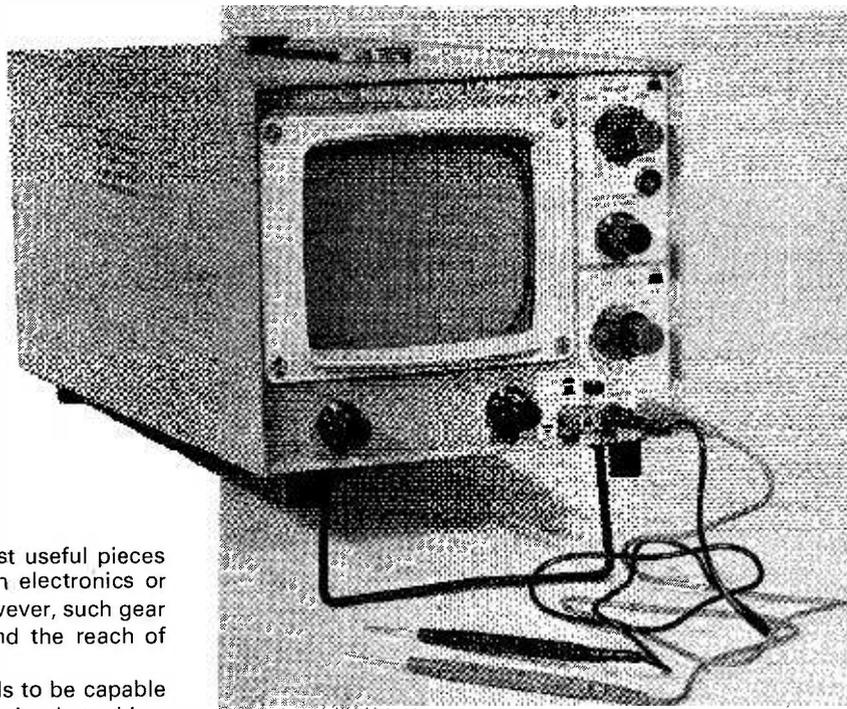

The oscilloscope is probably one of the most useful pieces of equipment anyone seriously interested in electronics or radio can possess. For most enthusiasts, however, such gear is out of the question as the cost is beyond the reach of most budgets.

For a scope to be of any great use it needs to be capable of looking at signals of 10MHz and, although simple to drive, should offer useful trigger facilities and a wide input range.

Above all the price should be low enough to put the instrument within reach of all but the most impoverished amateur.

The Radat 3106C almost fulfills these criteria except for price. It is a single beam unit with a frequency response of d.c. to 10MHz (6dB) and an input voltage range of 400V.

The display is a flat 8 x 10cm c.r.t. with a graticule ruled at 1cm divisions and rise-time reference lines at 10 and 90 per cent provided. The trace can be rotated to align with the horizontal axis using a preset control mounted on the rear panel. On the instrument tested this control proved adequate and simple to use.

Controls were the barest minimum, a timebase switch, vernier control for the timebase, horizontal trace position and x5 magnification switch are all that are provided for the timebase. No controls are provided for triggering which is fully automatic. The trigger worked without any problems during the test period and was adequate for simple repetitive waveforms. For looking at more complex waveforms and pulses and edges an independent trigger control would be useful to allow one to look at any part of the waveform, especially with the trace expanded.

The X amplifier controls again are of the simplest, a concentric switched attenuator with the vertical trace position controlled by the centre knob. The attenuator gives X sensitivities ranging from 10mV per cm to 50V per cm in 12 calibrated steps. A push-button selects a.c. or d.c. coupling of the input.

Intensity and focus complete the front panel controls with the mains on-off switch operated by the intensity switch.


In use the instrument was simple to use, the trace locking well with inputs over 1cm deflection on the screen. The trace free-runs when no input is applied or the repetition rate is below 5Hz. The trace was bright enough at all sweep speeds.

★ Specification

Display: 8 x 10cm with 1cm graticule squares
Tube: 130BE/P31
EHT: 1.6kV
VERTICAL AMPLIFIER
Sensitivity: 10mV/cm to 50mV/cm in 12 steps
Bandwidth: DC to 6MHz -3dB; DC to 10MHz -6dB
Risetime: 55ns
Input Impedance: 1MΩ and 30pF
Input: ±400V max.
HORIZONTAL AMPLIFIER
Sensitivity: 720mV/cm to 50V/cm
Bandwidth: DC to 1.5MHz -3dB
X-Y Phase Shift: 5° d.c. to 50kHz
TIME BASE
Range: 0.5μs/cm to 10ms/cm in 6 ranges
Magnifier: x5 (100ns/cm fastest sweep speed)
Calibration: 5%
Vernier: 12:1 continuous
Trigger Sensitivity: 1cm deflection 10Hz to 8MHz
Automatic no manual controls
Power Supplies: 100 to 135V and 200 to 265V
48-440Hz 15W
Dimensions: 182 x 200 x 405mm 4.5kg
Accessories: Main test prods and leads, Handbook
Price: £172.44 inc. 15% VAT and carriage

The instrument reviewed was loaned by Kramer & Co.,
9 October Place, Holders Hill Road, London NW4 1EJ. Tel:
01-203 2473.

continued on page 33

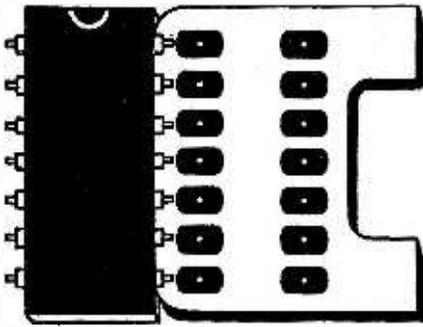

OF THE MONTH 76

Brian DANCE M.Sc

THOMSON-CSF TDE 2608

Thomson-CSF TDE 2608 device is considerably more complex than the well known 555 timer, offering a wider range of facilities. It is especially versatile in its operation, being similar to Thomson-CSF TDB 2068, but can operate over a greater temperature range (-25°C to $+85^{\circ}\text{C}$).

The connections of the TDE 2608 are shown in Fig. 1 and the internal circuit in block form in Fig. 2, together with a few of the more important external components. Although one can use the device by merely constructing the circuits given, its versatility can only be fully realised if the internal circuit of Fig. 2 is understood.

This comprises an operational amplifier (marked A1 in Fig. 2), a comparator (marked A2), five current generators (marked I_A , I_B , I_C , I_D and I_N) and various other amplifiers and components.

The operation may be very briefly summarised by saying that when the potential of the start logic input at pin 5 is raised above a critical value, capacitor C commences to charge due to the small current I_D which is fed to it. The voltage across this capacitor rises and when the voltage at the pin 14 exceeds that at pin 13 the comparator A2 switches so that pin 8 output changes from high to low and the output at pin 6 from low to high. The two outputs return to their original state when the pin 5 voltage is reduced so that the internal transistor Tr2 conducts and the timing capacitor C is discharged. The time delay is equal to the time taken for the current I_D to charge the capacitor C to a voltage equal to that at pin 13.

Detailed Operation

Let us now consider the operation in much more detail. The voltage reference in the base circuit of the transistor T1 causes this device to pass a constant collector current which is taken from the current generator circuits of I_A and I_B . This enables the current generators to pass equal currents (each about $250\mu\text{A}$) to pins 11 and 1 respectively.

The current I_B develops a voltage equal to $I_B R1$ across resistor R1 which is applied to the non-inverting input of the operational amplifier A1. This amplifier and the current generator I_C are in a feedback loop which stabilises with the potentials at pins 1 and 2 equal. The potential is equal to the product of I_C and R2 and remains constant as R2 is changed; thus R2 may be used to set I_C . Quantitatively $I_C = R1 I_B / R2$.

The bias applied to the current generator I_C is also applied to the generator I_D and the internal circuit of the device is so designed that $I_C = 20 I_D$. The current I_D is made twenty times smaller than I_C so that timing capacitor C charges relatively slowly and long time delays can easily be obtained. Hence $I_D = R1 I_B / 20R2$.

The constant current I_D flowing to the capacitor C causes the potential across the capacitor to increase linearly with time, this potential V_C being given by the

equation $V_C = I_D T / C$ where T is the time for which the current I_D has been passing.

The timed period ends when the potentials at pins 13 and 14 become equal: that is when $I_D T / C = R3 I_A$. Substituting for I_D we obtain $R1 I_B T / 20R2 C = R3 I_A$ which may be rearranged to show the time delay, T being given by the equation:

$$T = 20CR2 R3 / R1 \text{ (since } I_A \text{ and } I_B \text{ are equal).}$$

In case the reader feels that this is a complex method of charging a capacitor, it should be pointed out that any change in temperature or supply voltage (or some other parameter) will cause almost equal changes in I_A and in I_B and hence a proportional change in I_D . If I_A is increased, the voltage across R3 ($= I_A R3$) to which the capacitor C must charge to end the timed period also increases, but as the charging current I_D increases in proportion, the timed *period* is unaltered.

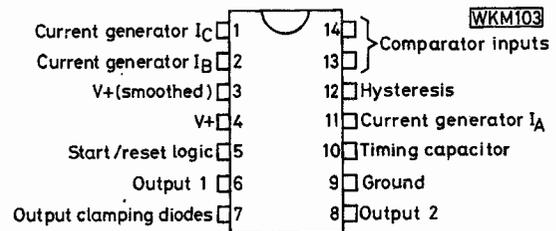


Fig. 1: The connections of the TDE 2608 device

This somewhat complex circuit design enables the time delays to change by only 100 parts per million per $^{\circ}\text{C}$ if only the circuit itself is considered. However, changes in component values due to temperature increase this value to about 500 parts per million per $^{\circ}\text{C}$. Changes in the supply voltage alter the delay time by about 0.05% per volt. Successive time delays should differ by less than 0.1%.

Power Supply

The TDE 2608 can be operated from a power supply between +15V and +35V applied to pin 3, the supply current being typically 5mA when the pin 5 voltage is low and 3mA when pin 5 is high. Otherwise an alternating potential can be applied to pin 4, in which case a smoothing capacitor will be required between pin 3 and ground.

The output or outputs being used at pin 6 or pin 8 must be returned to a suitable positive line through a resistor or other load. When the output concerned is "low"; it can accept a current of 100mA through the load without the output potential rising above +1.5V. Pin 7 is normally connected to the positive supply line to which the load(s) are returned; if the load is inductive, the internal clamping diodes D4 and D5 will then prevent damage to the TDE 2608 from the transient reverse voltages which occur when the current ceases to flow through the load. An example of such an inductive load would be a relay.

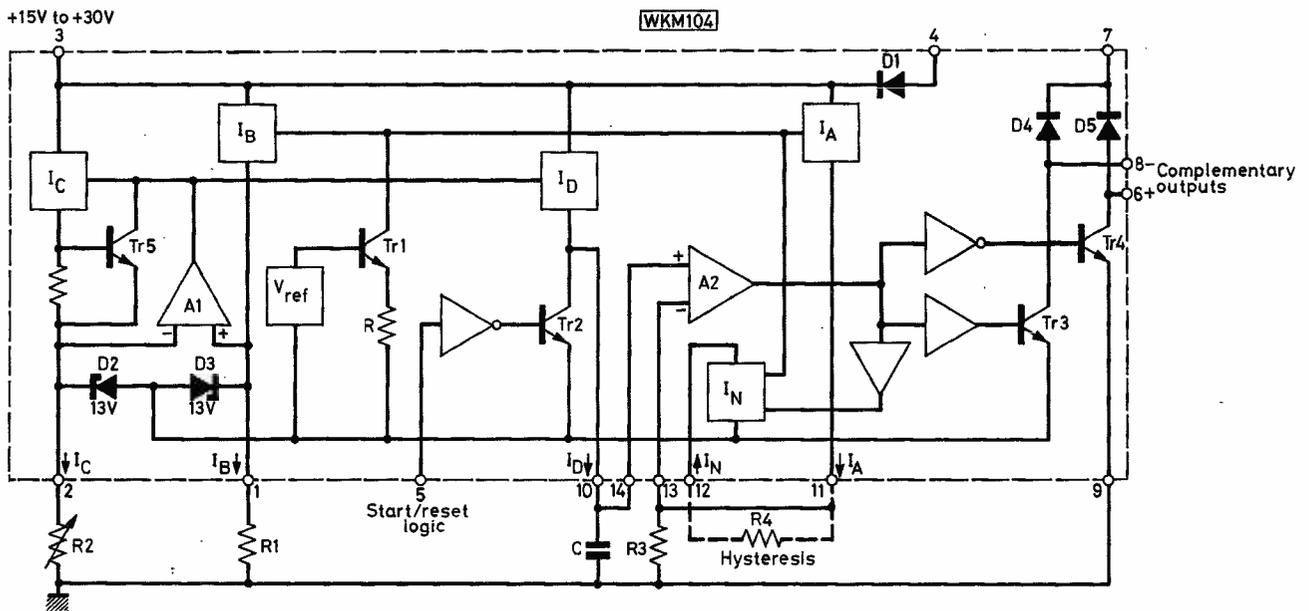


Fig. 2: The internal circuit of the TDE 2608 in block form

Recommended Values

It is recommended that the value of R1 and R3 should not exceed 40kΩ. The value of the timing capacitor charging current at pin 10 should be between 0.5 and 100μA, although the data sheet states that the circuit may operate with a reduced performance with values of this I_D current between 0.1 and 300μA.

Despite the minimum value of the positive supply voltage being given as nominally 15V, the circuit will operate down to 8V if it is designed so that the potential at pin 11 is less than (V⁺ - 2).

The voltage at pin 5 must be raised to at least +8V to start the timing cycle and must be reduced to no more than +7V to reset the circuit and to discharge the timing capacitor.

generator I_N; this only occurs after the circuit has switched at the end of the timed period and reduces the pin 13 voltage so that there is no tendency for the circuit to switch back to its former state. Thus the connection between pins 11 and 12 provides some hysteresis so that unwanted switching is prevented.

Typical Timer

A typical timer circuit using the TDE 2608 is shown in Fig. 3; with the values shown the timed period is just under 8 seconds. It is easy to increase this delay by a factor of ten by placing a 2.2kΩ resistor in parallel with the existing resistor R1. Other time delays up to about 16 minutes can be obtained using the values of C, R1, R2 and R3 shown in Fig. 4.

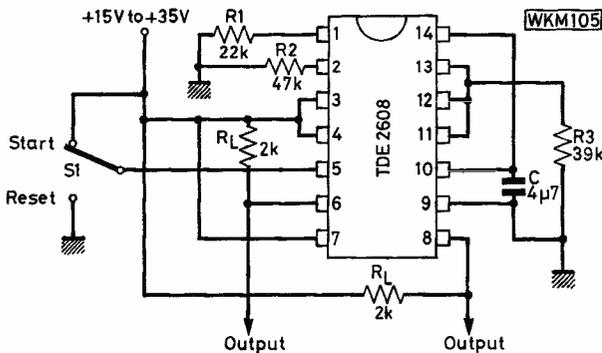


Fig. 3: A typical TDE timer

Hysteresis

Once the potential across the timing capacitor has reached the pin 13 potential and the timed period has elapsed, any small increase in the voltage at pin 13 or any small reduction in that at pin 10 could cause the circuit to revert to its former state. However, this can be prevented by connecting pins 11 and 12 together either directly or by means of a resistor. Part of the current I_A will then be diverted from R3 into pin 12 and so to the current

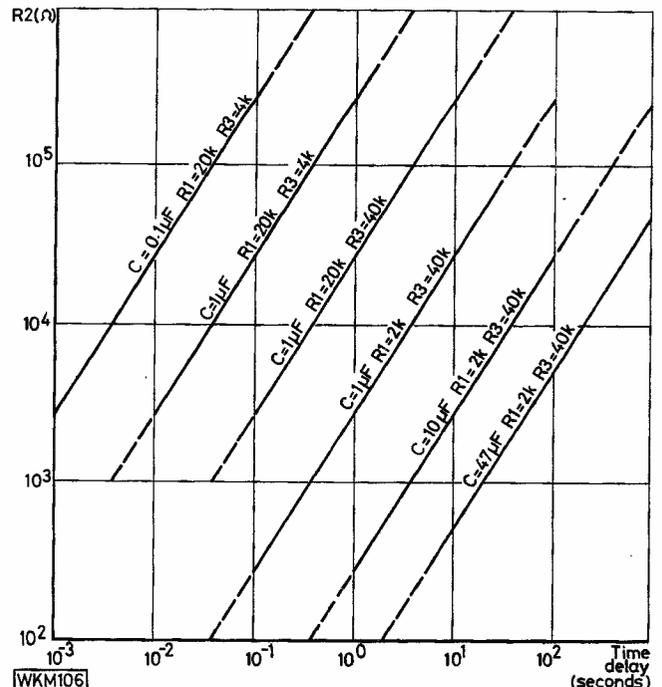


Fig. 4: Time delays available with various component values

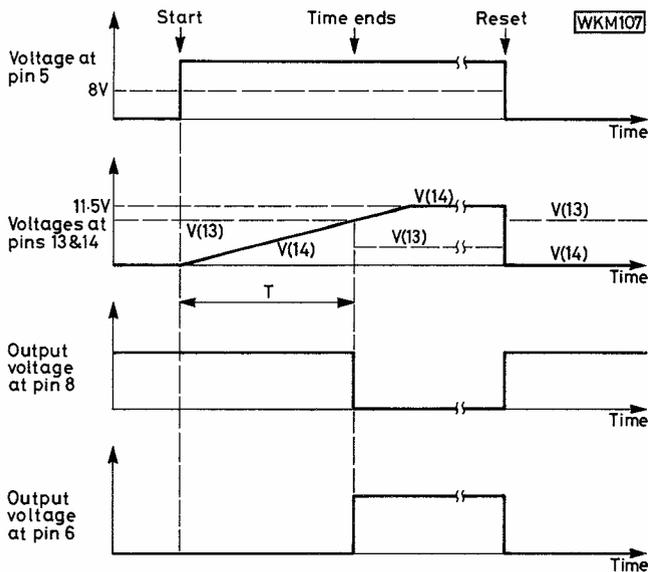


Fig. 5: TDE 2608 timer waveforms

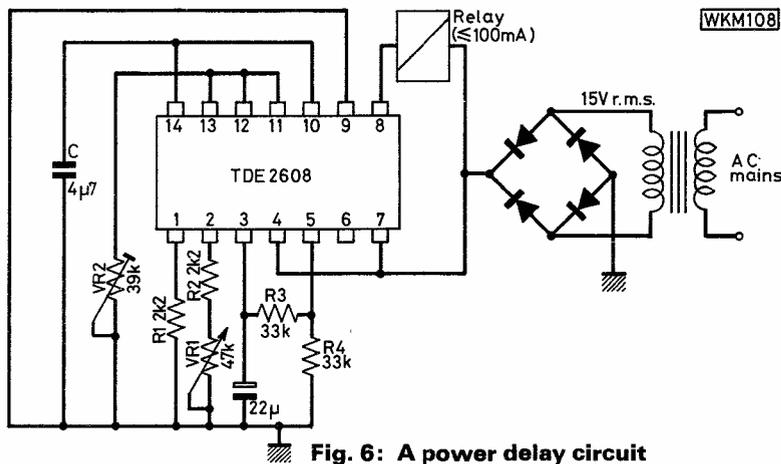


Fig. 6: A power delay circuit

It is important to note that the timing capacitor C should not be an electrolytic, since electrolytic capacitors take a variable leakage current and alter in value with time, to some extent. For optimum stability of delay, C should be a polycarbonate capacitor and R3 a metallic film resistor, but in most applications any non-electrolytic capacitor is satisfactory.

The two load resistors shown are marked 2kΩ in Fig. 3, but naturally their value may be chosen according to the application concerned, provided that it is not so small as to cause a current exceeding 100mA to flow. A small relay may be used as a load, for example.

The circuit waveforms are shown in Fig. 5. It can be seen that when the potential at pin 5 rises above 8V, the voltage at pin 14 commences to rise as the capacitor C charges. When this voltage becomes equal to that at pin 13, the timed period T ends and the output voltages change as shown. At the same time, the voltage at pin 13 falls to provide hysteresis. When the pin 5 potential falls, the circuit is reset to its initial state. It should be noted that there is no change in the output voltages when the timed period commences.

In many cases a circuit which provides variable delay times is required. With the circuit of Fig. 3, the time can be made variable by replacing R2 by a 47kΩ potentiometer in series with a 2.2kΩ fixed resistor. A range of time delays around 20:1 can then be obtained by adjusting the potentiometer.

Power Delay Circuit

The circuit of Fig. 6 shows how the TDE 2608 circuit may be used to close a relay after a certain time, following the application of a.c. mains input. This may be used, for example, to apply power through the relay contacts to certain parts of another circuit after the mains power has been applied for long enough to warm up other sections.

If the values shown are used, when the potentiometer VR2 is set to its maximum value, time delays of about 3.7 to 82 seconds may be obtained by the adjustment VR1. VR2 may be set to a lower value for shorter delay times. Pin 5 is connected to a positive potential at all times when the mains voltage is applied.

Function Generator

A circuit which will generate triangular and square waves simultaneously is shown in Fig. 7. The triangular wave rises during the time pin 6 is in the low voltage state,

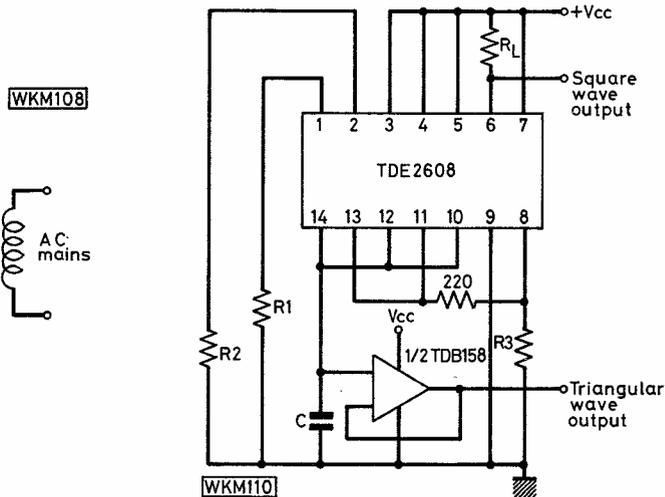


Fig. 7: A waveform generator circuit

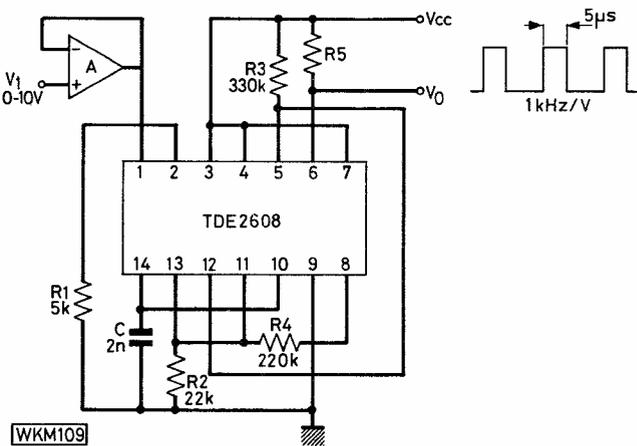


Fig. 8: A voltage-to-frequency converter

this time $20CR3 R1/R2$. The falling part of the triangular wave occurs when the pin 6 voltage is high for a time of $CR3 I_A/I_N$ or about $1.8 CR3$. The circuit values may be chosen to obtain a wide range of waveform times.

The TDB 158 operational amplifier is used so that the output utilising the triangular wave does not load the part of the circuit containing the timing capacitor C, as this would affect the waveform.

Voltage to Frequency Converter

The circuit of Fig. 8 provides a square wave output proportional to the input voltage to the operational amplifier A (which may be a 741 device). The frequency is equal to $200 V_1/R_1 R_2 C$ which corresponds to 1kHz per volt. The high part of the output waveform has a period of $5\mu S$ and the low voltage part varies with the input voltage.

Better temperature stability can be obtained if R_2 is replaced by a Zener diode whose Zener voltage, V_z , is less than 10V. In this case the frequency = $V_1/20 V_z R_1 C$.

The TDE 2608 is a very versatile device which is available from Phoenix Electronics Ltd., 139 Havant Road, Drayton, Portsmouth PO6 2AA.

AERIAL DESIGN USING SCALE MODELS

continued from page 28


The photographs Figs. 6–10 were taken with a Polaroid 350 camera, using a lens aperture of about $f/16$ and exposure time equivalent to one rotation of the timebase, i.e. about 3 seconds. The facilities of the display are illustrated as well as actual patterns from model aerials and the captions provide a short explanation of each photo. The pattern of the 2-element ZL Special in vertical mode (Fig. 8) may be of particular interest to users of this aerial, as it has a virtually perfect cardioid shape which makes it very suitable for v.h.f. direction finding because of the very well-defined null to the rear. In fact it is used by a certain authority for this purpose.

The pattern in Fig. 9 is from an experimental high-gain beam aerial using a square-loop radiator, a square-loop parasitic reflector and a series of parasitic directors. The square-loop reflector proved to be inefficient, however, as is the case with Quad aerials, owing to the large lobes to the rear. This was replaced by a larger plane reflector which almost completely eliminated the spurious lobes and provided a greater forward gain.

Experimental work of this nature can be carried out very rapidly with scale models, in conjunction with the PPI display described in the foregoing paragraphs. This set-up has been put to good use in the design and development of numerous v.h.f. aerials, some of which *PW* readers are already familiar with, the latest being a colinear version of the "Slim Jim" which it is hoped to publish shortly.

Direction Finding

The PPI display can also be used in conjunction with full-size 2 metre aerials, not only for performance measurement etc., but for direction finding as well. It can be coupled to an aerial that rotates continuously in synchronism with the rotation of the timebase. The signals from the aerial are taken to a sensing circuit that provides a short duration squarewave when the signal from a particular direction is at maximum amplitude. The bright arc produced on the display by this squarewave is about 5 degrees wide and its centre denotes the actual bearing. A similar bright arc is produced for a "north" or 0/360 degree reference. The photo in Fig. 10 shows an actual readout from a station bearing 290 degrees with respect to north or 0/360 degrees. Directions of stations obtained with this system are to within better than 2 degrees and a bearing can be registered even if a signal is present for only 5 or 6 seconds. Continuous rotation of the aerial is obtained by an inductive loop coupling method devised by the author, and which with continued development, may prove to be the means of achieving a low-cost beam aerial rotation system.

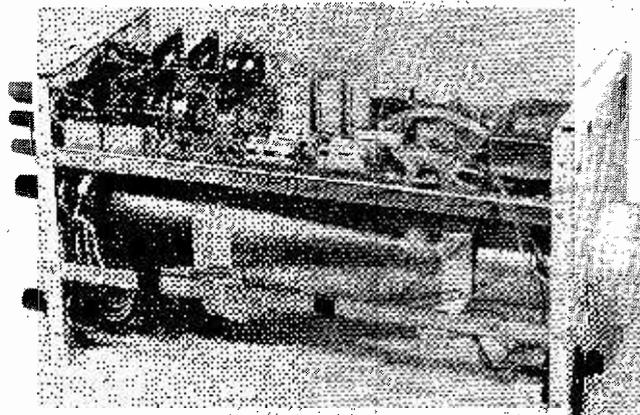

A set of plain test leads with plain prods fitted was supplied and plugged firmly into the input terminals mounted on the front panel. No provision was made for using a b.n.c. plug such as would be fitted to a 10:1 passive divider probe. This is a pity since the instrument is good enough to warrant the use of such an accessory.

The scope was well constructed and the case dismantled easily to give access to the single printed circuit board.

Most important, the instruction manual gives full circuit diagrams and instructions for servicing and setting up the instrument. The instructions are excellent, taking the user through the use of the scope and explaining what it can do, how the circuits work and how to get the most out of it.

Dick Ganderton

KINDLY NOTE!

"Logical Noughts and Crosses" Part 2, June 1979

The following constructional information was unfortunately missed:

Fig. 10 Component placement layout for PCB 2:

After inserting components and links as shown, use insulated wire to connect all like numbered pins to top end of appropriate resistor. Link positive supply to all i.c. top left hand pins and negative supply to all i.c. bottom right hand pins.

Fig. 8 Component placement layout for PCB 1:

After inserting components and links as shown, use insulated wire to link i.c. pins as shown:-

IC 2.4 — IC 10.20 — IC 7.3
IC 2.9 — IC 10.18 — IC 5.13
IC 4.1 — IC 10.6 — IC 5.11
IC 4.13 — IC 10.4 — IC 5.5
IC 5.2 — IC 14.2
IC 5.4 — IC 12.5
IC 6.1 — IC 10.22 — IC 7.2
IC 6.9 — IC 10.16 — IC 7.13
IC 7.5 — IC 10.8

Positive supply to all top left hand pins, negative supply to all bottom right hand pins.

Reset to IC 10.1 — IC 10.13 — IC 11.1 — IC 13.9 — IC 14.1 — IC 15.1.

Fig. 5 Component placement layout for PCB 3:

Connect positive supply to one dropping resistor (top end).

TELEPHONE BELL



B. BARNARD

It is surprising how many domestic problems and irritations can be overcome by the sensible application of quite simple electronic technology.

One such problem in many households is the difficulty—sometimes impossibility—of hearing the telephone bell when one is working in some remote part of the house.

I found, particularly when working in the garden or garage and alone in the house, that the phone bell was quite inaudible and any calls remained unanswered. They might have been important, and as I do get a fair number of important telephone calls, it became a major source of worry.

TV Phones

In my case there was another aspect. The phone is installed in the hall which is adjacent to the room in which we do our listening and viewing. With normal listening levels, we can hear the phone when it rings, but whenever a phone rings off-stage as part of a TV programme (we have hi-fi sound from the TV) we are often halfway out of our seats before identifying the source of the noise. This can be very irritating and a clear, immediate indication of the source adds greatly to relaxation and enjoyment of programmes.

I suspect that this problem applies in many households and the Telephone Bell Repeater is a simple and reasonably cheap answer. Apart from the relay, most of the components will be found in the average experimenter's spares box: the values of resistors and capacitors are not particularly critical and all the transistors are commonly used types.

No connection whatever is made to the telephone instrument or its wiring. The method employed is to pick up the sound of the ringing bell with a cheap crystal microphone which is mounted on a plinth on which the phone stands. The audio signal from the microphone is amplified and then applied to a d.c. amplifier which operates the relay: the relay contacts make and break the circuits of independent battery-operated visual audible indicators.

Circuit Operation

The circuit of the unit is shown in Figure 1. Tr1 and Tr2 are audio amplifiers and provide sufficient drive to operate the d.c. amplifiers Tr3, Tr4 and Tr5 so that they activate the relay in the collector circuit of the final *pn*p transistor. There is nothing sophisticated about the circuit, the design being largely dictated by the components available in my spares box and considerable variations are permissible as we are not concerned with distortion—high gain, however, is required so that the system will be stable and certain in operation. Another reason for high gain is that the unit should work off the low pitched “hooting” telephone and this it does quite satisfactorily.

No attempt has been made to equalise the microphone input circuit as would have to be done for normal audio use. In this particular application, we are concerned only with the sound from a telephone bell which is of quite high frequency and the rising characteristic of the crystal microphone is an advantage in that it gives a useful output at the frequencies we want and a lower output for lower


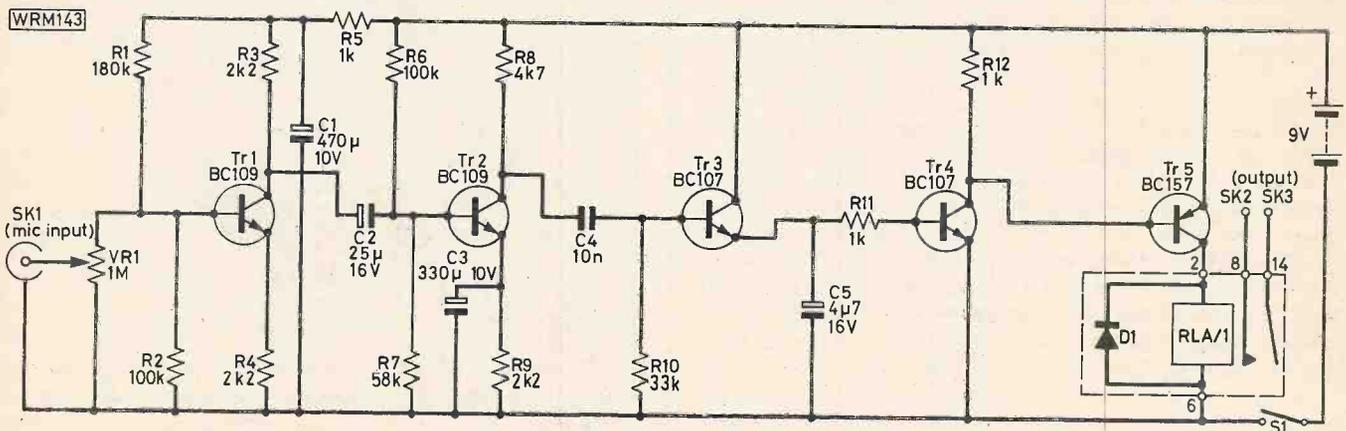


Fig. 1: Circuit diagram of the telephone bell repeater amplifier. D1 is fitted inside the relay specified but if a different relay is used then a diode (1N4148) must be fitted across the coil

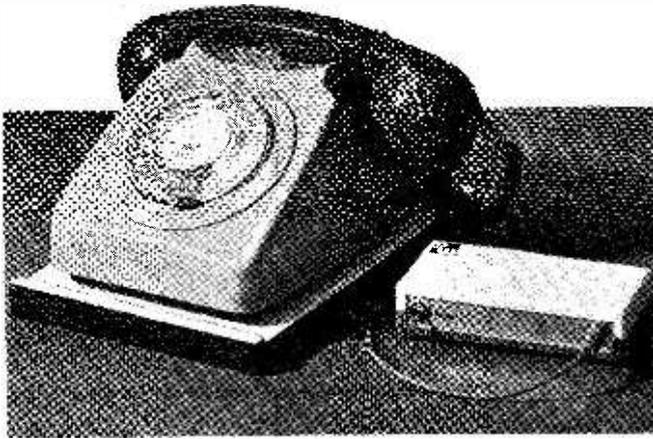

The telephone sits on the home-made plinth with the amplifier unit alongside

pitched extraneous noises which might occur in the vicinity of the telephone. For much the same reason, the 10nF coupling capacitor between the a.c. and d.c. stages is quite small—but if you have the lower pitched telephone, this can be increased to about 0.1 μ F with advantage.

The amplifier is battery-operated, and the quiescent current is about 2 milliamps rising to some 50 milliamps when the bell signal is applied.

The complete system comprises the amplifier, relay and battery in one box, the microphone plinth on which the telephone stands and a red indicator lamp with separate 4.5 volt battery housed in a small box. The microphone is plugged into the amplifier by means of a screened cable and miniature jack plug: the relay contact connections are taken to choc-strip connectors fixed to the rear of the amplifier container to which suitable extension wiring to the indicator can easily be joined.

Where a bell is required for outside use, extension leads are run to a convenient window frame which is drilled and a normal sized jack socket is fitted. The bell and its battery can then be plugged in as required. Obviously, some weather protection must be devised for the jack socket.

The construction of the microphone plinth is quite simple: it consists of a piece of hardboard about 12mm larger all round than the telephone instrument. Wood fillets are glued to the front and rear of the upper side to prevent the telephone slipping off. The edges of the lower side are strengthened with wood struts 18mm wide and of sufficient depth to allow the microphone to clear the table top on which it stands. These struts are covered with non-slip rubber so there is no tendency for the whole assembly to slip about when dialling.

A hole is cut in the hardboard large enough to accept the face of the microphone which is held in place by a single piece of strong wire clamped on either side by two small nuts and bolts. The microphone screened cable is held against the underside of the hardboard by a short length of adhesive tape and is then lead out through a hole in the rear. With the standard type of telephone, the hole for the microphone is located well to the front of the plinth so that it coincides with the bell position just beneath the telephone dial. I have fitted a small piece of foam rubber around the face of the microphone to cut out extraneous sounds.

The layout, construction and position of the visible warning device is a matter for each individual constructor. I was lucky enough to have on hand a small cigarette box 120 x 95 x 38mm deep which is just the right size to hold a 1289 pocket lamp battery and comfortably takes

on its front face a miniature red lamp indicator assembly. A light gauge twin-core flex emerges from the rear and connects with the extension wiring to the relay contacts. The unit sits on top of one of my stereo speakers and is neat and unobtrusive.

The bell and its battery, since they are not likely to be part of the house furnishings, can be a rather crude arrangement and, in my case, consists of a piece of plywood with the bell fixed to one side and the battery strapped to the other: a hook at the top enables it to be hung from a convenient nail when in use. The device is unplugged and brought indoors when not in use as this avoids problems of arranging weather protection.


Relays

Relays are available in a number of different types with different specifications, and although a d.i.l. reed relay with only one set of contacts has been used for the unit shown, the prototype used a different type with two sets of contacts. A larger case was used along with Veroboard instead of a p.c.b.


Alternative Relays

One relay suitable for this application operates in the voltage range of 5.5—17 volts and is generally referred to as the “12 volt type”. In addition to this information, the d.c. resistance of the coil should be of the order of 184 ohms. The contacts themselves are rated in the order of 1 amp at considerably higher voltages than are used in this system so there is no reason why more than one indicating device should not be connected to one set of contacts provided you do not mind them operating simultaneously. In choosing the relay, therefore, there is no reason to go beyond two sets of contacts.

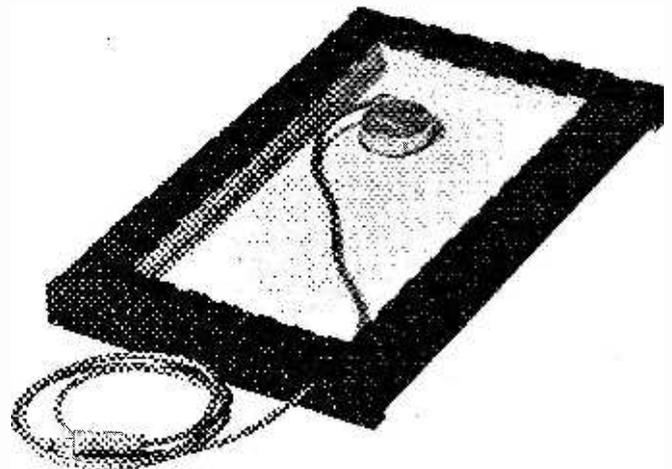There is another point worth mentioning. If you happen to have on hand a 27 volt relay (coil resistance 700 ohms) or can buy one very cheaply from a surplus stores, then by all means try it. In the early work on this system, I used one and it worked satisfactorily, albeit a little sluggish in operation but, as the load current on the contacts is so small, this is of little importance.



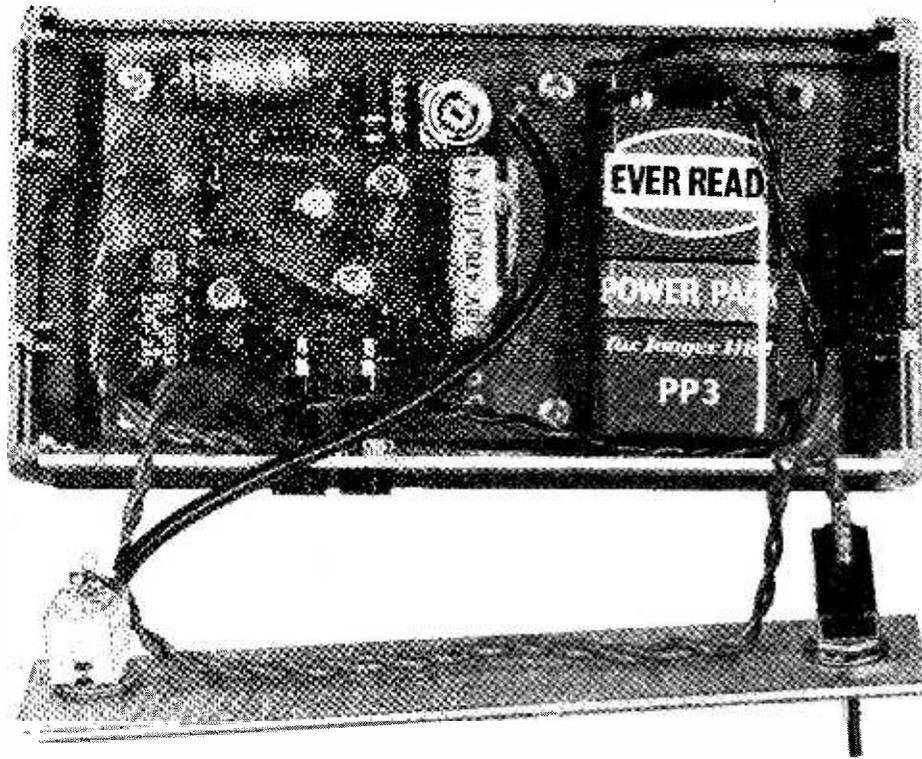The plinth is made from plywood or hardboard with rubber edging to prevent it slipping about when dialling. The crystal microphone insert is fitted into a cut-out in the base and is positioned so that it is underneath the bell



The printed circuit board fits neatly into the plastic Vero box together with the PP3 size battery. The board is held in position by four 6BA screws. Care must be taken when positioning the output sockets to ensure that they will clear components on the p.c.b.

Testing

Having completed the constructional work some bench tests are necessary.

Plug in the microphone jack and connect the visual indicator to its relay contacts: connect the battery and switch on. Set VR1 to maximum and *gently* stroke the face of the microphone with a finger. The relay should close and the lamp come on.

If this does not happen, check the constructional work for a fault. Another possibility is that the relay will close but remains on permanently: this almost certainly indicates that the amplifier is unstable and, in the absence of a fault condition, it is worth trying some decoupling in the supply lead to the first two stages. Another possibility is hum or noise introduced by poor connections to the microphone screened lead.

The next step is to connect a milliammeter in the battery lead and check the no-signal current, which should be about 2 milliamps, the actual value depending on the transistors used and the value of components chosen.

Now check the system on a signal. After a little experimenting, I found that a tin mug or china saucer "rattled" with a screwdriver, produced a sound closely approximating to that of a telephone bell and enabled sensible bench tests to be done.

Adjust VR1 to maximum and hold the mug about two feet from the face of the microphone: for each strike of the screwdriver against the mug, the relay should close, the indicator lamp light up and the milliammeter flick up to about 50 to 60 milliamps.

When these simple tests have been satisfactorily completed, back off VR1 to its halfway position and transfer all the units to their final installation positions.

continued on Page 58

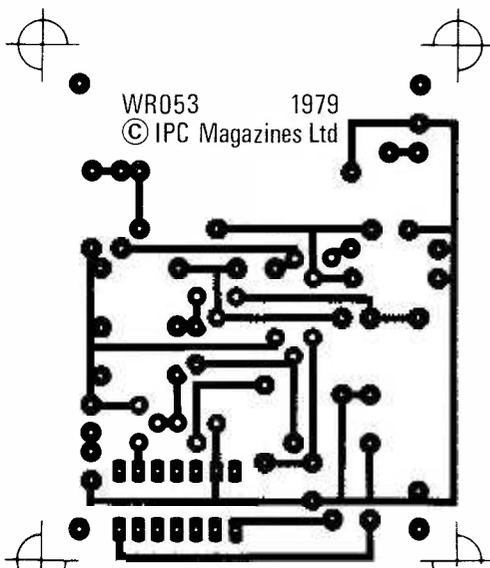


Fig. 2: The printed circuit board copper track pattern is shown full size

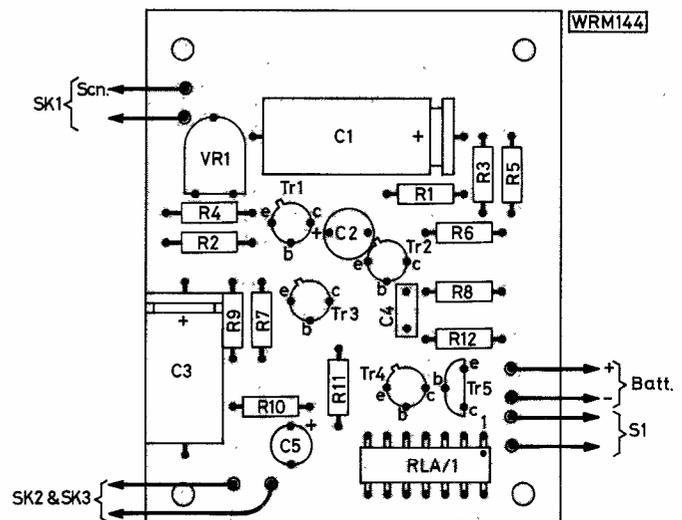


Fig. 3: The component placement for the p.c.b.

PRODUCTION LINES

alan martin

Low-loss trimmers



Two new tubular trimmer-capacitors with PTFE dielectric and silver-plated brass rotor and stator have been added to the range offered by Jackson Brothers (London) Ltd. Both show very low losses at v.h.f. and u.h.f. frequencies, and their multi-turn screwdriver adjustment permits the very precise setting required by electronic instruments and professional communications equipment.

The "Type 430" capacitor has minimum capacitance below 2pF, capacitance swing 30pF, and setting-resolution around 2pF per complete turn. Deviation from linearity is under 1%. The "Type 430" is horizontal mounting and its diameter is 6.3mm and maximum length is 38.9mm (at minimum capacitance).

The smaller "V" 3-pin trimmer is vertical mounting, diameter is 6.3mm and maximum height is 31.8mm. Minimum capacitance is below 2pF, swing 25pF and setting-resolution around 1pF per turn.

Both trimmers show excellent resistance to shock and vibration and remain stable at temperatures from -40°C to +70°C.

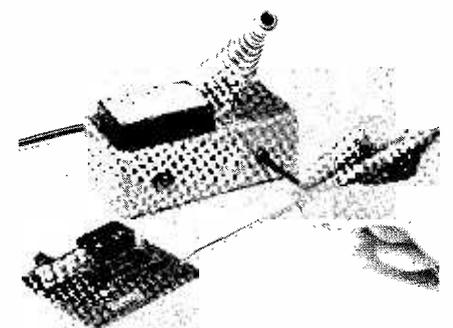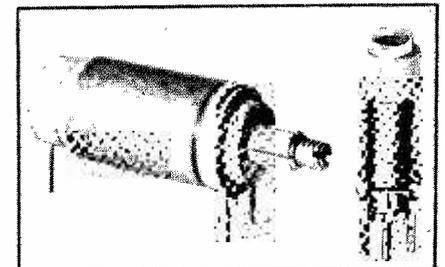Further information from: *Jackson Brothers (London) Ltd., Kingsway, Waddon, Croydon CR9 4DG. Tel: 01-681 2754/7.*



This well styled product represents excellent value at £9.95 plus VAT.


Available from: *Toolrange Ltd., Upton Road, Reading RG3 4JA. Tel: (0734) 29446 or 22245.*

Soldering aids

A set of three double ended soldering aids has been introduced by Adcola Products Ltd., manufactured in non-tinning steel with white plastic hexagonal handles.

The fork/brush tool can be used for wire twisting, unwinding, cleaning components and p.c.b.s, prior to soldering—the hook/spike tool can be used as an extractor to clean holes and for chassis marking—the knife/scrapper is useful for removing surplus solder, solder altering and repairing.

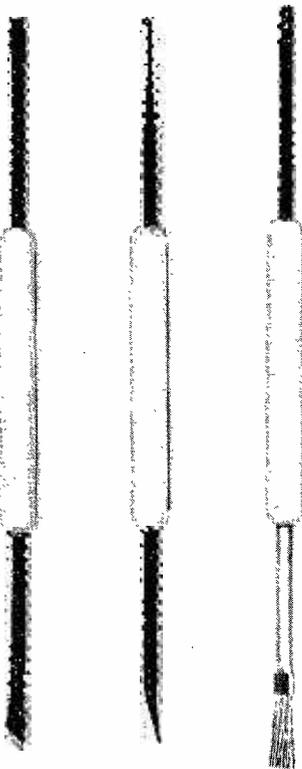The solder aid tool set is priced at £2.50. Further details may be obtained from *Adcola Products Ltd., Adcola House, Gauden Road, London SW4 6LH. Tel: 01-622 0291.*



15% VAT

Readers should check prices of items mentioned on this page.



IC sockets

Winslow Component Systems Ltd., the Kent based semiconductor accessory manufacturer, announce the recent launch of a brand new range of i.c. sockets.

Featuring low profile, glass reinforced polyester bodies—they have been designed to exceed the most stringent criteria demanded by today's high technology microprocessor user and yet are manufactured to be price attractive, even in consumer markets.

The phosphor bronze anti-wicking contacts are available in either gold or bright acid tin plated in 8-14-16-18-20-22-24-40 ways. Prices over the range are approximately between 15 and 60p.


Further details and technical data are available from: *Winslow Component Systems Ltd., Southon House, Edenbridge, Kent. Tel: (0732) 864488.*

Mini soldering station

Toolrange Ltd. have recently introduced the "Oryx PSU-6", a complete soldering station in miniature.

Ideal for work on micro-miniature circuitry, it has a fully isolated and fused transformer for safe operation, a miniature coil-spring iron rest with stainless steel insert, and a sponge tray for tip cleaning.

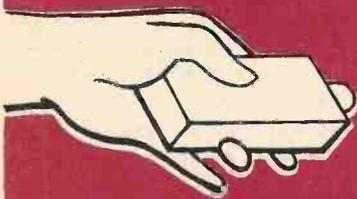The base, which has non-slip feet, a burnproof aluminium cover—to which solder will not adhere, an indicator lamp and measures only 120 x 65 x 50mm. The 6V, 6W iron has a stainless steel shaft, longlife element and a slide-on nickel plated tip only 2.4mm in diameter.



ULTRASONIC REMOTE CONTROL

M. J. DARBY

There are a number of ways by which a piece of equipment can be controlled at a distance without using connecting wires. Signals may, of course, be conveyed to the equipment as radio waves or microwaves using a suitable radio transmitter and receiver; indeed, this is the only satisfactory solution in many cases, such as model aeroplanes and model boats which move some considerable distance away from the person controlling the movement. Unfortunately, however, the transmitter and receiver can be fairly complex and expensive, and an operator licence is required before such equipment can be used.

It is not usually very practical to use light waves, since daylight will normally prevent a satisfactory communications channel being established. In television remote control systems, the current trend is for an infra-red link to be employed, since it is easy to provide the many channels of communication required to select stations, control volume, brilliance, colour, etc., over a reasonable distance in any room. However, infra-red systems are not always the simplest type of circuit for an inexperienced person to construct and a suitable filter is required to prevent daylight from falling onto the photocell in the receiver.

The circuits to be described have been chosen so that they are some of the simplest possible ones which can be made to operate reliably by anyone with little or no previous experience with remote control systems. There are no critical adjustments to be made and the component count is quite small.

The main problem imposed by the use of an ultrasonic link is the limited range which is possible. One cannot quote a definite value of the maximum range; generally it will be between 10 and 20 metres with the simple circuits discussed, but much depends on the gain provided by the particular integrated circuit used as even devices of the same type number can vary considerably in gain. In addition, the range can vary with various types of surroundings; if used in a corridor, the range is likely to be increased owing to the reflection of the waves from the transmitter unit towards the receiver. The range is limited by the attenuation of the waves as they pass through the air.

Ultrasonic waves are, of course, just like sound waves except that they have such a high frequency that humans cannot hear them. However, many animals including dogs, cats and small rodents can clearly hear them. Indeed, it is possible to remove vermin from premises by using a relatively high power ultrasonic generator, but this is not the purpose of the circuit described in this article. Never-the-less, the writer has found that most dogs will prick up their ears when the transmitter is switched on, and it would doubtless be possible to train a dog to come inside a house when the transmitter is operated without the need for the receiver.

The simple circuit to be described has been designed to cause a relay to close at a remote point. The closing of the relay can be used to cause any desired operation to be performed. For example, it could be used to signal to a person in a garden shed that he is wanted in the house.

If one mounts an ultrasonic transmitter unit on the bumper of your car, you could use the emitted waves to cause the garage door to open automatically when you arrive home. Similarly the door could be shut automatically as you leave home, but a suitable motorised door opening system would be required. The driver would not need to leave his car seat as a short pulse of an ultrasonic signal will cause automatic operation of the door.

A simple form of intruder alarm can also be made. The transmitter is placed on one side of a corridor and the receiver on the other side. When the ultrasonic beam is interrupted by a person, the relay in the receiver will open and can be made to initiate an alarm. One advantage of the use of an ultrasonic system is that the intruder will not know he has been detected unless the alarm is deliberately designed to sound in the area concerned to scare the intruder away.

The Transducers

A small ultrasonic transducer is required for use in the transmitter and a similar one in the receiver unit. These transducers are quite small, about 14mm diameter by 11mm long, and have two terminals. They contain piezoelectric ceramic bimorph elements mounted so as to minimise any mechanical damping. Each transducer has a natural mechanical resonant frequency and can be used only at frequencies close to this resonant frequency.

The circuits shown were designed using transducers resonant at a frequency of 40kHz, but they have also been successfully used with 25kHz transducers. The 40kHz transducers are rather more directional than the 25kHz types, but 40kHz waves are attenuated more rapidly in air than 25kHz waves. However, it is doubtful if most users would really notice very much difference between the performance of the two types of transducer.

In order to generate ultrasonic waves in air, an alternating voltage, usually a sine or square-wave, is applied across the terminals of the transmitter transducer. The frequency of this signal must be quite close to the resonant frequency of the transducer if a high efficiency is to be obtained. The transmitting transducer can be driven from a signal generator, but it will usually be much more convenient to make one of the simple circuits to be described in a small box incorporating the battery as well.

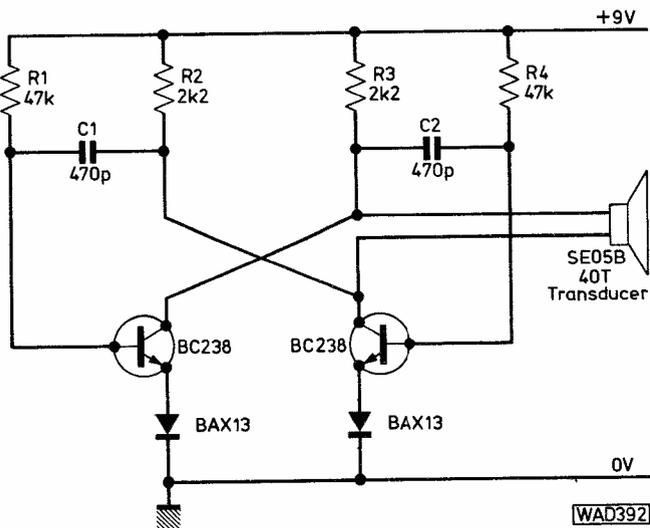


Fig. 1: Discrete component circuit to provide an ultrasonic signal

The transducers used are SE05B 40T for the transmitter, and SE05B 40R for the receiver operating at 40kHz and are available from Hall Electronics, 48 Avondale Road, Leyton, London E17 8JG. Somewhat similar 25kHz types are also available from this same supplier.

In the case of the 25kHz transducers, there is only one type, which is suitable for either the transmitter or for the receiver. However, with the 40kHz types optimum results will be obtained if the type with the suffix "T" is used in the transmitter and that with the suffix "R" in the receiver. The 40T and 40R transducers differ in that the 40R is much more sharply resonant in frequency, but if a wider frequency response is required, the 40R type can be damped by a suitable parallel resistor of about 3.3kΩ with a reduction in the sensitivity.

One connection of the transducer is directly connected to the case of the device, which should be earthed. Otherwise the two connections are interchangeable. The connections are at the back of the device so that the metal grille at the front is left clear for the passage of ultrasonic waves to or from the internal ceramic element.

Transmitter Circuits

The transmitter circuit must employ a low power oscillator which can provide a sine or a square-waveform of a few volts r.m.s. across the transmitter transducer at the correct frequency.

(i) Discrete component circuit. An astable multivibrator circuit capable of feeding an ultrasonic transducer with a square-wave is shown in Fig. 1. The resonance of the transducer automatically triggers the multivibrator circuit so that it operates at the transducer resonant frequency; no oscillator tuning is therefore required. The two BAX13 diodes can be omitted if a low supply voltage is to be used, but in this case the intensity of the ultrasonic waves emitted from the transducer will be reduced and hence the maximum range will be somewhat smaller.

(ii) Integrated circuit transmitter. An ultrasonic transmitter unit using the well-known 555 timer is shown in Fig. 2. The potentiometer VR1 is a preset type which is used for tuning the frequency of oscillation of the 555 circuit to match the resonant frequency of the transducer used. The adjustment is not critical and can be made by adjusting VR1 for maximum current from the power supply line, but it is

better to adjust the transmitter for maximum signal to the receiver as described later.

An alternative type of integrated circuit transmitter unit can be made using a 4011 integrated circuit with two of the four NAND gates as standard type of c.m.o.s. oscillator and the other two NAND gates as output buffers feeding the transmitter transducer in push-pull.

The Receiver

When ultrasonic waves from the transmitter transducer fall on the receiver transducer, a very small alternating voltage at the ultrasonic frequency is produced across the terminals of the receiver transducer. This may be considerably less than a millivolt and must therefore be amplified before it will operate a relay.

Although one can use about seven transistors in a discrete component amplifier and demodulator as the receiver, a very much simpler circuit can be made using one or more integrated circuits. Amplification at the ultrasonic frequency can be easily carried out by the use of an integrated circuit designed for radio or television intermediate frequency amplification, but a power amplifier is required for the operation of a relay of moderate size.

LM1808 Integrated Circuit

The National Semiconductor LM1808 is an 18 pin dual-in-line integrated circuit which contains an amplifier intended for use as a television i.f. amplifier, a volume control circuit and a power amplifier stage on the same silicon chip. The circuit of Fig. 3 shows how this device can be used without any other amplifier devices to close a 12V relay when ultrasonic waves fall on the receiving transducer.

When ultrasonic waves at resonant frequency fall onto receiver, a small alternating voltage at this frequency is applied to the internal amplifier between pins 12 and 13. Pin 12 is tied to ground as far as alternating voltages are concerned by means of the capacitor C5, but the steady bias voltage from pin 12 is applied through R2 to the input at pin 13 so that the amplifier can operate correctly.

The output from the 40kHz amplifier at pin 9 is applied through C4 to the diode pump circuit consisting of D1 and D2 together with the capacitor C3. The diode pump circuit is effectively a demodulator circuit which converts the 40kHz alternating voltage from pin 9 into a steady voltage which appears across C3. Thus when ultrasonic waves fall onto the transducer, the junction of D1 and C3 becomes negative.

A current flows from the positive supply line through the resistor R3 into the inverting input of the power amplifier stage at pin 16. The flow of this bias current results in a

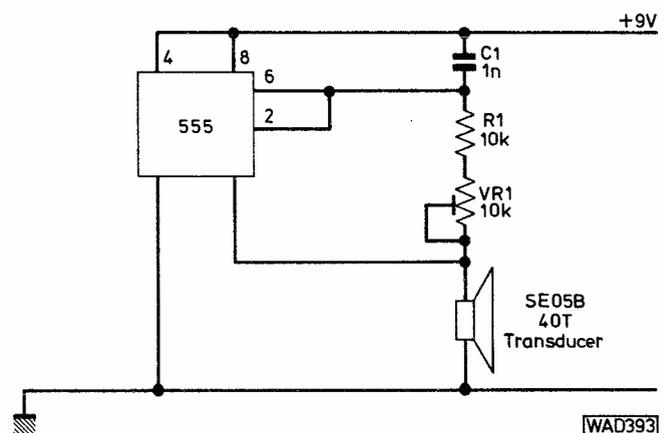


Fig. 2: Ultrasonic generator circuit using a 555 timer

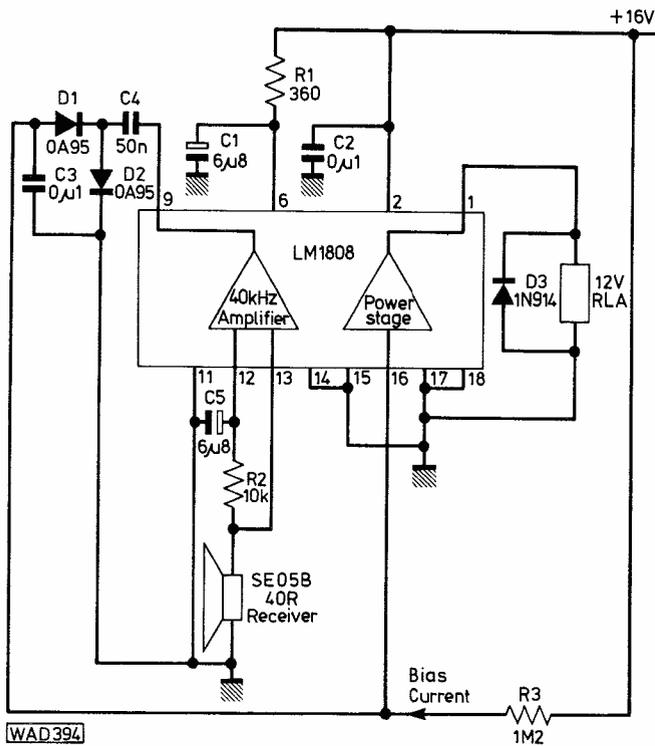


Fig. 3: Receiver circuit using an LM1808 integrated circuit

quiescent voltage of about +2V at the output of the power amplifier stage at pin 1 when no ultrasonic waves are falling onto the transducer. Pin 16 cannot become more positive than about +0.3V, since if the potential at this pin should tend to rise above this value, a current would flow through D1 and D2 to ground; these diodes are germanium types which operate at low forward conduction voltages.

The quiescent voltage of about +2V at pin 1 is not enough to cause the relay to close. However, when the upper end of C3 becomes negative due to ultrasonic waves falling on the transducer, this negative voltage is applied to the inverting input of the power amplifier at pin 16 and the output at pin 1 rises to about +13V so that the relay closes. The diode D3 by-passes the voltage transients developed when the current ceases to flow through the inductive relay coil. If D3 is omitted, these transients could damage the power amplifier stage of the LM1808 device.

It is normally required that the relay will open again when the ultrasonic waves no longer fall on the receiving transducer. A relay should therefore be selected which will

open when the potential across its coil falls to +2V. If one wishes to use a relay which does not open when the coil voltage falls to this value, one should include either a low voltage zener diode in between the relay and pin 1 or alternatively up to three forward biased silicon diodes so that the quiescent voltage across the relay is reduced to below +2V.

General Comments

Good decoupling is very desirable with such a high gain circuit. The electrolytic decoupling capacitors (6.8μF) suggested are much higher than would be used when the LM1808 is used as an intermediate frequency amplifier simply because the operating frequency in this ultrasonic application is much less than in the television application for which the device is primarily intended. The LM1808 has been designed for use from a 24V supply, but the +16V supply has been found to be suitable for this application.

As shown in Fig. 5, the SE05B 40R transducer is sharply resonant when no load is connected across it. In the circuit of Fig. 3, however, the resistor R2 is effectively connected across the transducer and reduces its mechanical Q factor so that the matching of the transmitter and receiver resonant transducer frequencies becomes much less critical. This resistor is, in any case, required to provide the appropriate bias as already discussed.

The volume control section of the LM1808 device is not employed in this application. The power amplifier section of the LM1808 incorporates protection both against short circuiting of the output and against an excessive rise in the temperature of the silicon chip. The use of the resistor R1 in Fig. 3 is essential, since the voltage at pin 6 is stabilised by the internal circuit at between 10.5 and 12.5V and no attempt must be made to try to increase the potential of this pin above the stabilised value.

The Relay

The LM1808 device can switch enough power to operate a substantial relay of the type which often fits into an octal socket. The coil resistance should not be less than about 120Ω so that the current from pin 1 is kept to a reasonable value and dissipation in the LM1808 is minimised. However, this enables a relay to be used which can switch up to about 10A at reasonably high a.c. voltages.

continued on page 64

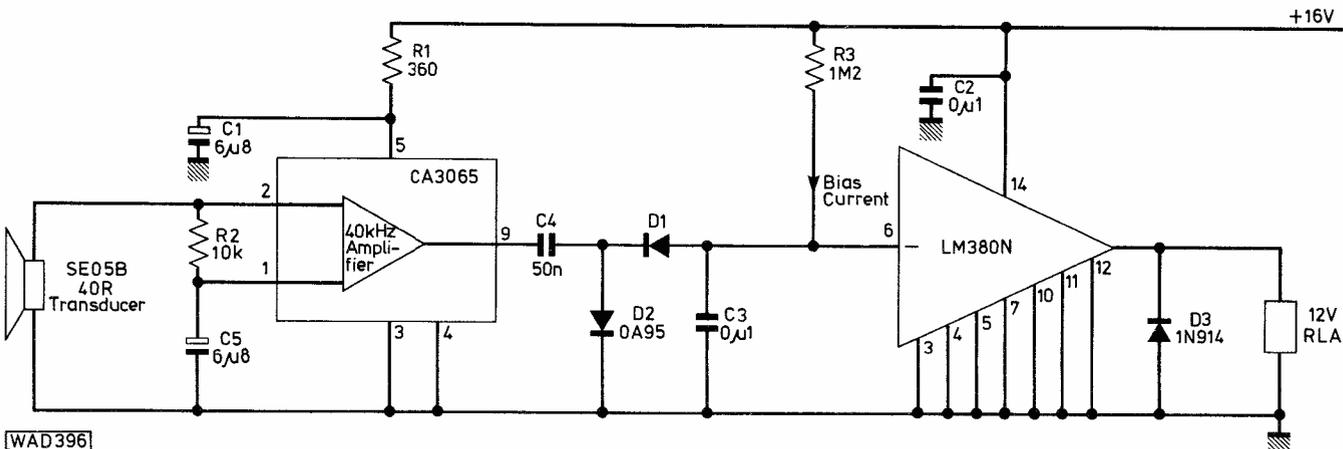


Fig. 4: Circuit using the 3065 and LM380 integrated circuits

Changes in BROADCAST-BAND LISTENING on Short Waves

PART 2

Jonathan MARKS

One point which soon becomes apparent when tuning in to short-wave broadcasting stations is the overcrowding problem. Thousands of stations are competing for only a few frequencies, with resulting mutual interference. The problem is not helped by the presence of jamming transmitters which "broadcast" white noise or distorted music thus blocking a large number of frequencies. Their existence is due to politics and the fear by some governments that listeners will tune in to broadcasts from abroad which disagree with the party line.

Hopefully, the situation should improve with the World Administrative Radio Conference (WARC) 1979 in Geneva which will re-examine frequency allocations. Some are optimistic, forecasting a doubling of existing broadcasting space. But one wonders whether all the military and point-to-point services will be quite so eager to give up their s.w. frequencies in favour of satellite links, as the optimists suppose.

In 1977, the Home Office invited members of the public to send in their suggestions and observations for WARC. Two prominent British clubs, the World DX Club and the Twickenham DX Club, accepted this offer and a number of their members, professionally involved with radio communications, got together to compile a 39-page document of proposals, including a survey of active jamming stations in the broadcast bands. This has since been submitted to the Home Office for examination.

Studios and Equipment


The s.w. stations themselves seem rather optimistic about the media's future. Some still run from ancient studios far inferior to those used by their country's domestic service, yet the standard of presentation is often amazing. In the past five years though, many stations have moved to more modern studios or have renovated the old ones. The Austrian Radio External Service for example, moved in 1976 from wooden "barracks" in down-town Vienna to brand-new studios in the television centre, making it one of the most modern stations in Europe. Likewise, Adventist World Radio in Portugal uses extremely expensive studio facilities to make its religious programmes. Meanwhile at Radio Budapest, work goes on to convert an old tenement block near the broadcasting house into studios for the s.w. service.

All international s.w. stations use reel-to-reel tape machines running at a speed of $7\frac{1}{2}$ or 15 i.p.s. (19 or 38 cm/s), a point to bear in mind if you ever send a station a tape, as few can accommodate the domestic $3\frac{3}{4}$ i.p.s. (9.5 cm/s) very easily. In addition, the Voice of America in Washington uses instant-start cartridges for correspondents' despatches during news programmes, in order to facilitate easy "flow" and fast continuity. The identifying

signals which most stations use before each transmission, to help the listener tune in, are also on endless-loop cartridges, being triggered automatically if the landline from the studio fails. In most cases, stations keep a recording of their output using a very slow-speed tape machine. Tape is usually kept for about a month before being erased, while written scripts are filed for between two and four years.

Broadcast channels on s.w. are 5kHz apart, which means the audio range a station can put out is very limited and far from hi-fi. Still, this is perfectly adequate for speech, which forms the main output from most stations. Music does suffer, however, not only because of the limited audio range, but also because the ionosphere itself introduces fading and phase distortion which sometimes make listening to music programmes very trying.

To help punch their signals through the noise more clearly, most s.w. stations employ compressors and filters before the signal from the studio is fed into the transmitters. The compressor is designed in the same way as the automatic level control in a tape recorder, turning the studio signal level up on quiet music passages and down again during loud orchestral sequences. This ensures that the transmitter is almost 100 per cent modulated (i.e. working at maximum efficiency) for most of the air-time. The filters cut the upper audio frequencies, which are not permitted if the station is to remain within the 5kHz channel allocation. Some stations also boost the remaining treble frequencies to enable voices to be more easily understood through white-noise jamming.

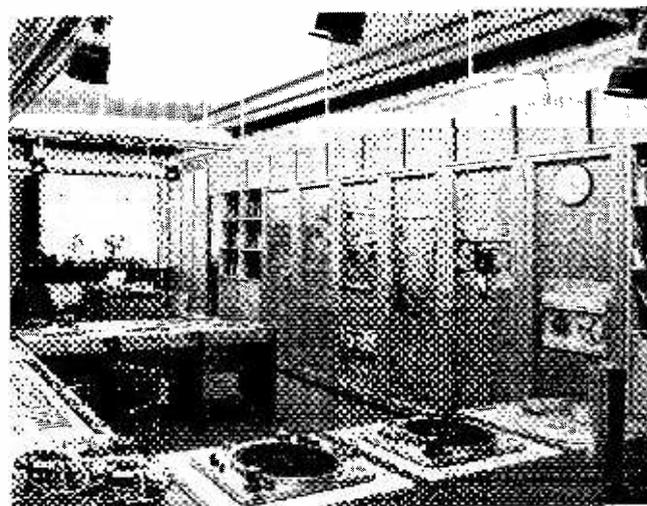

Austrian Radio continuity suite (SW Service). Note the slow-running tape machine under the clock for 24-hour recording of studio output

Photo courtesy ORF, Vienna

Transmitters

Short-wave stations these days find themselves in an unofficial power race whether they like it or not. Ten years ago, stations with 100kW were giants, now 500kW is thought by many to be the normal working power for each transmitter! Such high power operation brings its own headaches. Getting a reliable high voltage power supply is often difficult and running costs are high. Electric arcing in the final power stage of these huge transmitters, where the anode is at a potential of several kilovolts, is a serious problem: HCJB, a religious station in Quito, Ecuador, has had to redesign a new 500kW transmitter to prevent arcing when it is used at exceptionally high altitudes up in the Andes mountains. There have been a number of cases where engineers have received lethal shocks while undertaking maintenance on the transmitter or aerials. Sometimes a transmitter has been overloaded and caught fire!


Choosing a transmitter site presents further problems. Ideally it should have a high water table for good soil conductivity, something which FEBA in the Seychelles solved by putting the antennae on the beach! For the majority of broadcasters though it means a compromise. Quite often there is fierce hostility from local residents near the transmitters when they discover the station's output breaking through over their hi-fi equipment or causing weird effects on electrical equipment. One landlord in the Netherlands though, whose pub stands not far away from Radio Nederlands transmitting complex in Lopik, tuned up a number of coils of wire, connecting the ends to light bulbs. The strong radio frequency power in the vicinity is enough to provide him with free lighting 24 hours a day!

Once on the air, the engineers have to make sure that the transmitters remain on the correct frequency without wandering and are not putting out a distorted signal. Hence most broadcasting organisations run a monitoring service in another part of the country. This set-up checks the station's output regularly and, in the case of s.w. monitoring, is often done for other stations abroad on an exchange basis. Probably the most famous monitoring station in the world is at Caversham, near Reading, home of the BBC Monitoring Service, which not only does the former tasks but also monitors the content of news bulletins from s.w. stations abroad to provide a very important independent news source.

In order to overcome some reception problems in distant countries, several stations have constructed relay transmitters nearer the target zone. Deutsche Welle, the Voice of Germany, for example, serves much of its African audience via transmitters in Kigali, Rwanda. These remote transmitters are fed by landline, s.w. single sideband links, or more recently via satellite. However, the relay bases bring with them problems, when some governments suddenly object to the presence of foreign transmitters in their country, putting out material over which they have no control. This has happened in many cases, notably between China and Albania. Radio Peking has been using the transmitters of Radio Tirana, Albania, for many years for broadcasts beamed to North America. At the beginning of 1978, however, relations between the two countries became strained and in July the relay of Peking was stopped by the Albanians. Whether it will ever start again depends on politics.

Future Developments

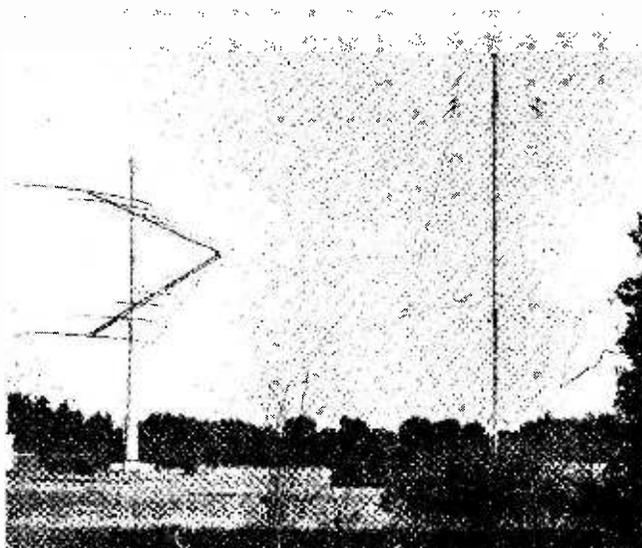So what of the future? At present some broadcasters are looking towards single sideband (s.s.b.), a mode of transmission which amateur radio operators have been using for years. The advantages include reduced



Two aerials at the Austrian Radio Transmitting Centre in Moosbrunn, Lower Austria. On the left, a log-periodic for beaming signals to distant targets, on the right an omni-directional cage antenna for European broadcasts

Photo courtesy ORF, Vienna

bandwidth, the possible use of less transmitter power, and clearer music and speech which is less susceptible to distortion by the ionosphere on the signal's path between transmitter and receiver. But there are problems. For the SWL it means a new receiver with an extremely stable reference oscillator to receive the transmissions, far more stable in fact than SWLs use to listen to s.s.b. on the amateur bands. For if the receiver drifts only slightly during a musical programme the music changes key and the results are awful! Technology is there to overcome this, but at present it is expensive. So for the time being, s.s.b. broadcasts from stations such as the Swiss Broadcasting Corporation are experimental and beamed to North America, where listeners own the most up-to-date equipment. Meanwhile, ordinary a.m. broadcasts will remain for a long time yet, especially to developing countries.

However, there might be a rival to s.s.b., the so-called digital system, and experiments are at present under way. Here, the studio signal is analysed, broken down into very small time segments, and the amplitude of each segment is then described in number form. These numbers or digits in the form of tones, are then broadcast by the s.w. transmitter. The receiver at the other end performs the reverse process, using the digital information to reconstruct the studio signal. The results are an excellent quality signal instead of the usual clipped and distorted transmission via conventional means, with superb fidelity and the minimum of interference. Of course, it needs a special receiver to pick up digital broadcasts, but then so does s.s.b., and with most of the money these days in digital research, integrated circuits for digital radios could beat s.s.b. research to the post.

Other ideas include programme labelling. A frequency modulated (f.m.) signal is encoded into the original amplitude modulated (a.m.) signal, which would not interfere with the programme material on existing sets. Cheap, simple circuitry could be incorporated into the average radio to identify the encoded f.m. signal and by changing the form of the latter with each language you could programme your s.w. radio of the future to check, for example, all the English-language broadcasts in the 49 metre band at any particular time. The technology for this is already with us!

continued on page 64

Practical Wireless, August 1979

NEXT MONTH IN...

practical

WIRELESS



SPECIAL


PULL-OUT FEATURE

YOUR HOLIDAY

radio & tv guide



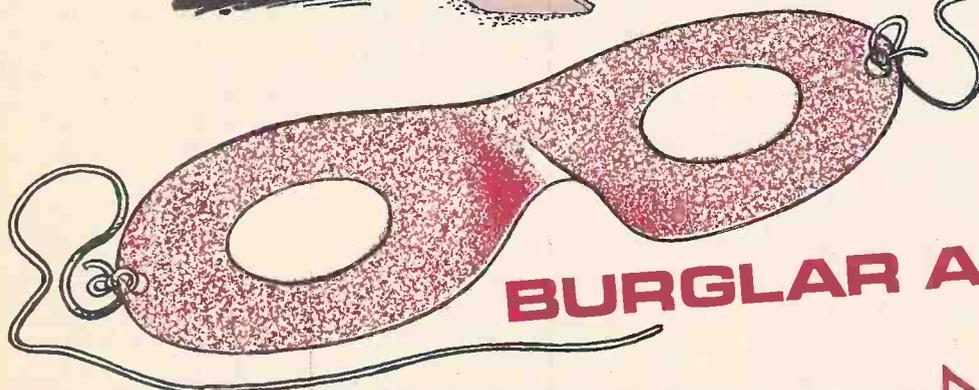
Do you have trouble finding your favourite radio programmes when you are sitting sunning yourself on the beach? Then you definitely need our guide to help you tune into the local transmitter. National and local radio stations as well as TV transmitters are pin-pointed on our special maps.






BURGLAR ALARMS

Stop Thief!! A new series describing not how to build a simple alarm that wouldn't stop a granny, but how to design an effective and *individual security system*. Basic approach, devices and installations (basic or to BS1 standard) are discussed in detail.

BUILDING DISCO CABINETS

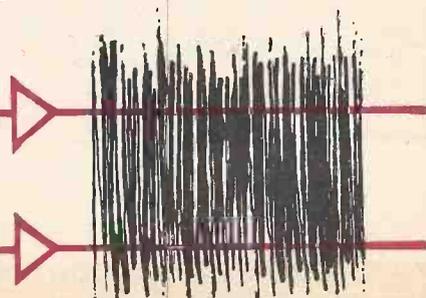

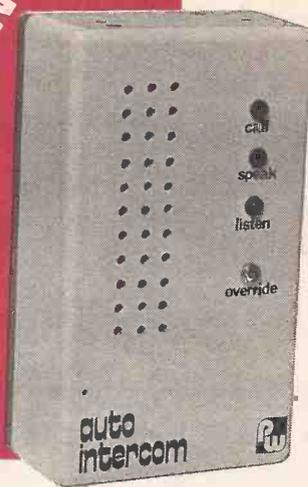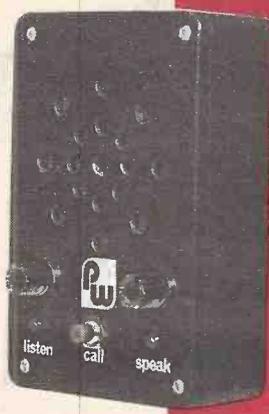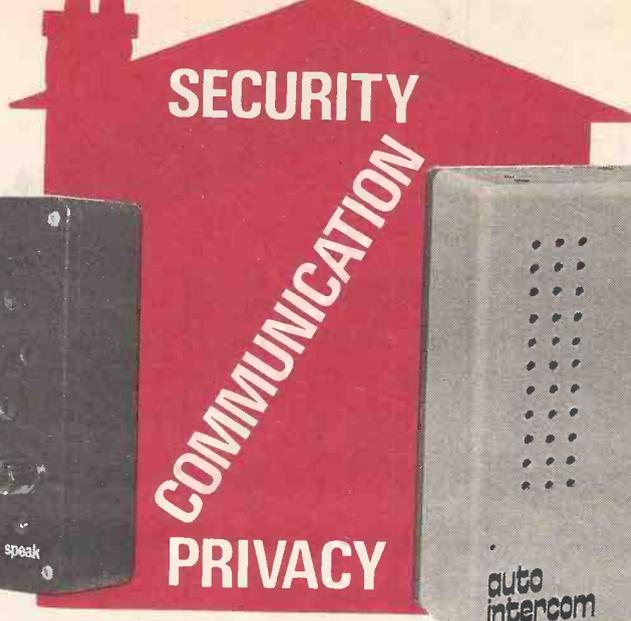

Automatic Intercom

PART 1

Keith CUMMINS

Are you embarrassed and annoyed to be dragged away from a good book or your favourite programme only to find that your caller is a smooth-talking hawker, intent on selling you something you cannot afford and don't even want? If you are, or you want simply to tackle an interesting and reasonably technical project that will provide an additional and useful facility about the house (or that of an elderly relative, perhaps?)—you might consider getting your tools together and starting work on PW's Automatic Intercom.

The system is designed to provide two-way speech, completely automatically, between the front door of a house and a convenient position inside; the lounge or kitchen, for example. The remote door-unit originates an electronic call-tone which gives instant warning of the caller's presence. The occupant, having determined the visitor's identity, can then decide to open the door or otherwise as he sees fit.

Enhanced Security

The intercom affords obvious advantages, foremost among these, naturally, being that of enhanced security for one's home and family. One is able to diplomatically discover a caller's name and the purpose of his visit without opening (or even approaching) the front door—an important consideration in these days of increased petty crime. Therefore the system described in this article is worthy of serious consideration, particularly if you own one of those modern, mainly-glass front doors that were designed to be aesthetically pleasing rather than as an effective barrier to entry. If the logic of fitting good locks and chains to a structurally weak door is lost on you as well as on me, this system may provide a reassuring answer! You may even find that, after dark, the illuminated door-unit will, in itself, act as a deterrent to the nuisance caller. The implications to the elderly or chairbound are quite obvious, particularly when all that is necessary is to keep within reach of a microphone.

Automatic



Why *automatic*? Mainly because under most conditions, the caller having "opened" the system with his push at the door-unit button, there will be no further need for a lot of fiddly button-pressing, in order to conduct a normal visitor-occupant chat. The direction of speech is determined by the system itself sensing whether it is the caller or the occupant who is doing the talking, changing the speech-flow accordingly and closing the system down fifteen seconds after conversation ceases. The system will not then reopen without another push at a button—so if a motor-mower is being used a few feet from the door-unit, its melodic rattle will not be unavoidably relayed into the house interior!

Other worthwhile features include a manual override button on the indoor main unit so that events on the door-step can be monitored or, alternatively, so that it is always the householder who has the last word! The system also incorporates an automatic gain control which will maintain a nearly constant volume under practical conditions—two potentiometers enable the a.g.c. characteristic to be "trimmed" to suit a particular environment, be it central London or a rustic porch. If someone calls while you are out, the event is "remembered" and a flashing "call" indicator remains flashing until cancelled by the householder, on his return.

Integrated Circuits

The reader will probably appreciate that, to provide the facilities and automatic control described is a complex process. In fact, the intercom is rendered practically viable and cost-effective only by the use of integrated circuits—ten i.c.s are used, five in the control logic and five in the audio circuitry. Fortunately, most of these are reasonably priced; the CMOS chips particularly so.

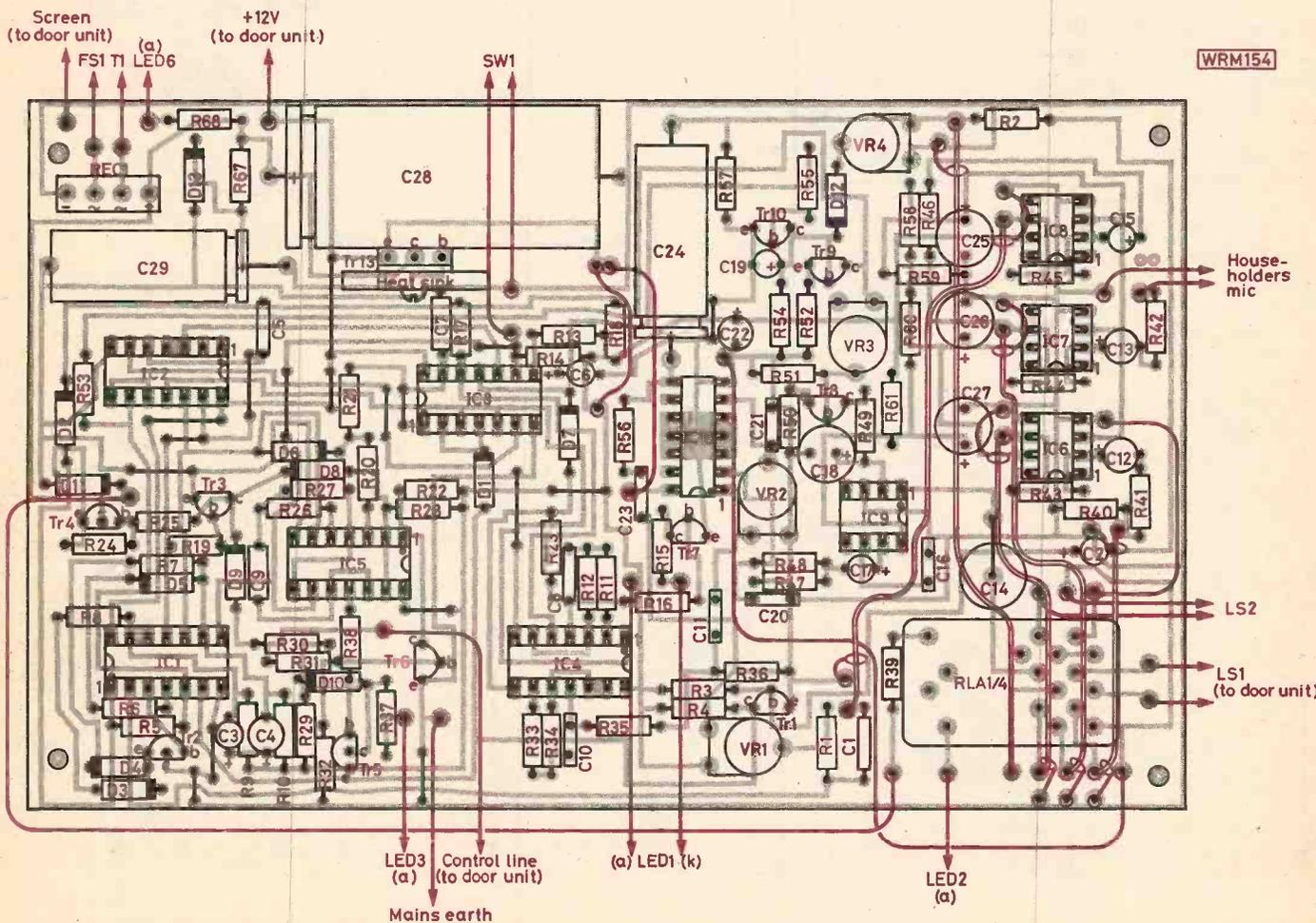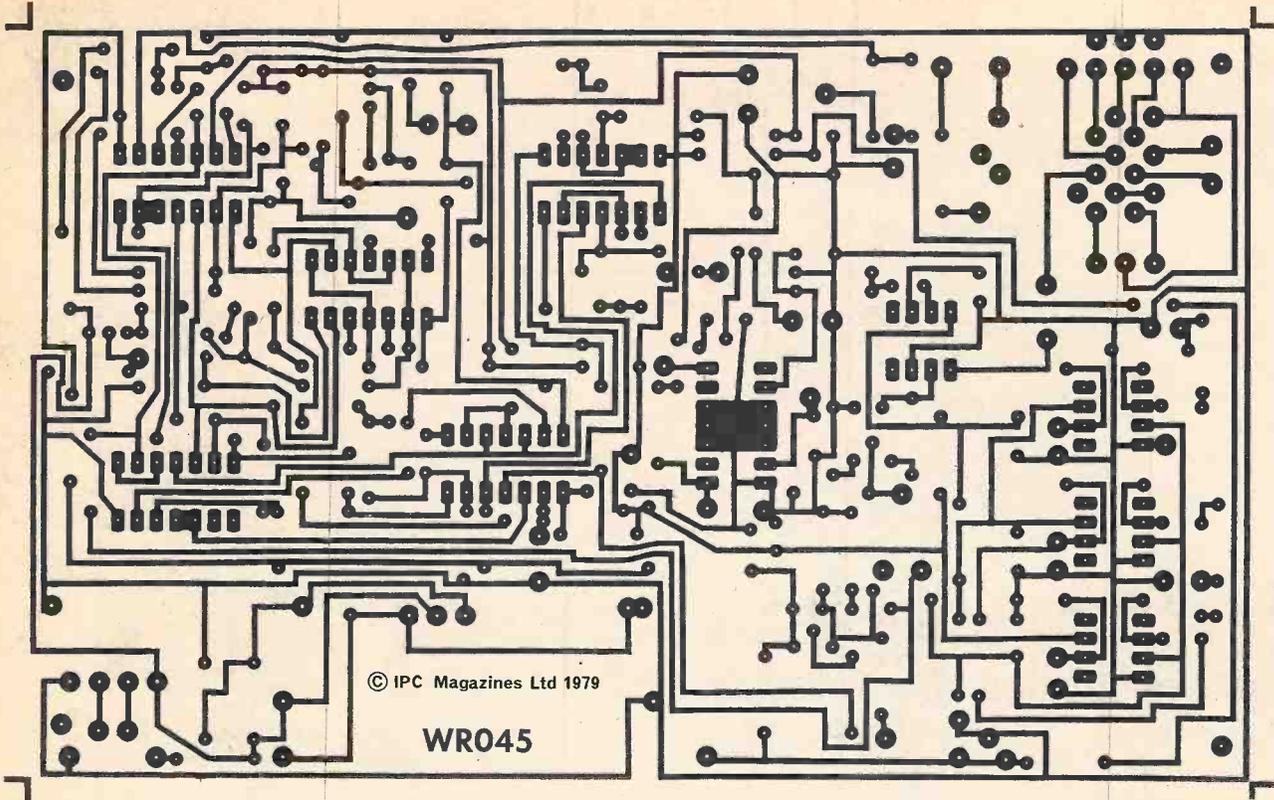Two considerations led to the choice of CMOS devices: the high input impedance allows for simple long time-constant circuits, and a common +12V supply can be used for both logic and audio components. Transistors



Printed circuit board details for the main unit. The copper track pattern is shown full-size at the top with the component placement drawing underneath. Note: C17 is a non-polarised ceramic capacitor

* Items mounted off board

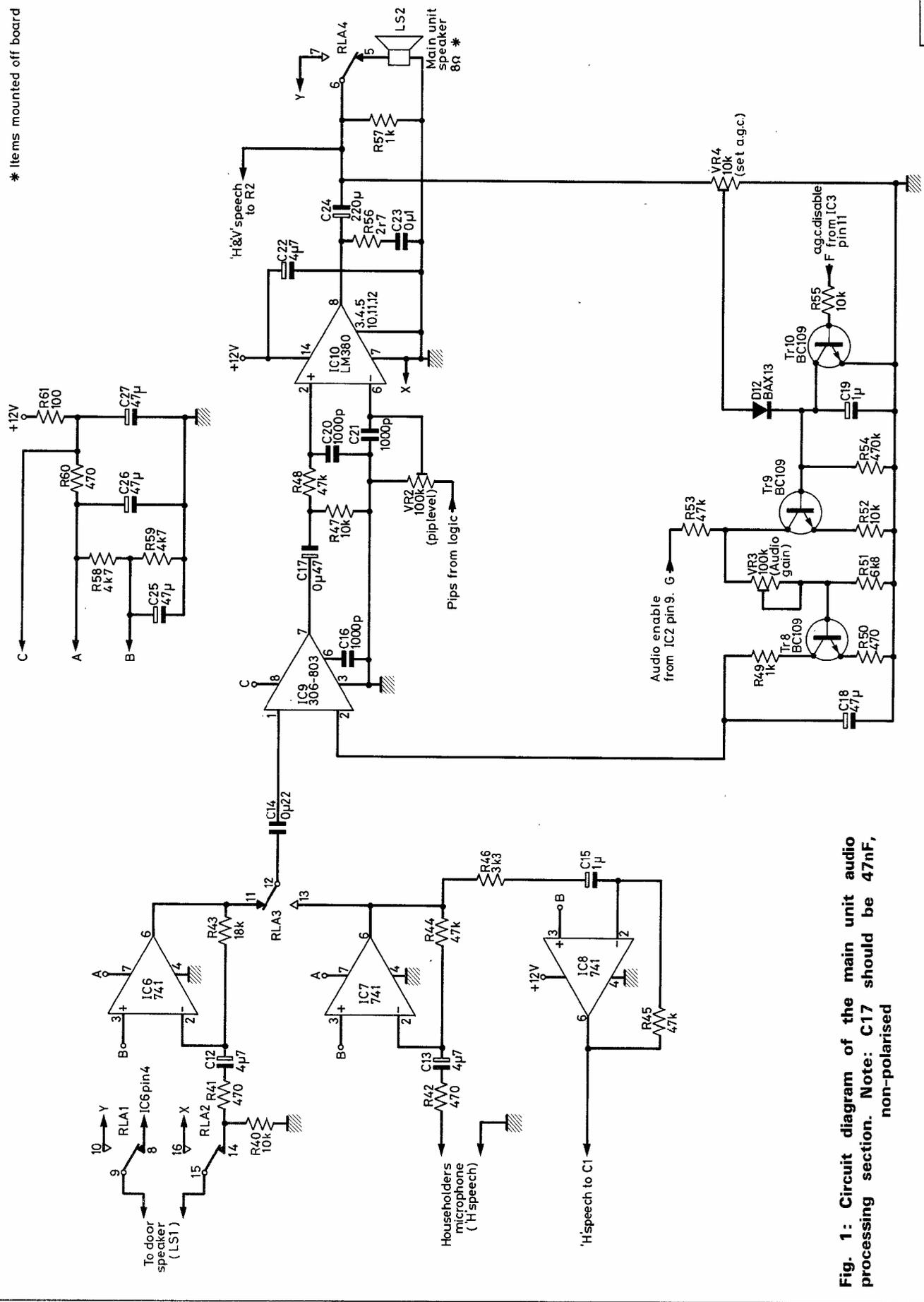


Fig. 1: Circuit diagram of the main unit audio processing section. Note: C17 should be 47nF, non-polarised

are used peripherally to buffer the CMOS logic and to perform certain functions in the a.g.c. circuitry.

As a constructional project, the intercom provides an interesting combination of digital and analogue techniques—not all constructors are familiar with both, and either may present “new ground”. It is convenient that, for ease of description, the circuit may be broken down into these same two areas: control and call-tone generation (digital) and the audio-processing components (analogue). The audio circuit is shown in Fig. 1 and is mounted, together with the logic components, on the p.c.b. within the main unit.

Door unit

However, before considering these major areas of the design, it would be best to deal with the much simpler door-unit (Fig. 2) and the cable which connects it with the main unit. Five connections are required between the door and main units and these are conveniently provided by a screened four-core cable; care was naturally taken to devise a system which depends upon only a single cable connection between the two units. The screen is used, fairly obviously, to provide a common earth connection between the units: the four inner conductors provide a speech pair (kept separate from other functions in order to avoid noise and hum), the +12V supply and the “control line”, which conditions the logic in the main unit and provides the appropriate indications to the caller.

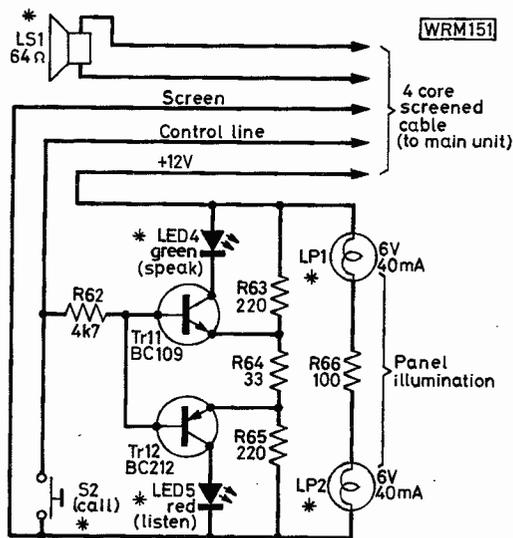


Fig. 2: Circuit of door unit. Starred items are mounted on front panel

The unit itself consists of a 64Ω loudspeaker (doubling as a microphone), the indicator circuit which responds to the d.c. voltage present on the control line, and the power supply to the two 6V lamps.

In the quiescent “standby” condition, the control line is at approximately +6V (“half-rail”). If it moves positively (towards “rail”), Tr11 turns on and LED4 lights, whereas if it moves negatively (towards earth) Tr12 turns on and LED5 illuminates; thus “Speak Now” and “Listen” are signalled to the caller. Push-button S2, which the caller presses on first arrival, short-circuits the control line to earth causing the “Listen” l.e.d. to light and the logic circuitry in the main unit to produce the call-tone, alerting the attention of the householder. Resistor’s R63, 64 and

65 bias the emitters of Tr11 and Tr12 slightly either side of +6V; therefore, if the control line is at half-rail neither l.e.d. illuminates. R62 limits the base current in these two transistors. R66 reduces the applied voltage to the 6V lamps in order to increase their life.

Audio

The audio circuit is shown in Fig. 1, and uses three 741 op. amps (IC6, 7, 8), an MC3340P variable attenuator (IC9) and an LM380 as the audio output chip (IC10). IC9 is controlled by Tr8, 9, 10 and provides the a.g.c. The direction of speech through the system is switched by a miniature relay, RLA, and its contacts are all shown in Fig. 1. Their method of connection has been carefully chosen to avoid feedback problems—for example, the earth return of the door-unit speaker is switched through to the earthing of the output chip IC10, and contacts RLA1 and RLA4 are effectively in cascade when the door speaker is used as a microphone, resulting in excellent isolation between input and output.

With RLA de-energised, the 64Ω door speaker is used as a microphone and is connected to earth and the inverting input of IC6 via R41 and C12. The gain of IC6 is determined mainly by the ratio R43:R41—in this case, approximately 32dB. It is contact RLA3 which connects the output of IC6 to the input of IC9, the variable attenuator, and thence to the output stage and the main-unit speaker, via contact RLA4.

Considering the circuit in greater detail, the three 741 op. amps have their non-inverting inputs biased to half-rail by the common divider network R58-59, this bias rail being decoupled by C25. Because all the inverting inputs are a.c. coupled, the outputs will stand at half-rail because of the 100% d.c. feedback applied through R43, 44 and 45. As the difference in d.c. voltage between the outputs of the three op. amps is therefore negligible, the input to IC9 via C14 can be directly switched by contact RLA3 without clicks in the audio output.

The speech from the door-unit (“V” speech) is amplified by IC6 (32dB) and that from the householders microphone (“H” speech) by IC7 which is arranged to have a higher gain (R44:42 = 40dB). An output additional to that which is fed to IC9 via contact RLA3 is taken to IC8 which provides another 23dB gain. Thus “H” speech from the microphone, amplified by a total of 63dB, is taken to the logic circuits (via C1) which recognise its source and energise RLA. The contacts of RLA then route the speech so that the householder can address the caller.

Automatic gain control is accomplished by IC9 (more of this later) before the signal is passed to the non-inverting input of IC10 via C17, R47, R48 and C20 which form an audio filter restricting the speech bandwidth roughly to the limits imposed by a normal telephony system. C17 and R47 attenuate low frequencies while R48 and C20 form a low-pass filter with a cut-off frequency of around 3kHz. The output from IC10, which has a gain of the order of 50dB, is fed via contact RLA4 to whichever speaker is selected by the logic—naturally, these are both inductive loads and the Zobel network R56/C23 compensates for this so that the LM380 sees a constant and resistive load. An additional output from IC10 is taken to the logic circuits so that the end of speech in either direction is recognised, and the system returned to the “standby” mode 15 seconds later. The LM380 is also used to amplify the pips generated by the logic when S2 is operated by a visitor; they are fed via VR2, the pip volume control, to the inverting input of IC10 avoiding the need to buffer both pips and audio.

★ components

Resistors			Semiconductors		
<i>¼W 5%</i>			<i>Integrated circuits</i>		
2.7Ω	1	R56	LM380	1	IC10
33Ω	1	R64	MC3340P	1	IC9
100Ω	3	R39, 61, 66	741	3	IC6, 7, 8
220Ω	4	R15, 37, 63, 65	4000BE	1	IC2
470Ω	7	R8, 30, 41, 42, 50, 60, 68	4011BE	3	IC3, 4, 5
1KΩ	4	R24, 49, 57, 67	4093BE	1	IC1
2.2kΩ	2	R7, 32	<i>Light-emitting diodes</i>		
3.3kΩ	2	R25, 46	3mm yellow	1	LED6
4.7kΩ	5	R29, 31, 58, 59, 62	5mm green	2	LED2, 4
6.8kΩ	2	R2, 51	5mm red	2	LED3, 5
10kΩ	10	R6, 16, 19, 21, 36, 38, 40, 47, 52, 55	5mm yellow	1	LED1
18kΩ	1	R43	<i>Diodes</i>		
47kΩ	5	R34, 44, 45, 48, 53	BZY88C12	1	D13
100kΩ	10	R4, 11, 14, 17, 20, 22, 23, 26, 28, 33	1N4001	12	D1-12
470kΩ	3	R3, 35, 54	<i>Transistors</i>		
1MΩ	4	R1, 12, 13, 18	BC109	8	Tr1, 3, 6, 7, 8, 9, 10, 11
<i>¼W 10%</i>			BC212L	4	Tr2, 4, 5, 12
1.5MΩ	3	R5, 9, 27	TIP31	1	Tr13
3.3MΩ	1	R10	<i>Bridge rectifier</i>		
Potentiometers			BY164	1	REC1
<i>Miniature pre-sets (horizontal mounting) 0.1W</i>			Switches		
10kΩ	1	VR4	Min toggle s.p.d.t.	1	S3
100kΩ	3	VR1, 2, 3	Push-to-make, s.p.	2	S1, 2
Capacitors			DIL sockets		
<i>Ceramic</i>			8-way	4	for IC6, 7, 8, 9
1nF	4	C11, 16, 20, 21	14-way	3	for IC3, 4, 5
10nF	1	C10	14-way (low-profile)	2	for IC1, 2
22nF	1	C8	NB: IC10 is soldered directly to the p.c.b.		
47nF	1	C17	Miscellaneous		
0.1μF	4	C1, 5, 7, 23	64Ω 66mm dia. loudspeaker (1). 8Ω 5in x 3in loudspeaker (1). Mains transformer 14V 1A (Greenweld XO27 or similar) (1). 200Ω microphone (1). Cases—188 x 110 x 60 (Vero 65-2522K or similar) (1). 120 x 98 x 45 (Greenweld V216, 219 or similar) (1). "Continental" type 185Ω 4-pole c/o relay (1), plus 0.1in p.c.b. mounting socket (1). 6V 0.36W T1½ L.E.S. lamps (2), plus clear lampholders (2). 400mA 20mm antisurge fuse (1), plus holder (1). Main unit p.c.b. (1). Door unit p.c.b. (1).*		
<i>Polycarbonate</i>			Equipment wire for interconnections, sleeving, terminal pins, 3-core mains lead, 4-core screened cable for interconnecting units, grommets, polystyrene foam, aluminium strip, nuts, bolts, washers and adhesives as required.		
0.22μF	1	C14	* Door unit components can be constructed onto Veroboard if desired.		
0.33μF	1	C9			
<i>35V tantalum bead</i>					
0.22μF	1	C2			
0.47μF	2	C3, 6			
1μF	2	C15, 19			
4.7μF	4	C4, 12, 13, 22			
<i>16V electrolytic</i>					
220μF	2	C24, 29			
<i>25V electrolytic</i>					
47μF	4	C18, 25, 26, 27			
2200μF	1	C28			

Gain control

Now we come to the a.g.c. circuit. A third output from IC10 is taken to VR4 ("Set a.g.c.") and is then rectified by D12, charging C19 to a voltage proportional to the speech level—but only if Tr10 is not turned on. The a.g.c. must be disabled while the call-pips are being produced so that C19 does not become overcharged. If this occurred and the householder answered immediately, his speech

would be severely attenuated before the a.g.c. system recovered. Tr10 is therefore turned on by the logic while the pips are being produced, effectively disabling the a.g.c. system and avoiding the problem.

The overall gain of the speech path depends on the d.c. potential applied to pin 2 of IC9, for it is this that determines the gain of the device. When the system is activated, either by a caller at the front door or by the

householder pressing the "override" button on the main-unit, the logic sends an "audio enable" command to the a.g.c. circuit. This takes the form of approximately +11V (or logic "high") applied to the base of Tr8 via R53 and VR3; Tr8 then turns on to a degree determined by the setting of VR3, pulling down the potential on pin 2 of IC9 and enabling it to pass the audio signal to the input of IC10. It is, then, this conduction through Tr8 that determines the gain of IC9 and therefore VR3 is the master gain control of the system. The voltage across C19, which depends on the signal voltage rectified by D12, progressively turns Tr9 on, reducing the voltage at the junction of R53 and VR3 and turning Tr8 off, consequently lowering the overall gain. The degree of volume compression (or the percentage change in the system gain brought about by a given rise or fall in the audio level at the output of IC10) is set by VR4 ("Set a.g.c.").

Of course, it is not simply the degree of a.g.c. that is important, but the manner in which it is applied. Obviously, it is necessary for the a.g.c. to react quickly to a sudden increase in volume (i.e. have a fast attack) and to decay at a slower rate; this is so that each syllable is not attacked individually. This produces a most unnatural effect! C18 has been chosen, together with C19, to produce the required a.g.c. characteristic.

Power Supplies

Before passing on to the logic itself, it might be best to briefly consider the power supply arrangements as these are fairly standard and uncomplicated, using a Zener-stabilised emitter-follower as a series regulator. The circuit is shown in Fig. 3.

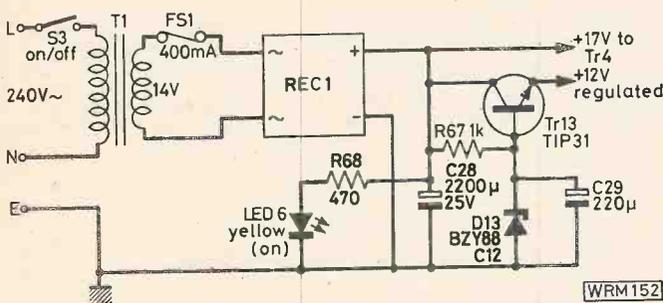


Fig. 3: Power supply

Approximately 14V a.c. from the mains transformer T1 is rectified by REC1 to produce a +17V supply, smoothed by C28. This 17V directly feeds the coil of RLA, the collector of Tr13 and also supplies the current feed to the Zener D13 via R67. It is the stabilised voltage across D13 further smoothed by C29 that is applied to the base of Tr13—the stabilised +12V is then obtained from the emitter of Tr13.

It is also worth noting the rail filtering network (Fig. 1) (R61, C27, R60, C26) which supplies the early stages of audio amplification. It is required in order to prevent feedback snags and "glitches" from the logic which would produce clicking in the audio output.

Next Instalment

The project is concluded in Part 2, in which we shall describe the operation of the logic side of the system. The second instalment will also include the constructional drawings and details of how to set up the intercom on completion.

Practical Wireless, August 1979

Follow-up to THE **Pw** VMOS TRANSMITTER

Readers who are building the Top-Band VMOS Transmitter featured in our July issue may be interested in the arrangements made on the prototype for push-to-talk operation, via the 4-pole microphone input.

The best way of incorporating this facility would be to use a miniature changeover relay of the Siemens type and to switch the 0V to ground via the push-to-talk switch embodied in the microphone case. Where the microphone lead is supplied with separate insulated conductors for this purpose—i.e. where there is no common connection to the audio circuit—it is possible to switch the 12V supply directly. However, having regard to the possibility of a fault condition causing heavy current to flow, the best approach would still be to employ a relay for this function.

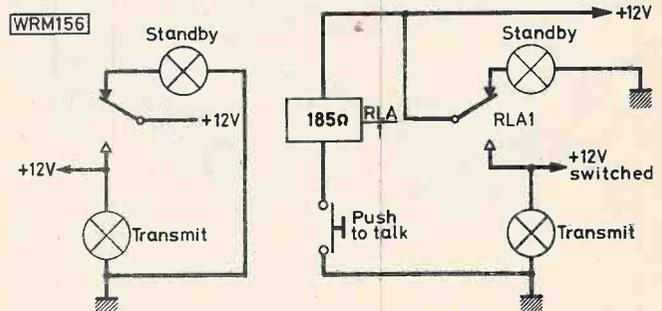


Fig. 1: (Left) Simple toggle switch wiring. Fig. 2: (Right) Wiring for p.t.t. facility using a relay

In the drawings, Fig. 1 shows the simple wiring of a toggle switch which is used to key the transmitter. If p.t.t. is required, Fig. 2 should be used as a working basis. The 4-pole socket can be any suitable type, such as a Tuchel or similar Japanese equivalent, often fitted to Trio or Yaesu transceivers and readily available as a "service spare."

**DUE TO THE RECENT INCREASE
IN VAT, READERS SHOULD
CHECK WITH ADVERTISERS
FOR CURRENT PRICES**

SPECIAL INTRODUCTORY OFFER

Logic Probe Kit


Checking out digital circuits can be very difficult especially if they are complex and operate at high speeds. The usual test gear available to the amateur is not ideal as the main interest lies in edges and pulses and changes of logic states rather than analogue signals and voltages. Hence the multi-meter and single beam scope are of little or no use in troubleshooting the problems of these circuits.

A logic probe is the answer enabling you to rapidly check the logic conditions at any point on the circuit. These probes are normally expensive but with the introduction of the CSC Logic Probe Kit LPK-1 it is now within the budget of most enthusiasts to own one of these useful tools.

Practical Wireless reviewed this kit in the July issue and found it to be easy to build and extremely useful when completed. The indication of the state of the test point is by three l.e.d.s.

The recommended retail price of the probe kit is £13.71 incl. VAT but as a special introductory offer it is available to *PW* readers for £11.75 incl. 15% VAT, postage and packing.

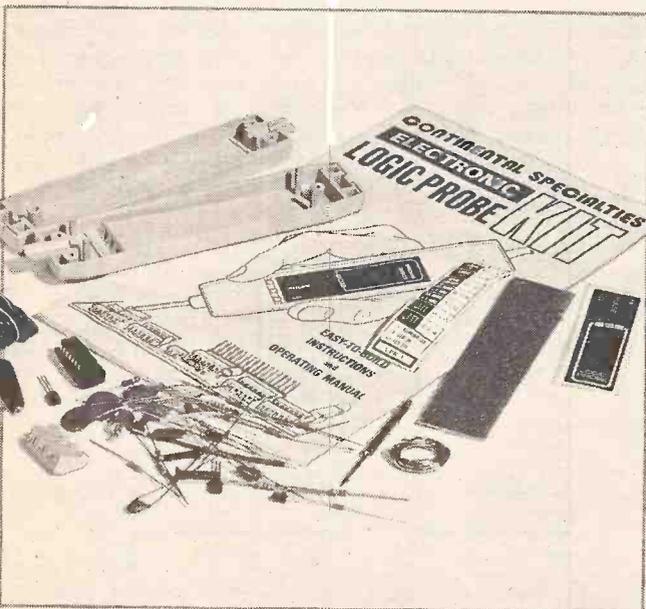Complete both parts of the coupon and send it with your remittance to "Practical Wireless", Dept PWL4, Rochester X, Kent ME99 1AA.



★ Specification

- Input impedance:** 3kΩ.
- Detectable pulse width:** 300 nanoseconds minimum.
- Threshold:** Logic '1' 0.7 Vcc.
Logic '0' 0.3 Vcc.
- Input frequency:** 1.5MHz maximum.
- Input voltage:** ±50V continuous. 120V a.c. for less than 15 seconds.
- Pulse detector:** High-speed pulse train or single events (positive or negative transitions). Active pulse stretcher 0.1 seconds.
- Power:** 5V Vcc at 30mA or 15V Vcc at 40mA. 25V maximum. Reversal protection.
- Physical size:** 147 x 25.4 x 17.8mm, weight 85 grams.
- Power leads:** 61mm with colour coded insulated clips.

HOW TO ORDER

Please complete both parts of the coupon below in **BLOCK CAPITALS**. Remittances must be by postal order or cheque (name and address on back of cheques, please) crossed, and made payable to IPC Magazines Ltd. This offer is open to readers in England, Scotland, Wales, Northern Ireland, and Channel Islands only. It is not available in Eire or Overseas. Orders are normally despatched within 28 days but please allow time for carriage. You will be notified if a longer delay may be expected.

THE CLOSING DATE OF THIS OFFER IS 26th October 1979.

**To: PRACTICAL WIRELESS,
Dept. PWL4, Rochester X, Kent ME99 1AA.**

Please send me the CSC Logic Probe Kit(s) as indicated below at £11.75 each, incl. P & P.

I enclose P.O./Cheque No. _____ Value _____

No. of kits required

Name:

Address:

Tel. No. (Home or Work)


No. required

Name:

Address:

**From: PRACTICAL WIRELESS,
Dept. PWL4, Rochester X, Kent ME99 1AA.**

_____ Cut Round Dotted Line _____

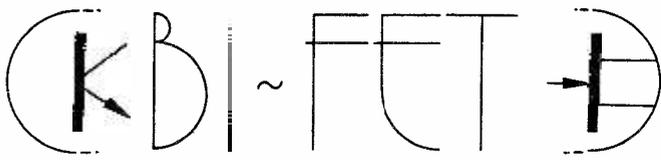

Integrated Circuits

D. F. BOWERS BSc

Although the MOSFET has made a tremendous impact upon digital i.c. design, the benefits of f.e.t.s to linear i.c.s have not been forgotten.

The junction f.e.t. is the most common device in linear applications, but until recently f.e.t.s integrated on the same chip as bipolar transistors have been noted for their unpredictable characteristics. Although monolithic devices, such as operational amplifiers, have often incorporated JFETS in their design, their use has generally been restricted to such applications as constant-current generators—as in the case of the 301 and 4136. Operational amplifiers requiring the very low input currents which JFETS can offer have usually been hybrid types, where the f.e.t.s are diffused on a separate piece of silicon, although there have been monolithic devices, such as the μ A740 and NE536, with less-than-ideal d.c. characteristics.

The development of the BI-FET process has done much to alter this situation, but before going into more detail, it is worth examining the benefits f.e.t.s can provide.

It has already been stated that the very high input impedance exhibited by the f.e.t. can reduce the input currents of operational amplifiers to mere picoamps. Additionally, the f.e.t. has a much lower transconductance than the bipolar transistor which, although poor from the d.c. characteristics aspect, makes a significant increase in speed possible. More speed can be obtained by replacing slow, lateral *pnp* transistors with *p*-channel JFETS or MOSFETS. Furthermore, f.e.t.s make excellent current sources, a feature which is fully exploited in i.c. design to improve the gain of common-emitter stages, the linearity of common-collector stages and the rejection capabilities of long-tailed pairs.

Another use of the f.e.t. is as an analogue switch—a characteristic used extensively in the design of multiplexers, chopper amplifiers and sample/hold devices. In short, the

f.e.t. makes possible many designs which would otherwise be quite impractical using bipolar transistors.

The BI-FET process, introduced in 1975 by National Semiconductor, provides a means of integrating well-matched JFETS on the same silicon chip as bipolar transistors.

A typical integrated JFET, produced by the old diffused process, is shown in Fig. 1. Here the successive doping is achieved by “soaking” the silicon wafer in vapour of the required (*p* or *n*) impurity at high temperature. As can be seen, the channel thickness of the f.e.t.—a critical factor in the determination of its ultimate characteristics—is very much dependent on the diffusion length of the gate, which is difficult to control. This situation is aggravated by the necessity to produce a very thin channel to keep the pinch-off voltage (analogous to the V_{be} of a bipolar transistor) to reasonable proportions.

Ion Implantation

To overcome this problem, the ion implantation process has been developed (see Fig. 2). With this system, the critical doping is achieved by bombarding the silicon wafers with a controlled flow of high-energy dopant ions, derived from an arrangement which is, in essence, a giant mass-spectrometer.

Ion implantation is in fact extremely useful wherever shallow doped regions need to be produced with high accuracy, and has applications outside the production of precision f.e.t.s.

The BI-FET Process

A typical *p*-channel JFET formed by the BI-FET (Bipolar compatible field-effect transistor) process is shown in Fig. 3. This type is the most common, since bipolar integrated circuits are almost always diffused on an *n*-type epi-layer, which forms part of the gate (the remainder being produced by implanting a thin *n*-type layer on top of the channel). This “sandwich” arrangement provides a very low pinch-off ($< 2V$) and the implant process ensures repeatable characteristics.

Besides the extra processing steps, the only major disadvantage of the BI-FET is that the lower gate section has an increased leakage to the substrate and isolation walls, which can be troublesome at high temperatures.

Operational amplifiers can greatly benefit from the use of f.e.t.s and there are several BI-FET op. amp. families currently on the market.

The first series of BI-FET op. amps. to be introduced was the 155/156/157 range (designated 355/356/357 for commercial applications) by National Semiconductor and shown in Fig. 4. This series featured offset drifts as low as $5\mu V$ per $^{\circ}C$ and input currents as low as $30pA$. The


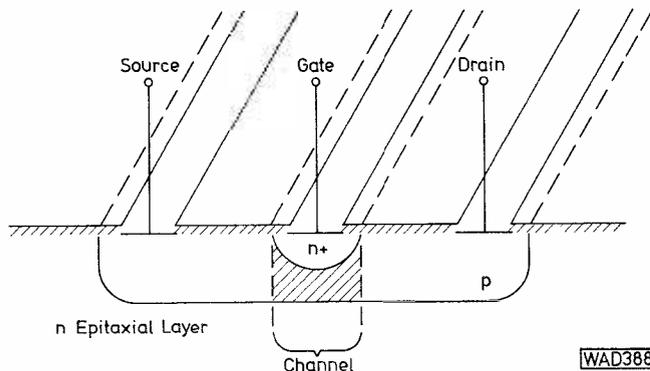


Fig. 1

Fig. 2

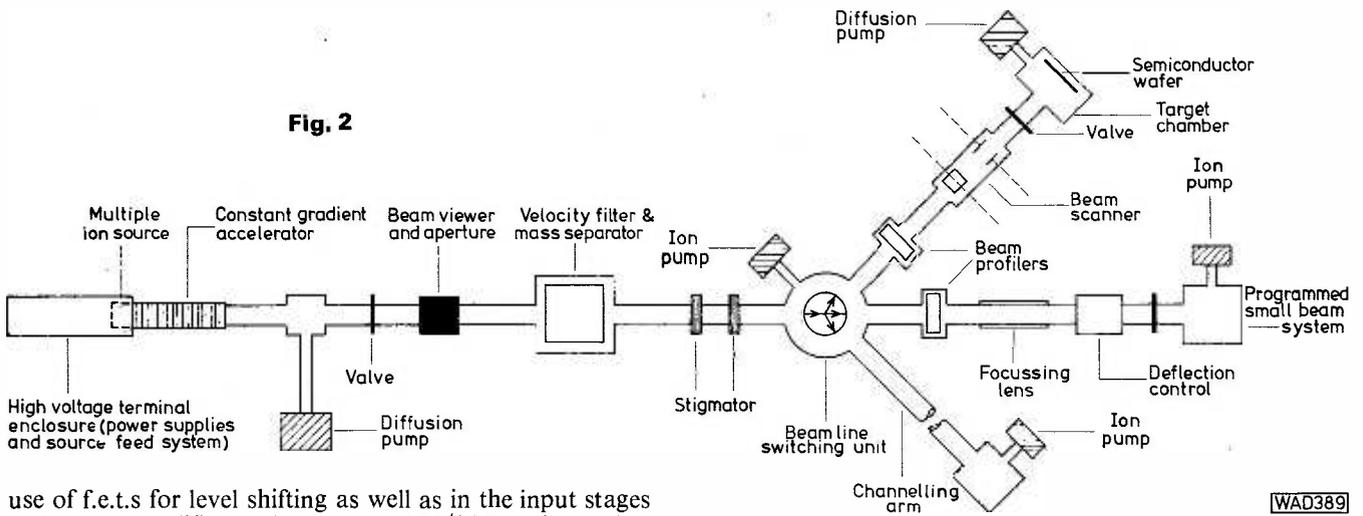

WAD389

use of f.e.t.s for level shifting as well as in the input stages makes the amplifiers quite fast, the 156/356 having a slew rate of $12V/\mu S$. The 155/355 is a low power version with lower speed and the 157/357 a high-speed compensated version.


This range is now sourced by many manufacturers, some of whom have developed their own proprietary BI-FETS. Fairchild are introducing the $\mu AF771/772/774$ series of BI-FETS and Motorola have also developed devices of their own. Texas Instruments have launched a complete BI-FET family which includes low-noise devices optimised for audio applications and National have recently introduced a new low-cost series (LF351/353/347) as well as a 741 with f.e.t. input, designated LF13741.

Progress is still continuing, but two improvements are especially worthy of attention. Despite ion implantation, BI-FET operational amplifiers still have a higher input offset voltage than bipolar types, and for precision applications at the upper end of the market, both Texas and National have developed a laser-less trimming process known as "Zener-zap", which also provides offsets of less than $0.5mV$ for use on their proprietary BI-FET series.

Another problem is that f.e.t. input currents tend to double for every $10^{\circ}C$ increase in junction temperature, a property which can prove awkward at high ambient temperatures or in cases where the internal (chip) dissipation rises steeply.

Fairchild produce devices with copper lead frames which act as efficient heat sinks to alleviate the latter problem and Precision Monolithics have developed an ingenious input-current cancellation system which employs current "mirrors" to lower input currents at high temperatures.

Fig. 4: (Below)

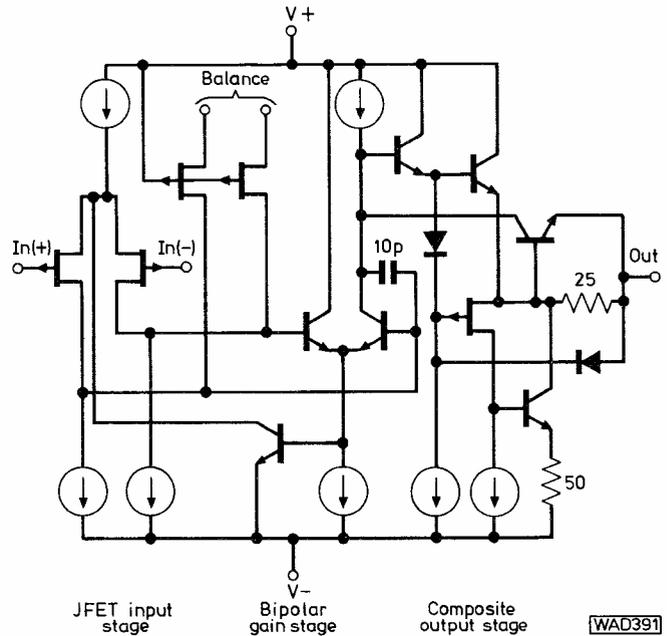


WAD391

Overall Impact

It can be seen that BI-FET operational amplifiers have been produced to satisfy all sectors of the industry, and it would appear inevitable that the low-cost devices will become readily available to the amateur. The advantages of high-speed, low-noise and low input currents make them eminently suitable for most general-purpose applications. It must be made clear, however, that with the larger chip area and new technology, BI-FETS will not be as cheap as 741s!

The BI-FET technology is by no means confined to the production of operational amplifiers; devices such as comparators, instrumentation amplifiers and sample-and-hold circuits have all been produced. Analogue switches are also in production and have several advantages over conventional m.o.s. types, including lower "on" resistance and freedom from static discharge problems.

It seems certain that an increasing proportion of the linear i.c. market will ultimately be claimed by BI-FETS—a view which is obviously held by the manufacturers, who are investing quite heavily in BI-FET production.

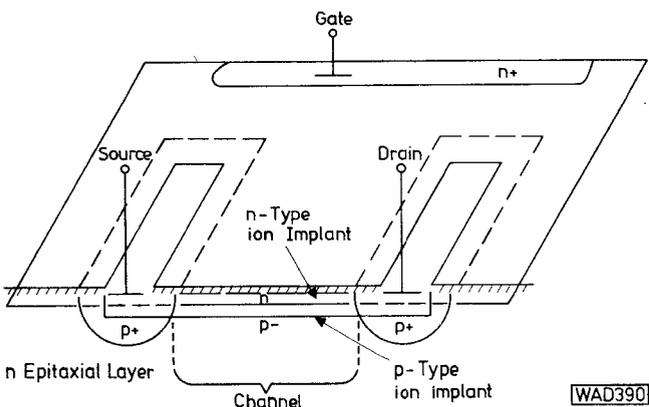

WAD390

Fig. 3



SOUTH MIDLANDS COMMUNICATIONS LTD.

OSBORNE ROAD, TOTTON
SOUTHAMPTON SO4 4DN

Cables: Aerial Southampton
Telex: 477351 SMMCOMM G
Tel: Totton (0703 86) 7333



21 YEARS OF PROFESSIONAL EXPERIENCE

Main importers of Yaesu Musen Communications Products
"2 Year Guarantee – Free Securicor Delivery"

THE FRG7

Synthesised General Coverage Communications Receiver.




The FRG7 is solid state mains and 12v. receiver offering continuous coverage 0.5-30 MHz with specifications unparalleled in its price range.

Its advanced circuitry provides superb performance either as a standby receiver or for SWL's (Broadcast and Amateur Bands alike)

PRICE: FRG7 £210.37 (Carr. Foc.) Analogue
FRG7D £270.00 (Carr. Foc.) SMC Digital
AS REVIEWED IN THIS ISSUE

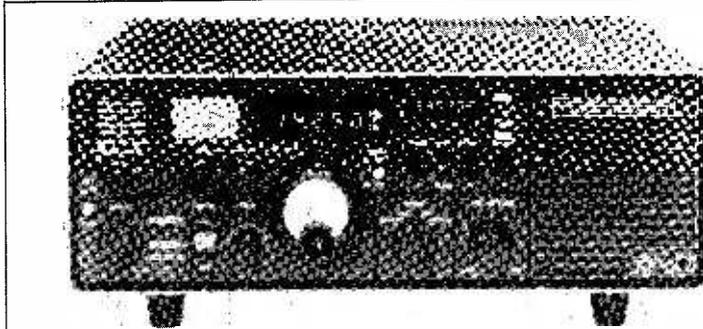SMC YOUR SINGLE STOP SOURCE FOR: TRANSCEIVERS, RECEIVERS – HF, VHF AND UHF. ANTENNAS AND ROTATORS CABLE – CONNECTORS – TOWERS – MASTS AND FITTINGS



FRG7000 COMMUNICATIONS RECEIVER

THE FRG7000 IS A HIGH PERFORMANCE ALL SOLID STATE COMMUNICATIONS RECEIVER DESIGNED TO COVER THE ENTIRE HIGH FREQUENCY SPECTRUM OF 0.25 TO 30MHz. WITH BRIGHT 7 SEGMENT LED'S PROVIDING DIGITAL READOUT TO 1kHz. Also included is a 24-hour digital clock for both local and GMT time, with a timing feature for automatic receiver (and/or tape recorder through rear panel relay contacts) on/off switching.

The Barlow Wadley loop (Triple conversion Superhetrodyne) system used, proffers extremely stable (better than 500Hz/hr. A.W.U.) performance. Ceramic IF filters with a 6dB bandwidth of 3kHz for SSB & CW (8kHz at 50dB) and 6kHz bandwidth for AM (14kHz at 50dB) provide optimum intelligibility coupled with good rejection of interference.

The Mosfet RF amplifier offers an outstanding sensitivity of 0.7µV for 10dB S/N on SSB and 2µV for 10dB S/N on AM, without sacrificing strong signal performance. Wide provisions are made for antenna connections: for MW broadcast (0.25-1.6MHz) a high impedance binding post, for 1.6-30MHz a SO239 socket (to take a 50-75 ohm unbalanced coaxial feed) plus binding post (for random low impedance length SW antenna). Also the antenna terminal strip is the earth and a mute (earth for standby) connector.

Audio output of up to 2 Watts drives the internal speaker, but plugging in an external 4 ohm unit or headphones (¼" Jack) disables this. A socket for tape recording produces about 50mV independent of the volume control setting. A built-in mains power supply allows operations from 100/110/117/220/230V AC (50 or 60Hz).

To reduce the power consumption (of 25W) the front panel lamps and displays may be extinguished.

For high reliability FET's and IC's are used extensively throughout the receiver providing maximum performance within a compact cabinet (36(w), 12.5(h), 20.5(d) and 7Kg.). For ease of service plug in boards are employed widely.

A switchable RF attenuator, AM noise limiter and amplified AGC, assist in reception under adverse conditions of strong adjacent signals, impulse noise and deep signal fading. The continuously variable audio filter minimises the high or low audio responses as required, and a fine Tune (0.2-5kHz) allows easy zeroing of a desired station.

Frequency readout is taken directly from the digital display. The first two digits are controlled by the "MHz set" oscillator, the remaining three by the VFO (both via a CPU). The receiver front end is a narrow band with preselector and rangeswitch colour coded for ease of use, to provide the maximum in sensitivity and rejection of out of band signals.

Accessories included are the handbook, plugs (for every socket in the receiver) and 3 and 10m wire antennas.

PRICE: £367.87

G3ZUL Brian Stourbridge (03843) 5917
GM3ZBE Alex Aberdeen (065183) 328

GMBGEC Jack Edinburgh (031665) 2420
G13WVY Mervyn Tandragee (0762) 84056

GW3TMP Howarth Pontybodkin (035287) 846/324
GW4GSW Alan Swansea (0792) 24140

Send all mail orders direct to H.Q. (in Totton).

S.M.C (Jack Tweedy) LTD
Roger Baines, G3YBO
79 Chatsworth Road,
Chesterfield, Derbyshire
Chesterfield (0246) 34982
9-6: Tuesday-Saturday

NORTHERN (Leeds) BRANCH
Colin Thomas G3PSM
257 Otley Road,
Leeds 16, Yorkshire.
Leeds (0532) 782326
9-5: Mon-Wed & Fri-Sat.



S.M.C. (Jack Tweedy) LTD
Jack Tweedy, G3ZY
Ham Shack, 150 Hornecastle Road,
Woodhall Spa, Lincolnshire
Woodhall Spa (0626) 52793
9-5: Tuesday-Sat (+ appointments)



STOP! ... THIS IS WHERE SHORT WAVE LISTENING BEGINS

THE SHOP THAT SPECIALISES IN HAM RADIO

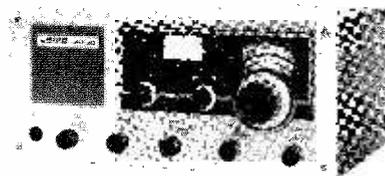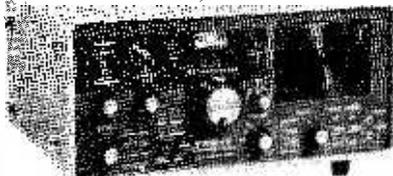RECEIVERS - TRANSMITTERS
TRANSCEIVERS - HF - VHF - UHF



£210 inc. VAT

FREE SECURICOR DELIVERY

£175 inc. VAT

This month we present to you two excellent short wave receivers that give you top value for money. Last month we mentioned how the FRG7 was the perfect receiver for both the beginner and experienced listener or radio amateur alike. And, of course, our many hundreds of satisfied customers know that we have a special test schedule that every receiver has to pass before it is despatched to its proud new owner.

We can now tell you that we are stocking the latest version of the Lowe SRX30 receiver. Now this receiver is very similar in many respects to the FRG7. In fact, electrically, there's not a great deal of difference between the two receivers. In other words, the ability of the SRX30 to pull the stations in is every bit as good as the FRG7. But there is a difference and only you, the potential purchaser, can judge which model is for you.

The SRX30 is definitely not so pretty as the FRG7 and lacks the nice looks of the latter. Obviously, the manufacturers have spent less money on the front panel design and this is reflected in the price. Also, mechanically it has less of a solid feel to it. But, whichever model you choose, you'll not be disappointed. Both have passed our stringent pre-delivery tests and, yes, a few of both models do fail. So if you really want to be sure that your receiver is performing at its best, buy from us - all our staff are amateur radio enthusiasts and will ensure that the receiver you select is working as well as the one they themselves would wish to own.

AERIALS? Forget those magic 6ft. long wonder poles! The best general coverage aerial is a length of wire as long as possible. For better performance try the Mosley RD5. It covers all short wave amateur bands and is fed with coaxial cable for really low noise reception. Length is 69ft and functions as a true dipole.

WATERS & STANTON ELECTRONICS

31, SPA ROAD, HOCKLEY, ESSEX. TEL: HOCKLEY (03704) 6835

Opening hours MON-SAT 9.00 a.m.-5.30 p.m. E.C. Wed 1.00 p.m.



Opposite South Harrow
Tube and Bus Stations

AMCOMM SERVICES

194A Northolt Road
South Harrow, Middx.
London. Tel: 01-864 1166

**General Coverage
Communications Receiver
FRG-7**



● 0.5-29.9MHz Coverage with 10kHz Readout
The FRG-7 is a precision-built all-purpose communications receiver featuring all solid state construction for long life and high performance. Utilizing the Wadley Loop drift cancellation system, in conjunction with a triple conversion super-heterodyne circuit, the FRG-7 boasts high sensitivity along with excellent stability. It provides broadcast listeners with such features as a 3-position tone selector, an RF attenuator, and an automatic noise suppression circuit. For many years of satisfying reception, the FRG-7 is the receiver for you.

Free Delivery Securicor

£210.00

FIT A DIGITAL DISPLAY TO YOUR FRG7 OR SRX30.

These units come complete, with only three wires to connect. The FDU7 for the Yeasu FRG7 can be fitted in place of the KHz dial, or can be supplied for external use. (Please state when ordering)
The FDU3 for the SRX30 is supplied for top of the set use only.

(Full Fitting Instructions are supplied.)

(FDU7) for FRG7
(FDU3) for SRX30

@ £44.77
@ £44.77

We also manufacture an R.T.T.Y. Converter.
The MB6R (Receive only) and the MB6R/T (Receive/Transmit).
We supply these units with single or double current loops for connection to teleprinter To Order.
T.T.L./C-MOS Logic Levels and Oscilloscope Outputs are provided. Dimensions (84X304X210).

(MB6R Double or single current) @ 77.96
(MB6R/T Double or single current) @ £83.25

(All Units are fully Guaranteed, and come complete)

(No extras needed)

(All prices inclusive of postage and V.A.T.)
(Payment by P.O., Cheque or Access)

**B. BROOKES ELECTRONICS, 69 Leicester Street,
NORWICH NR2 2DZ, ENGLAND.
Tel: 0603-24573.**

STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA

ENGLAND

Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers—transceivers. Mobile equipment pre-selectors—filters—antennas. Stabilised power supplies from 2 to 20 Amp. Antenna switches—converters. Aluminium masts—clamps. Antenna rotators.

Yaesu
FRG7-FRG7000

Drake
SSR-1 * SPR4 * R4C *

Secondhand Equipment

Our secondhand equipment stock changes daily. Send S.A.E. for latest price list. Part exchanges welcome.
Access-Barclaycard and H.P. facilities.

TRIO

R-300-R820S

Lowe SRX30 Receiver

Antenna Multituners

Designed and manufactured by ourselves.
Over 1000 sold in over 50 countries.

Mk2 covers 550 Khz 30Mhz
Prices include VAT and postage.

£25.00

THE 'TRENT' 150W BROADBAND R.F. LINEAR AMPLIFIER PART TWO

The following data is a resumé of the basic design considerations involved in the early stages of the "Trent" amplifier.

Input Voltage Transformation Ratio

Typical values are given in Table 1, obtained from the expression $Z_{in} = R + jX(\Omega)$

In order to achieve a good match at high frequency, Z_{in} is considered at 25MHz. The *real* part at this frequency is 1.5Ω , which means that for a push-pull configuration it is 3Ω between the two transistor bases.

The voltage transformation ratio is determined by

$$n = \sqrt{\frac{50}{3}} \approx 4$$

$$n_{in} = 4$$

Output Voltage Transformation Ratio

The transistor equivalent output circuit is given in Fig. 10. With $C_c \approx 270\text{pF}$

$$R_c = \frac{(V_{cc} - V_{sat})^2}{2P_o}$$

where V_{cc} is the collector voltage = 13.5V
 V_{sat} = r.f. saturation voltage = 1.0V
 P_o = output power for one transistor (75W)
 $R_c = 1.1\Omega$

The output transformer matches $2 \times Z_{out}$ to 50Ω for the push-pull configuration. The voltage transformation ratio is defined by

$$n = \sqrt{\frac{50}{2.2}} = 4.7 \approx 5$$

In fact, it was discovered empirically that the best ratio is $n = 4$.

Transformer Types

Since the input and output transformation ratios are 4, we can use the small, practical transformer shown in Fig. 8 (Part 1). The low impedance winding always consists of one turn, which limits the available impedance transformation ratio to 1, 4, 9.

Transformer Volume Estimation

Output Transformer

The ferrite used is 4C6 material, manufactured by R.T.C., whose reference is 14/9/5 — 4C6 4322.020.97.180. The relative permeability is $120 \pm 20\%$, and dimensions are shown in Fig. 11.

Table 1

$Z_{in} = R + jX (\Omega)$ Typical values

WAD381

F (MHz)	2	5	10	15	20	25	30
R (Ω)	15	8	5	3	2	1.5	1.2
X (Ω)	-8	-11	-7.5	-5	-4	-3.5	-3

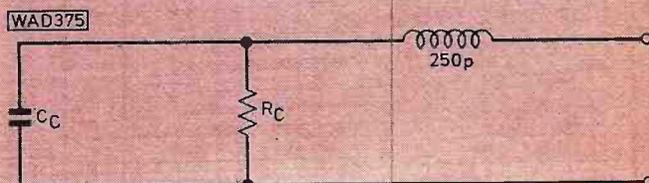


Fig. 10: Transistor equivalent output circuit

The primary inductance can be calculated from the following formula

$$L_p = \mu_o \mu_r n^2 \frac{S}{l} \dots\dots\dots \text{Eq. 1}$$

where L_p is the inductance in henries

$$\mu_o = 4\pi 10^{-7}$$

μ_r is the relative permeability

S is the ferrite cross-section (m^2)

l is the average length of lines of force (m)

n is the number of turns

The value of L_p must be chosen high, but not higher than necessary, otherwise the performance at the top end of the band will be degraded.

So, we take

$$2\pi L_p F_{min} \approx 3R$$

in which R = load impedance (50Ω)

$$F_{min} = 2\text{MHz}$$


$$L_p = \frac{150}{2\pi \cdot 2 \cdot 10^6} = 12\mu\text{H}$$

The ferrite cross-section is:

$$S = N l \frac{D-d}{2}$$

in which N is the number of toroids
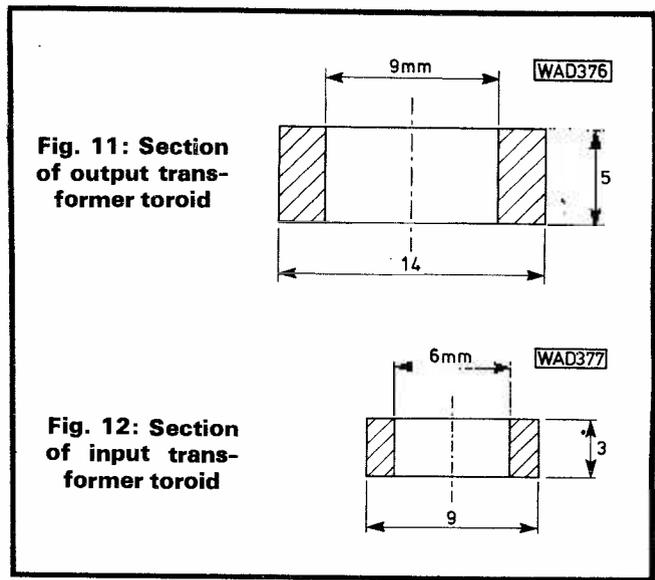
$$S = N \cdot 5 \cdot 10^{-3} \cdot 2.5 \cdot 10^{-3} = 1.25 \cdot 10^{-5} N \text{ (m}^2\text{)}$$



From Eq. 1 we can calculate N :

$$N = \frac{L_p l}{\mu_o \mu_r n^2 \cdot 1.25 \cdot 10^{-5}}$$

$$= \frac{12 \cdot 10^{-6} \cdot 36.1 \cdot 10^{-3}}{4\pi \cdot 10^{-7} \cdot 120 \cdot 16 \cdot 12.5 \cdot 10^{-5}}$$

$$N \approx 14 \text{ toroids.}$$

In fact, 16 cores are used, which give

$$L_p = 13.7\mu\text{H} \text{ and } S = 2 \cdot 10^{-4} \text{ (m}^2\text{)}$$

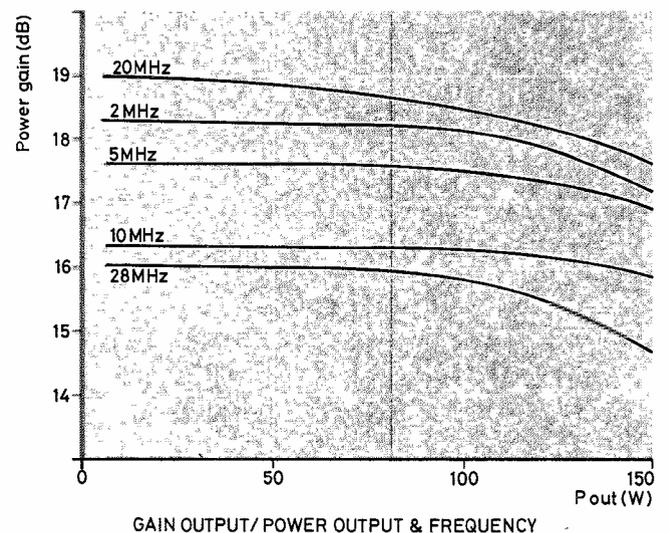
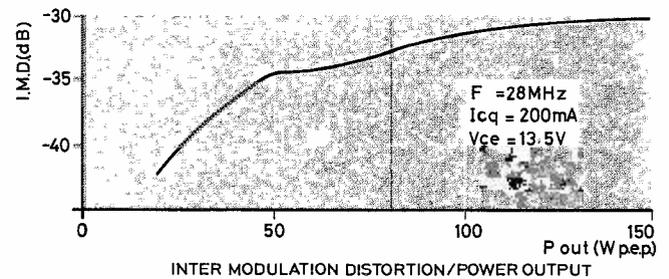
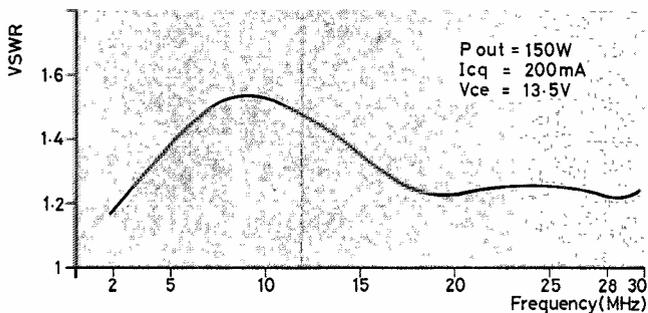
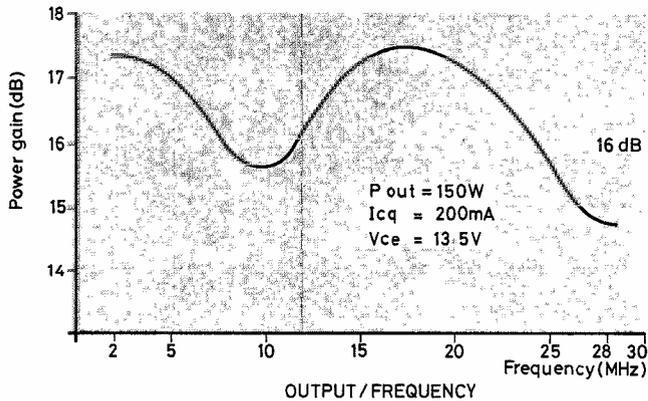


Fig. 13: Typical performance characteristics of the PW "Trent" prototypes

The highest toroid losses occur in this case at 2MHz under large-signal conditions. The power loss density, i.e., the power loss related to the unit of volume versus the maximum induction and the frequency, is given by R.T.C. in their relevant data. The maximum induction \hat{B} can be calculated with the following formula:

$$\hat{B} = \frac{\hat{V}}{2\pi F S n} \dots \text{Eq. 2}$$

in which \hat{B} = maximum induction (T)
 S = ferrite cross-section (m²)
 n = number of turns
 \hat{V} = max. value of voltage across n turns (V)
 F = frequency

\hat{V} is given by:

$$V = \sqrt{2P_o R_L} \dots \text{Eq. 3}$$

where P_o is the output power
 $R_L = 50\Omega$

$$\hat{V} = \sqrt{2 \cdot 150 \cdot 50} = 122.5V$$

$$\hat{B} = \frac{122.5}{2\pi \cdot 10^6 \cdot 2 \cdot 10^{-4}} = 1.2 \cdot 10^{-2} T$$

For $\hat{B} = 12mT$ and $F = 2MHz$ the power loss density is $2 \cdot 10^2 mW/cm^3$.

The ferrite volume is:

$$\begin{aligned} \hat{V} &= \frac{\pi}{4} (D^2 - d^2) h N \\ &= \frac{\pi}{4} (14^2 - 9^2) 5 \cdot 16 \cdot 10^{-3} \\ &= 7.2 cm^3 \end{aligned}$$

This gives a loss α :

$$\alpha = 2 \cdot 10^2 \cdot 7.2 = 1440mW \text{ or } \frac{1.4}{150} = 1\%$$

This 0.05dB loss in the ferrite is quite acceptable.

Input Transformer

The ferrite used for the input transformer is 4C6 material by R.T.C., whose reference is Tore 9/6/3 — 4C6 4322.020.97170. Its relative permeability is $120 \pm 20\%$.

The toroid dimensions are given in Fig. 12. In order to contain these, a transformer with a primary inductance at 2MHz of:

$$2\pi L_p F_{min} \simeq R_s \dots \text{Eq. 4}$$

where $R_s = 50\Omega$

is used. This inductance is compensated at low frequencies by the circuit of Fig. 14, and Fig. 15 is the Smith chart.

From Eq. 4:

$$L_p \simeq \frac{50}{2\pi \cdot 10^6} = 4\mu H$$

The ferrite cross-section S is:

$$\begin{aligned} S &= N \frac{D-d}{2} h \\ &= N \cdot 1.5 \cdot 10^{-3} \cdot 3 \cdot 10^{-3} \\ &= 4.5N \cdot 10^{-6} (m^2) \end{aligned}$$

where N is the number of toroids.

The average length of the line of force l is:

$$\begin{aligned} l &= \pi \frac{D+d}{2} \\ &= \pi \cdot 7.5 \cdot 10^{-3} \\ &= 23.6 \cdot 10^{-3} (m) \end{aligned}$$


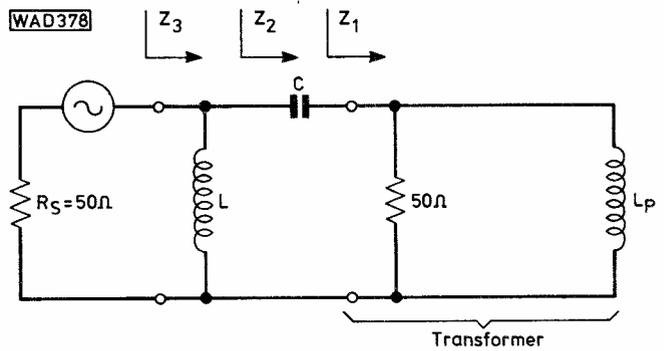


Fig. 14: Low-frequency compensation circuit for input transformer inductance

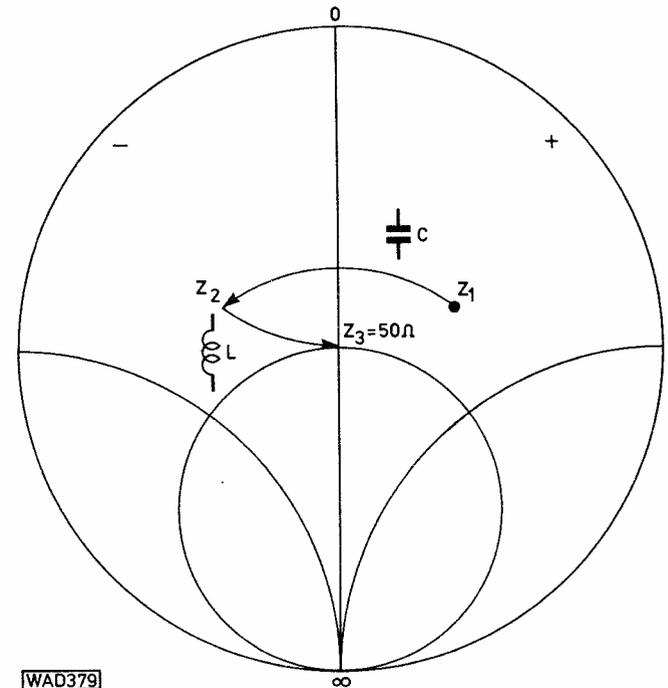

WAD379

Fig. 15: Smith Chart plot for the circuit of Fig. 14

N may be calculated from Eq. 1:

$$\begin{aligned} N &= \pi \frac{L_p l}{\mu_o \mu_r n^2 \cdot 4.5 \cdot 10^{-6}} \\ &= \frac{4 \cdot 10^{-6} \cdot 23.6 \cdot 10^{-3}}{4\pi \cdot 10^{-7} \cdot 120 \cdot 16 \cdot 4.5 \cdot 10^{-6}} \\ N &= 8.7 \simeq 9 \end{aligned}$$

In fact, we used $N = 10$ toroids, which means $L_p = 4.6\mu H$.

By using the same reasoning and formula as for the output transformer:

$$P_{in} \simeq 3W @ 2MHz$$

$$\hat{V} \sqrt{2P_{in} R} = \sqrt{2 \cdot 3 \cdot 50} = 17.3V$$

$$\hat{B} = \frac{\hat{V}}{2\pi FS_n}$$

$$= \frac{17.3}{2\pi \cdot 10^6 \cdot 4.5 \cdot 10^{-5} \cdot 4}$$

$$= 7.6 \cdot 10^{-3} \text{ T}$$

For $\hat{B} = 8\text{mT}$ and $F = 2\text{MHz}$ the power loss density is $70\text{mW}\cdot\text{cm}^{-3}$.

The ferrite volume is:

$$V = \frac{\pi}{4} (D^2 - d^2)hN$$

$$= \frac{\pi}{4} (9^2 - 6^2)3 \cdot 10 \cdot 10^{-3}$$

$$= 1\text{cm}^3$$

This gives a loss \propto :

$$\propto = 70 \times 1 = 70\text{mW} \text{ or } \frac{70}{3000} = 2.3\%$$

This 0.1dB loss in the ferrite is acceptable.

Modifications

For those interested in a more sophisticated biasing arrangement for the amplifier, the circuit of Fig. 16 may provide a working basis. This produces a lower internal resistance than that originally shown.

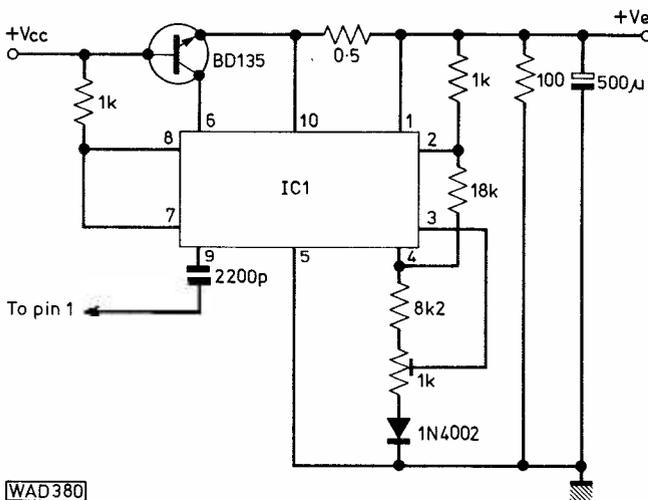


Fig. 16: Alternative biasing circuit offering a lower internal resistance. IC1 is a 723 voltage regulator. The diode should be mounted in the same manner as shown for D2 in Figs. 5 and 7 (Part 1). All resistors can be ½ watt rating

Changing the relative permeability of the input transformer ferrites (to, say, 400) will give a better balance with regard to the signal applied to the transistors. Devices are available (with a μ_r of 400) from the supplier quoted in the components list in Part 1, and are of Ceramic Magnetics manufacture.

★ components

Resistors

½W ±5%

1kΩ	3	R5, 11, 12
2.2kΩ	3	R3, 4, 9
4.7kΩ	1	R8
33kΩ	1	R10
56kΩ	1	R7
100kΩ	2	R2, 6
180kΩ	1	R1

Potentiometers

1MΩ	1	VR1 <i>Min. skeleton preset</i>
-----	---	---------------------------------

Capacitors

Electrolytic axial lead

330µF 10V	1	C3
470µF 10V	1	C1

Tantalum bead

4.7µF 16V	1	C5
25µF 16V	1	C2

Disc ceramic

10nF	1	C4
------	---	----

Semiconductors

Transistors

BC107	2	Tr3, 4
BC109	2	Tr1, 2
BC157	1	Tr5

Miscellaneous


Case Verobox 221 (125 x 65 x 30mm). Miniature toggle switch s.p. 3-5mm jack and plug. 2mm plug and socket (2). Battery clip for PP3. Reed relay d.i.l. 5V s.p. (RS349-383 or similar), p.c.b. Crystal microphone insert.

It now remains to set VR1 so that the system actuates on the sound of the telephone bell. Persuade a co-operative friend to dial your number and when the bell rings, adjust VR1 so that the relay closes and opens at the start and end of each ring. Leave VR1 at the minimum position where this happens as this will reduce the battery drain on signal and also make the system less susceptible to extraneous sounds.

Other Applications

I believe that individual experimenters will find other applications for this type of system to deal with individual domestic problems; one other that I have found useful is to relay the warning buzzer on the electric cooker—which is scarcely audible outside the kitchen—to the lounge so that it is possible to sit in relaxed comfort, confident that the small lamp beside you will tell you when the cooker needs attention. For people who are hard of hearing the possibilities are considerable.

These other applications often involve much less intense sounds than the phone bell and it is seldom possible to fix the microphone so close to the sound source: for this reason gain will be required. It will be noticed that in the phone bell application, Tr1 contributes no gain at all as its emitter resistor is not by-passed; in fact it serves to raise the impedance to approach that of the microphone and makes the setting of VR1 less critical: to obtain extra gain for special applications it is only necessary to connect about 250µF across Tr1 emitter resistor. Connected this way, I found it quite easy to make the indicator lamp follow the ticking of the kitchen clock!

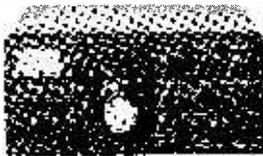

R820

The ultimate in receiver design. Trio R820. With more features than ever before available in a ham band receiver. This triple-conversion (8-83 MHz, 455 KHz and 50 KHz I.F.s.) receiver, covering all amateur bands from 160 through 10 metres, as well as several short wave broadcast bands, features digital and analog frequency readouts, notch filter, I.F. shift, variable bandwidth tuning, sharp I.F. filters, noise blanker, stepped R.F. attenuator, 25 KHz calibrator, and many other features providing more operating conveniences than any other ham band receiver. Price £790.00, including V.A.T. Carriage £3.50.

SP820

Matching speaker to fit the R820, with built-in filters, 8 ohms impedance. Price £39.00, including V.A.T. Carriage £1.16.

SRX30

The SRX-30 represents a new step forward for the keen short wave listener or the radio amateur who needs to tune frequencies outside the amateur bands.


In the past, the performance of general coverage receivers has been limited by the difficulty inherent in setting to a known frequency - OK, so you know that Radio Peking is on 8547 KHz but how do you set the receiver dial?

The SRX-30, due to application of new technology solves the problem by utilising a drift cancelling loop system converting to a very high (40 MHz) first IF so as to remove image interference problems. This is followed by a stable VFO controlled tunable second IF with excellent selectivity. The frequency range covered by the SRX-30 is 500 KHz - 30 MHz in thirty bands, each 1 MHz wide. If you wish to tune to say 14250 KHz, simply set the MHz dial to 14, the KHz dial to 250 and there you are, no fuss, no twiddling, no need to use calibrators, etc. (remember the drift cancelling system).

The SRX-30 is housed in a rugged metal case and operates from 240V ac mains or 12V dc supply. Reception modes are USB/LSB/AM/CW to cater for all HF operation and the receiver is equally at home on VHF using an external converter.

This receiver combines small size, accurate readout, ease of use, all mode operation, mains/battery power supply and excellent performance at a remarkably low price. See it, use it and you will like it.

Price £178.00 including V.A.T. Carriage £3.50.

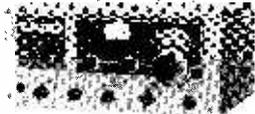

FS10

The FS10 VHF FM monitor receiver is a high performance unit in such a small lightweight package that it will fit into a pocket. The receiver is available in two versions, to cover 70-80 MHz or 130-170 MHz and is therefore suitable for all amateur radio, marine radio or business radio use.

The FS10 automatically scans up to ten crystal controlled channels, stopping on any channel where a signal is present. Manual selection of any channel is also provided. Complete with rechargeable battery pack, charger and personal earphone with provision for external antenna.

Price £82.00, including V.A.T., crystals extra. (Fitted ten channels £107.25, including V.A.T.) Carriage 86p.



AMR217B

The AMR217B VHF FM monitor is an outstanding receiver suitable for either the 2 metre amateur band or the VHF marine FM band and can be supplied for either band on request. The AMR217B has an eight channel scanning facility and can also accommodate up to ten additional switched channels to extend its versatility even further. The receiver is extremely sensitive and is one of the best monitor receivers available to either the amateur or professional user. It is completely self-contained with a built-in speaker and operates from 240V AC mains or 12V DC supplies. A matching mobile mount is supplied to allow easy installation in boat or car.

Price £120.75, including V.A.T. (fitted 8 crystals), Carriage £1.06.



SR9

The SR9 represents the finest value for money ever offered in the FM monitor receiver market. Available in two versions to suit the 2 metre amateur band or the VHF marine FM band the SR9 gives fully tunable coverage of either band and

also incorporates the facility for installing optional crystals which will provide up to eleven fixed channels for the most popular frequencies. The SR9 is completely self-contained with built-in speaker and requires only 12V DC at around 200 mA to operate. Mounting hardware is provided for easy installation anywhere.

Price £46.00, including V.A.T. Carriage 86p.



AP12

The AP12 is a 12 channel crystal controlled airband monitor receiver covering a frequency range from 108 to 136 MHz which utilises a micro-computer which automatically peaks the R.F. oscillator and mixer stages in accordance with the crystal frequency in use. This means that you can install crystals for any frequency in the entire band without any drop in performance. Supplied complete with rechargeable battery pack, charger and personal earphone. Price £89.70, including V.A.T. Fitted 12 channels: £118.45, including V.A.T. Carriage 86p.



R512

The R512 airband receiver is a high performance unit which automatically scans up to eight crystal controlled channels. The receiver will stop on any channel on which there is a transmission, stepping on again at the end of transmission. You may lock the receiver onto any channel of your choice for continuous monitoring and if any channel should be more or less permanently occupied you may also lock out the channel to permit scanning of other channels. These facilities are available on any or all channels.

Covering the full band from 108-136 MHz, the R512 is completely self-contained including built-in speaker and is supplied with mains and 12V DC power leads, whip antenna, mobile mounting bracket and personal earphone. Price including five fitted channels is £138.00, including V.A.T. Carriage £1.06.



PET
FULL RANGE OF
COMPUTERS AND
PERIPHERALS.
NEW 16K IN
STOCK.

For all that's good in Amateur Radio, contact;
LOWE ELECTRONICS LTD., 119 Cavendish Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817.
For full catalogue, simply send 45p in stamps and request catalogue CPW.



IF YOU ARE INTERESTED IN
AMATEUR RADIO

AND LIVE IN OR NEAR KENT
WHY NOT COME AND VISIT US
(or Phone us for a copy of our Catalogue)

WE STOCK

TRANSCEIVERS **POCKET RECEIVERS**
BOOKS **RECEIVERS** **POWER SUPPLIES**
ROTATORS **AERIALS**

FOR

AMATEUR, MARINE & PRIVATE MOBILE RADIO

THANET ELECTRONICS


143 RECLVER ROAD, HERNE BAY, KENT

Tel: (02273) 63859

Telex: 965179

Western

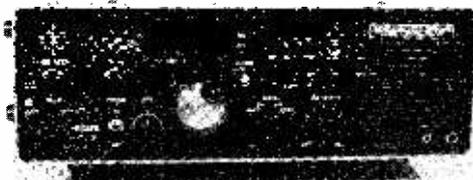THE COMMUNICATIONS SPECIALISTS
EVERYTHING FOR THE RADIO AMATEUR



YAESU FRG-7000

£349

The New Performance Standard in Communications receivers!

A high quality general coverage receiver for the discerning SWL and a worthwhile addition as a second receiver for the transmitting amateur.

How often have you wanted a true general coverage receiver of this calibre but been put off by the price.

The FRG-7000 is a cost-effective answer to your prayers.

★ Full and continuous coverage 250kHz to 29.999MHz ★ Operation on SSB/AM/CW ★ Switched selectivity and fine tune control for maximum efficiency on SSB ★ Accurate digital frequency readout to 1kHz, using advanced CPU techniques ★ Built-in digital clock with facilities for setting two time zones (GMT and local), selected at the flick of a switch ★ CPU controlled timing clock switches receiver on or off at preselected times; also enables control of external unit such as tape recorder ★ Wadley loop circuitry for minimum drift and maximum stability ★ Simple and accurate frequency selection: easy-to-use colour coded bandswitch and preselector.

Send large SAE for further details of this and other equipment - or use our Answerphone after hours.

Western Electronics (UK) Ltd

HEAD OFFICE (All Mail/Enquiries)

FAIRFIELD ESTATE

LOUTH, LINCS, LN11 0JH

Tel: Louth (0507) 604955/6/7

ACCESS
VISA
DINERS CLUB
H.P.

RADIO

**SPECIAL
PRODUCT
REPORT**



**LOWE
ELECTRONICS
LTD.**

SRX-30 GENERAL COVERAGE RECEIVER




The Lowe SRX-30 is a general coverage receiver, principally for the serious short-wave listener and covers the range 500kHz to 30MHz.

A variety of "on-air" tests were made with this equipment using both long wire and beam aerials and in all respects, save perhaps the actual audio quality it performed well. Selectivity was quite adequate in all but the most difficult cases of crowding and the overall stability of the receiver was particularly good.

In conjunction with a Trio transmitter, many contacts were made with W, VK and several of the more exotic countries and the SRX-30 gave a good account of itself throughout—lacking only in bandspread, of course, which is to be expected in most receivers of this type.

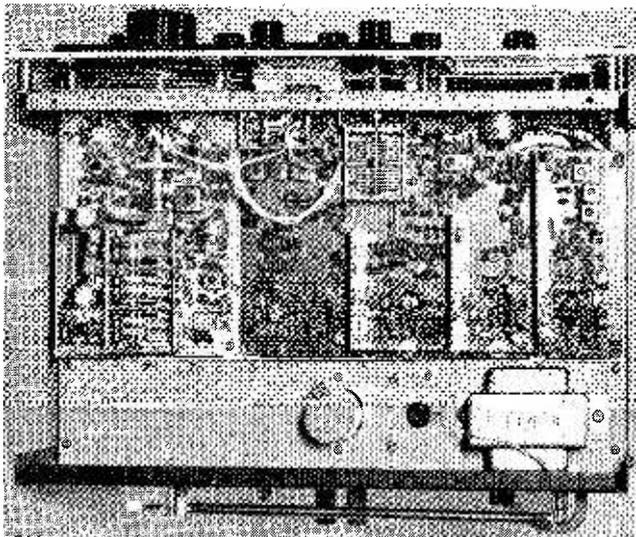Several converters were tried with the receiver, and here some little difficulty was experienced. It is not possible to disconnect the telescopic aerial fitted to the receiver, unless one is prepared to get inside and unsolder it, and this can,



under strong-signal conditions, cause breakthrough of 10m signals. The aerial input arrangements too may cause some problems if outboard converters are to be used and a simple solution would be to fit an SO239 coaxial socket and detach the fixed telescopic aerial altogether.

The controls of the SRX-30 are all mounted on the front panel and are widely spaced ensuring that even the largest hands do not get tangled up. The tuning unit is mounted on the front panel at the top right and has the pre-selector, MHz tune and kHz tune controls with the concentric tuning scales visible through the window above the kHz knob. The dials are illuminated and were easy to read, the MHz dial being calibrated into distinct separate 1MHz bands while the kHz dial is calibrated from 000 to 1000 in steps of 10. The kHz control is operated via a 6:1 slow motion drive which proved to be smooth in action. This made the tuning of the set relatively easy and it was possible to return to a frequency, even after an appreciable time, without any great difficulty.

Like most modern communications receivers the SRX-30 uses the Wadley Loop triple-conversion superheterodyne system which was fully described in the July issue of *Practical Wireless*. The front end of this receiver was remarkably stable, making tuning a pleasure.

The pre-selector was also simple to operate with no dials or drums to worry about, the knob being merely turned until maximum signal is found. An r.f. attenuator control is fitted which provides some 30dB of attenuation in the fully clockwise position.

A clear S meter, illuminated when the supply is on, is mounted next to the tuning dial and proved easy to read.

The Clarify control, calibrated from -5 to +5 gives fine tuning over a frequency range of ± 3 kHz to enable the pitch of a station operating on s.s.b. or c.w. to be accurately set.

The audio side of this receiver is a bit of a let-down and certainly did not match the rest of the set. Using the small internal speaker was a disappointment, the quality of reproduction being poor. This is probably a function of the speaker used and its mounting in the metal cabinet, as, using an

THE CHOICE IS YOURS!



YAESU MUSEN General Coverage Communications Receiver FRG-7



£182.75 PLUS VAT

● **0.5-29.9MHz Coverage with 10kHz Readout**

The FRG-7 is a precision-built all-purpose communications receiver, featuring all solid state construction for long life and high performance. Utilizing the Wadley Loop drift cancellation system, in conjunction with a triple conversion superheterodyne circuit, the FRG-7 boasts high sensitivity along with excellent stability. It provides broadcast listeners with such features as a 3-position tone selector, an RF attenuator, and an automatic noise suppression circuit. For many years of satisfying reception, the FRG-7 is the receiver for you.

YAESU MUSEN Digital Display Communications Receiver with CPU Digital Clock & Timer FRG-7000



£327 PLUS VAT

● **0.25 Thru 29.9MHz Coverage with 1kHz Readout**

Computer technology and convenience features are brought together in the FRG-7000, a digital-display general coverage receiver for the discriminating SWL. The digital clock and timer, controlled by a CPU (Central Processing Unit) chip, will read out both local and GMT time, and will control peripheral station equipment such as a tape recorder. Improved SSB selectivity, ease of operation, and rugged construction are yours with the new FRG-7000 from YAESU.

FULL DETAILS OF THESE EXCITING RECEIVERS FROM THE NUMBER ONE IMPORTER - PLUS EX-STOCK FREE SECURICOR DELIVERY!

(36 pence in stamps brings Illustrated Brochure and our Credit Voucher value £3.60) - A 10 to 1 Winning Offer!

AMATEUR ELECTRONICS UK

508-514 ALUM ROCK ROAD
BIRMINGHAM 8

Tel: 021-327-1497/6313
Telex: 337045



Meet 'Uncle Tom'. He's on your wavelength.



Tom Beaumont - a radio enthusiast for 25 years - sells radio equipment for love! And he particularly loves Lowe - Trio for quality, value and reliability.

Tom is the sole authorised Lowe - Trio distributor for Yorkshire and North East England, and he offers the best before-and-after-sales service around on units like the top-value SRX-30 receiver illustrated.

THE LOWE SRX-30

All the facilities of a top-class communications receiver in one top-quality, economically priced unit. Covers 500 KHz to 30 MHz with excellent dial readout and re-set accuracy. AM, CW, SSB reception. The SRX-30 is equally at home in broadcast or amateur bands.

Other features include RF gain, fine tuning selectable sidebands, built-in loudspeaker, AC mains or 12V DC operation and rugged construction at an attractive price - Just £175.00 inc. VAT.

Buy by post or call in - or phone your Barclay Card or Access number. For speedy delivery on your SRX-30, please send cheque/P.O. made out to Leeds Amateur Radio for £178.00 which includes £3.00 carriage and packing. We will deal with your order by return.

Alternatively, call in for a chat at 'Uncle Tom's Cabin'. The shop is just 10 minutes from Leeds City Station, and there's easy parking if you travel by car.

● Instant H.P. for Licenced Amateurs. ● Extended Credit Terms Available. ● Send 50p for Catalogue and Price List.

LOWE TRIO DISTRIBUTOR



Leeds Amateur Radio are area distributors for Jay Beams, Antenna specialists and Hilomast products.



LEEDS AMATEUR RADIO
Reliability in Radio

Leeds Amateur Radio, 27 Cookridge Street, Leeds 2, West Yorkshire. Tel. Leeds 452657.

PRE-AMPLIFIER CP-P1

Shown here mounted with its associated components (and the CP-TM1 Peak Programme Monitor) on the CP-MPC1 interconnection board; the CP-P1 is a complete stereo pre-amplifier and tone control module. Performance features >70 db S/N ratio and >30 db overload margin (both ref. 3 mV) and distortion of 0.02%. The internal R.I.A.A. feedback compensation around the low-level pre-amp may be replaced with external networks and the tone control circuits can be programmed to give different turnover frequencies if required (including separate bass and treble 'defeat' facilities).

CP-P1 £14.95 incl. (U.K.) £16.95 incl. (Export)

Also Available: Power Amplifiers, Filters, Stereo Image Width Control, Compressor/Expander, Active Crossovers, Power Supplies plus all pots, switches, etc.

MAGNUM AUDIO Ltd.

DEPT PW7, 13 HAZELBURY CRESCENT
LUTON, BEDS. LU1 1DF
TEL: 0582 28887

SEND LARGE S.A.E. FOR DETAILS

★ specifications

Frequency Coverage: 0.5 to 30MHz in 1MHz bands with 10kHz graduations on dial

Reception Modes: CW, USB and AM

Sensitivity: At least 10dB (S+N) N under following conditions:

Mode	Frequency	Input Level
SSB	0.5-2MHz	1.0μV
	2-30MHz	0.3μV
AM	0.5-2MHz	3.0μV
	2-30MHz	1.0μV

(AM: 1000Hz at 30% modulation)

These voltages are half the open circuit signal generator voltage, i.e., the voltage read on the meter of a HP Model 606 Generator

Output: 200mW output on SSB at 2MHz with input signal of 0.5μV and 2W output with 5μV input

Audio Distortion: Less than 5% at 2 watts

Calibration Accuracy: Within 5kHz at all frequencies
Bandwidth (-6dB): SSB 3kHz ±25%; AM 5.5kHz ±25%

Image Rejection: Greater than 50dB

IF Rejection: Greater than 50dB at f_d below 20MHz.
 Greater than 40dB at f_d above 20MHz

Antenna: External connection to terminal strip (75Ω input impedance unbalanced). A self-contained telescoping whip is provided for strong local signals

Audio Output Provisions: Internal 8Ω speaker. A phone jack on the front panel which disables the internal speaker

Power Supply: 100, 117, 220, 240V a.c. 50-60Hz; External 12V d.c. supply connected via rear panel connector

Current Consumption: Less than 100mA quiescent at 12V d.c.

Clarifier: Tunes minimum of ±2KHz and maximum of ±3KHz

Size: 325mm W. 230mm D. 140mm H

Weight: 5kg

external speaker, which plugs into a socket on the rear panel, improved the audio quality.

The small telescopic whip aerial mounted on the rear panel and hinged so as to be stowable when not in use was useful but proved to be a nuisance when not in use as it cannot be disconnected from the aerial input to the set. A useful modification might be to make the whip dismantlable if not required.

Construction is of a sound standard throughout, the majority of components being mounted on glass-fibre printed circuit boards.


The instruction book was rather spartan with no maintenance information given and only a roughly drawn circuit diagram included on a separate sheet.

The main attraction of the SRX-30 must be its simplicity of operation, especially for the newcomer to the hobby. It is a pity that the audio performance does not do the r.f. side justice.

Prices

SRX-30 receiver £178.00 including 15% VAT. The SRX-30 receiver reviewed was kindly loaned by Lowe Electronics Ltd., 119 Cavendish Road, Matlock, Derbyshire. Tel: 0629 2430, and we would like to thank them for their invaluable assistance in this respect.

So You Want to Pass the RAE?

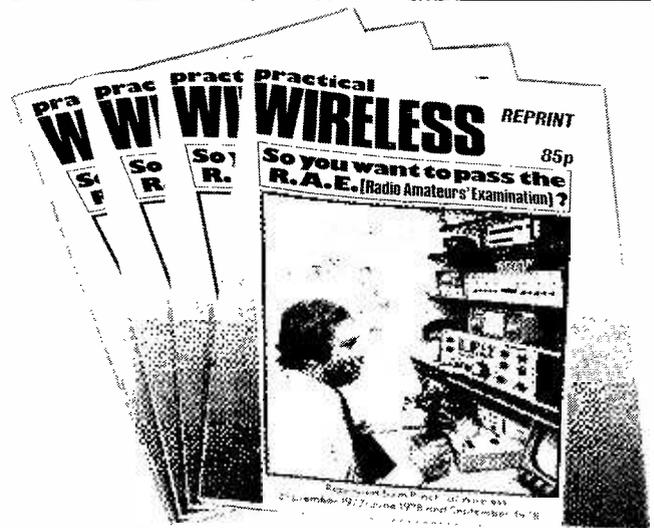

A reprint of the complete series, including details of the new examination format being introduced in 1979, is now available. The reprint costs 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
 Lavington House, 25 Lavington Street,
 London SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No. Value

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
 (BLOCK LETTERS)

ADDRESS
 (BLOCK LETTERS)

.....

 Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

Cut round dotted line

William Munro (Invergordon) Limited

distributors for

NEC

Amateur Radio Equipment

- CQ-P2200E 2M FM Portable 12 Channel Transceiver.** Complete with Mic and Accessories. Switchable 1W/3W. Send for full Spec. 3 Channels £179 VAT incl. All Repeater Channels available and S0, S20, S21, S22, S23 ex stock at £3 per channel. Choose your channels from these and we will fit them.
- CQ-R700 6 Band General Coverage Receiver.** 170kHz to 30MHz – AM, SSB, CW, RTTY. Built-in Mains Power Supply and Speaker with the new Auto-spread VFO. (Send for full Spec.) £220 VAT incl.
- CQ 110E HF bands Digital Read-out Transceiver.**
- CQ 301 Matching Linear Amplifier.**
- CQ 201 Matching VFO** (Three oven controlled VFOs in one and acts as Digital Freq. Counter as well.)
- M 110 Matching Table Microphone.**
- SP 110 Matching Speaker Unit/Digital Clock.**
- (Full Spec. Prices and current availability on receipt of your enquiry.)

100 HIGH STREET, INVERGORDON, ROSS-SHIRE V18 0DN
Telephone 0349 852351 Telex 75265
ACCESS BARCLAYCARD HIRE PURCHASE

BREDHURST ELECTRONICS

The SOUTH COAST CENTRE for communications receivers and all your Amateur Radio requirements.

Examples:

HF receivers

Yaesu FRG7 0.5-30Mhz Wadley loop	£210.00
Yaesu FRG7000 As FRG7 but digital readout de-luxe	£367.00
Lowe SRX30 0.5-30Mhz Wadley loop	£175.00

2 Metre receivers

Daiwa SR9 2M FM VFO + 11 xtal positions	£59.00
FDK TM56B 2M FM 12 channel + 4 auto scan	£105.00
Belcom AMR217B 2MFM 10 channel + 9 auto scan	£120.00

Marine receivers

Daiwa SR11 Tuneable 156-162Mhz + 6 channel scan	£95.00
FDK TM56B FM 12 channel + 4 auto scan	£115.00

Aerials

Jaybeam VHF + Antenna Specialists VHF mobile full ranges PLUS transceivers, convertors, plugs, microphones etc. All on-the-air in our showroom.

Carriage free. All prices include VAT.

Just phone your credit card number for same day shipment.

**REGAL HOUSE,
PENHILL ROAD,
LANCING,
SUSSEX.**

Lancing (09063) 63119
Open 9-5 Mon-Sat
Access
Barclaycard
Instant HP

LISTEN IN ON A MILLION LIVES TONIGHT.




The Bearcat® 250 with more than 30 separate and distinct functions is designed with the professional scanner in mind. Since it's crystalless, programming 50 frequencies in infinite frequency combinations is as easy as pushing a few buttons. With its incredible "non-volatile" memory, the Bearcat 250 searches out frequencies, stores them in memory for later retrieval, and even counts transmissions by frequency. It's also a fine quartz crystal clock. The capabilities of the Bearcat 250 almost defy imagination. If you want the ultimate scanner available today, this is it.

Bearcat 250

RADIO SHACK LTD

188 BROADHURST GARDENS, LONDON NW63AY.
TELEPHONE: 01 - 624 7174. TELEX: 23718.

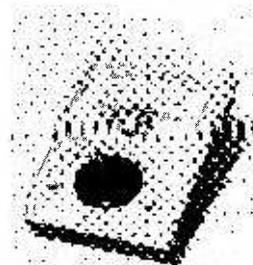GOOD QUALITY INEXPENSIVE POCKET SIZE MULTIMETER



SPECIFICATIONS

- DC VOLTAGE: 0-10, 50, 250, 1000 volts
2000 ohms/volt
- AC VOLTAGE: 0-10, 50, 250, 1000 volts
2000 ohms/volt
- DECIBEL: - 10 to + 22dB
- DC CURRENT: 0-100mA
- OHMMETER: 0-1 0 kilohms, 0-1 megohms,
60 ohms centre scale
- POWER SUPPLY: One 1.5V size "AA"
cell ohmeter
- SIZE: 3-5/8", 2-3/8" x 1-1/8"
- WEIGHT: 4oz

Price: £5.30 inclusive V.A.T. & P & P
Cash with order


ARMON PRODUCTS LIMITED

COTTFERELL HOUSE, 53-55 WEMBLEY HILL ROAD, WEMBLEY, MIDDX, HA9 8BH
TEL: 01-902 4321 TELEX: 923985

If it is not required to switch more than 5A at up to 250 a.c., one can select a Keyswitch relay type MS1B which has a 12V, 26mA coil. Thus the use of this relay ensures that the supply current is kept quite small.

Other Devices

The LM1808 device is equivalent to an CA3065 television sound i.f. device and an LM380 power amplifier in a single package, although there are minor differences in the volume control circuit—which is not used in the ultrasonic application. The circuit of Fig. 4 shows a receiver which uses the 3065 and the LM380 as separate devices, but it is equivalent to the circuit of Fig. 3. The CA3065 is a 14 pin dual-in-line amplifier. The LM380N is a 14 pin dual-in-line device, but a miniature version is also obtainable as the LM380N-8 in an 8 pin d.i.l. package.

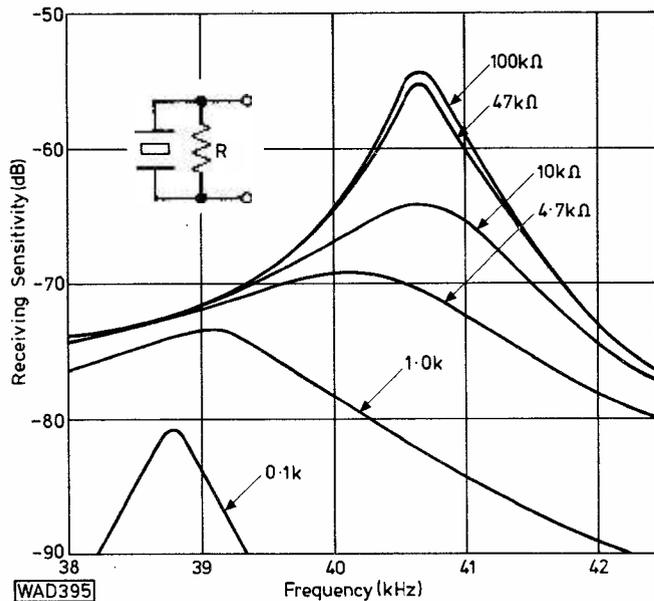

WAD395

Fig. 5: Graph showing the response of the SE05B 40R ultrasonic receiver

If the transmitter circuit of Fig. 2 is used, it will be necessary to adjust the potentiometer VR1 so that the frequency of oscillation of the 555 circuit matches that of the two transducers used in the system as closely as possible. This can best be done by connecting a sensitive voltmeter of high impedance across C3 of either Fig. 3 or Fig. 4.

When the transducers are placed close together with power applied to both of the circuits, the voltmeter should read a few volts. The transducers should now be separated and pointed away from one another until the meter deflection decreases. The preset VR1 in the transmitter should now be adjusted for maximum deflection of the meter in the receiver circuit. If necessary, this process should be repeated with the transducers spaced farther apart until the control is set in its most sensitive position. It is also possible to carry out this adjustment using a 100mA f.s.d. meter in series with the relay or by using a voltmeter across the relay.

Conclusion

Various circuit options have been given so that the reader has some choice. The circuit using the LM1808 is more compact than the Fig. 4 circuit, but the CA3065 and LM380N are more readily obtainable.



BBC External Services Control Room, Bush House, London, responsible for the co-ordination of all the simultaneous language broadcasts leaving Bush House

Photo courtesy BBC

Satellite broadcasts of world-wide television are also possible now, but here technology is over-ruled by other factors. Most broadcasting organisations have enough problems scraping money together to finance programmes for licence-fee paying domestic viewers, let alone free TV programmes for viewers abroad. Secondly, politics is such that countries with different social systems would no doubt be loath to let their people have free access to possibly contradictory propaganda from abroad via a TV antenna dish pointed upwards to a satellite. This method, remember, is far more difficult to jam.

In the meantime, s.w. broadcasting is the cheapest, most immediate and direct form of international communications. It will never overtake the popularity of the local radio station, but for those who take an interest in events beyond their back garden, s.w. radio will be there for a long time to come.

List of Publications for Further Reading

1. *World Radio TV Handbook and World DX Guide* edited by Jens Frost. Published by Billboard publications, and available through bookshops.
2. *DX Catalogue*. A list of free courses for the DXer and SWL offered on request by Radio Nederland, PO Box 222, Hilversum, Holland.
3. *List of Broadcasting Stations for Europe*. Up-to-date schedule of frequencies registered by International stations at the International Frequency Registration Board. Sent free of charge by the Austrian Radio Technical Department, A-1136 Vienna, Austria.
4. *European DX Council Reporting Guide*. Hints on making out useful reception reports in English and a number of other languages. Enquiries (with one International Reply Coupon) to EDXC, Postfach 25 03 25, D-4630 Bochum 25, Federal Republic of Germany.

List of organisations involved with Broadcast Listening

1. International SW League, 1 Grove Road, Lydney, Glos. GL15 5EP.
2. Twickenham DX Club, 37a Pope's Grove, Twickenham TW1 4JZ.
3. European DX Council, Postfach 25 03 25, D-4630 Bochum 25, Federal Republic of Germany.
4. Handicapped Aid Programme (UK), c/o Mr John Rose, 5 Hall Street, Wombwell, Barnsley, Yorkshire. This very worthwhile organisation is also in need of volunteers with or without technical experience.
5. UK DX Camp, c/o J. Marks, 12 South Bailey, Durham DH1 3EE.
6. Danish SW Clubs International, Greve Strandvej 144, DK-2670 Greve Strand, Denmark.

Since the above are non-profit-making organisations, please enclose return postage with all enquiries.

Follow-up to


PW Sandbanks

METAL DETECTOR

P. J. WALES

No. 2

Response from readers to the *PW* "Sandbanks" article of January 1979 has taken two forms, faults which cannot be located, and requests for variations on the theme. The most common fault reported has been that of the output of IC4 going negative when a large piece of metal is brought near the search coil. A few letters were selected at random and the writers were asked to send the offending p.c.b. in for examination. In only one case was the 709 faulty. This particular device is running in its fastest possible mode, and so all stray capacitance and inductance around it should be at a minimum. This means that the i.c. must **not** be a socket, and it should preferably be a TO5 version. All of the associated components should have short leads and be mounted as close to the board as possible. If these precautions are observed, it is very unlikely that IC4 will go unstable.

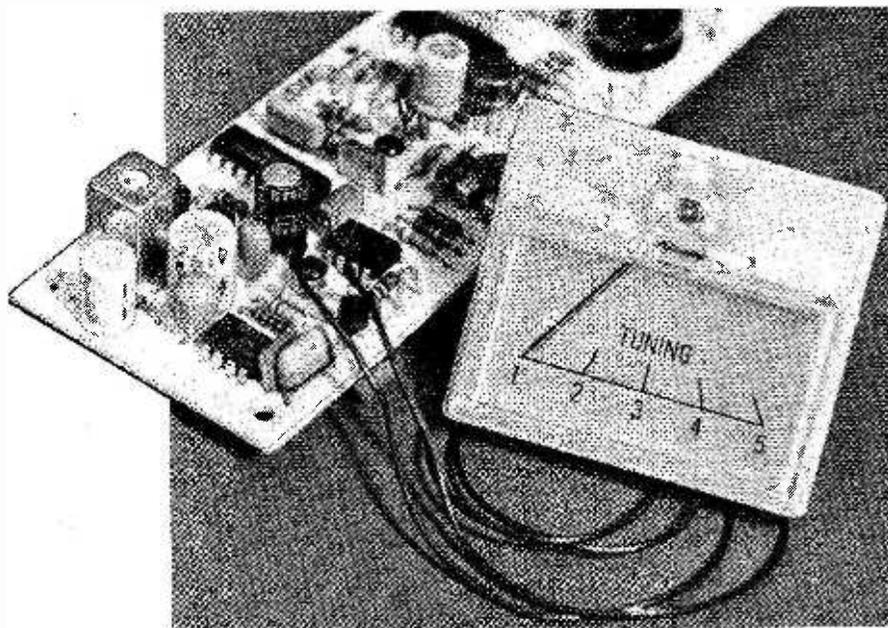

Power Supply Problems

The second phenomenon which can cause the output to go negative is poor power supply regulation. If your "Sandbanks" has this problem, then check the $-5V$ rail and the $+12V$ rail. If they are more than one volt out then that is the fault. If they are correct, then try adjusting VR1 whilst monitoring the $12V$ rail. If it varies or if it is low anyway then that is the fault. The cure is not so easy to find, but is frequently due to either the 709 or the 741 taking too much current, so disconnect pin 7 on each i.c. and measure the current. The 709 should take $2.6mA$ and the 741, $1.7mA$. If either or both is taking more then change them, but the figures are only manufacturers' typical figures, the devices are not faulty.

A very large number of these circuits have been tested, and less than one per cent of them have had to have any changes made to the circuit values as published in *PW*. The only fault that it has not been possible to cure was

that of drift. The circuit should remain absolutely stable once set, and if any reader has had this problem and cured it, the author will be very pleased to hear from him or her.

Response Speed

To get the very best from your "Sandbanks" several things can be optimised, but the first step is to fit a printed circuit coil, as described in the April 1979 issue. This really does increase the sensitivity to gold and silver tremendously. Having fitted this and made the appropriate changes to the sampling circuit, the next improvement is in the response speed. This is defined by two things, the pulse rate of IC1, and the integration time of IC5. The pulse rate can be increased to $500Hz$ by changing C2 to $33nF$. This change allows the integration capacitor C12 to be reduced from $0.47\mu F$ to $47nF$. The circuit now is 10 times as fast as it was and will detect a coin being thrown through the coil.

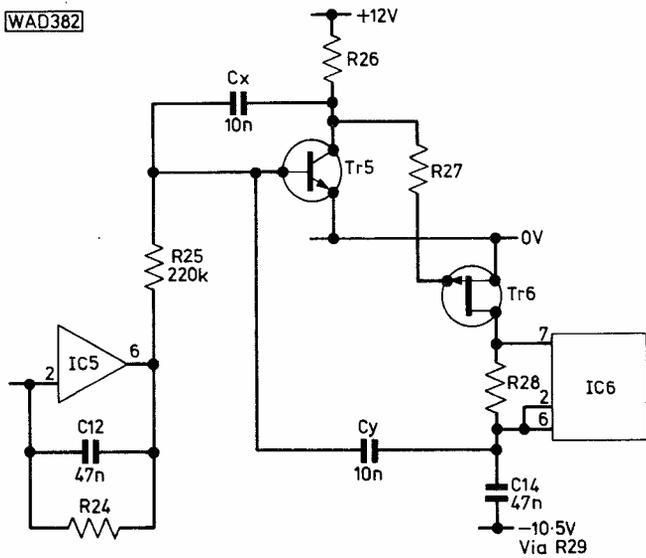


Fig. 1: Improving the audio quality. Only those components with values indicated are subject to change

Audio Changes

Checking the machine's performance now, will prove that the next step of improving the quality of the audio is a good one to take. The first problem with the audio is that it is too low in frequency, and when a coin is detected at maximum range, the change in audio frequency is so slow that it is very easy to have passed the coin and miss it. To remedy this, change R25 to 220kΩ and C14 to 47nF. This now gives a much higher pitch but the tone comes on too fast and it is very difficult to tell how deep the find is by the tone. It is also very unstable due to the short integration time of IC5. The instability can be cured by wiring C_x (10nF) from base to collector of Tr5 on the back of the p.c.b. The speed of the audio can be corrected by wiring another 10nF, C_y on the back of the board, this time between pin 2 of IC6 and the base of Tr5. This has a great feedback effect and now the audio is super-smooth from a fast clicking to a very high pitch indeed (Fig. 1).

Having got the audio working correctly, the next step is to balance all of the tolerances in the circuit. This should be effective for 95 per cent of all "Sandbanks" but if it does not work on yours, then do not worry, your machine is still very powerful.

To peak the sensitivity, connect a meter between the output of IC4 and the 0V rail. Set the audio, with no metal near the coil, to about half-pitch. Adjust VR1 so that the audio is at its lowest frequency with the meter reading between 0V and 8V. If the meter reads outside these limits when at the lowest pitch, then re-adjust VR1 for 0.5V and leave it there; it is very near the optimum setting at this point. If you can get a minimum between 0 and 8V then expect to see about 5V typically.

Meter Option

Some readers have requested a meter option for the "Sandbanks", but adding one which will improve the sensitivity is not easy. Ambit International do make a suitable meter, scaled "1" to "5" and legended "Tuning", and with a bit of fiddling it should be possible to fit this into the end of the handle. There are two different ways to wire this into the circuit; the easiest way is if you intend to discard the audio stage completely. This makes the machine more sensitive, but you do have to watch the meter all of the time. If this is the way you want to do it, then remove Tr5 and R25. Solder a 10kΩ resistor R_z between the base and emitter connections in the p.c.b. and connect the meter into the holes for R25 (Fig. 2).

To retain the audio stage, it is necessary to build the audio modifications as previously detailed, but leave out R25, and leave C14 as 0.1μF. R25 now becomes a 27kΩ but the meter is connected in series with it, and measures the base current of Tr5. It will be found when adjusting VR2, that the meter will just leave the "1" mark before the audio starts. This is the correct position for VR2 and so it is easy to verify that the setting has not changed when the machine is in use (Fig. 3).

Component Problems

The demand for the "Sandbanks" kit was much greater than was anticipated and so Ambit have had some problems in supplying some of the less common parts of the kit, such as IC2, which has been modified in some kits. The biggest problem has been the supply of the cases, but I am assured that these are available now, and so if you were disappointed before, it is worth contacting Ambit again.

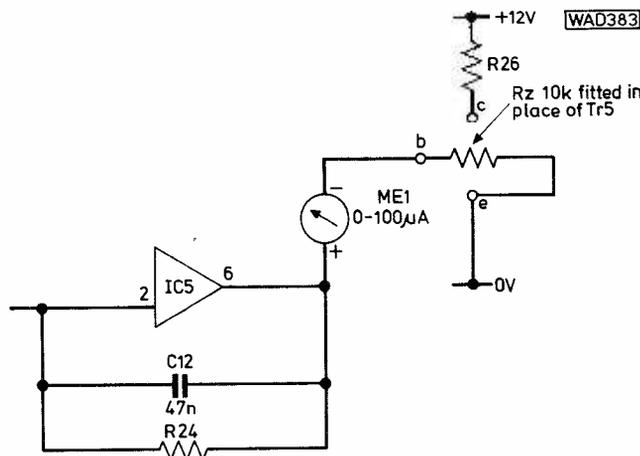


Fig. 2: Providing a meter readout instead of the audio indication

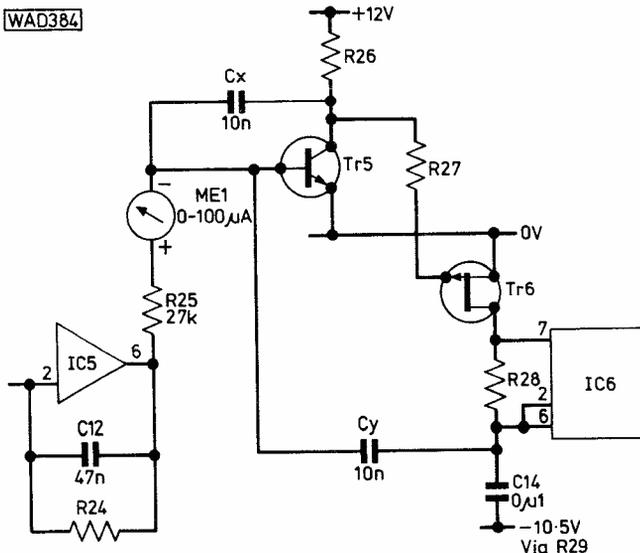


Fig. 3: Providing a meter readout but retaining the audio indication

HOTLINES

A REVIEW OF RECENT DEVELOPMENTS

In general, the author does not have any more information on products than appears in the article.

Whistle Stop

A popular circuit in many electronics construction journals is the sound switch. A bright young man in America has come up with the idea of taking things a step further in order to aid handicapped people. He's brought out a "Whistle Switch".

The basic idea is simple, you just whistle and the device switches from one state to another—from on to off and/or vice versa. A step further than that has been to include a digital display and to make the instrument a multi-channel, multi-purpose unit. The arrangement causes the digital display to illuminate a series of numbers in sequence—1, 2, 3, 4 and so on. When the desired number, corresponding to the task required, comes up, it only needs a whistle to cause the unit to switch on or off. Thus one could have a light turned on or off, television receiver switched, telephone answered, nurse called, etc.

Believe it or not, there's even circuitry that allows the unit to be tailor-tweaked to your own particular brand of whistle, from bass to contralto (actually adjustable from around 800Hz to 2.5kHz). The first few have sold in the US for just under \$1,000 and patents have been applied for. Not available in the UK as far as I know.

Micro Magic

The integrated circuit designers are always trying to make yesterday's i.c.s obsolete. The problem for us, the users, is that they succeed all too well—and all too often. The very latest piece of micro magic to come my way is a new breed of linear creatures that will function effectively and efficiently right down to a miserly 1V power supply. They're not delicate little specialities, either, and will work over the temperature range from -55°C to $+125^{\circ}\text{C}$ (means you can listen to the miniature

receiver you make with them in both the oven and the refrigerator!).

At present, only sketchy details have arrived, but the i.c.s do look very interesting. For example, there's mention of a high performance op amp which needs only 1.2V. A device with similar function performance to a Darlington circuit can provide a 20mA output current but only takes a diminutive 10 μA of standby current.

Television Developments

I was interested to read a report from America giving figures for the consumer section of the electronics, radio and TV markets. According to the report, video tape recorders will hit around 400,000 this year on projected figures. Colour receivers are topping around 710,000 per month, while radio receivers (a.m./f.m.) dropped a little and could only manage a mere 1.3 million sets—per month.

In the other direction, a German company is forecasting a growth potential for projection colour television receivers. Up until now, acceptance (or perhaps purchases) have been slow, but the company has confidently launched a new projection receiver with some impressive technical claims.

First, the projected colour image is very clear and extremely bright—some 140 candelas per square metre (about 40 foot-lamberts). This intensity would make it easily and clearly visible even in daylight. The image size is some 965 by 1270mm. Hi-fi buffs will be relieved to hear that the projector is capable of providing 14W of high quality sound. The estimated price tag is around the £1,900 mark. Can you imagine a 1 x 1.25 metre version of Crossroads or Coronation Street? No way Brothers, no way!

Optical Fibres

It never ceases to amaze me—the speed at which things happen electronically. Signals being whizzed round computers in thousandths, even millionths of a second. Having admitted difficulty in visualizing that, you can imagine my gasp of credulity on hearing of happenings at the famous Bell Labs. Apparently (or should that be transparently) they've got this 700 metres-plus length of single mode optical fibre that's only nine meagre micrometres in diameter. And current experiments are showing the possibility of transmitting digital information along this fibre at the rate of 200 gigabits per second! The one watt laser doing this generates pulses only five picoseconds wide with little or no broadening. When the laser power was stepped up to 60W, problems arose with smearing at the output end of the fibre.

If someone had shot a 60W pulse loaded with 200 gigabits of information down my fibre, I reckon I'd be smearing, too.

Cheaper Printers

Home computer addicts will be pleased to hear of a new printer launched recently in America. It can print at 150 characters per second and is claimed to give "letter quality copy". It's a dot matrix printer, but the makers tell that the dots print so close that they overlap thus avoiding the "broken up image" appearance of many units of this type. Price on the US market is less than \$3,000, which is very much cheaper than the popular daisy wheel printers.

Ginsberg



by Eric Dowdeswell G4AR

I have always been concerned over the fact that one can pass the Radio Amateurs' Examination and get on the air with a 400W p.e.p. transmitter without ever having touched a transmitter before, or a receiver for that matter. While the commercial "black boxes" that almost every newly-licensed amateur seems to start up with these days are pretty foolproof, they can still be tuned wrongly leading to severe interference to TV sets over a wide area. Whether h.f. or v.h.f. bands are used is immaterial.

Even with the transmitter properly run and operating into a well-matched aerial system, the sheer power output can be just as harmful to neighbouring TVs. Complaints roll in, tempers get frayed, and the inexperienced operator wonders if there is anything he can do about it. Many just give up when faced with this problem, as evidenced by the ads in our magazines for the sale of almost brand-new equipment by recently licensed amateurs.

Surely there cannot be any justification for the present system other than bureaucratic convenience. The ideal practical examination of a would-be licence holder is totally impossible today, but we did have a much better way of bringing up the amateur operator in days gone by. Such a method deserves consideration by those who deprecate the present "appliance operator" syndrome which can only deprive the amateur of his "experimental" status, the sole justification for the amateur licence in this country.

It is also a very good stick with which to beat the amateur when the third-world countries, in particular, start grabbing the frequencies at the World Administrative Radio Conference in Geneva later this year.

So, I wonder if there is any hope of reviving the "artificial aerial" licence which existed before the last war, whereby permission was granted to use transmitting equipment with a dummy aerial load in order to gain experience with operating transmitters and knowledge of the equipment, thus virtually eliminating the objectionable QRM caused by the present system. A licensed amateur could verify that such work had been carried out before a full licence was granted.

Alternatively, a novice type licence for, say, c.w./telephony operation on a maximum of 25W input for six months for the h.f. bands, or 10W on telephony on the v.h.f. bands, with the log book as evidence of experience. Some intermediate step in our present licensing procedure is badly wanted. Considering some of the questions I get asked by newly licensed operators I wouldn't trust them with a walkie-talkie!

From all Around

Congratulations are in order this month for **Phil Charlesworth** of Southport, who dropped his BRS41107 in favour of G8SNG and wisely is swotting on the code to get his G4 as soon as possible. He uses PA0AA on Friday evenings for code practice around 1930hrs on 1827, 3600 and 14100kHz following news bulletins on telephony.

Felicitations too for **Ed Phillips** living in Wales who passed his RAE in December. He has a TCS8 receiver for the time being, but would feel happier if he had a handbook. He lives at Rhos-Y-Coed, Rosebush, Clunderwen, Dyfed, and feeds his set from a 90ft wire and a.t.u.

Keith Taylor is 12 and hopes to take his RAE this year, but as I have pointed out many times, the exam is now a costly exercise and since Keith cannot get a ticket for another couple of years he'd be well advised to hang on and make sure he passes at the first attempt in a year or so's time. For the moment Keith has an R1155 and 75ft of aerial but mentions that he has a 300ft garden and a 60ft tree at the far end! Bliss, indeed, in Camborne, Cornwall.

Edgar Powell (Canton, Cardiff) joins the fray with a BC779, a version of the famous Super Pro, but he's stuck a three-valve preselector in front which, probably, helps not at all! Anyway, I've suggested trying it in and out of circuit on such as JX9WT, Jan Mayen Island, one of Edgar's better bits of DX. A sour note from **John Powell** (Southwold, Suffolk) abroad for very many years but happy to pick up *PW* again and re-arouse his interest in

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

the amateur bands again. He's written twice to the RSGB for info on joining same and guidance on local reps and clubs but to no avail. This is the sort of treatment that is calculated to put a newcomer off amateur radio for good but I'm sure John is made of sterner stuff.

Regular writer **Bill Rendell** down in Truro, Cornwall, reveals that his AR3 set plus preselector has a total of 17 knobs! He reckons a newcomer would need a two-day course on it before getting any results. From his DX log it's obvious that Bill screws every circuit to the maximum from such a simple outfit. He wants me to keep on urging readers to use the long wire plus a.t.u. for best results, which I'll be pleased to do! At 336 Bocking Church Street, Braintree, Essex, **R. Oliver** has an EC10 Mk 1 and has problems with drift and wonders if anyone has any ideas on how to cure the trouble. Write to him direct.

About DX

Both **Lawrence Woolf** GJ3RAX (St. Brelade, Jersey) and **Bob Round** (Camborne, Cornwall) were kind enough to send me lists of the American callsign prefixes following my comments on AG5H. Pretty obviously things are completely out of hand over there in that field. AC3 was a time-honoured prefix for Tibet but now becomes commonplace, a great pity. Incidentally, I wonder what happens when our own G8ZZZ gets issued in the not too distant future!

John and **Steven Goodier** have been chasing UA0I, North Pole DX-expedition around 21181kHz without luck, but did find A35RB on Tonga and lovely FW8AD in the Willis & Fortuna Islands, a pretty rare catch. J3AAE (an old Japanese callsign!) popped up from Grenada while VK0PK on MacQuarrie Is. is not one that is heard very often. All these were on 20m s.s.b. **Pete Lucas**, Padarn Hall, Great Darkgate Street, Aberystwyth, Dyfed, has an AR88 but is sans manual or circuit, so can anyone oblige? Pete wisely leaves the heaters on most of the time to cut drift, always a good idea with valved sets, if one can stand the electricity bill! Anyway, he logged J28BN (QSL F6UYG), FG7XA, S79MC and FR7BJ on 10m s.s.b. so he's not doing so badly.

In Loscoe, Derbys, "**C.P.**" **Palfreyman** got out his old and trusty 0-V-1 t.r.f. set (a two-valve set, detector and audio stage for those who are not so very old) and looked for some interesting c.w. finding VP9JC on 40m, HI8LC and ZL1AJU on 20m and EA8QP on the 15m band, using indoor dipoles! **Peter Hawkes** and his DX160 found VO1OB on 80m and VP8QG on 20m s.s.b. but feels he could do with a better receiver. Don't throw it away, will you, OM? I've still got several young readers on my waiting list for a set!

Bill Rendell, already mentioned, still seeks islands as his main target and came up with OH0NA, Aaland Is, quite close but still not heard all that often, VK0PK on MacQuarrie Is. and "find of the year" VR6TC on Pitcairn, all 20m s.s.b. On 15m OK3TAB/D2A in Angola (QSL OK3ALE) was interesting for Bill as was VK1FT of which there are very few around. **Dennis Sheppard** reports on RTTY matters from Sheerness, Kent, once again with finds on 10, 15 and 20m like JA1JDD, PY2YFG and TI3DJT (10m), AL7J (Alaska), A4XFW and HI8JSM on 15m and KL7JHD, PS7JA and VR6BJ on Pitcairn for his 20m DX, although Dennis has since reported trouble with the 20m band on his receiver.

The Drake of **Bernard Hughes** (Worcester) is earning its keep with things like CO3VR, VP2ABC and VP5GT on 80m, CO2GS, HK0BBD on 40m and BV2B, JT1BG, VQ9TC and TA1SU on the 20m band. In West Wickham, Kent, **John Dainty** has been having problems with Band

1 TV breakthrough on his SSR1 receiver via the i.f. stage working in the region of 45MHz. Any suggestions would be welcome.

A couple of quickies. **Lee Humphrey**, 49 Altwood Road, Maidenhead, Berks, would like circuit/manual on the R1155 receiver, while **Alan Billingham**, BRS40845, 3 Hale Carr Grove, Heysham, Lancs, is anxious to contact other amateur band listeners in his area.

Club Info

Edgware and District RS, second and fourth Thursday of the month at the Watling Community Centre, 145 Orange Hill Road, Burnt Oak, Edgware, at 8pm where Morse instruction is given to suit those present. Slow Morse also from club station G3ASR on Top Band and 2m. Details of this and forthcoming meetings from Sec. Dennis Lisney G3MNO, 119 Draycott Avenue, Kenton, Middx. 01-907 1237.

If you live in the **Stevenage** area your RS meets first and third Thursdays at 8pm at the British Aerospace QTH, Gunnels Wood Road, Stevenage, Herts. A DF hunt takes place on July 12 and July 19 sees the h.f. and v.h.f. equipment being given a workout at the club. Contact Peter Byrne G8MCV, EM2.3 Hitchin Exchange or ring 0462 4231 in working hours.

Now a first notice of the **Derby ARS Mobile Rally** on August 12 which should not be missed if there is any chance of getting there. Details from Jenny Shadlow G4EYM, 19 Portreath Drive, Darley Abbey, Derby. A fox hunt (radio, not animal!) is planned for July 10 by the **Bury RS** with an electronic and radio brains trust on August 14. The club meets at Mosses Centre, Cecil Street, Bury, every Tuesday night and visitors are doubly welcome. The club has an operational FT101 G3BRS and extensive library so contact M. Bainbridge G4GSY, 7 Rothbury Close, Bury, Lancs.

I am still getting letters either too early so that the news content is out of date by the time it would be published, or too late to meet the **15th of the month** deadline. General letters not involving publication are welcome at any time, of course.

From the Logs

B. Hughes:—80m CO3VR VP2ABC VP5GT ZF2CL ZB2CJ 40m CO2GS FY7BC HK0BBD 20m A7XAH BV2B J3AAE JT1BG S2BTF VR6HI VQ9TC 15m C6ANU FR7ZN HS1ABD TJ1BB 10m KC4B VK9NI 4M5A 6T2NI

J. Dainty:—20m D4HXA ZL2QY ZF1SV

D. Sheppard:—RTTY 20m JH1HWN KL7JHD PS7JA VR6BJ ZP5CD 3D2BM 15m AL7J (Alaska) A4XFW HI8JSM YV2BSV 5N2ZBH 10m JA1JDD PY2YFG TI3DJT YV2RD

W. Rendell:—80m YV5ANS ZF2CL ZL4AP 6W8DY 20m C5ABM J6LFZ (St. Lucia) KB6EX VK0PK VP2KT VP2VGI VP8PU VP9JR VR6TC XT2AV 15m C6ANU J6LFZ OK3TAB/D2A (Angola) SU1DP VK1FT VP2MDG VP8SB YB6IB 6W8DY

P. Hawkes:—20m VP8QG 15m 8P6FU

C. Palfreyman:—c.w. 80m UA9CM 40m LU8DQ VP9JC 20m HI8LC ZL1AJU 15m EA8QP

J. & S. Goodier:—20m A35RB (Tonga) D4CBS FW8AD J3AAE VK0PK 3D2ER (Fiji) 5T5ZR 15m TU2ID 10m YB0ADW ZE1AD

P. Lucas:—20m VS5TX (Box 980 Brunei) 10m J28BN FG7XA S79MC FR7BJ

All reports in s.s.b. unless indicated otherwise.

LCD Multimeter

£69.99+ VAT

TOP SECRET




We're about to lift the wraps off the most exciting new instrument of the year!! Our new 3½ digit LCD multimeter is less than half the cost of competing products and brings ownership of these incredibly useful instruments within reach of everyone. The LMM 100 multimeter features 25 voltage current and resistance ranges and has a large 0.5in. LCD display. Up to 2,000 hours use from one transistor battery. The LMM 100 is the first portable LCD multimeter with a digital hold facility for data-logging etc. Send off immediately for full details of specification and price. First 100 brochures will be sent out with a '£5 off' voucher so take full advantage of this unique opportunity by contacting :

LASCAR ELECTRONICS · BASILDON (0268) 727383
Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH

'WINTON'

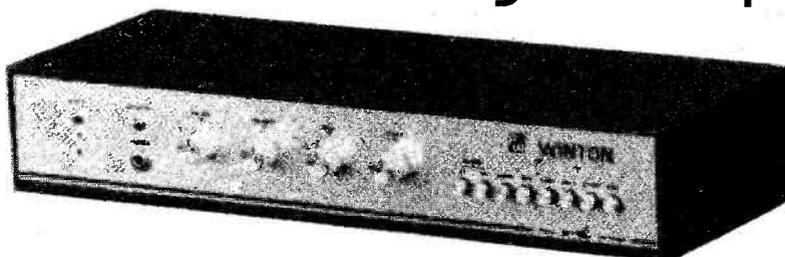50+50 watts, of quite extraordinary amplifier.



Why Extraordinary? Well, the P.W. WINTON is the first Amplifier for the home constructor to offer the enormous benefits of POWER MOS-FETS, and to do so at such low cost.

Power MOS-FET technology is available commercially, and the couple of Amplifiers we have seen are superb examples of the HI-FI designers art, but, and here's the bad news you will have to shell out about SIX HUNDRED POUNDS to enjoy them.

The alternative? - do it yourself, build the WINTON and when it is completed we defy anybody without ten thousand quid's worth of sophisticated lab equipment to tell the difference, but your Wallet will certainly assure you that you've made the correct choice.

What about looks? We think the slimline Burmese Teak veneered cabinet and the Brushed Aluminium fascia look superb, but we are horribly biased, besides we lie a lot too.

So! to discover the truth for yourself send a 9p stamp to T. & T. - nice people to deal with - and we'll send you a totally biased, utterly patronising, and irritatingly smug 'gen sheet (sent in plain brown wrapper, nudge nudge), or alternatively take our unashamedly immodest word for it and send us your cheque for the best Amplifier buy of your life, or perhaps you'd rather settle for an ordinary Amp.?

The Superlative WINTON is available for your convenience packed as follows:

- Pack (A) All Capacitors and Fixed Value Resistors. (inc. 7 Amp ripple Res. Caps.) **£21.45**
- Pack (B) Switch Bank, Switches, Potentiometers, Pre-Sats & all Knobs **£13.26**
- Pack (C) Printed Circuit Board (Tinned, Drilled, & Overlay Printed) & Pins **£8.10**
- Pack (D) Hardware Pack, consisting of precision formed & punched Chassis, Black Epoxy finish Heat Sinks, Teak Veneered Cabinet, all screws, wire, fuseholders, etc., and a super Brushed Silver Aluminium Fascia Panel. **£32.99**
- Pack (E) All Semiconductors, (including HITACHI POWER MOS-FETS) **£30.53**
- Pack (F) Special LOW HUM FIELD Toroidal Transformer **£17.22**

COMPLETE KIT, of all parts necessary to build the P.W. WINTON **£120.00**

Order with complete confidence (C.W.O. only please) from:

T. & T. ELECTRONICS
Green Hayes, Surlingham Lane,
Rockland St. Mary, Norwich, NR14 7HH.

Please Allow 28 Days For Delivery.

ALL PRICES INCLUSIVE OF V.A.T. & CARRIAGE

MEDIUM WAVE DX

by Charles Molloy G8BUS

Long Wave Across the World is the name of a 12-page booklet written by Adrian Peterson and published by the Australian Radio DX Club. It traces the history of broadcasting on the long waves in Europe, the Americas, Asia and Australia, and is illustrated with reproductions of QSL cards, early photographs and even a set of postage stamps.


Broadcasting on the long waves was much more extensive during the early days of radio than it is now—the consequence of the longer daytime range of l.f. stations compared with those on the medium waves and the absence of short-wave broadcasting which had not yet been developed. It will come as a surprise to many to learn that there was l.w. broadcasting during the 1920s in Ceylon, Hongkong, India, Afghanistan, Brazil and Chile.

This booklet makes absorbing reading and I would recommend it to anyone interested in the early days of broadcasting. It is obtainable from the Australian Radio DX Club, PO Box 54, Melton South, Victoria 3338, Australia for six International Reply Coupons (or US \$2.00) airmail or 4 IRCs (\$1.00) seamail to anywhere in the world.


Ramadan

In 1979, the month of Ramadan starts on 26 July and ends on 24 August, some 10 days earlier than last year. This advance through the calendar occurs annually because the Moslem year is based on the lunar month rather than on the calendar month as in the west. It has the effect of moving Ramadan through the seasons of the year in a 33-year cycle.

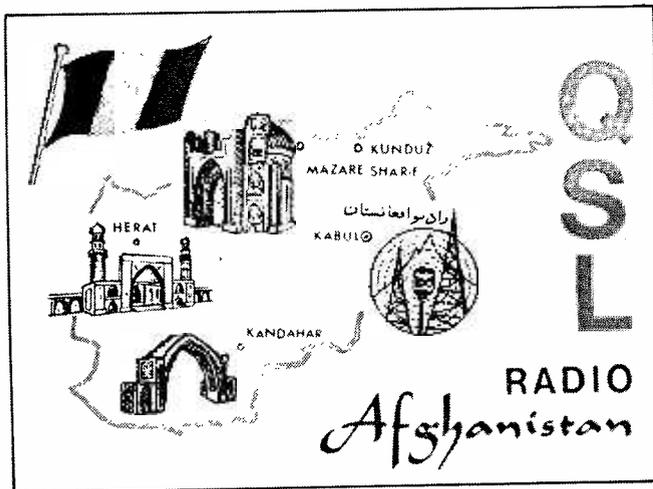During Ramadan, broadcasting in Moslem countries continues throughout the night. The majority of the states involved are in Time Zones ahead of GMT and conse-



Practical Wireless, August 1979

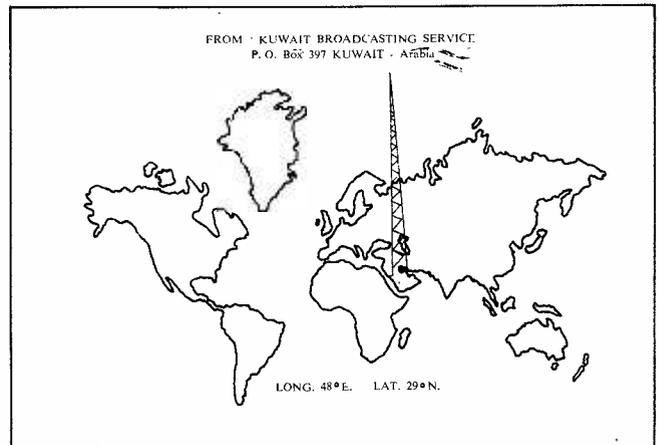

quently, sign-off normally occurs before European QRM has had a chance to subside. Of course sign-on is earlier too but during this time of the year much of the path from the more easterly countries will be in daylight and reception will not be possible. The occurrence of Ramadan in the summer is therefore a welcome event, at any rate to the DXing fraternity who do not have to participate in the rigours of fasting through the long hours of daylight!

RADIO BAGHDAD transmits 37 hours daily.
Programmes in nine languages: Arabic, Kurdish, Turkish, Turcoman, Persian, Urdu, English, French, German.
Three medium wave programmes 222, 330 and 360 meterband.
Nine short wave programmes 19, 25, 31, 41, 48, (2) 49, 75, 92 meterband.
RADIO BAGHDAD sendet täglich 37 Stunden.
Programme in neun Sprachen: Arabisch, Kurdisch, Türkisch, Türkmenisch, Persisch, Urdu, Englisch, Französisch, Deutsch.
Drei Mittelwellenprogramme im 222, 330, 360 Meterband.
Neun Kurzwellenprogramme im 19, 25, 31, 41, 48, (2) 49, 75, 92, Meterband.
RADIO BAGHDAD émet nos programmes en neuf langues 37 heures par jour : Arabe, Kurde, Turque, Turcomane, Urdu, Persane, Anglaise, Française, Allemande.
Programmes sur trois ondes moyennes 222, 330, et 360 bandes mètres.
Programmes sur neuf ondes courtes : 19, 25, 31, 41, 48, (2) 49, 75, 92, bandes métre.

DX to be Heard

In past years I have listed some of the easier stations and also a few of the more difficult ones that might be picked up. This year, owing to the Geneva Plan and its almost universal non-observance in the Middle East, it is anyone's guess what will be heard during Ramadan 1979. Reports from readers will be very welcome as these will give an indication what Ramadan will mean to the m.w. DXer in the future.

One spin-off from the current situation is the production of 1kHz heterodynes between stations operating on the pre-Geneva channels and those on the new channels which are 1kHz higher. Tune round the band after dark and you should hear a number of 1kHz "hets" on the low frequency side of European broadcasts. They reveal the presence of a station 1kHz below this strong local signal. Make a note of the **weak** hets and go back to them later on when

hopefully the European may have signed off. You may then be on to some real DX.

The following is a list of the authorised frequencies of the stronger stations in the Arab world. Look for Algeria on 549, 576, 891 and 981kHz, Egypt on 621 and 1107, Kuwait on 540, 1134 and 1341, Libya on 828, 1125 and 1251, Morocco on 612, 963 and 1044, Turkey on 1017 and 1062, Tunisia on 630 and 1566, Syria on 747 and 783, and Saudi Arabia on 585 and 882. Do not forget the long waves. Azilal in Morocco is on 209kHz, Tipaza in Algeria is on 254kHz and Turkey is on 182 and 245kHz.

Identification

The identification of Middle East stations can be a problem. The language is Arabic except in Turkey and Iran, which is a help. Listen for Burasi in Turkish. Burasi Turkiyem Sesi Radyosu is the Voice of Turkey. In Farsi (Persian) Inja Teheran means Here is Teheran. The key word in Arabic is Huna. Huna al Kuwait means This is Kuwait, also there is Sout el Arab, the Voice of Arabs, from Egypt.

Reception Reports

A few years ago an enterprising DXer in Germany produced an Arabic reception report form complete with vocabulary, which really is an example of dedication to a hobby. Problems could arise though if it fell into the hands of a DXer who did not realise that Arabic is written from right to left! I have never used anything but English when writing to the Middle East as it seems to be widely understood. The problem is not so much the language to use as what to put into the report. "Arab music and singing" is not really much use. Time signals, news bulletins, station identification, clock chimes (Egypt uses the Post Office clock in Cairo), are the sort of items to look for, but if you really pick up something special then a short tape recording sent to the station is really the only way to be sure, in spite of the cost.


Language Identification

Last month, reader **S. Donnelly** raised the question of key words and their use as an aid to identifying a foreign language. This brought to mind the Foreign Language Recognition Course which was produced by the now defunct Radio Canada Short Wave Club. The course is still available on tape, either as a cassette or reel-to-reel, for £1.98 through the British or Canadian branches of the Handicapped Aid Programme. It is compiled by the well-known author, linguist and DXer, Dr Richard E. Wood. It plays for over 80 minutes, gives spoken examples of 55 different languages and includes key words and hints on pronunciation. Broadcasts examples are made from studio tapes and not from over-the-air recordings.

Further information about this and other Radio Canada SW Club tapes can be obtained, for return postage from the HAP, 5 Hall St, Wombwell, Barnsley, S. Yorkshire S73 0JL or direct from CHAP, RR3, Colbourne, Ontario, Canada KOK ISO. Proceeds from the sale of these tapes are used to finance the world-wide activities of the Handicapped Aid Programme which includes the introduction of the handicapped or housebound to the hobby of DXing.

Language identification is of some importance to the m.w. DXer as interval signals are infrequently used on this band and national anthems are generally played only

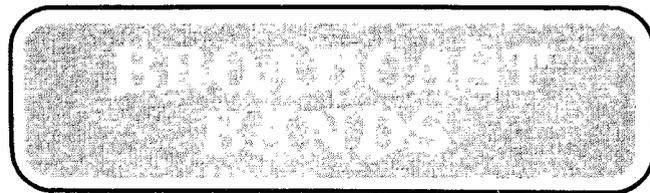at the end of a day's transmission. It is possible to become quite adept with language recognition even to the extent of being able to identify the particular brand of Spanish spoken in some regions of South America. The harsh and clipped variety spoken in Venezuela is often heard on the m.w.s and is easily recognisable.



SHORT-WAVE BROADCASTS

by **Charles Molloy G8BUS**

A note from **Jonathan Marks** of Austrian Short Wave Panorama mentions the new schedule for this well-known English DX programme. It is now on the air on Sundays at 0900 GMT on 6155 and 7170kHz (Europe) 9770 (SE Europe), 21 610 (Australasia and SE Asia), at 1805 on 6155 (Europe), 15 435 (E Africa), 15 560 (Middle East), 21 740 (S Africa), at 2305 on 5945 and 9770 (N America), 12 015 (S America). Reception reports and comments on the new timings can be sent to Austrian SW Panorama, Austrian Radio SW Service, A-1136 Vienna, Austria. (See also Part 2 of Jonathan's article on Short Wave Broadcasting in this issue—Ed.)

Frequency—Wavelength Conversion

Retired reader **Dorothy Porter** (Broxbourne) collects old radios from rummage sales etc., and she is currently using a Convair 1 receiver which is marked out from 13 metres to 1800 metres. She wonders if there is a table available which gives the equivalent values for metres and kHz. I hope Table 1 will fill the need. It is based on the formula: frequency times wavelength = 300 000 so that:

$$\text{kHz} = \frac{300\,000}{\text{metres}} \quad \text{and} \quad \text{metres} = \frac{300\,000}{\text{kHz}}$$

13m and 16m Bands

The 13 and 16 metre bands, which cover 21 450 to 21 750kHz and 17 700 to 17 900kHz respectively, are long-distance daytime bands. They go dead at night, but during daytime signals from all over the world can be heard. Radio Australia on 21 570 and 21 680kHz together with Radio Japan on 21 610, 17 710 and 17 810kHz are to be heard at breakfast time, while Radio New Zealand is on 17 770 until 0815. Later in the day, try for Radio Pakistan on 21 485 and 17 830, Radio RSA on 21 535 and 17 780, Sri Lanka on 17 850, Kuwait on 21 600, Lebanon on 17 710 and Radio Bangladesh on 21 670kHz.

There is some DX to be heard during the late evening on 16m from stations to the west, as the path in this direction is still mainly in daylight. Look for R. Havana Cuba on 17 750 and 17 855, Sao Paulo, Brasil on 17 815, Voice of Chile on 17 715. HCJB in Quito, Ecuador is normally conspicuous at this time but services from this

ELECTROVALUE

Your leading direct suppliers for

RESISTORS

Carbon Film ●

1/2 watt 1 to 10	E24 values (E12 over 1M)	ea. 2p
1/2 watt 47 to 4M7	E12 values	ea. 2p
1/2 watt 47 to 10	E24 values	ea. 2p
1 watt 4.7 to 10M	E12 values	ea. 3p

Metal Oxide ●

1/2 watt ElectroSil TR5 10 to 1M	2% E24 values	ea. 5p
-------------------------------------	---------------	--------

Metal Film

0.4 watt Mullard MR25 5.1 to 300K	2% E24	ea. 5p
--------------------------------------	--------	--------

Wirewound

1 watt 0.22 to 3.9	E12 values	ea. 15p
2.5 watt 1 to 1K	E12 values (vitreous)	ea. 26p
3 watt 1 to 10K	E12 values	ea. 16p
7 watt 1 to 10K	E12 values	ea. 16p

THERMISTORS ●

Discs - VA1039 500 **19p.** VAT1040 130, VA1100 15 **19p.**
VA1104 15-25 **59p.**

Plate and Bead (vacuum) types also available from **22p** to **£4.80** each.

Buying from **Electrovalue** can cost you even less when purchased together with other items from our Catalogue 9 (See pages 85/86 and discounts scheme). You will find practically everything you want in our Catalogue at good prices backed by good service - so start buying the Electrovalue way today.

V.A.T. Add 8% to all prices quoted here except those marked ● which carry 12½%. Prices subject to alteration without prior notice.

Discounts non-allowable on Barclaycard or Access.

ELECTROVALUE LTD

Dept. PW6, 24 St. Judes Road, Englefield Green, Egham, Surrey, TW20 0HB.
Phone Egham 3603. Telex 264475
Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester M19 1NA.
Phone (0611) 432 4945.

● **We pay postage.**
in U.K. on cw orders list value £5 and over. If under add 27p handling charge.

● **We give discounts**
On cw orders only 5% on list value £10 or more. 10% on orders list value £25 or more.

● **We stabilise prices**
By keeping to our printed price lists which appear, but three or four times a year.

● **We guarantee**
All products brand new, clean and to makers specs. No seconds, no surplus.


● **WE WILL SEND YOUR OUR 100 PAGE CATALOGUE NO. 9 FREE ON REQUEST**

Write, phone or call for your copy together with latest price list.

THE NEW EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £6.80 inc. VAT & P.P.

THE UNIQUE EUROBREADBOARD

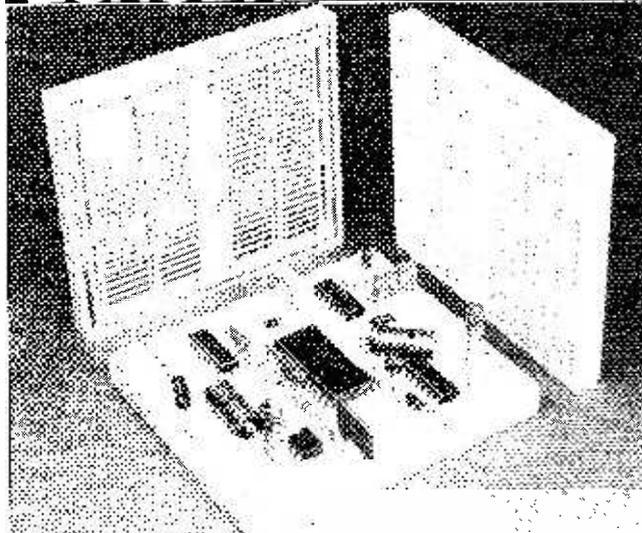

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF



PW879

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

Please send me 1 EuroSolderSucker @ £6.80 Please
or 1 EuroBreadBoard @ £5.80 Tick
or 2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).

Name

Company

Address

.

.

Tel. No.

Please make cheque/P.O.'s payable to David George Sales

SPECIAL OFFER SEMICONDUCTORS

TBA800 **50p.** LM3900 **40p.** 741 8 pin 6 for **£1.00.** NE555 **22p.** ZN414 **75p.** IN4005 10 for **35p.** 723 REGS **35p.** OC140 TRANS. **40p.** BX504 opto isolators **25p.** 2N5062 (100V 800MA SCR) **18p.**

MINIATURE TOGGLE SWITCHES. SPST 8x5x7mm **49p.** DPDT 8x7x7mm **53p.** DPDT centre off 12x11x9mm **78p.** **HEAVY DUTY TOGGLE DPDT 240V AC 10 amps 35p.**

MINIATURE SOLID STATE BUZZERS. 33x17x15mm white plastic rectangular case, output at 3 feet 70dB. Low consumption only 15mA. 4 voltage types available. 6-9-12 or 24V DC **75p** each. **LOUD BUZZER.** 50mm diameter 6 or 12 volts **60p.** **GPO ADJUSTABLE BUZZER, 6-12V DC 25p.**

DE-SOLDERING TOOL. Good suction. Teflon nozzle. **£4.75p.**

MOTORS. Miniature model motors 1.5-6V DC **20p.** 12V DC 5 pole motors **35p.** 8 track replacement motors 12V DC **55p.** 'Big inch' tiny precision motor 115V AC 3 rpm **30p.** Smiths Clock Motor Synchron. 240V AC 1 rev. per hour **£1.75p.**

SURPLUS BOARDS

No. 1 has 11 50V 2.5 amp scr's., one relay and various transistors including UJT **£1.95p.**
No. 2 car radio RF/IF boards 2 transistors, LM382 IC trimmers IF's etc. **85p.**
No. 3 car radio boards with 6 transistors including power output types IF's choke etc. **75p.**

TELEPHONE PICK UP COIL. Suction type with lead and plug **55p.**


Terms - Cash with order (or official orders from schools etc.) Postage **30p.** (Overseas at cost) VAT inclusive.
SAE for illustrated lists.

PROGRESSIVE RADIO

31, Cheapside,
Liverpool, L2 2DY

WEST HYDE CASES FOR P.W. PROJECTS

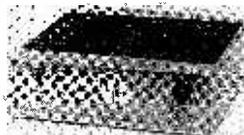VMOS TOP BAND TRANSMITTER (July 1979).
Classic case CL2 ADK **£11.02.**



CAR TEST PROBE (May 1979) Case PRB LPO **£1.78.**
P.W. HYTHE RECEIVER (February 1979).
Brightcase BC2 121X **£29.43.**

All the above prices include P. & P. and V.A.T.
Send for your free catalogue describing literally hundreds of cases
- see Feb. '79 "Production Lines".

WEST HYDE DEVELOPMENTS LTD.,
Unit 9, Park St. Industrial Estate, Aylesbury HP20 1ET
Aylesbury 20441. Telex 83570

station have had to be severely restricted as a result of a drought. This has affected the station's hydroelectric power station according to a report in Sweden Calling DXers.

The move to higher frequencies which is demonstrated by the amount of activity on the 11m band is also apparent on 16m and 13m. New channels are opening up, such as the Voice of Greece on 21 455 and 21 655 so it is worthwhile tuning carefully round both bands.

Table 1
Frequency/Wavelength Conversion Short, Tropical, Medium and Long wave Bands

Band	kHz	Metres
11m	25 600—26 100	11.72—11.49
13m	21 450—21 750	13.99—13.79
16m	17 700—17 900	16.95—16.76
19m	15 100—15 450	19.87—19.42
25m	11 700—11 975	25.64—25.05
31m	9500—9775	31.58—30.69
41m	7100—7300	42.25—41.10
49m	5950—6200	50.42—48.39
60m	4750—5060	63.16—59.29
75m	3900—4000	76.92—75.00
90m	3200—3400	93.75—88.24
120m	2300—2500	130.43—120.00
Medium Waves	531—1602	564.97—187.26
Long Waves	155—281	1935—1068

Digital Readout

"Is there a frequency counter on the market that would serve as a frequency readout for my receiver?" asks C. Smith of Pembroke, who admits to being confused by some of the adverts in current literature. The situation is rather confusing, mainly because an ordinary frequency counter will not do the job properly.

A frequency counter adds up the number of complete cycles occurring in a short period of time, and displays the result as the number of kHz (complete cycles in one second \times 1000). It is a marvellous product of modern technology, and on the face of it all one has to do is to join a counter to the receiver. Problems arise though when you try to do this. If you attempt to measure the incoming signal at some point, say at the input to the mixer, then there will be no display at all until you tune in a station! Moreover, there will be problems when measuring weak stations and the counter may get confused if there is interference. Why not measure the local oscillator (l.o.), whose strength is constant (more or less), and which is always generating something that can be measured? This is what is done but you will get an incorrect display because the frequency of the l.o. is not the same as the station the receiver is tuned to. The l.o. is usually higher than the incoming signal by the value of the intermediate frequency (i.f.). For example, if the i.f. is 465kHz and the receiver is tuned to 6055kHz then the l.o. will be generating $6055 + 465 = 6520$ kHz. Well, all you have to do is to subtract 465 from the value displayed, but if your mental arithmetic is anything like mine you will soon run into trouble. You could use a pocket calculator but this will be tedious if you are tuning around the band a lot. What you need is a counter that will do the subtraction for you. Such a counter would have an "offset" equal to the receiver's i.f.

Offset Counters

Chips are being produced that can be programmed by means of diodes to give one of a number of offsets. Ambit International (2 Gresham Road, Brentwood, Essex) produce an offset counter based on the OKI MSM5524 while Lowe Electronics (119 Cavendish Avenue, Matlock, Derbyshire) advertise a readout suitable for use with the Trio 9R59D or E. Rocquaine (Aldebaran, Le Coudre, Rocquaine, Guernsey, CI) offer their RG-3 frequency counter kit with an additional p.c.b., the RQ-30M which will "correct for any offset". All of the above advertise in *PW*.

For those wanting to build their own counters, two designs have appeared in *Practical Wireless*. The *PW* "Gillingham", published in the October 1978 issue with further information in May 1979, covered the band from medium waves up to 30MHz. The final page of the original article shows how to connect a counter to the local oscillator, and gives details of a suitable buffer amplifier should one be required. The second design, AM/FM Frequency Readout, appeared in the July 1979 issue and is based on another OKI integrated circuit, the MSM 5526. This unit is intended for the m.f. and v.h.f. broadcast bands only, and may therefore have limited appeal for readers of this column.

It cannot be long before all but the cheapest receivers will be equipped with digital readout. The cost will, to some degree, be balanced by the saving in tuning scales, drive mechanisms and bandsread arrangements. In the meantime, those of us like reader C. Smith will look around to see if there is any way we can up-date our existing gear.

Readers' Letters

Reader **Cliff Middleton** (Nottingham), who retired recently, has taken up DXing and he writes to say that he would like to be able to choose a country, set up a frequency and know that he is listening to the country of his choice. It is not too difficult to set a receiver onto a precise frequency, either by means of a crystal calibrator or with the aid of digital readout. To guarantee reception on any particular path is another matter. Propagation on the short waves is variable and this is one factor that makes the hobby so interesting. If you could tune in and be certain of perfect reception then DXing would soon lose interest, for me at any rate.

"Could you give me details of the Standard Frequency Transmissions on the h.f. bands?" asks **Roger Shepherd** of Whitstable, who uses a National Panasonic RF1105 with telescopic aerial. These stations are to be found on 2.5MHz, 5MHz, 10MHz, 15MHz and 20MHz, where they can be identified by the continuous clock ticking type of pulses they transmit. They are very useful for receiver calibration. 2.5MHz is the upper limit of the 120m band; 5MHz is within the 60m band; 10MHz is at the h.f. end of the 31m band; 15MHz below the l.f. end of the 19m band. These stations have been covered more fully in recent issues of this column especially in October 1978.

Radio New Zealand

Mrs D. L. Bonar (High Wycombe) has a National Panasonic RF2200 Direct Readout receiver and she says "This little portable with telescopic aerial surprises me." DX heard includes South America, Australia and Japan, but New Zealand has still to be logged. It is a difficult country to hear in the UK as the transmitters are low power (7.5kW) and they are not beamed to Europe.

COMPUKIT UK101 LOW COST SUPERBOARD IN KIT FORM



SPECIAL I.C. OFFER INTERSIL 7216A

D.C. to 10MHz counter/timer. Measures frequency, period, time intervals, etc. Drives 8 digit L.E.D. display direct. Low component count.

Normal price over £21 + V.A.T.

OUR SPECIAL PRICE INCLUDING FULL DATA, ONLY

£18.95

Including P&P and V.A.T. Displays available.

COMING SOON - 2 metre mobile rig. Fully synth. L.E.D. display. 50 Watt O/P.

ORDER FROM:-

COMTECH.

23B HIGH STREET,
STANSTEAD ABBOTTS,
WARE, HERTFORDSHIRE

SEND ONLY £10.00 DEPOSIT TO RESERVE ONE

A tape of 10 programs on cassette - educational games, etc. will be supplied free of charge with each kit.

Simple Soldering due to clear and concise instructions compiled by Dr. T. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

ONLY £219 + VAT + DEL.
including RF Modulator & Power supply.
Absolutely no extras.

INTRODUCTORY OFFER
ORDER BEFORE JULY 31st AND CLAIM
£10 DISCOUNT

FOR FURTHER DETAILS
Telephone: Harlow (0279) 415717.

The CompuKIT UK101 has everything a one board 'superboard' should have.


- ★ Uses ultra-powerful 6502 microprocessor.
- ★ 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays).
- ★ 48 chars by 16 lines - 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs.
- ★ Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen.
- ★ 8K full Microsoft Basic in ROM compatible with PET, APPLE SORCERER hence taking the headache out of programming by using simple English statements. Much faster than currently available personal computers.
- ★ Professional 52 Key keyboard in 3 colours - software polled meaning that all debouncing and key decoding done in software.
- ★ Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF.
- ★ Fully stabilised 5V power supply including transformer on board.
- ★ Standard KANSAS city tape interface providing high reliability program storage - use on any standard domestic tape or cassette recorder.
- ★ 4K user RAM expandable to 8K on board £49 extra.
- ★ 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller. (Ohio Scientific compatible).
- ★ 6502 machine code accessible through powerful 2K machine code monitor on board.
- ★ High quality thru plated P.C.B. with all I.C.'s mounted on sockets.

FULL CONSTRUCTION DETAILS IN P.E. AUG 1979 EDITION

Delivery date June 1979
at the 1979 MicroComputer Show
Customer orders in strict rotation only.

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

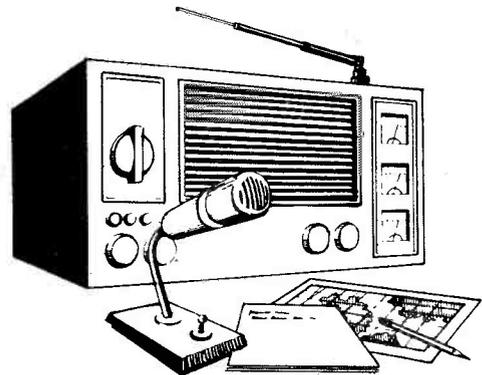

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure without obligation to:

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

WL879

Free!

WINDSCREEN WIPER CONTROL

Very speed of your wiper to suit conditions. All parts and instructions to make £3.75.



MICRO SWITCH BARGAINS

Rated at 5 amps 250V. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 (two types) for £1.25.



RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set £3.95.

MULTISPEED MOTORS

Six speeds are available 500, 800 and 1,000 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 3/8 in. diameter and approximately 1 in. long. 230/240V. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price £2.50



6 DIGIT COUNTER

One pulse at mains voltage moves 1 digit—not resettable—real bargain at 50p.



MAINS BLOWER

The Torin—quiet but powerful outlet size 2 1/2 x 1 1/2 for cooling equipment etc. Will extract of outlet is blowing outwards price £5.50. Other models from £2.00.



INDUCTION MOTORS

One illustrated is our reference MM11 made for ITT 3 stack 1 1/2 spindle £2.25 1 stack model £1.75. 1 stack £2.75. 1 1/2 stack £3.25.



EXTRACTOR FAN

Ex computers—made by Woods of Colchester. Ideal for fixing through panel—reasonably quiet running—very powerful 2500 rpm. Choice of two sizes 5" or 6 1/2" dia. £5. £6.



MAIN RELAYS

With triple 10 amp changeover contacts—operating coil wound for 230V a.c. Chassis mounting one screw fixing. Price £1.25.

BURGLAR ALARM ITEMS

(Circuit free on application) Trigger mats 24" x 18" £2.45 13" x 10" £1.95

Relay 24 volt 95p

9-12 volt 95p

Alarm Bell 24 volt £7.50

9-12 volt £2.25

Mains on application

Reset, Switch, ordinary 45p

Secret type with key 95p

Wire—100 metres £1.50

24v Power unit mains operated £5.35

MERCURY BATTERIES

Bank of 7 Mercury cells type 625 which are approx. 3/8 in. diameter by 3/4 in. thick in plastic tube giving a total of 10-7V. Being in a plastic tube it is very easy to break up the battery into separate cells and use these for radio control and similar equipment. Carton of 25 batteries £1.60.



PP3/PP9 REPLACEMENT

Japanese made in plastic container with leads size 2in. x 1 1/2in. x 1 1/2in. This is ideal to power a calculator or radio. It has a full wave rectifier and smoothed output of 9V suitable for loading of up to 100mA. £2.53.



MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.95.



CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electrically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45

Made up model £1.00 extra

8 POWERFUL BATTERY MOTORS

For models, Meccanos, drills, remote control planes, boats, etc. £2.




ROTARY PUMP

Self priming, portable, fits drill or electric motor, pumps up to 200 gallons per hour depending upon revs. Virtually uncorrodable, use to suck water, oil, petrol, fertiliser, chemicals, anything liquid. Hose connectors each end. £2.



SHORTWAVE CRYSTAL SET

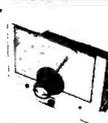Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 10, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1.94—crystal earphone 55p including VAT and postage.



MULLARD UNILEX

Ac mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of speakers this should sell at about £30—but due to a special 'bulk-buy and as an incentive for you to buy this month we offer the system complete at only £15 including VAT and postage.




HUMIDITY SWITCH

American made by Honeywell. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive micro-switch, quite sensitive—breathing on it for instance will switch it on. Micro 3 amp. at 250V a.c.




DELAY SWITCH

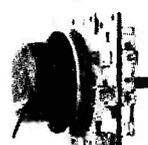Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact £1.50



25A ELECTRIC PROGRAMMER

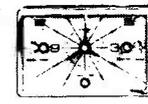Learn in your sleep. Have radio playing and kettle boiling as you wake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp on/off switch. Switch-on time can be set anywhere to stay on up to 8 hours independent 60 minute memory jogger. A beautiful unit. £4.50



MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied Model 1153 500mW, power, output £1.69. Model 1175—10 watts power output £3.94 Model 1172 1W, power output £2.25. Model EP9004 4 watt power output £2.90 EP 9001 twin channel or stereo pre-amp £2.90.



Absolutely brand new, in fact still in the makers packing cases. The H1200 primarily is a VDU with Ascii Keyboard, but it has many features which makes it ideal for almost any application from main frame to home MPU systems. Main features are:

- * 1920 Characters (80 c/24 lines)
- * V24/RS232 Interface
- * Selectable Baud Rates (110-9600)
- * Local, Half or Full Duplex
- * Screen Size 12" Diagonal
- * 55 Key TTY Format Keyboard
- * Automatic Scroll UP
- * Parity Error Indication
- * Ascii Code
- * Full Service Manual Available



Export and Trade enquiries welcome.

Sorry our quantity price does not apply to these but we welcome trade enquiries and where possible some small discount will be given, Price for the Terminal £350 + £24 Carriage.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £9.95.



MINI-MULTI TESTER

Amazing, deluxe pocket size precision moving coil instrument. Jewelled bearings—1000 opv—mirrored scale. 11 instant ranges measure:—DC volts 10, 50, 250, 1000 AC volts 10, 50, 250, 1000 AC amps 0-1mA and 0-100 mA DC continuity and resistance 0-150K ohms. Complete with insulated probes, leads, battery, circuit diagram and instructions. Unbelievable value only £6.50 + 50p post and insurance.

FREE Amps ranges kit enable you to read DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one send £1.50p.

TERMS: Cash with order—but orders under £6 must add 50p to offset packing, etc. BULK ENQUIRIES INVITED. PHONE: 01-688 1833. ACCESS & BARCLAYCARD ACCEPTED.

J. BULL (ELECTRICAL) LTD

(Dept. PW), 103 TAMWORTH RD., CROYDON CR9 1SG

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interest free list and it's free to send S.A.E. Below are a few of the Bargains still available from previous lines.

TELEPHONE ANSWERING MACHINES

We supply these machines on the understanding they are broken up or at least not used for their original purpose. The machines are second hand but so far as we can see they are complete and quite possibly in good working order. We do not test them but guarantee to replace any part of the machine should it be missing or faulty.

This Month's Snip is a brand new two piece intercom, with 50ft inter-connecting lead. Master station and sub-station in neat cream coloured cases suitable for office or home or as a baby alarm etc. These are new stock but some we understand may need slight attention. Offered at half regular price only £3.74.

Portable Fluorescent Lamp Ideal for camping but really a must for you if you are a motorist. You never know when you need a light and unlike the average torch this lamp will illuminate the whole engine. With a lead which you can plug into the car lighter socket thus its saving internal batteries. A real bargain complete with 9" tube ready to operate. Price £7.99.

Setting up a Weather Station? We have two only professional Anemometers. Quite complete i.e. a generator with its rotating cups weather proofed for mounting on a mast, and the measuring instrument which directly indicates wind speeds of up to 100 mph. Furthermore there is a facility for setting off an alarm should the wind speed reach a pre-determined level (adjustable) say 80 mph. These are brand new and complete with handbook. Price £189.

Enamelled Copper Wire Available on one pound reels or four ounce reels. We keep a stock of even numbered sizes but will also get odd numbered sizes to order. Price for 10, 12, 14, 16, 18 SWG £2.70 per pound, 20 SWG £2.70 per pound, 22 SWG £3.24 per pound, 24 SWG £3.78 + 25p per pound, £1.26 per quarter pound. Thinner sizes also available to order price on request.

Want a Cheap Electric Fan We can offer the 3" stack induction motor with a 6" 5 bladed fan, mount this on a stiff wire frame or a piece of handy angle and you will be able to keep yourself cool this summer.

Want a Million Resistors These are 1/2 watt, 1 watt and 2 watt types, all neatly packed in boxes with values clearly marked. Resistors themselves are colour coded and are perfectly standard, not every value of the range is included but they are reasonably spread over and there is not an unreasonably quantity of any one value. Ideal stock for retail shop or service depot. Price £1,000 + VAT.

Service Engineers Assortment I.F.'s and OSC Coils Standard for many Jap and Hong Kong portable radios and cassettes etc. 100 assorted price £5.60.

Heating Pad 11" x 8 1/2", water thin 250 watt. Price £1.16.

Heat and Light Lamp 500 watt tubular like a short fluorescent tube, ideal for paint drying etc. Price £3.95 + 20p, post and special packing £1.25.

Radiomobile Car Radio 12 volt L & M push button operation. £28.12.

Car Radio L & M and with F.M. good quality, Far Eastern make 12 volts. Price £19.95.

Maine Transformer 30 volts 2 amp secondary upright mounting, primary and secondary wound on separate bobbins for additional safety. Price £3.84.

Relay Plug in, 3 changeover in clear plastic case 12 volt D.C. or 25 volt A.C. (or 3 volt D.C.) same price.

Mercury Operated Switch Glass encapsulated, 15 amp with 12" very flexible leads. Price £1.62.

Special Multi-Core Cables 14-0076 cores, PVC insulated and colour coded and each core with metal screen, PVC outer cover. The following types in stock: 4 core 75p, 6 core 90p, 7 core £1.15, 12 core £1.50. All per metre + VAT. Cut to any length, carriage extra if order under £6.

0-1mA Panel Meter Flush mounting and in a waterproof case made for American equipment, scale divided into zones but not numbered. Price £2.70.

Tape Head Cleaners Suitable for any cassette or reel to reel machine. Special fluid (Isopropanol) in felt tipped dispenser. Price 35p.

Uniselecter Base mounting Tamsa 9 pole 12 way 50 volt operation. Price £4.86.

Plug in Uniselecter Ref No: AP 212958 definitely a piece of precision equipment, it measures approximately 5" high x 1 1/2" wide x 1" thick, plugs into a 20 pin base. Probable cost would be at least £20 each. We only have a few. £5.40.

Redoing Your Living Room? If you are thinking of making a log effect fire place, we have the fibre glass logs, which when lit up give the full log effect. Size approximately 7" x 10 1/2". Price £2.35.

Paper Motors Sometimes described as the motor with the built in fly wheel. These are used in many good quality tape recorders and in other equipment where wow and flutter has been reduced to a minimum. We have five different motor in stock, these are all physically about the same size (about 3" dia. x 2 1/2" deep). We quote their type numbers but we have no other technical information. Price includes the capacitor required. HSZ 20.50 - 4-540D dual voltage 125/220 50Hz. Price £7.50 + 60p + 50p p.p.

HSZ 20.50 - 4-255D 110V 50/60Hz £5.50 + 44p + 50p p.p. KLZ 20.50 - 4-540D 220V 50Hz £7.50 + 60p + 80p p.p. KLZ 20.50 - 4-425D 115V 60Hz £5.50 + 44p + 50p p.p. KLZ 20.50 - 4-468D 110V 50Hz £5.50 + 44p + 50p p.p.

Battery Condition Tester Suitable for most batteries. That is zinc carbon types, mercury, manganese, nicad, silver oxide and alkaline batteries. The tester puts dummy load on the battery and the meter scale indicates the condition by settling in a zone labelled 'Replace', 'Weak' or 'Good' etc. Complete in case, size approximately 3 1/2" x 6 1/2" x 2" with leads, probes and instructions. Price £5.95.

Torque Motors Elico (USA) make ref no: NCH3/1 1600 1/30 horse 150V 50Hz brand new condition. Unused spares for computers. Price £2.95.

Two Track Record/Playback Heads For transistor circuits with separate erase head. Special offer this month £1.08.

Cassette Mechanism Jap made to rigid specification. These will fit many music centres and cassette players. Chassis size approx. 4 1/2" wide x 5 1/2" deep. 6V motor and tape position control at the rear. The six levers for 'play', 'fast forward', 'rewind', 'stop', 'record' and 'eject' are all at the front, as is the auto mechanism to stop the motor when tape and is reached. These are new and unused and have stereo heads. Limited quantity. Price £15.25.


COOKER CLOCKS

All are less knobs and glass fronts, but you will no doubt be able to take these from the clock you are replacing. Replacements for Tricity and other well known cookers, these are also suitable for other timing operations, all are 230/40 working, with switches rating at 25-30 amps famous makes. Cat. No. 5856 L 40 amp, large clear dial size 5" x 3 1/2" approximately. Made by Lux Time Canada Ltd. This has a normal stop and start facility plus 60 second minute minder. Price £2.80. Cat. No. DDS 0863/2 made by Smiths, dial size approximately 4 1/2" x 3" this has the clock on the right hand side and the stop and start switches on the left hand side. There is no minute minder. Price £1.62 + 12p.

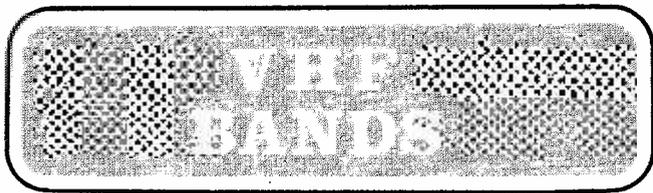A. D. Scholifield (South Shields) has been listening to the new RNZ outlet on 17770kHz between 0630 and 0815 with QRM at times from Radio RSA. He also picked up the transmission on 15345kHz on one occasion at 0340. Details of receiver and aerial were not given. Reception reports to RNZ should go to the Overseas Programmes Manager, RNZ, PO Box 2092, Wellington, NZ accompanied by two IRCs.

The B40 Receiver

"I must tear you off a strip for advising John Markey to connect a 50pF variable across his B40 r.f. stage. Severe misalignment would be the result," writes **A. J. Dixon** from Weymouth, who goes on to say that the anti-crossmodulation control on this set is a pretty useless gimmick and is best removed. Well, the capacitance will only be 50pF when the vanes are fully meshed; in the minimum position there should only be a few picofarads in circuit. The anti-crossmodulation control, which must be unique on receivers, applies an adjustable positive potential to the control grid of the first r.f. valve and this should, I think, have some effect on crossmodulation. Has anyone tried using this control? Perhaps it was intended for use in close proximity to a transmitter such as would occur on board ship. Reader **Roderick Williams** would like to form a club for B40 owners, replies direct to Roderick please, who lives at 54 Woodlands Avenue, Talgarth, Brecon, Powys LD3 0AT, not forgetting to enclose return postage.



by Ron Ham BRS15744

Although no major v.h.f. disturbance took place between April 18 and May 21, my readers, as usual, concentrated their efforts on the many less important events which often occur and may otherwise have passed by unrecorded, showing once again that the v.h.f. bands are never dull.

Solar

An eleven-day period of solar activity began on April 24 when **Cmdr Henry Hatfield**, Sevenoaks (on 136MHz) and myself (on 146MHz) recorded a mild noise storm followed by four days of small, short-duration bursts. Further noise storms were recorded on April 29 and May 1 and a few individual bursts again on the 4th and 5th. **Robin Knight**, South East Essex Astronomical Society, recorded solar noise at 60MHz on April 29 and at 134MHz when they were testing their new radio telescope. Henry Hatfield received three bursts of solar noise at 1296MHz between 0800 and 1000 on the 30th and, later in the day, he saw five sunspot groups with his spectrohelioscope, two of which were large groups accompanied by five long filaments and two arched filaments. Henry saw another arched filament on May 2 and was delighted

when, at 1250, he recorded a burst of noise at both 1296 and 136MHz giving him his first positive correlation between these two widely-separated radio frequencies.

The 134MHz instrument now in use by SEEAS comprises a Yagi aerial, home-brew BFW10 f.e.t. pre-amplifier, Microwave Modules converter, an early Eddystone communications receiver, followed by a 741 d.c. amplifier driving an Evershed and Vignoles pen recorder. Robin Knight told me that the members of SEEAS all thoroughly enjoyed Henry Hatfield's talk, early in May, about his spectrohelioscope and radio telescopes. Further bursts of solar noise were recorded on May 12, 14 and 19 at 136 and 146MHz, and at 1500 on the 18th a 10 minute burst was recorded at 60MHz.

The brief auroral event during the late afternoon of April 25, reported by **John Branegan** GM8OXQ, Saline, Fife, was no doubt caused by the solar storm on the previous day.

The 10 Metre Band

The solar activity also upset the 10m band, because frequent checks between 0700 on the 22nd and 1100 on the 24th, found the band dead, as it was at midday on the 25th and early on the 26th. Strange things were happening, because at midday on the 26th and early on the 27th, the only signal I heard on 10m came from the Cyprus beacon, 5B4CY. The band was also dead during the early mornings on the 28th, 29th and 30th, confirmed by **Ron Nugent** G2FTS, Polegate, Sussex, yet, at times on these days it would open up, as **Steve Harris** RS41444, Goring-by-Sea, Sussex, pointed out. During the evening of the 29th he received strong c.w. signals from PY2ZBO and PY5EG. While in France, Steve held the call-sign F6LUC, and now, at home he enjoys listening on the DX bands with a Trio 9R59D fed with a Hygain, 18 AVT/WB-A vertical aerial. For portable use he has a National Panasonic DR28, which he also uses for Band II DX.

Gordon Goodyer, Petworth, has changed his rig to a Drake R4B, fed with a long wire in the loft for 80m and a dipole for 20 and 10m, and is delighted with the set's performance on all bands. **Neil Clarke** BRS34306, Knottingley, West Yorks, has heard strong signals from the Mauritius beacon, 3B8MS, on its new frequency, 28.210MHz and, like myself, has frequently heard the beacons in Bahrain A9XC, Cyprus 5B4CY and much less frequently, the German beacon, DLOIGI. Neil also reports hearing a new beacon around 1700 on 28.315MHz, sending its call-sign, ZS6DN, every 18 seconds. Strong signals, often peaking 599, were heard from the Cyprus beacon around 1300 on April 27 and 30, May 3, 4, 10, 13, 14, 16 and 18.

From the USA

John Keegan is now back in Steyning, Sussex, after a 6 month business trip to New York. While there, John used a 40-channel scanner for CB listening and often heard families returning home in their cars, with mum, at home, as base station net controller. "It's not uncommon" said John, "to see homes with high, ground-plane aerials for their 5 watt rigs, or notices on highway bridges telling motorists which CB channel to use if help is required." Like most of us, John has mixed feelings about CB, because, at times, in the cities the band is unusable through overcrowding. "On the other hand," he said "it's a godsend on the highway, if you are in real trouble, like a puncture, breakdown or witness an accident, you reach for your CB and call 'Smokey' for help".

DX TV

With the 1979 sporadic-E season close to hand it was not surprising to see bursts of test card from Poland on Channel R1, 49.75MHz, at 0815 on April 24, 0752 on the 27th, and 0807 on May 2. At midday on May 18, I feel sure an F2 opening to Scandinavia occurred, because I received strong test cards from Norway, Melhus, on E2 and Sweden, TV1 on E3 but none of the usual evidence of Sp.E. This event gave me a chance to try my new National Panasonic T5001G, with a vertical dipole on the European v.h.f TV band, channels 2-4, 48-68MHz, and I am very pleased with its performance. **Ian Roberts**, Glenstantia, Rep. South Africa, writes "F2 has been monitored as usual and has been quiet of late, but suddenly picked up on April 23 with Spain on E2 and Italy on 1A. On the 24th, Spain was again very strong." Many thanks for the report Ian, and congratulations on passing your Morse test.

The first real sporadic-E disturbance of 1979 took place during the afternoon of May 21 when **John Matthews** G3WZT, Horsham, worked YU and SV on 2m s.s.b. and **Ian Rennison**, also in Horsham, received Italian Television pictures on his JVC 3040 and heard many Italian f.m. broadcast stations in Band II. **Peter Penfold** in nearby West Chiltington, also using a 3040, watched Italian adverts, **Guy Stanbury** received pictures from Rumania and Spain, and I saw a cartoon film from Poland on Channel R1.

CQ Air Cadets

David Whitfield, G8RVK, Worthing, is busy building a unit to change his 2m Yagi from horizontal to vertical and back again and hopes in the near future to start constructing gear for 10GHz. David, himself a Sergeant cadet in the Worthing 45F squadron, ATC, wishes to contact any readers who are also in the Air Training Corps with a view to having skeds with them and possibly a regular net.

DX Ladder?

John Cleaton G4GHA, Wareham, Dorset, uses a Trio 700S and a linear to a 6-element quad aerial and gets a great deal of enjoyment just listening around the bands. John also suggests that we should run a Countries or QRA Squares ladder; what about it readers? Let me know how you feel on this one.

Satellites

"OSCAR 7B is working well" writes John Branegan, "I have quite a few QSOs with old and new friends. OSCAR 8J is as good as ever" and several new stations have come on who John hopes to work. All of them, old friends and new, will have to get used to a new call-sign because he has passed his Morse test and by now may be a GM4.

Tropospheric

Throughout the period, April 18 to May 20, v.h.f. conditions were generally good, because, for at least 23 days, the atmospheric pressure was above 30.0in and at times reached 30.4in. Continental broadcast stations were just audible in Band II on April 21, and I received pictures from Lichfield on Channel 8, 189MHz, and strong signals through the Bristol Channel repeater GB3BC, R6. On the same day, **Alan Baker** G4GNX, Newhaven, was working into France on 2m s.s.b., and between 1300 and 1600 on the 22nd he made c.w. contacts on 2m with

ON5FF, ON5UN and F6FDR. At 2022 on the 27th, F6AID worked Alan via the Brighton repeater GB3SR, R3, and around 2200 on the 29th, Ron Nugent, **Dermot Cronin** G4GRO, on the Royal Sovereign Light and G4GNX had a round-table QSO, first among themselves and then with F1FHA in Paris via GB3SR.

Conditions were good on May 5 and 6 for a Continental 2m contest and during the evening of the 5th, G4GNX worked F1ENH/P, two ONs and a PAO on 2m s.s.b., and ON7DV on c.w. **John Cooper** G8NGO, Cowfold, Sussex, worked 23 stations, including four ONs, three PAOs, a DJ and PA0NIE/LX/P in Luxembourg on s.s.b. during the same event. John is eagerly awaiting QSL cards for his many contacts on 2m because he is after the QRA Locator Square Award offered by the RSGB.

I heard an interesting QSO during the early afternoon on May 9 between EA2OZ/MM aboard ship in the English Channel and G8PTC/push-bike mobile, near Croydon, through the Hampshire repeater GB3SN, R5. On May 13, John Cooper worked 29 French stations and a GU, all with 12 watts, and heard DJ and PAO on 2m s.s.b. Both **Derek Knight**, Storrington, Sussex, using a Sharp stereo and **John Bugler**, Wimborne, Dorset, using a Grundig Yacht Boy, reported that Band II was open to the Continent and northern UK for most of the 13th and 14th. Also on the 14th, I heard signals through the Malvern Hills repeater GB3MH, R3 and a QSO between G8PMU, Hornchurch, Essex and G8RAL/P, Southend, via the Bristol Channel repeater. F3NW and G4GNX took advantage of these conditions for a QSO through the new French repeater FZ2VHF, at Boulogne on R5. By now this repeater, situated some 210 metres a.s.l., should be running about 50 watts and your reports will be welcomed by F2XO and F3NW, QTHR.

BBC Programme for Sussex Amateurs

Seven members representing the Brighton and District Radio Society, the Mid-Sussex Amateur Radio Society and the Worthing and District Amateur Radio Club met producer Ian Collington at the studios of BBC Radio Brighton on May 14 to inaugurate a fortnightly programme for radio amateurs in the Radio Brighton area.

A joint broadcasting committee consisting of one delegate from each club was formed and the first programme, aptly named *Call-Sign* and presented by Ron Ham, was then recorded and transmitted at 1848 on the 16th. Future programmes of ten minute duration will be planned by committee members, **Nigel Hewitt** G8JFT, Brighton, **Jack Brooker** G3JMB, Mid-Sussex and **Bob Jones** G3YIQ, Worthing and presented by Ron Ham.




First recording of *Call-Sign* in the Radio Brighton studio. Left to right . . . Ron Ham and Ian Collington and programme guests, **Eric Godsmark** G5CO, **Alan Baker** G4GNX and **Ron Kingstone** G4HHB

THREE FOR FREE FROM CSC

ELECTRONICS BY NUMBERS
FREE PROJECTS
No 1, No 2,
& No 3.

ELECTRONICS BY NUMBERS LED BAR GRAPH UNIVERSAL INDICATOR

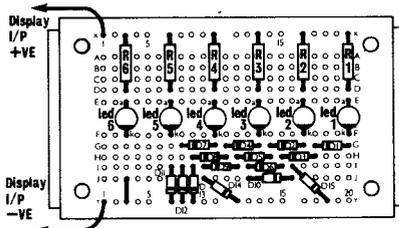Now using **EXPERIMENTOR BREADBOARDS** and following the instructions in "Electronics by numbers" ANYBODY can build electronic projects. Look at the diagram and select R1, this is a resistor with a value between 120 to 270 ohm. Plug it into holes X20 and D20, now take LED 1 and plug it into holes E20 and F20. Do the same with the Diodes e.g. plug D7 into holes G7 and G10.



YOU WILL NEED

EXP- ANY EXPERIMENTOR BREADBOARD

D1 to D15 - Silicon Diodes (such as 1N914)
R1 to R6 - From 120-270 ohm resistors ¼ watt.
LED1 to LED6 - Light emitting diodes.

LED BAR GRAPHS are replacing analogue meters as voltage-level indicators in many instances.

This circuit uses the forward voltage drop of diodes to determine how many LEDs light up. Any type of diode can be used but you must use all the same type. For full working details of this circuit fill in the coupon. If you have already built the Two-transistor Radio and the Fish'n'cliks projects you will find that you can reuse the components from these projects to build other projects in the series.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE FULL COPIES OF "ELECTRONICS BY NUMBERS" PROJECTS No 1, No 2 and No 3.

PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



PC - 16 pin. £2.75.
PC - 16 pin with cable. £6.00.
PC - 16 with cable and 16 pin clips at both ends. £10.25.



Europe, Africa, Mid-East: CSC UK LTD.
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: SAFFRON WALDEN 21682.
Telex: 817477.

EXPERIMENTOR BREADBOARDS.


No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


EXP.325. The ideal breadboard for 1 chip circuits.
Accepts 8,14,16 and up to 22 pin IC's.
ONLY £1.60.




EXP.350. £3.15.
270 contact points with two 20-point bus-bars.

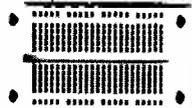

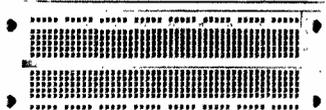EXP. 300.
550 contacts with two 40-point bus-bars.
£5.75.



EXP. 650 for Micro-processors. **£3.60.**

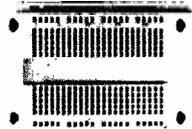

EXP 4B.
More bus-bars.
£2.30.




ALL EXP.300 Breadboards mix and match with 600 series.

PROTO-BOARDS.

THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST. TWO EASILY ASSEMBLED KITS.



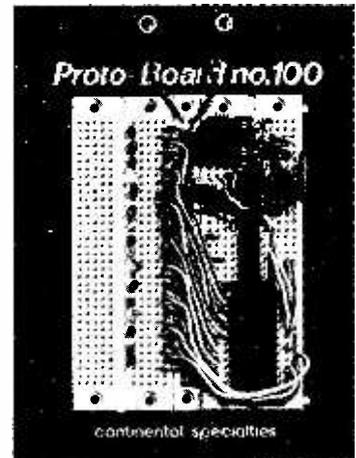PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.
PROTO-BOARD 6 KIT. £9.20.



PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.
PROTO-BOARD 100 KIT £11.80.

HOW TO ORDER AND RECEIVE FREE COPY OF TWO-TRANSISTOR RADIO PROJECT, FISH'N'CLIKS AND LED BAR GRAPH.

CSC UK LTD. Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
TEST CLIPS			
PC. 16.			£ 3.78
PC.16-18.			£ 7.56
PC. 16-18 Dual Clip.			£12.15
PROTO-BOARDS.			
PB. 6.	630	6	£11.01
PB. 100.	760	10	£13.82

NAME
ADDRESS
DEPT. 6T2

FILL IN COUPON & RECEIVE FREE COPY OF ELECTRONICS BY NUMBERS PROJECTS Nos 1, 2 AND 3

TTLs BY TEXAS		74291		160p		74LS192		140p		74C157		250p		LINEAR I.C.s		TRANSISTORS		TIP41C		2N3866		DIODES	
7400	13p	7497	180p	74291	140p	74LS193	140p	74C160	155p	*AY1-0212	600p	*MC1496	100p	AC127/8	20p	BFY51/2	22p	TIP42A	70p	2N3903/4	18p	*BY127	12p
7401	14p	74100	130p	74295	250p	74LS195	140p	74C161	155p	*AY1-1313	688p	*MC3340	120p	AD149	70p	BFY56	33p	TIP42C	82p	2N3905/6	20p	*OA47	9p
7402	14p	74104	85p	74295	90p	74LS196	120p	74C162	155p	*AY1-5050	212p	*MC3360	120p	AD161/2	45p	BFY90	90p	TIP2955	78p	2N4036	85p	*OA81	15p
7403	14p	74105	65p	74278	290p	74LS221	100p	74C163	155p	AY5-1224A	225p	*MFC4000B	120p	BC107/8	11p	BLY83	700p	TIP3055	70p	2N4058/9	12p	*OA85	15p
7404	17p	74107	34p	74279	190p	74LS240	175p	74C184	120p	*AY5-1315	800p	*MC50998	750p	BC109	11p	BRV38	45p	BX19/20	20p	2N4060	34p	*OA90	9p
7405	18p	74109	55p	74284	400p	74LS242	175p	74C174	160p	*AY5-1320	320p	*NE540	200p	*BC147/8	9p	*BU105	190p	*T1S93	30p	2N4061/2	18p	*OA91	9p
7406	32p	74110	55p	74285	400p	74LS243	175p	74C175	210p	*CA5019	800p	*NE543K	225p	*BC151/8	10p	*BU108	250p	*ZTX108	12p	2N4123/4	22p	*OA95	9p
7407	32p	74111	70p	74290	150p	74LS245	175p	74C192	150p	*CA5046	70p	NE555	25p	*BC159	11p	*BU205	220p	*ZTX500	11p	2N4125/6	22p	*OA200	9p
7408	19p	74118	200p	74293	150p	74LS251	200p	74C193	150p	*CA3048	225p	NE556	70p	*BU208	240p	*BU208	240p	*ZTX502	15p	2N4289	20p	*OA202	10p
7410	15p	74119	210p	74294	200p	74LS257	120p	74C194	220p	CA3080E	72p	NE561B	425p	*BU406	145p	*BU406	145p	*ZTX504	30p	2N4401/3	27p	*OA205	10p
7411	24p	74120	110p	74298	200p	74LS259	175p	74C195	110p	*CA3089E	225p	NE562B	425p	MJ461	175p	MJ461	175p	*ZTX507	250p	2N4427	60p	*OA206	10p
7412	20p	74121	28p	74356	150p	74LS373	200p	4000	SERIES	CA3090A/Q375P	100p	NE566	155p	BC179	18p	MJ2501	225p	2N697	25p	*2N5089	27p	1N4003/4	6p
7413	30p	74122	48p	74367	150p	74LS374	195p	4000	SERIES	CA3130S	100p	NE567	175p	*BC182/3	10p	MJ2955	100p	2N697	45p	*2N5172	27p	1N4005	6p
7414	60p	74123	55p	74368	150p	81LS95	120p	4001	17p	CA3160E	75p	RC4151	50p	*BC184	11p	MJ3001	225p	2N706A	20p	2N5179	27p	1N4006/7	7p
7416	27p	74125	55p	74390	200p	81LS98	160p	4002	17p	FX209	750p	*SN7603N	140p	*BC187	30p	*MJE340	85p	2N708A	20p	2N5191	83p	1N5401/3	14p
7417	27p	74126	60p	74393	200p	81LS99	120p	4006	95p	ICL7106	925p	*SN76013N	140p	*BC214	12p	MJE2955	100p	2N918	45p	2N5194	80p	*ZENERs	4p
7420	17p	74128	75p	74490	225p	81T28	230p	4007	18p	ICL8038	340p	*SN76013ND	140p	*BC461	36p	*MJE3055	70p	2N930	18p	*2N5245	40p	2.7V-33V	19p
7421	40p	74132	75p	74 LS	9301	160p	4008	80p	LM301A	36p	*SN76023N	140p	*BC477/8	30p	*MJE3055	70p	2N1131/2	20p	2N5245	40p	400 W	9p	
7422	22p	74136	75p	SERIES	9302	175p	4009	80p	LM311	190p	*SN76023ND	140p	*BC516/7	30p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	1 M W	15p	
7423	34p	74141	70p	18p	9303	160p	4010	80p	LM312	200p	*SN76033N	175p	*BC547/8	18p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 741	4p	
7425	30p	74142	70p	74LS02	18p	9308	316p	4011	17p	LM324	70p	*SP8515	750p	*BC557B	18p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7426	40p	74145	90p	74LS04	20p	9310	275p	4012	17p	LM339	90p	*S8515B	750p	*BC557B	18p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7427	34p	74147	190p	74LS08	22p	9311	275p	4013	50p	LM348	95p	*S8515B	750p	*BC559C	18p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 555	4p
7428	36p	74148	150p	74LS10	22p	9314	165p	4014	84p	*LM377	175p	*S8515B	750p	BCY70	18p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7430	17p	74150	100p	74LS10	22p	9314	165p	4015	84p	*LM380	75p	*S8515B	750p	BCY71/2	22p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7432	30p	74151A	70p	74LS13	38p	9316	225p	4016	84p	*LM381AN	150p	*S8515B	750p	BD131/2	50p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 741	4p
7433	40p	74152	70p	74LS14	100p	9322	150p	4017	80p	*LM389N	140p	*S8515B	750p	BD156	20p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7434	35p	74154	100p	74LS20	22p	9322	150p	4018	89p	*LM399	140p	*S8515B	750p	BD200	32p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7438	35p	74155	90p	74LS22	28p	9368	200p	4019	45p	LM710	50p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 555	4p
7440	17p	74156	90p	74LS27	38p	9374	200p	4020	100p	LM733	100p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7441	70p	74157	70p	74LS30	22p	9601	200p	4021	110p	LM741	29p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7442A	60p	74159	190p	74LS37	90p	9602	175p	4022	110p	LM747	29p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 555	4p
7443	112p	74160	100p	74LS38	60p	9603	60p	4023	110p	LM747	70p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7444	112p	74161	100p	74LS38	60p	9603	60p	4023	110p	LM747	70p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7445	100p	74162	100p	74LS74	40p	9603	60p	4023	110p	LM748	35p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 555	4p
7446A	93p	74163	100p	74LS75	50p	9603	60p	4023	110p	LM748	35p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7447A	70p	74164	120p	74LS75	50p	9603	60p	4023	110p	LM748	35p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7448	80p	74165	130p	74LS83	110p	MC1488	100p	4025	20p	LM3800	70p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 555	4p
7449	17p	74166	140p	74LS85	100p	MC1489	100p	4025	130p	LM381AN	150p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7451	17p	74167	140p	74LS86	100p	75107	160p	4025	50p	LM4136	120p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7452	17p	74168	140p	74LS86	100p	75182	230p	4025	50p	MC1310P	150p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	100+ 555	4p
7453	17p	74170	240p	74LS90	60p	75182	230p	4025	100p	MC1458	55p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	*SPECIAL	4p
7454	17p	74172	240p	74LS93	60p	75450	120p	4030	55p	MC1495	400p	*S8515B	750p	*BF256B	70p	*MJE3055	70p	2N1131/2	20p	*2N5401	50p	OFFERS	4p
7460	17p	74173	120p	74LS107	45p	75451/2	72p	4031	200p	VOLTAGE REGULATORS													
7470	36p	74174	93p	74LS112	75p	C-MOS I.C.s		4033	180p	Fixed Plastic TO-18													
7472	30p	74175	85p	74LS123	100p	74C00	25p	4033	200p	1A -1-ve													
7473	34p	74176	90p	74LS132	90p	74C02	25p	4034	110p	5V 7805	75p	5V 7805	100p										
7474	30p	74177	90p	74LS133	90p	74C04	27p	4041	80p	12V 7812	75p	12V 7912	100p										
7475	36p	74178	160p	74LS138	60p	74C08	27p	4042	80p	15V 7815	75p	15V 7915	100p										
7476	35p	74180	93p	74LS139	60p	74C10	27p	4043	90p	18V 7818	90p	18V 7918	100p										
7480	50p	74181	200p	74LS151	60p	74C14	90p	4044	90p	24V 7824	90p	24V 7924	100p										
7481	100p	74182	60p	74LS159	60p	74C20	27p	4047	110p	100mA TO-32		100mA TO-32											
7482	84p	74184	150p	74LS159	60p	74C20	27p	4047	110p	5V 7805	35p	5V 7905	80p										
7483A	90p	74185	150p	74LS160	100p	74C22	36p	4048	55p	12V 7812	35p	12V 7912	80p										
7484	100p	74186	700p	74LS161	100p	74C42	110p	4049	32p	15V 7815	35p	15V 7915	80p										
7485	110p	74190	100p	74LS162	140p	74C48	250p	4050	49p														
7488	34p	74191	100p	74LS163	100p	74C73	75p																

PE SINGLE BOARD COMPUTER

PE presents...

COMPUKIT UK 101


It compares very favourably with machines three times its price and is similar to Superboard II (recently reviewed by us) using the same 8K *Microsoft, full feature, BASIC* which runs faster than other currently available personal computers. Faster than some business computers.

Its features are:

- **Up to 8K RAM on board.**
- **Fully expandable via on board sockets.**
- **Cassette interface (CUTS).**
- **VDU — with its own dedicated RAM (1K).**
- **Full ASCII keyboard.**
- **U.H.F. modulator on board.**
- **P.S.U. on board, transformer included in kit.**
- **Full machine code monitor (2K) and I/O utilities in ROM.**
- **Upper and lower case plus graphics and gaming characters.**

It will mate with all Superboard extras. For example:

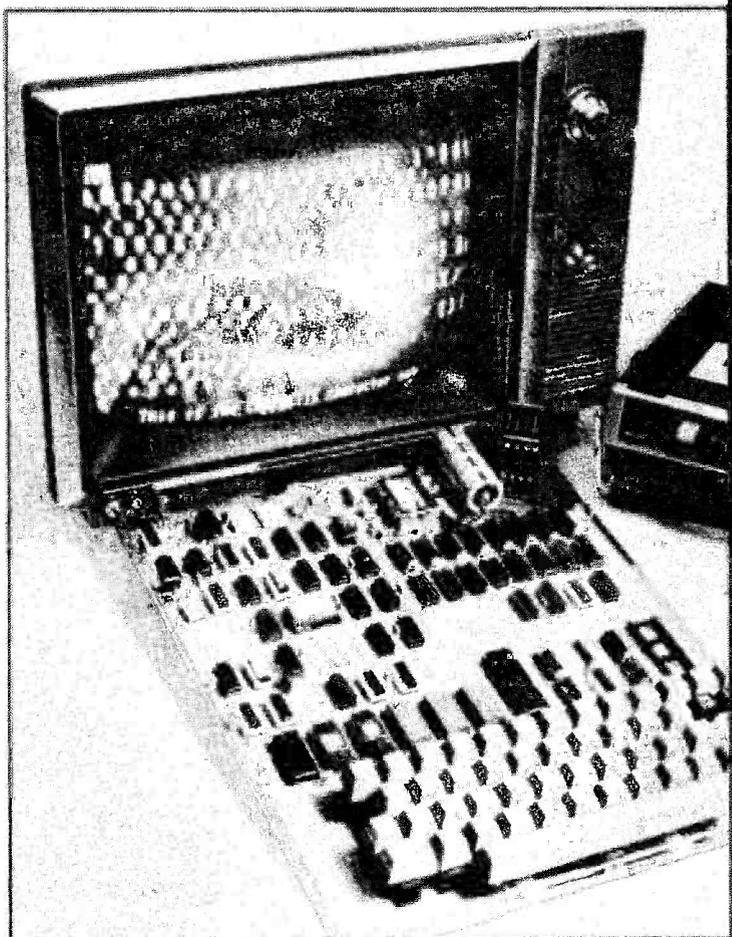- **Expander board for up to 24K static RAM.**
- **Mini-floppy interface.**
- **Port adaptor for printer and modem.**
- **OSI 48 line expansion interface.**



CompuKit UK 101 will sweep the board in the hobby computer field. It is an excellent design with full feature (not Tiny) BASIC. A complete kit will be available from *Computer Components* for £219+VAT.

FULL CONSTRUCTIONAL DETAILS STARTING IN

PRACTICAL ELECTRONICS

AUGUST ISSUE ON SALE FRIDAY, 13 JULY



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7, & 10 mfd. — 5p.
22, 47—5p. (50V—6p.), 100—7p. (50V—8p).
220—8p. (50V—10p.), 470—11p. (40V—16p).
1000/15V—15p. 1000/25V—18p. 1000/40V—35p.

Subminiature bead tantalum electrolytics.
0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 6.3V—9p.
2.2/35V & 4.7/25V—10p 10/25V, 15/16V—14p.
22/16V, 33/10V, 47/6V, 68 & 100 @ 3V—16p.

Mullard Miniature Ceramic E12 Series 63V 2%,
10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.

Vertical Mounting Ceramic Plate Caps 50V.
E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p.

Polystyrene E12 Series 63V, Hor. Mounting.
10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p.

Mullard Polyester 250V Vert. Mtg. E6 Series.
.01 to .1—4p., .15, 22—5p., 33, 47—8p.
.68—11p. 1.0—14p. 1.5—20p. 2.2—24p.

Mylar (Polyester) Film 100V. Vertical Mtg.
.001, .002, .005—3p., .01, .02—4p., .04, .05—5p.

Miniature Film Resistors Highstab. E12 5%.
0.125 watt 10 Ω 2MΩ.....1p
0.250 watt 1 Ω to 10MΩ, (10% over 1M).....1p
0.500 watt 10 Ω to 2MΩ.....2p
1.000 watt 10 Ω to 10MΩ.....2p

1N4148—2p, 1N4002—4p, 1N4006—6p, 1N4007—7p
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—9p.
8 Pin DIL ICs 741s—18p. 555s—24p.

20mm. fuses .15, 25, 5, 1.0, 2.0, 3.0 & 5A—3p.
20mm. fuseholders P.C. or Chassis Mtg.—5p.
Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

AM/CW/SSB COMMUNICATION RECEIVER and preselector modules. 453.5 kHz Mech. Filter Modules 2.1 kHz BW, with diode-switching.

CRYSTALS Brand new high precision HC33/U: 1.0, 2.0, 3.0, 1.008, 2.5625 MHz £3.35, 1.28 MHz £4.15. HC13 100 kHz £3.25. HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 10.0, 10.7 MHz £3.00, 18.0, 20.0, 38.6667, 48.0, 100.0, 116.0 MHz £3.50. HC25/U 8.08333 MHz (S20) £3.00.

Large stocks of standard freqs for MPU etc. Any freq made to order 6 weeks from £3.75.

WINKLE PICKERS. Winkle out DX from the QRM with pin-sharp 250 Hz 8-pole crystal CW filters specially manufactured to fit TRIO and YAESU: FT/FR-101, FT-301, TS-520, TS-620, £25-30 each.

All prices inc. VAT and UK post. SAE Lists.

P. R. GOLLEGE ELECTRONICS

G3EDW, Marriott, Somerset, TA16 5NS
Tel: 0460 73718

THE VINTAGE WIRELESS COMPANY

1920 to 1950

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet.

THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.

SMALL ADS

The prepaid rate for classified advertisements is 22 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Tel: 31803. No Lists. Enquiries S.A.E.

D.Y.M. THERMOMETER KIT

Based on the ICL7106 single chip DVM the kit contains a 3 digit LCD, a PCB ICL7106, and all components and instructions to make a 0-200mV FSD DVM. Components also supplied to enable this to be converted to a digital thermometer. Requires a 2mA 9V supply (PP3 battery). **ONLY £20.75**

TOUCH CONTROLLED LIGHTING KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touch plates. Easy to follow instructions. **£5-50**

NEW! TD300K—TOUCHDIMMER! Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. **£5-50**

—Extension kit for TD300K permits operation from another location, two-way switching, etc **£1-50**

TS300K—ON/OFF TOUCHSWITCH. Two touch plates **£4-30**

TS4300K—AUTOMATIC TOUCHSWITCH. Time delay variable 2 secs to 3½ mins. **£4-30**

LD300K—300W LIGHTDIMMER KIT 10% discount on any 4 lighting control kits. **£2-90**

TS300K—ON/OFF TOUCHSWITCH. Two touch plates **£4-30**

LD300K—300W LIGHTDIMMER KIT 10% discount on any 4 lighting control kits. **£2-90**

24 HR. CLOCK/APPLIANCE TIMER KIT

Switches any appliance of up to 1kW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs and full instructions. **£14-90**

White box 56 x 131 x 71 mm with red Acrylic window **£2-20**

White box as above ready drilled for kit Ready-built in box, incl. mains cable **£22-50**

400V PLASTIC TRIACS	OPTO	COMPONENTS
3A 49p	0.2" dia LEDs	555 24p (4 for 90p)
3A 62p	Red 12p (£1/10)	741 22p (5 for 90p)
12A 70p	Green 17p	LM3911
18A 90p	Yellow 17p	Temperature control IC £1.00
25A 185p	DL727 £1.50	ZN1034E £1-80
25A 190p	LCD 0.5" £8-10	ICL7106 £7-50
5A with trigger 80p	LDR slm	TC106D SCR 50p
8A* 80p	ORP12 50p	2N6027 34p
*isolated tab	Neon 8p	AY-5-1230 £4-50
DIAC 18p		

QUANTITY DISCOUNTS ON REQUEST
ADD 8% VAT + 25p P&P. Callers by appointment only.
Tel: 01-579 9794
T. K. ELECTRONICS
106 STUDLEY GRANGE ROAD, LONDON W7 2LX

100 MIXED COMPONENTS £2.75, 10 LEDs 90p. Lists 15p. Sole 37, Stanley Street, Ormskirk, Lancs. L39 2DH.

VALVES

Radio - T.V. - Industrial - Transmitting
Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 30p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.
Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN
West Wittering 2023 (STD Code 024366)

Aerials

SHORT WAVE LISTENERS, Indoor Aerials £10.88 and £17.95. Outdoor £19.95 and £30.50, lists large SAE. New Publication "Indoor and Invisible Aerials" £3.24. G2DYM, Uplowman, Tiverton, Devon.

AERIAL BOOSTERS

Improves weak VHF Radio and Television reception.
B45-UHF TV, BII-VHF Radio.
For next to the set fitting.
Price £5. S.A.E. for Leaflets.

ELECTRONIC MAILORDER LTD,
Ramsbotton, Bury, Lancs, BLO 9AG.

Books and Publications

Build your own P.A., GROUP & DISCO SPEAKERS
by R. F. C. Stephens
Save money with this practical guide. Plans for 17 different designs, line source, I.B., Horn and Reflex types, for 8"-18" drive units. **£3-95** post free (£8 overseas).

THE INFRA-BASS LOUDSPEAKER
by G. Holliman
(full constructional details for versions using 15", 12" and 10" drive units.) **£2-95** post free (£6 overseas)

THE DALESFORD SPEAKER BOOK
by R. F. C. Stephens
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. **£2-20** post free (£5 overseas).

VAN KAREN PUBLISHING
5 SWAN STREET, WILMSLOW, CHESHIRE

For Sale

NEW BACK ISSUES OF "PRACTICAL WIRELESS" available 70p each, post free. Open P.O. Cheque returned if not in stock—**BELL'S TELEVISION SERVICE,** 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

SEEN WHISTONS CAT? 5000. odds and ends. Mechanical/Electrical Cat Free. WHISTON, (Dept. PW), New Mills, Stockport.

COMMUNICATION RECEIVER TRIO R300 New April 1978 £90. O.N.O. Securicor Delivery Arranged. Evening Dingwall 4640.

EQUIPMENT CLEAROUT. R/TV Test Gear. Scope. Valves. Military Radios. Many bits & pieces. Alton (0420) 63623.

REALISTIC D.X.160 Solid state communications receiver £90. Excellent condition. Four Months old. Hardly used. A. Redfern, 104 Prenton Hall Rd., Prenton, Birkenhead, Merseyside. Tel: 051 608 5320.

Ladders

LADDERS varnished 21' extd. £31.97. Carr. £3. Leaflet. Alloy Ext. to 62½'. Ladder Centre (WLS3) Halesfield (1) Telford 586644.

Service Sheets

HUGE G.T. TV/RADIO/ETC. CATALOGUE (with £4 worth of useful vouchers)

Lists thousands of service sheets, manuals, etc. Many unobtainable elsewhere. Plus up dated Chassis Guide, newsletter, etc. Essential for every firm/engineer - Save ££s - only £1 plus large S.A.E. S.A.E. for details of our Giant Service Sheet Collections - not available elsewhere.

G.T. TECHNICAL INFORMATION SERVICES

76 Church St, Larkhall, Lanarkshire ML9 1HE

Largest stocks of manuals, etc. anywhere. £1 + large S.A.E. brings any requested full size single service sheet. **Service sheets from 50p**: S.A.E. for full details of this plus unique T.V. Publications. The new 1979 British Colour T.V. Repair Manual and the new First Foreign Colour T.V. Repair Manual for £4.90 each - both for £9.50.

S.A.E. brings full details of these and other unique publications.

LARGE SUPPLIER OF SERVICE SHEETS

and Colour Manuals, TV Mono Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E. except colour TV and Car Radios. State if Circuit will do, if sheets are not in stock. All TV Sheets are full lengths 24 x 12, not in Bits & Pieces. Free Fault Finding Chart or TV Catalogue with order. All crossed PO's returned if service sheets not in stock.

C. CARANNA (Mail Order)

71, Beaufort Park, London, NW11 6BX
01-458 4882

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc., with free fault-finding guide, from 50p and S.A.E. Catalogue 25p, and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1.00 plus SAE Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 King's Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 24p, plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

Educational

TELEVISION & VIDEO SYSTEMS ENGINEERING

15 MONTHS full-time Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO & COLOUR TELEVISION
- CLOSED CIRCUIT TELEVISION
- VIDEO CASSETTE RECORDING
- DIGITAL TECHNIQUES
- TELETEXT & TV GAMES

Shortened courses for applicants with suitable electronics background.

Next session starts September 17th.

(Also available 2 1/2 year course in Marine Electronics & Radar for employment as ships Radio Officer.)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. B8, 20 Penywern Road,
London SW5 9SU. Tel. 01-373 8721.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood, FY7 8JZ.

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford, RM7 0XU. (Tel: Romford 66841).

Practical Wireless, August 1979

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. K277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. K277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. K277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

Situations Vacant

VIDEO ENGINEER

Experienced all-round Video Engineer required by leading company in North London. Good pay, Bonus, Pension, Company Car. Phone J. Rabin or A. Brown

01-951-0466

Wanted

ELECTRONIC COMPONENTS PURCHASED. All Types Considered - Must be new. Send detailed list - Offer by return - WALTONS, 55A Worcester Street, Wolverhampton.

Miscellaneous

GUITAR/PA MUSIC AMPLIFIER

100 watt with superb treble/bass overdrive, 12 months guarantee. Unbeatable at £42; 60 watt £37; 200 watt £58; 100 Watt twin channel sep. treble/bass per channel £55; 60 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves 100 watt £32; 200 watt £49; fuzz boxes, great sound, £8.50; bass £9.50; overdriver; fuzz with treble and bass boosters £14; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable, £89; twin channel £99; bass combo £99; speakers 15in, 100 watt £35; 12in, 100 watt £22.50; 60 watt £14.50. 10 watt 10in. £3.50, 8in. £3.00.

Send Cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Ave., Dukinfield, Cheshire.

Tel 061-344 5007 or 061-308 2064

LOSING DX?

RARE DX UNDER GRM? Dig it out with a Tunable Audio Notch Filter, between rx and speaker, £8.90.

V.L.F.? Explore with a 10-150KHz Receiver, £10.70.

OFF FREQUENCY? Dial up the DX with a Crystal Calibrator, 1MHz, 100, 25KHz markers, £15.80.

TIME? MSF 60KHz Receiver, data output, £13.70.

Sequential year, month, date, day, hours, minutes, seconds Display (no case or pcb) for rx £10.70.

RADIO 4 GONE? FRG7? 200KHz to Medium Wave Converter, coax output, built-in antenna, £11.40.

SIG. GEN., 10Hz-200KHz, logic/sine/square, £10.80.

PROGRAM YOUR OWN tunes on a Musical Doorbell, 120 programs - FREE, £23.50, needs speaker.

LONG WAVE DX? 100-600KHz Converter, built-in antenna tuner, 4-1-4.6MHz output, £10.90.

Each easy-assembly kit includes all parts, printed circuit, case, instructions, battery when used, postage etc. money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (PV) Old School Lane,
Milton, Cambridge.

ALFAC etch resist transfers and other p.c. board drawing materials available from stock. SAE details. Ramar Constructor Services, Masons Road, Stratford-upon-Avon. CV37 9NF.

BELLS AND SIRENS

CARTERS SIREN £5.95

INDUSTRIAL SIX INCH BELL £8.95

PRICES INCLUSIVE.

SEND CHEQUE. P.O. to:

CWAS ALARM

11 Denbrook Walk,
Bradford BD4 0QS

6 to 12v D.C.

12v D.C.

SAE for full Price list of Professional Burglar Alarm Equipment.

JORDAN SECURITY SYSTEMS

ALARM COMPONENTS

201	Pressure Pad 29" x 15"	£2.30
202	Pressure Pad 22" x 6 1/2" (Stair Tread)	£1.68
203	Window Foil (To British Standards) 30 metres	£2.95
204	Foil Blocks (Self Adhesive)	.15p
205	Outdoor Bell Case (Plastic Coated Metal)	£8.50
206	High Output 6" Bell (12 volts D.C.)	£12.55
207	Siren (12 volts D.C.)	£5.40
208	Security Control Panel - Mains/Battery Anti-Tamper Circuitry	£32.00
209	Vibration Contacts	£2.35
210	4 Core Wire (100 metres)	£7.99
211	Flush Magnetic Switch	.94p
212	Surface Magnetic Switch	.94p

All prices include VAT & Postage

170, Cromwell Road, Grimsby,
South Humberstone.
Tel 0472-41451/2



CALLERS WELCOME



TIRRO's new mail order price list of electronic components now available on receipt of SAE. **TIRRO ELECTRONICS**, Grenfell Place, Maidenhead, Berks.

PRACTICAL WIRELESS Projects P.C.B's all in Glass Fibre tinned and drilled. November 78. Sarum Meter 210p. Standard charge timer 175p. Porch Light Timer 60p. Battery Indicator 60p. December L.W. Converter 350p. (Two Boards). Door Chimes 250p. January 79. Delay Line 250p. Sandbanks 250p. February. Hythe Receiver 400p. March. Hythe Receiver 210p. Soundlite Converter 400p. Toneburst Generator 110p. Wideband Noise Source 70p. April. F.M. Multitester 150p. May Xtal Calibrator 110p. Car Probe with Free Fascia Panel 70p. IMP 110p. Gillingham follow up 90p. Prices include dispatch by First Class Post. Please enquire for P.C.B's for current issues. H.T.E. (Dept P.W) 50 Milnefield Avenue, Elgin, Morayshire. IV30 3EL.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
Reg. Office 22 Coningsby Gdns

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

14, 16, 18	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT
SAE brings list of copper & resistance Wires
Dealer Enquiries Invited

AUDIO OSCILLATOR Sine-Square - R.I.A.A. outputs. 15Hz to 200KHz in four ranges. Thermistor stabilised. Assembled P.C.B. ready to use. 9V supply required. S.A.E. data. £16.30 inclusive. Quantec, 40 AIn Court, Ellington, Morpeth, Northumberland. Morpeth 860101.

BULK PURCHASE. Battery intercoms to clear. 50ft. lead & volume control £6.95 pair. J. HARMSWORTH (PW2) 34 Victoria Street, Eccles, Maidstone, Kent.

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP7 (AA) £1-13. SUB C £1-47. HP 11 (C) £2-15. HP 2 (D) £3-27. PP3 £4-09. PP3 not suitable for fast charge. PP3 charger £5-81. All above Nickel Cadmium batteries are guaranteed 'EVER READY' full spec, and are supplied complete with solder tags (except PP3). Just in stock—New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc. 1-2 amp hr 6v. £4.40 2-6 amp hr. 6v £5-65.

Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type), all prices include VAT. Please add 10% P & P on orders under £10. 5% over £10.

Cheques, postal orders, mail order to: **SOLID STATE SECURITY DEPT PWY 10, Bradshaw Lane, Parbold, Wigan, Lancs. 02575-4726.**

OFFERS for 80 used Tapes 1/4 inch for Helical Scan V.T.R., one Sony 19 inch Video Monitor. Wellingborough 223527.

STOCK of downgraded capacity cells, type AA, Sub C, C, D and F. Cells are of the rechargeable Sealed Nickel Cadmium type. Please write to Box No. 143.

SOLAR CELLS, Batteries, Panels, Thermoelectric Generators, Heat pipes, Books etc. Details; Edencombe Ltd., 34 Nathans Road, N. Wembley, Middx. HA0 3RX.

SUBERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry and the Trade. **BAZELLI**, (Dept No.25) St. Wilfrids, Foundry Lane, Halton, Lancaster. LA 6LT.

Please mention
PRACTICAL WIRELESS
when replying to
advertisements

Record Accessories

STYLI, Cartridges For MUSIC CENTRES, etc. FREE List No. 29 For S.A.E. includes Leads, Mikes, Phones etc. **FELSTEAD ELECTRONICS**, (PW), Longley Lane, Gatley, Cheshire. SK8 4EE.

Equipment

COMMUNICATIONS RECEIVERS made by **PYE** for R.N. part of Navy CAT equipment. General coverage Rx 60Kc to 30Mc/s in 8 bands cont coverage, uses 12 miniature valves with dual conversion on H.F. ranges IFs 1.4 & 460Kc controls, RF & L.F. gain. AVC on/off. BFO freq, Selectivity 4 pos with dual crystal filter, Main tune, Band sel. Phone jack. tuning scale similar to Eddystone. As O/P for 100 ohm phones or 2 watts into 500 ohm. Size in case 10 1/2 x 13 1/2 x 14" weight 44lbs. These require ext supplies of 250v DC HT at 130Ma & 6.3v AC at 4 amps supplied tested with copy of handbook & circ good cond, fuller spec on request £108.

A. H. SUPPLIES.

122, Handsworth Rd. SHEFFIELD. S9. 4AE.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions

I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME.....

ADDRESS

Send to: Classified Advertisement Manager
PRACTICAL WIRELESS,
GMG, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5846

Rate
22p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

TRANSFORMERS

30 VOLT RANGE
Pri 220/240 sec 0.12-15-20-24-30V
Voltages available 3, 4, 5, 6, 8, 9, 10,
12, 15, 18, 20, 24, 30V or 12V-0-12V
and 15V-0-15V

Ref	Amps	Price	P & P
112	0.5	2.64	0.78
79	1.0	3.57	0.96
3	2.0	5.77	0.98
20	3.0	6.20	1.14
21	4.0	7.99	1.14
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.64
90	12.0	19.17	1.95
91	15.0	21.96	2.08
92	2.0	29.45	O.A.

Continuous Ratings
EX-STOCK—
SAME DAY DESPATCH
+ VAT 8%

TRANSFORMERS

END OF LINE OFFERS

Ref	Description	Price	P & P
30	Isolator 240V:240V 200VA	£4.54	P&P £1.04
62	Isolator 240V:240V 250VA	£5.62	P&P £1.04
63	Isolator 240V:240V 500VA	£11.50	P&P £2.15
6	250-0-250 @ 100ma 1) Sec 6-3V @ 3.5A 2) Sec 0-5V, 6.3V @ 2/1 amp	£3.20	P&P 78p
7	350-0-350V @ 100ma 1) Sec 6-3V @ 3.5A 2) Sec 0-5V, 6.3V @ 2/1 amp	£4.10	P&P 96p
218	250-0-250V @ 150ma 1) Sec 6-3V @ 4A 2) 0-5V, 6.3V @ 2/1 amp	£3.50	P&P 78p
27	250-0-250 @ 60ma 1) Sec 6-3V @ 2.5A 2) Sec 6-3V @ 1 amp	£3.00	P&P 78p
220	410-0-410V @ 180ma 1) Sec 6-3V @ 4 amp CT 2) Sec 6-3V @ 2A 5V @ 2 amp	£5.30	P&P 96p
82	4 amp lead acid Battery Charger (transformer only)	£4.81	P&P £1.04
86	6 amp lead acid Battery Charger (transformer only)	£5.80	P&P £1.04

50 VOLT RANGE
Pri 220/240V Sec 0-20-25-33-40-50V
Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V and 25V-0-25V

Ref	Amps	Price	P & P
102	0.5	3.41	0.78
103	1.0	4.57	0.96
104	2.0	7.15	1.14
105	3.0	8.56	1.32
106	4.0	11.41	1.50
107	6.0	15.06	1.64
118	8.0	20.26	2.08
119	10.0	24.38	O.A.
109	12.0	28.90	O.A.

MAINS ISOLATORS (SCREENED)
PM 120/240 Sec 120/240V CT

Ref	Va	Price	P & P
107	20	4.20	0.79
149	60	6.70	0.96
150	100	7.62	1.14
151	200	11.16	1.14
152	250	13.28	1.50
153	350	18.43	1.84
154	500	20.47	2.15
155	750	29.06	O.A.
156	1000	37.20	O.A.
157	1500	51.38	O.A.
158	2000	61.81	O.A.
159	3000	96.66	O.A.

*Pri 0-220-240V Sec 115 or 240V.
State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

Va	Price	P & P	Ref
20	5.95	0.90	56W
25	7.73	1.14	64W
150	10.01	1.14	4W
200	10.92	1.45	65W
250	11.59	1.45	69W
500	19.17	1.54	67W
1K	27.88	2.30	84W
1.5K	26.02	O.A.	93W
2K	49.97	O.A.	95W

12 OR 24V OR 12-0-12V
Pri 220-240 volts

Ref	12V	24V	Price	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
71	2	1	3.51	0.78
18	4	2	4.03	0.96
85	0.5	2.5	5.00	0.96
108	8	4	7.42	1.14
72	10	5	8.12	1.14
116	12	6	8.99	1.32
17	16	8	10.72	1.32
115	30	10	13.95	2.08
187	30	15	17.93	2.08
226	60	30	36.74	U.C.

COMPONENT PACKS

- 65 1W Metal Oxide Resistors.
- 65 1W Metal Oxide Resistors.
- 150 Mixed Value Capacitors.
- 10 Reed Switches.
- 50 Wire Wound Resistors.
- 10 3000mf 30V Capacitors.
- 25 Assorted presets.
- 50 3 tag terminal strips.
- Hardware BA nuts, bolts.
- 20 Mixed Resistors.
- 10 mixed valve electrofitic caps
- 32 mf to 2000 mf.

70p + 12 1/2% VAT
P&P 40p + 8% VAT

BRIDGE RECTIFIERS £2-10

100V	25A*	£2-10
200V	2A	£0-45
400V	4A	£1-25
400V	6A	£1-25
500V PM7A6	12A*	£2-85
VAT 12 1/2% P & P 15p. VAT 8%		

AMPLIFIER MODULES

10W (AL30)	£3-75	
25W (AL60)	£4-95	
35W (AL80)	£7-79	
125W (AL250)	£18-74	
Power Supply PS12	£2-05	
Power Supply SPM80	£4-25	
VAT 12 1/2%	PA12	£6-70
P & P 35p	PA100	£13-88
VAT 8%		

TEST METERS

AVO 8 MK5	£88-10
AVO 71	£38-00
AVO 73	£48-70
AVO MMS minor	£32-95
Wee Megger	£74-25
TT169 in circuit transistor tester	£39-53
EM272	£57-80
DA116	£68-00
BMT Megger	£51-76

All accessories available.
P&P £1-15 8% VAT

15V RANGE

Ref	500 mA	2.09	P & P
171	1A	2.96	0.78
172	2A	3.99	0.78
173	3A	3.75	0.86
174	4A	5.73	0.96
175	4A	5.73	VAT 8%

MINI-MULTIMETER

DC-1000V AC-1000V DC-100mA Res-150kΩ
1000Q/V Bargain £7-20 P&P 62p VAT 8%

S-DECS

Solderless bread boarding
S Dec 70 contacts £3-55
T Dec 208 contacts £4-50
U Dec 'A' for I.C.s etc £2-50
U Dec 'B' for I.C.s etc £6-99
P & P 40p. VAT 8%

20,000 ohm/v Multimeter, mirror scale.
Ranges AC/DC to 1000V DC current to 250mA
Resistance to 3 Mohms
5" x 3 1/2" x 1 1/2" £14.36 P&P £1.05 VAT 8%

Electronic Construction Kit
Home electronic starter. Start simply and progress to a TRF radio or electronic organ. No soldering. All parts included in presentation box. Full instructions.
£8-29. P & P 96p. VAT 8%

NEW RANGE TRANSFORMER
Pri 120V or 220/240V. Sec 0-36-48 twice to give 36-0-36V 48-0-48V 72V or 92V. P & P

Ref	Price	P & P
3A	14-70	1.48
4A	18-77	1.84
5A	26-84	2.15

VAT 8%

ABS PLASTIC BOXES inset brass nuts, internal slots to take P.C. cards, flush fitting lid.

Size	Price
PB1 180mm x 62 x 40	65p
PB2 100mm x 75 x 40	73p
PB3 120mm x 100 x 45	87p
PB4 215mm x 130 x 85	£2.54

P & P 29p. VAT 8% (*P & P 40p)

PANEL METERS

43mm x 43mm	82mm x 78mm
0-50A	6-20
0-200A	6-55
0-1mA	5-95
0-30V	5-95
VU ind. Panel 48mm x 45mm	3-36
VU ind. Edge 90mm 250µA	2-60
54mm x 14mm 250µA FSD	
VU ind. Edge 54x14mm	2-60
250µA F.S.D.	
Carriage 65p. VAT 8%	

ANTEX SOLDERING IRONS

15W	3-95
25W	3-95
Stand	£1-52 VAT 12 1/2%
P & P 46p. VAT 8%	

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

PRACTICAL WIRELESS

is looking for someone with a comprehensive knowledge of the Radio/Electronic industry, who would like to enter the field of Advertisement Selling. The suitable applicant, based in London would be responsible for approaching advertisers or their Agents with a view to persuading them to advertise in **Practical Wireless**. Attractive salary, Company Car etc...

Applications, initially in writing please, should be made to Mr. I. P. Stamp, Group Advertisement Controller, IPC Magazines Ltd, Westover House, West Quay Road, Poole, Dorset BH15 1JG.

J. BIRKETT

Radio Component Supplies
25 The Strait, Lincoln LN2 1JF. Tel: 20767

MINIATURE ELECTROLYTICS .8uf 300v.w. @ 10 for 60p. 10uf 250v.w. @ 10 for 60p. 30uf 250v.w. @ 10 for 60p.

VARIABLE CAPACITORS 25-25-25pf @ 75p.

4 watt 100K LINEAR WIRE WOUND POTENTIOMETERS @ 30p each.

MOULDED TRACK POTENTIOMETERS 1K linear @ 25p.

2 1/2" 1 VERNIER DRIVES at £1.40.

50. BC 107-8-9 TRANSISTORS assorted untested @ 57p.

50. AC 128 TRANSISTORS Branded but untested @ 57p.

50. 1 AMP THYRISTORS untested @ £1.

25. 5 AMP STUD MOUNTING THYRISTORS untested @ 75p.

50p. OC 71 TRANSISTORS untested @ 75p.

25. 10 AMP STUD MOUNTING SILICON DIODES untested @ 57p.

10. 20 AMP STUD MOUNTING SILICON DIODES untested @ 57p.

50. VARI-CAP DIODES like BA 102 untested @ 57p.

100 MULLARD C280 CAPACITORS assorted @ 57p.

LED's TIL 209 .6 for 50p, .2" type Red @ 6 for 70p.

50. 2 watt ZENERS untested assorted @ 57p.

X BAND GUNN DIODES CXY 11A @ £3 each.

VERNITRON FM 10.7 MHz FILTERS at 50p, 3 for £1.

ERIE REDCAP .01uf 100v.w. **MINIATURE CAPACITORS** @ 5p each.

10 AMP S.C.R.'s @ 100 PIV @ 25p, 400 PIV @ 50p, 600 PIV @ 50p.

R. F. SIGNAL TRANSISTORS AF 239 @ 50p, 2N 5179 @ 50p, BF 362 @ 25p, 2N 515 @ 50p, BF 90 @ 50p, MPS 6514 @ 10p, BF 177 @ 15p.

200 ASSORTED 1/2 RESISTORS for 75p.

COIL FORMERS 3/16" Dia. with core at 6 for 25p.

SOLID DIELECTRIC VARIABLES 195-80pf @ 40p each.

SUB-MINIATURE TANTALUM CAPACITORS 4.7uf 10v.w. @ 6 for 25p.

DAU TRIMMERS 2 to 9pf @ 15p, 3 to 35pf @ 15p, 6 to 45pf @ 15p, 0 to 125pf @ 15p, 8 to 140pf @ 15p.

SILICON DIODES 50 PIV 2 1/2 amp @ 7p, 8 for 25p.

400mW ZENERS unmarked good. 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36v. All at 10 for 40p.

MULLARD TRANSISTORS BC 548, BC 549 Both 10p ea. 8 for 50p.

10 ASSORTED PUSH BUTTON BANKS less knobs for £1-30.

VHF TUBULAR TRIMMERS 5pf @ 10p, 15pf @ 18p, 5pf @ 10p.

MINIATURE VARIABLE CAPACITORS 5pf @ 75p, 10pf @ 75p, 30pf @ 85p, 125-125pf @ 55p, 100-200pf @ 55p, 200-300pf @ 55p.

10 ASSORTED SLIDER POTENTIOMETERS for £1.

CRYSTAL FILTER 10.7MHz 910 ohm B.W. @ 7.5 KHz @ £5.

1000pf SOLDER-IN FEED THRU CAPACITORS @ 20p doz.

30. ASSORTED 10XAJ CRYSTALS @ £1-10, 20. FT 243 CRYSTALS assorted @ £1-10, 20. FT 271A CRYSTALS assorted @ £1-10.

MINIATURE BUTTERFLY PRE-SET VARIABLES Spindles easily extended. 25x25pf @ 50p, 38x38pf @ 60p, 38x38pf. Wide Spaced @ 85p.

600 MHz FREQUENCY COUNTERS HFC 600 S.A.E. for leaflet @ £115.

CRYSTALS 10K type 8010 KHz @ 40p, 100 KHz plus 1 MHz @ £2.

WIRE ENDED GLASS CRYSTALS 28 KHz, 28.5 KHz, 29.75 KHz, 31.5 KHz. All at 50p each.

HCGU type CRYSTALS 37.7777, 38.1481, 38.3333, 39.6667, 39.7037, 39.7407, 39.8889, 40.37, 40.11111, 40.2963, 41.11111, 44.3, 45.7, 45.9, 46.1, 46.3, 46.5, 46.612, 46.7, 48.3, 50.1 MHz. All 50p each, or 3 for £1-30.

MINIATURE NON POLARISED CAPACITORS 1uf 63v.w. @ 5p, 4.7uf 63v.w. @ 10p, 10uf 63v.w. @ 15p.

MIDGET AIRSPACED TRIMMERS 3 to 20pf @ 15p each.

Please add 20p for post and packing on U.K. orders under £2. Overseas postage at cost.

TOPS THE PACK!

ACE

COMPONENTS — Now over 1,000 types in stock!

KITS — See the new range of low-cost 'ELEKITS'.

SERVICE QUALITY — 1st Class same day despatch. All guaranteed products. Many reductions!

PRICES —

MAGAZINE PROJECTS — Trouble-free!

S.A.E. for list of PW projects

I enclose 30p*, please send catalogue.

Name _____

Address _____

*Refundable with future orders over £5.00.

WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	15	1A/100V	25	1A/50V	20	2A/100V	22	4A/100V	44
AA129	25	1A/50V	20	2A/100V	22	4A/100V	44	2A/200V	48
AA930	25	1A/50V	20	2A/100V	22	4A/100V	44	2A/200V	48
AAZ15	15	1A/100V	22	4A/100V	44	2A/200V	48	2A/400V	53
BA100	10	1A/200V	25	2A/400V	53	4A/100V	72	2A/500V	65
BY100	24	1A/50V	29	2A/100V	44	4A/100V	72	2A/500V	65
BY126	12	1A/50V	29	2A/100V	44	4A/100V	72	2A/500V	65
BY127	12	2A/100V	44	4A/100V	72	2A/500V	65	2A/500V	65
CRO33	148*	2A/200V	48	2A/400V	53	4A/100V	72	2A/500V	65
OA9	75*	2A/200V	48	2A/400V	53	4A/100V	72	2A/500V	65
OA47	12	4A/100V	72	2A/500V	65	2A/500V	65	2A/500V	65
OA79	12	4A/100V	72	2A/500V	65	2A/500V	65	2A/500V	65
OA81	15	4A/800V	105	8A/800V	108	12A/100V	60	12A/400V	70
OA85	12	6A/200V	35	12A/800V	130	6A/400V	85	12A/800V	130
OA90	6	6A/400V	85	12A/800V	130	6A/400V	85	12A/800V	130
OA91	6	6A/400V	85	12A/800V	130	6A/400V	85	12A/800V	130
OA95	8	VM18DIL	40	16A/400V	105	16A/400V	105	16A/400V	105
OA200	9			25A/800V	160	25A/800V	160	25A/800V	160
OA202	8			25A/800V	160	25A/800V	160	25A/800V	160
IN914	4	Rng: 2V7-39V	9p						
IN916	5	Rng: 3V3-33V	9p						
IN4002*	5	1-3W	15p						
IN4003*	6								
IN4004/5*	6								
IN4006/7*	7								
IN4148	4								
IS44	20								
3A/100V*	18								
3A/400V*	20								
3A/600V*	27								
3A/1000V*	30								
SCR's*									
Thyristors									
0.8A30V	28	3x2x1"	48	4x4x1"	68	4x4x1"	68	4x4x1"	68
0.8A100V	28	4x4x1"	68	4x4x1"	68	4x4x1"	68	4x4x1"	68
0.8A200V	35	4x2x1"	64	4x5x1"	78	4x5x1"	78	4x5x1"	78
1A600V	70	4x5x1"	78	4x5x1"	78	4x5x1"	78	4x5x1"	78
5A300V	35	4x2x1"	64	4x5x1"	78	4x5x1"	78	4x5x1"	78
5A600V	43	4x5x1"	78	4x5x1"	78	4x5x1"	78	4x5x1"	78
8A300V	48	6x4x2"	98	6x4x2"	98	6x4x2"	98	6x4x2"	98
8A600V	55	7x5x2"	132	7x5x2"	132	7x5x2"	132	7x5x2"	132
12A300V	59	8x6x3"	168	8x6x3"	168	8x6x3"	168	8x6x3"	168
12A500V	92	10x7x3"	192	10x7x3"	192	10x7x3"	192	10x7x3"	192
12A800V	150	12x8x3"	192	12x8x3"	192	12x8x3"	192	12x8x3"	192
15A700V	195	12x8x3"	192	12x8x3"	192	12x8x3"	192	12x8x3"	192
BT106	150	12x8x3"	192	12x8x3"	192	12x8x3"	192	12x8x3"	192
C106D	38	12x8x3"	192	12x8x3"	192	12x8x3"	192	12x8x3"	192
TIC44	22								
2N4444	140								

OPTO ELECTRONICS*			
LEDS Plus Clip			
TIL209 Red 125*	13	7 Segment Displays	
TIL211 Grn 125*	18	LS400	
TIL212 Yellow	22	TIL307	
TIL32 Infra Red	58	TIL312 & 313 3"	
0.2" Red	25	TIL321 5" C.An	
0.2" Yellow	19	TIL322 5" C.th	
Grn. Amber	19	DL704 3" C.Cth	
Square LEDES	48	DL707 3" C.Anod	
OCPT1	120	DL747 6" An	
ORP12	63	FND357	
2N5777	45	MAN3640	
OPTO Isolators			
IL74	48	Liquid Crystal Display	
TIL111/2	85	XAN351 3" Green	
TIL117	110	3 1/2 OR 4 digit	

"PURBECK OSCILLOSCOPE"

Author Approved Parts including PCBs available. Send SAE for Leaflet.

Cathode Ray Tube 3PB1 £7.75* (p&p insured add 95p)

SWITCHES*			
TOGGLE 2A 250V	28		
DPST	34		
DPDT	38		
4 pole on off	54		
SUB-MIN TOGGLE			
SP changeover	59		
SPST on off	54		
SPST biased	85		
DPDT 6 lags	70		
DPDT C/OFF	79		
DPDT Biased	115		
3 pole C/Over	150		
SLIDE 250V			
1A DPDT C/OFF	14		
1A DPDT	13		
4 pole 2-way	24		
PUSH BUTTON Spring loaded			
Latching	60		
SPST on off	60		
SPST C/Over	65		
DPDT 6 Tag	85		
MINIATURE Non Locking			
Push to make	15		
Push Break	25		
ROCKER:			
5A, 250V, SPST	23		

VOLTAGE REGULATORS*			
1A TO3 +ve			
5V 7805	145p	7905	220p
12V 7812	145p	7912	220p
15V 7815	145p		
18V 7818	145p		
24V 7824	85p	7924	90p
100mA TO92 Plastic Casing			
5V 7805	80p	7905	90p
12V 7812	80p	7912	90p
15V 7815	80p	7915	90p
18V 7818	85p	7918	90p
24V 7824	85p	7924	90p
5V 7805	30p	7905	65p
6V 7812	30p		
7V 7818	30p		
12V 7812	30p	7912	65p
15V 7815	30p	7915	65p
CA3085	95	LM323K	625
LM300H	170	LM325N	240
LM305H	140	LM326N	240
LM309N	85	LM327N	270
LM317K	350	LM723	39
TAA550	50	TBA6258	95
TDA1412	150		

VDU Hardware*

AY-3 1015 UART 550
 AY-5 1013 UART 450
 SF96364E 1099
 SFC71301 820
 SF580102 205
 7812 205
 SN74LS163 118
 SN74S262 895
 SN75450 120
 SN75451 70
 SN75452 70
 SN75454 225
 TMS6011 355
 UHF Modulator 250

Wide Bandwidth Modulator Special for Computer 470
 Thompson SFEX 68364-1-1, ready built and tested low cost VDU BOARD only: £69.00

Full Ascii KEYBOARD Model 756

Low cost, ready-built, tested & Guaranteed. Full technical details supplied. Only £49.75*.

KEYPADS*

4x4 matrix, push button read switches assembly. Extremely reliable. Only 450p*.

VEROBOARD*	Pitch	0-1	0-15	0-15
		(copper clad)	(plain)	
2 1/2 x 3 1/2	46p	39p	31p	24p
3 1/2 x 3 1/2	55p	50p	50p	31p
3 1/2 x 5	62p	67p	50p	43p
3 1/2 x 17	218p	180p	141p	120
4 1/2 x 17	280p			183p
				22p
				85p
				120p
VERO WIRING PEN*	Spool	325p		
Spare Wire (Spool)	80p;	Combs	7p ea.	
FERRIC CHLORIDE*	1lb bag Anhydrous	70p	+ 35p p. & p.	
DALO ETCH RESIST PEN*	Plus spare tip		75p	
COPPER CLAD BOARDS*				
Fibre Single Double	SRBP			
Glass sided sided	8-5" x 8-5"			
6" x 6"	75p	90p	80p	
6" x 12"	130p	175p		
SOLDERCON PINS*	100 pins 50p;	500 pins	200p	
DIL SOCKETS*	Low Profile (TEXAS)			
8 pin 10p;	14 pin 12p;	16 pin 13p;	18 pin 16p;	20 pin 22p;
22 pin 25p;	24 pin 26p;	28 pin 39p;	40 pin 50p;	64 pin 220p

ROCKER:	Lights red when on	52
	Bezel. 3A 250V. SPST	
ROTARY:	"Make-A-Switch" Make your own multiway Switch. Adjustable Stop Shafting Assembly. Accommodates up to 6 Wafers	75
	Mains Switch DPST to fit	34
	Break Before Make Wafers to fit: 1 pole/12 way, 2p/6 way, 3p/4 way, 4p/3 way, 6p/2 way	47
	Spacer and Screen	5
ROTARY: (Adjustable Stop)	1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way	41
ROTARY:	Mains 250V AC. 4 Amp	45
PW PROJECTS	General Coverage Receiver, Chroma-chase, 'JUBILEE' Electronic Organ, General Purpose SW Receiver, Gas & Smoke Sensor Alarm, 'PURBECK' Oscilloscope, Audio Distortion Meter, 'AVON' 2m FM Transmitter, 'HYTHE' Jumbo Walk Clock, 'IMP' 3-Waveband Receiver, AM-FM Frequency Readout. Automatic Intercom. Send SAE plus 5p per list.	

EDGE CONNECTORS*	15" spacing 2x10way 85p; 2x15way 99p; 2x18way 120p; 2x22way 135p; 2x25way 160p.										
74LS* (Manufactured by Texas)											
74LS00	11	74LS47	63	74LS123	70	74LS173	105	74LS251	134	74LS353	228
74LS01	11	74LS48	120	74LS124	180	74LS174	106	74LS252	142	74LS356	85
74LS02	12	74LS49	120	74LS125	80	74LS175	110	74LS253	110	74LS357	85
74LS03	12	74LS51	24	74LS126	60	74LS181	398	74LS254	110	74LS358	85
74LS04	12	74LS54	28	74LS132	95	74LS183	298	74LS255	160	74LS359	80
74LS05	23	74LS55	30	74LS136	55	74LS189	430	74LS256	52	74LS370	160
74LS06	22	74LS63	150	74LS138	85	74LS190	140	74LS257	244	74LS371	155
74LS07	22	74LS73	46	74LS139	85	74LS191	140	74LS258	250	74LS372	212
74LS10	20	74LS74	41	74LS145	108	74LS192	132	74LS259	68	74LS373	184
74LS11	22	74LS75	48	74LS147	170	74LS193	130	74LS260	250	74LS374	215
74LS12	23	74LS76	40	74LS148	173	74LS194	166	74LS261	450	74LS375	180
74LS13	38	74LS78	40	74LS151	96	74LS195	136	74LS262	52	74LS376	160
74LS14	35	74LS82	115	74LS153	76	74LS196	100	74LS263	128	74LS377	155
74LS15	30	74LS85	118	74LS156	96	74LS197	140	74LS264	250	74LS378	212
74LS16	20	74LS86	43	74LS157	76	74LS200	348	74LS265	185	74LS379	184
74LS17	22	74LS90	38	74LS158	96	74LS202	345	74LS266	468	74LS380	230
74LS18	22	74LS92	89	74LS160	128	74LS204	236	74LS267	175	74LS381	215
74LS19	28	74LS93	89	74LS161	98	74LS206					

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Reg No. 242 1255 03

Please send all correspondence and Mail-Orders to Head Office

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES


1B3GT	0-84	6AX46TB	1-13	6CY5	1-13	12AT6	0-68	ECF200	1-01	EM84	0-68	PCL81	0-73	PY82	0-62	UCC84	0-84
IR5	0-56	6AX5GT	1-46	6CY7	1-13	12AT7	0-56	ECF201	1-01	EM87	1-13	PCL82	0-80	PY83	0-79	UCC85	0-68
1X2B	1-35	6BA6	0-51	8008B	1-63	12AU6	0-73	ECF801	1-07	EY81	0-62	PCL84	0-84	PY88	0-84	UCF80	0-84
5AT8	0-90	6BE6	0-54	80T6	0-90	12AU7	0-53	ECF802	1-07	EY87	0-56	PCL86	0-86	PY500A	1-69	UCH42	1-13
5T4	0-84	6BF5	0-96	80T8	0-90	12AV6	0-96	ECH42	1-24	EY88	0-82	PCL805	0-90	TT21	10-69	UCH81	0-73
5U4G	0-68	6BF6	0-64	80W4	1-01	12AV7	1-13	ECH81	0-62	EY500A	1-69	PD510	3-78	TT22	10-69	UCL81	0-79
5U8	0-84	6BG6G	0-34	8ES5	1-13	12AX7	0-62	ECH200	0-90	EZ80	0-56	PL36	1-24	U25	1-13	UCL82	0-84
5V4G	0-68	6BH6	0-96	6EV5	1-69	12AY7	0-96	ECL80	0-68	EZ81	0-56	PL81	0-90	U26	1-13	UCL83	0-90
5X4G	0-90	6BJ6	1-35	6EW6	0-90	12BA6	0-73	ECL81	0-84	GY501	1-01	PL82	0-62	UABC80	0-65	UF41	1-13
5X8	1-01	6BJ7	0-73	6GH8A	0-90	12BF6	0-75	ECL82	0-68	GZ30	0-73	PL83	0-56	UAF41	0-90	UF80	0-56
5Y3GT	0-73	6BK4B	1-58	6GK5	0-79	12BH7A	0-84	ECL83	1-30	GZ32	0-73	PL84	0-84	UBC41	0-79	UF85	0-56
5Z4GT	0-73	6BN4A	1-01	6GK6	1-01	12BL6	0-79	ECL84	0-79	GZ33	4-28	PL504	1-35	UBC81	0-65	UL84	0-96
6AB7	0-68	6BN6	0-90	6J4	1-35	12B06	1-01	ECL85	0-73	OA2	0-70	PL508	1-58	UBF80	0-68	UM80	0-68
6AC7	0-90	6B07A	0-79	6J5GT	0-90	12BY7A	0-90	ECL86	0-96	OA3	0-81	PL802	3-15	UBF89	0-68	UM81	0-84
6AD8	0-68	6BR8A	1-35	6J6	0-62	12CU6	1-01	EF80	0-45	OB2	0-76	PY81	0-79	UBL21	1-01	UM84	0-51
6AF4A	0-90	6BS7	2-59	6J7	0-90	19A05	0-84	EF85	0-54	OB3	0-81						
6AG5	0-73	6BU8	0-96	6K5GT	0-84	19BG6G	0-56	EF86	0-68	OC2	1-51						
6AG7	0-96	6BW7	1-13	6K6GT	0-96	35A3	0-79	EF92	1-13	OC3	0-92						
6AH6	1-07	6BZ6	0-73	8L6GT	1-24	35B3	0-73	EF97	0-79	OC3	0-81						
6AJ5	0-73	6BZ7	0-79	6N7GT	0-96	35C5	0-96	EF98	1-01	PABC80	0-51						
6AK5	0-62	6C4	0-62	607	1-01	50C5	1-13	EF183	0-79	PC86	1-01						
6AK6	0-84	6C5GT	0-68	6SA7	0-90	50EH5	0-96	EF184	0-79	PC88	1-01						
6AK7	0-96	6C6	0-56	6SG7	0-90	DAF96	0-68	EF200	1-80	PC96	0-56						
6AL5	0-45	6C8G	0-68	6SK7	0-90	DF96	0-68	EH90	0-68	PC97	1-07						
6AM6	1-35	6CB6	0-62	6SL7GT	0-79	DK92	1-13	EL33	2-81	PC900	1-13						
6AM8	0-79	6CG7	0-79	6SN7GT	0-79	DL96	0-68	EL36	1-69	PCF84	0-56						
6AN5	2-81	6CG8A	0-84	6S07	0-90	ECC84	0-68	EL81	0-90	PCC85	0-68						
6AN6	0-96	6CM7	0-90	6SR7	0-90	ECC85	0-54	EL82	0-68	PCC88	0-73						
6AQ5	0-96	6CN7	1-35	6V6GT	0-90	ECC86	1-41	EL83	0-68	PCC89	0-84						
6AS6	1-13	6C08	0-84	6X4	0-79	ECC88	0-84	EL84	0-73	PCC189	1-13						
6AS7G	1-35	6CS7	0-96	6X5GT	0-68	ECC89	0-90	EL86	0-84	PCF80	0-96						
6AT6	0-84	6CU5	1-13	6X8	0-90	ECC189	0-90	EL95	0-79	PCF82	0-51						
6AU6	0-56	6CU6	1-13	12A6	0-68	ECF80	0-68	EL504	1-07	PCF84	0-73						
6AV6	0-84	6CW4	3-75	12AL5	0-73	ECF82	0-62	EM80	0-73	PCF86	0-84						
6AW8A	0-84	6CX8	1-13	12AD5	0-68	ECF86	0-90	EM81	0-68	PCF806	1-13						

OSCILLOSCOPE TUBES

current production. Made in USSR
One inch Tube Type 3L0 11. This tube is a good replacement for 1CP31. Tube characteristics are identical with those of 1CP31. As the connections are different the tube is supplied complete with base, connection diagram and technical data **£12.00** plus £0.96 VAT. **Three-inch tube Type 3BP1.** This well known tube used in "PURBECK" Oscilloscope can be supplied for **£7.50** plus £0.65 VAT. 14-pin base for the above **£0.80** plus £0.06 VAT.

Prices are inclusive of VAT (at current rates) except where shown separately. Postage and packing charges are **£0.10** per £ subject to a minimum of **£0.30**. Minimum order charge for Approved Credit customers **£20.00**. Minimum Transaction Charge for mail orders **£1.00**.

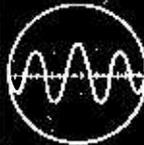
OUR NEW 1978/1979 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR **£0.30**




TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
PHONE 01-672 3137/672 9080
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING CONTROL SYSTEMS

NEW FROM TUAC

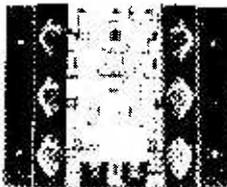

TD500

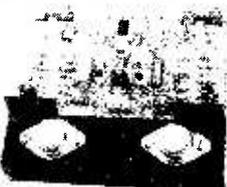

TD150

7" x 9" x 1 1/2" ULTRA QUALITY HIGH POWER 5" x 5" x 2"
New D.C. Coupled Design
AMPLIFIERS

Featuring—Electronic Short Open and Thermal Overload Protection.
Brief Spec.—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms.
Frequency Response 20 Hz - 20 KHz. T.H.D. at full power 0-1%.
Hum and Noise—100 dB Relative full output.

T.D. 500 300W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms.....	£45.00
Power supply P.S.300.....	£30.00
T.D.150 150W into 4 Ohms. 100W into 8 Ohms.....	£26.25
Power supply P.S. 150.....	£19.75
T.D. 150 60 Version 60W into 8 Ohms. 40W into 15 Ohms.....	£19.75
Power supply P.S.60.....	£15.50

Note—P.S. 300 will drive 2 T.D. 150 amplifiers
All output ratings are R.M.S. continuous sine wave output.

TO ORDER BY POST
Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclay Card No. (We accept holders phone orders 01-672 9080)
Post to—
TUAC LTD., 119 CHARLTON ROAD, LONDON SW17 9AB.
Send stamp for our free 28 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.

FOR YOUR GUIDANCE VALUE ADDED TAX


Unless otherwise shown, all prices in advertisements are inclusive of VAT. Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

Export orders are not subject to the addition of Value Added Tax.

EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.25 with a free bargain list. Send your cheque or postal order now.

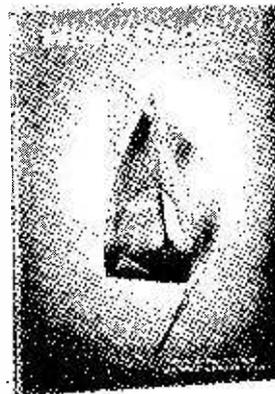**HOME RADIO
COMPONENTS LTD.**
Dept. PW, 234 London Road
Mitcham, Surrey CR4 3HD



Why buy colour films?

When you get a Kodak colour film

FREE

for every one you send in for processing by the Practical Wireless Colour Print Service!



Reliability at less cost

Photography can cost you a lot less these days. If you know how to go about it. Like the hundreds of thousands of magazine readers who are delighted with this reliable Colour Print Service – and the replacement films that come FREE to every customer! So why don't you give it a try? Here's what you do. Send us any make of colour print film inside the envelope enclosed in this issue. Or fill in the coupon below and send it with your film in a strong envelope to: The Practical Wireless Colour Print Service, Freepost, Teddington, Middlesex, TW11 8BR. No stamp is required.

Send no money

But don't send any money until you see the colour of your prints. We're so confident in the reliability of the service and the quality of our prints, every one of which is checked by professionals at our laboratories.

Luxury colour prints

You'll be amazed at the crisp, sharp, high-definition sheen finish of the prints we supply . . . borderless to give you maximum picture area. And coming with the prints will be your FREE Kodak colour film, worth around £1, the same size as the one you sent us for processing.

Unbeatable value

What about prices? Ours are certainly much less than those you would pay in most shops – quite apart from the free film you get every time we develop and print for you.

Our Colour Print Service charges you only 15p for each print, plus 85p towards developing, postage and packing. The minimum charge is 85p inc. VAT (that is, if no prints can be made). The offer is limited to the UK, Eire, CI and BFPO.

More benefits to you

You benefit in two additional ways. Firstly, you enjoy a personal service with every care taken over each individual order. And secondly, you pay only for what you get – with no credit vouchers as with many other companies. An invoice comes with your prints so it's a straight business transaction.

Use this label if you haven't got an envelope, or pass it to a friend who might like to take advantage of our offer. It is used to send your prints and free film.

(Offer Exc. Minolta & Sub-miniature. Roll Film 10p surcharge 400 ASA 20p surcharge).

From: Practical Wireless Colour Print Service,
Freepost, Teddington, Middlesex TW11 8BR

Mr/Ms _____

Address _____

Postcode _____



Speakers from 1 1/2 inch to 15 inch: megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.




A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



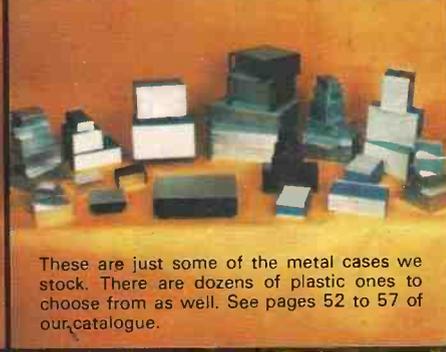A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD


All mail to:-
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.

Shop: 284 London Road,
Westcliff-on-Sea, Essex.
(Closed on Monday).

Telephone: Southend (0702) 554000.



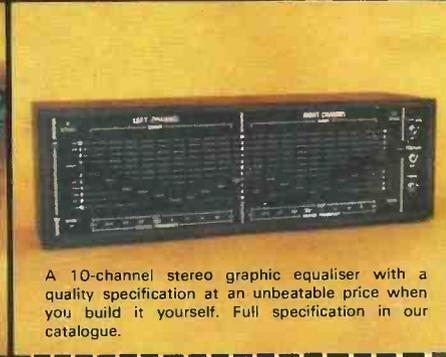Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 75p.
Please send me a copy of your 280 page catalogue I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____

P.W. 879