


practical WIRELESS

55p

Australia 95c
New Zealand \$1.10
South Africa 90c
Malaysia \$2.75

JAN 1980

AF Speech Processor

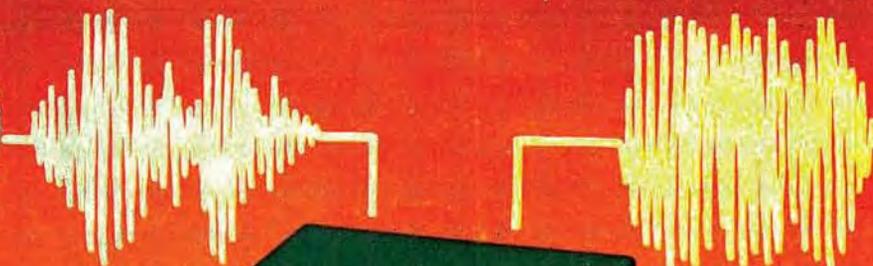

ALSO:

**WIDEBAND RF PREAMPLIFIER
RELIABILITY IN ELECTRONIC CIRCUITS**

SEIKO MEMORY BANK

Calendar watch M354
Hours, mins, secs.
Month, day, date in
12 or 24 hour format
all indicated continuously.
Monthly calendar display
month, year and all dates
for any selected month over
80 year period.
Memory bank function.
Any desired dates up to 11
can be stored in advanced.
2 year battery life.
Water resistant.
Metac Price



£79.50

M11

SEIKO Alarm Chronograph

With WEEKLY Alarm.
Hours, mins, secs, month,
date, day, am/pm.
Weekly alarm - can be set
for every day at designated
time e.g. 6.30 am on Mon,
Wed and Friday.
Alarm set time displayed
above time of day.
Full stopwatch functions,
laptime, split etc.



£89.95

M10

SEIKO Melody Alarm Chronograph

Chiming Alarm,
plus chrono.
Hours, mins, secs, date,
day, 24 hour alarm, 12
hour chronograph, 1/10th
secs, Laptime, Back light,
Stainless steel, mineral
glass.



METAC PRICE

£92.95

M19

SEIKO Calculator Watch

Full specification
calculator with
memory, plus multi
function watch.
Hours, mins, secs,
day, date, backlight,
Automatic calendar.
Long life battery.



£99.95

M27

CASIO CHRONO 95QS-3LB

Stainless steel case,
water resistant to 66 feet.
Hours, mins, secs, am/pm,
year, month, date, day.
Auto-calendar
pre-programmed
until the year 2029.
12/24 hour. Stopwatch
function.
Range 7 hours, 1/100 sec.
(Mode) Net time/lap-time/
1st-2nd place times.
Dual time function.
Accuracy 15 secs per month.
Battery life approx 4 years.



£22.95

M22

CASIO LADIES 86CL-23B-1

Elegant slim line.
Stainless steel bracelet,
fully adjustable.
Hour, mins, 10 sec symbol
second by flash, am/pm.
Month, date, day.
Auto-calendar preprogrammed
for 28th day in Feb.
Accuracy per month 15 secs.
Battery life approx 15 months.



£29.95

M23

CASIO F-200 Sports Chrono

Attractive Mans watch
in black resin with
mineral glass.
Hours, mins, secs, am/pm.
Month, date,
alpha-numeric day.
Auto-calendar set
28th Feb.
Stopwatch working
range 1 hour,
units 1/100 sec. Mode,
Net Time/lap/time/
1st-2nd place times.
Accuracy approx 15 secs
per month.
Battery 12 months.



£14.95

M24

CASIO ALARM CHRONO 81CS-36B

Hours, mins, secs, day,
and also day, month and year
perpetual automatic calendar.
100th sec chronograph to
7 hours.
Net time/lap/time/1st
and 2nd place times. User
optional 12/24 hr display. 24
Alarm. User optional,
hourly chime.
Backlight, mineral glass,
stainless steel.
Water resistant to
100ft.
Battery life approx 4 years.



£34.95

M25

BELTIME Chronograph

(9-Functions)
Hours, mins, secs,
day, date, month,
interchange feature,
automatic calendar,
backlight, Net
time/lap/time.
Stainless steel bracelet.
Battery life 1 year.



£14.95

M34

BELTIME Multi Alarm

29 Functions
Hours, mins, secs,
date, day.
Alarm, chronograph.
Light.
Watch 8 functions,
Alarm 4 functions,
chronograph 17
functions.
Stainless steel
bracelet.



£29.95

M35

CASIO F-8C 3 Year Battery life.

Hours, mins, secs,
am/pm, date, day.
Auto calendar set
28th Feb.
Stopwatch function.
Accuracy 15 secs per
month. Battery life
approx 3 years.



£9.95

M36

CASIO CALENDAR 200

47CS-23B-1 Black.
Stainless steel.
Hours, mins, 10 second
symbol, second (by flash),
am/pm. Month, day, date.
Auto-calendar set from
1901 to 2009.
Full month calendar display,
Dual time function.
Accuracy 10 secs per
month. Battery life
approx 15 months.



£59.95 M37

MELODY Multi Alarm Chronograph

Hours, mins, secs,
Day, Date, Count-
down alarm,
Dual time zone,
1/100th sec
stopwatch.
Lap/split time,
1st and 2nd place
times, Melody test
function.



£26.95

M30

DUAL TIME-ALARM CHRONOGRAPH

Incorporating module
of world famous
Japanese watch
manufacture.
Hours, mins, secs,
days of week, month,
day and date,
24 hour alarm,
12 hour chronograph,
1/10th secs,
lap time, Back light,
stainless steel case
and bracelet,
Mineral glass,
Battery hatch,
long life battery.



£35.00

M12

PICOQUARTZ Microprocessor Alarm Chronograph

Multilanguage-day of
the week can be set
to English, French,
German, Italian or
Spanish.
Chime - every full
hour combined with a
response signal,
beeping at every
pressing of the
functions.
Can be switched off.
12-24 hour format.
Backlight.
Chrono - 1, full scale
chrono with lap,
counting hours upto
24 hrs. Mins, secs,
1/100th secs.
Two Alarm systems.
Two time zones.



£37.95

M32

SEIKO CHRONOGRAPH

Hours, mins, secs
and day of the week.
Month date and
day of the week.
Stopwatch display -
Hours, mins, secs
up to 12 hours
(mins, secs, 1/100 secs
up to 20 minutes).
Lap timing.
Continuous time
measurement of two
competitors.
Stainless steel,
mineral glass.



£56.00

M33

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

practical WIRELESS

JANUARY 1980
VOLUME 56
NUMBER 1
ISSUE 875

BRITAINS LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "*Practical Wireless*" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 85p each, including post and packing to addresses at home and overseas.

Binders are available (Price £3.75 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.**

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

NEWS & VIEWS

- 20 **Editorial:** Service
- 20 **PW Personality:** Brian Dance
- 21 **News . . . News . . . News . . .**
- 31 **Special Product Report**
Radat Industries 2301 Function Generator
- 40 **Production Lines** Alan Martin
Information on the latest products
- 42 **Radio Special Product Report**
KDK FM2016E Synthesised 2m Transceiver
- 46 **Letters**
Comments from *PW* readers
- 54 **Kindly Note**
Burglar Alarms, Sep./Oct. 1979
- 55 **Assessing the New RAE** Arthur Harada
- 67 **PW QSL Card Announcement**

FOR OUR CONSTRUCTORS

- 22 **Model Radio Control—2** J. Burchell & W. S. Poel
The transmitter and its construction
- 38 **Wideband RF Pre-amplifier** M. Tooley & D. Whitfield
A versatile 20dB "gain-block"
- 48 **AF Speech Processor** E. A. Rule
Increase your transmitter talk-power
- 60 **Burglar Alarms—3** P. J. Wales
The *PW* "Parkhurst" microwave motion detector

GENERAL INTEREST

- 32 **Wembley to the Weser** Joe Bishop
Bringing TV to the British Forces in Germany
- 56 **Reliability in Electronic Circuits** Ben J. Duncan
Considerations for trouble-free operation
- 68 **On the Air**
Amateur Bands Eric Dowdeswell
Medium Wave DX Charles Molloy
Short Wave Broadcasts Charles Molloy
VHF Bands Ron Ham

We regret that Hi-Fi Glossary Part 4 has had to be held over

Our February issue will be published on 4 January
(for details see page 47)

All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronic D.I.Y. world. It has been tried, tested and proven to be a totally reliable. Assembly only takes 1-2 hours and installation is even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the normal.

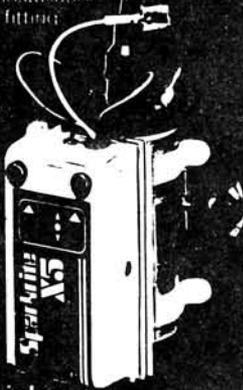There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light systems, function light and security changeover switch. Will work all rev counters.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISE SE VERYTHING NEEDED

Die pressed case. Ready drilled, aluminium extruded base and heat sink. coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.

Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy"



Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates,
82 Bath Street, Walsall, WS1 3DE.

Electronics Design Associates, Dept. PW180
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D.

I enclose cheque/PO's for

X5KIT £16.95

£

Cheque No. _____

ACCESS OR BARCLAY CARD No. _____

Send SAE if brochure only required.

WE STOCK THE PRODUCTS OF

EAGLE
WELLER
DRAPER
SPIRALUX
KNIPEX
SERVISOL
BARNARD'S
& BABANI
NEWNES
JAYBEAM
LIDEN PLASTICS
GREENPAR

B. BAMBER ELECTRONICS

5 Station Road, Littleport Cambs.
Telephone: (0353) 860185

1980 ELECTRONICS CATALOGUE now available price 75p + 20p postage. If you send £1.55 you will receive our catalogue plus six bi-monthly shortform catalogues to keep you up to date with prices and special offers.



£125.00
SAFGAN
ST-45

SINGLE TRACE
OSCILLOSCOPE

- 10mv/div ● 5MHz
- BRITISH

ST-45 SPECIFICATION

VERTICAL SYSTEM

Sensitivity: 10mv/div - 5V/div in 9 cal. steps. Bandwidth (3dB): DC Coupled: DC - 5MHz, AC Coupled: 5Hz - 5MHz. Rise time: 70nsec. Input Impedance: 1MΩ +22p approx. (for all ranges). 50Ω for 10mv/div - 50mv/div. Input coupling: AC, GND, DC. Max Input volts: ±400V peak. Accuracy: ±5%.

HORIZONTAL SYSTEM

Timebase speeds: 50ms/div - 1μsec/div in 15 cal. steps. with x5 Multiplier to 250m sec/div and x5 Expansion to 200n sec/div. External - x sensitivity: 1V/div. External - x Bandwidth: 500KHz. Accuracy: ±5%.

ACCESSORIES

Passive Probe switched (X1; REF; X10) 100MHz bandwidth £11.50 + VAT. BNC to 4mm Socket Adaptor £2.95 + VAT.

TRIGGER
Internal: 0.5div (10Hz - 2MHz), 1div (2MHz - 5MHz). External: 100mv (10Hz - 2MHz), 200mv (2MHz - 5MHz). Bright Line Auto; trace free-runs in absence of signal. Trigger Level: Selects triggering point. Trigger (+)ive and (-)ive slope selection.

DISPLAY

Graticule: Blue, ruled 8x10 div's (6.4cm x 8cm). CRT: Thorn - Brimar 1.5Kv Monoaccelerator/P31.

GENERAL

Power consumption: 10VA approx. Mains Selection: 200V - 220V - 240V rms (40Hz - 60Hz). Size: W - 165mm; H - 215mm; D - 300mm. Weight: 10lbs - 4.5 kg approx. Case, aluminium with black PVC finish and black handle; front panel white with black control knobs. Black feet and tilt-bar.

ORDERS TO: SAFGAN ELECTRONICS LTD.,
56 Bishops Wood, St. Johns, Woking,
Surrey GU21 3AB or TEL: Woking 66836

Please send me ST-45 Probe Adaptor

I enclose PO/Cheque (Goods + 15% VAT + P&P £3.00)

Name

Address

*Ex. VAT UK



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator, tape jack socket Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary Rear panel features fuse holder, DIN speaker and input sockets: 20 x 20 watts RMS 40 x 40 watts peak for use with 8 to 15 ohm speakers
Size 14 1/4" x 3" x 10" approx. **NEW** feature—units now includes a built in four channel stereo sound facility

£31.90
£3.00 p&p

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak for use with 4 to 15 ohms speakers



£31.50 p&p £3.00

SPECIAL OFFER

30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge.

£57.00
+ p&p £6.00

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max 8 ohm impedance

£15.25
Per stereo pair
£3.65 p&p



BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device.

£25.50
p&p £2.60

A.O.C. QLM 30 Mk III Magnetic Cartridge to suit.

£7.95



BSR Manual single play record deck with auto return and cueing lever fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use
OUR PRICE £11.25 p&p £2.75

GARRARD DECK MODEL CC 10A


Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth

£8.15 p&p £2.05 Size 12" x 8 1/2"

UNIT AUDIO STAND

Can be used with TV too! Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors

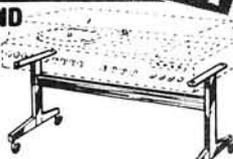£3.95 £1.50 p&p
24" x 12 1/2" x 11 1/2" approx.



BARGAIN FOR PERSONAL SHOPPERS ONLY
Altone UA4 Stereo System

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones
complete with speakers **£35.75**

Micro Cassette Recorder
Pocket size—home or office use or when travelling.

£14.25

Battery operated fluorescent camping lamp.

£4.80

Runs off 8 U2 batteries.

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE
PRICE & AT OVER 25 PER PACK

SEE OUR PRICES

1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input
OUR PRICE p+p £1.00 £5.00

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs
OUR PRICE p+p £1.00 £7.65


illus. £7.65

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit

Size approximately 9 1/4" x 8 1/4" x 4"

p&p £2.25 **£12.25**

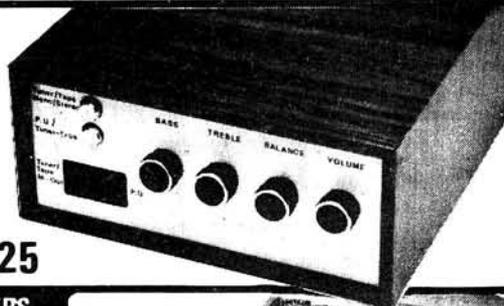

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS

ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance **£3.00**

plus £1.50 p&p

Two Way Speaker Kit

Comprising of two 8" x 5" approx 4 ohm bass and two 3 1/2" 15 ohm mid range tweeter with two cross-over capacitors **£4.05**

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT per stereo pair plus £1.55 p&p

BARGAINS FOR PERSONAL SHOPPERS

LCD Solar 5 function with backlite stainless steel finish case and strap **£7.40**

LCD Solar Chrono 9 function with backlite stainless steel finish case and strap **£9.55**

Chrono stop watch 9 function with back lite stainless steel finish case and strap. **£8.95**

Solar Alarm LCD stainless steel case and strap. **£21.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer **£12.20**



100 Watt Power Amp Module **£14.25**

Mains power supply for above unit **£3.60**

DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3/4" approx tweeter inc crossovers **£20.45**

VIDEOMASTER Super Score TV Game with pistol mains operation **£15.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation **£42.90**

ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop. **£24.50**

100 WATT MONO DISCO AMP

Size approx 14" x 4" x 10 1/4"
Brushed aluminium fascia and rotary controls

Five vertical slide controls, master volume, tape level mic level, deck level, L PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to B No. 2 or vice versa Pre fade level control (PFL) lets YOU hear next disc before fading it in VU meter monitors output level Output 100 watts RMS 200 watts peak p&p £4.05 **£66.45**



50 WATT MONO DISCO AMP

£30.60
p&p £2.70

Size approx. 13 3/4" x 5 1/4" x 6 1/4"
50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



BARGAIN OFFER
Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00.

OUR PRICE £11.95
P. & P. £2.50



323 EDGWARE ROAD, LONDON W2
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Prices correct at 1.8.79 and subject to change without notice
NOTE: Persons under 16 years not served without parent's authorization.

BOOBS



No, not THAT kind, we mean the mistake kind of boob, but don't worry they are not serious, at least as far as you are concerned.

As the acknowledged kit leaders in POWER MOS-FET technology, (as far as we can see about the ONLY ones), we did make a couple of boobs when we designed the WINTON.

1. We did it so dammed well we don't know what to do for an encore, and
2. We grossly underpriced it.

The very few prestigious names using POWER MOS-FETS are still currently about £400 above us, and with the pound sinking slowly against the Yen will probably continue to do so.

Thus, as we see it the WINTON is one of the biggest HI-FI bargains ever, gather a few details of what the £600 devices on the market offer you, then send us a 10p stamp and in return we'll send you our indescribably biased Bumph sheet, if you compare the two we think you will be in for a very pleasant surprise.

Forget the 2nd Mortgage, build the affordable WINTON, and sit back to listen to the Music NOT the sound of the amplifier.

The Superlative WINTON is available for your convenience packed as follows:

- Pack (A) All Capacitors and Fixed Value Resistors, (Inc. 7 Amp ripple Res. Caps.) **£21.93**
- Pack (B) Switch Bank, Switches, Potentiometers, Pre-Sets & all Knobs **£15.93**
- Pack (C) Printed Circuit Board (Tinned, Drilled, & Overlay Printed) & Pins **£8.28**
- Pack (D) Hardware Pack, consisting of precision formed & punched Chassis, Black Epoxy finish Heat Sinks, Teak Veneered Cabinet, all screws, wire, fuseholders, etc., and a super Brushed Silver Aluminium Fascia Panel. **£40.25**
- Pack (E) All Semiconductors, (Including HITACHI POWER MOS-FETS) **£31.21**
- Pack (F) Special LOW HUM FIELD Toroidal Transformer **£23.55**

COMPLETE KIT, of all parts necessary to build the P.W. WINTON **£133.50**

Order with complete confidence (C.W.O. only please) from:

T. & T. ELECTRONICS
Green Hayes, Surlingham Lane,
Rockland St. Mary, Norwich, NR14 7HH.

ALL PRICES INCLUSIVE OF V.A.T. & CARRIAGE

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all . . .

. . . our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.Cs, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.


Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including I.Cs, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

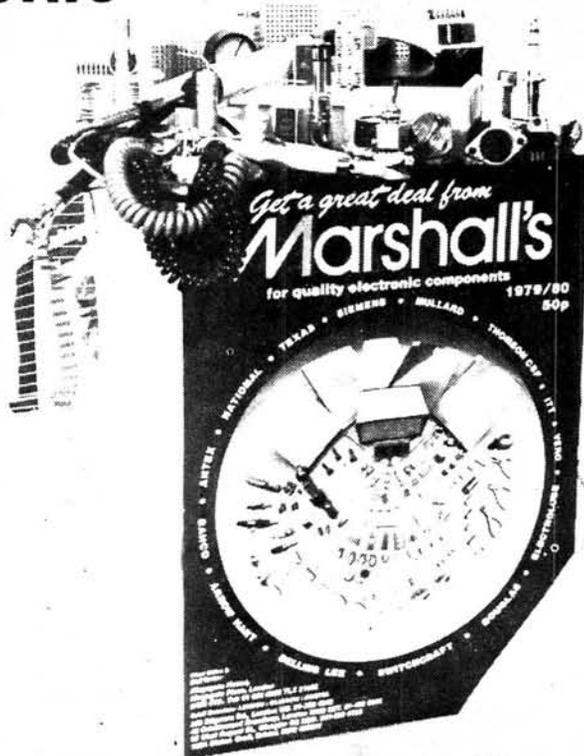Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept. Q276 Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number

The new Toolrange catalogue



still the only catalogue of its kind

The New Toolrange Catalogue is still the only comprehensive single source of electronic tools and production aids.

The product range has almost doubled since last year and now over 2,000 tools, toolkits and service aids are illustrated in full colour.

Products from over 100 top manufacturers are available from stock.

Over 60,000 catalogues are now in circulation. If you don't have one simply write, telephone or telex Toolrange for your free copy.

toolrange


Upton Road, Reading, Berks. RG3 4JA
Telephone: Reading (0734) 22245 Telex: 847917

RADIO EXCHANGE LIMITED

New master kit EMK Mark II

A completely Solderless construction kit, with Ready Drilled Bakelite Panels, Nuts, Bolts, Wood Screws, etc. Also in the Kit, Transistors, Capacitors, Resistors, Silicon and Germanium Diodes, Integrated Circuit and LED, Potentiometer, Switch, Tuning Capacitor, Wire Sleeving, Knobs, Dials, Loudspeaker and Speaker Case, Crystal Earpiece, Ready Wound Medium Wave and Long Wave Ferrite Rod Aerial. **A range of Circuits with Pictorial Diagrams and Instructions are supplied with the Kit.** Covering Medium Wave and Long Wave Radio Receivers

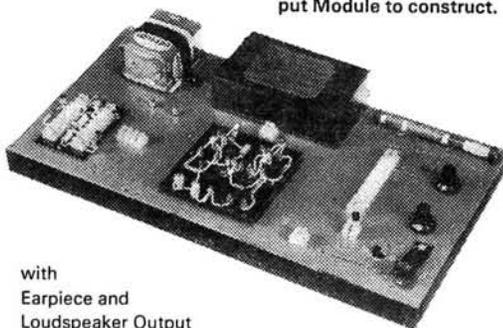With special Power Output Module to construct.



with Earpiece and Loudspeaker Output Stages, Amplifiers, Test Equipment, Metronome and Noise Generators, Morse Code Practise Oscillator with Key and Circuits using the IC and LED supplied. Everything necessary to build and


operate the Projects supplied in the Kit. Battery used PP9 volt (not supplied). Size 19" x 9 1/2" x 1 3/8".

New model RX002

Wave-band coverage as RX001 but with Tone Control, extra Transistor, for more power, 39" Telescopic Aerial and Battery Economiser Switch. Uses Ever-Ready PP7 battery. Flat Area Size 13" x 9 1/2" x 1 3/8".

Kit comes complete with instruction manual pictorial and circuit diagrams.

£12.99 + P & P £1.30

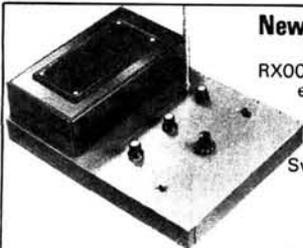

8 Transistors and Four Diodes. Multiband AM Receiver.

£17.99 + P & P £1.30

SXB2 — powerful two band short wave loudspeaker receiver



8 Transistors and 4 Diodes. A world of listening on the Short Wave Frequencies, with this highly sensitive self contained Short Wave Radio. Complete with Telescopic Aerial, Loudspeaker, Gain and Tuning Controls and all components necessary to build it. Covering approximately 60 metres to 18 metres. Uses Ever-Ready PP9 volt battery. Kit comes complete with Instruction Manual, Pictorial and Circuit Diagrams. Size 6 3/8" x 6 3/8" x 6 3/8".

£10.95 + P & P £1.30

New model RX001



A highly sensitive multiband AM Receiver giving Room Filling Volume; Covering Medium Wave, Long Wave, Trawler Band and Three Short Wave Bands. Seven Transistors and four Diodes, Push-Pull output stage with quality Loudspeaker

and internal Ferrite Rod Aerial. Kit includes all parts to build it up including rubber feet and ready drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses 9 volt battery not supplied. Flat area size 9 1/2" x 6 1/2" x 1 1/2".

£10.70 + P & P £1.30



Self contained Multiband VHF Receiver Kit.

8 Transistors and 4 Diodes. Push-Pull output. Quality Loudspeaker, Gain Control, Swivel, Chrome Plated Telescopic Aerial, VHF Tuning Capacitor, Resistors, Capacitors, Transistors etc. Will receive T.V.

New model ECK2-(M.)


Sound, Public Service Band, Aircraft, VHF local Stations etc. Operates from 9 volt battery (not supplied with Kit).

Size 12 1/2" x 6 1/2" x 1 1/2".

Complete kit of parts. Kit comes complete with manual pictorial and circuit diagrams.

£9.99 + P & P £1.10

New Roamer Ten model R.K.3.

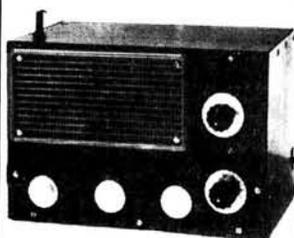

Multiband V.H.F. and A. M. Receiver. 13 Transistors and Six Diodes.

Quality Loudspeaker with Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multi-band A. M. section with separate Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Powered by PP9-9 volt battery.


Complete kit of parts including carrying strap. Building Instructions and operating Manuals

£16.95 + P & P £1.30

V.H.F. AM multiband receiver VX8

This is an updated version of our excellent RK3 Model; Employing a new Flat Look, different layout, extra Slider Switch and projected loudspeaker Case.

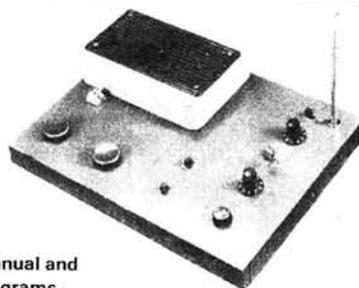Waveband Coverage and components including 39inch Telescopic Aerial as the RK3. Complete with VX8 instruction



manual and diagrams, uses 9 volt battery.

Size 13" x 9 1/2" x 1 3/8".

£17.95 + P & P £1.30

V.H.F. air converter kit



Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome-plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. Size 5 1/2" x 1 1/2" x 3 1/2". All parts including case and plans.

£6.05 + P & P 90p

E.V.6 Plus One



Build this exciting new design. Now with 7 Transistors and 4 diodes.

MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and 2 1/2"

loudspeaker. Attractive case with speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. All parts including Case and Plans.

Total Building Costs: £8.20 + P & P £1.10

Fill in the coupon and send to:
RADIO EXCHANGE LTD.
61A High Street, Bedford MK40 1SA Tel: 0234 52367

All prices include VAT

● Callers side entrance "Lavelis" Shop. ● Open 10-1, 2.30-4.30 Mon.-Fri, 9-12 Sat. Reg. No. 788372

I enclose £ _____ for _____
NAME _____
ADDRESS _____

PW180

Eddystone

The Leaders in Short Wave

at **SONIC SOUND AUDIO**
BRITAIN'S No. 1
AUDIO STORE

SOLE UK
DISTRIBUTORS
FOR EDDYSTONE.



Sonic Sound, the premier home entertainment store have now added yet another big name in the field of sound equipment to further enhance their prestige in London's centre of the audio/visual and Hi-Fi field in Tottenham Court Road.

Eddystone, at the top of the tree since short wave began, have now appointed Sonic Sound Audio as sole retail distributors in the United Kingdom.

Anyone even contemplating purchasing short wave equipment, be they looking for the best possible available for their Embassy, press department or home use, should visit or contact Sonic where they will be able to view and listen to the most comprehensive range of the latest short wave equipment on the market today.

Listen and choose in comfort at Britain's most up-to-date air conditioned sound demonstration studios. Full ranges of Hi-Fi, Video equipment, In-car and portables, etc., from all leading manufacturers; B & O, Sanyo, Sony, Hitachi, Pioneer, J.V.C. . . .



THE COMMUNICATION CENTRE

SONIC SOUND AUDIO

248-256 TOTTENHAM COURT ROAD LONDON W1 TEL: 01-637 1908

Eddystone

A Marconi Group Company.



HOME COMPUTING BARGAINS

Full keyboard, cassette interface, use your TV as a VDU - Ohio Scientific Superboard II fully assembled, 8K basic, 4K ram, special offer price now includes free power supply and modulator kit £188 + 15% VAT. Tandy TRS80 level 2 basic, 16K ram, includes modulator and psu £450 + 15% VAT.

SCINLAIR PRODUCTS

PFM200 £51.95, case £3.40, adaptor £3.40, connector kit full £11.27. Microvision TV £91.44, mains adaptor £3.40, case £3.40. DM350 £71.82, DM450 £102.17, DM235 £51.95. Accessories for all 3 models - rechargeable batteries £7.99, mains adaptor/charger £3.94, case £9. Enterprise prog calculator £23.27. New 10MHz scope £145.

COMPUTER GAMES

Chess challenger 7 £84. Voice challenger £228. Checker challenger 2 £46. Checker challenger 4 £84. Atari video computer £147. Cartridges £14.32. Star Chess £62. Chess champion 6 £49.95.

CONTINENTAL SPECIALITIES PRODUCTS

EXP300 £6.61. EXP350 £3.62. EXP325 £1.84. EXP650 £4.14. EXP48 £2.64. LP2 £20.70.

TV GAMES

Tank battles kit £6.34. AY-3-8500 chip £5.27, kit £4.26. Stunt cycle AY-3-8760 chip £13.63, kit £4.00. 10 game paddle 2 AY-3-8600 chip £10.25, kit £7.03. Racing car chip AY-3-8603 £13.63. Modified shoot kit £5.28. Rifle kit £5.27. Colour generator kit £9.05. Joystick 220K £11.80.

MAINS TRANSFORMERS

6-0-6V 100ma 76p, 1 1/2 £2.60. 9-0-9V 75ma 76p, 1a £2.22. 23 £2.89. 12-0-12V 100ma 92ma, 1a £2.75. 15-0-15V 1a £3.09.

JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 Watts £2.08. JC20 10 Watts £3.14.

FERRANTI ZN414

IC radio chip 85p, extra parts and pcb for radio £4.10, case £1.06.

PRINTED CIRCUIT MATERIALS

PC etching kits - economy £2.32, standard £4.36. 40 sq ins pcb 66p. 1 lb FeCl £1.30. etch resist pens - economy 50p, dalo 84p. drill bits 1/32" or 1mm 27p. etching dish 89p. laminate cutter 82p.

S-DECS AND T-DECS

S-Dec £3.79. T-Dec £4.59. u-Dec £4.69. u-DecB £7.16. 16 dil adaptor £2.31.

BATTERY ELIMINATORS

3-way types with switched output and 4 way multi-jack - 3/4/6V 100ma £2.39. 6/7/9V 300ma £3.14. 100ma radio types with press stud connectors 9v £3.57. 6v £3.57. 4v £3.57. 9 + 9v £4.79. 6 + 6v £4.79. 4 + 4v £4.79. cassette recorder mains unit 7 1/2 100ma with 5 pin din plug £3.57. fully stabilized type 3/6/7 1/2 9v 400ma £5.76. car converters 12v dc input, output 9v 300ma £1.19. output 7 1/2 300ma £1.19. output 3/4/6/7 1/2 9/12v 800ma £2.66.

BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4 1/2 v £1.49. 6v £1.49. 9v £1.49. 4 1/2 - 4 1/2 v £1.92. 6 + 6v £1.92. 9 + 9v £1.92. cassette type 7 1/2 v 100ma with din plug £1.49. heavy duty 1 1/3 way types 4 1/2 v 7/8 1 1/3 1 1/4 1 1/2 1 1/2 2 1/2 2 1/2 3 1/4 4 1/2 1A £4.95. 2A £7.72. car converter input 12v dc, output 6/7 1/2 9v 1A stabilized £1.35.

STABILIZED POWER KITS

The first price is for kit without transformer, the bracketed price includes transformer. 8-way types 3/4/6/7 1/2 9/12/15/18v 100ma £1.74 (£2.50). 1A £2.98 (£5.10). 2A £4.10 (£6.87). variable voltage models 2-18v 100ma £2.12 (£2.98). 1-30v 1A £2.98 (£5.95). 1-30v 2A £4.98 (£11.24).

BI-PAK AUDIO MODULES

AL30A £4.08. PA12 £8.38. PS12 £1.58. T538 £2.70. S450 £25.06. AL60 £5.06. PA100 £17.33. SPM80 £4.74. BMT80 £6.08. Stereo 30 £21.57. MA60 £38.27.

COMPONENTS

1N4148 0.3p. 1N4002 3.1p. 741 8 dil 18p. 723 14 dil 31p. NE555 8 dil 25p. bc183. bc212. bc547. bc549 4.2p. bc182. bc184. bc212. bc214. bc548 5p. tip31c. tip32c 30p. tip41c 39p. bd131. bd132 27p. plastic equiv bc107 5p. fuses 20mm x 5mm cartridge 15. 25. 5. 1. 2. 3. 5 Amp quickblow 1p. anti-surge 3.6p. resistors 5% 1W £12 10R to 10M 1p. 0.8p for 50 + of one value. polyester capacitors 250v .015. .068. 1mf 1.5p. .01. .033. .33 2.8p. .022. .047mf 3.3p. 22. 47mf 4.9p. polystyrene capacitors £12 63v 10 to 1000pf 3p. 1n2 to 10n 4p. ceramic capacitors 50V E6 22pf to 47n 2p. electrolytic capacitors 50v 5. 1. 2mf 5p. 25v 5. 10mf 5p. 16v 22. 33mf 5p. 47. 68mf 3.5p. 100mf 6p. 330. 470mf 9p. 1000mf 10p. zeners 400mW E24 2v7 to 33v 7p. preset pots subminiature 0.1W horiz or vert 100 to 4M7 6p. potentiometers 1W 4K7 to 2M2 log or lin single 27p. dual 67p. 1 1/2 red LEDs 9.7p. ic sockets 8 dil 8.7p. 14 dil 10.1p. 16 dil 12p.

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ainslie)

Copy of original article supplied on request

- IF Sub-Assembly (G8) **£7.82**. P&P 85p.
- Mullard ELC1043 V'cap UHF Tuner **£6.33**. P&P 40p.
- 3-way Station Control Unit **£1.38**. P&P 30p.
- 6-way Station Control Unit (Special Offer) **£1.15**. P&P 35p.
- Power Supply Prtd Circuit Board **£1.15**. P&P 35p.
- Res. Caps, Semiconds, etc. for above **£6.67**. P&P 45p.
- Mains Transformer for above **£2.88**. P&P 35p.
- P&P all items 95p.

(Price of goods and P&P includes 15% VAT)

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6

(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

S.W.T.P.C. and M.S.I. EQUIPMENT IN STOCK

We have limited stocks of the following items for immediate delivery:
ASSEMBLED DISPLAY MODELS

UNUSED

CT-64 Terminals	£255
CT-VM Monitors	£120
GT-61 Graphics Terminal	£85
AC-30 Cassette Interface	£65
FD-8 Single & Double Disk Drives	£760
PIA-1 and Bootstrap	£1335
PRR-68 Prom/Ram Board	£25
	£60

KITS

CT-64 Terminals	£225
GT-61 Graphics Terminal	£65
AC-30 Interface	£50
Also available - RT68	£25
Micro-term terminals	£300-£700

Phone now while stocks last to:

Mr. Watts: 01-636 4876.

Please phone the above number if there are any queries.

SWANLEY ELECTRONICS

DEPT PW, 32 Golds Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 30p to the total cost of your order for postage. Prices include VAT unless stated. Lists 24p post free. Overseas customers deduct 13%. Official credit orders welcome.

P.C.B'S FOR PRACTICAL WIRELESS PROJECTS

Dec. 78.	Car Radio L.W. Converter	R032	Price £2.79 & 20 pence p & p.
Jan. 79.	Acoustic Delay Line	R018	Price £3.77 & 20 pence p & p.
Jan. 79.	Dorchester	R033	Price £11.00 & 30 pence p & p.
Jan. 79.	Sandbank Met. Det.	R035	Price £3.41 & 20 pence p & p.
Feb. 79.	Hythe Receiver	WR037	Price £6.34 & 20 pence p & p.
March 79.	Hythe Receiver	WR038	Price £2.98 & 20 pence p & p.
March 79.	Soudlite Converter	WK001	Price £6.33 & 20 pence p & p.
March 79.	Tone Burst Generator	R023	Price £1.71 & 15 pence p & p.
March 79.	Wide Band Noise Source	WR036	Price £0.74 & 12 pence p & p.
April 79.	FM Multitester	WR040	Price £3.05 & 15 pence p & p.
May 79.	Car Test Probe	WR042	Price £0.96 & 15 pence p & p.
May 79.	Follow up to PW Gillingham	WR044	Price £1.45 & 15 pence p & p.
May 79.	PW Imp	WR043	Price £1.52 & 15 pence p & p.
May 79.	Inline Crystal Calibrator	WR041	Price £1.68 & 15 pence p & p.
June 79.	Jumbo Clock		Price £9.52 & 30 pence p & p.
June 79.	Logical O's+X's	WR046/ 7/8/9	Price £12.84 & 30 pence p & p.
June 79.	Trent	WR050	Price £4.06 & 20 pence p & p.
July 79.	AAM/FM Frequency Readout	WR052	Price £3.66 & 20 pence p & p.
	V.MOS Top Band Transmitter	WR056	Price £4.08 & 20 pence p & p.
	Sound Operated Switch	WK005/6	Price £3.74 & 20 pence p & p.
	Inexpensive A/F Voltmeter	WR055	Price £1.15 & 15 pence p & p.
August 79.	Telephone Bell Repeater	WR053	Price £1.15 & 15 pence p & p.
August 79.	Automatic Intercom	WR043	Price £6.20 & 20 pence p & p.
Sept. 79.	Automatic Intercom Part 2	WR058	Price £0.60 & 12 pence p & p.
Sept. 79.	Noise Blanker	WR057	Price £1.24 & 12 pence p & p.
Oct. 79.	Burglar Alarms	WR059	Price £1.23 & 15 pence p & p.
Oct. 79.	Burglar Alarms	WR060	Price £1.91 & 20 pence p & p.
	Radio Control Receiver	WR064	Price £2.92 & 20 pence p & p.

FULL RANGE OF R.S. COMPONENTS

AVAILABLE

P.W. JUMBO CLOCK KIT £31.00

All prices include V.A.T.

Send

C. BOWES & CO. LTD.,
4, Wood Street, Cheadle, Cheshire SK8 1AQ.
Tel. 061-428-4497.

Please state type number and enclose cheque or postal order.

POWER UNIT INVERTOR I/P 115v 50c/s provides a high & low voltage O/Ps at 25Kc contains 6 pot cores inc types FX2240/42/43, 2xHV TO. 3 pwr trans, 4x400v 3 amps diodes, 8xBC107, 2xBFY52, (transistor types may vary) 2xThyristors, Zener & swt diodes, elec conds, 3x20mm fuse holders, all in screened case size 9x3½x4" with circ. £4.50 or 2 for £8.

RECEIVER UNIT. small high performance receiver uses 7 min. plug-in valves covers 2.5 to 20Mc/s in 3 bands as RF stage, B.F.O. volt stab, provides O/P for high res or crystal earphones, direct freq cal with geared drive, size 5 x 3¼ x 3½" these req ext supplies of 200v 40Ma DC & 6.3v AC 1a. Supplied tested with circ, no ext case. £25.00.

SELECTIVE CALLING UNITS contain telephone dial small 500Ua meter, low volt stab power unit, 9 circ brds, lamps, relays, swts etc thought to generate dialling tones that can be selected on front panel, 200/250v I/P transis units new cond with circ details £22.

MAINS TRANS pria 200/250v sec 340-250-0-250-340v at 210Ma plus 6.5 at 5 amps twice & 5v ct at 5 amps size 5x5x6" we have tested these a 700v DC at 250Ma using full sec with no L.T. load, will also give 17.6v at 5 amps new boxed £8.50.

RECEIVER UNIT small 5 valve, Superhet inc BFO covers 2 to 8Mc/s in two bands direct calibration reqs 135v HT & 1.5V DC in case size 8x5x4" for use with high or low res phones with circ. £13.

INDICATOR UNIT with 3" CRT type 3WP1 (more modern than 3BP1) plus 13 miniature valves in case size 10x8x21" contains 400c P.U. with circ £25.

PANEL METERS mixed mostly 2 & 3" dia types 4 different for £4.

TRANSMITTER ASS. Small low power 15/25w 2.5 to 20Mc/s Tx unit crystal controlled sold for breakdown contains 2x 175Pf Tun cond, miniature 500Ua meter, morse key, coils, swts, RF chokes, knobs etc. Supplied less valves, contains most parts for Rx or Lp Tx ATU with circ. £8.50.

TRANSIS INVERTOR 12v DC I/P O/Ps 425v DC at 120Ma or 180v DC 40Ma also 6.3v DC at 2.5 amps in case size 5½x4x3" tested with circ. £10.50.

MAINS TRANS Pria 200/250v sec 225-135-0-135-225 at 70Ma 6.3 2a & 6.3 700Ma. £4 matching choke £1.50 also C core trans sec 250v 60Ma & 6.3v 3 amps £3.

MOTOR for use on 115v AC rated 1/18th HP int at 5000 RPM brush type size 5" by 2¼" dia with pinion 3/8th by ¼" fitted governor reqs ext 220 ohm 25 watt res & .luf cond, new American spares okay for PCB Drills. £6.50.

VARIABLE STABILISED P.U. Solartron bench type 200/250v I/P O/P var from 0 to 500v DC at up to 150Ma floating O/P also 6.3v 5a fitted Volt/Ma meter overload protection on 19" panel size 9" high 13½" deep no ext case £35. We have a few table cases intended to take two of these units at £12.

GRID DIP OSC. American Services pattern PRM-10 covers 2 to 400Mc/s cont uses set of 7 plug in coils with direct calibration as 4 functions Grid Dip, Osc Det, Absorbion W.M. & Sig Gen for use om 115v 50c/s 25 watts, the head unit with indicating meter can be removed from carrying case which contains P.U. and function selector swts, the head unit measures 7x4x3 exc coil, meter 100 Ua.5 valves inc rect. All contained in carrying case size 11x9x5" with circ. £55 new cond or £45 good S/Hand cond.

HELIPOTS & DIALS standard 10 tr dial to fit 3/8th bush £1.50 or with 100K helipot £2.

ROTARY SWTS larger inst type 2p 23w & 8p 12w both £1.60 U.H.F. TV tuner transis manual tuned type new with circ £2.50.

HEADPHONE LEAD ext cord type with stereo jack ¼" approx 30" ext new £1.

DIODES Sil pwr diodes stud type rated 10 amps ea 100 PIV 4 for £1.60 1000 PIV 4 for £2.50 new unused.

CRYSTALS 10X & 10XJ types two pin in range 5 to 7.5Mc/s 20 mixed for £2.20.

Above prices include Carr & Vat goods ex equipment unless stated new, SAE for list 23/1 or enquiry.

A. H. SUPPLIES.

122, Handsworth Rd. SHEFFIELD. S9 4AE.

Telephone 444278 (0742).



add a new dimension to your stereo enjoyment

FF1
STEREO SPEAKER WALL MOUNTING KIT

- Vibration proof
- Swivel adjustment

FF1..... £6.89
FF2..... £18.99
FF3..... £19.99

These are recommended retail prices and include VAT at 15%.

FF2
STEREO SPEAKER FLOOR STANDS

- Unique speaker Tilt device
- Adjustable height



FF3
ADJUSTABLE STEREO SPEAKER TROLLEYS

- Easy manoeuvrability
- Easy to fit and install



FIDELITY FASTENINGS LTD.
The Ridgeway, Iver
Bucks SL0 9HW
Tel: Iver (0753) 654222

NEW LOW PRICES ALL EX-STOCK

REAL-STATE-OF-THE-ART

**NEW AC/DC/BATTERY PORTABLE
FREQUENCY COUNTER
FROM OPTOELECTRONICS USA**

Model OPTO 7000

7 DIGITS 10Hz to 600MHz

ONLY £141.45 inc. (was £168)
(£120 + £3 p&p + VAT £18.45)

Complete with built-in NiCads, charging circuits & rear panel switch for 1Hz resolution.



Size only 1 1/4" H x 4 1/4" W x 5 1/4" D.
The miniature go anywhere counter that gives you more range, visibility accuracy and versatility than any comparable unit at anywhere near as low price.

* TCXO time base 0.8PPM/°C (0.0001% accuracy) less than 2PPM per year aging * Deluxe gold and black anodised aluminium case * H1Z and 50 ohm inputs * 1 sec and 1/10 sec gate times * Built in prescaler and preamps standard * Auto decimal * BNC connectors * No direct current required for RF pick up * State of the art LS1 circuitry * Sensitivity 10mV to 60MHz 25mV to 150MHz 50mV to 450MHz (less than 75mV guaranteed) * Power requirement 7.5V AC/DC - less than 250mA.

ELENCO PRECISION DMM 1200B

ONLY £66.70 inc.
(£55 + £3 p&p + VAT £8.70)
(for a limited period only)

The most versatile DMM we have ever offered at lowest ever price!

* 3 1/2 digit jumbo LED (0.56") display
* 0.05% basic accuracy * Measures AC/DC voltages from 100 microvolt to 1000 volts, AC/DC current from 1 microamp to 2 amp and resistance from 0.01 ohm to 20 Megohm * Fully overload protected to 1000 volts.



* High input impedance to 10 Megohm * Mains (with adaptors not supplied) or battery (both disposable and Nicads) operation * Uses 1% precision resistors not unstable trim pots * Hi Lo power ohms. Hi for diodes, Lo for resistors in circuit (on how many DMM's costing less than £100 do you find this feature!)

ELENCO POWER SUPPLY MODEL XP-90
13.8V - 8 amps Regulated only £63.25 inc.

Elenco Precision Power Supplies let you operate your mobile or marine or mobile two way radio, CB, tape player AM/FM car radio, or other mobile equipment right in your own home. Elenco provides the exact output voltage no matter what current you use. No loss of power when you transmit due to dropping voltage. Fool proof current protection minimizes surge current that may damage your expensive equipment, works 1000 times faster than any fuse, automatic self resetting. Special circuit protects equipment, user and itself!

SPECIFICATIONS:-

Input Voltage 240V AC
Output Voltage 13.8V DC
Output Current 8 amps
Load Regulation -15V
Line Regulation -15V
Ripple Max. RMS -0.1V
Current Protection 8A Limit
Short Protection
1A Fold back
Crowbar Protection Yes
Output Impedance 0.25 ohms



BE THE HIT AT PARTIES!
YAP BOX - 3 Discreet Sounds
ONLY £9.95 inc.

- Laser Gun
- Siren
- Ray Gun
- Plus many others



Use on car PA system, bicycle horn, or protection against would be attackers.


Invent your own sound effects, make believe you're the police or fireman.
GREAT FOR KIDS OF ALL AGES.

Maclin-Zand Electronics Ltd.
38 Mount Pleasant, London WC1 0AP
Tel: 01-837 1165

Please send me..... PW12
Name.....
Address.....

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

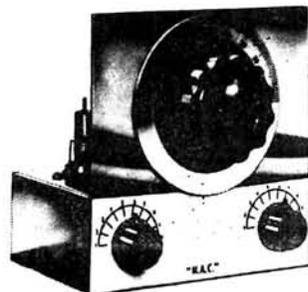

'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories which have been up-dated to suit the novice and the expert. £12.00 INCLUSIVE—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £14.50 this receiver is outstanding value, and will give you hours of interest and entertainment.

NEW TRIPLE T to replace our previous 'K' Kit will be available early this year. WATCH THIS SPACE for further information. All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ

OSMABET LTD

We make transformers amongst other things.

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.
6.3V 1.5A £3.00; 3A £4.15; 6A CT £7.90; 12V 1.5A £3.75; 3A CT £7.90; 6A CT £9.75; 15V 0.5A £3.00; 1.5A CT £7.90; 24V 1.5A CT £7.90; 3A CT £9.75; 5A CT £18.00; 8A CT £29.25; 12A CT £37.50; 40V 3A/CT £13.50.

TWIN SEC TRANSFORMERS: Prim 240V ac.
6V 0.6A - 6V 0.6A; 9V 0.4A - 9V 0.4A; 12V 0.3A - 12V 0.3A; 20V 0.15A - 20V 0.15A; all at £4.15 each; 15V 0.75A - 15V 0.75A £6.40; 15V 1.5A - 15V 1.5A £8.25; 18V 1A - 18V 1A £7.90; 18V 1.5A - 18V 1.5A £9.75; 20V 1.5A - 20V 1.5A £9.75; 12V 4A - 12V 4A £12.00; 25V 2A - 25V 2A £12.00.

MIDGET RECTIFIER TRANSFORMERS: Prim 240V ac.
6.0-6V 1.5A or 9.0-9V 1A £3.40 each; 12.0-12V 1A or 20.0-20V 0.75A £4.15 each; 9.0-9V 0.3A or 12V-0.12V 0.25A or 20V-0.20V 0.15A £3.00 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.
0.10-12.14-16-18V 2A £7.50; 4A £9.40; 0.12-15-20-24-30V 2A £8.25; 4A £12.00; 0.20-30-60V 1A £9.00; 2A £12.00; 0.40-50-60-80-100-110V 1A £12.00.

AUTO TRANSFORMERS 110/240V ac.
30 watt to 4000 watt ex stock, lists.

MAINS TRANSFORMERS, SPECIAL OFFER: Prim 240V ac.
250.0-250V 60 Ma, 6.3V 1A £2.50; 250V 100Ma, 6.3V 2A £3.50; 9V 3A £2.50; 25V 300 Ma 90p.

LOUDSPEAKERS
2 1/2in, 2 1/4in, 2 1/2in, 8 ohm, 3in 35Ω, 3 1/2in 3, 8, 16 or 80Ω all £1.50 each; 8x5in, C/M, 4, 8 or 25Ω, £3.50 each. Many other types available.

"INSTANT" BULK CASSETTE TAPE ERASER
Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V ac, leaflet £7.50.

EDGWISE LEVEL METER FSD 200/μA
Size 1 1/8 x 1 3/8 x 20mm 800Ω £1.50.

CHARGING METERS 1 1/2in diameter
2A or 3A £1.25 each; 5A or 10A £1.50 each.

SYNCHRONOUS GEARED MOTORS, 240V ac.
Brand new, built in gear box, 1 r.p.m. £1.25 each.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS
P.P. sec tapped 3.5-15Ω A-A 6KΩ, 30W £17.50; A-A 3KΩ 50W £28.00; 100W (EL31, KT88 etc) £35.00.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covers valve amplifiers 30W to 400W £1.25.

MULTIWAY SCREENED CABLE, PVC COVERED
35 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; 4 way individually screened 30p; fig 8 twin stereo do screened 15p, metre.

CONDENSERS
Electrolytic 400 μ 400V 75p; 2000/30V 30p; 2200/40V 40p; 8 8mfd 450V 40p; Paper tubular, W/E, 4/160V; 6/160V 30p each, 2mfd 150V 25p.

CARRIAGE EXTRA ON ALL ORDERS
ALL PRICES INCLUDE V.A.T.

Callers by appointment only. S.A.E. Enquiries, Lists.

46, Kenilworth Road, Edgware, Middx.
HA8 8YG. Tel: 01-958 9314

Sonic
HI-FI DISCOUNT CENTRES

**DISCOUNT
SPEAKERS**



Imp 8 or 15 as app.
Guarantees:

**TITAN 5 years
FANE LIFETIME
OTHERS 1 year**

**ALL PRICES
INC. VAT**

Prices correct at 29.10.79

GENERAL PURPOSE

	Rec. Ret. Price	Sonic Price
5" FANE 501	—	£4.95
8" AF MODEL 80	—	£6.95
8" AF MODEL 83	—	£6.95
8" FANE 808T DUAL CONE	—	£3.95
10" ELAC 10RM 10 WATTS	—	£2.50

HI-FI KITS

AF FRI 8" + TWEETER	—	£14.95 pr
FANE MODE ONE 8" + TWEETER	—	£19.99 pr
WHARFEDALE DENTON KIT	£42.41 pr	£30.95 pr
WHARFEDALE SHELTON KIT	£54.32 pr	£38.95 pr
WHARFEDALE LINTON KIT	£75.53 pr	£62.95 pr
WHARFEDALE GLENDALE KIT	£92.78 pr	£85.95 pr

GROUP/DISCO TYPES

12" TITAN T12/50R	£20.20	£16.95
12" TITAN T12/100A	£39.95	£26.95
12" CELESTION G12H 30W	£22.48	£14.95
12" CELESTION G12/50 50W	£19.68	£12.95
12" GOODMANS PD	—	£22.95
12" GOODMANS PG	—	£21.95
12" FANE SPECIALIST PA85	£33.81	£23.95
12" FANE SPECIALIST DISCO 80/2	£34.88	£24.95
12" FANE SPECIALIST DISCO 100/2 £37.01	—	£26.95
12" FANE SPECIALIST GUITAR BOL	£33.81	£23.95
12" FANE SPECIALIST GUITAR 80B/2	£34.88	£24.95
12" FANE CRESCENDO 80	£53.20	£39.95
12" FANE CRESCENDO BOLT	£57.24	£36.95
12" FANE CRESCENDO 12E	£74.50	£51.95
15" TITAN T15/70 70W	£36.95	£24.95
15" TITAN T15/85	£42.95	£28.95
15" TITAN T15/100 100W	£47.95	£35.95
15" FANE SPECIALIST BASS 100	£51.07	£34.95
15" FANE CRES. COLOSSUS 15E 200W	£129.88	£89.95
18" GOODMANS 18P	—	£48.95
18" TITAN T18/100 100W	£59.95	£46.95
18" CELESTION G18/200 std.	£68.88	£48.95
18" FANE CRESCENDO 18E	£122.42	£85.95
18" FANE CRES. COLOSSUS 18E 200W	£138.40	£96.95

HORN UNITS

CELESTION MH1000 25W	£20.95	£14.95
FANE J44	£8.47	£5.95
FANE J73	£13.79	£8.95
FANE J104	£20.18	£13.95

CROSSOVERS (FOR ABOVE)

FANE HPX1R OR HPX2R	£4.21	£2.95
---------------------	-------	-------

Mail Orders/Export enquiries to above, Add £1 carr. on Hi-Fi spkrs. or kits. Otherwise add £1.25 (12" Spkr), £1.50 (15") £2.50 (18")

**SPECIAL OFFER!
COLLARO RECORD DECKS**

- * 'S' Shaped Arm * Auto or Manual
- * 11" Turntable * Ideal for Disco
- £15.95 ea. or 2 for £30.**
- Carr. £1.00 ea.

Also for personal shoppers only

**AMPS, TTABLES, JINGLE MACHINES,
DISCO CONSOLES, LIGHTING, CABINETS,
CREDIT TERMS AVAILABLE** orders £20 over



**GREENTHORPE MILLS
GREENTHORPE
LEEDS LS13 4LQ**



How to make a hobby

The opportunities in electronics, today, and for the future are limitless – throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics – especially for the servicing of radio, TV and all associated equipment – can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.

We give modern training courses in all fields of electronics – practical D.I.Y. courses – courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.

All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.

and a career.


COURSES AVAILABLE:-

- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free 32 page Colour Booklet.

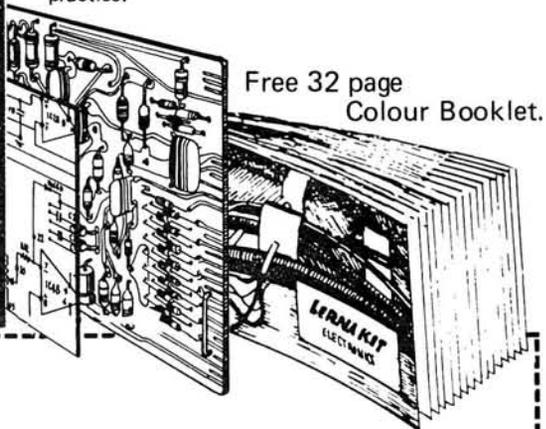

WE ARE AN INTERNATIONAL SCHOOL SPECIALISING IN ELECTRONICS TRAINING ONLY AND HAVE OVER 40 YEARS EXPERIENCE IN THIS SUBJECT.

WA180

NAME.....
 ADDRESS

Block Caps Please

Post now, without obligation, to:-
BRITISH NATIONAL RADIO and ELECTRONICS SCHOOL
 P.O. Box 156, Jersey, Channel Islands.

Beat VAT with VAO (Value added offers) from G3CED

We've proved our point, our Value Added Offers have attracted reams of orders from enthusiasts wishing to purchase our wide range of receivers and transceivers. WE ARE IN BUSINESS TO SAVE YOU MONEY!
All goods come carriage paid, insured and inclusive 15% VAT AND LESS OUR APPROPRIATE VAO!

TRANSCEIVERS RECEIVERS VALUE ADDED OFFER/1

Just send 4 10p stamps for the latest YAESU fully illustrated Catalogue which comes to you with our VAO CREDIT VOUCHER worth £3.60 for your eventual TRANSCEIVER purchase. Or a couple of 10p stamps brings you the Swan leaflets.

VALUE ADDED OFFER/2

Include a World Record Joystick VFA .5-30 MHz. Antenna System 'J' as part of your Transceiver order - System will only cost £40.50 inclusive - SAVING £13.50!

RECEIVERS - PACKAGE DEALS VALUE ADDED OFFER/3

Along with our VAO the savings on packages have increased from £14.15 to £21.45! Complete radio stations, all cables, headphones, Joystick System 'A' antenna - ON THE AIR IN SECONDS!

SUPER PACKAGE R.1.

Features FRG7 RX

£240.80

SUPER PACKAGE R.2.

Features the "ROLLS" FRG 7000

£409.00

SPACE DOES NOT PERMIT US TO LIST ALL OUR WIDE RANGE OF Tx/Rx/Tx-Rx AND OTHER GEAR. IT'S WORTH A STAMP FOR OUR CURRENT LITERATURE.

RECEIVERS ONLY

FRG7 £204.40 FRG7000 £372.60

JOYSTICK ANTENNA SYSTEMS (0.5-30 MHz)

SYSTEM "A"	150w p.e.p. or for the SWL	
SYSTEM "J"	500w p.e.p. Improved "Q" on receive	
		£48.55
		£54.00



Just telephone your card number - 0843 62535 (ext. 5) or 62839 (after office hours) or write (Send 10p) for details of Value Added Offers or general literature. Prices correct as at press.

5 Partridge House, Prospect Road, Broadstairs, CT10 1LD (callers by appointment).

G3CED
G3VFA



CHORDGATE LTD. SWINDON

SILICON TRANSISTORS FULL SPEC.

TIP31B 25p comp. TIP32B 25p, 5 pairs £2.00 or 10 either type £2.00. BFY51 15p 10 for £1.20. 2N3707 gen. pur. NPN 10 for 50p. 2N5293 NPN 75V 4A TAB collector 20p 10 for £1.75. TIP34A PNP 60V 10A 40p 10 for £3. 1N914 25p 10 for 60p. BD525 30p comp. BD526 30p useful up to 50MHz. 5 pairs £2.50 10 either type £2.50.

Fairchild FND10 7 seg. displays 0-15" red common cathode 60p.

Pye dynamics thick film 1MHz clocking oscillator, 5 volt supply, drives 1 TTL load 60p.

368-640KHz XTAL PCB MTG HCU ÷ 2¹⁰ = 360Hz 75p.

444-8KHz XTAL wire end £1.95.

Beehive trimmer 3-30PF 10 for 50p.

1-5-2.5PF min trimmer 5mm x 5mm HOR MTG 12p 10 for £1.

Stettner 3-15PF CER trimmer 10mm dia. vert. MTG 15p 10 for £1.20.

Denco transistor 1FTs interstage 1FT13 60p. Det. output 60p 470KHz.

10 MFD 6-3V tantalum caps bead type 7p. 10 for 60p.

As above 10 MFD 16V 8p. 10 for 70p.

1 MFD 15V tantalum min caps 4mm x 1.5mm 8p. 10 for 70p.

As above 2-2 MFD 5mm x 1.5mm 8p. 10 for 70p.

Colvern 1 watt wire wound pots 25R, 100R, 1K, 2K, 2-5K, 10K, 30K, 40p. 10 for £3. State value.

Electrolytic caps single end tag. 680 MFD 63V 60p. 4700 MFD 16V 60p. 6800 MFD 10V 60p. 15000 MFD 10V 60p. Screw terminal 4700 MFD 40V 60p.

6F10 stud rect. 100V P.I.V. 6A 25p. 4 for 80p.

LA4245 mullard core 15p.

Mullard pot cores. All supplied with data sheet. LA1 50p. LA2 60p. LA4 70p. LA7 80p.

Waveform generator kit. PCB and all components to build 20Hz-20KHz generator with sine square and triangle outputs. 10-30V supply, complete with data sheet £9.95.

For all above supplies add 35p post and packing. Orders over £4.00 post and packing inclusive.

Printed circuits detailed below add 35p post and packing 1-3 boards. Larger quantities post and packing inclusive.

PCB contains 2 IP 10W wafer switches. 2 x 7440 I/C 2 x 74141 I/C. Various logic I/Cs 1N4148s and over 50 components 70p.

PCB with GEC G424 triac control I/C. 2 SGS transistors. Three 9 watt WW resistors and 12 other components supplied now with G424 data and application sheet £1.00.

PCB with 4 x 0-1 MFD 1000V caps 2 pre-sets, 1 bridge rect., 4 x 1N4007, 9 resistors 70p.

PCB with 2 x 741. 2N4921 and over 40 other components and multiturn 20K pot 70p.

PCB with 8 x BC107 8 x BCY70 4 pre-set pots and over 70 other components 80p.

Special bargain 10 Kilo inclusive of packing parcel of PCBs, resistors, capacitors, etc. etc. and items not listed above £5.50.

Avo in circuit transistor tester type TT169 complete in case with instructions for testing transistors diodes and SCRs £17.50. Excellent condition fully tested.

(Dept B.) 194 A DROVE ROAD, SWINDON, WILTS.

ALL OUR PRICES INCLUDE VAT

28 PIN I/C holder 28p.

30 turret tags 50p.

500 OHM multi-turn PCB MTG pot 20p. 10 for £1.50.

Airflow Developments snail blower 110V 50Hz £4.50.

Citenco 48V motor with right angle drive geared for 4 R.P.M. torque 24 oz-ins. 3/8" round or for 5/32" square shaft £9.50.

Honeywell plastic snap panel MTG push button DP/CO switch, latch or non latch 15p. 10 for £1.25. State type.

Alma push button reed switch ideal for keyboard 30p. 10 for £2.50.

Min. glass reed switches 20mm length 10 for 60p.

Mercury battery 1-35V 1000 MA/H 16mm dia. 16mm high 15p. 10 for £1.20.

LM324N quad op-amp I/C 60p.

LM1303N stereo pre-amp I/C 60p.

SN76110 P.L.L. FM stereo multiplex decoder I/C 75p.

0-2" red LEDs 12p. 10 for £1.00.

0-125" red LED 12p. 10 for £1.00.

4-7V 400MW zener 6p. 10 for 50p.

13V 400MW zener 6p. 10 for 50p.

Min cermet trimmers HOR MTG 220R and 10K 15p. 10 for £1.20. State value.

1/2W carbon resistors, 100 packed in manufacturers cartons. 15R, 39R, 47R, 150R, 560R, 2-K, 22K, 68K, 100K, 50p per carton. State value.

Resistor pack 200 assorted 70p.

Min electrolytic pack approx. 100 assorted values, few types unmarked 75p.

CHROMASONIC electronics

your soundest connection in the world of components

The items shown in this advert are just a small selection taken from our 1979 Catalogue containing everything from Resistors to the latest in Microprocessors. Order your copy today FREE with all orders upon request of S.A.E.

Dept PW1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

TEL: 01 883 3705 01 883 2289

VOLTAGE REGULATORS	DENCO COILS	QUARTZ CRYSTALS	RESISTORS	VEROBOARD	LINEAR IC'S	IC SOCKETS
Positive 78L SERIES 100mA 5v, 6v, 8v, 12v & 15v. All 32p each 78M SERIES 500mA 5v, 6v, 8v, 12v, 15v, 20v & 24v. All 64p 7800 SERIES 1A 5v, 8v, 12v, 15v, 18v & 24v. All 89p Negative 79M SERIES 500mA 5v, 6v, 8v, 12v, 15v, 20v & 24v. All 78p 7900 SERIES 1A 5v, 8v, 12v, 15v, 18v & 24v. All 89p VARIABLES µA723 (DIL) .43 L200 1.95 LM304H 2.55 LM323K 6.66 LM325N 2.77 LM328N 2.77 LM345K 6.51 ZENERS BZY88 400MW Range 8p each BZX61 1.3 WATT Range 15p each	ROD AERIALS FRA1 L & MW (300pf) 1.17 FRA2 L & MW (500pf) 1.17 I.F. TRANSFORMERS 1FT 13 465KHz .87 1FT 15 10.7MHz .87 1FT 16 1.6MHz .97 1FT 17 1.6MHz .97 1FT 18 465KHz 1.14 1FT 18 1.6MHz 1.14 TRANSISTOR RANGE 1T BLUE 2T YELLOW } £1.06 3T RED 4T AND 5T WHITE DUAL PURPOSE RANGE DP1 BLUE DP2 YELLOW DP3 GREEN } 97p DP4 RED DP5 AND DP6 AND DP7 WHITE	100KHz 3.85 1.0MHz 3.45 2.0MHz 3.45 2.097152MHz 3.45 2.5625MHz 3.45 3.27680MHz 3.45 4.194304MHz 3.45 4.433619MHz 1.27 5.0MHz 3.45 8.0MHz 3.45 10.0MHz 3.45 10.7MHz 3.45 TUNING CAPACITORS DILECON TRIMMERS 100pf 1.94 40pf Max 25 300pf 2.29 500pf Max .36 500pf 2.52 C804 5pf, 10pf, 15pf, 25pf 2.23 20pf, 50pf 2.41 60pf, 75pf, 100pf 2.77 TYPE 'O' 365pf 3.97 365pf + 365pf 3.67 '00' 208pf + 176pf 3.67 ELEMENTS AND BITS 1.80 50, 51, and 52 .57 1.80 6/1106.53p 7/1101.86 X25 4.25 1100, 1101, 1102, 1103 .53 CCN 4.25 CCN 4.25	1Watt HI/STAB 5% 270-10M 1Watt HI/STAB 5% 10Q-1M All 2p each 100 + £1.75 PRESETS 0.1 Watt Carbon .07 0.5 Watt Cermet .82 POTENTIOMETERS Log/Lin L/S .31 Log/Lin W/S .72 Dual Log Lin L/S .90 Dual Log Lin W/S 1.28 SLIDERS Single .41 Dual .61 CAPACITORS Polyester Silver Mica Polystyrene Mylar Ceramics All in stock send Electrolytics For catalogue S.A.E. Tantalum Bead AUDIO AMP KITS 75B 7 Watts 3.67 75 x 10 Watts 4.60 3 1/2 DIGIT METER KITS 7106 L.C.D. 26.99 7107 L.E.D. 23.99	Size inches 0.1 c/c/d 2.5 x 1 .12 2.5 x 3.75 .45 2.5 x 5 .52 3.75 x 3.75 .52 3.75 x 5.0 .80 17 x 2.5 1.55 17 x 3.75 2.06 17.9 x 4.7 2.68 Pin insertion tool .98 Spot face cutter .84 Veropins per 100 .42 VERO BOXES 2523E 8.78 1798K 5.09 G RANGE 2672A 5.88 2673G 9.17 2674B 12.49 PLASTIC 2514F 1.99 2516G 2.27 2518H 2.53 2520J 2.87 2522K 3.85 SERIES 2 CASE BOX 2037C 3.83 2088B 5.21 2073K 7.08 RESISTOR NETWORKS 150Q, 270Q, 1K, 4.7K, 10K, 47K, 100K 81p each	741 8 Pin .23 748 8 Pin .38 LM301 .28 LM307 .51 LM308 .75 LM324 .65 LM380 .85 LM381 1.77 LM390 .55 MC1310 1.26 NE555 .30 IBA8 104S .99 TCA940 1.75 TDA2020 3.58 ZN414 .75 TRANSISTORS BC107 .10 BC108 .10 BC109 & C .10 BC147 .08 BC148 .08 BC149 .09 BC157 .09 BC158 .09 BC159 .09 BC182L .12 BC183L .12 BC184L .12 BC212L .12 BC213L .12 BC214L .12 BC327 .12 BF194 .10 BF195 .10 BF196 .18 BF197 .10 BFY50 .23 2N1111 .22 2N2905 .23 2N2925 .10 2N2926G .12 2N3055 .51	

ANTEX SOLDERING IRONS
 1.80 50, 51, and 52 .57
 1.80 6/1106.53p 7/1101.86

ELEMENTS AND BITS
 1.80 50, 51, and 52 .57
 1.80 6/1106.53p 7/1101.86
 X25 4.25 1100, 1101, 1102, 1103 .53
 CCN 4.25
 CCN 4.25

DESOLDERING GUN
 Gun 8.37
 Spare Nozzle .98
 Desolder Braid .63

REELS OF SOLDER
 18 SWG Size 5 .62
 22 SWG Size PC115 .74
 18 SWG Size 12 .29
 ST3 Soldering Iron Stand 1.70

V.A.T. Inclusive prices 15%. Export Customers deduct V.A.T. 3/23.

Postage and Packing 25p. Trade and Export Inquiries most Welcome. Hours 9.00am - 5.00pm.

Now available our ORDER-RING line, just phone your order through with your Access or Barclaycard number and providing the order is received by 3.00pm the components will be despatched the same day (min tel order £5.00).



FANE

STILL TOP VALUE and

LIFETIME GUARANTEE

INTRODUCING THE 'CLASSIC 55' 12" 55 WATT MULTI-PURPOSE BASS - LEAD GUITAR - P.A. - DISCO

A HIGH PERFORMANCE SPEAKER AT A REMARKABLY LOW PRICE

FULL CLASSIC RANGE		
Classic 45 12"	45 Watts	
Classic 55 12"	55 Watts	
Classic 80 12"	80 Watts	
Classic 85 15"	85 Watts	
Classic 150 15"	150 Watts	
Classic 125 18"	125 Watts	
Classic 175 18"	175 Watts	

Impedances 8 ohms or 15 ohms as required.



£19.94

Rec. Retail Price (inc. V.A.T.)

LOOK AT THESE TYPICAL PERFORMANCE FIGURES and it's a BUDGET SPEAKER
 Total distortion at rated output 3%
 Sensitivity 98d.b.
 Frequency range 50-5000Hz

Also Available
 HIGH FREQUENCY HORN UNITS
 SPECIALIST RANGE SPEAKERS
 CRESCENDO 'E' SERIES SPEAKERS

Available from YOUR LOCAL DEALER or if in difficulty post free direct from

BRITAINS LARGEST PRODUCERS OF HIGH POWER CHASSIS SPEAKERS
FANE ACOUSTICS LTD, HICK LANE, BATLEY, YORKS.
 Telephone: (0924) 476431 Telex: 556498 FANE G

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

—WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS—

STEREO PRE-AMPLIFIER POWER AMPLIFIER



MC 1

CPR 1

CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < 0.05% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio is 85dB; slew-rate 3V/uS; T.H.D. 20Hz-20kHz < 0.08% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 x 80 x 20mm. Supply to be ± 15 volts.

MC 1—PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details.

X02 : X03 — ACTIVE CROSSOVERS

X02 — two way, X03 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS


It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically 0.1% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/uS; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 x 80 x 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

PRE-AMPLIFIER KIT

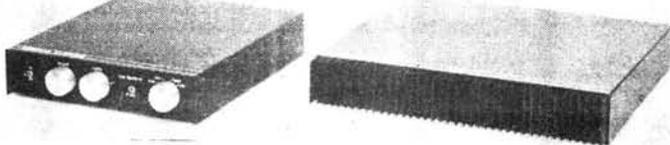This includes all metalwork, pots, knobs etc. to make a complete pre-amp with the CPR 1 (S) module and the MC 1 (S) if required.



ACTIVE CROSSOVERS

X02 £15-16 X03 £23-58

POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-0-35V £19-52

CE 1004 100W/4 ohms 35-0-35V £23-02

CE 1008 100W/8 ohms 45-0-45V £25-96

CE 1704 170W/4 ohms 45-0-45V £31-00

CE 1708 170W/8 ohms 60-0-60V £33-97

TOROIDAL POWER SUPPLIES

CPS1 for 2 x CE 608 or 1 x CE 1004 £16-56

CPS2 for 2 x CE 1004 or 2/4 x £18-80

CE 808 £19-75

CPS3 for 2 x CE 1008 or 1 x £17-12

CE 1704 £24-15

CPS4 for 1 x CE 1008 £17-12

CPS5 for 1 x CE 1708 £24-15

CPS6 for 2 x CE 1704 or 2 x CE £25-53

CE 1708 £25-53

HEAT SINKS

Light duty, 50mm, 2°C/W £1-44

Medium power, 100mm, £2-35

1-4°C/W £3-04

Disco/group, 150mm, 1-1°C/W £19-70

Fan, 80mm, state 120 or 240V £19-70

Fan mounted on two drilled £31-05

100mm heatsinks, 2 x 4°C/W, £1-54

65°C max. with two 170W £31-05

modules. £31-05

THERMAL CUT-OUT, 70°C. £1-54

PRE-AMP KIT

..... £38-07

POWER AMP KIT

..... £35-03

PRE-AMPS:

These are available in two versions—one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPR1 £31-65

CPRIS £40-87

MC1 £21-28

MCIS £33-17

POWER SUPPLY

REG1 £6-90

TR6 £1-97

BRIDGE DRIVER, BDI

Obtain up to 340W using 2 x 170W amps and this module BDI £5-75

CRIMSON ELEKTRIK

1A STAMFORD STREET,

LEICESTER, LE1 6NL

Tel: (0533) 553508

U.K.—please allow up to 21 days for delivery.

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

Distributors:—

BADGER SOUND SERVICES LTD.

46 WOOD STREET,

LYTHAM ST. ANNES,

LANCS FY8 1QG.

"MINIC TELEPRODUKTER

BOX 12035, S-750 12

UPPSALA 12, SWEDEN"

LISTEN TO VHF MARINE or AMATEUR BAND with an SR9 RECEIVER



FROM

The SR-9 represents the finest value-for-money ever offered in the FM monitor receiver market. Giving fully tunable coverage of the 2 metre amateur band from 144-146 MHz, or Marine Band from 156-162 MHz, the SR-9 also incorporates the facility for installing optional crystals which will provide up to ELEVEN fixed channels for the most popular frequencies — mobile calling channel, local repeater channels, distress channel etc.

The SR-9 is completely self contained, even to the loudspeaker, and needs only 12 volts dc (negative earth) at around 200 mA to operate. Mounting hardware is provided for installation.

SR9 Receiver £49.50 (- £1 carr.) — State Amateur or Marine version.

Special Package Deal No.1: SR9 + Mains Power Supply + Loft/Roof Aerial for £69.80 (+ £2 carr.)

Special Package Deal No.2: SR9 + Car Window Clip Aerial for £53.65 (+ £1.50 carr.)

Note: S.P.D. No.1 is only available in Amateur Band Version

Catronics FOR BEST VALUE IN THE FINEST SHORTWAVE RECEIVERS

Low SRX30 as featured in Aug. issue of P.W. Utilises a drift cancelling loop system to give performance plus. 500 KHz — 30 MHz coverage. USB/LSB/AM/CW. 240Vac/12Vdc supply. £179

Trio R300 with dual conversion on higher frequency band (above 18MHz). 170KHz-30MHz coverage. USB/LSB/AM/CW. 120Vac/240Vac/12Vdc supply or internal batteries. £189

Both currently available from stock. Please add £4 for Securicor delivery.

ALL OUR PRICES INCLUDE VAT

EASY TERMS available. Access and Barclaycards welcome

CATRONICS LTD. (Dept. 81) COMMUNICATIONS HOUSE,

20 WALLINGTON SQUARE,

WALLINGTON, SURREY SM6 8RG

Phone: 01-669 6700. Mon.-Fri. 9 a.m.-5.30 p.m. Sats. 1 p.m.

PROGRESSIVE RADIO

ALL ORDERS DESPATCHED BY RETURN POST

SEMICONDUCTORS. 2N5062 (100V 800mA) SCR 18p. 8X504 opto isolator 25p. CA3130 95p. TBA800 50p. C106D 400V 2-5A SCR Cropped Heatsink 20p. TDA1151 25p.

SWITCHES. Min. toggles. SPST 8x5x7mm 52p. DPDT 8x7x7mm 62p. DPDT c/off 12x11x9mm 77p. HEAVY DUTY-DPDT 240VAC 10 Amp 35p. PUSH TYPE, push on 16x6mm 15p, push to break version 17p. 16 pin D.I.L. switch 40p.

SURPLUS BOARDS. No 1 car radio IF. Board 2 transistors and IM382 I.C. I.F.'s etc.. 65p. No.2 with 11 50V 2.5 Amp SCRS, relay and various transistors. Including unijunction type £1.75p. No.3 with 2 BDY61 T03 transistors 45p.

LIGHT DIMMER. Wall mounting 250VAC 800 watts max., has built in photo cell for automatic switch on when dark £4.50p.

RECORDING TAPE. Low noise Mylar, supplied spooled unboxed, 7" 1200' £1.00, 7" 1800' £1.45p, 10 1/2" 3600' £5.00. BLANK CASSETTES C60 10 for £2.75p, C90 10 for £3.85p. TAPE HEAD DEMAGNETISER, 240VAC curved probe £2.65p. LOW COST 1/2" tape splicer £1.95p.

TOOLS. 5 piece precision screwdriver sets, individual handles only £1.05 set.

JUMPER TEST LEAD SETS. 10 pairs of leads with insulated crocs each end 90p.

MURATA 40KHZ TRANSUCERS, RX/TX £3-50 pair.

TELEPHONE PICK UP COIL suction type with lead and plug 62p.

MINIATURE SOLID STATE BUZZERS. 33 x 17 x 15mm, output at 3 feet 70db., 15ma drain, 4 type, 6-9-12 or 24 volts 80p. LOUD 12 volt buzzer 63p.

Cash with order please, official orders welcome from schools etc., please add 30p postage and packing. VAT inclusive. SAE for latest illustrated stock list.

31, CHEAPSIDE, LIVERPOOL L2 2DY

NEW QUALITY KITS FROM DENMARK

Easy-to-build, sure-fire kits with full English instructions Latest IC circuit designs

JK01 AF Amp	£6.75	JK06 27MHz Xtal TX	£9.85
JK02 Mic Amp	£6.75	JK07 Tone Decoder	£9.85
JK03 Sig. Gen	£9.85	JK08 Triac Control	£6.95
JK04 FM Tuner	£9.95	JK09 Birdie Bleeper	£5.95
JK05 27MHz Xtal RX	£10.50	HF61 Beginners radio	£6.50

Prices include VAT Add 50p for post and packing Stocks limited due to world-wide demand

ORDER NOW SAE for FREE Kit Guide

Full money back guarantee Mail order only

TECHNOCENTRE LTD 54 Adcott Road

Middlesbrough TS5 7ES

MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current; 0-150 mA. Resistance: 0-100,000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges, $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE


£6.95



6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less than ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Req. 9V battery. 22-351. REG. PRICE

£79.95

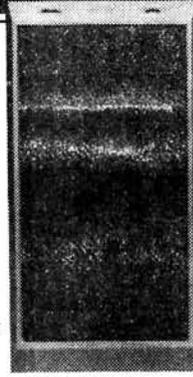


MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300k-301C-1 megaohm. 0-100-1k-101C-100K-3 megaohms. Req. 9V battery. 22-209.

REG. PRICE

£29.95

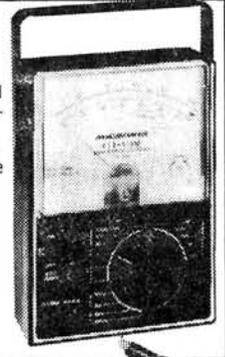


TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

£9.95

REG. PRICE

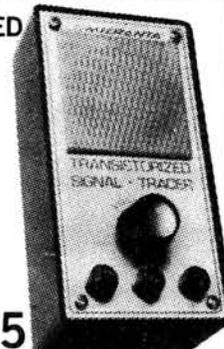

DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE

£19.95



SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.


REG. PRICE **£2.79**

AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE

£1.99

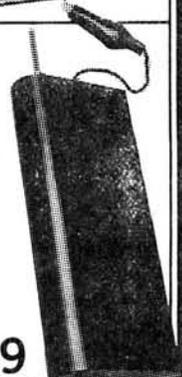

REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout, 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.

REG. PRICE **£229.95**




DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.

REG. PRICE

£9.95

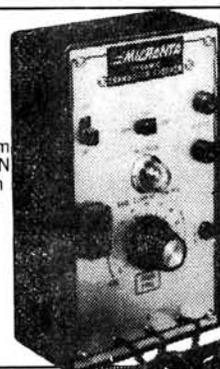

VARIABLE POWER SUPPLY

Power project boards, IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE

£35.95



You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access. Barclaycard and Trustcard welcome. Prices may vary at individual stores.

TRANSFORMERS

30 VOLT RANGE			
Ref	Amps	Price	P & P
112	0.5	2.90	0.90
79	1.0	2.93	1.10
3	2.0	6.35	1.10
20	3.0	6.82	1.31
21	4.0	8.79	1.31
51	5.0	10.86	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.98	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	2.0	32.40	O.A.

Continuous Ratings + VAT 15%

50 VOLT RANGE			
Ref	Amps	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	12.82	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	O.A.
109	12.0	31.79	O.A.

MAINS ISOLATORS (SCREENED)			
Ref	VA	Price	P & P
*07	20	4.84	0.91
149	30	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

CASED AUTO TRANSFORMERS			
VA	Price	P & P	Ref
20	6.55	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	4W
200	12.02	1.67	65W
250	12.55	1.67	69W
500	20.13	1.89	67W
1K	30.67	2.65	84W
1.5K	33.02	O.A.	93W
2K	54.97	O.A.	95W

60 VOLT RANGE			
Ref	Amps	Price	P & P
124	0.5	4.27	1.10
126	1.0	6.50	1.10
127	2.0	8.36	1.31
125	3.0	12.10	1.31
123	4.0	13.77	2.12
40	5.0	17.42	1.89
120	6.0	19.87	2.12
121	8.0	27.92	O.A.
122	10.0	32.51	O.A.

END OF LINE OFFERS

Ref	Description	Price	P & P
30	Isolator 240V:240V 200VA	£4.54	£1.04
62	Isolator 240V:240V 250VA	£5.62	£1.04
M616	0-240V: Screen 1) 13-0-13 1A. 2) 12V 150mA	£2.10	60p

M489	0-240V: 1400V * 150mA, 6.3V * 4A	£5.50	£1.04
M708	6K to 3KΩ matching trans. 5 watt	90p	40p
M679	0-120V * 2:36V 1 6A	£3.00	78p
M865	100V Line to 4Ω 10 watts	£1.90	60p
M973	100V Line to 8Ω 40 watts	£2.90	60p
M1015	Choke 8A * 5mH 150A Surge	£1.50	45p
M1020	0-240V 12-0-12V * 50mA	75p	30p
M1126	120/240V: 9-0-9V * 1A	£1.79	71p
M1130	0-240 4500V * 10mA	£4.86	£1.08
M1165	0-115-240V: 14V 50mA	75p	30p

Metal Oxide Resistors 1/4W 5% TR4 (Electrosil)			
Ref	Value	Price	P & P
390Q/470Q/510Q/560Q/820Q/1K/1K1/1K2/1K6			
1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K			
110K/120K/130K/180K/220K/270K/300K			
£1.50/100 + VAT.			

Antex Soldering Irons 15W & 25W	£4.58	each
Safety Stand	£1.75	P & P 52p each

P.W. Purbeck oscilloscope transformer 250-0-250: 6.3V: 12.9V	£7.51	£1.04
--	-------	-------

12 OR 24V OR 12-0-12V			
Ref	12V	24V	Price
111	0.5	0.25	2.42
213	1.0	0.5	2.90
71	2	1	3.86
18	4	2	4.46
85	0.5	2.5	6.16
70	6	3	6.99
108	8	4	8.16
72	10	5	8.93
116	12	6	9.89
17	16	8	11.79
115	20	10	15.38
187	30	15	19.72
226	60	30	40.41

SPECIAL OFFER			
Ref	Description	Price	P & P
Multimeter 20KΩ B/V			
with combined audio/F. test oscillator at 1 KHz and 465 KHz			
AC/DC to 1000 volts DC current to 500mA resistance to 1KΩ. Size 160x97x40mm			
£8.50 P & P £1.00			
VAT 15%.			

SCREENED MINIATURES			
Ref	mA	Volts	Price
238	200	3-0-3	2.83
212	1A	0-6-0-6	3.14
135	100	9-0-9	2.95
235	330	0-9-0-9	2.19
207	500	0-8-9-0-8-9	3.05
208	1A	0-8-9-0-8-9	3.88
236	200	0-15-0-15	2.19
214	300	0-20-0-20	3.08
221	700	20-12-0-12-20	3.75
206	1A	0-15-20-0-15-20	5.09
203	500	0-15-27-0-15-27	4.39
204	1A	0-15-27-0-15-27	6.64
239	50	12-0-12	2.88

BRIDGE RECTIFIERS			
Ref	Current	Price	P & P
100V	25A*	£2.10	
200V	2A	£0.45	
400V	4A	£0.85	
400V	6A	£1.25	
500V	PM7A6 12A*	£2.85	
P & P 17p/VAT 15%			

AVO TEST METERS			
Ref	Description	Price	P & P
AVO 8 MK5		£91.50	
AVO 71		£38.00	
AVO 73		£50.70	
AVO MM5 minor		£35.95	
Wec Megger		£76.28	
TT169 in circuit transistor tester		£21.53	
EM272 316KΩ - Volts		£59.80	
DA116 Digital		£110.90	
BM / Megger		£53.76	
Clamp Meter to 300A		£54.60	

20,000 ohm/V Multimeter, mirror scale			
Ranges AC DC to 1000V DC current to 250mA			
Resistance to 3 Mohms			
5" x 3 1/2" £14.36 P & P £1.00/VAT 15%			

U4315 Budget Meter. 20KΩ/V Ranges to 1000V, 2.5A AC/DC 500KΩ Res. In steel case			
£15.85. PP £1.15/VAT 15%			

NEW RANGE TRANSFORMERS			
Winding	Ref	Price	P & P
2 windings: 0-36V-48V/36V-0-36V 48V-0-48V 72V or 96V			
1	430	4.88	0.76
1	431	8.12	0.99
2	432	13.35	1.31
3	433	16.17	1.40
4	434	20.65	2.11
5	435	29.30	2.77
6	436	36.69	O.A.
8	437	40.03	O.A.

PANEL METERS			
Ref	Size	Price	P & P
43mm x 43mm			
0 50mA	6-20	6-70	
0 500µA	5-95	6-70	
0 1mA	5-95	6-70	
0 30V	5-95	6-70	
VU ind. Panel 48mm x 45mm		2.60	
VU Ind. Edge 54 x 14mm		2.60	

VU ind. Panel 48mm x 45mm			
VU Ind. Edge 54 x 14mm			
750µA F S D		2.60	
Carriage 76p/VAT 15%			

HIGH QUALITY AMPLIFIER MODULES			
Ref	Description	Price	P & P
10W (AL30)		£3.75	
25W (AL60)		£4.95	
35W (AL80)		£7.79	
125W (AL250)		£18.74	

F.M. Tuner 4 push buttons		£23.60	
Pre-Amps and Power Supplies available			
P & P 40p/VAT 15%			

Split Bobbin Type			
Ref	Description	Price	P & P
0-12-15-20-24-30V			
Ref 009 1 Amp		£2.98	P & P £1.10
Ref 010 2 Amp		£4.62	P & P £1.10

15V RANGE (7.5-0-7.5V) 0-CT-15V			
Ref	Description	Price	P & P
171	500mA	2.30	0.52
172	1A	3.26	0.90
173	2A	3.95	0.90
174	3A	4.13	0.99
175	4A	6.30	1.10

Mini Multimeter: DC1000V AC 1000V/V DC 100mA Res-150K		£7.20	P & P 71p/VAT 15%
---	--	-------	-------------------

Maina Eliminator: fits into 13A Skt 3-6-9-12V multipug outlet		300mA	£4.60 P & P 55p/VAT 15%
---	--	-------	-------------------------

Electronic Construction Kit Home electronic starter. Start simply and progress to a TRF radio or electronic organ. No soldering. All parts included in presentation box. Full instructions.			£8.29. P & P £1.10/VAT 15%
---	--	--	----------------------------

AUTO TRANSFORMERS			
Ref	VA (Watts)	Price	P & P
113	15 0-115-210-240	2.73	0.81
84	75 0-115-210-240	4.41	1.10
4	150 0-115-200-220-240	5.70	1.10
67	500 0-115-200-220-240	12.09	1.91
84	1000 0-115-200-220-240	20.84	2.39
93	1500 0-115-200-220-240	25.81	O.A.
95	2000 0-115-200-220-240	38.31	O.A.
13	3000 0-115-200-220-240	65.13	O.A.
80S	4000 0-115-200-220-240	84.55	O.A.
57S	5000 0-115-200-220-240	88.45	O.A.


Barrie Electronics Ltd.
 3, THE MINORIES, LONDON EC3N 1BJ
 TELEPHONE: 01-488 3316/7/8
 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

STARCHASER 4000

THE NEW FOUR CHANNEL LIGHTING CONTROLLER



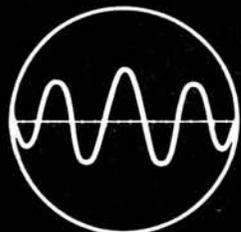- 4 channels 750W each
 - over 1000 different sequence patterns and effects
 - 3 alternative sound triggers
 - A.G.C.
 - simulated strobing
 - zero reference triac firing
 - superb TUAC quality and reliability
- £99.00 inc. VAT.



TUAC

TUAC Ltd., 119 Charlmont Road, SW17.
 Tel: 01-672 3137/9080
 PRICE INCLUDES VAT. P+P FREE (at 1.10.79)

- TUAC MAIN DISTRIBUTORS (Callers Only)**
- Birmingham, George Matthews, 85/87 Hurst Street, (Tel: 622 1941).
 - Canterbury, Socodi, 9 The Friars, (Tel: 60948).
 - Crews, Cookies Disco Centre, 126/128 West Street, (Tel: 4739).
 - Exeter, Electrosure, Fore Street, (Tel: 56687).
 - London, Garland Bros., Deptford Broadway, (Tel: 01-692 4412).
 - London, Session Music, 163 Mitcham Road, Tooting, (Tel: 01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.
 - Luton, Luton Disco Centre, 88 Wellington Street, (Tel: 411733).
 - Manchester, A1 Music, 88 Oxford Street, (Tel: 236 0340).
 - Middlesborough, Salcoglen, 43 Borough Road, (Tel: 242851).
 - Southampton, Memhouse, 82 St. Mary Street, (Tel: 28028).



NEW FOR 1980 MAGNUM 100

MAGNUM 100
inc. PAIR DISCO 80C
SPEAKERS as illustrated
£275.00
normal Retail Price £325.00
Deposit **£55.00** and 18
monthly payments of **£16.00**
Total Credit
Price **£313.00**
Carr £8

ANOTHER DISCO WINNER
FROM THE SPECIALISTS
RSC PROUDLY PRESENT
THE MAGNUM 100
FEATURES GALORE AT A
PRICE YOU CAN AFFORD

**SAVE
£50**

- Full 100 watts output • Mike Input with Separate Treble/ Bass • Full Headphone Monitor Facilities
- Autofade • Master Volume • 11" Turntables with Independent Illuminated Mains Switches • Twin Speaker Sockets • Slave and

Sound to Light Outputs ITEMS SOLD SEPARATELY

RSC SPECIALS

FR1 Speaker Kits
Inc. 8" Bass/Tweeter/
Crossover **£15.95**
Per pair ONLY (Post £1.50)

Speaker Wall Brackets
Support up to 50 lbs. Per pair JUST
£12.95
(Post £1.50)

Eagle Stereo Headphones
Super buy at JUST **£3.95**
(Post 40p)

Kagusa Radio Cassette Recorder
3 Short Wave Bands & MW **£49.95**
(Post £1.50)

MAGNUM 100 SUPER VALUE AT ONLY
Deposit **£45.00** and 18 monthly payments of **£13.10**
(Total Credit Price **£280.80**) (Carr £5)

£225.00

TITAN DISCO 80C Inc. basic model Fane Specialist Range Disco
80 Full range 12" 80 watt chassis speaker fitted linen cone surround for low
Resonance, and large Tweeter cone for extending frequency range to 15
KHz Imp 8 15 ohms. An exceptionally efficient unit

£50.00 each
Special Offer
£90.00 per pair

TITAN GROUP DISCO SPEAKERS



Rating RMS
Imp 8 15 ohms

				R.S.C. S.R.P. Price
T12/50R	12"	50w	£20.20 ..	£16.95
T12/100A	12"	100w	£39.95 ..	£26.95
T15/70	15"	70w	£36.95 ..	£24.95
T15/85	15"	85w	£42.95 ..	£28.95
T15/100	15"	100w	£47.95 ..	£35.95
T18/100	18"	100w	£59.95 ..	£47.95

Special Import Purchase

Exclusive to R.S.C.
AS-1 FOLK ACOUSTIC GUITAR
Just **£17.95** (Carriage £1)

OR £5 DEPOSIT & 8 MONTHLY PAYMENTS OF £2 (TOTAL CREDIT PRICE £21)

RSC Realistic Sound Centres

- OPEN ALL DAY SATURDAY
- BRADFORD** 10 North Parade (Closed Wed.) Tel. 25349
 - BIRMINGHAM** 30/31 Great Western Arcade (Closed Wed.) Tel. 021-236-1279
 - CARLISLE** 8 English Street (Closed Thurs) Tel. 38744
 - COVENTRY** 17 Shelton Square, The Precinct (Closed Thurs.) Tel. 25983
 - DERBY** 97 St. Peter's Street (Closed Wed.) Tel. 41361
 - DEWSBURY** 9/11 Kingsway (Closed Tues.) Tel. 468058
 - DONCASTER** 3 Queensgate, Waterdale Centre (Closed Thurs) Tel. 63069
 - EDINBURGH** 101 Lothian Road (Closed Wed.) Tel. 229 9501
 - GLASGOW** 403 Sauchiehall St (Closed Tues) Tel 041 332 0700

- HULL** 7 Whitefriargate (Closed Thurs.) Tel. 20505
- LEICESTER** 32 High Street (Closed Thurs.) Tel. 56420
- LONDON** 238 Edgware Road, W.2. (Closed Thurs.) Tel. 723 1629
- *LEEDS** 16-18 County (Mecca) Arcade, Briggate (Closed Wed.) Tel. 449609
- *LIVERPOOL** 35 Dawson Way, St. John's Precinct (Closed Wed.) Tel. 708 9380
- *MANCHESTER** 60A Oldham Street (Closed Wed.) Tel. 236 2778
- MIDDLESBROUGH** 103 Linthorpe Road (Closed Wed.) Tel. 247096
- *NEWCASTLE UPON TYNE** 59 Grainger St. (Closed Wed.) Tel. 21469
- NOTTINGHAM** 19/19A Market Street (Closed Thurs.) Tel. 48068
- SHEFFIELD** 13 Exchange Street (Castle Mkt. Blds.) (Closed Thurs.) Tel. 20716

*WOLVERHAMPTON 6 Wulfrun Way (Closed Thurs.) Tel. 26612
*MUSICAL INSTRUMENTS & ACCESSORIES in stock at these branches

ALL PRICES INC. VAT.

Mail Orders and Export Enquiries to:
**DEPT. GC AUDIO HOUSE,
HENCONNER LANE, LEEDS 13.**
Tel: 0532 577631



Barclaycard, Access & Trustcard
Phone orders quoting card number accepted

MAIL ORDERS MUST NOT BE SENT TO SHOPS

BI-PAK SEMICONDUCTORS

TRANSISTORS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	£0.25	BC137	£0.21	BD184	£1.27	BFX88	£0.25	ZTX504	£0.29
AC113	£0.23	BC139	£0.37	BD185	£0.78	BFX90	£0.43	ZTX531	£0.29
AC115	£0.23	BC140	£0.35	BD186	£0.78	BFX90	£0.43	ZTX550	£0.18
AC117	£0.23	BC141	£0.35	BD187	£0.78	BFX91	£0.18	ZN388	£0.41
AC117K	£0.39	BC142	£0.25	BD188	£0.86	BFX92	£0.18	ZN3772	£1.84
AC121	£0.23	BC143	£0.25	BD189	£0.90	BFX95	£0.18	ZN390A	£2.53
AC122	£0.16	BC145	£0.53	BD190	£0.90	BIP19	£0.44	ZN404	£0.23
AC125	£0.21	BC147	£0.08	BD195	£1.04	BIP20	£0.44	ZN424	£0.46
AC126	£0.21	BC148	£0.08	BD196	£1.04	BIP19/20	£0.92	ZN458	£0.46
AC127	£0.21	BC149	£0.08	BD197	£1.04	BIP20	£0.44	ZN458	£0.46
AC128	£0.18	BC150	£0.23	BD198	£1.09	BSX19	£0.21	ZN458	£0.46
AC128K	£0.30	BC151	£0.25	BD199	£1.14	BSX20	£0.21	ZN458	£0.46
AC132	£0.23	BC152	£0.25	BD200	£1.14	BSY25	£0.18	ZN458	£0.46
AC134	£0.23	BC153	£0.29	BD201	£0.92	BSY26	£0.18	ZN458	£0.46
AC137	£0.23	BC154	£0.29	BD202	£0.92	BSY27	£0.18	ZN458	£0.46
AC141	£0.25	BC157	£0.12	BD202	£0.92	BSY28	£0.18	ZN458	£0.46
AC141K	£0.35	BC158	£0.12	BD201/2	£1.96	BSY29	£0.18	ZN458	£0.46
AC142	£0.42	BC159	£0.12	BD202mp	£1.96	BSY38	£0.22	ZN458	£0.46
AC142K	£0.35	BC160	£0.30	BD203	£0.92	BSY39	£0.22	ZN458	£0.46
AC151	£0.23	BC161	£0.44	BD204	£0.92	BSY40	£0.33	ZN458	£0.46
AC153	£0.25	BC167	£0.14	BD203/4	£1.96	BSY41	£0.33	ZN458	£0.46
AC153K	£0.35	BC168	£0.14	BD204mp	£1.96	BSY61	£0.29	ZN458	£0.46
AC154	£0.23	BC169	£0.10	BD205	£0.92	BSY95	£0.15	ZN458	£0.46
AC155	£0.23	BC169C	£0.12	BD206	£0.92	BSY95A	£0.15	ZN458	£0.46
AC156	£0.23	BC170	£0.10	BD207	£0.92	BRY39	£0.52	ZN458	£0.46
AC157	£0.29	BC171	£0.10	BD208	£0.00	BU105	£1.84	ZN458	£0.46
AC161	£0.23	BC172	£0.10	BD209	£0.60	BU201	£1.81	ZN458	£0.46
AC166	£0.23	BC173	£0.10	BD210	£0.54	BU204	£1.81	ZN458	£0.46
AC167	£0.23	BC174	£0.17	BD211	£0.63	BU205	£1.81	ZN458	£0.46
AC168	£0.29	BC175	£0.40	BD212	£0.55	BU208	£2.19	ZN458	£0.46
AC169	£0.23	BC177	£0.18	BD213	£0.63	BU208/2	£2.59	ZN458	£0.46
AC171	£0.21	BC178	£0.18	BD234	£0.63	MJE2955	£1.04	ZN458	£0.46
AC176	£0.21	BC179	£0.18	BD235	£0.63	MUE3440	£0.60	ZN458	£0.46
AC176K	£0.30	BC180	£0.29	BD237	£0.63	MPB113	£0.60	ZN458	£0.46
AC178	£0.29	BC181	£0.10	BD238	£0.63	MPF104	£0.40	ZN458	£0.46
AC179	£0.29	BC182	£1.25	BD239A	£0.58	MPF104	£0.40	ZN458	£0.46
AC180	£0.23	BC182L	£0.10	BD240A	£0.58	MPF104	£0.40	ZN458	£0.46
AC180K	£0.35	BC183	£0.10	BDY11	£2.07	MPSA05	£0.23	ZN458	£0.46
AC181	£0.23	BC183L	£0.10	BDY11	£2.07	MPSA05	£0.23	ZN458	£0.46
AC181K	£0.32	BC184	£0.10	BDY11	£2.07	MPSA05	£0.23	ZN458	£0.46
AC187	£0.21	BC184L	£0.10	BDY20	£1.04	MPSA56	£0.23	ZN458	£0.46
AC187K	£0.32	BC186	£0.25	BDY27	£1.04	MPSA56	£0.23	ZN458	£0.46
AC188	£0.21	BC187	£0.25	BF115	£0.86	ND120	£0.21	ZN458	£0.46
AC188K	£0.32	BC188	£0.25	BF116	£0.86	ND120	£0.21	ZN458	£0.46
AC197	£0.40	BC208	£0.13	BF118	£0.86	OC22	£1.73	ZN458	£0.46
AC198	£0.40	BC209	£0.14	BF119	£0.86	OC23	£1.73	ZN458	£0.46
AC199	£0.40	BC212	£0.10	BF121	£0.86	OC24	£1.55	ZN458	£0.46
AC200	£0.40	BC213	£0.10	BF123	£0.69	OC25	£1.15	ZN458	£0.46
AC201	£0.40	BC214	£0.10	BF125	£0.58	OC26	£1.15	ZN458	£0.46
AC202	£0.40	BC215	£0.10	BF126	£0.58	OC27	£1.15	ZN458	£0.46
AC203	£0.40	BC216	£0.10	BF127	£0.58	OC28	£1.15	ZN458	£0.46
AC204	£0.40	BC217	£0.10	BF128	£0.58	OC29	£1.09	ZN458	£0.46
AC205	£0.40	BC218	£0.10	BF129	£0.58	OC30	£1.04	ZN458	£0.46
AC206	£0.40	BC219	£0.10	BF130	£0.58	OC31	£1.04	ZN458	£0.46
AC207	£0.40	BC220	£0.10	BF131	£0.58	OC32	£1.04	ZN458	£0.46
AC208	£0.40	BC221	£0.10	BF132	£0.58	OC33	£1.04	ZN458	£0.46
AC209	£0.40	BC222	£0.10	BF133	£0.58	OC34	£1.04	ZN458	£0.46
AC210	£0.40	BC223	£0.10	BF134	£0.58	OC35	£1.04	ZN458	£0.46
AC211	£0.40	BC224	£0.10	BF135	£0.58	OC36	£1.04	ZN458	£0.46
AC212	£0.40	BC225	£0.10	BF136	£0.58	OC37	£1.04	ZN458	£0.46
AC213	£0.40	BC226	£0.41	BF137	£0.58	OC38	£1.04	ZN458	£0.46
AC214	£0.40	BC227	£0.41	BF138	£0.58	OC39	£1.04	ZN458	£0.46
AD130	£0.31	BC238	£0.18	BF139	£0.58	OC40	£1.04	ZN458	£0.46
AD140	£0.69	BC251	£0.17	BF157	£0.32	OC41	£0.23	ZN458	£0.46
AD142	£0.98	BC251A	£0.18	BF159	£0.32	OC42	£0.25	ZN458	£0.46
AD143	£0.86	BC301	£0.32	BF160	£0.35	OC71	£0.17	ZN458	£0.46
AD144	£0.86	BC302	£0.33	BF162	£0.35	OC72	£0.28	ZN458	£0.46
AD161	£0.40	BC303	£0.33	BF163	£0.35	OC73	£0.28	ZN458	£0.46
AD162	£0.40	BC304	£0.44	BF164	£0.55	OC75	£0.35	ZN458	£0.46
AD161/2	£0.81	BC327	£0.18	BF165	£0.55	OC76	£0.40	ZN458	£0.46
AF124	£0.35	BC328	£0.17	BF167	£0.28	OC77	£0.58	ZN458	£0.46
AF125	£0.35	BC337	£0.17	BF173	£0.23	OC81	£0.25	ZN458	£0.46
AF126	£0.35	BC338	£0.17	BF176	£0.44	OC81DD	£0.28	ZN458	£0.46
AF127	£0.37	BC340	£0.35	BF177	£0.44	OC82	£0.25	ZN458	£0.46
AF139	£0.40	BC441	£0.35	BF178	£0.30	OC82D	£0.35	ZN458	£0.46
AF178	£0.69	BC460	£0.44	BF179	£0.35	OC83	£0.30	ZN458	£0.46
AF179	£0.69	BC461	£0.44	BF180	£0.35	OC84	£0.44	ZN458	£0.46
AF180	£0.69	BC477	£0.23	BF181	£0.35	OC139	£0.92	ZN458	£0.46
AF181	£0.69	BC478	£0.23	BF182	£0.35	OC145	£0.25	ZN458	£0.46
AF186	£0.58	BC479	£0.23	BF183	£0.35	OC169	£0.40	ZN458	£0.46
AF239	£0.44	BC547	£0.12	BF184	£0.23	OC170	£0.40	ZN458	£0.46
AL102	£1.38	BC548	£0.12	BF185	£0.23	OC171	£0.40	ZN458	£0.46
AL103	£1.38	BC549	£0.12	BF186	£0.30	OC200	£0.44	ZN458	£0.46
ASX16	£0.35	BC550	£0.16	BF187	£0.30	OC201	£1.09	ZN458	£0.46
ASX27	£0.46	BC551	£0.16	BF188	£0.30	OC202	£1.09	ZN458	£0.46
ASV28	£0.44	BC557	£0.15	BF194	£0.12	OC203	£0.98	ZN458	£0.46
ASV29	£0.44	BC558	£0.14	BF195	£0.12	OC204	£1.04	ZN458	£0.46
ASV50	£0.35	BCV30	£0.63	BF196	£0.12	OC205	£1.32	ZN458	£0.46
ASV51	£0.35	BCV31	£0.63	BF197	£0.14	TC44	£0.33	ZN458	£0.46
ASV52	£0.35	BCV32	£0.63	BF198	£0.14	TC45	£0.21	ZN458	£0.46
ASV54	£0.35	BCV33	£0.63	BF199	£0.16	TP29A	£0.46	ZN458	£0.46
ASV55	£0.35	BCV34	£0.69	BF200	£0.35	TP29B	£0.48	ZN458	£0.46
ASV56	£0.35	BCV70	£0.17	BF202	£1.04	TP29C	£0.51	ZN458	£0.46
ASV57	£0.35	BCV71	£0.17	BF222	£1.04	TP30A	£0.46	ZN458	£0.46
ASV58	£0.35	BCV72	£0.17	BF224	£1.04	TP30B	£0.48	ZN458	£0.46
AU103	£1.38	BC213	£0.69	BF240	£0.20	TP30C	£0.51	ZN458	£0.46
AU104	£1.61	BC211	£0.69	BF241	£0.20	TP31A	£0.46	ZN458	£0.46
AU110	£1.61	BC212	£0.69	BF244	£0.35	TP31B	£0.48	ZN458	£0.46
AU113	£1.61	BD115	£0.58	BF257	£0.29	TP31C	£0.51	ZN458	£0.46
BC107	£0.09	BD116	£0.92	BF258	£0.29	TP32A	£0.46	ZN458	£0.46
BC17A	£0.09	BD121	£0.75	BF259	£0.40	TP32B	£0.48	ZN458	£0.46
BC107B	£0.09	BD122	£0.75	BF262	£0.69	TP32C	£0.51	ZN458	£0.46
BC107C	£0.12	BD124	£0.81	BF263	£0.69	TP41A	£0.51	ZN458	£0.46
BC108	£0.09	BD131	£0.40	BF270	£0.41	TP41B	£0.53	ZN458	£0.46
BC108A	£0.09	BD132	£0.40	BF271	£0.36	TP41C	£0.55	ZN458	£0.46
BC108B	£0.10	BD133	£0.40	BF272	£0.44	TP42A	£0.51	ZN458	£0.46
BC108C	£0.10	BD134	£0.40	BF273	£0.41	TP42B	£0.53	ZN458	£0.46
BC109	£0.09	BD137	£0.46	BF274	£0.44	TP42C	£0.55	ZN458	£0.46
BC109A	£0.09	BD135	£0.44	BF324	£0.40	TP2955	£0.69	ZN458	£0.46
BC109B	£0.10	BD136	£0.40	BF336	£0.35	TP3055	£0.53	ZN458	£0.46
BC109C	£0.12	BD137	£0.40	BF337	£0.35	TS43	£0.25	ZN458	£0.46
BC113	£0.18	BD138	£0.41	BF338	£0.35	TS43	£0.25	ZN458	£0.46
BC114	£0.18	BD139	£0.41	BF457	£0.43	TS46	£0.23	ZN458	£0.46
BC115	£0.22	BD140	£0.41	BF458	£0.43	ZTX107	£0.12	ZN458	£0.46
BC116	£0.22	BD139/140mp	£0.92	BF459	£0.44	ZTX108	£0.12	ZN458	£0.46
BC116A	£0.22	BD155	£0.92	BF596	£0.32	ZTX109	£0.12	ZN458	£0.46
BC117	£0.23	BD155	£0.92	BF597	£0.28	ZTX300	£0.14	ZN458	£0.46
BC118	£0.23	BD175	£0.69	BF598	£0.29	ZTX301	£0.14	ZN458	£0.46
BC119	£0.29	BD176	£0.69	BF599	£0.32	ZTX302	£0.18	ZN458	£0.46
BC120	£0.46	BD177	£0.78	BF599	£0.32	ZTX303	£0.18	ZN458	£0.46
BC125	£0.20	BD178	£0.78	BFX29	£0.25	ZTX304	£0.23	ZN458	£0.46
BC126	£0.25	BD179	£0.86	BFX30	£0.35	ZTX330	£0.17	Z	

Send your orders to:

DEPT. PW1, PO BOX 6, WARE, HERTS. Tel: 0920-3182

Visit our NEW shop: 3 BALDOCK ST., WARE, HERTS. Telex: 817861

BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	£0-50
BP14	2nd Book Transistor Equivs. & Subs	£1-10
BP24	52 Projects Using IC741 (or Equiv.)	£0-95
BP26	Radio Antenna Book Long Distance Reception & Transmission	£0-85
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	£0-68
BP32	Build Metal & Treasure Locators	£1-00
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	£1-25
BP36	50 Ccts use Germ/S11/Zener Diodes	£0-75
BP39	50 Field Effect Trans Projects	£1-25
BP40	Digital IC Equiv. & Pin Connection	£2-50
BP41	Linear IC Equiv. & Pin Connection	£0-75
BP42	50 Simple LED Circuits	£2-75
BP43	How to make Walkie-Talkies	£1-25
BP45	Projects on Opto-electronics	£1-25
BP46	Radio Circuits Using IC's	£1-35
BP47	Mobile Discotheque Handbook	£1-35
BP48	Electronics Projects for Beginners	£1-35
BP49	Popular Electronic Projects	£1-45
BP50	IC LM3900 Projects	£1-35
BP55	Radio Stations Guide	£1-45
BP160	Coil Design & Construction Manual	£0-75
BP202	Handbook of Integrated Circuits Equivalents & Substitutes	£1-00
BP205	1st Book Hi-Fi Speaker Enclosures	£0-75
BP213	Circuits for Model Railways	£1-00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	£0-85
BP217	Solid State Power Supply Handbook	£0-85
BP221	28 Tested Transistor Projects	£1-25
BP222	Short-wave Receivers for Beginners	£0-95
BP223	50 Projects using IC CA3130	£0-95
BP224	50 CMOS IC Projects	£0-95
BP225	A Practical Intro to Digital IC's	£1-15
BP225	Build Advanced Short-wave Receivers	£1-20
BP227	Beginners Guide to Building Electronic Projects	£1-25

NEWNES BOOKS

216	Transistors 3rd Ed.	£1-00
217	Integrated Circuits	£1-00
218	Radio & Television	£1-25
219	Electronics	£1-15
220	Colour TV 2nd Ed.	£1-15
221	Hi-Fi	£1-15
222	20 Solid State Proj. for Car	£1-95
223	20 Solid State Proj. for Home	£1-95
224	110 Int. Circ. Proj. for Home	£2-95
225	110 Thyristor Projects	£2-50
226	Operational Amp. Proj. for Home	£2-50
228	Electricity	£1-80
229	Beginners Guide to Electronics	£2-25
230	Beginners Guide to Television	£2-25
231	Beginners Guide to Transistors	£2-25
232	Beginners Guide to Electric Wiring	£2-25
233	Beginners Guide to Radio	£2-75
234	Guide to Colour TV	£2-25
235	Electronic Diagrams	£1-80
236	Electronic Components	£1-80
237	Printed Circuit Assembly	£1-80
238	Transistor Pocket Book	£3-90
239	50 Photoelectric Circuits	£1-80
240	Semiconductor Handbook Part 1	£5-25
241	Semiconductor Handbook Part 2	£2-28
242	Electronics Pocket Book	£3-90
244	Beginners Guide to Integrated Circuits	£2-75
209	BI-PAK TTL Data Book	50p
	BI-PAK CMOS Data Book	50p

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0-18
DPDT standard slide	1974	£0-17
Toggle switch SPST 12 amp 250V ac	1975	£0-38
Toggle switch DPDT 1 amp 250V ac	1976	£0-48
Rotary on-off mains switch	1977	£0-58
Push switch—Push to make	1978	£0-16
Push switch—Push to break	1979	£0-21

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST—moulded in high insulation material available in a choice of colours ideal for small apparatus	RED BLACK WHITE BLUE YELLOW LUMINOUS	1980 1981 1982 1983 1984 1985	£0-35 £0-35 £0-35 £0-35 £0-35 £0-35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0-81
Miniature SPST toggle 2 amp 250V ac	1959	£0-86
Miniature DPDT toggle 2 amp 250V ac	1960	£0-91
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1-07
Push-button SPST 2 amp 250V ac	1962	£1-04
Push-button SPST 2 amp 250V ac	1963	£1-09
Push-button DPDT 2 amp 250V ac	1964	£1-34

MIDGET WAFER SWITCHES	No.	Price
Single bank wafer type—suitable for switching at 250V ac 100mA or 150V dc non-reactive loads make-before-break contacts. These switches have a spindle 0.25 in dia. and 30 indexing.		
Description	No.	Price
1 pole	1965	£0-55
2 pole	1966	£0-55
3 pole	1967	£0-55
4 pole	1968	£0-55

MICRO SWITCHES	No.	Price
Plastic button gives simple 1 pole change over action		£0-29
Rating 10 amp 250V ac	1970	

NEW INCREASED RANGE—ALL 1ST QUALITY

LEDs (diffused)	O/No.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (-125)	RED	£0-12	
1502	MIL3232 (TIL211)	3mm (-125)	GREEN	£0-22	
1503	MIL3301 (OPL212A)	3mm (-125)	YELLOW	£0-22	
1504	ARL4850 (FLV117)	5mm (-2)	RED	£0-12	
1505	MIL5251 (TIL222)	5mm (-2)	GREEN	£0-22	
1506	MIL5351 (MV5353)	5mm (-2)	YELLOW	£0-22	
1509	FLV111	5mm (-2)	CLEAR (Ill. Red)	£0-13	

SUPER 'HI BRITE' TYPE	O/No.	Type	Size	Colour	Price
1521	MIL32	3mm (-125)	RED	£0-12	
1522	MIL52	5mm (-2)	RED	£0-12	
1514	ORP12	Light dependent resistor		£0-63	
1520	OC71	Photo transistor		£0-40	

LED CLIPS	O/No.	Type	Price
1508/125	pack of 5	125 clips	£0-17
1508/2	pack of 5	2 clips	£0-21

DISPLAYS	O/No.	Type	Price
DL703	7 segment D P left (30" height)	Common Anode	
RED Single Digit	O/NO. 1523		£0-85
DL707	7 segment D P left (30" height)	Common Anode	
RED Single Digit	O/NO. 1510		£0-92
DL527	7 segment D P left (50" height)	Common Anode	
RED Two-Digit Reflector	O/NO. 1524		£2-08
DL727	7 segment D P right (5"10" height)	Common Anode	
RED Two-Digit Light Pipe	O/NO. 1512		£2-07
DL747	7 segment D P left (630" height)	Common Anode	
RED Single Digit Light Pipe	O/NO. 1511		£1-73

OPTO-ISOLATORS	O/No.	Type	Price
CIL74	Single Channel 6 pin DIP standard type—optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor	O/NO. 1497	£0-81
CILD74	Multi-Channel 8 pin DIP Two Isolated Channels	O/NO. 1498	£1-22
CILQ74	Multi-Channel 16 pin DIP Four Isolated Channels	O/NO. 1499	£2-69

MELL II (TIL81) NPN LIGHT DETECTOR	O/No.	Type	Price
Silicon Photo Darlingon Amplifier—VC80, 30V VECO 10V 1c 100mA Prot 300mW IL Min. 0.5 Type 2mA 1D 100mA mA	O/NO. 1495		£0-29

TEACH-IN 80

We can offer a stock all the parts required (except battery and euroboard) for this project as listed in part 1 of the October issue of Everyday Electronics.

KIT 1 TUTOR DECK

Comprising of all parts except 2 PP3 Batteries

ONLY £14.00 INC. P & P AND VAT.

KIT 2

Additional components for parts 1 to 6.

ONLY £1.75 INC. P & P AND VAT.

FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0-18
1in. x 1/2in. chassis mounting	507	£0-14
1 1/2in. car inline type	508	£0-18
Panel mounting 20mm	509	£0-23
Panel mounting 1 1/2in.	510	£0-37

QUICK BLOW 20mm	Type	No.	Type	No.	Price	
150mA	611	7p 1A	615	6p 3A	619	6p
250mA	612	6p 1.5A	616	7p 4A	620	10p
550mA	613	6p 2A	617	6p 5A	621	6p
800mA	614	6p 2.5A	618	7p		

ANTI-SURGE 20mm	Type	No.	Type	No.	Price
100mA	622	1A	625	2.5A	628
500mA	623	2A	626	3.15A	629
250mA	624	1/6A	627	5A	630

QUICK-BLOW 1 1/2in.	Type	No.	Type	No.	Price
250mA	631	500mA	632	800mA	634

1A	2.5A	3A	4A	5A	6A
635	638	639	641	642	

NUTS AND BOLTS

BA BOLTS—packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50.	Type	No.	Price
1in. OBA	839	£1-38	
1in. OBA	840	£0-88	
1in. 2BA	842	£0-75	
1in. 2BA	843	£0-52	
1in. 2BA	844	£0-60	
1in. 4BA	845	£0-51	

BA NUTS—packs of cadmium plated full nuts in multiples of 50.	Type	No.	Price
OBA	855	£0-83	
2BA	856	£0-55	

BA WASHERS—flat cadmium plated plain stamped washers supplied in multiples of 50.	Type	No.	Price
OBA	859	£0-18	
OBA	860	£0-14	

SOLDER TAGS—Hot tinned supplied in multiples of 50.	Type	No.	Price
OBA	851	£0-46	
OBA	852	£0-32	

AUDIO LEADS

No.	Type	Price
107	FM indoor Ribbon Aerial	£0-69
113	3.5mm Jack plug to 3.5mm Jack plug length 1.5m	£0-86
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m	£0-98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4 length 1.5m	£0-98
116	Car aerial extension screened insulated lead. Fitted plug and socket	£1-44
117	AC mains connecting lead for cassette recorders and radios 2 metres	£0-78
118	5 pin DIN phono plug to stereo headphone. Jack socket	£1-21
119	2 + 2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£1-04
120	Car stereo connector. Variable geometry plug to fit most car cassettes. 8-track cartridge and combination units. Supplied with inflated fuse power lead and instructions	£0-69
123	6.6mm Coiled Guitar Lead Mono Jack plug to Mono Jack plug Black	£1-72
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0-85
125	5 pin DIN plug to 5 pin DIN plug. Length 1.5m	£0-85
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0-85
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1-49
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0-92
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1-21
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0-78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5 Length 1.5m	£0-95
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1-13
133	5 pin DIN plug to 2 Phono plugs. Connected pins 3 & 5. Length 1.5m	£0-86
134	5 pin DIN plug to 2 Phono sockets. Connected pins 3 & 5. Length 23cm	£0-78
135	5 pin DIN socket to 2 Phono plugs. Connected pins 3 & 5. Length 23cm	£0-78
136	Coiled stereo headphone extension lead. Black. length 6m	£2-01
178	AC mains lead for calculators, etc	£0-52

TRANSFORMERS

MINIATURE MAINS Primary 240V	No.	Secondary	Price
	2021	6V-0-6V 100mA	£1-04
	2022	9V-0-9V 100mA	£1-04
	2023	12V-0-12V 100mA	£1-29

MINIATURE MAINS Primary 240V	No.	Type	Price
with two independent secondary windings			
	2024	MT280-0-6V 0-6V RMS	£1-84
	2025	MT150-0-12V 0-12V RMS	£1-84

1 AMP MAINS Primary 240V	No.	Secondary	Price
	2026	6V-0-6V 1 amp	£2-88 P & P 45p
	2027	9V-0-9V 1 amp	£2-30 P & P 45p
	2028	12V-0-12V 1 amp	£2-00 P & P 55p
	2029	15V-0-15V 1 amp	£3-16 P & P 66p
	2030	30V-0-30V 1 amp	£3-97 P & P 86p

STANDARD MAINS Primary 240V	No.	Secondary	Price
Multi-tapped secondary mains transformers available in 1/2 amp, 1 amp and 2 amp current rating. Secondary taps are 0-19.25-33-40-50V. Voltages available by use of taps. 4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 25-0-25V			
	2031	1 amp	£3-91 P & P 85p
	2032	1 amp	£5-06 P & P 85p
	2033	2 amp	£6-27 P & P 81
	2035	240V Primary 0-55V + 2A Secondary	£7-30 P & P 81

SPECIAL OFFER

2042 240V Primary 0-20V + 2A Secondary. By removing 5 turns for each volt from the secondary winding any voltage up to 20V + 2A is easily obtainable ideal for the experimenter. £1-50 P & P 86p

CASES AND BOXES

INSTRUMENT CASES	In two sections vinyl covered top and sides, aluminium bottom, front and back.	No.	Length	Width	Height	Price
		155	5in	5		



Service

EDITOR
Geoffrey C. Arnold

ASSISTANT EDITOR
Dick Ganderton C. Eng., MIERE

ART EDITOR
Peter Metalli

TECHNICAL EDITOR
Malcolm Cummings G8KPN

NEWS & PRODUCTION EDITOR
Alan Martin

TECHNICAL SUB-EDITOR
Joe Bishop

TECHNICAL ARTIST
Rob Mackie

ASSISTANT ART EDITOR
Keith Woodruff

SECRETARIAL
Sylvia Barrett
Sharron Breeze

EDITORIAL OFFICES
Westover House,
West Quay Road,
POOLE, Dorset BH15 1JG
Telephone: Poole 71191

ADVERTISEMENT MANAGER
Telephone: 01-261 6636
Dennis Brough

CLASSIFIED ADVERTISEMENTS
Telephone: 01-261 5762
Colin R. Brown

MAKE UP & COPY DEPARTMENT
Telephone: 01-261 6570
Dave Kerindi

ADVERTISEMENT OFFICES
King's Reach Tower, Stamford St.,
London, SE1 9LS
TELEX: 915748 MAGDIV-G

AS I've mentioned on this page a couple of times in recent months, we've been having considerable trouble with delays to publication. These delays have stemmed from a variety of causes, and as fast as we've got over one difficulty, another one has arisen to plague us. We know it's been a frustrating time for you, and it's been frustrating for us too, not least because there was no practical way of keeping you informed on the situation.

I hope that steps recently taken to overcome the problems will prove to have been successful, and that you are able to read this on the scheduled publication date, which is the first Friday in December. Thank you for bearing with us so patiently.

A further apology is due to readers who have written to us and have sometimes had to wait a long time for a reply. This has been due to editorial staff shortages, which are hopefully now a thing of the past.

Unfortunately, we do have to impose certain rules on readers' queries, otherwise we'd spend most of the day answering them, and the magazine just wouldn't get published. We ask you to note the following:

1. We cannot deal with technical queries by telephone. Please put your problems in a letter, and enclose a stamped addressed envelope or, for overseas readers, an International Reply Coupon (three IRCs for an Airmail reply).
 2. We cannot provide information or advice on service or spares for commercially-made items of radio, TV, etc.
 3. We cannot provide information on modifications or adaptations of our published projects.
 4. We will try to provide advice on problems related to projects published in *Practical Wireless*, including sources of components for those projects. To allow us to give an efficient service on such queries, I regret that we will in future have to limit them to projects published within the previous three years.
- Details of corrections or any additional information on projects are published in the first available issue, in our "Kindly Note" section or as a "Follow-up", and are listed in the annual indexes. To save time and postage, you are advised to look there first, whenever possible.

Finally, on a somewhat more positive note, I would like to thank all those readers who took the trouble to complete and return our recent questionnaire card. Broadly speaking, you seem to like the magazine the way it is, but we plan to make some minor changes over the next few months as a result of your suggestions. And we have one or two ideas of our own which we hope will prove to be of interest.

* * * *

May I take this opportunity to wish all our readers a very happy Christmas and a healthy and prosperous 1980, on behalf of all the staff on *PW*.



J. Brian Dance, M.Sc.—Contributor to *PW* since 1959

Brian's interest in electronics started way back in the post-war years whilst working for Chemistry degrees at Birmingham. Except for a year in Harwell's "Zeta" group, he has been employed as a lecturer and has worked on neutron spectroscopy and on the thermoluminescence of meteorites at universities. He lectures at North Worcestershire College, Bromsgrove.

Brian is the author of 7 books and about 500 other technical publications.

He is single and suggests this is the reason he can find time for so much writing. He is especially interested in the latest i.c.s and in space developments, but finds some relaxation in playing tennis.

He feels the major attraction of authorship is the wide variety of topics about which one learns (unlike research where a problem can take many years), but feels it is a pity he does not meet more of his readers.

Surround-Sound Test

The first experimental transmissions of an improved stereo-compatible system of "surround-sound" broadcasting developed by IBA engineers have been made on the Independent Local Radio station "Radio Victory" at Portsmouth.

On Sunday, 23 September 1979 a two-hour concert recorded by IBA and Radio Victory engineers at Chichester Cathedral last July was broadcast in surround-sound on Radio Victory's v.h.f./f.m. service on 95.0MHz.

The surround-sound system uses a 3-channel matrix transmission system that has been developed at the IBA engineering centre at Crawley Court, Winchester, to improve stereo-compatibility beyond that found possible with "2-channel" and "2½-channel" systems.

These experiments are part of an IBA investigation into surround-sound techniques with particular reference to the "ambisonics" techniques of the National Research Development Corporation.

Continuing IBA work has underlined the advantages of a full "3-channel" system using a new IBA matrix, particularly in respect of the excellent compatibility for listeners using conventional mono or stereo equipment. The penalties imposed by such a system may be a slight reduction of coverage area and non-compatibility with the earlier "surround-sound" systems.

IBA engineers stress that these "3-channel" experiments are not yet at a stage where it is possible to recommend a "surround-sound standard" for national or international use. It is, however, felt that any such standard, if it is to be worthwhile, must provide the highest achievable technical quality for all listeners and be shown to offer a significant improvement over the existing high-quality v.h.f./f.m. stereo system currently used on all ILR services.

It is anticipated that further experimental transmissions will be made during the next few months and will be announced locally.

To assist in this work the IBA has equipped two vehicles as a special "surround-sound" mobile recording unit, believed to be the most technically-advanced "surround-sound" unit yet built.

IBA, 70 Brompton Road, London SW3 1EY. Tel: 01-584 7011.

Sanken in the UK

Following a fact finding mission to the UK and a study of the potential market for their products, Sanken Electric Co Ltd. of Tokyo have chosen FieldTech Ltd. of London Airport to be their principal distributors in the UK.

FieldTech will now be marketing Sanken's comprehensive range of power amplifiers, servo amplifiers and voltage regulator modules; power transistors, diodes, rectifiers, varistors, etc. Sanken also manufacture a competitive range of indicators and round or rectangular l.e.d.s.

Further details from: *FieldTech Ltd., Heathrow Airport-London, Hounslow, Middx. TW6 3AF. Tel: 01-759 2811.*

New Catalogues

TK Electronics, the electronic component and kit supplier have their latest catalogue ready for distribution. The catalogue offers many devices at very competitive prices and a digital thermometer that is claimed to be probably the lowest priced on the market. The catalogue is available free on receipt of a 9in x 6in s.a.e. *TK Electronics, 106 Studley Grange Road, London W7 2LX. Tel: 01-579 9794.*

Bernard Babani (Publishing) Ltd. inform me of the availability of their latest catalogue of Radio and Electronics books which includes many titles that will be produced early in 1980.

To obtain your free copy of this catalogue, apply enclosing an s.a.e. and a copy will be sent by return. *Bernard Babani (Publishing) Ltd., The Grampians, Shepherds Bush Road, London W6 7NF. Tel: 01-603 2581/7296.*

South West Aerial Systems catalogue and price list is now available. One aspect of the service the company provides, is that of a customer consultancy and system planning, or in the case of reception problems, the company will assist in resolving it. The catalogue costs 20p, and is available from: *South West Aerial Systems, 10 Old Boundary Road, Shaftesbury, North Dorset. Tel: (0747) 4370.*

Verospeed's latest catalogue is now available. This free, 84-page catalogue, is available on application to: *Verospeed, Barton Park Industrial Estate, Eastleigh, Hants. Tel: (0703) 618525.*

Doram returns

One of the early leaders in the home electronics market, Doram Electronics Ltd. is shortly to be relaunched under new ownership. Doram was formed by the Electrocomponents Group in 1974 to distribute the products of its subsidiary RS Components, by mail order, to electronics enthusiasts.

The new owners, the de Boer organisation, based in Eindhoven, centres around a shop and mail order business and was established over six years ago by Mr Ruud de Boer. The acquisition of Doram will enable the Dutch group to expand in the fast growing UK home electronics market. The product range will include both kits and components and will be based on the current Dutch catalogue, rather than any lists or catalogues previously issued by Doram.

Further details from: *Doram Electronics Ltd., Fitzroy House, Market Place, Swaffham, Norfolk PE37 7QH. Tel: (0760) 21627.*

Pointing the Right Way

The RSGB have reprinted a second edition of their *Great Circle DX Map*.

This colourful wall map, measuring 760 x 620mm, shows the true bearing from the UK of countries throughout the world. It is therefore invaluable for radio enthusiasts with directional antennas. Amateur radio prefixes are included, and the map is plastic laminated for extra durability.

The UK price is £1.50 through normal outlets, or £1.99 direct from the RSGB, which includes p&p.

RSGB, 35 Doughty Street, London WC1N 2AE. Tel: 01-837 8688.

Meetings

The East London RSGB Group have arranged the following meetings at *Wanstead House, 21 The Green, Wanstead, London E11*. All meetings commence at 3pm on 3rd Sunday of the month.

December 16—Annual business meeting and bring-and-buy sale.

January 20, 1980—Ken Smith G3JIX, will talk about Radio Astronomy, Ken has a great knowledge of radio and astronomy and the lecture should be fascinating.


Further details from: *Hon Sec, Rod Holmes G3PKQ. Tel: 01-558 2928.*

Model Radio Control

PW

Part 2

THE PW FM-80 SYSTEM

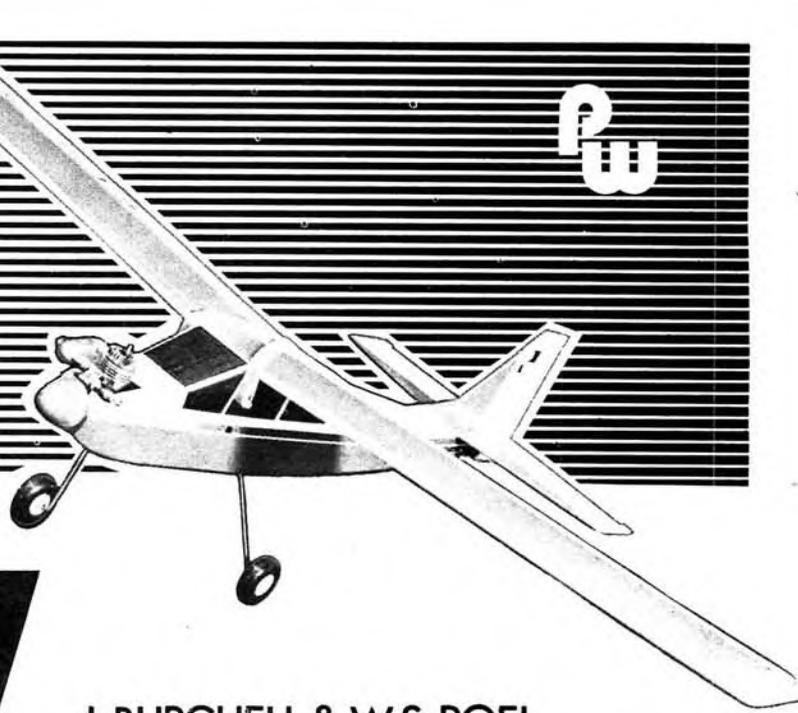

J. BURCHELL & W.S. POEL

The receiver described in the first article is for a 5-channel control system, with four proportional channels, and one switched function channel. For the majority of models, this is sufficient, and the advanced modeller requiring more channels would usually be trying to control some very exotic model and in most cases probably has little interest in building the radio equipment as well as the model.

Encoder

To encode the 5-channel system, it was necessary to choose an approach that would be reliably repeatable, with as few setting up functions as possible. The circuit of Figure 2 is such a system, using common c.m.o.s. since the high impedance presented by c.m.o.s. enables the values of the timing RC constants to be accurately predetermined, as long as reasonably tightly toleranced components are used. The operation is quite easy to understand.

The master clock squarewave, simply derived from a c.m.o.s. two-inverter oscillator (IC2, R9, 10 and C5) could be used to drive a 4017 i.c. to sequentially select the appropriate timing resistors in conjunction with a common timing capacitor, but this type of selection circuit involves the use of isolating diodes, and some experiments revealed that the use of diodes in the near vicinity of the transmitted

r.f. field was a source of potential nuisance. And a timing circuit is not the sort of thing that is readily decoupled with 10nF ceramic discs!

The approach used employs separate RC combinations at each output, with $2.2\mu\text{F}$ and $5\text{k}\Omega$ being the values of the capacitor and stick pot respectively. Since the c.m.o.s. does not load this combination, it is easy to scale the values of the timing capacitor to suit different values of stick pot that may be encountered. It should be noted that the control stick potentiometers do not cover more than a fraction of their potential travel, usually swinging some 60 degrees. The standard servo control period is 1ms to 2ms with the centre point at 1.5ms so the values of R and C are chosen to permit this timing range with only a small proportion of the total track travel. Sufficient latitude to allow for the use of a mechanical trim is also necessary, to ensure that the sticks may be fully "zeroed" with respect to the servo output positions. Having read one channel of the encoder, the 4017 is clocked to look at the next, and so on until the final pulse, when the decoder is wired to skip a pulse, and then reset. The missed pulse thus effectively provides the synchronising period of the system, and is always related to the data rate. This is a fixed frame transmission, where the channel length is constant, and the period between the information pulses is simply the difference between T2 and the information pulse.

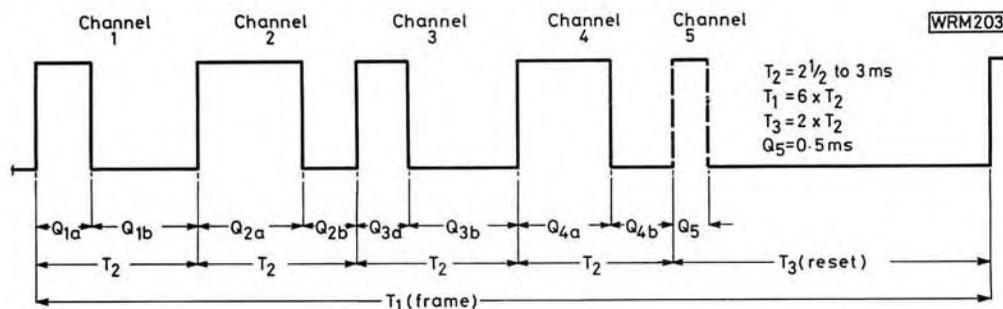


Fig. 1: The encoder output waveform showing the fixed frame length, the reset or synchronising pulse and the individual channel pulses (Q1a etc). Channel 5 is non-proportional and is intended for such applications as retracting under-carriages



Galaxy Models' Mini-Escort trainer fitted with Flash 15 motor

more deviation of a tolerably linear fashion than trying to waggle a 3rd overtone crystal configuration. Thus the crystal operates in a parallel load fashion, with a varicap in the load circuit, providing deviation at a level set by VR1. CT1 provides a trim adjustment of the output frequency, but it should be remembered that as the total load capacity is increased by altering TC1, so the deviation caused by the varicap is slightly decreased, as it is a smaller proportion of the total load capacity.

In any case, the larger the load capacity gets, the less is the effect on the crystal frequency. Capacitors C2 and C3 provide feedback in true Colpitts fashion, and the tuned collector load formed by L1, C4 and C5 selects the 27MHz component for subsequent amplification, thus turning the basic Colpitts circuit into a Clapp oscillator.

The next stage is self biased in Class C with a small choke (L8) in the base circuit. Here the ubiquitous FX1115 ferrite bead is used to good effect, since it must be noted that with only 5 turns or so, a rather surprisingly large amount of inductance may be achieved. About 15–20 μ H, in fact. This is so large that it was checked and re-checked, since this implies an enormous permeability for the material used. Little wonder it is so effective in various decoupling and isolation functions.

Tr2 is operated with a grounded emitter, and originally it was proposed to vary the power level of this stage to control the overall output, by switching an emitter resistor in and out of circuit. However, subsequent development showed this caused too much of a detuning effect on the L1/C4/C5 arrangement due to the variation of input capacitance of Tr2, that this feature was moved forward a stage to the output transistor, where the detuning effect had less effect on the spectral purity of the equipment. The feed from Tr2 to the output stage is similar to the preceding stage, except that a 7KN series Toko coil is used.

For low powered applications, the aerial may be taken directly from the tapping. It is also screened which, because of the proximity of L1, helps to prevent input-output feedback problems.

Output Stage

The output stage uses a TO39 case transistor. Nothing very special here, since although a v.m.o.s. f.e.t. was tried and tested, they are not intended for this type of work and while one batch of devices just about worked, another batch did not.

All v.m.o.s. f.e.t.s are not really suited to working with a power rail lower than 12V, and since the battery supply for the transmitter was designed around NiCad style cells it is far better to work with 12V down to 5V as the operational range. The device chosen performs admirably between 5 and 12V, with little discernible output change. The output at 9V being in excess of 1W in high power

mode, and about 400mW with a 5V supply. A small heat-sink is required for the output device to ensure longevity, and a zener diode is placed from the collector to ground, to catch any high voltage spikes that occur either during tune up operations, or when the antenna length is varied in the field.

The output network itself has evolved from a simple pi-network, to a more complex arrangement. However, the reasons are twofold, since although simplicity of tune-up is desirable, it rarely leads to an optimised output spectrum. The circuit around T1 is necessary to optimise the 27MHz drive, and minimise the remnants of the 13MHz fundamental, so L4 and L5 are essential to provide an r.f. output that can be accurately set up using a field strength meter. Since this circuit is capable of more power than the average, it is necessary to keep the stray fields to a minimum, or the encoder will be found to malfunction due to extraneous r.f. pickup on control leads. At 27MHz this isn't too serious, but as the frequency increases, it gets progressively worse. This basic circuit will retune easily enough to frequencies up to 50MHz.

Output Monitoring

The performance of the circuit is monitored via L5 and L6 which form a small current transformer with negligible loading on the transmitter circuit. Monitoring in this way is a far more satisfactory means of checking circuit behaviour than many of the age-old practices seen in r.c. Simple proximity "wavemeters" can be positioned such that it is the field from the tank coil, rather than the aerial itself, which is being monitored.

In the set-up process, the number of turns of L7 may be slightly increased to improve sensitivity, but in most instances, the circuit will set up almost instantly, simply tuning for maximum meter deflection with the chosen aerial. The meter should have a f.s.d. of 200 μ A.

Generous decoupling is provided throughout the circuit and is probably rather more than necessary. Ceramic capacitors should be used throughout.


The Hi-Lo power switch selects the value of the emitter resistor in the output stage, whereby the power is cut to a level set by the resistor value. A value of 22 Ω drops the power down to 100mW, although individual users may wish to change this to suit a particular application. The use of f.m. enables easy power changes, whereas a.m. usually requires a retune for best modulation characteristics when switching such power levels around. Also, of course, f.m. allows easy frequency multiplication remembering to reduce the deviation accordingly.

Although 27MHz is a long way from the 459MHz band available at u.h.f. in the UK, it just so happens that 459 is exactly 17 times 27, so those of you familiar with v.h.f. and u.h.f. might like to bear that in mind!

Construction

The complete transmitter is built on two printed circuit boards, one of which is the encoder and the other the actual transmitter unit. Both of these boards are straightforward and should present no problems to the constructor. Sockets are used for the i.c.s on the encoder board and, of course, all the normal precautions should be taken when handling these c.m.o.s. devices.

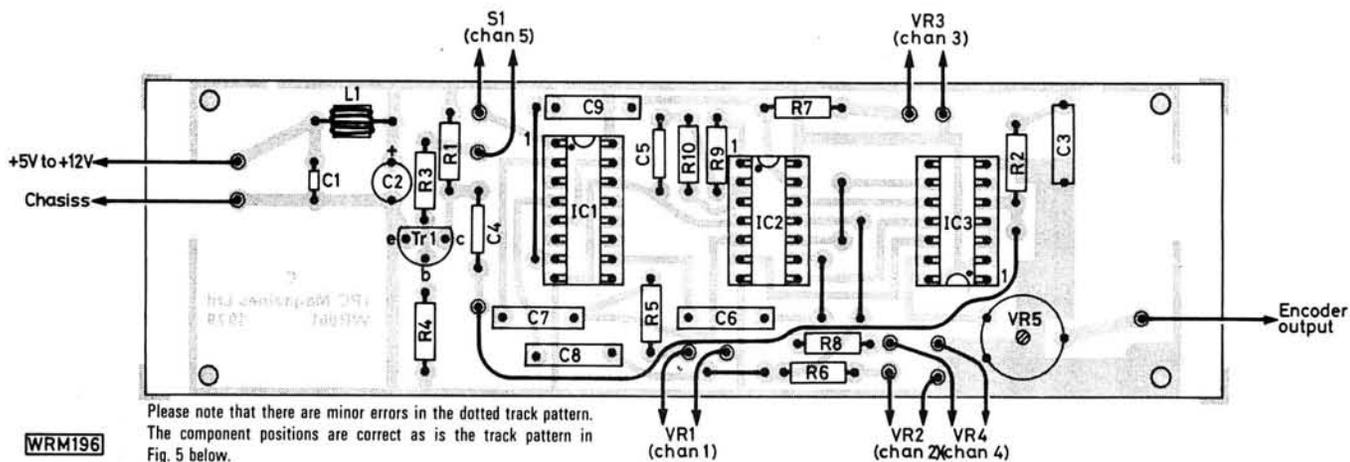The transmitter board has several r.f. chokes which are wound on ferrite beads as shown in Figure 9. When winding these care must be taken not to scrape the enamel coating off of the wire on the edges of the beads.



Please note that there are minor errors in the dotted track pattern. The component positions are correct as is the track pattern in Fig. 5 below.

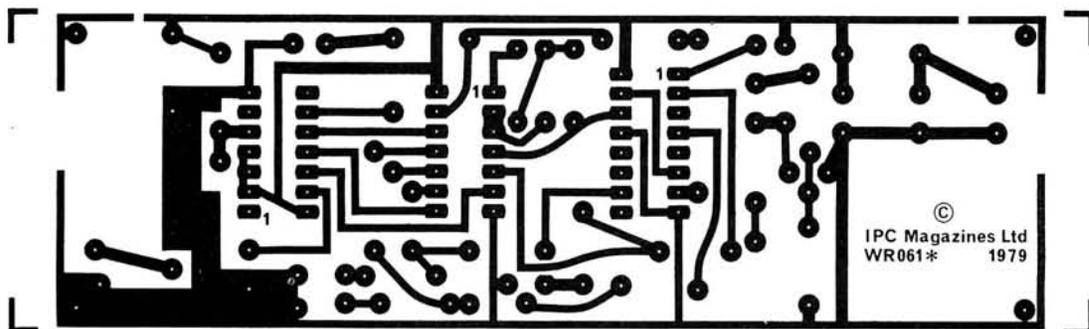


Fig. 4 (top): The component placement for the encoder board. Fig. 5 (above): The copper track layout is shown full size

The chokes which are wound on the torroidal dust cores should give no trouble if the drawings are followed.

The r.f. power output transistor should have a push-finned heatsink fitted and to give sufficient clearance between the transistor can and the aerial fixing screw, the transistor should be mounted close to the p.c.b., preferably using a transistor mounting pad.


The passive components should be as small as possible and in general capacitors are the sub-miniature disc ceramic varieties.

The transistors used are from Texas Instruments' Silect range and care must be taken to ensure that the lead con-

figuration of each is checked. The component placement drawing (Figure 6) shows BC224B types.

The encoder board is straightforward. The remarks on component size applies equally to this board as available height above the board when installed in the case is limited. The four timing capacitors are small tantalum bead types and the positive lead of each should go to the appropriate pin on IC1.

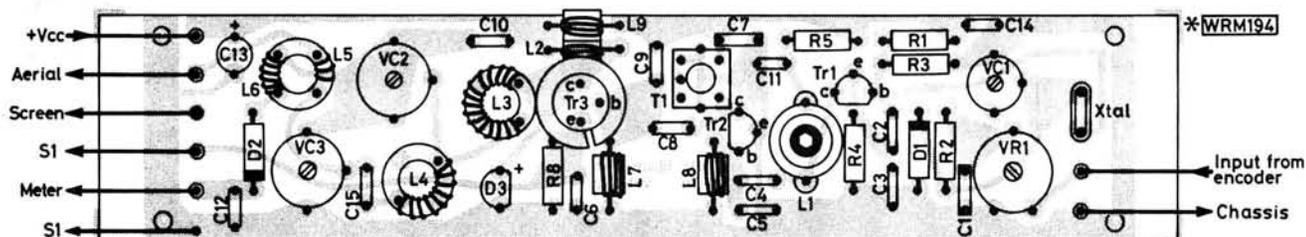The case chosen for the *PW* FM-80 transmitter is a red and black version of Micron's de-lux PL7-D case. This is elegantly styled, robust and easily assembled, giving the transmitter a really professional look. The case is supplied



Figs. 6 and 7: The component placement and copper track plan for the transmitter board shown here full size. Care must be taken to ensure that the lead-outs of Tr1 and Tr2 are checked carefully

Transmitter

Resistors

$\frac{1}{4}$ W 5% Carbon Film

10 Ω	1	R8
22 Ω	1	R5
150 Ω	1	R4
5.6k Ω	1	R3
10k Ω	1	R2
12k Ω	1	R1

Potentiometers

Min. horizontal preset

10k Ω	1	VR1
--------------	---	-----

Capacitors

Ceramic disc

22pF	1	C9
68pF	1	C8
100pF	1	C2
150pF	1	C3
220pF	2	C4,5
10nF	7	C1,6,7,10,11,12,15
22nF	1	C9

Tantalum

47 μ F 16V	1	C13
----------------	---	-----

Trimmer

2-22pF	1	VC1
5-60pF	2	VC2,3

Inductors

Toko 113CN2K509ADZ	1	T1
Toko M-20068	1	L1
L2,7 to 9 wound on FX1115 ferrite beads (see text)		
L3 to 6 wound on Micrometals T37-12 ferrite cores (see text)		

Semiconductors

Diodes

BA102	1	D1
OA91	1	D2
1N5866A	1	D3

Transistors

BF224	2	Tr1,2
2N4427	1	Tr3

Miscellaneous

Crystal (see text); Cambion miniature jacks (see text) (2); T05 heatsink (1); 28 s.w.g. self-fluxing enamelled copper wire (2m); p.c.b.(1); s.p.d.t. min. rocker switch (1).

Encoder

Resistors

$\frac{1}{4}$ W 5% Carbon film

150 Ω	4	R5,6,7,8
1k Ω	1	R1
4.7k Ω	1	R3
47k Ω	1	R4
100k Ω	2	R2,9

Potentiometers

Min. horizontal preset

4.7k Ω	1	VR5
---------------	---	-----

Capacitors

Disc ceramic

10nF	1	C4
47nF	1	C1

Polyester

0.1 μ F	1	C5
0.22 μ F	1	C3

Tantalum

2.2 μ F 35V	4	C6,7,8,9
10 μ F 16V	1	C2

Inductors

L1 wound on FA1115 ferrite bead (see text)

Semiconductors

Transistors

BC238	1	Tr1
-------	---	-----

Integrated circuits

4017	1	IC1
4069	1	IC2
4068	1	IC3

Miscellaneous

14 pin d.i.l. sockets (2); 16 pin d.i.l. socket (1); p.c.b.(1); s.p.d.t. min. rocker switch, Micron (1).

Mechanical parts

Case, Micron de lux Red MRC30 (1); Open gimbal stick units, Micron MRC27, with 5k Ω pots (2); Meter (see text); Telescopic aerial; Miniature toggle switch d.p.d.t.; Battery charger socket, SLM; 4.8V NiCad battery packs (2); Cable tie and base, self adhesive (2); Solder tags, 6BA (4).



in knocked-down form with two plastics moulded end cheeks, a plastics front panel, top and bottom metal pressings, the back and all necessary screws. A removable cover fills the crystal access hole and the aerial mount fits into a punched hole in the top panel.

The Case



The case should be assembled and the two open gimbal stick units screwed into position on the front panel. It helps if this is done before the case is screwed together.

The meter and on-off switch should also be fitted along with the neck strap attachment. The SLM charger socket is mounted in the cut-out in the bottom of the case.

With the case assembled the two boards can be positioned as shown in the pictures. The transmitter board mounts in the top of the case with the crystal positioned under the crystal access hole. The front edge of the board rests on the plastics lip of the front panel held in place by the small moulded pins. The board is anchored by two short lengths of 18 s.w.g. tinned copper wire soldered into the two vacant corner holes on the back edge of the board

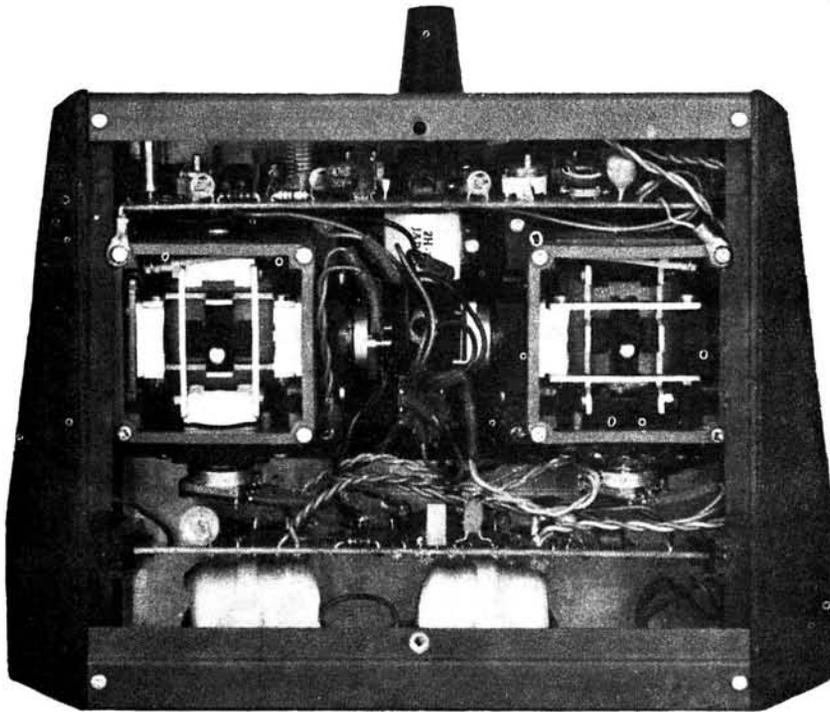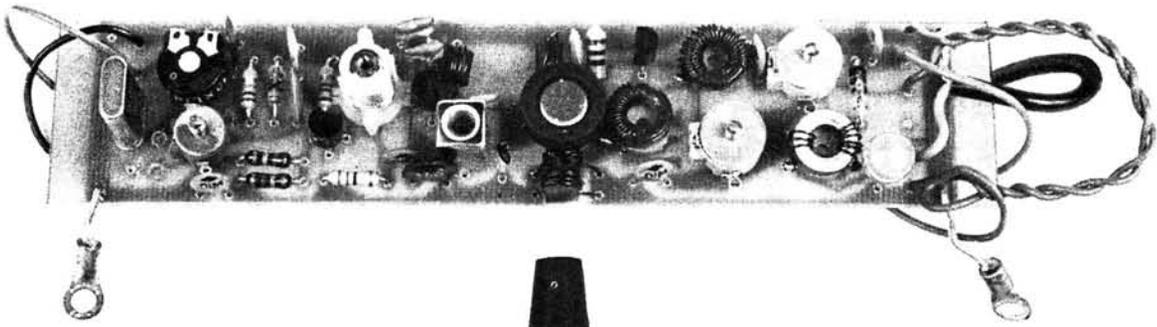

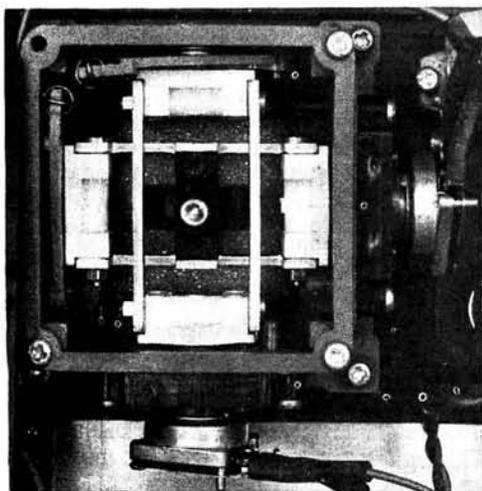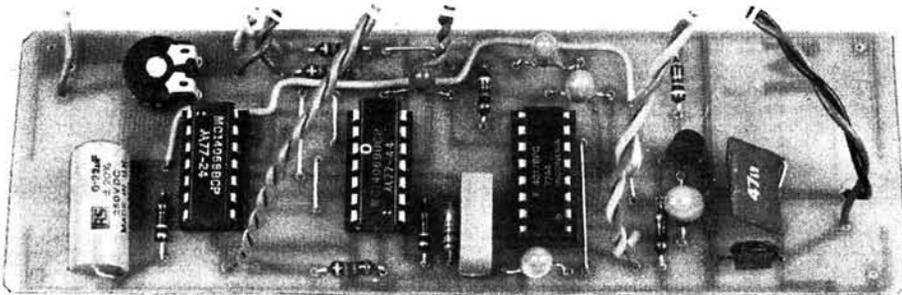The photograph on the left shows the completed transmitter with both boards and the control sticks correctly positioned. The transmitter board is shown at the top and the encoder board below the case



A close up of the open-gimbal stick used in the FM-80 transmitter (left) with the complete transmitter on the right



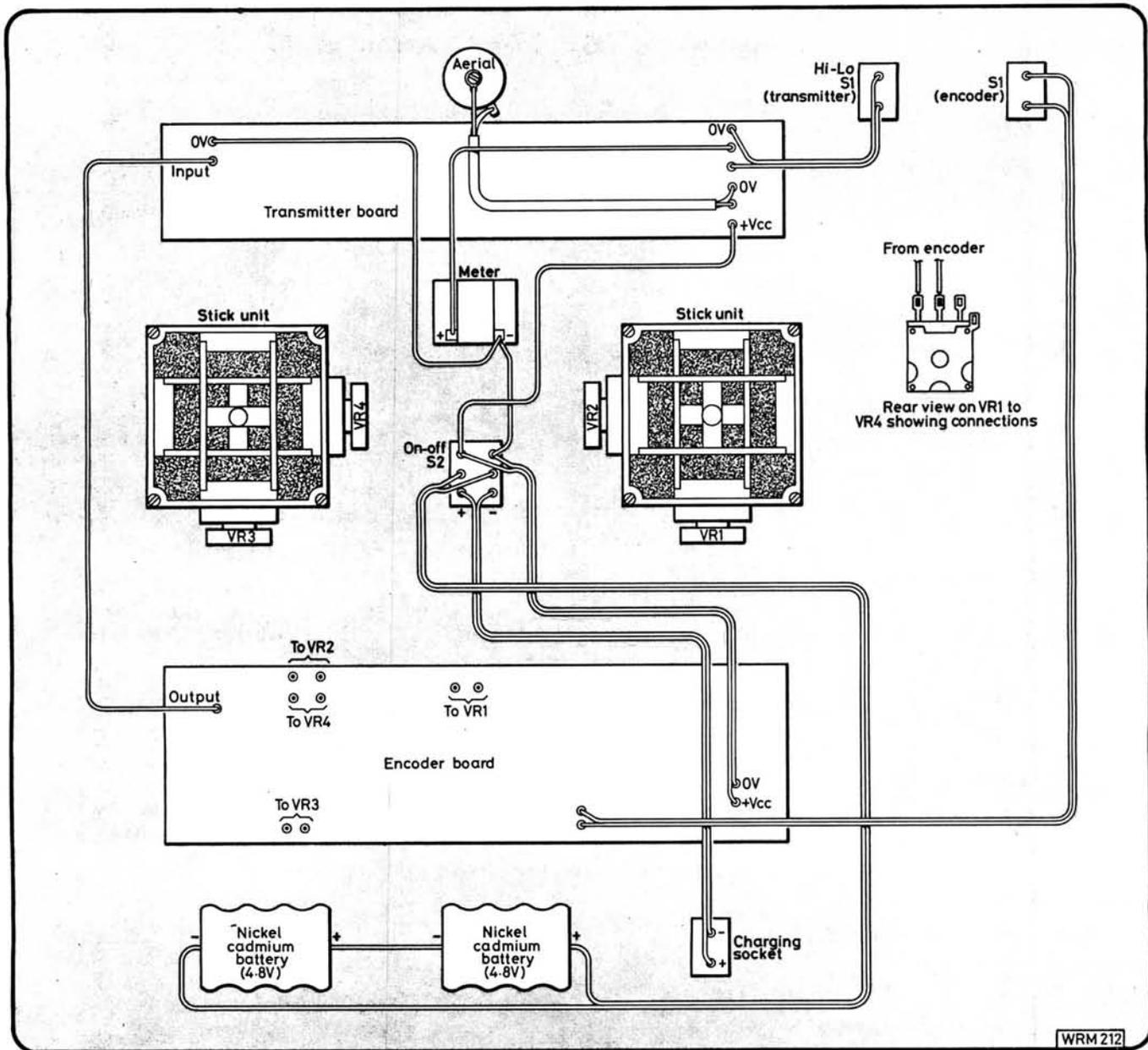


Fig. 8: The wiring layout of the complete transmitter and encoder. Care must be taken not to short out the battery terminals. The stick unit pots VR1 to VR4 must be set to 1.5kΩ before connecting wires are attached

and suitably bent to allow the wires to be soldered to two 6BA solder tags trapped under one fixing screw of each stick unit. The transmitter p.c.b. should be held by these wires so that the back of the board is almost touching the meter case. The crystal is mounted in a pair of Cambion low silhouette jacks (450-3704-1-03).

The encoder board is fitted into a pair of plastics slides which clip to the end cheeks of the case and are held in place with a small dab of Araldite Rapid epoxy adhesive. This allows the encoder board to be slid out of the case for access to the batteries and also to make wiring-up easier. With both boards in position and the lead-out wires soldered to the p.c.b.s the connections can be made to the stick pots. Only two leads go to each pot., the other end of the track may be connected to the wiper by a short wire link at the pot. Small rubber sleeves should be used at the pot. terminations to give extra strength to the joint. Each pot. should be set to about 1.5kΩ with the stick centred and the connections made to this end of the pot.

Batteries

The batteries, two 4.8V packs of NiCad rechargeable cells connected in series to give 9.6V, are held in two self-adhesive nylon cable ties which are fixed to the metal bottom of the case. The leads from the battery packs are taken around the end of the encoder board and to the centre tags of the on-off switch. The battery charger socket is connected to this switch to allow the charger to be connected to the batteries only when the switch is in the off position. The other tags on the switch are taken to the two p.c.b.s.

The aerial is wired to the transmitter board using a short length of r.f. screened cable which is connected to the aerial retaining screw by a solder tag. The braid is connected to another tag which is simply trapped between the aerial holder and the metal case while the retaining screw is tightened. The telescopic aerial is then screwed finger tight into the holder.

GALAXY MODELS

SPECIALIST MODEL SHOPS


IPSWICH 160 FELIXSTOWE ROAD
IPSWICH IP3 8EF
Telephone 0473 79279

NORWICH 88 CATTON GROVE ROAD
NORWICH NR3 3AA
Telephone 0603 42515

THETFORD 17 WHITE HART STREET
THETFORD IP24 1AA
Telephone 0842 4918

FORFAR
126 CASTLE STREET
FORFAR, ANGUS, SCOTLAND
Telephone: 0307 66531

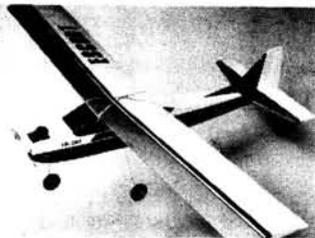ALTRINCHAM
116 MANCHESTER ROAD
BROADHEATH, ALTRINCHAM
Telephone: 061 928 0426



CLOUD MODEL AND FLASH SUPERDEAL

Escort + Flash 35 R/C. £32.95
Mini Escort + Flash
15 R/C. 24.95
Mini Escort (A/W) Flash
15 R/C. £27.25

All Engines include Silencers

★ ESCORT

54" simple beginner's Radio Trainer for 2-3 functions radios and 19 to 36 motors using rudder and elevator or rudder, elevator and throttle. Kit contains superb illustrated step by step plan with separate building instructions, all ply and balsa parts machine cut, preformed U/Cart, plus accessory pack containing tank, motor mount, horns, hinges, push rods and clevises, etc.

£16.25

SUITABLE ACCESSORIES

3 2 1/2" Wheels £1.80
3m Film Covering £3.15
Wheel Collets 65p
Fuel Pipe (2 ft) 34p
Spinner 2 1/4" 65p
2 volt Sealed Accumulator £5.55
5 Min Epoxy £1.12

★ MINI ESCORT

44" 2-3 function Sport or Trainer model for .09 motors. Also available 4 function aileron wing version for .15 motors. Kit contains all parts machine cut, veneered foam wings, motor mount, tank, preformed U/Cart, horns, hinges, push rods, clevises, plan and instruction booklet.

Standard Mini-Escort. £14.95
Aileron Mini-Escort £17.25

SUITABLE ACCESSORIES
3 2 1/2" Wheels £1.80
2 1/2m Film Covering £2.68
1 1/4" Spinner 50p
5 Min Epoxy £1.12
Wing Joining Kit £1.05

HOBBYCARD QUADBOND
BARCLAYCARD ACCESS

MAIL ORDER

Please add £1.00 post/packing on Escorts. Accessories if ordered with kits are post free Barclaycard. Access and Hobbycard customers, phone card number for immediate attention. Overseas orders sent airmail at cost - please add reasonable amount. Any excess will be credited. 24 hour despatch on all goods unless otherwise notified.

R/C SERVICE CENTRE

Derek Hughes runs our fully equipped Service Centre at the Ipswich branch. We are officially appointed Service Agents for Savielair and Sarnwa and have Full spares backing for Futaba and most other makes. Send Direct to Derek for expert individual attention

UNBEATABLE OFFERS & SERVICE

NICADS

VARTA & SAFT
Rechargeable Batteries.

14 day money back guarantee if not totally satisfied.

"DEAC" DKZ Button Cells

4.8v Receiver Pack
225mA £3.00
500mA £5.35
9.6v Transmitter Pack
500mA £10.70
Rx/Tx conversion
12 pencils, charging holders and Rx/Tx charger £20.50

"VENTED" CELL (for fast charge)

0.5Ah* Pencil/HP7 £1.30
1.2Ah RSH Electric flight. Tags only £1.65
1.2Ah VR Electric flight Tags only £1.65
1.8Ah* U11 replacement £2.35
4.0Ah* U2 replacement £3.20
*Tags available extra 10p per cell.

CONSTANT CURRENT CHARGER - ideal for all nicads - switched 25mA/50mA/120mA/200mA/400mA output - charges up to 12 cells in series without adjustment - £13.45 see for further details.

PHOTOGRAPHER'S CHARGER - Charges 1 to 4 HP7 size nicads £6.45.

FIELD CHARGER 12v input/two 50mA constant current outputs - ideal for charging up to eight 0.5Ah nicads or two "Deacs" per output £8.30.

UK POST AND PACKING - ADD 50p PER ORDER.

V & F SMALLCRAFT (POPLAR) LTD.

38 Stoneleigh Road, Clayhall, Ilford, Essex. Tel: 01-550 6642

PRACTICAL WIRELESS PRINTED CIRCUIT BOARDS

Dec 78	Digital Door Chimes	£2.90	Jan 79	Delay Line	£2.90
Jan 79	P.W. Sandbanks	£2.90	Feb 79	Hythe Rx	£4.60
Mar 79	Hythe P.S.U.	£2.40	Mar 79	Soundlite	£4.60
Apr 79	F.M. Multitester	£1.70	May 79	Xtal Calibrator	£1.30
Jun 79	0 + X (4 Boards)	£11.00	Jul 79	Frequency Meter	£3.20
Jul 79	V.M.O.S. Tx	£3.20	Aug 79	Telebelt Repeater	£0.90
Aug 79	Intercorn	£4.75	Sep 79	Noise Blanker	£0.90
Sep 79	Door Unit	£0.40	Oct 79	Burglar Alarm WR060	£0.90
Oct 79	Burglar Alarm WR059	£0.90	Nov 79	Radio Rx WR064	£1.50

H.T.E. 4 Watt Electronic Siren Kit £2.99. P.C.B. + CCT Details £0.90
H.T.E. Domestic Touch Sensitive Light Dimmer P.C.B. + CCT Details £0.90

For full list of P.W. CCT Boards see your Nov issue or send S.A.E

FASCIA PANELS TO YOUR DESIGN

Low cost/high quality self adhesive panels in mono or coloured. Hundreds of uses. Control panels, nameplates, warning notices, call signs etc. Gives homebuilt equipment the professional look. Sending 50p for useful sample labels and full details could be your wisest move today. We can also make P.C.B.'s to your design.

H.T.E. (Dept P.W.) 50 Milnfield Ave., Elgin,
Morayshire IV30 3EL

WHOLE NEW WORLD OF ELECTRONICS



COMPETITION DEVELOPED RADIO CONTROL KITS & ACCESSORIES

LARGE S.A.E.

LISTS & CATALOGUE

KIT SAMPLES:

MRC 08 AM 6 CHAN TX	£33.60
MRC 02 AM 7 CHAN RX	£13.95
MRC 03 UNIVERSAL SERVO	£10.95
MRC 12 FM 4 CHAN TX	£39.50
MRC 22 AM RF MODULE	£6.40
MRC 23 FM RF MODULE	£6.40
MRC 25 SERVO AMP ONLY	£4.95
MRC 24 CMOS ENCODER	£8.13
MRC 26 STD STICK UNIT	£5.00
MRC 27 COMP STICK UNIT	£6.95
MRC 18 SERVO TESTER	£3.58
MRC 15 SERVO REVERSER	£1.48
MRC 29 PUNCHED TX CASE	£5.62
MRC 38 CENTRE LOAD AERIAL	£3.30
MRC 37 FAIL SAFE UNIT	£2.56

micron

ACCESS
BARCLAYCARD
Tel 0607 395418

Hayworth Road, Sandacre, Nottingham.

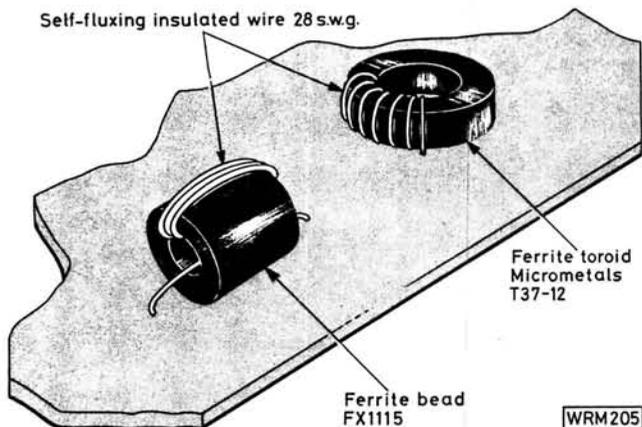


Fig. 9: The correct method of winding the r.f. chokes and toroidal inductors

The stick movement should be checked together with the action of the trim tabs, making sure that the connections to the pots do not foul any part of the encoder board.

Finally, if you opt to fit the fifth channel and the Hi-Lo power switches these are mounted on the top of the case at the opposite side to the crystal access hole. Micron can supply ready punched cases and switches to fit if required.

Setting Up

All wiring and p.c.b.s should be carefully checked before switching on and the NiCad batteries should be checked to ensure that they are fully charged and connected correctly.

The output level preset on the encoder board and the input level preset on the transmitter board should be set to give a low level of modulation before switching on.

If all seems to be in order the power can be switched on and the transmitter checked for operation. The meter should deflect to show that r.f. power is being pushed up the aerial. To tune the transmitter for maximum output it is necessary to have the p.c.b. removed from the case to enable the various trimming capacitors and coils to be reached. The total current taken should be about 200mA with a 9V supply rail and S1 in the high power position.

Tune L1, T1 followed by VC2 and VC3 to give maximum output as indicated by the meter. If you have a frequency counter capable of measuring at 27MHz this can be used to check the frequency of the output. Slight adjustment of the frequency can be made with VC1.

To check the operation of the encoder a scope is really needed. However it is possible to use the receiver and a known good servo to set the pulse width for each channel to the correct 1.5ms centre and 1 to 2ms swing.

The modulation can be set using the frequency meter by disconnecting the input from the encoder and holding the top of VR1 on the transmitter board to the positive supply rail, noting the frequency at the transmitter output. The deviation can be set by adjusting VR1 to give the desired 2 or 3kHz change in transmitter frequency.

Next month we will describe the servos to suit the PW FM-80 system. For the model boat or car enthusiast a simpler 2-channel transmitter will be outlined later in the series together with details of installing the complete system in various types of models.

A licence is required to operate radio control equipment. This costs £2.80 for five years. Application forms are available from: The Home Office, Radio Regulatory Dept., Waterloo Bridge House, Waterloo Road, London SE1 8UA

SLM MODEL ENGINEERS LTD.

Chilton Road, Prestbury,
Cheltenham.

Telephone: 25488 Telex: 437172.

In conjunction with the present series of articles in **PRACTICAL WIRELESS**. The items that we manufacture comprise:

- Transmitter Cases ● Control Sticks ●
- Receiver Boxes ● Battery Boxes ●
- Auxillary Levers ●
- Plugs & Sockets ●
- Aerials etc. ●

Tool range facilities manufacturing moulding dyes and press tools. We can supply precision turned parts on swiss sliding head automatics. We can cut spur gears up to 2" diameter 4 bevel gears and our moulding capacity is up 6oz in virtually any material.

WE DO NOT HANDLE

● **ELECTRONICS** ●

OR

● **ELECTRONIC COMPONENTS** ●

FLEET R/C SERVO - TYPE FPS-3

A COMPLETE KIT FOR THE HOME CONSTRUCTOR



This small, powerful servo (size 1.55 x 1.5 x .73", weight 1.4 ozs.) employs the latest Ferranti 419 I.C. amplifier driving a top quality 5 pole servo motor with a CTS cermet feedback potentiometer (5K) assembly. Transit time is .4 seconds with up to 6 lbs. thrust available. The body and gears are moulded in a tough acetal copolymer (Hostaform), with a gear ratio of 250:1. Resolution is $\pm 1\%$, with near perfect damping; while the output can be rotary or a linear rack type - all parts are supplied with the kit.

FPS-3 servo kit complete (less plug)**£11.45**
 Special price for Practical Wireless readers.....**£11.45**
 FPS-3 Amplifier kit with 419 I.C.**£4.75**
 Ferranti 419 I.C. with circuit board and instructions.....**£2.95**
 FPS-3 servo mechanics (inc. motor & pot.).....**£7.20**

Fleet 3-pin plug**27p** Fleet 3-pin socket.....**27p**
 Spare gears etc.....**15p** Spare body parts**30p**

The FPS-3 servo is suitable for use with the P.W. F.M., R.C.M. & E.F.M., E.T.I./REMCON and virtually all modern commercial R/C outfits.

All prices include VAT. Order by mail (add 30p p&p), telephone, or in person. Payment by cash, cheque, ACCESS, Barclaycard, Hobbycard, etc.


FLEET CONTROL SYSTEMS 47 FLEET RD., FLEET, HANTS. TEL: FLEET 5011

**SPECIAL
PRODUCT
REPORT**

2301

FUNCTION GENERATOR

RADAT INDUSTRIES

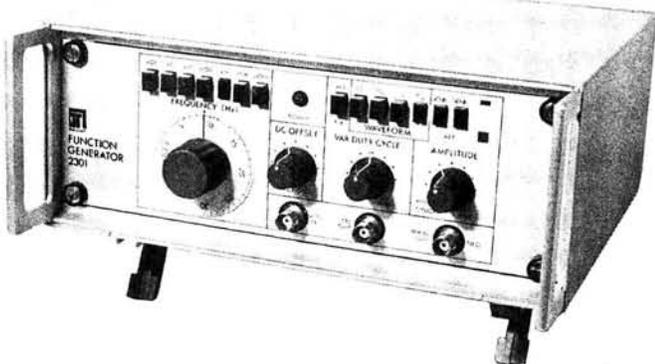

A function generator is of much more use in a lab than a simple sine wave oscillator. The ability to produce a wide variety of different shaped waveforms gives the user the means with which to test the correct functioning of most of the projects he is likely to build.

The Radat 2301 Function Generator is a well built instrument which can produce rectangular pulses, triangular and sinusoidal waveforms, each type having a variable duty cycle. A simple d.c. level can also be set.

The frequency range covered starts at 0.1Hz and goes up to 3MHz. Seven push buttons are used to select the range multiplier with one calibrated dial to vary the frequency setting over the range 1 to 30.

All the controls are mounted on the front panel and are simple to use, being clearly labelled. The two output sockets are 50Ω BNC types and one is intended to provide a suitable output for matching into TTL logic.

Push-buttons are also used to select the waveform shape,

continued on page 54▶▶▶

★ specification

Waveforms

Main output: sine, square, triangle, adjustable d.c. level. Without offset, all waveforms are symmetrical about ground. All waveforms may be offset. Output impedance 50Ω.

TTL output: TTL signal, coherent with the signal at the main output. Fan-out minimum 2TTL loads, rise and fall time, max: 50ns, typ: 15ns.

Waveform Characteristics

Sine distortion: 1% 10Hz to 200kHz.

Triangle linearity: deviation from best straight line better than 1%, 1Hz to 100kHz.

Square rise and fall time: 50ns into 50Ω.

Total aberration: less than 5%.

Duty cycle: 50% ± 1% in NORMAL mode
5% to 95% adjustable in VAR DUTY CYCLE mode.

Duty cycle change vs. frequency change: 2%.

Stability of frequency, amplitude, and offset better than 1% for 24 hours.

External sweep: External 10V d.c. or a.c. voltage at the VCO input changes the output frequency over a 1000:1 range. Bandwidth 100kHz, maximum slew rate 0.3 V/μs, input impedance 10kΩ.

Frequency:

Range: 0.03Hz to 3MHz in 7 decade ranges.

Dial accuracy: 3% of full scale.

Dial range: 100:1.

Amplitude (main output)

Max output: 20V p.p. into o.c.

10V p.p. into 50Ω.

Step attenuator: 0 to 60dB in 20dB steps.

Amplitude vernier: 10:1 (20 dB) continuous.

Sine flatness: better than 2%.

15V. 1A output amplifier protected against short-circuit or external voltage.

D.C. Offset continuously variable ±10V o.c., with on-off switch on front panel. Total signal plus offset limited to ±10V o.c. independent of vernier control and attenuated proportionally with step attenuator.

Power: 220–230 Vac ±10% or 110–115 Vac ±10%
50–60Hz, 15W.

Dimensions: 278 × 110 × 250mm.

Weight: 3.5kg.

From Wembley to the Weser...

Joe BISHOP

A New Television Service For British Forces Germany



Since the end of the Second World War, a substantial portion of the British armed services has been stationed in West Germany. First as a part of the Forces of Occupation and then, after the birth of the new Federal Republic of Germany in 1949, as part of NATO's answer to the ever-burgeoning armies of the Warsaw Pact, the United Kingdom has maintained this continuous military presence on the European mainland.

British servicemen and their families have come and gone in their many thousands, and each has played a major or minor role throughout this long period in "keeping the peace"—enabling Britain to honour her expensive but vital obligations. The aim of all this effort has been to preserve some balance in a situation of almost complete impasse.

After a staggering 34 years, both sides are still implacably staring at each other across barbed-wire, minefields and bare earth, stretching in an unbroken ribbon from the Baltic to Czechoslovakia. Watchtowers stand like sad sentinels along this shabby divide, where two ideologies stand face-to-face.

Background

Away from the frontier and despite the passage of time many other old problems also remain; problems which exist mainly because the British Forces community in West Germany is, despite its air of permanence, a transplanted one. Only a relative handful of the British people working for the forces in Germany have spent a substantial part of their working lives there and have, as a result, been able to integrate with, and understand the culture of their host nation. There is often, therefore, a sense of isolation and solitude to which the young families, in particular, are subject. For many people, accustomed to everyday life among their relatives and friends in the UK, life becomes a battle against loneliness when the breadwinner is away on manoeuvres or perhaps completing a tour of duty in Ulster.

Senior officers have always recognised this problem, but in a defence environment the resources that can be deployed to overcome it are limited. The British Forces in Germany have, in addition to the traditional "mess"


facilities, their own cinema circuit and same-day newspaper distribution system, their own newspapers in fact. German language training is taken seriously and, out of the British Forces Network of the days of occupation, was born the British Forces Broadcasting Service which has for many years provided the forces community with home-grown radio entertainment—f.m. and now in stereo as well.

To improve the lot of the serviceman still further and to bring him into line with his NATO colleagues, it was decided that a single-channel colour television service should also be provided. The technical, legal and organisational problems were formidable in the extreme and delays have been plentiful. But now BFBS is in the TV business with a vengeance, providing programmes to an eager audience which is growing rapidly as the British Forces Germany Television Project expands towards completion. The contract for the design and supply of the system was placed with Marconi Communication Systems Limited as probably the only British company with sufficient total capability, but also no less involved are a host of civil servants and serving soldiers without whose efforts the project would never have got off the ground.

Certainly, the new service has added a new and much-needed dimension to life in married quarters, and the feeling is that it has also had a quite marked and beneficial effect on welfare statistics.

Planning

There is no doubt that, from its inception, the project presented the engineers and planners with an interesting and unusual problem. Under normal circumstances, once the decision to introduce a broadcasting service has been made, the priority is to get it going for the most people as quickly as possible. It is generally, therefore, the most populous areas that benefit first—and it is in the most populous areas (the big cities) that the studios etc. are normally located. Thus BBC Television, for example, started at Alexandra Palace in 1936 and gradually expanded outwards (WWII permitting) as public demand increased and the state of the art improved. It was only many years later that TV reached the nethermost regions of the British Isles.

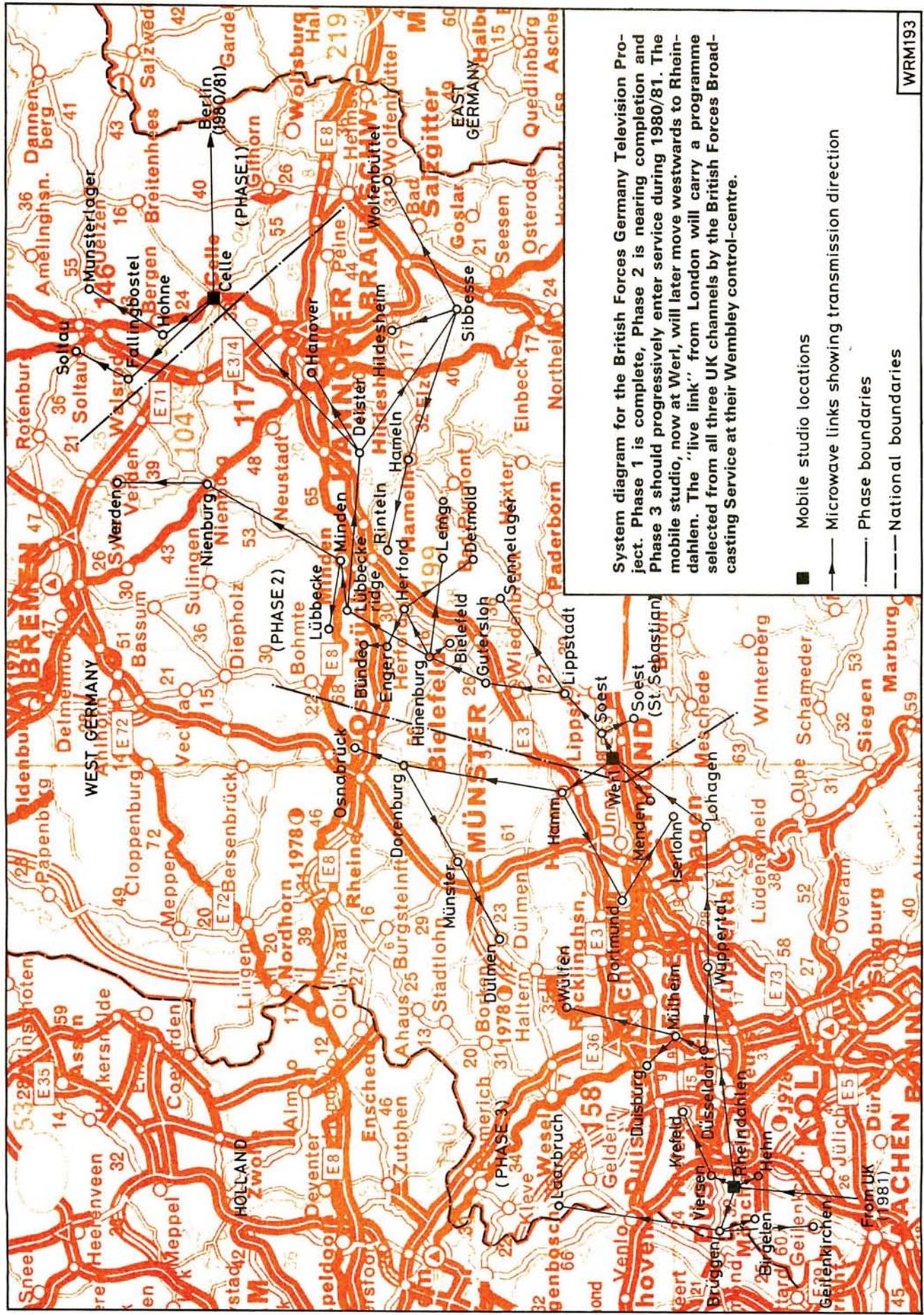

In BAOR, however, the situation and needs are very different from those of a normal civil population. Here, the initial priority was to provide the service to the people in most need; those who were furthest from the United Kingdom, whose social amenities were the most rudimentary and whose geographical location and environment were the most bleak. It was decided that the Army garrisons in the north-east of the region, immediately adjacent to the East German frontier, should receive the service first. The system had to be installed, as it were, "back to front".

Phase 1 of the system (see map) consisted of only five stations fed by a videotape control centre located at Celle. Studio complexes and direct reception from London were out of the question, so tapes were flown out daily for onward transmission to the audience (and still are).

As the system expanded the VTR centre would be required to move and so it was put on wheels—this successful example of typically British innovation was designed for BFBS by London Weekend Television, and is now parked at Werl, where it arrived on 11 December 1978 after an overnight move from Celle. Its final resting place will be at Rheindahlen, sometime in 1981.

The reversal of normal priorities was only a facet of the overall problem, however. To make matters more difficult, not only were the snags geographical in nature. There were questions of copyright and points involving national broadcast agreements to be resolved; planning permission for towers to be obtained; frequency planning to be carried out and agreed with the Deutsche Bundespost (DBP), the licensing authority; plans for towers, power supplies and fenced enclosures to be drawn up by the Property Services Agency.

It was also necessary to restrict the audience, as far as possible, to the British Forces and their families stationed in Germany. Thus it is CCIR television System I that is used (6MHz separation between sound and vision channels as in the UK) instead of System G (5.5MHz separation)

An existing steel-lattice tower, modified to carry BFBS TV as well as military traffic

Photo courtesy MoD



Videotape operator Maria Linne in BFBS TV's mobile control room at Werl, W. Germany

Photo courtesy BFBS

which is used for German national TV. Transmitter output power is deliberately limited to the minimum required to achieve an acceptable signal throughout the service area and in many cases, the transmitters are rated at only 2.5W; the most powerful will be rated at only 200W. Naturally, the less power the greater the number of transmitters that are required to provide the desired coverage.

With over 3000 television transmitters already on the air in West Germany, the planning required in order to avoid mutual interference was, to put it mildly, very intricate!

Distance

Additional problems that had to be overcome at an early stage stemmed from the sheer distance between London and the furthest transmitter in Germany. In any system, television signals are conveyed from the studio and switching complex to the broadcast transmitters via a "bearer network". Nowadays, this could consist of a mixture of coaxial or fiberoptic landlines, line-of-sight microwave paths or satellite communication links. The particular snag with the Forces system, of course, was that the bearer network would cross the territory of five different nations—each with its own laws, procedures and quirks.

Initial studies, not unnaturally, centred around finding a method of conveying the BFBS channel directly from the UK to Germany without troubling the French, Belgian and Dutch authorities. All the extra planning and negotiations that this would involve made these studies eminently worthwhile: but after careful consideration of tropospheric scatter, a satellite link and even the use of a balloon as a sky-reflector, it was a chain of microwave stations coupled with some rented capacity that was selected as the optimum method of crossing the Channel, France and the Low Countries.

At the present time, negotiations are substantially complete and it should be possible, barring unforeseen difficulties, to "feed" the BFBS transmitters direct from London sometime in 1981. Particularly when it is borne in mind that planning and feasibility studies are well advanced to extend the system onwards into Berlin, this will create, in terms of physical size, what is probably the largest private colour television system in Europe; the path-length from end to end will be over 1000km. From Wembley to the Weser and beyond . . .

Composite Signal

A television video signal is a complicated waveform at the best of times. Although its basic shape grew out of the work of John Logie Baird, technology has moved on. The advent of u.h.f. 625-line television, offering the consumer firstly enhanced definition and then (wonder of wonders!) colour, has transformed the archetypal waveshape into the somewhat complex form depicted in Fig. 1(a), actually a standard UK vision test signal.

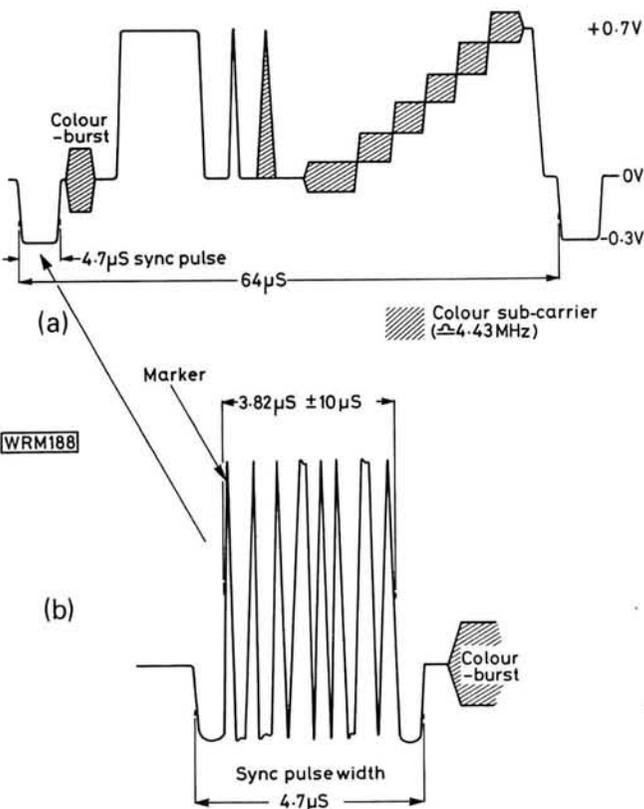


Fig. 1(a): Test signal without sound-in-syncs. Fig 1(b) shows how the encoded audio is inserted into the sync pulse

To complicate matters further, the waveform can also be made to incorporate "sound-in-syncs" information, hence this complete signal might properly be described as a "composite television signal". It is a baseband (pre-modulation) signal such as this that is fed into the BFBS system; the audio is combined with the video by encoding the sound into digital form, and then neatly slotting the resulting data stream into the sync pulses of the video waveform. It therefore becomes possible, throughout the bearer network, to process the sound and vision as a single entity. Using digital techniques means that there is no appreciable loss of sound quality beyond that introduced by the encoding and decoding process itself—you either have sound, or you don't!

Microwave System

The composite waveform, which contains frequency components extending from d.c. to 6MHz, is fed through the microwave bearer system by causing it to frequency-modulate a 70MHz carrier, with a deviation of ±8MHz. As 70MHz is the CCIR-recommended i.f. mainly employed in wide-band radio transmission, up and down conversion from s.h.f. is accomplished using well-tryed and established techniques. As far as the microwave system is concerned, the composite TV signal might just as well be 1500 telephony channels! This modulated 70MHz carrier is fed directly from equipment to equipment through the microwave chain. It is demodulated only on arrival at a site where it is required to drive a broadcast transmitter.

With such a large bandwidth to accommodate, one of the principal design considerations for the bearer equipment is to incorporate effective "amplitude response equalisation" and "group delay equalisation". The former consists simply of ensuring that, whatever frequency the equipment is passing through its designed bandwidth at any given moment, the amplitude of the output signal remains unchanged. Amplitude variations in an f.m. system appear as the arch-enemy, distortion—to be avoided at all costs! The latter is a more difficult concept to grasp.

Without going into a singularly indigestible explanation, one has "delay" problems if components of the signal fail to have the same relationship *in time* at the output of the demodulator as they possessed at the input to the modulator—in other words, parts of the signal arrive late. With the PAL system of colour television, depending very much as it does on the relationship between the black-and-white (luminance) and colour (chrominance) information, the effects of this type of non-linearity can be pretty revolting!



A microwave antenna being mounted onto one of the modern concrete pylon towers preferred by environmentalists

Photo courtesy MoD



The studio control room at the London Control Centre. Left to right Amanda Craig, David Gray, Corinne Schnabel and John Harrison

Photo courtesy BFBS

The necessity of obtaining an above-average link performance was a problem encountered while the project was still at the planning stage. By the time the signal arrived at one of the furthest extremities of the system (Munsterlager, for instance, 941km from London), it would have passed through 30 equipments in tandem—was there a line-of-sight equipment of British manufacture (costs, and particularly foreign-exchange costs, had to be kept to an absolute minimum) which possessed the exacting performance parameters required? It transpired that there was certainly none available “off the shelf” and the Phase 1 stations, in order to meet the original deadline, employed Norwegian-made NERA microwave equipment.

The sub-contract for the microwave used in later phases was subsequently awarded to Ferranti Limited, who produced a terminal complete with “hot standby” and logic-controlled automatic changeover. The equipment is accommodated within a single 19in rack and uses frequencies allocated within the 8GHz military band—the Werl area is an exception, where frequencies in the 9–10GHz band were used to avoid interference from an adjacent Belgian forces system.

Broadcasting Stations

On completion, there will be over 40 broadcast transmitters operating throughout the system—each will have been individually planned and approved and many will have been the subject of a local-planning argument. The photograph shows the Marconi B7303 u.h.f. transmitter which is standard throughout the system—either as a transmitter in its own right or, in the case of the more highly-powered stations, as a “drive unit” for a triode power-amplifier (manufactured by Magnetic AB of Sweden), which is then rated according to the e.r.p. (effective radiated power) required from the broadcast aerial array.

The “polar diagram” for a typical transmitter is shown in Fig. 2—this depicts the necessary and, indeed, licensed radiation characteristics for the broadcast aeri- als as determined by the distribution of the British Forces population in the service area, and the terrain within that area. A broadcast array to produce the desired radiation

pattern is arrived at by means of computer calculations. In essence, the array consists of a number of standard broadcast panel-aerials positioned and differentially fed so as to squirt the required e.r.p. in each direction.

Some of the transmitters will be housed in existing buildings and will use existing towers which may have been strengthened to cope with the extra loading. However, in the majority of cases, neither suitable buildings or towers were available within the area selected for the transmitter site. For ease of installation and to minimise the amount of on-site installation work required, Marconi developed a special vehicle-transportable container. The idea was to save time and to keep costs to a minimum—containerisation effectively means that some in-station testing can be accomplished before the equipment leaves the factory. This reduces the amount of installation effort required on site, and means that the complete station can be moved from the factory at Chelmsford to its German destination as a single entity.

The containers themselves are designed to require minimum maintenance and were especially developed for the project; normal airtransportable containers were ruled out as being unsuitable and too costly for this particular application.

Planning Delays

The most obvious thing about any broadcast station is, of course, the tower on which the broadcast and microwave aeri- als are mounted. And, it was in seeking planning approval for such towers from local authorities that many of the delays in bringing the project to fruition occurred. This is really quite understandable as the process of obtaining planning permission is necessarily complicated and time-consuming. The overall priority must be to protect the environment.

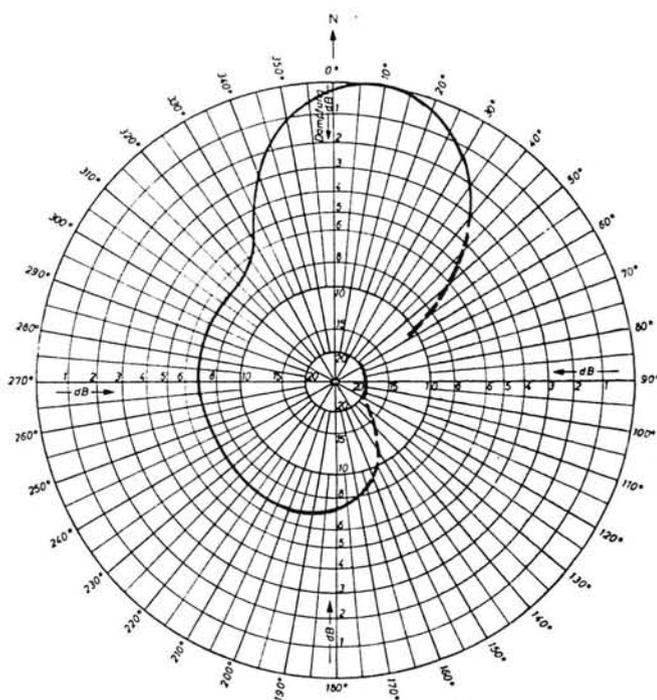


Fig. 2: Polar diagram for a typical transmitter used in the system described

Therefore, in many cases, plans were submitted, were rejected and then re-submitted and so on. It has taken two years or more in such instances, for the planning approval procedure to be completed.

Where existing towers have been used, they are generally of lattice form, but today the type of structure that is preferred from an aesthetic point of view is the self-supporting concrete pillar. The photograph shows the type of tower being used in the new system. This type is manufactured by the Pfeleiderer company of West Germany and has the advantages of requiring only nominal ground area, very little maintenance and being very stable in high winds. The broadcast aerials can be conveniently mounted at the top with an unobstructed view in all directions.

Programmes and Organisation

The television service for the British Forces in Germany consists of only a single channel. As the aim is to enable the viewer, as far as possible, to enjoy the same programmes as he would "back home", the bulk of the broadcast material is taken from the output of all three UK channels—some of the more popular "oldies" are interleaved for good measure. Therefore, the scope and quantity of TV material available to BFBS is enormous and the new channel should be able to pick and choose from the best of the UK's national television output. At the same time, a number of programmes are specially produced—German lessons are an obvious example.

One delight that the BFG viewer is denied, however, is the full-length feature film. Copyright aspects of the service mean that BFBS are not able to screen *The African Queen* or *The Great Escape* once, let alone twenty times, or any of those other old movies that the British public holds dear (or does it?). The philosophy

underpinning the selection of material, BFBS's Programme Controller John Harrison told me, is a concern to maintain a balance between news, shows, quizzes etc. as close as possible to that of the total UK national output.

At the present time, all the programmes, "trailers" and announcements are pre-recorded in London—the tapes are flown out to Germany on a daily basis. They are then fed into the system from the mobile VTR centre at Werl. With the establishment of the direct microwave link with London next year, principal control of the programme output will move from Germany to England—in fact, to BFBS's own control-centre in Wembley. It will be at this time that the Forces viewer will be able to receive television news programmes for the first time.

Technical support, maintenance of studio facilities and the supply of pre-recorded material will continue to be provided by London Weekend Television (as BFBS's contractor) but presentation, content and broadcast control will be the firm responsibility of BFBS as at present.


The maintenance of the broadcast transmitters and the bearer network within West Germany itself is directly provided by the Royal Corps of Signals—as the routes and towers used by existing military communications systems were employed wherever possible in the new TV system, it made sense, of course, to combine to military and TV maintenance commitments. Unnecessary duplication is therefore avoided and the cost of maintaining the new system is reduced to a minimum. Maintenance of the new network is accordingly the responsibility of specialist engineers employed by the MoD.

Test equipment, training and numbers of staff are gradually being augmented to take account of this new commitment but there is no doubt that this could be an area of difficulty—nowadays there simply are not sufficient people around with the wide range of requisite skills!

And Next?

In no time at all, the BFG community will have become completely used to having a unique television channel which caters to its specific needs, the programmes presented by people who have a detailed knowledge of, and insight into the military way of life. Proposals are already in hand for a BFBS television studio at Rheindahlen and even the possibility of transmitting Teletext over the new system is being studied, perhaps with a view to inserting a few pages especially for military use.

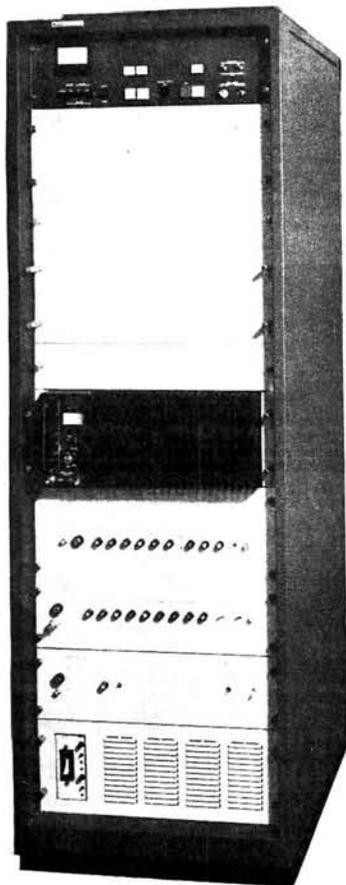Television is in BAOR to stay, taking its place alongside the other organisations whose prime concern is the morale and welfare of their British Servicemen and their families overseas. ●



Marconi B7303 u.h.f. transmitter of the type used throughout the system

Photo courtesy Marconi Co.

Acknowledgements

The Author would like to thank The Directorate of Military Communications Projects (Ministry of Defence), The British Forces Broadcasting Service, Marconi Communication Systems Limited and The Chief Signal Officer, BAOR for their kind cooperation and assistance in the preparation of this article.

A WIDEBAND RF PREAMPLIFIER


M. TOOLEY BA G8CKT & D. WHITFIELD BA MSc G8FTB

The wideband r.f. pre-amplifier described in this article provides a gain of greater than 20dB over a wide range of frequencies from 200kHz to over 50MHz, making it ideal for use with a large variety of test equipment including oscilloscopes, r.f. voltmeters, digital frequency meters and wavemeters. The unit can enable a considerable increase in sensitivity to be achieved which is particularly useful when measuring very low voltage signals. It can also be used as an untuned pre-amplifier for use with receivers on all bands from l.f. to v.h.f.—it will give a useful boost to the performance of any receiver when an inefficient aerial system is being used, for example.

The pre-amp is powered by an internal 9V battery—this further adds to its versatility when it is used as an r.f. “gain block”. In this role, it can be inserted into the signal line whenever the need arises.

Circuit

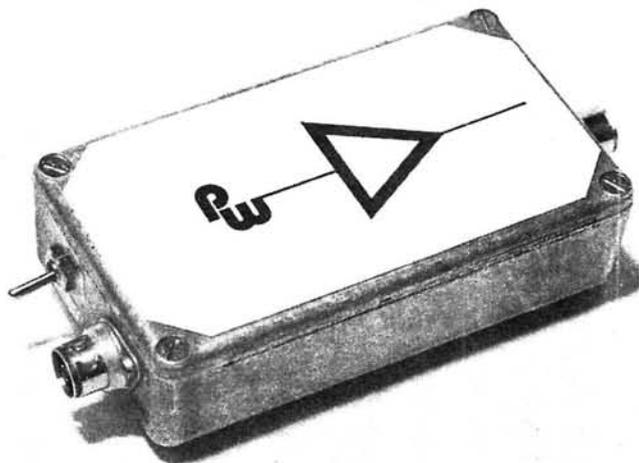The complete circuit of the device is shown in Fig. 1. The transistor is operated in the common-emitter mode; its base bias is made adjustable by means of VR1. A relatively low value of collector load resistor is employed



and this, together with the very high transition frequency (2GHz at 10mA collector current) of the specified transistor, ensures a flat response over a very wide frequency range. Signals are capacitively coupled into and out of the stage; the values of coupling capacitor were chosen so that low frequency roll-off occurs at approximately 200kHz.

★ specification

Amateur Band Performance

Frequency (MHz) Gain (dB)

1.8	
3.5	22
7	
14	
21	21.5
28	21
70	19.5
144	17

Input Impedance

250Ω (measured at 10MHz)

Output Impedance

400Ω (measured at 10MHz)

Gain

20dB over the range 200kHz to 50MHz
10dB over the range 30kHz to 200MHz
(measured with 50Ω source and load impedances)

Minimum Source and Load Impedance


50Ω

Power Requirements

9V at 17.5mA (typical)

Construction

With the exception of the coaxial sockets, battery and switch, all the components are mounted on a small printed circuit board; the copper track pattern and component layout are shown in Fig. 2. Constructors are strongly advised to follow the recommended p.c.b. layout as the performance at high frequencies (50MHz and upwards) largely depends upon the stray reactances present in the circuit. If the layout is not used then it is most important to

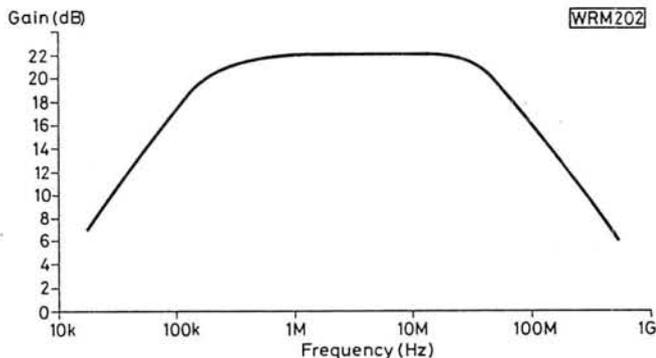

Frequency response

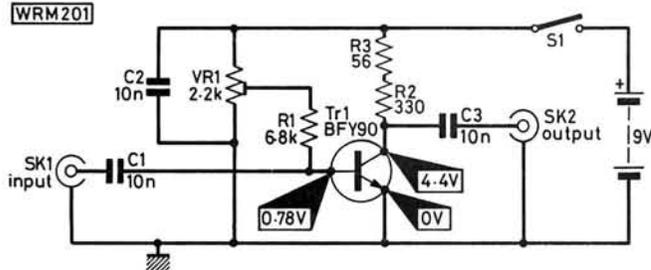


Fig. 1: Circuit diagram. Note that the top end of C2 should go to the junction of R2/R3, not to +9V as shown

keep the wiring as neat and compact as possible, and to ensure that an adequate earth plane (e.g., copper foil or tinplate) is used for all common earth connections. Take care to insert the transistor correctly and to cut the lead-wires as short as possible (about 2.5mm); the object is to mount Tr1 so that its underside is flush with the surface of the p.c.b.

The circuit board is mounted in a diecast or aluminium box using four short threaded spacers—these should be of metal in order to ensure an effective earth connection to the case. The input connection should be taken directly from the input socket (SK1) and a short length of coaxial cable (miniature 50Ω) should be used to link the p.c.b. to the output socket (SK2). The choice of type of socket is left to the individual constructor as it must obviously be compatible with the rest of his equipment. Suitable types are 50Ω BNC, "UHF" (SO239) or standard Belling-Lee sockets.

The PP3 or similar type of battery should be housed inside the box adjacent to the p.c.b. and may be retained by means of a small aluminium bracket. For the electrical connection, use a snap-fit battery connector.

Initial Checks and Use

Having carefully inspected the printed circuit board and its associated wiring, connect the battery, switch on and measure the supply current which should be 10–20mA. If this is not the case, adjust VR1 until 15mA is being drawn from the battery. Now connect the pre-amplifier into the coaxial line between aerial and receiver and then tune to a steady carrier between 5 and 15MHz. Adjust VR1 for maximum indication on the receiver's signal-strength meter and then repeat the procedure at v.h.f. (a receiver for the 144MHz band would be ideal for this purpose), once more adjusting VR1 for maximum "S" meter indication. The wideband r.f. pre-amp. is now ready for use.

It is recommended that the device is used only with screened coaxial input and output leads. It is also worth noting that when the pre-amplifier is used in an unmatched system, it is important to keep the lengths of coaxial cable to a minimum.

Fig. 2: Copper pattern and component layout, shown full size



★ components

Resistors

$\frac{1}{3}$ W 5% Carbon film

56Ω	1	R3
330Ω	1	R2
6.8kΩ	1	R1

Capacitors

10nF	3	C1,2,3
------	---	--------

Transistor

BFY90	1	Tr1*
-------	---	------



Potentiometer

Horizontal mounting, sub-miniature pre-set		
2.2kΩ	1	VR1

Miscellaneous

Coaxial sockets (2) to suit individual preference; sub-miniature toggle switch s.p.s.t. or s.p.d.t.; printed circuit board; snap-fit battery connector for PP3 battery; diecast aluminium box; 6BA threaded spacer (4) 6mm long.

* Available from Marshalls, R.S.T., etc.

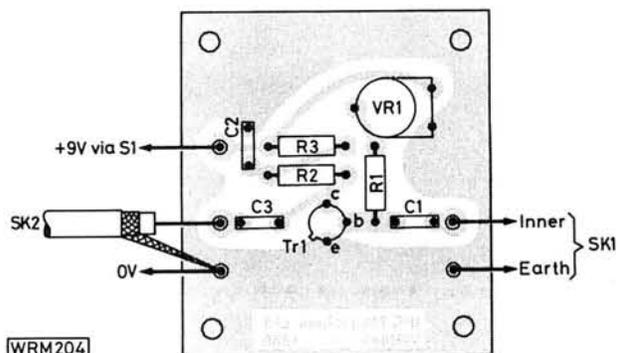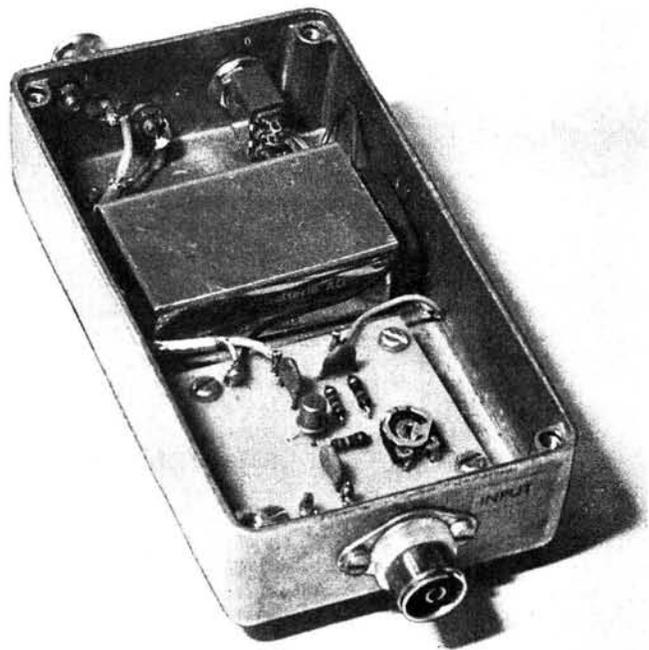

PRODUCTION LINES

alan martin

New Kits

Suretron Systems (UK) Ltd. announce the availability, in kit form, of two proven-quality electronic ignition systems. Called the Surefire C300 and ES200, they are suitable for vehicles with up to eight cylinders.

The C300 is a high energy capacitive discharge system incorporating a high output short-circuit-proof inverter, pulse processor circuit (overcomes contact-breaker problems) and transient overload protection. Available in negative and positive earth versions with coil ignition. Ideal for fuel injection, sports carburation, oily engines and two strokes.


The ES200 is a high performance inductive discharge system incorporating a selected output Darlington, electronic variable dwell circuit to maximise spark energy at all engine speeds, pulse processor circuit, coil governor to protect the coil and produces a long-burn output that is suitable for all negative earth cars.

The kits comprise an anodised extruded aluminium case, p.c.b., static

timing light, p.c. mounted security changeover switch, selected power semiconductors, capacitors, resistors, in fact everything down to the last nut and bolt and fully illustrated instructions.

The prices which include VAT and P&P are: ES200-£13.95 and the C300-£17.95. A special introductory offer of £2.00 off is available now.

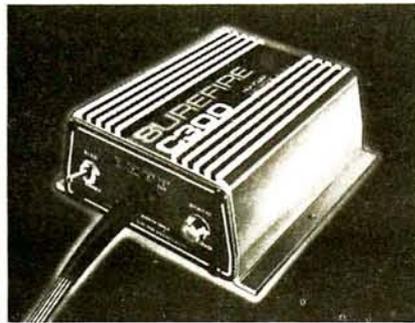Further details from: *Suretron Systems (UK) Ltd., Piccadilly Place, London Road, Bath BA1 6PW. Tel: (0225) 23194/313846.*



Voltage tester

The "Universal Voltage Tester ABO70", is designed to detect voltages between 4.5V and 380V without switching. It indicates the polarity of d.c. voltages by the illumination of an l.e.d. against positive or negative symbols, alternate flashing of the l.e.d.s indicate a.c. voltages. The tester requires up to 1.5mA to operate and has a response time of 3ms.

Ideal for many applications in the telecommunications, R & D, automotive and servicing industries, the tester costs £4.50 (excluding VAT) and is available from: *Verspeed, Barton Park Industrial Estate, Eastleigh, Hampshire SO5 5RR. Tel: (0703) 618525.*

Light Show

Using the latest developments in CMOS and Schottky Bipolar integrated circuitry, TUAC introduce the "Starchaser 4000", a programmable, four-channel—750W per channel—sound-to-light system.

The Starchaser 4000 initially provides 16 distinctive and varied patterns selectable by four switches, which form the basis. A further five additional effects switches allow the operator the scope to obtain over 1000 different patterns and effects.


Automatic gain control (a.g.c.) is a standard feature, and zero reference triac firing is incorporated to eliminate all interference. Smooth operating sliders ensure accurate control settings, and l.e.d. panel indicators enable the user to instantly determine each programme selected.

Additional features include a master dimmer control, speed control and crossfade which allows each channel light to brighten and dim at a con-

trolled rate, producing a merging effect, a short-on-time facility reduces the lamp-on time of any channel during sequencing, producing a simulated strobe effect.

The Starchaser 4000 measures 330 x 150 x 100mm, weighs 2.3kg (5lb), costs £99.00 inc. VAT and carries a full 12 month guarantee.

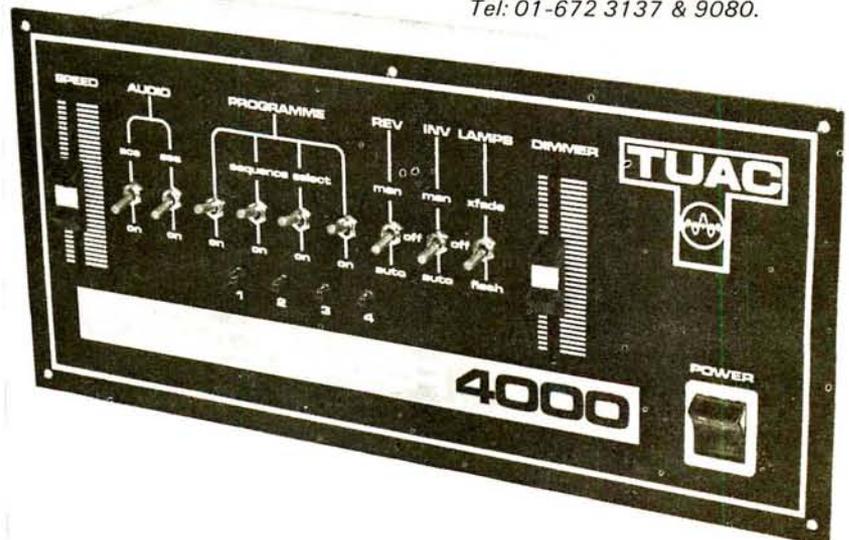Further details from: *TUAC, 119 Charlmont Road, London SW17 9AB. Tel: 01-672 3137 & 9080.*




Test Equipment

Maclin-Zand Electronics Ltd. offer two test instruments, the OPTO-7000 miniature 600MHz digital frequency meter and the M-1200B digital multimeter.

General specification of the OPTO-7000 includes: Two switch-selectable frequency ranges; Range 1, 10Hz to 60MHz and Range 2, 10 to 600MHz. Input impedance; (Range 1) 1M Ω shunted by 20pF and (Range 2) 50 Ω . Input protection; 100V up to 10MHz, 50V up to 60MHz and 2V max. Gate sampling time; (Range 1) 100 milliseconds, (Range 2) 1 second. Resolution; (Range 1) 10Hz and (Range 2) 100Hz. Sensitivity; (Range 1) <10mV, (Range 2) <75mV. Counter accuracy; ± 1 count, dependent on temperature stability and ageing. The display incorporates seven 10mm (0.4in) red l.e.d.s and the decimal point is autoranging on both ranges. Power requirement is 7.5 to 15V a.c./d.c. at 1.5W, with optional four AA size Ni-Cad batteries and constant current charger. Weighing 14oz the OPTO-7000 measures 130 x 108 x 32mm and costs £120 plus VAT and £3 P&P.

General specification of the M-1200B includes: Five d.c. and five a.c. volt ranges between 200mV and 100V. Four d.c. and four a.c. current ranges between 2mA and 2A. Accuracy over d.c. ranges 1% ± 1 digit, resolution 100 μ V and 1 μ A with overload protection of 100V max. on volt ranges and 2A fuse and diodes on current ranges. Accuracy over a.c. ranges 1.5% ± 2 digits, resolution 100 μ V and 1 μ A with overload of 600V on the 200mV scale, 1000V max. and 2A fuse and diodes on current ranges. Resistance is measured over six ranges between 20 Ω and 20M Ω , accuracy is 1% and resolution 0.01 Ω . The M-1200B is powered by four HP11 batteries with provision for a 6-9V d.c. adaptor. Weighing 2 $\frac{1}{4}$ lb and measuring overall 210 x 146 x 57mm, the M-1200B costs £55 plus VAT and £3 P&P.

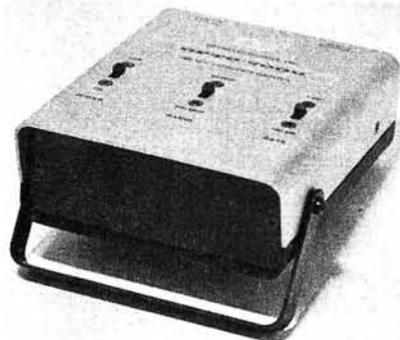Both units are available from: *Maclin-Zand Electronics Ltd., 38 Mount Pleasant, London WC1X 0AP. Tel: 01-837 1165.*




Low-Cost Mini-Scope

The Safgan ST-45 is a single trace oscilloscope with 5MHz bandwidth, 10mV/division sensitivity and a fairly large display area of 80 x 64mm with a graticule ruling of 10 x 8 divisions. The vertical amplifier which has 1M Ω plus approx. 22pF input impedance uses an f.e.t. input stage followed by stages consisting of transistor arrays in order to achieve minimal drift of trace with temperature changes. Overall amplifier bandwidth is close to 6MHz (although it is specified at 5MHz) with good pulse response characteristics. Input attenuator stages are set for best pulse shapes and has $\pm 5\%$ accuracy on all ranges. 50 Ω input impedance attenuator settings are useful for r.f. work. Overall timebase speed range from 250ms/div to 200ns/div including multiplier and $\times 5$ expansion facilities; all timebase speeds are calibrated to $\pm 5\%$ accuracy. External X-sensitivity is 1V/div with 500kHz bandwidth. The trigger system offers solid triggering below 0.5 div for internal and 100mV for external modes for a wide range of frequencies and incorporates an auto bright line facility. Trigger level and +ve, -ve slope selection on both internal and external trigger modes is incorporated. The c.r.t. is a 1.5kV mono-accelerator made by the Thorn



Brimar Group and has a very bright, clear, well defined display even at the fastest sweep speed of 200ns/div. The instrument is mains powered with a power consumption of approx. 10 watts. Overall dimensions of the black p.v.c. finished aluminium case are 216 x 165 x 280mm deep and the cream-white front panel is silk-screened with black annotations.

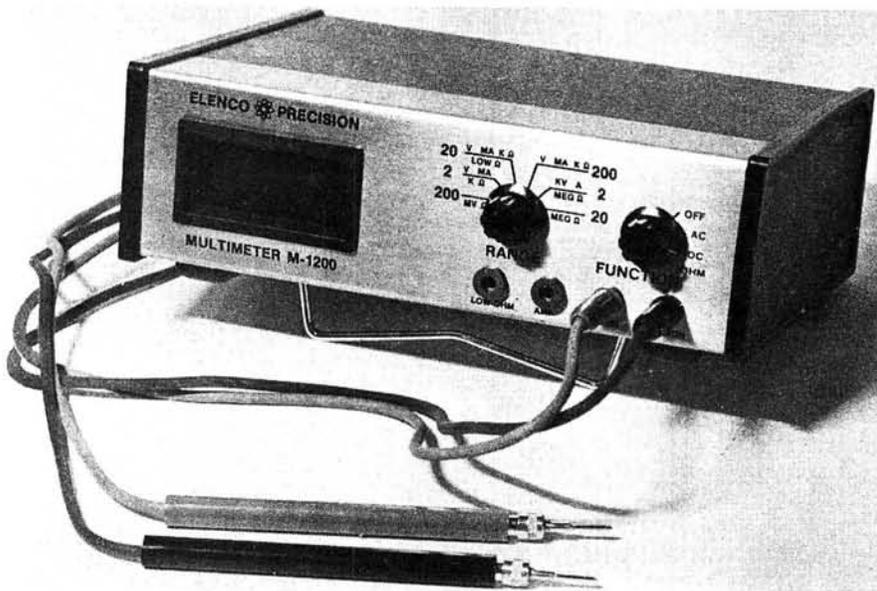The ST-45 costs £125 plus VAT and is available from: *Safgan Electronics Ltd., 56 Bishops Wood, St John's, Woking, Surrey GU21 3QB. Tel: (04862) 66836.*



Above shows the M-1200B digital multimeter and left the OPTO-7000 digital frequency meter

If you please

Would readers kindly mention "Production Lines", when applying to manufacturers or suppliers featured on these pages.

QSL Cards

Since the introduction of the "PW QSL Cards" service for the radio amateur and short wave listener, the service has proved to be highly successful. For details and order coupon, see page 67.

May I also take this opportunity to wish all our readers a very happy Xmas and a prosperous 1980.

SPECIAL PRODUCT REPORT



FM 2016E 2m FM Digital Synthesized Transceiver



With the vast amount of fully synthesised 2-metre transceivers on the market today, the amateur contemplating the purchase of such an item has to ask himself the following questions:

1. What can I afford?
2. Is the price indicative of the performance and quality?
3. Am I going to buy something which will give me years of service?

A fairly recent arrival on the scene is the FM-2016E from Kyokuto Denshi Kaisha Ltd. (KDK for short). From the gen given in the adverts, this looks a very interesting rig, offering a lot of facilities at a reasonable price, but not too much seems to have been heard of it. So, we thought we would give it a trial.

Obviously, the most important part of any synthesised rig is the synthesiser, so the examination began there. The CMOS unit provides a good, clean and pure f.m. signal. The receiver uses dual-gate MOSFETS for the r.f. amplifier and first mixer, providing superior intermodulation and cross-modulation characteristics as well as excellent sensitivity. An all-electronic tuning circuit using varicap diodes tracks the receiver front-end throughout the frequency range. Selectivity is provided by a crystal filter in the first i.f. and a ceramic filter in the second i.f. A ceramic discriminator is used to provide greater temperature stability and long-term stability. Adjustment of the received frequency by the RIT (Receiver Incremental Tuning) control is by varicap in the second local oscillator.

The transmitter is of the single conversion type, employing a balanced mixer. Five stages of electronic tuning, similar to that employed in the receiver, plus a four-stage low-pass filter in the transmitter output, results in a very clean f.m. signal. Modulation is by direct varicap control of the v.c.o. in the synthesiser. The transmitter is very tolerant of mismatched loads, and will stand up to an infinite v.s.w.r. The output transistor is a new silicon device, the 2SC1729.

Under normal mobile conditions, the FM-2016E proved to be a very exciting rig to use. The front panel of the set has eleven easily accessible controls which, after a short while, can be operated without even looking. This is, of course, exactly what you want for safe driving and easy operation. If

you're thinking "I want a rig I can use as a base station as well as a mobile", don't worry—this little fellow has all you could look for in an f.m. transceiver for either application.

Facilities

Probably the best way of conveying the facilities offered is by a brief run-down on the functions of the front-panel controls. First, the top row, running from left to right.

1. High Power/Off/Low Power. Switches the set on and off and selects transmitter power level by varying the gain of a buffer stage. Measured power output of the evaluation model was 19.2W and 1.9W respectively.

2. Tone/Off/RF Attenuator. With the switch in the up position, pressing the microphone p.t.t. gives 0.5s of 1750Hz tone for repeater access. In the down position, the gain of the receiver r.f. amplifier stage is reduced by 10dB, for protection against strong signals.

3. Close/Off/Open. This switch allows the scanner to look for either a busy channel or a free channel, at will. Once a channel has been found, setting this switch to off allows it to be held indefinitely.

4. Digital Readout of Frequency/Tx-Rx Indicators. Two l.e.d.s show transceiver status. The Rx Indicator is lit only if the incoming signal is strong enough to open the squelch.

5. Main Tuning Knobs. Concentric selectors for 100kHz and 10kHz steps. End stops allow the frequency to be set by counting "clicks", rather than having to look at the display when on the road (see also "9").

6. Meter. This has three functions, selected by a push-pull switch combined with the RIT control below it (see "7"). On receive, the meter can be either an "S" meter, or a discriminator, allowing accurate tuning by means of the RIT control. On transmit, the meter gives an indication of output power.

Now we move on to the bottom row, starting at the right-hand end.

7. RIT Control/Meter Control. This has been covered under "6" above. The range of the RIT control is approximately ± 5 kHz.



KYOKUTO

KYOKUTO DENSHI COMPANY LIMITED



KDK FM2016E 2m FM DIGITAL SYNTHESIZED TRANSCEIVER



The KDK FM-2016E is a 12V DC two metre FM transceiver for mobile and base station use. It has been compactly designed with emphasis on maintenance and ease of use by using the latest CMOS IC digital PLL circuitry. Rx 144.000-148.995MHz and Tx 144.000-145.995MHz. Direct readout of operating frequencies by large size LEDs.

The most commonly used, 100kHz and 10kHz, switches are mounted coaxially. These will not go below the 0 or above 9 position facilitating frequency changing by feel only, for "eyes-on-the-road" motoring and use by those with impaired sight.

An electronic memory using CMOS RAMs (Random access memory ICs drawing only 25nA!) allows any four of the 1,000 channels to be written-in (stored) at a flick of a switch. An auto-charging back up NiCad battery maintains the RAMs contents after disconnection from the power.

The plus 600kHz and minus 600kHz positions of the mode switch provide for normal repeater operation. In position 1T-2R the set Tx's on the frequency in memory channel 1 and Rx's on memory channel 2 (likewise the 3T-4R position). This provides for non-standard shifts, and is also convenient for use in conjunction with up-converters.

The memory may be scanned in the "closed" mode, (the scanner will stop at the first channel in use) or in the 'open' mode, (stopping at the first empty channel). Scan-hold allows transmission immediately the scanner stops.

Dual-gate MOS-FETs are used for the RF and mixer to provide superior inter-modulation characteristics with high sensitivity. Performance is held constant across the wide frequency range covered, by automatic electronic tuning.

A monolithic crystal in the first IF and a commercial quality 15-pole ceramic filter in the 2nd IF provides extremely sharp selectivity. The 2nd IF is built with discrete components to keep stray coupling to a minimum and a ceramic discriminator has been adopted for excellent temperature stability and long-term alignment.

The RIT (Receiver incremental tuning) and centre zero meter for contacts with off-frequency or drifting stations.

The single conversion transmitter uses a balanced mixer, five stages of electronic tuning, and a four-stage low pass filter for a clean, spurious-free signal.

The ultra-modern silicon transistor in the final will survive even on infinite VSWR.

Power: HIGH (15 Watts) and LOW.

Direct FM of the VCO results in superb audio.

A two mode (burst or continuous) tone generator is adjustable from 1,750 to sub-audible frequencies.

A 5-pin "DIN" connector is provided on the rear panel for a KDK SC-12A SELCALL (tone encoder-decoder) unit, headset-microphone combinations or similar.

The 2016E is supplied with microphone, mounting bracket, leads, and an excellent handbook.

£250 inc. VAT at 15% (SEE ONE TODAY)

In addition to offering an enormous range of major communications equipment, masts and antennas SMC are proud to be your single stop source for all those necessary but often hard to get accessories. Why not call us for details of our range. 30p in stamps brings a 24

page stock/price list, catalogues etc. Personal callers are welcome at any branch. Mail orders - c.w.o. please. Telephone orders - quote your access or visa card number. Hire purchase - speedily and discreetly transacted.



SOUTH MIDLANDS COMMUNICATIONS LIMITED

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND

Tel: Totton (0703) 867333, Telex: 477351 SMCMM G, Telegram: "Aerial" Southampton

S.M.C. (Jack Tweedy) LTD

Roger Baines, G3YBO
79 Chatsworth Road,
Chesterfield, Derbyshire
Chesterfield (0246) 34982
9-6: Tuesday-Saturday

NORTHERN (Leeds) BRANCH

Colin Thomas, G3PSM
257 Otley Road,
Leeds 16, Yorkshire.
Leeds (0532) 782326
9-5: Mon-Wed & Fri-Sat.

S.M.C. (Jack Tweedy) LTD

Jack Tweedy, G 3ZY
150 Horncastle Road,
Woodhall Spa, Lincolnshire
Woodhall Spa (0526) 52793
9-5: Tuesday-Sat (+ appointments)



G3ZUL Brian Stourbridge (03843) 5917	GW3TMP Howarth Pontybodkin (035287) 846/324	GM8GEC Jack Edinburgh (031665) 2420
GW4GSW Alan Swansea (0792) 24140	G13KDR John Bangor (0247) 55162	G13WVY Mervyn Tandraee (0762) 84056

MAIL ORDER

AT BREDHURST ELECTRONICS

0444 THE HIGH STREET
400786 HANDCROSS SUSSEX

BARCLAYCARD ACCESS
INSTANT H.P. ●
PART EXCHANGE ●
ALL PRICES INCLUDE VAT -
CARRIAGE - INSURANCE

H.F. RECEIVERS

Lowe SRX 30	£179.00
Yaesu FRG 7	£213.00
Trio R1000	£299.00
Yaesu FRG 7000	£372.00
Trio R 820	£790.00

2 METRE FM RECEIVERS

Search 9	£59.00
FDK TM56B + scan	£106.00
Belcom AMR 217B + scan	£120.00
HF 12 Pocket	£79.95

MARINE VHF RECEIVERS

Search 9	£59.00
FDK TM 56B + scan	£115.00
Belcom AMR 217B + scan	£120.00
HF 12 Pocket	£79.95
SR 11 + scan	£87.00

AIR BAND RECEIVERS

Lowe AP 12	£120.00
SCC R517	£50.00
Waltham W144	£29.95

POPULAR ACCESSORIES

Jaybeam Antennas	P.O.A.
ASP Mobile Antenna	P.O.A.
Hygain H.F. Antenna	P.O.A.
G. Whip Mobile H.F. Antenna	P.O.A.
Microwave Modules	P.O.A.

SPECIAL OFFER

12v 3A cont. power supply	
5A surge fully protected	£19.50

R1000



NEW!
NEW!
NEW!
NEW!

ONLY **£299** inc. VAT & Carriage

The new R1000 general coverage receiver incorporates all the features you would expect on a high quality product from TRIO.

A PLL synthesiser covers 30 switch selected bands up to 30MHz with both digital and analogue tuner for ease of use.

Three IF filters match every mode - wide for AM with good tonal quality, narrow for DX work and custom designed for SSB communication.

Built in noise blanker to cut pulse type noise. Simple RF tuning without pre-selector. Band pass filters are automatically switched in on the MHz band switch.

Other features include built in digital clock, large speaker, RF attenuators, tone controls, recording jacks, multiple antenna inputs etc. etc.

Why not try this new receiver? It would look good on any bookshelf and out performs many receivers presently available.

To order any of the above items simply write to the above address or telephone 0444 400786, giving your address or Barclaycard number to ensure same day despatch.

REMEMBER 0444 400786

H.F. TRANSCEIVERS

Denton HF 200A	£399.00
Trio TS 120V	£408.00
Yaesu FT 7B	£430.00
Trio TS 120S	£495.00
Trio TS 520S	£542.00
Yaesu FT 101Z	£574.00
Yaesu FT 101ZD	£661.00
Trio TS 180S	£825.00
Trio TS 820S	£832.00

2 METRE F.M. MOBILES

ICOM IC 240	£193.00
FDK Multi 700E	£229.00
Trio TR 7600	£247.25
Yaesu FT 227R	£244.00
Trio TR 7625	£273.70
Yaesu FT 227 RBS	£295.00

2 METRE F.M. HANDHELDS

Yaesu FT 202 R	£99.00
FDK Palm II	£99.00
FDK Palmsizer	£159.00
Yaesu FT 207R	£199.00
AOR AR 240	£165
TRIO TR 2400	£P.O.A.

2 METRE MULTIMODES

ICOM IC 245E	£399.00
FDK Multi 3000	£519.00
Trio TS 770	P.O.A.
ICOM IC 211E	£549.00
Yaesu FT 225RD	£615.00

2 METRE SSB

Mizuho SB 2M	£165.00
Trio TR 7010	£193.00
ICOM IC 202S	£199.00



IF YOU ARE INTERESTED IN

AMATEUR RADIO

AND LIVE IN OR NEAR KENT

WHY NOT COME AND VISIT US

(or Phone us for a copy of our Catalogue)

WE STOCK

TRANSCEIVERS POCKET RECEIVERS
BOOKS RECEIVERS POWER SUPPLIES
ROTATORS AERIALS

FOR

AMATEUR, MARINE & PRIVATE MOBILE RADIO

THANET ELECTRONICS

143 RECVLVER ROAD, HERNE BAY, KENT

Tel: (02273) 63859

Telex: 965179



... the sign of fine communications

SRX30 SWL RECEIVER £178.00

(plus £4.50 Securicor Delivery)

TRIO EQUIPMENT

	Price inc. VAT	Carr
	£	£
R1000 SLL	298.00	4.50
R820	790.00	4.50
YG455C	81.50	.50
YG455CN	89.00	.50
SP820	39.00	1.50
HS5	23.50	.75
HS4	10.75	.75
VHF AMATEUR RECEIVERS		
SR9	48.00	.86
AMR217B	120.75	1.50
ROTATORS, TUNERS & SWITCHES		
AR40	54.63	£4.50
FU200	40.39	£4.50
CL22	16.10	.75
CX3	7.20	.50
DAIWA	11.98	.50
KW SWL	14.80	.50
AIR BAND RECEIVERS		
FX-213-AU	16.00	1.00
SHARP		
LOWE AP12	118.45	1.00
	12.95	1.00

All prices include new VAT rate

Buy by post or phone your Barclay Card or Access number.

Alternatively, call in for a chat. The shop is just 10 minutes from Leeds City Station, and there's easy parking if you travel by car * Instant H.P. for licenced Amateurs * Extended Credit Terms Available * Send 50p for Catalogue and Price List.



LEEDS AMATEUR RADIO
27 Cookridge Street,
Leeds. W. Yorks. Tel. 452657

LOWE TRIO DISTRIBUTOR



LAR are area distributors for Jay Beams, Antenna Specialists, HiIomast ICOM and Microwave Modules Products.

8. Write/Off. When this switch is moved to the "Write" position, the frequency selected on the tuning knobs will be written into memory. If a memory channel is selected by the switch "11", the previous frequency stored in that position will be over-written. If a memory channel is not selected, the new frequency will be automatically stored in channel 4.

This is a very attractive feature of the rig. Suppose you're driving through an area and tuning around, and come across the local "natter" channel. A quick flick to "Write" will store it in position 4 ready for use on your return journey, without having to make any other adjustments.

The selected frequency data is stored in CMOS RAMs (random access memories), which are powered by a nickel cadmium battery when the transceiver is disconnected from the external power supply. Consumption from the battery is around 25nA (yes, nano-amperes) and the battery is kept charged whenever the rig is in use.

9. 5 Up/Off. This allows the units kHz digit of the selected frequency to be set to 0 or 5.

10. 144/145/146/147/148MHz. This is obviously the band selector switch, but be careful. Although the transmitter is limited to 144-145.995MHz, by switching to +600kHz on the Mode switch (see "12"), you could transmit out of band without realising it. The next thing you'll know, the man from the Home Office could be knocking on your door.

11. Off/1/2/3/4/Scan. This is the Memory switch, allowing you to store and recall your four favourite frequencies,

★ specification



Frequency Coverage:	144.000-148.995MHz (receive) 144.000-145.995MHz (transmit)
Memory:	4 channels
Scanning:	Scanning of 4 memory channels for open and closed channels
Frequency Stability:	Better than $\pm 0.002\%$
Useable Temperature Range:	-20° to +60°C
Power Source:	13.8V d.c. $\pm 10\%$, negative earth
Aerial Impedance:	50 Ω nominal, unbalanced
Current Consumption:	Less than 0.6A (receive) Less than 3A for 15W (transmit) Less than 1.3A for 1W (transmit)
Dimensions:	180 x 60 x 195mm
Weight:	2.5kg

TRANSMITTER

Power Output:	15W (HIGH), 1W (LOW)
Emission:	F3 (direct varicap f.m. of v.c.o.)
Deviation:	± 5 kHz (factory set)
Spurious Emissions:	More than 60dB below carrier
Microphone:	600 Ω dynamic with p.t.t.
Repeater Tone:	1750Hz, continuous or tone-burst

RECEIVER

Sensitivity:	Less than 1 μ V input for 30dB S/N Less than 0.25 μ V for 20dB quieting
Squelch Sensitivity:	Less than 0.2 μ V
Bandwidth:	± 8 kHz (6dB), ± 16 kHz (70dB)
Intermediate Frequencies:	16.9MHz (1st), 455kHz (2nd)
Image Rejection:	Better than 70dB
Audio Output:	More than 1.5W at 10% t.h.d.
Output Impedance:	8 Ω internal loudspeaker 4-8 Ω external loudspeaker

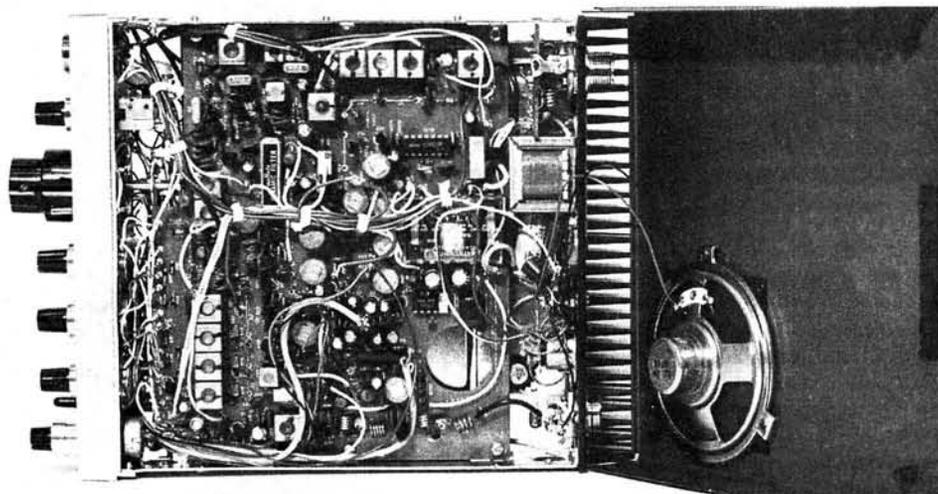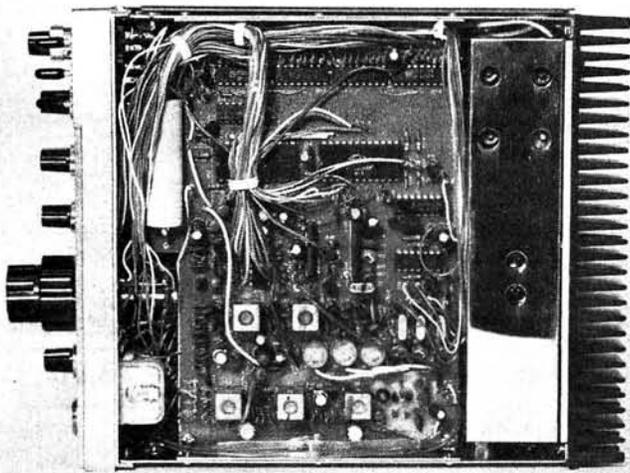

Top and bottom views of the FM2016E with covers removed. In use, some space is required under the set, for sound to escape from the loudspeaker

continued on page 66 ►►►

The Editor,
PRACTICAL WIRELESS,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG

CB in Germany

Sir: I read with interest the item concerning CB in the USA in *VHF Bands* in the August 1979 issue of *PW*, and am pleased to note that the seemingly controversial subject of CB is getting more of an airing in popular technical publications in England.

As an expatriate who has lived in Bavaria for the last six years, I have taken advantage of the privilege granted by the PTT in 1975 and installed a mobile CB set in my car and a fairly sophisticated base station at home. As you probably know, maximum output power is restricted to 500mW, 12-channels in the 27MHz band being set aside exclusively for CB. Directional antennae are forbidden, although ground plane elements are permitted with base stations.

Every "approved" transceiver has an FTZ number stamped somewhere on its chassis (Funk Technische Zulassungstelle Pruf Nummer), indicating that the design has been checked and approved by the appropriate government authorities. I say "approved" transceivers, because it is easy to buy a Japanese or American imported set which does not comply with the emission regulations, i.e., 4W, 40-channel, and of late a very sophisticated 18W, 120-channel s.s.b. job. "After-burners" ("add-on" power amplifiers) are also available, capable of increasing a 500mW to some 20W or more. It is not known whether legislation is in the pipeline to block the import and sale of this equipment.

When one purchases an approved apparatus for use in the car, a set of rules and regulations (a commodity for which the Germans are noted!), an FTZ certificate corresponding to the set purchased, and a licence granting the purchaser permission to use the equipment in accordance with the regulations, is included. These documents must be kept with the car papers, and may be inspected together with the set at any time by a policeman or any authorised agent for the PTT. The latter are also empowered to carry out tests on the equipment to ascertain whether any "modifications" have been incorporated. There is no licence or registration fee for mobile installations.

Operators of home stations however, must register with the Post and Telecommunications authority and pay a monthly fee of DM15.00 (about £4). Call signs (or more precisely, call names) are either dreamed up by the operator or allocated by the PTT, where several "Tweeties" or "Bushy Bears" might cause confusion.

As with most privileges granted by any authority, there are regrettably those who abuse them as well as those who avail themselves of the opportunity in a responsible manner. No one would deny that Germany has its quota (albeit tiny when compared with the majority) of rogue CBers. There are those, for example, who squirt 18 watts of r.f. down a transmission line, oblivious of output transistor parameters, s.w.r.s, etc., but since this invariably results in TVI and breakthrough on approved sets operated by the serious CBER, they don't operate for long, at least in our area!

It seems to me that there are three distinct "types" of CBERs: the 120-channel, 18W cowboys (a tiny minority); the CBER who uses his (or her) set as an extension to the telephone—particularly useful for the house-bound or for invalids—for old people living on their own, and as your own correspondent John Keegan mentioned, in an emergency on the highway, especially at night; and finally, there is the chap who is considering amateur radio as a hobby, but for the moment content to carry out experiments in propagation using very low power equipment. I for one, enjoy this aspect of the hobby, particularly as my QTH is in a valley surrounded by mountains, buildings and forests, and "getting out" is sometimes a real challenge.

In conclusion, it must be significant that in this area alone, the number of applications to sit the German radio amateurs' examination has tripled in the last four years. The local education committee is running for the first time two RAE courses at the nearby Hochschule. I shall be enrolling this week.

So I would say to all anti-CBERs: accept the fact that CB is here to stay, and it will certainly come to England. Better to have a properly controlled CB facility available to those who can show they'll use it responsibly, than illegally imported sets, illegally and irresponsibly operated.

"Bird Dog"
V. A. Sancto
Miesbach
West Germany

Pen-Pals

Sir: I am very interested in radio and would dearly like to correspond with someone in Great Britain, whose interests include amateur radio.

Marc de Moor-Vulsteke,
Vredestraat 13,
B-9720 de Pinte,
Belgium

Sir: I am a regular reader of *Practical Wireless* and would like to correspond with other readers, with the object of exchanging ideas, books, circuits, etc.

Sam Hosenbocus
11 Claremont Grove
Leeds
LS3 1AX

?????

Sir: I wonder if any of your readers could settle a difference of opinion between two "old timers"?

I remember one cold and wet December evening in 1929, 30, 31?, when my brother and I walked into our local radio shop, with the current issue of *Popular Wireless* to purchase the parts to build the *Popular Wireless* "Super Quad".

The Question is was the design by the late John Scott-Taggart and what was the date of the issue in which it was published?

R. Roebuck,
19 Park Road,
Ashley,
New Milton,
Hampshire

NEXT MONTH IN...

practical

WIRELESS

UPDATE

your




'PURBECK'

OSCILLOSCOPE

with our

DUAL TRACE UNIT

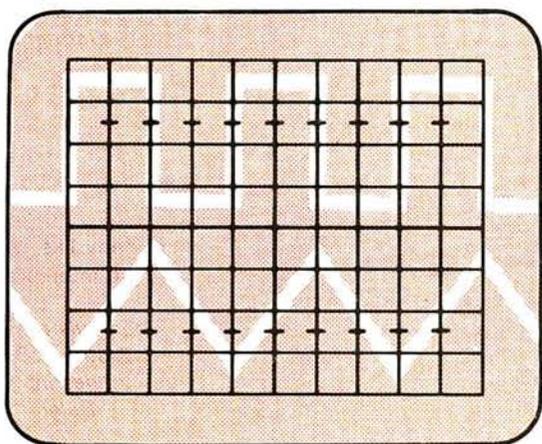Extend the versatility of your Purbeck by adding a second trace, with a choice of chopped or alternate modes. The unit can also double as a pre-amplifier with a gain of $\times 10$, and can be used with other 'scopes if a suitable power supply is available



Watch out for


PW NIMBUS

Modular 2-metre Transceiver System

It's Coming!



s.s.b.	base-station
hand-portable	crystal-controlled
	f. m.

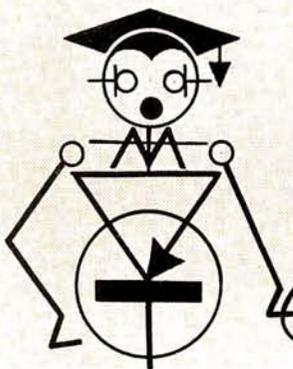

ELECTRONICS IN SCHOOLS

A look at some of the fascinating electronics projects being undertaken in schools today, in this case a logic tutor and an electrocardiograph

WINDSCREEN WIPER DELAY

A "universal" intermittent wipe with facility for multiple wipes when first switched on or when weather conditions demand

With any communication system it is important that the greatest amount of information is passed with the minimum amount of expense and effort. For some years the use of single sideband transmission has been a very popular method of achieving this aim, especially among Radio Amateurs, and it has proved to be a very efficient system in comparison with double sideband a.m. or f.m. transmission. Nevertheless, it is possible to improve the communication efficiency still further by "processing" the speech waveform before applying it to the transmitter.

In practice it is possible to obtain an effective increase in "talk power" equivalent to a tenfold increase in transmitter power—a 200W transmitter sounds like a 2kW one at the receiving end! When it is considered that this can actually be achieved without using bigger power supplies or final stages, but by using only a relatively simple speech processor, the advantage in cost alone is considerable.


This circuit is not "just another processor", but the result of much painstaking research into the reasons why some processors work and others do not. Many hours of testing prototypes and examining other methods of enhancing communication efficiency, have resulted in a device that is as effective as the best but remains simple to construct. As such, it does not incorporate any expensive components.

Response

The overall frequency response is one of the most significant parameters in any communication system. A study of s.s.b. transmitters in amateur use showed that, in general, the frequencies below 300Hz and above 3kHz are internally filtered out; there are slight differences between the various designs but 300Hz to 3kHz is the normal audio pass-band.

It may be considered that if a transmitter already possesses filters intended to tailor the response then no further filtering is required—nothing could be further from the truth and it is this misconception that causes so many designs to fail. It is of paramount importance, moreover, that the filtering in the processor is carried out in the correct sequence.

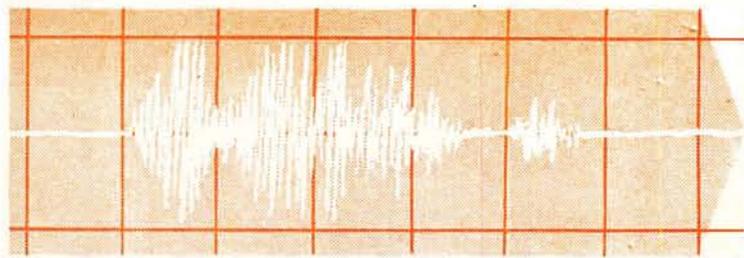In the circuit of the *PW* Speech Processor, frequencies



AF Speech Processor

E. A. RULE G3FEW

below 300Hz are removed before the limiter stage by an 18dB/octave filter so that the unwanted frequencies do not produce harmonics which would fall into the wanted 0.3–3kHz band. These harmonics would be produced by the limiter stage which, of course, is a non-linear device. If these lower frequencies were not removed, their harmonics would add considerably to the distortion in the final transmission thus wasting power. The frequencies above 3kHz are also removed, but after the limiter stage so that the harmonics produced from the 0.3–3kHz audio band are prevented from reaching the transmitter.

If they did reach the transmitter, all manner of nastiness would result, of course. Transmission bandwidth would be increased, interference would be caused to adjacent transmitters and so on. Now that the mean voltage of the audio signal has been stepped up by the processor action, the built-in filtering is no longer really able to cope. It would, of course, reduce the unwanted harmonics—but not by a sufficient amount and hence the filtering provided

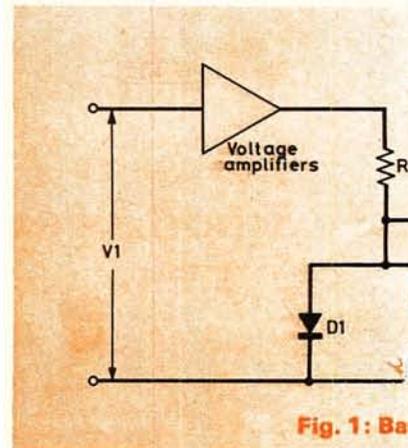
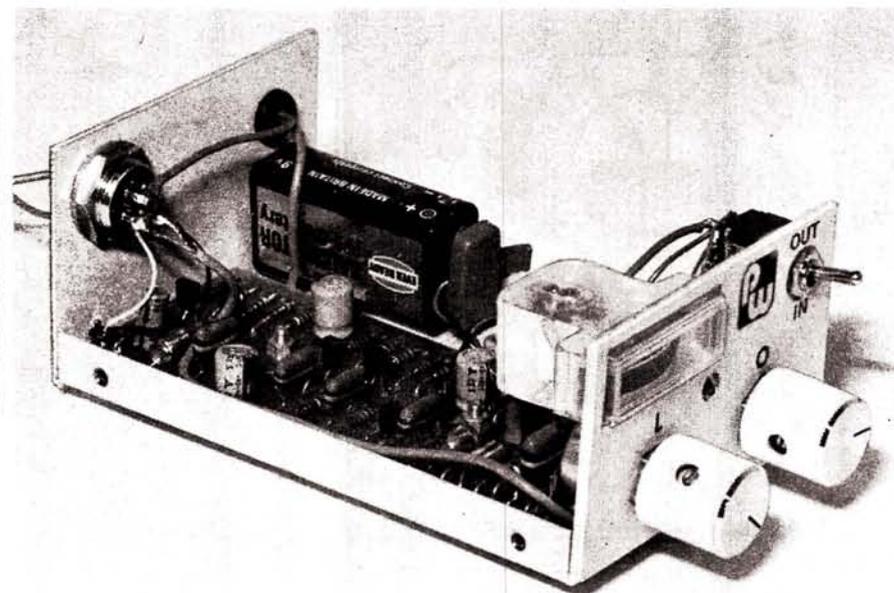


Fig. 1: Bas

Front view of the *PW* Speech Processor

Use of negative feedback and careful selection of transistor type has resulted in a total distortion of less than 0.1% before the limiter.

S/N Ratio


A very high signal-to-noise ratio is vital in any speech processor. A normal transmitter may have an overall S/N ratio of 40dB (the noise constitutes 1% of the total signal, in voltage terms), but if this same S/N ratio of 40dB applied to the processor also, however, the noise would only be 20dB down on the signal at the transmitter output (it would constitute 10% of the total transmitted signal). In practice, the situation would be worse as the existing noise in the transmitter would be added to the processor noise ($N_{io} = \sqrt{N_p^2 + N_t^2}$ where N_{io} = total noise, N_p = processor noise and N_t = transmitter noise).

For a 3mV input signal the pre-limiter stages of the *PW* design have a S/N ratio of 60dB—with the use of a high output microphone this figure can be further improved to 80dB. From this it can be seen that with 20dB of extra gain applied to the speech by the processor, the noise will still be more than 40dB down overall and can be ignored for all practical purposes, even when a low output microphone is being used (Fig. 2).

Basic Principle

The simple “block diagram” of the *PW* processor is shown in Fig. 1. If a silicon diode is fed from a high impedance source, then the voltage across the diode will follow an approximate log law relationship relative to the current through the resistance (R). Therefore the output voltage (V2) will have a log law relationship to the input voltage (V1); it is upon this relationship that the action of the device is based (Fig. 2).

Figure 3 shows the effect on a sine-wave signal as the input voltage is increased. Even with a 20dB gain applied, the signal is not being clipped, but has rounded edges. Figures 4(a)-(e) show the results obtained from the

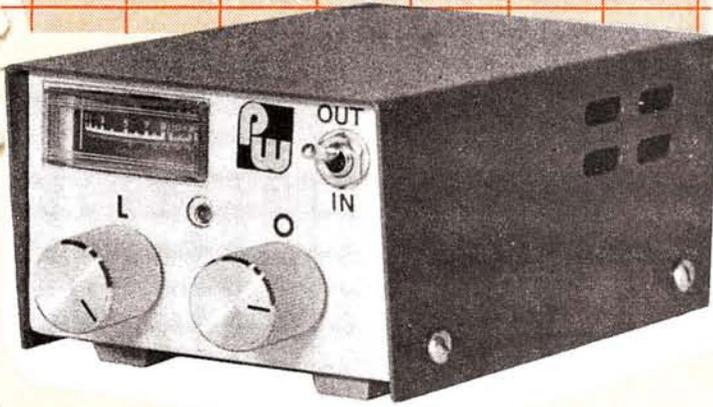


within the processor itself. Naturally, it is important that the filter used and the subsequent amplifying stages do not themselves introduce harmonics! Again, the final transmission would then occupy an excessive bandwidth.

The *PW* processor uses an active filter and any spurious products are of a very low order.


Distortion

This is another very significant parameter, of course. The main aim must be to keep the distortion in the audio signal applied to the processor to a minimum; any distortion present will be worsened by the limiter action. Similarly, the input stages of the device must be designed with low distortion in mind.

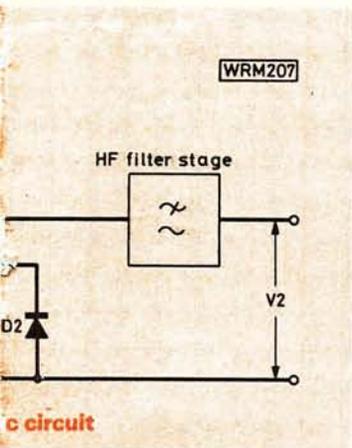Such stages are used throughout the *PW* Speech Processor and employ methods common to the hi-fi scene.



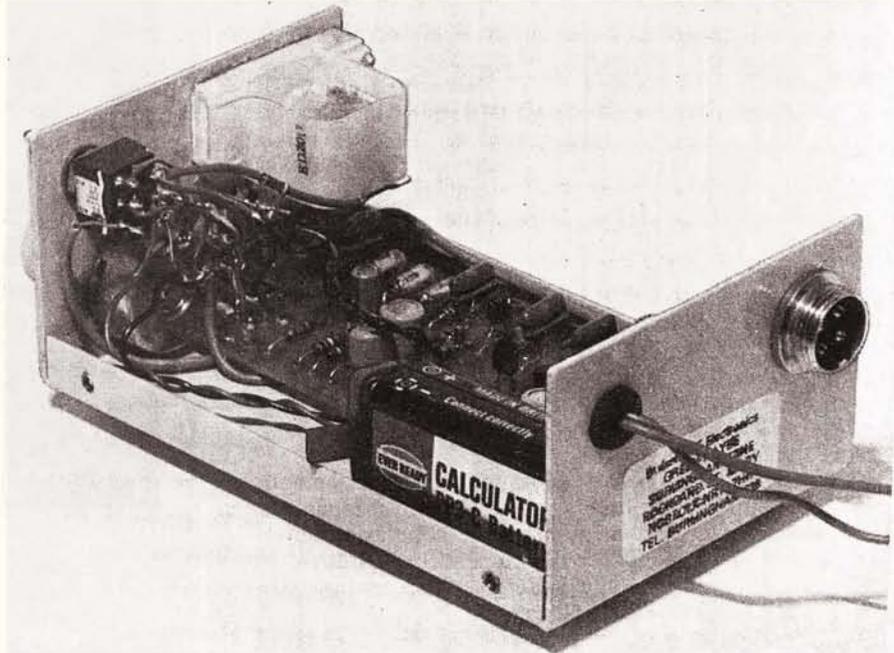Rear view: Note how R16 is connected between S1 and the meter



completed processor—the effects of the high frequency filter are quite plain. The output waveform, although distorted, is reasonably clean, simplifying the task of the built-in transmitter filter.

The photograph in Fig. 5 shows the effect of the processor on the word “Hello”. Note the spread above and below the main body of the trace—this consists mostly of wasted speech peaks which do not contribute anything to the readability of the transmission. The lower trace shows how these peaks have been removed after “processing” and how the mean signal voltage has been considerably increased.

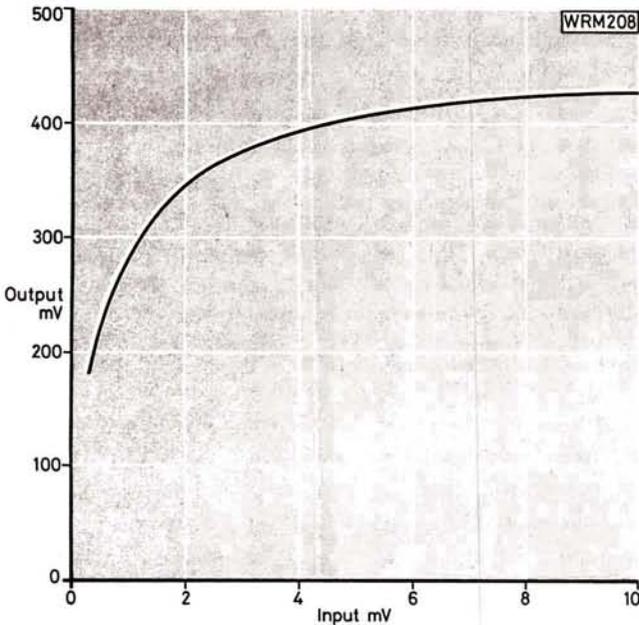


Fig. 2: The output signal voltage is progressively limited as the input voltage is increased

Circuit

The circuit diagram of the device is shown in Fig. 6. The microphone is connected via an r.f. filter C1/R1/C3 to the low-noise amplifier Tr1/Tr2. Negative feedback is applied to minimise distortion and to stabilise the d.c. bias conditions. The signal is then passed to Tr3 and Tr4 via VR1, the limiter gain control. Transistors Tr3 and Tr4 form a second low distortion amplifier with similar characteristics as Tr1/Tr2. The signal is now at an appropriate level for feeding to the limiter stage R14/D1/Tr5. Low frequency filtering is provided by the combined action of C5/VR1, C6/R11, C8/R14 and is aided by the small values of decoupling capacitor used in the emitter circuits of Tr2 and Tr4 (C4 and C7).

The limiter stage differs slightly from the basic form shown in Fig. 1. Resistor R14 forms the high impedance feed to the two diodes which consist of D1 and the base-emitter junction of Tr5. Substituting Tr5 for the “D2” shown in Fig. 1 makes it possible to connect an l.e.d. or moving coil meter (or both!) in series with its collector. This provides a good indication of the actual amount of processing being applied, for the current flow through the collector of Tr5 is roughly similar to the current flow through D1 and D2 in our elementary circuit (Fig. 1). A 100µA f.s.d. meter is capable of showing the full range of

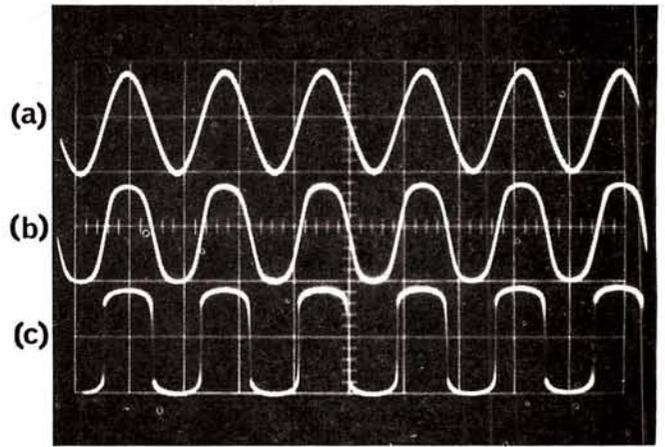


Fig. 3: Traces (a), (b) and (c) show the output wave shape of the basic circuit for inputs 0dB, 6dB and 20dB above the diode conduction point

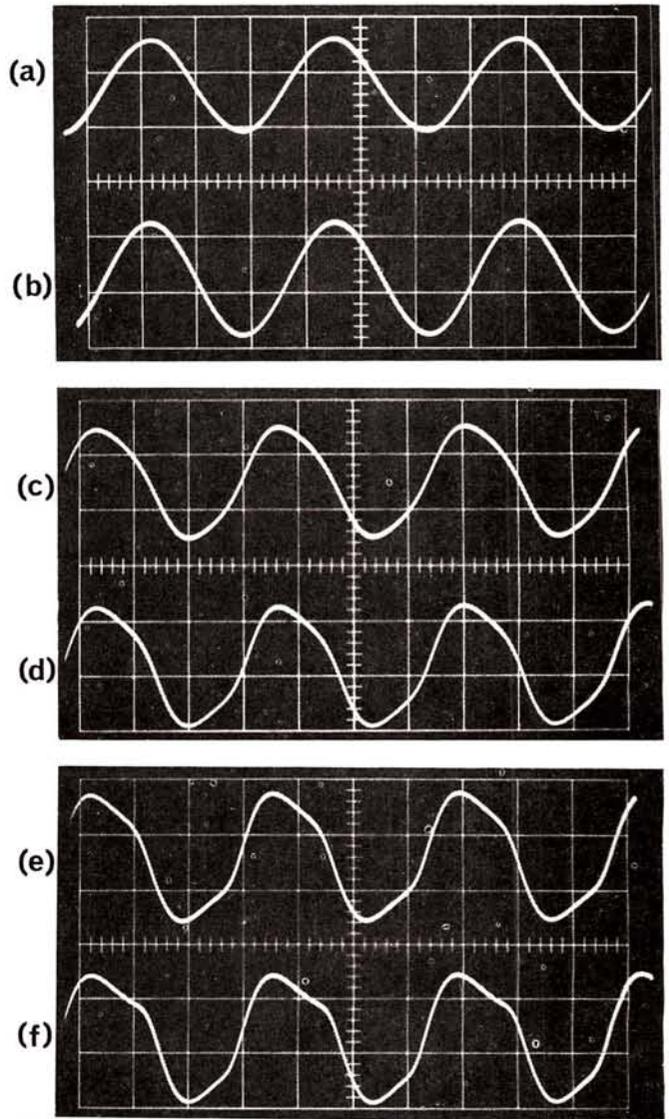


Fig. 4: The traces show the processor output for increasing input signal voltage. (a) and (b) are the outputs below and at the limiting threshold, (c)–(f) are those for inputs 6dB, 12dB, 18dB and 24dB above it

processing if connected as shown—from the threshold of limiting to the maximum practical level. If an i.e.d. is substituted for the meter, the range of indication is naturally not so sensitive.

From the limiter stage the signal is fed to the high frequency filter which consists of R17/R18/R19 and C12/C13/C14. Transistor Tr6 is "bootstrapped" to provide a high impedance input for the filter and to obtain a better slope; the component values have been selected to avoid "ringing". The combined response of both filters is shown in Fig. 7—the output is taken from the emitter circuit of Tr6 via the output level control, VR2.

Power Supply

The author used an internally mounted 9V PP3 battery, but it is suggested that, if possible, the supply voltage should be obtained from within the transmitter itself. A supply of 8–15V should be quite satisfactory but it should be well decoupled and a Zener diode (D2) used as a precaution against hum, etc. A suitable method of doing this is shown in the circuit diagram.

Setting Up

After connecting a microphone to the input of the processor and a transmitter to its output, the following method of setting up is suggested. Having switched the device out of circuit (S1), adjust the transmitter for the normal modulation level and then turn VR1 and VR2 to minimum. Switch the processor into circuit and, talking normally into the microphone, adjust VR1 until the i.e.d. or meter starts to indicate; the i.e.d. should flash only on speech peaks or, if you wired in a meter, its pointer should deflect to approximately two-thirds f.s.d.

Now adjust VR2 so that the transmitter is modulated to a suitable level—this will normally result in a higher reading than without the processor in circuit. Taking the FT200 as an example, normal modulation caused the meter to read 180mA; with the processor in circuit the p.a. meter hovered around the 400mA mark. Some trial and error may be needed in optimising the settings for a particular rig, but normally only VR2 will require adjustment.

A more precise method of setting up is to use an oscilloscope, if one is available. Connect the output of the

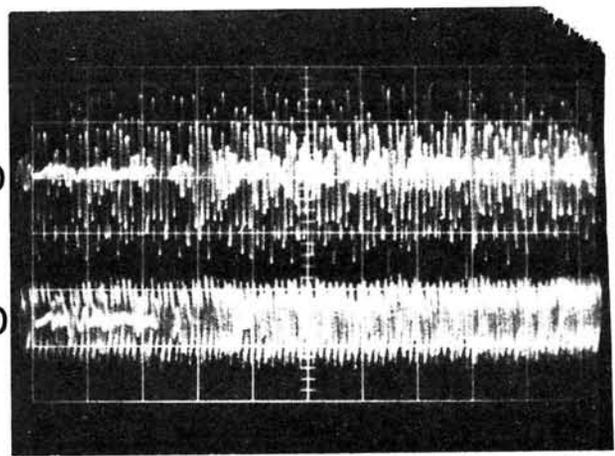


Fig. 5: The word "Hello" before and after processing

processor to the input of the 'scope and the microphone to the input of the processor. Now, with the processor switched out of circuit, speak into the microphone adjusting the sensitivity of the oscilloscope until the voice peaks can be seen. Note the level of these peaks for these represent the 100% modulation point in normal use with that particular microphone. Switch the device into circuit, turn the limiter control to maximum and then adjust the output control until the output is the same peak level as given by the microphone. Now reduce the limiter control until the meter is deflecting to about two-thirds f.s.d. The processor is now correctly set up for the microphone and transmitter in use (providing that these were being correctly used in the first place!).

Some readers may feel concerned about the effect of the extra audio on the p.a. dissipation of the transmitter. Tests carried out by the author on the p.a. of the FT200, using a temperature probe, showed no measurable increase in temperature provided that the p.a. was kept correctly tuned. In other words, be sure to re-tune after a change of transmitting frequency—after all, we do want as much of the power as possible to go into the aerial!

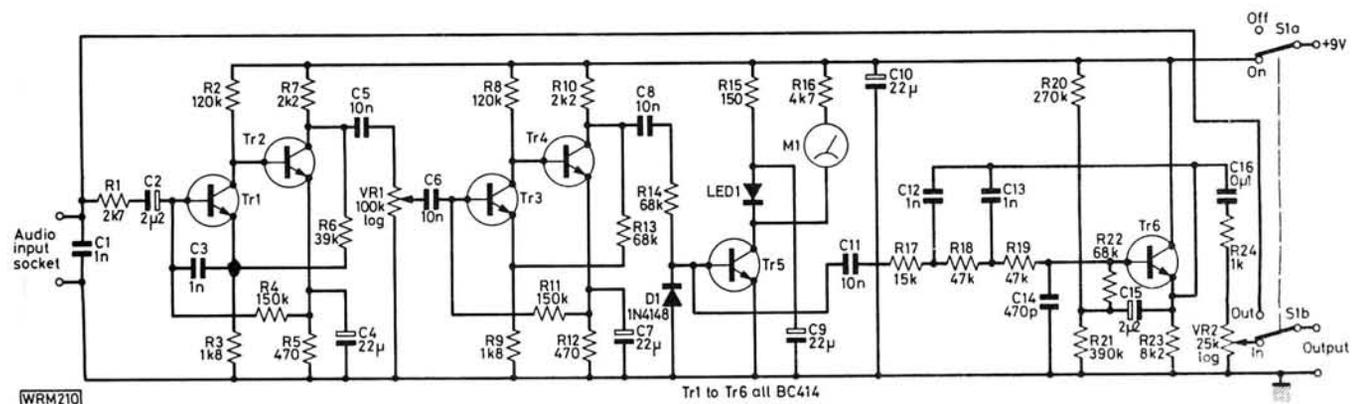
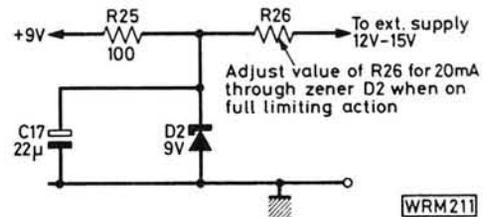


Fig. 6: Circuit diagram. Components R16, M1 and LED1 are not p.c.b. mounted

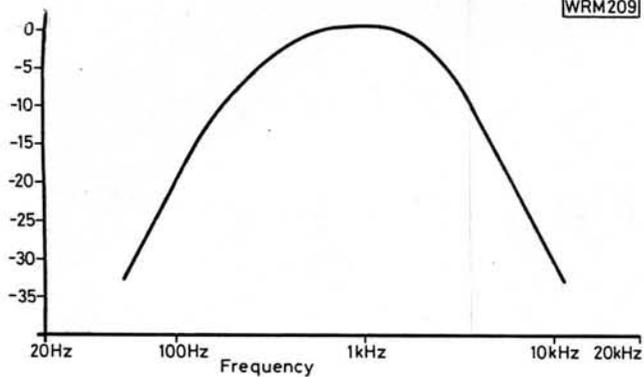


Fig. 7: Overall frequency response

Construction

The construction method will depend on the personal choice of the individual, naturally, and also to a certain extent on matching the style to that of his existing equipment. The final wiring layout is not critical as long as the p.c.b. is as shown in Fig. 9. An enclosed metal box *must* be used in order to prevent r.f. from getting into the processor wiring.

The author has made two versions of the device, one in a diecast box with pre-set controls (as it is always used with the same transmitter, no further adjustment was needed after the initial setting-up) and the other built into an RS Components metal box (Type 509-715—135 × 80 × 55mm). The drilling details are shown in Fig. 8. The dimensions of the meter cut-out will, of course, depend on the type used; therefore, none have been specified. The same applies to the audio input socket; this will depend on the type of microphone used.

The output leads are brought through a grommet at the rear and are terminated in a plug that is compatible with the constructor's transmitter. The dimensions that are given suit the listed components—if other types or larger components are used then it is suggested that a larger box would house the device more comfortably (for example, RS Type 509-967—179 × 97 × 74mm).

The p.c.b. is mounted on 6BA screws with a nut acting as a spacer between the p.c.b. and box. These screws are earthing points for the board and it is therefore important to obtain a good contact—using a lockwasher will assist here. The remainder of the wiring is straightforward and only the lead between the input and S1 needs to be screened.

All components are mounted on the p.c.b. except for C1 and R16. The value of R16 may need to be varied, in fact, to suit the particular type of meter used. Choose its value so that f.s.d. is indicated at the point where

[continued on page 54 ▶▶▶]

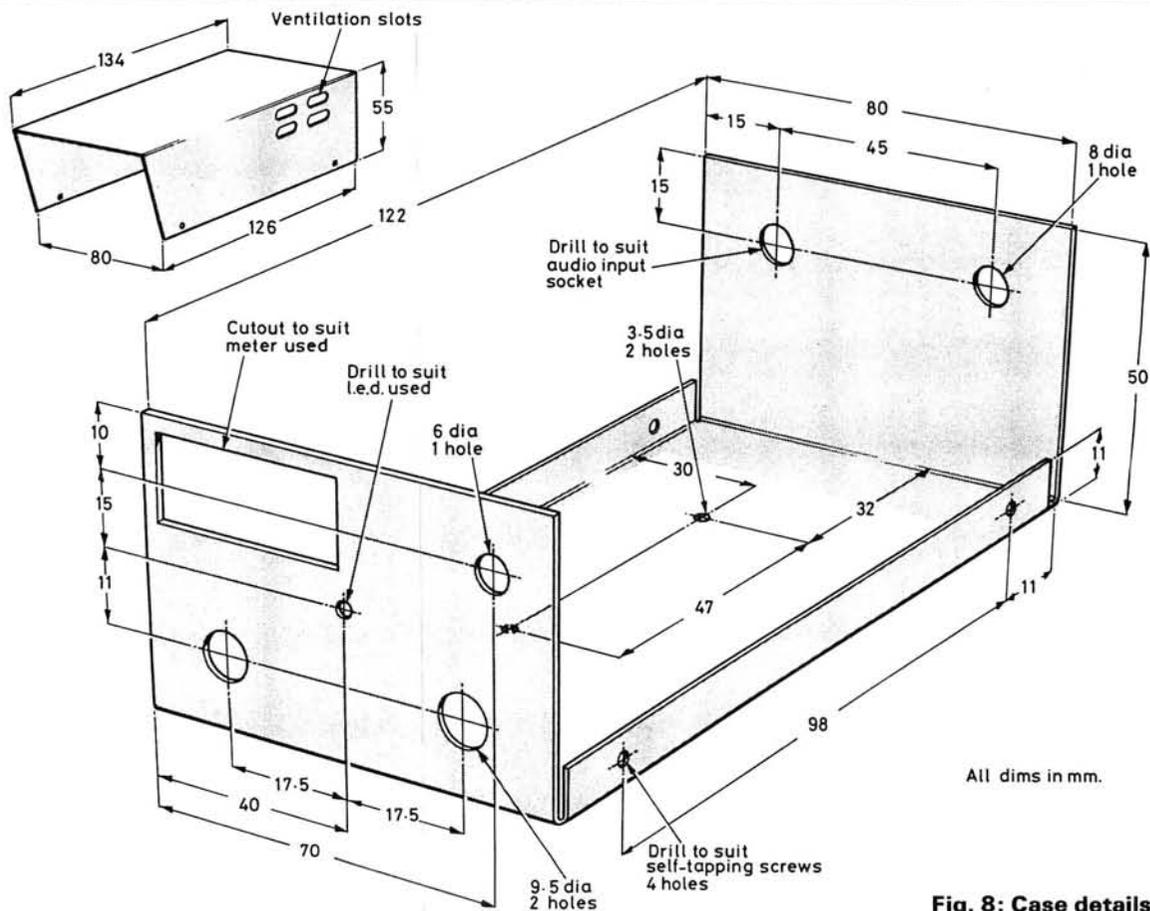


Fig. 8: Case details

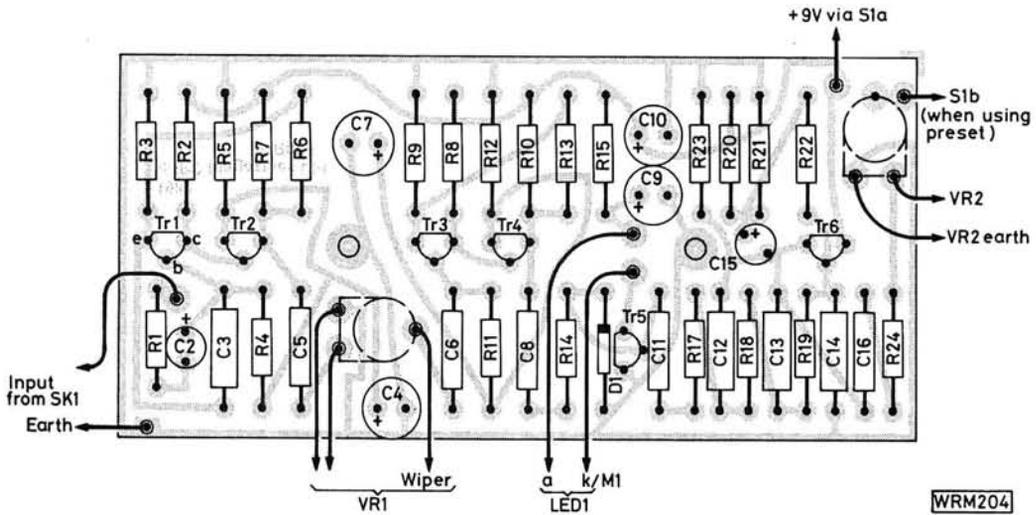
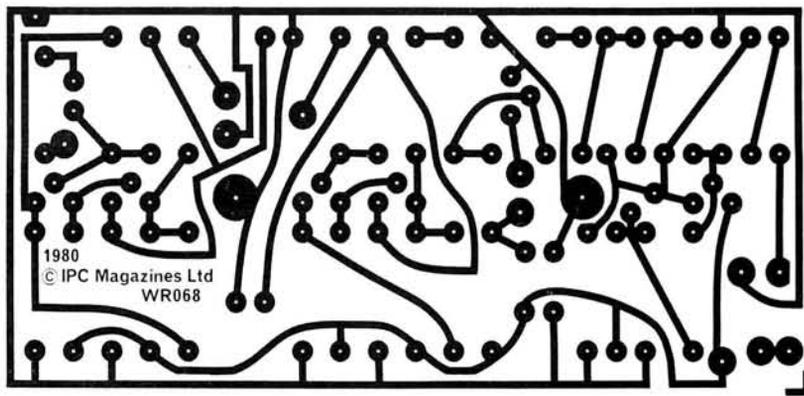


Fig. 9: Copper pattern and component layout shown full size

★ components

Resistors			Capacitors		
$\frac{1}{4}$ W 5%			<i>Polystyrene</i>		
100 Ω	1	R25	470pF	1	C14
150 Ω	1	R15	1nF	4	C1,3,12,13
470 Ω	2	R5,12	<i>Polyester</i>		
1k Ω	1	R24	10nF	4	C5,6,8,11
1.8k Ω	2	R3,9	0.1 μ F	1	C16
2.2k Ω	2	R7,10	<i>Electrolytic 63V</i>		
2.7k Ω	1	R1	2.2 μ F	2	C2,15
4.7k Ω	1	R16	22 μ F	5	C4,7,9,10,17
8.2k Ω	1	R23	Semiconductors		
15k Ω	1	R17	<i>Light-emitting diodes</i>		
39k Ω	1	R6	TIL209	1	LED1
47k Ω	2	R18,19	<i>Diodes</i>		
68k Ω	3	R13,14,22	BZY88C9V1	1	D2
120k Ω	2	R2,8	1N4148	1	D1
150k Ω	2	R4,11	<i>Transistors</i>		
270k Ω	1	R20	BC414	6	Tr1-6 BC109 may also be used
390k Ω	1	R21			
Potentiometers					
25k Ω	1	VR2 (log) (use miniature horizontal-mounting type if to be p.c.b. mounted)			
100k Ω	1	VR1 (log)			
Miscellaneous					
100 μ A f.s.d. meter (1); d.p.d.t. toggle switch (1); suitable metal box (1); coaxial sockets (2); battery lead (if used); printed circuit board (1).					

maximum limiting is achieved (where there is no increase in meter reading for an increase in applied signal). Capacitor C1 is mounted directly across the audio input socket and the l.e.d. is a push-fit in the front panel.

In Use

Once the correct settings have been arrived at, do not make continual adjustments in an effort to improve things. Reports will vary and will, as ever, depend very much on the type of receiver in use, operator experience, etc.

Do *not* turn the limiter gain control up too high—if the meter or l.e.d. is indicating as described under "Setting Up", the talk-power will be impressively increased.

With some microphones, it may be found that the output may be too low to drive the processor into limiting—if this is so, changing R6 from 39k Ω to 68k Ω will double the gain of the processor pre-amp. stage. If this is still insufficient, a low-noise pre-amp. should be inserted between the microphone and processor input.

Although designed for s.s.b. transmission, the processor will work just as effectively with a.m. and f.m. The author has found that improvements of 2 or 3 "S" points can be anticipated in reports. When the prototype was first tried, a large number of stations were surprised that a processor was in use—evidently they had thought that a linear, at the very least, was being used! ●

KINDLY NOTE!

Burglar Alarms, Sept.–Oct. 1979

In describing how the home-constructor might go about installing a security system capable of satisfying British Standard Institute specifications, we erroneously referred to "BS3545". The relevant BS dealing with intruder alarms is BS4737.

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS**

SPECIAL PRODUCT REPORT Radat 2301 Function Generator

▶▶▶ *continued from page 31*

switch in the variable duty cycle control and also select the output attenuator setting. This has 20 and 40dB stages and the two buttons pressed in together provide 60dB of attenuation.

Output amplitude is continuously variable with the amplitude control which also incorporates the power on-off switch.


A third BNC socket allows an external voltage to be applied to control the frequency of the f.g.

Construction

The construction of the instrument was of a high standard, the metal case having a removable bottom panel which allowed easy access to the one printed circuit board carrying most of the components.

Results

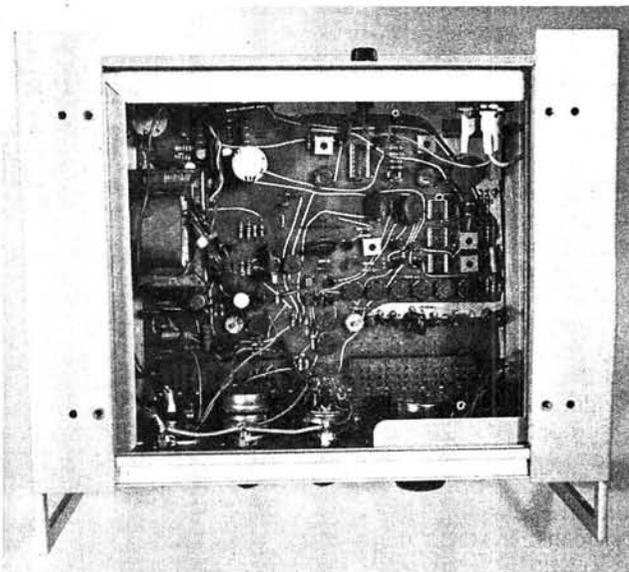Without very accurate test equipment it was not possible to check the performance against the manufacturers specifications, but using a Scopex 4D10A oscilloscope to monitor the output waveforms it would appear that the function generator does what the makers claim, although it needed setting up internally to give repeatable mark-space ratios.




The TTL output varied with the waveform selected and the setting of the d.c. offset control although, of course, the TTL output should not have been affected. The frequency scale was not accurately calibrated between 0.3 and 5 making it virtually unusable. However these faults could probably have been adjusted out. Full instructions are given to enable maintenance and alignment to be carried out and the handbook provides a full components list, p.c.b. layout and specifications.

Price

The 2301 function generator. £159.85 inc. VAT.
The 2301 function generator was supplied by Kramer & Co., 9 October Place, Holders Hill Road, London NW14 1EJ.
Tel: 01-203 2473.

Assessing the new RAE

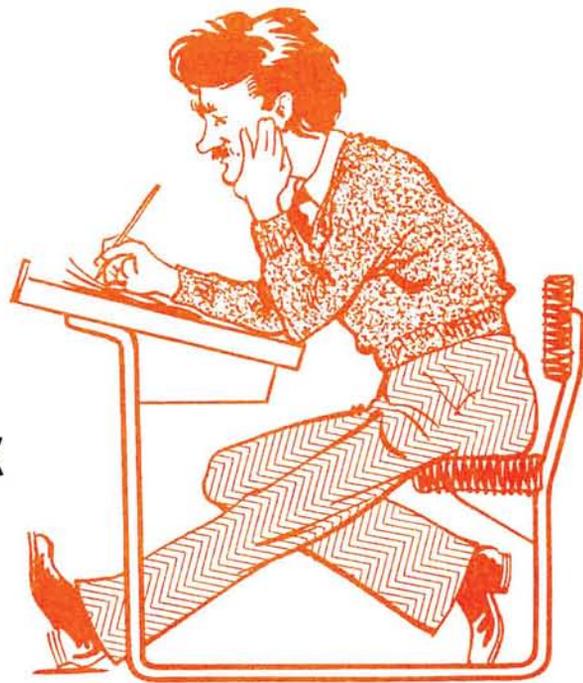by *Arthur HARADA M.Ed, Dip.SP.Ed, ACP, G4INX



Undoubtedly, the results of the latest RAE have caused pleasure to many and disappointed others, be they candidates or qualified radio amateurs. The latter are mentioned as there still exist amongst them certain misgivings and misunderstandings about the present RAE. The twofold purpose of this article, then, is first to reiterate in part the rationale behind the present exam being based on answering multiple choice items. Secondly, to provide some suggestions as to how the RAE may be diversified in order to encompass and encourage, amongst other things, the needs of the candidate with practical ability in amateur radio construction, in contrast to one who knows the theory but is useless with a soldering iron.

Multiple Choice

The main arguments for the use of multiple choice items are applicable to all examinations using this type of evaluation. First, such questions are objective as each question and its alternative answers are so structured as to free the result from interference by the examiner. Secondly, many more questions can be posed in the time allowed, resulting in a more even sampling of the syllabus and thus improving the reliability of the scores. Finally by avoiding the need for candidates to write out their answers, more opportunity is given for less hasty thinking as well as the avoidance of over-elaborated, tangential and lengthy answers to questions not asked. Since reliable and valid objective tests necessitate a great deal of skill and time in their construction, the City and Guilds of London Institute are endeavouring to build up an item bank—questions of known difficulty for a specific span of ability. This explains the non-availability of the last RAE's contents. Into this bank the Institute might wish to consider in future accepting questions (and their answers!) from candidates and licensed radio amateurs, thus fostering stronger bonds of personal participation in the hobby.

It is very deceptive thinking on the part of candidates or anybody else to think that guesswork will gain at least a pass in both sections, the choices accompanying each question tend to differ marginally. In fact the pass rate for the RAE May 1979 was 63.5% (1771 successful candidates) compared with 63% for the December 1978 exam and 65.3% for the one held in May 1978, the last two requiring written answers. To conclude whether the new

RAE format significantly improves or reduces a candidates chances of passing is too premature. Furthermore, it would be a highly questionable exercise to try to draw sound comparisons between the past and present systems using the pass rate as a criterion. This is because one must recognise also the very real possibilities that future candidates will be better prepared—the growth in RAE classes, the increasing number of readily available and relevant publications in electronics, and the incorporation of that subject into many schools' curriculum being just some of the contributory causes.

Practical

The failure rate in each section of the RAE May 1979 was 27.7% in Part 1 and 40.9% in Part 2, rates which were in keeping with the general trend of past RAE's, and a feature that brings me to my final point, namely, the RAE's excessive theoretical bias. Perhaps what is needed to strike a balance is the addition of a practical section. For example, the candidate under examination conditions may be asked to tune up an h.f. transceiver and then conduct a series of suitable but differing mock QSOs, or be required to construct a simple device using his/her own components but following a circuit supplied by the examiners. Instead of having to solder (sic) on without help, candidates would have more incentive to join amateur radio clubs where they could receive guidance and tuition plus the opportunity of being examined in the RAE's practical part by practising amateurs. As at present special arrangements would have to be made for disabled candidates. There is also the possible problem of subjectivity by an examiner which could be avoided by a committee of examiners at local level. By using this new form of assessment pirating and obscene QSOs may be eradicated or reduced, the spirit of home-brewing equipment will be maintained if not improved, and candidates will feel that more of the spectrum of their hobby has been appreciated.

The author acknowledges the assistance of Susan Conacher, RAE section, City and Guilds of London Institute, in providing the statistical information. ●

*Department of Professional Studies, Chester College of Higher Education

Entropy, symbolised by the Scorpion throughout history, is the universe's tendency to destruction, dissipation, death and decay. Because of this immutable principle, 100 per cent reliability for any length of time is a myth. Fortunately, great reliability is rarely required for more than a few years, with the exception of massive capital investments in military, aviation and telecommunications systems. Even these have to be serviced! A knowledge of the required lifespan of the equipment is helpful, so that effort is not wasted in attaining an unwanted lifespan. Reliable equipment need not be expensive provided the designer has the skill to make a circuit no more reliable than it needs to be.

Contrary to popular opinion, well designed electronic equipment is inherently very reliable. Most failures in well designed equipment are due to mechanical components, or in areas of high electrical stress. Much of the skill in equipment design lies in identifying such areas, and choosing appropriate components.



RELIABILITY IN ELECTRONIC CIRCUITS

BEN J. DUNCAN

The General Pattern of Reliability

The bathtub curve in Fig. 1 depicts the general pattern of component failure. In the infant mortality phase, weak and faulty components are weeded out. This phase usually lasts for 100 to 300 hours. High reliability equipment is often soak tested for this period in order to weed out faults before the equipment passes into service. Thereafter, component failures are infrequent and occur at a constant rate. The wear out phase may begin after 500 hours in the case of a highly stressed component (a) or it may occur after some 100 000 hours (b) in small signal circuitry. Component failures then become increasingly frequent. It is important to appreciate that this graph does not imply nor preclude the failure of any given component *at any time whatsoever*. It merely represents a general pattern.

If we are producing millions of identical items, say, television receivers, then we can make use of statistical information on component failure rates to calculate the typical reliability of any given sample. This is usually expressed as a confidence figure, for example: we can be 37 per cent certain that the receiver will operate for 5000 hours or 90 per cent certain that it will operate for 500 hours. These figures are meaningless when equipment is constructed in small quantities. In this case, all one can do is to identify the areas and types of stress in a circuit and rate or protect components appropriately; attention will now be turned to component stresses.

Component Stresses

Temperature has a great effect on the lifespan of components. The rate of chemical reactions is doubled for a 10°C rise in temperature. This fundamental thermodynamic law affects particularly the diffusion of impurities in components, especially semiconductors. Although most silicon power transistors, for instance, will happily operate at 100°C, the rate of deleterious chemical reactions will be some 256 times greater than at 20°C. Moreover, leakage current increases by the same order of

magnitude. *Small changes in temperature significantly affect component lifespan.* A good rule of the thumb for longevity is to maintain temperatures as close to 20°C as possible.

Extremes of temperature, whether high or low, can result in differential contraction or expansion of encapsulation materials, quite apart from chips and internal connections. For instance, glass-metal seals on metal-can transistors can split at low temperatures, allowing the ingress of moisture and contaminants.

Another aspect of temperature, of particular interest to designers of power semiconductor circuits, is thermal cycling. As a power transistor heats up, the internal connections expand. After use, they cool down and contract. After, say, 5000 cycles of heating and cooling, metal fatigue occurs internally. Localised hot spots then occur, and eventual failure may be due to thermal runaway or lead fracture. Specially constructed and

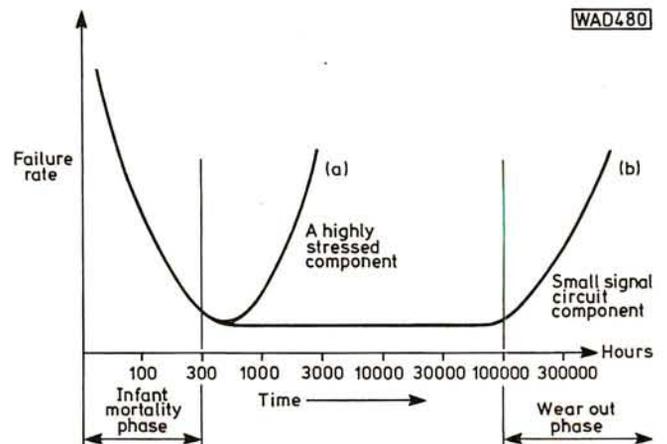


Fig. 1: General pattern of component failure, the familiar "bathtub" curve

selected transistors are available which can withstand extremes of thermal cycling, in high power relay drivers for example. Careful selection of standard devices and good heatsinking is an alternative solution. If the change in temperature (Δt) is reduced by 20°C, from 80°C to 60°C, the endurance of a 2N3055 transistor is increased eight times to 650 000 cycles. Conversely, for $\Delta t = 125^\circ\text{C}$, endurance is only 15 000 cycles. (These figures refer to 10 watts dissipation—at higher powers, endurance is lessened).

Thermal cycling stress also affects passive components, but to a lesser degree. It is obviously of most significance in equipment that starts off in low ambient temperatures and runs at high temperatures. Cycling stress can be minimised by resisting the desire to turn equipment off (and hence let it cool down) when it is to be used again shortly.

Finally, passive components, particularly resistors, must be derated at high ambient temperatures, in order to compensate for self-generated heat.

Other Physical Stresses

Other physical stresses are of relatively minor importance when compared to temperature induced stresses. They can be avoided to an extent by careful component selection and enclosure design. The stresses referred to are typically vibration, humidity and sunlight. Vibration and shock, unless extremely severe, will usually only be of concern in circuits utilising relays, thermionic valves, transducers and filament lamps. However, large wire-ended components mounted on tags are prone to metal fatigue and contact loosening when subjected to vibration. Close-mounted components on printed circuit boards are relatively free from problems of this nature.

If high humidity is anticipated, metal-cased transistors are preferred to plastic encapsulations. In mildly corrosive atmospheres, silver-plated or tinned pressure contacts (on connectors, switches and relays) are prone to degradation; gold-plated contacts and wiping switch contacts are to be preferred in these circumstances. Other contact materials are available for extreme environments. Note that the copper to aluminium leadout connections on electrolytic capacitors are prone to oxidation and decay. Silicone grease is a good barrier against moisture and corrosive vapours.

Equipment that is exposed to strong sunlight is prone to degradation of plastics components; the sun is a very potent source of ultraviolet radiation, which catalyses chemical reactions which would normally occur only over a very long length of time.

Electrical Stresses

The electrical ratings of components are naturally well documented and data is readily available. However, awareness of transient electrical stresses is not common. Because electronic components can be destroyed or damaged in extremely short periods—typically a few milliseconds—a knowledge of transient overcurrents and overvoltages is essential if the components in many circuits are to be adequately rated.

Current surges are caused by motors, incandescent lamps and capacitive loads. Inductors, logic circuits, incandescent lamps, fuses, contactors, relays (and other high-speed switches), transformers and rectifiers are capable of generating voltage transients of a high magnitude.

Secondary breakdown is an aspect of power transistor selection that can pass unnoticed. It is a localised form of

Table 1
Temperature range of common components

Component	*Rated temp. °C	Ambient temp. range	
		Min. °C	Max. °C
Resistor, carbon film	70	-40	+125
Resistor, oxide	70	-55	+150
Resistor, wirewound	70	—	+310
Bridge rectifier, 25A	25	-55	+150
Op. amp., LM741C	—	0	+70
Op. amp., LM741A	—	-55	+125
Switch, push-button	—	-30	+55
Mains transformer	45	—	—
Wire, 1.5mm ² , pvc ins.	25	—	—
Capacitor, polycarbonate	—	-55	+100
Edge connector, 0.1in	—	-55	+110
Box, ABS plastics	—	-20	+85
Light emitting diode	25	—	—

*Temperature when the component is run at maximum rating.

thermal runaway, and for a given voltage, may well limit the useful power handling capabilities to a figure well below that implied by the " P_{tot} " value given in short-form data sheets. The secondary breakdown characteristics of transistors are shown in an "SOA" graph. (Safe Operating Area.) In audio applications, the d.c. curve must be used. Fig. 2 shows the SOA characteristics of a common power transistor.

Voltage derating can provide useful increases in component lifespan, particularly with regard to incandescent lamps and capacitors. For instance, if a lamp is operated at a voltage 10 per cent below its nominal rating, its lifespan will be typically five times as great. The lifespan of lamps can also be extended by limiting the surge current that occurs at switch on; hence the use of a thermistor in projection lamp control gear.

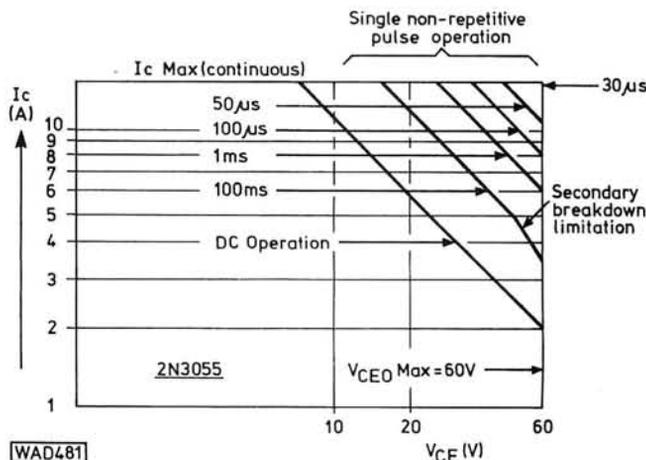


Fig. 2: A power transistor Safe Operating Area (SOA) graph

Miscellaneous Considerations

Mechanical stresses on component encapsulations are infrequently considered. Compromise is required when power semiconductors are mounted. For this reason, metal clips are the most reliable way of mounting plastic power transistors; the mounting pressure is sufficient to maintain low thermal resistance yet at the same time excessive pressure, which may crack the case, is avoided. Stud-mounted thyristors and rectifiers can suffer internal deformation if the stud nut is tightened excessively. On the other hand, it must be sufficiently tight for good heat transfer and moreover, must remain tight for reliability. Fortunately, the optimum torque can be found in data sheets. As a rule of thumb, the tightness attained by using a pair of pliers is usually sufficient for 28UNF studs. It is not unknown for plastic power devices to be torn from their header by careless mounting; alternatively, a small crack may appear, rendering the chip vulnerable to contaminants. *All electronic components are inherently fragile*, particularly until they are safely mounted.

Even if a piece of recently completed equipment is already working, inspection for physical defects is strongly advised. Residual solder waste and wire slivers may float around and cause problems, such as short-circuits, at a later date. Accumulations of flux should be cleared from high voltage or high impedance circuit boards; methylated spirits is the usual solvent. Nuts should be inspected for tightness and shakeproof washers used, particularly if the equipment is to be carried around regularly.

Finally, the equipment should be soak tested, preferably under full load or at full power, and if possible, under the design environmental limits. At this point, internal temperatures should be monitored and "hot spots" and other anomalies should be investigated. Heat sensitive recording labels are an expedient way of performing these investigations. As the ambient temperature inside a well-ventilated case may take two hours to reach equilibrium, immediate measurements are of little value.

Practical Circuit Considerations

The high current power supply shown in Fig. 3 is typical of circuits intended for high power audio amplifiers. Electrical aspects are considered first:

1. Transformer T1 causes an inrush current, typically an order of magnitude greater than the nominal supply current, when it is initially energised. Consequently S1 must be rated at some 10 to 15 amps for longevity.

2. The fuse FS1 must be able to withstand the inrush current, yet must blow swiftly if the output terminals are short-circuited. If a "quick-blow" fuse is used, it will have to be rated at such a high current to meet the first criterion that it is likely to take several minutes to blow in the case of a short-circuited output—if at all! An antisurge fuse must be used. Because fuse tolerances are wide and the magnitude of the inrush current cannot be accurately determined, the lowest rating which will not blow on account of inrush current is usually found by trial and error. A suitable rating is 1A, and whilst slightly lower ratings will give better protection, there is the risk of "nuisance blowing".

3. Mains supplies can be rife with transient voltages; their magnitude and likelihood cannot, unfortunately, be predicted. C1 and voltage-dependent resistor VDR1 are added to protect the bridge rectifier and power amplifier semiconductors.

4. Although the mean supply current is nominally 2 amps, the bridge rectifier is rated at 12.5A. Such a rectifier will have an adequate I_{FSM} (maximum forward surge current)

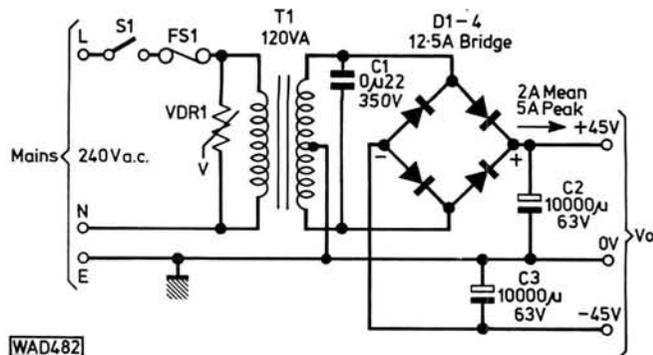


Fig. 3: Circuit of a typical high-current power supply, such as might be used in an audio amplifier

rating when C2 and C3 are initially charged. Furthermore, a short-circuited amplifier output is capable of drawing a large current from the supply before protection circuitry has time to operate. A generously rated bridge has a better chance of survival under these circumstances.

5. The rectifier's peak reverse voltage rating (V_{RRM}) is 200V. This gives additional protection against transients, including those generated by the transformer at switch-on, should C1 fail. In general, the rectifier V_{RRM} rating should be at least 50 per cent greater than the input voltage. This allows for supply voltage variations, harmonic content and transformer regulation; when the supply is unloaded, the output voltage may be 5–15 per cent higher than normal. Likewise, C2 and C3 are given generous voltage ratings.

Physical Aspects

1. Transformer T1 will run at some 50°C, or higher if ventilation is poor and the amplifier is driven hard. The

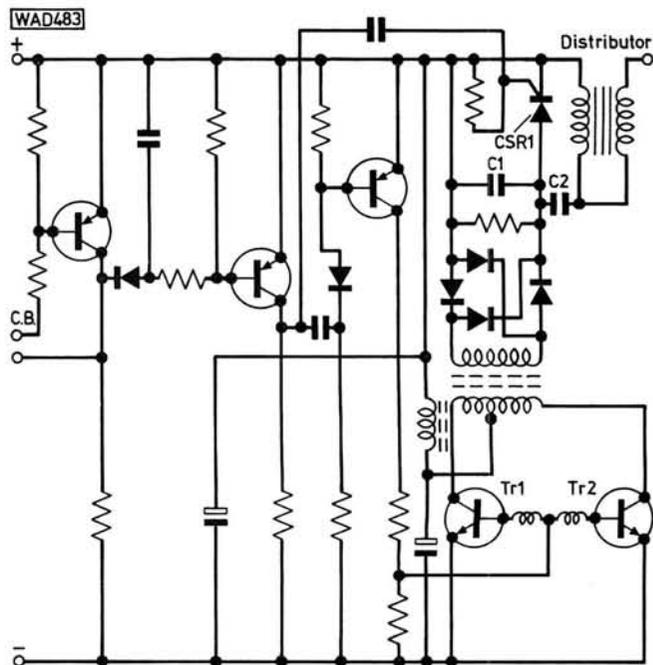


Fig. 4: Circuit of an electronic ignition system, with critical components identified

Table 2
Component selection for reliability

Component	Failure rate	Notes
Resistors: Carbon film, high stability Metal oxide and metal glaze	Low Very low	—
Capacitors: Polycarbonate Polystyrene Metallised polyester Polypropylene Electrolytic	Very low Very low Very low Very low High	Self healing, low loss Unsuitable for high temperatures Self healing. For arduous conditions, e.g., mains supply Withstands high voltage pulses Ripple current and ambient temperature critical. "Computer" types are more reliable
Connectors and switches	Low	Identify surge currents. Use appropriately plated contacts
Indicators: Light emitting diodes Incandescent filament	Very low High	Good vibration immunity. Use minimum current For high temperature applications
Relays, d.i.l.	Low	Excellent environmental protection
Potentiometers, Cermet preset	Low	Excellent environmental protection. Suitable for high temperatures
Integrated circuits, ceramic case	Very low	Excellent environmental protection
Alarm annunciators: Solid state Electromechanical	Very low Low	Good vibration resistance For extremes of temperature, e.g., outdoor use
Transistor, power	High to medium	Take account of effect of high temperature on parameters, also thermal cycling and secondary breakdown characteristics

transformer is the main source of heat and its siting with regard to ventilation should reflect this. If it is necessary to mount C2 and C3 close to the transformer, a heat-shield may be constructed of bright aluminium or stainless steel. C1 will usually be wired across the transformer; therefore it should be chosen to withstand high temperatures.

2. The tags on C2 and C3 are prone to failure through mechanical stress. This is largely avoided by careful routing of the wiring.

3. Switch and fuse contacts are prone to tarnishing and oxidisation. Fortunately, a small amount of contact resistance is rarely a problem here. Wiping contacts can be used in difficult circumstances.

The circuit of Fig. 4 is a typical electronic ignition system. Electrical rating considerations are not pursued in detail because they are relatively specialised, although strobes, invertors and flashguns are close relatives. The key considerations are:

1. Tr1 and Tr2 should be chosen for good thermal cycling characteristics.

2. C1 and C2 are highly stressed by the fast high voltage pulses (2kHz, 400V) from the invertor. Voltage derating is usually necessary at the aforementioned frequency if mixed dielectric types are used. A polypropylene capacitor is unlikely to require derating at 2kHz and is eminently suited to this application.

3. The thyristor, CSR1, must be protected from transient voltage spikes of around 1kV to which it can be subjected if the secondary is unloaded, i.e., a spark plug is removed.

Environmental conditions can be extremely taxing in an application of this nature. Night-time winter temperatures may be lower than -15°C . When a car that has been cruising at high speeds comes to a standstill, the engine compartment temperature may exceed 80°C . This is *ambient* temperature—power semiconductors will be considerably hotter. At low temperatures, the gain of semiconductors decreases. In perpetually cold temperatures, germanium devices are to be preferred, but cannot be used here because of the high temperature extreme. At -10°C , the gate sensitivity of the thyristor will be poor. More current can be readily applied, but this aggravates gate dissipation when the ambient temperature rises. At high temperatures, thyristor leakage current (I_{DROM}) may become troublesome, causing C2 to be discharged prematurely. C1 and C2 may require derating for the same reason. Finally, thyristor commutation capability is degraded at high temperatures.

Protecting the circuit from salt, oil, grease and moisture is relatively easy if a diecast box is used. Silicone grease gives added protection. However, Tr1 and Tr2 should ideally be mounted externally, to minimise temperature rise inside the box. In this case they are vulnerable to heat

radiated from the engine, quite apart from the aforementioned contaminants. Mechanical damage is also a possibility. Plastics covers and diligent location will largely obviate these problems.

Conclusion

Reliability is most difficult to attain in harsh environments and power circuits. In many circuits, considerable experience or knowledge is required in order to seek out highly stressed components. Even then, further skill is needed in order to locate suitable components or to modify the circuit in order to remove or reduce the stress. Once this has been achieved however, there is great beauty in equipment that works—and goes on and on working—with minimal attention. Unlike large manufacturers of consumer goods, the home constructor can afford a few pennies in order to make his equipment reliable. In this sense, he wins!

BURGLAR

ALARMS PART 3



P.J.WALES

The **PW** 'PARKHURST'

A MICROWAVE MOTION DETECTOR UNIT

In Parts 1 and 2 of our Burglar Alarms series, we described how the d.i.y. fanatic can instal a security system in his home to his own specifications and design. Mass-produced devices and home-assembled electronics are combined to provide a system as simple or as complicated as the constructor requires—either very basic or providing protection to British Standard BS 3545. We described how the security devices functioned, what type of intrusion they are designed to combat and how they, and the whole system, can be constructed so as to be “self-protecting”, using a 24-hour live loop.

One device that we mentioned but did not describe in detail, however, was the “microwave motion detector”. All the other devices incorporated in our security loop are “trap sensors” requiring the intruder to physically disturb some form of electro-mechanical gadget.

With the *PW* “Parkhurst”, however, all he has to do is move and the alarm is sounded, even if there is a door or wall between him and the unit. Thus the level of protection that is provided is very high indeed if the detector is carefully sited and set up.

Basic Principle


Microwave detection devices work by exploiting the phenomenon of “Doppler effect”—the small change in frequency arising from a difference in velocity between a source of wave radiation and a point of perception. The rising and falling note of a passing car-horn is the most obvious illustration—the received frequency is slightly different from the transmitted frequency.

In the case of a microwave motion detector, providing everything in the area under surveillance remains motionless, the frequencies received by the mixer diode stay exactly equal and it produces no output. If motion does occur, however, then the received signal, having been reflected from the moving object, undergoes a Doppler shift of approximately 30Hz/mph. The mixer diode thus produces a low frequency a.f. output with a level of a few microvolts which is processed and used to trigger the alarm.

Development

It was the introduction of the CL 8960 “twin cavity module for presence detection” by Mullard Limited which enormously simplified the manufacture of microwave detection devices. Mullard quickly dominated the UK market with the new device and other manufacturers could only respond by making variants claiming to have an improved performance.

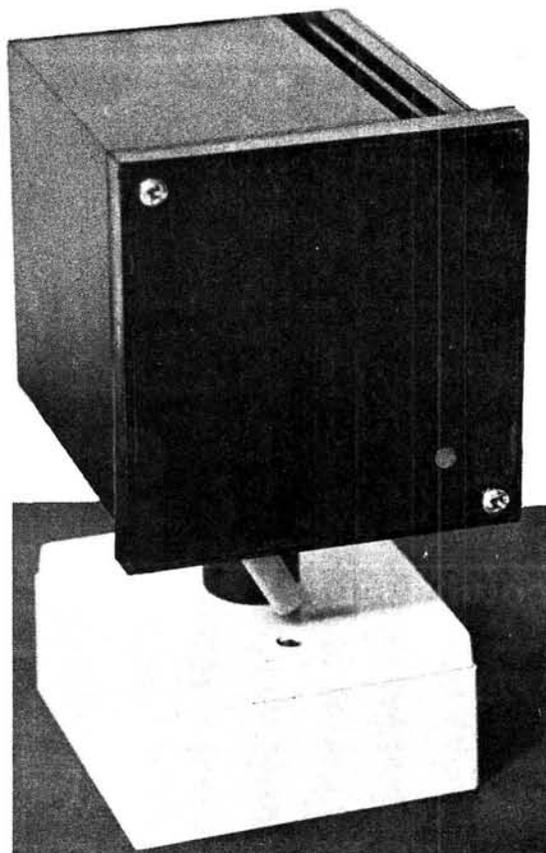It is one of these developments on the original theme



that forms the heart of the PW "Parkhurst"; the GDHM series manufactured by Plessey Microwave and Optoelectronics Limited. This type was evolved in order to capture a share of the European market—larger, but with much more stringent regulations limiting out-of-band harmonic radiation.

The early devices were mostly unable to satisfy these requirements. With the GDHM, however, by introducing cleverly-designed thin metal filters in and around the resonant cavity, the spurious content of the transmitter output was drastically reduced.

The microwave head itself consists of two special-purpose diodes, one acting as an oscillator and the other as a mixer, mounted in a tuned resonant cavity. Fixed to this is a detachable horn antenna which produces the required radiation characteristic. The current drain of the diodes used in the original versions was 150mA or so from a 7V supply; the diodes incorporated in the "Parkhurst" require only 50-60mA from an 8V supply and this has led to a significant improvement in performance compared with that achieved in the early days. If the current required is low, then producing a low-noise power source is made much easier.

The nominal frequency used for these devices is 10-6879GHz and is set by the supply voltage and the resonant frequency of the cavity within which the diode is located. In the case of the GDHM, the frequency varies at a rate of 1MHz/volt and thus a variation of one microvolt in the supply voltage will produce a frequency shift of 1Hz. The need, therefore, is for a really well regulated supply and that used in the "Parkhurst" has been devised es-

pecially for the GDHM and *cannot be used with other types of microwave head.*

The author has designed a horn antenna which is particularly suitable for this application and, for the "Parkhurst", Plessey Ltd. have made available one of their antennae with very similar characteristics.

With a gain of 7dB, it enables the "Parkhurst" to produce a detection volume which is capable of picking up movement a staggering 175ft away! However, in the interests of very high reliability the gain of the amplifier which is fed by the output from the mixer diode is reduced so that the range is deliberately limited to 75ft. This should, of course, be quite adequate for all but the most stately of homes!


Circuit

The circuit diagram is shown in Fig. 1. Integrated circuit IC1 is an LM723 voltage regulator which has a very low output noise level. With decoupling provided by C3, and the 10 μ F capacitor—which is supplied ready-wired to the GDHM, the noise level applied to the Gunn diode via the supply rail is around 0.1 μ V. Diode D1 and R1 provide +6V for the op. amplifiers and their c.m.r.r. (common-mode rejection ratio) effectively nullifies any noise voltages on the supply line.

The f.e.t. input amplifier IC2 has characteristics similar to those of the ubiquitous 741 except that the LF356 takes a very low input current and possesses a very low input noise level. The amplifier is arranged in an a.c.-biased configuration and has a maximum gain of 270; its frequency response is shaped to be 0.1-100Hz (at the 6dB points) by C6 and C7. Variable resistor VR2, its minimum resistance fixed by R11, enables the installer to set the effective range between the limits of six and 75ft.

Resistors R12, 13 and 14 together with C8, C9 and C10 further restrict the frequency response to 0.5-50Hz. The bandwidth is reduced still more as the signal passes through IC3—another a.c.-biased amplifier with a gain of 47. The response is restricted to such narrow limits in order to prevent 50Hz mains hum from activating the alarm. The restriction in no way affects the sensitivity of the device because there are always Doppler shifts of less than 30Hz, even with a fast-moving target.

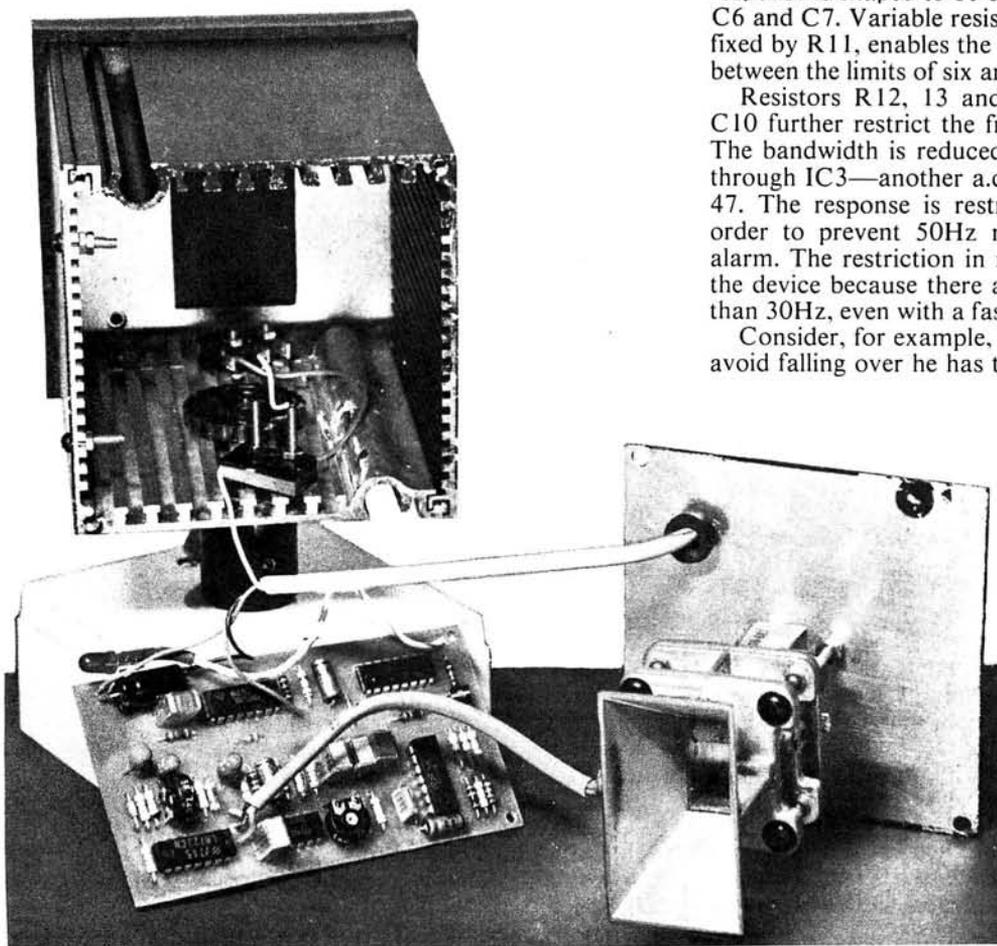Consider, for example, a fast-running man—in order to avoid falling over he has to place each foot on the ground



The PW "Parkhurst"—a view showing the major components

in turn. Obviously, when the foot is on the ground it is stationary—therefore, when it is lifted in the act of taking the next pace it must cause Doppler shifts in the range 0-30Hz as it accelerates from rest to 1mph!

Resistors R18 and 19 provide a 1V hysteresis on the input of IC3b to remove the effects of any low level noise at the output of IC3a. The output of IC3b swings from one rail voltage to the other as motion is detected. Its output is fed into the digital filter via inverter IC6a and also drives the "Walk Test" i.e.d. via Tr1. This causes the LED1 to flash when motion is detected.

The "high-pass digital filter" is used to remove any false alarms caused by occasional transients (the fridge switching on perhaps). Any received signal causes D2 to conduct and remove the "reset" condition from pin 15 of the decade-counter IC4. If no further alarm signals are received before C13 can recharge, the counter is reset and any further alarm signals must restart the count from zero. When there is an actual intruder walking in front of the device the delay introduced by this part of the circuitry, it must be pointed out, is infinitesimal.

The remainder of IC6 (gates c-f) is connected as a latch which, when set, will reset itself after five seconds. Gates c-f would behave as a normal bistable latch; it is the addition of R24, C14 and D3 which cause it to self-reset after five seconds. The effect of the latch is to switch R2 to the 0V rail at all times when the unit is not detecting motion, and to the +12V rail when it is.

Resistor R2 is connected as Rx(loop) when the "Parkhurst" is connected into the security system described in Parts 1 and 2 of the series. Its value can be varied in the way described in Part 2.

WIRELESS TELEGRAPHY ACT 1949

Readers are advised that they will require a "Telapproach" licence before they can legally use this apparatus. The PW "Parkhurst" has been type-approved and application should be made to Licensing Branch, Radio Regulatory Dept., Home Office, Waterloo Bridge House, Waterloo Road, London SE1 8UA quoting "PW Parkhurst". The licence costs £1.40 and is valid for five years.

Assembly

Whether you have purchased the "Parkhurst" as a complete kit or section by section when you get to the GDHM—LEAVE IT ALONE!! The diodes used are extremely sensitive to static and if you touch their ends with your fingers you have a 90% chance that the junctions will be destroyed. By the same token, the devices can *not* be tested by means of a multimeter switched to the ohms range either—that is an even quicker way of destroying them! The mixer diode is a Schottky device with no protection diodes and is therefore particularly prone to damage by static discharge—it you thought that CMOS i.c.'s were easily damaged in this way, this item will make them appear about as sensitive as valves by comparison!

Start by assembling the p.c.b.—this should be quite straightforward. Remember to take the usual precautions with the CMOS i.c.'s. Use a well-earthed soldering-iron, avoid touching the pins with your fingers and keep them in the conductive foam until required.

To test the board, first set the output of IC1 to exactly 8V by adjusting VR1 and then, with the mixer diode side of C5 shorted to the 0V rail check the d.c. voltage present at the outputs of IC2 and IC3a. This should be within 0.5V of 6V. Briefly removing and replacing this short-circuit should cause LED1 to glow dimly for a short period, and the voltage applied to R2 to go positive for about five seconds. This procedure checks that the alarm is being correctly triggered when 50Hz is fed through the amplifier—the fact that LED1 glows only dimly at this stage is nothing to worry about (it is, in fact, only being illuminated for 50% of the time).

Now, if you wish, you may connect the GDHM itself. Before starting, however, take extra care and time in taking the necessary precautions to avoid that dreaded static. In general terms, everything must be earthed—including you!

One good way of achieving this is to carry out the work on the draining surface of a stainless-steel sink unit; this is well earthed through the water supply system and placing the p.c.b., GDHM and tools on it will ensure that they are all at the same static potential. Rather than chain yourself to the same sink, it should be sufficient if you touch it with the palms of your hands occasionally during the operation of soldering the connections to the oscillator and mixer diodes. This should make sure that your skin has the same potential as the other items; take particular care to touch the earthing surface (i.e. the sink) after picking up or setting down tools. Which leaves only the soldering iron. Here the main hazard, as far as the diodes are concerned, is from leakage within the iron itself. Accordingly, before contact is made between the iron and the work, pull out the mains plug and use the residual heat to do the job.

Start by preparing a piece of twin-core screened cable of the correct length and then attaching one end of it to the p.c.b. as per the connections shown on the component layout. Now attach the screen to the body of the GDHM (see photo; no special precautions are needed for this) before pulling out the mains plug and quickly soldering the connection to the oscillator and mixer diodes. Check after completion that (a) the joints are sound and (b) that you have connected the wires the correct way round! The mixer diode is the one nearest the antenna with a 10kΩ resistor attached to it.

Now you are ready to begin testing. Before you apply 12V however, examine the mixer diode very carefully and you will see that there is a circlip just underneath the resistor which is designed to protect the devices against static discharge during transit (this does *not* mean that the precautions detailed above are any less necessary!)

After you have carefully removed this, switch on and wave your hand in front of the antenna—the i.e.d. should flash wildly, indicating that the device has detected the movement of your hand. Do not, at this stage, try range tests—the head has to be mounted in its case in order to prevent rearwards transmission before meaningful results can be obtained.

Case

The specified case is one supplied by West Hyde Developments Limited. Any case can be used, providing that it satisfies the requirements that it (a) should be of all-metal construction and (b) that a thin plastic cover for the microwave aperture is available. Strictly speaking, this should be manufactured from 0.5mm Cobex sheet—this is very rigid and is virtually transparent to microwave radiation.

The West Hyde case is offered with an option of metal



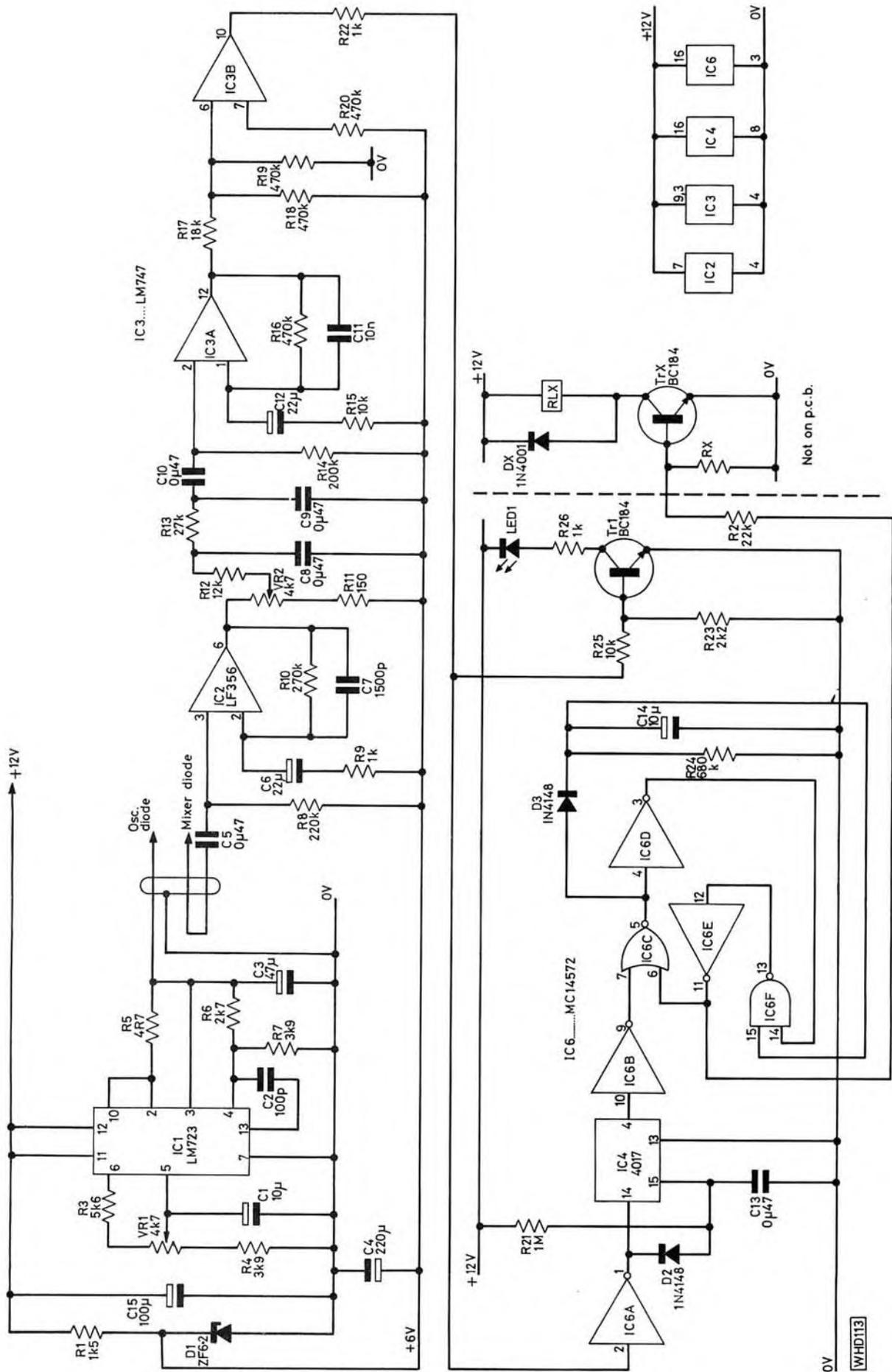



Fig. 1: The circuit diagram of the PW "Parkhurst" motion detector

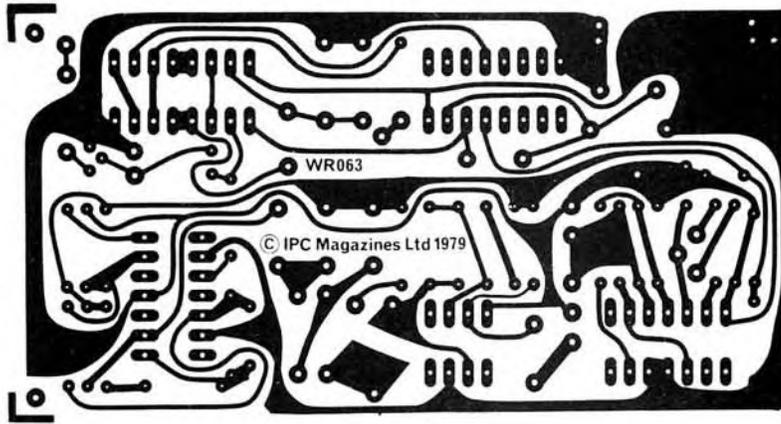

Copper track pattern (full size)

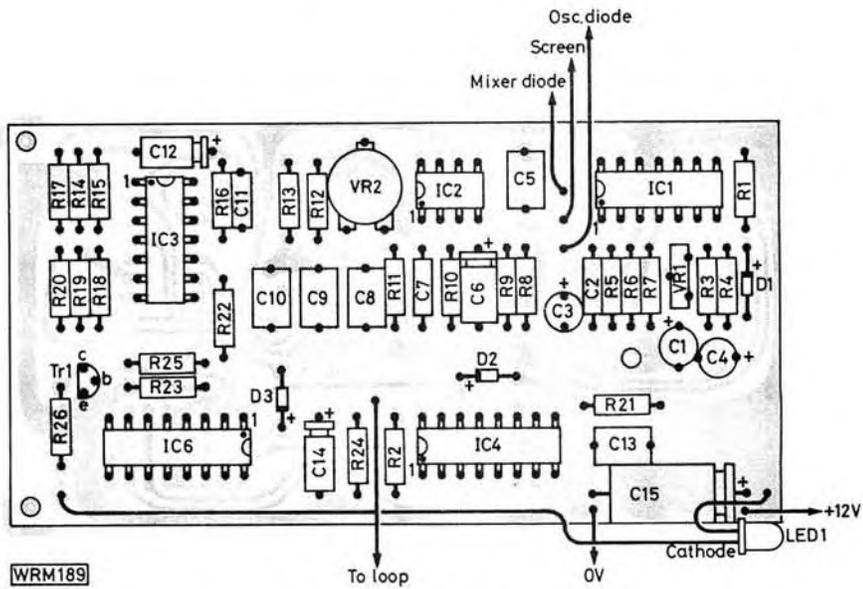

Component layout

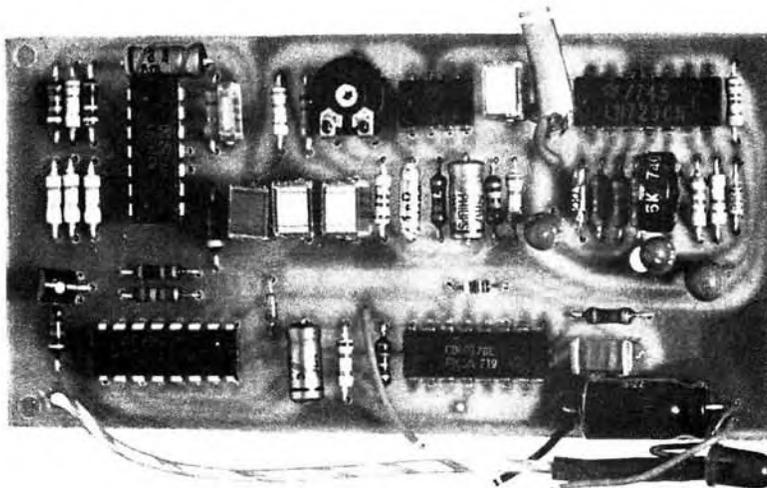

★ components

Resistors

¼ W 5%		
150Ω	1	R11
1kΩ	3	R9,22,26
1.5kΩ	1	R1
2.2kΩ	1	R23
2.7kΩ	1	R6
3.9kΩ	2	R4,7
4.7kΩ	1	R5
5.6kΩ	1	R3
10kΩ	2	R15,25
12kΩ	1	R12
18kΩ	1	R17
22kΩ	1	R2
27kΩ	1	R13
220kΩ	2	R8,14
270kΩ	1	R10
470kΩ	4	R16,18,19,20
680kΩ	1	R24
1MΩ	1	R21

Capacitors

Tantalum

10μF 16V	2	C1, 14
22μF 16V	2	C6, 12
47μF 16V	1	C3

Electrolytic

100μF 25V	1	C15
-----------	---	-----

Polycarbonate

10nF	1	C11
0.47μF	5	C5, 8, 9, 10, 13

Polystyrene

100pF	1	C2
1500pF	1	C7

Potentiometers

4.7kΩ	2	VR1, 2
-------	---	--------

Semiconductors

Diodes

1N4001	1	DX
1N4148	2	D2, D3
ZF6.2	1	D1
Red l.e.d.	1	LED1

Transistors

BC184	2	Tr1, X
-------	---	--------

Integrated Circuits

LM723	1	IC1
LF356	1	IC2
LM747	1	IC3
CD4017BE	1	IC4
MC14572	1	IC6

Miscellaneous

GDHM microwave head; case CONTIL-DIN (West Hyde); Relay. Microswitches V3 lever (2).

or plastic front panels—in the construction of the prototype both were used. The metal front panel has a cut-out for the microwave horn and a hole to enable LED1 to be visible (Fig. 3).

For an attractive appearance, spray the case with a matt black finish—spray one side of the plastic panel also. Assemble the metal and plastic panels into the front of the case with the painted surface of the plastic panel to the inside. Carefully scribe a circle through the l.e.d. hole in the metal plate—this will be visible from the outside as a neat red circle when LED1 is illuminated.

Mount the two tamper-proofing microswitches into the slots in the case using 2.5mm screws. Adjust the positions of the switches so that removing the front or rear panels will cause them to open—these are connected in parallel so that the operation of either will break the 24 hour loop and cause the main security alarm to be sounded.

The GDHM itself is fixed to the rear panel using long 3mm screws, with two nuts per screw. Use the nuts to adjust the position of the microwave head so that the edges of the horn fit snugly against the cut-out in the front panel.

The p.c.b. can now be mounted on 6BA screws using two nuts as spacers. The l.e.d. can now be lined up with the hole in the front panel. The final wiring can now be completed and the unit assembled for range testing.

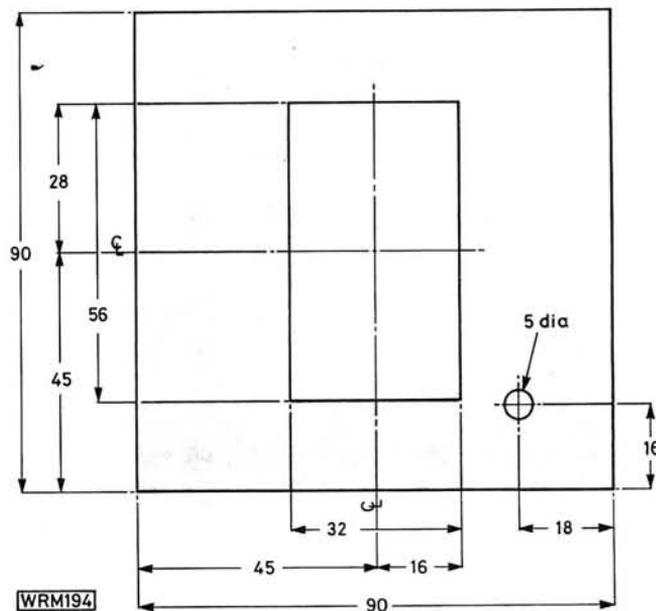


Fig. 3: Front panel details

Siting

Before final testing, the performance required should be evaluated; siting the unit requires careful consideration. Firstly, the possibility of false alarms must be considered—fluorescent lights are one source of them as the ionised gases cause reflections of the microwave radiation at 100Hz. It is therefore necessary to keep well away from them.

Other sources of false alarms include any slow-moving objects—clock-pendulums for example. Movement outside the protected area may also set off the alarm: people passing by windows or thin doors could trigger the unit if it is pointed towards them. Fig. 4 shows some suggested sitings for the unit.

The module must be firmly mounted and, at the same

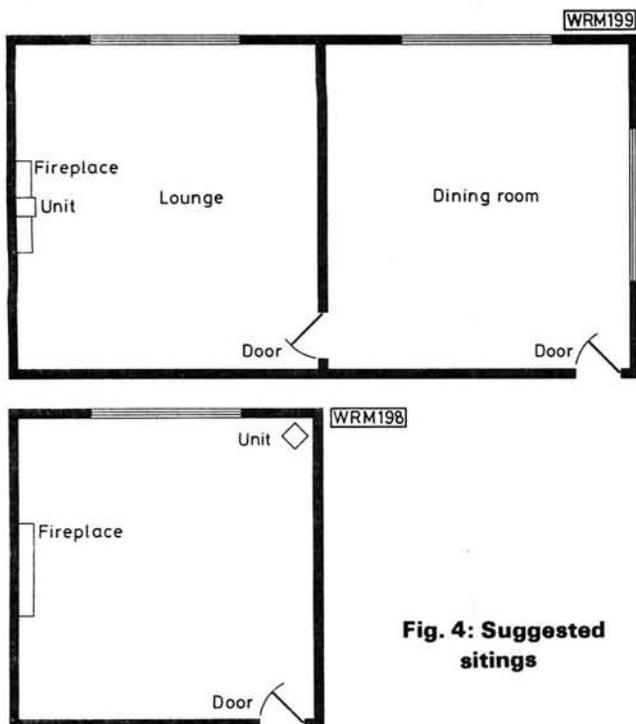


Fig. 4: Suggested sitings

time, remain adjustable. The easiest way to do this is to mount it on a ball-joint which can then be set into a domestic switch panel with a blanking-plate. Suitable ball-joints are available from good photographic shops.

The light-switch fitting (from any electrical retailer) should be firmly screwed to the wall or shelf etc. Bear in mind, though, that a cable has to be run to the unit—it is better, naturally, if this can be concealed in some way. Having decided on the best location, mount the unit and wire it into the security loops.

Testing

Testing is carried out using only the "Walk Test" i.e.d.

Given that the maximum range of the unit is 75ft, gauge the approximate setting of VR2 and, having replaced the front panels, walk carefully around the room ensuring that the i.e.d. flashes appropriately. The next step is to seek the aid of an assistant who should sit motionless in the room and watch the i.e.d. as you walk around outside the protected area, testing for spurious alarms. Alternatively, you could watch LED1 through windows or an open door as you carry out the test.

As a final check, secure the area, turn the system on and then walk outside the protected area to test for spurious alarms. Now turn the system off, enter the microwave-protected room and close the door. An assistant should now turn the system on and ensure that the alarm is triggered every time you move.

Conclusion

The "Parkhurst", when added to a complete system will certainly add tremendously to the level of security. It can be installed on its own—but do not forget that security can still be enhanced by the addition of the locks, protection devices etc. that we described in Parts 1 and 2.

With the addition of the "Parkhurst" to the complete and comprehensive system that we have described in this series, you should definitely be able to rest easy in your bed at night!

or to scan them for a free or busy channel. Remember, though, that you should programme your least favourite channel into position 4. As mentioned under "8", this is the channel that will be over-written if the "Write" feature is used without a memory channel selected.

12. Sim/-600/+600/1T-2R/3T-4R. This selector allows normal simplex operation in the Sim position. The -600 position is for use with UK repeaters, where the input channel (mobile transmit) is 600kHz below the output channel (mobile receive). The +600 position gives the opposite shift, for reverse or continental repeater operation. The remaining two positions allow two non-standard shifts to be programmed in by storing the appropriate transmit and receive frequencies in memory channels 1 to 4. This facility is useful if the rig is to be used with an up-converter for the 70cm band.

13. Volume/Squelch. The outer (larger) knob controls the squelch threshold, and the inner (smaller) knob controls the volume.

On the rear panel are the aerial connector (SO-239, "UHF" type), d.c. power connector, external speaker jack (4-8Ω) and Sel-call connector. The last one also offers a connection point for remote microphone/headset combinations, etc.

Results

Now to the results of our trials. We gave the rig just about every test we could think of, and it acquitted itself admirably on both speech and RTTY. Aerials used were a Ringo Ranger Colinear for base station tests and a 5/8λ magnetic mount when going mobile. The set comes complete with a good installation kit, comprising a power cable 2m long, with line fuse-holder and a spare 5A fuse; miniature jack plug to fit external speaker jack; mounting bracket suitable for mobile (under-dash) or base station use, with mounting hardware. The handbook includes a good circuit diagram, operating instructions, basic internal adjustment details, internal photographs identifying principal sections (component references are printed on the p.c.b.s), block diagram, comprehensive circuit description and specification. About the only thing missing is a components list.

The one criticism that we would make of the set is the difficulty of turning the small control knobs with even the slightest amount of grease or oil on the fingers. Eating chicken and chips when operating mobile is very definitely out! Obviously, the knobs have to be small to get all those controls onto such a small panel area. They could, though, be of a type providing a more positive grip, without being any larger.

There it is then, a rig worthy of serious consideration by anyone looking for a versatile base station-cum-mobile. By the visible quality of construction, it should go on performing well for a long time to come.

Costing £250.00 including VAT, the KDK FM-2016E transceiver reviewed was kindly loaned by South Midlands Communications Limited, S.M. House, Osbourne Road, Totton, Southampton SO4 4DN, Tel: 0703-867333, and we would thank them for their invaluable assistance in this respect.

MICROWAVE MODULES LTD

DON'T WORK IN THE DARK!!

Measure the frequency of your radio control system to an accuracy of 0.0001 MHz with our world-famous digital frequency counter.



Just apply a 12 volt D.C. supply to the counter and your transmitted frequency will be displayed on the bright 6 digit L.E.D. readout. A handy plug-in whip aerial is supplied with the frequency counter together with a suitable D.C. power lead. **PRICE: £69 inc. VAT.** Delivery from stock.

SPECIFICATION

DIGIT HEIGHT: 10mm
 DISPLAY WIDTH: 45mm
 CASE SIZE: 111 x 27mm
 FREQUENCY RANGE: 0.45-50 MHz
 SENSITIVITY: BETTER THAN 50mV
 INPUT CONNECTOR: 50 OHM BNC
 INPUT IMPEDANCE: 50 OHM
 POWER CONNECTOR: 5 pin DIN SOCKET
 POWER REQUIREMENTS: 12 VOLTS D.C. 300mA

FEATURES


- IDEAL FOR ALL RADIO CONTROL APPLICATIONS
- HANDY-SIZE UNIT COMPLETE WITH PICK-UP AERIAL
- 12 VOLT D.C. OPERATION
- BRIGHT LED DISPLAY
- ACCURATE TO 0.0001 MHz

Any further information on this product may be obtained by contacting our Sales Dept. All Microwave Models products are fully guaranteed for twelve months.

MICROWAVE MODULES
 BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND
 Telephone: 051-523 4011 Telex: 628608 MICRO G

practical WIRELESS QSL CARDS

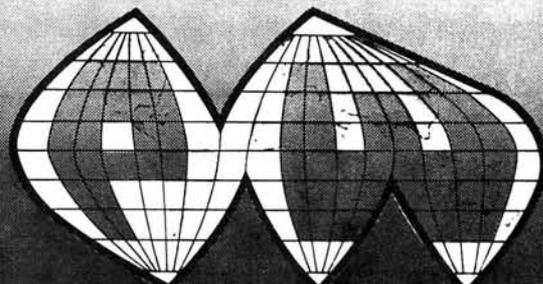YOUR CALL SIGN, NAME & ADDRESS PRINTED HERE



PRACTICAL WIRELESS Britain's leading radio magazine, read all over the world.

(Sample sent on receipt of s.a.e.)

For the radio amateur or short wave listener, an attractive card incorporating a world map and the initials of your favourite radio magazine, printed in blue and green.

Your callsign, name and address will be overprinted in black, at the top of the card. The reverse of the card will have the usual form for reception report, etc., and address space.

The cards measure 102 x 152mm (4 x 6in) and are available in the following quantities:

- 250 off— £6.25
- 500 off— £10.00
- 1000 off— £16.00

These prices include VAT and packing and postage to any United Kingdom address. Please send your order with a cheque or postal order for the appropriate amount to: Practical Wireless, Westover House, West Quay Road, Poole, Dorset BH15 1JG, giving full details on the coupon provided, or on plain paper if you do not want to cut your copy of Practical Wireless. Please make your remittance payable to IPC Magazines Ltd.

Now, complete your system!



Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system 4/6 ch mono. inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU £89.70.

The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor. 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.80, or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only £6.32 each.




Projectors

Come and see our specially selected projectors from £50.60 (Square Multifect 150) to £83.37 (Tutor IIE DDU) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration.



Turntables

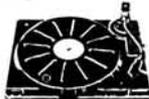Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive. ONLY £28.75



Repelights Great effect at discos. 7 metres long. Multiway connectors. 4 channel. £46.00 (inc pack of spare bulbs)

Bulgin Octal plugs and sockets There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.69 P551 PLUG £1.72.

Multiway Cables
 4 core (6A) 63p/metre
 5 core (6A) 78p/metre
 6 core (6A) 92p/metre

Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES

ALL SHOPS OPEN TUE.SAT.
 LATE NIGHT WED.
 (UP TO 8 PM)

PERSONAL CALLERS ONLY

Roger Squire's

Disco Centres

LONDON 176 Junction Road, N19. 50yds Trafalgar Park Tube Station. Tel: 01 272 7474

BRISTOL 125 Church Road, Redfield (Near St. George) 1 mile from end of M32

MANCHESTER Tel: 0272 550580

GLASSGOW 251 Deansgate 3, 15 mins from City Centre
 Tel: 061 831 7676
 Margaret Drive) Kelvinside 20, just behind the BBC.
 Tel: 041 946 3303

Please supply:
250/500/1000* PW QSL CARDS
 Information to be printed on card (please print):

Callsign:

NAME

ADDRESS

Post Code

I enclose remittance for £ made payable to
IPC MAGAZINES LTD.
 * Please circle number required.



AMATEUR BANDS

by Eric Dowdeswell G4AR

Some readers who have decided to fit a digital frequency readout to their receiver have mentioned one or two problems that have arisen in consequence. Usually, when the display is reading the frequency correctly from a known station, the signal strength is down, but may be peaked by slight retuning when the frequency indication then becomes incorrect.

Now there are some inter-dependent points here that ought to be understood. First of all, it is the receiver's local oscillator frequency that is actually being measured and not the signal itself. But because the oscillator is operating, in a simple superhet, at the signal plus the frequency of the intermediate amplifier stages (i.f.) this "offset" equal to the i.f. has to be allowed for in the digital readout circuitry. So if the readout unit has a fixed offset of, say, 455kHz and your set has an i.f. of 465kHz then the signal will be very weak or even inaudible at 10kHz off the i.f. but can be peaked by retuning, when the readout frequency will be wrong by about 10kHz.

So it is very important for best results that the offset should be adjustable, and this should be ascertained either from the circuit diagram of the digital display or from the supplier. The precise centre of the i.f. passband may vary from the nominal figure quoted in the manual, such as 455, 465 or 470kHz, and must never be taken as gospel. This particularly applies to older sets with tunable i.f. transformers, where the set may have been aligned several times in its lifetime and the original i.f. shifted considerably from its nominal value, especially if it has been done by ear rather than with proper test equipment.

So the answer to adding a digital display to a receiver is to tune in to a broadcast station of known frequency and to peak it carefully using the set's S-meter, or a d.c. voltmeter connected across the a.g.c. line and earth, and then to adjust the digital display offset until the indicated frequency is correct. This procedure is particularly essential with a receiver having a crystal or mechanical filter in the i.f., where the passband may be quite narrow and careful tuning is necessary.

When tuning to s.s.b. stations it should be remembered that to resolve speech correctly the set's carrier insertion oscillator (or b.f.o.) has to be adjusted very precisely indeed to place the signal on the right part of the i.f. response

curve. When the tuning is correct the indicated frequency will be slightly different from the nominal carrier frequency of the transmitter, but this is not of great importance in amateur work.

One last warning. When using a broadcast station to check the digital display indication, use a station belonging to a network of known repute such as the BBC. Avoid stations in obscure places in Asia, Africa and South America who make changes to their nominal frequencies, often to avoid interference. A crystal calibrator can be used of course but it is nice to pick up a station of known frequency and see the display agree with it!

Here and There

It's hallo and congrats to **Bill Kerr** of Aldershot, Hants, who passed his RAE and intends to get the code test over with so that he can get his G4 straight away. The new format for the RAE instituted this year does not seem to have had any effect on the speed at which the exam results are issued but let us not condemn the system until after the forthcoming exam this month.

In Haverfordwest, Dyfed, **Andrew Price** has got off to a good start in amateur radio with an HAC straight receiver, courtesy of Dad, but so far it's mostly DX like Radio Moscow! However Andrew realises that it is better if he gets a communications style set in due course.

An interesting letter from **Tim Harrowell** G3IMI of Harrow, Middx who wrote to Yaesu about an improved filter for his FRG-7 and got back a detailed description on fitting one of the filters as used in the FRG-7000 digital readout receiver. If anyone with an unmodified FRG-7 is interested I'll send a copy of Tim's letter. Send me a s.a.e. with the outside envelope marked "FRG-7" and I'll oblige, but do not include any other correspondence. Tim is now happy with his FRG-7 on s.s.b!

The response to my bit on CB radio evoked a lot of agreement on the attractiveness of "illegality" to those who use CB here, but I'd like to make it clear that I support CB in the UK provided it is put on the right frequency, preferably v.h.f. or u.h.f. One or two readers still thought it ought to be a quick way to working the world!

Around the World

Yards of copy from RTTY addict **Dennis Sheppard** (Sheerness, Kent) convinces me that he is quite active in that mode! He's very pleased with the results obtained with a delta loop on 10m and is hoping to get two more masts up soon to support other loops. He is using a Windom for other bands. He found stuff like JA1DSI, K7BV, KE4V, PS7JA, PY2YFG, VE3JKZ, and 4X4MR on 10m with JA1ACB, TI2CAH, VK2ADZ and 5R8AL in

STOP! ... THIS IS WHERE SHORT WAVE LISTENING BEGINS



£214 inc. VAT

THE SHOP THAT SPECIALISES IN HAM RADIO

RECEIVERS - TRANSMITTERS
TRANSCEIVERS - HF - VHF - UHF
FREE SECURICOR DELIVERY



£178 inc. VAT

The above are two firm favourites and as our many hundreds of customers know, each receiver we sell has to pass a stringent pre-delivery check. If they don't meet the specification they are rejected (that's why you'll only find certain models in stock with us!) As we supply many Government departments with our equipment, we have to maintain this very tight control but this extra service we provide is absolutely free. So is our 24 hour Securicor delivery.

A good bit of news for 1980 is that the beautiful, new R1000 receiver from Trio should be available by the time you read this. This is sure to be a winner at its expected price of just under £300 with complete coverage of the medium wave and shortwave spectrum, 3 filters and digital readout. Our initial deliveries will be limited and, of course, not a single unit will be released by us until our standard performance checks have been carried out on each individual unit. It takes time but isn't it worth the peace of mind to know that the unit you buy from us will be operating at the peak of performance.



AND NOW VHF!

Yes, the TM56B receiver is ideal for home and car, having both 12v DC and 240V AC mains supplies built-in. We've already sold hundreds. It covers all the popular amateur VHF channels and repeaters. It also features automatic scanning of up to 4 channels of your choice. The amateur band version is £106. We can also supply a marine version with 10 channels fitted at £115 - as used by coast guards and river pilots, etc.

STOP PRESS NEW R-1000 receiver is the latest receiver from Trio. 200KHz-30MHz and digital readout at a very realistic price. Send 10p stamp for full details.
Opening hours **MON-SAT 9.00 a.m.-5.30 p.m. E.C. Wed 1.00 p.m.**

WATERS & STANTON ELECTRONICS
18-20 MAIN ROAD, HOCKLEY, ESSEX. TEL: HOCKLEY (03704) 6835



TRIO R1000

THIS RECEIVER IS SO ADVANCED, IT MAKES EVERYTHING ELSE OBSOLETE
200KHz-30MHz continuous. Digital Readout. All Mode. Switched Filters. Clock & Timer.
AND ONLY £298 inc. VAT.

For all that's good in Amateur Radio, contact;
LOWE ELECTRONICS LTD., 119 Cavendish Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817.
For full catalogue, simply send 45p in stamps and request catalogue CPW.



NEW! ONLY FROM US

The HELISCAN Wall-to-Wall Aerial

A specially developed high-tensile receiving antenna giving superb results. Use it indoors or out — from wall-to-wall, from point-to-point, or even from pillar-to-post!

INTRODUCTORY PRICE — JUST £15.00 INC. VAT

SPECIAL OFFER

The finest-value general-coverage synthesised communications receiver in its class.



FRG-7
£210 inc. VAT and Heliscan aerial

NOW AVAILABLE. External digital display giving accurate frequency readout while still retaining the analogue tuning facility. **A MUST** for the serious FRG-7 owner.



£49 inc. VAT

AMATEUR RADIO EXCHANGE 2 Northfield Road, Ealing, London, W13.

Easy terms up to 2 years

Credit Card sales by telephone

Closed all day Wednesday

Phone 01 579 5311

for details of current stocks, new and secondhand

General Coverage Communications Receiver FRG-7



● 0.5-29.9MHz Coverage with 10kHz Readout

The FRG-7 is a precision-built all-purpose communications receiver featuring all solid state construction for long life and high performance. Utilizing the Wadley Loop drift cancellation system, in conjunction with a triple conversion super-heterodyne circuit, the FRG-7 boasts high sensitivity along with excellent stability. It provides broadcast listeners with such features as a 3-position tone selector, an RF attenuator, and an automatic noise suppression circuit. For many years of satisfying reception the FRG-7 is the receiver for you. Free Securicor Delivery £210.

WIDE RANGE OF NEW and USED RECEIVERS and TRANSCEIVERS



Open 7 days a week. Sundays 11-3.00 pm.

AMCOMM SERVICES

194A Northolt Road, South Harrow, Middx.

01-864 1166

01-422 9585

Western

THE COMMUNICATIONS SPECIALISTS EVERYTHING FOR THE RADIO AMATEUR TWO METRE FM PORTABLE

TR-2300

A compact 80 channel FM transceiver for the 2 metre band. Engineered with all the latest techniques.

- ★ Small and lightweight.
- ★ Full coverage 144-146MHz in 25kHz steps.
- ★ Repeater shift and tone access.
- ★ Fully synthesised — no crystals to buy.
- ★ Charger and case included

OPTIONAL ACCESSORIES

RA-1	Helical antenna	£6.90
MB-2	Mobile bracket	£18.95
VB-2300	10 watt amplifier	£59.00
NICAD	Set of 10 nicads	£10.35

£193 inc. VAT



Send large SAE for further details of this and other equipment — or use our Answerphone after hours.

Western Electronics (UK) Ltd

HEAD OFFICE (All Mail/Enquiries)

FAIRFIELD ESTATE

LOUTH, LINCS, LN11 0JH

Tel: Louth (0507) 604955/6/7

ACCESS
VISA
H.P.

Madagascar on 15m. Twenty metres came up with AH6D in Hawaii, FK8BH in New Caledonia, FP8DF, PS7CP, VK2EG, VK7HV, ZS1Z and 3D2BM. Dennis has been monitoring conditions on 10m via the VP9BA beacon on 28.283MHz.

The Drake R4C receiver of **Bernard Hughes** of Worcester has not been idle with catches like D4CBC, FM7WS, KP4AAL, OX3HA, PY7FUP, XE1ABC and YS9RVE for some pretty good DX on 3.5MHz. On 21 it was CO2OM, KX6SA, VR3AH, VS6YV, and 9LIAP while 28MHz brought in S8AAT, VP8QJ, VU2RYX, YB0WR, 3B8CF and 9L1CA. Bernard has dipoles for each band plus a 66ft wire for general use.

Bill Rendell, down in Truro, Cornwall, is engaged on a personal target of hearing the antipodes at least daily and to date had done so for 130 days. He got worried one day when VK3MO was down to a 5 and 8! For those who have not heard him, VK3MO sports an 8-element (yes, eight!) quad, four of them at 47ft and the other four at 120ft! A rarity was VK8OB of Alice Springs on 15m at 1428GMT where he has also found VK1KB, VP8SB, VS6HG, VQ9DS on Diego Garcia (QSL Box 6168, APO San Francisco 96519) and also VQ9JJ of the same place but QSL W5RU. Also on 15m were: 3B8CF (QSL WA2NHE), 3D6BP (QSL W10X) and 3V8ONU (QSL DK6NF). On 20m Bill found C5AAP, HP1XOJ, VP8QI on Argentine Is and XT2AZ who, says Bill, is a new mate for XT2AV.

A new a.t.u. built by **Dave Coggins** (Knutsford, Cheshire) also has a crystal calibrator in it which he is finding invaluable, as the calibrator "on" position switches the aerial out, leaving good clean markers. His DX160 and 66ft aerial found good DX from 10 to 160m like AP2KS, VS6FI, VU2DK and VQ9JC on 10m, KG6SW and TR8RG on 15 and C21AM (Nauru), FO8AK, YJ8PD, ZK1BQ, and 3D2WR on Fiji on 20m. Top Band came up with VP2KAD on St Kitts working into Europe in the early hours of the morning, around 1850kHz.

Bob Bell of Blyth, Northumberland, has been spending his hard-earned cash on a new garden shed to accommodate his FRG-7, thereby losing all the TV mush plaguing him in the past. Double glazing looks like some long winter sessions are in the offing! Personally, I have always maintained, quite wrongly of course, that the best DX is got on a cold crisp winter's night when there is a lovely full moon shining! On 28MHz it was ZS6PP, HK4EIM for Bob, with VK8NDZ, JA6GDP, ZF1MT, PS7JD and VK1KB on 21MHz using a.t.u. and a 75ft wire or 33ft vertical.

A short log from brothers **John and Steven Goodier** (Marple, Manchester), who have both been hard at it for the RAE, so let's wish them luck and hope *PW* is out soon enough for them to read this. Their FRG-7 snagged a nice one in J27AW in Djibouti, on the mainland across from Aden if you look at the map, plus another lovely in VK0PK on MacQuarrie Is, VP8VN on South Sandwich

Is and VR1PS in the Gilberts, not to mention YJ8XR in the New Hebrides, so it seems the lads have their own propagation duct to that part of the world! From one extreme to the other, with **David Rhymes**, living near Oxford, dumping his 1155 set he's had for 30 years for a digital readout FRG-7000! I imagine he noticed a difference! He has three long wires so it is not surprising he logged C6ACY, HH2A, J6LCT, N6AFH on US Samoa, VP2KC, and VP8SB of Adelaide Is, all on 20m, with CP8AB and 9N1MM of Kathmandu on 15m, and C5AAP with VS6FI on the 10m band.

Allan Stevens (Crowthorne, Berks) expresses the hope that *PW* will soon be back on its publication schedule so that the DX info will be of some use to him! Several readers have suggested that a note giving the reasons for the delays might not come amiss but, so far, not a peep from Hon Editor! Allan was pleased to find K2ODX who became HP1XPK when the Canal Zone changed status recently, plus 3D6BW, 6Y5HM and VU2GO on 28MHz. 15m produced 3B8CF, 4N0MP (Yugoslavia) and UM8FK.

Peter Hawkes of Stourbridge (W. Mids) was delighted to find that G8RTP was a workmate so a firm link has been forged. His DX160 and 55ft aerial stuck mainly to the higher frequency bands with 10m providing 5Z4CD, HZ1AB, with VQ9DS and "579WARC" on 15m. Looks like a wise guy here! 20m looked like SU1ER, C6ACM, and VP8PU. However, a brief look on 7MHz found 8P6AH and CM1RH for a rare one with 80m bringing K6SVL/VP9, YV5ANS and C31LC.

All the above reports except the first are for s.s.b.

Winter Sports

With winter upon us there is only one place to be, if not in the shack, and that is at the local radio club! So it's the **St Helens ARC**, Wednesdays at YMCA, 107 Corporation Street with a warm welcome at 7.45pm and don't forget the Morse classes beforehand. Write to: Paul Gaskell G8PQD, 131 Greenfield Road, or ring 25472. **Maidenhead ARC**, first Thursday and third Tuesday every month at 7.45pm at the Red Cross Centre, The Crescent, with details of meetings from John Patrick G3TWG, Bedford Lodge, Camden Place, Bourne End, Bucks, or ring 25275.

Only programme detail I have for the **Edgware RS** is a bumper pre-Christmas junk sale on Dec 13 which ought to be well worth while. Otherwise meetings on second and fourth Thursdays at the Watling Community Centre, 145 Orange Hill Road, Burnt Oak at 8pm. Innovation in October was a DF hunt using Top Band and, says the *Edgware Ham News*, "no complicated or expensive gear. Complexity is oft the way to get lost in a superior fashion." Too true! Incidentally, the Edgware "B" station was leader in the open section on 1.8MHz in this year's NFD and second in the restricted section. Publicity Officer (no less!) is Howard Drury G4HMD, 39 Wemborough Road, Stanmore, Middx.

Ken Crouch has got himself a handy callsign G8KEN! He's been telling me about the **Dover RC**, of which he is chairman, and which meets at the YMCA, Godwin Road on Wednesdays. Club call is G3YMD and the "Young Men of Dover" would welcome new members so trot along on Dec 12 for a talk, amongst other attractions, on radio isotopes or/and Dec 19 for a grand Christmas party, venue to be announced later. Contact: G4EGQ on Dover 203000.

Last meeting of the year for the **Torbay ARS** is Dec 15 when the society's Christmas party will be held at the club's HQ at Bath Lane, rear of 94 Belgrave Road, Torquay. Recent issue of the club magazine *Tars Talk*

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

encloses a complete membership list which must be of great value especially to the newcomer to the club. I wonder how many other clubs could benefit from issuing such a list. Membership Sec is C. Coker G4FCN, 2 Causeway Cottages, Ipplepen, Devon or telephone 812117.

Society secs, etc., should note that information on club meetings and the like must reach me at least six weeks in advance of publication in *PW*, and by the 15th of the relevant month, not forgetting that *PW*, normally, is published on the first Friday of the month but dated for the following month.

Let me wish all readers of *PW* and especially those who wade through this column all the very best of season's greetings. May Father Christmas's sledge be full of nothing but amateur radio goodies! Once again every good wish for the success of those who will be taking the December RAE.

BROADCAST BANDS

MEDIUM WAVE DX

by **Charles Molloy G8BUS**

There is a widely held belief that m.w. DXing is very difficult, that it requires a receiver with high sensitivity and narrow selectivity, that a directional aerial such as the m.w. loop is essential, and that considerable DXing experience is required before worthwhile results can be obtained.

There is an element of truth in all this but on the other hand there is a lot of DX to be found without too much difficulty. The correct time to listen is of major importance. Tune round the band during the day. Only a few signals will be heard as only the ground wave is being received. Sky wave reception (DX) is only possible when the path between transmitter and receiver is in darkness.

The medium waves are intended for local broadcasting and only a small number of signals will be beamed towards the DXer. He is really an eavesdropper into domestic broadcasting in other parts of the world. This means interference from stations nearer home and variable propagation on the DX path. Your signal may be good one night and absent the next. Slow fading is normal and can cause a DX signal to be missed very easily.

For Beginners

In order to introduce newcomers to DX on the medium waves I have rigged up an Eddystone EB36 broadcast receiver, an a.t.u. and a 60ft end-fed outdoor aerial and I hope to report DX heard with this set-up over the next month or two. The EB36 is intended for use as a marine receiver and is similar to the EC10. It has a tuned r.f. stage. The selectivity is fixed at 5kHz at the 6dB points, wider than I would like for DXing but similar to many receivers used by DXers.

Locate the French network on 1404kHz. It signs off at 2300 and when the carriers go off you should hear Conakry in the Republic of Guinea. The language is French, the announcement is "La voix de la Revolution" and it often broadcasts music which has been called

African Pops. Conakry is nearly always audible and is on the air most of the night. It suffers from occasional QRM from a Russian on the same channel.

Tune to Brussels on 927kHz. It signs off at 2245 and when the final tuning notes and the carrier are off you ought to hear Zykanthos in Greece. Reception is a bit variable but it can usually be heard until 2305 when it goes off for the night. Now tune up to 930kHz. With a bit of luck you may hear CJYQ in St John's Newfoundland. Remember though, slow fading is normal and conditions vary from night to night.

Beacons

"While tuning around the l.w. band with my 5-valve Philco and 60ft long wire I managed to pick up some odd signals in Morse between 300 and 375kHz," writes **G. R. Perry** from Cardiff. The signals you heard are navigation beacons and the identification in Morse is not a callsign but is an abbreviation based on locality. ORM on 316kHz is at Ormskirk near Southport.

Radio Officer **Colin Stewart** has listed some beacons in the range 290 to 310kHz that might be generating harmonics on the medium waves. The problem however has already been solved by **Geoff Halligey** who reports that SW on 930kHz is not a harmonic. It actually transmits on this frequency and it is located at Vyhkma in Estonia. Evidently there are quite a number of air navigation beacons operating on the medium waves, a band that is supposed to be reserved exclusively for broadcasting. Presumably they are sited so that no interference is caused in the service area of any medium wave transmitter and it is only the m.w. DXer who experiences this type of QRM.

Loop Problems

A tuning capacitor of 500pF is specified for use with the standard 40 inch m.w. loop. Although this value is not critical, for example a variable capacitor with a value of 470pF would do instead, a tuner of only 250pF is much too low. If a variable capacitor of this value is used then the loop will tune over the high frequency part of the medium waves only.

This happened to reader **A. C. Jacklin** who used a small, totally enclosed type of variable capacitor recovered from a scrap radio, reasoning that since the radio covered the medium waves then the tuner must have a value of 500pF. Unfortunately this is not so. Modern radios use high inductance tuning coils which are tuned by variable capacitors of around 250pF in value which are not suitable for use with a loop.

Why can't we have a loop with a high value of inductance? Because it would also have a high value of self capacitance. Modern tuning coils use ferrite cores which permit a high inductance to be obtained with low self capacitance. Ideally a loop should resonate with its own self capacitance at the highest frequency to be used. Then a variable capacitor is connected to it, which has a great enough value to tune to the lowest frequency required. In practice this is what happens with the 40 inch loop. It self-resonates around 1600kHz and 500pF is required to tune it to 540kHz. The number of turns determines the highest frequency, the capacitance of the tuner determines the lowest frequency.

Remotely Controlled Loops

There are occasions when a loop cannot be used beside the receiver, perhaps because of lack of space or because

the location is unsuitable. The solution is to have a remotely controlled loop higher in the house, probably in the loft.

Such a loop can be attached to a rotator of the type that Radio Amateurs use with their v.h.f. aerials, or it can be left pointing in the best direction for North American DX, for example. A fixed loop can even be wound round the rafters, held in position by cup hooks.

How do you tune the loop? One method is by a varicap, using a circuit like the one in this column is the September issue. Why use a varicap? Why not run a length of cable from the main winding of the loop to a tuning capacitor located beside the receiver? Reader **George Harpur** tried this and found he could not tune the loop. The reason is that the capacitance of the cable was in parallel with the tuning capacitor and was detuning the loop. A 15ft length of coaxial cable with a capacitance of 20pF per foot would put 300pF in parallel with the tuner. The range of capacitance would then be from 300 (0+300) to 800pF (500+300) instead of 0 to 500pF.

It is possible to get round this problem by using cable that has a low capacitance. Standard 300Ω flat twin feeder has a separation of half an inch between conductors and a capacitance of 4pF per foot, so that a 15ft length will put only 60pF across the tuner. This may be enough to prevent the loop being tuned to a high enough frequency and you may have to remove a turn or two from the loop to counter this.

In order to tune to the l.f. end of the band, a higher value than 500pF may now be required but it is at least feasible to tune a remotely situated loop by this method. I have used 20ft of feeder and a 1000pF variable (twin gang 500pF) with success.

There is no problem with the normal connection between the single (link) turn and the aerial and earth inputs to the

receiver though you might just as well use 300Ω feeder for this as well. Twin 300Ω feeder is available from shops that cater for Radio Amateurs, who use it with folded dipoles.

Long Wave DX

"Is there such a thing as long wave DX?" asks **Christopher Steele** (East Ham) who is a newcomer to the hobby. Indeed there is and logs do appear in this column from time to time. Many receivers do not cover the long waves though. Propagation is similar to the medium waves but the ground wave travels much further. There are a few exotic catches to be made, such as Azilal in Morocco on 209kHz, Tipaza, Algeria on 256 and Turkey on 182kHz. The QSL cards shown here are from Europe No 1 on 182kHz which is not DX, and from Reykjavik, Iceland on 209kHz which is.

BROADCAST BANDS

SHORT-WAVE BROADCASTS

by **Charles Molloy G8BUS**


It is from readers of this column that I receive the stimulus for much of what I write, and a letter from **John Dainty** (BRS42293) is no exception. John says that information is difficult to come by on the listening (receiving) efficiency of aerials, most of the published material being orientated towards transmitting. He feels that one could get away with Paxolin insulators for receiving instead of ceramic or glass types.

Whatever the relative merits of Paxolin, glass or ceramic might be, there is no doubt that available information about aerials is orientated towards transmitting efficiency, the one notable exception being the information produced by G2DYM and mentioned in the October 1979 issue of this column.

Although the sensitivity of a receiver is measured in microvolts and consequently the current flowing into the receiver aerial socket will be in microamps or of that order, the wire usually specified for receiving aerials is capable of carrying enough current to supply an electric fire. If such heavy gauge wire is required for electrical reasons then why isn't it used for the winding on a ferrite rod aerial? High voltage insulators are clearly unnecessary for an aerial used solely for receiving, but they are often supplied in aerial kits. How has this situation arisen?

Reciprocity

In a contact between two radio amateurs, the same aerials are often used alternately for transmitting and receiving. A good transmitting aerial will also be a good receiving aerial. This statement is justified by the law of reciprocity which means simply that an electric circuit will have the same properties in either direction, which is only common sense. Consequently, amateur radio literature concentrates on transmitting aerials.

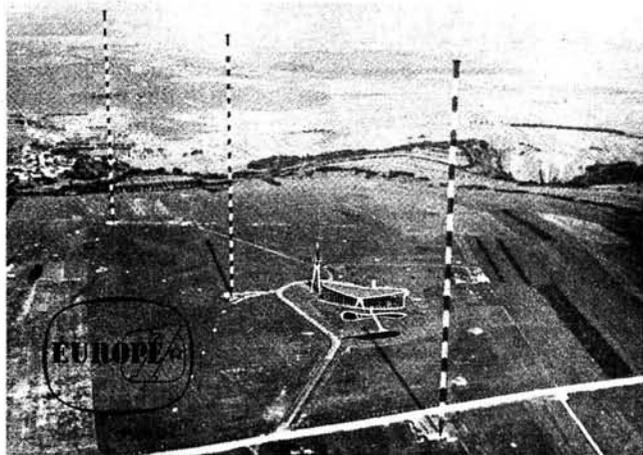

Receiving Aerials

One must be careful though how to apply reciprocity. If I tune into a broadcasting station which is pumping 100kW into an 800ft mast then clearly it would be to my advantage to swap places with the transmitter. I had a letter from a reader not so long ago who tried an 800ft mast for DXing and the results were phenomenal. But would the transmitting engineer care to have my long wire, to say nothing of a ferrite rod aerial? Obviously not. So a good receiving aerial need not match up to the standards required for transmitting.

This leaves the field wide open for the experimenter. He can try anything as there are few precedents. The proverbial piece of wet string will not do, but it is worth remembering that in the early days of wireless bedsprings were often tried as an aerial. I tried it myself as a schoolboy though not, I may add, with a mains operated receiver.

For a number of years I used nothing else for outdoor aerials except the plastic-covered steel wire available in garden shops. It is cheap, easily obtainable in lengths up to 600ft and withstands gale force winds from the Irish Sea. A couple of years ago I replaced this wire on my 90ft long wire with plastic-covered, copper-coated steel wire which in theory should give better results. I haven't noticed any improvement and when the 90 footer is next due for an overhaul it will be changed back to garden wire.

120 Metre Band (2300 to 3498kHz)

"Is it possible to hear any broadcasting stations on the 120m band," asks **Jim Edwards** who lives near Wigan. Jim has been successful on the 75m and 90m tropical bands but so far he has heard nothing on 120.

It is difficult on 120. Reception is similar to the medium waves with slow fading, and of course a path of darkness between Tx and Rx is essential in order to hear anything other than MSF on 2500kHz. MSF is the time and frequency standard station at Teddington and is useful for locating the h.f. end of the band. An added disadvantage on 120 is telegraph interference as the band is only used for broadcasting in tropical areas. I do listen a bit on 120m and a few extracts from my log may help. The receiver is a BRT 400 with digital readout, connected to a 60ft long wire via an a.t.u.

On 18 August I picked up a Chinese station on 2490kHz at 2030 GMT, SIO 232 and another on out-of-band 2600kHz, SIO 333 a few minutes later. These two can usually be heard and 2490 is easy to locate as it is just below MSF. The two stations were carrying different programmes which agrees with the *WRTVH* which lists them both at Fuzhou. September 13 brought Gweilo in Zimbabwe/Rhodesia on 2425kHz at 2130. It was only audible on peaks and could easily have been missed. Two harmonics of m.w. stations were picked up on September 16. BBC Radio 3 was SIO 322 on 2430kHz (twice 1215) at 2035 and a Yugoslav was heard on 2466 (2 X 1133), SIO 232 at 2040.

World Radio and TV Handbook

The 1980 edition of the *WRTVH* will be available in January at an unchanged price of £8.50. It is supplied by Argus Books, 14 St James Road, Watford, Herts, though copies can be ordered from W. H. Smith. **Andy Sennitt**, who is the Assistant Editor, tells me that the *Listen to the World* section will be re-instated with articles on receivers,

propagation, etc. Perhaps the most valuable part of the handbook is the country by country sections which give addresses, interval signals, frequencies and schedules. There is also a Newsletter which up-dates the schedules in May, August and September.

Readers' Letters

An SRX-30, a.t.u. and 40ft inverted "L" aerial are in use in Leeds by **B. Woodcock** who has heard two unidentified stations. On 5300kHz he picked up a broadcast calling itself Shannon Volmet, which he cannot trace in the *WRTVH*. This is not a broadcasting station. It is a "met" station and is not intended for reception by the general public. The second was on 17 820 and requested postcards giving details of reception to Mailbox 1, Libreville. The country is the Republic of Gabon in West Africa which is conducting test transmissions on a number of frequencies. The *WRTVH* lists 6030, 7200, 15 300 and 9650kHz with powers of 500kW.

Reader **T. J. Jordan** is looking for a photocopy or an original instruction handbook for his newly acquired Trio 9R-59D receiver. Replies direct to: 12 Upton Lane, Forest Gate, London E7 9PA. Postage and copying costs will be refunded. The QSL policy of Radio Finland is referred to by **James Jackson** of Dunfermline. Frankly this station puzzles me. Over the air they say QSL cards are out, Listeners cards are in. If you write, you get a QSL card.

"I have found a number of stations operating between 8 and 9MHz," writes **Richard Everitt** who uses a Telefunken domestic receiver with 40ft long wire. They are probably images of 31m band stations which are usually suppressed in the r.f. stages of a more complicated receiver. A station can be received on two positions on the dial: when the local oscillator is higher than the station by the amount of the i.f. (correct), and when it is lower than the station by the same amount (incorrect). The two are separated by twice the value of the i.f. which is usually 910kHz (2 times 455) or 930kHz (2 times 465). Images of the 31m band will be found between 8.5 and 9MHz approximately.

"Has anyone succeeded in obtaining a QSL from the Voice of Chile?" enquires **Dave Jones** of Normanton, West Yorks, who sounds rather exasperated. Logging a Latin American is only the start of the trail Dave, you should try to get a QSL from some m.w. Latin Americans. Although Dave now uses a DR26 with digital readout he mentions his earlier receiver, a Grundig TR600, which he bought for £15 in 1973. It pulled in 68 countries and he heartily recommends this set to newcomers, if they can find one, as the model has gone off the market.

Roy Patrick (Derby) points out that many South Americans are now excellent signals in the 16 and 19m bands. He has heard the Voice of Chile in English at 2100 on 17 715, Radio Nacional Brazil at 2000 on 15 270, HCJB Quito Ecuador on 17 785 and 15 295 with DX Party Line at 2130 on Mondays, Thursdays and Saturdays.

Brian Davis (Bath) has "rejoined the scene" after some 20 years and he now has a National Panasonic DR28 with built-in telescopic aerial. He does his late evening DXing in real comfort in bed. If I brought all my gear into the bedroom there would be a domestic crisis! Brian is puzzled with Radio Amateurs on radiotelephony who are unreadable as though with the b.f.o. on. This is s.s.b. and you have to switch on the b.f.o. to receive them. Further information from Eric Dowdeswell.

The Bristol Pathfinders DX Club now has a new Editor/Secretary who is Philip Grainger, 26 Beattie Street, South Shields, Tyne and Wear. The club issues a newsletter every two months and the annual subscription is £1.

VHF BANDS

by Ron Ham BRS15744

Although modern technology has provided us with very fine radio equipment, DX hunting will always depend upon the user's own ability to recognise and take advantage of the unusual ionospheric and tropospheric conditions when they prevail.

Solar

On September 24, **Cmdr Henry Hatfield**, Sevenoaks, using his spectrohelioscope, observed 13 sunspot groups, two of them large, and recorded a 5-minute burst of radio noise at both 136 and 1296MHz. During the same day, **Ted Waring**, Bristol, counted 61 individual spots, so there was little surprise when, at 0300 on the 25th, the BBC World Service announced that an ionospheric disturbance was affecting their north-Atlantic signal paths. Ted also counted 59 spots on the 27th, 63 on the 29th, 53 on October 1, 31 on the 5th, 63 on the 7th, 55 on the 9th and 34 on the 13th. Both Henry and I recorded varying degrees of solar noise, at 136 and 146MHz respectively, almost daily between September 30 and October 16. Around 1150 on the 5th, we both recorded an individual burst, Fig. 1, which lasted for four minutes as did **Robin Knight** of the South East Essex Astronomical Society, at 60MHz. While Robin was recording noise at 60MHz on the 10th and 11th, I heard strong individual bursts on 50MHz at 0730 and 0920 on the 12th, with only a vertical dipole feeding my R216 receiver. The general solar noise was very strong on the 13th and during the late afternoon, **John Cooper** G8NGO, Cowfold, Sussex, also heard the noise when he turned his 2m beam toward the west and the setting sun.

The 10 Metre Band

"10 metres has really improved," writes **N. Clarke** BRS 34306, Knottingley, West Yorkshire, on October 10.

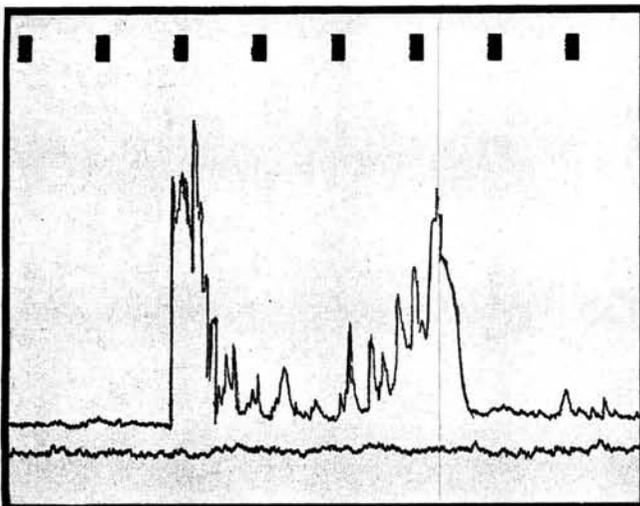


Fig. 1: Four minute solar burst recorded by the author at 146MHz at midday on October 5. The lower trace is the normal receiver noise level recorded on the 4th

"From around 1130, US stations were rolling in and remained so for the next nine hours. On favourable days, Florida beacon N4RD, 28.207MHz, has been riding above S9 for hours at a time and the Canadian beacon VE3TEN, 28.175MHz, has been S9 at times but faded out an hour or so before N4RD." Like **Alan Baker** G4GNX, Newhaven, **Ted Waring**, N. Clarke and I have heard the beacons at Bahrain A9XC, Bermuda VP9BA, Cyprus 5B4CY and Germany DL0IGI, on most days between September 20 and October 21. During one afternoon Alan had a c.w. QSO with W3LG, who was mobile at the time. On almost every day throughout the period Russian stations were very strong, and frequently so were the Australians, Japanese and north-Americans. At 1258 on the 4th, I heard a UA tell a W; "Your signal is fantastic" and the W replied with a report of 59 plus 15dB.

Harold Brodribb, St Leonards-On-Sea, Sussex, heard many harmonics of lower frequency broadcast stations between 28 and 31MHz on days when the band was wide open, "Imagine getting huge loudspeaker reception when both AR88LF and CR100 were tuned to these", writes Harold, who also reported hearing "marked round-the-world echo" on the BBC World Service transmissions in the 11m band on the 13th and 18th. During the early morning of the 16th, there were many strange noises on the band, some c.w. signals were chirpy and several s.s.b. stations were echoing. Around 0800 on the 17th there was a very strong echo on a German and a Hungarian station which stood out in a crowded band.

In his letter on October 8, **John Branegan** GM4IHJ, Saline, Fife, said that the m.u.f. was steadily climbing above 40MHz. Well, this continued John, because on several days I heard a multitude of beacons, broadcast harmonics, pagers, teleprinters and radiotelephone signals between 30 and 50MHz, above which there seemed to be a sharp cut off.

Aurora

During the late afternoon of September 18, John Branegan had c.w. contacts, via aurora, with G6GN and GW4FJK and heard tone-A signals from GM4DIJ, G4DSC, LA3WU, PE1BZD and the 2m beacons in Cornwall GB3CTC, Germany DL0PR, Northern Ireland GB3GI and Wrotham GB3VHF. John also had an auroral QSO with GM4IDR during the afternoon of the 20th and, by using the high scintillations on OSCARs 8J and 7A, located brief aurorae on October 6, 7 and 8.

Satellites

"I am still getting excellent DX on OSCAR-7B," writes John Branegan, and during the first week in October, he worked K0RZ in Boulder, Colorado, about 4350 miles and very close to 7Bs limit. "OSCAR-8 is still going well," says John. "I had five transatlantic QSOs in ten days." A weather satellite observer is now warning John when the auroral oval advances far enough south to interfere with his pictures.

DXTV

Stephen Haywood, Higham, Barnsley, is a keen s.w.l. and has now added a JVC 3050 television receiver to his station for DXTV work, **Denis Kenneally**, Co Cork, has already received pictures in Band 1, during the sporadic-E season, from stations in Austria, Germany, Iceland, Norway and Poland on a 12in Bush portable using its own telescopic aerial. "From 1700 on September 18, I received weak, unidentified, periodic bursts of video from the east on Ch. R1, lasting an hour or so," writes **Sam Faulkner**,



Fig. 2: Programme introduction, believed to have originated from Bulgaria, received by Sam Faulkner at 1650 on September 5 on Channel R1 49.75MHz

Burton-on-Trent. "All very tantalising," says John Branegan, who, like me, has seen many short bursts of picture on R1 during the early mornings of late September and early October. Although these bursts were brief I did catch a glimpse of a familiar Russian test card at 0639 on October 14.

"During the latter half of September, I was able to log RTE 1 (Radio Telefis Eireann) in Band III on several occasions", says Sam, and during the morning of the 29th he watched part of the Pope's visit to Ireland. Sam also sent a photograph of a DXTV signal, Fig. 2, which he received on Ch. R1 on September 5.

Band I conditions were even more tantalising during the early mornings of October 16 to 21 inclusive because there was a mixture of signals on the screen and what looked like several images on each one. Although the signals were strong, captions were out of focus, and often there were one or more wobbly black lines, also with images, down the centre of the picture. At 0825 on the 17th, I saw an announcer's face just to the left of a vertical line and an image each side of it. At 0900 on the 18th a clock appeared from the jumble, but there were too many images to see the time. This was followed by a caption, from which I could see the letters CCCP and then an announcer became predominant for about two minutes, after which the signals and their images returned to a jumble. An extra letter from John Branegan says: "A lot of co-channel interference with several stations present at once. Azimuth 070 to 080 degrees suggests origin in central Russia."

Slow Scan Television

After finding the 10m band in such good shape on September 22, Sam Faulkner, using a KW202 and Robot 400 with Hitachi 9in CCTV monitor, began monitoring 28.680MHz and up to October 12, had found some really excellent SSTV signals coming across the Atlantic. During the period, Sam logged two stations from Argentina, two from Canada, one from England and 20 from the USA, Fig. 3. On October 7, Sam received pictures from VE3JW who was operating the exhibition SSTV station at the Museum of Science and Technology in Ottawa and, apart from seeing the operator and his gear, there were pictures of some of the many people attending the museum. "I enjoy this side of the hobby very much", writes Sam, "and its rising popularity is reflected by the increasing number of new calls on the bands. Between September 15 and October 12, Sam logged signals from DL,

EA, F, HB, I, JA, LA, OE, OH, OK, SM and YU on the 20m band, proving that there are plenty of SSTV enthusiasts about.

Tropospheric

Conditions on v.h.f. were greatly improved while the atmospheric pressure was above 30.0in between September 22, and October 3, reaching a maximum of 30.5in on the 28th. Around 0800 on September 24, 27, 30 and October 3, I received strong signals from the *Bristol Channel* repeater GB3BC, plus at times the Kent repeater GB3KR, and pictures from the IBA transmitter at Lichfield on Channel 8, 189MHz.

During the early evening of October 1, **Ken Smith** BRS20001, Horsham, Sussex, heard several French broadcast stations in Band II and I heard them again at 0806 on the 3rd. At 2107 on the 2nd, G4GNX worked F6FLB via the French repeater FZ2VHF, R5, Boulogne. The pressure remained low until midnight on the 16th when it rocketed up from 29.9in to reach 30.4in by 1800 on the 18th and, true to form, the v.h.f. bands opened up. During the evening of the 18th, Ken Smith, using a Bush VTR 178 portable with an outside rod aerial, heard about seven French broadcast stations in Band II and I received strong signals through GB3BC, R6, GB3KR, R4, and pictures from Lichfield. Around 2240 on the 19th, Alan Baker worked DD3AW and OS7EH and at 2326 F1EWP, in Chateauraux (500km) on 2m s.s.b. At 2240 on the 20th, Alan again worked a German station, DF3PR/P, on 2m s.s.b. and during the morning of the 21st, **Graham Matthews** G8SAG, worked a GW from Horsham, Sussex, using 1 watt from a TR2300 into a 5-element quad aerial.

New VHF operators

Congratulations to **Gerry Cogger**, **Margaret Hill**, **John Trimmer** and **Chick Tutt** on passing the RAE. They now have the callsigns: G8TUQ, G8TTT, G8TMX and G8TOZ respectively. All are active on 2m and I look forward to hearing more from them in the future.

News Items

Graham Kehily G4IBQ, has worked 40 countries on 20 and 10m, using a KW2000A since he was licensed last April. Graham wants to renovate an old Hallicrafters Super Sky Rider, SX28 communications receiver and requires a manual or technical gen, any offers please to: G4IBQ, 59, Bradbourne Park Road, Sevenoaks, Kent.

Before **David Wakefield** G8RVK, Worthing, joined the RAF on October 10, he took part in the RSGB 2m contest and worked seven countries in 2½ hours including F, GJ and PAO.

Plans are well in hand for the Sussex Mobile Rally to be held at Brighton Race Course on June 1, 1980, which will include demonstration and talk-in stations on the h.f., v.h.f. and u.h.f. bands. This venture is a joint effort of the Sussex radio clubs and the officers of the organising committee are G4GNX, Chairman, G8JVE, vice-Chairman, G8TMX, Secretary and G8TOZ, Treasurer.

Alan Manning, Bonnyrigg, Midlothian, has recently joined the British Astronomical Association and is particularly interested in satellite tracking by radio and radio astronomy, and is constructing gear for 23 and 13cm.

If you know of a handicapped person who could benefit from short-wave radio as a broadcast listener, then put them in touch with Handicapped Aid Programme "UK",



Fig. 3: Slow scan TV pictures received in the 10m band from Argentina, Canada and the USA by Sam Faulkner

c/o European DX Council, PO Box 4, St Ives, Huntingdon, Cambs PE17 4FE. The idea of HAP UK is to promote the hobby of short-wave radio broadcast band listening among the physically disabled and housebound, many of whom are unaware that radio can bring the world into their home. HAP-UK also need help with local organising, giving advice and installing sets and aerials and will be pleased to send you all details.

Microwaves

A microwave round table was held at the headquarters of the Martlesham Amateur Radio Society on September 30. "There was an excellent lecture with talks on propagation, microwave feeds for dishes, and Moonbounce complete with tape recordings of echoes from the Moon," writes **John Tye** G4BYV, Dereham, Norfolk. One of the outstanding features was a 10GHz receiver which was working and receiving signals from **Mike Walters** G3JVL, in Hayling Island. The organisers plan to hold another event there next year, and hope to invite some Continental amateurs over.

Stop Press

John Branegan reports the 6 metre band wide open between 1526 and 1740 on October 25. Strong signals were heard on 50.0MHz (c.w.) and 50.1MHz (s.s.b.), including stations W2UTH, W1XM and VE2CRA. More details next month.



Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with the PRACTICAL WIRELESS logo. Gold Letra-set supplied for self blocking of volume numbers and years.

Price £3.75 including postage, packing and VAT. Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

it's easy with **EASIBIND**

✂

Order form PRACTICAL WIRELESS

I enclose P.O./cheque value
for.....binders

Years required
(BLOCK LETTERS PLEASE)


Name

Address

Date

Simply ahead . .

ILP'S NEW GENERATION OF HIGH

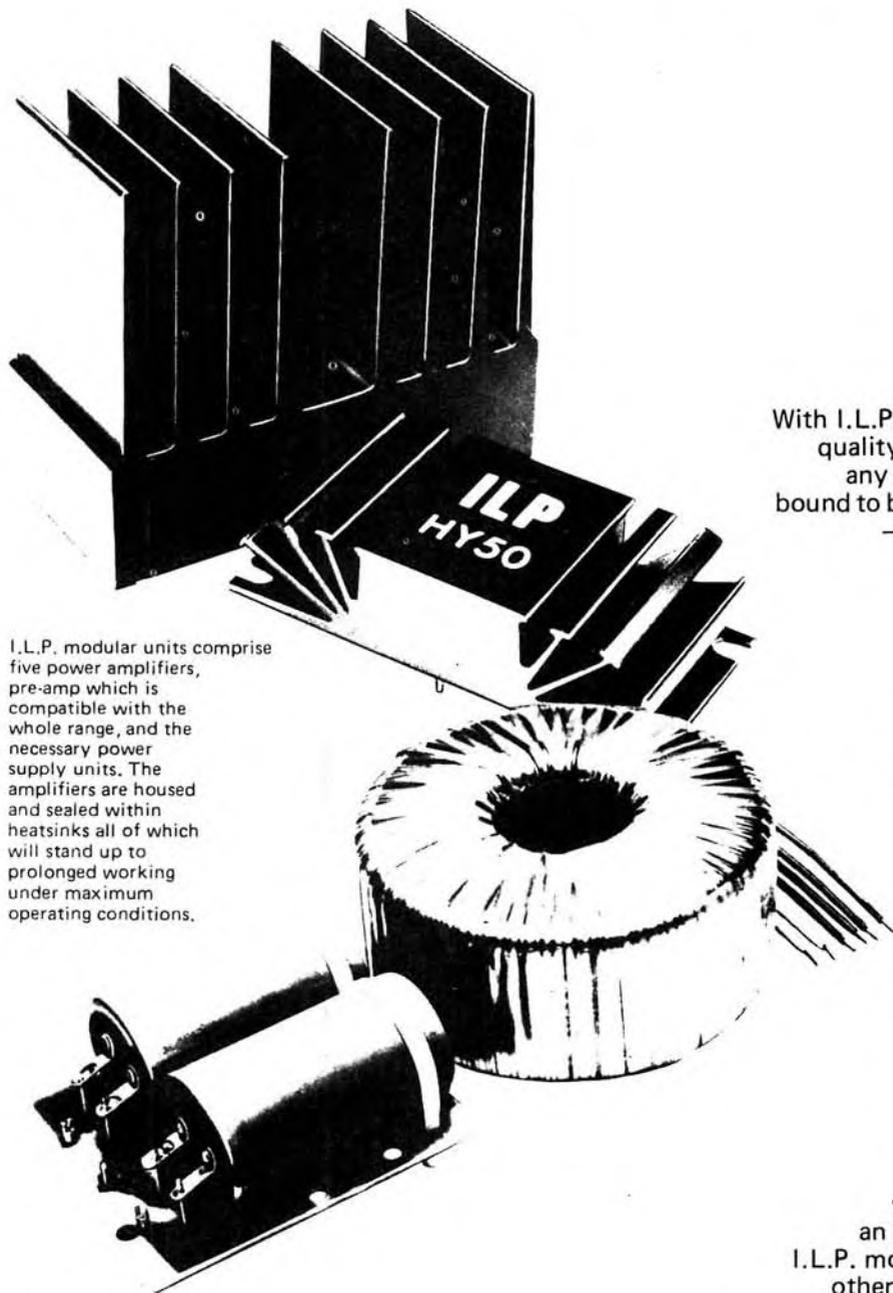

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.



With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance — and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain — the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.

**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

and staying there

PERFORMANCE MODULAR UNITS


HY5 PRE-AMPLIFIER

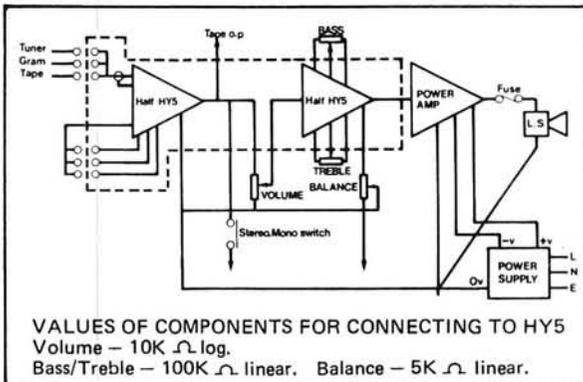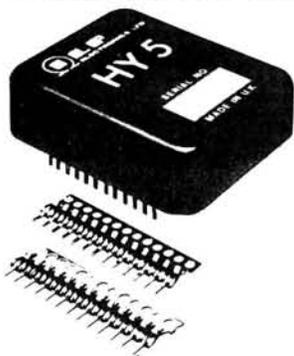

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm, and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz - 0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

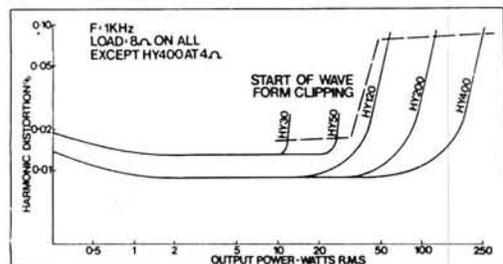

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance - all models 4 - 16 Ω
 Input sensitivity - all models 500 mV
 Input impedance - all models 100K Ω
 Frequency response - all models 10Hz - 45Hz - 3dB

THE POWER SUPPLY UNITS

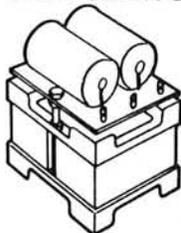

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30	$\pm 15V$ at 100ma to drive up to five HY5 pre-amps	£4.50 + £0.68 VAT
PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU 180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT

**NO QUIBBLE
5 YEAR GUARANTEE**

7-DAY DESPATCH ON ALL ORDERS

INTEGRAL HEATSINKS

BRITISH DESIGN AND MANUFACTURE

FREEPOST SERVICE - see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope - we pay postage on all letters sent to us by readers of this journal.



**I.L.P.
ELECTRONICS LTD.**

FREEPOST 1 Graham Bell House, Roper Close,
 Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 Telex 965780

Please supply Total purchase price £

I enclose Cheque Postal Orders International Money Order


Please debit my Account/Barclaycard Account No.

NAME

ADDRESS

Signature

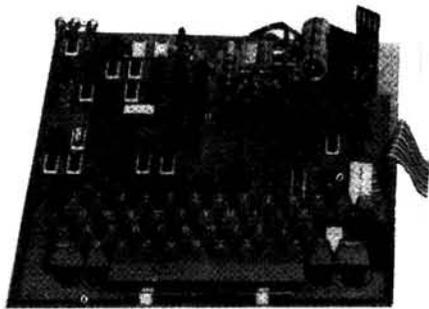COMPUKIT UK101 LOW COST SUPERBOARD IN KIT FORM



COMPUKIT UK101

ELENCO - 3½ digit D.V.M. as nationally advertised.

ONLY £55 + V.A.T. + DEL.

ORDER FROM:-

Contour Electronics

23 HIGH STREET,
STANSTEAD ABBOTTS,
WARE, HERTFORDSHIRE

SEND ONLY £10.00 DEPOSIT TO RESERVE ONE

An extended monitor on cassette will be supplied free of charge with each kit.

Simple Soldering due to clear and concise instructions compiled by Dr. T. Berk, BSc.PhD

NO EXTRAS NEEDED JUST HIT 'RETURN' AND GO.

Build, understand, and program your own computer for only a small outlay.

ONLY £219 + VAT + DEL.
including RF Modulator & Power supply.
Absolutely no extras.

FOR FURTHER DETAILS
Telephone: Ware 870218

The CompuKit UK101 has everything a one board 'superboard' should have.

- ★ Uses ultra-powerful 6502 microprocessor.
- ★ 50Hz Frame refresh for steady clear picture (U.S.A. products with 60Hz frame refresh always results in jittery displays).
- ★ 48 chars by 16 lines - 1K memory mapped video system providing high speed access to screen display enabling animated games and graphs.
- ★ Extensive 256 character set which includes full upper and lower case alphanumerics, Greek symbols for mathematical constants and numerous graphic characters enabling you to form almost any shape you desire anywhere on the screen.
- ★ 8K full Microsoft Basic in ROM compatible with PET, APPLE SORCERER hence taking the headache out of programming by using simple English statements. Much faster than currently available personal computers.
- ★ Professional 52 Key keyboard in 3 colours - software polled meaning that all debouncing and key decoding done in software.
- ★ Video output and UHF Highgrade modulator (8Mz Bandwidth) which connects direct to the aerial socket of your T.V. Channel 36 UHF.
- ★ Fully stabilised 5V power supply including transformer on board.
- ★ Standard KANSAS city tape interface providing high reliability program storage - use on any standard domestic tape or cassette recorder.
- ★ 4K user RAM expandable to 8K on board £49 extra.
- ★ 40 line expansion interface socket on board for attachment of extender card containing 24K RAM and disk controller. (Ohio Scientific compatible).
- ★ 6502 machine code accessible through powerful 2K machine code monitor on board.
- ★ High quality thru plated P.C.B. with all I.C.'s mounted on sockets.

FULL CONSTRUCTION DETAILS
IN P.E. AUG 1979 EDITION

AVAILABLE NOW

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln. LN2 1JF

VHF-UHF 800 MHz FETS BF 256C # 4 for 75p.
VHF POWER TRANSISTOR TYPE R5174 10 watt 175 MHz 13 volt # £2.50.
5 ASSORTED PIECES OF BLOB BOARD for £1.50.
VHF TRANSMITTING VARIABLE CAPACITORS 30-30pf # £2.20.
WIRE ENDED PIN DIODES for Transmit-Receive Switching # 40p each.
PAPER CAPACITORS 10uf 370V.A.C.W. 5½" x 2½" x 1½" # £1.50 each.
10K TYPE CRYSTALS 80M 3710KHz, 40M 7090KHz, 2M 8010 KHz all 40p.
1024 BIT FULLY DECODED STATIC RAM TYPE P2102 # £1.
VERNITRON FM 4 10.7MHz FILTERS # 50p, 3 for £1.
E304 VHF-UHF FET at 30p, 4 for £1.
FERRITE BEADS FX1115 at 15p doz.
OPTO ISOLATORS 1L-74 with data # 50p.
MINIATURE 12 WAY CERAMIC TAG STRIPS # 15p.
300 to 75 ohm BALUM TRANSFORMERS # 20p.
ELECTROLYTIC CAPACITORS 2000uf 450 v.w. 5½" x 3" # £2.25.
MULLARD POLYESTER CAPACITORS 1uf 160v.w. # 20p doz.
5 WATT to 39 NPN DARLINGTON TRANSISTOR at 3 for 50p.
SOLDER-IN FEED THRU's # 6.8pf, 300pf, 1000pf, All 20p doz.
COMPRESSION TRIMMERS 10pf, 30pf, 50pf, All at 10p each.
R.F. CHOKES 3 U.H., 5 U.H., 10 U.H., 22 U.H., 27 U.H., 60 U.H., All at 7p ea.
CERAMIC VALVEHOLDERS FOR PL 504 etc. # 15p each.
10 AMP TWO POLE MAKE TOGGLE SWITCH # 50p.
R.F. TRANSISTORS AF 239 # 50p, 2N 5179 # 50p, 2N 5180 # 50p, 8FY 90 # 50p, 2N 918 # 25p, MULLARD STRIPLINE BF 362 # 25p.
12 VOLT MINIATURE 2 POLE CHANGE OVER RELAY # 60p.
LED's 0.2" Red # 15p, Green # 18p, TIL 209 # 15p.
TEXAS BRIDGES 100 PIV 1 amp # 30p, 200 PIV 4 amp # 60p.
PLESSEY 34 WAY PLUG AND SOCKET # £1 pair.
NON POLARISED CAPACITORS 1uf 63v.w. # 5p, 4.7uf 63v.w. # 10p, 10uf 63v.w. # 15p.
VARIABLE CAPACITORS 5pf # 75p, 10pf # 75p, 50-50pf # £1, 125-125pf # 60p, 100-200pf # 60p, 200-300pf # 60p, 25-25-25pf # 75p, 250-250-20-20-20-20pf # 75p.
MIDGET AIRSPACED TRIMMERS 20pf # 11p each.
10 ASSORTED PUSH BUTTON BANKS less knobs # £1.30.
10 ASSORTED SLIDER POTENTIOMETERS # £1.
DAU TRIMMERS 2 to 9pf, 7 to 35pf, 6 to 45pf, 8 to 125pf, 8 to 140pf. All at 15p each.
400mW UNMARKED GOOD ZENERS 3.6v, 6.8v, 10v, 11v, 12v, 13v, 16v, 18v, 24v, 30v, 33v, 36v, All 10 for 40p.
50. OC 71 TRANSISTORS untested for 75p.
WIRE WOUND POTENTIOMETERS 2K 2W, 10K 2W, 5K 4W, 100K 4W, All at 25p ea.
50. 1 AMP S.C.R.'s to 5 Untested for £1.
25. 5 AMP S.C.R.'s Stud Mounting Untested # 75p.
20. STUD MOUNTED 10 ANP DIODES untested # 60p.
10. STUD MOUNTED 20 AMP DIODES untested # 60p.
50. BC 107-8-9 TRANSISTORS untested # 60p.
200. ASSORTED RESISTORS ¼" ¼ watt for 75p.
1000pf 6 K.v.w. DISC CERAMICS at 6 for 20p.
50. PLASTIC NPN TRANSISTORS untested for 60p.
50. PLASTIC PNP TRANSISTORS untested for 60p.
250 VOLT A.C. INPUT TRANSFORMERS 24 volt tapped at 14 volt 1 amp # £1.30 (P&P 30p), 30-0-30 Volt 500mA # £1.30 (P&P 30p).
HIGH SPEED CMOS HEF 4518BF # 55p 5 for £2.
Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2.
Overseas postage charged at cost.

FIT A DIGITAL DISPLAY TO YOUR FRG7 OR SRX30.

These units come complete, with only three wires to connect. The FDU7 for the Yeasu FRG7 can be fitted in place of the KHz dial, or can be supplied for external use. (Please state when ordering) The FDU3 for the SRX30 is supplied for top of the set use only.

(Full Fitting Instructions are supplied.)

(FDU7) for FRG7
(FDU3) for SRX30

@ £44.77
@ £44.77

We also manufacture an R.T.T.Y. Converter.

The MB6R (Receive only) and the MB6R/T (Receive/Transmit).

We supply these units with single or double current loops for connection to teleprinter To Order.

T.T.L./C-MOS Logic Levels and Oscilloscope Outputs are provided. Dimensions (84X304X210).

(MB6R Double or single current) @ 77.96
(MB6R/T Double or single current) @ £83.25

(All Units are fully Guaranteed, and come complete)

(No extras needed)

(All prices inclusive of postage and V.A.T.)

(Payment by P.O., Cheque or Access)

B. BROOKES ELECTRONICS, 69 Leicester Street,
NORWICH NR2 2DZ, ENGLAND.

Tel: 0603-24573.

CASH & CARRY PRICES SHORT-WAVE RECEIVERS

SONY-ICF 6700. 5 band. General coverage. Digital readout. B/I spkr. and ant. **£198.00**

SONY-ICF 6800. 31 band. Dual conversion. Crystal synthesizer. Digital. Fet balanced mixer. Tuned RF pre-selector **£318.00**

NATIONAL DR26. 6 band portable receiver. Digital read-out. Preselector **£159.00**

NATIONAL DR48. 11 band communication RX. Digital. 2 speed tuning. Rugged steel cabinet **£270.00**

GRUNDIG 3400 PROFESSIONAL SATTELITE. Latest model of this famous receiver. Superb audio. £ to be announced.

Established over 50 years on good service.

G3ST **PARK ELECTRIC** G8HGE
211 Streatham Road, Mitcham, Surrey 01-648 6201

IT'S HAPPENED AGAIN!

THE PART THREE CATALOGUE IS PUBLISHED & WE HAVE MOVED TO BIGGER PREMISES.

Yes, it's here at last - the all new Part Three Catalogue. Fun for all the family, and the usual update on all that is new, worthwhile and exciting in the world of Radio and Communications. A big section on frequency synthesis techniques covering broadcast tuners, to communication quality transmitter systems. More new products than ever - RADIO CONTROL parts, crystal filters, ceramic filters for 455kHz and the new range of TOKO CFSH low temperature coefficient types for 10.7MHz. Details on new radio ICs, including the new HA11225, the CA3381F look-alike with 84dB signal to noise, and adjustable muting threshold. Radio control ICs - and an updated version of the RCM&E 8 channel FM receiver - now with an Ambit designed screened front end, with 27MHz ceramic bandpass filter, LCD panel clock timer modules - the neatest and best LCD panel DVM yet (only £19.45 each + VAT), the new 5 decade resolution DFM3 for LW/HF/VHF with LCD readout. The DM6 with fluorescent display to 10kHz resolution on VHF, 1kHz on SW. A 1kHz HF synthesiser with five ICs - the list is endless. Get your copy of the catalogue now. Post publication price is 60p (inc PP etc). The previous two sections are also required for a complete picture: Parts 1 & 2 of the pair. All 3 £1.50. And don't miss our spot the gibbon contest, together with a quiz to see if you can spot the differences between a genuine cave drawing and a circuit diagram of one of our competitor's tuners. (* Yes, we still haven't learnt how to spell!)


Updated RCM&E FM radio control RX kit



- 8 Channel RC receiver (FM)
- Single IC RF/IF/Detector
- Single IC recoder
- 27MHz ceramic filter input
- FET RF stage with double tuned bandpass filter
- Dual ceramic filter IF
- Based on RCM&E FM system
- Best quality SLM servo connector block
- ONLY £16.10 inc VAT (kit) (includes new SLM case)


DOES YOUR ONE GLOW GREEN IN THE DARK?

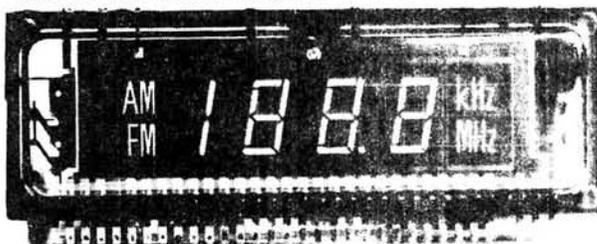Our DFM4 does, since it uses a vacuum fluorescent display for direct readout of MW/LW/FM. Basically the same as the DFM2. (LCD Version) £26.45 (inc VAT) Transformer with all necessary windings for DFM4 - £2.50 inc VAT.



Not illustrated here - but also now available is the DFM6. This is a vacuum fluorescent display version of our immensely popular DFM3 (LCD). Resolution is 100Hz to 3.9999MHz, 1kHz to 39.999MHz, and 10kHz to 200.00MHz; all standard IF offsets (inc. 10.7MHz on shortwave) are available via diode programming.

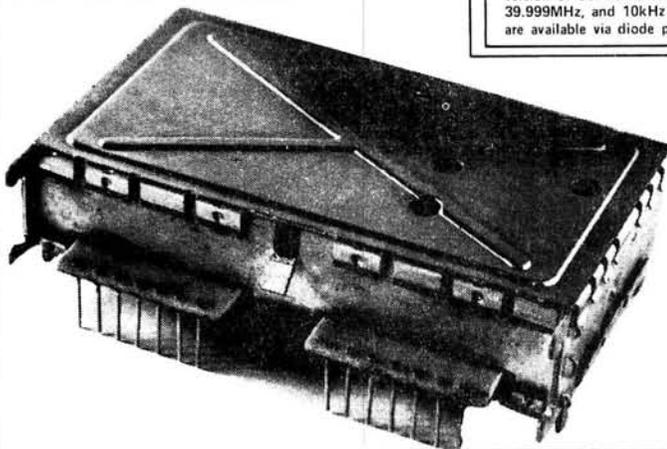New series of radio modules in fully screened cans:



UM1181 VHF band 2 VARIOMETER HEAD

5 tuned circuit, with image reject filter (has 40dB rejection at output), MOSFET RF stage, FET IF preamp, main A to MPX, 10 dB, -9dBm 3rd order intercept. Full price £12.00 inc VAT. (9904) (9A)

911225 FM IF strip with all mod cons for the HF tuner

All types use 80+dB S/N Hitachi hi, with muting, AFC, AVC meter outputs for signal level and centre zero IF preamp stage.
 'A' Dual linear phase ceramic filters, with MOSFET VARIOMETER IF preamp and a 3rd narrow filter with DC filter selection. Dual tuned FM detector stage. £23.95 inc VAT. (9404)
 'B' Dual ceramic filters, single tuned detector stage £14.95 inc VAT. (All 'A' series units are set up with a spectrum analyzer for best THD)

91072 AM RADIO TUNER MODULES - DC TUNED and DC SWITCHED Available February '80

All include buffered LO output, mechanical IF filter (TOKO GEMO) 1-10v tuning bias, switching by a single slide switch.
 A MW/LW (150 to 350kHz LW range) with ferrite rod antenna.
 B As 'A' but also including SW1 or SW2 (capacitor).
 SW1 = 1.8 to 4MHz SW2 = 5 to 15MHz
 C With both SW ranges.
 Prices one off INC VAT
 'A' £14.43 'B' £15.90 'C' £17.90 (Custom types 0A)

There is a danger - when advertizing in some magazines - that because we do not find space to list everything we sell in every ad., that some readers forget about half the ranges we stock. So to summarize the general ranges:

TOKO Chokes, coils for AM/FM/SW/MPX, Audio filters etc
 Filters: Ceramic for AM/FM, LC for FM, MPX etc.
 Polyvaricons
 ICs for radio, clock LSI, radio control, MPX decoders etc

Micrometals Dust iron cores for toroids for resonant and EMI filters
 Toroid mounts

Hitachi Radio/audio/mpx linear ICs
 100W MOSFETs, small signal FETs, MOSFETs and bipolar

And the following groups of products from a broad range of sources:

Semiconductors -specializing in radio devices, Plessey SL1600, EUROPE's best selection of AM/FM and communications devices. Power MOSFETs, WORLD'S LOWEST NOISE AUDIO small signal transistors, BAR graph LED drivers for linear and log.
 CD4000 series CMOS, TTL/LPSNTTL, standard linears (741, 301, 3080 etc). MPUs, memories. Small signal transistors from AEG BC237/8/9 families etc. (1000 off BC239C : 5.2p ea)
 LEDs: AEG 3mm/5mm round, 2.5x5mm flat, red, green, orange, yellow. The best prices you will find for quality products.
 MOSFETs for RF signal processing, including the BF960 UHF device, and 3SK51 for VHF. Varicap diodes for 17:1 capacity ratio tuning

FREQUENCY READOUT (LSI from GKI) with a one-chip answer to most digital frequency display needs (and various modules).
Crystal and ceramic ladder filters from leading manufacturers, ferrite rods, various ferrite beads and a range of crystals for standard frequencies and both AM and FM radio control at 27MHz. Trimmer capacitors
METERS - a new range of linear movement types, plus many 'indicator' types for VU, all types of tuning indicators etc.
SOCKETS - a new range that are better quality than Texas low profile, yet better priced.
Modules for AM/FM/STEREO, complete kits for tuners, audio amplifiers from Earshot.
SWITCHES complete low cost DIY systems for push button arrays, keyboard switches.
DOUBLE BALANCED MIXERS MCP SBL1 replacement for MD108 etc. And cheaper.

OUR LATEST MOVING EXPERIENCE :: At last, we have moved to the address below. There is car parking for customers approaching via North Service Road (an extension of North Road Avenue, entrance opposite the Brentwood Fire Station.) Pedestrian access from the High Street (alongside 117 High Street). The new building is six times bigger than our Gresham Road offices, and we will be installing a much expanded sales counter in the fullness of time. NEW TELEPHONE NUMBER (0277) 230909, TELEX NUMBER (as before) 985194 AMBIT G. See you there!

200 North Service Road, Brentwood, Essex.

ELECTROVALUE

CATALOGUE

10

Ready early December

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

FREE

(You don't even have to pay postage)

IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

● We give discounts

on C.W.O. orders, except for a few items market Net or N in our price lists.

5% on orders, list value £10 or more

10% on orders list value £25 or more.

Not applicable on Access or Barclaycard purchase orders.

● We pay postage in U.K.

on C.W.O. orders list value £5 or over. If under, add 30p handling charge.

● We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.

● We guarantee

all products brand new, clean and maker's spec. No seconds, no surplus.

● Appointed distributors for SIEMENS, VERO, ISKRA, NASCOM and many others.

OUR NEW CATALOGUE No 10

Over 120 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

ELECTROVALUE LTD

HEAD OFFICE (Mail Orders)

28(A) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London prefix 87. STD 0784) Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)

680 Burnage Lane, Burnage, Manchester M19 1NA Phone: (061) 432 4945.

MAIL ORDER DEPT.

CRESCENT RADIO LTD

1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ. 01-888 3206



"FLIP"
PUSH BUTTON HEADS OR TAILS
Complete kit and full instructions supplied.
A pocket game, easy to build and great to play.
KIT PRICE = £5.25 + 15% VAT. Post free.

75 OHM
2 1/2" (57mm) LOUDSPEAKER BARGAIN
This ever popular many project loudspeaker.
Only while stocks last. **90p + 15% VAT each.**

U.S.A. COAXIAL CONNECTOR
Standard coaxial male plug
PL259
Price **50p + 15% VAT**

PSI. STABILIZED POWER SUPPLY

240v AC input: Outputs:- 3, 6, 7.5 and 9 volts DC at maximum 400 ma. Three switches:- On-Off, Polarity Reversing and Voltage Change. Regulated to supply exact marked voltages from no load up to maximum current. Dimensions:- 5 x 3 x 2 1/4 inches.
Only **£7 + 15% VAT.**

MOBILE P.A. MICROPHONE

For all outdoor P.A. Work. **50K ohms.** On-off switch and volume control. Complete with curly lead. Incorporates unique built-in unwanted noise rejection mechanism.
Price = **£9 + 15% VAT.**

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT
1000W lighting per channel, max. A 3 channel sound to light unit housed in a robust metal case, with a sensitivity control for each channel i.e. Bass, middle and treble. Full instructions make this unit easy to connect to your present amplifier.
S.A.E. for spec. sheet.
Still only £20.00 + 15% VAT.

CR. 4110. DESOLDERING PUMP
ONLY £8 + 15% VAT
High suction pump with automatic ejection. Knurled, anti corrosive casing. Teflon nozzle.

CR. LV1. 12v DRILL
£12.00p. + 15% VAT

BRITISH MADE "Versadrill", 12 volts DC. Compact battery operated power tool, sufficiently powerful to perform all the operations associated with 240v drills. Dimensions:- 150 x 50mm (dia.)

C.180-"KEYNECTOR" MAINS CONNECTOR

Essential equipment for the showroom, workshop, factory, laboratory, home and hobby bench, the 'Keynector' provides quick, efficient and safe temporary mains connection.
£6.25 + 15% VAT

FOOTSWITCH C.338

250v, 5 amp. Non-slip base. Lead with 2.5mm plug. Body dims:- 88 x 66 x 25mm.
£3.75 + 15% VAT



P & P. Orders up to £5, add 30p. Orders £5-£10, add 50p. All orders over £10 post free! Please add V.A.T. as shown. S.A.E. with all enquiries please.



Personal callers welcome at: **21 Green Lanes, Palmers Green N13.** Also **13 South Mall, Edmonton Green, Edmonton.**

A. S. COOPER

RADIO REPAIRS

11a Kingsholm Road, Gloucester GL1 3AY
Tel: DAY (Glos.) 422259 NIGHT (Glos.) 27223

CLEARANCE SALE

Capacitors and Trimmers - all Ceramic. All must go. All at **£1.00** per pack.



Please tick box and number required.

- | | | | | | |
|--|--------------------------|--------------------------|--|--------------|-------------|
| 1 | <input type="checkbox"/> | <input type="checkbox"/> | Trimmers 0.5 to 5 pf | PC mount | 10 per pack |
| 2 | <input type="checkbox"/> | <input type="checkbox"/> | Trimmers 2.0 to 2.5 pf | PC mount | 15 per pack |
| 3 | <input type="checkbox"/> | <input type="checkbox"/> | Trimmers 3.5 to 13 pf | PC mount | 15 per pack |
| 4 | <input type="checkbox"/> | <input type="checkbox"/> | Trimmers 4.5 to 20 pf | PC mount | 15 per pack |
| Next 6 boxes fixed pf values, all 25 per pack. | | | | | |
| Circle required pf value. | | | | | |
| 5 | <input type="checkbox"/> | <input type="checkbox"/> | 0.5, 2.0, 2.7, 3.3, 3.9, 4.0, 4.7, 6.8, 12.0, 15.0 | | |
| 6 | <input type="checkbox"/> | <input type="checkbox"/> | 18, 20, 25, 27, 30, 33, 36, 40, 47, 50 | | |
| 7 | <input type="checkbox"/> | <input type="checkbox"/> | 60, 68, 75, 82, 220, 240, 250, 300, 330, 360 | | |
| 8 | <input type="checkbox"/> | <input type="checkbox"/> | 400, 560, 620, 750, 820, 2.2k | | |
| 9 | <input type="checkbox"/> | <input type="checkbox"/> | 2.5k, 2.7k, 3.0k, 3.5k, 4.0k, 4.7k | | |
| 10 | <input type="checkbox"/> | <input type="checkbox"/> | 7pf, 8pf tab type disc | Packs of 100 | |
| 11 | <input type="checkbox"/> | <input type="checkbox"/> | 1k pf leadless disc | | |

Buy any 10 packs and get one Bumper Pack of mixed values FREE. Cut out and order today while stocks last.

P & P Orders up to £5 add 30p. Orders £5 to £10 add 50p. Orders over £10 free. UK ONLY.

Overseas enquiries very welcome. SAE with enquiries only.

Name.....

Address.....

..... Post Code.....

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200 250V.

PRICE £18.40, P. & P. £1.20.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200 240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w x 4" h x 9 1/2" d approx.

LIMITED NUMBER ONLY at £29.00 + £1.50 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 50p + SAE (Free with parts). All parts sold separately. ONLY £18.40, P. & P. £1.40. Also available ready built and tested £22.50, P. & P. £1.40.

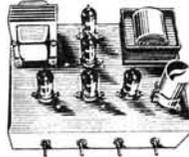

STEREO DECODER MK.II

SIZE 1 1/2" x 2 1/2" x 1 1/2" ready built. Pre-aligned and tested for 10-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions supplied. £7.00 plus 20p P. & P. Stereo beacon light if required 40p extra.

Mullard LP1159 RF-IF module 470kHz £2.50 + P. & P. 20p. Full specification and connection details supplied. Pye VHF FM Tuner Head covering 88-108MHz 10.7 MHz I.F. output. 7.8V + earth. Supplied pre-aligned, with full circuit diagram with precision geared F.M. gang and 323PF + 323PF A.M. Tuning gang only £3.40 + P. & P. 35p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £2.30 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp.

Overall Size 12" w. x 8" d. 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £14.95 P. & P. 80p (Magnetic input components 33p extra)
POWER PACK KIT £6.20 P. & P. 95p
CABINET £6.20 P. & P. 95p

SPECIAL OFFER—only £25.80 if all 3 items ordered at one time plus £1.25 p. & p.

Full after sales service Also avail. ready built and tested £32.20, P. & P. £1.50.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec. play socket are mounted on the printed circuit panel, size approx. 9 1/2" x 2 1/2" x 1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10.40 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at £2.15 + 40p P. & P. if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 30 watts music power. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12 1/2" wide x 5 1/2" high x 7 1/2" deep. Special introductory price £29.00 + £2.50 carriage and packing.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE, ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.80 each + p. & p. (one 90p, two £1.10). Now available in 8" round version. 10 watts RMS 60Hz 20KHz £6.30. P. & P. (one 65p, two 75p).

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2" x 2 1/2" x 1 1/2" H. £3.20 + 20p P. & P.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19.
A few minutes from South Wimbledon Tube Station.

LONDON, S.W.19.

Tel.: 01-540 3985

Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.



A Conference and Exhibition to help you come to terms with the Second Industrial Revolution

at the WEMBLEY CONFERENCE CENTRE

JANUARY 30-FEBRUARY 1 from 9.30 am each day



CONFERENCE SESSIONS enable you to share the experience of experts in the microtechnology field.

A BUYERS' FORUM helps you to establish effective criteria for selection of goods and services.

A PROFESSIONAL DEVELOPMENT SEMINAR introduces managers to the use of microprocessors in business and industry.

AN EXHIBITION where you can talk personally with the suppliers of microtechnology products and services.

Admission to the exhibition is free. You may book in on the spot for conference sessions, or obtain further details of fees and a booking form from:

MICROSYSTEMS CONFERENCE Room 821, Dorset House, Stamford Street, London, SE19LU.

T.M.P.

ELECTRONIC SUPPLIES SPECIALISING IN AMATEUR RADIO SUPPLIES

Full range of YAESU MUSEN equipment in stock with SMC 2 Year guarantee, also secondhand receivers, transceivers & accessories.

North Wales Appointed distributor for Jaybeam.

UK distributor for Amidon Toroidal Cores/Micrometals & Microwave Filter Co Inc who produce the W2AU antenna balun and many other antenna accessories.

We can in short, supply anything you want to start in the amateur radio hobby or improve your existing station.

For full stock list and prices please send a stamped addressed envelope to the address below or if in the area call in the shop and have a look around.

Britannia Stores, Leeswood, Nr. Mold, Clwyd, CH7 4SD


Telephone: Pontybodkin 846 STD 035 287

Open daily 9.30-5.00 Early closing Tues & Sat 1pm.

SUPER SPOT DISCO SYSTEM 1

★ Sound Sequencer units in metal cases ★
★ Bulgin 8 way sockets ★ Fused & Suppressed ★
8A Triacs ★ 600W max per channel ★

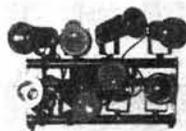3 channel built & tested £26.95
4 channel built & tested £29.95
More than 4 channels built to order.



System 2 full set ups see previous adverts.
Multiposition surface mounting E.S. Spotholders £3.25
3 Spots on a bank £14.60
for each additional spot add £3.45

Send S.A.E. for lists.

Prices include VAT, P.&P. & Guarantee.

NOBLE ELECTRONICS (PW)

26 Lloyd Street, Altrincham, Cheshire WA14 2DE.

Tel: 061-941 4510

Trade enquiries welcome


BIMENCLOSURES



ALL METAL BIMCASES
Red, Grey or Orange 14swg Aluminium removable top and bottom covers. 18 swg black mild steel chassis with fixing support brackets.
BIM 3000
(250x167.5x68.5mm)
£15.52



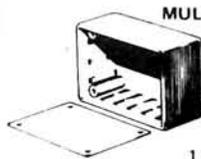MINI DESK BIMCONSOLES
Orange, Blue, Black or Grey ABS body incorporates 1.8mm pcb guides, stand-off bosses in base with 4 BIMFEET supplied. 1mm Grey Aluminium panel sits recessed with fixing screws into integral brass bushes.
BIM 1005 (161 x 96 x 58mm) £2.48
BIM 1006 (215 x 130 x 75mm) £3.48




MULTI PURPOSE BIMBOXES
Orange, Blue, Black or Grey ABS with 1mm Grey Aluminium recessed front cover held by screws into integral brass bushes. 1.8mm pcb guides incorporated and 4 BIMFEET supplied.
BIM 4003 (85x56x28.5mm) £1.34
BIM 4004 (111x71x41.5mm) £1.84
BIM 4005 (161x96x52.5mm) £2.48



ALL METAL BIMCONSOLES

All aluminium, 2 piece desk consoles with either 15° or 30° sloping fronts, sit on 4 self-adhesive non-slip rubber feet. Ventilation slots in base and rear panel for excellent cooling. See latest catalogue for new styles and sizes

15° Sloping Panel	30° Sloping Panel	Colour Code	Top Panel	Base
BIM7151 (102x140x51[28] mm)	BIM7301 (102x140x76[28] mm)	A	Off White	Blue
BIM7152 (165x140x51[28] mm)	BIM7302 (165x140x76[28] mm)	B	Sand	Green
BIM7153 (165x216x51[28] mm)	BIM7303 (165x183x102[28] mm)	C	Satin Black	Gold
BIM7154 (165x211x76[33] mm)	BIM7304 (254x140x76[28] mm)			
BIM7155 (254x211x76[33] mm)	BIM7305 (254x183x102[28] mm)			
BIM7156 (254x287x76[33] mm)	BIM7306 (254x259x102[28] mm)			
BIM7157 (356x211x76[33] mm)	BIM7307 (356x183x102[28] mm)			
BIM7158 (356x287x76[33] mm)	BIM7308 (356x259x102[28] mm)			

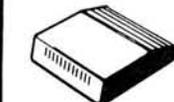


ABS & DIECAST BIMBOXES

6 sizes in ABS or Diecast Aluminium. ABS moulded in Orange, Blue, Black or Grey. Diecast Aluminium in Grey Hammetone or Natural. All boxes incorporate 1.8mm pcb guides, stand-off supports in base and have close fitting flanged lids held by screws into integral brass bushes (ABS) or tapped holes (Diecast).

	ABS	Diecast	Hammetone	Natural
(50x50x25mm)	N/A	BIM5001/11	£1.54	£1.23
(100x50x25mm)	BIM2002/12	BIM5002/12	£1.66	£1.32
(112x62x31mm)	BIM2003/13	BIM5003/13	£2.24	£1.70
(120x65x40mm)	BIM2004/14	BIM5004/14	£2.81	£2.11
(150x80x50mm)	BIM2005/15	BIM5005/15	£3.19	£2.72
(190x110x60mm)	BIM2006/16	BIM5006/16	£4.94	£3.96


Also available in Grey Polystyrene with no slots and self-tapping screws
BIM 2007/17 (112x61x31mm) £1.06

LOW PROFILE BIMCONSOLES

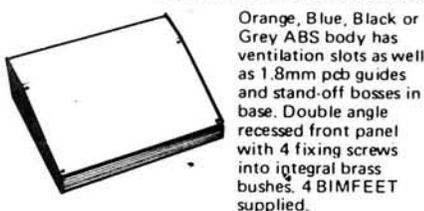

Orange, Blue, Black or Grey ABS body has ventilation slots as well as 1.8mm pcb guides and stand-off bosses in base. Double angle recessed front panel with 4 fixing screws into integral brass bushes. 4 BIMFEET supplied.
BIM 6005 (143 x 105 x 55.5 [31.5] mm) £2.76
BIM 6006 (143 x 170 x 55.5 [31.5] mm) £3.58
BIM 6007 (214 x 170 x 82.0 [31.5] mm) £4.83

EUROCARD BIMCONSOLES

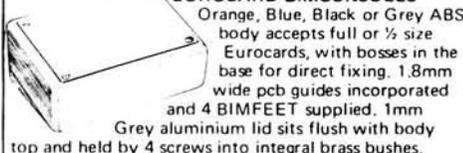

Orange, Blue, Black or Grey ABS body accepts full or 1/2 size Eurocards, with bosses in the base for direct fixing. 1.8mm wide pcb guides incorporated and 4 BIMFEET supplied. 1mm Grey aluminium lid sits flush with body top and held by 4 screws into integral brass bushes.
BIM 8005 (169x127x70[45] mm) £4.71
BIM 8007 (243x187x103[66] mm) £6.70

BIMTOOLS + BIMACCESSORIES



MAINS BIMDRILLS


Small, powerful 240V hand drill complete with 2 metres of cable and 2 pin DIN plug. Accepts all tools with 1mm, 2mm or .125" dia. shanks Drills brass, steel, aluminium and pcb's. Under 250g, off load speed 7500 rpm. Orange ABS, high impact, fully insulated body with integral on/off switch £11.21

Mains Accessory Kit 1 includes 1mm, 2mm, .125" twist drills, 5 burrs and 2.4mm collet £2.64

Mains Kit 2 includes Mains BIMDRILL as above, 20 assorted drills, mops, burrs, grinding wheels and mounted points, 1mm, 2mm, 2.4mm and .125" collets. Complete in transparent case measuring 230x130x58mm £23.57

BIMDAPTORS

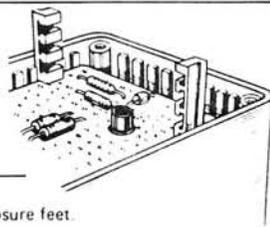Allows pcb's to be flat mounted sandwich fashion in BIMBOXES, BIMCONSOLES, and all other enclosures having 1.5mm wide vertical guide slots. One plastic BIMDAPTOR on each corner of pcb(s) enables assembly to be simply slid into place. 54mm long, 10 slots on 5mm spacing and can be simply snapped off to length. £1.15 per pack of 25.



BIMFEET

11mm dia. 3mm high, grey rubber self-adhesive enclosure feet. £0.81 per pack of 24.

12 VOLT BIMDRILLS

2 small, powerful drills easily hand held or used with lathe/stand adaptor. Integral on/off switch and 1 metre cable.

Mini BIMDRILL with 3 collets up to 2.4mm dia. £ 8.62
Major BIMDRILL with 4 collets up to 3mm dia. £14.49

Accessory Kits 1 have appropriate drills and collets as above plus 20 assorted tools. Mini Kit 1 - £16.10, Major Kit 1 - £20.70. Accessory Kits 2 have appropriate drills, collets plus 40 tools and mains-12V dc adaptor. Mini Kit 2 - £36.22, Major Kit 2 - £41.97. Accessory Kits 3 as appropriate Kits 2 plus stand/lathe unit. Mini Kit 3 - £48.30, Major Kit 3 - £54.05.

BIMPUMPS



2 all metal desoldering tools provide high suction power and have easily replaceable screw in Teflon tips. Primed and released by thumb operation with in-built safety guard and anti-recoil system.
BIMPUMP Major (180mm long) £8.51
BIMPUMP Minor (150mm long) £7.24

BIMIRONS



Type 30 General Purpose 27 watt iron with long life, rapid change element, screw on tip, stainless steel shaft and clip on hook. Styled handle with neon. £4.37
Type M3 Precision 17 watt iron, quick change tip, long life element, styled handle with clip on hook. £4.71

BIMBOARDS



DIL COMPATIBLE BIMBOARDS



Accept all sizes (4-50 pin) of DIL IC packages as well as resistors, diodes, capacitors and LEDs. Integral Bus Strips up each side for power lines and Component Support Bracket for holding lamps, switches and fuses etc. Available as single or multiple units, the latter mounted on 1.5mm thick black aluminium back plate which stand on non slip rubber feet and have 4 screw terminals for incoming power.

BIMBOARD 1 has 550 sockets, multiple units utilising 2, 3 and 4 BIMBOARDS incorporate 1100, 1650 and 2200 sockets, all on 2.5mm (0.1") matrix.

BIMBOARD 1 £ 8.22
BIMBOARD 2 £19.98
BIMBOARD 3 £29.06
BIMBOARD 4 £38.13

DESIGNER PROTOTYPING SYSTEM

1, 2, or 3 BIMBOARDS mounted on BIM 6007 BIMCONSOLE with Integral Power Supply (±5 to ±15Vdc @ 100mA and fixed +5Vdc @ 1A) All O/P's fully isolated. Short circuit and fast fold back protection. Power rails brought out to cable clamps that accept stripped wire or 4mm plug.

DESIGNER 1 £58.65
DESIGNER 2 £64.97
DESIGNER 3 £71.30

U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE

BAKER "STAR-SOUND" SPEAKERS Post £1.60
 'Group 100-12' 'Group 45-12' 'Group 100-15'

12 inch 100 watt 8 or 16 ohm	12 inch 45 watt 4 or 8 or 16 ohm	15 inch 100 watt 8 or 16 ohm
£29	£15	£35

BAKER LOUDSPEAKER, 12 INCH, 60 WATT.
GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER
 FULL RANGE PROFESSIONAL QUALITY
 RESPONSE 30 16 000 CPS
 MASSIVE CERAMIC MAGNET
 WITH ALUMINIUM PRESENCE CENTRE DOME
£23

4 CHANNEL TRANSISTOR MONOMIXER
 Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated.
£7.50
 Two channel stereo version **£9.**

HEATING ELEMENTS WAFER THIN
 Size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250W approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or similar. ALL POST PAID - Discounts for quantity.
ONLY 40p EACH (FOUR FOR £1.50)

MINI MODULE BAFFLE KIT Post £1.
 EMI 15 x 8 1/2 in. 3-way Loudspeaker System
 5in. Bass 5in. Middle 3in Tweeter with 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response-60 to 20000 C.P.S. 12 watt RMS. 8 ohms. **£10.95** per kit. Two kits **£20.** Suitable Bookshelf Cabinet **£9.50** each. Post £1.60.



RSC RECORD DECK
 Fitted with auto stop, stereo cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable Size 7in. diameter a.c. mains 240V 3 speeds plays all size records.
£9.95
 Two for £18.00. Post £1 one or two.

NEW BSR SINGLE PLAYER **£24.50**
 Model P182 3-speeds flared aluminium turntable. "S" shaped arm, cueing device, stereo ceramic cartridge
 B.S.R. De-Luxe Autochanger with stereo cartridge, plays all size records. Post £1.60. **£20.00**

BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER
 Ideal for Groups, Disco, P.A. and Musical instruments. 4 inputs speech and music 4 way mixing, 3 separate outputs
 Matching 4/8/16 ohm, a.c. Mains 240V.
 Separate treble and bass controls.
 100 volt line model **£14 extra.**
£85 Post **£1.60**

BAKER COMPACT 50 WATT AMPLIFIER

IDEAL FOR DISCOS, GROUPS, PUBLIC ADDRESS
 Two inputs with volume controls. Master treble bass and volume controls. Suitable for all loudspeakers. **£65.** Post **£1.60**

R.C.S. SOUND TO LIGHT DISPLAY MK II
 Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200Vv. stereo source. CABINET extra **£4** KIT **£18.00**

R.C.S. 10 WATT AMPLIFIER KIT
 This kit is suitable for record players, tape play back, guitars, electronic instruments or small PA systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductor. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms 7W into 15ohms. Response 20c.s. to 30Kc.s. Input 100MV. high imp. Size 9 1/2 x 3 x 2in. A.C. mains operated.
 Mono kit **£12.50** Stereo kit **£20** Post **45p**
 Easy to build. Full instructions supplied

LOW VOLTAGE ELECTROLYTICS
 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p, 500mF 12V 15p; 25V 20p; 50V 30p, 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p, 2000mF 40V 60p; 25V 42p, 2500mF 50V 62p, 3000 mF 25V 47p; 50V 85p, 2700mF 76V **£1.** 4700mF 63V **£1.20.** 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p, 5600mF 76V **£1.75.** 1200mF 76V 80p.

HIGH VOLTAGE ELECTROLYTICS
 8-350V 22p 8-8450V 50p 50-90 300V 50p
 16-350V 30p 8-16450V 50p 32-32450V 75p
 32-500V 75p 16-16450V 50p 100-100-275V 65p
 50/500V **£1.20** 32-32350V 50p 150-200-275V 70p
 MANY OTHERS IN STOCK 50-50-50/350V 90p

TINTED PLASTIC COVERS ONLY
 Sizes 14, 12, 3in **£3.50**, 16, 14, 3 1/2in **£5.**
 15, 13, 4in **£4.17**, 9, 3 1/2in **£3.**
 14, 14, 2 1/2in Rosewood sales **£4.**
 18, 13 1/2, 3in, 6in, 18, 12 1/2, 3in **£6.**
 Ideal for record racks, tape decks, etc. Post **£1.60**

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS Post 45p **£2.95**
 All parts and instructions with Zenier diode printed circuit, rectifiers and double wound mains transformer input 200 240V a.c. Output voltages available 6 or 7, 5 or 9 or 12V d.c. up to 100mA or less. Size 3 1/2 x 1 1/2 in. Please state voltage required.

RECORD DECK REPLACEMENT MOTORS POST £1.
 Garrard 2025 5300, 3000 5550, Garrard SP5 6550, BSR C129, C141 P182 5550, BSR P128, MP60 6550, BSR tape deck motor TD2 6550

MAINS TRANSFORMERS ALL POST 75p each

250 0.25V 20mA 1 x 2A	£3.45
250 0.25V 40mA 6 3V 1.5A 6 3V 1A	£8.50
400 0.30V 200mA 2 x 6 3V 2A 5 1 x 3V 2A	£2.50
220V 45mA 4 3V 2A	£2.50
HEATER TRANS 6 3V 3A £2 2 amp	£2.20
GENERAL PURPOSE LOW VOLTAGE Tapped outputs	£6.00
A 4 4 1/2 6 6 1/2 8 8 1/2 10 10 1/2 12 12 1/2 14 14 1/2 16 16 1/2 18 18 1/2 20 20 1/2 24 24 1/2 28 28 1/2 32 32 1/2 36 36 1/2 40 40 1/2 48 48 1/2 56 56 1/2 64 64 1/2 72 72 1/2 80 80 1/2 96 96 1/2 112 112 1/2 128 128 1/2 144 144 1/2 160 160 1/2 180 180 1/2 200 200 1/2 220 220 1/2 240 240 1/2 280 280 1/2 320 320 1/2 360 360 1/2 400 400 1/2 450 450 1/2 500 500 1/2 560 560 1/2 630 630 1/2 720 720 1/2 800 800 1/2 900 900 1/2 1000 1000 1/2 1100 1100 1/2 1200 1200 1/2 1300 1300 1/2 1400 1400 1/2 1500 1500 1/2 1600 1600 1/2 1700 1700 1/2 1800 1800 1/2 1900 1900 1/2 2000 2000 1/2 2200 2200 1/2 2400 2400 1/2 2600 2600 1/2 2800 2800 1/2 3000 3000 1/2 3200 3200 1/2 3400 3400 1/2 3600 3600 1/2 3800 3800 1/2 4000 4000 1/2 4200 4200 1/2 4400 4400 1/2 4600 4600 1/2 4800 4800 1/2 5000 5000 1/2 5200 5200 1/2 5400 5400 1/2 5600 5600 1/2 5800 5800 1/2 6000 6000 1/2 6200 6200 1/2 6400 6400 1/2 6600 6600 1/2 6800 6800 1/2 7000 7000 1/2 7200 7200 1/2 7400 7400 1/2 7600 7600 1/2 7800 7800 1/2 8000 8000 1/2 8200 8200 1/2 8400 8400 1/2 8600 8600 1/2 8800 8800 1/2 9000 9000 1/2 9200 9200 1/2 9400 9400 1/2 9600 9600 1/2 9800 9800 1/2 10000 10000 1/2 10200 10200 1/2 10400 10400 1/2 10600 10600 1/2 10800 10800 1/2 11000 11000 1/2 11200 11200 1/2 11400 11400 1/2 11600 11600 1/2 11800 11800 1/2 12000 12000 1/2 12200 12200 1/2 12400 12400 1/2 12600 12600 1/2 12800 12800 1/2 13000 13000 1/2 13200 13200 1/2 13400 13400 1/2 13600 13600 1/2 13800 13800 1/2 14000 14000 1/2 14200 14200 1/2 14400 14400 1/2 14600 14600 1/2 14800 14800 1/2 15000 15000 1/2 15200 15200 1/2 15400 15400 1/2 15600 15600 1/2 15800 15800 1/2 16000 16000 1/2 16200 16200 1/2 16400 16400 1/2 16600 16600 1/2 16800 16800 1/2 17000 17000 1/2 17200 17200 1/2 17400 17400 1/2 17600 17600 1/2 17800 17800 1/2 18000 18000 1/2 18200 18200 1/2 18400 18400 1/2 18600 18600 1/2 18800 18800 1/2 19000 19000 1/2 19200 19200 1/2 19400 19400 1/2 19600 19600 1/2 19800 19800 1/2 20000 20000 1/2 20200 20200 1/2 20400 20400 1/2 20600 20600 1/2 20800 20800 1/2 21000 21000 1/2 21200 21200 1/2 21400 21400 1/2 21600 21600 1/2 21800 21800 1/2 22000 22000 1/2 22200 22200 1/2 22400 22400 1/2 22600 22600 1/2 22800 22800 1/2 23000 23000 1/2 23200 23200 1/2 23400 23400 1/2 23600 23600 1/2 23800 23800 1/2 24000 24000 1/2 24200 24200 1/2 24400 24400 1/2 24600 24600 1/2 24800 24800 1/2 25000 25000 1/2 25200 25200 1/2 25400 25400 1/2 25600 25600 1/2 25800 25800 1/2 26000 26000 1/2 26200 26200 1/2 26400 26400 1/2 26600 26600 1/2 26800 26800 1/2 27000 27000 1/2 27200 27200 1/2 27400 27400 1/2 27600 27600 1/2 27800 27800 1/2 28000 28000 1/2 28200 28200 1/2 28400 28400 1/2 28600 28600 1/2 28800 28800 1/2 29000 29000 1/2 29200 29200 1/2 29400 29400 1/2 29600 29600 1/2 29800 29800 1/2 30000 30000 1/2 30200 30200 1/2 30400 30400 1/2 30600 30600 1/2 30800 30800 1/2 31000 31000 1/2 31200 31200 1/2 31400 31400 1/2 31600 31600 1/2 31800 31800 1/2 32000 32000 1/2 32200 32200 1/2 32400 32400 1/2 32600 32600 1/2 32800 32800 1/2 33000 33000 1/2 33200 33200 1/2 33400 33400 1/2 33600 33600 1/2 33800 33800 1/2 34000 34000 1/2 34200 34200 1/2 34400 34400 1/2 34600 34600 1/2 34800 34800 1/2 35000 35000 1/2 35200 35200 1/2 35400 35400 1/2 35600 35600 1/2 35800 35800 1/2 36000 36000 1/2 36200 36200 1/2 36400 36400 1/2 36600 36600 1/2 36800 36800 1/2 37000 37000 1/2 37200 37200 1/2 37400 37400 1/2 37600 37600 1/2 37800 37800 1/2 38000 38000 1/2 38200 38200 1/2 38400 38400 1/2 38600 38600 1/2 38800 38800 1/2 39000 39000 1/2 39200 39200 1/2 39400 39400 1/2 39600 39600 1/2 39800 39800 1/2 40000 40000 1/2 40200 40200 1/2 40400 40400 1/2 40600 40600 1/2 40800 40800 1/2 41000 41000 1/2 41200 41200 1/2 41400 41400 1/2 41600 41600 1/2 41800 41800 1/2 42000 42000 1/2 42200 42200 1/2 42400 42400 1/2 42600 42600 1/2 42800 42800 1/2 43000 43000 1/2 43200 43200 1/2 43400 43400 1/2 43600 43600 1/2 43800 43800 1/2 44000 44000 1/2 44200 44200 1/2 44400 44400 1/2 44600 44600 1/2 44800 44800 1/2 45000 45000 1/2 45200 45200 1/2 45400 45400 1/2 45600 45600 1/2 45800 45800 1/2 46000 46000 1/2 46200 46200 1/2 46400 46400 1/2 46600 46600 1/2 46800 46800 1/2 47000 47000 1/2 47200 47200 1/2 47400 47400 1/2 47600 47600 1/2 47800 47800 1/2 48000 48000 1/2 48200 48200 1/2 48400 48400 1/2 48600 48600 1/2 48800 48800 1/2 49000 49000 1/2 49200 49200 1/2 49400 49400 1/2 49600 49600 1/2 49800 49800 1/2 50000 50000 1/2 50200 50200 1/2 50400 50400 1/2 50600 50600 1/2 50800 50800 1/2 51000 51000 1/2 51200 51200 1/2 51400 51400 1/2 51600 51600 1/2 51800 51800 1/2 52000 52000 1/2 52200 52200 1/2 52400 52400 1/2 52600 52600 1/2 52800 52800 1/2 53000 53000 1/2 53200 53200 1/2 53400 53400 1/2 53600 53600 1/2 53800 53800 1/2 54000 54000 1/2 54200 54200 1/2 54400 54400 1/2 54600 54600 1/2 54800 54800 1/2 55000 55000 1/2 55200 55200 1/2 55400 55400 1/2 55600 55600 1/2 55800 55800 1/2 56000 56000 1/2 56200 56200 1/2 56400 56400 1/2 56600 56600 1/2 56800 56800 1/2 57000 57000 1/2 57200 57200 1/2 57400 57400 1/2 57600 57600 1/2 57800 57800 1/2 58000 58000 1/2 58200 58200 1/2 58400 58400 1/2 58600 58600 1/2 58800 58800 1/2 59000 59000 1/2 59200 59200 1/2 59400 59400 1/2 59600 59600 1/2 59800 59800 1/2 60000 60000 1/2 60200 60200 1/2 60400 60400 1/2 60600 60600 1/2 60800 60800 1/2 61000 61000 1/2 61200 61200 1/2 61400 61400 1/2 61600 61600 1/2 61800 61800 1/2 62000 62000 1/2 62200 62200 1/2 62400 62400 1/2 62600 62600 1/2 62800 62800 1/2 63000 63000 1/2 63200 63200 1/2 63400 63400 1/2 63600 63600 1/2 63800 63800 1/2 64000 64000 1/2 64200 64200 1/2 64400 64400 1/2 64600 64600 1/2 64800 64800 1/2 65000 65000 1/2 65200 65200 1/2 65400 65400 1/2 65600 65600 1/2 65800 65800 1/2 66000 66000 1/2 66200 66200 1/2 66400 66400 1/2 66600 66600 1/2 66800 66800 1/2 67000 67000 1/2 67200 67200 1/2 67400 67400 1/2 67600 67600 1/2 67800 67800 1/2 68000 68000 1/2 68200 68200 1/2 68400 68400 1/2 68600 68600 1/2 68800 68800 1/2 69000 69000 1/2 69200 69200 1/2 69400 69400 1/2 69600 69600 1/2 69800 69800 1/2 70000 70000 1/2 70200 70200 1/2 70400 70400 1/2 70600 70600 1/2 70800 70800 1/2 71000 71000 1/2 71200 71200 1/2 71400 71400 1/2 71600 71600 1/2 71800 71800 1/2 72000 72000 1/2 72200 72200 1/2 72400 72400 1/2 72600 72600 1/2 72800 72800 1/2 73000 73000 1/2 73200 73200 1/2 73400 73400 1/2 73600 73600 1/2 73800 73800 1/2 74000 74000 1/2 74200 74200 1/2 74400 74400 1/2 74600 74600 1/2 74800 74800 1/2 75000 75000 1/2 75200 75200 1/2 75400 75400 1/2 75600 75600 1/2 75800 75800 1/2 76000 76000 1/2 76200 76200 1/2 76400 76400 1/2 76600 76600 1/2 76800 76800 1/2 77000 77000 1/2 77200 77200 1/2 77400 77400 1/2 77600 77600 1/2 77800 77800 1/2 78000 78000 1/2 78200 78200 1/2 78400 78400 1/2 78600 78600 1/2 78800 78800 1/2 79000 79000 1/2 79200 79200 1/2 79400 79400 1/2 79600 79600 1/2 79800 79800 1/2 80000 80000 1/2 80200 80200 1/2 80400 80400 1/2 80600 80600 1/2 80800 80800 1/2 81000 81000 1/2 81200 81200 1/2 81400 81400 1/2 81600 81600 1/2 81800 81800 1/2 82000 82000 1/2 82200 82200 1/2 82400 82400 1/2 82600 82600 1/2 82800 82800 1/2 83000 83000 1/2 83200 83200 1/2 83400 83400 1/2 83600 83600 1/2 83800 83800 1/2 84000 84000 1/2 84200 84200 1/2 84400 84400 1/2 84600 84600 1/2 84800 84800 1/2 85000 85000 1/2 85200 85200 1/2 85400 85400 1/2 85600 85600 1/2 85800 85800 1/2 86000 86000 1/2 86200 86200 1/2 86400 86400 1/2 86600 86600 1/2 86800 86800 1/2 87000 87000 1/2 87200 87200 1/2 87400 87400 1/2 87600 87600 1/2 87800 87800 1/2 88000 88000 1/2 88200 88200 1/2 88400 88400 1/2 88600 88600 1/2 88800 88800 1/2 89000 89000 1/2 89200 89200 1/2 89400 89400 1/2 89600 89600 1/2 89800 89800 1/2 90000 90000 1/2 90200 90200 1/2 90400 90400 1/2 90600 90600 1/2 90800 90800 1/2 91000 91000 1/2 91200 91200 1/2 91400 91400 1/2 91600 91600 1/2 91800 91800 1/2 92000 92000 1/2 92200 92200 1/2 92400 92400 1/2 92600 92600 1/2 92800 92800 1/2 93000 93000 1/2 93200 93200 1/2 93400 93400 1/2 93600 93600 1/2 93800 93800 1/2 94000 94000 1/2 94200 94200 1/2 94400 94400 1/2 94600 94600 1/2 94800 94800 1/2 95000 95000 1/2 95200 95200 1/2 95400 95400 1/2 95600 95600 1/2 95800 95800 1/2 96000 96000 1/2 96200 96200 1/2 96400 96400 1/2 96600 96600 1/2 96800 96800 1/2 97000 97000 1/2 97200 97200 1/2 97400 97400 1/2 97600 97600 1/2 97800 97800 1/2 98000 98000 1/2 98200 98200 1/2 98400 98400 1/2 98600 98600 1/2 98800 98800 1/2 99000 99000 1/2 99200 99200 1/2 99400 99400 1/2 99600 99600 1/2 99800 99800 1/2 100000 100000 1/2	

BLANK ALUMINIUM CHASSIS, 18 x w, 2 1/2 in. sides, 6 x 4 in. 5p, 8 x 6 in. **£1.40**, 10 x 7 in. **£1.55**, 14 x 9 in. **£1.90**, 16 x 6 in. **£1.85**, 12 x 3 in. **£1.20**, 16 x 10 in. **£2.20**, 12 x 8 in. **£1.70**.
ALUMINIUM PANELS, 18 x w, 1/4 in. 4 in. **24p**; 8 x 6 in. **38p**; 10 x 7 in. **54p**; 12 x 9 in. **50p**; 14 x 9 in. **70p**; 16 x 6 in. **70p**; 12 x 8 in. **94p**; 12 x 12 in. **£1.**; 16 x 10 in. **£1.16**.
ALUMINIUM ANGLE BRACKET, 1/2 x 1/2 in. **20p**.
ALUMINIUM BOXES, MANY OTHER SIZES IN STOCK
 2 x 2 x 2 in. **85p**; 3 x 2 x 2 in. **65p**; 4 x 2 x 2 in. **85p**; 5 x 6 x 6 in. **£1.50**; 6 x 4 in. **4in** **£1.70**; 10 x 7 in. **£2.20**; 12 x 8 in. **£2.50**; 12 x 8 x 3 in. **£2.50**.

THE "INSTANT

THE NEXT STEP FORWARD IN TIME

CASIO MEANS DIGITAL – New Lithium batteries lasting up to 5 years or more, totally eclipse most SOLAR watches

FOR THE EXECUTIVE WHO DOESN'T WANT HANDS ON HIS TIME



THIS YEAR'S STAR BUY

THE NEW 83QS – 27B ALARM CHRONOGRAPH

Optional display of hours, minutes, seconds, date, am/pm; or alternatively: Hours, minutes, alpha day, date, am/pm. The automatic calendar is set for 28 days in February. Casio's new Lithium battery lasts up to 4 YEARS or more. The chronograph times in 1/10 second units up to 12 hours, measuring net, lap and first and second place times. An indicator shows the chronograph is running when normal time is displayed. The 24 hour alarm can be set very easily to 1 minute intervals with an indicator to show the alarm is set. In addition the watch can be set to chime every hour, on the hour, with a separate indicator to show this function is on. A micro light illuminates the display at night time. This superb watch is stainless steel encased, has a mineral glass face and is guaranteed water resistant to 66 feet (2 at).



RRP £31.95 **£27.95**

COMPUTER GAMES

Fairchild Grandstand (Microprocessor). Video Entertainment Computer. (Special offer) **£69.50**
UFO Master Blaster Station. Guide missiles to destroy UFO's. Score against the clock. **£22.50**
Grandstand 4-in-1. Calculator/Auto Race/Code Breaker (as Mastermind)/Blackjack. **£22.50**
Grandstand Adam. Tune Memory/Pathfinder/Ditto (as Simon Says)/Bounce. **£22.50**
Amaze-A-Tron. Over 1 million mazes. 8 games. 1 or 2 players. Electronic sound effects. **£17.25**
Grandstand Solitaire. Absorbing. **£14.95**

CASIO CALCULATORS

AQ-2000. Clock, calendar, 2 alarms, stopwatch, time memory, countdown alarm. **£24.95**
MQ-11. Micro version of above. **£26.95**
CQ-82. Clock, 4 alarms, snooze, light. **£19.95**
HQ-21. Quartz clock and calculator. **£10.95**

Scientifics with non-volatile memory
FX-310 (8 digits) 50 sci functions. **£17.95**
FX-510 (10 digits) 50 sci functions. **£19.95**
FX-2600 (8) 43 sci funct. Ultra slim **£19.95**
FX-3200 (10) 43 sci funct. Ultra slim **£21.95**
 Others: **FX-80** £19.95, **FX-68** £19.95

Non-volatile Programmables
FX-501P £54.95, **FX-502P** £74.95
FA-1 Adaptor/Cassette interface **19.95**

There is no present like the time

CASIO LADIES WATCHES

Superbly styled stainless steel cases, with mineral glass face, water resistant to 100 feet, LC display of hours, minutes, 10 seconds, seconds by flash, am/pm; and with day, date and month.



86QL-10B **£26.50**



86QL-12B **£31.95**



26CGL-20L Gold plated **£53.25**

SUPER VALUE CHRISTMAS PRESENT

HQ-21 6 digit clock and calculator with full memory, %, Two AA batteries last 1 year. $\frac{1}{2} \times 3 \times 5\frac{1}{2}$ inches. **ONLY £10.95**

You cannot fight against the future Time is on our side. W. E. Gladstone

81CS-36B

LC Display of hours, minutes, seconds, day; And with day, date, month and year calendar pre-programmed to 2029.

4-5 YEAR BATTERY
 1/100 second chronograph to 7 hours.

Net, lap and first & 2nd place times.
 User optional 12 or 24 hour display.
 24 hour alarm.

User optional hourly chime.

Backlight.
 Mineral glass.
 Stainless steel case.

Water resistant to 100ft (3 at.)

RRP £39.95 **£35.95**



WE ARE NEVER KNOWINGLY UNDERSOLD AND WILL TRY AND MATCH OR BEAT ANY OTHER ADVERTISED PRICE PROVIDING THE ADVERTISER HAS STOCKS

IF YOU WANT A WATCH WITH Chrome plating that may wear off after a few months. A plastic glass that will scratch and scuff and you may not be able to replace. A module with around 25% failure rate, that may take weeks to repair. A dubious or non-existent spares service. If you want a watch that the manufacturer doesn't put his name on

THEN DON'T BUY A CASIO

GET THE MIDAS TOUCH BEFORE YOUR FRIENDS DO SUPERSWITCH Midas Touch Dimmer

The softest touch on the brushed aluminium panel of this beautifully styled control is all that is required to switch lights on and off and to vary lighting brilliance. Touch Midas with the fingertips and the light is on. Touch again and it's off. Allow the finger to rest on the panel and the light intensity changes smoothly through a cycle from bright to dim and back again. Removing the touch during the cycle sets the lighting at the level required. Once set, this brightness level will be maintained during normal on/off operations.

Meets latest BS for RF interference.

£14.95

CASIO CHRONOGRAPHS

Constant display of hours, minutes, seconds, am/pm and day (12 or 24 hour) Dual time (12 or 24 hour). Automatic day, date, month, year calendar pre-programmed to 2029. Chronograph measures net, lap and 1st and 2nd place times from 1/100 second to 7 hours. Backlight. Mineral glass face. Guaranteed water resistant to 66 or 100 feet.

NEW MODEL

95QS-32B

4 YEAR BATTERY
 Superbly styled brass case heavily chrome plated.
 Water resistant to 66 feet.
 (RRP £27.95)

£23.95



95QS-31B

(Left)
4 YEAR BATTERY
 S/S jacket.
 W.R. to 66 feet.

(£27.95)

£23.95



95CS-31B

(Right)
5 YEAR BATTERY
 Solid S/S case.
 W.R. to 100 feet.

(£34.95) **£29.95**



Time never stands still with Casio

F-200 SPORTS CHRONO

Hours, minutes, seconds am/pm. Day, date, month, 1/100 sec. chrono to 1 hour. Net, lap and 1st and 2nd place times. Backlight. Resin case/strap. Mineral glass, W.R. to 66 feet. Silver oxide battery.

(£17.95) **£15.95**



F-8C time/date 3 YEAR BATTERY

Hours, minutes, seconds, date, day, am/pm. Auto 28, 30, 31 day calendar. Backlight. Resin case/strap. Mineral glass. W.R. to 66 feet.

(£12.95) **£10.95**

NB. This watch does not have a stopwatch.



Most CASIO products available from stock. Send 25p for illustrated brochures and membership of our CHRISTMAS CLUB. EXTRA DISCOUNTS on many items.

Price includes VAT, P&P. Send your cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:-

TEMPUS

Dept. PW, Beaumont Centre, 164-167 East Rd., Cambridge CB1 1DB. Tel. 0223 312866

TRANSISTORISED DC TO AC INVERTERS

12v-24v-48v DC input models
110v or 240v AC off load
output models
Square-wave output or
optional filtered models
Frequency 50Hz or 60Hz models
(±5% typical)



All silicon power transistors
Separate driver and output
transformers
Designed for cool continuous
operation
Aluminium vented cased units
DC input fused

12v dc inputs/110v or 240v outputs
50Hz or 60Hz

N12/A—8"×6"×6" 40 watts	£21.00
N12/B—8"×6"×6" 60 watts	£27.00
N12/C—8"×6"×6" 100 watts	£33.00
N12/D—8"×6"×6" 150 watts	£38.00
N12/E—8"×6"×6" 200 watts	£46.00
N12/F—8"×6"×6" 250 watts	£54.00
N12/G—8"×6"×6" 300 watts	£60.00
N12/H—10"×8"×6" 400 watts	£75.00

Filtered waveform models available at 15% extra.

All post paid U.K.

24v DC inputs/110v or 240v outputs
50Hz or 60Hz

N24/A—8"×6"×6" 40 watts	£24.00
N24/B—8"×6"×6" 100 watts	£34.00
N24/C—8"×6"×6" 150 watts	£40.00
N24/D—8"×6"×6" 200 watts	£48.00
N24/E—8"×6"×6" 250 watts	£58.00
N24/F—8"×6"×6" 300 watts	£64.00
N24/G—10"×8"×6" 400 watts	£77.00
N24/H—10"×8"×6" 500 watts	£88.00
N24/I—12"×8"×8" 700 watts	£116.00
N24/J—12"×8"×8" 1000 watts	£170.00

Filtered waveform models available at 15% extra.

All post paid U.K.

48v DC inputs/110v or 240v outputs
50Hz or 60Hz

N48/A—8"×6"×6" 50 watts	£25.00
N48/B—8"×6"×6" 100 watts	£34.00
N48/C—8"×6"×6" 150 watts	£40.00
N48/D—8"×6"×6" 200 watts	£49.00
N48/E—8"×6"×6" 250 watts	£58.00
N48/F—8"×6"×6" 300 watts	£67.00
N48/G—10"×8"×6" 400 watts	£78.00
N48/H—10"×8"×8" 500 watts	£92.00
N48/I—12"×10"×8" 700 watts	£120.00
N48/J—12"×10"×8" 1000 watts	£180.00
N48/K—12"×10"×10" 1500 watts	£240.00

Filtered waveform models available at 15% extra.

All post paid U.K.

Please add £5.00 carriage per unit U.K. overseas at cost
Delivery 10 to 21 days subject to availability — Cased sizes subject to variations
Callers strictly by appointment — Telephone enquiries 01-736 0685, — 01-748 5778
Prices subject to fluctuation

ELECTROVANCE

104a Brackbury Road,
London W6

NEW FROM MAGNUM

DIGITAL INDICATION OF RADIO FREQUENCY using a unique combination of FUTABA FLUORESCENT DISPLAY (the 'Green One') and OKI COUNTCR/DRIVER.

Combination 1	Special Price Offer £21.38
OKI MSM 5524RS	AM, FM, SW
OKI MSL 2318	Pre-Scaler
FUTABA 6-LT-09	5 digits + MHz, KHz
Crystal	3.2768 MHz
Combination 2	Special Price Offer £18.32
OKI MSM 5525RS	AM, FM
OKI MSL 2318	Pre-Scaler
FUTABA 6-LT-06	3½ digits + MHz, KHz + AM, FM
Crystal	6.5536 MHz
Combination 3	Special Price Offer £24.57
OKI MSM 55271	AM, FM, SW
OKI MSL 2318	Pre-Scaler
FUTABA 7-LT-02	5 digits + MHz, KHz + AM, FM
Crystal	6.5536 MHz

Send today for your Combination (suggested circuit details and FREE I/C Socket are included) and enjoy "spot on" visual tuning.
OUR NEW CATALOGUE IS NOW READY. Send S.A.E.

MAGNUM AUDIO Ltd.
DEPT. PW1, 13 HAZELBURY CRESCENT,
LUTON, BEDS. LU1 1DF.
TEL: 0582 2887

VALVES

A1065 1.40	ECL85 0.75	GZ37 2.80	PY80 0.70	UY85 0.60	6AS5 0.90	6SK7 1.05
A2293 8.50	ECL86 0.75	KT66 5.75	PY81/800 2.15	VR105/30 2.15	6AT6 0.85	6SL7GT 0.85
A2900 8.00	EF37A 1.70	MH4 1.15	PY82 0.60	VR150/30 1.45	6AU6 0.85	6SN7GT 0.85
AR8 0.70	EF39 3.30	ML6 1.15	PY83 0.60	X66 1.05	6AX4GT 0.95	6S07 0.85
ARP3 0.70	EF40 0.80	N78 10.45	PY88 0.80	X61M 1.70	6AX5GT 1.15	6V6GT 0.95
ATP4 0.60	EF41 0.85	OA2 0.65	PY500 1.55	Z800U 3.45	6BA5 0.50	6X5GT 1.15
B12H 3.35	EF80 0.50	OB2 0.70	PY801 0.70	Z801U 4.00	6BE6 0.60	6Y6G 0.60
CY31 1.20	EF83 1.70	PC85 0.60	00V03/10 2.85	Z900T 2.55	6BG6G 1.15	6Z4 0.75
DAF96 0.70	EF85 0.55	PC86 0.95	00V03/12 2.85	1A3 0.50	6BJ6 1.25	6-30L2 2.05
DF96 0.70	EF91 1.30	PC88 0.85	00V06/40A 15.4	114 0.50	6BD7A 0.70	7B7 0.90
DK96 1.05	EF92 0.85	PC900 1.45	00V06/40A 16.10	154 0.45	6BR7 2.70	7V4 0.90
DH76 1.00	EF95 0.95	PCC89 0.85	PCC89 0.85	155 0.45	6BW6 3.20	902 0.70
DL92 0.60	EF183 0.85	PCC189 0.75	0V03-122.80 114	174 0.45	6C4 0.70	90B 0.85
DY86/87 0.85	EF184 1.85	PCF80 0.95	SCL400 4.50	104 0.80	6C5 0.70	10C2 0.70
S551 13.80	EF200 0.95	PCF84 0.75	SCL600 4.50	1X2B 1.30	6C6 7.50	10F18 0.70
EB8CC/11.60	EH90 0.80	PCF86 0.80	SP61 0.95	2021 0.80	6CH6 1.15	11E2 12.40
E180CC 1.60	EL32 1.10	PCF200 1.05	U25 1.15	2X2 0.90	6C15 1.70	12A6 0.70
E180F 6.80	EL34 1.75	PCF201 1.05	U26 1.00	3A4 0.70	6D6 0.85	12AT6 0.55
E182CC 3.95	EL37 3.45	PCF801 1.05	U27 1.15	30B 0.50	6E8 3.20	12AT7 0.65
EA76 2.25	EL38 4.60	PCF802 0.75	U91 0.85	30D1 23.00	6F6G 0.85	12AU6 0.60
EABC80 0.60	EL41 0.95			3E29 0.60	6F8G 0.85	12AV6 0.80
EB91 0.65	EL81 1.20			3S4 0.60	6F12 0.90	12AX7 0.65
EB93 1.15	EL82 0.70			5B/254M 8.80	6F14 0.90	12BA6 0.80
EBF80 0.60	EL84 0.90	PCF805 2.10	U281 0.85	5B/255M 8.80	6F15 1.30	12BE6 1.25
EBF83 0.60	EL86 1.05	PCF806 0.95	U301 0.85	5B/258M 8.80	6F17 1.15	12BH7 1.10
EBF89 0.80	EL90 1.50	PCF808 2.05	UGD0 11.50	5R4G1 1.30	6F24 4.75	12C8 0.85
EC52 0.50	EL91 3.25	PCH200 0.95	UB01 0.90	5R4G2 1.30	6F33 4.75	12E1 4.95
EC58 1.05	EL95 0.80	PCL81 0.70	UABC80 0.90	5U4G 1.10	6H6 1.90	12J5GT 0.80
EC62 0.65	EL104 1.85	PCL82 0.75	UAF42 0.85	5U4G 1.10	6J4 1.60	12K6GT 0.80
EC63 0.65	EL102 1.70	PCL84 0.80	UBF80 0.70	5V4G 0.80	6J6 0.85	12Q7 0.65
EC64 0.55	EL122 7.50	PCL86 0.80	UBF89 0.60	5Y3GT 0.60	6J7 0.90	12SH7 0.65
EC68 0.60	EM31 0.85	PCL805/85 0.85	UBL1 1.15	5Z3 1.15	6J7G 0.60	12SJ7 0.85
EC68 1.40	EM80 0.70	PO500 4.35	UBL2 2.50	5Z4G 0.85	6K7 0.80	12S07 0.85
EC68 0.75	EM81 0.70	PH200 2.80	UCC84 0.75	5Z4GT 0.90	6K7G 0.50	12Y4 0.55
EC68 0.95	EM84 0.50	PL36 0.95	UCC85 0.80	6AB7 0.70	6K8GT 0.85	1306 0.70
ECF80 0.50	EV81 1.15	PL36 0.95	UCF80 0.50	6AC7 0.70	6L6M 2.15	14S7 1.15
ECF80 0.55	EV81 0.55	PL81 0.95	UCF81 0.70	6AH6 1.15	6L6GT 1.75	19A05 0.90
ECM34 1.15	EV86/87 0.85	PL82 0.60	UCL82 0.85	AK5 0.65	6L7G 0.75	19C3 11.50
ECM35 1.70	EV88 0.65	PL83 0.60	UF41 0.90	6AK8 0.60	6L8 0.70	19G6 6.90
EDH42 0.55	F280 0.55	PL84 0.75	UF80 0.60	AL5 0.50	6L020 0.90	19H5 19.55
EDH81 0.60	Z281 0.10	PL504 1.50	UF85 0.70	6ALSW 0.80	607G 0.95	2001 0.75
EDH84 1.20	GY501 1.05	PL509 3.85	UL84 0.85	6AM5 1.85	6SA7 0.65	20F2 0.75
ECL80 0.70	GZ32 0.75	PL802 3.15	UM80 0.70	6AN8 3.60	6S7G 0.90	20E1 1.30
ECL82 0.65	GZ33 3.95	PL80 3.45	UM84 0.70	6AN8 3.60	6SJ7 0.80	20P1 0.65
ECL83 1.40	GZ34 2.30	PY33 0.70	UY82 0.85	6AD5W 1.45	6SL7GT 0.80	20P3 0.80
						20P4 1.30

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 80p; over £10 free, minimum order £1.
A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.


VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors, etc.; retail 749 3934, trade and export 743 0899.

COLOMOR 907353/
907353/
LONDON
(ELECTRONICS) LTD.
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

It's on it's way . . .
the brand new **1980** edition of the

World Radio TV Handbook.

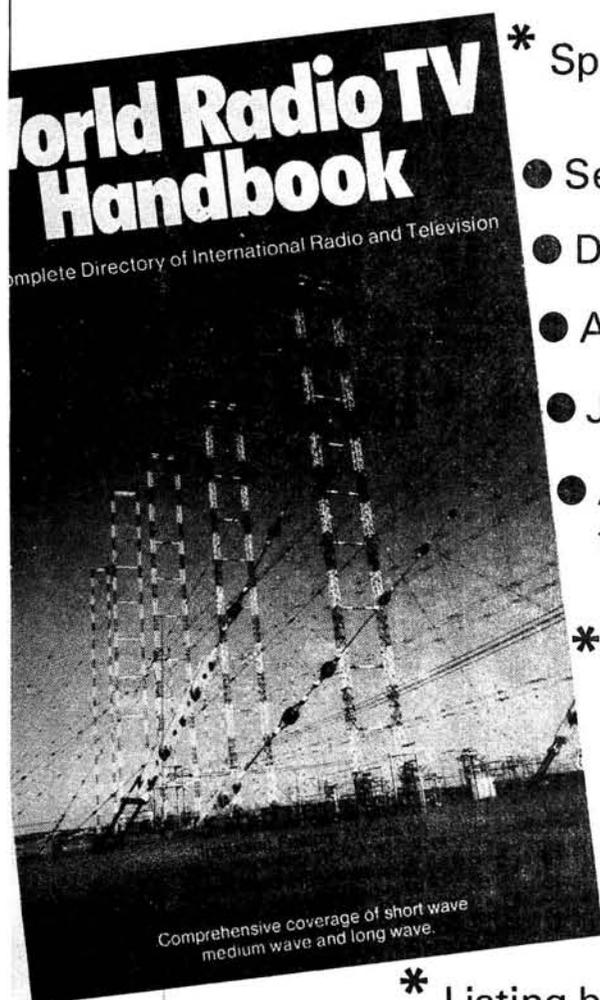The *only* directory of International Broadcasting!
The standard reference of DXer's, SWL's and professionals!



* Special articles will include:-

- Selected previews of New Receivers
- DX Clubs and their Activities
- Aspects of propagation
- Jamming and its problems
- A variety of features covering the main interests of DXer's/SWL's

* Completely updated reference section with frequencies, times, languages, addresses, and details of all known SW, and most MW stations

* UK price unchanged £8.50

* Listing by frequency of the worlds SW/MW/LW stations, and *essential* information for the active listener

W.R.T.H. will be published 5th January 1980

Available from your bookseller or direct from:-

UK
Billboard Ltd
7 Carnaby Street
London W1
439 9411

UK TRADE
Argus Books Ltd
14 St. James Rd.
Watford
Herts.

USA
Billboard Publications
Watson Guptill
One Astor Plaza
New York 10036

EUROPE
J. Frost
Soliljevej 44
2650 Hvidovre
Denmark



Receivers and Components

VALVES

Radio - T.V. - Industrial - Transmitting
Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 50p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN
West Wittering 2023 (STD Code 024366)

LARGE RANGE of specialised components for radio controlled home construction. SAE for lists please. Trio Instruments Limited, (Dept. PW.) Dartford Road, Farningham, Kent. DA4 0DZ.

SURPLUS TO INDUSTRIAL REQUIREMENTS

100 mixed Min. Electrolytics	£3.00
300 pack 220mfd 10V	£1.50
25 mixed Large Can	£3.00
10 4700mfd 40V Tag 3 x 1 1/2	£1.20
10 200mfd 70V Tag 1 1/2 x 2 1/2	£1.20
10 200mfd 450V Tag 4 1/2 x 1 1/2	£1.20
100 mixed Preset Spindle Pots.	£3.00
10 100K Dual 1/2 watt Lin. Pots.	£2.00
24 mixed Voltage S/pole Relays	£3.00

Add 30p per item P&P. All prices inc. VAT.

BLORE-BARTON

Reedham House, Burnham, Bucks.

VHF TUNERHEAD 45-220MHz. 30MHz IF output, ideal feed HF receiver. £6.00, 60p post. 45-220, 440-870MHz tuner £14.00 60p post. SAE data & lists on many items. H. Cocks, Bre Cottage, Staplecross, Robertsbridge, E. Sussex. Tel: 058083-317.

Southern Valve Co.,

2nd Floor, 6 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. **NO CALLERS**, SAE Lists, Cash with order. Same Day Postal Despatch.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 6 Potters Road, New Barnet, Herts.
Tel: 01-449 1934/5 (1934 Recording Machine).

AM/CW/SSB COMMUNICATION RECEIVER and preselector modules. The cheapest way to good amateur and BC DX.

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc: HC33/U. 1.0. 1.008. 2.5625 MHz. **£3.50**. 1.280 MHz. **£4.15**. HC18/U. 4.0. 5.0. 6.0. 7.0. 8.0. 9.0. 10.0. 10.7. MHz. **£3.00**. 12.0. 15.0. 16.0. 18.0. 20.0. 6.9375. 38.6667. MHz. **£3.25**. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 6 weeks from **£3.90**.

FILTERS Your best source for 6 and 8 pole and monolithics for AM, CW, SSB, FM, on 455 kHz. 1.6. 9.0. 10.7. 21.4 MHz. etc.
Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEDD ELECTRONICS
G3EDW, Marriott, Somers, TA16 5NS.
Tel: 0460 73718

SMALL ADS

The prepaid rate for classified advertisements is 22 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

ELECTRONIC COMPONENTS. Quick delivery, wide range from stock catalogue on request. J. R. Hartley Electronic Components, 78B High Street, Bridgnorth, Salop WV16 4DY.

TUNBRIDGE WELLS COMPONENTS, BALLARD'S, 108 Camden Road, Tunbridge Wells, Tel: 31803. No Lists. Enquiries S.A.E.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7, & 10 mfd. — 5p.
22, 47—5 1/2p. (50V—6p.). 100—7p. (50V—8p.).
220—8p. (50V—10p.). 470—11p. (40V—16p.).
1000/15V—15p. 1000/25V—18p. 1000/40V—35p.

Subminiature bead tantalum electrolytics.
0.1 0.22, 0.47, 1.0 = 35V 4.7 = 6.3V—14p.
2.2/25V, 4.7/25V—15p. 10/25V, 15/16V—15p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V—20p.
15/25V, 22/25V, 47/10V—26p. 47/16V—36p.

Mullard Miniature Ceramic E12 Series 63V 2%.
10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.

Vertical Mounting Ceramic Plate Caps 50V.
E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p.

Polystyrene E12 Series 63V. Hor. Mounting.
10 pf. to 820 pf.—3p. 1000 pf. to 10000 pf. 4p.

Miniature Polyester 250V. Vert. Mtg. E6 Series.
01—068—4p. 1—5p. 15, 22—6p. 33, 47—10p.
68—12p. 1.0—15p. 1.5—22p. 2.2—24p.

Mylar (Polyester) Film 100V. Vertical Mtg.
.001, .002, .005—3 1/2p. .01, .02—4 1/2p. .04, .05—5 1/2p.

Miniature Film Resistors Highstab. E12 5%.
0 125 watt 10 Ω 2MΩ — 1p
0 250 watt 1 Ω to 10MΩ (10% over 1M). — 2p
0 500 watt 10 Ω to 2MΩ — 2p
1 000 watt 10 Ω to 10MΩ. — 2p

1N4148—2p, 1N4002—4p, 1N4006—6p, 1N4007—2p
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—10p.
8 Pin Dil. i.c.s. 741's—18p. 555's—24p.

20mm. fuses 15, 25, 5, 1.0, 2.0, 3.0 & 5A—3p.
20mm. fuseholders P.C. or Chassis Mtg.—5p.
Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

100 7400 SERIES IC + 100 Diodes 4148 type. Marked and Unmarked, Untested. 100 + 100 £1.50. STE LTD., Uni-Com Building, Edenbridge, Kent. TN8 6EW.

100 MIXED COMPONENTS E12-75. Sole Electronics, 37 Stanley Street, Ormskirk, Lancs. L39 2DH.

Books and Publications

WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS. A genuine opportunity to success. **LARGE PROFITS.** You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. **NO PREVIOUS KNOWLEDGE IS REQUIRED,** as the manual covers in 13 chapters, where to obtain all the work you need, materials required, all instructions, rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. £4.00 plus 30p P&P. UK. CWO, to INDUSTRIAL SUPPLIES, 102, Parrswood Rd., Wittington, Manchester 20, Dept. PW.

RADIO BOOK SERVICE

WORLD RADIO TV HANDBOOK 1979 Edition. £9-25
Radio Stations Guide. £1-55
Long distance Television Reception for the Enthusiast. £1-55
Popular Electronic Projects. £1-55
Electronic Projects for Beginners. £1-45
Mobile Discophone Handbook. £1-45
Radio Circuits using IC's. £1-45
Projects in Opto-Electronics. £1-35
How to make Walkie-Talkies. £1-35
Radio Antenna H'book for Long Distance Reception. £1-35
How to build your own Metal & Treasure Locators. £1-35
How to build Advanced Short Wave Receivers. £1-30

PRICES INCLUDE POSTAGE & PACKING...
4 CHILCHESTER COURT, WICKHAM RD, BECKENHAM KENT BR3 2QW

FREE. World-famous manufacturers convenient, pocket-sized electronic construction guide (nearly 200 full-colour illustrations). Limited period offer. Send S.A.E. now to TECHNOCENTRE, 54 Adcott Road, Middlesbrough.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

Build your own

P.A., GROUP & DISCO SPEAKERS

by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, line source, I.B., Horn and Reflex types, for 8"-18" drive units. **£3.95** post free (\$6 overseas).

THE INFRA-BASS LOUDSPEAKER

by G. Holliman

(full constructional details for versions using 15", 12" and 10" drive units.) **£2.95** post free (\$6 overseas)

THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. **£2.20** post free (\$5 overseas).

VAN KAREN PUBLISHING

5 SWAN STREET, WILMSLOW, CHESHIRE

For Sale

NEW BACK ISSUES of "PRACTICAL WIRELESS" available 70p each, post free. Open P.O. Cheque returned if not in stock - BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

YAESU FRG. 7 Communications Receiver. Mint Condition. £155. (01) 572 2504 (Evenings) Hounslow.

PAIR OF used Facsimile Telecopiers £200 o.n.o. 01-366 7101 evenings.

90W AM TX. Class D Wavemeter. Chilton, 30 Bleakhouse Rd., Warley, West Midlands.

REALISTIC DX160 COMMUNICATIONS Receiver. Under Year old. Condition as new £80. Telephone Rhayader 810493.

HRO RECEIVER immaculate. Five Coils, P.S.U. HRO Spares. Coils, S.A.E. Details. Box 147.

GARRARD Turntable offers. Ring Penzance 67313.

Auction Sale

Auction of Vintage and Post Vintage Radio Equipment

100 Lots including: National VHF and three Eddystone Receivers, Muirhead Condenser and Radio Components etc. **SALE: 12th DECEMBER 1979 AT 10.30 A.M. - AT NEWBURY SALEROOMS**
VIEW: 10th and 11th DECEMBER 1979, 9.30 A.M. - 4 P.M.
CATALOGUES: 40p (including postage) from Drewett Watson and Barton, 22 Market Place, Newbury, Berks. Tel:(0635) 46000 Telex: 848580.

Business Opportunities

IN VIEW OF CURRENT Government moves towards free enterprise in sale of telephones and their installation we may be presented with the largest instant growth industry opportunity of the decade. We are the largest reproduction telephone manufacturers and importers in the U.K. We wish to grasp these opportunities. You are interested in handling sales and/or installation of a wide variety of decorative telephones. You wish to grasp these opportunities. Please write for details, enclosing 2 x 10p stamps for a brochure of our telephones if required, and enclosing relevant details about yourself which will be held in strict confidence. **CONVERSATION** Pieces, 55 Swindon Road, Cheltenham, Glos. Cheltenham 35707.

Instrument Mechanics and Instrument Fitter/ Machinists

To work in the following areas of the Instrument Department:-

* Machining and fitting * Assembly * Wiring * Test * Maintenance * Calibration * Engine test preparation.

The Aero Division of Rolls-Royce Limited are seeking to employ experienced and qualified men and women to join the existing teams based at Derby.

The work involves a wide range of equipment from simple voltage and current meters to complex microprocessor and computer based systems.

Applicants should have served a recognised apprenticeship or H.M. Services equivalent in radio/TV, radar, instrumentation, electrics, precision instrument making, fitting, machining or other relevant field. Whilst experience of instrumentation would be an advantage it is not essential.

The posts are on our dayshift (with 3 shift working as and when required) and on our permanent 3 shift system.

The work is interesting and challenging offering scope for promotion.

A high basic wage is offered with generous additional premiums for overtime and shift working. In addition attractive fringe benefits include free safety shoes and overalls, subsidised meals and full factory staff conditions after only 12 months service. In addition the Company provides a comprehensive pension scheme with life assurance, excellent sport and welfare facilities. Assistance with relocation expenses will be given in appropriate cases.

To apply either fill in the quick response coupon and mail FREEPOST, (no stamp required) to:-

M. Barnard, Employment Office, Aero Division, Rolls-Royce Limited, P.O. Box 31, Derby DE2 8XA.

or telephone Derby (0332) 42424 ext 569 for an application form or call in at the:

Employment Office, Nightingale Road, Derby, 8.30am until 5pm Monday - Thursday and 8.30am to 4pm Friday, or 9am to 12 noon Saturday.

Quick Response Coupon: Ref. PQ/160 

Name..... Age.....

Address.....

Telephone (if any).....

Apprenticeship served with (name of company or H.M. Services).....

Present employer (if you wish to state).....

Tick times preferred for informal interview

Weekdays Evenings Saturday mornings



AERO DIVISION
Come with us into the 21st century

TESTERS Test Technicians, Test Engineers - Earn what you're really worth in London working for a World Leader in Radio & Telecommunications. Phone Len Porter on 01 874 7281 or write - REDIFON TELECOM-MUNICATIONS LTD., Broomhill Road, Wandsworth, London SW18.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood, FY7 8JZ.

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. Q277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. Q277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. Q277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

Courses

COURSES-RADIO AMATEURS EXAMINATION. City & Guilds. Pass this important examination and obtain your G8 licence, with an RRC Home Study Course. For details of this, and other courses (GCE, professional examinations etc) write or phone - THE RAPID RESULTS COLLEGE, DEPT JX 1, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service) or for prospectus requests ring 01-946 1102 (24hr Recordacall).

Aerials

AERIAL BOOSTERS

Improves weak VHF Radio and Television reception. B45-UHF TV, B11-VHF Radio, B11A-2 metres For next to the set fitting.
Price £6. S.A.E. for Leaflets. ACCESS

ELECTRONIC MAILORDER LTD,
62 Bridge Street,
Ramsbottom, Bury, Lancs, BLO 9AG.

COPPER AERIAL WIRE 14swg hard drawn 70' £3.50. 140' £7.00. inc. VAT. Postage £1.00. T.M.P. Electronic Supplies. Britannia Stores, Leeswood, Nr. Mold, N. Wales.

KILL THAT INTERFERENCE

G2DYM ANTI-T.V.I. TRAP DIPOLES:

S.W.L. Indoor models £14.50 & £27.50

S.W.L. Outdoor models £30.00 & £34.50

Tx-ing models £36.00, £46.00 & £54.75

Lists 10x8in SAE. Aerial Guide 50p.

Indoor and invisible aerials for S.W.L.'s £3.50.

G2DYM, Uplowman, Tiverton, Devon.

Record Accessories

STYLI, Cartridges For MUSIC CENTRES, etc. FREE List No. 29 For S.A.E. includes Leads, Mikes, Phones etc. **FELSTEAD ELECTRONICS, (PW),** Longley Lane, Gatley, Cheshire, SK8 4EE.

Service Sheets

G.T. THE TECHNICAL INFORMATION SERVICE

76 CHURCH ST., LARKHALL, LANARKS ML9 1HE

1000's of service sheets - any single sheet £1 + L.S.A.E.

1000's of service manuals in stock for immediate despatch.

1000's of repair manuals in stock for immediate despatch.

S.A.E. for full details, quotations, newsletter, bargain offers eg. service sheets under 40p each - by return post.

FREE £4 vouchers when you send very large S.A.E. with £2 for our 2 GIANT SERVICE SHEET & MANUALS CATALOGUES + free gift.

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 24p. plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BEL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1.00 plus SAE Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 King's Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

Wanted

WANTED ANY Information concerning Mullard Oscilloscope CIRCA 1945 model number E805 RT 122 also for sale unused 2-volt glass lead - acid battery by Oldham, Easingwold 810354.

ELECTRONIC COMPONENTS PURCHASED. All Types Considered - Must be new. Send detailed list - Offer by return -. **WALTONS, 55A Worcester Street,** Wolverhampton.

Miscellaneous



BELLS AND SIRENS
CARTERS SIREN £5.95
INDUSTRIAL SIX INCH BELL £9.52
PRICES INCLUSIVE.
SEND CHEQUE. P.O. to:
CWAS ALARM
11 Denbrook Walk,
Bradford BD4 0QS



6 to 12v D.C. 12v D.C.
SAE for full price list of Professional Burglar Alarm Equipment.

SUBERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry and the Trade. **BAZELLI, (Dept No. 25) St. Wilfrids, Foundry Lane,** Halton, Lancaster. LA 6LT.

QUALITY ELECTRONIC COMPONENTS AT LOW PRICES

Write or Telephone for free pamphlet to:

HARRISON BROS, Dept. P.W.

P.O. Box 55, Westcliffe-on-Sea,

Essex SS0 7LQ.

Telephone:- Southend-on-Sea 32338

YOU SIMPLY cannot buy a more sophisticated intruder alarm system for any less. Prices from £45 to £125 for complete systems. Details from **KRAM ELECTRONICS,** 30 Hazlehead Road, Anstey, Leicester.

KEEP ONE HANDY IN THE WORKSHOP



The unique aerosol treatment for minor burns and scalds. From Boots and other Chemists.

Miscellaneous

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
Cassette B: 12-24 w.p.m. for professional examination preparation. Each Cassette are type C90.
Morse Key and Buzzer unit for sending practice.
Price each Cassette (including booklets) £4.75. Morse Key and Buzzer £4.75.
Prices include postage etc. Overseas Airmail £1-50 extra.

MHEL ELECTRONICS (Dept P.W.), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

NORTHERN IRELAND. Build your own computer. Nascom-1 Microcomputer kits. From P&O Computers (N.I.). 81 Dublin Road, Belfast, BT2 7HF. Tel: 22010. Evenings. Donaghmore 312. Belfast 621706.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
Reg. Office 22 Coningsby Gdns

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

14, 16, 18	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT
SAE brings list of copper & resistance Wires
Dealer Enquiries Invited

SOLAR CELLS, Batteries, Panels, Thermoelectric Generators, Heat pipes, Books etc. Details; Edencombe Ltd., 34 Nathans Road, N. Wembley, Middx. HA0 3RX.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call, Sandwell Plant Ltd. 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764, or see them at T.L.C. 32 Craven Street, Charing Cross, London WC2.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for thicker 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/packing 60p. **WHITE HOUSE ELECTRONICS,** P.O. Box 19, Castle Drive, Penzance, Cornwall.

144 MHz MKII Converter with OSC Trimmer £18.00, Board & Parts £9.00.

144 MHz MKII Converter with 116 MHz Output for Transverter £19.00, Board & Parts £9.30.

144 MHz Class A PA 2w in >10w out £22.00, Board & Parts £10.92.

Units supplied with Belling Lee Sockets. BNC or SO239 at 80p extra.

SPECTRUM COMMUNICATIONS

12 Weatherbury Way, Dorchester, Dorset DT1 2EF
Prices inclusive of P. & P.

REEL RECORDERS, Ferrograph, Tandberg, UHER, Vortexion, etc. From £36. SAE details. A. E. Wright, Sunningdale, Broadheath, Worcester.

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for fast charge HP7 (AA) £1.05. SUB C £1.36, HP II (C) £1.98, HP 2 (D) £3.02, PP 3 £3.79, PP 3 charger £5.40.
 All the above nickel cadmium batteries are brand new and are guaranteed full spec. devices.
 All cells are supplied complete with solder tags (except PP 3).
 Brand new full spec. RECHARGEABLE SEALED ACID maintenance free batteries suitable for burglar alarms etc.
 1.2 amp hr. 6v £4.07. 2.6 amp hr. 6v £5.23.
 Quantity prices available on request. Data and charging circuits free on request with orders over £10, otherwise 30p post and handling (specify battery type). Please add 10% P&P on orders under £10 - 5% over £10. VAT at the current rate should be added to total order. Cheques, Postal Orders, Mail order to:-

SOLID STATE SECURITY DEPT. (PW),
 10 Bradshaw Lane, Parbold, Wigan Lancs.
 Tel: 02675 4726.

MSF CLOCK

NEW! Shows continuous Date, Hours, Minutes, Seconds, 8 digit LED - larger digits for Hours and Minutes, also parallel BCD output, auto-reset after power failure, auto GMT/BST and leap year, only 5x8x15cm, built-in 60KHz antenna, 1000Km range, all parts, case, printed circuit, instructions, postage etc. money back assurance, send £48.80 for the RIGHT TIME - NOW.

CAMBRIDGE KITS

45 (PA) Old School Lane, Milton, Cambridge.

SEEN MY CAT? 5000 Odds and ends. Mechanical. Electrical. Cat free. Whiston Dept. PW, New Mills, Stockport.

GUITAR/PA/MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive. 12 months guarantee. Unbeatable at £44; 60 watt £37; 200 watt £59; 100 watt twin channel sep. treble/bass per channel £58; 60 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves: 100 watt £32; 200 watt £50; fuzz boxes, great sound £8.50; bass fuzz £9.50; overdriver fuzz with treble and bass boosters £15.50; 100 watt-combo superb sound overdrive, sturdy construction, castors, unbeatable £90; twin channel £100; bass combo £100; speakers 15in. 100 watt £35; 12in. 100 watt £23; 60 watt £15; microphones Shure Unidyne B £26.

Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Avenue, Dukinfield, Cheshire.
 Tel: 061-344 5007 or 061-308 2064

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME.....

ADDRESS

Send to: Classified Advertisement Manager

PRACTICAL WIRELESS,
 GMG, Classified Advertisement Dept., Rm. 2337,
 King's Reach Tower, Stamford Street,
 London SE1 9LS Telephone 01-261 5846

Rate
 22p per word, minimum 12 words. Box No. 60p extra.


Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

Electronics

Make a job~or hobby~of it.....

The opportunities in electronics, today, and for the future are limitless - throughout the world - jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics - especially for the servicing of radio, T.V. and all associated equipment - can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on the world market.

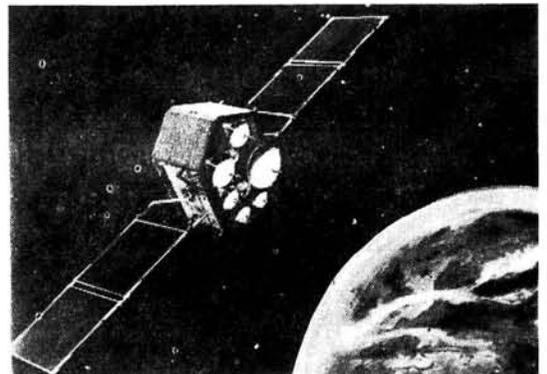We give modern training courses in all fields of electronics - practical D.I.Y. courses - courses for City and Guild exams, the Radio Amateur Licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years of experience in the subject. - Details sent without any obligation from . . .



Free! Brochure without obligation to.

British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

WB180

Block caps please

TTLs BY TEXAS		74221		160p		74LS192		140p		74C157		250p		LINEAR I.C.s		MC1496		TRANSISTORS		TIP41C		2N3856		DIODES																																																																																																																																																																					
7400	11p	7401	12p	7402	12p	7403	14p	7404	14p	7405	18p	7406	32p	7407	32p	7408	19p	7409	19p	7410	15p	7411	15p	7412	20p	7413	30p	7414	60p	7415	27p	7416	27p	7417	27p	7420	17p	7421	40p	7422	22p	7423	34p	7424	34p	7425	30p	7426	40p	7427	34p	7428	36p	7429	30p	7430	17p	7431	17p	7432	30p	7433	40p	7434	35p	7435	35p	7436	17p	7437	17p	7438	17p	7439	17p	7440	17p	7441	70p	7442A	60p	7443	112p	7444	112p	7445	100p	7446A	93p	7447A	70p	7448	80p	7449	17p	7450	17p	7451	17p	7452	17p	7453	17p	7454	17p	7455	17p	7456	17p	7457	36p	7458	36p	7459	36p	7460	36p	7461	36p	7462	36p	7463	36p	7464	36p	7465	36p	7466	36p	7467	36p	7468	36p	7469	36p	7470	36p	7471	36p	7472	36p	7473	36p	7474	36p	7475	36p	7476	36p	7477	36p	7478	36p	7479	36p	7480	36p	7481	36p	7482	36p	7483A	36p	7484	36p	7485	36p	7486	36p	7487	36p	7488	36p	7489	36p	7490A	36p	7491	36p	7492A	36p	7493A	36p	7494	36p	7495A	36p	7496	36p

All you need for listening!



PRACTICAL HI-FI

Every month

Listen with the complete hi-fi magazine

RED LEADS
0.125" 12p 50-10p
0.2" 12p 50-10p

For full lists please send S.A.E. or see our full page advertisements in P.E., E.T.I., Wireless World.

Please add 30p p&p and VAT at 15%

TECHNOMATIC LTD

Govt., Colleges, etc. orders accepted. Callers welcome


17 BURNLEY ROAD

MON-FRI 9.30-5.30 SATURDAY 10.30-4.30

LONDON NW10

Tel: (01) 452 1500 Telex: 922 800

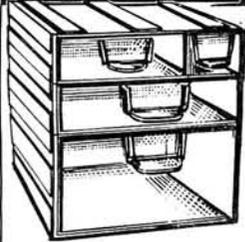NEAT! TIDY! HANDY! 1D 2D 3D 6D
INTERLOCKING PLASTIC STORAGE DRAWERS



AS SUPPLIED: TO POST OFFICE & GOVT DEPTS

SINGLE UNITS (1D) (5in x 2 1/2 in x 2 1/2 in) £3.70 DOZEN
 DOUBLE UNITS (2D) (5in x 4 1/2 in x 2 1/2 in) £5.90 DOZEN
 TREBLE (3D) £5.90 for 8.
 DOUBLE TREBLE 2 drawers, in one outer case (6D2) £8.90 for 8.
 EXTRA LARGE SIZE (6D1) £7.90 for 8.

PLUS QUANTITY DISCOUNTS
 Orders over £20, less 5%. Orders over £60, less 7 1/2%.
PACKING/POSTAGE/CARRIAGE: Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES.
 Please add 15% V.A.T. to total remittance.
 All prices correct at time of going to press.

124 Cricklewood Broadway, London N.W.2
 Telephone 01-450 4844


FLAIRLINE SUPPLIES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.
 As supplied to Post Office, Industry and Government Depts.

24 TUNE DOOR CHIMES

DOOR TUNES £17.13 + VAT.

Waddington's Videomaster announce a doorbell that doesn't go Brrringgg, Ding-Dong or Bzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.

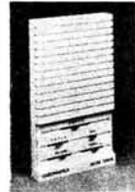

T.V. GAMES

PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/left/right) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played.
 Manufactured by Waddington's Videomaster and guaranteed for one year.



EXTRA CARTRIDGES:

- ROAD RACE - £8.87 + VAT.** Grand Prix motor racing with gear changes, crash noises
- SUPER WIPEOUT - £9.17 + VAT.** 10 different games of blasting obstacles off the screen.
- STUNT RIDER - £12.16 + VAT.** Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.
- NON PROGRAMMABLE TV GAMES**

- 6 Game - COLOURSCORE II - £13.50 + VAT.**
- 10 Game COLOUR SPORTSWORLD £22.50 + VAT.**

CHESS COMPUTERS

STAR CHESS - £56.09 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

using your own TV to display the board and pieces. Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



CHESS CHALLENGER 7 - £86.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.
 Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.



ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT.


A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £17.17 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game night up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 6 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

DRAUGHTS COMPUTERS

CHECKER CHALLENGER 2 LEVELS £43.00 + VAT. 4 LEVELS £78.00 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

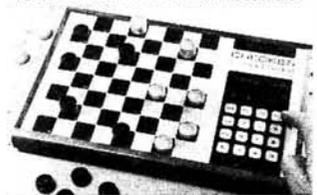PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.
 Callers welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm Mon-Sat 10am-1pm Wed
 To order by telephone please quote your name, address and Access/Barclaycard number
 Postage and Packing FREE.

AJD DIRECT SUPPLIES LIMITED, Dept. PW1 102 Bellegrave Road, Welling Kent DA16 3DD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)

INDEX TO ADVERTISERS

A. H. Supplies	9	M.H.E.L. Electronics	92
A. J. D. Electronics	95	Maclin-Zand	10
Amateur Radio Exchange	70	Magnum Audio	88
Ambit International	81	Manor Supplies	8
Amcom Services	70	Micron	29
Antex	Cover III	Microwave Modules	67
Audio Amateur	86	Maplin Electronic Supplies	Cover IV
Bamber B.	2	Marshall A (London) Limited	4
Barrie Electronics	16	Metac Limited	Cover II
Bearman, Phillip	90	Monolith Electronics Limited	86
Bi-Pak Limited	18, 19	Noble Electronics	84
Birkett J.	80	Osmabet	10
Blore Barton Ltd.	90	Park Electronics	80
Boss Industrial Mouldings Ltd.	85	Partridge Electronics	12
Bowes C.	9	P.C. Radio (Colomor)	88
British National Radio & Electronics School	11, 93	Progressive Radio	14
Bredhurst	44	Radio Book Service	92
Brooks B.	80	Radio Component Specialists	86
Burneze	92	Radio Exchange	7
Cambridge Kits	93	Radio & T.V. Components Ltd.	3
Catronics	14	Rolls Royce	91
Chordgate Ltd.	12	R.S.C. (Realistic Sound Centres Limited)	17
Chromasonics Electronics	13	R.S.T. Valve Mail Order Co.	83
Contour Electronics	80	Sandwell Plant Ltd.	92
Cooper A. S.	82	Scientific Wire Co., The	92
Cox Radio (Sussex) Limited	90	Sedgetor Ltd.	8
Crescent Radio Ltd.	82	S.L.M. Models	30
Crimson Elektrik	14	Smallcraft, V. & F.	29
C. & R. Supply Co.	90	Safgan Electronics	2
C.W.A.S. Alarm	92	Solid State Security	93
Dreweatt, Watson & Barton	90	Sonic Discount	10
Electronic Design Associates	2	Sonic Sound Audio (Eddystone)	8
Electronic Mail Order Limited	92	South Midlands Communications Limited	43
Electrovalue	82	Spectrum Communications	92
Electrovance	88	Squires, Roger	67
Fane Acoustics	13	Swanley Electronics	8
Fidelity Fastenings	9	Tandy Corporation Limited	15
Flairline	95	Technocentre Ltd.	14
Fleet Control Systems	30	Technomat	94
Galaxy Models	29	Tempus	87
Golledge Electronics, P. R.	90	Thanet Electronics	44
G. T. Information Services	92	T.M.P. Electronics	84
G2 DYM Aerials	92	T.O.P. Range	6
H.A.C. Shortwave	10	T. T. Electronics	4
Harrison Bros.	92	TUAC	16
Harversons Surplus Co.	84	Van Karen Publishing	90
Home Radio	96	Waters & Stanton Electronics	69
H.T.E. Electronics	29	Watford Electronics	5
Illiffe Promotions	84	Western Electronics	70
I.L.P. Electronics	78, 79	Williamson Amplification	93
Intertext I.C.S.	6, 92	Wilmslow Audio	96
Leeds Amateur Radio	44	World Radio T.V. Handbook	89
Lowe Electronics	69	Z & I Aero Services	96

A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

1B3GT 0.86	6AX5GT 1.49	6DT6 0.92	12AV6 0.98	ECF802 1.09	EY88 0.63	PCL84 0.86	PY83 0.81	UCC85 0.69
1R5 0.57	6BA6 0.52	6DT8 0.92	12AV7 1.16	ECH42 1.27	EY500A 1.73	PCL86 0.98	PY88 0.86	UCF80 0.86
1X2B 1.38	6BE6 0.55	6DW4 1.03	12AX7 0.63	ECH81 0.63	EZ80 0.57	PCL805 0.92	PY500A 0.92	UCH42 1.15
304 0.75	6BF5 0.98	6ES5 1.15	12AY7 0.98	ECH200 0.92	EZ81 0.57	PDS10 0.57	PY800 0.81	UCH81 0.75
5AT8 0.92	6BF6 0.85	6EV5 1.73	12BA6 0.75	ECL80 0.69	GY501 1.03	PL36 1.27	PY801 0.81	UCL81 0.81
5T4 0.86	6BG6G 1.49	6EW6 0.92	12BF6 0.77	ECL81 0.86	GZ30 0.75	PL81 0.92	U25 1.15	UCL82 0.86
5U4G 0.69	6BH6 0.98	6GH8A 0.92	12BH7A 0.86	ECL82 0.69	GZ32 0.75	PL82 0.63	U26 1.15	UCL83 0.92
5U8 0.86	6BJ6 1.38	6GK5 0.81	12BL6 0.81	ECL83 1.33	GZ33 4.38	PL83 0.57	UJABC80 0.66	UF41 1.15
5V4G 0.69	6BJ7 0.75	6GK6 1.03	12B06 0.81	ECL84 0.81	GZ34 2.88	PL84 0.86	UJAF41 0.92	UF80 0.57
5X4G 0.92	6BK4B 1.61	6J4 1.38	12BY7A 0.92	ECL85 0.75	OA2 0.75	PL504 0.75	UBC41 0.81	UF85 0.57
5X8 1.03	6BN4A 1.03	6J5GT 0.92	12C06 0.92	ECL86 0.98	OA3 0.86	PL508 0.86	UBC81 0.66	UL84 0.98
5Y3GT 0.75	6BN6 0.92	6J6 0.63	12C06 0.86	EF80 0.46	OB2 0.86	PL509/519 2.87	UBF80 0.69	UM80 0.69
5Z4GT 0.75	6BQ7A 0.81	6K5GT 0.86	19B6G6 0.57	EF85 0.55	OB3 0.81	PL802 3.22	UBF89 0.69	UM81 0.86
6AB7 0.69	6BR6A 1.38	6K6GT 0.98	30C18 2.25	EF86 0.69	OC2 1.61	PY81 0.81	UBL21 1.03	UM84 0.52
6AC7 0.92	6BS7 2.85	6LGGT 1.27	30FL2 1.20	EF92 1.16	OC3 0.98	PY82 0.63	UCC84 0.86	UY85 0.69
6AD8 0.69	6BU8 0.98	6N7GT 0.98	30FL14 2.00	EF97 0.81	OD3 0.86			
6AF4A 0.92	6BW7 1.15	6O7 1.03	35A3 2.81	EF98 1.03	PABC80 0.52			
6AG5 0.75	6BZ6 0.75	6SA7 0.92	35B3 0.75	EF183 0.81	PC86 1.03			
6AG7 0.98	6BZ7 0.81	6SG7 0.92	35C5 0.98	EF184 0.81	PC88 1.03			
6AH6 1.09	6C4 0.63	6SK7 0.92	50C5 0.98	EF200 1.84	PC96 0.57			
6AJ5 0.75	6LSGT 0.69	6SL7GT 0.81	50EH5 0.98	EH90 0.69	PC97 1.09			
6AK5 0.63	6C6 0.57	6SN7GT 0.81	DAF96 0.69	EL33 2.87	PC900 1.15			
6AK6 0.86	6C8G 0.69	6SR7 0.92	DF96 0.69	EL36 1.73	PCC84 0.57			
6AK7 0.98	6C8E 0.63	6SR7 0.92	DK92 1.16	EL81 0.92	PCC85 0.69			
6AL5 0.46	6CG7 0.81	6v8GT 0.92	DL96 0.69	EL82 0.69	PCC88 0.75			
6AM6 1.38	6CG8A 0.86	6X4 0.81	ECC84 0.69	EL83 0.69	PCC89 0.86			
6AM8 0.81	6CA7 0.92	6X5GT 0.92	ECC85 0.55	EL84 0.75	PCC189 1.15			
6AN6 2.87	6CN7 1.38	6X8 0.92	ECC86 1.44	EL86 0.86	PCF80 0.98			
6AN8 0.98	6L09 0.86	7GS7 0.92	ECC88 0.86	EL95 0.81	PCF82 0.52			
6AD5 0.98	6CS7 0.98	12A6 0.69	ECC89 0.92	EL504 1.09	PCF84 0.75			
6AS6 1.15	6C05 1.15	12AL5 0.75	ECC189 0.92	EL509/519 2.85	PCF86 0.86			
6AS7G 1.38	6C06 1.15	12A05 0.69	ECF80 0.69	EM80 0.75	PCF86 1.38			
6AT6 0.86	6C04 4.05	12A05 0.69	ECF82 0.63	EM81 0.69	PCF801 1.27			
6AU6 0.57	6CX8 1.15	12AT6 0.69	ECF86 0.92	EM84 0.69	PCF802 0.75			
6AV6 0.86	6CY5 1.15	12AT7 0.57	ECF200 1.03	EM87 1.15	PCF806 1.15			
6AW8A 0.86	6CY7 1.15	12A06 0.75	ECF201 1.03	EY81 0.63	PCL81 0.75			
6AX4CT8 1.15	6D08 1.67	24L7 0.54	ECF801 1.09	EY87 0.57	PCL82 0.92			

OSCILLOSCOPE TUBES

current production. Made in USSR

One inch Tube Type 3L0 11. This tube is a good replacement for 1CP31. Tube characteristics are identical with those of 1CP31. As the connections are different the tube is supplied complete with base, connection diagram and technical data **£12.00** plus £1.80 VAT. **Three-inch tube Type 3BP1.** This well known tube used in "PURBECK" Oscilloscope can be supplied for **£7.50** plus £1.12 VAT. 14-pin base for the above **£0.80** plus £0.12 VAT.

Prices are inclusive of VAT (at current rates) except where shown separately. Postage and packing charges are **£0.15** per £ subject to a minimum of **£0.40**. Minimum order charge for Approved Credit customers **£20.00**. Minimum Transaction Charge for mail orders **£1.00**.



Wilmslow Audio

THE firm for speakers!

SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNON ● VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount Hi-Fi Etc. at 5 Swan Street

Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213



FIRST and STILL BEST!

We've been producing our Electronics Components Catalogue for over 20 years. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation *second to none* for our catalogue - and for the service that backs it up. Experience both for yourself. Just send £1.30 with the coupon and a catalogue will come by return of post.

TREAT YOURSELF FOR XMAS!

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4-size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD., Dept. PW., 234-240 London Road, Mitcham, Surrey CR4 3HD Phone 01-648 8422.

POST THIS COUPON with cheque or P.O. for £1.30

Please write your Name and Address in block capitals

NAME _____

ADDRESS _____



HOME RADIO (Components) LTD Dept PW 234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No. 912966 London



Micro-precision soldering

ANTEX TCSU1 with CTC

... its the perfect kit

Model TCSU1

Micro-Soldering Station

Model CTC - 24volts Priced at **£9.75** (1 87)



Model CTC - 24volts Priced at **£9.75** (1 87)



Accurate pin point temperature control between 65° and 400°C. Heating element and sensor built in tip of the iron for fast response. Interchangeable slide-on bits from 4.7mm (3/16") down to 0.5mm. Zero voltage switching, no spikes. No magnetic field, no leakage. Supplied with miniature CTC (35-40 watt) iron or XTC (50 watt). TCSU1 soldering station with XTC or CTC iron **£36** (6.44). Nett to industry.

Model CX 17watts - 230 volts



A miniature iron with the element enclosed first in a ceramic shaft, then in stainless steel. Virtually leak-free. Only 7 1/2" long. Fitted with a 3/32" bit **£4.20** (98). Range of 5 other bits available from 1/8" down to 3/64". Also available for 24 volts.



Spare element Model CX230E

Model X25 25 watts - 230 volts



A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at **£4.20** (98). Range of 4 other bits available. Also available in 24 volts.



Spare element Model X25 24V E

Model SK3 Kit

Model SK4 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at **£5.70** (1.49). It makes an excellent present for the radio amateur or hobbyist.



With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at **£5.70** (1.49).


Model SK1

Model MLX 12 volts

ST3 Stand.



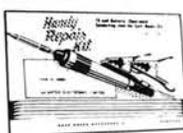This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet. How to Solder. Priced at **£5.95** (1 53).



The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price **£4.55** (1 14).



A strong chromium plated steel spring screwed into a plastic base of high grade insulating material provides a safe and handy receptacle for all ANTEX models soldering irons. Priced at **£1.50** (57).

V A T + P & P as shown in brackets ()



Stocked by many wholesalers and retailers or direct from us if you are desperate

Please send me the Antex colour brochure I enclose cheque/P.O./Giro No 258 1000

Please send the following

Name

Address

Antex Ltd., Freepost, Plymouth PL1 1BR Tel. 0752 67377

PW18D

MAPLIN



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.




Our catalogue even includes some popular car accessories at marvellous prices.




A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



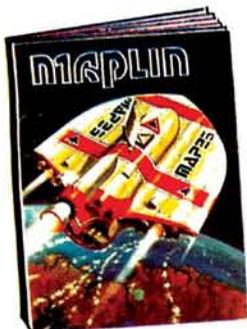These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.



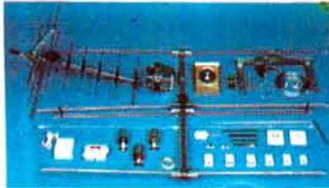Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £750. Full specification in our catalogue.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £18.38 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).

MAPLIN

ELECTRONIC SUPPLIES LTD

www.americanradiohistory.com


Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p & p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.07.

NAME _____


ADDRESS _____

P. W. 180

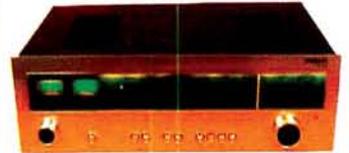


A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.

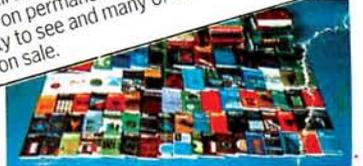Maplin will be there in force with all our projects on permanent demonstration. There will be plenty to see and many of our interesting lines will be on sale.



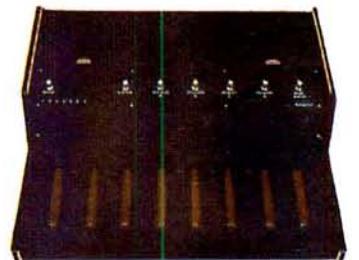A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road, Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554000.