

APRIL 1984 90p

Australia \$1.50
New Zealand \$1.75
Malaysia \$4.95

Practical Wireless


THE RADIO MAGAZINE

Another 8-Page Pull-Out of

PW Valve & Semiconductor Codes RADIO DATA

Ga As-f.e.t. Pre-amp for 430MHz

Upgrading the Realistic DX-160

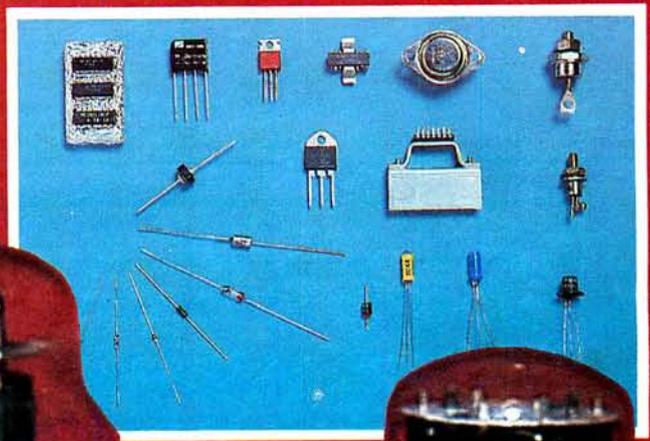



REG. WARD & CO. LTD.



REG G2BSW

1 WESTERN PARADE, WEST STREET,
AXMINSTER, DEVON, EX13 5NY. (Tel: 0297-34918)

RODNEY G6LJ



THE SOUTH-WEST'S LARGEST AMATEUR RADIO STOCKIST



YAESU		£ c&p	TRIO		£ c&p	LINEAR AMPS		£ c&p
FT1	HF Transceiver	P.O.A. (-)	TS930S	9 Band TX General Cov RX	1150.00 (-)	TOKYO HY POWER		
FT980	HF Transceiver	1265.00 (-)	TS830S	160-10m Transceiver 9 Bands	731.00 (-)	HL 32V	2m 30W (1-5W drive)	53.50 (1.50)
SP980	Speaker	58.65 (2.00)	AT230	All Band ATU/Power Meter	139.00 (2.00)	HL 82V	2m inc preamp (2-12W in 35-85 + out)	144.50 (2.00)
FT102	HF Transceiver	685.00 (-)	SP230	External Speaker Unit	42.09 (1.50)	HL 160V	2m inc preamp (1-10W in 160W + out)	242.40 (2.00)
FC102	Tuner	179.00 (2.00)	TS530S	160m-10m Transceiver	638.00 (-)	HL 45U	70cm inc preamp (2-15W in 10-45W out)	119.75 (2.00)
FV102DM	VFO	230.00 (2.00)	TS430S	160m-10m Transceiver	P.O.A. (-)	MICROWAVE MODULES		
SP102	Speaker	52.50 (2.00)	PS430	Matching Power Supply	115.00 (3.00)	MML144/30-LS	inc preamp (1/3 w i/p)	69.95 (2.00)
AM/FM	Unit	46.75 (1.00)	SP430	Matching Speaker	29.90 (1.50)	MML144/50-S	inc preamp, switchable	92.00 (2.00)
FT77	Mobile HF Transceiver	459.00 (-)	MB430	Mobile Mounting Bracket	11.50 (1.50)	ML144/100-S	inc preamp (10w i/p)	149.95 (2.50)
FP700	PSU	125.00 (5.00)	FM430	FM Board for TS430	35.19 (1.00)	MML144/100-HS	inc preamp (25w i/p)	149.95 (2.50)
FC700	Tuner	98.90 (2.00)	TS130S	8 Band 200W Pep Transceiver	555.45 (-)	MML144/100-LS	inc preamp (1/3w i/p)	169.95 (2.50)
FT77s	10w. version	425.00 (-)	TS130V	8 Band 20W Pep Transceiver	456.00 (-)	MML432/30L	inc preamp (1/3w i/p)	129.95 (2.00)
FMU77	FM Board for FT77	27.20 (1.00)	SP120	Base Station External Speaker	27.14 (1.50)	MML432/50	inc preamp (10w i/p)	129.95 (2.00)
FT757	HF Transceiver	685.00 (-)	AT130	100W Antenna Tuner	95.45 (1.50)	MML432/100	linear (10w i/p)	245.00 (2.50)
FT480	2m M/Mode Transceiver	399.00 (-)	MC50	Dual Impedance Desk Microphone	31.97 (1.50)	B.N.O.S.		
FL2050	Linear Amplifier	115.00 (2.00)	MC35S	Fist Microphone 50K ohm IMP	14.95 (0.75)	LPM 144/3-100	(3 watt input) inc preamp	172.50 (2.00)
FT290	2m M/Mode Port/Transceiver	269.00 (-)	MC30S	Fist Microphone 500 ohm IMP	14.95 (0.75)	LPM 144/10-100	(10 watt input) inc preamp	149.50 (2.00)
FT290	With Mutek front end fitted	299.00 (-)	LF30A	HF Low Pass Filter 1kW	21.85 (1.00)	LPM 144/25-160	(25 watt input) inc preamp	189.50 (2.00)
FL2010	Linear Amplifier	63.25 (1.00)	TR9130	2M Multimode	442.52 (-)	LPM 144/10-180	(10 watt input) inc preamp	212.50 (2.50)
FT790	70cm M/Mode Port/Transceiver	299.00 (-)	TW4000A	2M/70cm mobile	469.00 (-)	TONO		
FL7010	Linear Amplifier	91.00 (1.00)	TM201A	2M 25W mobile	269.00 (-)	MR 100	2m (10w in 90w out) inc preamp	129.00 (2.00)
MMB11	Mobile Bracket	26.55 (1.00)	TR3500	70cm Handheld	256.45 (-)	MR 150	2m (10w in 120w out) inc preamp	169.00 (2.00)
NC11	Charger	9.95 (0.75)	TR2500	2M FM Synthesised Handheld	237.82 (-)	SWR/PWR METERS		
CS1	Carrying Case	4.20 (0.75)	ST2	Base Stand	53.13 (1.50)	HANSEN		
YHA15	2m Helical	5.35 (0.75)	SC4	Soft Case	14.03 (0.50)	FS200	1.8-150MHz 20/200 Pep	55.95 (1.00)
YHA44D	70cm λ wave	9.00 (0.75)	SMC25	Speaker Mike	16.56 (1.00)	FS210	1.8-150MHz 20/200 Auto SWR	59.80 (1.00)
YM49	Speaker Mike	18.40 (1.00)	PB25	Spare Battery Pack	25.53 (1.00)	FS5E	3.5-150MHz 20/200/1000W HF	41.00 (1.00)
FT230	2m 25w FM	259.00 (-)	MS1	Mobile Stand	32.89 (1.00)	FS500H	1.8-80MHz 20/200/2000W Pep	77.80 (1.00)
FT730	70cm 10w. FM	259.00 (-)	R600	Gen. Cov. Receiver	263.12 (-)	FS7	145 & 432MHz 5/20/200	44.85 (1.00)
MMB15	Mobile Bracket	13.95 (1.00)	R2000	Synthesiser 200KHz-30MHz Receiver	421.36 (-)	FS710H	1.8-60MHz 15/150/1500W Pep	97.75 (1.00)
FT208	2m H/Held	199.00 (-)	HC10	Digital Station World Time Clock	69.46 (1.50)	FS711U	430-440MHz 5/200W Head	41.00 (1.00)
FT708	70cm H/Held	209.00 (-)	HS5	Deluxe Headphones	23.65 (1.00)	FS711H	2-30MHz 20/200 W Head	41.00 (1.00)
MMB10	Mobile Bracket	8.05 (0.75)	HS4	Economy Headphones	11.27 (1.00)	WELZ		
NC9C	Charger	8.80 (0.75)	SP40	Mobile External Speaker	14.49 (1.00)	SP15	1.8-160MHz PWR/SWR	39.00 (1.00)
NC8	Base/Station Charger	54.05 (2.50)	DATONG PRODUCTS			SP45	130-470MHz PWR/SWR	55.00 (1.00)
PA3	Car Adaptor/Charger	15.35 (0.75)	PC1	Gen. Cov. Con.	137.40 (1.00)	SP10X	1.8-150MHz PWR/SWR	26.50 (1.00)
FNB2	Spare Battery Pack	21.45 (0.75)	VLF	Very low frequency conv.	29.90 (1.00)	SP200	1.8-160MHz PWR/SWR	75.00 (1.00)
YM24A	Speaker Mike	21.50 (1.00)	FL2	Multi-mode audio filter	89.70 (1.00)	SP250	1.8-60MHz PWR/SWR	55.00 (1.00)
FT726R	2m Base Station	739.00 (-)	FL3	Audio filter for receivers	129.00 (1.00)	SP300	1.8-500MHz PWR/SWR	106.00 (1.00)
430/726	70cm Module for above	250.00 (2.50)	ASP/B	r.f. speech clipper for Trio	82.80 (1.00)	SP350	1.8-500MHz PWR/SWR	65.00 (1.00)
FRG7700	HF Receiver 15-30MHz	369.00 (-)	ASP/A	As above with 8 pin conn	89.70 (1.00)	SP400	130-500MHz PWR/SWR	75.00 (1.00)
FRG7700M	As above with memory	435.00 (-)	ASP	Manual RF speech clipper	56.35 (1.00)	SP600	1.8-500MHz PWR/SWR	106.00 (1.00)
FRT7700	A.T.U. for above	46.00 (1.00)	D75	Morse Tutor	56.35 (1.00)	TOYO		
MH18B	Hand 600 8pin mic	14.95 (1.00)	D70	Keyboard Morse sender	137.40 (1.00)	T430	144/432 120 W	39.49 (1.00)
MD18B	Desk 600 8pin mic	53.60 (1.00)	MK	RF switched pre-amp	33.90 (1.00)	T435	144/432 200 W	43.50 (1.00)
YH77	Lightweight phones	11.75 (0.75)	RFA	Active dipole with mains p.s.u.	51.75 (2.00)	YAESU		
YH55	Padded phones	11.75 (0.75)	AD270-MPU	Active dipole with mains p.s.u.	69.00 (2.00)	YS200	1.8 60MHz	52.90 (1.00)
YH1	L/waight Mobile H/set-Boom mic	14.95 (0.75)	AD370-MPU	Mains power unit	6.90 (1.00)	YS2000	1.8 60MHz	69.79 (1.00)
SB1	PTT Switch Box 208/708	16.25 (0.75)	MPU	2m converter	39.67 (1.00)	POWER SUPPLIES		
SB2	PTT Switch Box 290/790	13.80 (0.75)	DC144/28	Tone squelch unit	46.00 (1.00)	DRAE		
QTR24D	World Time Clock	34.50 (0.75)	PTS1	Automatic notch filter	67.85 (1.00)	4 amp	30.75 (2.00)	BNOS
FF501DX	Low Pass Filter	27.60 (0.75)	ANF	Auto Woodpecker blanker	86.25 (1.00)	6 amp	49.00 (2.50)	12 amp
YF150	Wattmeter/Dummy Load 150w	98.00 (1.00)	SRB2			24 amp	74.00 (3.00)	24 amp
							105.00 (4.00)	40 amp

ICOM PRODUCTS

IC751	HF Transceiver	1049.00 (-)
IC745	HF Transceiver	839.00 (-)
IC730	Mobile HF Transceiver	659.00 (-)
PS15	P.S. Unit	119.00 (4.00)
PS30	Systems p.s.u. 25A	229.00 (-)
SM6	Base microphone for 751/745	34.50 (1.00)
IC290H	2m 25w M/Mode	469.00 (-)
IC271E	2m 25w M/Mode Base Stn.	629.00 (-)
IC271H	100W version of above	P.O.A. (-)
IC25H	2m 45w FM	359.00 (-)
IC27E	25W FM mobile	299.00 (-)
IC45E	70c 10w FM	329.00 (-)
ICBU1	B/U Supply for 25/45/290	24.50 (1.00)
ICR70	General Coverage Receiver	549.00 (-)
ICR71	General Coverage Receiver	P.O.A. (-)
IC02E	General Coverage Receiver	P.O.A. (-)
IC2E	2m H/Held	169.00 (-)
ML1	2m 10w Linear	69.00 (2.00)
IC4E	70cm H/Held	219.00 (-)
BC30	Base Charger	56.35 (-)
HM9	Speaker mic	16.50 (0.75)
IC3	Carry Base	5.00 (0.75)
ICBP3	Std Battery Pack	25.00 (0.75)
BP5	High Power Battery Pack	48.00 (0.75)
CP1	Car Charging Lead	4.95 (0.75)
DC1	12v Adaptor	12.50 (0.75)

MUTEK PRODUCTS

SLNA 50	50MHz Switched preamp	37.10 (2.00)
SLNA 144s	144MHz Low noise switched preamp	37.10 (2.00)
SLAN 145sb	Preamp intended for 290	27.40 (1.20)
TLNA 432s	70cm Switched preamp	74.90 (1.20)
RPCB 144ub	Front end FT221/225	71.00 (1.20)
RPCB 251ub	Front end IC251/211	76.90 (1.20)
BBA 500u	20-500MHz Preamp	29.00 (1.20)
GFBA 144e	2m Mast head preamp	129.90 (2.50)
SBLA 144e	2m Mast head preamp	79.90 (2.50)
RPCB 271ub	Front end for IC271	79.90 (1.20)

HQ1 MINI BEAM
10 - 15 - 20
ONLY £169.00 (4.00)

**AERIALS BY:- JAYBEAM -
HYGAIN - G. WHIP - TET -
MINIBEAM - USUALLY
IN STOCK**

LAR products also in stock

OPEN MON-FRIDAY 9:00-5:30. SATURDAY 9:00-5:00. WED 9:00-1:00 (closed for lunch 1.00-2.00)

Instant credit also available



NEW LARGER SHOWROOM NOW OPEN

STOCK ITEMS NORMALLY DESPATCHED WITHIN 48 HOURS

Mail/Telephone orders by Cheque or Credit Card. Cheques cleared before goods despatched.

Delivery prices shown in brackets



Practical Wireless

FOR THE **Radio** ENTHUSIAST ...

APRIL 1984 VOL. 60 NO. 4 ISSUE 925

Contents

Staff

- 20** **A GaAs-f.e.t. Pre-amplifier for 430MHz**
Sam Jewell G4DDK
- 28** **Midlands VHF Convention Report**
- 29** **Kindly Note**
PW "Dart"—November 1983
- 30** **Upgrading the Realistic DX-160**
Charles Molloy
- 34** **Top Band Direction Finding—2**
Chris Plummer G8APB
- 39** **PW Radio Data—2 "Valve and Semiconductor Codes + Trademarks"**
Special Pull-out Feature
- 51** **PW Review**
ICOM IC-R70 Communications Receiver
- 54** **Building an HF Linear Amplifier and ATU—1**
I. Buffham G3TMA
- 60** **Value for Money?**
G8YDK

EDITORIAL OFFICES

Practical Wireless
Westover House
West Quay Road
Poole, Dorset BH15 1JG
☎ Poole 671191

Geoff Arnold T.Eng(CEI) G3GSR
Editor

Dick Ganderton C.Eng., MIERE, G8VFN
Assistant Editor

Steve Hunt
Art Editor

John Fell G8MCP
Technical Editor

Alan Martin G8ZPW
News & Production Editor

Elaine Howard G4LFM
Technical Sub-Editor

Rob Mackie
Technical Artist

Keith Woodruff
Assistant Art Editor

Sylvia Barrett
Secretarial

ADVERTISEMENT OFFICES

Practical Wireless
King's Reach Tower
Stamford Street
London SE1 9LS
Telex: 915748 MAGDIV-G

Dennis Brough
Advertisement Manager
☎ 01-261 6636
☎ 01-261 6872

Roger Hall G4TNT (Sam)
Ad. Sales Executive
☎ 01-261 6807

Claire Gerrish
Secretary
☎ 01-261 6636

Barbara Blake
Classified Supervisor
☎ 01-261 5897

Ian Sweeney
Make-up & Copy
☎ 01-261 6570

Regulars

- | | | |
|-----------------|-----------------|--------------|
| 87 Advert Index | 61 Next Month | 17 Services |
| 38 Benny | 64 On the Air | 27 Swap Spot |
| 17 Comment | 38, 59 Products | 62 Uncle Ed |
| 18 News | | |

COPYRIGHT © IPC Magazines Limited 1984 Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Practical Wireless, April 1984

LOWE SHOPS in matlock,

TELEPHONE 0629.2817 2430 4057 4995
Lowe Electronics in Matlock, located on the Chesterfield road out of Matlock, that is the A632 and open Tuesday to Friday from 9am to 5.30pm (closed for lunch 12.30 to 1.30) and Saturday, open all day from 9am to 5pm. A visit to Matlock can be an outing for the family, the local scenery, the Heights of Abraham, Lovers Walk etc. Ample free parking in our car park and when you have browsed then lunch in one of the towns pleasant restaurants. Amateur Radio with the family in mind.

in glasgow,

TELEPHONE 041.945.2626
Lowe Electronics in Glasgow, located at 4/5 Queen Margarets Road, which you will find off Queen Margarets Drive (take Great Western road out of the City and turn right at the Botanical Gardens traffic lights). A quiet sedate part of the city, easy street parking and a warm welcome from Sim, our shop manager. Open all day from Tuesday to Saturday, 9 am till 5.30pm during the week and 9am till 5pm on Saturday. Whilst in the area the Botanical Gardens are well worth a visit. The Glasgow Shop has a full display of our range of amateur radio products and a stock room to meet your every demand. For your Amateur Radio needs visit Lowe Electronics in Glasgow.

in darlington,

TELEPHONE 0325.486121
Lowe Electronics in the North East of England, set in the delightful market town of Darlington, the shop displays the full range of amateur products sold by the company. Our address in the town is 56 North Road, that is the A167 Durham road out of Darlington. Open Tuesday to Friday from 9am till 5.30pm, Saturday from 9am till 5pm (closed for lunch 12.30 to 1.30). A huge free car park across the road, a large supermarket, bistro restaurant and banking facilities combine to make a visit to this delightful market town a pleasure for the whole family.

in london,

TELEPHONE 01.837.6702
Lowe Electronics in London, our shop in the Capital City, easily found on the lower sales floor of the Hepworths' shop on Pentonville Road, within 3 minutes walk of Kings Cross railway station. Open all day Monday to Saturday, six days a week, from 9.30am to 5.30pm during the week and from 9.30am to 5pm on Saturday, a warm and courteous welcome, together with sound advice awaits those who enter. The entire range of amateur products is on display, backed by a considerable amount of stock. When in the City, visit Lowe Electronics.

We cannot seem to keep the TR9130 in an "in stock" situation. No sooner has a shipment arrived than we are "out of stock". I must say that even I am surprised by its popularity. Based on the renowned TR9000, the TR9130 has additional features that make it the most popular multimode on today's market. We are still getting requests for second-hand TR9000's and even they are a rarity on our second-hand shelf. Having a clear green readout, reverse repeater, the



TR9130

ability to tune whilst transmitting, 25 watts output, 6 memories and of course memory scan: TRIO's two metre multimode, the TR9130.

TR9130 £442.52 inc. VAT. carriage £6.00

There are two schools of thought regarding two metre mobile FM equipment. One group are of the opinion that the simpler the

rig the better and refer to the TRIO TR7500 as the ultimate mobile transceiver ever made. There are others who require their mobile rig to have memory channels and all associated facilities in order to gain operational flexibility. TRIO cater for both.

The TM201A and the TM401A are simple rigs, designed to fit into the smallest of today's cars and provide the simple functions that make mobile operation a pleasure. Repeater shift and lockable reverse repeater are included as well as superb receive performance. 25 watts from the 2 metre TM201A and 12.5 watts from its 70 centimetre cousin, the TM401A, ensures a strong transmitted signal. A separate 77 mm (3 inch) speakers in a solid enclosure gives high quality receive audio even whilst mobile.



TM201A

TM201A £269.00 inc VAT. carriage £6.00
TM401A £299.00 inc VAT. carriage £6.00

A remote controller with a green backlit LCD frequency readout is also available as an optional accessory. The FC10 simply plugs into the side of the transceiver and comes complete with mounting bracket and velcro pads to ease fixing without drilling holes in the car's dashboard.



TW4000A

FC10 £41.20 inc VAT. carriage £6.00

For a mobile transceiver having more operating features the TR7930 is the model to choose. The TR7930 is TRIO's logical progression from the very popular and

reliable TR7800. The design of the TR7930 takes into account the minor and justifiable criticisms levelled against the TR7800. You will now find the frequency readout is a green backlit liquid crystal display that can be read in the brightest of sunlight. The memory allocation has been increased to a total of 21 channels and the rig can be instructed to hold on the received signal for either a timed period or until the signal disappears. Programmable band scan is also available between user defined limits. To make mobile operation safer the transceiver is pre-programmed so that if you select for example, 145.450 then the rig will adopt the simplex mode, if you select 145.650 then, automatically, you will get repeater mode. Of course TRIO have made it easy to over-ride this feature as you would naturally expect. I can say no more about the TR7930, a comprehensive rig for the mobile enthusiast.

TR7930 £312.00 inc VAT. carriage £6.00

To improve mobile operation there is the TRIO MC55 boom microphone. Not just an electret condenser microphone but having a transmission timer, up/down frequency shift switch, adjustable microphone gain and fitted with either a 6 or 8 pin microphone plug. To monitor the swr/output power of your mobile installation TRIO have produced the SWR100A/B. (model A: 1.8 to 150 MHz and model B: 140 to 450 MHz) Compact and easily fixed to your dashboard, be the first to know something is wrong with your mobile station.

MC55 £38.64 inc VAT. carriage £2.00
SWR100A/B £37.26 inc VAT. carriage £2.50

LOWE IN LONDON, Open monday to saturday, six days a week
lower sales floor, Hepworths, Pentonville Rd, London. telephone 01.837.6702
LOWE IN GLASGOW, Open tuesday to saturday
4,5 Queen Margarets Rd, Glasgow. telephone 041.945.2626



We don't sell our sets until we know them inside out

The new IC-02E Push-button Perfection



ICOM introduces the new top-of-the-line IC-02E to compliment its existing line of popular handheld transceivers and accessories. The new direct entry microprocessor controlled IC-02E is a 2 meter handheld jam packed with excellent features.

Some of these features include: scanning, 10 memories, duplex offset storage in memory & odd offsets also stored in memory. Internal Lithium battery backup and repeater tone are of course included.

Keyboard entry is made through the 16 button pad allowing easy access to frequencies, duplex, memories, memory scan and priority. The IC-02E has an easy to read custom LCD readout indicating frequency, memory channel, signal strength, transmitter output and scanning functions.

A battery lock, frequency lock and lamp on/off switch are also featured, as is an aluminium case-back, providing superior heat sinking.

A variety of batteries will be available for the IC-02E, including new long-life 8.4 volt and 13.2 volt packs. Top panel connector for 13.8 volts which will power transceiver operation.

The IC-02E continues to be available, and its complete range of accessories work with the new IC-02E.


The IC-02E comes with the BP3 Nicad battery pack, BC25E wall charger, flexible antenna, wrist strap and belt clip as standard equipment. A truly excellent product destined to a great future.

We do not sell any sets until we know them inside out. A bold claim, but true. Our engineers have been trained by ICOM in Japan, and can guarantee the best after-sales maintenance service available.

As well as the 02E, 751, 745, 271, 471, R70, 290D, 490E, 25H, 45E, 2KL, AT100, AT500, 120, 2E, 4E in the ICOM range we also stock such famous names as Tono, Telereader, Cue Dee, Versatower, Yaesu, Jaybeam, Datong, Welz, G-Whip, Western TAL, Bearcat and RSGB Publications. Thanet Electronics can offer you the most comprehensive and thorough service.

Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM

...any of ...we know ...side-out.

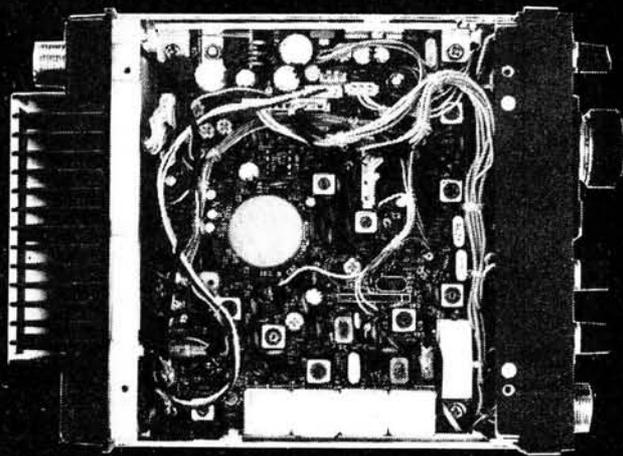

IC-745, Latest HF Transceiver

Hearing is believing, the IC745, a new all band HF transceiver with SSB, AM (receive only), CW, RTTY, FM option, and a 100KHz-30MHz general coverage receiver.

The IC745 has a terrific combination of features found on no other transceiver, at such a low price. The IC745 is the only transceiver today that has so many standard features, options and accessories.

The IC745 is another superlative set in the ICOM range, see it in our retail shop at 95 Mortimer Street Herne Bay Kent, or contact our Reculver Road address for more information. Your own local ICOM dealer will be able to help you too.



IC-27E, Latest and smallest FM Mobile



And we thought that the IC25E was small! ICOM have now produced a new and even smaller 25W FM 2 meter mobile – the IC27E.

We have little information on the IC27E at the moment, but by the time you read this they should be available.

Briefly, the IC27E offers two VFO's, 9 memories, priority channel and scanning. The easy to read LCD displays frequency, memory channel, power, S-meter and functions. All this is packed into a case W140 x H38 x D177mm, and weighing only 1.2 Kgs.

The price has not yet been announced but give us a call for this and other information.

Interest-free credit available
Securitor or post despatch free,
same day if possible.

Our local RETAIL premises have now
moved to 95 Mortimer St. Herne Bay Kent.

Agent Please telephone first, anytime
between 0900 – 2200 hrs.
Gordon, G3LEO Tel: Knutsford (0565) 4040

Thalet Electronics
 143 Reculver Road, Herne Bay, Kent
 Tel: (02273) 63859 / 63850



AMATEUR ELECTRONICS UK

SERVING YOU SINCE 1962!



Your number one source for **YAESU MUSEN**

THE SYMBOL OF TECHNICAL EXCELLENCE

Mail Order - All stock items same day service

When you buy from Amateur Electronics UK you are dealing with the **FACTORY APPOINTED IMPORTER** with the largest stocks of equipment and spares in the country. Our delivery and after-sales-service is second to none and for your convenience we offer the following facilities ● On-the-spot credit sales (against recognised bank or credit cards) ● Interest free finance (50% deposit - balance over 12 months) ● Free Securicor delivery on all major items ● **FACTORY BACKED EQUIPMENT** ● Extensive showroom demonstration facilities ● Private large car park ● Your choice just has to be **YAESU** - write or phone for all the details.

Large stocks of: TET ANTENNAS • JAYBEAM • HI-MOUND • TOKYO HY-POWER • DATONG • MICROWAVE MODULES • BNOS • DAVTREND • WELTZ • MUTEK • RSGB PUBLICATIONS

FT-757GX The latest all-mode HF rig from YAESU

How do they do it? - To get so much in so small a package - Just look at the features.

- All-mode operation SSB, CW, AM and FM are included as standard features. ● Full CW break-in. ● Dual VFO plus eight memories. ● Programmable memory scanning.
- 600Hz CW filter fitted. ● Iambic keyer with dot-dash memory.
- IF shift and width filters. ● TX coverage 160 thru 10 metres.
- High performance general coverage RX 500KHz - 29.999MHz.

Optional P.S.U.'s FP-757 (plinth type) FP-700.



FT-77 HF transceiver




Not just a mobile rig - with matching PSU and ATU this makes a first class budget station. FT-77s - (10W version)

FT-102 HF transceiver



The superb 102 - Still the buy of a lifetime

FRG-7700 General coverage receiver

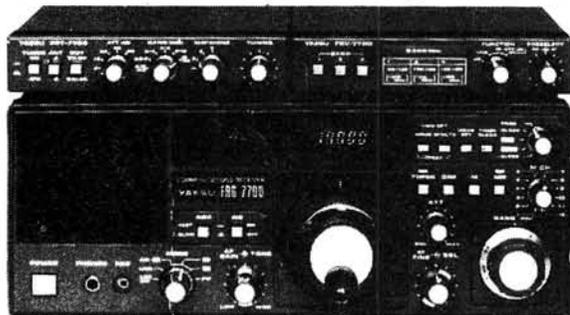

Attention FRG-7700 owners!

See us for your special requirements in converters and active antennas - complete range ex stock - Post free.

FT-980 All-mode HF transceiver



The ultimate HF rig - Superb all-mode operation plus full general coverage receiver. Rolls Royce performance

LATEST!

**COMING SOON - FT-203R
NEW COMPACT 2m FM HAND-HELD**



FT-480R 2 metre multi-mode



Now the finest value on the market back in town by popular demand!

FT-290R 2 metre multi-mode portable



10 memories,
2 VFO's, LCD display,
C size battery, easy car mounting tray,
FT-290R 0.5 low/2.5 high watts out

**FT-726R
VHF/UHF
multi-mode**

Fitted 2 metres with 70cm, 6 metres or HF options. Satellite unit available provides complete satellite operation with full Duplex.



FT-230R 2 metre 25 watt FM mobile



- Two independent VFO's ● 10 memories
- Priority function ● Memory and band scan
- 12.5/25KHz steps (25/100KHz FT-730R)
- Large LCD readout.

FT-208R 2 metre FM hand-held

The finest hand-held bar none

ACCESSORIES:

- NC-7 - Standard charger
- NC-8 - Standard/quick charger/DC Power supply
- NC-9C - Compact charger (220-234V) ● PA-3 - Car adapter
- YM-24A - Speaker/microphone
- FL-2010 - 10 watt power amplifier for FT-208R
- FL-7010 - 10 watt power amplifier for FT-708R



XIV Olympic Winter Games Sarajevo 1984



BRANCHES

For your convenience we now have fully stocked branches at the following locations where you will be assured of prompt and personal service.

NORTHERN

Amateur Electronics UK/
Holdings,
45 Johnston St., Blackburn.
Tel: 0254 59595
Contact Harry G3LLL
for all your requirements
and specialised advice.

Open: 9.15 am - 5.15 pm
closed Thurs.

SOUTH-WEST

Amateur Electronics UK/
Uppington,
12-14 Pennywell Rd.,
Bristol. Tel: 0272 557732
Call Peter or Bert G2BAR
for prompt and
friendly service.

Open: 9 am - 6 pm.
Sat: 9 am - 1 pm

YORKSHIRE

Amateur Electronics UK/
Hooker, 42 Nether Hall Rd.,
Doncaster.
Tel: 0302 25690
Alan G4OEM has a large
stock of our product range -
why not give him a ring and
save yourself some petrol?

Open: 9 am - 6 pm Mon. - Sat.

AGENTS

Wales & West - Ross Clare, GW3NWS (0633) 880 146
East Anglia - Amateur Electronics UK, East Anglia, Dr. T. Thirst (TIM) G4CTT Norwich (0603) 667 189
North Staffs - Bob Ainge W5MJQ (0538) 754553
Shropshire - Syd Poole G3IMP, Newport, SALOP (0952) 814275

For full details of these new and exciting models, send today for our latest SHORT FORM CATALOGUE. All you need do to obtain the latest information about these exciting developments from the World's No.1 manufacturer of amateur radio equipment is to send 36p in stamps and as an added bonus you will get our credit voucher value £3.60 - a 10 to 1 winner!

As factory appointed importers we offer you -
widest choice, largest stocks, quickest deal and
fast sure service right through -

**504-516 Alum Rock Road - Birmingham 8 Telephone: 021-327 1497 or 021-327 6313
Telex: 334312 PERLEC G Open: 9.30 to 5.30 Tues. to Sat. CLOSED all day Monday.**

OUR WORKSHOPS ARE EQUIPPED FOR 3GHZ

YASEU - TRIO/KENWOOD SPECIAL PURCHASE SALE

TRIO/KENWOOD - TR7950 (r.r.p. £375.00)	R.W.C. price - Phone
TRIO/KENWOOD - TR7850 (r.r.p. £279.00)	R.W.C. price - Phone
TRIO/KENWOOD - DFC230 (r.r.p. £159.00)	R.W.C. price - £59.95
TONO 100W Linear (inc pre-amp) 10W in (r.r.p. £145.95)	R.W.C. price - £99.50

YAESU QTR24D CLOCK £25.95
 YAESU FT290R (with mods) .Lowest price - Phone

YAESU YH77 Headphones (70 to clear) £9.95
 YAESU FRA7700 Active Antenna Only £35.00
 YAESU FRV7700 Convertors (A.B.C. & D) Phone for price and we will shock you.
 YAESU FC7000 a.t.u. (only 20 to clear) Phone
 YAESU FT102 Phone for Britain's best price - only 6 available.

PERSONALISED SERVICE

REVCO COMPUTER SCANNER
 70 Memories - 60 to 515 MHz (in 5 bands) AM-FM-AIRBAND
 SPECIAL DEALER PRICE £249.00.

ALWAYS IN STOCK

We also have in stock a massive once only supply of Yaesu Mics, Speakers, Speaker/Mics, Linears (25W-1.2kW assorted) P.M.R. (one line - 100 pieces) £59.95. Please pay us a visit and see how you are treated. We pride ourselves on our service and our after sales facilities. Some of these lines are also available at the C.Q. Centre in London.

LOMBARD TRICITY FINANCE
BIRMINGHAM SPECIALS

WE TRY HARDER!

We would like to thank all the customers who have shopped at the C.Q. Centres in Birmingham and London for their marvellous response in supporting the Birmingham Branch and we wish all old and new customers a belated and prosperous New Year.

CABLE
 We have in stock a full range of cables - RG58-H100-300Ω Ribbon-drawn Copper etc. etc.

HERE IN BIRMINGHAM WE SPECIALISE IN PMR SALES AND SERVICE. WE CAN ALSO OFFER A 24 HOUR CRYSTAL SERVICE AT £5.50 + p&p.

10 metre converted rig £47.50

G4HXZ & G6DSS
 10 MERTON PARK PARADE
 KINGSTON ROAD
 (JUNCTION MERTON HALL RD.)
 LONDON S.W.19,
 TEL: 01-543 5150/4212
 MON-FRI 9.30-6.00. SAT 9.30-4.30
 STOCK ITEMS NORMALLY DELIVERED WITHIN 7 DAYS

G4KZH & G6KZH
 584 HAGLEY ROAD WEST
 OLDBURY, BIRMINGHAM
 B68 0BS
 TEL: 021-421 8201/2
 CLOSED MONDAY
 TUES-SAT 9.30-4.00



THE WAY AHEAD

SLIMLINE MASTS or LATTICE TOWERS
FIXED TOWERS or MOBILE TRAILERS

PORTABLE MASTS or WINDOW MOUNTING
YOU NAME IT! WE PROBABLY MAKE IT!

SOME TYPICAL DESIGN FEATURES

- VERSATILE MOUNTING, POST, WALL OR TRAILER.
- UNIQUE 15FT SECTIONS FOR MINIMUM LOWERED HEIGHT AND EASY TRANSPORT.
- PURPOSE DESIGNED AND ENGINEERED TO B.S.I. STANDARDS: WIND LOADS TO CP3 CHAP. PT 2.
- ROBUSTLY CONSTRUCTED IN QUALITY STEEL (TO BS 1775, BS 980, BS4360).
- OPTIONAL HEAD UNITS (Extra)
- WELDED BY ELECTRONICALLY CONTROLLED M.I.G. FOR EXTRA STRENGTH TO BS 4872.
- MORE THAN 50 TYPES OF MAST OR TOWER FROM 30FT TO OVER 100FT.
- TELESCOPIC TILTOVER FOR EASY ACCESS.
- SAFETY LATCH TO RELIEVE CABLE.
- SIMPLE WINCH OPERATION (Single and Double).
- HOT DIP GALVANIZED FOR PROTECTION (BS 729).

A FEW POPULAR MODELS FROM OUR WIDE RANGE

SLIMLINE MASTS - SM30 Unobtrusive, Telescopic, Tiltable, up to 30ft. SM30WM (Wall Mount) £230.00. SM30PM (Post Mounting) £241.00. Optional Reducer Tube RT1 £12.50. Rotor Head RH1 £30.50. Ground Socket GS1 £23.50.

LATTICE TOWERS - TELESCOPIC - TILTOVER
 Series 1. 32ft. model. AT32PM for £323.00. AT32WM £312.00 Series 2. Heavy duty 44ft. model AT42PM £418.00. AT42WM £401.50. 56ft. model AT52PM £538.00. AT52WM £524.00. Head unit RH2 (ny.bmg.) £39.50.

Models include all winches, luffing gear, brackets etc.
 Prices may vary. Stock goods normally despatched in 7 days.

★ NEW ★ Altron AQ6-20 compact 2 el. beam, 4 bands 6, 10, 15, 20M.

Fully sealed coils price £114.50 plus £4 p+p U.K. mainland.

We design - we make - we supply direct. At manufacturers prices. You get best value and service. We offer no gimmicks. No free gifts. Just competitive prices, quality, reliability and knowhow.

Callers welcome. Samples on display. Opening hours: Mon-Fri. 9 am-5 pm.
 Sat. 9 am-12.45 pm.

Price includes VAT @ 15% and U.K. mainland carriage terms. C.W.O., Access or Visa, S.A.E. for details now.

ALL ALTRON PRODUCTS ARE EXCLUSIVELY MANUFACTURED IN THE U.K. BY

ALLWELD ENGINEERING
 UNIT 6, 232 SELSDON ROAD, SOUTH CROYDON, SURREY CR2 6PL.
 Telephone:
 01-680 2995 (24 hr) 01-681 6734



BI-PAK BARGAINS

MINIATURE TOOLS FOR HOBBYISTS

-  Miniature round nose side cutters - insulated handles 4 1/2 inch length. Order No: Y043.
-  Miniature long nose pliers - insulated handles 5 1/2 inch length. Order No: Y044.
-  Miniature bend nose pliers - insulated handles 5 1/2 inch length. Order No: Y045.
-  Miniature end nippers - insulated handles 4 1/2 inch length. Order No: Y046.

FLEKEY DRIVER

A flexible shaft screwdriver for those awkward to get at screws. Overall length 8 1/2 inch. Order No: FS-1 Flat blade 4mm FS-2 Cross point no. 1 £1.75 each.



GRIP-DRIVER

8 inch long screwdriver with spring loaded grip on end to hold screws in position while reaching into those difficult places. Order No: SD-1 Flat blade 4mm SD-2 Cross point no.0. £95p each.



Miniature snipe nose pliers with side cutter and serrated jaws - insulated handles 5 1/2 inch length. Order No: Y042.

ALL AT **1.25** each

VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/4 Watt Pre-Formed	£1.00
VP3	200	150 1/2 Watt Resistors 100 ohm-1M Mixed	£1.00
VP4	200	Assorted Capacitors All Types	£1.00
VP5	200	Ceramic Caps Miniature - Mixed	£1.00
VP6	100	Mixed Ceramic Disc. 1pf - 56pf	£1.00
VP7	100	Mixed Ceramic Disc. 68pf - 0.15pf	£1.00
VP8	100	Assorted Polyester/Polystyrene Caps	£1.00
VP9	60	C280 Type Caps Metal Foil Mixed	£1.00
VP10	100	Electrolytics - All Sorts	£1.00
VP11	60	Bead Type Polystyrene Min Caps	£1.00
VP12	50	Silver Mica Caps Ass. 5.6pf - 150pf	£1.00
VP13	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP14	50	High Voltage Disc. Ceramic 750v - 8Kv Mixed	£1.00
VP15	50	Wirewound Res. 9W (avg) Ass. 1 ohm - 12K	£1.00
VP16	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP17	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP18	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP19	20	Pcs. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1.00
VP20	20	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00
VP21	20	Assorted Slider Pots. Mixed Values	£1.00
VP22	10	Slider Pots. 40 mm 22K 5 x Log. 5 x Lin	£1.00
VP23	10	Slider Pots. 40 mm 47K 5 x Log. 5 x Lin	£1.00
VP24	20	Small 125° Red LED'S	£1.00
VP25	20	Large 2° Red LED'S	£1.00
VP26	10	Rectangular 2° Green LED'S	£1.00
VP27	30	Ass. Zener Diodes 250mW - 2W Mixed Vts. Coded	£1.00
VP28	10	Ass. 10W Zener Diodes Mixed Vts. Coded	£1.00
VP29	5	5 Amp SCR'S TO-66 50-400v Coded	£1.00
VP30	20	3 Amp SCR'S TO-66 Up To 400v Uncoded	£1.00
VP31	200	Sil. Diodes Switching Like IN4148 DO-35	£1.00
VP32	200	Sil. Diodes Gen. Purpose Like OA200/BAX13/16	£1.00
VP33	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP34	8	Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vts. Coded	£1.00
VP35	8	Black Instrument Type Knobs With Pointer 1/2 Std	£1.00
VP36	10	Black Heatsinks To Fit TO-3, TO-220 Ready Drilled	£1.00
VP37	4	Power-Fin Heatsinks 2 x TO-3 2 x TO-66 Size	£1.00


TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year! This collection of Components & Semiconductors for the

hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc., PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for just £6.50 ONLY at BI-PAK. Remember, stocks are limited so hurry! You can call us on 0920-3182/3412 and order with your Barclaycard or Access Card - 24hr Answerphone Service NOW. Order No. V.P. 85.

SILICON BRIDGE RECTIFIERS

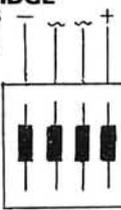Comprising 4 x 1 1/2 amp rectifiers mounted on PCB.



VRM - 150 volts
IFM - 1.5 Amps
Size: 1 inch square
10 off £1.00
50 off £4.50
100 off £7.50

Order No. As:4R1 BRect.

REGULATED VARIABLE Stabilised POWER SUPPLY

Variable from 2-30 volts and 0-2 Amps. Kit includes - 1 - VPS30 Module, 1 - 25 volt 2 amp transformer, 1 - 0.50v 2" Panel Meter, 1 - 0-2 amp 2" Panel Meter, 1 - 470 ohm wirewound potentiometer, 1 - 4K7 ohm wirewound potentiometer, Wiring Diagram included. Order No. VPS30 KIT £20.

MINIATURE FM TRANSMITTER

Freq: 95-106MHz. Range: 1 mile
Size: 45 x 20mm. Add: 9v batt. ONLY £5.50
Not licenced in U.K.
Ideal for: 007-MIS-FBI-CIA-KGB etc.

8 Bit MICROPROCESSOR

National INS8080AN 40 Pin DIL N Channel Silicon GATE MOS TECHNOLOGY As used in National's N8080 Micro Computer Family
Instruction Cycle Time 2 uS
Supplied with functional Block Diagram

BRAND NEW - NOT seconds or reclaims
100% perfect ORDER NO. SX8080
Normal Sell price £4.50 each
Our BI-PAK Special Price
SO HURRY - LIMITED STOCKS

40 Pin IC Socket to fit SX8080 Offer price
ORDER NO. 1609 30p

TRANSISTOR CLEARANCE

All Sorts Transistors. A mixed Bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes Instructions For Making Simple Transistor Tester. Super Value. Order No. VP60 £1.00

MULTITESTERS

1,000 opv including test leads & Battery
AC volts - 0-15-150-500-1,000
DC volts - 0-15-150-500-1,000
DC currents - 0-1ma-150ma
Resistance - 0-25 K ohms 100 K ohms
Dims - 90 x 61 x 30mm



0/No.1322.OUR PRICE £6.50 ONLY

5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm £1.75

5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm. £1.75

5T41 TOOL SET

5 precision instruments in hinged plastic case. Crosspoint (Philips) screwdrivers - H0 and H1 Hex key wrenches. - 1.5, 2 and 2.5mm £1.75

5T51 WRENCH SET

5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm £1.75

ELECTRONIC SIREN 12v DC

Red plastic case with adjustable fixing bracket. Emits high-pitched wailing note of varying pitch - 100 cycles per minute. Dims - 90mm (dia.) 60mm (depth). Power - 12v DC.



Our Price: £5.50

BRAND NEW LCD DISPLAY MULTITESTER

RE 188m
LCD TO MEGOHM INPUT IMPEDANCE
*3 1/2 digit *16 ranges plus hFE test facility for PNP and NPN transistors *Auto zero, auto polarity *Single-handed, pushbutton operation *Over range indication *12.5mm (1/2-inch) large LCD readout *Diode check *Fast circuit protection *Test leads, battery and instructions included.

Max indication 1999 or -1999
Polarity indication Negative only
Positive readings appear without a sign

Input Impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range -5°C to 50°C

Power Supply 1 x PP3 or equivalent 9V battery
Consumption 20mW
Size 155x88x31mm

RANGES £35.00
DC Voltage 0-200mV
0-2-20-200-1000V. Acc. 0.8% each
AC Voltage 0-200-1000V
Acc. 1.2% DC Current 0-200uA
0-2-20-200mA, 0-10A. Acc. 1.2%

Resistance 0-2-20-200K ohms
0-2 Megohms. Acc. 1%
BI-PAK VERY LOWEST PRICE

DIGITAL VOLT METER MODULE
3 x 7 segment displays Basic Circuit
0-2V = instructions provided to extend voltage & current ranges
Operating voltage 9/12v
Typ. Power Consumption 50mA
0/NO: SX99 Once only price £9.95

Leather Case for 188m £2.50 EACH

Our Price: £5.50

OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We have vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

SIREN ALARM MODULE

American Police type screamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. 5 watt, 12v max.

£3.85
Order No. BP124.



The Third and Fourth Hand . . .

. . . you always need but have never got until now. This helpful unit with Rod mounted horizontally on Heavy Base Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 1/2 diam magnifier giving 25x magnification. Helping hand unit available with or without magnifier. Our price with magnifier as illustrated ORDER NO. T402 £5.50. Without magnifier ORDER NO. T400 £4.75



MW398 NI-CAD BATTERY CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid Charge/Test switch. LED indicators at each of the five charging points.

Charges - Power -
PP3 (9V) 220-240V AC
U12 (1.5V penlite) Dims -
U11 (1.5V "C") 210 x 100 x 50mm
U12 (1.5V "D") £6.95



POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug Input - 240V AC 50HZ, Output - 3, 4, 5, 6, 7.5, 9 & 12V DC Rating - 300 ma MW88.

TRIACS - PLASTIC

4 AMP - 400v - T0202 - TAG 136G.
1 OFF 10 OFF 50 OFF 100 OFF
40p £3.75 £17.50 £30.00
8 AMP 400v - T0202 - TAG 425
60p £5.75 £27.50 £50.00

VOLTAGE REGULATORS T0220

Positive + Negative +
7805 - 40p 7905 - 50p
7812 - 40p 7912 - 50p
7815 - 40p 7915 - 50p
7824 - 40p 7924 - 50p

BI-PAK

Send your orders to Dept PW4 BI-PAK PO BOX 6 WARE, HERTS
SHOP AT 3 BALDOCK ST. WARE, HERTS
TERMS CASH WITH ORDER. SAME DAY DESPATCH. ACCESS.
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7006
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your Total order. Postage add 75p per Total order.

DRESSLER AMPLIFIERS

These are high power 240V linears using 4C x 150 or 4C x 250 or 4C x 350 Eimac Tubes NOT using the grounded Grid system.
Fully protected, no thermal damage to PA finals possible.



DRESSLER AMPLIFIERS

D70 70cm 200wfm 400 PEP £700.00
D200 2mtr 300wfm 600w PEP £595.00
D200S 2mtr 400wfm 1KW PEP £695.00
D200C 2mtr 100w. Few left at £275.00

GASFET DRESSLER PRE-AMPS

VV2 £44.00
VV2GAAS 150W £75.00
VV200GAAS 750W £85.00
VV200GAAS 1KW Non switching £22.00
VV2RPS N Type £24.00
VV7RPS S0259 £22.00
VV7RPS N Type £24.00
New VV200 VOX £84.00 250w PEP VOX
Powered by the linear or with separate interface.
0.7 - 0.9dB signal to noise
0.2dB insertion loss




GASFET MASTHEAD PRE-AMPS

3SK97 GASFET Available separately £5.00

SPECIAL OFFER
TRIO/KENWOOD
TR9130 25W
MULTIMODE COMPLETE
WITH TONNA 9XY
ANTENNA
£430.00

FRG 7700

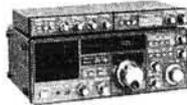

With or without memory
For price phone 01-556 1415

FT 102 £625.00



FT 726



INC. 70CMS + SATELITE

COMPUTERISED ROTATOR



PRICE SLASHED
£350

NOW £315.00

ICOM R70




PHONE DRESSLER
01-556 1415

ICOM IC251



£469

ICOM IC2E

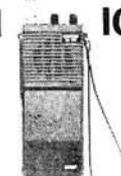

149 SPECIAL

ICO2E
LCD Push button up to 5W FM latest portable

POA

G4JDT HARVEY LEXTON EAST LONDON HAM STORE

DRESSLER (U.K.) LTD.,

191 FRANCIS ROAD LEYTON E 10
TEL 01-558 0854 TELEX 8953609 LEXTON G
01-556 1415

YAESU

FT1 Gen. Coverage Tx/Rx
FT980 Gen. Cov. Cat System
FT757 Gen. Coverage
FT102 150W 10m-160m
FC102 A.T.U.
FV102 V.F.O.
SP102 Speaker
FT77 - NEW - inc. M/C
FP700
FC700
FTV700 D.M.
FRG7700 Gen. Coverage Rx
FRG7700 M
FT790 FM/SSB
FT290R with mods FM/SSB
FT208 2mtr portable FM
FT708 70cm portable FM
FT230 2mtr FM mobile
FT730 70cm FM mobile
FT726 16-20-70 (X Band)
FRV7700A 118-150
FRV7700B 50-60/118-150
FRV7700C 140-170
FRV7700D 70-80/118-150
FR7700 Aerial Tuner
FRA7700 Active Antenna
FF5 Filter
MMB11 FT290 Car Mount
NC11C Charger
NC8 Base Charger FT208/708
FT203 New Model



FOR THE VERY LATEST DRESSLER PRICE
01-556 1415

DAIWA

CN620A. £57.00
CN1001. Auto A.T.U. £150.00
CNW419. 500W PEP. Gen. Coverage A.T.U. £130.00
AF406. Active filter
AF606 P.L.L. Active filter £60.00
DR7500X £110.00
DR7500R £120.00
DR7600X £160.00
DR7600R £170.00
Kenpro KR400 inc lower clamps £110.00
KR250 £45.00
Hirshman Hitro 250 £55.00

TRIO/KENWOOD

TS930 Gen. Coverage Rx/Tx £1150.00
AT930 ATV £139.00
TS530 H.F. P.O.A.
R2000 £385.00
TS430 H.F. £690.00
TR9130 + 9XY Tonna £430.00
TR2500 2mtr portable £219.00
AT230 ATU £135.00
PS430 PSU £110.00
R600 Receiver. AM/SSB £230.00
TR3500 70cm portable £245.00
SMC 25 speaker mic £16.00
PB 25 battery pack £25.00
MSI Strand mobile £30.00
R2000 Receiver £380.00
VC10 - Converter £110.00
R600 Receiver £220.00
SWR 100A £37.00
SWR 100B £37.00
SWR 200 £78.00
MC55 Mobile mic £45.00
TW400 UHF/VHF £425.00
VSI Voice synthesizer £24.00
TM201A 2HTR £259.00
FC10 Remote display P.O.A.

DATONG

D70 Morse Tutor £56.35
PC1 Gen. Coverage converter £137.00
FL1 Agile filter £89.70
FL2 Active filter £129.37
FL3 Angle filter & notch £82.80
ASP Auto clipper £56.35
D75 Manual clipper £29.90
RFC Speech clipper £47.15
AD270 Indoor active ant. £64.40
AD370 Outdoor active ant. £33.92
RFA Wide band AMP £67.85
ANF Auto notch & filter

STANDARD

See the new Standard C5800 Multimode 25W
SSB/FM/CW 2mtr £359.00
C58 2mtr FM/SSB/CW
C78 70cm portable
C7900 70cm mobile £239.00
C8900 2mtr mobile £219.00
C5800 2mtr FM/SSB 25W £359.00
C1100 2mtr portable £139.00
Plus All Accessories

TONNA

50 5 ele £34.00
144 4 ele £14.00
144 9 ele £17.00
144 9 ele cross £32.00
144 9 ele portable £20.00
144 13 ele portable £31.00
432 21 ele £29.00
432 21 ele ATV £29.00
432 19 ele £20.00
432 19 ele cross £34.00
1296 23 ele £25.00
144/432 9+19 ele cross £34.00
Power splitters and portable masts in stock.

MORSE KEYS

Morse keys Swedish brass key £49.00
HiMound HK707 £12.95
HiMound MK705 £11.50
HiMound HK702 £12.95
Kenpro squeeze key KP100 electronic key £65.00
Kenpro KR200 Memory keyer £149.00
Daiwa DK210 Electronic £47.00

ICOM

IC751 HF
IC745 HF
IC271 2 HTR

P.O.A.
P.O.A.
P.O.A.

IC251 Special
ICR70 Receiver + New R71 soon
(Infra-red)

IC290E
IC290M
IC25E
IC120 1296
IC2E
ICO2E
IC4E
ICAT500
ICAT100
IC2KL Linear
IC2KLPS
SP3 Speaker
HP1 Headphone
SMS Base mic
PS35 IC751 PSU
Voice Box 751/271/471
IC DC1 DC Car, IC2E
IC CP1 DL Lead
All ICOM Accessories Stocked

PHONE DRESSLER FOR LATEST PRICE - 01-556 1415

TONO SPECIAL OFFER TASCOS TERMINALS

CWR 685E VDU TX/RX Keyboard
RTTY 1 Morse £695.00
CWR 675 As above reader £425.00
CWR 670 Reader No VDU £285.00
CWR 610 Basic model £160.00
6550 RTTY/CW Terminal £285.00

SCANNING RECEIVERS

JIL SX200N £285.00
CD6000 Air £99.00

JAYBEAM ANTENNA

All Jaybeam Antenna In Stock P.O.A.

SPECIAL PRICES FROM DRESSLER 01-556 1415

ALL ACCESSORIES AVAILABLE - PLUGS SKTS CO-AX 2MTR COLINEAR £33.00 70CM COLINEAR £33.00



PRICES INCLUDE VAT AT THE PRESENT RATE OF 15%
OPEN MON-FRIDAY 9:00-5:30. SATURDAY 10:00-5:00. INSTANT HP FACILITY AVAILABLE
EASY ACCESS M2-M11-M1 NORTH CIRCULAR ROAD - EASY PARKING

VISA

S.E.M.

UNION MILLS, ISLE OF MAN Tel: MAROWN (0624) 851277



SEMFACT 2. Our products are in 120 countries.

S.E.M. TRANZMATCH. Now has wider range on 160m. The best aerial matching system. Matches 15-5,000 ohms BALANCED & UNBALANCED up to 1Kw. Air coupled BALUN means no connection to equipment which can cure TVI both ways. NO TOROIDS. SO239s & 4mm sockets for CO-AX, ENDFED or TWIN FEED, 3.5-30MHz £74. 1.8-30MHz £83. EZITUNE built in £29.50 extra. (See below for the much acclaimed EZITUNE) All Ex Stock. Please note that 90% we sell have the EZITUNE option.

S.E.M. IMABIC KEYS. We have replaced its plastic box, with an attractive plated steel case. No better fully auto keyer anywhere. Uses Curtis chip. R.F. proof. £38. A first class twin paddle key £15 Ex stock.

BRAID BREAKER/HI PASS FILTER. Stop TVI at TV. £6.50 Ex stock.

RF NOISE BRIDGE. Adjustable 0-1,000 ohms, 3" x 1 1/2" x 2" only. SO239s, 1-170MHz. Neat, accurate & economical. £29.50 Ex Stock.

3 WAY ANTENNA SWITCH 1Kw SO239s. Good to 2 metres. £15.00 Ex stock. Or 4th position to earth output £17.50 Ex stock.

S.E.M. 2 METRE TRANZMATCH. 5 1/2" x 2", 3" deep. SO239s. £24.90 Ex stock.

S.E.M. EZITUNE. New circuit. Gives MORE noise & bomb proof operation.

Because no similar unit is made, it's usefulness is not appreciated until you have used one. Eliminates need for S.W.R. bridge.

Clean up the bands by tuning up without transmitting.

Connects in aerial lead, produces S9 + (1 - 170MHz) noise in receiver. Adjust A.T.U. or aerial for minimum noise. You have now put an exact 50 Ohms into your transceiver. Fully protected, you can transmit through it, save your P.A. and stop QRM. SO239s, 3" x 1 1/2" x 2". £34.50 Ex Stock. P.c.b. + fixing + instructions to fit in TRANZMATCH or any ATU £29.50 Ex Stock.

SENTINEL 2M LINEAR POWER/PRE-AMPLIFIERS

Feature either POWER AMP alone or PRE-AMP alone or both POWER AND PRE-AMP or STRAIGHT THRU when OFF. Plus a gain control on the PRE-AMP from 0 to 20dB. N.F. around 1dB with a neutralised strip line BF981.

Ultra LINEAR for all modes and R.F. or P.T.T. switched. 13.8V nominal supply. SO239 sockets.

Three Models:

- SENTINEL 35** Twelve times power gain, 3W IN 36W OUT. 4 amps. Max. drive. 5W, 6" x 2 1/2" front panel, 4 1/2" deep. £65 Ex stock.
- SENTINEL 50** Five times power gain, 10 W IN 50W OUT. Max drive 16W 6 amps. Same size as the Sentinel 35. £79.50 Ex stock.
- SENTINEL 100** Ten times power gain, 10W IN 100W OUT. Max. drive 16W. Size: 6 1/2" x 4" front panel, 3 1/2" deep. 12 amps. £115 Ex stock.

POWER SUPPLIES for our linears 6 amp £34. 12 amp £49.

SENTINEL AUTO 2 METRE or 4 METRE PRE-AMPLIFIER (R.F. Switched) 1dB N.F. and 20dB gain, (gain control adjusts down to unity) 400W P.E.P. power rating. Use on any mode. 12V 25mA. Sizes: 1 1/2" x 2 1/2" x 4". £29.50* Ex stock.

PA5 Same specification as the Auto including 240V P.S.U. £33.00*

SENTINEL STANDARD PRE-AMPLIFIER. No R.F. switch. £15.00* Ex stock.

S.E.M. AUDIO MULTIFILTER (A very good filter at a very good price). To improve ANY receiver on ANY mode. The most versatile filter available. Gives "passband" tuning, "variable selectivity" and one or two notches. Switched Hi-pass, Lo-pass, peak or notch. Selectivity from 2.5KHz to 20KHz. Tunable from 2.5KHz to 250KHz. PLUS another notch available in any of the four switch positions which covers 10KHz to 100KHz. 12V supply. Sizes: 6" x 2 1/2" front panel, 3 1/2" deep, all for only £57.00 Ex stock.

SENTINEL AUTO H.F. WIDEBAND PRE-AMPLIFIER 2-40MHz, 15dB gain. Straight through when OFF, 9-12V. 2 1/2" x 1 1/2" x 3". 200W through power. £19.55* Ex stock.

SENTINEL STANDARD H.F. PRE-AMP. No R.F. switching. £12.62* Ex stock.

S.E.M. VISA 80 METRE RECEIVER

Already a great success. If you want an 80 metre (3.5-3.8MHz) Rx. Only 2 1/2" x 6" x 3". 12 volt operation. I.W. o/p. This is for you. £45.

12 MONTHS COMPLETE GUARANTEE INCLUDING ALL TRANSISTORS.

Prices include VAT and delivery. C.W.D. or phone your credit card number for same day service. *Means Belling Lee sockets, add £1.90 for SO239s or BNC sockets. Ring or write for more information. Place orders or request information on our Ansaphone at cheap rate times.

Goods normally by return.



PM COMPONENTS LTD. VALVE & COMPONENT SPECIALISTS

SELECTRON HOUSE, WROTHAM ROAD, MEOPHAM GREEN, MEOPHAM, KENT
PHONE 0474 813225. TELEX 966371 PM COMP



NEW BRANDED VALVES

A2087	11.50	ECC83	0.65	EL519	6.95	6AM5	6.00	12AT6	0.65
A2134	14.95	ECC85	1.35	EL821	8.50	6AN5	3.95	12AT7	1.15
A2293	6.50	ECC85	1.35	EL822	12.95	6AQ5	1.20	12AT7WA	2.50
A2900	11.50	ECC88	0.60	EM80	0.70	6AS5	1.50	12AU6	1.50
CL148A	115.00	ECC88	0.60	EM81	0.70	6AS7G	7.50	12AU7	0.55
DAF91	0.70	ECC91	2.00	EM84	1.65	6AT6	0.75	12AV6	0.80
DAF96	0.65	ECC94	0.60	EM85	1.10	6AU6	0.85	12AX7	0.65
DET72	28.00	ECC97	2.50	EM87	2.50	6AW8A	2.95	12AY7	4.00
DET23	38.00	ECC98	0.85	EN81	1.10	6B8A	3.50	12BA6	1.50
DET24	35.00	ECC98	0.85	EN82	4.40	6BE6	0.72	12BE6	1.05
DF91	0.70	ECC98	1.70	EY84	6.95	6BD6	1.00	12BH7	1.80
DF92	0.60	ECC98	1.70	EY86/87	0.50	6BQ6	1.95	12BY7A	2.75
DF96	0.65	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7A	1.75
DK91	0.90	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7B	1.75
DK92	1.20	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7C	1.75
DK96	2.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7D	1.75
DL32	0.60	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7E	1.75
DL36	2.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7F	1.75
DL310	13.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7G	1.75
DL316	10.00	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7H	1.75
DM160	2.75	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7I	1.75
DY86/87	0.65	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7J	1.75
DY802	0.72	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7K	1.75
EB8CC	7.00	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7L	1.75
EB8CF	10.00	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7M	1.75
EB8F	13.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7N	1.75
EB8G	11.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7O	1.75
EB8HC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7P	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Q	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7R	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7S	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7T	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7U	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7V	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7W	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7X	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Y	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Z	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7A	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7B	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7C	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7D	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7E	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7F	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7G	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7H	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7I	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7J	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7K	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7L	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7M	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7N	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7O	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7P	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Q	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7R	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7S	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7T	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7U	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7V	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7W	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7X	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Y	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Z	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7A	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7B	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7C	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7D	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7E	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7F	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7G	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7H	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7I	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7J	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7K	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7L	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7M	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7N	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7O	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7P	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Q	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7R	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7S	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7T	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7U	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7V	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7W	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7X	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Y	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7Z	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7A	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7B	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7C	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7D	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7E	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7F	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7G	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7H	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7I	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7J	1.75
EB8CC	3.50	ECC98	1.70	EY88	0.55	6BQ6	1.95	12C7K	1.75
EB8CC	3.50	ECC98	1.70	EY88					

Tandy

Tune In To The World With Realistic™

A Direct-Entry PLL Communications Receiver



- Hear International News, Music, Ham or Shortwave and Marine

£199⁹⁵

Realistic™ DX-400. Our finest portable receiver ever! Microprocessor controlled with phase-locked-loop and direct entry pushbutton tuning, you can use Auto-Scan to find new stations or manual tuning with 1-3 kHz stepping on AM/SSB/CW, 50 or 100 kHz on FM. Bands: AM/SSB (USB and LSB)/CW, 150-29,999 kHz; FM 87.4 MHz, 240 VAC, 12VDC neg. gnd. or six "C" batteries (not incl.). Telescopic antenna, loop stick for AM and built-in speaker. Jacks for external speaker, external antenna and headphones. Requires two "AA" batteries for memory backup. **20-207**

16-Channel Portable Programmable Scanner

Covers 68-88 MHz VHF-Lo, 144-148 MHz Ham, 108-136 MHz AM Aircraft, 138-144 MHz, 148-174 MHz VHF Hi, 380-450 MHz Ham, 450-470 MHz UHF-Lo, 470-512 MHz UHF-Hi


£229⁹⁵

- Now You Can Listen To Aircraft, Hams and More - Wherever You Go No Crystals To Buy!



Realistic PRO-30. Scan up to 16 of your favourite channels continuously, or search a selected frequency range for new or unpublicised channels. Scan and Search in two speeds. Two-second Scan Delay, selectable for each channel prevents missed replies. Has jacks for external antenna and earphones. Requires six "AA" batteries or mains or DC adapter. Memory backup requires four silver-oxide batteries. **20-9131**

...And A 60-Channel Programmable Scanner

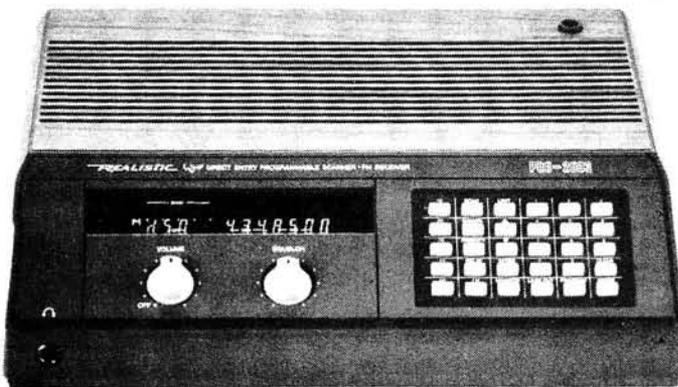

£259⁹⁵

- 50 Public Service and Aircraft Channels

Realistic PRO-2003. No crystals to buy - direct keyboard entry of 20,584 frequencies! Use the search circuit to find new channels. When you find one that sounds interesting, store it in memory! Has 2-speed scan and search, Scan Delay, individual channel lockout, priority function and variable squelch control. Bands: VHF-Lo 68-87 MHz; FM Broadcast 88-107 MHz; VHF-Air AM 108-136 MHz; Ham 138-148 MHz; VHF-Hi 148-174 MHz; 410-450 MHz; UHF-Lo 450-470 MHz; UHF-Hi 470-512 MHz. **20-9117**

OVER 340 STORES AND DEALERSHIPS NATIONWIDE

Check your phone book for the Tandy Store or Dealer nearest you

Pro: to this advertisement. All quoted regular prices have been charged during the last six months at the Tandy Store, Tameaway Tower, Bridge Street, Walsall, West Midlands, WS1 1LA

Known As Radio Shack In The U.S.A.

Prices may vary at Dealers
Offers subject to availability

Technology
Tandy
ou

FREE CAREER BOOKLET

Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

Name

Address

ICS
Dept EE144
160 Stewarts Road,
London SW8 4UJ.



01-622 9911
(all hours)

Ex-Gov. 27ft telescopic aerial close to 5ft. Good condition, complete with all base & fittings **£45**. P&P paid. Callers welcome **£25**.

Pye Pocketfone Nightcall for PF1/TX/RX. New boxed **£17.00**.

Whip aerial Ex-Gov. 4ft collapsible **£1.00**.

Steel 2 in. Interlocking Mast sections 4ft. Price **£3.50** each p&p paid min. 5.

Crystals HC6U Ex. Equip. 5,000 mc/s, 7,000 mc/s, 8,000 I.M.C mc/s, 9,000 mc/s. Also Glass Crystal 100 Kc/s, to fit B7G base. All at **£2** p&p paid.

Telephones – Type 706 good condition **£5** p&p paid.

Small 230V fans, 4 in. x 2½ in. 2,500 r.p.m. **£4.50** p&p paid.

Pye Pocketfone PF1, battery charger, 12 way with meter **£10** p&p paid. PFI TX batteries **£2** each p&p paid.

We have also for sale the following items which are too numerous to advertise. Callers only, valves, transformers, tuning units, receivers, bases, wave-guide, scopes, plugs, sockets, power units, capacitors, aerials, headsets, cable, signal generators, BC221.

Ni-Cad batteries for Pye PF1 RX. 5 for **£2** p&p paid. Min. order 5. All these batteries are ex-eq. but good condition.

Bargain Parcels 14 lbs at **£10**, 28 lbs at **£20** and 56 lbs at **£40**, p&p paid. Contains pots, res., diodes, tagboards, caps., chassis, valve holders etc. Good value save **£££**'s. Lucky dip service.

AVO multiminor test meter. Tested. **£20**. Ex eq. p&p paid.

AVO 7X. Tested. Ex. eq. **£40** p&p paid.

Opening times:

Monday-Friday 8.30am-5.00pm, Saturday 8.30am-12am

Please allow 14 days for delivery.

A. H. THACKER & SONS LTD
HIGH STREET, CHESLYN HAY
NEAR WALSALL, STAFFS.

Greater LTD
Electronics
DISPLAY & COMMUNICATION PRODUCTS

Hay Lane, Braintree, Essex CM7 6ST

Telephone:
(0376) 27117 (24-Hr Ansaphone Service)
(0376) 42494
Telex: 987911



R. F. POWER TRANSISTORS

R. F. POWER TRANSISTORS						VALVES National, G.E., RCA, ...	
2N2857	£ 2.06					6AH6	£ 3.50
2N3137	£ 2.70	2N6082	£ 9.00	MRF421	£31.57	SD1143	£10.41
2N3375	£ 9.20	2N6083	£12.00	MRF422	£13.35	SD1219	£17.50
2N3553	£ 2.00	2N6084	£13.20	MRF433	£16.21	SD1229FL	£ 8.80
2N3632	£10.00	2N6094	£ 8.00	MRF449A	£14.90	SD1272FL	£11.20
2N3733	£13.20	2N6095	£30.00	MRF450	£15.00	SD1285	£12.75
2N3866	£ 0.85	2N6096	£20.20	MRF450A	£11.40	SD1272	£11.20
2N3926	£11.26	2N6097	£13.30	MRF453	£20.00	2SC495	£ 0.70
2N3927	£11.82	2N6255	£ 3.45	MRF454	£18.80	2SC496	£ 0.70
2N4416	£ 0.75	MRF221	£12.05	MRF455	£16.00	2SC730	£ 4.50
2N4427	£ 0.75	MRF223	£13.83	MRF458	£15.00	2SC1096	£ 0.75
2N4440	£ 9.50	MRF224	£12.50	MRF460	£18.75	2SC1165	£ 6.80
2N5016	£ 8.72	MRF226	£16.35	MRF464	£35.00	2SC1172	£ 7.80
2N5090	£13.90	MRF227	£ 3.76	MRF472	£ 3.50	2SC1173	£ 0.90
2N5109	£ 2.00	MRF231	£12.36	MRF475	£ 2.50	2SC1177	£18.14
2N5160	£ 4.80	MRF232	£11.35	MRF476	£ 2.20	2SC1306	£ 0.90
2N5179	£ 0.86	MRF233	£10.00	MRF477	£18.75	2SC1307	£ 1.40
2N5190	£ 1.50	MRF234	£ 6.50	MRF485	£ 3.13	2SC1449L	£ 0.70
2N5485	£ 0.82	MRF237	£ 2.70	MRF486	£ 3.20	2SC1678	£ 1.05
2N5486	£ 0.88	MRF238	£12.60	MRF604	£ 3.30	2SC1909	£ 2.50
2N5589	£ 5.70	MRF239	£16.00	MRF607	£ 4.50	2SC1968A	£18.54
2N5590	£ 8.50	MRF240	£18.55	MRF629	£28.24	2SC1953	£ 0.90
2N5591	£ 8.90	MRF243	£28.08	MRF643	£28.24	2SC1969	£ 1.70
2N5635	£ 6.20	MRF245	£30.10	MRF901	£ 3.00	2SC1970	£ 2.50
2N5636	£12.50	MRF247	£30.10	SD1005	£ 8.20	2SC1978	£ 8.00
2N5637	£14.25	MRF260	£ 5.00	SD1006	£ 2.00	2SC2028	£15.00
2N5641	£ 7.35	MRF261	£ 9.00	SD1012FL	£ 8.35	2SC2029	£ 1.40
2N5642	£ 9.90	MRF262	£11.00	SD1013	£ 8.25	2SC2078	£ 1.40
2N5643	£13.00	MRF264	£11.00	SD1019	£20.80	2SC1945	£ 2.10
2N5913	£ 2.50	MRF313A	£15.09	SD1049	£ 1.95	2SC2166	£ 1.50
2N5944	£ 8.20	MRF314	£25.90	SD1088	£28.00	2SC2297	£15.00
2N5945	£ 8.95	MRF317	£73.00	SD1089	£28.80	2SC2314	£ 0.70
2N5946	£16.63	MRF327	£70.00	SD1098	£40.10	2SC2538	£ 1.82
2N6080	£ 6.00	MRF401	£11.84	SD1127	£ 2.60	2SC3020	£12.72
2N6081	£ 8.75	MRF406	£12.83	SD1135	£ 8.42		

A replacement guide to dozens of Motorola Transistor part numbers. Stocks of original RF Devices from such manufacturers as: MOTOROLA, RCA, GE, TRW, MSC, ACRIAN, TOSHIBA, FUJITSU, NEC, MITSUBUSHI, PHILLIPS, AMPEREX and others. Normally Stock Items are Shipped by return post.


OTHER PRODUCTS

High Voltage Vacuum Capacitors
Diodes Display Devices Vidicons
Power Tube Accessories
Connectors Finger Stock
Chimneys Sockets

TERMS: Cash/Postal Order/Cheque/Access
CREDIT: Accounts available subject to approved references
POSTAGE: Add £1.00 to order
VAT: All prices are excluding VAT, please add 15% to order and postage
GUARANTEE: All goods brand new and to specification


6201	£ 6.00
6360	£ 5.00
6550A	£ 8.00
6686	£12.00
6689	£ 1.00
6809	£ 3.00
7350	£14.00
7551	£ 6.00
7558	£ 7.00
7591A	£ 4.00
7869	£ 5.40
811A	£15.00
812A	£28.00
8400	£20.00
8298	£ 5.00
8417	£ 5.00
866A	£15.00
872A	£20.00

ambit international

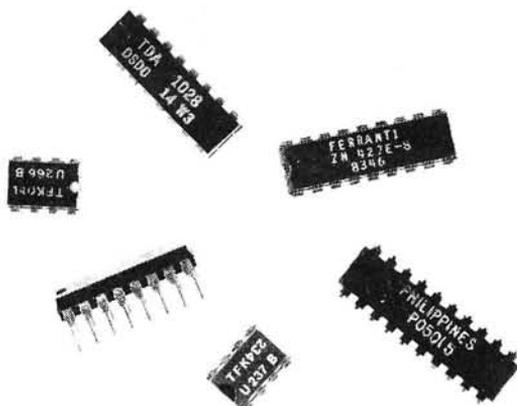


the first name for:-
Linear ICs

ambit international

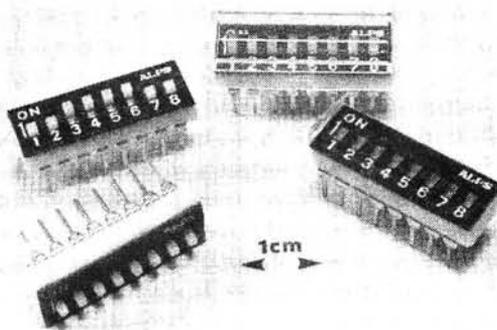

the first name for:-
ALPS switches

ambit international

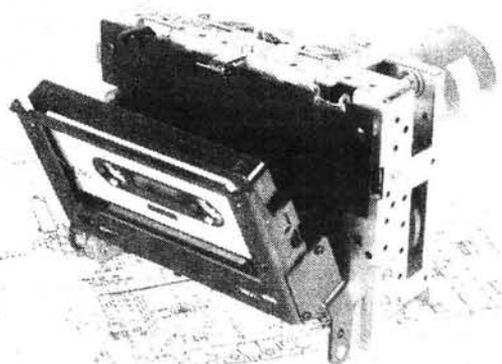

the first name for:-
Solenoid cassette mechanisms

ambit international



The first name for:-
Value in electronics, communications and computing

ambit international

the first name for:-

Value in electronics, communications and computing

Ambit's Spring '84 catalogue continues the theme we pioneered on the magazine stands with a concise 'price on the page' presentation of over 5,000 stock lines for the hobbyist. Whether your interest is communications, computing, audio or general electronics, there's something in it for you. Three £1 discount vouchers inside ensure that your initial investment of 80p is amply repaid with substantial interest.

200 North Service Road, Brentwood, Essex. CM14 4SG tel 0277-230909 tlx 995194.



Amcomm OF LONDON



01-422 9585 FOR FAST DELIVERY

ICOM IR70 GENERAL COVERAGE RECEIVER

If you are one of the many hunting for a second hand ICOM R70... PLEASE! SAVE YOUR MONEY... DON'T CALL AMCOMM... WE'VE NEVER HAD ONE!

This says it all for the high performance and classy appearance of the R70. "YOU BUY IT TO KEEP IT". We keep repeating it... PERFORMANCE SILKY SMOOTH, APPEARANCE SILKY SMOOTH, OPERATION SILKY SMOOTH... PRICE? we think also SILKY SMOOTH, certainly smooth enough for you to call us on 01-422 9585 and become one of the "YOU BUY IT TO KEEP IT" R70 owners.




THE KEY ELEMENT

Are you REALLY SATISFIED with the performance of your station? Getting OPTIMUM PERFORMANCE? Or is that microphone not quite doing what you expected? It's not surprising, most of the microphones used in communication today were designed for use with paging systems. Listen to the MARVELOUS AUDIO from the other side of the Atlantic, that's not surprising either for a large number of the American operators are using the HEIL MICROPHONE CAPSULE, THE KEY ELEMENT in reproducing communication sound as it should be. Not for them the "this is mic one, this is mic two, this is mic three etc." syndrome, all you get from that test is three different opinions from three different stations. We know you are looking for INTELLIGIBILITY from first class ARTICULATION. It's now available in the UK. The HC 3 is a tiny capsule which rolls off sharply under 350Hz and above 3100Hz and virtually flat in between. If you care about PERFORMANCE, INTELLIGIBILITY and BEING LISTENED TO RATHER THAN JUST HEARD, then the HEIL HC3 capsule is for you. Easily fitted in a matter of minutes to almost any microphone case and available at £17.99 including VAT and post.

AMTECH 300B ANTENNA COUPLER

BRITISH MADE and MADE TO LAST and PRICED TO SUIT YOUR POCKET, thousands already in use throughout the world. Rated at 300W pep the 300B is suitable for all coaxial feed or random wire antennas. Whats more it comes with a twin meter (3.5 to 170MHz) S.W.R. bridge ABSOLUTELY FREE. Compare the price with anything else available and you'll see why it has become our STAR BUY. CALL AMCOMM 01-422 9585 for FAST DELIVERY AND SUPER VALUE.

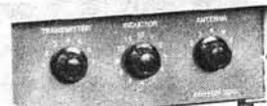

YAESU FT290RB MULTI MODE TRANSCEIVER

Looking back a year or so we're extremely surprised that the 290 has not had to face up to any competition. TRYING to see the other manufacturers attitude to it isn't easy, could they better it? or did Yaesu GET IT RIGHT FIRST TIME. We know they did, why else has it become the world's Biggest and fastest selling rig of all time? CAN IT BE IMPROVED? functionally we can add a few refinements, you might like to add the MUTEK board if you feel you need it, we'd be happy to do anything like that for you but it still adds up to Yaesu's team doing the big bit GETTING IT RIGHT FIRST TIME and leaving the opposition STRANDED. CALL AMCOMM 01-422 9585. We'll quote you a price and delivery... FAST DELIVERY.

DON'T FORGET THE OTHERS IN THE YAESU FAMILY... THE FT230, THE 730 AND OF COURSE THE 790... ALL IN STOCK LOOKING FOR A GOOD HOME.

YAESU FT290RB 2m ALL MODE TRANSCEIVER

The world's BIGGEST AND FASTEST SELLING TRANSCEIVER EVER, still without a competitor in sight. This transceiver is a real seasonal gift from AMCOMM to you at a price YOU'LL NEVER SEE AGAIN... You don't believe us? Call 01-422 9585 FOR YOUR BIG SURPRISE.



COMPETITORS PLEASE CALL AFTER 6 PM OR ANYTIME SUNDAY OR MONDAY.

THE FM MOBILES

There are many on the market these days and it must be difficult for the buyer to make a decision... DON'T LET IT WORRY YOU for we have exactly the same problem... We've searched the specs, tested the performance and analysed the reliability and our findings are simple... THEY ARE ALL GOOD... some have this and some have that, some are black, some are grey but they all have one thing in common... VALUE FOR MONEY. If you like it and it suits you then it's the one for you... It leaves only one problem... THE PRICE. We're always helping where it hurts - Try us on 01-422 9585 Now. We'll ease the pain.

WHAT INFLATION

Cast your mind back seven or eight years to the introduction of the Yaesu FT 101E, it proved A WINNER FOR YAESU and a DELIGHT TO OWNERS. At £579 it was considered to be GOOD VALUE THEN. Reflect on this! and ask these questions: Did it have GENERAL COVERAGE... IF SHIFT/WIDTH CONTROL... TWO VFO'S... MEMORIES... A KEYS... FM... UNRESTRICTED RIT... AN RF PREAMP... FULL BREAK IN... SWITCHABLE AGC... SCAN FACILITY? Both you and we know it didn't. Yet despite the passing of the years, and MASSIVE INFLATION affecting other markets Yaesu can still offer you a transceiver with all these facilities AT VIRTUALLY THE SAME PRICE AS THE FT 101E WAS ALL THAT TIME AGO. Amateur radio expensive? Answer that one yourself. Oh! By the way the transceiver we are talking about is the FT 757GX.

ROTORS

HIRSCHMANN 250... There is no better buy on the market than this... A lightweight Rotor suitable for most VHF antennas... It's yours for £45... Carr and ins. £1.50.

SKYKING SU4000... An outstanding Rotor for large VHF arrays or light HF beams... A delightful illuminated compass readout... NICE ONE AT \$85.00 GARR & INS. £1.50.

SKYKING 2000... A super little rotor ideal for the smaller VHF array, already in use at G5VS and doing a grand job, he is delighted and so will you be at the performance and PRICE £39.95... CAN YOU BELIEVE IT? Add £1.25 carriage and you will, we'll have it off to you at once.

ANTENNA PARTS AND KITS

Includes the world's finest traps - REYCO, which are guaranteed for five years no condenser used - no blow up possible. Precision moulded coil forms with stainless hardware - aluminium iridite finish - fully waterproofed and suitable for wire, vertical and beam antennas, rated at 2.5Kw and weigh only 4oz per trap - available for 7Mhz (KW40), 14Mhz (KW20), 21Mhz (KW15) and 28Mhz (KW10). £18.99 including VAT and carriage.

The BALUN - The Unadilla W2AU is famous because it's the best, same rating as the traps and has a built-in lightning arrester - available 1:1 and 4:1 - get it right first time with W2AU Balun - guaranteed for five years. £18.99 including VAT and carriage.

THE KITS - AMCOMM 40 - 1 pair KW40 traps, 1 PL259, 1 W2AU Balun, 1 pair insulators and of course 120ft soft drawn copper wire - coverage 80-10 metres (including 10Mhz). Full instructions included. £43.50 including VAT and carriage.

AMCOMM 20 - 1 pair KW20 Traps, 1 W2AU Balun, 1 PL259, 1 pair insulators and 65ft soft drawn copper wire - coverage 40-10 metres, full instructions included. £41.50 including VAT and carriage.

AMCOMM 38 - 1 pair KW10 traps, 1 pair KW15 traps, 1 PL259, 1 W2AU Balun, 1 pair insulators and 30ft soft drawn copper wire - coverage 20m, 15m and 10m. Full instructions included. £47.50 including VAT and carriage.

NEW WARC TRAPS - KW12, KW17 and KW30 now available from stock. £18.99 including VAT and carriage.

OUR MAIL ORDER SERVICE

The words we hear most frequently are "I REALLY DIDN'T EXPECT IT UNTIL NEXT WEEK". THEY REFER TO OUR MAIL ORDER SERVICE and come both by telephone and letter. When we say "IT WILL GO TODAY" we really mean that, the same day via red label special Securicor or first class post. You have very little to do, refer to the list below, pick up the telephone, quote your credit card number and the product is on the way to you... or drop a cheque in the post and goods will be despatched on receipt. WE PROMISE YOU ONE THING, the very least you'll save is the cost of a telephone call... TET, HYGAIN, YAESU, ICOM, TRIO/KENWOOD, MICROWAVE MODULES, BNOS, DATONG, JAYBEAM, TONNA, MORSE KEYS including HI-MOUND and the SWEDISH BRASS, UNADILLA, SKYKING, HIRSCHMANN, TONO, TASCOS, JVC PADDLE, VALVES, WELZ, MUTEK, HANSEN, DAIWA and many more. If you need it we probably have it. If you've got the time we've got the phone lines... We guarantee you'll save more than a phone call. All the year round call 01-422 9585 for fast quotes and fast delivery BACKED UP BY FIRST RATE AFTER SALES SERVICE.

YAESU FT980

GENERAL COVERAGE TRANSCEIVER

Yaesu said the FT1 was an adventure in electronics and we agreed. The FT980 is something quite different... ITS AN ACCOMPLISHMENT IN ELECTRONICS providing the operator with a brilliantly designed transceiver with a wealth of features. Every feature has been carefully designed in to ensure the operator has MAXIMUM BENEFIT without gimmicks while allowing INCREDIBLE EASE OF OPERATION. We'd need more than this page to do justice to the FT980 so we suggest you call in and try it for yourself or call 01-422 9585 for a beautifully illustrated leaflet with a full description... Yes it is expensive... the best usually is unless a way can be found to ease the pain... AMCOMM ARE EXPERTS AT THAT... TRY US.

THE HANDHELDS

As we said last month "It's been a great year for the handhelds, especially the Yaesu FT208R, they are all extremely versatile BUT THE 208 HAS THE EDGE. Did you see the reviews? They certainly told you a lot... WHAT THEY DIDN'T TELL YOU WAS HOW TO OPERATE YOUR HF RIG FROM THE 208, from the garden, from the car, even the bath if you are willing to chance it. Whichever handheld you're interested in - Marine P.M.R. or Amateur: call us and we'll tell you, we'll even send you the information. Call 01-422 9585.

YAESU FT726R 2m/70cms/SAT

If you've been enjoying your annual winter break in ULAN BATOR you've probably missed the VOLUMES OF SUPERLATIVES being liberally dispersed about the YAESU 726R... They're coming from all sources... THE REVIEWERS... LUCKY OWNERS... FRIENDS OF LUCKY OWNERS... even from the VERY UNLUCKY DREAMERS... LITTLE WONDER!... ALL OF 2 MTS... ALL OF 70cms... and a large portion of the HF SPECTRUM... MORE... if rumours coming from JA prove correct it won't be too long before we have a 1296 FACILITY... add the SATELLITE DUPLXER to that lot and you really have yourself a DREAM OF A RIG... Performance figures? Like the rest of it TOP NOTCH... but don't take our word for it, call AMCOMM ON 01-422 9585



CALL 01-422 9585 FOR PRICE

UNION ELEC. WORLD TIME GLOBE

INSTANT TIME AT HOME AND ABROAD... simply turn the globe to the required country and it displays a red FLASHING LIGHT on that country... Beneath, IT DISPLAYS THE TIME IN THE UK AND THE COUNTRY OF YOUR CHOICE... Long life of batteries guaranteed by automatic switch off after 30 seconds... a beautiful and practical addition to the shack at any time... £47.50 post paid... Call now 01-422 9585 FOR FAST DELIVERY.



Amcomm

SERVICES LTD., 194 NORTHOLT ROAD, SOUTH

HARROW, MIDDX. HA2 0EN. ENGLAND. (Opp. South Harrow Underground Station) TEL: 01-422 9585. TELEX: 24263



I Wonder Why

THE REVISED UK CB RADIO LICENCE, which comes into effect on 5 March 1984, is mainly a "tidying-up" job in the light of the experience of the first two years of the service. The prohibition on transmitting music, or re-transmitting radio and TV broadcast material, is clearly spelled out now. The only signals permitted are speech, selective calling or digital identification signals, plus K-tone or pip-tone signals to indicate the end of a transmission. Repeater stations are ruled out, though they may later be authorised in the 934MHz service. Use of a CB on board ship requires the consent of the ship's Master.

The restrictions on the form of antenna permitted for 27MHz installations have been relaxed somewhat. The loading coil may now be placed anywhere in the antenna, instead of just at the base, but the length of the antenna is now limited to 1.65m and its diameter to 55mm, in both cases including the loading coil but excluding any ground-plane elements.

The requirement for transmitter power to be reduced when the CB rig is used with an antenna more than a certain height above ground has been totally revised, so that the power limit is stated in watts, rather than in dB relative to full power as previously.

Two changes have been made to the limitations on who may operate a CB set under a particular licence. The first allows any person to operate the apparatus under the direct supervision of the licensee—a reasonable relaxing of the rules. The second change prevents anyone under the age of 14 holding a CB licence. In future a child under 14 can operate only under the direct supervision of

the licensee, or of another member of the licensee's household appointed to do so.

I was not aware that there had been any particular problems from young CBers, and I wonder why this rule has been made. After all, we have a minimum age limit of 14 for the Amateur Licence, but we still get plenty of "children" of all ages who abuse their licences and spoil other people's enjoyment of the hobby in the process.

Another "I wonder why" topic is the choice by British Telecom of the name Teletex for its new telephone data service. Surely, when the name Teletex is already in widespread use for the quite unrelated broadcast data services on TV (Ceefax and Oracle in the UK), it would have been wiser to select a name that didn't sound virtually identical when spoken. It's already caused confusion, for one national TV rental chain had a whole lot of display material printed for its shops proclaiming that several of their sets incorporated Teletex facilities. They didn't—they were Teletext sets!

Geoff Arnold

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the **Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG**, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

INSURANCE

Turn to the following page for details of the PW Radio Users Insurance Scheme, exclusive to our readers.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

SUBSCRIPTIONS

Subscriptions are available at £13 per annum to UK addresses and £14 overseas, from "**Practical Wireless**" **Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS**. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at £1 each, including post and packing to addresses at home and overseas.

Binders are available (Price £5.50 to UK addresses, £5.75 overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF**. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

Be Prepared

Following *PW's* most successful first venture into organising an open 144MHz contest last year, we will be repeating the event this year.

The "PW QRP 144MHz Contest 1984" will take place on Sunday 17 June between 0900 and 1700GMT (10am to 6pm local time).

Look out for further details nearer the date.

Tapes Catalogue for SWLs

The Handicapped Aid Programme—UK and the Canadian Handicapped Aid Program can supply twelve professionally produced tape recordings devoted to various aspects of the hobby of DXing, designed specifically for shortwave listeners everywhere.

Their publication entitled *Tapes Catalogue* contains descriptions of the subjects covered by the twelve tapes, order form and prices.

To obtain a free copy of the *Tapes Catalogue*, apply, enclosing return postage, to either: HAP-UK, PO Box 4, St Ives, Huntingdon, Cambs. PE17 4ST, or CHAP, 6 Coolbreeze Avenue,

The 1983 Girl Technician Engineer of the Year

Mrs Frances Dagg, age 23, a Software Development Engineer from Coundon, Coventry, is the 1983 Girl Technician Engineer of the Year. At a ceremony in London on 19 January 1984, Baroness Platt of Writtle, Chairman of the Equal Opportunities Commission, presented her with a prize of £250 and an inscribed rose bowl. A special award of £100 was made to the runner-up, Mrs Lynne Holt, 29, also a Software Development Engineer from Coventry. Employed by GEC Telecommunications in Coventry, Frances work involves all aspects of computer programming, however, she is primarily concerned with writing CAD (computer-aided design) programs for electronic design purposes and assisting hardware engineers in their use. Her responsibilities also include training graduate engineers in the use of the Circuit Design System.

Seeing her software in action, providing increased efficiency in hardware design for a wide variety of applications, proves to be particularly rewarding for Frances. Her main leisure interests include, inevitably, her home computer, plus the works bridge club which she organises.

Pt Claire, Quebec, Canada H9S 5G4.

The Handicapped Aid Programme is an international organisation that promotes s.w. radio amongst handicapped people and offers them practical assistance. All profits from sales of the tapes are ploughed back into the organisation.

Royal Television Society

It will soon be 50 years since the termination of the contract between the Baird Company and the BBC, whereby the 30-line television service was broadcast on frequencies in the medium waveband, and received mainly in the homes of enthusiastic amateurs and experimenters.

The Midland Centre of the Royal Television Society plans to mark this anniversary with an event to be held towards the end of March and initially wishes to identify as many of those pioneer viewers as possible.

The Society, therefore, invites any of the original Baird viewers to contact their *Honorary Secretary, John Grantham, BBC Network Production Centre, Pebble Mill Road, Birmingham B5 7QQ.*



This Award, which is sponsored by The Caroline Haslett Memorial Trust and The Institution of Electrical and Electronics Incorporated Engineers, aims to focus attention on electrical and electronic engineering as a worthwhile professional career for women.

For details of the Award and how to nominate candidates for the 1984 award, contact: *The Institution of Electrical and Electronics Incorporated Engineers, 2 Savoy Hill, London WC2R 0BS. Tel: 01-836 3357.*

Rallies and Events

The RSGB National VHF Convention will be held at Sandown Park Racecourse, Esher, Surrey, on Saturday 24 March 1984.

This one day event will include an exhibition by the trade, specialist groups and an equipment test facility will be operated by Don Hamilton G8DON. Also, a full lecture programme on v.h.f., u.h.f. and microwave subjects will run through the afternoon.

The Convention starts at 10.30am until 6.00pm, with the address and presentation of trophies by RSGB President, Bob Barrett GW8HEZ, at 1.45pm.

Refreshments and a licensed bar will be available throughout the day and admission will be £1.00 for adults, £0.50 for under 18 year olds and free for those under 14 years.

Buxton Mobile Rally, organised by the Buxton Amateur Radio Rally Group, will be held at The Transport Museum, Buxton, Derbyshire, on Sunday 8 April 1984.

Doors open at 11a.m. (10.30a.m. for RAIBC) and admission will be 50p, with under 14 year olds admitted free, provided they are accompanied by an adult.

There will be numerous trade stands, refreshments, talk-in on 144MHz and 430MHz, plus ample car parking is available.

For details, contact: *Dave Cooper G6MIF, tel: Buxton (0298) 6174.*

The White Rose Amateur Radio Society will be holding their 17th annual rally, for the third year running, at the University of Leeds, on Sunday 1 April 1984.

Starting at 11a.m. there will be approximately 50 stands offering new and used amateur radio gear, components, computer products, surplus equipment, books, etc., plus repeater groups and BYLARA will be represented.

Talk-in will be available on 144MHz and 430MHz, and a demonstration station, GB2WRR, will be in operation. Car parking is free, but an entrance fee of 50p will be charged (children and OAPs free).

Further details from: *The Rally Manager, Alan Bramley G4NDU, tel: Leeds (0532) 689880.*

Insurance

Readers who are interested in applying to the *PW Radio Users Insurance Scheme* are advised to use the coupon published on page 18 of last month's issue.

Practical Wireless, April 1984

Special Event Station

A special event station, GB2RBL, will be run on behalf of the Royal British Legion Branch, London N12, starting at 1100GMT on 31 March 1984 until 8 April 1984—a total of nine days.

Dependent on operators being available and propagation conditions permitting, GB2RBL will be active on 144MHz v.h.f. and the 14, 7 and 3.5MHz bands on h.f. For overseas DX, the station will be working 14.185MHz. Special event QSL cards will be available to all confirmed contacts, via the RSGB Bureau.

Further details from: *Terry F. Owen G4PSH, 5 Station Close, Holden Road, London N12 7EG. Tel: 01-446 0266.*

For Your Diaries

Amateur radio rallies and exhibitions during 1984 we've had dates for so far are:

NARSA Amateur Radio Weekend, Saturday/Sunday April 7/8 at Pontins Holiday Village, Southport, Lancs.

RSGB National Amateur Radio Exhibition, Saturday/Sunday April 28/29 at NEC, Birmingham.

27th Northern Mobile Rally, Sunday May 13 at the Great Yorkshire Showground, Harrogate, N. Yorkshire.

RNARS Mobile Rally, Sunday June 17 at HMS Mercury, Leydene, near Petersfield, Hants.

Longleat Amateur Radio Rally, Sunday June 24 at Longleat Park, Warminster, Wilts.

RSGB Woburn National Mobile Rally, Sunday August 5 at Woburn Abbey, Beds.

RAIBC/FRARS Hamfest '84, Sunday August 19 at Flight Refuelling Sports Ground, Merley, Wimborne, Dorset.

Scottish Amateur Radio Convention, Saturday September 8 at Cardonald College, Mosspark, Glasgow.

Welsh Amateur Radio Convention, Sunday September 30 at Oakdale Community College, Blackwood, Gwent.

Practical Wireless will be at all these events with recent copies of the magazine plus reprints and computer program cassettes, and *PW* parabolic dishes. We hope we'll see you there.

50MHz Licences to be Increased

The Department of Trade and Industry has asked the RSGB to make recommendations to them with regard to 60 additional stations taking part in 50MHz experimental work. Originally, 40 special research permits for Class A licenses were issued.

Those amateurs who have already submitted a full questionnaire to the Society's VHF Manager, need only confirm, in writing, that they wish to be reconsidered.

Questionnaires from new applicants must be with the Society by 31 March 1984. They are obtainable from RSGB Headquarters, marking the envelope "The Secretary—50MHz".

Completed questionnaires must then be sent to: *The VHF Manager, Keith Fisher G3WSN, RSGB, Alma House, Cranborne Road, Potters Bar, Hertfordshire EN6 3JW. Tel: (0707) 59015.*

Lowes Grows

Low Electronics, the Matlock based Trio main agents, are at it again, that is opening yet another branch, this time in the university town of Cambridge.

The new shop is located at *162 High Street, Chesterton, Cambridge, tel: (0223) 311230*, and will be opening at the beginning of April.

On Sunday 18 March, Lowes have booked the Trinity Suite in the Cambridge Post House Hotel at Lakeview, Bridge Road, Impington, Cambridge, between 2.00 and 4.30pm. The purpose of this will be to introduce both themselves and the Trio range of equipment to the local amateur population and any other interested parties—all are welcome.

The manager of the new shop, Tony Collet G4NBS, a lad who rises from that neck of the woods, will be there to welcome everyone and early arrivals will receive a glass of vino and the odd peanut. Additionally, Lowes will be running a station at the Post House using the callsign G8LOW and talk-in will be available on S22.

For further information, contact: *Low Electronics Ltd., Chesterfield Road, Matlock, Derbyshire DE4 5LE. Tel: (0629) 2817/2430/4057 and 4995.*

On the Move

Would readers please note that one of the suppliers of p.c.b.s for *Practical Wireless* projects has moved.

C. Bowes Electronics Ltd. is the company, and their new premises are at: *Unit 7, Kenwood Road, Reddish, Stockport, Cheshire SK5 6PH. Tel: 061-432 9434.*

Repeater Management Group—Open Meeting in Poole

Would all licensed amateurs, short-wave listeners or anyone who is interested in the UK repeater network, please note that *Practical Wireless* are sponsoring an Open Meeting with members of the RSGB Repeater Management Group (RMG), to be held in Poole.


All who are able to get to Poole on a Saturday afternoon, are very welcome to attend the meeting, which will be held at *The Mariner, West Quay Road, Poole, Dorset* on Saturday 10 March, between 1.30 and 5.00pm.

At the meeting, interested parties will learn of the very latest state in the development of UK repeaters, join in discussions and put questions to RMG officers.

PW staff will be running a talk-in station and listening for initial contacts through the Bournemouth located 144MHz repeater GB3SC on channel R1.

The Mariner has excellent luncheon facilities and a large comfortable licensed lounge bar, plus ample car parking space is available.

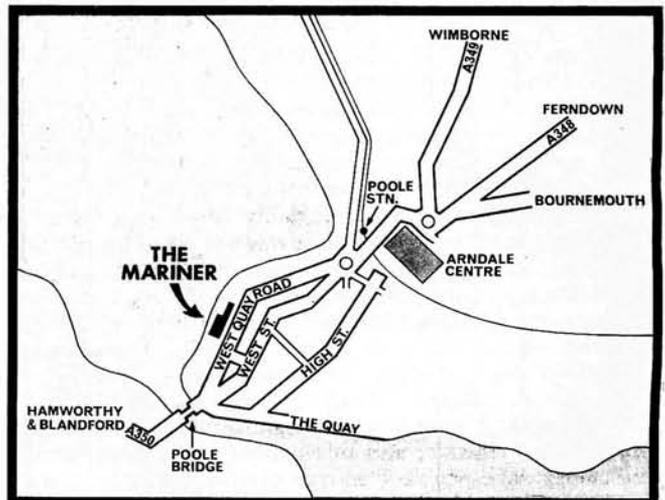We look forward to meeting all who are able to attend, but would ask you to bear in mind that the conference room must be vacated at 5.00pm, so the meeting will start promptly at 1.30pm.



The walk from the Station to the Mariner will take approximately 10 minutes

GaAs-f.e.t. PRE-AMP FOR 430MHz

by Sam Jewell G4DDK

The author's favourite band is undoubtedly 430MHz. This is reflected in the wide range of home constructed equipment he has produced since gaining an amateur radio licence, always with the constant objective of improving the performance of the home station. It was realised early in this process that a masthead pre-amplifier could give a marked improvement in receive sensitivity.

One problem was what device to use? An early attempt at a masthead pre-amplifier used a wideband design by DJ7VY which appeared in the German publication *VHF Communications*. This performed well at first but its great advantage of broadband operation soon became a disadvantage. A newly licensed G6+3 moved in just 50m away and began operating on 144MHz. The "DJ7VY" provides 17dB of broadband gain covering both 144 and 430MHz—the results when G6 . . . began operating were disastrous! Several attempts were made to add selectivity ahead of the pre-amplifier but the loss of the various filters tried just degraded the noise performance to the point where no advantage was gained in having a masthead pre-amplifier.

The answer lay in using a Gallium Arsenide f.e.t. with high Q , low loss input matching to give a degree of inherent selectivity. Conventional microwave GaAs-f.e.t. devices are relatively expensive and rather fragile and, since the author has an aversion to paying good money for something likely to be destroyed in an instant, they were avoided. Fortunately an alternative exists, the consumer dual-gate GaAs-f.e.t.

These devices were developed by the semiconductor industry as a low-cost solution to the problem of reducing the noise figure of TV tuners. Dual-gate GaAs-f.e.t.s are designed for operation up to approximately 900MHz. Because they operate at lower frequencies than their microwave counterparts they are able to use lower tolerance dimensions. This has resulted in low cost and less fragility—just what the author was looking for. The device chosen from those available was the Toshiba 3SK112 which is readily obtainable.

Pre-amplifier Design

The design of a pre-amplifier is largely dictated by its operating conditions. Unfortunately the data sheets for dual-gate GaAs-f.e.t.s do not usually give the optimum operating conditions for low-noise performance at 430MHz. Therefore it was necessary to extrapolate values from the available data and then confirm these values once the pre-amplifier was built. Table 1 gives the d.c. operating conditions for optimum low-noise performance of a 3SK112 at 430MHz.

Details of the input and output impedances are similarly not readily available, and this caused the greatest design difficulties. The problem was resolved by adopting wide-range matching circuitry from a conventional GaAs-f.e.t. amplifier and empirically determining the correct values for the 3SK112. The final circuit is shown in Fig. 1.

Circuit Description


The gate 1 bias voltage V_{G1S} is developed automatically by placing resistor R1 in the source circuit. This form of auto-bias will be familiar to anyone who has designed and built valve equipment. The value of R1 is derived as follows:

$$\begin{aligned} R1 &= \frac{V_{G1S}}{I_d} \\ &= \frac{1.75}{10^{-2}} \\ &= 175\Omega \end{aligned}$$

In practice the nearest preferred value of 180 Ω is used.

Gate 2-to-source voltage is set at zero by coupling the connections together through a 15k Ω resistor, R2.

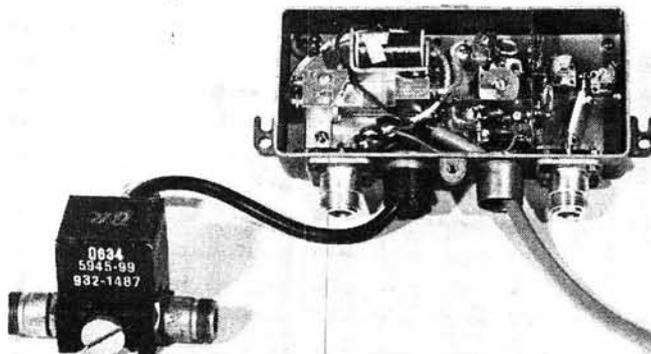The source and gate 2 leads must be thoroughly bypassed to ground at 430MHz and this is achieved by soldering the leads directly onto the leadless disc capacitors, C3 and C4. The actual value of capacitance of these two components is not too important, as long as it is




BUYING GUIDE

Air spaced trimmers C1/2, 5/6 (Type SC8/18/A3) can be obtained from Oxley Developments, Priory Park, Ulverston, Cumbria (Tel: 0229 52621). The approximate cost shown below is for the pre-amplifier only without relays and enclosure.


Approximate
Cost
£27

Construction
Rating
ADVANCED

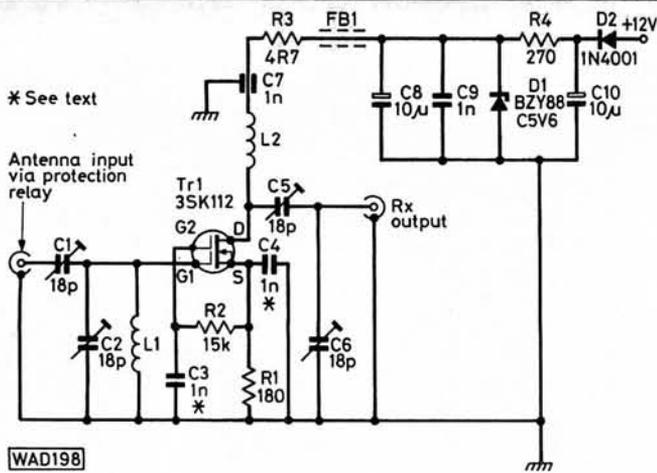


WAD198

Fig. 1: Circuit diagram of the 430MHz GaAs-f.e.t. pre-amplifier

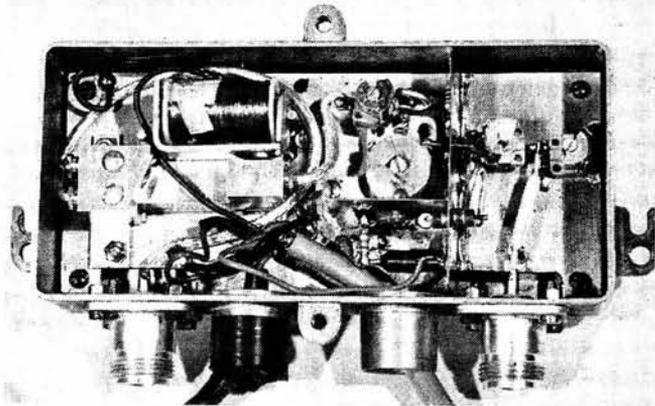

An internal view of the author's prototype pre-amplifier

Fig. 2: The final constructional arrangement of the pre-amplifier. Most components are mounted on or above the earthed ground plane. The drain of the GaAs-f.e.t. device, Tr1, passes to the output circuit through a 6 x 4mm rectangular hole cut through the vertical screen between the leadless disc capacitors C3/4. Resistor R2 is positioned under Tr1, across C3/4

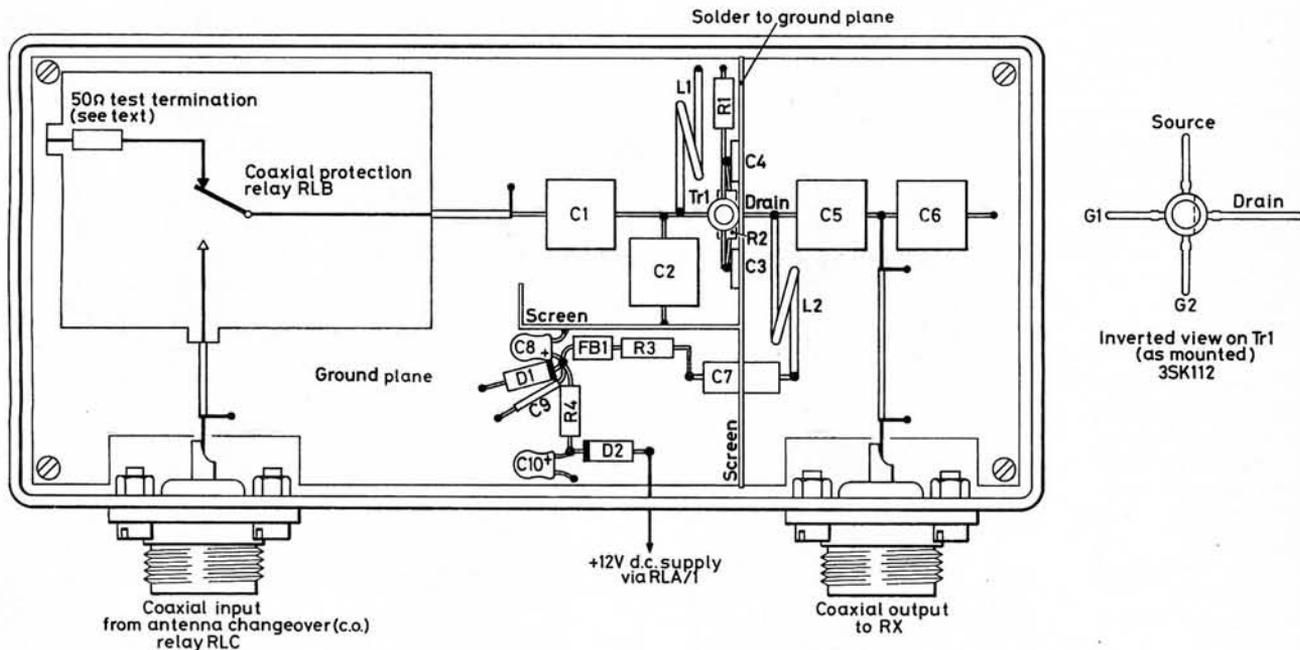

WRM003

within the range 220 to 1000pF. Of greater importance is their size, which means using slightly higher voltage components. Leadless disc capacitors are notorious for exploding when heated during soldering. The use of higher voltage devices will lessen the likelihood of this happening.

Very high Q (low loss) components must be used in the input matching circuit if lowest noise performance is required. Air-spaced, silver-plated trimmers and silver-plated copper wire **must** be used. Output matching is not so critical, but a silver-plated coil and capacitors were again used to ensure the lowest loss and highest gain.

Protection Relay

A protection relay is used to give extra isolation between the transmitter and pre-amplifier. If a good quality relay is available for the antenna changeover then the protection relay may not be necessary. Most relays

measured by the author gave less than 40dB crosstalk isolation between the transmitter and receiver. This means that with 100 watts output power more than 10mW would appear at the pre-amplifier input. At this level of input the GaAs-f.e.t. would be driven into compression and could over dissipate, with a consequent risk of self-destruction. A protection relay can provide over 20dB of extra isolation and virtually eliminate the problem.

A 50Ω non-inductive resistor may be connected to the receive port so that when transmitting the pre-amplifier input is correctly terminated, since this reduces the chances of self-oscillation. This resistor can also be useful as a built-in test if the protection is arranged such that it can be controlled separately from the main relay. By connecting the resistor to the input of the pre-amplifier, in place of the "cold" antenna, an increase in receiver noise output should be apparent. The difference in level will depend on what the antenna is "seeing" within its beam pattern.

If the antenna can see only "cold" sky an increase in the noise level of several dB can be expected when the pre-amplifier is connected to the resistor. A relay which shorts the receive port to ground whilst transmitting is obviously not suitable for this purpose, although it may be possible to remove the shorting contact by "tweaking" the receive lever spring of the relay. Great care should be exercised if this is to be attempted however.

Construction

No attempt has been made to produce a printed circuit board for the pre-amplifier as the design is better suited to the form of construction shown in Fig. 2.

Construction starts by cutting thin brass or copper sheet to form the screens. Suitably-sized holes are drilled in the screens to fit the GaAs-f.e.t. Tr1 and the feed-through capacitor C7 in the positions shown. Once the holes are drilled the leadless disc capacitors C3 and C4 should be soldered into place, as shown in Fig. 2. These capacitors must be located on the input side of the screen if complete stability is to be assured. The leadless discs are best fitted by tinning the part of the screen where they are to be located and then sliding the disc into place. Finally solder the disc into place by heating the screen from the reverse side. Wet tissue paper can be used to prevent the first disc from moving whilst the second one is being soldered into place.

Once the leadless discs are in position it is advisable to fit resistor R2 between them, as shown in Fig. 2; resistor R1 may also be fitted at this stage.

Next the screens should be soldered together and also soldered to the base plate. The base plate can be made of brass or copper sheet, or of copper-clad p.c.b. material. Its size will depend upon the box used to house the pre-amplifier. The author used a salvaged Belling Lee TV distribution amplifier box. This type of box has a rubber sealing gasket around the lid and two very convenient mounting lugs. Unfortunately no regular source of this type of box has been discovered, so it may be necessary to use an alternative, such as that sold by RS Components.

When the screens and base plate are assembled it is possible to solder into place the remaining components.

The input trimmer capacitor, C1, is supported at one end by the junction of C2 and L1. The other end of C1 is left floating and will eventually connect to the protection relay. The GaAs-f.e.t. should be mounted last and the correct orientation of the leads strictly observed.

When soldering any static-discharge-prone device such as the GaAs-f.e.t., certain precautions should be taken. It is wise to ensure that the soldering iron is at all times properly earthed and the author usually switches off the power to the iron whilst actually soldering the device into place. These types of GaAs-f.e.t.s are reasonably rugged, but there is no need to prove it!

A short length of ptfе coaxial line is used to connect the output trimmer to the output socket. The braid of this line should be connected to ground at both ends.

Power Supply and Control Unit

This unit would normally be situated in the shack in a convenient position, where the l.e.d.s can easily be seen. It contains a power supply for the pre-amplifier and a separate supply for the switching relays. A schematic diagram is shown in Fig. 3.

Desirable characteristics for any regulator used to power a masthead pre-amplifier are that it should produce a low noise output and be completely stable when connected to long supply leads. It is also desirable to have adjustable output volts to allow for voltage drop along the supply leads. Finally the regulator should be short-circuit proof, as it is all too easy to short the supply leads together when commissioning the new pre-amplifier. An LM317M adjustable regulator was chosen for the power supply and has given many months of reliable service without any problems.

Supervision of the control unit is provided by two l.e.d.s. Normally these are arranged to both be ON when receiving and OFF when transmitting. The l.e.d.s are connected across the supplies to the two changeover relays. A single switch on the control unit is used to release the protection relay in order to terminate the pre-amplifier input in 50Ω as discussed earlier. A press to talk (p.t.t.) connection needs to be made to the control unit from the

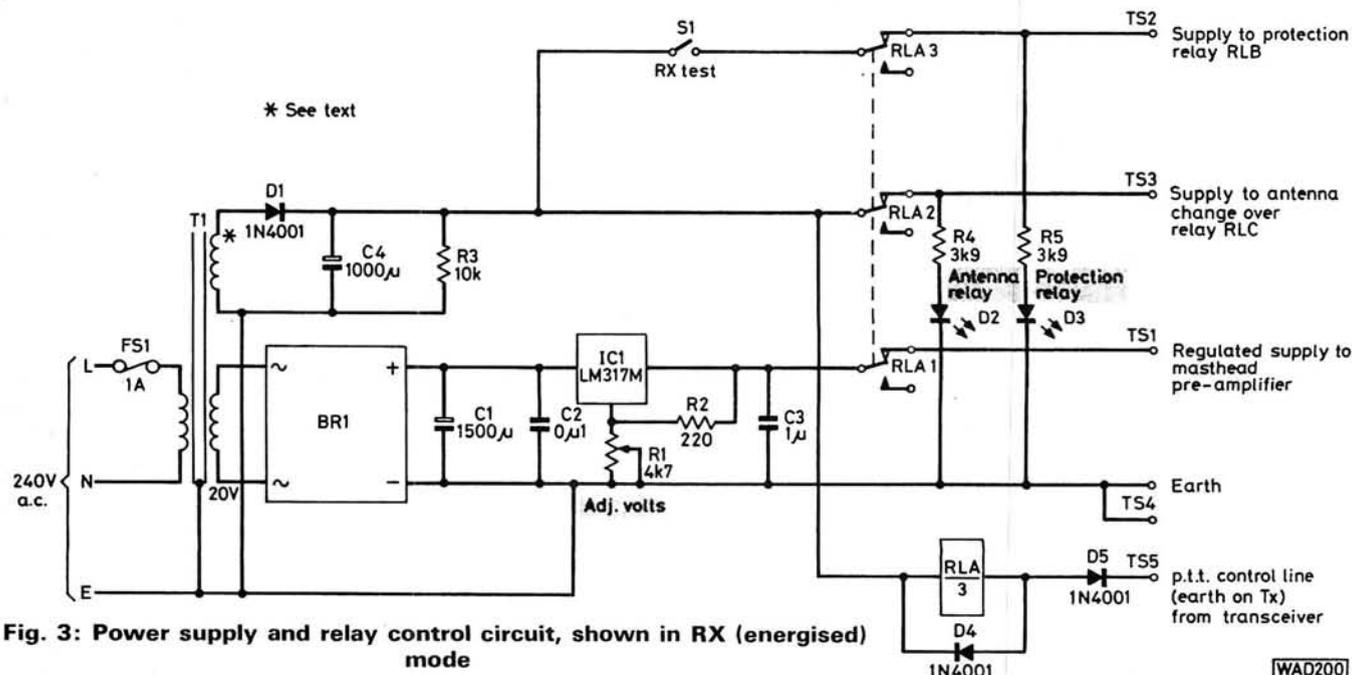


Fig. 3: Power supply and relay control circuit, shown in RX (energised) mode

WAD200

★ components

PRE-AMPLIFIER

Resistors

High stability carbon film $\frac{1}{4}W$ 5%

4.7 Ω	1	R3
180 Ω	1	R1
270 Ω	1	R4
15k Ω	1	R2

Capacitors

Silver plated air-spaced trimmer

18pF	4	C1,2,5,6 (see buying guide)
------	---	-----------------------------

Leadless ceramic disc

1nF	2	C3,4
-----	---	------

Ceramic feedthrough

1nF	1	C7
-----	---	----

Tantalum bead

10 μ F 16V	2	C8,10
----------------	---	-------

Ceramic plate

1nF	1	C9
-----	---	----

Semiconductors

Diodes

1N4001	1	D2
BZY88 C5V6	1	D1

Transistors

3SK112	1	Tr1
--------	---	-----

Miscellaneous

Silver plated copper wire 1.6mm diameter; Ferrite bead FX1115 (1); Weatherproof enclosure (see text); N type chassis sockets (2)

POWER SUPPLY/CONTROL UNIT

Resistors

Carbon film $\frac{1}{4}W$ 5%

220 Ω	1	R2
3.9k Ω	2	R4,5
10k Ω	1	R3

Potentiometers

Min. horizontal preset

4.7k Ω	1	R1
---------------	---	----

Capacitors

Tantalum bead

0.1 μ F 35V	1	C2
1 μ F 35V	1	C3

Electrolytic (axial)

1000 μ F 35V	1	C4
1500 μ F 35V	1	C1

Semiconductors

Diodes

1N4001	3	D1,4,5
1A 50V p.i.v. bridge	1	BR1
Red l.e.d.	2	D2,3

Integrated circuits

LM317M	1	IC1
--------	---	-----

Miscellaneous

Mains transformer (see text); 20mm fuse holder with 1A anti-surge fuse; s.p. switch, S1; 4 pole c.o. relay (Continental series or equiv.) RLA; Coaxial c.o. relay (RS349-686 or equiv.) RLB; Coaxial c.o. relay (CX520D or equiv.) RLC; Mounting box.

transceiver. This "hard wired" connection controls relay changeover.

It should be noted that the masthead relays are both arranged to be operated (energised) whilst on receive. Should the pre-amplifier fail this does allow the transmit feeder to be used for normal operation until the fault can be dealt with.

The power unit supplies the operate voltages for these relays and the choice of transformer will be dictated by the types of relays that the constructor is able to obtain. Most surplus relays seem to have 24-28 volt d.c. operate coils. Details of interconnections between the control unit and the masthead unit are shown in Fig. 4.

Control Unit Construction

The power supply and control unit is built into a vinyl-clad steel enclosure approximately 75mm square by 150mm deep. Again no p.c.b. is used as the majority of the components are large, and therefore better mounted directly to the box itself.

No mains ON/OFF switch is provided, therefore the unit is ON as soon as it is plugged into a mains socket outlet. A 1 amp anti-surge fuse is fitted for protection.

Alignment

Pre-amplifiers are always difficult to align properly unless an automatic noise-figure meter is available. Assuming such equipment is not to hand, the most popular method of tuning is to listen to a distant signal of reasonably constant strength, such as that from a beacon.

The output circuit is first tuned for maximum signal strength followed by the input circuit for the largest signal to noise ratio.


Using this method it can be very difficult to convince yourself that an improvement in signal to noise ratio has actually been made. The adjustments are not made any easier by the vagaries of propagation.

For those enthusiasts who build more than the occasional pre-amplifier the answer is to build an alignment aid, such as the excellent device described by G4COM in the January 1976 issue of *Radio Communication*. The alignment aid is a simplified noise figure meter and although it does not indicate absolute noise figures, it does indicate any improvement in signal to noise ratio. If alignment of the pre-amplifier is carried out carefully, and everything is working as it should, then the pre-amplifier will not be far off optimum and even a professional noise-figure meter would not enable you to improve the results.

Fitting the Masthead Unit

Probably the biggest deterrent to fitting a masthead pre-amplifier is the problem of weatherproofing. If the pre-amplifier is housed in a properly sealed box, such as the previously mentioned RS Components box, and care is taken to ensure all leads and sockets connected to the box are properly sealed, then few problems should be encountered.

The arrangement used by the author for mounting the prototype system is shown in Fig. 5. A separate box is used to enclose the antenna changeover relay and this may seem unnecessary, but there is good reason for this. If a single larger box was used to house the pre-amplifier and

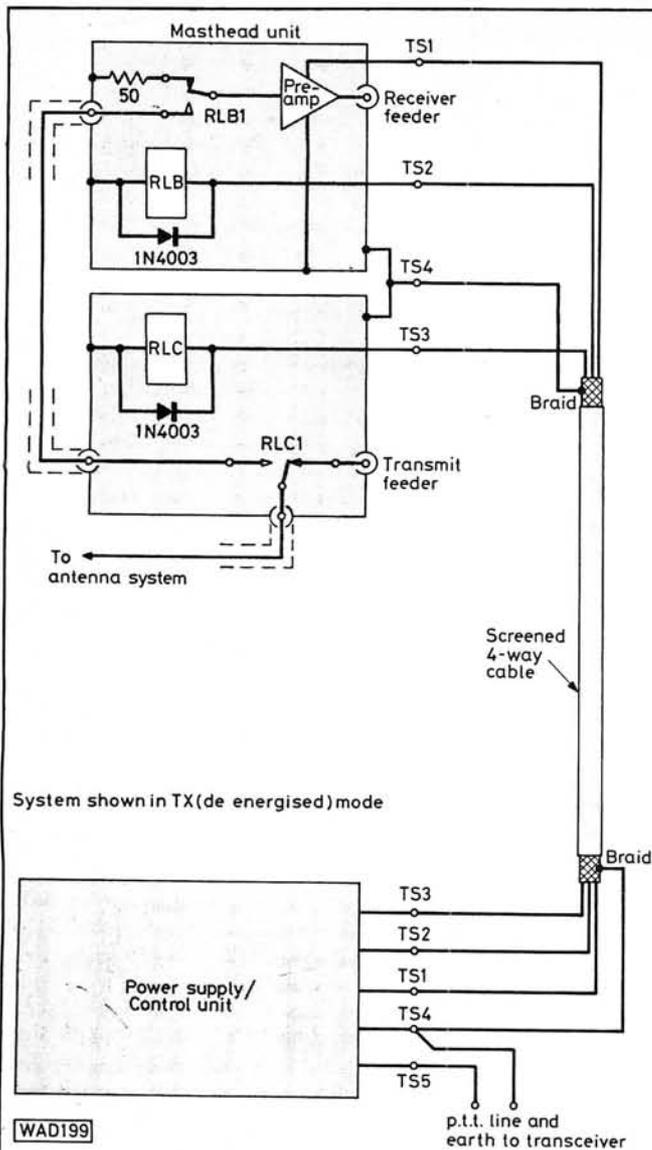

WAD199

Fig. 4: System interconnections and relay control arrangements of the masthead pre-amplifier

both relays then the ultimate isolation between the antenna and pre-amplifier during transmit conditions would not be realised, due to crosstalk between the two relays. For low transmit power levels it may not be too important, but should be seriously considered if you are contemplating using high power.

Four-way screened lead is used to connect the masthead unit to the power supply and control box. The braid of this cable should be earthed at both ends of the run to maintain screen integrity. Using screened cable helps to prevent unwanted pick-up of noise and r.f. if the cable run happens to be close to other antennas.

Table 1

Parameter	Value
Drain Source Voltage V_{DS}	5V
Gate 1 Source Volts V_{G1S}	-1.75V
Gate 2 Source Volts V_{G2S}	0V
Drain Current I_D	10mA
Operating Parameters for 3SK112 at 430MHz	

WAD201

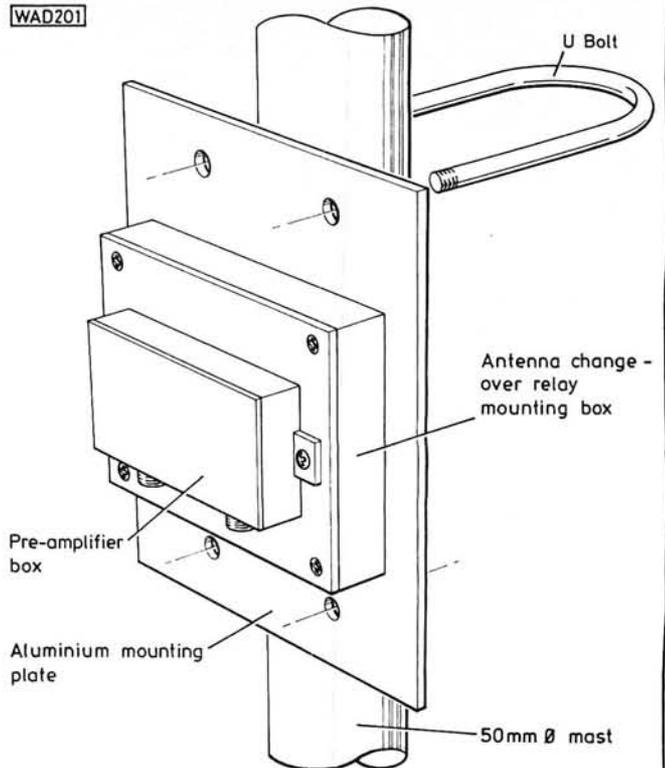


Fig. 5: Masthead mounting arrangements adopted by the author. For increased isolation on TX the antenna C/O relay RLC is fitted inside a separate weatherproof enclosure

Results

Within days of installation of the prototype masthead pre-amplifier system a widespread tropospheric opening occurred. During the opening much DX was worked from the author's Midlands QTH. What was unusual was that many of the stations worked were running only 5 or 10 watts output and were received at signal strengths of only a few dB above noise. It is certain that they would have been inaudible without the extra performance of the GaAs-f.e.t.



Solar noise runs consistently at 3dB over "cold" sky using two 4-2λ long Yagis. When the transmit feeder is used to connect directly into the receive converter no solar noise is detectable at all.

The pre-amplifier has survived severe icing, one of the wettest Springs on record, and several weeks of British Summer heat-wave!

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISERS**

PHOTO ACOUSTICS LTD.

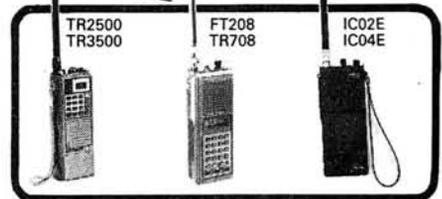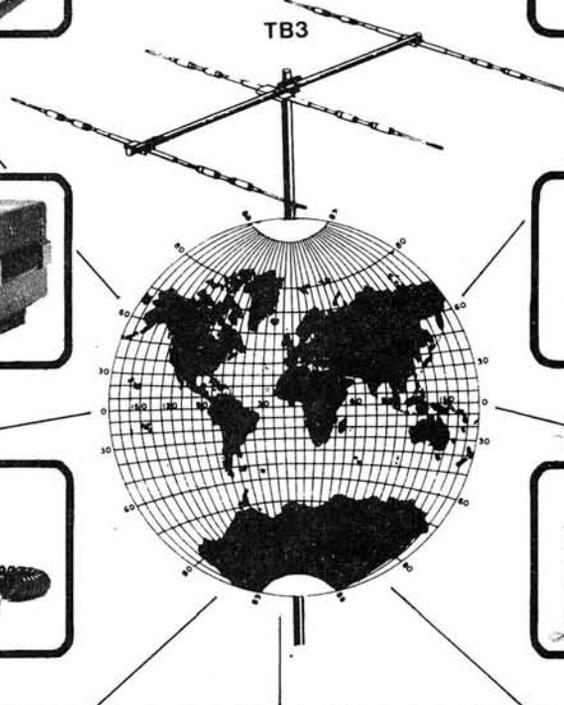58 HIGH STREET, NEWPORT PAGNELL, BUCKS, MK16 8AQ Tel: 0908 610625



We also stock a comprehensive range of products from:

- YAESU — TRIO — ICOM — FDK
- TASC0 — WELZ — MUTEK —
- ADONIS — DIAMOND
- HALBAR — SATELLITE DISHES
- BENCHER — DRAE — BNOS —
- DAIWA — DATONG — TONNA —
- JAYBEAM — MICROWAVE
- MODULES — RSGB & ARRL
- PUBLICATIONS — REVCO

ORGANISE YOUR STATION

Eliminate clutter and provide lots of space for everything you need.

FEATURES:

- Angled rear shelf
- Easy assembled flat pack
- Wood Grain finish
- Width 3' by 2'5" depth
- height 4'2"




SPEND UP TO £1,200 INSTANTLY WITH A PHOTO ACOUSTICS LTD. CREDIT CHARGE CARD — APPLY FOR DETAILS PART EXCHANGE WELCOME, ASK FOR KERRY OR DEREK



Monday-Friday 9.30-5.30 — Saturday 9.30-5.00



The Plug says 'No' to dirty power.

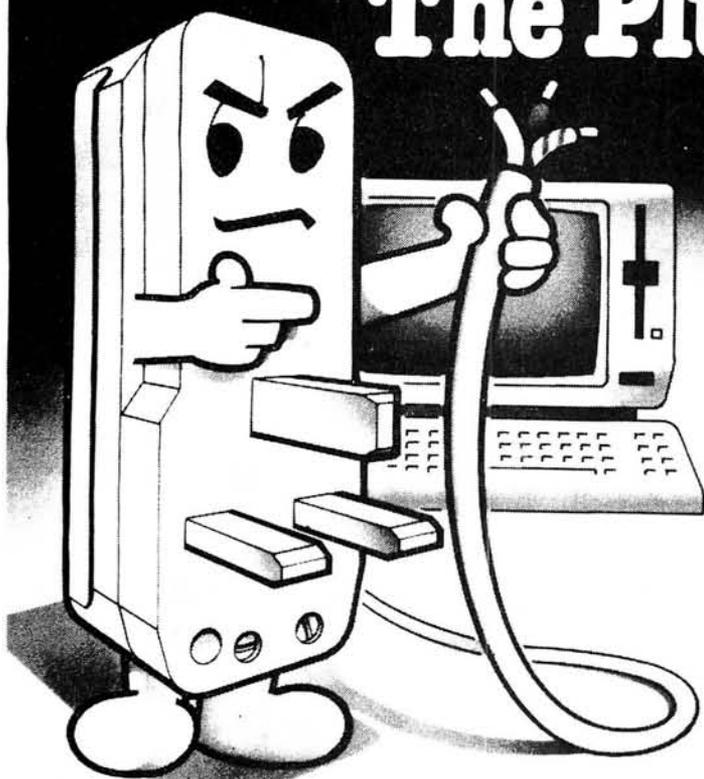

WARNING: Unfiltered power can damage your computer's health.


WHY

Because dirty power is the most likely cause of the unexplained errors and circuit malfunctions which can upset all micro based products and their users.

HOW

The Plug with its own built in filter and transient suppressor reduces the effect of electrical noise and spikes and increases the reliability of both hardware and software.

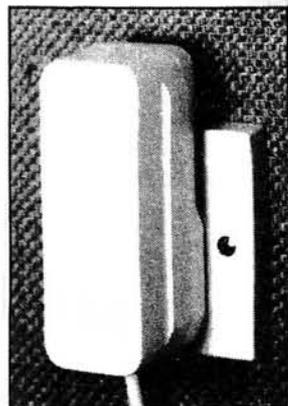Protect your computer from unnecessary power problems, say 'No' to dirty power.



R.R.P. £15.50 including p.p.
Dealer enquiries welcome

The Plug is available from dealers or direct from the manufacturer

FOR FURTHER INFORMATION CONTACT:

Power International Limited 2A Isambard Brunel Road,
Portsmouth, Hampshire. PO1 2DU. Tel. (0705) 756715

THE INTERNATIONAL VHF-FM GUIDE

Sixth Edition — 128 Pages.

A unique source of information for anyone who works through
VHF REPEATERS IN U.K. & ABROAD

Maps of coverage areas and locations of all UK VHF amateur repeaters together with full details of callsigns, channels, access and reaccess requirements, talk-through times, QTH locators etc. In fact everything you need to know to work through every repeater in the UK with confidence.

The overseas section covers most of Europe/Scandinavia plus S. Africa & Australasia with country by country maps showing repeater locations keyed to full listings of callsigns, channels, locators, powers etc.

Anyone planning to operate abroad will find the

RECIPROCAL LICENSING INFORMATION for 35 countries

to be invaluable. In what is undoubtedly the most comprehensive and up-to-date publication of its type in the world, we have collected addresses of licensing authorities, with details of the advance notice, payments and info that they each require to issue you with a licence to operate on your holiday or business trip.

The book also includes charts of FM repeater and simplex channel frequencies, 10 metre, 6 metre and VHF & UHF beacons and a wealth of other useful information.

Now in its tenth year of publication the GUIDE has received world-wide acclaim and is perhaps the best value for money of any book published by and for Radio Amateurs.

Available from many Amateur Radio dealers or by post at £2 + 30p p&p direct from the publisher:

J. Baldwin G3UHK
41, Castle Drive,
Maidenhead,
Berks. SL6 6DB
NATIONAL GIRO No. 22 442 4009

Silver 70 ANTENNA

Superb 70cms band aerial still at only £31.95

For the discerning DX man who wants only maximum performance!

Tiger LY6	£15.95
Tiger LY8	£20.95
Tiger LY10	£32.95

Plus £5.00 Securicor delivery

Excellent range of two meter antennae



GREAT VALUE FOR MONEY!
Send cheque or money order TODAY

Ant Products

Trade enquiries invited

All Saints Industrial Estate Baghill Lane
Pontefract West Yorkshire

Telephone: (0977) 700949

Swap Spot

Have UK101 computer with manuals, value £80, signal generator a.m./f.m., 350kHz–20MHz in 5 bands with wobblator output, TCS12 receiver, B41 v.l.f. receiver. Would exchange for 144MHz gear, HRO coilpacks, Heathkit Mohican info w.h.y. Jim G6ETV. Tel: Kidderminster 3674. *U514*

Have Trio 2200GX mobile/portable 144MHz TX/RX, NiCads, charger, rubber duck, mobile bracket, carry-case. Would exchange for Sony ICF2001. Keith. Tel: 0543 376366 (West Midlands) at weekends. *U515*

Have brand new 25 watt W & D linear and mobile mount for FT-290, gutter mount 7/8 Oscar. Would exchange for working 430MHz 3 or 4-channel set, i.e. Palm IV. R. Goodge, 29 Adamson Court, Broadfield, Crawley, West Sussex. Tel: 0293 25032. *U520*

Have 500pF four-gang variable capacitor. Would exchange for reel-to-reel tape recorder in working order. Chris Aubrey. Tel: 01-370 3992. *U522*

Have an IC $\frac{1}{8}$ scale model stock car, never races, with a Futaba radio system. Would exchange for TR-2500 or similar 144MHz portable hand held or w.h.y. Tel: 0223 862666 (Cambridge). *U528*

Have CB radios, 1 JWR and 1 Tandy hand held TCR 1001. Recent RAE. Struggling with Morse (have Datong will travel). W.h.y? Reg. Tel: 0943 609551 (Ilkley). *U529*

Have Video Genie 1 16K computer. Would exchange for FRG-7000 or FRG-7. W. E. Gates, 16 High Mill Drive, Scarborough. Tel: 0723 365093. *U532*

Have Realistic 140kHz to 30MHz DX 100 L receiver plus Binatone 12 channel hand held CB. Both as new. Would exchange for small dual beam oscilloscope. T. Nolan. Tel: Chester 313857. *U533*

Have Transcom GBX4000 CB radio complete with many accessories. Would exchange for ZX Spectrum 48K or similar computer. Or 144MHz hand held (prefer IC-2E). Peter. Tel: Romford 46538. *U535*

Have MMT144/432R transverter 1-6 shift, 10W out. Standard attenuator plus 7dB attenuator. Would exchange for 144MHz portable or something interesting. Tel: 01-446 4932 (evenings). *U543*

Have Eddystone 730 communications receiver, value £120. Would exchange for good oscilloscope. Can deliver Lancashire or Cheshire area. W. E. Moore, 18 Brunswick Terrace, Stacksteads, Bacup. Tel: Bacup 874928 (7 p.m.) *U563*

Have a 144MHz f.m. full range hand held 1 and 5 watt transceiver including charger. Would exchange for 48K Spectrum Mark III or dual beam oscilloscope. M. Ellis, 13 Dilworth Close, Summit, Heywood. *U566*

Have Racal diversity unit, CB Persuader speech processor, medals, large collection military models 1/96 scale die cast, two h.d. 12V 125Ahr batteries (new). Would exchange for EX W.D. receivers working or not. Can collect. Tel: 0908 314095 (3 p.m.) (Milton Keynes). *U573*

Have Sony ICF 6800W general coverage receiver f.m.—m.w., 29 s.w. bands, s.s.b. s.w. frequency counter, digital readout in good working order. Value approximately £225. Would exchange for VHS video recorder. Mr. Gordon, 24 Stanley Road, Poole, Tel: Poole 686521. *U579*

Have Seagull Sentry 40+ outboard motor. Has had only four hours use from new. Would exchange for IC-2E plus accessories or consider other hand helds. G6XJB. Tel: Waterlooville (Hants.) 4587 (evenings). *U583*

Have AR 88D receiver in perfect working order. Would exchange for good three row button key accordion. R. MacMaster, Shielbridge, Acharacle, Argyll. *U584*

Have parts for H.F. valve linear; valves (813, 805, T100, TZ40) and bases, capacitors (fixed/variable), coils, switches, meters, transformers, and chokes. Would exchange for HRO, Heathkit/USA transceiver, good or faulty, or w.h.y. G4KWL. Tel: 0734 871330 (Reading). *U585*

Have Kodak Carousel S-AV slide projector, good condition with case. Would exchange for 144MHz rig. Full details to Peter G6UMG, 252 Wilson Ave., Rochester, Kent. *U586*

Have Krokus 35 photographic enlarger with lens and trays. Would exchange for 8–10dB 144MHz Yagi beam with mast fittings. C. Gurney. Tel: Rochdale 41462 (evenings). *U587*

Have LCL 40 channel f.m. CB transceiver, s.w.r./power meter, whip antenna, antenna matcher, no p.s.u. Would exchange for ZX81 plus 16K RAM and etc., or amateur gear. W.h.y. Mr. McConnell, 415 Charter Ave., Coventry. *U588*

Have Icom IC-451E 432MHz multimode base station in very good condition. Original packing, all leads etc. Would exchange for Icom R70 or Trio R2000 receiver. Ian. Tel: 0509 502989 after 6 p.m. (Shepshed, Leics.) *U599*

Have TR9000 144MHz multimode, power supply adjustable to 30 volts, microwave modules MML 144/100–5 10 watt in 100 watt out 144MHz linear. Would exchange for FT-221 in very good condition. W.h.y? Tim. Tel: 0795 75093 evenings and weekends (Sittingbourne). *U600*

Have Sony TC-651 reel to reel stereo tape recorder. Logic control, auto reverse, echo, dubbing and mixing facilities. In immaculate condition and including tapes and accessories. Would exchange for modern h.f. transceiver or separates. D. Andrews G4NNP. Tel: 0271 65522 (North Devon). *U601*

Have professional 32K add-on memory for Pet computer. Would exchange for anything 430MHz or TV related. P. Saul. Tel: Worcester 0327-51716. *U614*

Have Nikon EM Camera f1.8 as new. Would exchange for modern communications receiver or scanning monitor. Also have pair Goodmans twinaxioms and monitor audio micromonitor loudspeakers. W.h.y? Mr. Michaels. Tel: Watford 33034 (Room U). *U615*

PW "SWAP SPOT"

Got a camera, want a receiver? Got a v.h.f. rig, want some h.f. gear to go with your new G4? In fact, have you got anything to trade radio-wise?

If so, why not advertise it FREE in our new feature SWAP SPOT. Send details, including what equipment you're looking for, to "SWAP SPOT", *Practical Wireless*, Westover House, West Quay Road, Poole, Dorset BH15 1JG, for inclusion in the first available issue of the magazine.

A FEW SIMPLE RULES: Your ad. should follow the format of those appearing above; it must be typed or written in block letters; it must be not more than 40 words long including name and address/telephone number. Swaps only—no items for sale—and one of the items MUST be radio related. Adverts for ILLEGAL CB equipment will not be accepted.



Midlands VHF Convention

This year's Midlands VHF Convention was held on Saturday, October 15 at the British Telecom Training College, Stone. The change from the previous venue at Wolverhampton Polytechnic was generally welcomed, particularly in view of the ample free on-site parking. The organisers had hoped that visitors might have set up demonstrations in the car park, unfortunately typical v.h.f. contest weather (horizontal rain) sent everyone scurrying for the warmth and comfort of the tea lounge.

A convention is very different from a rally with emphasis being placed on comfortable surroundings, really good catering and the social and technical aspects of the hobby to the virtual exclusion of the frantic commercial flavour of most amateur gatherings.

Throughout the afternoon the measurements area was busy measuring the special characteristics of numerous transceivers up to 10GHz, a considerable quantity of test equipment having been made available by the British Telecom Training College. By far the most popular measurement was sensitivity of 144 and 430MHz handheld f.m. equipment.

Two microwave enthusiasts tested out their 10GHz narrowband systems and were able to see their output spectrum. Several wideband 10GHz systems were also tested and a problem of stability was observed. One intrepid builder brought along a 133MHz v.f.o., for use with a homebrew 144MHz rig, to be aligned and measured.

After the interest shown in the f.m. sensitivity tests it would appear possible to stage a contest for "best on the day" f.m. receiver sensitivity. This would give far less trouble than the previously attempted noise figure contest.

As well as a few select trade stands there was a well stocked bookstall and a busy bring and buy stall. The large and comfortable social area included an exhibition of maps, charts, and other matters of radio interest. After the afternoon lecture session, the evening was rounded off with a buffet and evening bar accompanied by musical

entertainment from the South Manchester Radio Club.

The afternoon lecture session was opened by Keith Fisher G3WSN, the RSGB's VHF Manager. He also reported hopes for extended 50MHz operation in the near future including the involvement of Class B licence holders in cross-band operations and the use of c.w. by Class B licence holders in the context of normal telephony QSOs.

He noted the vast quantity of information and reports received about the use of 50MHz. He also said that the 144-875MHz frequency in the beacon sub-band should have been vacated by RAYNET by January 1984, the traffic on this frequency moving to 144-775MHz. RAYNET use of 144-850MHz would continue for the time being. He was less happy about the future of the 430MHz band, the secondary status of the band in the UK and the Syledis problem were particularly worrying. There were various proposals to be discussed at the IARU Region 1 1984 conference to reorganise the 430-435MHz band plan including putting the high-power DX stations near 435MHz. He felt that the implementation of this proposal in the UK could result in us losing 432-433MHz, and reported that the RSGB, in conjunction with the Danish society, EDR, were preparing a paper on the problems of 430MHz. All comments and suggestions would be welcomed and should be forwarded via G3ZNU, the VHF Committee chairman.

The first speaker was Brian Bower G3COJ, who described his experience of 50MHz operation and the history of the band in the UK. He started by recounting the details of a few pre-war transatlantic 5m loggings.

The 1947 WARC found most European societies defunct so the 50MHz allocation was lost in Region 1. However, there was some activity during the 1947 sunspot maximum, permits being generally available. Much of it featured MD5KW (Egypt) who, as G5KW, was sitting in the front row. The first UK transatlantic QSO was recorded in November 1947. By the 1956 sunspot maximum



Keith Fisher G3WSN, introduces
Tony Whittaker G3RKL



Testing microwave gear in the
Measurement Area



The Bring and Buy stand was
popular throughout the day

Practical Wireless, April 1984

Band I TV was very well established and only one UK station had a 50MHz permit. There was much cross-band working and American stations worked all continents.

Brian noted the considerable variety of anomalous propagation modes likely to be encountered on 50MHz. These include conventional v.h.f./u.h.f. troposcatter, meteor scatter, aurora and ionospheric modes including F-layer reflection and single and multi-hop sporadic E-layer reflection.

In 1977 it became clear that Band I TV was declining and hope was raised that some permits might be obtained for the forthcoming (cycle 21) sunspot maximum. After some administrative hiccups, near disasters and false starts 40 permits for operation outside TV hours were issued in response to 200 applications for use from 1 February, 1983.

Brian explained how to get started on 50MHz. All that is necessary is a dipole, a converter and some form of talk-back. The most popular time seems to be 0700 to 0830 and there is an active UK 50MHz group with G4JCC, QTHR, as Secretary. It was reported that the final close down of Band I TV was scheduled for 2 January, 1985.

After a brief interval allowing everybody to stretch their legs and get a cup of tea, Tony Whittaker G3RKL, took the stand to describe the GB3SF experimental pilot s.s.b. repeater project. Tony explained that he was not professionally involved in radio and went to some trouble to correct the common misapprehension that GB3SF was to be a linear repeater when it was actually intended to be a single-channel voice repeater. Tony reported that GB3SF was now licensed but unlikely to be operational for some time since it was being built as a student project.

Tony had gone to considerable effort to analyse the channel usage and geographical spacing of existing v.h.f. and u.h.f. repeaters finding 62 144MHz f.m. repeaters equally distributed among eight 25kHz channels and 104 u.h.f. repeaters on nine channels with comparatively low occupancy of the recently designated odd numbered channels. There is considerable geographical overlap on some channels, the average separation between co-channel repeaters on 144MHz being about 150km and on 430MHz about 95km. An "average" 144MHz repeater had its antennas at 250m above sea level which gives a line of sight range of about 55km to a station at sea level and 75km to a station at an altitude of 30m. Tony suggested that an idealised network would have co-channel repeaters every 150km so the 30m a.s.l. station would experience considerable areas of overlap. Tony produced many more charts and statistics to underline his contention that there is a significant need for more repeater channels.

The obvious solution, Tony explained, seems to be to use s.s.b. and an easily realisable 5kHz channel spacing; this would give 40 channels rather than eight in a 400kHz sub-band allowing v.h.f. repeaters to be much more closely spaced without overlap problems. Using this system the country could be covered with a network having only 2 or 3 repeaters per channel.

Tony then outlined the design principles of GB3SF which will have an input frequency of 145.185MHz and an output frequency of 145.785MHz.

After a detailed discussion of the GB3SF frequency plan Tony went on to describe the construction of the 100dB isolation tuned coaxial cavity filters needed for the repeater, showing photographs of these. They provide an attenuation notch of almost 120dB with an insertion loss of some 2-3dB.

Peter Chadwick G3RZP, made a welcome return to give the third lecture on the subject of amplifiers. Peter is well known for his forthright exposition of the home truths associated with many aspects of radio. The purpose of amplifiers, he said, was to make things bigger. An am-

plifier consisted of a supply, a load and an input control, but even this simple model must run into linearity problems and saturated at some power level.

Peter illustrated his lecture with several fascinating slides, some of which showed actual amplifiers.

The final formal part of the convention was a v.h.f. forum with a panel comprising Jack Hum G5UM, Tom Douglas G3BA, Brian Bower G3COJ, and Keith Fisher G3WSN. This was an opportunity for all those present to raise any v.h.f. topic of interest and get the panel's reactions and thoughts. It was also a useful opportunity for the panel members to discover what topics were of particular concern to the v.h.f. community.

It was clear that the use of the 430MHz band was a very sensitive topic. In spite of this there was much informal encouragement of the use of the 430MHz band both from the panel and from the floor. The possibility of IARU societies agreeing to trade some of the width of some of the u.h.f. and microwave bands for protected, primary status, narrower bands was commented on by panel members, as was IARU concern about the increasing incompatibility of national u.h.f. and microwave allocations.

Much discussion centred around band planning and novice licences. A suggestion that 20kHz f.m. channel spacing be adopted instead of the current 25kHz spacing received very little support. RTTY calling arrangements centred around 145.3MHz were discussed and it seemed that most of the problems arose from the channelised mentality of operators in that part of the 144MHz band.

There seemed to be little real support for the perennially discussed novice licence, the American style novice licence involving limited c.w. only with access to small parts of the h.f. bands would be welcome but a novice licence allowing use of commercial v.h.f. phone equipment would not get much support. The panel expressed hopes that a regular UK 50MHz allocation for Class A and Class B licence holders would be forthcoming by 1986.

Some concern was expressed about the abuse of the UK band plan, particularly by newly licensed operators on the 144MHz band. Several panellists expressed the opinion that, whilst some of the abuse was deliberate, most of it was due to ignorance. It was felt that the incorporation of the band plans into the licence would be a bad thing; however, suggestions to provide information sheets to new licence holders were being actively pursued and a suggestion that band planning be incorporated in the RAE was welcomed and noted for further investigation.

The panel outlined the background to the extraordinary situation which had overtaken their Belgian colleagues, many aspects of this only serving to underline the importance of a strong national amateur radio society enjoying the support of the majority of the country's licensed amateurs and a good working relationship with the licence issuing authority. ●

Kindly Note

PW Dart, November 1983

Diode D2 in the circuit diagram, Fig. 1, should be an 8.2V Zener diode BZY88. Also capacitor C3, 1nF, should be inserted into the line joining the top ends of C2 and C4.

UPGRADING THE DX 160

by Charles Molloy


The Realistic DX160 communications receiver was for several years available from Tandy in the UK and Radio Shack in the United States. There are still quite a few in use according to a recent survey reported in *DX Party Line* from HCJB (Voice of the Andes) and they can be picked up secondhand for quite a modest sum. This set has five bands. One from 150kHz to 400kHz includes long-wave broadcasting and navigation beacons while four others give continuous coverage from 535kHz to 30MHz. In addition to features one would expect, such as bandspread, antenna trimmer, r.f. gain control, noise limiter, S-meter, and product detector, there are also facilities one would normally find only in a more expensive set. There is amplified a.g.c., a front panel a.g.c. time constant switch with fast and slow action, a socket and plug for standby operation and the "front end" uses f.e.t.s.

The DX160 is a rather interesting, well-made set, attractive in appearance, easy to use and probably underrated performance wise. It operates either from the mains or 12 volts d.c., the latter feature attracting it to the writer who was looking for a receiver for use in a caravan and boat. Rather than leave it idle during the winter it was decided to try to hot it up so that it could be used as a second receiver for DXing. The only constraint was that it should be easy to restore it to its original state. This was imposed, not so much to maintain any resale value as to ensure that the set was still fit for mobile use the following season. Drilling holes or making changes to the printed circuit wiring, was out.

Digital Readout

Once you have used digital readout you cannot do without it. Tuning round the bands is so easy. As an Honest Frequency Meter model FC5M was in use with another receiver, a coaxial socket was fitted to the rear of the DX160 so that the FC5M could be plugged into this set as well.

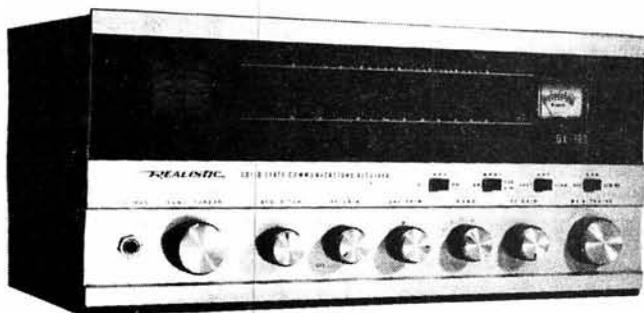In principle it should be easy to connect up an external digital readout. All you have to do is to tap onto the



The Realistic DX160

receiver's local oscillator. Provided the frequency meter has the correct offset, i.e. it will subtract the value of the i.f., the correct frequency will be displayed. The problem is how to do it without upsetting the local oscillator. A small amplifier acting as a buffer would certainly solve the problem but it is possible to manage without one. Tap a fixed capacitor onto the junction of C12, R32 and the drain of Q8, a convenient soldering point being at C12 (Fig. 1). C12 is located on the main p.c.b. which is on the left hand side of the set as viewed above from the front. It is signwritten on the top side of the board. The other end of the new capacitor goes to a coaxial socket fitted in place of the EXT STD BY socket at the rear. The wires from the latter are tied back and insulated from each other so that

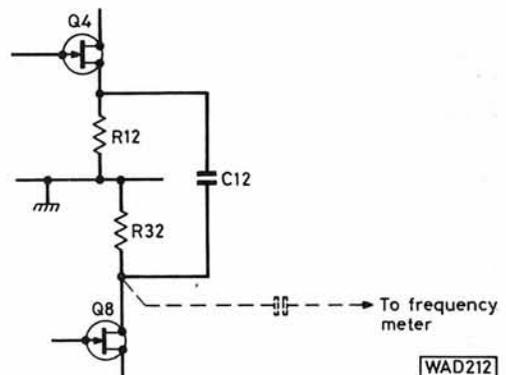


Fig. 1: DX160 digital readout

the external standby facility can be restored in future. The type of coaxial socket that stands proud will fit into the space available, even the holes for the self tappers line up.

A 10pF fixed capacitor was used but the value may have to be found by trial and error if another frequency meter is used. It is a compromise between providing sufficient voltage at the lowest frequency and causing the least disturbance at the highest. A value of 33pF gave a good steady reading with the set tuned to 150kHz but detuned it by 7kHz and weakened the signal slightly on the 26MHz band, 4.7pF gave an unstable reading on the long waves.

Band E

On this band (13MHz to 30MHz) the frequency displayed was 910kHz lower than it should have been. This value is double the i.f. (455kHz) and occurs because the local oscillator is adjusted to a frequency lower than the signal. On the other four bands the oscillator is higher than the incoming signal. This is not such a disaster as might at

Practical Wireless, April 1984

first appear. Subtract 90kHz and the last three digits of the display will be correct. If you want to set up on a particular channel there is always the pocket calculator to fall back on.

An examination of the circuit showed that while pad- ders (C37, C39, C40, C41) were in use for bands A to D, there was none for band E so the oscillator could just as easily be set above as below the signal frequency. It turned out to be a simple job to make the changeover. Since the tracking points were unknown it was assumed they would be 14MHz and 28MHz. Set the pointer to 28MHz and make a note of the actual reading on the digital display (not what it should be). Add 910kHz and call this f1. Now set the pointer to 14MHz, add 910 to the figure displayed and call this f2. Adjust the reading on the display to f2 using a non-magnetic trimming tool on the core of T15. Now set the pointer to 28MHz and adjust trimmer CT10 until f1 is displayed. Go back to 14MHz and readjust T15 and come back to 28MHz for a final touch on CT10. A 10pF capacitor bridged across CT10 will extend its range if necessary, the most convenient place to fit one being on the oscillator section of the wavechange switch, from the tag with the black wire to chassis.

If the mod is done this way there should be no need to re-align the r.f. circuits. If a signal generator is available then check the alignment and while you are at it check bands A to D as well.

Selectivity


According to the users' handbook the bandwidth of the DX160 is 4kHz at the 6dB points and 18kHz at 40dB. Not bad for short wave programme listening but not so good for DXing. Selectivity is obtained from a ceramic filter and three adjustable single tuned i.f. transformers T16, T17 and T18. The ceramic filter is housed in the same can as T16. The DX160 is an inexpensive set which is likely to have been "aligned" on the assembly line. Some may never have been really spot-on, a conclusion reached as a result of the widely different accounts given of this set's performance.

It is not difficult to check if T16, T17 and T18 are peaked onto the ceramic filter. They are located in a row, parallel to the front panel on the top of the left hand printed circuit board as viewed from the front of the set. They are clearly signwritten, each slug being a different colour. T16 is red, T17 is white, T18 is black. You will need a trimming tool and preferably a signal generator though you can get away with tuning the set to a weakish signal giving a peak around 4 on the lower scale of the S-meter. The medium or long-waves in daylight should deliver a suitable signal. Mark the position of the slug's screwdriver slot in pencil on the can so that you can go back to it if necessary. Adjust the core slowly in either direction for a peak on the S-meter. Do one at a time and check if the receiver is functioning properly before moving to the next.

Sharpening the I.F. Responses

If you are adept enough to work on a p.c.b. with a small soldering iron then you can sharpen up selectivity. Simply replace the emitter bypass capacitors C16 and C19 with ceramic resonators. These capacitors are used to prevent negative feedback with consequent drop in receiver gain. Remove one and the output drops dramatically. Replace with a 455kHz resonator and the gain is restored but only close to 455kHz. The result is an improvement in selectivity.

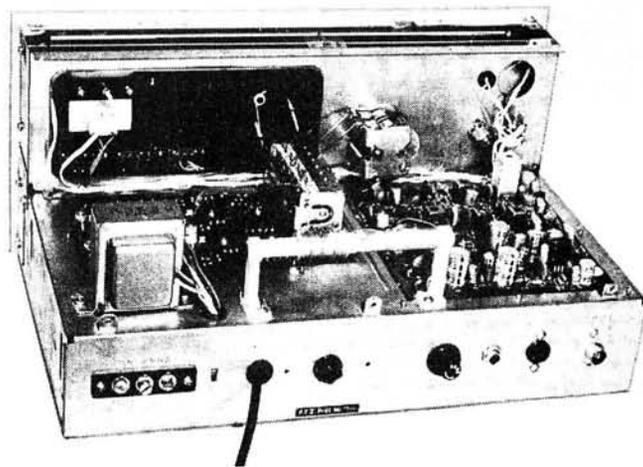Start with C16 which is the easier of the two. It is found between T16 and T17 close to Q5, all being signwritten on the component side of the board. The emitter, base and



collector of Q5 are labelled e, b, c on the lower side of the board, which helps in locating the solder points of C16. Using a small size soldering iron and a desoldering aid such as solder braid or a suction device, remove C16. The hole spacing on the board corresponds to the pin spacing of the resonator so the latter pushes in easily in place of C16. Solder below the board, check T16, T17 and T18 and try out the set.

If a further increase in selectivity is required, repeat the operation with C19 which lies between T17 and T18 and close to Q6. This time there is a problem as the hole spacing is wider but it is possible to spread out the flat pins of the resonator so that the tips partially enter the holes left by C19, from below the board, where they are soldered in place.

The ceramic resonators used are available from Ambit—ask for CFE455, 455kHz series type, stock number 16-45575. The dimensions are approx. 9 × 8 × 3mm with 5mm pin spacing and they are, if anything, slightly smaller than C16 and C19 which they replace.

Wide/Narrow Selectivity

A receiver with fixed selectivity must be a compromise. If the selectivity is narrow, sideband cutting will occur. If it is wide, better quality audio will be paid for by an inability to winkle out DX. After C16 and C19 were replaced with resonators, sideband cutting was evident and detuning had to be resorted to for programme listening. The capacitor C19 value 40nF, which was now spare, was tapped across the resonator fitted in its place. This brought an immediate improvement to audio quality. One wire from this capacitor was now soldered onto the live side of the resonator (farthest from front panel) and a lead from the other wire led off to a switch and chassis. The front panel standby switch and its wiring, which comes to the main board, were used. The two wires from the switch, red and mauve, were cut at the board and leaving behind a couple of millimetres with insulation so that the solder points could be found again in the future. The red wire was soldered to chassis and the mauve wire to the "free" end of the 40nF capacitor (ex-C19).

In order to prevent the receiver being permanently on standby, go back to the two wires removed earlier from the standby socket and solder them together. If the standby socket was not removed, then insert a shorting plug in it. The standby switch now offers wide selectivity when in the REC position and narrow when moved to STD BY.

Using a Medium Wave Loop

Although there is a version of the DX160 that has a screened antenna tuning inductor (T2), the model in the possession of the writer has a ferrite rod antenna. It is mounted above the chassis close to the hardboard back and replaces T2 and also T3, the latter being the longwave coil. This ferrite rod performs a dual function being a tuning inductor as well as antenna. If it is removed then the receiver will not work on the medium waves or long waves.

Although there is a coupling winding on the ferrite rod which goes to the A1 and A2 terminals so that a loop antenna can be connected up, the loop is virtually useless. It cannot null out a signal picked up by the ferrite rod so its directional properties are masked. Since the cabinet is made of metal it is only through the hardboard back that signal pickup is possible. Replace the back with a metal one and the ferrite rod should be screened and the loop will be effective. As an experiment, the hardboard back was covered in kitchen foil. When refitted, the medium wave band, without antenna connected, was quiet except for a few strong local stations which now were barely audible. The loop performed very well and even when a few ventilation holes were cleared through the foil, near the sides, it continued to do so.

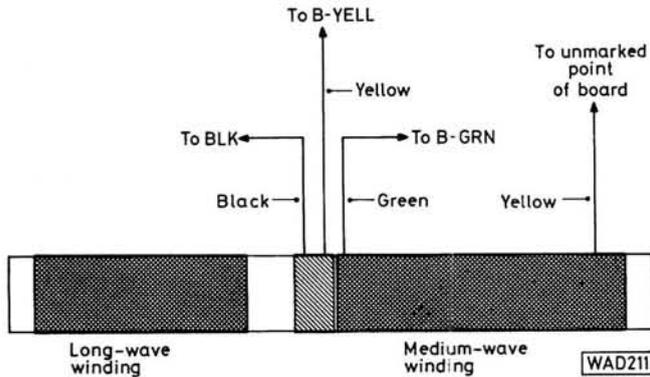



Fig. 2: Ferrite rod antenna, viewed from rear

Sensitivity on Medium Waves

Poor sensitivity on the medium waves is a complaint often made about the DX160 and one that is justified by the receiver specification. This quotes $50\mu\text{V}$ for band A, $100\mu\text{V}$ for band B (medium wave) and either $3\mu\text{V}$ or $4\mu\text{V}$ for bands C to E, all for a signal-to-noise ratio of 10dB, measured as $(S+N)/N$. It seems likely that the DX160 has been deliberately downgraded on the medium waves to ensure freedom from overloading on a band normally used for picking up local entertainment.

A modern screened r.f. transformer as a replacement for the ferrite rod antenna ought to provide a remedy and such a component, RW06A6408, stock number 35-64080, was obtained from Ambit. The base connections are shown in Fig. 3 and the ferrite rod antenna as viewed from the rear, is shown in Fig. 2.

There are four wires coming from points on the p.c.b. to the medium wave winding on the ferrite rod. These should be cut near the winding and taken to the new r.f. transformer instead. Start with the yellow wire on its own on the right (Fig. 2). It is cut near the winding and the free end soldered to pin 1 (Fig. 3). Move now to the three wires on the left hand side of the winding. The green one which comes from a point marked B-GRN is now terminated on

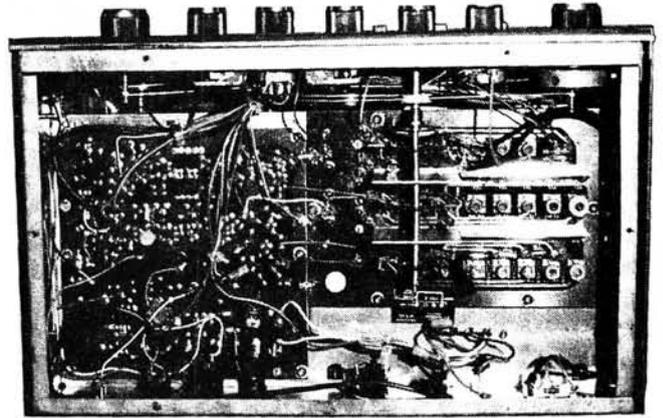

pin 6, the black one from BLK goes to pin 3 and the remaining yellow wire coming from B-YELL is soldered to pin 4. The new r.f. transformer is soldered to a small bracket which is attached to the rear of the main tuning capacitor using the small screw that holds on a wiring clip. The four short ends of the wires left on the medium wave winding on the ferrite rod are tied onto the rod so that they are available in the future.

All that remains is to peak up at the l.f. end of the band using the slug on the new transformer, making sure that the antenna trimmer on the front panel is operative at the h.f. end. If not, then re-adjust the slug. There is no need to replace the hardboard back with a metal one as the ferrite rod antenna is now inoperative.

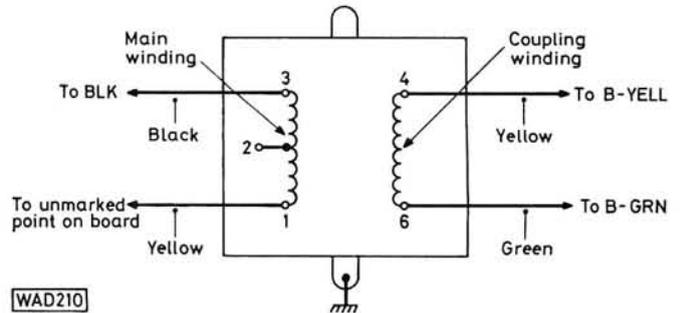


Fig. 3: Medium wave r.f. transformer connections

General Information

A copy of the DX160 circuit diagram, along with some notes, is available from the European DX Council, PO Box 4, St Ives, Huntingdon, PE17 4FE. Send 50p or three IRCs if abroad, and ask for the DX160 Receiver File. The circuit is of the version that does not have a ferrite rod antenna and the common end of the r.f. coupling windings instead of going to A2 are shown connected to chassis. This is probably an error in the drawing otherwise there would be no balanced antenna input.

The power socket at the rear of the DX160 allows 12V d.c. to be connected in place of the mains supply. There is no switching but there is a diode to protect against reverse polarity. The pilot lamps are run from their own winding on the mains transformer and do not light up when the set is run from batteries. As a result the power consumed is only 37mA with the volume at minimum which makes it

Take a look at the world's most advanced range of 2 metre Linear Amplifiers


Over 40 years of design experience has gone into what is fast becoming acclaimed as the biggest break-through in linear technology. Performance and reliability have been designed in, which gives us the confidence to offer a free 5-year warranty. Why not take a closer look at our products and see where value for money really counts.

The LPM144 Range

This sophisticated, but simple to use, range of amplifiers have performance characteristics and extra features previously not available in the UK. The pre-amplifier uses the highly regarded BF981 MOSFET, and an LED bargraph power meter is provided, to highlight only two of the amazing number of features.

The L144 Range

To complement the LPM range, we have introduced the L series linear-only versions for the amateur who may already be equipped with a good pre-amplifier and power meter. The excellent linear performance is maintained and both RF Vox and hard-wired changeover are standard.

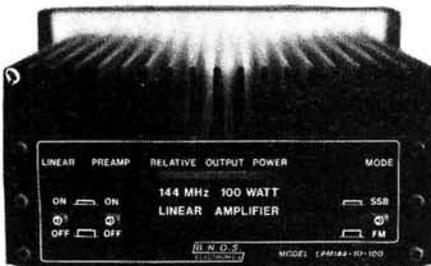


LPM144-1-100	£172.50
LPM144-3-100	£172.50
LPM144-10-100	£149.50
LPM144-25-160	£189.50
LPM144-3-180	£215.50
LPM144-10-180	£212.50

- Linear all mode operation
- Continuous rated RF output power (RMS)
- RF & HARD switched changeover with selectable delay
- Trouble-free RF switching at low drive levels
- Straight-through mode when switched off
- Unique over-drive protection circuit
- Mobile mount on all 100 Watt models



L144-1-100	£138.00
L144-3-100	£138.00
L144-10-100	£115.00
L144-25-160	£155.00
L144-3-180	£181.00
L144-10-180	£178.00

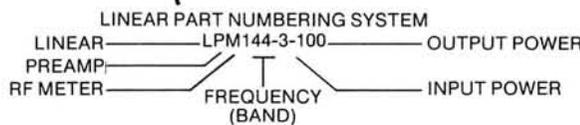

BNOS 'A' Series Power Supplies

12/6A £48.30

- 13.8V, 6A continuous output
- 7A maximum output current
- 10A current meter
- 10A output terminals
- LED shut down indicator
- Fully protected




12/12A £86.40

- 13.8V, 12A continuous output
- 15A maximum output current
- Large 20A current meter
- 15A output terminals
- LED shut down indicator
- Fully protected

12/25A £125.45

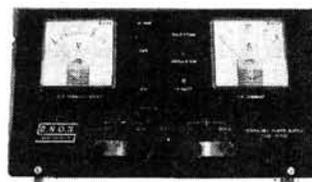- 13.8V, 25A continuous output
- 30A maximum output current
- Large 30A current meter
- 30A output terminals
- LED shut down indicator
- Fully protected



12/40A £225.40

- 13.8V, 40A continuous output
- 50A maximum output current
- Large 50A current meter
- Large output meter
- LED shut down indicator
- LED out of regulation indicator
- Output sensing terminals
- Fully protected

Our Guarantee Our aim is to provide you with high quality products at realistic prices, to give you the best value for your money.

All products that carry our logo are designed and built by our engineers in the UK and carry a full 12-month guarantee, which includes all parts and labour.

We are so confident that our linears are simply the best that we offer to repair your unit at component cost for up to 5 years from date of purchase. That means we will repair, calibrate and return to you free of charge.

All other products sold by us carry our standard 12-month guarantee.

Available direct or from one of our many UK agents — or come and see us at most rallies and exhibitions



BNOS Electronics (Dept PW) Greenarbour, Dutton Hill, Great Dunmow, Essex, CM6 3PT
Telephone (0371 84) 767 SAE for further details

All prices include VAT. Postage free on all Mainland UK orders, goods normally despatched by return.

Top-Band Direct

by Chris Plummer G8APB

In the second part of this article the author's receiver is described with sufficient detail to enable you to build one for yourself.

The receiver was developed by Bill North G3TRY and the author and is constructed on a single printed circuit board.

The Circuit

The basic set is designed around the now elderly TAD100 integrated circuit, but the newer TAD110 can be used as a direct substitute. The oscillator, mixer, detector, and audio pre-amp. stages are in the i.c. and a separate f.e.t. r.f. amplifier and a bipolar audio amplifier and beat frequency oscillator are also provided. The TAD100 has, unfortunately for our purposes, internal a.g.c. but this can be disabled by putting a preset d.c. bias voltage on pin 1 via the mixer coil.

Looking at each of the stages separately and noting their particular features you will see that all r.f. signals enter the set via a tuned frame or ferrite rod antenna if the case screening is effective. The construction of a frame or loop is relatively simple, the size can be adjusted to suit the case chosen for the set and can form the carrying handle for the unit. Construction can be of wood bound with sticky insulation tape and the wire let into a groove, or a metal frame screen such as a trough of aluminium, with the wire inside the trough. Make sure, however, that the aluminium trough does not act as a shorting loop to the antenna or you won't hear much. The gap in the trough can be bridged with wood or a plastic material. A ferrite rod antenna is fairly simple to make by winding the coil on the centre of the rod and fitting it either in an insulating tube mount, or a metal tube with a slot (Fig. 2.3). As with the frame antenna the rod mounting can be used as the carrying handle. One thing to remember is that the bearing is taken along the axis of the coil, i.e. at right angles to a frame antenna and along the axis of a ferrite rod.

The r.f. stage is a fairly common arrangement, but here screening is important as leakage from the antenna across the r.f. stage can cause errors and confusion when close in to the transmitter. Attenuation of the incoming signal is by a variable resistor in the base of the 2N3819 f.e.t.

The TAD100 forms most of the circuitry with the exception of the tuned circuits. The oscillator is fairly standard and tends to be relatively easy to get going, the tuning range is (1.81-2.0+i.f.)MHz, i.e. 2.275-2.465MHz plus a small amount at both ends to allow for calibration. The local oscillator is deliberately set on the high side of the received signal to avoid i.f. image interference from medium wave signals.

The audio stage is self explanatory and needs no alignment. It will drive any commonly available high-impedance headphones. Headphones are used, of course, to keep your information to yourself and also help concentration, as well as being lighter, both in weight and battery consumption, than a more powerful amplifier and a loudspeaker.

The b.f.o. is a transformer feedback oscillator and only requires that the feedback winding is connected the right way round followed by a quick tune and adjustment of the injection to maintain oscillation and correct operation.

The final stage to consider is the sense amplifier. This is an untuned stage that amplifies the signal from the separate telescopic whip antenna and combines it with the signal from the main antenna at the correct level and phase relationship. This enables the operator to determine the correct direction from the main antenna, as previously described. The only adjustment required is to select the values of R1 and R2 to give the best sense operation.



BUYING GUIDE

Most of the components used are readily obtainable from advertisers in *PW*. The TAD100 can be obtained from Watford Electronics. The p.c.b. is available from the usual suppliers or from the author QTHR. Toko coils and formers can be obtained from Ambit International. A suitable "vernier slow-motion drive" is available from Maplin Electronics as RX40T vernier dial medium. Electrovalue stock Jackson variable capacitors.

Approximate Cost

£34

Construction Rating

INTERMEDIATE

ection Finding

Part 2

The set has been built by some 150 people either for use as a good simple Top Band receiver or as a d.f. set and very few problems have arisen. The p.c.b. design, which is a single-sided board approximately 150 × 50mm, is set out with plenty of room to use "junk box" components. Toko coil formers are recommended for the local oscillator and mixer coils, but unfortunately no prewound coils are available and to use these coil formers you need 42 s.w.g. enamelled wire or finer to be able to get all the turns required on the bobbin. It is of course possible to use other formers without problems but the turns will probably have to be adjusted. The filter is a standard Toko CFT455C,

similarly the b.f.o. coil is a standard prewound unit. Three forward-biased 1N914 silicon diodes have been used to produce a reference voltage of about 1.4V as it was the cheapest way, but a 1.5 to 2V Zener could be used.

The complete receiver is built into a die-cast box. The author's prototype used a box 222 × 146 × 55mm in size. Remember that in use the receiver will probably be subjected to rain, mud, floods and other extremes of climate and temperature so make sure that there are no unnecessary holes in the case. The two-gang capacitor (C21,22) could be a Jackson C808 or other split-stator type according to price and availability.

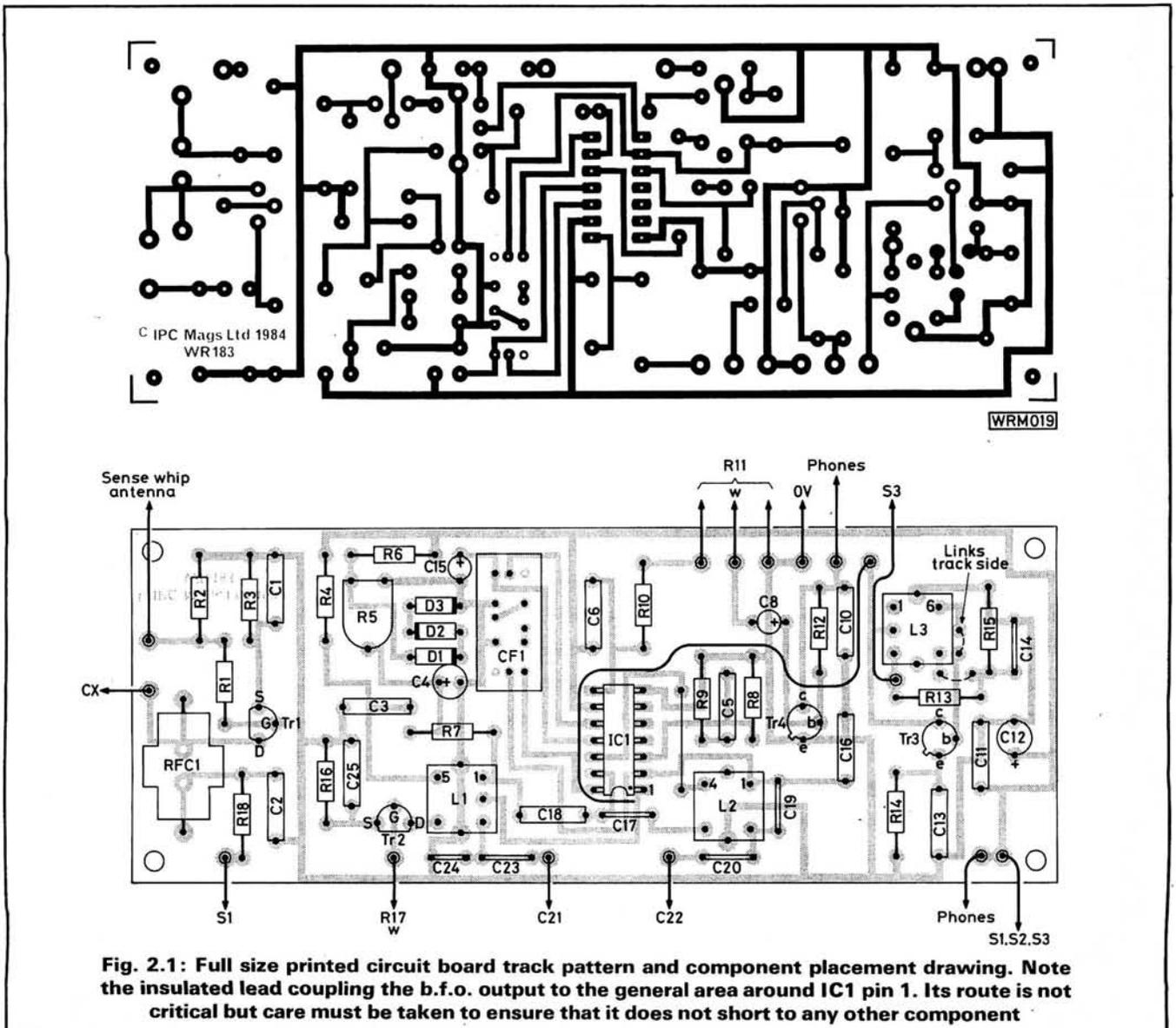


Fig. 2.1: Full size printed circuit board track pattern and component placement drawing. Note the insulated lead coupling the b.f.o. output to the general area around IC1 pin 1. Its route is not critical but care must be taken to ensure that it does not short to any other component


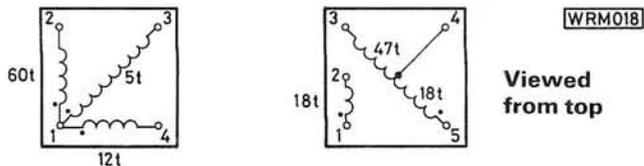


Fig. 2.2: Coil winding details for (left) L2 and (right) L1

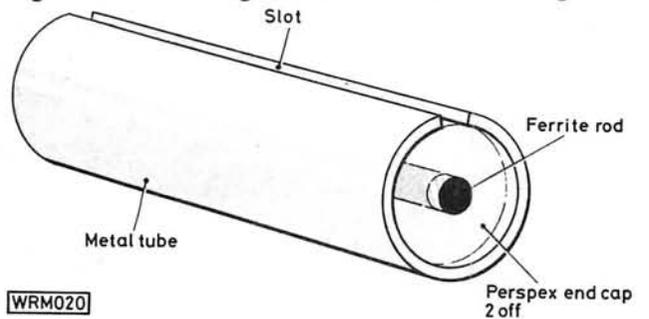

WRM021


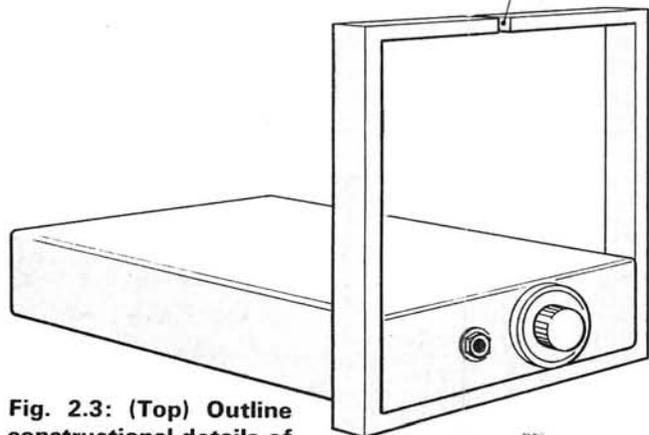


Fig. 2.3: (Top) Outline constructional details of the ferrite rod antenna. (Above) Frame antenna details

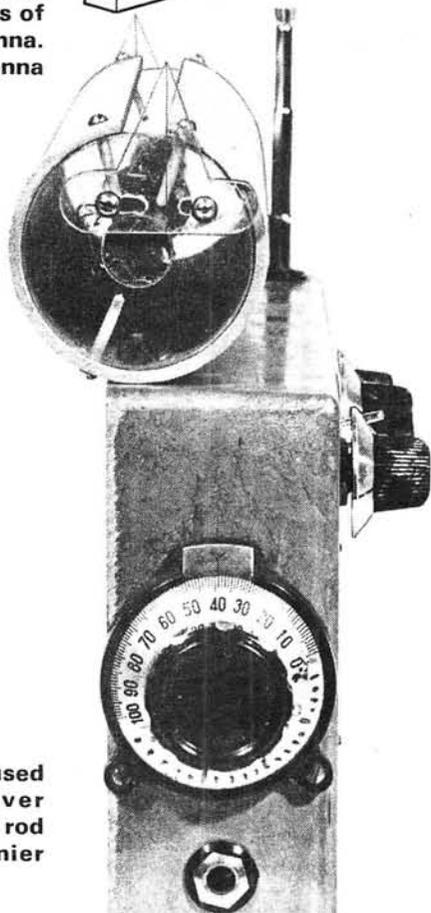

The author's much used prototype receiver showing the ferrite rod antenna and vernier tuning dial

★components

Resistors

Carbon Film $\frac{1}{4}W$ 5%

150 Ω	1	R18
180 Ω	1	R9
220 Ω	2	R4,16
470 Ω	1	R10
820 Ω	1	R8
1k Ω	1	R14
3.3k Ω	1	R6
4.7k Ω	1	R3
5.6k Ω	1	R7
10k Ω	1	R15
47k Ω	1	R2
68k Ω	1	R13
470k Ω	1	R12

Potentiometers

Min. Horizontal Preset

5k Ω	1	R5
-------------	---	----

Midget Carbon Track

5k Ω (Log)	1	R11 (with switch)
100k Ω (Lin)	1	R17

Capacitors

Polyester

10nF	9	C1,2,3,7,9,10,11,13,25
47nF	3	C5,6,18
100nF	1	C16

Ceramic Plate

100pF	2	C19,24
220pF	2	C20,23
1nF	1	C14
2.2nF	1	C17

Tantalum Bead

0.33 μ F	2	C8,15
4.7 μ F	1	C4

Electrolytic

22 μ F	1	C12
------------	---	-----

Air-spaced Variable

50pF	1	C26 (Jackson C804)
50+50pF	1	C21,22 (Jackson C808)

Semiconductors

Diodes

1N914	3	D1,2,3
-------	---	--------

Transistors

BC108	2	Tr3,4
2N3819	2	Tr1,2

Integrated Circuits


TAD100	1	IC1
--------	---	-----

Miscellaneous

Ceramic filter (CF1) Toko CFT455C; Coil (L3) Toko YRCS12374ACS; Coil formers Toko 10K (2); Min. toggle switches s.p.d.t. (2); Slow motion dial; Jack socket $\frac{1}{4}$ inch; Battery holder; Diecast box; Telescopic antenna; Ferrite rod (see text); Knobs (3); Choke (RFC1) 2.5mH; Material for ferrite rod or frame antenna (see text).

Alignment Notes

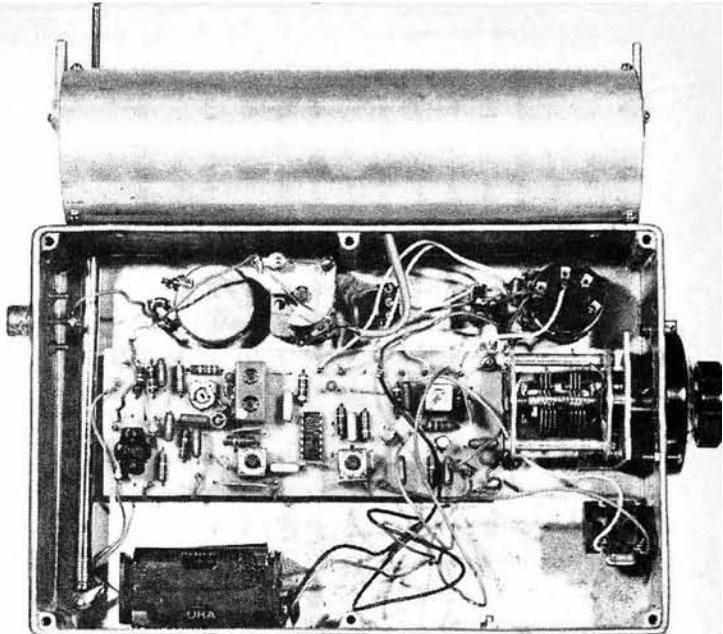- 1) Beat frequency injection is achieved by taking an insulated wire from the collector of the b.f.o. transistor to somewhere near the TAD100. No direct connection will be required.
- 2) Set the i.f. gain control preset for maximum signal.
- 3) Depending on the local oscillator and mixer coil windings select those capacitors marked * (Fig. 1.4) to achieve correct bandsread and tracking.
- 4) The main antenna frame (200 × 250mm) can be made of hardwood or metal (remembering the break if metal is used), with windings to suit tuning, say about 13 turns. A 200mm long ferrite rod 10 or 12.5mm diameter with about 25 turns wound on it mounted in a plastics or split metal tube could also be used.
- 5) Select resistors R1, R2, R3 and R4 to give best operation. Typical values would be R1 = 7.5kΩ, R2 = 620Ω, R3 = 220Ω, R4 = 230Ω. Use a 10kΩ preset in place of R1 for setting up. Set R1 to about 7.5kΩ and select R2 to give a drain current of about 3mA. To select R1 to give best sense operation use the following method. Set up a friend with a transmitter and travel about 5km away into open countryside. Adjust R1 to give the best sense circuit operation, i.e. greatest front to back ratio. Measure the value of the preset and replace with the nearest preferred value resistor.
- 6) Capacitor Cx is approximately 2pF and is made from a twisted pair of insulated wires 30mm long.
- 7) Set the local oscillator range on high side of 1.81–2.0MHz and then peak the mixer coil at midband.



Acknowledgements

My thanks must go to Bill North for the initial design work and trials, to Eric Mollart for the urge to write it down and Roy Powers G8CKN for being the "Devil's Advocate."


Good luck and good d.f.ing de Chris G8APB.

Further Developments

The receiver described is obviously of a specialised nature but can form the basis of a Top-Band monitor receiver and this will be described in another article.

PRACTICAL NEW GUIDES

A Guide to Printed Circuit Board Design

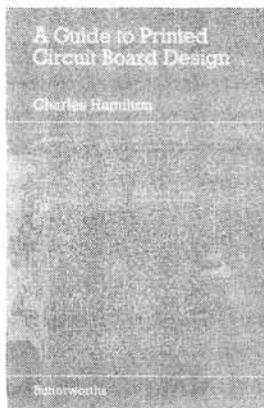

Charles Hamilton

Printed circuit boards can look, and sometimes are, extremely complicated. The high density of components on modern boards combined with the mass tracking can deter the would-be designer. This new book strips away the aura of mystique surrounding PCB design. A practical book covering design methods and practice currently employed in the modern drawing office, it describes a logical step by step approach to PCB design. Fully illustrated throughout, the book is an

invaluable guide and practical aid to the young or inexperienced designer in the drawing office.

Softcover 104 pages 216 × 138 mm
Illustrated 0 408 01398 2 £7.50 March 1984

Foundations of Wireless and Electronics Tenth Edition



M G Scroggie
assisted by S W Amos

A completely updated edition of this famous book. It has been revised to take account of recent changes and developments in electronics – in particular non-sinusoidal signals, waveform generators, computers and power supplies. All the circuit diagrams have been redrawn using the graphical symbols recommended by BSI. Ideal text book for higher BTEC and undergraduate students as well as the enthusiast.

Softcover 576 pages 0 408 01202 1 1984 £8.95

A Newnes Technical Book
Available from your nearest bookseller




Butterworths, Borough Green, Sevenoaks, Kent.TN15 8PH

Products

New British Oscilloscope

A new general-purpose, dual trace oscilloscope announced by Bridge Scientific Instruments Ltd. of Skipton, costs only £195 (excluding VAT) and is British built. Designated the Bridge DB242, the instrument has been specially developed to take into account the needs of educational and industrial laboratories, test bays and service departments. Compact and highly portable, the new oscilloscope is also suitable for radio and TV maintenance, electronics enthusiasts and radio amateurs.

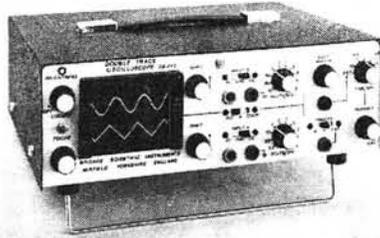Speed and simplicity of use are two important parameters that have been applied in producing this instrument, which is both easy to understand yet highly versatile. This is immediately apparent in the display, in which a medium persistence phosphor gives



good trace readability on the 60 x 50mm display screen on which a calibrated graticule is superimposed. Considerable time savings in use may be achieved, utilising the trace location button which returns overscanned traces to the screen regardless of the setting of other operating controls and the auto brightline triggering system.

Simple, reliable, advanced circuit

techniques are employed to provide a worthwhile specification. Sensitivity can be varied from 50mV/cm in independent switched sequences for each channel. Sweep speeds can be varied between 1µs/cm and 0.2s/cm using calibrated switch positions.

Designed and manufactured in Britain, the Bridge DB242 oscilloscope uses safety approved components that comply with British and EEC standards. An even more economically priced single trace version, the Bridge DB121, possesses a similar general specification, but without the twin channel facilities, and costs only £175 (excluding VAT).

For further details contact the manufacturers: *Bridge Scientific Instruments Ltd., 63-65 High Street, Skipton, North Yorkshire BD23 1EF. Tel: (0756) 69511.*

New DF System

The latest radio direction finding system from Datong Electronics Ltd. is the Model DF2, which utilises a proprietary error-cancelling version of the Doppler principle and is intended for general professional applications from h.f. to u.h.f., both in mobile and base station situations. It can handle signals carrying most types of modulation including f.m., a.m. and s.s.b.

Being microprocessor-based, the system offers a high degree of operational flexibility plus special signal processing techniques which reduce bearing jitter under multipath conditions or heavy signal modulation. This is achieved by real-time digital averaging of the incoming data. The averaging period is panel selectable from 0.065 to 6 seconds yet the

special software always ensures that the response time to new signals remains constant at 260ms.

Bearings are immediately presented in both polar and digital form. The polar display gives five degree resolution on a circle of 36 l.e.d.s, while the 3-digit display in the centre of the circle gives one degree resolution. A separate 20-

l.e.d. bar array indicates signal strength (when connected to the receiver's a.g.c. line).

Other advanced features of Model DF2 include: storage and display of last received bearing without errors caused by "squelch tail"; remote display option; "sample-and-hold" mode; regular autozeroing for non-digital circuits; single coaxial cable link to head unit; cancellation of errors due to receiver phase-shifts.

For further details, apply to: *Datong Electronics Ltd., Spence Mills, Mill Lane, Bramley, Leeds LS13 3HE. Tel: (0532) 552461.*



More on page 59

Benny



SPECIAL PULL-OUT FEATURE

PW RADIO DATA

part 2 - Valve & Semiconductor Codes + Trademarks

Every valve and semiconductor carries a type number. Some can tell you a lot about the characteristics of the device—others are not much better than a serial number. This month we list some of the more useful codes, both past and present; some of them are "House Codes" used by just one manufacturer, others are more widely used, like the European Pro-Electron code. Knowing these

codes can help you find your way through unfamiliar circuits.

When you want to find out more about a particular component, knowing who made it can be a great help. Often the identification is just a trademark; no room for the company's name. The last three pages of our Radio Data feature this month show the trademarks of 75 radio/electronics manufacturers.

MULLARD House Code Semiconductors

e.g. **0 0 A 9 0**

IDENTITY	CLASS	SERIAL NUMBER
The letter O indicates a semiconductor device	A Diode or Rectifier AP Photodiode AZ Voltage Regulator Diode (Zener) C Transistor CP Phototransistor RP Photoconductive cell	Has no significance except: DIODES Germanium—2 figure serial numbers Silicon—3 figure serial numbers TRANSISTORS Germanium—serial numbers up to 199 Silicon—serial numbers 200 and over

SEMICONDUCTORS

JEDEC Code (USA)

- 1N --- Diode
- 2N --- Transistor
- 3N --- 3-junction device (e.g. dual-gate f.e.t.)
- 4N --- 4-junction device (e.g. opto-isolator)
- 6N --- 6-junction device (e.g. Darlingon opto-isolator)

GEC/Mullard House Code

- GEX --- Germanium Diode
- GET --- Germanium Transistor

HUGHES (EMIHUS) House Code

- HG --- Germanium Diodes
- HS --- Silicon Diodes

LUCAS House Code

- DD --- Diode
- DT --- Transistor

TEXAS House Code

e.g. **2 S 1 0 4**

DEVICE	MATERIAL	SERIAL NUMBER
1 Diode	G Germanium	
2 Transistor	S Silicon	

PRO-ELECTRON Semiconductors

e.g. **B C 1 0 7 -**

MATERIAL	CONSTRUCTION	SERIAL NUMBER	RANGE NUMBER
A Germanium	A Signal diode	Devices for domestic use—3 figures	Additional information covering a range of variants of a basic type
B Silicon	B Variable capacitance diode	Devices for industrial use—	Rectifier Diodes & Thyristors:
C Compound materials such as gallium arsenide	C Small AF transistor	one letter (Z, Y, X, etc) followed by 2 figures	The group of figures indicates the p.i.v. rating
R Compound materials such as cadmium sulphide	D AF power transistor		The final letter R denotes a reverse polarity (stud anode)
	E Tunnel diode		version, (n.b. Thyristors, by convention, are normally stud anode, and therefore end in R)
	F Small RF transistor		Voltage Regulator Diodes:
	G Multiple device		The first letter gives the voltage tolerance:
	L RF power transistor		A = 1% D = 10%
	N Photo-coupler		B = 2% E = 20%
	P Radiation sensitive device (Photodiode etc.)		C = 5%
	Q Radiation generating device (i.e.d.)		The group of figures indicates the working voltage, the letter V being used to denote the decimal point. The final letter R denotes a reverse polarity (stud anode)
	R Small thyristor		version
	S Small switching transistor		
	T Power thyristor		
	U Power switching transistor		
	X Multiple diode (e.g. Varactor or step recovery diode)		
	Y Rectifying, boost or efficiency diode		
	Z Voltage regulator diode		

NEWMARKET House Code
Semiconductors
Silicon

e.g. **NKT 3 5 2 1 9**

FABRICATION	FREQUENCY (f _T)	GAIN (h _{FE})	V _{clm}	SERIAL NUMBER
1 Epitaxial <i>npn</i>	0 Less than 100MHz	0 Less than 10	0 Less than 15V	
2 Epitaxial <i>ppn</i>	1 100MHz minimum	1 10 min.	1 15V min.	
3 Diffused <i>npn</i>	2 200MHz minimum	2 20 min.	2 30V min.	
4 Diffused <i>ppn</i>	3 300MHz minimum	3 40 min.	3 45V min.	
8 FET	9 900MHz minimum	4 80 min.	4 60V min.	
	etc. up to	5 160 min.	5 90V min.	
		6 320 min.	6 120V min.	
		7 640 min. etc.		

PRO-ELECTRON
Integrated Circuits

e.g. **T B A 5 7 0 A 0**

SOLITARY DIGITAL FAMILY CTS	S Digital T Analogue U Mixed	H Hybrid otherwise no special significance	A Not specified B 0 to +70°C C -55 to +125°C D -25 to +70°C E -25 to +85°C F -40 to +85°C G -55 to +85°C	A 4-digit number or A Serial Number (combination of figures and letters)	C Cylindrical D Ceramic d.i.l. F Flat pack P Plastics d.i.l. Q Quad-in-line U Uncased chip Z Customised	ONE-LETTER SUFFIX	
						SHAPE	MATERIAL
						-C Cylindrical -D Dual-in-line -E Power d.i.l. -F Flat (leads on 2 sides) -G Flat (leads on 4 sides) -K Diamond (TO-3 family) -M Multiple-in-line (more than 4 rows) -Q Quad-in-line -R Power q.i.l. -S Single-in-line -T Triple-in-line	
	TWO FAMILY IDENTITY LETTERS						
	TYPE LETTERS MA Microcomputer or Central Processing Unit MB Slice Processor MD Correlated Memories ME Other correlated circuits (interface, clock, peripheral controller, etc.)						
*Except for Z, the meanings given are recommended only							

MAZDA
Receiving Valves
(Signal)

e.g. **10 F D 12**

P/S	FILAMENT OR HEATER RATING	CONSTRUCTION	SERIAL NUMBER
1	1-4V	C Frequency changer with special oscillator section	
6	6-3V	D Signal diodes	
10	0-1A	F Voltage amplifier tetrode or pentode	
20	0-2A	K Small gas triode or tetrode	
30	0-3A	L Voltage amplifier triode or double-triode including oscillator triode	
		M Tuning indicator	
		P Power amplifier, tetrode or pentode	

Parallel or Series operation

NOTE—2 letters may be used for multiple valves

MAZDA
Power Rectifier Valves (High Vacuum)

CONSTRUCTION	SERIAL NUMBER
U Half Wave	
UU Full Wave	

NEWMARKET House Code
Semiconductors
Germanium

e.g. **NKT 6 1 3**

TYPE	SERIAL NUMBER
1 RF <i>ppn</i>	
2 AF <i>ppn</i>	
3 Intermediate Power <i>ppn</i>	
4 Power <i>ppn</i>	
6 VHF <i>ppn</i>	
7 AF <i>npn</i>	

M.O./G.E.C./OSRAM
Receiving Valves e.g.

X 6 1 M

CONSTRUCTION	SERIAL NUMBER
A Valve for specialised industrial application	NOTE The suffix "M" indicates external metallising
B Double triode	
D Diode or double diode	
GU Gas-filled rectifier	
GT Gas-filled triode (thyatron)	
H High-impedance triode	
KT Kinkless tetrode (beam tetrode)	
L Low-impedance triode	
N Output pentode	
U Rectifier	
W Variable- μ screened pentode	
X Frequency changer	
Y Tuning indicator	
Z Sharp cut-off screened pentode	

MULLARD
Transmitting &
Industrial Valves
CURRENT SYSTEM

e.g. **Y L 1 0 2 0**

CLASS	CONSTRUCTION	SERIAL NUMBER
X Photosensitive tube	A Diode	A group of four figures. The last figure is 0 for basic types; variants of the basic type are indicated by the figures 1-9
Y Vacuum } *	C Trigger tube	
Z Gas-filled } *	D Triode or double-triode	
	G Miscellaneous counter tube	
	H Travelling-wave tube	
	J Magnetron	
	K Klystron	
	L Tetrode, pentode, double-tetrode or double-pentode	
* valve or tube (not photodevice)	M Cold-cathode indicator or counter tube	
	P Photomultiplier or radiation counter tube	
	Q Camera tube	
	T Thyatron	
	X Ignitron, image intensifier or image converter	
	Y Rectifier	
	Z Voltage stabiliser	

MULLARD
Transmitting Valves
OLD SYSTEM

e.g. **Q Q V 0 6 - 4 0 A**

FUNCTIONAL CLASS	STRUCTURAL PROPERTY	RATING (I)	RATING (II)	SUFFIX
B Backward-wave tube	A Output up to 1W	(a) Approx V_a in kV for transmitting valves & rectifiers (peak voltage in the case of pulse valves)*	(a) Approx P_a in W for transmitting valves (total for multiple valves)	When used, usually a serial letter indicating a particular design or development
J Magnetron	B Output 1W or over	(b) Approx p.i.v. in kV for thyratrons*	(b) Max I_{pk} in A for pulse transmitting valves (prefixed by P)	
K Klystron	D Disc seal construction	(c) Approx operating frequency in GHz for microwave devices	(c) For backward & travelling-wave tubes output power in mW or W	
L Travelling-wave tube	G Mercury vapour-filled	*Below 1kV, zero followed by a figure indicating tenths of a kV. e.g. 06=600V.	(d) Pulse output power in kW for magnetrons	
M LF amplifying or modulator triode	H Hydrogen-filled		(e) Output power in mW for klystrons	
P RF power pentode	N External magnet reqd. } Magnet- Packaged construction } rons		(f) Output current in mA for rectifiers	
Q RF power tetrode	R Inert-gas filled		(g) Max $I_{A,MEAN}$ in mA for thyratrons	
R Power rectifier	S Reflex construction } Klystrons			
T RF power triode	T Multi-resonator			
X Large thyatron	V Indirectly-heated oxide-coated cathode			
NOTE	X Directly-heated tungsten filament			
2 letters may be used for multiple valves	Y Directly-heated thoriated-tungsten filament			
	Z Directly-heated oxide-coated filament			

VOLTAGE STABILISERS

British Systems

1. The type number consists of OS followed by two groups of figures separated by an oblique stroke.
e.g. OS75/20

The first group is the nominal running voltage, the second the nominal maximum tube current.

2. The type number consists of OS followed by a four-figure serial number which has no numerical significance.

3. The type number consists of a group of figures, a letter, and a final figure.
e.g. 150C4

The initial figures indicate the nominal running voltage. The remainder of the type number has no significance.

USA System

The RMA Valve system is used. The first figure is always 0 (no heater) and the final figure is generally 2 (for 2 useful electrodes). The primer or link are not counted as useful electrodes.

**PRO-ELECTRON
Receiving Valves**

e.g. **E C H 8 1**

FILAMENT OR HEATER RATING	CONSTRUCTION	BASE TYPE	SERIAL NUMBER
P S S/P S/P P P S S P S S S S	A Diode (excluding rectifier) B Double diode, common cathode (excluding rectifier) C Triode (excluding power output) D Power output triode E Tetrode (excluding power output) F Pentode (excluding power output) H Hexode or heptode (hexode type) K Octode or heptode (octode type) L Power output tetrode or pentode M Turning indicator Y Half-wave rectifier Z Full-wave rectifier NOTE—2 or 3 letters may be used for multiple valves	1 Miscellaneous 2 B10B (Min 10-pin) ^(a) 3 International Octal 4 B8A 5 B9D (Magnoval) & Noval ^(b) 6 Various subminiature 7 J or wired-in 8 B9A (Noval) 9 B7G (Min 7-pin) NOTES (a) 2 was previously used for B8B/B8G (Loctal) (b) 5 was previously used for B9G	(a) One figure for early valves (b) Two figures for recent entertainment valves NOTE: In some type numbers with three figures, if the first figure is 1 then the second indicates the type of base, e.g. EF183-B9A base. (c) Three figures for recent professional valves

Parallel or Series Operation

**USA RMA
Receiving Valves**

e.g. **6 S N 7 G T**

FILAMENT OR HEATER RATING	SERIAL & CODE LETTERS	NUMBER OF "USEFUL ELEMENTS" BROUGHT OUT	SUFFIX LETTERS
0 Cold cathode 1 1-6V 5 4-5-5-6V 6 5-6-6-6V 7 5-6-6-6V with Loctal base above this, figures represent nominal working voltage NOTE For tapped filaments or heaters figure indicates rating of both sections in series	Allotted in sequence commencing with A (omitting I and O). (Rectifiers follow the sequence backwards from Z). When all the single letters are exhausted, the sequence commences again with two letters commencing from AB (combinations of identical letters are not normally used). The initial letter S indicates a single-ended valve, when the second letter may be that of the nearest equivalent in the double-ended range. The initial letter L indicates a Loctal base valve in the battery range	(a) Metal valve envelopes, lock-in metal bases & internal shields having separate & exclusive terminals are counted as useful elements (b) A filament or heater counts as one, except as two when there are unequally-rated tapped sections (c) In octal based glass valves add 1 for pin No. 1 whether it has an element connected or not (d) Combinations of elements connected to the same terminal or terminals count as 1	(a) A, B, C, D, E & F indicate a later & modified version which can be substituted for a previous one but not vice-versa (b) X & Y indicate low- & medium-loss bases respectively (c) W indicates a military type (d) In Octal valves G Large glass bulb GT Smaller glass tube M Metal envelope

SPECIAL QUALITY VALVES

These are made by a number of manufacturers for applications where high reliability is required under adverse operating conditions. They are electrically similar to a number of standard types, but use improved mechanical construction to give greater freedom from microphony and vibration failures. They are also more carefully controlled in manufacture and testing than their standard counterparts.

NUMBERING SYSTEMS FOR SPECIAL QUALITY VALVES

MULLARD System 1

This is based on the Pro-Electron code but the Base Type and Serial Numbers are placed between the first and subsequent letters.

e.g. Standard Special
ECC88 E8CC

System 2

The initial letter is "M" followed by a four-figure serial number beginning with 8.

MARCONI-OSRAM

The prefix "Q" is added to the standard type number

e.g. Standard Special
Z77 OZ77
B309 QB309

AMERICAN System 1


A four-figure reference number.

System 2

The RMA System, followed by the suffix "W" for a Military type, and often a further suffix "A" for a modified type.

MILITARY VALVES AND SEMICONDUCTORS

Selected, close-tolerance, versions of both Standard and Special Quality valves meeting government specifications are marketed by a number of manufacturers. In the United Kingdom, identification numbers commence with the letters "CV" (Common Valve) followed by a three- or four-figure serial number. Special Quality Valves mostly have numbers in the CV4000 group. In the USA normal type numbers are generally used, prefixed by USA (army), USN (navy) or JAN (joint army navy).

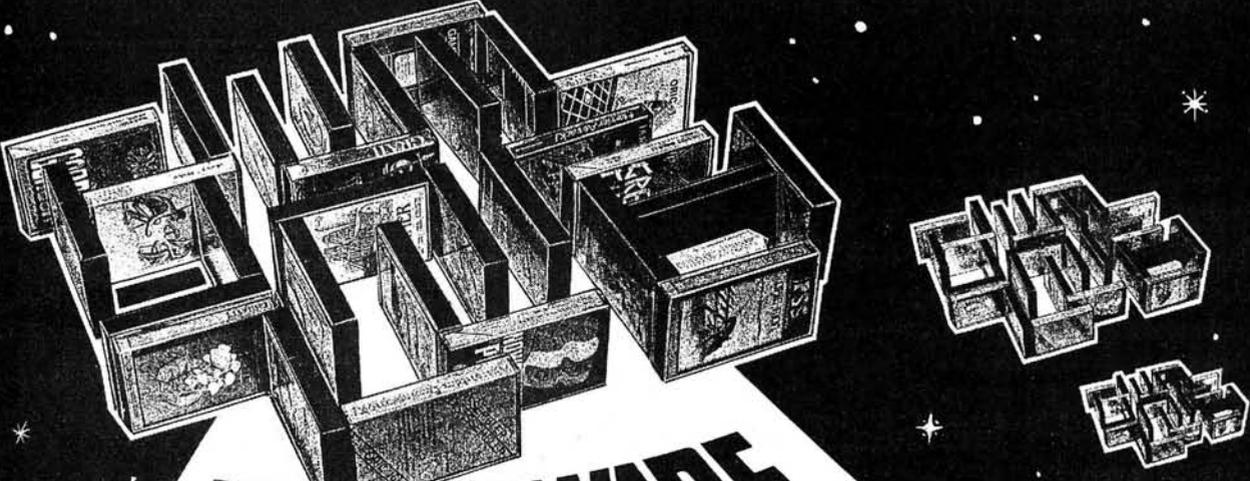

IS SOFTWARE YOUR BASIC PROBLEM?

Are you bewildered by the choice of Software Programs on the market? Not sure what Program you really need, what it does or where to get it?

SOFTWARE INDEX Is your answer

The most comprehensive magazine listing of Software programs for the eight leading Microcomputers.

- BBC ● COMMODORE 64 ● DRAGON ● VIC 20
- ORIC ● ATARI 400/800 ● SPECTRUM ● ZX81

Software Index takes the headache out of choosing the programs suited to your Micro. For people involved in electronics and specialist programs, Software Index will provide the information you need and be a valuable time-saving guide. Games, education, business and personal management are also covered.

DON'T LET SOFTWARE GIVE YOU A HARD TIME, GET THE USER GUIDE TO MICROCOMPUTER SOFTWARE—

**OVER
2,500
PROGRAMS
LISTED**

**IN YOUR
NEWSAGENT'S
NOW**

User Guide to Microcomputer Software

SOFTWARE INDEX

1984 No.2 £1.50



AMATEUR RADIO

★ INSTANT HP FACILITIES ★ ACCESS ★ BARCLAYCARD ★ FREE FINANCE ★ MAIL ORDER

YAESU	
0010 FT1	Gen Cov HF t'ceiver
0020 KC1	Curtis keyer for above
0030 DCT1	DC power cable
0040 RAMT1	Non-volatile mem board
0050 FMU1T	FM unit
0060 XFB9KCN	300Hz CW filter
0070 XFB9K	600Hz CW filter
0080 XFB9KA	6kHz AM filter
0090 XF107KC	CW filter
0100 FT980	Gen cov HF t'ceiver
0110 SP980	Matching speaker
0130 FT102	9 band HF transceiver
0140 FC102	9 band matching at
0150 VFI02DM	Remote vfo for above
0160 SP102	External speaker
0240 FM AM	Unit for above
1341 MH1B8	Scanning hand mic
0390 FT77	8 band 100 watt t'ceiver
0450 Marker unit	
0460 FM Unit	
0410 FP700	PSU for FT77
0420 FC700	ATU for FT77
1449 FL2100Z	160-10m linear amp
0810 FT290R	2m Multimode portable
0840 FT790R	70cm Multimode Portable
0860 NC11C	FT290/790 AC charger
0880 CSC1A	FT290/790 carrying case
0870 MMB11	FT290/790 Mob mount
0900 FL210	290R Linear amplifier
0700 FT208R	2m FM handheld 2½W
0710 FT708R	70cm FM handheld 1W
0750 NG3C	Slow charger
0720 VFB2	Spare Ni-cad battery pack
0740 FBA3	Charging sleeve
0760 NCT7	Base master charger
0770 NG3C	Base master quick charger
0780 PA3	Charger 12v DC
0800 MMB10	Mobile mounting bracket
1010 FT230R	2m 25W FM mob t'ceiver
1010 FT730R	70cm 10W FM mob t'ceiver
1020 FT226R	3 band all mode base station
1030 430T26	70cm module
1050 S01T26	6 metre module
1051 HF726R	HF module
1060 SA726	Full duplex x/band unit
1090 FRG7700	0.2-30MHz gen cov rec
1100 FRG7700M	7700 with memory unit
1110 MEMGR7700	Memory module
1120 CDG7700	DC modification kit
1130 FR7700	Antenna tuner unit
1201 FRA7700	Active Antenna
1140 FF5	Low pass filter
1150 FRV7700A	118-130, 130-140, 140-150MHz
1160 FRV7700B	118-130, 140-150, 50-59MHz
1170 FRV7700C	140-150, 150-160, 160-170MHz
1180 FRV7700D	118-130, 140-150, 70-80MHz
1190 FRV7700E	118-130, 140-150, 150-160MHz
1200 FRV7700F	118-130, 150-160, 170-180MHz
0490 FT757GX	Multi Mode Gen Cov.

ICOM	
2005 IC751	* NEW * 100W H.F.
2021 IC745	* NEW * 100W H.F.
2008 RC10	Keyboard Freq. cont.
2006 FSU(int.)	230v AC power supply
2030 FMU(X242)	FM module for above
2040 KEYER(X243)	Keyer module for above
2100 IC730	100w HF trans 12v DC
2120 FL30	SSB pass band filter
2190 IC720A	100w HF trans plus gen. cov.
2200 PS15	230v p.s.u. for HF t'ceivers
2210 PS20	230v chopper type unit
2060 FL45	500Hz filter for 740/730
2130 FL44	2.4kHz SSB filter
2220 FL32	CW narrow filter for 720
2230 FL34	AM filter for 720
2150 EX202	LDA unit for 730
2050 EX203	CW audio filter for 730
2170 EX205	TRV unit for 730
2240 B10	Memory back up for 720
2290 IC2KL+PSU	500W solid state linear
2310 AT100	100 watt HF Auto ATU
2320 AT500	500 watt HF Auto ATU
2340 CF1	Cooling fan
2970 SP3	Matching ext speaker
2980 HP1	Communication phones
2960 SM5	Base microphone
2250 IC7R70	Comms rec 230v AC
2260 FM unit	Plug in module
2270 FL53	CW narrow filter
2130 FL44	Xtal filter
2410 IC290H	Multimode 2m 12v DC
2430 BU1	Back up supply
2440 IC471	Multimode 70cm

ICOM CONT.	
2450 IC490	Multimode 70cm 12v DC
2480 IC2E	2m synth h'held 1.5w Special
2490 IC4E	70cm synth h'held 1.5w
2475 IC02E	144MHz h'held with k/b+LCD
2476 IC04E	432MHz h'held with k/b+LCD
2810 MMB3	Mobile mounting bracket
2840 MMB12	Mobile mounting bracket
2870 HM7	8 pin hand mic.
2890 HM9	L/S mic for IC2E/4E
2900 HM10	Up/down scan mic.
2950 SM2	4 pin desk mic.
2960 SM5	8 pin desk mic.
2962 SM6	Desk mic (745/751/271/471)
2970 SP3	External loudspeaker
2520 LC3	Cases for IC2E/4E
2570 BC25	Standard mains charger
2590 BC30	Base hot type charger
2610 BP2	Low voltage pack
2620 BP3	Standard pack
2630 BP4	Empty battery box (AA cells)
2640 BP5	High power battery pack
2650 CP1	Charger lead for 12V supply
2660 DC1	12V Regulator pack

TRIO/KENWOOD	
1450 TSS30S	160-10m t'ceiver with gen cov
1460 AT93J	Automatic ATU 80-10m
1470 SP93J	External speaker unit
1490 YK88A-1	6kHz AM filter
1500 YK88-1	500Hz CW filter
1510 YG45C-1	500Hz CW filter
1520 YG45C-1*	270Hz CW filter
1530 TS430S	160-10m with gen cov rec
1540 PS430	Mains PSU for TS430S
1550 SP430	Speaker for TS430S
1570 FMA40	FM option unit TS430S
1580 YK88C	500Hz CW filter
1590 YK88CN	270Hz CW filter
1600 YK88SN	1.8kHz SSB filter
1650 TLS22	160-10m 2kw linear
1670 MCE0 N4	Desk microphone
1680 MCE0 S6	Desk mic with up/down
1890 MCE0A	Desk mic with pre-amp
1900 MCE2S	Fist mic 50K imp
1910 MCE0S	Fist microphone 500ohm imp
1920 MCE0S	160-10m mic for TR9000/7800
1930 MCE2S	Up/down mic (TSS30S)
1940 LF30A	LF low pass filter
1950 TS790	2m/70cm all mode t'ceiver
1980 TR9-30	2m multi mode mobile
1934 TW-000	2m FM transceiver 2m/70cm
1680 TR2-300	2m FM synth handheld
1710 ST2	Base stand and charger
1710 SC4	Soft case and belt hook
1720 MS1	Mob stand and power unit
1730 SM-22S	Speaker/microphone
1750 LH2	Deluxe leather case
1770 DC15	Power supply from 12V
1780 TR3-500	70cm handheld trans.
1790 TR3-500	70cm multimode mob
1800 R600	Gen cov rec 150kHz-30MHz
1820 R2000	Gen cov rec
1821 HC 0	World time clock

DATONG	
3880 PC1	Gen cov converter
3870 VLF	Very low frequency converter
3670 ANF	Freq agile audio filter
3660 FL2	Multi-mode audio filter
3660 FL1	Auto filter for receivers
3700 ASP/B	r.f. speech clipper for Trio
3700 ASP/A	r.f. speech clipper for Yaesu
3710 D75	Manual RF speech clipper
3740 D73	Morse Tutor
3750 MIC	Keyboard morse sender
3910 RFA	RF switched pre-amp
3800 AL270	Active dipole indoor
3820 AL370	Active dipole outdoor
3810 AL270-MPU	As above with mains p.s.u.
3830 AL370-MPU	As above with mains p.s.u.
3890 MPU	Mains power unit
3730 RFC/M	RF speech clipper module
3920 P1S1	Tone squelch unit
3640 SFB2	Auto Woodpecker blanker

MICROWAVE MODULES RANGE	
3130 MML28/100-S	10m 100W lin/preamp
3140 MML70/50	4m 50 watt lin/preamp
3150 MML70/100-S	4m 100W lin/preamp
3160 MML144/300-S	2m 30W linear amp
3170 MML144/50S	2m 50W lin/preamp
3180 MML144/100-S	2m 100W lin/preamp
3190 MML144/100LS	2m 100W (1 or 3W i/p)
3200 MML432/30L	70cm 30W lin/preamp
3210 MML432/50	70cm 50W lin/preamp
3220 MML432/100	70cm 100 watt linear
3250 MML435/51	70cm ATV con., VHF out
3260 MML435/600	70cm ATV con., UHF out
3270 MVT435	70cm ATV 20W t'mitter
3290 MML206/144	Converter with keyboard
3300 MML200	RTTY to TV converter
3320 MML4001KB	RTTY term with keyboard
3330 MMS1	The MORSETALKER
3340 MMS2	Advanced morse trainer
3350 MML28/144	10m linear transverter
3360 MML70/28	4m linear transverter
3370 MML70/144	4m linear transverter
3380 MML144/28	2m linear transverter
3390 MML432/28-S	70cm linear transverter
3400 MML432/144-R	70 cm linear transverter
3410 MML21296/144	23cm linear transverter
3425 MMLC27/MW	27MHz to med wave conv
3430 MMLC50/28	10m to 2m up conv
3440 MMLC50/28	6m to 10m down conv
3450 MMLC70/28	4m to 10m down conv
3460 MMLC70/28L	2m to 10m down conv
3470 MMLC144/28L	2m to 10m down conv
3490 MMLC32/28-S	70cm to 10m down conv
3500 MMLC32/144-S	70cm to 2m down conv
3510 MMLC1296/28	23cm to 10m down conv
3520 MMLC1296/144	23cm to 2m down conv
3530 MML1691/137.5	1691MHz Meteoros con
3540 MMA28	10m low noise preamp
3550 MMA14V	2m RF switched preamp
3560 MMA129V	23cm low noise preamp
3570 MML050/500	500MHz digital freq meter
3580 MML050P	600MHz-10 prescaler
3590 MML0P1	Freq counter amp/probe
3620 MMR384	384MHz freq source
3630 MMR15/10	15dB, 10W attenuator

AZDEN	
4000 PCS4000	2m FM transceiver 25W
4130 MEX35	Mobile boom safety mic

FDK	
5779 M.7500X	2m FM/SSB/CW 10W t'ceiver
5782 EXP 430	N 750 70cm transverter
5772 KP100	AC/VFO Electronic Keyer
5780 ATC720	Synth air monitor 110-138MHz
5781 RX40	Synth FM mon 140-180MHz

MUTEK LTD	
5850 SLNA 50s	50MHz low noise switched preamplifier using BF981
5860 SLNA 70s	70MHz low noise switched preamplifier using BF981
5870 SLNA 70u	70MHz low noise unswitched preamplifier using BF981
5880 SLNA 70ub	Unboxed version of SLNA 70u
5890 SLNA 144s	144MHz low noise switched preamplifier using BF981 (0.9dB noise figure)
5900 SLNA 144u	144MHz low noise unswitched preamplifier using BF981
5910 SLNA 144ub	Unboxed version of SLNA 144u
5920 SLNA 145ub	Transceiver optimised preamplifier with antenna c/o switching using BF981. Intended for the FT290R, but has many other applications!
5930 GFBA 144e	Ultra-high performance environmentally housed switched gasfet preamplifier using advanced negative feedback circuitry for superb dynamic performance. Supplied with ATCS 144s controller
5940 TLNA 432s	Very high performance bipolar transistor switched preamplifier for 430-440MHz using BFG69 for 1.4dBm and 0dBm input intercept performance
5950 TLNA 432u	Unswitched boxed variant of TLNA 432s
5960 TLNA 432ub	Unboxed TLNA 432u
5970 GLNA 432u	Series 432 MHz gasfet unswitched preamplifiers
5980 BLNA 432ub	Sub-miniature 1.3dBm BFG69 preamplifier

MUTEK LTD CONT.	
5990 BLNA 1296ub	Noise matched N
6000 RPCB 144ub	Complete replace
6010 RPCB 251ub	for the FT221 and
6020 HDRA 95u-1	Complete replace
6030 HDRA 95u-2	for the IC211 and
6040 BBBA 500u	1.5dB gain varia
6050 BBBA 850u	range 88-108MHz
6060 XBPF 700ub	250-500MHz broad
6070 PPSU 012	dynamic range p
6080 CISA 001	250-860MHz broa
6090 ATCS 144s	amplifier
	Microstrip line
	12V (nominal) ma
	HDRA95 & BBBA
	'UHF' fit to BNC
	Transmit/receive
	sequence and con

WRAASE ELECTRONICS	
4720 SC140	SSTV receive
4730 SC160	SSTV transceiver
4740 SC42A	SSTV TX/RX
4750 SC41	SSTV + FAX
4760 FG42A	Light pen
4760 KB422A	Keyboard
4780 Prince	12" green displ

SLOW SCAN H.F. EQUIPMENT	
5574	Power supply mains, for above
5580	Bearcart BC100 synthesised h/h
5590	Bearcart BC2020B AM/FM VHF/UHF
5550	JII SX200N AM/FM VHF/UHF
5551	JII SX400 26-510MHz AM/FM
5559	Gomscan Synthesised VHF/UHF
5561	AOR2001 Synth. 26-520 AM/FM
5770	Fairmate AS3230 AM/FM VHF/UHF
5780	Corona CD6000 AM airband rec
5781	FDK RX40 pocket synthesised
5782	180MHz
5780	FDK ATC720 pocket synthesised
	receiver

SCANNING RECEIVERS	
5574	Sony ICF7600D Digital receiver
5574	Power supply mains, for above
5580	Bearcart BC100 synthesised h/h
5590	Bearcart BC2020B AM/FM VHF/UHF
5550	JII SX200N AM/FM VHF/UHF
5551	JII SX400 26-510MHz AM/FM
5559	Gomscan Synthesised VHF/UHF
5561	AOR2001 Synth. 26-520 AM/FM
5770	Fairmate AS3230 AM/FM VHF/UHF
5780	Corona CD6000 AM airband rec
5781	FDK RX40 pocket synthesised
5782	180MHz
5780	FDK ATC720 pocket synthesised
	receiver

VHF/UHF AMPLIFIERS	
5340	2M-50W
5350	2M-100W
5360	MR-150W
5370	MR-250W
5380	MR250
5390	AM50

TONO PRODUCTS	
5340	2M-50W
5350	2M-100W
5360	MR-150W
5370	MR-250W
5380	MR250
5390	AM50

TOKYO HY-POWER LABS INC	
5670	HC-150
5680	HC2000
5690	HL-82V
5700	HL-160V
5709	HL-45U
5711	HL90U

ALINCO ELECTRONICS	
5720	ELH230E
5730	ELH710
5740	ELH730
5741	ELH230D
5742	ELH250D

DAVETREND LTD	
4670	VHF/W
4680	4APSU
4690	6APSU
4700	12APSU
4710	24APSU

MAIN BRANCH AT
LONDON
01-992 5765/6
MAIL ORDER PRICES CORRECT AT TIME OF PRESS

NORTHERN BRANCH AT
EARLESTOWN
373 UXBRIDGE ROAD,
ACTON,
LONDON W3 9RH
092 52 29881

38 BRIDGE STREET
EARLESTOWN,
NEWTON LE WIL
MERSEYSIDE



EXCHANGE



EVER AVAILABLE ON ALL LISTED ITEMS ★ RAPID DESPATCH ★ PART EXCHANGE ★

4535 1.3GHz	26.90
ant front-end T225	71.00
ant front-end 251	76.90
high dynamic amplifier	32.90
nd high amplifier and low noise	29.00
ass tv filter 5 psu for 0	6.90
coaxial adaptor angeoveroller	22.60
ard	179.00
oard	299.00
olour	695.00
RX	795.00
	40.25
	149.00
udu	119.00
HF/VHF/UHF	
IEW*	169.00
	6.00
I VHF/UHF	345.00
IHF	258.75
	299.00
P.O.A.	259.00
canner *NEW*	259.00
P.O.A.	
IHF + military	149.00
ver, digital	99.00
iver 140-	132.00
airband	149.00
metres	69.00
metres	129.00
etres	169.00
2 metres	325.00
10 metres	65.00
3cms	159.00
z ATU. 150W	62.50
z ATU. 2Kw	276.55
in 80W O/P	144.50
preamp	
in 150W O/P	242.40
eamp 3 or 10W	
10W I/P 40-	115.00
10W I/P 100W	259.00
3W O/P 1/3W I/P	49.00
10W O/P-1/	59.00
W O/P	
with pre-amp	59.95
O/P 1/3W I/P	99.00
edi)	
ve Module amplifiers!	
450MHz	27.50
J prot.	30.75
J prot.	49.00
su prot.	74.00
u prot.	105.00
mains psu	49.00

MORSE KEYS		
HI-MOUND KEYS		
5430 HK702	Up/down on marble	26.94
5440 HK704	Up/down super deluxe	17.65
5450 HK705	Up/down deluxe	13.80
5460 HK706	Up/down economy	14.60
5461 HK707	Up/down popular	13.75
5470 HK708	Basic unit up/down	13.26
5480 MK704	Squeeze keyer manipulator	12.65
5490 MK705	As 0548 with metal base	21.28
5501	Ex-ministry No. 8 key, original packing	4.95
Bencher Products		
5220 BY1	Keyer paddle (black base)	37.95
5230 BY2	Keyer paddle (chrome base)	48.30
5240 BY3	Keyer paddle (gold plated)	92.00
5250 ZA1A	Balun 3.5-30MHz for dipoles	15.00
5260 ZA2A	Balun 14-30MHz for beam antennas	17.25

RTTY/CW READERS		
Tasco Products		
5400 CWR685E	Tele reader - RTTY/CW/ASCII	769.00
5410 CWR670	Tele reader - as above, RX only	349.00
5420 CWR610E	Tele reader - as above, basic unit	159.00
Tono Products		
5270 9000E	CW/RTTY/ASCII/Editor/lite pen, term L	669.00
5280 550E	CW/RTTY/ASCII/Terminal RX	299.00
5290 350	CW/RTTY/ASCII/Terminal RX only	259.00
5300 CRT120G	VDU 12 inch green screen - mains power	125.00
5310 CRT1200G	VDU 12 inch for 80 columns	136.00
5320 HC800	Line printer centronics	449.00
5330 SK7	Plug adaptors for printers	8.50
ICS Electronics		
4900 AMT-1	Amtor RX/TX	265.00

BNOS ELECTRONICS		
5800 12/6A	Power supply 13.8V 6 amp, fully protected	48.30
5810 12/12A	Power supply 13.8V 12 amp, fully protected	86.40
5820 12/24A	Power supply 13.8V 25 amp, fully protected	125.45
5830 12/40A	Power supply 13.8V 40 amp, fully protected	225.40
5831 L144/1/100	1 watt input linear	138.00
5832 L144/3/100	3 watt input linear	138.00
5833 L144/10/100	10 watt input linear	115.00
5834 LPM144/1/100	1 watt input linear/preamp	172.50
5835 LPM144/3/100	3 watt input linear/preamp	172.50
5836 LPM144/10/100	10 watt input linear/preamp	149.50
5837 L144/25/160	25 watt input linear	155.00
5838 LPM144/25/160	25 watt input linear/preamp	189.50
5839 L144/10/180	10 watt input linear	178.00
5840 LPM144/10/180	25 watt input linear/preamp	212.50

TONNA ANTENNAS F9FT			
50MHz	L(M)	W(Kg)	
6100 5 element	3.5	3.2	34.30
144MHz			
6103 4 element	0.87	0.5	14.95
6110 9 ele fixed	3.3	1.9	17.71
6120 9 ele portable	3.3	1.7	20.00
6130 9 ele crossed	3.5	2.0	32.43
6140 13 ele portable	4.5	2.5	31.05
6150 17 ele fixed	6.60	4.5	37.66
435MHz			
6190 19 element	3.2	1.1	20.70
6199 19 ele crossed	3.3	1.8	34.27
6200 21 element	4.6	2.6	29.62
6210 21 element ATV	4.6	2.6	29.67
144/435MHz			
Oscar Special			
6160 9 & 19 element	3.3	2.0	34.27
1,250MHz or 1,296MHz			
6213 23 element	1.8	0.9	25.90
6214 4 x 23 ele antennas - power splitter - stacking frame			149.00

Full range of J Beam, T.E.T. and Yaesu antennas available!

WELZ		
4980 SP200	1.8-160MHz PWR/SWR	69.95
4990 SP300	1.8-500MHz PWR/SWR	97.00
5000 SP400	130-500MHz PWR/SWR	69.95
5010 SP500	1.8-500MHz PWR/SWR	97.00
5040 SP10X	1.8-150MHz PWR/SWR	24.45
5020 SP15M	1.8-160MHz PWR/SWR	35.00
5030 SP45M	130-470MHz PWR/SWR	51.00
5050 SP250	1.8-60MHz PWR/SWR	49.50
5060 SP350	1.8-500MHz PWR/SWR	59.95
5080 AC38	3.5-30MHz ATU 400w PEP	65.00
5160 TP95X	50-500MHz 0-5W meter	13.95
5121 CA35A	Static protector	10.75
5122 CA23N	Static protector	12.60
5020 CT15A	15/50W dummy load PL259	7.95
5100 CT15N	15/20W dummy load N plug	13.95
5110 CT150	150/400W dummy load	35.50
5120 CT300	300/1KW dummy load	49.50
5130 CT03N	3W dummy load 1.3GHz	30.00
5140 CH20A	2 way coax switch SO239	17.95
5150 CH20N	2 way coax switch N socket	31.95
5133 DF72C	144/430MHz duplexer	18.95

A.R.E. SPECIALS - OUR OWN IMPORTS

ALINCO VHF/UHF AMPLIFIERS	
5720	2m linear 30W O/P 1-3W I/P 49.00
5730	70cm linear 10W O/P 1-3W 59.00
5740	AS 5730 30W O/P 119.00
5741	AS 5720 but with switched pre-amp 69.95
5742	ELH260D 2m linear 50W O/P 1-3W I/P switched pre-amp 114.95

VHF/UHF SCANNING RECEIVER

5770	Fairmate Airband VHF and UHF	149.00
------	------------------------------	--------

ROTATORS

9121	EMR400 Alinco med. duty rotator	79.00
9271	EMRBB Lower mast clamp	10.00

BOOKS

9680	Confidential Frequency List	10.95
------	-----------------------------	-------

WRAASE SLOW SCAN

4730	SC160 TX/RX slow scan boards	299.00
4740	SC422A Complete TX/RX memories	645.00
	Display models of above	475.00
4775	SC1 Full s/scan + Fax TX/RX	795.00

VHF/UHF TRANSVERTERS

FTV107	Yaesu Transverters modified for use with:	
	YAESU	
FT102/FT980/FT ONE/FT757	= £125	
	TRIO	
TS930/TS430	= £135	
	ICOM	
IC740/IC745/IC751/IC720A	= £125	
All above complete with 2M module, cables.		
Fitted with 2M/70cm card - £359		
Free carriage on all A.R.E. Specials		

Just write or pick up the phone, quote the Stock Number together with your Access or Barclaycard and the goods are despatched within 24 hours!

If the particular item you require is not listed, dial 01-992 5767 or 092 52 29881 - Brenda and Bernie pride themselves in supplying anything in Amateur Radio!

All items over £100 carriage free. For 24 hour Securicor add £6.00. Below £100 add £2, Books £1. All Beam Antennas Securicor only. Goods despatched within 24 hours if held in stock.

FULL DEMONSTRATION FACILITIES AVAILABLE AT LONDON AND MERSEYSIDE. POP-IN, HAVE A CHAT ABOUT THAT NEW RIG AND A CUP OF BRENDA'S COFFEE!

24 HOUR ANSWERPHONE SERVICE AT BOTH PREMISES AVAILABLE

OPENING HOURS
ACTON: 9.30 to 5.30. Closed Wednesday
EARLESTOWN: 10.00 to 5.00. Closed Monday



Put the thrill-power back into your programs with **BIG K!**

KEVIN WAS ONCE AN OBSESSIVE, INTROVERTED MIDNIGHT HACKER...

DURN BUG'S GOT TO BE IN HERE SOMEWHERE - YAWN!

...UNTIL ONE DAY HE DISCOVERED **BIG K!**

GOSH! THIS IS A-MAZE-ING!

NOW BUGS ARE A THING OF THE PAST...

...THANKS TO **BIG K!**

BIG K is the nation's most colourful, fact-filled, stylish, unusual, obnoxious and irritatingly well-informed computer games magazine.

BIG K gives you -
Great games listings for the top micros. Reviews to drive you insane with excitement. Technical know-how to make your fingers itch. Facts to help you expand your micro and your brain.

FREE C15 COMPUTER CASSETTE WITH EVERY COPY

BIG K - On sale 15th March

85p

**MULLARD
Cathode-ray Tubes
OLD SYSTEM**

CONSTRUCTION		PHOSPHOR COLOUR	SCREEN SIZE	SERIAL NUMBER
FOCUS	DEFLECT			
A	ES	Blue	The diameter or diagonal of the luminescent screen in cm	
D	ES	Purplish Blue		
M	Mag	Orange		
		Yellow-Green		
		Green		
		Blue		
		Green		
		Orange		
		Purplish Blue		
		Yellow-Green		
		Purplish Blue		
		Blue		
		Purplish Blue		
		White		
		Tricolour Screen		
		Yellow-Orange		

**PRO-ELECTRON
Cathode-ray Tubes**

PRIMARY APPLICATION	SCREEN SIZE	SERIAL NUMBER	SCREEN PROPERTIES COLOUR GROUP	SCREEN PROPERTIES SERIAL LETTER
A Domestic TV	The diameter or diagonal of the luminescent screen in cm	Two or three figures	A Purple	Indicating colour shade/persistence, etc.
D Single-trace oscilloscope			B Blue	
E Multiple-trace oscilloscope			D Blue-green	
F Direct-viewing radar			G Green	
L Display storage			K Yellow-green	
M Professional TV (direct-viewing)			L Orange	
P Professional TV (projection)			R Red	
Q Flying-spot scanner			W White	
			X Tricolour screen	
			Y Yellow	

e.g.

A 6 3 - 2 0 0 X

**MULLARD
Cold Cathode Tubes
OLD SYSTEM**

BASE TYPE	SERIAL NUMBER	FUNCTION
Z indicating a cold cathode gas-filled tube	As in Pro-Electron receiving valve code	A Amplifier tube (continuous operation)
		B Binary counter or switching tube
		C Multi-stage counter tube
		E Electrometer trigger or amplifier tube
		G Gating tube
		M Indicator (metering) tube
		S Multi-stage switching tube
		T 3-electrode Trigger Tubes
		U 4-electrode
		V 5-electrode

e.g. Z 8 0 3 U

**MAZDA
Cathode-ray Tubes
for television**

CONSTRUCTION	SCREEN SIZE	SERIAL NUMBER	SUFFIX LETTER
MONOCHROME TUBES	The overall diameter or diagonal of the screen in inches		
FOCUS DEFLECT			
CME E/S Mag CRM Mag Mag			
COLOUR TUBES			
CTA			Indicates some modified feature

e.g.

C M E 2 0 1 3

**MULLARD
Photocells**

BASE TYPE	SERIAL NUMBER	PHOTOCATHODE SURFACE	CLASS OF PHOTOCELL
As in Pro-Electron receiving valve code	As in Pro-Electron receiving valve code	A Caesium-antimony	G Gas-filled
		C Caesium on oxidised silver	V High-vacuum

e.g. 9 0 C V



Advanced Micro Devices

AMI.

American Microsystems Inc.



Analog Devices



Avel-Lindberg Ltd.



AVO Ltd.



Belling Lee



Burr Brown International



Cherry



Corin Tech Ltd.

DATTEL

Dattel Systems



Eimac



Emihus Microcomponents Ltd.

EMM SEMI

EMM/Semi. Div. of Electronic Memories and Magnetics



English Electric Valve Company Ltd.




Eurotechnique



Exar Integrated Systems

FAIRCHILD

Fairchild Semiconductor Systems

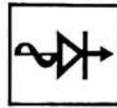

Ferranti Semiconductors



The General Electric Co. PLC



General Instrument



General Radio Company
Now GenRad



Gould Electronic Components Division



Harris Semiconductor



Hewlett Packard



Hitachi



Hybrid Systems



International General Electric of New York



International Rectifier



Intel




INTERSIL

Intersil Incorporated



ITT Semiconductors

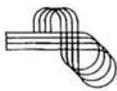

Jackson Bros.



Lambda Electronics Co.



Lansdale Transistor & Electronics Inc.

Lucas

Lucas Electrical Co. Ltd.



Mallory Distributor Products



Matsushita Electronics Corp.



Merrimac Industries Inc.



Micro Electronics Ltd.



Microwave Associates Inc.




Microwave Semiconductor Corp.



Mitsubishi Electric Co.



Motorola Semiconductor Products

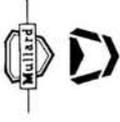

Mullard



National Semiconductor



New Jersey Semiconductor Products Co. Inc.

NEC

Nippon Electric Co. Ltd.



North American Semiconductor

PHILCO

Philco Radio Television Ltd.



Philips



Pioneer



The Plessey Company



Rendar Components



Rank Electronic Tubes



Raytheon



RCA



Remo Components



Rockwell International



RS Components Ltd.



Sanken



SGS-ATES Group of Companies



Siemens



Signetics



Siliconix Ltd.



Silicon General



Solid State Scientific Ltd.



Standard Microsystems Corp.



Standard Telephones & Cables



Sylvania Radio Tubes



Texas Instruments



Thompson-CSF



Toshiba



Transistor AG (TAG)



Wandel & Goltermann



Welwyn Electric Ltd.

DW REVIEW

ICOM IC-R70 Communications Receiver



Icom's first h.f. receiver, the IC-R70 uses microprocessor technology to provide the alternatives of a general coverage receiver with 1MHz bands or an amateur bands receiver with rapid band selection.

The use of a microprocessor to control all the mode switching as well as band selection offers versatility although, of course, the front panel is now covered with a multitude of push-buttons rather than knobs.

The set, or rather the two sets tried, were fitted with the optional f.m. module. Two sets were tried as the first one had a pre-amplifier that was lacking in gain and not working at all at the lower frequencies. The second set met specification throughout.

Description

The receiver uses a quadruple conversion system using the third and fourth conversions to give a continuous bandwidth control. The first i.f. is at 70.451MHz and the second is 9.0115MHz. This is then mixed with the output of a variable crystal oscillator to give the third i.f. of 455kHz. This signal is then passed through the appropriate 455kHz crystal filter and mixed again with the output of the v.x.o. to restore the signal back to 9.0115MHz. This allows the pass-band to be varied to reduce interference from signals that are close in frequency to the desired signal.

The R70 uses two digital v.f.o.s which can be used independently on any desired band. The triple phase locked loops are controlled by the microprocessor system and frequency can be changed in either 10Hz, 100Hz or 1kHz steps at the press of the appropriate button.

At the front-end, band-pass filters d.c. switched under the control of the MPU, are provided for each band. The signal then passes either through the attenuator or pre-amplifier, or neither,

as decided by the front panel switching. After mixing twice in two double balanced mixers the second i.f. signal passes through the appropriate band-pass filter, again selected by the MPU system, before being mixed down to the third i.f. for pass-band tuning. A noise blanker operates on the second i.f. ahead of the band-pass filters. If the f.m. option is fitted the signal, at third i.f., is once again filtered before passing to the limiters and discriminator. On a.m. or s.s.b. the third i.f. passes through the appropriate crystal filter before remixing with the v.x.o. output to produce the fourth i.f., which is the same as the second i.f. This is then passed through the variable notch filter before being demodulated. The squelch switching operates on all modes, the switch following the detectors.

The use of separate filters for each band together with the MPU control means that band changing is simply a matter of button pushing. When changing bands the MPU system automatically selects a frequency 1MHz up or down when set for GENERAL COVERAGE but selects a reference frequency 100kHz above the bottom band edge when in the HAM mode. The frequency "rolls over" at the band edges and for the amateur bands these are set to give coverage of all the variations worldwide.


Controls

The display is of the green luminescent type and shows the frequency tuned on the right with the mode and v.f.o. selected on the left.

An analogue S-meter is fitted alongside the frequency display. The main tuning knob, which has an adjustable brake, is comfortable to use, and in fact all the controls are easy to operate and grouped reasonably well. The exceptions to this being the dual concentric controls for AF GAIN/RF GAIN and SQUELCH/TONE. Both of these had the legends on the panel printed underneath the knobs which made it impossible to read when viewed normally. The control system automatically switches from u.s.b. to l.s.b. below 10MHz. Hence above 10MHz SSB-N refers to u.s.b. while below 10MHz it refers to l.s.b.

Memory

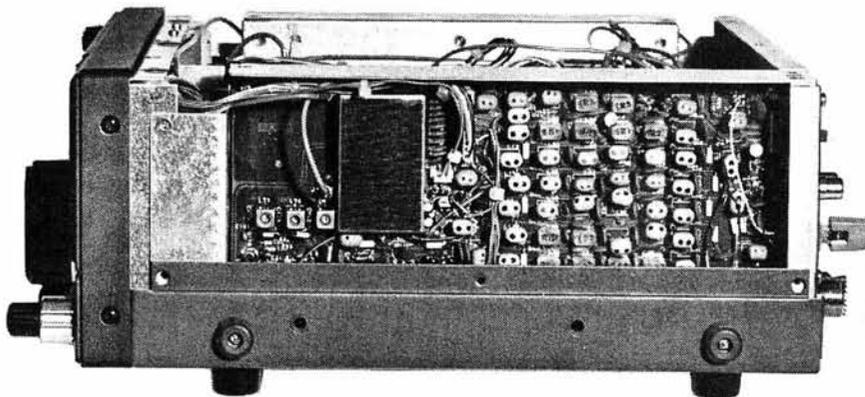Either of the two v.f.o.s can be selected and when changing v.f.o.s the frequency of the initial v.f.o. is stored in the memory enabling it to be used again. Re-selecting the first v.f.o. stores the frequency of the second v.f.o. in the same manner. The frequencies of both v.f.o.s can be equalised, either setting VFO A to the same frequency as VFO B or vice versa.



★ test measurements

Sensitivity:

Freq. (MHz)	Input e.m.f. (μ V) for 10dB (S + N)/N		Input e.m.f. (μ V) for S9 (s.s.b.)	Pre-amp gain (dB)
	c.w.*/s.s.b.	a.m.		
1.81	0.34	2.3	248	6.5
3.51	0.36	2.2	254	7.1
7.01	0.27	2.0	219	8.4
10.11	0.27	1.9	215	8.9
14.01	0.26	1.9	237	7.3
18.11	0.30	2.2	265	5.9
21.01	0.34	1.9	231	7.1
24.91	0.28	2.1	271	5.7
28.01	0.26	2.1	231	7.1
29.01	0.26	2.0	226	7.3
29.01	0.67 μ V e.m.f. for 12dB SINAD on f.m. (3kHz dev. at 1kHz)			

* The CW-N position improves sensitivity by 3dB

Squelch threshold: 0.4 μ V min.
1.2 μ V max.

S-Meter calibration: (At 14.01MHz u.s.b.)

Reading	Input required	
	μ V e.m.f.	dB μ V
S1	6.0	16
S2	8.2	19
S3	11.7	22
S4	17.7	25
S5	28.0	29
S6	45.0	33
S7	76.0	38
S8	134.0	43
S9	237.0	48
+20dB	1.3mV	63
+40dB	15mV	84

★ specification

Frequency coverage:

Amateur Bands: 1.8— 2MHz (160m)
3.5— 4.1MHz (80m)
6.9— 7.5MHz (40m)
9.9—10.5MHz (30m)
13.9—14.5MHz (20m)
17.9—18.5MHz (17m)
20.9—21.5MHz (15m)
24.5—25.1MHz (12m)
28.0—30.0MHz (10m)

General coverage: 0.1—30.0MHz in 30
1MHz segments

Tuning steps: 1kHz, 100Hz or 10Hz

Frequency readout: 6-digit, 100Hz resolution

Sensitivity (min) with pre-amp ON:

Mode	Input for 10dB (S+N)/N	
	<1.6MHz	>1.6MHz
SSB/CW/RTTY	1 μ V	0.15 μ V
AM	3 μ V	0.5 μ V
FM	—	0.3 μ V for 12dB SINAD

RF Attenuator: 20dB

Image rejection: Better than 79dB

I.F. rejection:

Receiver tuned to (MHz)	Input signal (MHz)	I.F. rejection (dB)
29.01	70.4515	76

Selectivity:

WIDTH control at maximum, I.F. SHIFT centred

Mode (B/W)	-6dB	-60dB
SSB	2.1kHz	3.4kHz
CW (N)	550Hz	1.4kHz
AM	5.5kHz	11kHz
FM	14kHz	21kHz

RIT: \pm 1kHz

AGC: Output change for 110dB input change, relative to 9 μ V threshold: 0.5dB

RF attenuator: 20dB

Notch filter: 30dB approx. at 1kHz
Tunable 250Hz—2.1kHz

Audio output: 1.2W into 8 Ω with 0.6% t.h.d. on 1kHz, for 100 μ V input at 14MHz.

Adjacent channel rejection:

a.m. 60dB at 950kHz (9kHz channel spacing)
f.m. 80dB at 29.6MHz (25kHz channel spacing)

Frequency stability: Less than 250Hz from 1 min. to 60 min. after switch-on
Less than 50Hz thereafter
Less than 500Hz from -10° to +60°C

Selectivity: WIDTH control at maximum

Mode	-6dB	-60dB
SSB/CW/RTTY	2.3kHz	4.2kHz
CW (N)/RTTY (N)	500Hz	1.5kHz
AM	6kHz	18kHz
FM*	15kHz	25kHz

* Option

Spurious response rejection ratio: More than 60dB




Audio output: More than 2W in 8 Ω

Antenna impedance: 50 Ω unbalanced (or single wire below 1.6MHz)

Power requirements: 117V or 235V \pm 10%, 50/60Hz, 30VA (110/200/220V by internal modification)

Dimensions: 111 x 286 x 276mm

Weight: 7.4kg

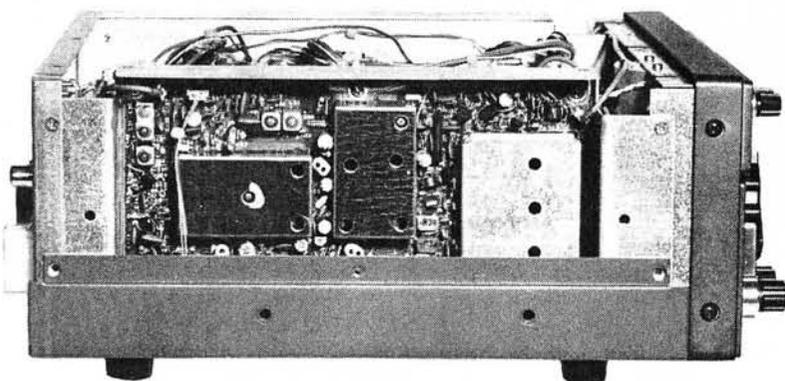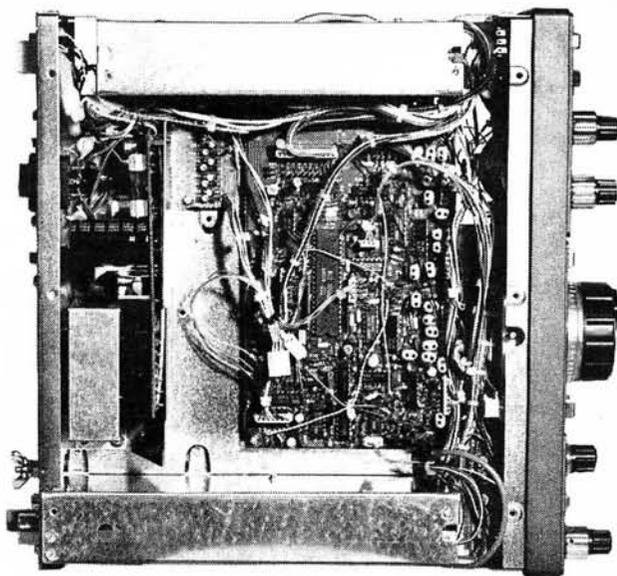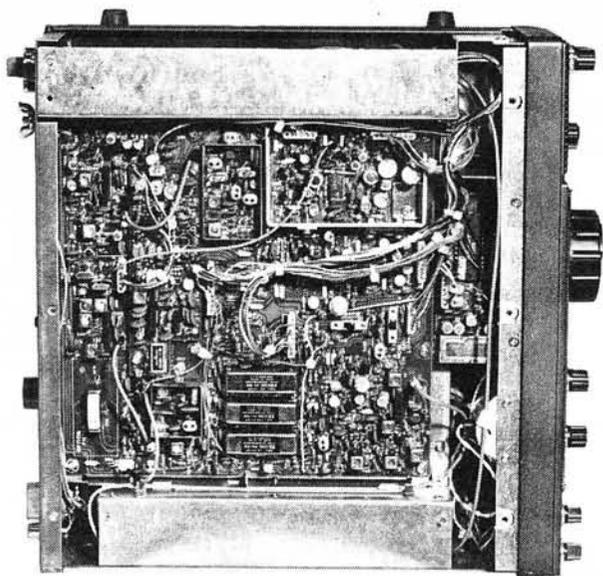

The squelch threshold is controlled by the inner knob of a dual-concentric knob, the outer being TONE, and the squelch is operative on all modes. If you are not aware of this initially then you could be caught out and think that the set was faulty—we were!

The back panel carries the antenna sockets on one side and the external speaker jack, mute terminal and accessory socket on the other. The mute terminal is for use with a transmitter, grounding it mutes the set and monitors the transmitter. The 24-way accessory socket provides access to various parts of the control system as well as supply rails and signals.


Handbook

The handbook follows the usual Icom layout explaining the operation of the various controls together with a circuit description and block diagrams. A full circuit diagram and printed circuit board layout drawings are also provided. Full instructions are given in the handbook for the installation of the various options and this is followed by a troubleshooting table to enable you to find out just what controls you have not set correctly!

Price

The IC-R70 costs £499 incl. VAT. The sets tested were loaned by **Thanet Electronics, 143 Reculver Road, Herne Bay, Kent. Tel: 02273 63859** to whom we extend our thanks.

Dick Ganderton

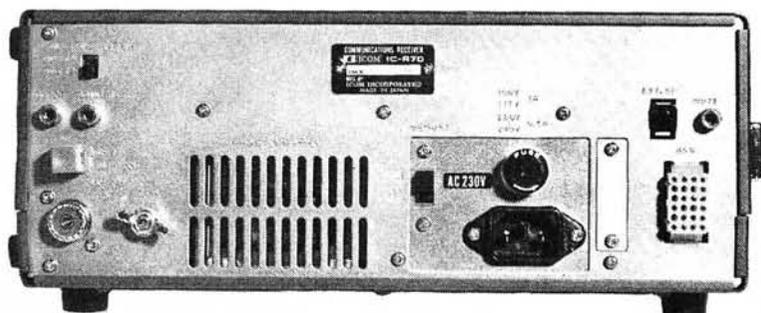

Building an HF Linear Amplifier and ATU



Part 1

by I. Buffham

BSc CEng MIEE G3TMA

In these days of increasingly complex equipment packed with dozens of integrated circuits and microprocessors it is becoming more and more difficult for the average amateur to build transmitters or receivers to compare favourably with the latest Japanese black boxes.

Fortunately two areas remain where the resourceful amateur can still beat the commercial manufacturers at their own game and save a great deal of money in the bargain! These two areas are h.f. linear amplifiers and antenna tuning units and examples can be seen in the photographs which show the author's station consisting of a Drake "C" line driving a home-made linear amplifier and a.t.u.

The purpose of this article is to serve as a guide to the production of similar equipment. It is not intended that the equipment described should be built exactly as described because of the difficulty of finding suitable identical components in sufficiently large quantities.

Outline Specification

It probably goes without saying that the aim of most constructors in

building an h.f. linear will be to achieve a p.e.p. output of at least 400 watts at the highest frequency of interest.

However, the one factor which has the greatest influence on the design of the amplifier is not the required power output but the available driving power from the station transmitter.

Some transceivers only have an r.f. output of 10 watts and so the linear preamplifier will be required to have a high power gain. This is only achievable by the operation of a valve in class AB1 or AB2 with the attendant complications of having to provide a stable screen grid supply, negative bias supply, neutralisation, and input tuning of the amplifier.

Fortunately most transceivers have a power output of around 100 watts p.e.p. permitting the construction of a class B grounded-grid amplifier with low power gain. Class B amplifiers are relatively easy to construct since they do not require screen grid or negative bias supplies or neutralisation. Also, in some amplifiers input tuning may be dispensed with.

The amplifier constructed by the author is a class B design and the front view is shown in the photographs.

Choice of Valve

After choosing the class of operation of the amplifier the next most important decision is the choice of the valve to be used. Many power triodes are available which are suitable for use in grounded-grid amplifiers and most of them may be rejected on the grounds of cost. Another consideration is the h.t. voltage required. In general the lower the h.t. voltage the simpler the construction of the amplifier. High h.t. voltages present problems with pi network component ratings and power supply construction.

The input impedance of the valve is also of interest. For grounded-grid amplifiers the input impedance, Z_{in} , is given by:—


$$Z_{in} = \frac{(\text{Peak r.f. driving voltage})^2}{2 \times \text{driving power}}$$

Provided Z is in the range 40–100 ohms then input tuning of the amplifier can be avoided.

A further consideration is the maximum frequency at which the valve may be used at full ratings, especially if the full 400 watts p.e.p. output is required on 28MHz!

Finally, in the interests of constructional simplicity, it is worth trying to

Practical Wireless, April 1984

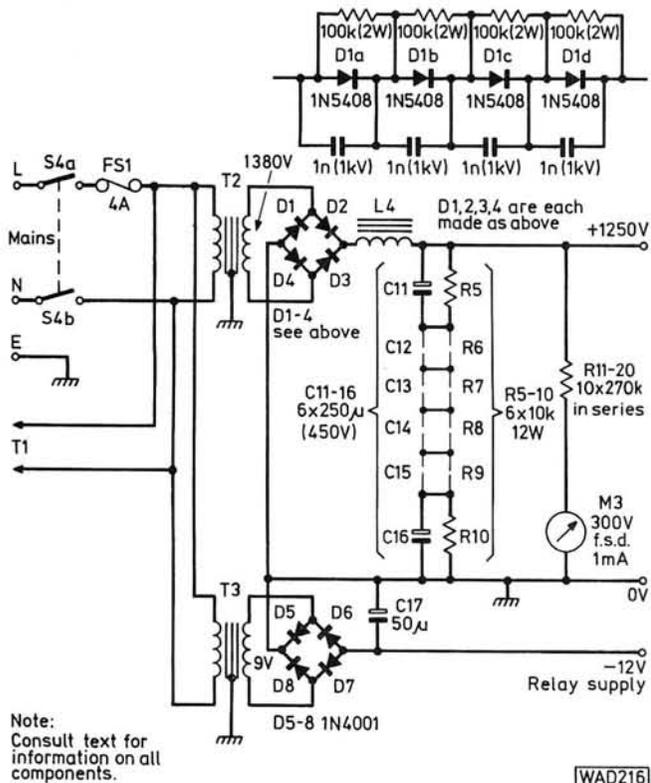

Note:
Consult text for
information on all
components.

WAD216

Fig. 1.1: Circuit of the power supplies for the linear amplifier


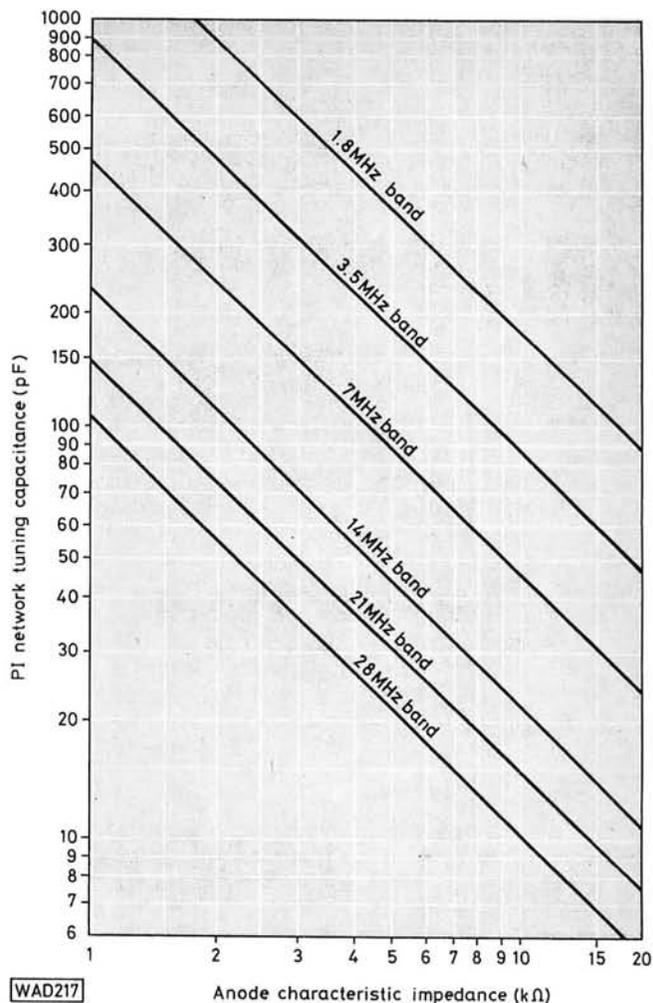
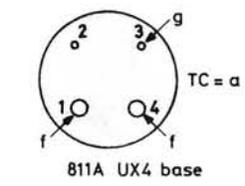


Fig. 1.2: Graph for determining the pi network tuning capacitance for the different amateur bands

(Courtesy of ARRL Radio Amateurs Handbook, 1966)

WAD217

Fig. 1.3: Circuit of the h.f. linear amplifier described in this article

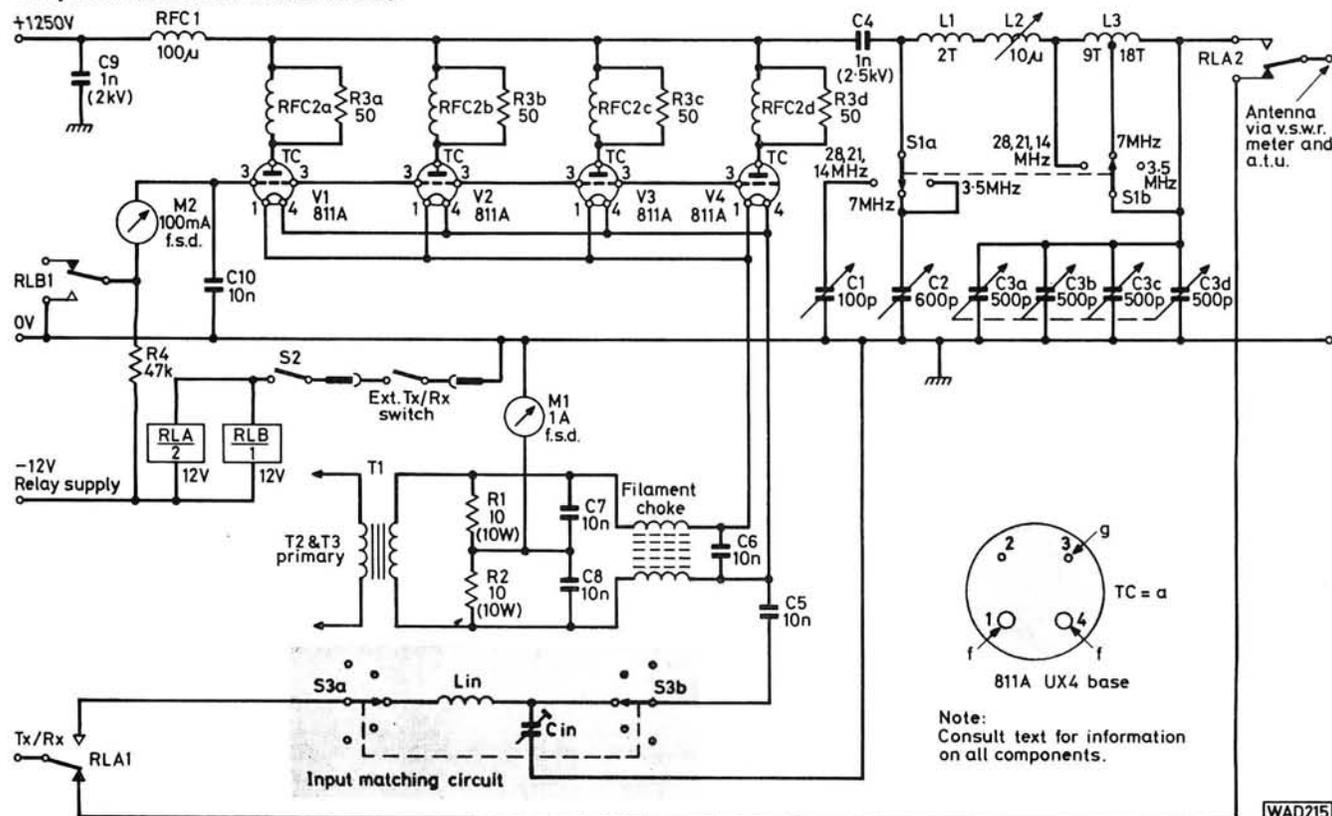

Note:
Consult text for information
on all components.

WAD215

choose a valve which does not need any forced air cooling.

The characteristics of some common valves are listed in Table 1.

After much deliberation it was decided to construct the amplifier based on four 811A valves in parallel. The input impedance of such an arrangement will be 322/4 ohms i.e. 80 ohms so input tuning can be avoided. Also, as the 811A only requires an h.t. rail of 1.25kV the voltage ratings required for the pi network components are modest. One further advantage of the 811A is that despite being a pre-1939 design it has instant-heat filaments and so is ready for use immediately on switch on—just like a transistor!

The possibility of building a transistor amplifier was briefly considered but discarded on grounds of cost and technical difficulty. No doubt in the future home-built 400W solid-state amplifiers will become commonplace but valves are a much better bet for the time being.

Circuit Design

Having selected a valve for the amplifier it is then possible to proceed with the circuit design. A suitable circuit is shown in Fig. 1.3.

Filament Circuit: It can be seen from Fig. 1.3 that a bifilar wound r.f. choke is included in the filament circuit. This is to enable the filaments to be kept above r.f. ground. Such a choke can be simply constructed by making a bifilar winding of 1.5 mm² pvc insulated copper wire along the entire

Table 1. Parameters of some common valves

Valve	Supply (kV)	Max. Frequency (MHz)	Input Impedance (Ω)	Power Output (W)	Notes
811A	1.25	60	322	165	Grid and screen joined
813	2.5	30	376	219	
572B	2.5	30	275	400	Needs chimney and blower
3-500Z	3.5	110	80	750	

length of a ferrite rod 150mm long. Voltage drop across the choke should be very small but it is important to measure the filament volts **at the valve pins**. If necessary the primary taps of T1 should be adjusted to ensure the correct voltage at the valve pins (6.3V at 4A per valve). T1 should be mounted close to the valves to minimise lead lengths and voltage drops.

Ideally the secondary of T1 (7.5V r.m.s. at 16A) should have a centre tap to provide the h.t. ground return, but if such a transformer cannot be found a centre tap can be artificially provided by means of two resistors (R1,2) as shown in Fig. 1.3.

Input Circuit: A generalised input circuit is shown in Fig. 1.3. As explained earlier, with the correct choice of valve no input tuning will be necessary. If input tuning is required then this can be provided by a separate "L" network (Lin/Cin) for each band. The "L" network can be set up by connecting a v.s.w.r. bridge between the transmitter and amplifier

and adjusting the trimmer capacitor (Cin) for 1:1 v.s.w.r.

Anode Circuit: The principal component in the anode circuit is the r.f. choke, RFC1. This is designed to isolate the h.t. supply from the anode circuitry and so must have a sufficiently high reactance at the lowest frequency of interest. A value of inductance of 100μH will usually suffice. (i.e. a reactance of 2200 ohms at 3.5MHz.) The choke must be capable of handling voltages of up to twice the h.t. voltage and it must be capable of handling the anode current. Also, the choke must have no resonances within the amateur bands. If there are any such resonances the choke will absorb large quantities of r.f. energy and emit smoke. This problem may be overcome by adding or removing a few turns from the choke and checking all bands again. A suitable choke can be made by winding 24 s.w.g. enamel wire to a length of approximately 87mm on a 20mm diameter ceramic former.


Also in the anode circuit are the antiparasitic chokes RFC2/R3. Identical chokes are fitted in each valve anode and they consist of four turns of 14 s.w.g. wire, 15mm in diameter wound over a 50 ohm 2W solid carbon resistor. The object of fitting these chokes is to suppress any possible v.h.f. parasitic oscillations in the amplifier.

The final component to be considered in the anode circuit is the capacitor C4. The task of C4 is to block the h.t. from the pi network whilst allowing the r.f. power through. The d.c. rating of the capacitor must be at least twice the h.t. voltage and a suitable value would be 1nF.

PI Network Design

The purpose of the pi network is to efficiently transfer energy from the high output impedance valves into the 50 ohm load presented by the antenna. In Fig. 1.3 the components in the pi network are C1, C2, C3, L1, L2 and L3. The transfer of energy can be accomplished by more than

Practical Wireless, April 1984

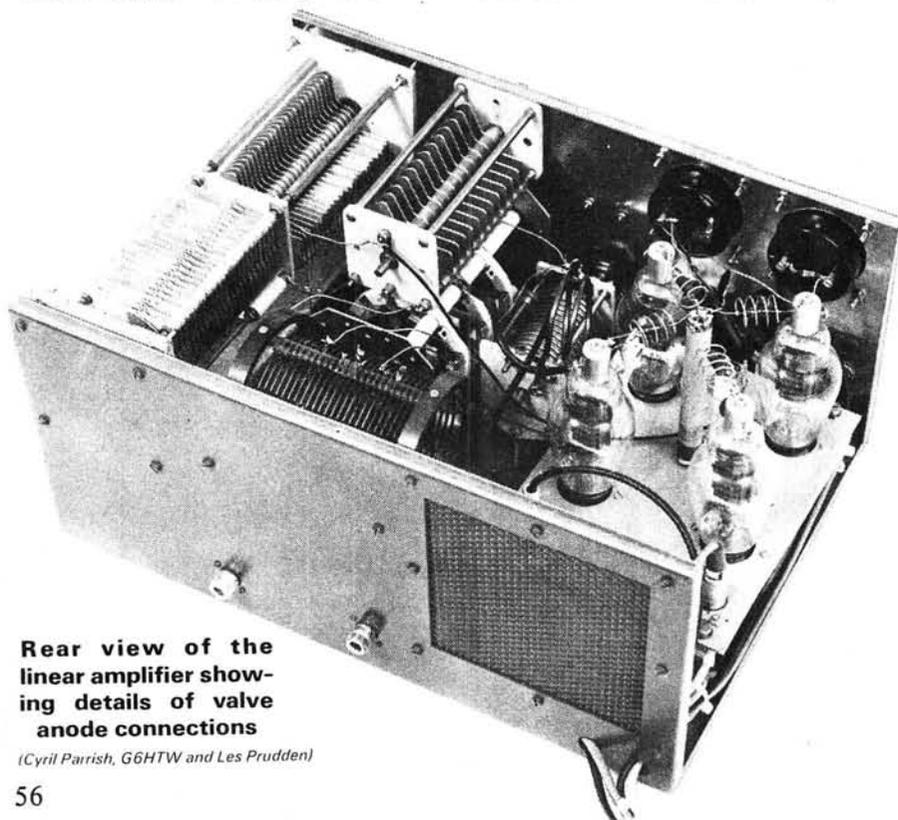

Rear view of the linear amplifier showing details of valve anode connections

(Cyril Parrish, G6HTW and Les Prudden)

Most of the components used in this project will have to be painstakingly gathered together from amateur radio rallies. Only attempt this design if you have the ability to modify the construction and design to suit the components available. Please do not ask *Practical Wireless* or the author for information on how and where to obtain the components.

one set of values of L and C at one particular frequency. However, by varying the L/C ratio the Q of the pi network changes. If the Q is too high then there will be very high circulating currents in the pi coil causing losses. If the Q is too low then the network will provide reduced harmonic suppression. An optimum value of Q is around 10 and Fig. 1.2 provides a means of determining the value of pi tuning capacitance on various amateur bands. For four 811As in parallel the ratio of anode voltage to anode current (anode characteristic impedance) is 1250V/400mA or about 3.1k Ω .

Hence the value of tuning capacitance required for 3.5MHz is 300pF. The value of tuning capacitance required for 28MHz is 35pF. However, the output capacitance of the four valves in parallel is 22.4pF and so the pi tuning capacitor is only required to have a value of 12.6pF. It is difficult to find 300pF tuning capacitors which have a minimum capacitance of 12pF and so it was decided to fit two tuning capacitors in the amplifier. C1 is a 100pF capacitor with a minimum capacitance of 8pF and is switched in on the bands 14–28MHz. C2 is a 600pF and is switched in for the 3.5 and 7MHz bands. C3 is the loading capacitor and consists of four ganged 500pF broadcast capacitors.

The pi tank coil consists of L1, L2 and L3. L1, the 28MHz coil, is two turns of 10 s.w.g. copper wire, 45mm diameter and 32mm long. (L2 is set to minimum for 28MHz.) L2 is the pi coil for 21 and 14MHz and consists of a small "roller coaster" of approximately 10 μ H inductance. This coil will also be suitable for the 18 and 24MHz bands as they become available and the use of a "roller coaster" obviates the need for a 7 position bandswitch.

Practical Wireless, April 1984

The pi coil for 3.5 and 7MHz (L3) consists of 27 turns of 12 s.w.g. wire 100mm diameter and 124mm long with 9 turns used for 7MHz and 27 turns for 3.5MHz. When initially tuning the amplifier on each band it is worth comparing the value of pi tuning capacitance actually used with the value obtained from Fig. 1.2. If necessary the pi inductor value should be changed so that the correct value of tuning capacitance is used. This will ensure operation of the pi network at the correct value of Q .

Metering and Tx/Rx Switching

Meters are included in the amplifier for measuring anode current and grid current. The anode current meter M1 is included in the negative lead of the h.t. supply to ensure that the meter is not at a high potential above ground. The grid current meter is M2. It is important to monitor grid current since this will give an indication of the tuning state of the amplifier.

If the correct pi network values are used and the amplifier is connected to a 50 ohm load the grid current will rise linearly with anode current as r.f. drive is applied. However, if incorrect pi network values are used or if the antenna has a high v.s.w.r. then grid current will rise rapidly as r.f. drive is applied with no corresponding increase in anode current.

Two heavy duty relays, RLA and RLB, are used to control the am-

plifier's transmit/receive switching. In the receive position the amplifier is by-passed enabling the antenna to be connected directly to the transmitter/receiver. Switch S2 is a front panel switch enabling the amplifier to be switched in and out of circuit as required.

Power Supply


In the receive condition it is necessary to apply a small negative voltage to the valve grids in order to cut them off. This is achieved by RLB. A 12V negative supply is used for the relay coils and this supply is also used to cut-off the valves.

The power supply for the amplifier is shown in Fig. 1.1.

An h.t. supply rail of 1250V is required and this can be achieved in a number of ways depending on the components to hand. I was able to track down an h.t. transformer having a 1380V secondary. This will give the required 1250V d.c. with a choke input filter (d.c. voltage is 0.9 \times a.c. voltage). However, an h.t. transformer with a secondary of 884V will give 1250V d.c. when used with a capacitor input filter (d.c. voltage is 1.414 \times a.c. voltage).

The capacitor input filter approach is the preferable one but the final choice of circuit depends on the h.t. transformer which can be obtained.

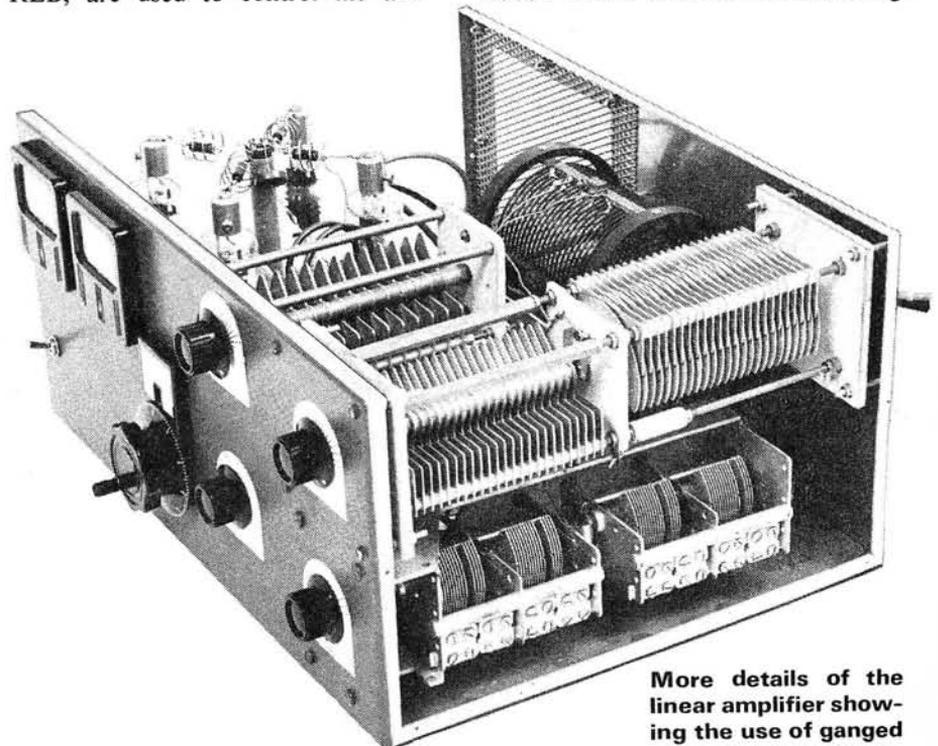Each of the diodes D1–D4 consists of four 1N5408 diodes in series to give a total peak inverse rating of 4000V and a forward current rating



More details of the linear amplifier showing the use of ganged variable capacitors

(Cyril Parrish, G6HTW and Les Prudden)

of 3A. Each diode is shunted by a 1nF 1kV disc ceramic capacitor to give protection from mains spikes and a 100kΩ 2W resistor to equalise reverse voltages across the diodes. The theoretical reverse voltage rating for D1-D4 is 1.4 × transformer secondary voltage i.e. 1.4 × 1380V, 1932V, but it is good practice to have a substantial safety margin.

A disadvantage of the choke input filter is its poor regulation at low currents. At low currents the filter behaves as a capacitor input filter and the output voltage will rise to 1380 × 1.414V i.e. 1952V. However, once a critical value of current is taken from the supply the output voltage will drop to the correct level of 0.9 × secondary voltage. This critical level of current is determined by the size of the choke L4 and can be determined from:

$$L4 = \frac{\text{Required Supply Voltage (H)}}{\text{Supply Current (mA)}}$$

The standing current taken by four 811As in parallel is 100mA, hence a choke with an inductance equal to or greater than 1250/100, i.e. 12.5H, is required. So the h.t. supply will give an output voltage of 1952V off load but will immediately drop to the required value of 1250V when the amplifier is switched to transmit.

The smoothing capacitor bank C11-16 consists of six 250μF, 450V capacitors in series to give a total capacitance of 41μF at a working

WARNING

The h.t. voltage used in this project is dangerous. Treat all parts of the circuit with respect. Play safe and keep one hand in your pocket.

voltage of 2700V. The resistor chain R5-10 is fitted to equalise the voltage across the capacitors and also to discharge them on switching off. Each resistor is rated at 10kΩ, 12 watts, giving a total resistance rating of 60kΩ at 72 watts. A resistance of 60kΩ connected across a 1952V supply will give a current flow of 32mA. This is not sufficient to cause the voltage to drop to its final stable voltage of 1250V but it is sufficient to drop the voltage to some intermediate value. In the case of the author's supply the resistor chain drops the off-load voltage to approximately 1450V.

The voltmeter (M3) used was a 300V d.c. 1mA f.s.d. meter with 10 resistors, each 270kΩ, in series to give a 0-3kV meter.

A -12V supply is also required for the relays and to cut-off the valves during receive periods. This is simply provided by the transformer T3 with a bridge rectifier and capacitor input filter. The diodes D5-D8 are rated at 100V p.i.v., 1A and the capacitor (C17) is 50μF, 25V working.

Component Collection

Once the design of the amplifier has been established the most difficult

and time consuming part of the exercise can begin. This is the collection of suitable tuning capacitors, coils, valves, transformers, chokes etc. The nature of the components is such that it is not economic to try and buy brand new ones from manufacturers. However, six months of determined visits to mobile rallies, junk sales, exhibitions and local amateurs should be long enough to assemble a formidable collection of heavy duty components!


Metalwork

Having collected the major components it is then necessary to consider how they should be housed. There may be a great temptation to use a cabinet which is already to hand but Murphy's Law generally dictates that such a cabinet will be either slightly too small or the wrong shape. The only way to achieve a reasonable finished product is to design and build a cabinet specially to house the components which have been collected. The first step is to determine the physical layout of the major components and the only precaution to take is to ensure that the valves, the h.f. pi coil and the h.f. tuning capacitor are kept as close together as possible in order to minimise lead lengths. A sketch can then be made of a cabinet of ideal size to house the components. The sketch made for the author's amplifier is shown in Fig. 1.4. The cabinet consists of two parts. A heavy duty chassis of 14 s.w.g. aluminium and a wrap-over cover of 20 s.w.g. aluminium. Two 150mm square cut-outs are provided for ventilation of the valves. Some lucky amateurs may have sufficient workshop facilities to be able to build the cabinet themselves but most of us will have to resort to getting the names of local sheet metal workers from Yellow Pages. Three or four local sheet metal companies should be sent a copy of the sketch with a request for a quotation. In these difficult times of recession it should be possible to get quite reasonable quotations!

Once the cabinet has been constructed then follows the relatively easy task of mounting and wiring all the components. In the case of the author's amplifier the valves are mounted on a small subchassis plate. A separate cabinet is used to house the power supply unit. Any large, sturdy metal box can be used.

Part 2 of this article will cover the design and construction of a suitable v.s.w.r. meter and a.t.u. for use with the linear amplifier.

Fig. 1.4: Sketch of the author's metalwork

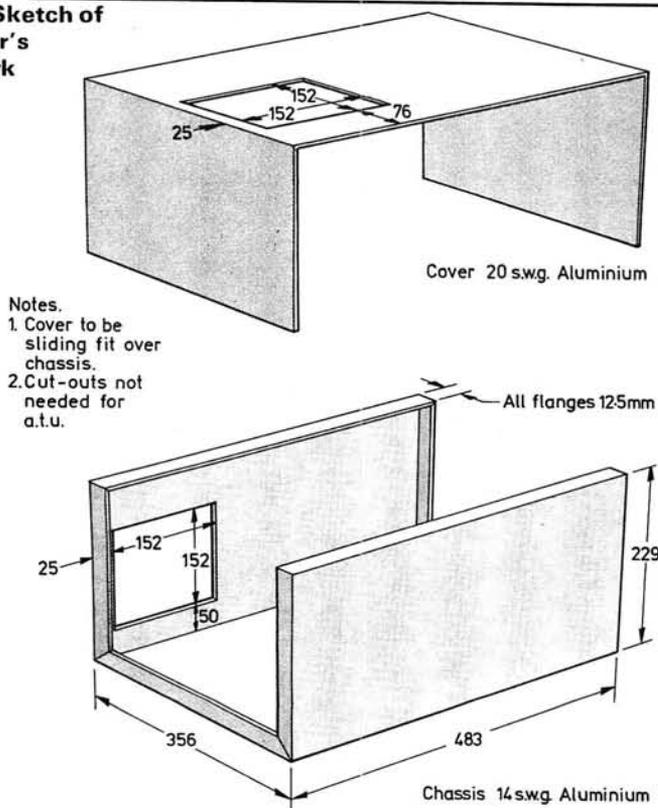

WAD218

Products

VOX Option Handie

South Midlands Communications Ltd. have supplied me with information on the very latest Yaesu 144MHz f.m. handheld transceiver, entitled the FT-203R.

The FT-203R follows the trend for smaller and smaller units and is housed in a high-impact plastics case that measures only 153 x 65 x 34mm, weighs 450g yet delivers 2.5W r.f. output power into 50Ω using the standard 10.8V power pack.

Frequency range is 144 to 146MHz in 5kHz steps, selected via a three-digit thumbwheel switch and a push button for 0 or 5kHz. Simplex or repeater shift operation is selected by a switch on the rear panel, whilst the p.t.t. and tone burst switches are located on the side of the unit.

The top control panel has, in addition to, volume, on/off, squelch, frequency and power select, earpiece and microphone sockets, and a signal/power out meter, which allows the transceiver to be used for general direction finding and "foxhunting" when a directional beam antenna is employed.

A very useful feature is the VOX system in the FT-203R, that when



used in conjunction with the optional YH-2 headset, provides voice-actuated transmit/receive switching, allowing the operator to have both hands free during QSOs.

Supplied as standard is a 10.8V-425mAh NiCad pack, soft case and helical rubber antenna. Optional accessories include a 12V-500mAh NiCad pack (which will increase the r.f. power out), battery case for six AA size dry cells, d.c. car adaptor/trickle charger, mains charger, speaker microphone and, of course, the YH-2 headset which costs £13.80 inclusive of VAT and carriage.

The FT-203R costs £169, which includes VAT and carriage, and is available from: *South Midlands Communications Ltd., S. M. House, Rumbridge Street, Totton, Southampton SO4 4DP. Tel: (0703) 867333.*



Top-band Mobile/Base Transceiver

Latest information from Northampton Communications describes a dedicated top-band transceiver that has been designed and built in Northampton, and is suitable to fulfil the much needed requirement of mobile operation on the band.

The 1.8MHz enthusiast will know that obtaining equipment for this band usually means either buying high-priced, imported, multiband rigs, or build your own.

This rig, entitled the Lencom LC160, is suitable as a base station, whilst being compact enough for mobile operation. Of modular, solid state, construction which permits easy access for servicing or owner modification, the LC160 is tuned via a central control knob, linked to a 12:1 reduction drive and readout is via a 150mm long analogue dial. Frequency coverage is, of course, between 1.8 and 2.0MHz.

Switchable modes are s.s.b. and a.m., with c.w. being automatically obtained on insertion of the key jack, carrier and side tone being electronically switched.

Excellent i.f. selectivity is obtained with a 2.1kHz mechanical filter at 455kHz; further selectivity is effected with the integral audio filter, which can provide a tuned notch or peak function.


The bandwidth of notch and peak are variable.

The rugged p.a. delivers an r.f. power output of over 30W p.e.p., into 40-70Ω, and is fully controllable from the front panel. Audio output is 2W into 3Ω, by way of an external speaker (available separately), and with the microphone supplied, audio clipping is set at a 12dB level, the microphone gain being fixed.

For ease of mobile operating the audio output can be muted by a front panel control and an indicator light will be activated should any signals be present. Also transmit/receive may be switched either from the front panel or the p.t.t. on the microphone.

Other specifications include: stability of the v.f.o. less than 100Hz/hr, c.i.o. less than 50Hz/hr; bandwidth on s.s.b. 2.1kHz, a.m. 8.0kHz; carrier suppression is better than 40dB and the transceiver requires a 12 to 14V d.c. power source with current consumption at 1.2A on receive and 4A on transmit.

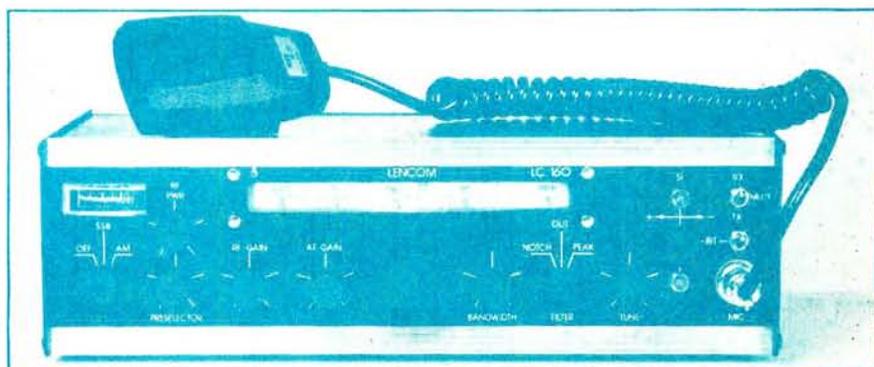The LC160 top-band transceiver is housed in a case measuring 300 x 165 x 90mm, is priced at £199 which includes VAT and is available exclusively from: *Northampton Communications Ltd., Communications House, 76 Earl Street, Northampton NN1 3AX. Tel: (0604) 33936 or 38202.*



VFM?

Value For Money

by G8YDK

A colleague had persuaded me to "have a quick look at it". The complaint was that when switched on the radio would work for just a few minutes and then stop. I suggested he buy a new battery, but he assured me that he kept buying new batteries, and had already spent more on batteries than he had on the radio!

The little red radio was still in its cardboard box with a price label clearly marked £2.50, so whatever I did could not be cost effective. When tested it was completely dead, the 6-F22 (PP3) battery was flat, measuring 2.2 volts, but then the switch was ON when I took the radio out of its box, so the battery would be flat wouldn't it? With a 9 volt supply applied to the battery clip the little radio worked reasonably well, but if the supply was reduced to lower than 8 volts it stopped.

Now, there are many technical procedures to establish if the local oscillator has stopped oscillating, but the "subject" didn't seem worthy of any of them. Anyhow, I *knew* that the oscillator stopped whenever the supply went below 8 volts.

With the two small retaining screws removed the 50mm square p.c.b. came out easily enough, but the leads to the speaker were a bit short. It wasn't too difficult to work out the details of the "front end" circuitry, and this is shown for reference in Fig. 1. I applaud the designer of this miniature superheterodyne receiver with its minimum of components.

With the supply set to 9 volts the first checks were made on the frequency changer transistor, Tr1: collector 5.9V, emitter 0.6V, base 1.1V. Emitter volts, 0.6, divided

by R3 at 3.3k Ω , using good old Ohm's Law, gave 182 microamps emitter current—low, even for a frequency changer stage. Collector volts also seemed to be low for the 9V input and it was found that 3 volts were being dropped across R8. The 3 volt drop divided by R8 at 330 Ω indicated a current of 9mA—well it certainly wasn't going to Tr1.


Back to Tr1; ignoring what should be the very low base current of Tr1, the potential at point A can be calculated to be the 6 volts measured at point B, divided by R1 + R2, multiplied by R2. This calculation worked out to be 1.95 volts, but point A measured 1.1 volts. So was R1 or R2 of incorrect value, or was capacitor C1 leaky? It was possible to unsolder the lead to the base coupling winding on the ferrite rod antenna at point A, and with Tr1 base isolated, resistance checks were made between points A and B and from point A to the 0V supply rail. The readings obtained were 56k Ω and 27k Ω respectively, showing both R1 and R2 to be correct, and suggesting that C1 was also OK. A voltage check at point A now gave a reading of almost 2 volts, so it was Tr1 upsetting the potential.

By juggling with the figures it could be seen that Tr1 was requiring 47 microamps of base current, which was ridiculous considering the calculated 182 microamp emitter current—no wonder it was affecting the base potential divider network which would normally be designed to draw ten times the expected base current. Current in R1 and R2 from the 6 volts available is 72 microamps.

Still, I was only "having a quick look at it", so the line

WRM013

Fig. 1

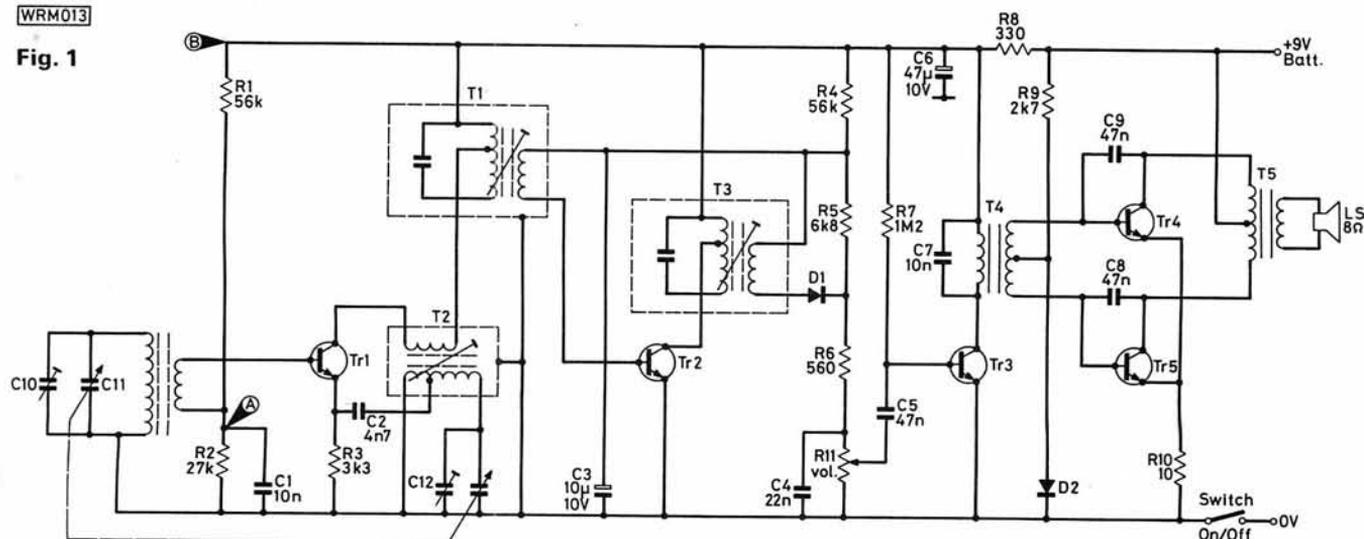

of least resistance . . . changing R1 from 56kΩ to 39kΩ allowed the oscillator to function until the supply fell to 7.1 volts. I put the set back together at this stage, and it *did* work, but my conscience eventually got the better of me! I convinced myself that there were too many "birdies" as I tuned across the band. Where were the 9 milliamps through R8? And I really wasn't happy about changing the value of R1.

The Second Session

I first put back the original R1, and became an honest man again. Now, where were the 9 milliamps going? I already knew it wasn't to Tr1. A screwdriver blade shorting the base/emitter junctions of Tr2 and Tr3 gave the clue; by switching off Tr3 the current through R8 (calculated each time by the measured voltage drop across it) reduced by approximately 1.5mA. No substantial difference could be noticed when attempting to switch off Tr2, although the voltage across R8 did fluctuate. Even if the current was leaking through some other route, I was expecting to see a reduction proportional to the current in Tr2, but I didn't.

I next removed Tr2 and my May 1975 *Television* transistor tester showed it to have an infinite hFE—obviously leaky. Now, what to replace it with? None of the transistors had any markings on them, although those long Japanese numbers don't mean much to me anyway—each piece of oriental equipment seems to have its own range of transistor numbers. Right! Silicon, npn, r.f., what did I have? I didn't really want to use something I had paid good money for. What was in that 50p "goodies" pack I couldn't resist at the Electronics Hobbies Fair? A 2N2369A, used for fast switching and v.h.f. multiplier

stages, was located—should work OK at 455kHz. This was rapidly fitted into the Tr2 position, making sure that the collector "can" didn't touch the adjacent i.f. transformer.

With the supply set to 9 volts the current through R8 was now 4.5 milliamps, much better! However, even with the higher voltage this gave at point B, the oscillator still stopped when the supply was reduced much below 8 volts. I had already proved that Tr1 was unhappy, so I went yet another 2N2369A. This transformed the frequency changer stage, giving the expected d.c. conditions; i.e. with point B at 7.5 volts, emitter 1.8 volts, base 2.4 volts and emitter current therefore 545 microamps. The set would now continue to work with the supply as low as 5 volts.

The p.c.b. was again refitted, with necessary repairs to the fraying speaker leads. The radio was now re-aligned, naughtily using the "known transmitter" method, which was in fact perfectly adequate for the dial calibration used. The radio was now considered to be giving a very respectable performance, for its simple pedigree, but in keeping with my usual pessimism I decided to "live with it" for a while and soon became aware of the background audio hiss, even with the volume control at minimum!

The Third Session

That hiss must be generated after the volume control and a screwdriver blade across the base/emitter junction of Tr3 stopped it dead. In went the third 2N2369A—all now beautifully noise free and radio still working just as well.

Final reassembly, and triumphant return to owner—"Thanks very much, I'll buy you a pint at Christmas". Still, I did know that I was only doing it in pursuance of my *hobby*, and there's only one thing I enjoy more than my radio hobby—it's not a pint at Christmas!


Next month in *Pw* On Sale 6th April

FREE WITH THIS ISSUE

70cm Repeaters



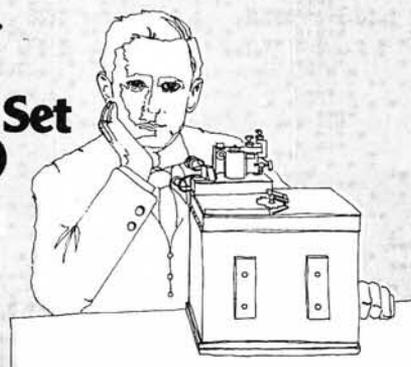"An HF Tune-up Aid"
 Let's Build a Crystal Set
 (just like Grandad's)





INTERMEDIATE FREQUENCY

The second topic highlighted for attention in the report on the May 1983 RAE results is the choice of the intermediate frequency in a superhet receiver.

Selectivity

What are we looking for in a radio receiver? The most important thing is an ability to receive just one signal at a time, without interference from other stations. This ability to select one station and reject the rest is called, appropriately enough, the **selectivity** of the receiver. It's achieved by having tuned circuits—coils and capacitors—which are arranged to resonate at the frequency of the wanted signal.

Unfortunately, you can't make a tuned circuit resonate at one frequency only, or even just across the narrow band of frequencies carrying the signal from a single station. It will still have some response at frequencies above and below the wanted station (Fig. 1), and you'll hear signals on those frequencies too. The sharpness of a tuned circuit is called its **Q factor** (or just *Q* for short). The sharper the circuit the higher the *Q*.

There are several formulas for calculating *Q*, but the one of most use to us in our present discussion is

$$Q = \frac{f_0}{B}$$

where f_0 is the resonant frequency of the tuned circuit and *B* is its **bandwidth**—the difference between the frequencies above and below f_0 at which the output voltage from the tuned circuit is reduced to 0.707 times that at resonance (Fig. 2). If the output voltage has fallen to 0.707, the output power will be 0.707² or roughly 0.5 (remember, power is proportional to voltage squared). Those frequencies are therefore called the half-power points, or (for those of you into such things) the -3dB points.

Putting that formula into words, the *Q* factor is the ratio of the centre frequency to the bandwidth. Say you had a tuned circuit with a *Q* of 100. If its resonant frequency was 800kHz in the medium-wave broadcast band, then its bandwidth would be $800 \div 100 = 8\text{kHz}$ (because the formula can be turned round to say $B = f_0 \div Q$). On the other hand, if the resonant frequency was 14MHz (14 000kHz) at the bottom of the 20m amateur band, its bandwidth would be $14\ 000 \div 100 = 140\text{kHz}$. You can get an awful lot of stations into 140kHz, so that wouldn't be much use to us, would it?

If you cascade several tuned circuits one after the other, in a suitable way, you can achieve a much sharper response

than each circuit produces on its own, but they must be very carefully adjusted if you are to get a good response. If you have a receiver that is intended to receive on only one frequency there is no great problem, but if you want to tune to several stations, even just across the medium-wave broadcast band, for example, it means you've got to arrange to alter the resonant frequency of all the tuned circuits at the same time, keeping them in step with each other, a process called **tracking**. If each circuit has a reasonable *Q* factor, that's going to be very difficult, if not impossible. So, what's the solution?

The Superhet

The solution is the superhet receiver, or the supersonic heterodyne to give it its full name. The idea is that you convert the incoming wanted signal, whatever its frequency may be, to another frequency which is constant. This new frequency is called the **intermediate frequency (or i.f.)**, so called because it is an in-between stage in converting the incoming radio-frequency signal to an audio-frequency one to feed the loudspeaker or headphones. All the selectivity needed to get rid of interfering signals on channels adjacent to the wanted station is put into the i.f. amplifier.

What should the intermediate frequency be? Well, we've already found out that it's easier to achieve narrow bandwidths at low frequencies than at high ones. So, let's go for a low frequency. Problem solved? No, because there's another snag we've not talked about yet, and it comes about just because we've converted the incoming signal to the *i.f.*

How is that conversion done? By taking an output from an oscillator in the receiver, called the **local oscillator (l.o.)** and mixing or heterodyning it with the incoming signal, to produce an output at the intermediate frequency (Fig. 3). If we wanted to receive that station transmitting on 800kHz, and we chose a nice low i.f. of 100kHz, our local oscillator could run at 900kHz so that the "difference" frequency coming out of the mixer was $900 - 800 = 100\text{kHz}$. There would be a "sum" frequency output too, at $900 + 800 = 1700\text{kHz}$,

Fig 1

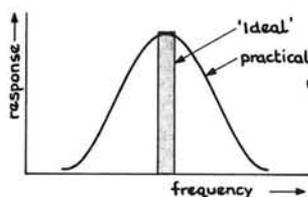


Fig 2


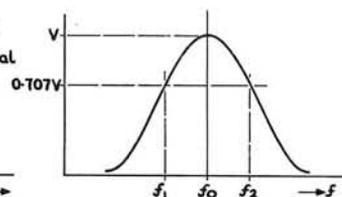


Fig 3

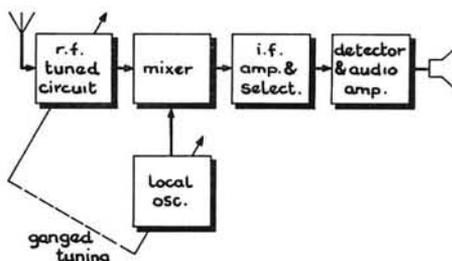

but that would be rejected by the i.f. amplifier tuned circuits, so no problem there.



Second Channel

But say there was another station, transmitting on 1000kHz, and his signal arrived at the input to our mixer too. With our local oscillator at 900kHz, this will produce a "difference" frequency of $1000 - 900 = 100\text{kHz}$ too. We can put a tuned circuit between the antenna and the mixer, tuned to 800kHz, and that will cut down the response to the 1000kHz signal, but it won't suppress it entirely (Fig. 4). If that r.f. tuned circuit had a Q of 100, it would reduce the interfering signal at 1000kHz by around 33dB. But that interfering signal might be 33dB stronger than the wanted one, maybe even stronger than that, so obviously we need a lot more selectivity ahead of the mixer. Adding another tuned circuit would help, but we're back to the problem of tracking the adjustment of all the tuned circuits.

It's therefore better if we use a higher intermediate frequency, because somehow we've got to achieve much better rejection of interference from stations on frequencies $2 \times$ i.f. away from the wanted signal. This sort of interference is called **second-channel**, because of the fact that there are two signal-frequency channels that can mix with the local oscillator to give an output at the i.f., or **image**, because if you imagine the oscillator frequency to be a mirror, the unwanted signal is like the reflection of the wanted signal.

For simple receivers covering the long- and medium-wave broadcast bands an i.f. around 450-470kHz is chosen as giving a good compromise between the demands of adjacent-channel and second-channel rejection. With a single tuned circuit ($Q = 100$) ahead of the mixer, the lowest second-channel rejection figure (achieved when tuned to 1500kHz) would be a useful 40dB. If you tried to use that same i.f. on short waves, then at 21.5MHz in the 13m band you'd get no more than 20dB of second-channel rejection, and you'd certainly need to add at least one more tuned circuit ahead of the mixer.

Using a still higher i.f. will improve second-channel rejection,

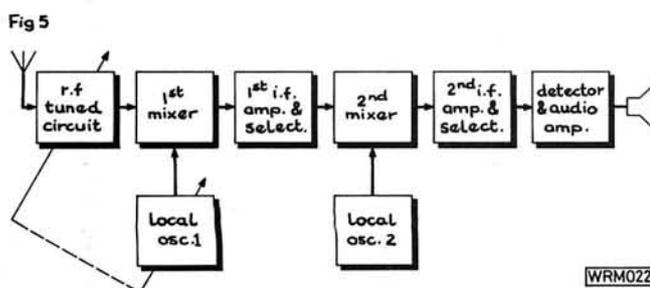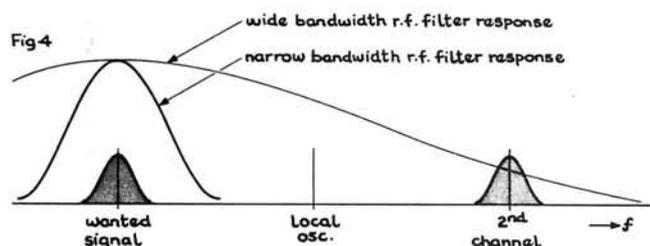

WRM022

tion, and frequencies of 9MHz or 10.7MHz are often used. You've still got to find some way of getting back a reasonable adjacent-channel selectivity, but I'll look at that later.

General Coverage

Intermediate frequencies of 9MHz or 10.7MHz are alright providing your receiver covers only amateur bands (or broadcast bands) because they fall between bands. If you want a general-coverage receiver to listen to any frequency from, say 1.6 to 30MHz, you've got a new problem, because you can't tune past the intermediate frequency without all sorts of nasty things happening!

There are two ways round this one. The first is to have a choice of two i.f.s, controlled by the receiver band-selector switch, so that the i.f. in use is always outside the frequency band selected. This method is used sometimes, but it means two lots of i.f. tuned circuits are needed, and the tracking between the local oscillator tuning and the signal frequency tuning is complicated. The other way is to have an i.f. which is higher than the highest frequency covered by the receiver. For a receiver covering up to 30MHz, i.f.s of around 47MHz or between 60 and 75MHz have been used.

The advantage of this method is that, regardless of what frequency the receiver is tuned to, the second-channel is always above the highest frequency covered. For example, when tuned to 150kHz, the second-channel frequency for a receiver with a 47MHz i.f. is 94.15MHz. So instead of having to tune the signal-frequency circuits and keep them all tracking together, we can have a fixed low-pass filter ahead of the mixer which passes all frequencies below 30MHz and rejects all frequencies above that point. This system is ideal for synthesised receivers, because there is no need to tune the front-end amplifiers.

So, we've got round the problem of second-channel or image interference, but that high i.f. means that adjacent channel selectivity will be very poor indeed. The solution is the double superhet circuit (Fig. 5). The idea here is that the first i.f. signal is fed to a second mixer stage where it's converted to a second i.f., at a lower frequency where adequate adjacent channel selectivity is easy to achieve. There's no problem with second-channel interference at the second mixer, because there should be no signals at the image frequency of the first i.f.

Summing Up

To summarise—because the bandwidth of a tuned circuit is proportional to its tuned frequency (for a given Q factor), you get smaller bandwidths at lower frequencies. We can achieve a constant bandwidth by using the superhet principle, converting all incoming signals to a fixed frequency, called the i.f., where we concentrate our adjacent channel selectivity.

The mixer in the superhet brings with it the problem of second-channel (image) interference. To get rid of the image we need a high i.f., but to give good adjacent channel selectivity we need a low i.f. We can get both by the double superhet. The first i.f. is high, for good image rejection, the second is low, for adjacent channel rejection.

For a domestic long/medium wave broadcast receiver, a double superhet would be too expensive. Instead, a compromise i.f. of around 460kHz is chosen.

on the air

AMATEUR BANDS by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR, 57 The Kingsway, Ewell Village, Epsom, Surrey, KT17 1NA.

Logs by bands in alphabetical order.

In view of the excellent DX reports that I get from my regular listeners it is not perhaps surprising if other readers sometimes express an element of doubt as to whether these stations have really been heard. After all, it is very easy to just sit on one of the DX nets that abound these days and copy the calls being worked by the net control station without bothering to copy the DX stations themselves.

However, after a while one gets to know pretty quickly whether a log is genuine or not and it is not hard to spot the spoofer! Given two somewhat similar station set-ups it is up to the operator as to what DX is heard and logged and I've come to the conclusion that a lot of DX is lost by the incorrect use of the r.f. gain control on the receiver. On most sets, according to the set's manual, the S-meter reading is correct only when the r.f. gain control is at maximum so there is a tendency to leave it there all the time in order to compare S-meter readings between stations, and that is just about the worst possible practice when looking for DX.

The r.f. gain control should never be advanced more than is necessary and to hell with the S-meter! It is one of the biggest menaces on the average communications receiver yet its alleged virtues are taken for gospel by the user. It does not indicate actual signal strength since the set's sensitivity varies greatly from one end of a band to the other and more so between bands, and all it can ever tell you is that one signal is weaker or stronger than another. On the i.f. bands in particular using maximum r.f. gain will bring all kinds of problems, principally cross-modulation or overloading so that any signal strength indication is meaningless. CW signals that are really quite clean can sound awful with clicks and thumps if the front end is being overloaded. Turn back the r.f. gain and the signal sounds as it should do. Unfortunately many stations get adverse reports of their signal quality both on s.s.b. and c.w. when in fact the distortion is being generated in the receiver itself.

The golden rule is to turn up the audio to somewhere near maximum and then the r.f. gain as far as is necessary to copy the signal cleanly. The reduction in general noise level is quite remarkable and that is when the DX can be copied quite easily. I find it possible to copy DX stations that are perfectly readable yet make no movement on the S-meter at all and a genuine report would be something like 51 or 52 but turn the r.f. gain to maximum and they disappear in the attendant

noise. According to the report in *PW* (July 1982) on the receiver side of my TS530S transceiver it is possible to copy a c.w. signal of 0.035 microvolt on the 21MHz band and I can well believe it.


Listeners to the amateur bands often hear operators referring to transmitter power as "100 watts p.e.p.", or whatever, which does not convey very much if one doesn't know the meaning of p.e.p. (peak envelope power) so a few words of explanation might be useful.

In a simple c.w. transmitter the maximum power output is realised when the key is down and is zero when the key is up. A few Morse characters are shown in Fig. 1(a) as they would appear on the screen of a suitably adjusted oscilloscope. Such a sharp turn-on of the output would produce heavy key clicks and thumps and would create a lot of interference in nearby radios. In practice suitable resistor/capacitance networks round off the keying waveform as in Fig. 1(b). The power input is simply output stage voltage times output stage current.

Next take an amplitude modulated transmitter as we are accustomed to listening to on the medium, long and s.w. broadcast bands. Here we have a constant carrier of the same amplitude as the c.w. case. The speech or music is impressed (modulated) on to the carrier and for the condition of 100 per cent modulation the carrier level either doubles in value or is reduced to zero, Fig. 1(c). If the modulating signal is excessive the positive excursion is more than double but the negative excursion cuts the carrier off, causing distortion and creating interference generally.


Since, with full modulation, the carrier level is doubled the input current to the output stage is also doubled, and derived from Ohm's Law, doubling the current in a constant resistance quadruples the power ($W = I^2R$), theoretically anyway! If a sine wave is used to modulate the transmitter then the carrier envelope is as shown in Fig. 1(c). It should be remarked that the carrier is being radiated continuously even in the absence of modulation, a very inefficient state of affairs. The act of modulation mainly produces two similar sidebands. The carrier is needed at the distant receiver in order to demodulate the signal and produce an audio signal at the headphones or speaker.

If the wanted carrier can be reproduced in the receiver at exactly the same frequency (and preferably in the same phase) then the carrier can be sup-

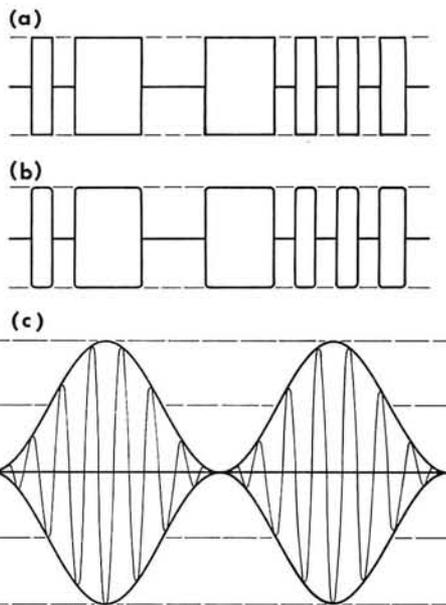

WRM023*

Fig. 1: (a) Typical c.w. or Morse code characters where the power output is either maximum or zero. The sharp rise time would create a series of undesirable harmonics which are suppressed in the transmitter to produce a rounded waveform as in (b). In (c) a sinewave modulates the carrier to give twice the amplitude of the c.w. carrier

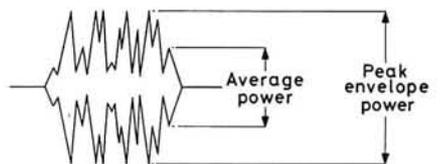

WRM024*

Fig. 2: Showing a typical speech waveform of an s.s.b. signal with average and peak envelope power indicated

pressed as well as one of the unwanted sidebands resulting in the well-known s.s.b. signal. Without going into technicalities it is generally reckoned that for a given power supply to a transmitter the effective peak power output on s.s.b. can be up to eight times that of an a.m. signal.

The waveform in Fig. 2 shows a typical s.s.b. signal with the upper and lower limits of the envelope similar to the 100 per cent a.m. condition. With the

human voice this only occurs for about 30 to 50 per cent of the time due to the peaks and troughs of the voice so that in order to keep this duty cycle as high as possible on s.s.b. it is now the fashion to incorporate or add speech processors to an s.s.b. transmitter to raise the value of the duty cycle. When done properly this can be very effective, especially when DXing but, as usual, this procedure has been abused on the amateur bands with severe speech clipping causing audio distortion and resulting interference to other stations, rather like over-modulation on a.m.

If you look at the S-meter on a receiver while copying s.s.b. without speech processing the signal level will rise and fall corresponding with the contours of the speech. With full speech processing the needle will stay virtually at the maximum level of the signal all the time the operator is speaking and the signal will have a great deal more punch and readability. What amazes me is the selfishness of operators who do not switch the speech processor off when working comparatively local stations but continue to inflict horribly distorted speech on our ears! Every intake of breath sounds like a hurricane!

General Notes

Paul Drinkwater up in Sutton Coldfield has been copying a few amateurs on s.s.b. the hard way using a m.w./l.w. pocket set and a Binatone clock radio with the local oscillator of one providing the necessary injection voltage for copying s.s.b. but it all sounds a bit haphazard and unrepeatable. Still, it is a start. From his report he seems to have copied a DL or two on the 3.5MHz band.

We G's have a habit of carping at and criticising our liberal AR regs but perhaps we should consider ourselves lucky compared to, of all countries, Sweden. In a QSO with an SM on 3.5MHz recently I was very surprised to learn that it is an offence for an amateur to possess any radio transmitter that will work outside the amateur bands. In this case my SM friend quoted an SM1 who bought a secondhand v.h.f. transceiver covering the maritime bands intending to modify it for the 144MHz band, something fairly commonplace over here. However the SM1 was arrested and the offending transceiver confiscated plus all his amateur bands gear! Eventually the case came to court and he was acquitted and his gear returned only for the matter to go to a higher court when his gear was confiscated again! The outcome is awaited with interest by the SM amateurs.

Incidentally, the Top Band allocation for SM is only 1.83 to 1.845MHz and 10W p.e.p. input and I was surprised to learn that the new WARC bands have not yet been released in SM-land.

One reader, **Arthur Ryall** in Stafford, is thinking of putting up a G5RV antenna for his JR310 receiver but wonders why flat twin feeder is frequently recommen-

ded over coaxial cable. Twin feeder is a balanced system to earth and any local electrical noise or TV timebase interference will have a better chance of being reduced or eliminated than with coaxial cable which is inherently unbalanced making cancellation of the interference less likely. Coaxial cable should not be connected to what is essentially a balanced antenna system, such as a simple dipole, unless a balun (balanced-to-unbalanced transformer) is fitted between the feeder and the antenna. One other factor mitigating against coaxial feeder is its great weight compared to flat twin feeder thus dragging down the centre of an antenna unless a support such as a mast is provided. This may account in part for the great popularity of the inverted-V antenna.

Round the Bands

As this is being written the l.f. bands, particularly the 3.5MHz and 1.8MHz bands, are really producing the DX once dusk falls and on for an hour or so after sunrise. It is very important to ensure that the antenna is the best that one can get up for these bands with as much of the wire as possible in the vertical plane and either a resonant length, if you have enough garden, or brought to resonance by means of an antenna tuning unit.

If you can lay down some radial wires underneath the antenna so much the better and now is the time to do it before the grass starts growing again. A slot for the wire, a couple of inches below the surface, can be made with the edge of a spade and the wires can be as long as is practicable and need not be related to the wavelength in use. The inner ends of the wires should be soldered together and a heavy copper wire taken back to the station earth. Triple ("twin-and-earth") pvc-covered wire as used for domestic electrical wiring is eminently suitable for this.

On to **Marcus Walden** of Harrogate and his Realistic DX302 and a 20m-long wire in the attic and an a.t.u. being constructed. Good lad! Around 3.8MHz he logged A71AD (QSL Box 4747 Doha, Qatar), A92HH (QSL W8LU), FM7WE, J88BC on St Vincent, OH0JN, OY8R, PJ2FR, VK3DWJ, VK6LK, VK2AVA, 5N2ARY, 6Y5IC and 7X5AB all on s.s.b. Due to the general QRM on 7MHz only HZ1AB, YC4FW and 6V0DY were worth logging but on 14MHz he caught HV3SJ (QSL I0DUD), J6LLO Box 800 St Lucia, plus ZF1GC. Finally on 21MHz it was FM7BX (QSL Box 152 Martinique), HH7BV, J28DN, J37AE on Grenada, TA2WCY, TL8DX, V2AS on Antigua with cards to OE3ALW, VP2MSS, VQ9BC (QSL WB6WUH), 3X4EX, and 5T23RD for an odd one.

From Plymouth a very long log from **Bob Stone** from which the following are culled. On 3.8MHz or thereabouts EA9JV, CT3CM, HK3DD, J88BC, VU2GI on the Laccadive Islands, N0XA, N7NG, T77V in San Marino,



Neat station set-up of Eric Fielding G4IHF in Rochdale covering the v.h.f. and h.f. bands. Eric is very active with the Bury RS, running a code class, and is a past treasurer of the club

YV5ANF, FM7CD, HH2MC, J3HSA on Grenada, and 5B4LP. Bob queries a special event station in Santa Maria, Brazil, with the call he swears was PY/KWS31M/A and being worked by all and sundry. Bob forgot to give any info on his receiving set-up but should be rectified by the next time around.

In Wellington, Somerset, **Dave Price** has been covering the bands from 28MHz to 3.5MHz although on the former the only item of note was VK6AEK, but more on 21MHz and YV5EUX, C53BI, VK6AJW, ZS1AAQ, A82LC in Monrovia, Liberia and FY7CM. 14MHz gave up YA1BGD, OY2A, VU7WCY, T77V, and so on to 7MHz with TA8GM, 6V0Y in Senegal and cards to VE4SK, and T77B. Dave's 40m loop antenna came into its own on 3.8MHz with large numbers of US stations, A92P, VU2GI, with K0CS of note among the Americans. Dave's receiver is a Yaesu FRG-7.

Dave Shapiro ARS53844 has also been making the most of his receiver, a Realistic DX-200, plus a 20m-long wire, a practice with which I heartily concur. It does seem a bit daft to spend a lot of money on a set only to listen to the easy stuff on 14MHz s.s.b. when there are several other interesting bands available at the turn of a switch. Anyway, starting on the 1.8MHz band Dave found a very good one in 5N8ARY and then 4X4DX. On to more goodies on 3.8MHz and DF3NZ/ST2, JF1IST, HI8HLB, J37AH, J88BC, TA2BNK, TI5BPF, VP2MSS, VL6LK, YB0WR and 8R1RBF. More mouth-watering stuff on 7MHz like HP3FL, J6LCV, KX6OH, TU2LE, VU7WCY, ZL4BO, 3X4EX and 6WIDY. Dave notes the continued use of the WCY suffix although the WCY is now officially over. All of note on 14MHz were XT2BM, TZ6WFP and KV4AD with just 5R8AL and 8P6OV on 28MHz.

In Shepherd's Bush, London, the set-up of **Denis Norton** comprises an FRDX-500, Datong FL2 audio filter, SST6 a.t.u. all fed from a 20m-long antenna, a half-wave vertical for 28MHz and a five-eighths wavelength vertical for 144MHz. How did that thing creep in?? Good

enough to find VE1YX on 1.8MHz and then CT2EF, FC2XN, 3A2GL and familiar 4U1TU. Up to 14MHz and mainly JAs and ZLs during morning sessions, plus ZS6AOO and 7X2LS. Last band is 21MHz for HP1XEK, SV1OL/SV5, VK3WCY, VP9DL and 5N9MBT.

Reports from readers are always most welcome and should consist of a selection of around a dozen of the best DX heard on the bands from 1.8 to 28MHz and especially the new WARC bands on 10, 18 and 24MHz. Don't forget the c.w. stuff at the low end of each band. Time of day is rather important on the l.f. bands so that

others can make an effort to hear the DX. With everyone using a v.f.o. these days actual precise frequency is not important unless a station is consistently heard on a particular frequency. Rarity of the DX station is the main consideration rather than distance. Don't forget, reports direct to me by the 15th of the month.

Club Time

Club magazine Q5 of the North Bristol ARC rightly points out that many members regard the AGM as a bit of a "yawn", a date NOT to be noted in the diary, which is patently unfair when they are prepared to turn up and use the facilities of the club for the other 51 meetings during the year, arranged and provided by others of course. What makes AR an interesting hobby is seen from a different angle by every individual and the NBARC has been pressing its members to elect a committee that reflects these various interests and age groups.

Apart from that excellent precept, if every member voted at the AGM the club would get the committee it deserves and there would be no room for the all-too-frequent gripes and groans that come from those that shun AGMs.

Action, Brentford & Chiswick ARC G3IUU Tuesday March 20 will have G3XPC giving his postponed chat on his further experiences in DXing in foreign countries. That is at 7.30pm in the Chiswick Town Hall, High Road, Chiswick, London W4. Visitors and potential members always most welcome, according to W. G. Dyer G3GEH, 188 Gunnersbury Avenue, London W3, the hon sec.

Axe Vale ARC 7.30pm on the first Friday of the month at the Cavalier Inn, Axminster, according to sec Bob Newland G3VW available on Lyme Regis 5282 or try the publicity officer Roger Jones G3YMK on Upottery 468.

Bangor & District RS Where the sec is Stewart Mackay G14OCK of 11 Dellmount Park, Bangor, Co Down, NI, or you can meet him and the gang in the Sands Hotel, Bangor, at 7.45 onwards on the first Friday of the month with visitors assured of finding something to suit their interests. Advance notice now of the club's summer mobile rally in June with details later.

Biggin Hill ARC Third Tuesdays in St Marks Church Hall, Church Road, Biggin Hill, Kent, according to sec Ian Mitchell G4NSD, 37b The Grove, Biggin Hill, Westerham, Kent.

Bromsgrove ARS G4TUI Coming up to its first anniversary the club has been doing very well with lectures, demos, outside visits and generally promoting AR in the area. Second Tuesdays at Rigby Lane School, Bromsgrove at 8pm with Alan Kelly G4LVK, 8 Green Slade Crescent, Bromsgrove, Worcs available on 021-445 2088 with details of future club happenings.

Bury RS G3BRS Latest issue of club's comprehensive magazine *Feedback* lists over 100 members which can't be bad and attributable to the standards maintained by the club in the way of lectures, outings and its many other activities including the Bury Ham-

fest which I have been assured was a great success as usual. Every Tuesday at 8, in the club room at Mosses Centre, Cecil Street, Bury with the principal meeting on the second Tuesday but for details of the March highlight you'll have to chat with Brian Tyldesley G4TBT, 4 Colne Road, Burnley, otherwise Burnley 24254.

Cheshunt & District ARC G4ECT G6CRC From the newly-named club mag *Hamster* (!) I see the club holds meetings every Wednesday at 8 in the Church Room, Church Lane, Wormsley, near Cheshunt, Herts, with a junk sale slated for March 7 under the auspices of G4TQG and the 14th a natter-nite. The GB3PI repeater group has the floor on the 21st, with another natter period on the 28th. Filling in the details is sec Roger Frisby G4OAA, 2 Westfield Road, Hoddesdon, Herts, otherwise H'don 464795.

Chichester & District ARC Tuesday March 6 has John Outram discoursing on signal processing in microwave radar systems, in the Long Room of the Fernleigh Centre, 40 North Street, C'chester, at 7.30pm, with a regular meeting in the Green Room on the 15th. All of which makes it the first Tuesday and the third Thursday of the month. Meetings are complemented by a club net on the 144MHz band (S11) every Wednesday at 7pm. Make a note now of the AGM which is on Tuesday April 3 in the Long Room of the Centre. Club sec G4ETU has resigned so in the meantime I suggest you write to the club's chairman G4EHG, Marmanet, Salthill Road, Fishbourne, Chichester, Sx or have a chat on C'chester 789587.

Colchester RC Second and fourth Thursdays it seems, at the Colchester Institute, Sheepen Road, Colchester, at 7.30 with March 8 devoted to a talk by an RSGB rep on the AR repeater network and its administration while the 22nd will be Part 2 of a talk on Marconi and his work "Mainly Arcs and Sparks" by Stanley Wood. Note now the constructors' competition slated for April 5. Your sec is G3FIJ, 29 Kingswood Road, Colchester, otherwise (0206) 851189.

College of Technology, Belfast G12BX RTTY with the ZX81 forms the main part of the evening's action on Wednesday March 28, by Ray Bowring G18RKC, at 7pm sharp, Room B10, which is the lecture theatre at the College to which the public is also invited seemingly. Your contact at the College is Jim Barr G1ICET on Belfast 227244 ext 243 during any working day except Thursdays.

Coulsdon ATS You won't believe it but the club call of the CATS mob is G4FUR and that just can't be accidental! Anyway they meet on the second Monday at 7.45 for an 8pm start at St Swithun's Church Hall, Grovelands Road, Purley, Surrey, with the subject of d.f.ing on both 1.8 and 144MHz being given a thorough airing by G3NPF on

March 12. CATS Publicity Officer Richard Goring G6VYT can be contacted at 54 The Glade, Old Coulsdon, Sy, or Downland 54319.

Darlington & District ARS Nearing its first anniversary the club meets in the Hurworth Community Centre just south of the town on Fridays at 7.30. Activities run to Morse code and RAE classes by G3UTI and G3GUV and periods on the air with the club station. Sec C. Webb G4NYJ will be glad to hear from anyone interested in joining the club, at 34 Cleveland Terrace, Darlington, or ring him on D'ton 467271.

Dartford Heath DF Club This club is devoted it seems to the art of d.f.ing but there is precious little useful information on its activities in the club newsletter. Seems hunts start at NGR 525730 on Dartford Heath and are run by "Pete" G8DYF he is on Greenhithe 844467. Next hunt starts at the Horse & Groom on Tuesday March 6 with another the following Sunday. Mag editor is Rosie Keeling G8YDB, QTHR I suppose.


Derwentside ARC (Consett) G4PFQ The RAFA HQ is the spot every Monday at 7.30 in Sherburn Terrace, Consett, Co. Durham, where activities include code classes, Raynet participation and on-the-air sessions with the club's h.f. and v.h.f. gear. Potential members should get info from June Wallis G1AAJ, 10 Middlewood Road, Lanchester, Durham (0207) 520477.

Dudley ARC G4DAR The lecture by Joe Jacobs on "TV OBs 1950 to the 80's" was postponed and will now take place on Tuesday March 13. Meetings are on the second and fourth Tuesdays at 7.45 at the Central Library in Dudley. Interesting item for the 27th is a chat by G3ZPF on DXing from impossible situations, applicable to many amateurs I suspect! Cheryl Wilding G4SQP, 92 Ravenhill Drive, Codsall, Wolverhampton is also available on Codsall 5636 for information on the activities of the club.

East Kent RS G3LTY G6EKR The Cabin, Kings Road, Herne Bay, Kent, on the first and third Thursdays with visitors and others particularly welcome says sec Stuart Alexander G6LZG, 66 Downs Road, Canterbury, Kent who will be glad to tell you of the club's forthcoming events.

Exeter ARS G4ARE "Static and chips" by G3RSJ ought to be interesting on March 12, with advance notice of a visit to Radio Devon on April 9 and a strict limit to the number of places available for this outing. Main meetings at the Community Centre, St Davids Hill, Exeter, on the second Monday while on other Mondays it's informal gatherings at the Scout Hut, Emmanuel Hall, Okehampton Road, Exeter, which houses the club station for on-the-air activity plus code classes but R. R. Tipper G4KXR, 11 Chancel Court, Pinhoe, Exeter,

AMERICAN RADIO HISTORY

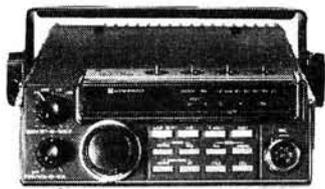

STANDARD C5800 MULTIMODE

Reception Specifications:
 Reception System: FM: Double Super Heterodyne; SSB, CW: Single Super Heterodyne
 Intermediate Frequency: FM: 1st IF 10.7 MHz; 2nd IF 455 KHz; SSB, CW: 10.7 MHz
 Sensitivity: FM: 0.19uV (12dB SINAD); SSB, CW: 0.15uV (10dB S/N)
 Pass Bandwidth: FM: ±6 KHz, SSB, CW: 4.2 KHz
 Selectivity (60dB): FM: 25 KHz, SSB, CW: 4.2 KHz
 Squelch Selectivity: 0.15uV (FM)
 AF Output: More than 2W (into 8 Ohms with 10% THD)
Transmission Specifications:
 Power Output: 25W/1W
 Modulation: FM: Reactance Modulation; SSB: Balanced Modulation
 Maximum Frequency Tolerance: ±15×10⁻⁶ (-10 - +50°C)
 Spurious Attenuation: 60dB
 Carrier Suppression: 40dB
 Undesired Side Band Suppression: 40dB
 Maximum Deviation: ±5 KHz

STANDARD COMMUNICATIONS EQUIPMENT

	Price
C5800 The most advanced 2M multi-mode mobile yet with 25 watts output in all modes. Spare Mounting Bracket	379.00 9.95
C8900 New slim fully synthesized 2M 10W Mobile with 5 memories, scanning facilities and digital read-out etc.	219.00
C7900 New slim fully synthesized 70cm 10W mobile with 5 memories, scanning 10MHz coverage and digital read-out etc. Spare Mounting Brackets for above	239.00 7.95
C58 2M FM/USB/LSB and CW portable with 1W RF Power and tuning down to 100Hz	249.00
C78 Fully synthesized FM 70cm 1W transportable	229.00

CMB8 Mobile mounting cradle for C58 and C78 with all the connections for antenna power etc. built in	21.51
CPB58 A 25W linear amplifier for C58 that bolts underneath the CMB8	82.50
CPB78 A 10W linear amplifier for C78 that bolts underneath the CMB8	69.43
CLC8 A carrying case for C58 and C78 with flap over top for added protection	6.95
C12/230 Charger for the C58 and C78 when Ni-Cads are used	7.75
CN10 Set of Ni-Cads for the C78/C58	9.00
C110 Synthesized 2M 2 watt hand held 144-148 MHz	139.95

C110 ACCESSORIES

CNB110 Heavy Duty Ni-Cad Pack	30.00
CSA110 Heavy Duty Base Ni-Cad Charger	30.00
CLC110 Leather Carry Case	6.75
CMC01 Car Power Adaptor	7.95
C10-230 Wall Type Charger with 6 Ni-Cads	12.50

DATONG PRODUCTS

PC1 Gen Coverage Converter HF on 2M	137.42
VLF Very Low Frequency Converter	29.90
FL1 Frequency Agile Converter	79.35
FL2 Multi-mode Audio Filter	89.70
FL3 Audio Filter & Notch	129.37
ASP Auto RF Speech Clipper (Trio or Yaesu Plug)	82.80
D75 Manually controlled RF Speech Clipper	56.35
RFC/M RF Speech Clipper Module	29.90
D70 Morse Tutor	56.35
AD270 Indoor Active Antenna (ex-PSU)	47.15
AD370 Outdoor Active Antenna (ex-PSU)	64.40
MK Keyboard Morse Sender	137.42
Codecall Selective Calling Device (Link Prog)	32.20
Codecall Selective Calling Device (Switch Prog)	33.92
RFA Wideband Pre-amplifier	33.92
MPU Mains Power Unit	6.90

METRES

SWR15 Single Meter SWR/Field Strength 3.5-10MHz	9.50
SWR25 Twin Meter SWR/Power/Field Strength 3.5-150MHz	13.00
UH-74 Single Meter SWR/Power 5/20/120W 144 and 432MHz	22.00
SWR200B Twin Meter SWR/Power 3.5-150MHz	40.25
TAL172 Single Meter Professional SWR/Power 5/25/100W 148-174MHz Optional Mounting Bracket available	37.95

T435 Twin Meter 144/432MHz SWR/Power 20W/120W	39.50
SWR150 Deluxe Twin SWR/Power Meter 3.5-150MHz	16.95
MORSE KEYS	
HK707 Straight Up/Down Keyer	14.00
BK100 Semi-automatic Bug	24.70
MK702 Up/Down Keyer On Marble Base	27.60
MK704 Squeeze Paddle	27.60
MK705 Squeeze Paddle On Marble Base	13.00
MK1024 Automatic Memory Keyer	27.60
EK150 Semi Automatic Keyer	120.00
EMK1A Morse Code Practice Oscillator	85.40
	9.20

LOW PASS FILTERS

TF30M 1Kw Low Pass Filters	19.95
----------------------------	-------

POWER SUPPLIES

PX402 3A continuous 4A Max 13.8VDC fully stabilised	19.95
PH5000 5A continuous 7A Max 13.8VDC fully stabilised	45.95
EP2510 25A continuous 30 Max 13.8VDC fully stabilised	109.25
DRAE 13.8 12 AMPS	74.00

DUMMY LOADS

T-25 DC-500 MHz 30W with PL259 connection	6.00
T-100 DC-500 MHz 100W with SO239 Socket	27.55
T-200 DC-500 MHz 200W with SO239 Socket	40.25

WELZ PRODUCTS	
SP300 1.8-500MHz 20W-200W-2KW Power/SWR meter	102.95
SP350 1.8-500MHz 200W Power/SWR	61.80
SP380 1.8-500MHz 200W Dash Mount	54.65
SP-10X 1.8-500MHz 200W Pocket size	24.95
SP15M 1.8-160MHz 5W-20W-200W Power/SWR meter	36.50
AC38 3.5-30 MHz coax ATU 200CW/400C PEP	68.70
CT15A 50W Dummy Load (3:1 Tx/Rx ratio - 4 minds) 25W cont.PL259 Plug	7.95
CT15N 5/50W Dummy Load 450MHz N. Plug	12.25
CT300 300/KW Dummy Load 250MHz PL259	51.75
CH20A 2 way Coax Switch 1KW SO239	18.35
CH20N 2 way Coax Switch 1KW "N"	32.80
CT-03M 3W Dummy Load 1.3GHz "N"	25.75

All prices are inclusive of VAT and are correct at time of going to press.
 Postage + Packing on Rigs £2.00
 Postage + Packing on all other items £1.00


**400 EDGWARE ROAD,
 LONDON W2
 01-723 5521 Tlx 298765**

Normally 24hr despatch but please allow 7 days for delivery.

**NORTHERN AGENTS:-
 JOE BELL, G4PMY
 134 CREWE ROAD,
 HASLINGTON,
 CREWE
 Tel. No. 0270-582849**

**AUDIO FILTERS
 MODELS FL2, FL3, FL2/A**

Model FL3 represents the ultimate in audio filters for SSB and CW. Connected in series with the loudspeaker, it gives variable extra selectivity better than a whole bank of expensive crystal filters. In addition it contains an automatic notch filter which can remove a "tuner-upper" all by itself. Model FL2 is exactly the same but without the auto-notch. Any existing or new FL2 can be up-graded to an FL3 by adding Model FL2/A conversion kit, which is a stand-alone auto-notch unit. Datong filters frequently allow continued copy when otherwise a QSO would have to be abandoned.

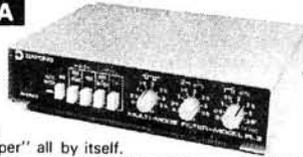

Prices: FL2 £89.70, FL3 £129.37, FL2/A £39.67

ACTIVE RECEIVING ANTENNAS

Datong active antennas are ideal for modern broadband communications receiver - especially where space is limited.

- highly sensitive (comparable to full-size dipoles).
- Broad-band coverage (below 200 kHz to over 30 MHz).
- needs no tuning, matching or other adjustments.
- two versions AD270 for indoor mounting or AD370 (illustrated) for outdoor use.
- very compact, only 3 metres overall length.
- professional performance standards.



Prices: Mod-1 AD270 (indoor use only) £51.75 Both prices include mains power unit.
 Model AD370 (for outdoor use) £69.00

MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.

- Practise anywhere, anytime at your convenience.
- Generates a random stream of perfect Morse in five character groups.
- D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.

Price: £56.35



Our full catalogue plus further details of any product are available free on request. All prices include VAT and postage and packing. Goods normally despatched within 3 days subject to availability.

write to dept. P.W.
 Spence Mills, Mill Lane
 Bramley, Leeds LS13 3HE
 England
 Tel (0532) 552461

**DEWSBURY
 ELECTRONICS**



West Midlands only authorised TRIO dealer

AR2001

CONTINUOUS COVERAGE FROM 25-550MHz WITH NO GAPS



FEATURES: 25-550MHz continuous coverage - Switchable modes (AM, FM narrow or FM wide) - Liquid Crystal display - memory channels that store frequency and mode - a full range of scan facilities - Definitely not deaf, on FM (n) the typical sensitivity is 0.2µV for 12dB SINAD across the entire range.

PROVISIONAL PRICE £325 + £3 p&p

Also stockists of DAIWA-WELTZ-DAVTREND-TASCO TELEREADERS
 MICROWAVE MODULES-ICS AMTOR-AEA PRODUCTS
 DRAE-BNOS-JRC

Dewsbury Electronics, 176 Lower High Street,
 Stourbridge, West Midlands.
 Telephone: Stourbridge (0384) 390063.
 After Hours: Kidderminster (0562) 851255.
 Closed Mondays

will be glad to bring you up to date on club happenings, or buzz Exeter 68065.

Fylde ARS The Kite Club, Blackpool Airport, first and third Tuesdays at 7.45 with a full house expected for the airport's senior air traffic controller on March 6 when he will describe how electronics have affected air navigation and air traffic control. G3AEP and G8GG will tackle something entirely different on the 20th with the construction of Top Band d.f. equipment the main topic. Next month's issue will be too late to tell you of the RTTY evening on April 3rd headed by G4RSA. Try H. Fenton, 5 Cromer Road, St Annes for an update on the club's programme, that is St Annes 723457.

Great Yarmouth RC G3YRC Every other Thursday which makes it March 15, 29 and so on, at the STC Sports & Social Club, Beevor Road, South Denes, G. Yarmouth, with old, new and potential members most welcome. PRO for the club is John Noy G8VPE, 14 Poplar Drive, Filby, G. Yarmouth, Norfolk or ring (049377) 673, who will be glad to give details of current events at the club.

Horndean & District ARC G4FBS Limitations of the club premises has forced a restriction to the membership of around 70. So with some 66 already on the books you'd better get along there pretty soon! Club facilities include a quarterly newsletter, computerised printout of membership list, special club QSL cards and a local award. Meetings at 7.30 at Merchistoun Hall, London Road, Horndean, Portsmouth, Hants, usually with club business followed by a talk, discussion or demo. On March 5 G4RLE will deal with the techniques of operating special event stations, and on to April 2 when G4BEQ talks on "A Year of Radio". Club Publicity Officer is R. E. Tribe G4SAQ, 32 Sutton Road, Cowplain, Portsmouth.

Leighton Linslade RC Gets together on the first and third Mondays in room A64 of the Vandyke Community College, Vandyke Road, Leighton Buzzard at 7pm usually running on to around 10pm. More details from club sec Peter Brazier G6JFN, Kingsway Farm, Miletree Road, Leighton Buzzard, Beds, otherwise Heath and Reach 270.

Maesteg ARC Still quite new the club gets together at the 7777 Club, Llangwynyd, Maesteg, on the first and third Tuesday evenings and, needless to say, new members will be very welcome as will be visitors. Try M. R. Carey GW6ZIH, 47 Heol Ty-Gwyn, Maesteg, Mid-Glam, for an update on club events.

Norfolk ARC G4ARN A new headquarters is the good news from the club, situated at the Valley Drive Community Centre, Plumstead Road, Norwich, with meetings every Wednesday evening at 7.45. A permanent station should be on the air by the time this appears in print and a new programme of events and fixtures is promised for the near future. Up-to-date info from sec Peter Forster G3VWQ, 12 Thor Road, Thorpe-St-Andrew, Norwich, or Norwich 37709.

North Bristol ARC G4GCT Future event for the diary is the RSGB film show on Friday March 30 which includes *The Secret Listeners*, a graphic account of how many amateurs used their talents to intercept enemy radio communications during the last war. Club meetings every Friday at the Self-Help

Enterprise, 7 Braemar Crescent, Northville, Bristol, with Ted Bidmead G4EUV, 4 Pine Grove, Northville, B'tol anxious to answer your every query.

Radio Club of Thanet G2IC Second and fourth Tuesdays at 8pm, the Grosvenor Club, Grosvenor Place, Margate, Kent, with an expose of the mysteries of Air Traffic Control being revealed by G6HXR on March 13. Ian Gain G4NEF, 17 Penshurst Road, Ramsgate, Kent, will tell you about the "do" on March 27 or anything else to do with the club, alternatively (0873) 54154.

Rhyl & District ARC GW4ARC GWIARC The venue is the 1st Rhyl Scouts' Hut, Tynewydd Road, Rhyl, on the first and third Mondays so be there at 7.30. Latest info on club happenings from sec John McCann GW4PFC, 67 Ashley Court, St Asaph, Clwyd or try (0745) 583467.

Ripon & District ARS The usual format at 7pm every Thursday is RAE and c.w. code classes, a coffee break and on to a talk, lecture or demonstration around 8pm. All this at the St John Ambulance Hall, Ripon, but more info from Peter Fautley G6CUG, Parkside, Thornton-le-Street, Thirsk or buzz Thirsk 24945.

Salop ARS G3SRT Weekly on Thursdays at the Albert Hotel, Smithfield Road, Shrewsbury, with March 8 a natter-nite and the first of four d.f. fox hunts on the 15th and another natter session on the 22nd. Don't forget to enter the construction contest due to be judged on April 12. More from Diane Parslow G6UDB, 1 Willington Close, Little Harlescote Lane, Shrewsbury, Salop (0743) 62737.

South Bristol ARC Every Wednesday at the Whitechurch Folk House, East Dundry Road, Whitechurch, the March 7 meeting featuring talks by G4KUQ and G4MCQ on AMTOR and ARQ respectively with the 14th a club project constructional evening. March 21 is for s.w.l.s. with computer addicts catered for on the 28th. Data communications on April 4 will be covered by G4MCQ. Active promotion of AR in the area has included visits by journalists from the *Bristol Journal* resulting in interesting write-ups and photographs of members' shacks and equipment. As can be seen club interests run from QRP operation to AMTOR technology. Right, contact sec Len Baker G4RZY, 62 Court Farm Road, Whitechurch, Bristol which also houses (0272) 834282.

South East Kent (YMCA) ARC G3YMD G8YMD At the Dover YMCA, Godwynehurst, Leybourne Road, Dover, Kent, with main meetings on Wednesdays, RAE coaching and operating practice on Monday evenings, plus code classes by G3VSU on Tuesdays. Further details from sec Alan Moore G3VSU, 42 Nursery Lane, Whitefield, Dover or Dover 822738.

Southend & District RS Liaison Officer John Weston G6XBM lives at 67 Victoria Road, Rayleigh, Essex (Rayleigh 742128) will update you on club fixtures, meetings taking place on Fridays at 7.30 at the Council Offices in Rayleigh, right opposite the church, where visitors are likely to be given a warm welcome.

Stevenage & District ARS On March 6 G4ISO will talk on the workings of the WAB award programme while the 28th is devoted to

the club's AGM which all members are expected to attend. That makes it the first and third Tuesdays at TS Andromeda, Fairlands Valley Park, Shephall View, Stevenage, Herts, at 8, but before that there are code practice classes from 7.15pm. Then there is the club net on Sundays at 7pm on 145-250MHz for the very latest news of club activities, or contact Cliff Barber G4BGP, 13 The Sycamores, Baldock, Herts, or more cheaply (0462) 893736.

Stourbridge & District ARS G6OI G6SRS New gathering spot is the Robin Woods Centre (used to be the Beauty Bank School), School Street, which is off Enville Street. S'bridge. Thoughtfully, an excellent map is now part of the re-vitalised *STARS Newsletter*. Meetings on first and third Mondays at 8 promptly, the informal one on March 5 covering constructional work, Morse code practice session and on-the-air activity, with the club's AGM down for the 19th. Interested? Then the contact is sec Malcolm Davies G8JTL, 25 Walker Avenue, Quarry Bank, Brierley Hill, also known under Lye 4019.

Street & District ARS G6XYI Thanks to the efforts of W. Scriven G4EGO this club has been formed at the Strode College for the benefit of both students interested in AR and local enthusiasts. He has also been running an RAE course that has proven very successful. Meetings of the club are held in the electronics lab on the first Tuesday of the month at 7pm with a collection of equipment for both h.f. and the 144MHz band. Already a rally in November is on the cards with trader support being sought. So those of you in the Street area should make every effort to support EGO after the great start he has given the club and he can be found at the College, Church Road, Street, Somerset or try Street 42277.

Sutton & Cheam RS Meetings either at the Sutton College of Liberal Arts or the Downs Tennis Club, Holland Avenue, Cheam. Surrey, that on March 16 being at the Downs Club where the winner of the club's constructional contest will be adjudged. The 35th annual dinner will be held at the Woodstock where a good time for all is promised. Club activity is maintained via three nets. Mondays at 8pm on 144-390MHz s.s.b., Tuesdays at 10.30am on 3-770MHz s.s.b. and Sundays at 10.30am on 144-5MHz f.m. Jack Korndorffer G2DMR, 19 Park Road, Banstead, Sy, will be pleased to supply the latest on club events and membership facilities.

Swansea ARS GW4CC Advance notice of a rally on Sunday April 8 at the Patti Pavilion, Swansea, next to the St Helens Cricket Ground which is on the A4067 Swansea to Mumbles coast road, from 10.30am to 5pm. Usual delights of trade stands, RSGB bookstall, local repeater groups, bring and buy sale, licensed bar and light refreshments plus talk-in on S22 and good parking facilities. What more could one want! If there is more to tell you, you can get it from Roger Williams GW4HSH, 114 West Cross Lane, Swansea, or (0792) 404422, who is the club sec if you want details of club membership.

Todmorden & District ARS Secretary Janet Gamble G6MDB of 283 Halifax Road, Todmorden, Lancs, tells me that the local lads and lassies have got together to form this new club, so let us all wish them well in this venture. It's first Mondays at the Queen Hotel,

Todmorden, with that on March 5 having a lecture asking "Satellites—How do they stay up?" and you'd better know now that April 2 is homebrew night. The 40-odd members already recruited will welcome even more potential members and visitors.

Vale of the White Horse ARS First and third Tuesday of the month at the Lansdown Club, Milton Trading Estate, at 7.30 for an 8pm start. Lucky lads on March 6 when Petra Suckling G4KGC will reveal all on the subject of operating in v.h.f. contests. Club nets are held on Thursdays at 7.30pm on 28.750MHz

and on Sundays at 8pm on 145.2MHz. Ian White G3SEK, 52 Abingdon Road, Drayton, Abingdon is the sec also to be raised on (0235) 31559.

Wirral ARS G3NWR Be at the Guide Hut, Westbourne Road, West Kirby, on the first and third Wednesdays at 7.45 if you want to join in the fun, like on March 7 when G3LEQ deals with h.f. propagation matters or on the 21st with G3EGX describing lessons learned about antenna masts, hopefully not the hard way! Must tell you now of the surplus equipment sale evening on April 4 while another

worthwhile event will be the video show of Dud Charman's *Aerial Circus* lecture on the 18th. Your club sec is Cedric Cawthorne G4KPY, 40 Westbourne Road, West Kirby (051-625 7311).

Photographs of club activities are very welcome for publication in this feature and should be black and white and well-focused. Do remove any beer glasses and sandwiches from the immediate area before taking a picture! Some otherwise excellent pics have had to be rejected because no effort had been made to set the scene.

MEDIUM WAVE BROADCAST BAND DX by Charles Molloy G8BUS

Reports to: Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG.

The part of the medium waves above 1550kHz is a fruitful source of DX both for the newcomer and the experienced DXer. Start off by locating Nice (France) on 1557kHz and Sarnan (Switzerland) on 1566kHz. The latter broadcasts in German and Romanisch.

Nice signs off for the night at 2300, clearing the channel for the English programme from Radio Mediterranean in Malta. This programme started at 2230 when it could be heard as a background to Nice but it is not practicable to separate the two with a loop as the bearings are too close together. The English programme from Malta which usually comes in well in the UK, lasts until 2330. The station does QSL and reports should be sent to PO Box 2, Valetta, Malta.

Now move up to 1562kHz and listen for the 1kW outlet at Covilhã in Portugal. This broadcaster is on the air 24 hours a day and isn't too difficult to hear in the UK as it operates 4kHz away from the nearest Geneva channel. Move now to 1566. Sarnan will have closed down for the night by now leaving the channel for Sfax in Tunisia, La Corruna in Spain and Leningrad in the USSR to fight it out between them. This is a frequency worth monitoring as you never know what may pop up.

Top End DX

Those who feel like staying up late will find the top end of the band can be rewarding. At this time of year it will be after midnight before Region 2 DX appears, two regulars from North America being WQXR on 1560kHz and CKLM on 1570kHz. WQXR is located in New York City so a loop will null out any QRM from Portugal on 1562kHz. WQXR is quite different from the majority of broadcasters in the United States. It is a serious music station owned by the *New York Times* and comes in well in the UK though it does fade to inaudibility at times. Write to WQXR Radio, 229 West 43rd Street, New York, NY 10036, USA, for a QSL.

CKLM is located at Laval in Quebec which is part of greater Montreal. This station is unusual in that the programm-

ing is in Quebec-style French, which may create problems when gathering material for a reception report. The address of the station is CKLM Radio, 1600 Est Boulevard St Martin, Laval, PQ, Canada.

There are three interesting and contrasting stations in the Caribbean that are heard frequently at the top end. Listen after 0030 on 1555kHz for Radio Cayman. Situated on a group of islands to the south of Cuba, Radio Cayman is sometimes quite a good signal in the UK. The time zone is GMT minus five hours, programming is in English and the address is PO Box 1110, Georgetown, Grand Cayman, British West Indies.

As a contrast listen on out-of-band 1610kHz for the religious Caribbean Beacon located on Anguilla, the most northerly of the Leeward Islands and then tune to 1580kHz for the Voice of America relay in Antigua which is also in the Leeward group. QRM can be a problem on 1580 but it does ease off considerably as sunrise approaches.

RSI

These letters stand for Radio Sweden International which is, as the name suggests, the external service of that country. Normally one would expect to find it on the short waves but owing to the proximity of Sweden to the UK, propagation is often better on the medium waves, especially after dark.

The daily programme, which lasts just half an hour, is varied, features such as *Panorama*, *Saturday in Sweden*, *Mailbag*, covering current affairs as well as different aspects of life in Sweden. Tuesday is the day for *Sweden Calling DXers* which has been on the air since 1948. It correctly styles itself as the longest running DX programme, appearing in five different language editions each week.

You can hear RSI on 1179kHz (254m) daily at 1830, 2100 and 2300 hrs UTC plus the s.w. channels 9-63MHz at 1100 and 6-065MHz at 1600 and 1830. The address, if you want to comment on the programme, ask for a schedule or send a contribution to *Sweden Calling DXers*, is RSI, S-105-10, Stockholm, Sweden.

Receivers for MW DXing


Last month we had a look at car radios and the possibility of adapting one for DXing. There is another specialised receiver almost tailor made for the DXer—a domestic style portable designed for taking radio bearings at sea.

I have such a set, the Hitachi "WH-1160 11 transistor 4 band radio." At first sight it looks like an ordinary portable, somewhat smaller in size than the Vega 204. There is a scale marked in degrees fixed to the top of the set, above which is a rotatable plastics box measuring 210 × 30 × 28mm which has a pointer that moves over the scale. The box contains the medium and longwave ferrite rod antenna. To use the set ashore just line the case onto true north, rotate the antenna box for a null and read off the bearing, or its reciprocal, from the scale. If you are not interested in d.f. then place the set in a convenient spot and rotate the antenna as required for optimum reception.

The circuitry of the WH-1160 is interesting. There is an r.f. stage for increased sensitivity and a b.f.o. selected by a switch at the rear. A front panel RADIO/DF switch, when in the DF position, helps one obtain a deep null by switching off the a.g.c. and switching in a level control in its place. The latter is a manually operated i.f. gain control. This arrangement really works well. It's a pity that the facility to switch off the a.g.c. is so rarely available on modern sets, even with quite expensive communications receivers.

The remaining two bands cover 1.6MHz to 12MHz using an internal ferrite rod antenna which has some directional properties. There is no provision for connecting an external antenna but a retractable whip is available to supplement the s.w. ferrite rod antenna.

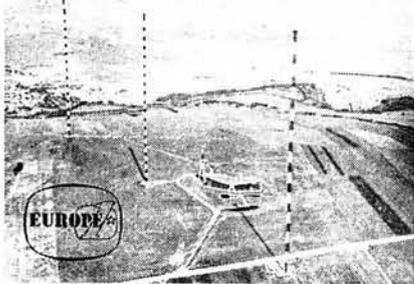This type of receiver is ideal for local radio DXing. It is very easy to use, is more sensitive on the medium waves than the average portable and it is possible to null-out TV buzz at my QTH with the rotatable antenna. The set performs well on the longwaves bringing in Sweden on 191kHz, Leningrad on 200, Morocco on 209, Oslo on 218, USSR on 236 and




QSL from Europe No. 1

Algeria on 254. The Hitachi WH-1160, which uses discrete components rather than i.c.s., is probably no longer available new but sets of this type are occasionally to be found on offer in radio shops though more often in small boat chandlers or in the advert columns of magazines such as the *Practical Boat Owner*. It would be interesting to hear from anyone who uses such a set for DX-ing.

Readers' Letters

Twelve year old **Paul McCarthy** who lives at Linwood in Scotland has been DXing for about a year using a Realistic DX200 receiver and a 25m long random wire antenna. Recent DX heard on the medium waves with this set-up includes Dubai on 1481kHz, Omdurman on 1295kHz which causes a heterodyne with the BBC on 1296kHz, Senegal on 765kHz, CJYQ St John's on 930kHz,

RADIO
MEDITERRANEAN
MALTA

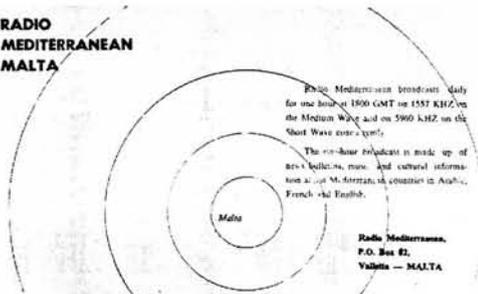

QSL from Radio Mediterranean, Malta

Schedule from Radio Sweden International

WMRE in Boston on 1510kHz, WNEW New York on 930, Radio Globo in Rio de Janeiro on 1220. Paul asks for the address of Europe No. 1 (185kHz), which according to their QSL card, is Europe No. 1, PO Box 209, D663 Saarbrücken, West Germany.

Reader **John Ratcliffe** has been modifying the internal ferrite rod antenna of two early transistor receivers—a National and an AWR Radiola. The first "mod" was to rewind the main m.w. winding using Litz wire, which sharpened up the tuning considerably. Then John fitted an additional 7 turn coupling winding on the rod, which was brought out for connection to an external antenna or a loop. This winding was moved along the rod to find the best position and then

fixed with adhesive. "There are no birdies, whistles, images or what have you. If any reader is interested in modifying receivers this way then I would be pleased to hear from him and will pass on any information". John's address is 1/37 Whiting Street, Southport 4215, Queensland, Australia.

My note about the Greek station on 981kHz in the February issue brought an interesting response from reader **Antony Vaughan** of Southampton. The station on 981kHz now carries the ERT2 programme of the Government owned network. A lettergram from ERT (Hellenic Radio) to Antony stated that ERT1 and ERT2 are to be merged and the address will be Messogion 102, Attiki, Greece.



SHORT WAVE BROADCAST BANDS

by Charles Molloy G8BUS

Reports: as for Medium Wave DX, but please keep separate.

Telling the time is normally not a problem for most of us, except perhaps on the two occasions each year when the clocks go forward, or back, an hour. The s.w.l. though will find that life is not so simple. Listening to other parts of the world brings us in contact with different time zones. If we monitor the Pacific Service of Radio Australia on 6-035MHz in the 49m band, which comes in well in the UK in the evening, we will hear programmes intended for a breakfast audience on the far side of the world! The DXer has his own problems. He must decide whether to keep his log in GMT, which is standard practice, even though it may be summertime. What time and date shall be quoted in a reception report? What do the letters UTC stand for?

What Time Is It?

Early last century it was agreed internationally that Greenwich Mean Time (GMT), centred on the Greenwich meridian, would be regarded as universal time. All other time zones are related to GMT, 15 degrees of longitude corresponding to

a one hour time difference. The east coast of USA for example, which is approx Long 75° West, has the time zone GMT minus five hours. This is called Eastern Standard Time (EST). Similarly, Sydney Australia, which is approx 150° E, is ten hours ahead of GMT.

Again by international agreement, it was decided quite recently that Co-ordinated Universal Time, denoted by the letters UTC, would be the new universal time for radio purposes. There is a slight difference between UTC and GMT but the two are brought into line either on June 30 or December 31 each year by what is known as a leap second. For practical purposes GMT and UTC are the same.

Unfortunately, UTC is not yet in general use, as a period of a few years was allowed for the changeover, so the listener at the moment will come across both GMT and UTC. There is an alternative method of denoting GMT and that is by the small letter z. This practice occurs in navigation and occasionally creeps into radio literature. There is no problem really as 1100GMT =


1100UTC = 1100z. The 24 hour clock is always used, there being no place for am and pm in international broadcasting.

Reception Reports—Date and Time


The golden rule when writing to international broadcasters is to use UTC (GMT), even although summertime may be in operation. Quote what is known as the Greenwich Date. To go back to Radio Australia. If we are listening at 8pm on March 26 this corresponds to 6am local time on the 27th in Australia. Write out the reception report in the form 2000 hours UTC (GMT) on March 26. Ignore summertime, as it will certainly lead to confusion. There is no common changeover date and summer in the northern hemisphere corresponds to winter in the southern and vice versa.

It is tempting, when writing to domestic broadcasters on the tropical bands or on the medium waves, to use the station's local time just in case GMT or UTC is not understood or there is a mis-


BUMPER SPRING ISSUES

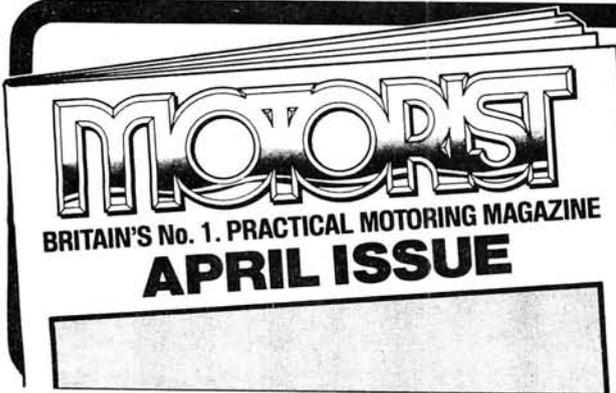

FREE GIFT
LITTLE CHEF MAP

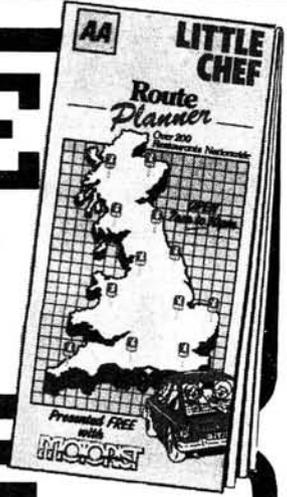

FREE GIFT
20 FISCHER WALLPLUGS

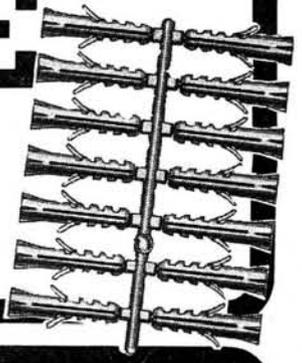

SPECIAL FEATURES:
AIDS TO BETTER GARDENING—
Hand Cultivators, Chemical
Weed Killers and sprayers.





QSL card from Argentina sent in by Andrew Hill

QSL card from Red Cross sent in by Glen Hocking

QSL card from Voice of Nigeria sent in by Kevin Lewis

QSL card from Voice of Vietnam sent in by Glen Hocking

understanding over the date. It is better not to do this unless you are absolutely sure of local time, say as the result of a time check over the air. Use the local date on your report if you use local time and to be safe, give UTC and the Greenwich date as well.

Logs

Reader **Simon Griggs** complains that "the short wave section has very little if any lists of what stations have been heard" while **D. Prince** (Llandyssul) likes reading about "other bods' logs". Stations heard by other DXers are of considerable interest and form the backbone of DX club bulletins, where there is space for lengthy lists that are able to include the easy as well as the DX type loggings. Anyone with more than a passing interest in the hobby should join a DX club. A copy of the EDXC club list referred to in the February issue will give the prospective member a chance to obtain a specimen copy of several club bulletins, before deciding which one suits him. Clubs, like people, vary a lot.

Logs for this column should supplement rather than compete with DX club bulletins. New stations, rarities, unusual loggings, even everyday ones if made by newcomers using simple equipment. Readers will want to know the gear in use, the antenna, the time of day, the frequency, as it will help them when they try to pick up the same broadcasts themselves. Contributors to club bulletins follow this practice. Users of simple receivers will not be able to provide the exact frequency but even "the h.f. end of the 15MHz band" would help others who might be tempted to try themselves.

Interval Signals

In order to assist listeners to home-in on a station before the start of the programme it has long since been the practice to transmit a distinctive interval signal. There is an infinite variety of them

ranging from a few bars of electronic music (AWR) to a recording of farmyard animals (Botswana). Perhaps the most famous and certainly the best known was the letter "V" in Morse used by the BBC during the last war to identify its transmission to occupied Europe.

The need for an interval signal will disappear as receivers with digital readout become the norm though one hopes they will remain as the station's signature tune. Interval signals are of great value to the DXer as an aid to station identification, that is if one can remember them. The *WRTH* tries to help with some stations by printing a few bars, if the signal is a musical one. Not everyone can read music though. *DX Party Line* from HCJB which is on the air on Mondays and Saturdays at 2130 UTC on 15.295MHz and 17.79MHz features the "interval signal of the week". This is played several times before the identity of the broadcaster is revealed, which does help to imprint it on the memory.

Tape recordings of interval signals have been compiled from time to time, one currently being available from the Handicapped Aid Programme. The list which accompanies the tape classifies signals according to type, which does help a lot. Further information on this and other tapes of interest to DXers, is available by sending a SAE to HAP(UK), c/o EDXC, PO Box 4, St Ives, Huntingdon, Cambs, PE17 4FE.

Readers' Letters

"A sample copy of *Contact*, the publication of the World DX Club, 17 Motspur Drive, Northampton NN2 6LY is available for 50p or 2 IRCs (3 IRCs airmail). The bulletin is directed towards m.w. and s.w. broadcast band enthusiasts and contains no amateur radio news" writes Arthur Ward who is the producer of *Contact*. He goes on to say that the WDXC has never gone over the 500 membership mark, always seeing that a quarter of the total reside overseas.

"I recently had a bargain of a lifetime" writes **John L. Hopkins** of Oxford who paid a "fiver" for a Codar CR70A with PR30 preselector and Joymatch antenna. John would like to know where he can purchase a manual for the CR70A as Codar are no longer in the radio business. Can anyone help?

"I now use a Tandy Realistic DX60 receiver" writes **Adrian Childs** of Dorchester who is full of praise for his latest acquisition which covers the medium waves, short waves: 3MHz to 26MHz in three bands, v.h.f. 88 to 108MHz and CB. Using the receiver's whip, Adrian heard Radio Bagdad in English on 9.61MHz at 2130. When used with a roof-top v.h.f. two-element antenna the DX60 pulled in All India Radio on 9.665MHz at 2015, the Voice of Nigeria on 15.12 at 1800, Radio Hanoi on 10.04 at 1800, all with programming in English. A v.h.f. or TV antenna often makes a good short wave antenna.

"A good catch I recently had was Radio Impacto, a new station in San Jose, Costa Rica—around 0500 on 6.15MHz" writes **Shoyab Patel** of Dewsbury who was using a Panasonic R50B receiver along with an 8 metre long external antenna. Our reader also mentions the Voice of Peace which is now on 6.24MHz with a power of 400 watts to be raised to 10kW. Reader **J.R. Sadler** of Bishop's Stortford picked up Radio Argentina on 15.345MHz with his Astrad 6010, time of reception not mentioned, while **S.R. Smith** of Crewe heard Radio Kuwait on 11.675MHz, no details of receiver or antenna quoted.

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISERS**



QTH: Loc
BL 40 G
99
FREDDY DE WITTE
Monsieur 1
104-40 (G) (G)
Zuidland
The Netherlands
TV - DX
VHF UHF - DX

NL-7357 **The Netherlands**
member of Veram 5044-4-85

Fig. 2



Fig. 3



Fig. 4

day on the 11th, only to fall again to average around 29.5 as gales swept across the country for several days.

Looking back to the opening on December 1 and 2, Simon Hamer, New Radnor, heard signals through the 144MHz repeaters in Buxton GB3HH R4, Horsham GB3BP R6, Lincoln GB3LN and Martlesham Heath GB3PO R3 and Dutch stations on one of the repeaters on R0. As I have said before, it is sometimes very difficult to identify a particular repeater during an opening because of the large number that use the same channel. On December 4, George Grzebieniak G6GGE, London, using his new antenna system, worked 4 OZs and a PA on 432MHz. During the opening on the 29th, he exchanged good reports with 3 stations in France, 1 in Guernsey and 2 in Germany on 432MHz and DK8SG on both 432MHz and 1296MHz. In his station, Fig. 3, George has an FRG-7 receiver fed by a 20m long wire antenna, a Plustron TVR5D for DXTV, an IC-211E for 144MHz and transverters for 430MHz and 1296MHz.

During the mornings of the 3rd and 4th, Fred Southwell G6ZRU, worked stations in France, Denmark and Holland and during the evenings of the 28th and 29th he worked into Belgium, France and Germany on 144MHz. At his home in Henfield, Sussex, Fred uses a FT-101ZD, FTV-901R transverter and 8-element quad antenna for 144MHz. Around 1730 on the 28th, I heard a Sussex G2 station, working through a repeater on R6 say "conditions are exceptional" and that he had heard French, Belgian and German stations on 144MHz as well as several continental repeaters. Alan Taylor heard many 144MHz repeaters on the 29th and a very strong signal from DJ2HH.

Band II

That early December tropo produced strong signals for Simon Hamer from stations in Belgium BRT II, Egem, France TDF Cultur from Abbeville, Boulogne, Caen, Lille, Rennes and Vannes, Inter from Caen, Musique from Lille, Niort and Rennes, Holland NOS-1 from Goes and Smilde. In addition there were BBC Radios Devon, Kent, Sussex and York and ILR Orwell, Trent and Southern Sound. A similar report for the period, with the addition of the ILR stations BRMB, Capital Radio, Chiltern and

2CR, came from 14-year-old **Damien Read** using an Amstrad TS35 and a Philips 901 music centre at his home in Newport.

Albert Moulder, Rainham, tells me that he has received confirmation from David Cox, Engineer in Charge of BBC Radio Sussex, for his reception report and says that following the World Administrative Radio Conference in 1979 many more broadcast stations will appear in the 102/104MHz region of Band II.

By the end of 1983, **Brendan McNamee**, Loughborough, using an Akai AJ500FL with its own telescopic antenna, added BBC Radios Cambridge and London, ILR Capital and Wiltshire and a French station to his DX score during the opening on December 29. Brendan has now received QSL cards from BBC Radios Sheffield and Sussex, ILR Chiltern and stickers from LBC and is looking forward to future openings when he can put his homebrew antenna pre-amplifier to the test. "On December 29 the Dutch, French and Germans were rocketing in", said Damien Read, who logged French stations on about 20 spots in Band II, heard Belgium for the first time and hopes that one day there will be a tropo big enough to receive stations from the USA. Don't we all Damien!

French stations were predominant in the logs of Harold Brodribb, St Leonards-on-Sea, who counted 23 in the band on the 28th and 15 on the 29th. Ian Kelly, Reading, added detailed accounts of the stations he also received from Belgium, Germany and Holland between the 28th and 30th. "On the 29th, ILR Signal Radio was strong and the DJ Erika Hughes couldn't believe she was receiving phone calls from listeners in places such as Essex, Farnborough, Luton and Oxford", writes Ian, who also identified the station SWF-2 from Hornisgrinde on 96.2MHz and heard other German stations in Band II on January 1.

In Belfast, Bill Kelly, using a Panasonic DR2800, heard French stations at 0515 on the 26th, French and German between 0500 and 0600 on the 29th and a German at 0420 on January 3. At times during December, Bill, with a Grundig Satellit 3000, received signals from BBC Radios Barrow in Furness, Cleveland, Clyde, Cumbria, Leeds, Scotland and Wales and ILR stations Ayr, BRMB, Manx and Red Rose.

Late on the 29th, Simon Hamer received signals from BRT-2 West Glan-

ders, the German stations NDR-1 and 2 from Aurich and Harz, WDR-1, 2 and 3 from Teutoburger Wald and at 0040 on the 30th he listened to *Rainy Days on Mondays* by Paul Williams, on the BFBS station at Langenberg.

RTTY

Congratulations to Ted Double G8CDW on being made an honorary life member of the British Amateur Radio Teleprinter Group for his long service as contest manager and to their retiring chairman "Smudge" Lundegard G3GJW on his unanimous appointment as BARTG's President at their AGM. Congratulations also to Eric Yeomanson G3IIR, one of the founder members of BARTG, on becoming honorary vice president of the Radio Society of Great Britain and to Tony Oakley G4HYD, former BARTG newsletter editor, on receiving the Norman Keith Adams Prize, awarded by the RSGB for his article in *RadComm* on a simple tuning indicator for AMTOR and RTTY signals.

Readers wishing to join BARTG, who celebrate their Silver Jubilee during 1984, should send an s.a.e. to John Beedie G6MOK, 161 Tudor Road, Hayes, Middx. The current membership fee is £5 per annum and their quarterly newsletter, free to members, is packed full of information on such subjects as AMTOR, Computers, FAX, Mechanical Hardware, RTTY, satellites and telemetry.

During the month prior to January 10, Peter Lincoln BRS42979, Aldershot, found RTTY signals on 14MHz coming mainly from Europe and a few from Asia in the daytime and occasionally from north-America during the late afternoons. On those days that the band remained open well into the evenings, Peter logged fairly strong signals from south-America. Although 21MHz was generally quiet throughout the period, Peter did log some stations from the USA during the afternoons.

Peter's RTTY equipment, MM2001 and Tono Theta 550 terminal units and Panasonic TC800G monitor, can be seen along with his Icom IC-R70 and Realistic DX300 receivers at his operating desk in Fig. 4.

At 1030 on December 25, I watched a station print a screen-filling Christmas tree made up of the letters "O" and "X" with the words MERRY CHRISTMAS

arranged in the middle. At 1102 on January 1, a Spanish station printed a large "73", taking up several lines on the screen, as he signed off with an IT9.

Although Norman found RTTY activity generally quiet during the month preceding January 14, he is very pleased with the signals he did receive on 14 and 21MHz from stations in DU, FG7, JA, OX, VK2, 3 and 6, XE, ZS6, 5N3 and from FB8WK on Crozet Island. At 1700 on December 18 he copied a Belgian station on 14-078MHz using 75 baud. Despite my limited operating between December 16 and January 15, I did copy RTTY signals from 11 prefixes, DL, EA, F, G, I, IT9, OE, OH, ON, SM and YU on 14MHz around 14-090MHz and 11

call areas, G, UW, VE, Ws 1, 2, 3, 4, 8, 9 and 0 and 9K on 21MHz around 21-090MHz.

Tailpiece

Last September, Simon Poysden ZR6AGN (G1BND), Hillbrow, Republic of South Africa, spent four weeks in Cyprus and using the callsign ZR6AGN/5B4 from Limassol found propagation excellent and had no trouble accessing 144MHz repeaters in Israel. During his trip, Simon worked stations in Cyprus 5B4 and ZC4, Israel 4X4 and 4X6, Lebanon OD5 and Island of Rhodes SV5 and among his interesting

QSOs was one with KJ1L/MM, sailing past the south coast of Turkey, via the Haifa repeater in Israel. Throughout the tour Simon used a Yaesu FT-480R and Araki 5/8 colinear antenna and says that amateurs in both Cyprus and Israel are busy building repeaters for 430MHz. Simon also managed a bit of h.f. working back to ZS from the station of 5B4BS.

"73s to all in UK" writes Edward Baker, Benidorm, Spain, who, with a Panasonic RF-3100 receiver and telescopic antenna, can hear stations in Alicante, Castellor and Valencia. He adds, "If one counts the RNE 2 and 3 outlets there are 32 f.m. stations audible so DXing is hard due to this many filling the band."

TELEVISION by Ron Ham BRS15744

Reports: as for VHF Bands, but please keep separate.

Once again the main cause of the DX under review this time, is tropospheric. **Roger Wallis**, Solihull, has sent two weather pictures that he received from Anglia TV last September and RTBF Belgium in November, Figs. 1 and 2. They provide a quick source of information about the progress of the high-pressure systems that are mainly responsible for the long-distance television pictures we all look for.

Amateur Television

The annual pram race for charity, which took place at Pagham, Sussex, on Boxing Day, attracted some 60 competitors and the event was recorded for posterity by **Ted Brodie** G6HTB, **Richard Butterworth** G6FDU, **Brian Dubbins** G8OCN and **Robin George** G6AII. Ted's home-brew transmitters feeding MBM48 antennas were installed at two points on the 3km route, the Lamb Inn, Fig. 3 and the Kings Beach Hotel, so that live pictures, including graphics and titles by **Caroline Butterworth** with a Commodore 64 computer, were seen at both places. **Charles Nightingale** G3IDX and wheelchair mobile **Alf Maynard** G3UPQ organised the 144MHz talkback and progress reports of the race. The group wish to thank messrs Jaysound Audio of Bognor Regis for the loan of a JVC GX-78E camera used by G6AII at the Lamb Inn (Fig. 4), and **Andy Hearny** G3UEQ for his technical assistance. Andy received the 150mW pictures from the event at his QTH in Chichester 10km away and a P2 reception report came from **Henry Kaminski** G5NBX who received the signals off the side of the beam. The edited tapes will be shown to the contestants and at local homes for the handicapped and hospitals. Congratulations to all concerned, I heard that at least 500 man hours went into organising and planning the filming of the race.

During the December openings **Steve Green**, Malvern received an ATV test card and picture, Figs. 5 and 6, from G6CUQ in Redditch and Ted Brodie,

Pagham, received ATV pictures from stations in Belgium and Germany with his 430MHz up-converter into a Ferguson TX receiver and MBM48 antenna. Ted also has a Sony HVC20000P camera which he used at the Kings Beach Hotel during the pram race.

SSTV

During 1983, **Richard Thurlow** G3WW, March, made 204 SSTV QSOs mainly on 14MHz with a few on 144MHz, spread over 29 countries. Of this number, 106 were first-timers bringing Richard's worked-first-time score, since November 1972, to 1956. Two-way colour pictures, including the new 24 seconds single-frame colour, were exchanged with more than 25 stations world-wide. "G4NJI has received the "print out" board from the SC-1 from Volker Wrasse, believed to be the first in the UK," writes Richard and adds, "G4DYB and G4NJI can be found, almost nightly, on 144.5MHz f.m. or 144.23MHz s.s.b. with G3CCH around 2100GMT". Thanks for the gen Richard, no doubt **Peter Lincoln**, well-known for his SSTV viewing with a Volker Wrasse SC-140, will look out for them. "Among the rarer signals was HB0AWQ calling CQ with no reply and stations from DJ, I, LA, YO and YU were seen quite often" writes Peter in his report for the month ending on January 10.

Over in Germany, **Allan Sancto** DD5FM/G6BWH is building the SSTV analogue-to-digital converter described in the RSGB journal *Radio Communication* by Brian Smith G3WCY. Two of Allan's colleagues are also building the device and Allan thanks one of his local radio club experts, Udo Elstner DF4MO, for his technical assistance. I look forward to hearing more from all of you Allan.

Band I

On December 17, **Ian Davidson**, Carmarthen, using a Vega 402DE receiver and pre-amplifier noted short bursts of

test card from Poland and an analogue clock showing 3 hours ahead of GMT on Ch. R1 49.75MHz. Between 1700 and 1900 on the 18th, he watched a puppet show from Switzerland on Chs. E2 48.25MHz and E3 55.25MHz, a caption Artwelt on E2, and the news from Poland was fighting for predominance on Ch. R1 with Swiss television on Ch. E2. Ian was surprised at these results, especially as he was using a Band II Yagi at the time, however, Ian has plans for a wideband antenna for Band I and is looking forward to the 1984 sporadic-E season. Between 1400 and 1700 on January 11, Ian received a cartoon film and a sort of quiz programme from RAI Italy on their Ch. B 62.25MHz.

During a sporadic-E opening on December 23, **Philip Heaney** received pictures from Poland with the dt caption behind the newsreader on Ch. R1, as did **Fraser Lees**, Ringmer. He also identified Russian pictures on both Chs. R1 and R2. At midday on the 21st, **Steve Green** received a test card from TV1 Sweden on Ch. E2, YLE TV1 Finland on Ch. E3 and during a similar event on January 7, he logged pictures, possibly from the USSR, on Ch. R1. It looks as though the upset hung about because early the following morning, I received pictures of some form of wrestling, followed by news with a YL presenter on Chs. R1 and R2. Both Steve and I logged bursts of activity on Chs. E2 or R1 with glimpses of test card from Sweden on Ch. E2 and Poland on Ch. R1.

The majority of Band I enthusiasts have seen Russian words appear on their screens, especially during the sporadic-E season. Thanks to **Cyril Fairchild** G3YY, Brighton, who sent the following translations for the benefit of TVDXers. BPEMR = Time(S), NEWS; CNOPT = Sport; HOB0CTb = News; NPORPAMMA = Programme; TACC = TASS News Agency; CCCP = S.S.S.R. (USSR); TB or MB = TV; COObWAET = Report or Information; YTPHEHNN-NOYTA = Morning-Post-



Fig. 1

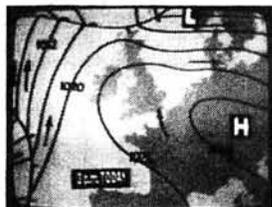


Fig. 2

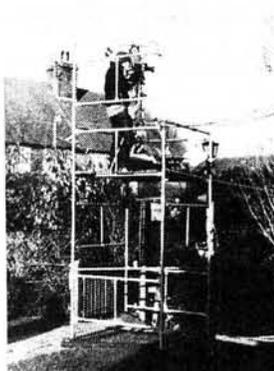


Fig. 3



Fig. 4



Fig. 5



Fig. 6

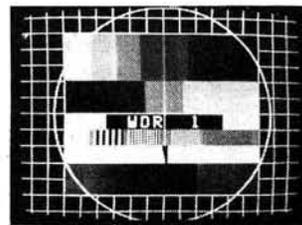


Fig. 8

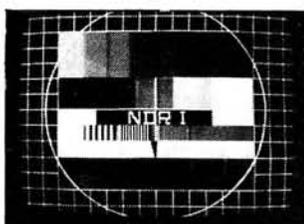


Fig. 9



Fig. 10



Fig. 7



Fig. 12



Fig. 13



Fig. 14



Fig. 11

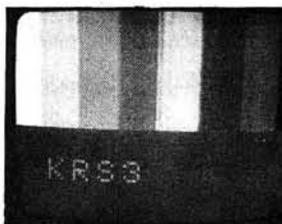


Fig. 15



Fig. 16

Programme; MOCKBA = Moscow; NPABAA = Pravda.

Readers, please remember, we cannot print some of the Cyrillic capitals correctly but our interpretation of the precise form sent by Cyril should suffice.

Tropospheric

Like many of us **George Grzebieniak** found Band III wide open when he received pictures from Belgium on Chs. E8, 10 and 11 and Holland on E5, 10 and 11 during the tropospheric openings on December 4 and 5 and 28 and 29. He also logged DR Denmark on Ch. E7 and the 3rd and WDR Germany on E11 on the 29th. Among the pictures George showed me was a clock caption, Fig. 7, that he received from Denmark on Ch. E10 during a similar event on August 29.

Like George, **Philip Heaney**, Norwich, received the test card from Denmark on the 3rd and 4th as well as seeing such captions as BRT-1, DR, FR3, PTT-NED 1 and 2, Sverige TV2, TDF and ZDF, plus a card showing a coat of arms with the words Niebull Canal and another saying Schleswig Canal 45, on the v.h.f. and u.h.f. bands.

On December 1, **Simon Hamer**, New Radnor, received pictures from France on 8 spots between Chs. 21 and 63 and on the 2nd he watched a documentary about the German occupation of Brussels in 1940, as excellent pictures from BRT TV1 and TV2 pounded into Wales from Egem on Chs. E43 and 46. Between 1800 and midnight on the 29th, Simon saw a clock and *Journal Televise* from RTBF-1, *Nos Journaal* from Holland, a programme *Orwell auf Jura* from Germany on ZDF and the captions Ard Hessischer Rundfunk-3 and ARD/WDR-1 spread between Bands III, IV and V.

"A really fine opening" said **Alan Taylor**, Coventry, whose report about Band III was similar to the others. He writes, "The u.h.f. band, Chs. 21 to 69, was so good that I received London ITV at a better strength than my local Central TV! and there were many Dutch and German stations on at incredible strengths".

In December, **Roger Wallis**, Solihull, was given a 19in Hitachi colour set and on the 29th he used a Belgian PM5544

test card to adjust it correctly. On the 3rd, Roger received pictures from Denmark, Germany and Holland. Like myself on the 29th he watched the afternoon programmes from Belgium on Ch. E8 and logged a test card on E10. Roger also watched colour Teletext information from RTBF on Ch. 41 and Anderlues test card on Ch. 61. At 1715 I watched an episode of *Chopper Squad*, with subtitles, in colour from Belgium on Ch. E10 and saw the captions Beste Wensen 1984 SPD above a news reader on Ch. E9 and BRT Journaal on E10.

"All together a very good trop" writes **Tony Palfreyman** about those first few days in December after he logged most of the continentals that were about. These included German regionals like NDR-1, Fig. 8, WDR-1, Fig. 9, WDR III, Fig. 10 and his best catch of all was DDR-2 from East-Germany on Ch. 34. Tony's pictures of the German newscaster, Fig. 11, and Teletext, Fig. 12, will give some idea of the strength of the DXTV pictures received during the December openings.

"On December 2, I tuned to ZDF

West Germany, they were transmitting an experimental stereophonic broadcast programme with various items with stereo sound including Henry Mancini and speech in stereo", writes **David Girdlestone**, Norwich, who photographed one of their captions Fig. 13.

Last November, **O.J. Jones**, Stoke-on-Trent, received bursts of signals between Chs. 6 and 8 in Band III and will no doubt be interested in the fluctuating conditions observed by Tony Palfreyman in Stannington during the late December tropo. "It started in the afternoon of the 29th, with snowy pictures from Holland on Chs. 39 and 45 and as the evening drew on these pictures became very strong. Checking the channels, I found Belgian stations on Chs. 42, 43, 46 and 62. The pictures received at this time were suffering from co-channel interference and for about 10 minutes hardly anything was identifiable, even local pictures were rolling. Then German stations were seen on the channels where there had been Belgian and Dutch", writes Tony. He added "On our local IBA Channel 4 from Belmont on Ch. 32, a WDR III test card could be clearly seen in the background and as the German stations went off the air a lot of British stations came up. This was certainly a hard tropo to work with the constant changing in selectivity of countries, but it was a very interesting

event". I am sure Tony that many newcomers to TVDXing will appreciate your description of this event and know now, that one can expect anything to happen when the atmospheric pressure is high and the troposphere is disturbed.

"TVDX on the 29th was remarkable", writes **Harold Brodribb**, who received a test card from RTL Luxembourg, Ch. E7, the film *Jack of Diamonds* and adverts for road safety and a building society on Ch. E5 and like the rest of us, some very strong continental pictures in Band III. He also saw a notice "RTE 1 regrets poor reception in some areas" on Ireland's Ch. D (175.25MHz, same frequency as Ch. E5). "I have never seen Eire before", said Harold.

Station Reports

My thanks to Filip Rogister, Overijse, for the information that BRT is the abbreviation for Belgian Radio and Television—Flemish section and BRT-TV1 and TV2 on the test cards are the first and second networks. RTBF is the French network in Belgium. Filip also tells me that the TV pictures, Figs. 5, 7 and 8 in our January issue are in fact Dutch and not German as I said (sorry about that) and that the NCRV in Fig. 7 is a Dutch programme company name as is Vara, Tros and Ikon. We often see

these names and enjoy the programmes when conditions are right Filip.

Thanks as well to Jan Van Der Horst, Arnhem, who also told me about the Dutch programme makers and adds the names Avro and Veronica and writes, "the programme company has broadcast time, NOS is the super-structure that coordinates everything, cameras, studios, etc, and the PTT provides the links between studios and the different transmitters."

While in Germany on Christmas Day 1982, Steve Green received a Merry Christmas caption from PTT-NL Holland, Fig. 14 at 200km and among the DX signals he logged in the UK last December was a set of colour bars inscribed KRS3, Fig. 15, any ideas readers?

I mentioned a test card with a digital clock and the name Wendelstein on it in a recent column and from Germany, **Allan Sancto** writes, "This could have been Germany 1 ARD, Wendelstein refers to the mountain on which the antennas are located, as the enclosed post-card, Fig. 16, shows. It's 1840m high and from the peak one can see through to Austria and Italy. Also located just below the antennas is a solar observatory". Allan tells me that his QTH is about 13km from Wendelstein and he has a superb view of the range from his shack window.

UPGRADING THE DX160

▶▶▶ continued from page 32

feasible to run the set from dry batteries as an alternative to a car battery. The socket connections are shown in Fig. 4. If the plug is missing then a Tandy 274-1210 plug can be made to fit by removing one of its pins.

DX150

This receiver, with either the suffix A or B, pre-dates the DX160 but superficially it looks the same. The DX150 has only four bands, the long waves being omitted. It has an internal loudspeaker, the external loudspeaker sockets for the DX160 at the rear being replaced by a switch for changeover from mains to 12 volt working.

Internally there is quite a difference between the two receivers though the circuitry appears to be the same. The main p.c.b. of the DX150 is not silkscreened though T16, T17 and T18 are easily located but it is more difficult to identify C16 and C19 below the board. The components associated with the "front end" are on a separate small

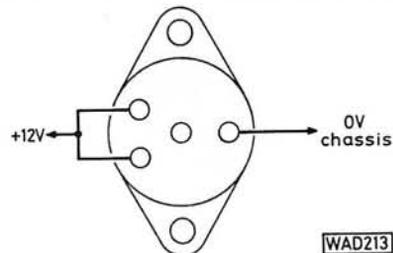


Fig. 4: Power socket connections

board mounted at right angles to the chassis beside the wavechange switch. Capacitor C16 can be found without difficulty as it is the large component adjacent to the oscillator section of the switch. Tapping on a fixed capacitor provided digital readout as before though this time 22pF was needed. The highest frequency band (D) has the oscillator on the l.f. side of the incoming signal. Un-screened coils are used in the r.f. and oscillator circuits but a space with hole is conveniently left for an r.f. coil for medium-wave use. ●

the things
people say



Mike is in hospital with appendix: He never did miss an opening!

... heard by John Tye G4BYV

I'm sorry about my transmission this evening, old chum, but my daughter has gone to bed in the next room and as I don't want to disturb her I've switched to low power.


... heard on 144MHz by M. Minns G4MIN

This repeater is very generous with its time-out; most repeaters only give you 90 seconds but this gives you 1½ minutes.

... heard on GB3SC by G6JYN

Do you know what time it is!

When the globe of this digital clock is revolved, a red lamp indicating a major city in the world will blink, and the current time of that city will be displayed. At a glance know the current times of 24 different time zones. This mini-globe clock stands 195mm. high and also has an alarm fitted. This useful device should stop you getting your Amateur friends, on the other side of the world, out of bed in the middle of the night.

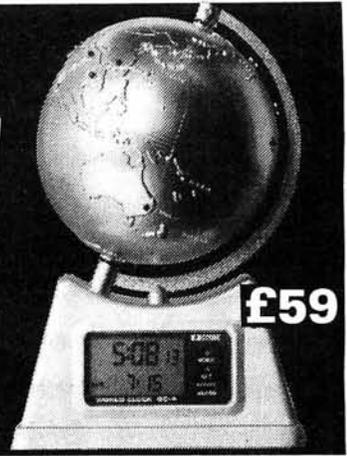

£59

Thanet Electronics 143 Reculver Road, Herne Bay, Kent
Tel: (02273) 63859/63850

LAR THE AMATEURS PROFESSIONAL SUPPLIER LAR

TRIO / ICOM / LAR PRODUCTS / AERIALS


BE SURE



WITH THE NOISE BRIDGE

Price £36.95 inc VAT P&P £2


SWITCH TO QUALITY

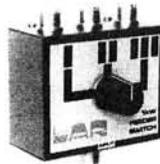

WITH THE FEEDER SWITCH

Price £19.95 inc VAT P&P £2

MORE POWER TO YOU

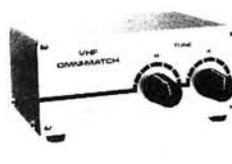

WITH THE VHF OMNI-MATCH

Price £34.95 inc VAT P&P £2

HEAR MORE



WITH THE SWL OMNI-MATCH

Price £39.95 inc VAT P&P £2

LEEDS AMATEUR RADIO 27, Cookridge Street, Leeds. LS2 3AG. Tel. 452657

Please send for our Catalogue and/or Antenna Catalogue

60p EACH or £1.00 FOR BOTH PLUS PRICE LIST

Goods By Return Subject To Availability

SALES/SERVICE/MAIL ORDER

PW



AT YOUR SERVICE 24 HOURS EVERYDAY THANKS TO Ansafone

Depts. 60, Green Road, Meanwood, Leeds. LS6 4JP. Tel. 782224

FREQUENCY COUNTERS

HIGH PERFORMANCE
HIGH RELIABILITY
LOW COST

EX-STOCK
DELIVERY


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz - 1.2GHz
- ★ Sensitivity < 50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100	(100MHz)	£104.36
METEOR 600	(600MHz)	£134.26
METEOR 1000	(1GHz)	£184.86

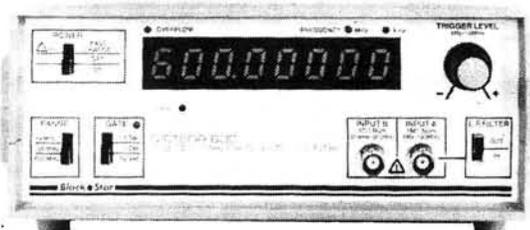Illustrated colour brochure with technical specification and prices available on request.



Designed and manufactured in Britain.

Black★Star

BLACK STAR LTD (DEPT. P.W.), 9A Crown Street, St. Ives, Huntingdon, Cambs. PE17 4EB, England.
Tel: (0480) 62440 Telex: 32339

GAREX (G3ZV1)

RESISTOR KITS a top-selling line for many years. E12 series, 5% carbon film, 10Ω to 1M, 61 values, ratings ½W or ¼W (state which). Starter packs 5 each value (305 pieces) **£3.10**
 Standard pack 10 each value (610 pieces) **£5.55**
 Mixed pack, 5 each ½W + ¼W (610 pieces) **£5.55**
 Giant pack, 25 each value (1525 pieces) **£13.60**
SR-9 MONITOR RECEIVER 2m FM with 144-146MHz full coverage VFO + 11 xtal controlled channels; ideal for fixed/M/P use. 12V DC operation **£47.50**. Mains adaptor **£9.50**
CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B All 2m channels from 0 (145.00) to 33 (145.825) incl. also 144.80, 144.825, 144.85 Raynet at **£2.60** (+ 20p post per order). Over 40 popular marine channels for SR-9, etc at **£3.00** (+ 20p post).
PYE RADIOTELEPHONE SPARES (see full list). Ex. equip., fully guaranteed. **CAMBRIDGE AM10** 10.7MHz I.F. **£3.65**. 2nd mixer **£3**. 455KHz block filter 12½KHz **£9.40**. Ditto 25KHz **£3**. 455KHz AM I.F. **£4.95**. Audio bd. **£1.95**. Aerial relays **£1.50**.
WESTMINSTER W15/W30 AM RX RF 68-88MHz or 148/174MHz **£6.95**. 10.7MHz IF (inc. 12½KHz xtal filter) **£8.25**. 2nd Osc **£2.10**. 455KHz IF **£5.65**. 455KHz block filter (12½KHz) **£7.35**. Squelch **£1.45**.

**SCOOP PURCHASE
 OF BRAND NEW PYE
 WESTMINSTER & PF70
 SERIES SPARES** s.a.e. list

GAREX FM DETECTOR & squelch conversion for Pye R/T equipment. Ready assembled, full instructions. Tailor-made, easy-fit design, replaces existing squelch board, with minimum of modifications. For AM Cambridge **£6.30**; for Vanguard AM25B (Valve RX) **£6.10**; for Transistor Vanguard AM25T **£6.95**.

★ REVCON ★

A superb quality 16-element, all British made, VHF/UHF broadband fixed station aerial from Revco. Ideally suited to SX200 and other VHF/UHF receivers. Covers 50 to 500 MHz. **PRICE £24.95 inc.**

MAIN DISTRIBUTOR OF REVCO PRODUCTS
 PRICES INCLUDE UK POST & PACKING & 15% VAT.



GAREX ELECTRONICS
 7 NORVIC ROAD, MARSWORTH, TRING, HERTS HP23 4LS.
 Phone 0296 668684. Callers by appointment only.

Goods normally despatched by return



SX200-N THE SUPERIOR SCANNER



- ★ THE CHOICE OF THE PROFESSIONALS
- ★ MICROPROCESSOR CONTROLLED 32,000 CHANNELS
- ★ AM & FM ALL BANDS
- ★ WIDER COVERAGE: 26-58, 58-88, 108-180, 380-514MHz; includes 10m, 6m, 4m, 2m, & 70cm Amateur bands.
- ★ 5KHz & 12½KHz FREQUENCY INCREMENTS
- ★ 16 MEMORY CHANNELS WITH DIRECT ACCESS
- ★ SPECIALLY DESIGNED FOR EUROPEAN MARKET
- ★ 2 SPEED SCAN SCAN DELAY CONTROL
- ★ 2 SPEED SEARCH UP AND DOWN
- ★ SEARCH BETWEEN PRESET LIMITS UP AND DOWN
- ★ 3 SQUELCH MODES inc. CARRIER & AUDIO
- ★ RELAY OUTPUT FOR Aux. CONTROL
- ★ INTERNAL SPEAKER, ALSO EXTERNAL SPEAKER & TAPE OUTPUTS
- ★ LARGE GREEN DIGITRON DISPLAY BRIGHT/DIM
- ★ AM-PM CLOCK DISPLAY
- ★ 12V DC 230V AC OPERATION
- ★ FACTORY BACKED SPARES & SERVICE, 12 MONTH WARRANTY & THE ALL-IMPORTANT PRE-DELIVERY CHECK BY GAREX. THE MAIN SERVICE & SALES AGENTS.

£299 INC. VAT Delivered

**EXCITING NEW RANGE
 OF SCANNERS AVAILABLE
 SOON INCLUDING THE SX-400**
 s.a.e. for details

WOOD & DOUGLAS

HAVE YOU an IC4E?

Would you like 10W output?
 Then you need our
NEW 70LIN10 UHF Linear



This module is based on our popular 70LIN3/10E pcb which incorporates not only a well designed linear amplifier stage but also a temperature compensated bias network and full r.f. changeover facility. The pin diode circuitry allows a straight through path during receive periods or when the power supply is disconnected making the unit failsafe to accidental damage.

If you wish to use it for SSB transmissions the internal 'hang-time' will be advantageous as will the hard switching capability. Just apply 1.5W of drive for 10W output or 1W for typically 7W output!

The board is available as a pcb kit or assembled tested module without external hardware although boxes and heatsinks are available if desired.

INTRODUCTORY PRICE Kit: £32.50 Assembled: £44.25

Have you seen our package offers?

	Kit
1. 500mW TV Transmit	(70FM05T4+TVM1+BPF433) 30.00
2. 500mW TV Transceiver	(As 1 above plus TVUP2+PSI 433) 50.00
3. 10W TV Transmit	(As 1 above plus 70FM10+BDX35) 50.00
4. 10W TV Transceiver	(As 2 above plus 70FM10+BDX35) 70.00
5. 70cms 500mW FM Transceiver	(70T14+70R5+SSR1) 70.00
6. 70cms 10W FM Transceiver	(As 5 above plus 70FM10) 90.00
7. Linear/Pre-amp 10W	(144PA4/S+144LIN10B) 36.00
8. Linear/Pre-amp 25W	(144PA4/S+144LIN25B) 40.00
9. 70cms Synthesised 10W Transceiver	(R5+SY+AX+MOD+SSR+70FM10) 120.00
10. 2M Synthesised 10W Transceiver	(R5+SY+SY2T+SSR+144FM10) 100.00

Delivery of our products is usually from stock but due to the heavy demand we have experienced in past months please allow 28 days maximum. Please include 75p for postage and handling on your total order and an SAE with any written enquiries. Telephone orders are gladly accepted or try one of our many agents such as:

ANNLEY TECHNICAL SERVICES Bristol 632622
AIRCOR Abergavenny 2566
DEWSBURY ELECTRONICS Stourbridge 390063
J. BIRKETT Lincoln 20767

Try a Kit - we know you will enjoy it!



UNIT 13,
 YOUNGS INDUSTRIAL ESTATE
 ALDERMASTON,
 READING RG7 4PQ
 Tel: 07356 5324 Telex: 848702



AMTRONICS (TONBRIDGE) G4 SYZ THE AMATEUR RADIO SPECIALISTS IN KENT

Closed Mondays.
 9-5.30 Tues.-Sat.
 Fridays 6pm.

We are officially Appointed Dealers for the following:
YAESU, FDK, ICOM, AZDEN, KDK, JAYBEAM, DIAMOND, SARGANT, MET, BNOS, DRAE, FORTOP (ATV), DATONG, TONO, AMTRON KITS, WELZ, ADONIS, UNIDEN AMATEUR.
 Comprehensive stocks of above.

Out of stock items can usually be obtained in 48 hours. We will be available at most of the major Amateur Rallies during the forthcoming season.

Send SAE for details or phone your ACCESS or VISA card no. for Fast Mail Order.



INSTANT CREDIT AT VERY COMPETITIVE RATES. FOR THAT NEW RIG CAN BE AVAILABLE TO YOU. ASK FOR DETAILS WHEN YOU CALL OR WRITE FOR A QUOTE STOCK ITEMS 24 HOUR DELIVERY



8 TOLLGATE BUILDINGS, HADLOW RD., TONBRIDGE. TEL: (0732) 361850

RECHARGEABLE BATTERIES AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME
 FULL RANGE AVAILABLE
 SEND SAE FOR LISTS

£1.45 for booklet "Nickel Cadmium Power"

- TRADE PRICES FOR SCHOOLS & COLLEGES ●

SANDWELL PLANT LTD

656 Chester Road, Erdington,
 Birmingham B23 5TE
 021-373 9487 After Hours Hitchin (0462) 733254
 Litchfield 57977

MET

ANTENNAS

High quality British Yagis to N.B.S.

GAIN OPTIMISED FOR MAXIMUM PERFORMANCE


Special Offer from MET

★ COMPLETE 2 metre E.M.E. PACKAGE ★

Join the growing E.M.E. stations. Just plug in your rig and Kilowatt amplifier and work the real DX!
OFFER INCLUDES ★ 8 144 19 Yagis Gain 23 dBd.
★ Full stacking frame Kit. ★ Power dividers and cable harness. ★ Elevation and azimuth rotators.
★ 60ft crank up tower ★ 100m LDF4/50 heliex (N plugs extra). ★ FREE MET Beacon map.

Vertical Non Metallic Mounting Kit available
Access those distant repeaters.

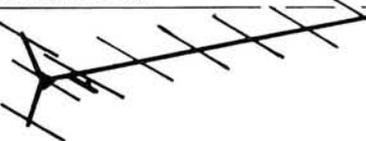SEND TODAY 1-4-84! Offer limited to one per person. ONLY £2813.47 including VAT.
Post & pack £200 extra. Please allow 366 days for delivery.



★ MATERIALS AND CONSTRUCTION

High strength 5mm elements from HE30 aluminium and a 19mm boom combine for low windage and long life. We use 19mm bracing struts on the 14 and 19 element 2M Yagis whilst aluminium fittings minimise any dissimilar materials problem.

★ 'N' SOCKET TERMINATION

Low loss 'N' sockets are used on all our antennas for an inherently weatherproof termination. Plug protection is provided by the silicon grease and universal cable boot we supply.

★ EASY ASSEMBLY

All elements are numbered and colour coded for fast assembly so you won't need a tape measure.

★ TILTING MAST CLAMP (included)

Not just any mast clamp! Ours allows the elevation of all our Yagis by up to 20° on a maximum of 2" mast. Horizontal, vertical, slant and in the case of crossed Yagis, X configurations are possible. The benefit to satellite users is obvious, but if you live in a low obstructed site, tilting your antenna can bring a vast improvement in signals. Clamp available separately - see accessories.

★ USER ADJUSTABLE MATCHING

All antennas are impedance matched using a gamma match with a PTFE dielectric for low loss. Both the tap point on the driven element and the coaxial capacitor are adjustable for minimum VSWR and better than 1 KW power handling.

★ PROMPT SPARES SERVICE

A comprehensive range of spares for our products are readily available from MET and our stockists.

★ FREE BEACON MAP

A wall map of the European 2M or 70CMS beacons is given free with each antenna supplied. Available separately.

Callers welcome by prior appointment - PLEASE

Please allow 14 days for delivery

Code	Model	Length	Gain	Price (inc. VAT)
70 cms				
432/19T	19 Ele	2.2 m	14.2 dBd	£33.90
432/17X	17 Ele crossed	2.2 m	13.4 dBd	£46.83
432/17T	17 Ele long	2.9 m	15 dBd	£37.33
2 M				
144/7T	7 Ele	1.6 m	10 dBd	£19.99
144/8T	8 Ele long	2.45 m	11 dBd	£31.26
144/14T	14 Ele	4.5 m	13 dBd	£44.49
144/19T	19 Ele	6.57 m	14.2 dBd	£53.22
144/6X	6 Ele crossed	2.5 m	10.2 dBd	£37.86
U.K. P&P on all above is £2.95				
4M				
70/3	3 Ele	1.7 m	7.1 dBd	£28.69
70/5	5 Ele	3.45 m	9.2 dBd	£43.56
U.K. P&P on above is £5.49				
144/GP	2 m Ground Plane			£14.41 + P&P £1.30
ALL antennas include Beacon map and tilting clamp				

★ MET ACCESSORIES

Tilting mast-head clamp. £2.25 inc VAT + 50p P&P
N-Plug (UR67 or RG213) £2.65 inc VAT + 20p P&P
Beacon Maps 70CMS or 2M. £0.50 inc VAT + 20p P&P

NEW

NON-METALLIC MAST

Exclusive from MET

Polyester reinforced 1½" diameter. 1.5 metres complete with fixing clamp.
RPM 1.5 £17.25 inc VAT + £1.95 P&P
3 metres complete with joiner and epoxy resin.
RPM3 £34.50 inc VAT + £2.25 P&P

METALFAYRE

Kingsdown Road, St. Margarets-at-Cliffe, Dover, Kent CT15 6AZ

Telephone: 0304 853021

Telex: 965644 LCL DOV

(Enquiries from Dealers and Overseas Distributors welcome)



J. BIRKETT 25 The Strait, Lincoln, LN2 1JF. Phone 20767
SUB-MINIATURE MULLARD GERMANIUM TRANSISTORS OC57, OC58, OC59 all 20p ea.
FURTHER SUPPLY OF EX-GPO MULTI-METERS 20K Per Volt, Movements OK @ £3 each, 4 for £10 Plus £1 for post and packing.
WIRE ENDED R.F. CHOKES, 2.5MH 100mA @ 50p.
V-MOS POWER TRANSISTORS VN10KM @ 50p, VN90AA @ 80p.
50 ASSORTED BC107-8-9 TRANSISTORS untested for 80p.
MINIATURE MICRO-SWITCHES WITH LEVER Ex-Equipment 10 for 75p.
20 ASSORTED TANTALUM CAPACITORS for 85p.
FETS. Like 2N3819, J304 @ 6 for £1, J230 @ 25p each.
MORSE OSCILLATOR KITS with instructions @ £1.95.
144MHz WAVEMETER KIT as in P.W. Oct. 1983 @ £4.65.
NUT FIXING FEED-THRU 3000V RMS insulation @ 6 for 50p.
50 ASSORTED COIL FORMERS Ceramic, Phenolic etc. for £3.65.
20 UNMARKED GOOD 2.5 WATT ZENERS, each Diode identified for £1.15.
CRYSTALS, 10K Type, 7010, 7070, 8000, 8000769, 801882, 803538, 803625, 806118, 10166KHz All 50p each, 10XAJ Type 7005, 701287, 7020, 7025, 7040, 7050, 7080, 7085, 7090KHz @ 80p each.
EX-SPARES FOR RADIO TELEPHONES Pre-Set Butterfly Variables, 25x25pf @ 50p.
20 ASSORTED COLOUR CODED R.F. CHOKES Wire ended for 50p.
50 ASSORTED STAND-OFF INSULATORS @ 45p, METAL SPACERS assort-ed 50 for 35p.
GOLD PLATED NUT FIXING 1" CERAMIC COIL FORMERS with core @ 20p.
FERRITE BEADS FX1115 @ 15p doz, 1" Long Type 6 for 10p.
RF POWER TRANSISTORS 2N5590 @ £4.95, 5878BLY @ £3, BLY55 @ £2.50, BLY90 @ £7.50, BLY97 @ £3, BFR64 @ £4.
BARCLAY AND ACCESS CARDS ACCEPTED. Post and Packing 50p under £5. Goods normally by return.



Northampton
Communications

Top Band Base/Mobile Transceiver
for only £199.00 inc. VAT! + carriage.

HOW?

With the new **LENCOM LC160**

Features ■ Solid state ■ Rugged PA ■ 30W PEP ■ Full RF drive control ■ SSB, AM, CW ■ Audio filter ■ Visual signal indicator
■ A compact 12" x 6½" x 3½".

UK SOLE DISTRIBUTOR (Spec Sheet Available)

Northampton Communications Limited
Communications House

76 Earl Street, Northampton NN1 3AX
Telephone: (0604) 33936 or 38202



COMMUNICATION CENTRE OF THE NORTH

The largest range of communications equipment available in the North. Full range of receivers, transceivers, antennas, power supplies, meters. Ali tubing - wall brackets etc.

We are the original amateur radio suppliers in the North West with 20 years experience in all types of equipment.

We are the only official TRIO stockists in the North West. Full range of equipment on display. Guaranteed after sales service.

RECEIVERS

TRIO R600 Solid State Receiver	£263.00
TRIO R2000 Solid State Receiver	£421.00
JRC NRD515 Receiver	£965.00
YAESU FRG7700 Receiver	£369.00
CD600A Airband Receiver	£99.00
Wide Band Scanning Receiver AR2001, 25-550 MHz	£325.00
R532 Airband Receiver	£159.40

Please send SAE for full information and up-to-date prices as these fluctuate to change in sterling rates. For the caller a wide range of Aluminium Tubing, Clamps, etc. at competitive prices, i.e. 12" x 2" Ali Tubing £9.00.

Part Exchanges welcome. Second hand lists daily.

Send S.A.E. for details of any equipment.

HP terms. Access/Barclaycard facilities.

Open 6 days a week. 24 Hour Mail Order Service.

Phone 0942-676790.

STEPHENS JAMES LTD.
47 WARRINGTON ROAD,
LEIGH, LANCS. WN7 3EA.

**NEW! SBLA 144e
Masthead 144 MHz Preamplifier**



muTek limited

SBLA 144e

- ☆ 250W pep through-power handling
- ☆ 1dB typical noise figure
- ☆ variable gain
- ☆ unique balanced pair of BF981's for excellent dynamic performance
- ☆ superb filtering (of course!)
- ☆ rf or hard switching facilities
- ☆ £79.90 + 2.50 p&p inc. vat

Want to know more? Then please ring or write for details.

If in stock, items usually delivered within seven days.

muTek limited the rf technology company



Dept PW, Bradworthy Holsworthy Devon EX22 7TU.
Telephone: 0409 24-543

**ALL
VALVES
& TRANSISTORS**

Call or phone for a
most courteous quotation
01-749 3934

We are one of the largest
stockists of valves etc. in the U.K.

Open Monday to Friday 9-1 pm, 2.00-5.30 pm.

TRADE & EXPORT 01-743 0899

Delivery by return of post

COLOMOR ELECTRONICS LTD. (01-907 3530 LONDON)
170 GOLDHAWK ROAD, LONDON W12

**38ft LATTICE MASTS
DOUBLE SECTION TELESCOPIC FOLDOVER**

£195 Ex works inc. VAT
NO EXTRAS

Complete, Base, winch, cables etc.
Delivery Service Available



For Details - S.a.e. or Phone

PEMBROKESHIRE COMMUNICATIONS

Panteg, Ambleston, Haverfordwest, Dyfed.

Tel. 0437-67820

Lombard Tricity Finance Available

TAPE RECORDERS M.O.D./E.M.I. 240v two chan, 2 speeds 7 1/2/15 takes up to 8" dia spools, in metal table case approx size 21x18x15" about 45kg, these have 3 & 600 ohm O/P with int. monitor speaker & level meter, have separate Rec & Playback amps for each chan plus mon amp, supplied with copy of handbook. **£65.** Also few only Ferrograph 2 chan units mounted in small 19" racks with amps. **£85. ARMY C.12. HF** Tx/Rx 1.6 to 10Mc/s in two bands AM/CW uses 13 min valves reqs ext P.U. set wired for 12v with book good cond. **£75. POWER UNIT** 240v, O/P stab 150v at 100 Ma DC & 6.3v AC at 3 amps limited adjustment, size 11x6x5" tested with circ. **£11.50. CAR C.B.** Aerials for 27/27.5Mc/s with flex aerial element & removable base loading coil with 11ft of RG58 & plug, approx 15" high, new. **£4.50, spare Ae & Coil. £1.50. MORSE KEYS** miniature type for use with A510 new. **£3.50. ADVANCE FREQ DIVIDERS** self-contained unit divides by 100 up to 40 Mc/s for use with old digital counters good cond. **£25. F.M. TUNER HEAD** 88/108 Mc/s 10.7 out reqs 12v DC makes converter when used with HF Rx new. **£4.75. NAVY H.F.** Tx 1.6 to 16 Mc/s 50 watts, in soiled condition, sold for breakdown, less valves, contains good selection of parts for making ATU. **£45. ARMY AERIAL KITS** comprise 30ft 1" dia mast 10 section plus two 16ft whip aerials with guys, adaptors, stakes, carrying bag, can be used as 30ft mast or 46ft ground plane aerial good cond. **£45. ARMY RADIO** No. 31 old manpack set covers 40/48Mc/s in 200Kc steps TX/RX F.M. reqs ext dry batts with book & battery box. **£24.50. ROTARY CONV** I/P 24v DC O/P 230v AC 50c 100 watts sine wave about 10 amps I/P for full O/P. **£27** or in case **£45. ARMY RECT** No. 7 110/200/250v 50c I/P or 12v DC gives 80-0-80v DC teleprinter magnet supply can also be used to give 240v AC at 40 watts from 12v DC I/P in case size 7x9x7" with circ. **£8.50. BELLS** general purpose 24v DC 6" dia red fire bells new. **£11.50. SOLENOIDS** for use on 12v DC approx size 2 1/2 x 1 1/2" plunger 3/8" dia 18mm stroke coil 10 watt cont new. **£3.80. R.T.T.Y. TERMINAL UNITS** Redifon CSF units for use with Rxs with IFs of 445/470Kc full spec on list. **£65. ARMY T.S.** Deviation No. 2 equiv to Marconi TF943 cal range 2.5 to 100Mc/s useable to 250Mc/s, three ranges 75/25/5Kc deviation, meter indication, in transit case with book for 240v. **£55. RADIAC SIMULATORS** training type Gieger Counter, hand held unit with meter read out in Rongtens, responds to RF signal on 40.68 Mc/s uses xtal controlled superhet Rx, reqs HP7 & PP3 batts: good basis for field strength meter. **£13.50.**

Above prices include carr/postage & V.A.T.

Allow 14 days for delivery, goods ex equipment unless stated new.

S.A.E. with enquiry or 2x16p stamps for List 33.

A. H. SUPPLIES

122, Handsworth Rd., SHEFFIELD S9 4AE

Tel. 444278 (0742)

POOLE LOGIC 49, KINGSTON ROAD, POOLE, DORSET
TEL. POOLE (0202) 683093

POWER SUPPLIES PRICE BRAKE

BREMI 10 AMP £49.90 + £2 p&p
BREMI 5 AMP £19.00 + £1 p&p
BREMI 3 AMP £14.00 + £1 p&p

ALL WITH CURRENT FOLD BACK AND OVERVOLTS PROTECTION
Please allow 14 days for delivery

ICOM H100 Super Low Loss RSGB PUBLICATIONS
TRIO 50Ω coaxial cable
YAESU 80p per metre (post 5p/m)
PRICE (10% off 50m - 20% off 100M) **TONNA AERIALS**

BARCLAYCARD
VISA
Buy it with Access
HAMCARD

ANTENNES TONNA (F9FT)

50MHz
5 element £34.30(a)
144MHz
4 element £14.95(a)
9 element fixed £17.71(a)
9 element portable £20.00(a)
9 element crossed† £32.43(a)
13 element portable† £31.05(a)
NEW 17 element fixed £37.68(a)
435MHz
19 element £20.70(a)
19 element crossed† £34.27(a)
21 element 432MHz £29.67(a)
21 element ATV £29.67(a)
144/435MHz
Oscar Special £34.27(a)
9 & 19 element †Denotes 50Ω ONLY - all others 50Ω or 75Ω impedance

YOUR NUMBER ONE CHOICE
1250MHz OR 1296MHz
23 element† £25.90(b)
4 x 23 ele antennas - power splitter - stacking frame £140.00(a)
Telescopic Portable Masts
4 x 1m £18.68(a) 3 x 2m £21.85(a)
4 x 2m £33.20(a)
ANDREW HELIAX LDF4-50 COAXIAL CABLE
Attenuation per 100ft. 144MHz-0.8dB
435MHz-1.6dB. 1296MHz-2.9dB
£3.40 per metre (a). 'N' Type connectors for LDF4-50 male or female **£12.00.**
MICROWAVE MODULES - ROTATORS - COAXIAL CABLES ETC.
POWER SPLITTERS AVAILABLE FOR 2 OR 4 ANTENNAS

PLEASE ADD CARRIAGE AS SHOWN (a) £4.00. (b) £1.95. ALL PRICES INCLUDE VAT AT 15%
Terms: Cash with order, ACCESS - VISA - telephone your card number.
FOR FULL SPECIFICATION OF OUR RANGE SEND 30p FOR CATALOGUE
Callers welcome, but by telephone appointment only please. Goods by return.

RANDAM ELECTRONICS (P)
12 Conduit Road, Abingdon, Oxon OX14 1DB. Tel: (0235) 23080 (24 hours)

B. BAMBER ELECTRONICS

Rohde & Schwarz Enograph Type BN18531 £60
 Rohde & Schwarz Sweep Signal Generator Type BN4242/2 50KHz to 12MHz £85
 Rohde & Schwarz U.H.F. Signal Generator Type BN41026 1000 to 1900MHz £125
 Rohde & Schwarz Group Delay Measuring Equipment Indicator £50
 Rohde & Schwarz Group Delay Measuring Equipment Mod./Demod. £50
 Rohde & Schwarz Power Signal Generator Type BN4105 30KHz to 300MHz £125
 Rohde & Schwarz U.H.F. Millivolt Meter Type BN1091 20mV to 10V £50
 Airmec Modulation Meter Type 210 3 to 300MHz £95
 Hewlett Packard S.H.F. Signal Generator Model 618B 3.8 to 7.6GHz £120
 Hewlett Packard Square Wave Generator Model 211A £60
 Pye 12 volt Power Unit Type AC15 £25
 Wandel Goltermann Carrier Frequency Level Meter Type TFPM76 £60
 Rohde & Schwarz Video Skop Type BN4241 £250
 Schomental Frequency Meter Type FD1 30 to 900MHz £50
 Tektronix Delay Cable Type 113 £50
 Bruel & Kjoer Vibration Meter Type 2502 £50
 Advance Pulse Generator Type PG54 £40
 Systron Donner L.F. Spectrum Analyzer Model 805 200Hz to 1.6MHz £550
 Ministry Oscilloscope Type CT436 Dual Beam D.C. to 6MHz £85
 Marconi Signal Generator Type TF995A/3/S (CT402) £95
 Marconi 100 Watt 7db Attenuator Type TMS280 150 to 185MHz £40
 Pye Aerial Tuner Unit Type ATU4 2 to 9MHz Pre set £15
 A.I.M. Electronics Pulse Generator with Clock Generator £65
 Marconi V.H.F. Signal Generator Type TF1064B/5M £125
 Marconi Tx & Rx Output Test Set Type TF1065 £85
 Marconi 1/2 Universal Bridge Type TF1313 £220
 Tektronix L-C Meter Type 130 £65
 Heathkit Harmonic Distortion Meter Type 1M-12U £20
 Rohde & Schwarz Polyskop 11 Type BN425/50 £350
 A.E.W. Process Cycling Oven £600
 Twin Clothes Lockers Nests of 2 with keys £20
 Loured Lin Bin Panels 4'6" x 4'6" £20
 Kodak Roll Film Drying Cabinet with Hangers £150
 Potter Line Printer Type LP3000 £150
 Digital Decwriter 11 Printer with keyboard £100
 Rohde & Schwarz Z-g Diagraph Type BN3562 300 to 2400MHz £85

Marconi V.H.F. Alignment Oscilloscope Type TF1104/1 £150
 Tektronix Sampling Oscilloscope Type 661 with 4S2 plug in £120
 Avo Valve Tester Type CT160 £30
 Advance Oscilloscope Type OS25A DC to 3MHz £120
 Teleguip Oscilloscope Type D43 DC to 10MHz £100
 Teleguip Oscilloscope Type S43 DC to 10MHz £85
 Teleguip Oscilloscope Type S51 £75
 Teleguip Oscilloscope Type S32A DC to 3MHz £65
 Tektronix Rack Mount Oscilloscope RM17 DC to 10MHz £85
 Tektronix Oscilloscope Type 317 DC to 15MHz £120
 Marconi R.C. Oscilloscope Type TF1101 £65
 Airmec Millivolt Meter Type 301A £75
 Advance Audio Generator Type H1 £20
 Tektronix Oscilloscope Type S43A with Type B Plug in £160
 Tektronix Oscilloscope Type S31A with Type H Plug in £160
 Sander Oscillator Type CLC2-4 2 to 4.5GHz £95
 Bruel & Kjoer Microphone Amplifier Type 2604 £50
 Bruel & Kjoer Microphone Amplifier Type 2603 £50
 EMI Oscilloscope Wide Band Amplifier Type 7/1 £25
 Airmec Sweep Signal Generator Type 352 20Hz to 200KHz £45
 Balix Variable Power Unit 0 to 50V @ 2 amp. £40
 BTR Silvertown Anti Static & Conductive Footwear Tester £25
 Dawe True RMS Valve Voltmeter Type 612A £20
 Rohde & Schwarz Power Signal Generator Type BN41001 0.1 to 30MHz £75
 Marconi Distortion Factor Meter Type TF142F £85
 Marconi A.M. Signal Generator Type TF144H/4S £125
 Tektronix Time Mark Generator Type 180A £125
 Marconi F.M. Signal Generator Type TF1066B/1 £280
 Marconi F.M. Signal Generator Type TF1066B/6 £300
 Marconi Carrier Deviation Meter Type TF791D £95
 Airmec Modulation Meter Type 403 £120
 Marconi Universal Bridge Type TF888 £50
 Marconi A.M./F.M. Signal Generator Type TF995A/5 £230
 Marconi R.F. Power Meter Type TF1020A/4 300W 75 ohm £65
 Marconi R.F. Power Meter Type TF1020A/1 100W 50 ohm £65

Surplus & Ex-Equipment		Valves	
A2293	£6.50	EL91	£6.00
DA41	£21.50	EL360	£7.75
DF61	£4.00	EL821	£8.00
DY70	£9.00	EL822	£12.00
E182CC	£9.00	EN91	£1.10
E282F	£19.00	EY81	£1.50
EAC91	£2.50	EY84	£6.50
EBC90	£1.00	GZ34	£1.00
EC88	£1.00	GZ37	£2.00
EC91	£7.00	KT66	£6.50
ECC35	£3.50	KT88	£8.00
ECC85	£1.00	N78	£14.00
ECC88	£1.00	OA2	£1.00
ECC91	£2.00	PL82	£1.00
ECF80	£1.00	QQV03-10	£4.00
ECF82	£1.00	QQV03-20A	£6.00
ECF84	£6.00	QQV06-40A	£15.00
ECL80	£1.00		£18.00
ECL82	£1.00		£4.00
EF39	£1.00	QV04-7	£4.00
EF54	£2.50	QZ06-20	£15.00
EF86	£1.25	R18	£2.50
EF91	£1.25	S11E12	£19.00
EF92	£2.50	U103	£2.40
EF95	£1.00	5B254M	£12.50
EF184	£1.00	5B255M	£12.50
EF732	£1.80	5V4	£2.25
EK90	£1.00	5Y3GT	£1.00
EL34	£2.25	6A5S	£1.50
EL37	£9.00	6AG6G	£2.00
EL71	£2.50	6AG7	£2.00
EL81	£6.75	6AN5	£3.95
EL84	£1.00	6AS6	£1.50
EL85	£4.50	6AS7G	£7.50
EL86	£1.00	6AL5	£1.00
EL90	£1.25	6AU6	£1.00
			£2.16
			£4.20

PYE POCKETPHONE PF1 UHF RECEIVER
 440-470 MHz, Single Channel, int speaker and aerial. Supplied complete with rechargeable battery and service manual. £6 each plus £1 p.p. plus VAT.

BREAKING TEK 545A SCOPES FOR SPARES
 CRT Type T543 P2 £12.00 each.
 Mains Transformers T601 £15.00
 High Voltage Transformer T801 With Valves £25.00. Also Switches, Knobs, Fans, Capacitor & Metalwork

RADIOSONDE RS21 METEOROLOGICAL BALLOON TRANSMITTER
 with Water Activated Battery, contains all weather sensors, fully solid state. £5 each plus £1 p.p. plus VAT.

P & P or Carriage and VAT at 15% on total must be added to all orders.
 Callers very welcome strictly between 9 am-1 pm and 2-5 pm Monday to Friday inc. Barclaycard and Access taken
 Goods in stock delivery by return
 Official orders welcome. PW4

5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE
 PHONE: ELY (0353) 860185

TELECOM

6 NEW ST, BARNSELY
 TEL 0226 5031

ICOM	YAESU/ SOKA	MICROWAVE MODULES	ALSO L.A.R. MODULES
IC720A	FT102	MML30LS	J BEAM
IC45	FT77	MML50S	CUSHCRAFT
IC740	FT790	MML100S	REVCO
IC290H	FT290R	MML100LS	DATONG
IC25E	FT707	MM2001	SUN
IC2E	FRG7700	MMC144/ 28	TONO
IC4E		MMA144V	
R70			

RING US FOR PRICES
 BARCLAYCARD/ ACCESS/ HP FACILITIES

(G8KBQ) AVCOMM LIMITED (G6HKT)

25 Northload Street, Glastonbury, Somerset, BA6 9HB. Tel: 0458 33145

New 45pf + 45pf Split Stator variable capacitor	£1.50
New 300pf wide spaced variable capacitor for 1KW	£15.00
New 45pf - 750pf TX variable capacitor	£12.50
New 4 gang 400pf RX variable capacitor	£2.50
Ex. Equipment 100pf variable capacitor	£1.50
Large 850pf + 850pf Split Stator variable capacitor suitable transmatch, (Ex. Equipment)	£17.50
1 pole 4 way high power ceramic switches for atu	£2.00
680pf & 1200pf 10KV. High power ceramic capacitors	£3.00
EIMAC SK.640 4CX250 HF bases, ex. equipment	£8.00
New Boxed QY4 - 250 Valves	£30.00. Bases £1.75
New Boxed ITT 4CX250B Valves	£17.50. OA2 valves 65p
New SIFAM 21mm dia. instrument Knobs in Black	each 35p
	or per 10 £3.00
27mm high & 32mm high ceramic standoff insulators	35p
1/2" shaft flexible couplers	35p

All prices exclusive VAT, p&p on small items 60p, on larger items extra. NEW March catalogue 30p All items by return.

PROGRESSIVE RADIO 93 DALE STREET LIVERPOOL L2 2JD 051 236 0982

Line Jack Socket, Surface Mounting, £2.65



'Break-in' Adaptor £5.00




Plug only 52p



Socket only 49p



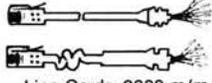Line Cords, 3000 m/m, STRAIGHT — £1.10
 CURLY — £2.45



BLANK COMPUTER PROGRAMME CASSETTES
 IN LIBRARY CASE
 C12 10 for £3.90
 C15 10 for £4.00
 C20 10 for £4.30

CHEQUE OR PO WITH ORDER PLEASE.
 SAE FOR CATALOGUE
 ALL PRICES INCLUSIVE OF VAT AND POSTAGE

MADE-UP COMPUTER LEADS

7 Pin Din To 7 Pin Din	£1.75
7 Pin Din To (2 x 3.5) (1 x 2.5)	£1.65
7 Pin Din To 3 Pin Din + 2.5 Jack	£1.40
7 Pin Din To 5 Pin Din Plug	£1.25
6 Pin Din To 6 Pin Din Plug	£1.25
5 Pin Din Domino To 5 Pin Din Domino	£1.00
Phono Plug To Co-Ax Plug	85p
2 x 3.5 Jack to 2 x 3.5 Jack	85p

SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Dept., Practical Wireless, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St, London, SE1 9LS. (Telephone 01-261 5785).

Software

MORSE TUTOR TAPES for Commodore 64, VIC 20, Dragon, Spectrum, ZX81-16K. Programmed learning from beginner to 30wpm+. Random characters and plain language. Simple to use, full instructions £6. R. WILMOT, Fron, Caernarfon, LL54 7RF. Tel. 0286 881886.

QTH LOCATOR TAPES for Commodore 64, Spectrum, ZX81-16K. Input locator or lat/long, gives distance, beam heading, context score. Worldwide coverage. Easy, accurate. £6. R. WILMOT, Fron, Caernarfon, LL54 7RF. Tel. 0286 881886.

ORIC PROGRAMS: RTTY (requires TU) £7.50, Morse Tutor £4.50, QTH Locator £4.50, also Electron, BBC. SAE details. Cheques to: VOMEK SOFTWARE, T. Tugwell, 11 The Dell, Stevenage, Herts.

RAE MATHS TUTOR tapes for Commodore 64, Spectrum, ZX81-16K. Comprehensively tests and gives practice in all RAE calculations. Don't let maths make you fail. £6. R. WILMOT, Fron, Caernarfon, LL54 7RF. Tel. 0286 881886.

48K SPECTRUM SOFTWARE, Q.R.A. Distance Bearing Log, Contest Score, Graphic Maps £4.95. Callsign Log with Search and List £4.95. Morse Tutor with dummy B.T. test £4.95 any two £7.95 all three £12.00. ALAN PARROTT, 72 Godstone Road, Kenley, Surrey CR2 5AA.

Veteran & Vintage

VINTAGE RADIO'S repaired/restored. Over 200 radios stocked. 1922-1960. RADIO VINTAGE, 250 Seabrook Road, Seabrook, Hythe, Kent CT21 5RQ. Phone anytime (0303) 30693.

EARLY WIRELESS. Always required: Crystal sets, Piptop valves, 1920s period wirelesses, bought, sold, exchanged. Stand 31/2, 288 Westbourne Grove, Portobello Market, London, W11 (Saturdays). Tel. 01-363 7494 (evenings).

Receivers and Components

RADIO CANADA

RADIO PEKING, RADIO AUSTRALIA, VOICE OF AMERICA

A Vega 206 (6xSV/MW/LW) pulls these and dozens more. £23.45. Year's guarantee. Return despatch. Corrigan-Radiowatch, Building 109, Prestwick Airport, KA9 2RT.



BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. FORRESTERS (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

VHF CONVERTERS. 140-150MHz, 118-136MHz, 146-174MHz. All mechanically tuned, 10-7MHz IF output. Mosfet RF stage. High sensitivity. £9.75 each. SAE data, lists: H. COCKS, Cripps Corner, Robertsbridge, Sussex. Tel. 058083 317.

CRYSTALS Made to order for any purpose and large stocks of standard frequencies for computers, modems, etc. Amateur CW (QRP) freqs £4.00 and CB conversion crystals at £4.50. PROGRAMMABLE OSCILLATORS (PXO) for baud rates, MPU, and freq markers £12.50.

FILTERS Crystal, monolithic, mechanical and ceramic for all standard IFs. Special 10.695MHz for big improvement to most CB rigs at £4.50 each.

S.A.E. FOR LISTS. PRICES INCLUDE VAT AND POST

P. R. GOLLEDGE ELECTRONICS
G3EDW, Merriott, Somerset, TA16 5NS
Tel. 0460 73718

NOTICE TO READERS

Whilst prices of goods shown in advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

COMPONENTS & EQUIPMENT - 1984 Catalogue 70p + 20p P&P. Callers: 18 Victoria Road, Tamworth. 369 Alumrock Road, Birmingham. 103 Coventry Street, Kidderminster. Express Mail Order Service. LIGHTNING ELECTRONICS, PO Box 8, Tamworth, Staffs.

TELEVISION VALVES Ecc82-EF85/183/184-DY86/802-PCF80/802-PCL82/84/85/86, PC86/88/92/97-PY88/800-PL36/504. All 35p Each, P&P 50p. ELECTRONIC MAILORDER, Ramsbottom, Lancashire, BL0 9AG.

Security

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DISPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C-TEC SECURITY, Dept PW
60 Market St, Wigan WN1 1HX
Telephone (0942) 42444



Aerials

50M (165ft) AERIAL WIRE. Strong PVC covered copper - £4.80 inc. Post. W. H. WESTLAKE, Clawton, Holsworthy, Devon.

G2VF D.I.Y. H.F. long and medium wave frame antennas. S.a.e. for details. F. RYLANDS, 39 Parkside Avenue, Millbrook, Southampton.

G2DYM AERIALS KILL THAT INTERFERENCE ANTI-TV ANTI-QRN

Data sheets, Large 23p SAE.
Aerial Guide 75p.

Callers for Appointment Tel. 03986-215
G2DYM, Uplowman, Tiverton, Devon.

AERIAL WIRE. Hard drawn Copper 140ft 14swg £6.90, 50 metres 16 swg £5.90 including postage. S. M. TATHAM, 1 Orchard Way, Fontwell, Arundel, W. Sussex.

AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20db, Tunable over the complete UHF TV band. PRICE £8.70.
B11-VHF/FM RADIO, gain about 14db, when on the off position connects the aerial direct to the radio. £7.70.
All Boosters we make work off a PP3/006p/6F22 type battery or 8v to 18v DC. P&P 30p PER ORDER.

ELECTRONIC MAILORDER, 62 Bridge Street, Ramsbottom, Lancs BL0 9AG. Tel (070682) 3036
Access/Visa Cards Welcome SAE Leaflets

Educational

COURSE FOR CITY & GUILDS, Radio Amateurs Examination. Pass this important examination and obtain your licence, with an RRC Home Study Course. For details of this and other courses (GCE, Career and professional examinations, etc.) write or phone: THE RAPID RESULTS COLLEGE, Dept JX7, Tuition House, London, SW19 4DS. Tel. 01-947 7272 (9am-5pm) or use our 24hr Recordcall Service: 01-946 1102 quoting Dept JX7.

Wanted

WANTED TO BUY T1154 and/or R1155 (in original condition and working) if possible. M. A. O'KEEFE, 1 Julie Street, Blackburn Nth, 3130 Vic, Australia.

Books and Publications

RADIO & RTTY BOOKS

CONFIDENTIAL FREQUENCY LIST lists 10,000 CW, aero, coastal, fax, etc., frequencies £8.25 + 60p P&P.
GUIDE TO RTTY FREQUENCIES lists 4500 commercial aero, UN, coastal, etc., frequencies £7.35 + 50p P&P.
WORLD PRESS SERVICES FREQUENCIES news RTTY services listing GMT, and country plus more £4.55 + 50p P&P. 2+ books P&P free.

INTERPRODUCT LTD.

PWS, Stanley, Perth PH1 4QQ. Tel: 073882-575

HANDY GUIDE TO EUROPEAN BROADCASTS for home listener or DX'er: new DIAL-SEARCH 1984. Now 48 pages: lists & maps Europe & UK (MW, LW); SW selection; signature tunes etc. £2.75 (abroad 15 IRCs) including postage. WILCOX (PW2), 9 Thurrock Close, Eastbourne BN20 9NF.

EARN CASH NOW

With New Published Manuals

Domestic appliance reconditioning and repair. Two volumes only £12.50 post free. Also, a professional guide to sewing machine repair for profit. Two volumes only £8.50 post free. Both with full repair and fault guides. Leaflets available.

MARCHANT (Dept PWT),
30 Chester Road East,
Shotton, Clwyd, N. Wales.

Courses

NEW!! Scientifically prepared courses to get you through the R.A.E. examinations. 01-346 8597 for free booklets.

CONQUER THE CHIP . . . Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. C1, Reading, Berks RG1 1BR.

Service Sheets

30,000 SERVICE SHEETS IN STOCK
COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £3.00. Tuners £3.00. Tape Recorders, Record Players £3.00. Transistors £3.00. Car Radio £3.00 + SAE. Stereograms & Music Centres £3.00. Radiograms £3.00. Also Colour Available. State if circuit will do if sheets are not in stock. Circuits £3.00 colour. All TV Sheets are full length 24 x 12 net in Bits & Pieces. All other Data full length. All sheets £3.00 except colour. SAE please. Old Valve Radios £3.00 + SAE 9 x 3. Ensure payment with order.

C. CARANNA,
71 Beaufort Park, London NW11 6BX. (Mail Order).

VINTAGE RADIO, T/V and Amplifier Service Sheets and Manuals, 1914-1960. S.A.E. or telephone for quotation. VINTAGE WIRELESS CP., Cossham Street, Mangotsfield, Bristol BS17 3EN. Tel. 0272 565472.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc., £1.50 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

TECHNICAL INFO SERVICES

76 Church St - Larkhall - Lanarks

FULL SIZE SERVICE SHEETS

£2 and I.s.a.e.

CTVs/MusC £3 & I.s.a.e.

Worlds largest collection service manuals 30's - date from £4.50-£35 each

Repair data/circuits almost any named TV/VCR £9.50

S.a.e. brings any quotation/
FREE 50p mag. inc. service sheet/
Pricelists unique elect. publications

**FOR FAST QUOTES
RING 0698 883334**

For Sale

COMMUNICATIONS SPECIALIST. Established 1952. G3EKX. Receivers, Transceivers, Scanners, Rotators, Beams, Co-Ax. Buying/Selling. S.S.B. PRODUCTS, Cornwall. 0872 862575.

YAESU FRG 7 RECEIVER. Excellent condition, £135 including delivery. 061-795 1765 evenings.

28 COPIES Practical Wireless, 1950s to 1962. Offers. Phone 09277-63703 after 6pm.

YAESU FT101ZD/AM FC 902 Tunnin Unit SP 902 ext. speaker. Yaesu Base Mike £550. Tel. Derby 675132.

AMATEUR EQUIPMENT BOUGHT sold exchanged. Telephone 040-24-55733; or send SAE for current list. G3RCQ, 65 Cecil Avenue, Hornchurch, Essex.

CALL SIGN BADGES professionally engraved, by return of post. £1.50 cash with order. (State name and callsign.) AYLMEER-KELLY (P), 2 Pickwick Road, Corsham, Wilts. SN12 9BJ.

PART-EXCHANGE FOR FT301D, FRG7, EC10-MK-2,640, AR88D, CR100, FRV7700, RS2000, Scanner, FC301, DX200, Century-21D, HA600A, Oscilloscopes, etc. In stock! S.S.B. PRODUCTS. 0872 862575.

Situations Vacant

TRAINEE ASSISTANT FILM RECORDISTS

Would you like to specialise in sound with the BBC TV's Film Department in West London?

Trainee Assistant Film Recordists work in Sound Transfer and Dubbing areas. Prospects exist for moving on to location recording work after several years.

Applicants, who should be at least 18 years of age, must possess a minimum of 'O' level standard of education or equivalent, including Physics and Mathematics, together with a knowledge of electronics. They must be able to demonstrate a practical interest in sound.

Normal hearing and colour vision are essential and applicants must hold a current driving licence or be prepared to obtain one within a reasonable period.

Successful applicants will start their three year training period in September 1984 at a salary of £5,809 (currently under review). An additional allowance is paid for shift work. Relocation expenses considered.

Contact us immediately for application form (quote ref. 1143/PW and enclose s.a.e.): **BBC Appointments, London W1A 1AA. Tel. 01-927 5799.**

Preliminary interviews are expected to be held in June.

We are an Equal Opportunities employer

Miscellaneous

MORSE CODE PREPARATION

RECEIVING

Cassette A: 1-12 wpm for amateur radio examination. Cassette B: 12-25 wpm for professional examination preparation. Each cassette is type C30.

Price of each cassette (including booklets) **£4.75.**

SENDING

Morse key with separate battery (PP3) - driven solid-state oscillator and sound transducer produces clear tone for sending practice; optional light (solid state) signal included. Price of key with electronic unit **£9.95.**

Price includes postage etc. Europe only.

MH ELECTRONICS (Dept PW)

12 Longshore Way, Milton,
Portsmouth PO4 8LS.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC. Faced steel. Vast range. Competitive prices start at a low £1.50. Punching facilities at very competitive prices. Suppliers only to Industry and the Trade. **BAZELLI**, (Dept. No. 25), St. Wilfrid's Foundry Lane, Halton, Lancaster LA2 6LT.

QSL CARDS, printed to your own design on white or coloured gloss card. Send for samples. **THE NUTLEY PRESS**, 21 Holmehorpe Avenue, Redhill, Surrey RH1 2NB.

WAVEGUIDE, FLANGES & DISHES. All standard sizes & alloys (new material only) from stock. Special sizes to order. Call **EARTH STATIONS**, 01-228 7876. 22 Howie Street, London SW11 4AR.

LOSING DX?

RARE DX UNDER QRM? DIG it OUT with a

Tunable Audio Notch Filter, between RX and speaker, **BOOST** your DX/QRM ratio, 40dB notch, hear **WEAK DX** **£16.40**

10-150KHz Receiver **£21.20**

ANTENNA FAULT? Measure resonance and radiation resistance with an Antenna Noise Bridge, **MORE DX** **£19.60**

Each fun-to-build kit includes all parts, printed circuit, case, by-return postage etc, list of other kits.

CAMBRIDGE KITS

45 (PD) Old School Lane, Milton, Cambridge.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

HIGH CLASS QSL cards fast delivery. S.A.E. for samples and prices to **J.S. COATES**, 57 Worrall Street, Morley, Leeds LS27 0PJ.

THE SCIENTIFIC WIRE COMPANY

811 Forest Road, London E17. Telephone 01-531 1568

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30 9.09 5.20 2.93 1.97

TINNED COPPER WIRE

14 to 30 3.97 2.41 1.39 0.94

Fluxcore

Solder 5.90 3.25 1.82 0.94

Prices include P&P VAT. Orders under £2 add 20p.

SAE for list of copper and resistance wire.

Dealer enquiries welcome.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for

insertions I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME

ADDRESS

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Dept.,

PRACTICAL WIRELESS

Classified Advertisement Dept., Rm 2612

King's Reach Tower, Stamford Street,

London SE1 9LS Telephone 01-261 5785

Rate 36p per word, minimum 12 words.

Box No. 60p extra.

4/84

1984

Northern Amateur Radio Societies Association

The Association is holding its 22nd Annual Radio/Electronics Exhibition at Pontins Holiday Village, Ainsdale, Southport on Saturday 7th April and Sunday 8th April 1984 opening at 11.00am each day. It will include inter club quiz, construction contest, grand raffle, R.S.G.B. book stall, amateur computers, N.A.R.S.A. stands and trophy, a demonstration station and trade stands featuring all types of radio/electronic equipment. Bring and Buy Sale.

Admission will be £1 per day but lots of 20 or more tickets may be booked in advance from Mike Bainbridge G4GSY, 7 Rothbury Close, Bury BL8 2TT at a 20% discount by sending the appropriate cash and s.a.e.

Chalets may be booked direct from Pontins 0704 77165 and range from £11 + V.A.T. (2 persons) to £31 + V.A.T. (6 persons).

Bar and restaurant facilities will be available during the day while the restaurant will be open for breakfasts and from 1700 to 1900 on the Saturday evening. There will be evening entertainment limited by the capacity of the entertainment hall. Children's play areas will be available during the days.

Car parking will be available at a small charge but please follow all instructions of attendants to avoid congestion.

Talk in will be available on S22 or other available simplex channels. Come along and enjoy yourself at this family weekend exhibition and make it a great success.

H.A.C.
SHORT-WAVE KITS
WORLD-WIDE RECEPTION

**NO H.T.
BATTERIES?**

We have an excellent
BATTERY ELIMINATOR KIT

£12.00

for the complete kit
It provides 90V H.T.
and a choice of 3V, 2V
or 1½V L.T.

Also we supply several super
short wave receivers in kit
form.

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C."

SHORT-WAVE PRODUCTS

P.O. Box No. 16, 10 Windmill Lane,
Lewes Road, East Grinstead,
West Sussex RH19 3SZ.

ELECTRO — TECH CO

72 PRIMROSE HILL, HAVERHILL, SUFFOLK CB9 9LS, U.K.

Tel: (0440) 61113 Prop: Seneviratne

TERMS: Cash, Postal Order, Cheque. Postage — 50 pence. Goods over £15 post free — (60p extra for every heavy item). All items brand new and guaranteed. Goods normally sent within 24 hrs. unless out of stock. Orders welcomed from clubs, schools, colleges, etc. **PRICES ARE INCLUSIVE OF A 5% DISCOUNT FOR A LIMITED PERIOD ONLY, so order soon.** No V.A.T. on Export. Catalogue 20p. S.A.E. for free lists. Phone for appointments.

Transistors AC 127 22p BCY 70 20p AC 128 31p BCY 71 20p AC 141 37p BFY 50 25p AC 142 33p BFY 51 22p AC 176 27p BFY 52 25p AD 149 88p BFX 85 27p AD 161 44p BRY 39 47p AF 127 80p NJE 340 55p BC 107 12p TIP 31A 38p BC 108 12p TIP 32A 38p BC 109 12p TIP 41A 45p BC 142 28p TIP 42A 45p BC 143 28p TIP 2955 66p BC 149 10p TIP 3055 55p BC 159 9p ZTX 300 15p BC 182L 9p ZTX 500 15p BC 184L 8p MPF 102 44p BC 212L 11p 35K 88 90p BC 213L 11p 2N 697 23p BC 214L 9p 2N 2222A 22p BC 307 10p 2N 2946 45p BC 327 9p 2N 2905 23p BC 327 15p 2N 2905A 24p BC 337 15p 2N 3053 25p BC 441 37p 2N 3054 60p BC 477 33p 2N 3055 60p BC 478 33p 2N 6027 32p BC 183L 11p 2N 3703 10p BD 115 61p 2N 3705 10p BD 131 39p 2N 3706 10p BD 135 44p 2N 3773 214p BD 136 33p 2N 3819 22p BD 244B 30p 2N 3820 44p BF 259 39p 2N 3904 11p BU 205 176p 2N 5306 11p BU 208 187p 2N 5457 35p Resistors: E24 Carbon film 1W 1p All Preferred Values ½W 2p	Mains Transformers 9-0-9 1Amp 297p. 12-0-12 1Amp 352p. Antex Soldering Irons CS 17 Watt 544p. XS 25 Watt 575p. C 15 Watt 535p. Spare tips 85p. IC Desolder bit XS 270p. ST4 Iron stand with sponge 190p. Hook and finger protector CS, XS 15p. Sponge for ST4 30p. Solder 5 core size 12, 18SWG 400p. Desoldering Pump 525p. Spare nozzle 77p. Switches (More in stock) Sub min toggle DPDT 71p. Min toggle SPST 88p. Min toggle SPDT 85p. Min toggle DPDT 99p. Min toggle Centre off 110p. DPDT. Min slide DPDT 20p. Min push to make 17p. Min push to break 24p. Plugs and Sockets PL 259 44p. Reducer, large or small 15p. BNC plug 110p. BNC socket round hole 110p. BNC socket square hole 130p. 4mm plugs/sockets 22p (banana type). 25mm croc clips 7p Red/Black. 35mm croc clips 9p insulated. Dalo Etch resist pen 95p. Assorted PCB transfers 65p. Ferric chloride crystals ½lb 110p. Verroboard 0.1 Pitch Size 95.25x127mm 95p. Neon mains tester 500m max. 60p.	0.2 LED's Led Red 8p. Led Green 11p. Led Yellow 11p. Clips 4p each. DRP 12 90p. MEL 111 NPN photo darlington, cost 35p each. Chokes High Q Ferrite Cored 2.5 mh 58p. 5 mh 64p. 7.5 mh 64p. 10 mh 65p. 1.5 mh 58p. 5 mh 65p. Trimmer Capacitor compression Type 3-40pf 33p. Type 50-450pf 34p. RG 58 50ohms 25p/yd. DRR2 High gain dual range coil 1, 2, IC receivers, build your own. Cost 190p. Jackson variable capacitors. Type 0 Dual gang 10-365pf 625p. Type 0 Single gang 100-365pf 440p. CB04 Type 10pf 500p. 25pf 540p. 50pf 540p. 100pf 600p. DILECON Variable capacitors, etc. 100pf 400p (other values in stock). Slow motion 6:1 drive 195p. Miniature trimmers. 2-10pf 35p. 2.2-22pf 35p. 5.5-65pf 30p. Ferrite Beads. FX 1115 2p each. ½" type 2p each. Brass spindle extenders 135p. Diodes (more in stock) 1N 4001 4p 1N 4005 6p 1N 4002 5p 1N 4006 7p 1N 4003 5p 1N 4007 7p 1N 4004 6p 1N 4148 3p	Bridge Rectifiers 1 Amp 50v 20p 2 Amp 100v 35p 1 Amp 100v 20p 2 Amp 200v 44p 1 Amp 200v 25p 6 Amp 200v 90p 2 Amp 50v 33p 6 Amp 400v 109p SCR C106D 33p 16 Amp 100v 110p 10 Amp 400v 90p 1 Amp 50v 65p 1 Amp 200v 75p Triacs 2 Amp 400v 80p 8 Amp 600v 110p 4 Amp 400v 82p 10 Amp 400v 140p Capacitors Electrolytic, suitable PCB 16v Radial. 10, 22mf 7p. 47, 100mf 9p. 470mf 13p. 1000mf 31p. 2200mf 41p. 35v Radial. 4.7mf 10p. 10mf 10p. 22mf 12p. 100mf 18p. 220mf 23p. 470mf 33p. 1000mf 50p. 2200mf 82p. 63v Range. 2.2mf 9p. 4.7mf 9p. 10mf 9p. 22mf 10p. 33mf 11p. 47mf 12p. 100mf 20p. 220mf 26p. 470mf 35p. 63v Range Axial. 0.47mf. 1, 2.2, 4.7mf 9p. 10mf 10p. 22mf 17p. 1000mf 85p. 2200mf 169p. 470mf 50v axial 37p. 1000mf 25v axial 30p. 4700mf 63v tag can 263p. Clip for above 10p. Polystyrene Caps. 160v DC 22pf — 3300pf, 9p. 5600pf 11p. 6800pf 12p. Mixed Dielectric. 1000v DC 0.047mf 51p. 0.01mf 46p. 0.1mf 62p.
--	---	---	---

INS 8080A 8 bit microprocessor 244p, TDA 1022 550p, ZN 414 90p, LM 3909 83p, CA 3140 40p. Heat sinks, Aluminium boxes, knobs, insulators, tools, plugs, capacitors etc., listed in our catalogue, and price lists.

ARE YOU TAKING THE RAE?

YOU MUST OBTAIN

THE

RADIO AMATEURS' QUESTION + ANSWER REFERENCE MANUAL

by R.E.G. Petri, T.Eng (CEI)
M.I.ELEC.I.E. G8CCJ

ISBN 0 9509335 0 3
Size A5 (210 × 148mm)

Containing over 300 pages. 21 sections and over 1100 progressive multiple choice questions and answers on the RAE syllabus, some useful computer programs and the City & Guilds examination syllabus.

Available from:

W.P. PUBLICATIONS

11 Wayville Road
Dartford, Kent DA1 1RL

PRICE £5.95 + £1 p&p

By return post subject to availability

INDEX TO ADVERTISERS

A.H. Supplies	82
Allweld Engineering	8
Amateur Electronics U.K.	6, 7, 88
Amateur Radio Exchange	44, 45
Ambit International	15
Amcomm Services	16
Amtronics	80
Ant Products	26
Avcomm	83
Barrie Electronics	71
B. Bamber	83
BBC Appointments	85
Bi-Pak	9
Birkett, J.	81
B.N.O.S.	33
Blackstar	79
British National Radio & Electronics School	71
Butterworths	37
C-Tec Security	84
C.Q. Centre	8, 87
Cambridge Kits	85
Caranna C.	84
Colomor Electronics	82
Corrigan Radiowatch	84
Datong Electronics	67
Dewsbury Electronics	67
Dressler (U.K.) Ltd.	11
Electronic Mail Order	84
Electro-Tech	86
Electrovalue	87
G2DYM Aerials	84
G.T. Technical Services	84
Garex Electronics	80
Golledge Electronics	84
Greatech Electronics	14
Greens Telecom	83
HAC Products	86
I.C.S. Intertext	14
International VHF-FM Guide	26
Inter-Product	84
Lee Electronics	67
Leeds Amateur Radio	79
Lowe Electronics	2, 3
Maplin Supplies	Cover 4
Marchant	84
Metalfayre	81
M.H. Electronics	85
Microwave Modules	10
Mutek	82
Northern Amateur Radio Society	86
Northampton Communications	81
Pembrokeshire Communications	82
Photo Acoustics	25
P.M. Components	12
Poole Logic	82
Power International	26
Radio Component Specialists	88
Radio Shack	Cover 3
Radssoft	87
Random Electronics	82
R.E.G. Petri	86
R.S.T. Valve	10
Sandpiper Communications	87
Sandwell Plant	80
Scarab Systems	10
Scientific Wire Co.	85
Selectronic	71
S.E.M.	12
Spectrum Comms.	88
Stephens-James Ltd.	81
South West Aerials	71
Tandy	13
Thacker, A.H.	14
Thanet Electronics	4, 5, 79
Ward & Co., Reg.	Cover 2
Western Electronics	88
Wood & Douglas	80

ELECTROVALUE

Your SPECIALIST SUPPLIERS for SOLDER TOOLS



From a simple 15 watt model to a precision temperature controlled iron, we stock solder irons to suit all manual requirements together with supporting stocks of bits, de-solder tools, materials, etc.

ANTEX

C.240 - 15W/240V;
CSCN - 15W/240V
CS - 17W/240V
CSBP - 17W/240V + 13A plug
XS - 25W/240V
XSBP - 25W/240V + 13A plug
Replacement bits from 3/32" to 1/2"

De-solder heads, stands, elements and handles.

ERSA

'Sprint' high speed iron: 80/150W, 240V. Heats in 10 seconds!

ORYX

Temperature controlled solder iron TC.82 45W/240V with scale.
Oryx 50 - 50 watt version of above.

Standard types

Oryx 30 - 30W/240V

Viking - 27W/240V

Oryx M.3 - 17 watts, 12 volts.

A wide range of replacement tips available for all models, also tips from 0.8 to 6.4mm dia. and flat tips.

Oryx safety stand.

Oryx de-solder tool.

MINIATURE SOLDER STATION

SOLDER and DE-SOLDER BRAID SOLDER in many grades.

Please mention this publication when contacting Electrovalue.

BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 32 PAGE A-Z LIST
ATTRACTIVE DISCOUNTS-FREE POSTAGE-GOOD SERVICE & DELIVERY

ELECTROVALUE LTD

28 St. Judes Rd.,
Englefield Green, Egham,
Surrey TW20 0HB.

(0784) 33603; Telex 264475.

North - 680 Burnage Lane, Manchester. 061-432 4945.

EV Computing Shop -

700 Burnage Lane, Manchester. 061-431 4866.

ACCESS AND BARCLAYCARD
Phoned Orders
Welcome

5

STAINLESS STEEL AERIALS SANDPIPER COMMUNICATIONS

	2 Meter	Standard	Kit DIY
P&P £2	2 x 5/8 Collinear	20.00	15.00
P&P £4	3 x 5/8 Collinear	30.00	20.00
P&P £2	5 el Yagi	12.00	9.00
P&P £4	10 el Yagi	20.00	15.00
P&P £4	17 el Yagi	32.00	28.00
P&P £4	10 el Crossed Yagi	28.00	24.00
P&P £3	7 el ZL	11.00	8.00
	70cm		
P&P £4	24 el Yagi	24.50	18.00
P&P £4	8 turn Helical (Oscar 10)	33.00	-
	23cm		
P&P £2	25 el Quad Driven Yagi	25.00	18.50
P&P £4	20 Turn Helical	30.00	-

Only a very small selection of Aerials shown - lots more inc. 4 mtr & 6 mtr, and H.F. Beams. Even a Crossed/Circular Quad & Power Splitters all available with Aluminium, Stainless Steel or Fibre Glass booms (aluminium as standard). 15" and 36" Aluminium/Polyester Resin Coated Parabolic Reflectors.

Specials

(S/Steel) HB9CV 70 cms - £5 HB9CV 2 mtrs £6 (Both £10) P&P £1
(S/Steel) Slim Jim 70 cms - £3 2 mtrs £6.50 (Both £9) P&P £1

SAE For Full Lists

40 Trehafod Rd, Trehafod,

Nr Pontypridd, Mid Glam.

Tel: Porth 685515 & Aberdare 870425

All parts sold separately Delivery normally by return

SPECIALS



JUST ARRIVED!

24cms A.T.V. CONVERTOR
(Plugs into domestic T.V.) £29.50

HB9-CV ANTENNA
(2 METRE 2 EL. BEAM) £8.50

AS ABOVE 70cms
(BOTH INC. MOUNTING CLAMP)
£8.50

Extra Special - Slim Jim £7.50 (inc. p+p)

EDDYSTONE RE1 MARINE GEN. COV. RECEIVER - FEW ONLY £450

Delivery normally within 7 days.

MORSE PRACTISE OSCILLATOR
£12.50 (inc. p+p)
(with key £26.50)

MORSE TUTOR TAPE
(INC. SIMULATED TESTS) £6.50

OSCILLATOR - KEY - TAPE
IF BOUGHT ALL TOGETHER
JUST £29.50 inc. p+p

30 FOOT TELESCOPIC MAST
(Not Mail Order) £28.50



See main ad.
on page 8



RECEIVE RTTY MORSE

Complete systems including machine language programs plus our ready-made & boxed terminal unit. Plug in and decode Morse 5-70 W.P.M. and RTTY at 45, 50, 56 and 75 baud. Please state your micro.

SPECTRUM COLOUR GENIE TRS80 VIDEO GENIE
Only £40 Only £40 Only £40

TRANSCIVE RTTY

Various systems from built-it-yourself to the all-made-ready-to-go. All systems include our m/c programs which incorporate many, many excellent features including SPLIT SCREEN, AUTO CW ID., CALLSIGN CAPTURE, 10 BUFFERS, 4TX/RX SPEEDS, etc. etc. Prices from £17.50 to £95. State your micro.

COLOUR GENIE TRS80 VIDEO GENIE
Send SAE for catalogue of these and other amateur radio programs

RADSOFT

8 Leighton Road, Sunderland, SR2 9HQ.

Great News From YAESU!

Thanks to the massive upsurge in 70cm activity in Japan, YAESU have now increased production on these popular and well proven models with the result that we can now offer the following most attractive prices. Now is your opportunity to get on this superb band at less outlay than for 2 metre operation.



FT-730R
10W/1W
FM mobile
Now only
£229

FT-708R
1W/200mw
FM portable

Dual VFO's 10 memories

FT-790R 1W/200mw multimode
All the features of the FT-290R on 70cms
Incredible value at
£249

10 memories
Keyboard entry
A must at only
£179

NOW IN STOCK!

The world famous SHURE 444D dual impedance magnetic desk microphone. Features tailored frequency response for optimum speech intelligibility. This is the mike with the pedigree.

£49-50 Carriage paid



Amateur Electronics UK
504-516 Alum Rock Road - Birmingham 8
Telephone: 021-327 1497 or 021-327 6313
Telex: 334312 PERLEG
Opening hours: 9.30 to 5.30 Tues. to Sat. continuous - CLOSED all day Monday.



BAKER LOUDSPEAKERS	Make	Model	Size	Watts	Ohms	Price
Baker Hi-Fi	Major	12in	30	4/8/16	£16	
Baker Hi-Fi	Superb	12in	30	8/16	£26	
Baker P.A.	Group 45	12in	45	4/8/16	£16	
Baker Hi-Fi	Auditorium	12in	45	8/16	£24	
Baker Hi-Fi	Auditorium	15in	60	8/16	£37	
Baker P.A.	DG75	12in	75	4/8/16	£20	
Baker P.A.	Group 100	12in	100	8/16	£26	
Baker P.A.	Disco 100	12in	100	8/16	£26	
Baker P.A.	Group 100	15in	100	8/16	£35	
Baker P.A.	Disco 100	15in	100	8/16	£35	

Baker Disco. twin turntables, twin speakers, Headphones. Microphone, Slide controls, 150W, £330, 300W, £399 carr. £30

LOW VOLTAGE CAPACITORS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p, 50mF 12V, 15p; 25V 30p; 50V 40p; 1000mF: 25V, 35p; 40V, 50p; 100V £1.20; 1200mF/76V, 80p; 2000mF 63V 25p; 25V, 42p; 40V, 60p; 2000mF/100V, £1.50. 2500mF 50V, 70p; 3000mF 50V, 65p; 3300mF 63V, £1.50; 1500mF 100V, £1.20. 4700mF 40V £1.00; 63V £1.80

HIGH VOLTAGE ELECTROLYTICS

8/450V	45p	15-16/450V	85p	32-32+32/325V	50p
16/450V	45p	32+32/350V	85p	32-32+32/450V	95p
32/350V	75p	32+32/500V	£2	100+100/275V	50p
8+8/500V	£1	50+50/300V	50p	150+200/275V	50p
8+16/450V	75p	32-32+16/350V	85p	125/500V	£2

GEARED TWIN GANGS 365 + 365 + 25 + 25p, £2.00
SLOW MOTION DRIVE 6:1 £1.50 Reverse Vernier 90p
SPINDLE EXTENDERS 85p; **COUPLERS** 65p.
VERNIER DIALS, 0-100, 36mm, £3.00, 50mm, £2.50.
BLANK ALUMINIUM CHASSIS, 6 x 4, £1.75; 8 x 6, £2.20; 10 x 7, £2.75; 12 x 8, £3.20; 14 x 9, £3.60; 16 x 6, £3; 16 x 10, £3.80, All 24in, 18 swg. **ANGLE ALL**, 6 x 2 1/2in, 30p.
ALUMINIUM PANELS, 18 swg, 6 x 4, 55p; 8 x 6, 90p; 14 x 3, 90p; 10 x 7, £1.15; 12 x 8, £1.30; 12 x 5, 90p; 16 x 6, £1.30; 14 x 9, £1.75; 12 x 12, £1.80; 16 x 10, £2.10.
BLACK PLASTIC box with aluminium fascia, 6 1/2 x 3 1/2 x 2 1/2in, £1.50.
ALUMINIUM BOXES WITH LIDS, 3 x 2 x 1, £1; 4 x 2 1/2 x 2, £1.20; 4 x 4 x 1 1/2, £1.20; 6 x 4 x 2, £1.90; 7 x 5 x 3, £2.90; 8 x 6 x 3, £3; 10 x 7 x 3, £3.60; 12 x 5 x 3, £3.60; 12 x 8 x 3, £4.30.

MAINS TRANSFORMERS	Rating	Price	Post
250-0-250V	80mA, 6.3V 3.5A, 6.3V 1A	£7.00	£2
350-0-350V	250mA, 6.3V 6A CT	£14.00	£2
250V	50mA, 6.3V 2A	£4.75	£1
220V	25mA 6V lamp	£3.00	£1
	220V 45mA 6V 2Amp	£4.00	£1

Tapped outputs available

2 amp	3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£6.00	£2
1 amp	6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00	£2
ditto	2 amp	£10.50,	3 amp £12.50, 5 amp £16.00
	5-8-10-16V, 1A	£2.60	£1
	15-0-15V 1A	£4.50	£1
	6V, 1A	£2.00	£1
	6-0-6V, 1A	£3.50	£1
	9V 250ma	£1.50	£1
	9V 3A	£5.00	£1
	9-0-9V 50ma	£1.50	£1
	9-0-9V 1A	£3.50	£1
	10-0-10V 2A	£4.00	£1
	10-30-40V 2A	£5.50	£1
	12V 100ma	£1.50	£1
	12V 750ma	£2.50	£1
	12V 3A	£4.50	£1
	12-0-12V 2A	£5.00	£1

RADIO COMPONENT SPECIALISTS
Dept 2, 337 WHITEHORSE ROAD, CROYDON,
SURREY, U.K. TEL: 01-884 1665
ACCESS Post 65p Minimum. Callers Welcome. VISA
Lists 32p. Same day despatch Closed Wed.
PHONE YOUR ORDER

SPECTRUM COMMUNICATIONS

NEW PRODUCTS

TRANSMIT AMPLIFIERS. 2 metre, 4 metre or 6 metre, linear all mode, 1-5 watt I/P, 10-25 O/P, carrier or DC switched. Types TA 2S/1, TA 4S/1, TA 6S/1. Boxed Kit £22.95, Built £34.95.

TRANSMIT AMPLIFIERS. 2 metre, 4 metre or 6 metre, linear all modes, 0.5 watts I/P, 25 watt O/P, unswitched, suits transmit converters. Types TA2/2, TA4/2, TA6/2. Unboxed Kit £23.65. Unboxed built £32.65.

RECEIVE PRE-AMPS. General purpose variable gain 0-20dB. Low noise 1dB typical. New carrier and DC switching with pre-set hang time. Types RP2S, RP4S, RP6S, RP10S. Boxed Kit £15.00. Built £19.50.

Plus the usual range of receive and transmit converters and other products.
YOUR DORSET SUPPLIER FOR YAESU, TRIO/KENWOOD & ICOM
Delivery within 7 days subject to availability. 24hr answering service
VAT inc. prices, add 35p for P&P. Send SAE for product price list.

UNIT B6, MARABOUT INDUSTRIAL ESTATE, DORCHESTER, DORSET. TEL 0305 62250

BARGAIN CORNER

WATCH THIS CORNER EVERY MONTH

KENWOOD TS-430S FITTED
FM-430 Unit £599 ONLY
Don't delay! Rush your Order in To-Day!
(Special Warranty Applies)

SECONDHAND EQUIPMENT

YAESU FT-101ZD (Shop Soiled - New)	£529
YAESU FT-101E, Mic, CW Filter	£399
YAESU FT-707 + FV-707DM + Mic	£550
YAESU FT-902DM, Mint Cond	£635
YAESU FP-4 Power Supply	£39

Western Electronics (UK) Ltd
Fairfield Estate, Louth, Lincs. LN11 0JH Tel. Louth (0507) 604955 Telex 56121 WEST G
Northern Ireland Agents: Tom & Norma Greer G14TGR/G14TBP Drumbo (023 126) 645

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon and Gotch (Asia) Ltd.; South Africa - Central News Agency Ltd. Subscriptions INLAND £13 and OVERSEAS £14 payable to IPC Magazines Ltd., "Practical Wireless" Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

RADIO SHACK

FOR EVERYTHING IN

AMATEUR RADIO



"The Oldest Name In Amateur Radio"

NEW



BRASS RACER IAMBIC

The newest addition to the Vibroplex family – the Brass Racer Iambic – A distinctive new design of Iambic paddle crafted from solid brass and mounted on a base of polished hardwood. No springs to fly off the middle of a contact. Superior Vibroplex quality. Always worth the difference and now a new Vibroplex look.



NEW




BRASS RACER EK-1

An even more exciting step is the new Brass Racer EK-1, an electronic keyer built into the base of our new Brass Racer Iambic paddle. Using the Curtis 8044 chip, this self-contained keyer and paddle is fully Iambic with dot/dash insertion and adjustable speed control. Use on either tube or solid state rigs. The perfect unit for mobile, DXpedition, or just plain fun.



THE IAMBIC

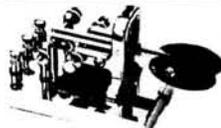The distinctive look and quality of the Vibroplex Original is fashioned into the finest Iambic paddle anywhere. The dual paddles allows the operator to utilize automatic dot/dash insertion and other unique features of the modern electronic keyer. Vibroplex distinction for the modern operator.



Standard or deluxe models available

THE VIBROKEYER

The Vibrokeyer is designed for "Bug" operators who want to move to electronic keyers without relearning keying. The single lever paddle initiates the automatic dots and dashes of the electronic keyer with the same motion used to operate the "Bug". For those who want to combine traditional skill with modern electronics.



Standard or deluxe models available

THE ORIGINAL

In 1890 Horace Martin Searched for relief from the "glass arm" telegraph operators were getting from pounding the straight keys. His answer, the Vibroplex Original was an instant success. The vibrating lever bar automatically produces dots while dashes are made manually. Still popular today, the distinctive sound of the "Bug" can still be heard. It is the signature of the true C.W. expert.



Presentation, standard or deluxe models available

All of our keys are available in Standard and Deluxe models. The Original and the Iambic are also available in the Presentation models.

Standard Model: All Standard models come with a neat, crisp, textured, painted base with polished and chromed top parts. Attention to detail in the finishing process gives Vibroplex an unexcelled quality appearance. Highly conductive large coin-silver contacts provide a clear, sharp signal, and non-skid rubber feet keep the keyer in its place.

Deluxe Model: All Deluxe models feature a chromed base, buffed and polished to a mirror finish. As in fine watches and other precision instruments, their jewelled movement serves to prolong life, maintain smoother, easier operation and prevent binding.

Presentation Model: The Presentation model is the top of the line at the top. Available in the Original and Iambic, the Presentation features 24 carat gold-plated base top, engraved with name and call and makes a truly personal gift. The Original has the adjustable super speed control main spring for a wider range of sending speeds.

Direct-Access Keyboard Tuning of 22,884 Frequencies

£229⁹⁵

Available 15th January, 1984
Covers 68-88 MHz VHF-Lo, 144-148 MHz Ham, 108-136 MHz AM Aircraft, 138-144 MHz, 148-174 MHz VHF Hi, 380-450 MHz Ham, 450-470 MHz UHF-Lo, 470-512 MHz UHF-Hi



Realistic PRO-30. A full-feature, micro-processor-controlled scanner with extended frequency coverage – in a compact size you can carry wherever you go! Scan up to 16 of your favourite channels continuously, or search a selected frequency range for new or unpublished channels. Scan and Search in two speeds. Two-second Scan Delay, selectable for each channel prevents missed replies. Lockout feature temporarily bypasses unwanted channels. Big LCD display shows channels and frequencies being monitored or programmed as well as the status of the channels. Priority function monitors your favourite frequency while you listen to others. Frequency-tracking front end assures top sensitivity on all bands. Squelch control eliminates noise between messages. Has jacks for external antenna and earphones. With flexible antenna. $7\frac{1}{2} \times 2\frac{1}{8} \times 1\frac{1}{8}$ ". Requires six "AA" batteries or mains or DC adapter. Memory backup requires four silver-oxide batteries. £229.95

Mains Adapter £6.99
DC Adapter £4.49


COLLINS KWM-380 Transceiver



DRAKE R7A



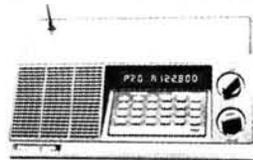BC-20/20FB
(with air band)
40 Channels
AM/FM



RADIO SHACK LTD

188 BROADHURST GARDENS,
LONDON NW6 3AY

(Just around the corner from West Hampstead Station on the Jubilee Line)

Giro Account No. 588 7151 Telephone 01-624 7174 Telex: 23718



Full-travel, full size
KEYBOARD
 Simply plugs into
 expansion port on your
SPECTRUM



KIT ONLY
 £39.95
READY-BUILT
 £44.95
 Case included in both prices

- * Single-key selection of all major multi-key functions.
- * Plugs directly into Spectrum expansion port and extends port for other peripherals.
- * Can accept Atari-type joysticks (optional extra).
- * Absolutely no soldering or dismantling of Spectrum.
- * Available in kit-form or ready-built.

The kit is sold in three parts — the Keyboard Main Kit which allows you to make your own arrangements for connection to the Spectrum — the Adaptor Kit which contains the extension board and socket for the expansion port and the cable between the

extension board and the keyboard — and the Case Kit which includes all the necessary mounting hardware.

Order As **LK29G (Keyboard Main Kit)** Price £28.50
LK30H (Adaptor Kit) Price £6.50
XG35Q (Case) Price £4.95

Full construction details in Projects Book 9.

Also available ready-built for direct connection and including case.

Order As **XG36P (Spectrum Keyboard)** Price £44.95

**HEATHKIT SUPERB QUALITY KITS BRING THE EXCITEMENT
 BACK INTO AMATEUR RADIO**

Experience the ultimate satisfaction of talking to someone on the other side of the world with a transceiver you actually built yourself. Just look at the wealth of state-of-the-art features on this quality HF SSB/CW Transceiver Kit. (HW-5400)

- * PLL synthesised stability gives high accuracy
- * Covers all amateur bands 80m to 10m
- * Output 100W PEP (80W on 10m).
- * Frequency display with resolution to 50Hz.
- * Split memory permits instant channel selection.
- * Excellent VSWR foldback protection.
- * Excellent image & I.F. rejection and I.F. shift tuning $\pm 600\text{Hz}$.
- * VOX facility eases sideband operation.
- * Optional frequency entry keyboard.
- * Optional 4-pole sideband filter.

Plus a whole host of other excellent features.

Other Heathkit Amateur Radio Kits include:

- 2 kW PEP Load Resistor (HN-31A) • SSB/CW/RTTY Active Audio Filter (HD-1418) • QPR Transceiver (HW-8) • Antenna Co-ax Switch (HD-1234) • HF/VHF Wattmeter & SWR Bridge (HM-9) • 50W Antenna Tuner with 4:1 Balun (HFT-9) • Morse Code Practice Oscillator (HD-1416) • Dual HF Wattmeter (HM-2140A) • Solid-State DIP Meter (HD-1250) • Ultra-Pro CW Keyboard (HD-8999) • Micromatic Memory Keyer (SA-5010).

Full details of all these quality kits in the Maplin catalogue. For details of the complete Heathkit range send 50p for the Heathkit full-line international catalogue.

Order As HK00A.



Maplin's Fantastic Projects

Full details in our project books. Price 70p each.

In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W MOSFET Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to 600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard • 100W 240V AC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Sounder.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 • Module to Bridge two of our MOSFET amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.

In Book 8 (XA08J) Modem (RS232) Interface for Dragon and Spectrum • Synchime • I/O Ports for Dragon • Electronic Lock • Minilab Power Supply • Logic Probe • Doorbell for the Deaf.

In Book 9 (XA09K) Keyboard with electronics for ZX Spectrum • Infra-Red Intruder Detector • Multimeter to Frequency Meter Converter • FM Radio with no alignment • Hi-Res Graphics for ZX81 • Speech Synthesiser for Oric • VIC Extenderboard • ZX81 ExtendIRAM • Dynamic Noise Limiter for Personal Cassette Players • TTL Levels to Modem/RS232 Converter • Logic Pulser • Pseudo-Stereo AM Radio • Ni-Cad Charger Timer • Adder-Subtractor • Syndrums' Interface • Microphone Pre-Amp Limiter.

Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packaging. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65

Name

Address

P.W.484



MAPLIN

ELECTRONIC
 SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 • Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926. • 8 Oxford Road, Manchester. Tel: 061-236-0281. • Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292. • 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000. • 46-48 Bevois Valley Road, Southampton. Tel: 0703 25831.

All shops closed all day Monday.

All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

Despatch by return of post where goods available