

RADIO & ELECTRONICS CONSTRUCTOR

MAY 1974


22p

6+6



STEREO STEREO AMPLIFIER

PART
ONE

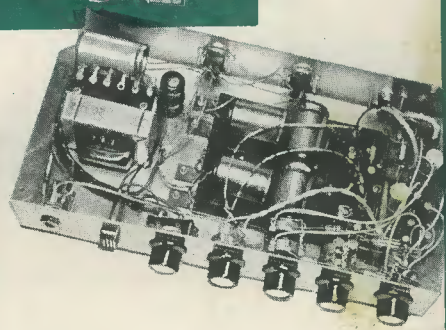


**ALSO
FEATURED**

MAINS-HUM TOUCH-BUTTON


Transmitter & Receiver Convertors from Wolffers Electronics

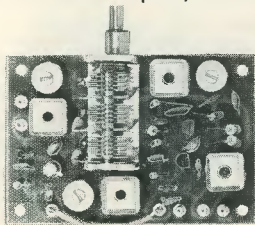Convert any MW Radio into an aircraft, amateur or VHF 142-162 MHz AM Receiver, simply by connecting the output of the converter to the aerial input, or wind three turns




WT7 AIRCRAFT BAND TUNER
110 MHz 130 MHz
Operates 9-12 Volt D.C. £14.45

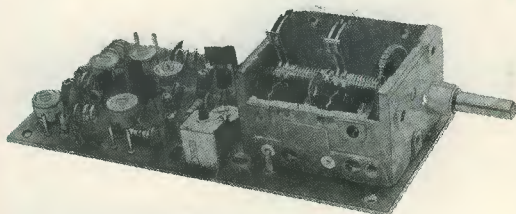WT9 VHF BAND TUNER
142-162 MHz
Operates 9-12 Volt D.C. £14.45



WZ9 FM TRANSMITTER (2 meter band)
VFO Controlled. Ready made and tuned.
Operates from 12 Volts D.C.
Output 200mW (WT15 & WZ9
make a complete receiver) £18.63

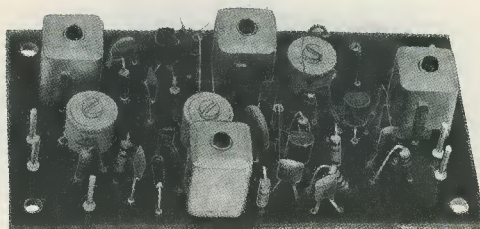round the Ferrite Rod, and tune your radio to 1500KHz Medium Wave. All these units are supplied on fibre glass printed circuit boards, ready tuned and tested.



WT15 TWO METER AMATEUR BAND TUNER
144-146 MHz (Varicap tuned)
Operates 9-12 Volts D.C. £14.08

ALSO AVAILABLE FROM WOLFFERS

WA7 ANTENNA AMPLIFIER
60-150 MHz
15dB gain at 100MHz
Operates from 9-12 Volt D.C. Supply. £2.97

TI1 CRYSTAL SET
In kit form—All parts including
earphone, ferrite rod, tuning cap
and P.C.Board. £2.29

ALL UNITS ARE SUPPLIED WITH FULL WIRING INSTRUCTIONS
AND ARE FULLY GUARANTEED

NOTE A Ministry of Posts & Telecommunications Licence is required for reception of transmissions by Aircraft, Fire Brigade etc.

All prices include VAT. Add 20p Post & Packing

Trade enquiries invited.

TRADER IMPORTS

4 & 7 CASTLE STREET, HASTINGS, SUSSEX. TN34 3DY. Telephone HASTINGS 437875

RADIO & ELECTRONICS CONSTRUCTOR

MAY 1974

CONTENTS

Vol. 27 No. 10

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

© Data Publications Ltd., 1974. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £2.70 (U.S.A. and Canada \$7.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maïda Vale, London, W9 1SN

The Radio & Electronics Constructor is printed by Carlisle Web Offset.


SHORT WAVE REGENERATIVE RECEIVER by R. A. Penfold	594
MAINS-HUM TOUCH-BUTTON (Suggested Circuit 282) by G. A. French	600
CAN ANYONE HELP?	602
R.F. COUPLED MORSE OSCILLATOR by M. H. George	603
NEWS AND COMMENT	604
TRANSISTOR GAIN BRIDGE by R. J. Caborn	606
CATALOGUE RECEIVED	608
MAKING PRINTED CIRCUIT BOARDS by Arthur C. Gee	609
6 + 6 STEREO AMPLIFIER by A. P. Roberts	612
R.F. 'NOSE' by James Kerrick	617
I.C. TRIAC TIMER by P. Manners	618
NEW PRODUCTS	622
SHORT WAVE NEWS – For Dx Listeners by Frank A. Baldwin	623
THE 'BIFLEXETTE' PORTABLE RECEIVER by Sir Douglas Hall, K.C.M.G.	625
IN YOUR WORKSHOP A.M. Diode Detectors	630
TWO-WIRE TWO-WAY BUZZERS by Barrie Gilbert	637
CONSTRUCTOR'S DATA SHEET No. 86 (Television Transmission Frequencies 1)	iii

JUNE ISSUE WILL BE
PUBLISHED ON 1st JUNE

SHORT WAVE REGENERATIVE RECEIVER

By R. A. Penfold

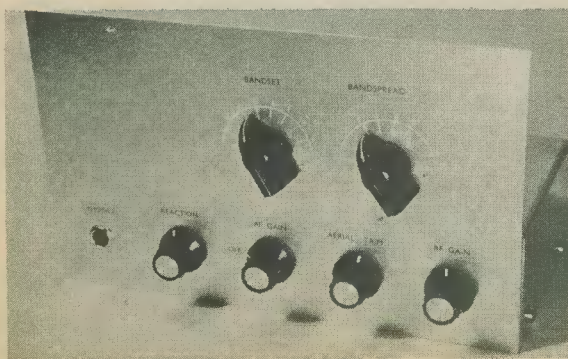This is a 3-transistor short wave receiver covering 17 to 4.8MHz for reception of the most popular broadcast bands. If desired, two additional coils may be employed, whereupon the receiver range includes the 80 and 160 metre amateur bands.



ONE OF THE MANY FASCINATIONS OF SHORT WAVE listening is that stations thousands of miles away can be received quite well using only a fairly simple receiver. Thus although the receiver described here has only modest gain by modern standards, when properly used with a good aerial world-wide reception is possible.

The set has been designed mainly for use on the short wave broadcast bands, and the frequency coverage with the specified Denco Range 4T plug-in coils extends from about 17 to 4.8MHz. This takes in five of the most popular bands at 19, 25, 31, 39 and 49 metres, and also includes the 20 and 40 metre amateur bands. Results on the amateur bands are not likely to be as good as they are on the broadcast bands due to the lower power of amateur transmissions. Many European stations can be received, however, and occasionally stations from further afield. If desired, the constructor can fit Denco Range 3T coils in addition to the Range 4T coils, whereupon the receiver will operate quite efficiently on the 80 and 160 metre amateur bands.

Power is obtained from an internal 9 volt battery, and the battery life is very good as the consumption is only 4mA. The receiver is intended for high impedance headphones, and the output may also be coupled to an a.f. amplifier.

RECEIVER CIRCUIT

The circuit diagram of the receiver is shown in Fig. 1. As can be seen from this, only three transistors are employed. The first, TR1, is used as an r.f. amplifier, whilst TR2 functions as a regenerative detector and TR3 as an a.f. amplifier. The aerial is coupled to the primary of L1 via the potentiometer VR1, which acts as an r.f. gain control. VC1 is the main tuning capacitor for L1, with VC3 operating as an aerial trimmer. The third winding on L1 couples to the base of TR1. This is a conventional r.f. amplifier using a standard germanium transistor biasing circuit.

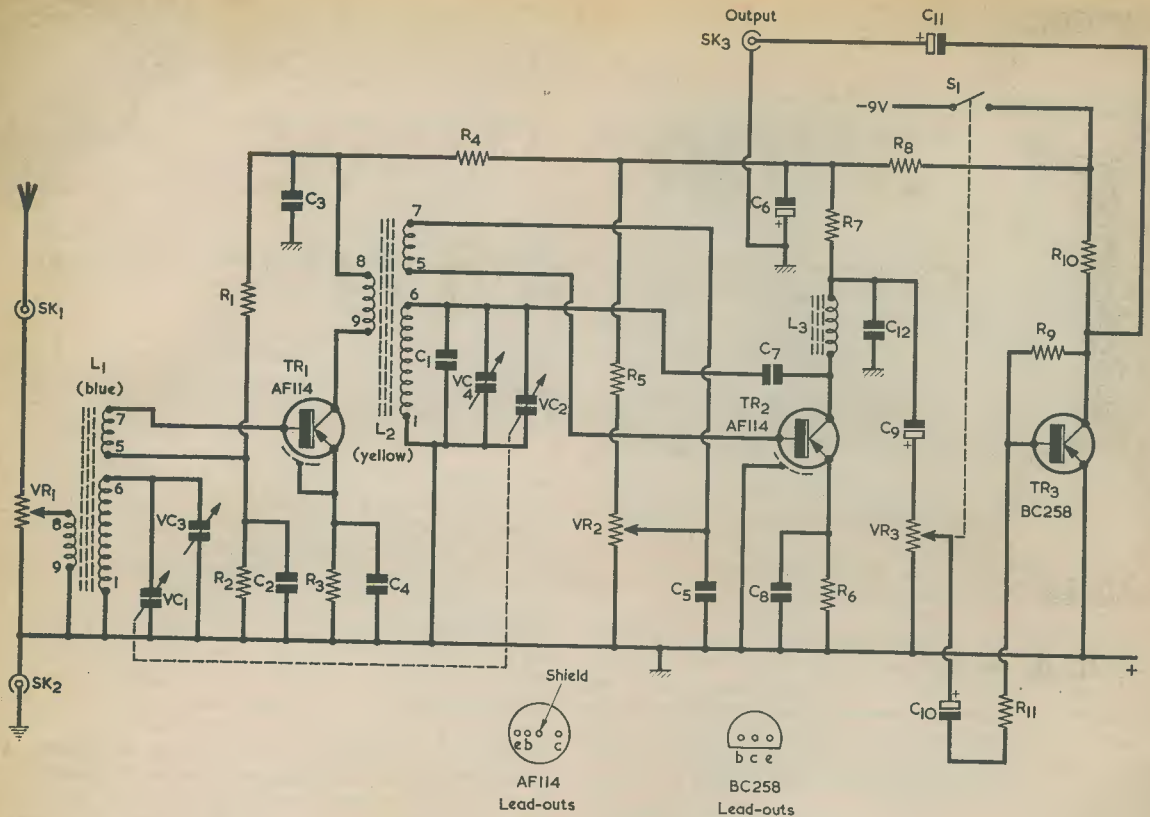


Fig. 1. The circuit of the regenerative short wave receiver.

The primary of L2 provides the collector load for TR1. VC2 and VC4 are connected across the tuned winding of L2. VC2 is the main tuning control and is ganged with VC1 in the aerial input stage. The 2-gang capacitor functions as a bandset control, and VC4 operates as a bandspread capacitor. The third winding on L2 couples into the base of TR2 and is connected such that the signal at the collector of TR2 is in phase with that at the upper end (pin 6) of the tuned winding. In consequence, regeneration is introduced via C7. Potentiometer VR2 controls the biasing current for TR2 and hence its gain. For the reception of a.m. signals this control is set just below the point at which the gain of the circuit is sufficient to cause oscillation. To receive c.w. and s.s.b. signals VR2 is set just above this point so that the detector is gently oscillating. Results on c.w. and s.s.b. are very good with regard to quality.

Apart from giving a very useful increase in gain, the r.f. amplifier also serves to prevent oscillations in the TR2 stage from reaching the aerial, where they could cause interference in neighbouring receivers.

L3 is the r.f. load for TR2 collector, and R7 is the a.f. load, with C12 providing r.f. decoupling. VR3 is the a.f. volume control and it feeds the a.f. stage by way of

C10 and R11. The last component offers final r.f. filtering. The a.f. stage, incorporating TR3, is quite conventional and has sufficient output to feed a pair of high impedance headphones. S1 is the on-off switch and is ganged with VR3. R4, R8, C6 and C3 are supply decoupling components.

The BC258 specified for TR3 is available from Electrovalue Ltd., 28 St. Judes Road, Englefield Green, Egham, Surrey. Many of the components are fitted to three tagstrips with horizontal tags, one of these being 6-way and the other two 8-way. The 6-way tagstrip is approximately 2.9in. long and the 8-way tagstrips approximately 3.7in. long. These were obtained by the writer from a local retailer, and identical types are not available from the usual mail order houses. However it will be in order to employ other tagstrips which are of around the same size or somewhat smaller, such as the Bulgin tagstrips available from Home Radio under Cat. No. BTS62 (6-way) and Cat. No. BTS64 (8-way).

CHASSIS AND PANEL

The chassis measures 8 by 4 by 2in. and can be home-made from 18 s.w.g. aluminium or purchased already made. The author obtained his chassis from H. L.


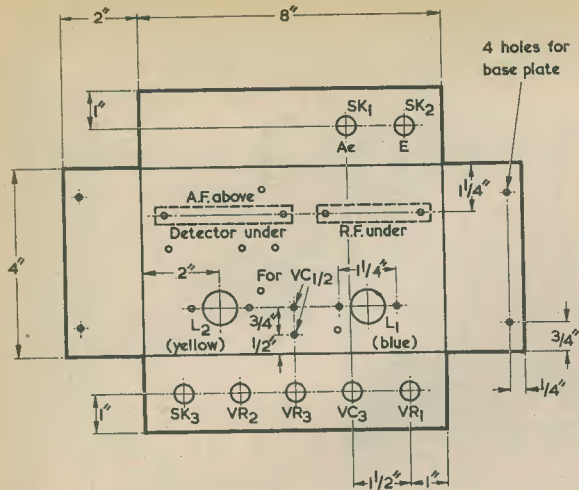


Fig. 2. Drilling details for the receiver chassis. Dimensions not shown are discussed in the text.

Smith & Co. Ltd., 287/9 Edgware Road, London, W.2. In Fig. 2, the chassis is viewed from the top with the four flanges opened out. When home-constructed, the flanges will be bent down, away from the reader. Coils L1 and L2 are plugged into standard B9A valveholders, which require a $\frac{3}{8}$ in. diameter cut-out. The valveholder tags should have the orientation with respect to chassis which is shown in the under-chassis wiring diagrams of Figs. 4 and 5 and, with some valveholders, this may mean that the two 6BA clear mounting hole positions for each holder may be displaced slightly from those shown in Fig. 2. The $\frac{3}{8}$ in. holes should be made first, the valveholders held in these to give the required tag orientation and the mounting holes then marked out using the valveholders as templates. A solder tag is secured, below the chassis, under each of the 6BA mounting nuts.

The mounting holes for VR1, VR2, VR3 and VC3 are $\frac{3}{8}$ in. diameter. The diameters of the holes for SK1, SK2 and SK3 depend upon the particular components employed. Fig. 2 also shows the positioning of the 6-way r.f. amplifier tagstrip, and the 8-way detector and a.f. amplifier tagstrips. The first two are below the chassis whilst the last is above. The two 8-way tagstrips share the same pair of mounting holes. All the tagstrip holes are marked out with the aid of the tagstrips themselves and are drilled 6BA clear or 8BA clear to suit the actual tagstrips to be used. Two mounting holes are shown for the 2-gang capacitor and these should be 4BA clear. The 2-gang capacitor is mounted by two $\frac{1}{4}$ in. 4BA screws passing through these holes, and its final positioning should be such that its spindle protrudes by about $\frac{3}{8}$ in. through the centre of the panel hole which is shown in Fig. 3. The capacitor should not

Fig. 3. The front panel of the receiver.

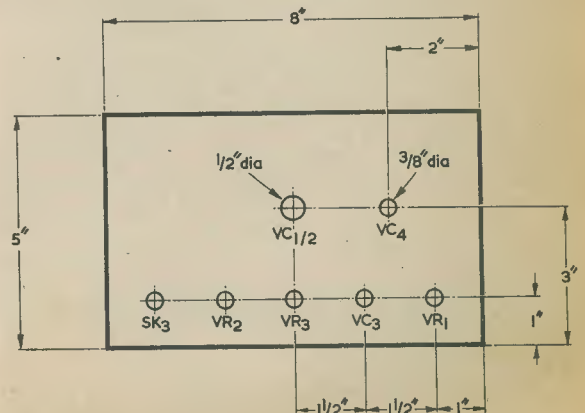


Material: 18 s.w.g. aluminium

be mounted until the front panel has been fitted.

There are five further holes shown in Fig. 2 on the chassis deck. These are intended for the passage of wires and are drilled $\frac{1}{8}$ in. diameter in the approximate places indicated. They are then fitted with grommets to protect the wires.

A base plate is fitted to the chassis. This can be obtained with the chassis, if this is commercially made, but the author chose to make one from an 18 s.w.g. aluminium sheet measuring $8\frac{7}{8}$ by $3\frac{7}{8}$ in. This has a $\frac{1}{2}$ in. flange bent up at 90° at each end, giving a $7\frac{7}{8}$ by $3\frac{7}{8}$ in. plate which pushes into place under the chassis. The four holes in the side flanges of the chassis are drilled clearance size for small self-tapping screws. The base plate is then temporarily placed in position and the required four holes in its flanges marked out with a pencil. These are then drilled out tapping size for the self-tapping screws. The base plate may be fitted with four small rubber feet near its corners.

The front panel, which as already been referred to, is shown in Fig. 3. This is cut from a sheet of 18 s.w.g. aluminium and measures 8 by 5in. The lower row of holes is identical to the corresponding holes in the front flange of the chassis and the front panel is, in fact, secured to the chassis under the bush mounting nuts of SK3, VR2, VR3, VC3 and VR1. Also required are the $\frac{1}{2}$ in. hole for the spindle of VC1, VC2 and a $\frac{3}{8}$ in. hole for VC4.

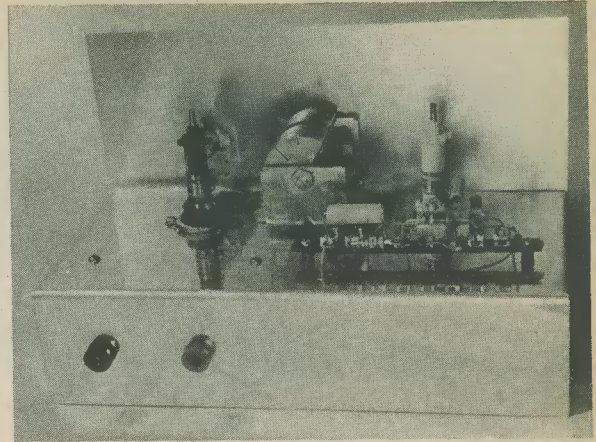

Rear view of the chassis. The two coils plug into B9A valveholders.

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1	12k Ω
R2	2.2k Ω
R3	1k Ω
R4	820 Ω
R5	56k Ω
R6	1k Ω
R7	2.2k Ω
R8	220 Ω
R9	820k Ω
R10	4.7k Ω
R11	2.2k Ω
VR1	25k Ω potentiometer, linear
VR2	10k Ω potentiometer, linear
VR3	5k Ω potentiometer, log, with switch S1

Capacitors

C1	18pF silvered mica
C2	0.022 μ F polyester
C3	0.022 μ F polyester
C4	0.01 μ F disc ceramic
C5	0.022 μ F polyester
C6	100 μ F electrolytic, 10 V. Wkg.
C7	1.8pF ceramic or silvered mica
C8	0.01 μ F disc ceramic
C9	10 μ F electrolytic, 10 V. Wkg.
C10	1 μ F electrolytic, 10 V. Wkg.
C11	10 μ F electrolytic, 10 V. Wkg.
C12	0.01 μ F polyester
VC1, VC2	365 + 365pF 2-gang variable, type 'O' (Jackson Bros.)
VC3	50pF variable, type C804 (Jackson Bros.)
VC4	15pF variable, type C804 (Jackson Bros.)

COMPONENTS

Inductors

L1	Miniature dual-purpose, transistor usage, Blue coil Range 4T and 3T (optional) (Denco)
L2	Miniature dual-purpose, transistor usage, Yellow coil Range 4T and 3T (optional) (Denco)
L3	R.F. choke, 1.5mH

Transistors

TR1	AF114
TR2	AF114
TR3	BC258

Switch

S1	S.P.S.T. toggle, part of VR3
----	------------------------------

Sockets

SK1	Wander plug socket
SK2	Wander plug socket
SK3	3.5mm jack socket

Miscellaneous

9-volt battery type PP3 (Ever Ready)
4 round knobs
2 pointer knobs
2 B9A valveholders
Battery connector
1 6-way tagstrip (see text)
2 8-way tagstrips (see text)
1 aluminium chassis 8 x 4 x 2 in. with base plate (see text)
1 aluminium panel, 18 s.w.g., 8 x 5 in.
4 rubber feet.

COMPONENT ASSEMBLIES

Most of the components are mounted on the tagstrips already discussed, and details of the wiring involved are given in Figs. 4, 5 and 6. Fig. 4 illustrates the r.f. stage wiring, Fig. 5 the wiring for the detector and Fig. 6 that for the a.f. stage. These diagrams show nearly all the other wiring for the receiver.

Start the electrical side of construction by mounting the various components on their tagstrips. In the diagrams the components are shown well spaced out for clarity. In practice, however, component leads are all kept fairly short, as can be seen in the photographs. It is advisable to cut the component leads to length, and to tin these with solder prior to attempting to mount the components.

When the strips have all their components fitted to them they may be mounted on the chassis. The r.f. stage is mounted on its own on the underside of the chassis, being spaced away from the chassis by about $\frac{1}{2}$ to 1 in. The detector and a.f. tagstrips are mounted by the same bolts or lengths of studding, and are also spaced away from the chassis by about $\frac{1}{2}$ to 1 in.

As can be seen from the diagrams, quite a lot of interconnecting wiring is required. This is carried out with thin p.v.c. insulated wire, and it must be kept reasonably short. C1, C5 and C7 are not mounted on the tagstrips, but in the manner shown in Fig. 5. It will be necessary to solder an extension lead to the base lead-out of TR1 in order to reach tag 7 of L1 coil holder. See Fig. 4. This lead should be covered with thin p.v.c. sleeving. Since TR1 and TR2 are germanium types, their lead-outs should be at least $\frac{1}{4}$ in. long, and the use of a heat shunt during soldering is advised.

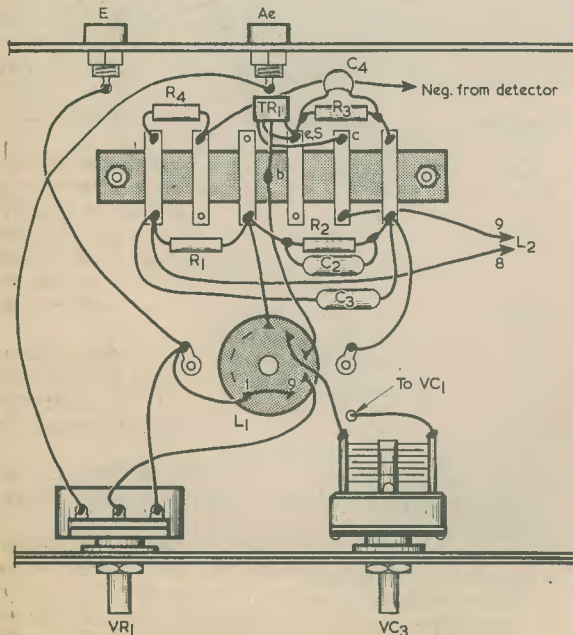


Fig. 4. The wiring around the aerial stage.

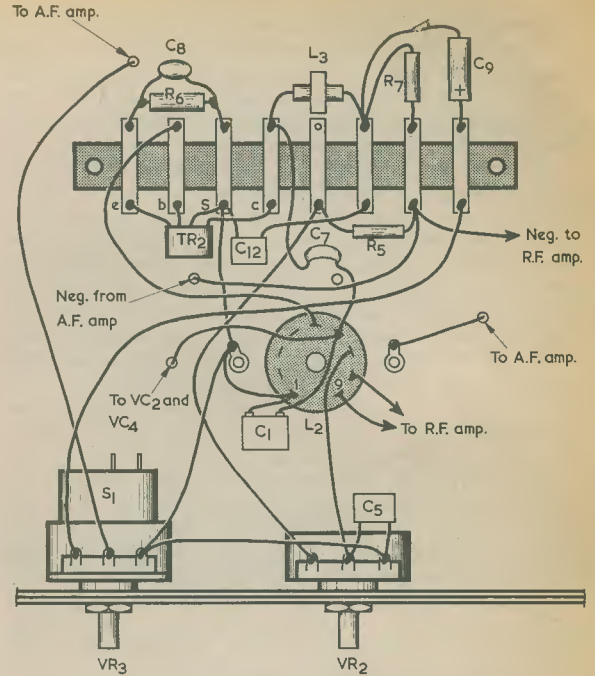


Fig. 5. The components and wiring at the detector tagstrip.

The fixed vanes of VC4 are connected above the chassis to the fixed vanes of VC2. Connection to the moving vanes of VC1, VC2, VC3 and VC4 is automatically made by way of their mounting on the chassis or front panel.

Only one lead is shown, in Fig. 6, passing to SK3.

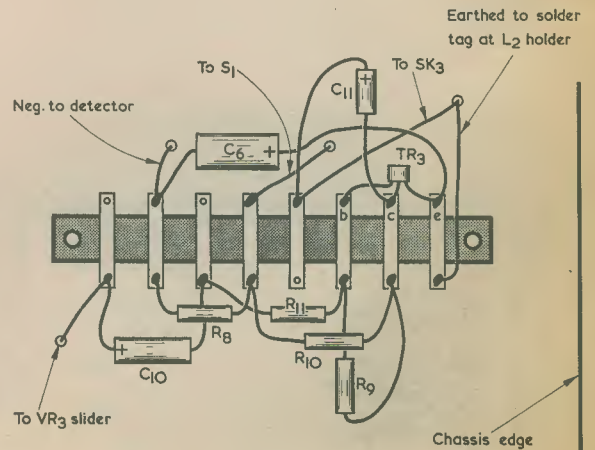


Fig. 6. The layout of the a.f. amplifier stage.

The tag on this socket which corresponds to the sleeve of the jack plug should automatically provide a chassis point by way of its mounting bush, and this tag takes the positive battery lead. If SK3 is of the type which is insulated from chassis, the tag in question is connected to the nearer solder tag under L2 coil holder mounting nut. A lead from the a.f. amplifier tagstrip passes through the chassis to one tag of S1. The negative battery lead connects to the remaining tag of S1. There are a number of convenient spaces under the chassis where the battery can be mounted vertically. It is held firmly in place when the base plate is screwed in position, a piece of foam rubber or plastic being glued to the plate to hold the battery firmly in place. A blue aerial coil plugs into the holder for L1 and a yellow r.f. coil into the holder for L2.

ALIGNMENT


Due to the presence of a panel operated aerial trimmer there is no necessity for precise alignment, as this trimmer can be adjusted to peak the aerial tuned circuit at the various settings of the main tuning control. The only setting-up required consists of initially adjusting the core of the yellow r.f. coil so that about $\frac{1}{8}$ in. of the threaded brass stem protrudes from the top. The aerial trimmer, bandspread and main tuning capacitors are then set to their central positions and the core of L1 adjusted for maximum sensitivity.

If Range 3T coils are also to be used these are set up in the same way. The cores can be held in position by passing a 6BA nut over each of the threaded stems and locking this gently against the top of the plastic former.


AERIAL AND EARTH

A normal long wire aerial should be used, and this should preferably be a proper outdoor type, some 50ft. in length and set as high as possible. A short indoor aerial will give some results and a surprisingly large number of stations can be received with such an aerial. It will not, however, give results which are comparable with those resulting from the use of a good outdoor aerial.

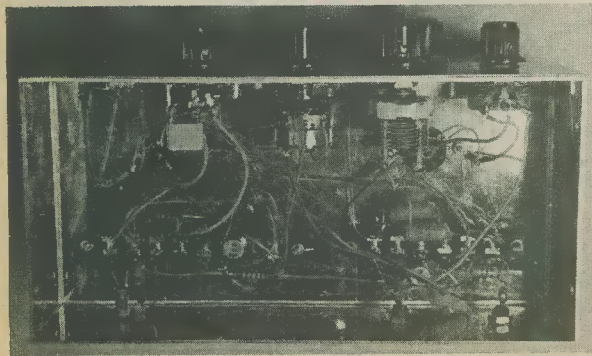A proper earth connection, consisting of a metal rod or plate with wire attached, and buried in damp earth, will probably slightly improve results. A mains earth connection is not usually of much help, and may even introduce interference.



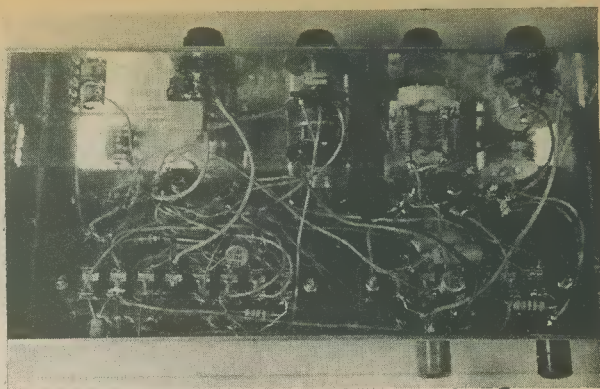The underside of the chassis. Most of the small components in the r.f. amplifier and detector stages are mounted on two tagstrips.



Another view of the parts fitted below the chassis.

OPERATING NOTES

The bandset control, VC1, VC2, is employed to search the dial for the required band. When this has been located and VC1, VC2 set to the band centre, the bandspread capacitor, VC4, is employed to tune across the band. VC4 has a much smaller value than the bandset control and so only covers a very restricted range of frequencies. This gives the same effect as tuning the bandset control by way of a high ratio reduction drive. VR3 and S1 function as a normal combined a.f. volume control and on-off switch. VR2 is the reaction control and, as stated earlier, is adjusted so that the detector is just below the point at which oscillation occurs when receiving a.m. signals. It is at this point that the receiver is most sensitive and exhibits its greatest selectivity. VR2 is set just above the threshold of oscillation for the reception of c.w. and s.s.b. signals. It is obvious when the detector is oscillating since there is a sudden increase in the noise level, and a loud whistle is heard as the set is tuned across an a.m. transmission.

It should be mentioned that the yellow Denco r.f. coil is basically intended for r.f. coupling without the provision of regeneration and there is a very slight possibility that its base coupling coil may be incorrectly phased. If no oscillation can be obtained, this point may be ascertained by temporarily transposing the connections to tags 5 and 7 of the holder for L2.

VR1 is the r.f. gain control and is normally set to maximum. It may be turned back somewhat with very strong signals, which can otherwise overload the detector and make it impossible to obtain oscillation. In extreme cases the overloading will be heard as a loud hissing noise in the headphones. Very strong s.s.b. signals will tend to sound a little distorted and their quality can be improved by reducing the r.f. gain.


The aerial trimmer VC3, is used to peak received signals and it is important to see that this is always correctly adjusted. Both VR2 and VC3 will probably need some slight adjustment each time the tuning controls are significantly altered.

Best results are given with 4,000 Ω headphones. Also, crystal headphones or even a crystal earpiece can be used.

Logging scales can be marked around the knobs of the bandset and bandspread controls. On the prototype a simple 0-10 scale is provided around each, but more comprehensive scales can be used if desired. The 0-10 scales were taken from 'Panel Signs' Set No. 5. Legends were also provided above each control to indicate function, and these were provided by 'Panel Signs' Set No. 4. 'Panel Signs' are available from the publishers of this journal.

MAINS — HUM TOUCH BUTTON

by G. A. FRENCH

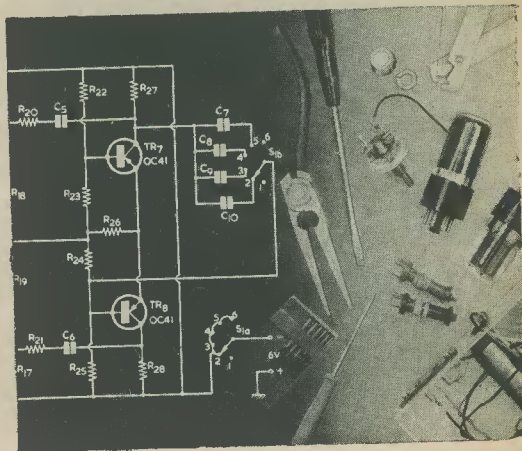

OPERATION OF ELECTRICAL AND electronic circuits by touch-button is by no means a new feature of technology, and buttons of this nature have been employed for the control of lifts and similar purposes in America for quite a few years. A touch-button sets a circuit in operation when it is touched by a human finger, and no pressure is required as occurs with a conventional push-button. One of the advantages conferred is that there is no mechanical wear on the button, but there is the accompanying disadvantage that the circuit required around the button is more complex than is given by the simple closure of two contacts in a push-button.

Touch-buttons are appearing more and more frequently in domestic entertainment equipment, a typical example being given in the Ferguson 4000 series of colour television receivers. Here, the touch-buttons are referred to as 'touch pads' and are used for channel selection. Each touch pad has two exposed contacts which are bridged by the finger tip when touched. This causes a small current to be passed to one of the inputs of an MOS integrated circuit. The i.c. latches on at the latest pad to be touched and provides a corresponding output which switches in one of a number of pre-set varicap tuning circuits.

HOME CONSTRUCTOR CIRCUIT

The device to be described in this article operates on quite a different

principle and employs pick-up of mains hum to actuate a relay by way of an a.f. amplifier and rectifier. All constructors will be familiar with the mains hum which is reproduced by the speaker of an audio amplifier when an input point is touched with a finger. Advantage is taken of this effect here; the touch-button is coupled to an a.f. amplifier input and a mains hum voltage is injected when the button is touched. The circuit has to be classed as experimental because it depends upon the mains fields which exist in the area where the button is located. In the writer's house, which has unscreened mains wiring, the circuit was sufficiently sensitive to be actuated by holding a finger very close to the button without actually touching it. In consequence it was possible to actuate the device even whilst wearing gloves. In houses which have screened mains wiring, the mains fields will be smaller in intensity, and sensitivity may be lower. It is possible that a field may be artificially introduced by running an unscreened mains wire near the touch-button and this point is dealt with later.

The circuit of the device appears in Fig. 1, in which the touch button couples via screened wire to capacitor C1 and then to the base of TR1. TR1 and TR2 appear in a high gain a.f. amplifier circuit. The collector of TR1 connects directly to the base of TR2, and the final amplified signal appears across R3. R1, the base bias resistor for TR1, is taken to the emitter of TR2, which is bypassed for a.f. by C4. Under d.c. conditions TR2 acts as an

emitter follower; its base, and hence the collector of TR1, takes up a potential which allows the corresponding bias current to flow into the base of TR1. The circuit thus stabilizes at this emitter potential in TR2, and the overall result is a high gain a.f. amplifier which requires few components.

The base of TR1 would normally be fed by a low impedance input circuit, but in the present application there is negligible loading on the base at all. Because of this it is necessary to screen the base wiring of TR1 to prevent capacitive coupling to the following components in the amplifier as, otherwise, r.f. instability can result. The circuit is quite stable provided that the screening is carried out efficiently. Capacitor C2 is included to reduce the gain at radio frequencies. The input impedance looking into TR1 base is low, but this base proves in practice to offer an adequate mains hum pick-up point.

When the touch-button is touched, the amplified hum signal at TR2 collector is fed, via C3, to the rectifier D1. The junction of C3 and D1 then takes up a rectified potential which is proportional to the signal amplitude from TR2 and which is negative with respect to the positive upper supply rail. This rectified signal has a very high alternating content at mains frequency and its harmonics, and needs to be 'smoothed' before it can be applied to the relay actuating section of the circuit. The 'smoothing' is carried out by R5 and C5, whereupon a negative-going signal is fed to silicon transistor TR3. This functions as an

RADIO & ELECTRONICS CONSTRUCTOR

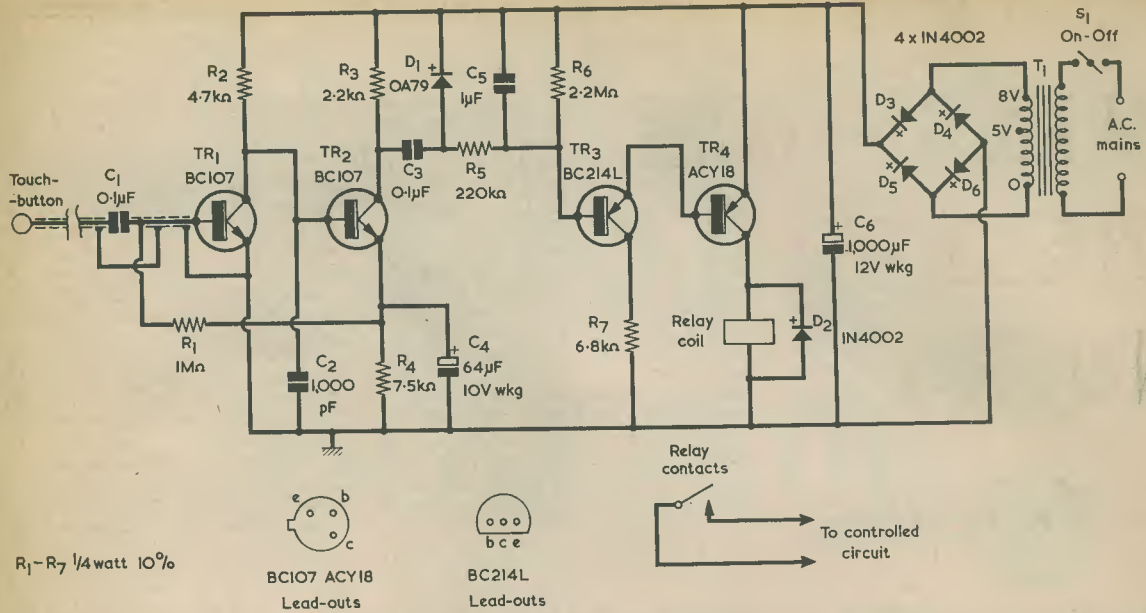


Fig. 1. Complete circuit of the touch-button unit.

emitter follower and passes an amplified current to the base of TR4. TR4 is a small robust germanium transistor and its collector current then energises the relay.

Overall circuit operation may be summed up in the following manner. When the touch-button is not touched, any signal present at TR2 collector is mainly amplified noise with possibly a low hum content. Should this signal voltage be sufficiently high to be rectified by D1, it will still be too low to take the base-emitter junction of TR3 up to the 0.6 volt level it requires for the transistor to become conductive. Thus TR3, and in consequence TR4, remains cut off. When the touch-button is touched, a rectified hum signal in excess of 1 volt appears at the junction of C3 and D1, and this is sufficient to make TR3 conductive and thereby turn TR4 fully on. The relay energises and its contacts switch on any external circuit which it is desired to have the touch-button control.

The power for the circuit is obtained from the a.c. mains supply by way of transformer T1 and the bridge rectifier given by D3 to D6. The only other power supply component is reservoir capacitor C6, which also carries out the secondary function of providing a signal frequency bypass across the supply rails.

PRACTICAL POINTS

The components employed in the circuit are all standard widely available parts. Like TR3, TR1 and TR2 are silicon transistors. Diode D1 is a

germanium component, whilst D2 to D6 are silicon rectifiers. The function of D2 is to prevent the appearance of a high reverse voltage across the relay coil when its energising current is turned off. It is important to connect D2 into circuit with correct polarity, or excess current can flow in TR4 and cause this transistor to be damaged.

Capacitors C1, C3 and C5 are polyester or polycarbonate components. A 1µF electrolytic capacitor having a working voltage of 4 volts or more could, alternatively, be fitted in the C5 position. Its positive lead-out should connect to the positive supply rail. Mains transformer T1 is a small bell transformer of the type which is available at the electrical counter of Woolworth's Stores. It has an 8 volt secondary with a 5 volt tap which is not used here. The relay can be any component having a coil resistance of 250Ω or more, and which is capable of energising at 8 volts or less. In the prototype circuit, the author used a P.O. 3000 relay with a 500Ω coil.

With the exception of the input wiring to TR1 base, layout is not at all critical. It is essential, however, to prevent interaction between the base of TR1 and the remainder of the a.f. amplifier section. C1 and R1 should be mounted several inches from the other components, and the connection between TR1 base and the junction of C1 and R1 should be carried out with screened wire, the braiding of which extends very nearly to the base lead-out of the transistor. The base lead-out should not be anchored to a tag on a tagstrip or, say, to a strip of copper foil

on a piece of Veroboard, as either of these would provide an excessive area of metal in contact with the base of the transistor which could couple by stray capacitances to the other components. The connection between the screened cable and the transistor base lead-out should take the form of a 'mid-air joint', as illustrated in Fig. 2. The braiding of the screened cable may be earthed at the emitter connection point of the transistor. The author used thin flexible screened wire having closely meshed braiding. This was also used for coupling C1 to the touch-button. Any flexible screened wire suitable for connecting a pick-up or a microphone to an a.f. amplifier would be suitable

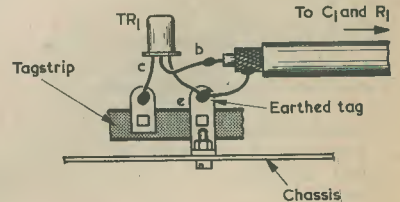


Fig. 2. The screened wire to the base of TR1 must connect to it in the manner shown here. It is assumed that the transistor is mounted on a tagstrip, but any other suitable means of anchoring the emitter and collector lead-outs to a tag on a tagstrip or, say, to a strip of copper foil can be used.

here. Television aerial coaxial cable might not be suitable and is best avoided.

It should be repeated that the precautions against instability just described apply only to the base of TR1. The circuitry around TR1 and TR2 may be looked upon as a simple a.f. amplifier involving no unwanted feedback problems, with the proviso that there is just one point, at the base of TR1, which is 'hot'.

The touch-button can be a small round metal disc having a diameter of about $\frac{1}{4}$ in. which is suitably mounted on an insulating material, as in Fig. 3. The screened wire between C1 and this disc can be any length up to 6 ft. or so. The mounting for the button must be a reliable insulator, and the disc should

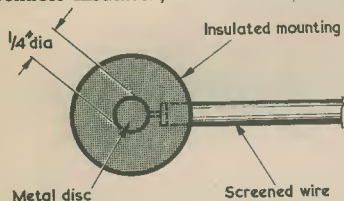


Fig. 3. The centre lead of the screened wire connects to the touch-button, which consists of a metal disc fitted on an insulated mounting.

not be fixed direct to a wooden surface.

Working from the writer's experience, the area of the button should be kept low or it will, itself, pick up an excessive hum signal. With the prototype it was possible to energise the relay when a flat piece of metal 2 in. square was rested, on its own, on the touch button. To give a further idea of sensitivity, the relay also operated when the author held one lead-out of a 4.7M Ω resistor between his fingers and applied the other lead-out of the resistor to the button. This high sensitivity means that the button could not be sited out of doors due to the problems of electrical leakage during and after rain. As was mentioned earlier, the results obtained depend on the strength of the mains fields in the vicinity of the button. If these are weak a single unscreened insulated wire connected to the live side of the mains could be positioned vertically on a wall about 2 yards away from the button. The wire could be about 5 ft. long and should provide a sufficiently high field for the touch-button, although this point would have to be determined experimentally and has not been checked out by the writer.

The operation of the a.f. amplifier section can be monitored by connecting a pair of high resistance headphones across diode D1. These should repro-

duce a low background hiss which rises to a loud hum when the button is touched. A loud hiss accompanied by erratic operation of the relay indicates that the amplifier is oscillating, and attention should then be paid to the screening of the lead to the base of TR1. Connecting the headphones will prevent the relay from operating because of the relatively low resistance then applied across the diode. Alternatively, the input of an external a.f. amplifier could be coupled to the diode, the earthy input terminal connecting to the negative supply rail and the non-earthly input lead to the junction of D1 and C3 via a 0.01 μ F capacitor. The external amplifier gain will need to be kept fairly low due to the high amplitude of the signal across D1.

As a final point, it will in many cases be found preferable not to have the chassis of the touch-button unit connected to earth. This will enable the chassis to carry a small mains voltage itself by way of the internal stray capacitances in transformer T1. In houses with screened mains wiring this will enable a hum voltage to be developed across the base and emitter of TR1 due to the capacitance to earth of the body of the operator touching the button, rather than through the pick-up of external mains hum fields. ■

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received for to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

Radio Constructor, November and December 1968 - K. Stephenson, "Red Screes", Mayo Street, Cocker-mouth, Cumberland, CA13 0BY - To Purchase.

BC 221 AL Signal Corps Frequency Meter - P. Berwick, 10 Selbourne Road, Hockley, Essex - Manual required, or any relevant information, to purchase or borrow.

Power Supply - R. G. Coombe, 45 Saxon Road, Exeter, Devon, EX1 2TD - Circuit of power supply to run Car Radio/Cassette Recorder from 240 volt a.c. mains, required.

Radio Constructor bound volumes, Nos. 20/21/22 (August 1966-July 1969) - Trevor F. C. Davis, 1064A London Road, Thornton Heath, Surrey, CR4 7ND - To purchase in unmarked condition suitable for private library.

Ferranti 194 Mains Receiver - J. Carver, 112 Merthyr Mawr Road, Bridgend, Glamorgan, CF31 3NY - circuit diagram required.

Mecablitz 500 Electronic Harp - W. Swann, 127 St. Wilfrids Road, West Hallam, Derbyshire, DE7 6HG - circuit diagram or information as to where obtainable.

R-C Bridge - T. R. Smith, 7 Purbeck Court, Park Barn, Guildford, Surrey - circuit diagram, preferably for transistorised R-C Bridge.

World Tapes for Education - A. J. Woodham, 18 Normanhurst Road, Borough Green, Sevenoaks, Kent - Information of this or any other known international organisation for the exchange of recorded correspondence tapes.

Phillips Communication Receiver and Power Unit - Type P.C.R. - V. R. Robb, 33 Stranmillis Gardens, Belfast, BT9 5AS, Northern Ireland - Circuit diagram and/or any other data.

R.F. COUPLED MORSE OSCILLATOR

By M. H. George

An unusual and inexpensive design which allows a Morse practice oscillator to be inductively coupled to an a.m. transistor radio.



THIS UNIT EMPLOYS A STANDARD UNIJUNCTION A.F. oscillator, and it has the unusual feature that it can be coupled to any medium or medium and long wave transistor radio without making any direct connections.

CIRCUIT OPERATION

The circuit of the unit appears in the accompanying diagram. The tone is produced by the unijunction transistor TR1, the frequency of oscillation being controlled by the pre-set potentiometer VR1. When the key is open, the unijunction pulses given by C1 discharging into R2 have a relatively long fall time. However, when the key is closed C1 is discharging more or less into a short-circuit, apart from the emitter - base 1 junction of TR1, and the pulses have correspondingly a very short fall time and a high current amplitude. These pulses can be picked up by the ferrite rod aerial of an a.m. transistor radio positioned about a foot from the leads to the key. The signal consists of r.f. harmonics of the unijunction tone modulated at the basic tone frequency. Thus, a loud tone is given by the speaker of the radio each time the key is pressed.


In the prototype the leads between the oscillator unit and the key are about 3 feet long and consist of two separate untwisted wires. Performance may vary according to the particular radio employed, but a little experiment will soon indicate the best mutual positioning required for this and the key leads.

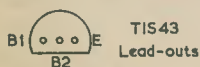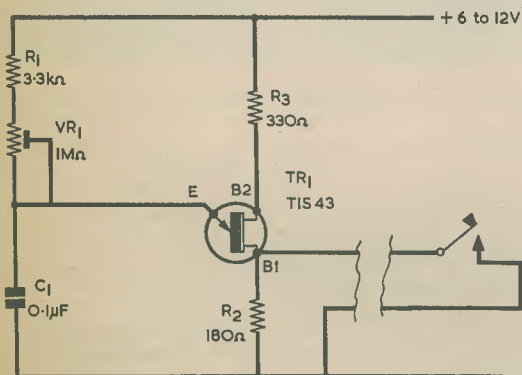The frequency of oscillation is set up by adjusting VR1. The range of oscillation is wide and VR1 needs to be adjusted fairly carefully for the desired frequency. The unit can operate from any d.c. supply between 6 and 12 volts. At 6 volts current consumption is 1.5mA, and at 12 volts it is 2.6mA. The current drawn from the supply alters only slightly when the key is pressed. ■



Circuit of the r.f. coupled Morse practice oscillator. The three fixed resistors are $\frac{1}{4}$ watt 10% and VR1 may be a skeleton potentiometer.

SIMPSON MULTIMETER

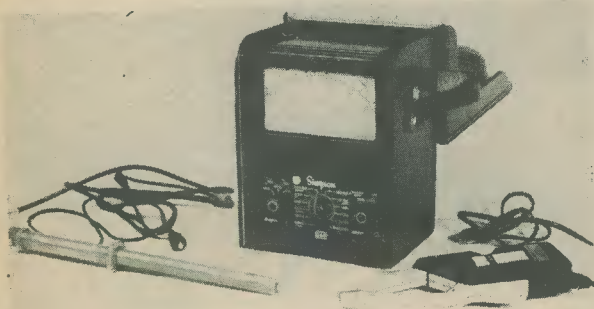

Electroplan Limited of Orchard Road, Royston, Herts., have signed an agreement to distribute the well-known Simpson Multimeter. This high performance, low cost American-made unit is an ideal alternative to centre pole multimeters currently available in the UK. It has twenty-nine ranges covering AC/DC, volts, current, ohms and decibels. Full scale voltage measurements are from 250mV to 1000V and current (DC only) from 50 μ A to 10A. DC accuracy is 2% over full operating temperature range. The Simpson has a high sensitivity of 20K ohms/volt DC and 5k ohms/volt AC with excellent overload protection using an extremely fast transistorised cut-out, with a reset button, diode protection of the meter movement and externally accessible fuse.

The multimeter is supplied complete with batteries and test leads. A wide range of accessories are available including an Amp-Clamp for AC current measurements up to 300A, a 30Kv high voltage probe and leather carrying case.

The Simpson Multimeter is available ex-stock from Electroplan at £39.50 (VAT extra).

AUDIO ENGINEERING SOCIETY MEMBERS VISIT EMI TAPE LTD.


Following a lecture presented to the Audio Engineering Society by Ray Gilson technical consultant to EMI Tape Ltd. members of the Society visited the Emitape manufacturing plant at Hayes in Middlesex recently.

The photograph below shows a group of A.E.S. members quizzing manager Tom Anderson on tape slitting techniques, during their comprehensive tour of one of the largest and most up to date tape making plants in Europe.

Particular interest was also shown in the test equipment used by the quality assurance laboratories of EMI Tape Ltd. Strict checks are carried out by the laboratories on both raw materials and finished product to ensure that high manufacturing standards are maintained.



E. F. JOHNSON RANGE OF BINDING POSTS

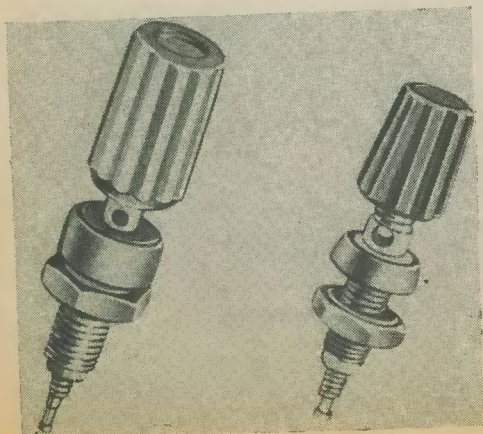

As part of the E. F. JOHNSON range of components, Vero Electronics Limited of Chandler's Ford, Eastleigh, Hants., are now able to offer deliveries from stock of their Terminals or Binding Posts. Two sizes of binding post are available to accept either .080 in. tip plugs, miniature banana plugs, or standard banana plugs. They offer excellent current capacity up to 15 amps and a high peak voltage up to 8000 volts. They are pre-assembled with a moulded body and silver plated shank. The fluted thumb is self-captivated and they are designed for use with a solder stud or lug for thumb screw retention, or a plug connection to the top end.

COMMENT

BEATING THE DUST PROBLEM

Do you have problems with dust, attracted by static electricity, on your favourite longplaying records? BBC World Service outlined a new device for dealing with the problem.

The Industrial Development Unit at the University College of North Wales in Bangor has invented an anti-static gun. The device looks like a water pistol but, instead of shooting out a stream of water, this pistol fires a stream of electrically charged air particles.

It contains a piezo-electric crystal. When the trigger on the pistol is squeezed the crystal is compressed and it generates a high voltage, about 12,000 volts, which is fed to a fine metal point in the nose of the pistol.

The fine point is in fact a sewing needle. Air particles become positively charged and as they strike the surface of the record, they neutralize all the negatively charged particles on that surface. Conversely when the trigger is released negative charge is emitted and this neutralizes any positive charge on the record.

The uncharged particles no longer stick to the record and can be shaken or blown off.

The pistol has a range of about two feet and has several advantages over existing methods of removing dust. While conventional record cleaning techniques may remove the dust effectively, the surface is often left sticky which in turn leads to a build-up of dust.

Cleaning cloths have a tendency to dry out and rubbing with them may just increase 'static'. The pistol's crystal is very rugged and will continue to function even after thousands of squeezes.

The device has wider applications, in industry where static is often a problem, for example, in manufacturing textiles or polythene bags. The hand-operated gun is at present being tried out in some firms to see whether an automated version would be appropriate. The device is expected to cost under £5.

LEARN ELECTRONICS WITH THE LADIES



An evening class in electronics at the Ernest Bevin School, Tooting, London, includes among the 40 students the two attractive young ladies pictured above - all the other students are male.

They are Jennifer Raggett and Shirley Hooper, employees of Home Radio Components Ltd of Mitcham. Mr. Alan Sproxton, Managing Director of Home Radio, suggested they joined the evening class and the idea is proving a great success.

1974 B.A.R.T.G. CONVENTION

The 1974 British Amateur Radio Teleprinter Group Convention will be held this year at the village hall, Meopham, Kent, on Saturday, 18th May, from 11.00 to 18.00 hours. The village hall is located on the east side of the A227 road, to the south of Meopham village centre. Transport will meet trains from London at Meopham station until 1 p.m.

Attractions will include - Trade Stands: A live station operating RTTY on the 14 MHz band, under the BARTG call, G4ATG; Lectures on 'Getting Started on RTTY' and 'Advanced Terminal Unit Design'; Bring and Buy Stand; Technical Advice Corner.

Food and refreshments will be available, and there is ample car parking space.

Further details may be obtained from the Hon. Secretary of BARTG, D. F. Beattie, G30ZF, 'Mayerin', Churchway, Aylesbury, Bucks.

MAY 1974



I gather that our friend from the 'Whizzbang TV Flying Doctor Service' does not regard this as a stock fault!

TRANSISTOR GAIN BRIDGE

by R. J. Caborn

A test circuit that is easy to build, calibrate and operate.

THE UNIT DESCRIBED HERE ENABLES THE CURRENT gain of small-signal transistors to be quickly measured. It is based on the circuit simplifications which are given when an emitter follower has an emitter potential equal to half the supply voltage.

HALF VOLTAGE OPERATION

To appreciate basic circuit operation, it will be helpful to look first at Fig. 1, which shows a transistor connected as an emitter follower with RE as its emitter load and RB as its base bias resistor. We will assume for the moment that there is zero voltage drop across the base-emitter junction of the transistor.

The values of the resistors are such that the voltage across RE, shown as VE, is equal to the voltage, VB, across RB. Now, the emitter follower has a current gain of $h_{FE} + 1$, so the current flowing in RE is $h_{FE} + 1$ times the current flowing in RB. Since the voltage across each resistor is equal it follows that the resistor values are in inverse ratio to the currents. So, the value of RB is $h_{FE} + 1$ times the value of RE.

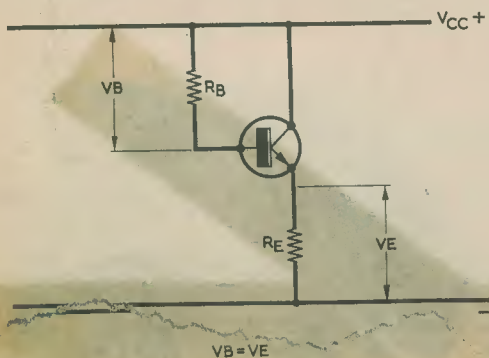


Fig. 1. The resistors here have values which cause emitter voltage to be half supply voltage.

We can use this state of affairs to make up a transistor gain bridge, as illustrated in simplified form in Fig. 2(a). The transistor shown here is the device whose current gain we wish to find, and R_B is now a variable resistor. The two resistors to the right, R_X and R_Y , have equal values, with the result that the voltage at their junction is equal to half the supply voltage. The meter is a centre-zero type and the similarity with a standard Wheatstone bridge can be seen straightway.

We next adjust R_B until the meter reads zero, which means that the transistor emitter is at half the supply voltage. The gain of the transistor, in terms of $h_{FE} + 1$, is then equal to the value given by R_B divided by the value of R_E . In a working version of the circuit we would know the value of R_E and we would have previously fitted R_B with a pointer knob and scale calibrated directly in terms of transistor gain.

We have to consider a few further points before we can bring the basic circuit of Fig. 2(a) up to a fully practical state. First of all, the transistor gain figure provided by the bridge is $h_{FE} + 1$. But unless the gain figure is very low we would introduce little error if we quite simply forgot the '+ 1' term and said that we are obtaining a measure of h_{FE} . We have also assumed that there is zero voltage drop across the base-emitter junction of the transistor being checked. If this is a germanium type the actual voltage drop in the base-emitter junction will be about 0.15 volt, and this will introduce a small error in the readings given by the bridge. Provided that the supply voltage is reasonably high, say 9 volts, this error should not be large enough to be significant.

If, on the other hand, the transistor being measured is a silicon type then there will be a voltage drop of approximately 0.6 volt across the base-emitter junction. This higher voltage can cause an error in bridge readings which is large enough to merit action, and it is necessary to modify the bridge by inserting a silicon diode between R_X and R_Y , as shown in Fig. 2(b). This diode similarly drops 0.6 volt, with the result that the voltages across R_X and R_Y are both equal to half supply voltage minus 0.3 volt. When R_B is adjusted for zero

reading in the meter the voltages across R_B and R_E are also equal to half supply voltage minus 0.3 volt. In consequence, the voltages across R_B and R_E are equal and the transistor gain is given accurately by R_B divided by R_E .

COMPLETE CIRCUIT

A complete working circuit for a practical transistor gain bridge is shown in Fig. 3. In the previous diagrams the transistor under test was an n.p.n. type but we will also want to check p.n.p. types as well. Switch S_3 selects the supply polarity required. There is no need to fit a polarity reversing switch to the meter, M_1 , because this is a centre-zero type and it does not matter which way its needle travels on either side of zero.

R_X and R_Y of Figs. 2(a) and (b) now appear as the equal value resistors R_7 and R_8 . The silicon diode of Fig. 2(b) is now replaced by D_3 and D_4 . When, whilst checking p.n.p. transistors, the upper supply rail is negative, D_3 conducts and drops the requisite 0.6 volt. When, with n.p.n. transistors, the upper rail is positive, it is D_4 which conducts and drops the necessary 0.6 volt. D_3 and D_4 are short-circuited by switch S_2 when measuring germanium transistors, whereupon the circuit behaves in the same manner as that of Fig. 2(a).

There are two back-to-back diodes, D_1 and D_2 , across the meter and R_6 as well, and their purpose is to prevent excessive current flow in the meter when the bridge is off balance. The internal resistance of the meter and the value of R_6 should add up to approximately $6k\Omega$, so that 0.6 volt is dropped across the pair at a current of $100\mu A$. Thus, if the internal resistance of the meter is $1k\Omega$, R_6 could be $5.1k\Omega$. R_6 may be a 5% component. It might be thought that germanium diodes instead of silicon diodes could be used for D_1 and D_2 , since these would enable the value of R_6 to be reduced and thereby allow the bridge to have higher resolution. However, the resolution given with the

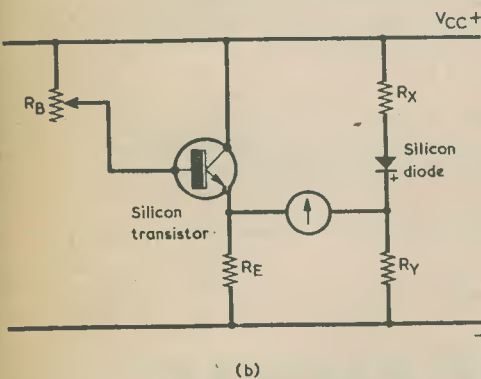
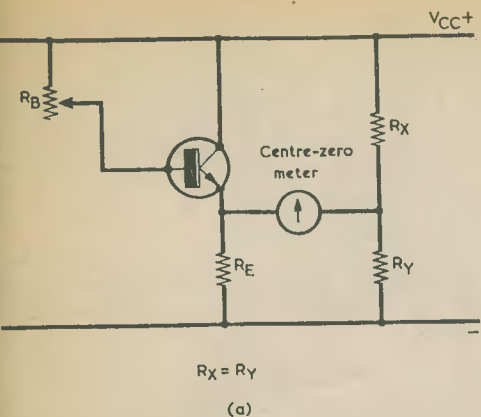


Fig. 2. (a) The basic transistor gain bridge.
(b) A silicon diode is added when balancing the bridge with silicon transistors.

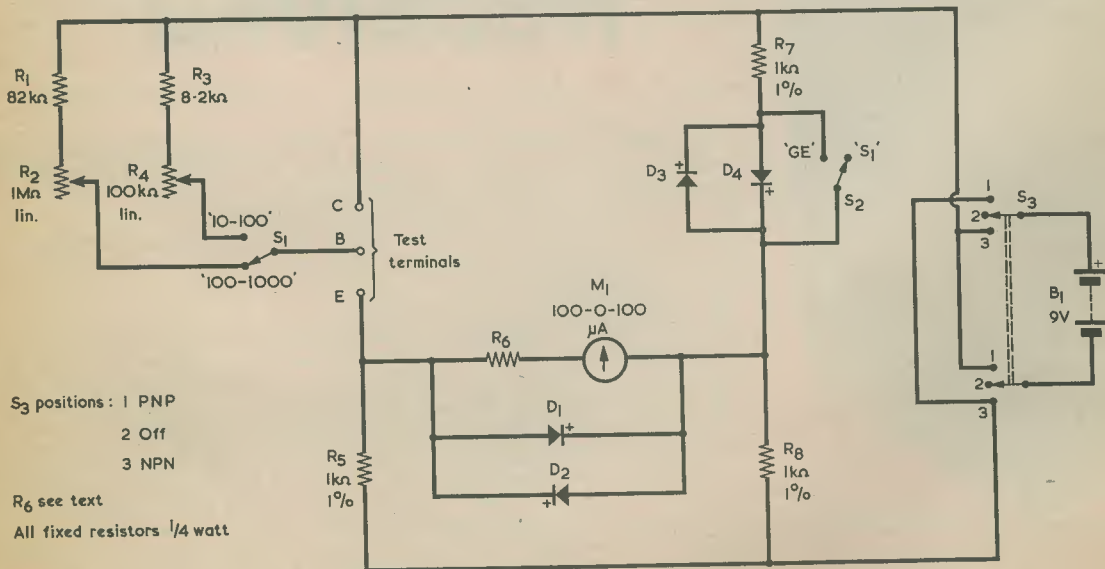


Fig. 3. Complete working circuit for the gain bridge. S_1 selects the desired range, S_2 sets up the circuit for germanium or silicon transistors and S_3 provides the required supply polarity.

circuit as it stands is quite adequate, and the silicon diodes have the advantage of low slope resistance and abrupt turn-on.

The four silicon diodes can be any small silicon rectifier such as the 1N4002.

Resistor RE of the preceding diagrams now appears as R5, and it is a close tolerance component with a value of $1k\Omega$. This value means that an emitter current of the order of 4 to 4.5mA flows when the bridge is balanced, and this should be high enough to ensure that no errors result due to leakage current in the transistor being checked.


The base resistance is given by R1 and R2 in series, or by R3 and R4 in series, according to the position of S1. The first of these pairs of resistors allows gain measurements from 100 to 1,000, and the second allows gain measurements from 10 to 100. The two potentiometers are fitted with scales which are calibrated with the aid of an ohmmeter. The ohmmeter is connected across R1 and R2 for calibrating the 100 to 1,000 range, and across R3 and R4 for calibrating the 10 to 100 range. The gain figure is the same as the number of kilohms in the resistors. When R2 is adjusted so that R1 plus R2 gives $100k\Omega$, the corresponding hFE figure is 100, and so on.

The test terminals for the transistor whose gain is being determined may consist of three terminals fitted with miniature insulated crocodile clips.

In use, the transistor to be checked is connected to the test terminals, S2 is set to 'Ge' or 'Si' as applicable, and S3 set to give the required polarity. The bridge is then balanced by R2 or R4, according to which of these allows a zero reading to be given in the meter, after which the hFE of the transistor is read from the appropriate potentiometer scale.

The maximum base current which can flow in the test transistor is limited by R1 and R3. If the transistor is turned hard on during a measurement, the maximum emitter current that flows is limited by R5 with R8 (coupled to it by D1 or D2 according to circuit polarity) effectively in parallel. This maximum current is approximately 18mA. If it is felt undesirable to allow even this low current to flow through the transistor, initially set R2 and R4 to the highest gain figures and S1 to the '100 to 1,000' range. Then switch on and take R2 down from 1,000 to 100 until the zero reading is observed. If no zero reading is given, switch S1 to '10 to 100' and repeat with R4. This procedure means that base current increases from an initial low value up to the level at which the bridge balances. ■

CATALOGUE RECEIVED

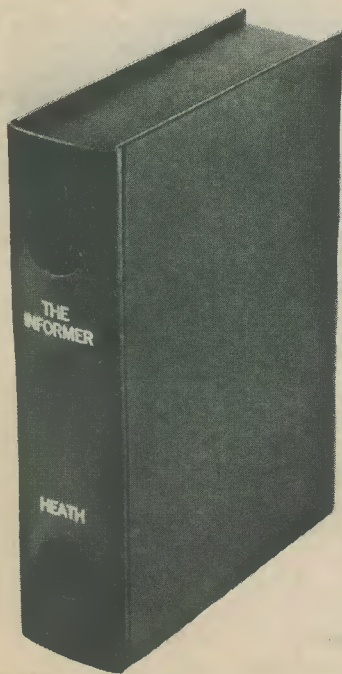

A new addition to the Heathkit range, the 'Informer' ultrasonic Intrusion Alarm is designed to have the appearance of a book.

Currently available is the latest Heathkit catalogue from Heath (Gloucester) Ltd., Bristol Road, Gloucester, GL2 6EE. This company also has a showroom at 233 Tottenham Court Road, London, W.1.

The catalogue lists an exceptionally wide choice of electronic kits. To be found amongst these are high fidelity receivers, tuners, amplifiers and speakers, amateur receivers, transceivers and transmitters, and a solid state monochrome television receiver. Further items are electronic calculators, a metal detector and an electronic digital clock. The section devoted to test equipment gives details of signal generators, oscilloscopes, multimeters and digital frequency counters. Amongst the more unusual items are an ultrasonic cleaner, an electronic thermometer and a complete weather station.

The catalogue also includes a particularly interesting addition to the Heathkit range, this being the 'Informer' Intrusion Alarm type GD-39. As can be seen from the accompanying photograph, this unit is designed to give the appearance of an unobtrusive book, and it may be left on a table or bookshelf in any premises it is desired to protect. Behind the two decorative circles on the spine are an ultrasonic transmitter and receiver. When the device is switched on, the room in which it is placed is filled with a frequency of 41kHz, this being reflected by walls and furniture, etc., back to the receiver. Any movement within the surveillance field is at once detected by the receiver, which triggers an alarm after 30 seconds.

The catalogue is available free from Heath (Gloucester) Ltd., at their Gloucester address, as also is a Technical Consultation service both before and after purchases.

MAKING PRINTED CIRCUIT BOARDS

How to make up printed circuit boards for your own or for published designs

by Arthur C. Gee, G2UK

IT IS BECOMING COMMONPLACE NOWADAYS FOR DESIGNERS of home-constructor radio and electronic equipment to produce their designs based on a printed circuit board layout. A typical example which comes to the writer's mind is of fairly recent origin, and it appeared in the December 1972 issue of this journal in the "Transistorised Oscilloscope" by R. A. Penfold. In Part 1 of that article, the circuit of the X Amplifier is shown in Fig. 8 and a full size reproduction of the prepared printed circuit board is shown in Fig. 9. These two figures are reproduced herewith as Figs. 1 and 2, so that readers can see just what we are talking about. The photograph shows a completed printed circuit board made to this design according to the procedure outlined in this article. Similar theoretical circuits and the corresponding printed circuit board layouts were given in Part 2 of the earlier article, these being for the time-base, the Y amplifier and the sync amplifier.

BOARD PREPARATION

Generally speaking, it is necessary for the constructor of such designs to make the printed circuit boards up himself. Occasionally, if they think the demand is going to be great enough, some commercial firms will make and market printed circuit boards for a published design, and they usually announce the fact by means of an advertisement or note in the journal concerned. Very occasionally you may find a firm who will undertake to make up "1-off" printed circuit boards on request. But this is likely to be pricey, and most constructors will prefer to make up the boards themselves. How then, do we go about it?

The printed circuit board, or "laminate", consists of a sheet of insulating material on one side of which is affixed a thin layer of copper foil. A piece of the board is cut to the shape and size required by the design and


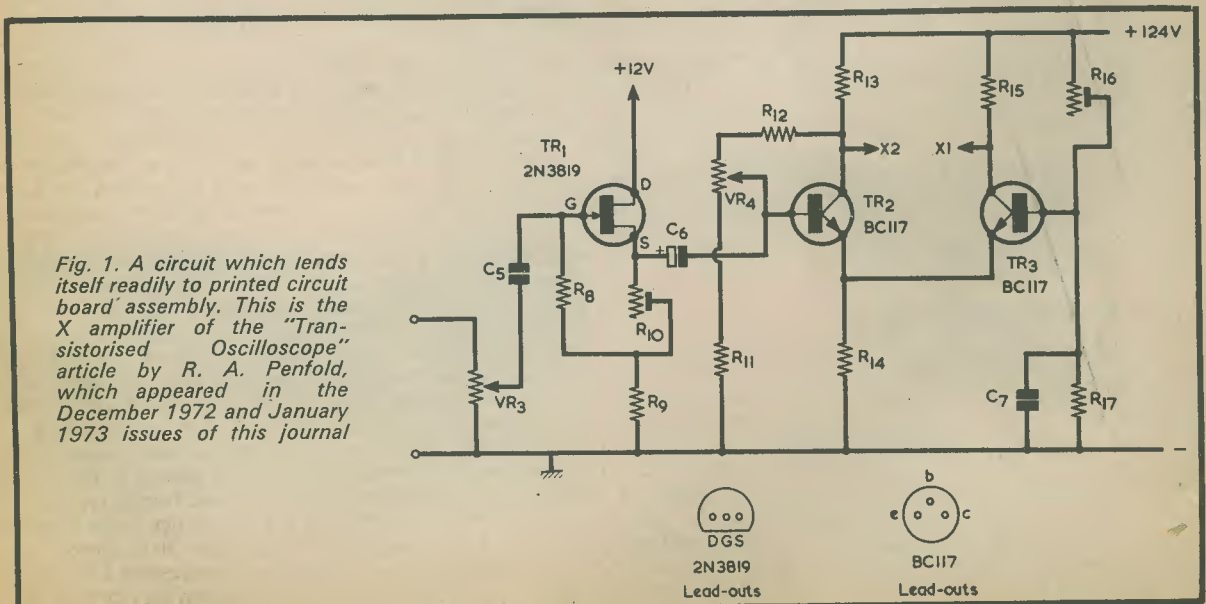


Fig. 2. The copper side of the board employed for making up the X amplifier. This is also reproduced from the earlier article. It is shown full-size and the copper pattern may be traced directly

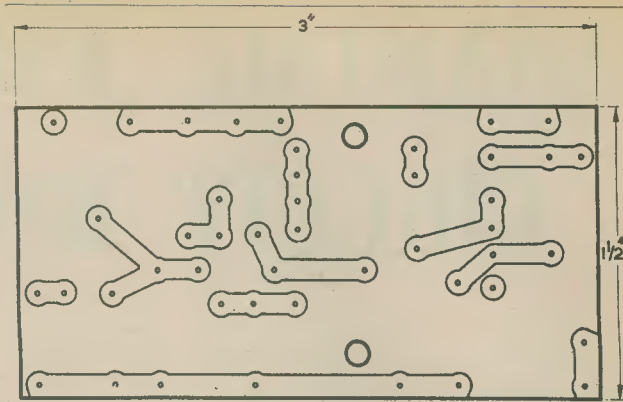

the required copper pattern is drawn on it, using an ink or paint material which is impervious to the etching fluid. The copper which is not required is etched away by immersing the board in the etching fluid. As an example, Fig. 2 shows the copper pattern illustrated in Fig. 9 of the previous article. If it is simple enough, the pattern can be drawn on the copper free-hand, alternatively it can be traced using duplicating paper. Very complicated circuit designs can be reproduced on the copper by photographic means, but such a method is outside the scope of the present article.

Special etch-proof fluid is available for marking the copper foil, but more of this later.

The insulating material forming, so to speak, the "backing" of printed circuit boards can be one of a variety of materials. Cheap boards employ a brown phenolic material which is referred to in engineering circles as "s.r.b.p.", the letters standing for "synthetic resin bonded paper". Amongst home-constructors, this material is perhaps better known as "Paxolin". Better quality boards use glass fibre, and for special purposes, such as v.h.f. or u.h.f. projects, laminate of epoxy resin can be obtained at greater expense. These special laminates are often hard to cut and drill. Cutting the laminate to shape is best done with a fine toothed, metal saw. Don't try to use an ordinary hack saw as this is too coarse and will bind badly. You will also need one or two fine twist drills to make the holes in the board through which the printed circuit boards component leads pass.

Laminate for making up printed circuit boards can be bought in various sizes from most component suppliers. Generally speaking it is sold in stock sizes and from these you will have to cut out the shape and size you need for the project.

ETCH-PROOF MATERIALS

Now to return to the etch-proof materials we use for marking out the copper we do not want to be etched away.

Special "resist" paint or varnish, specifically made up for this purpose, can be purchased. This can be painted on with an artist's fine brush. There are also "marking pens", and the makers of one such item describe their product as a "slim nylon-tipped marker, charged with a free flowing etch resistant ink offering complete immunity to attack from ferric chloride and other usual etchant solutions". The particular one used by the

writer, which works very well, is that made by Decon Laboratories Ltd., Ellen Street, Portslade, Brighton; and is called the Decon Dalo 33 P.C. Marker. Another useful resist material is automobile touch-in paint, the small brush included in the pack being fine enough for making quite neat printed circuit boards.

ETCHING SOLUTION

So to re-cap. We have obtained our piece of laminate, cut off the shape and size we want, traced on the copper foil the copper pattern we require and have painted over this pattern with the resist fluid. We now leave the resist fluid to dry until it is quite hard, and we must next give some thought to the etching fluid.

The function of the etching fluid is to dissolve away all the copper foil we don't need, so that we are left with the copper circuitry only. First of all, we need a small dish to take the printed circuit board for etching, just large enough to hold the board so that it can be just covered with the etching fluid. The ideal utensil for this purpose is a photographic plate developing dish - if you can still find one. Failing this, large glass Petri dishes as used in bacteriological laboratories or a deep saucer can be used. Receptacles of glass, china or plastic are suitable; but not metal or enamel ones as these will also be etched away! Again, various fluids are available for etching. Commercially produced etching fluids can be purchased but the most convenient one to use is a solution of ferric chloride, which one can make up



The copper side of a practical printed circuit board made up to the pattern in Fig. 2

oneself, from crystals, as required. It is easier, more convenient and safer to store away ferric chloride in crystalline or powdered form, than as bottles of etching fluid. Ferric chloride can be purchased from some radio component stores or from a pharmaceutical store, and a suitable etching fluid can be made up by dissolving 3oz. of the crystals in a quarter of a tumbler of tap water.

Make up the solution in an old jam jar which will not be required again, and throw the jar away after use. Add the ferric chloride slowly to the water, as a good deal of heat is produced as it dissolves. If, alternatively, you pour the water on the crystals they may "spit" and fly around, and this can be dangerous because ferric chloride is very corrosive. You certainly don't want it on the table top or around the sink; still more, you don't want it on your skin or, worse still, in your eyes. So be careful and treat both the crystals and the solution with respect! If you do get it where it should not be, wash it off instantly with copious quantities of warm water.

Having made up the solution, place the printed circuit board in the dish, copper side up, and cover with the ferric chloride solution. Again remember that the solution is corrosive, so keep your fingers out of it! Agitate the solution slowly by rocking the dish. The unwanted copper should be etched away in 20 minutes or so. When etching is complete, remove the board with a pair of tweezers, wash it thoroughly in tap water and leave it to dry.

SOLVENT

Next, remove the resist with a suitable solvent such as paint remover, nail varnish remover, acetone or, if a proprietary resist fluid has been used, whatever remover its manufacturer recommends. You'll then see the circuitry in the copper foil on the printed circuit board. Clean up with abrasive powder, such as is used for domestic purposes, and the printed circuit board is almost complete. Not quite, however, for we still have to drill the holes for the component leads. These will be indicated on the original design and usually present no problems.

Finally, give the board another good clean-up and, if necessary, straighten up the edges and corners of the copper foil sections with a scalpel or sharp fine-pointed knife. If desired, a coat of flux varnish can then be painted over the whole surface on the copper side to protect the copper, and to act as a soldering flux when the board is wired up.

It is possible to buy kits of the materials required for making printed circuit boards. The writer recently acquired one which contained a tube of resist paste, a small spatula for spreading it on to the copper foil, a bottle of resist remover, a bottle of etching fluid, a tube of polishing powder to clean up the copper after etching, two pieces of phenolic copper clad laminate for practising on, two sheets of tracing paper, and a stencil knife and a hole pricker to assist in transferring the tracing design onto the copper. These were all nicely packed in a plastic container, the lid of which could be used as the receptacle for the etching if you wished. Good, well illustrated, instructions were included. It was made in Japan and called the Hayato PK3 Printed Circuit Handicraft Kit. You may find one in your radio components store. It is a convenient way of getting all the bits and pieces you need for making printed circuit boards at one go, though it would probably be cheaper to shop around and buy the items separately. ■

MAY 1974

RADIO & ELECTRONICS CONSTRUCTOR

• JUNE ISSUE FEATURES

SIMPLE SQUARE WAVE GENERATOR

Incorporates a single integrated circuit, this square wave generator offers outputs up to 1 volt peak-to-peak at frequencies from 200Hz to 20kHz.

★ ★ ★

SHORT WAVE CRYSTAL SET

Employs a single germanium diode for detection, this receiver gives headphone reception of the more powerful transmissions over a wide range of short wave broadcast bands.

★ ★ ★

6+6 STEREO AMPLIFIER Part 2 - Conclusion

Deals with the construction and setting-up of this attractive full solid-state stereo amplifier.

★ ★ ★

PLUS

MANY OTHER ARTICLES

AND


DATA SHEET No. 87

Television Transmission Frequencies II

PRICE 22p

Copies may also be obtained direct from the Publishers, 28p including postage. Published by Data Publications Ltd., 57 Maida Vale, London W9 1SN.

RADIO & ELECTRONICS CONSTRUCTOR

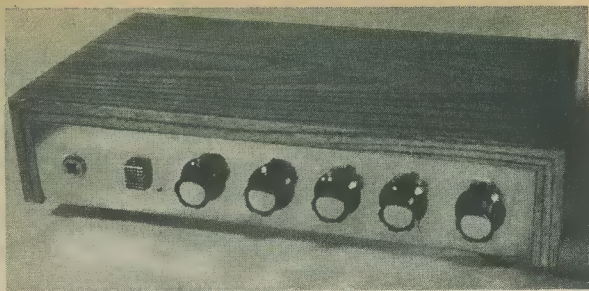

Front view of the completed amplifier.

6 + STEREO AMPLIFIER

SOME OF THE POPULAR INEXPENSIVE RECORD DECKS fitted with a ceramic or crystal stereo cartridge are capable of a surprisingly high quality of reproduction. The amplifier described in this and next month's issue was primarily designed for use with such a unit. It feeds two 8Ω loudspeakers, whereupon a complete stereo record player system is made available.

It was also a design requirement that the amplifier should have an input suitable for use with a radio tuner. As it happens, the input for the pick-up is at a sensitivity and impedance - 200mV and $1.5\text{M}\Omega$ - which are suitable for most tuners and therefore only one input socket is provided. The input impedance is really somewhat higher than is required for a radio tuner but, since it is on the high rather than the low side, this point is of no real consequence.

A maximum continuous power output of just slightly less than 6 watts r.m.s. per channel (both channels operating) is available into 8Ω loads. Speakers of 15Ω impedance can also be used, and the amplifier will give a lower distortion figure with these as it is working into lighter loads, but the maximum r.m.s. output will only be about 3 watts per channel. The peak power per channel into 8Ω loads is approximately 10 watts.

The amplifier is very compact, measuring 12 by 6 by $2\frac{1}{2}$ ins., excluding the control knobs and feet. There are five rotary controls, these being for on-off switching, balance, volume, bass lift and cut, and treble lift and cut. An output for a pair of stereo headphones is provided on the front panel. Excluding the power supply section the circuit uses 21 semiconductor devices, including 2 f.e.t.'s and 16 silicon transistors.

PRE-AMPLIFIER

A circuit diagram of one channel of the amplifier is shown in Fig. 1. In order to obtain the correct frequency response from a crystal or ceramic cartridge it must be matched into an impedance of 1 to $2\text{M}\Omega$. The amplitude of the signal from a cartridge of this type is quite high, and can be several hundred mV peak-to-peak on loud passages. The requirements of the pre-amplifier are, therefore, high input impedance, the capability to handle large signals with low distortion and, of course, low noise.

Either a Darlington pair in the emitter follower mode


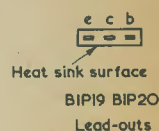
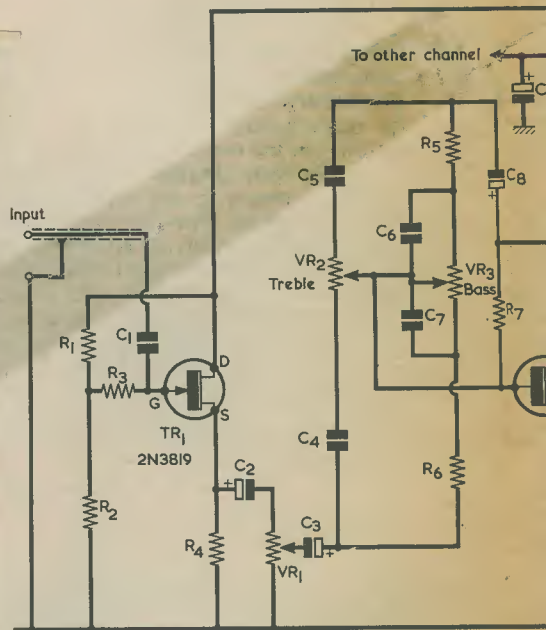


Fig. 1. Complete circuit diagram of one channel of the amplifier.

+ 6 STEREO AMPLIFIER

This is the first of a 2-part series describing the construction of a fully solid-state stereo amplifier having continuously variable treble and bass boost and cut controls. The concluding article, to appear next month, will describe the procedures of construction and setting up.

By A. P. Roberts

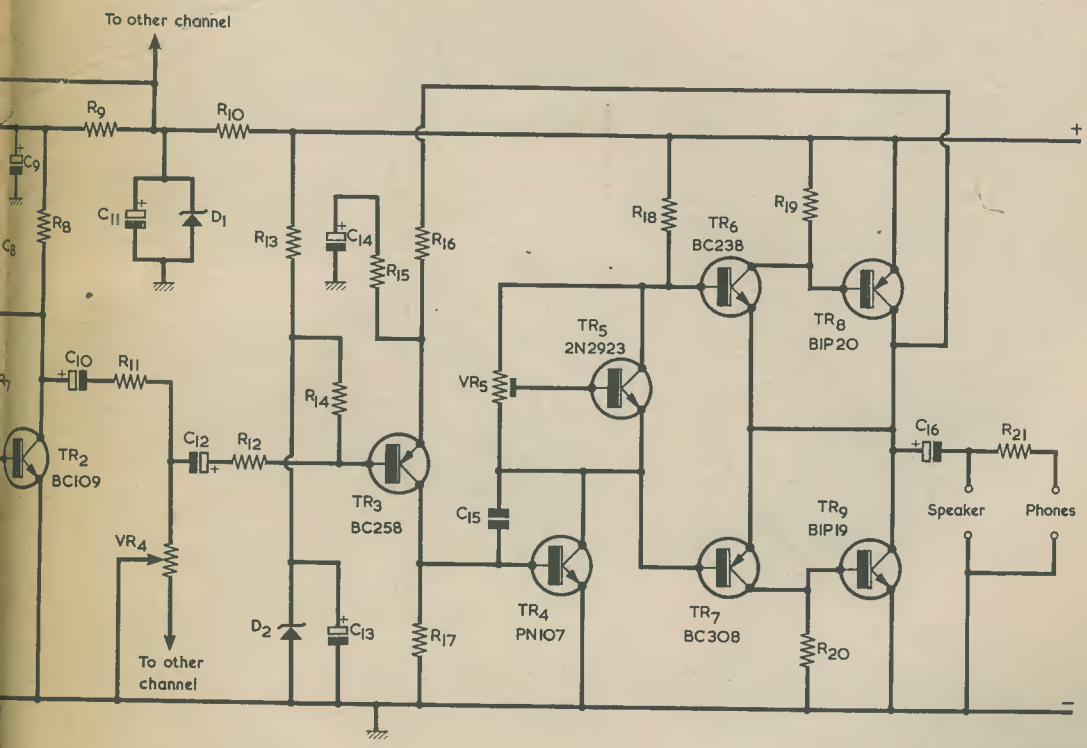

- 2N3819
Lead-outs
- BC109
Lead-outs
- BC258
Lead-outs
- BC238 BC308
Lead-outs
- PN107
Lead-outs

Diagram for one channel of the amplifier. Apart from R9, R10, VR4, C9, C11 and D1, components are duplicated in the amplifier for the other channel.

6 + 6 STEREO AMPLIFIER

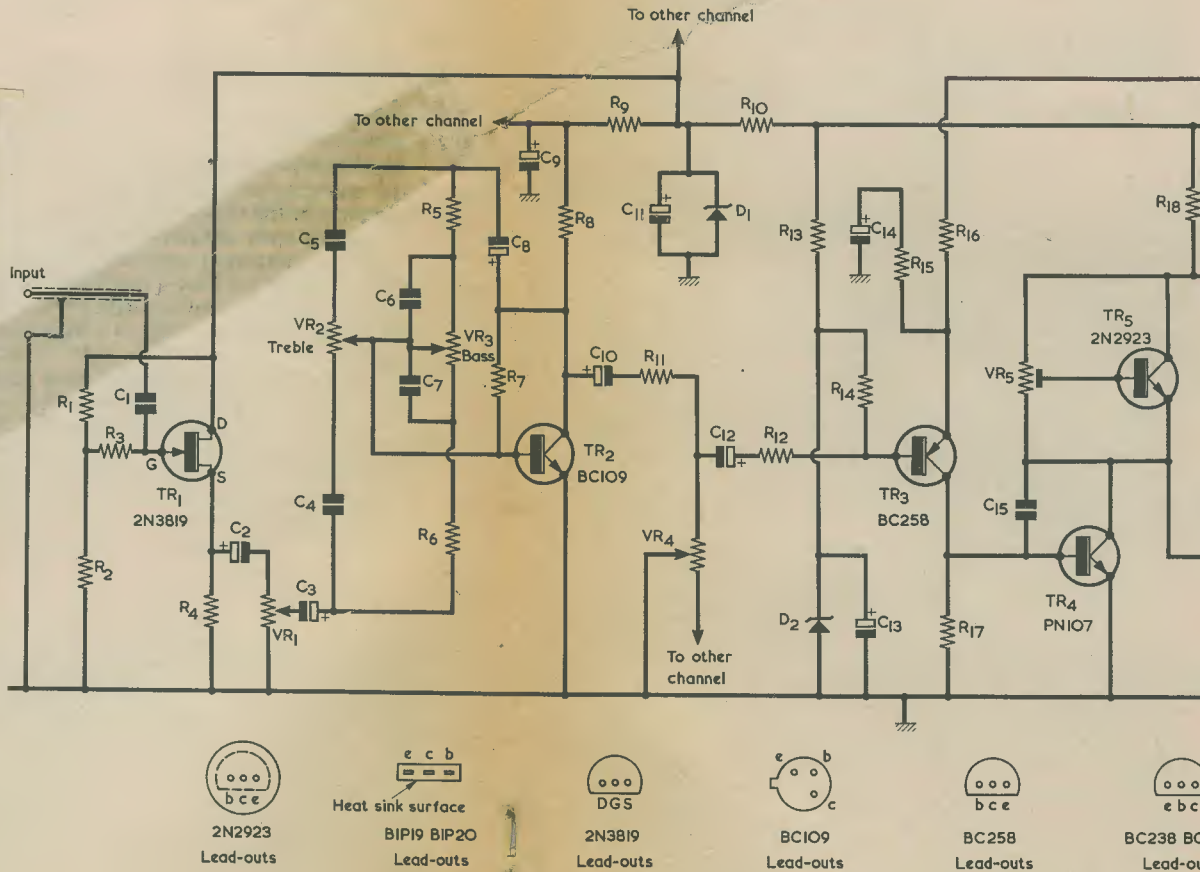


Fig. 1. Complete circuit diagram for one channel of the amplifier. Apart from R9, R10, VR4, C9, all components are duplicated in the amplifier for the other channel.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1, R101	270k Ω
R2, R102	150k Ω
R3, R103	1.5M Ω
R4, R104	10k Ω
R5, R105	10k Ω
R6, R106	10k Ω
R7, R107	2.7M Ω
R8, R108	10k Ω
R9	4.7k Ω
R10	1.5k Ω
R11, R111	4.7k Ω
R12, R112	2.2k Ω
R13, R113	33k Ω
R14, R114	100k Ω
R15, R115	22 Ω
R16, R116	1k Ω
R17, R117	1.2k Ω
R18, R118	2.2k Ω
R19, R119	820 Ω
R20, R120	820 Ω
R21, R121	100 Ω
VR1, VR101	5k Ω dual-gang potentiometer, log
VR2, VR102	50k Ω dual-gang potentiometer, linear
VR3, VR103	50k Ω dual-gang potentiometer, linear
VR4	50k Ω potentiometer, linear
VR5, VR105	5k Ω pre-set, sub-miniature skeleton, horizontal mounting

Capacitors

C1, C101	0.047 μ F, polyester, side wires
C2, C102	15 μ F electrolytic, 16 V.Wkg. (see text)
C3, C103	12.5 μ F electrolytic, 16 V.Wkg.
C4, C104	0.0068 μ F polyester
C5, C105	0.0068 μ F polyester
C6, C106	0.047 μ F polyester (see text)
C7, C107	0.047 μ F polyester (see text)
C8, C108	10 μ F electrolytic, 10 V.Wkg.
C9	220 μ F electrolytic, 16 V.Wkg.
C10, C110	10 μ F electrolytic, 10 V.Wkg.
C11	220 μ F electrolytic, 16 V.Wkg.
C12, C112	12.5 μ F electrolytic, 16 V.Wkg.
C13, C113	12.5 μ F electrolytic, 16 V.Wkg.
C14, C114	150 μ F electrolytic, 25 V.Wkg.
C15, C115	0.005 μ F ceramic
C16, C116	1,500 μ F electrolytic, 30 V.Wkg.
C17	5,000 μ F electrolytic, 30 V.Wkg. (2 x 2,500 μ F wire-ended in parallel, see text)

C18 3,000 μ F electrolytic, 30 V.Wkg. (2 x 1,500 μ F wire-ended in parallel, see text)

Inductors

T1 Mains transformer, secondary 9-0-9 volts at 1 amp, Osmabet type MT9V.
L1 Smoothing choke (see text)

Semiconductors

(TR8, TR9 and TR108, TR109 are matched pairs)
TR1, TR101 2N3819
TR2, TR102 BC109
TR3, TR103 BC258
TR4, TR104 PN107
TR5, TR105 2N2923
TR6, TR106 BC238
TR7, TR107 BC308
TR8, TR108 BIP20
TR9, TR109 BIP19
D1 13 volt zener diode type BZY88C13V
D2, D102 10 volt zener diode type BZY88C10V
D3-D6 Silicon bridge rectifier, 2 amp 100 p.i.v.

Switch

S1 D.P.S.T. toggle, rotary

Neon

NE1 240 volt panel-mounting neon assembly with integral resistor


Miscellaneous

5 control knobs
Veroboard panels 0.1 in. matrix (see text)
2 loudspeaker sockets (3-way DIN)
1 input socket (3-way DIN)
1 stereo jack socket, $\frac{1}{4}$ in.
2 TO3 mica insulating washers (see text)
Ferrite rod, $1\frac{1}{2}$ by $\frac{1}{4}$ in. dia. (see text)
10 yards of 24 s.w.g. enamelled copper wire (see text)
18 s.w.g. aluminium sheet
4 rubber feet
 $\frac{1}{2}$ in chipboard
Plastic veneer (see text)
Screened cable, grommets, etc.

or an f.e.t. in the source follower mode could be employed. An f.e.t. source follower has been chosen for the present design as this gives a lower noise level than would be the case if bipolar transistors were used.

The input circuit employs an offset gate biasing method, the appropriate components being R1, R2 and R3. C1 is the input coupling capacitor and R4 is the source load resistor. TR1 has a voltage gain of slightly

less than unity, but the amplitude of the signal from the cartridge is sufficiently high to drive the following power amplifier without any intermediate voltage amplification. TR1 mainly functions as a buffer stage to give an adequate input impedance. The output from TR1 is fed to the volume control, VR1, via C2. The slider of the volume control then couples into the tone control circuit by way of C3.

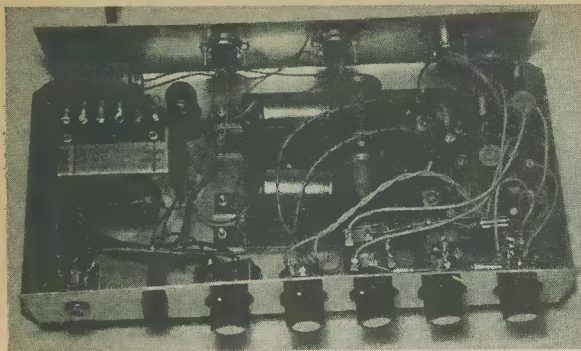

The amplifier with its cover removed. The components are mounted on one large Veroboard panel for the power amplifiers, and on two smaller Veroboard panels for the pre-amplifier and tone control sections respectively.

TONE CONTROLS

An active tone control system is used, and this has separate bass and treble controls. The stage is built around TR2, which is a common emitter amplifier. Normally one would expect this to have a very high voltage gain, but such is not the case here as a high degree of negative feedback is introduced via the tone control networks.

VR2 is the treble control. This works independently of the bass control. With VR2 slider at the bottom of its track, treble signals are considerably boosted. This is because treble signals are at higher frequencies than the middle and bass signals, and will therefore find a much easier path through C4 to the base of TR2. When VR2 slider is at the top of its track, treble signals are attenuated. The treble signals still have to pass through C4 to reach the base of TR2, but they now have to pass through the whole track of VR1, at the top end of which there is negative feedback, from TR2 collector, of the treble signals via C5. Thus there is maximum treble boost when the slider of VR1 is at the bottom end of its track and maximum treble cut when VR1 slider is at the top of its track. Intermediate settings of VR1 slider give intermediate levels of boost or cut.

VR3 is the bass control. When its slider is at the bottom end of its track C7 is virtually short-circuited and there is negative feedback of the middle and treble frequencies by way of R5 and C6. This results in bass boost. When VR3 slider is at the top of its track, C6 becomes virtually short-circuited. Negative feedback is still provided via R5 but this is not frequency selective. The signal from C3 now has to pass through R6, VR3 track and C7 to reach the base of TR2. C7 will offer a lower impedance for the middle and treble frequencies than it will for the bass signals, and so the circuit then gives bass cut. As with VR2, intermediate settings of VR3 will give intermediate levels of boost and cut. In both cases, the extreme instances have been described as these best demonstrate how the controls work.

Capacitor C8 has no effect on the tone control circuits as its capacitance is much higher than the frequency selective capacitors C4 to C7. It is merely a d.c. blocking component which prevents the flow of direct current through the tone control network.

POWER AMPLIFIER

The power amplifier employs a basic circuit configuration which is now used in many hi-fi amplifiers. The output stage is Class B push-pull.


There are two pairs of common emitter amplifiers in the output stage, one pair being TR6 and TR8 and the other pair being TR7 and TR9. Since in each case the emitter of the first transistor is connected to the collector of the second transistor there is 100% negative feedback in both pairs of transistors. They therefore produce a voltage gain of almost exactly unity, but have an extremely high current gain. The output impedance of this arrangement is sufficiently low to enable an 8Ω speaker to be driven directly via C16.

The output stage is fed by a common emitter amplifier TR4, the collector load for which is R18. TR5 and VR5 are employed to set, and when set to stabilize, the small biasing current required by the output stage. This current reduces crossover distortion to an unnoticeable level.

TR5 helps to stabilize against thermal shifts in the output transistors in the following manner. As the output transistors warm up they tend to draw a higher quiescent current. The heating of the output transistors causes the air inside the amplifier case to warm up also. This affects TR5 and it conducts more heavily, thereby reducing the voltage between the bases of TR6 and TR7 and, in consequence, the output stage quiescent current.

The input transistor for the power amplifier, TR3, is in another common emitter stage. This is a p.n.p. transistor with its emitter taken, via the bias stabilizing resistor R16, to the collectors of the output transistors. This gives the overall power amplifier circuit 100% d.c. negative feedback. C14 provides an a.c. bypass but R15 limits its effect, allowing the power amplifier to have a relatively low a.f. gain. The considerable amount of a.c. feedback which is still present produces noise and distortion levels which are both very low.

An unstabilized supply is used, and the various amplifier circuits have their own built-in stabilization networks. R10, C11 and zener diode D1 form a circuit which provides a stabilized supply voltage for the pre-amplifiers and tone control networks. As already stated, the power amplifier has unity d.c. voltage gain. The base of TR3 is stabilized by being returned via R14 to the zener diode D2, whereupon the collectors of TR8 and TR9 become d.c. stabilized in consequence. C13, across D2, removes any noise which might be introduced here and which could otherwise find its way into the amplifier.

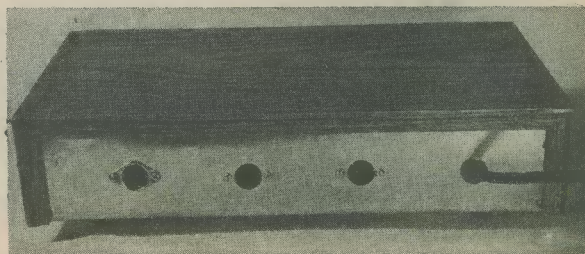

The rear of the amplifier has a neat uncluttered appearance.

With circuits of this type, which use large amounts of negative feedback, in the interests of stability it is normal to roll off the upper frequency response, which otherwise extends well into the r.f. spectrum. This is the purpose of C15.

An output suitable for a pair of headphones is provided, R21 giving the necessary attenuation.

Fig. 1 shows the circuit for one amplifier channel. This is duplicated in the other channel except that the latter does not have D1, C11, R9, R10 and C9. Similarly the balance control, VR4, is shared between the two channels. VR1, VR2 and VR3 are each one section of a 2-gang potentiometer, the remaining section being incorporated in the same circuit position in the other channel. Component numbering in the other channel commences at 101, whereupon R101 occupies the same circuit position as R1, and so on. It is not very important whether the amplifier shown in Fig. 1 is in the left channel or the right channel. In the author's amplifier it is in the right-hand channel.

POWER SUPPLY

The circuit of the power supply is given in Fig. 2. The 9-0-9 volt secondary of transformer T1 gives 18 volts a.c. overall, and this is rectified by D3 to D6. The smoothing components are C17, L1 and C18. Both C17 and C18 consist of two equal-value capacitors in parallel. So far as C17 is concerned this aids construction, although a single 5,000 μ F component could be used if it has wire lead-outs at the ends and fits physically into the layout.


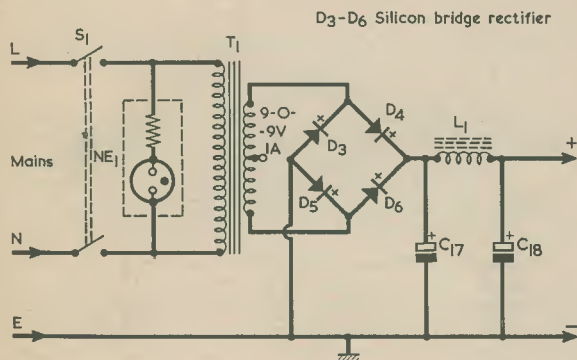


Fig. 2. The circuit of the power supply section.

The two capacitors which make up C18 are fitted separately on the amplifier board, one being close to the power amplifier on one channel and the other being close to the power amplifier on the other channel. In the type of amplifier employed here, where high currents are involved, instability can easily arise and it is advisable to have a large supply bypass capacitor mounted close to each amplifier. Thus, the two capacitors which form C18 carry out this function as well as providing smoothing.

A low value resistor was originally used in the position now occupied by L1. The ripple voltage was rather high, however, and a very marked improvement can be given by employing a choke here. A suitable commercially made choke seemed difficult to obtain,

and a home-made component was employed instead. This was wound on a small piece of ferrite rod and, whilst it is admittedly not very efficient, it is simple and inexpensive and works quite well in practice with this particular amplifier. It is probable that the ferrite rod saturates at the higher supply currents but, since these correspond with heavier output levels, any consequent reduced efficiency in the choke does not make any practical difference.

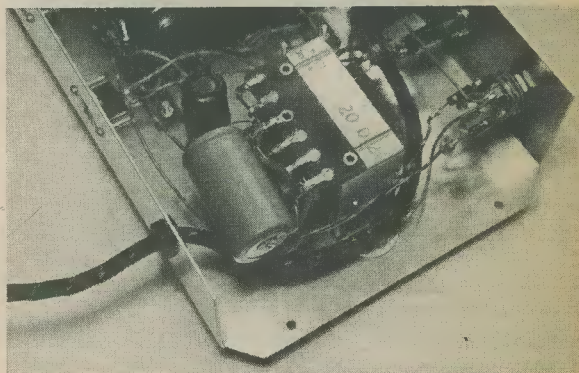

A view of the power supply section. The ferrite rod choke, vertical to the chassis deck, can be seen alongside the mains transformer. Note the two resistors soldered to the output jack tags.

COMPONENTS

The components are all standard types. The mains transformer, T1, is an Osmabet component type MT9V, and is listed by Home Radio under Cat. No. 4/TM55. The transistors type BC258 and PN107 are available from Electrovalue Ltd., 28 St. Judes Road, Englefield Green, Egham, Surrey. The BC238 and BC308 may be obtained from Henry's Radio Ltd., and the 2N2923 from Bi-Pak. Bi-Pak can also provide the B1P19 and B1P20 as a matched pair.

In the prototype, C2 and C102 were tantalum capacitors. Tantalum types were employed because these two capacitors connect to adjacent holes on a 0.1 in. Veroboard panel and the small physical size of tantalum capacitors enables them to be wired in more easily. Miniature aluminium electrolytic capacitors may be employed instead, of course, although the wiring may then be a little more difficult to carry out. Similarly for reasons of small size, C6, C7, C106 and C107 were disc ceramic capacitors. It is in order to use such capacitors in these positions provided that their capacitances are known to be close to their nominal values. Usually, high value disc ceramic capacitors are intended for r.f. bypass functions and have a very wide tolerance on value.

The full Components List accompanies this article. Quite a number of the items listed here will be discussed in the concluding article, to be published next month, with the consequence that any outstanding queries on the components will be satisfied when the next issue appears.

I.C.-TRIAC TIMER

By P. Manners

Coupling an integrated circuit timer directly to an a.c. mains triac.

A RECENT NEWCOMER TO THE INTEGRATED CIRCUIT scene is the '555' 8-pin dual-in-line timer. This has appeared as the NE555V, the LM555CN and, most recently, as the R.S. Components '555 Type' timer. The last version of the i.c. can be obtained from any retail supplier of R.S. Components products.

BASIC CIRCUIT

The '555' devices just mentioned all have identical pinning, and can be used in similar timing circuits. The devices may also be employed as continuously running multivibrators, but this aspect of '555' operation will not be considered in the present article.

There are several basic circuits in which a '555' i.c. may be employed as a timer, and a typical example of one of the simplest is shown in Fig. 1. In this diagram the timer is triggered by momentarily closing the push-button. The negative pulse thus applied to pin 2

causes an internal flip-flop to change states and to turn off an internal transistor which previously short-circuited the timing capacitor, CT. Capacitor CT now commences to charge via RT. Also, as soon as the flip-flop changes over, the output at pin 3 goes positive. When the voltage across CT reaches approximately two-thirds of the supply potential the internal circuitry in the i.c. turns the flip-flop back to its initial state, causing the output to go low again and once more turning on the internal short-circuiting transistor which discharges CT. The circuit is then ready for another timing run.

As is to be expected, the internal circuitry in the i.c. is more complex than this simple explanation of its operation would appear to indicate. In addition to several diodes and resistors, the i.c. incorporates about two dozen transistors.

The output at terminal 3 is capable of providing currents of up to 200mA, and the total dissipation rating for the i.c. is 600mW. The R.S. Components recommended range of supply voltage is 4.5 to 15 volts. Other manufacturers specify an absolute maximum of 18 volts. Operating temperature range is 0°C to +70°C.

The load in Fig. 1 is not specified, and this may be resistive or inductive. A resistive load could be given by a subsequent transistor or t.t.l. circuit. An inductive load would consist, typically, of a relay coil. When a coil is used as a load it is essential to add the diode which is shown connected into circuit via broken lines in Fig. 1. This diode prevents the formation of high reverse voltages when the supply to the relay coil is turned off, and such reverse voltages could damage the integrated circuit.

The inset in Fig. 1 shows the pinning for the device. This is a top view, with the pins pointing away from the reader. Pin 1 is 'ground', or negative supply input, whilst pin 8 is Vcc and takes the positive supply. Pin 2 is the trigger input and, as already mentioned, a negative pulse here changes over the state of the internal flip-flop. Pin 3 is the output, and is derived from two internal transistors in a totem-pole configuration. Pin 4 is a 'reset' input; if a negative pulse is applied to this terminal during a timing run the transistor which short-circuits the timing capacitor is turned on, the output falls to its low level and the timing run recommences at the end of the pulse. For simple timing

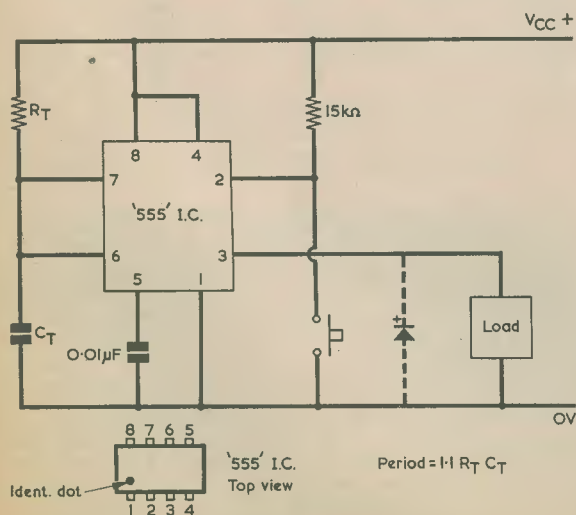


Fig. 1. A basic circuit incorporating a timer i.c. of the '555' type.

applications the reset facility is not required, and pin 4 is returned to the positive supply rail, as in Fig. 1. Pin 5 couples to the internal control reference voltage which determines the end of the timing period. In Fig. 1 this terminal is merely bypassed to the negative rail via a $0.01\mu\text{F}$ capacitor. Pin 6 is the 'threshold' input, and this causes the timing period to come to an end when the voltage applied to it from the timing capacitor is at the requisite level. Pin 7 couples to the internal transistor which, before and after the timing period, short-circuits the timing capacitor.

The length of a timing period is equal, in seconds, to 1.1 times the product of RT and CT in ohms and farads (or in megohms and microfarads). Timing periods can range from microseconds up to an hour or more. Since the threshold level at which the device causes the timing period to cease is a fraction of the supply voltage there is no need for a stabilized supply, although the supply potential should remain steady during a timing period.

Apart from its alternative use as a multivibrator, the timer i.c. can appear in more complex timing circuits than that shown in Fig. 1. The latter has, however, the advantage of considerable simplicity, since virtually the only external components are the timing resistor and capacitor, another resistor and capacitor, a push-button and the load.

OPERATION WITH A TRIAC

Home-constructor timer projects frequently incorporate relays, this being the case even when the controlled item is a mains-driven filament lamp. The use of relays tends to raise difficulties, particularly with respect to contact rating, and the author felt it would be of interest to check the operation of a '555' timer i.c. in conjunction with a triac. The triac chosen was the R.C.A. 40430, which has proved to be popular in recent home-constructor designs.

The full circuit of the timer incorporating the '555' i.c. and the 40430 appears in Fig. 2. In this diagram the

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

R1	15k Ω
R2	15k Ω
R3	100 Ω
R4	1k Ω
R5	560 Ω
R6	100 Ω
VR1	500k Ω potentiometer, linear

Capacitors

C1	32 μF electrolytic, 10 V. Wkg.
C2	0.01 μF plastic foil
C	1,000 μF electrolytic, 10 V. Wkg.

Transformer

T1	Heater transformer, secondary 6.3 volts at 0.5 amp or more
----	--

Integrated Circuit

NE555V, LM555CN, or '555 Type'

Triac

40430

Diodes

D1 - D4 1N4002
LED1 TIL209-

Lamp

LP1 240 volts, 100 watts maximum

Switches

S1 Push-button, push to make
S2 S.P.S.T., toggle
S3 D.P.S.T., toggle


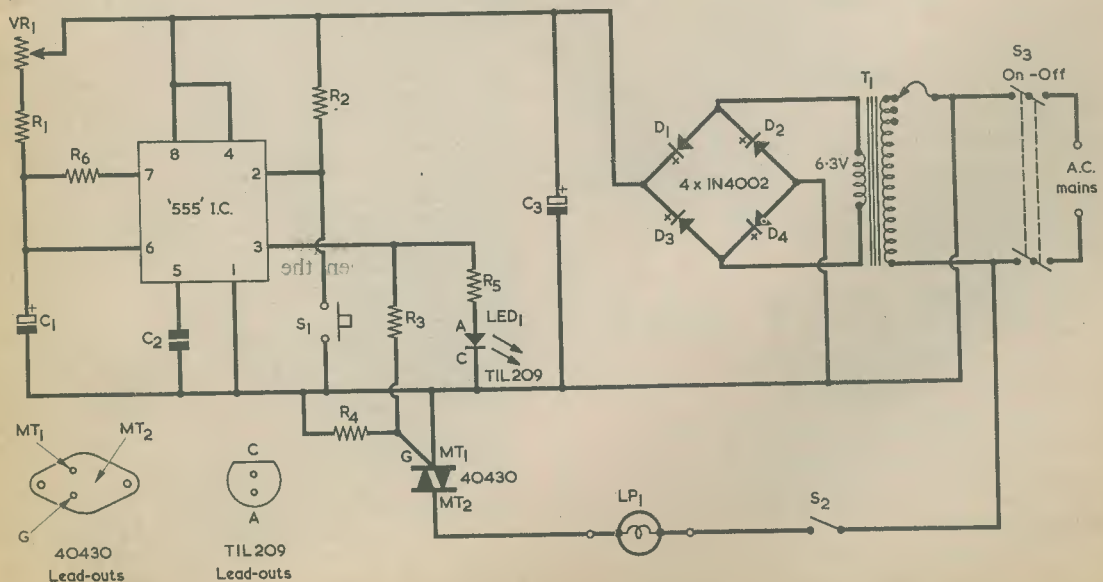


Fig. 2. A practical circuit incorporating the timer i.c. in conjunction with a triac.

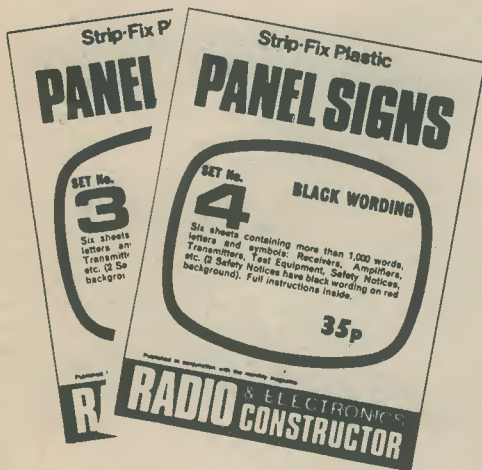Use the **NEW** Strip-fix Plastic **PANEL SIGNS**



- ★ SET 3 - Wording - WHITE
- ★ SET 4 - Wording - BLACK

Over 1,000 words and symbols,
covering more than 300 terms, in
each set

Illustration of actual size = RADIO

★ SET 5 - Dials
6 sheets containing one Large and
two Medium scales, Large Horizontal
Tuning scale, Frequencies 12 Control
Panels

- Easy to fix
- Stapled in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish

38p per set

including V.A.T.
(postage 3p)

The Perfect Transfer for
the Home Constructor

Available from
Data Publications Ltd.
57 Maida Vale, London W9 1SN

couple to the timing resistor, given by R1 and VR1 in series, and to the timing capacitor, which now appears as the electrolytic component, C1. R6 is added here to limit the discharge current from C1. Capacitor C1 has a nominal value of 32 μ F, whilst R1 is 15k Ω and VR1 is 500k Ω . Assuming that all three components have their nominal values, the longest timing period, which is given when VR1 inserts full resistance, calculates out as 1.1 times the product of 0.515M Ω (500k Ω plus 15k Ω) and 32 μ F, or 18 seconds. The shortest timing period, given when VR1 inserts minimum resistance, is 1.1 times the product of 0.015M Ω and 32 μ F, and this works out as 0.5 second. A range of timing periods from 0.5 to 18 seconds is suitable for a photographic timer, or for any similar application. In practice, tolerances on value in the timing resistors and capacitor will cause the timing periods to differ from the calculated figures, but it is still nevertheless a relatively simple matter to calibrate VR1 in terms of the periods actually obtained. The value of 500k Ω for VR1 is around the highest realistic figure for a timing circuit in which the timing capacitor is an aluminium electrolytic type having the usual leakage current associated with such a component.

When S1 is pressed at the start of a timing run, the output at pin 3 of the i.c. goes positive, causing a current to flow, via R3, through the gate and Main Terminal 1 of the triac. The triac turns on and the a.c. mains is applied via its Main Terminal 1 and Main Terminal 2 to the lamp, LP1. The fact that the timer output has gone positive is also indicated by the lighting of LED1. When the timing run comes to an end, the output at pin 3 drops towards the level of the negative supply rail, whereupon the triac becomes open-circuit and LP1 extinguishes. So also does LED1.

Resistor R4, between the gate and Main Terminal 1 of the triac, is probably unnecessary, but it was nevertheless added as a safety precaution to protect the integrated circuit. The current and voltage levels controlled by the triac are well in excess of those associated with a small i.c. output circuit, whereupon R4 damps down any high impedance voltage spikes which might, just conceivably, appear at the gate.

The power supply is quite standard. T1 can be any small heater transformer offering 6.3 volts at a current of 0.5 amp or more, and its 6.3 volt secondary connects to the bridge rectifier consisting of D1 to D4 inclusive. C3 is the reservoir and smoothing capacitor. The rather high value of 1,000 μ F employed here ensures satisfactory supply voltage regulation.

Switch S3 controls the mains input supply to both the timer circuit and the controlled lamp. Switch S2 is also in series with the lamp and this switch is included, in company with LED1, to guard against an occasional effect which occurs at switch-on. It was found with the prototype circuit that the i.c. would sometimes commence a single timing run immediately after S3 was closed, despite the fact that S1 had not been pushed. The reason for this effect is not known and is presumably due to the circuit settling down to its operating condition with C1 and C2 in their proper charge conditions. Because of this, effect the following sequence is employed in bringing the timer into use. S3 is initially closed, with S2 open. If the circuit should then start a timing run, this fact will be indicated by the illumination of LED1. The timing run will have a length which depends upon the setting of VR1 and, when it has come to an end, LED1 will extinguish. S2 may then be closed, whereupon the circuit is ready for

RADIO & ELECTRONICS CONSTRUCTOR

normal use.

There was no evidence of further untriggered timing runs in the prototype circuit after the occasional initial run immediately after switching on, and the circuit performed satisfactorily after these runs had taken place. If it is felt that the occasional untriggered run at switch-on would not cause any difficulties in use, the l.e.d. circuit, consisting of R5 and LED1, and S2 can both be omitted.

It should be noted that S1 need only be closed momentarily to start a timing period. If this push-button is held closed, the output at pin 3 will remain high even after the end of the period. The period commences when S1 is closed and it is only then required that S1 be opened again at any time before the end of the period. This point necessitates fairly quick operation of S1 when the period selected is of the order of 0.5 second, but the required quick pressure and release of the button is not at all difficult to accomplish. When LP1 is the bulb in a photographic enlarger, it may be desirable to have it turned on for a continual period for purposes of focusing. Pressing S1 and keeping it closed will provide the necessary continual illumination in LP1.

CONSTRUCTION

By far the most important thing to bear in mind, so far as construction is concerned, is that all points in the circuit of Fig. 2 are at, or near, mains potential. The parts should preferably be assembled in an insulated case. If a metal case is employed, this must be reliably earthed. Lamp LP1 will be external to the main unit and may be coupled to it by way of a suitable plug and socket. The push-button, S1, should have insulation suitable for mains voltages. The l.e.d. may be fitted so that it is central in a small grommet on the front panel of the unit. The l.e.d. type specified is available, incidentally, from Henry's Radio, Ltd.

In the prototype, the triac was mounted on a small heat sink about $1\frac{1}{2}$ in. square. It ran quite cool on this sink. The circuit was checked with domestic 240 volt bulbs up to 100 watts in rating. Bulbs of higher power than 100 watts should not be used. It was found that the triac was fully turned on by the circuit; short-circuiting its Main Terminals 1 and 2 when it was conductive caused no noticeable increase in the voltage across the bulb.

VR1 is a standard panel-mounting carbon potentiometer. A 'moulded track' type of potentiometer would represent a good choice and would offer a high degree of repeatability. It needs to be fitted with a pointer and scale which can be calibrated later in terms of seconds.

As with all d.i.l. integrated circuits, the terminal pins of the timer i.c. are fragile. Connections to these pins should be made by way of *thin* wire. It is a good plan to wire to an i.c. holder rather than directly to the i.c. itself, since any damage due to the wiring process can then only result in the loss of the less costly holder.

The layout of components in the timer unit is not important, provided that C2 is positioned close to the i.c. and R4 is positioned close to the triac.

The measured supply voltage across C3 in the prototype was 7.4 volts before and after timing runs, and 7.0 volts during a timing run. The voltage at terminal 3 of the i.c. during the run was 5.4 volts, which infers that 1.6 volts is dropped inside the i.c. when the output is positive. Assuming, for convenience of calculation, a forward voltage drop of zero across the gate and Main

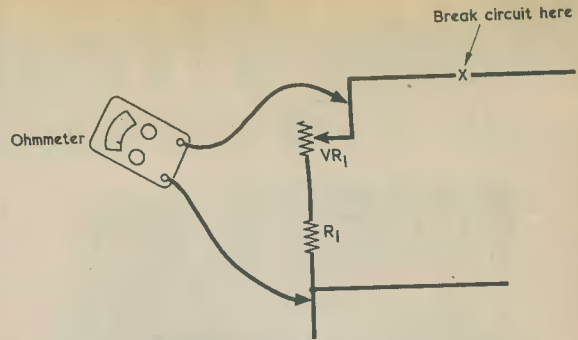


Fig. 3. A simple means, described in the text, of calibrating VR1 in terms of seconds.

Terminal 1 of the triac, the output current flowing through R3 is 54mA. The current in R5, assuming zero forward voltage drop in the l.e.d., is of the order of 10mA. Thus, the total output current is 64mA, which is well within the maximum of 200mA specified for the '555' device. The output current of 64mA, in combination with the 1.6 volts dropped inside the i.c. represents a dissipation inside the i.c. of 102mW. The i.c. circuits not directly associated with the output can be assumed to dissipate some 30mW, whereupon the total dissipation in the i.c. is well within the 600mW maximum rating.


The prototype circuit gave a maximum time period of 23 seconds, which is to be expected since the actual capacitance of electrolytic capacitors is usually in excess of their nominal values. When the unit has been completed, it should be run for a number of periods to check operation and to allow C1 to 'form', after which VR1 may be calibrated. One method of carrying out the calibration consists of timing a number of runs with VR1 in various positions and then making up a scale from the results obtained.

A less tedious approach is possible if an accurate ohmmeter is to hand, and it relies on the fact that the length of the timing period is proportional to the resistance of VR1 plus R1. The timer is initially run with VR1 inserting maximum resistance and the length of the period is measured and noted. The timer is then disconnected from the mains and the circuit to VR1 slider broken, as in Fig. 3. The ohmmeter is connected between the slider of VR1 and the lower end of R1, whereupon it initially indicates the resistance given by VR1 plus R1 when VR1 inserts maximum resistance. Resistance values in VR1 plus R1 for round-number periods of time can then be calculated, and VR1 calibrated by simply setting it up for these resistance values.

To give an example of this technique, it was found in the prototype circuit that the longest timing period of 23 seconds corresponded to a measured resistance in VR1 plus R1 of 520k Ω . Since, in this instance, 520k Ω corresponds to 23 seconds then it follows that 520k Ω divided by 23 corresponds to 1 second. The result of this division is 22.6k Ω . VR1 is adjusted to give this resistance in VR1 plus R1 and its scale is calibrated for 1 second. The 5 second point is then at 113k Ω , the 10 second point at 226k Ω , the 20 second point at 452k Ω , and so on. After calibration in this manner the ohmmeter is removed. The circuit connection to VR1 slider is then re-made and the timer is ready for use. ■

New Products

HEATHKIT ULTRASONIC CLEANER

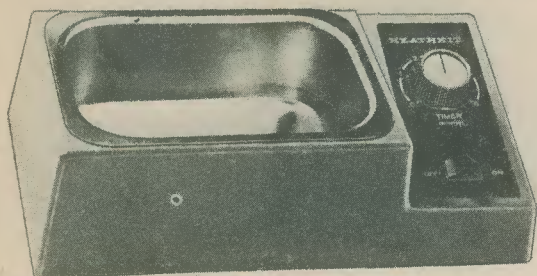

Art and decorating brushes, jewellery, watches, glasses, dentures etc. Simply fill the stainless steel tank with solvent, place the item to be cleaned into the tank, set timer and await results.

You'll be amazed how quickly and easily your

possessions become clean. Agitating cleansing power feeds into the smallest crevice of the most intricate object. This ultrasonic cleaner works by a 41 kHz signal driving a transducer to produce mechanical motion that creates pressure variations in the cleaning solvent which result in microscopic bubbles being formed. These tiny bubbles are the secret behind the fantastic effectiveness of ultrasonic cleaning. The comprehensive kit building manual makes assembly a snip, even for the beginner. This is a must for home or laboratory.


For 110-130 V AC mains operation (250 V AC Transformer available as extra). Mail Order Basic Price Kit K/GD-1150 £27.50. Carr. 44p.

For a FREE catalogue and further information, write to HEATH (Gloucester) LTD., Bristol Road, Gloucester, GL2 6EE.

LIGHT SWITCH AND DIMMER

The SECUREYE flush or surface mounted switch performs three functions: 1. Manual on/off switch; 2. Dimmer; 3. Automatic on/off switch - operated by ambient light level.

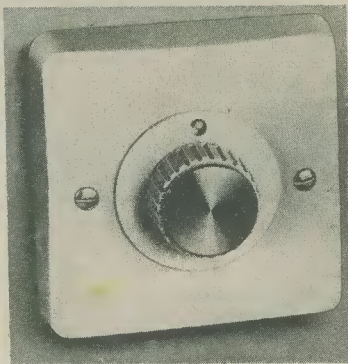Designed as an immediate replacement for an existing modern light switch, the SECUREYE embodies a light sensitive element which facilitates many security applications. As light falling upon the cell is reduced, power is allowed to flow through the switch progressively until approximately half brilliance is achieved. When ambient



light level is increased the control automatically operates as a dimmer until power is cut off completely.

In addition the SECUREYE operates in the same way as a conventional dimmer switch to provide sophisticated lighting control manually.

Recommended Retail Price for the SECUREYE combined Auto-Switch and Dimmer is £5.60 plus VAT.

Manufactured in Britain by Rendar Instruments Limited, Victoria Road, Burgess Hill, Sussex.

I.C. AUDIO AMPLIFIER

New from R.S. Components Limited is a 5W silicon monolithic integrated circuit audio amplifier, incorporating both pre and power amplifier stages.

Priced at £2.22 the device is suitable for the amplification of speech or music when fitted with a type 173 heat sink, also available from R.S. at 14 pence. The output is protected against short-term load faults, and input sensitivity suits most popular crystal and ceramic pick-ups. Full information is included with each device and covers the construction of a mono or stereo amplifier circuit with tone controls.

Further details are available from R.S. Components Limited, 13-17 Epworth Street, London E.C.2.




TWO-WAY RADIO BASE STATION MICROPHONE

Reslosound Limited, of Spring Gardens, London Road, Romford, Essex, RM7 9LJ today released a new base station, or paging, microphone, the Reslo Dispatcher which is available in both dynamic and capacitor electret versions.

A "press-to-talk" switch is incorporated in the base of the unit for operator use whilst sitting down, and if it is picked up by a standing operator an alternative press bar falls naturally under the operator's thumb.

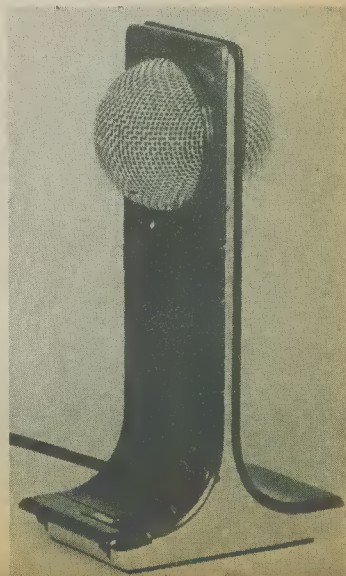The Reslo Dispatcher microphone is available in standard two-tone Post Office telephone colours, or to customer's requirements if ordered in substantial quantities.



SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

The opening gambit in the April issue dealt with three clandestine transmitters "Voice of the Middle East Peoples", "Voice of Palestine, Voice of the Palestine Revolution" and "Radio Korush". For news of more clandestine stations we present -

"Voice of the Arabian Peninsular People", an anti-Saudi transmitter operating from 1200 to 1300 on 7193, 9562 and 11850 in Arabic. This one has also recently been reported on an additional frequency of 8360. Also from 1800 to 1900 on 7193, 9560 and 9573.

"Voice of the Free Yemeni South" radiates from 1130 to 1445 on 5345.

"Voice of Peaceful Laos" is reported with daily programmes in Laotian from 2300 to 0200 and from 0500 to 1430 on 7385. Also in Vietnamese from 1430 to 1500 on the same channel.

With all the clandestine stations brought to readers' attention in this and previous issues of this magazine, one could well spend a fruitful series of operating periods trying to log them. Needless to say, some of them, such as the "Voice of Peaceful Laos", would prove rather difficult. Although many attempts have been made by the writer to bring this one to book, the log sheet shows no such entry. However we persist and, who knows, one day success might be our reward. Perhaps Dxers should appoint themselves a patron saint!

CURRENT SCHEDULES

Current schedules are of assistance to short wave listeners in that they may plan to some extent their listening periods. This is especially useful when the QSL card of a particular station is required in that most of the information presented under this heading deals with broadcasts in English directed to Europe and/or the U.K. In this manner both the times and frequencies are known to the operator and the language, English, understood.

● INDIA

The External Service of "All India Radio" Delhi directs a programme in English to East Africa, West Europe and the U.K., in the General Overseas Service, from 1745 to 1945 on 7215, 9525, 9575 and on 15080 with a newscast from 1800 to 1810.

MAY 1974

From 1945 to 2045 to North & West Africa, Australasia and the U.K. on 7215, 9525, 9755, 9912, 11620 and on 11880, newscast from 2000 to 2010.

From 2045 to 2230 to West Europe, Australasia and the U.K. on 7215, 7260, 9525, 9912, 11620 and on 11740, newscast from 2200 to 2010.

● LIBERIA

"E.L.W.A. Eternal Love Winning Africa", Monrovia, the radio voice of the Sudan Interior Mission, has an External Service in English and vernaculars as follows - from 0615 to 0700 (Saturdays to 0815, Sundays to 0800) to West and Central Africa on 11950.

From 1345 to 1615 (Sundays only) to West and Central Africa on 11950.

From 1615 to 1700 (Sundays only) to West and Central Africa on 11940.

From 1800 to 2100 to West and Central Africa on 11940. The vernaculars are Fulani, Hausa, Ibo, Igala, Kanuri, Nupe and Yoruba.

E.L.B.C. Liberian Broadcasting Corporation, Monrovia, operates a Home Service in English and Liberian from 0528 to 1000 and from 1200 to 2400 Monday to Friday, from 0528 to 2400 on Saturday and from 1558 to 2400 on Sunday as follows - 3255 (1915 to 2400), 6090 (0528 to 1000; 1200 to 1915; Sundays 0600 to 1915).

● ISRAEL

Still searching for clear channels, the Israel Broadcasting Authority currently (at the time of writing) has an English transmission for North America, Europe and Africa from 2000 to 2045 on 7335, 7395; 9009, 9495, 10250, 11700 and 15100.

● PAKISTAN

Radio Pakistan has a broadcast of news in English, at slow speed, to the Middle East from 1530 to 1545 on 11672 and 15520. To East Europe from 1745 to 1800 on 9690 and 11672.

● BANGLADESH

Radio Bangladesh is currently operating an External Service in English from 0615 to 0645 on 15520 and 17690; from 1230 to 1300 on 17690; from 1815 to 1915 on 7260 and 9495 with slow speed news from 1900 to 1915.

● PHILIPPINES

The "Voice of the Philippines", Manila, has an External Service in English, Japanese, Standard Chinese, Tagalog, Vietnamese and Indonesian from 0700 to 1900 on 9580.

● ALGERIA

The "Radio of the Democratic People's Republic of Algeria", Algiers, presents an External Service in English directed to East and West Africa and the Mediterranean area from 1900 to 1925 on 11910 with a newscast from 1900 to 1915.

The Home Service (Arabic Network) has an English lesson for schools (not Friday or Sunday) from 1015 to 1045 on 9610, 11715 and on 11965. This programme is also radiated on the French Network at the same time on 11835, 17825 and on 21715.

Broadcasts for the Palestine Liberation Organisation "Voice of Palestine, Voice of the Palestine Revolution", in Arabic, is radiated from 1830 to 1930 on 6145, 7195, 7245, 9610, 9665, 11715, 11810, 11965 and on 15160.

AROUND THE DIAL

Some of the stations recently logged on the HF bands which may interest some readers have been -

● ZAIRE

Radio Lubumbashi at 2020 on 11865 with African drums, chants, colourful African music by a local orchestra and announcements in French. This one is well worth logging by those equipped with a tape recorder and interested in African music.

● ROMANIA

Radio Bucharest at 1500 on 11940 with a newscast in English and station identification at 1508.

● CHINA

Radio Peking at 1515 on 11650 with the news in English read by YL announcer, identification at 1523 then into Chinese music.

Radio Peking at 1520 on 7350 with OM in Standard Chinese to South East Asia and South East Africa, Chinese music at 1522.

● VATICAN CITY

Vatican Radio at 1500 on 7250 with station identification and news of the Catholic church in English.

● PAKISTAN

Radio Pakistan at 2107 radiating on a measured 7082.5 with OM in vernacular, identification by YL in English at 2110 then into local music.

● SWITZERLAND

Berne at 2115 on 11720 with a programme in English about Swiss retailing methods and trade in general.

QSO

For the Dxr, mostly interested in the frequencies below 6MHz, recent loggings of possible interest may be -

● MALAYSIA

Penang at 2323 on 4985 with short musical items rendered on a piano with OM giving a short talk on each example.

● COSTA RICA

TIHB Radio Capital, San Jose, at 0042 on 4832 with discussion group talking about Guatemala in Spanish.

● PERU

OAX7Q Radio Quillabamba at 0020 on 5025 with LA music, announcements by OM. Identification and newscast in Spanish, after a few bars of classical music as an introduction at 0030 then into light classical music European-style.

● CHINA

Radio Peking at 2253 on 4800, YL in Chinese dialect; 4815 at 2300 with interval signal on chimes, identification by OM then orchestral rendering of "East is Red"; 4850 at 2304 YL in Chinese dialect; Wuhan at 2249 on 3940 OM in Chinese vernacular; PLA Fukien at 2148 on 4840 with YL talking and Kunming at 2340 on 4759.5 with OM in Chinese.

● BRAZIL

ZYS8 Radio Difusora do Amazonas, Manaus, at 0030 on 4806.5 (listed 4805) with identification then harangue by OM in Portuguese till 0040 tune-off.

● VENEZUELA

YVMG Radio Popular, Maracaibo, at 2325 on 4810 Latin American music, OM with identification at 2330.

● SOUTH AFRICA

SABC Johannesburg at 2100 on 4875 identification and a newscast in Afrikaans after 6 pips. Also on 3250 at 2258 with announcements in English.

● INDIA

AIR Delhi at 2350 on 3905 with local music, songs by YL.

● GHANA

Ejura at 2306 on 4980 signing off with "This is the Voice of the Revolution, Good Night" and National Anthem.

● NIGERIA

Lagos at 2236 on 4990 with OM in talk in English about Nigerian sports and facilities provided for them.

● ANGOLA


Radio Texeira da Sousa at 2117 on 4886.5 with OM in Portuguese, an endless talk, or so it seemed!

The above logging is only tentative, conditions were not good enough to enable a positive identification but the writer hopes to establish this in the immediate future.

At the moment, there is some confusion in the Dx world about this transmitter, a few Dxers maintain that the Texeira identification can be heard up to 2300 whilst another Dxr holds that it closes at 2100, the station then heard on this channel being Teresina (Radio Pioneira de Teresina) on 4887. Yet another Dxr states that "Programa A Voz do Zaire" has been heard at 2230. Is it Texeira or Voz do Zaire up to 2100 or 2300 and then Teresina? (Acknowledgement "Bandspread" 65/5).

● NEPAL

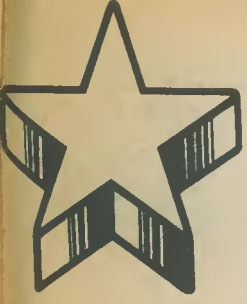Radio Nepal at 0016 on new 3425 sign-on with piano music, 6 chimes at 0020, announcements by YL then Indian-style music.



THE 'BIFLEXETTE'

PORTABLE RECEIVER

By Sir Douglas Hall, K.C.M.G., M.A. (Oxon)

A 2-transistor reflex receiver which offers loudspeaker reception of local stations on the medium and long wave bands.


THE RECEIVER TO BE DESCRIBED EMPLOYS A NEW circuit which requires only two transistors, an N-channel f.e.t. and a p.n.p. transistor, and a few other components. For signal pick up it employs a 6in. ferrite rod aerial only, and it is easy to build and set up. Yet it offers no less than four amplifying stages plus a detector stage and will give good loudspeaker results from local stations. In most parts of the country it will provide loudspeaker reception of two or three Continental transmitters as well. At a more modest output level, suitable for bedside listening, it will pick up many more. It covers the whole of the medium and long wave bands.

Right from the start the author must emphasise the importance of using the specified components. This is especially necessary with a very simple receiver such as the present design, which is designed to give the maximum possible performance with the minimum of parts.

SEMICONDUCTORS

The constructor must ensure that the semiconductors are genuine first grade components. If different transistors are used the receiver may not work at all, or only inefficiently. Both the diodes are R.S. Components parts, and may be obtained from an R.S. Components retailer such as Elekon Enterprises, 224A, St. Paul's Road, Highbury Corner, London, N.1. It is particularly important that D1 be the correct type; a different silicon diode here would almost certainly require a modification to the value of C2 at least. The volume control is a moulded track R.S. Components type, also available from R.S. Components retailers, and this type of control is essential for the circuit as others are liable to become noisy. Above all, use a sensitive speaker. At the risk of boring readers the author will emphasise once again that it is audible output and not electrical output which reaches the ear. The difference between a good high flux speaker and a normal rather cheaper

one is quite surprising. If a speaker having a 7,000 gauss magnet is compared with one having a 10,000 gauss magnet, using a switch to change them over when coupled to a low level signal, the difference will prove to be very marked. The author employed an Elac 3Ω 5in. speaker with a 10,000 gauss magnet in the prototype. This can be identified by the maker's name and the large 2¼in. diameter magnet. The Elac speaker is excellent in the present design, but may not be very easy to find. Constructors are advised to shop around for it or a similar high gauss unit. Many 8Ω high gauss speakers will match quite well with the LT700 transformer. The author obtained his own speaker from Radioparts, Market Way, Plymouth, and it is worthwhile contacting this firm, who should be able to supply the Elac speaker or a suitable equivalent. Also, high flux 5in. speakers are listed by Henry's Radio Ltd.,

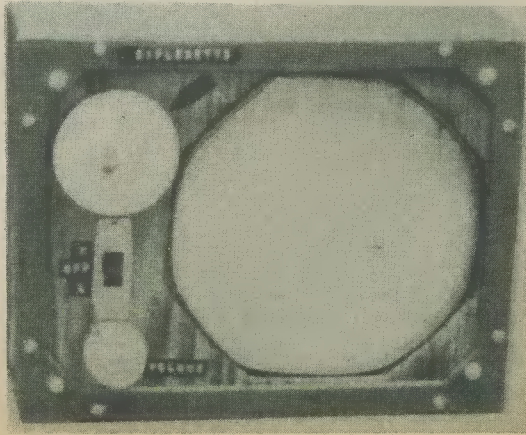

Front view of the 'Biflexette' receiver in its case.

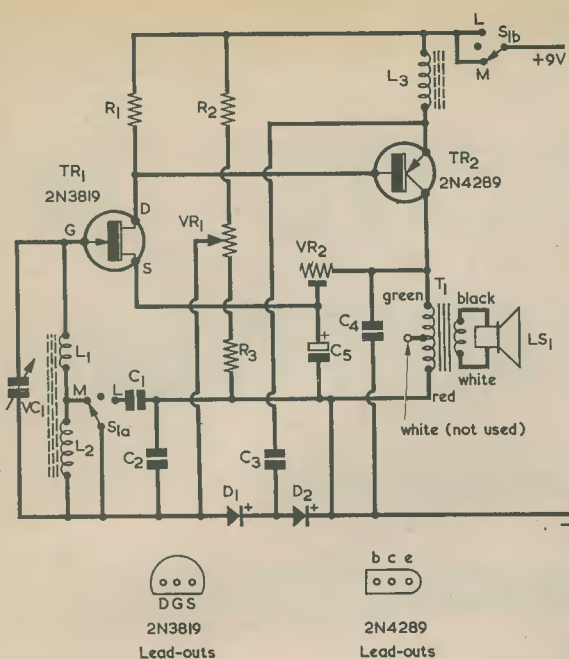


Fig. 1. The circuit of the 'Biflexette' receiver.

CIRCUIT

The theoretical circuit of the 'Biflexette' receiver is given in Fig. 1. When S1 (a) is in the position shown, signals are picked up by the medium wave winding, L1, on the 6in. ferrite rod, this being tuned by the 150pF air-spaced variable capacitor, VC1. The non-earthly junction of L1 and VC1 is applied to the gate of TR1, a field-effect transistor which functions as a grounded source radio frequency amplifier. The amplified r.f. signal appears across R1 and is applied to TR2 which, at radio frequencies, acts as a common collector current amplifier, or emitter follower. Its output appears across the r.f. choke L3 and is applied to the two diodes, D1 and D2. Note that D1 is a silicon diode and that D2 is a germanium type.

If there is a very low voltage only across D1 it will act as a very high resistance for current in both directions, and not as a diode. When the voltage across it approaches about 0.6 volt rectification will start, the impedance in the forward direction becoming less as the voltage increases. D1 and D2 then form a voltage doubler circuit. C2 has a value which allows an effective capacitive tap to be made into the tuned circuit such that oscillation can take place in the Colpitts mode, always provided that the voltage across D1 is sufficient to prevent it from offering too high an impedance in the feedback circuit. The level of regeneration is controlled by VR1, which first takes D1 into the conducting state as its slider moves upwards and then varies the current flowing in this diode. R3 is included because, if the lower end of VR1 track were connected direct to the negative supply point, the first 90 degrees of its travel would be wasted. With R3 in circuit the whole of the first half of the movement of VR1 slider is useful.

It can be seen that VR1 functions as a reaction control. When it is turned well back, i.e. with its slider at the negative end of its track, and when in

consequence D1 offers a very high forward impedance, a potentiometer is formed in which D1 is the upper arm and R3 the lower arm. The potentiometer given by D1 and R3 acts as a volume control across D2 which, being a germanium device, will still give some rectification even with a very low voltage across it. To sum up, the process of taking VR1 slider up from the negative end of its track initially allows detection to occur in D2, with D1 and R3 providing a control of volume. As the slider moves further up the track D1 is brought more and more into use as a detector in its own right and eventually a point is reached where the overall efficiency of the diode circuit allows oscillation to take place.

It is possible for a very powerful signal to overload the receiver detector circuit, whereupon a distorted output will be given even then the volume control is turned well back. Should this occur, advantage is taken of the directional properties of the ferrite rod aerial and

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1	3.3k Ω
R2	2.2M Ω
R3	68k Ω
VR1	1M Ω potentiometer, log, moulded track (R.S. Components)
VR2	22k Ω or 25k Ω , pre-set potentiometer, miniature skeleton

Capacitors

C1	2,200pF silvered mica
C2	82pF silvered mica
C3	2,200pF silvered mica
C4	2,200pF silvered mica
C5	100 μ F electrolytic, 6.4 V.Wkg.
VC1	150pF variable, air-spaced, type C804 (Jackson Bros.)

Inductors

L1, L2	see text
L3	1.5mH r.f. choke, ferrite cored, type CH5 (Repanco or equivalent)
T1	Output transformer type LT700 (Eagle)

Semiconductors

TR1	2N3819
TR2	2N4289
D1	Silicon diode type 1S150 (R.S. Components)
D2	Germanium diode type 1GP5 (R.S. Components)

Switch

S1(a)(b)	D.P.D.T. slide switch with centre off position (see text)
----------	---

Speaker

LS1	3 Ω 5in. speaker, high flux (see text)
-----	---

Battery

	9 volt battery type PP6 (Ever Ready)
--	--------------------------------------

Miscellaneous

	Battery connectors
	2 knobs
	18-way 'Miniature' group panel (R.S. Components - see text)
	6 \times $\frac{3}{8}$ in. ferrite rod (see text)
	Fablon or Contact
	Speaker fabric
	$\frac{1}{4}$ in. plywood, Paxolin, etc.

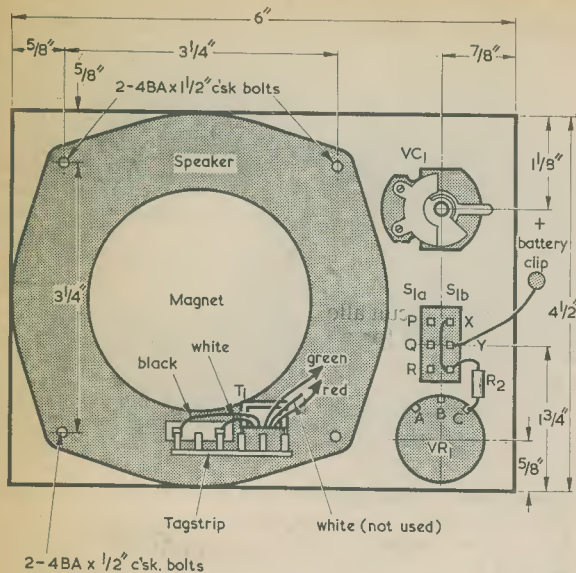


Fig. 2. Components and wiring on the front panel.

the receiver is turned so that signal pick up is reduced to a level where the overload distortion disappears.

The detected signal at the junction of D1 and VR1 slider is passed to the gate of TR1 via L1 (and via L2 when S1 (a) is set to long waves). TR1 next functions as a grounded source voltage amplifier at audio frequency with its drain coupling direct to the base of TR2. TR2 now acts as a high gain voltage amplifying output transistor. The presence of L3 in its emitter circuit causes negligible negative feedback of audio frequencies.

For TR2 to function correctly, about 0.65 volt needs to be dropped across R1. This means that TR1 must pass a current of about 200 μ A. The source bias of TR1 is adjusted by VR2 to produce this current. As there is heavy negative feedback at d.c. between the two transistors the setting of VR2 is not unduly critical and the circuit is very stable.

When S1 (a) is switched to long waves L2 comes into circuit. Also, capacitor C1 is switched across C2 to provide a suitable capacitive tap at the lower frequencies involved. In the prototype, a 2-pole slide switch was used for S1 (a) (b), this having a centre off position. If a switch of this type cannot be obtained, two separate small toggle switches mounted side by side can be employed instead. One switch can offer a single-pole double-throw action and it then replaces S1 (a). The other may give a single-pole single-throw action and replace S1 (b). The first switch is then the wavechange switch and the second the on-off switch.


CONSTRUCTION

Construction commences by cutting a piece of 1/4 in. plywood to measure 6 by 4 1/2 in., as illustrated in Fig. 2. The positions for VC1, S1 (a) (b) and VR1 are shown in this diagram and the requisite mounting holes should be cut out. If a slide switch with a central off position has been obtained for S1 (a) (b), a rectangular cut-out is made to take its body, which passes through the plywood. The front plate of the switch is on the front

of the plywood panel (the surface away from the reader in Fig. 2) and the switch is secured at the front with two small wood screws. If separate toggle switches are to be used, these may be mounted side by side with their centres 1 1/2 in. from the bottom of the plywood panel. The position of the speaker is also shown in Fig. 2 and a suitable cut-out should be made for it before it is mounted, over a piece of gauze. The 3 1/4 in. dimensions between speaker mounting holes apply to the Elac speaker used in the prototype. These dimensions may differ slightly with other speakers. The speaker is secured with 4BA countersunk bolts, these being 1/2 in. long at the two lower holes in Fig. 2 and 1 1/2 in. long at the two upper holes. As will be seen shortly, the longer bolts will also hold a Paxolin panel, and the 1 1/2 in. length is based on the construction of the Elac speaker. Longer bolts may be required if an alternative speaker with a different chassis shape is employed.

Two tagstrips are required in the receiver and these are cut from a single 18-way R.S. Components 'Miniature' tag panel. The tag panel can be obtained from R.S. Components retailers, or from Home Radio under Cat. No. BTS12. A 6-way tagstrip cut from the tag panel can be seen in Fig. 2, and it is used to mount the output transformer T1. The feet of the transformer clamp are bent in slightly and are then soldered to two of the tags on the tagstrip. Two of the remaining tags are soldered to the speaker tags as shown, as also are the black and white secondary leads of the transformer. Tag spacing on the tagstrip is correct for the Elac speaker. It might be necessary to use different tags, thereby necessitating a longer strip, with other speakers.

VC1, VR1 and S1 (a) (b), or the two separate switches which are employed instead, are all now mounted. The ends of the fixed vane lugs of VC1 may need to be clipped off or they may foul the back of the case when this is fitted on completion of the receiver. If, however, the constructor uses components different to those employed in the prototype it is possible that the case will have to be deeper in any event, and so the question of clipping the fixed vane lugs is left until later. During construction and testing, the connections to the fixed vane lugs may be made at their existing ends.

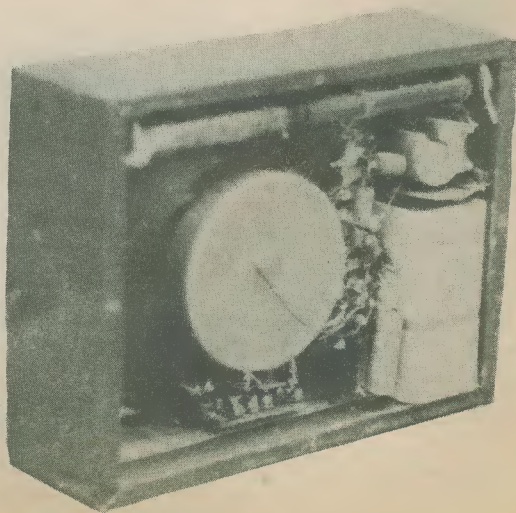

The receiver with the back of its cabinet removed.

Next to be cut out is a piece of Paxolin to the shape shown in Fig. 3. This has a large hole for the speaker magnet and two 4BA clear holes to pass over the longer 4BA bolts which secure the speaker. The dimensioning of the large hole and the two 4BA clear holes which is given in Fig. 3 applies to the Elac speaker. A 12-way tagstrip is cut out from the 18-way group panel and is secured to the Paxolin by two 10BA bolts passing through the holes in the end tags.

Next wind L1. The author employed blue grade ferrite rod for the aerial and this has a lower permeability than most of the ferrite rods currently available. The latter can be employed just as readily in the receiver but they will require somewhat fewer turns for coverage of the medium and long wave band. If the constructor has obtained blue grade rod (which is marked by a blue colour code at one end) the winding instructions which are given next will offer the correct frequency coverage. If another grade of rod is used the windings should be made up as described. After the receiver has been checked out it may then be found necessary to remove a few turns from the windings to obtain correct range. In most cases it will probably be necessary to take turns only from the medium wave coil, L1.

Take a piece of Fablon or Contact 2in. wide and 3in. long and remove a $\frac{1}{8}$ in. strip of the backing paper along one of the 2in. edges. Wind the piece onto the ferrite rod with the exposed adhesive at the outer end, so that the piece is secured in place by being stuck on itself. The tube should be loose enough to slide on the rod. Then close-wind 100 turns of 28 s.w.g. enamelled wire in a single layer on the outside of the piece of Fablon or Contact.

L2 is wound on an exactly similar tube, and consists of 6 pies of 38 s.w.g. enamelled wire. Each pie has 70 turns scramble-wound and is about $\frac{1}{8}$ in. wide. Separation between pies is approximately $\frac{1}{16}$ in. The exact form of the overall winding is not critical as long as there are 6 separate pies. Slide the two coils onto the

rod and fit rubber or p.v.c. grommets at the ends. The two inside wires of the coils are joined together, during wiring later, and they should be mutually aiding in terms of inductance when both are in circuit. The ferrite rod is held in place by means of nylon thread passed through 4 small holes in the Paxolin, at each end of the rod, the thread being knotted in the grommet grooves. Do not use bare wire to secure the ferrite rod as this will constitute shorted turns at the rod ends.

Thread a 4BA nut onto each of the longer 4BA bolts which secure the speaker, and pass the Paxolin piece over these bolts. Adjust the nuts so that the Paxolin settles as low down on the speaker as the construction of the latter permits. Then pass two more nuts over the bolt ends and tighten these up to hold the assembly secure.

Next fit small components to the 12-way tagstrip, and wire this up as illustrated in Fig. 3. In this diagram some of the components and wiring are shown spread out for reasons of clarity. In practice, all leads should be as short as is conveniently possible. This point does not apply to choke L3, however, and this component should have lead lengths which are sufficiently long to enable it to be oriented during setting-up of the receiver. It is necessary for the speaker magnet to be earthed to the negative supply point as, otherwise, it is possible for low frequency instability to occur due to unwanted coupling between T1 and the ferrite rod assembly. No attempt should be made to solder to the magnet. A suitable connection can be made by splaying out the cores at the end of a length of fine flexible wire and holding these down with Sellotape; and this serves quite satisfactorily in practice. If there is still evidence of low frequency distortion or instability when the set is tried out, the red and green leads from T1 primary may be transposed at the tagstrip, but it is unlikely that this will prove necessary.

SETTING UP

When the wiring is complete and has been checked, put the PP6 battery in position behind the body of VR1. If the slide switch type employed by the author has been used, the battery should be well clear of the tags of this switch. If separate toggle switches have been fitted it may be necessary to provide a means of insulation to prevent the metal body of the battery from touching their tags. Ensure that VR2 is adjusted to insert full resistance into circuit. This is the fully clockwise setting in Fig. 3. Connect up the battery with a current reading meter in one lead. Set VR1 fully anti-clockwise, switch on and slowly reduce the resistance inserted by VR2 until a reading of 7mA is given. There should be a small reading initially which will increase as VR2 is adjusted; if there is not, something is wrong. Do not adjust VR2 to insert zero resistance in an attempt to obtain the correct reading. Such a setting will not be necessary if all is well, and it could cause damage to the transistors.

Select medium waves and adjust VC1 until a local station is heard. It should be possible to make the receiver oscillate throughout the full range of settings of VC1, oscillation being denoted by a whistle if a station is tuned in or by a hiss if no signal is present. Should this not happen, adjust the orientation of L3 with respect to the ferrite rod. This adjustment will assist oscillation for settings in VC1 between half and full capacitance. Find an angle for L3 which gives good oscillation throughout the full range of VC1, without oscillation commencing too early in the advancement


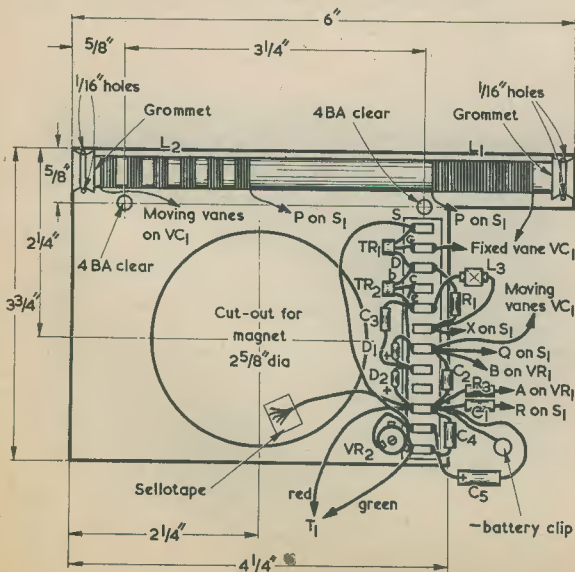


Fig. 3. The majority of components are fitted to a Paxolin panel, as shown here.

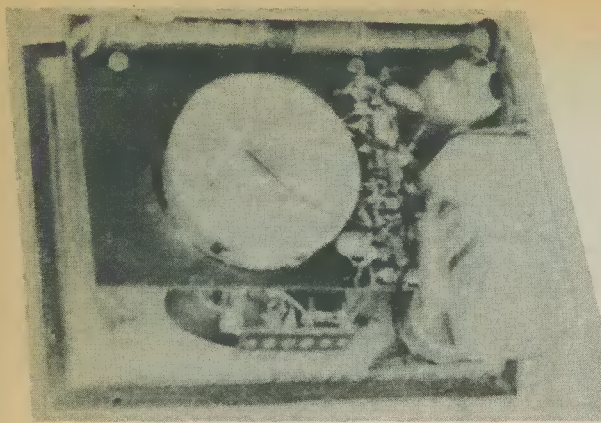

The internal construction of the prototype.


of VR1 at any setting of VC1. When all is well, oscillation should take place over the full range of VC1 with VR1 not too far from its central position.

Switch to long waves. Provided that L3 was correctly set for medium waves, oscillation will be satisfactorily available throughout the range of VC1, although it may be necessary to take VR1 a little further clockwise to obtain oscillation than was needed on medium waves.

If the ferrite aerial employed a ferrite rod other than the blue grade, it may now be necessary to remove a few turns from L1 to obtain the desired medium wave coverage. If necessary, turns may also be taken from L2, but it is doubtful whether this modification will be necessary in practice.

CABINET

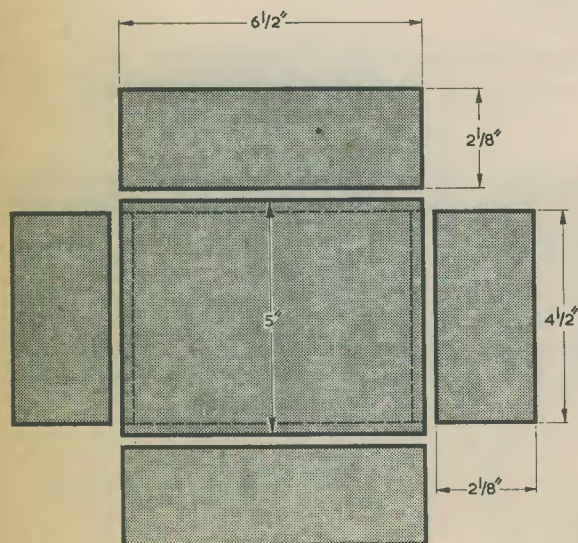A suitable case may be made up, with $\frac{1}{4}$ in. plywood, as shown in Fig. 4. The dimensions given here are for




Material: $\frac{1}{4}$ " plywood

Fig. 4. Making a case for the receiver. The dimensions given are for guidance and may need slight alteration in practice.

guidance only and assume that the plywood panel illustrated in Fig. 2 is made exactly to size and that the plywood of the panel and the case is exactly $\frac{1}{4}$ in. thick. The internal width and height of the case should be such as to fit comfortably over the plywood panel of Fig. 2. The $2\frac{1}{2}$ in. depth of the case corresponds to the instance where, as in the prototype, the Elac 5in. speaker and the slide switch S1 (a) (b) is employed. Other speakers, or other switches, may require the $2\frac{1}{2}$ in. dimension to be increased, whereupon it should be modified accordingly. If the depth of the cabinet is equal to that indicated in Fig. 4, or is only slightly greater, the outside ends of the fixed vane lugs of VC1 will need to be cut off, as mentioned earlier. The connections to these lugs should be unsoldered, the lugs cut short, and the connections re-made. When the case of Fig. 4 has been completed, it can be covered with Fablon or Contact.

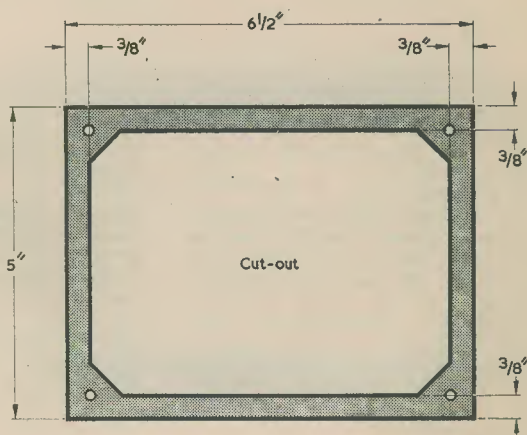Next, cut out a frame of Paxolin or Formica, as illustrated in Fig. 5, again checking exact dimensions.




Material: Paxolin or Formica

Fig. 5. A frame for the front of the receiver.

This frame covers the front edges of the case and the heads of the screws which secure the speaker, and its outside dimensions should be the same as those of the case. It is secured to the front of the plywood panel of Fig. 2 by small wood screws passing through the four holes shown. The receiver assembly, with the frame screwed to it, is then fitted into the case, being secured by wood screws passing through holes in the edge of the frame into the front edges of the case. The holes for these screws are not shown in Fig. 5.

Suitable knobs may be fitted to VR1 and VC1 and a tuning scale and labels for the controls added. The receiver is then complete. ■

In your workshop

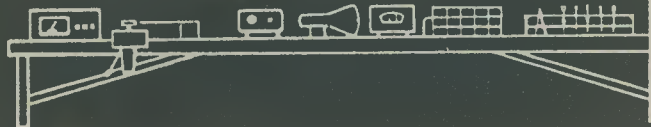

SEATED AT HIS BENCH, SMITHY studied the sheet of paper in front of him. He scratched his head irresolutely, then steeled himself towards making a decision.

"D6," he called out.

On the other side of the workshop, Dick gazed down at another sheet of paper. He picked up a pencil and made a mark at the point indicated by Smithy.

"Nothing," he called out cheerfully.

"Are you sure?"

"Absolutely positive," replied Dick.

"It's my go now and I'll have a bash at F6."

"Did you say F6?"

"I did."

"Then darn it all," snorted Smithy irritably. "You've scored your second hit on my battleship. Blow me, I've lost two subs, one destroyer and a cruiser, and now you've had two hits at my battleship. And you still say that I haven't hit anything of yours yet."

"That's right," replied Dick promptly. "You've been missing me all along up to now. Mind you, you've got very close at times."

"Well, I'll have another go," stated Smithy. "I'll try E7. There *must* be something there."

Dick examined his paper.

"Nope," he remarked happily. "You've missed again."

DETECTOR DIODES

Smithy threw his pencil down on his bench in disgust.

"I just," he remarked, "don't seem able to locate any of your ships."

Dick chuckled.

"You're as useful in detecting my ships," he grinned, "as a silicon diode

would be at detecting a.m. signals!"

Smithy considered this remark judicially.

"I don't think that's a very good comparison."

"Why not?" replied Dick. "You're no good at detecting ships and a silicon diode is no good at detecting a.m. signals."

"You *could* use a silicon diode as an a.m. detector," commented Smithy, thoughtfully, "provided it had a sufficiently fast response and low self-capacitance."

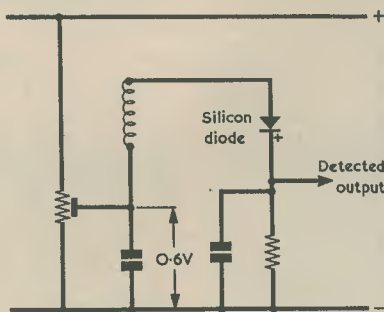


Fig. 1. Although not an attractive choice, it would be possible to use a silicon diode of sufficiently fast response and low self-capacitance as a detector by biasing it in the manner shown here. The r.f. signal appears across the coil, and both capacitors have a low reactance at radio frequency

This month we find Dick and Smithy engaged in a little recreational interlude. Also, Dick takes advantage of the situation to tap the Serviceman's brains on the basic aspects of a.m. diode detectors.

"Oh, come off it, Smithy," said Dick scornfully. "For a start, a silicon diode doesn't start to conduct until there's a forward voltage of around 0.6 volt across it. It wouldn't even notice the small signals and it would distort all the big ones!"

"It could work as a detector if you biased it so that it was just on the point where it started to conduct," replied Smithy. "It certainly wouldn't be a very attractive circuit, but the idea should be quite feasible, nevertheless." (Fig. 1.)

"What would be the point of providing a bias supply?" objected Dick. "You can use a point-contact germanium diode as a straightforward detector without any bias at all."

"You haven't been looking at your transistor radio circuits very closely," commented Smithy. "In nearly all transistor a.m. superhets the germanium diode detector has forward bias applied to it."

"You must be joking, Smithy," protested Dick. "Why, all you have in a transistor a.m. detector circuit is the secondary of the last i.f. transformer coupling into the diode and diode load in series, plus the usual i.f. filter resistor and capacitors, of course. There's no bias there." (Fig. 2.)

"I'll agree," conceded Smithy in reply, "that circuits like that are used occasionally in transistor radios. But you won't find them very often, and the vast majority of sets have the a.m. diode forward biased. Don't forget that even a germanium diode doesn't pass forward current until the voltage across it is around 0.1 to 0.2 volt. Giving it a small level of bias brings it on to a more linear part of its characteristic."

"Where does the bias come from, RADIO & ELECTRONICS CONSTRUCTOR

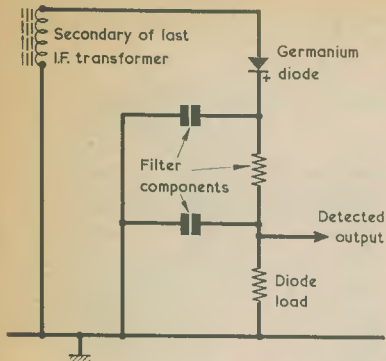


Fig. 2. A practicable diode detector circuit employing a germanium point-contact diode

then?"

"From the a.g.c. circuit," replied Smithy promptly. "The normal form of a.m. detector consists of the secondary of the last i.f. transformer feeding via the diode into the diode load, together with the i.f. filter components, just as you said. But also connected to the upper end of the diode load or the filter resistor is a resistor which takes an automatic gain control voltage back to one or more of the i.f. transistors. If the set uses p.n.p. i.f. transistors the diode will be connected so that the voltage at the upper end of the diode load goes more positive as signal strength increases. This positive voltage is passed to the base or bases of the controlled transistor or transistors, and reduces the i.f. gain accordingly." (Fig. 3.)

"Well?"

"If the circuit is examined closely," went on Smithy, "it can be seen that, in the absence of signal, there is a small forward current flowing from the positive supply rail, through the secondary of the last i.f. transformer, through the diode and then through the a.g.c. circuit to the negative supply rail. This circuit automatically ensures that, in the absence of signal, the diode detector is always forward biased up to the point at which it starts to conduct. If the set has n.p.n. i.f. transistors then the detector diode is turned the other way round and an increasing negative voltage is coupled back to the i.f. transistor base, or bases, as signal strength increases. The diode is still forward biased in the absence of signal because the supply polarity is also reversed." (Fig. 4.)

REVERSE BIAS

Dick absorbed this information for some moments.

"Humph," he remarked musingly. "I can see what you're getting at now. At any rate, when a signal is present

the diode should be well and truly forward biased."

"No, it won't," replied Smithy. "In the presence of signal the diode becomes reverse biased!"

"It becomes what?"

"It becomes reverse biased," confirmed Smithy. "Well now, I don't want to spend the rest of this lunch-break talking about diodes, so let's get back to our game of Battleships. Whose go is it?"

"Mine," said Dick absently. "F5." "F5?" repeated Smithy furiously. "Stap me, you've hit my battleship again. And you don't even seem to be trying."

And, indeed, judging from Dick's expression, it was obvious that his thoughts were far removed from naval engagements.

"How the deuce," he pursued doggedly, "can a detector be reverse biased in the presence of signal?"

"Oh, to heck with the diode," said Smithy impatiently. "It's my turn now and I'll try B4."

Dick looked down carelessly and made a mark on his paper with a pencil.

"You've hit a sub," he remarked indifferently. "Now, what about this diode?"

"I've hit a sub?" repeated Smithy

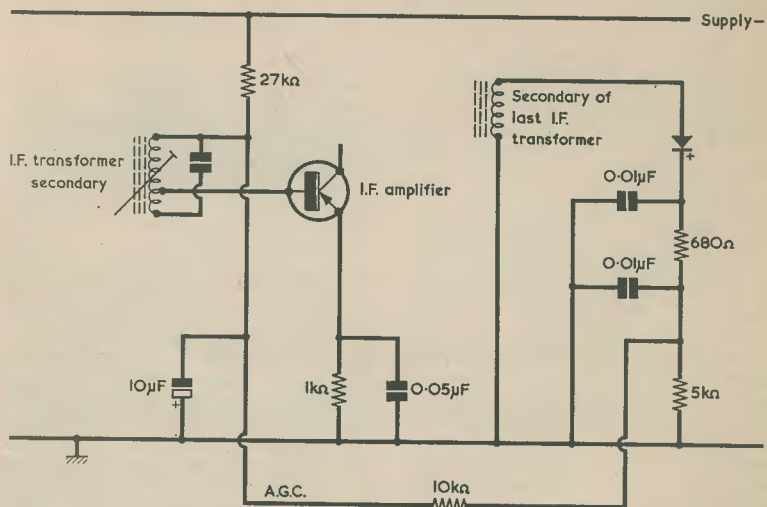


Fig. 3. A typical detector and a.g.c. circuit in a receiver having a negative supply rail and p.n.p. i.f. transistors. Frequently, the a.g.c. voltage is applied to two i.f. transistors instead of only one

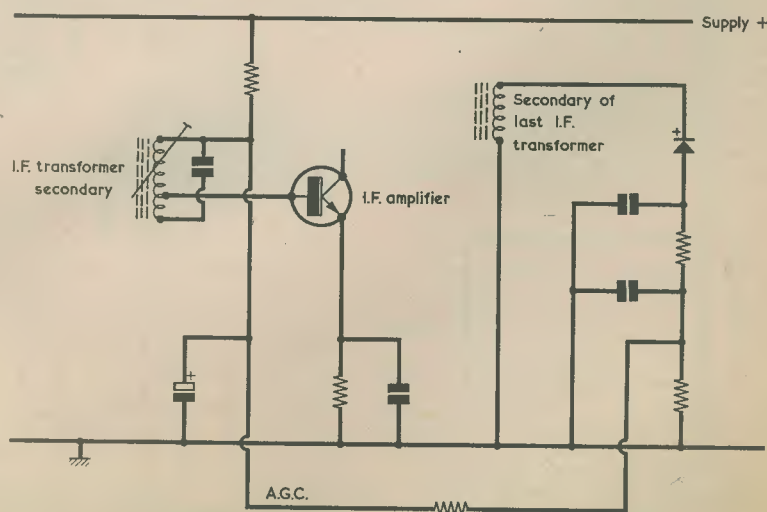


Fig. 4. If the receiver has n.p.n. i.f. transistors, the upper supply rail is positive and the diode detector polarity is reversed

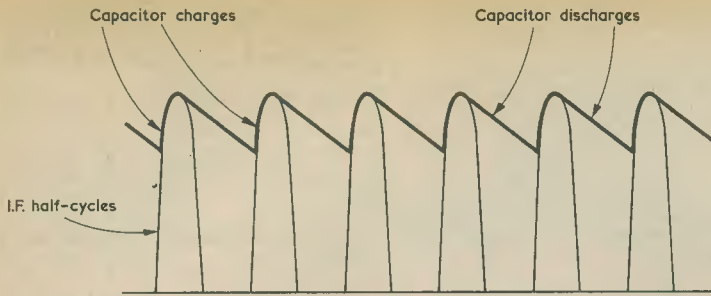


Fig. 5. When an unmodulated i.f. signal is applied to a detector diode, such as that of Fig. 3, the voltage across the first bypass capacitor resembles that shown here in heavy line

jubilantly. "Hooray, blood at last! What's this about a diode?"

"Why," persevered Dick, "is the detector diode reverse biased in the presence of signal?"

"Because of the charge in the capacitor across the diode load and filter resistor," explained Smyth. "That is to say, the filter bypass capacitor which immediately follows the diode. This capacitor charges up like the reservoir capacitor in a half-wave power supply circuit, with the exception that it discharges further between half-cycle tips than a reservoir capacitor of normal value would. Assume for the moment that an unmodulated r.f. carrier is picked up by the receiver. This will be applied as a steady unmodulated i.f. signal to the diode, which will then conduct on half-cycle peaks. If the diode is connected up with the polarity needed for a set having p.n.p. i.f. transistors, it will conduct on the positive half-cycle tips, with the bypass capacitor discharging slightly into the resistance across it between the tips." (Fig. 5.)

"I can visualise that," said Dick, frowning his brow. "What happens next?"

"Well," said Smyth, "the capacitor becomes charged such that the terminal which connects to the diode cathode is positive, with its other terminal negative. During the periods, between



Fig. 6. The first bypass capacitor following an a.m. detector diode charges up with the polarity shown here, whereupon the diode is reverse biased between half-cycle tips

half-cycle tips, when the diode is not conducting, the diode is then reverse biased due to the voltage across the capacitor." (Fig. 6.)

"Blow me," commented Dick. "It's obvious when you think about it. What happens when the signal is modulated, Smyth?"

"The reverse bias across the diode still corresponds to the voltage across the capacitor," explained Smyth, "but that voltage is now changing in sympathy with the modulation amplitude. The effect you get is that the capacitor discharges between half-cycle peaks and that the average voltage across it is proportional to the modulating voltage. In other words, the modulating a.f. voltage appears across the capacitor together with a certain level of intermediate frequency signal, which has to be filtered off before the modulation signal can be fed to the following a.f. amplifier."

"I suppose," remarked Dick, "that the bigger you make the first bypass

capacitor the lower the intermediate frequency level across the diode load becomes."

"That's true enough," agreed Smyth. "Also, the larger the first bypass capacitor, the greater the amplitude of the detected a.f. signal. This is to be expected, of course, because of the similarity between the capacitor and the reservoir capacitor in a half-wave power supply. When the capacitor has a larger value it discharges less between half-cycle peaks and so the average modulation voltage across it is higher. At the same time, though, you can't make the capacitor too large or you introduce a.f. distortion."

"Do you?" queried Dick. "What sort of distortion would that be; treble cut or something like that?"

"Oh no," replied Smyth. "What happens is that there is distortion of the actual modulation waveform, and it is liable to occur when the modulation amplitude falls very quickly from a high level to a low level. If the bypass capacitor has too high a value it won't discharge down to successive half-cycle peak levels during the fall in modulation amplitude, and it will merely discharge into the load resistance until the voltage across it is sufficiently low for it to start charging on half-cycle tips again." (Fig. 7.)

"I see," said Dick brightly. "Instead of following the modulation waveform, the voltage across the capacitor follows an epicyclic curve."

"A what curve?"

"An epicyclic curve," repeated Dick innocently. "Isn't that what you get when a capacitor discharges into a resistor?"

"You raving binner," snorted Smyth. "What you mean is an exponential curve. The word 'epicyclic' applies to tuning drives, for heaven's sake."

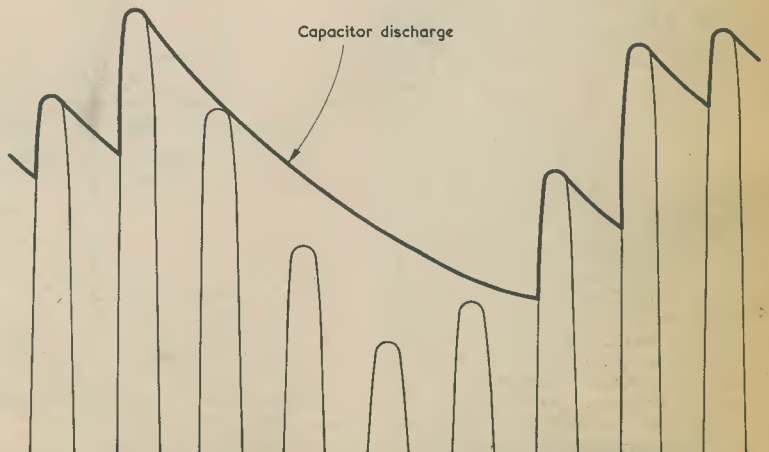


Fig. 7. If the first bypass capacitor has too high a value, the voltage across it may fail to follow the signal modulation when the latter changes quickly from a high to a low level

"Hey," said Dick defensively, "don't get so uptight about it. It's only a word."

"Oh, all right then," grumbled Smyth. "But you always put me right off my stroke when you come out with statements like that. And I don't like that other word you used either: 'uptight'. Nasty horrible modern word with all sorts of sinister connotations."

Wisely, Dick remained silent.

"Well now," grunted Smyth after some moments, "where were we? Oh yes, we'd just got to the point where we'd seen that too high a value of bypass capacitor can cause distortion when the modulation level drops very quickly from a high to a low level. This distortion can only happen when the modulation level falls and not when it rises. If the modulation level rises quickly, the successive half-cycles charge the first capacitor after the diode in the usual manner and the voltage across this capacitor then follows the level of the half-cycle peaks."

TIME CONSTANT

"Would that distortion occur during a quick transient sound?"

"It could," confirmed Smyth. "It could also happen on successive cycles of high frequency sound. If you think about it you'll realise that the distortion is dependent both on the frequency and the amplitude of the modulating signal. It could, for instance, occur with a low amplitude signal having an extremely high frequency, or with a high amplitude signal having a lower frequency. Fortunately, high frequency signals in speech and music normally appear at quite low amplitudes. Also, the higher frequencies are usually reduced in strength at the detector of an average a.m. superhet receiver because the i.f. amplifier cuts down the outer sidebands of the signal. Because of these two factors, the practical problem of preventing the type of distortion we are talking about is not very difficult. As a rule of thumb, it is pretty reasonable to say that we shouldn't have too much trouble if the time constant given by the first bypass capacitor and the diode load and filter resistance is less than the length of a half-cycle of the top audio frequency we expect the receiver to reproduce. Time constant is the time needed for a capacitor to discharge to 37 per cent of the initial voltage across its terminals, and a high frequency signal would have to have a very high amplitude to require the capacitor to discharge as much as all that on downward-going modulation."

"This sounds interesting," said Dick. "Let's try a few actual figures."

"All right," replied Smyth obligingly. "Let's say that the top frequency we expect the receiver to reproduce is 5kHz. Now, the length of a cycle at 5kHz is 0.2 millisecond, or 200 microseconds. So the length of a half-cycle is

100 microseconds. Let's say that the value of the detector diode load plus the filter resistor is $5k\Omega$, which is representative of what is given in many a.m. transistor sets. Now, what capacitance across $5k\Omega$ will give a time constant of 100 microseconds?"

Smyth busied himself with his pencil as he worked out the time constant.

"Ah yes," he remarked, "here we are. The value of capacitance is $0.02\mu F$. Which is pretty well the sort of thing you get in practical transistor a.m. detector circuits."

"What about," asked Dick, "the second bypass capacitor? If the filter resistor has a low value this second capacitor will almost be in parallel with the capacitor which comes immediately after the diode."

"True enough," agreed Smyth. "If the filter resistor has a relatively low value the two capacitors can be looked upon as being in parallel so far as the distortion we are talking about is concerned. Their total value should not then be greater than the calculated value for the single capacitor. If, on the other hand, the filter resistor has a high value then the second bypass capacitor will be less liable to contribute to the distortion and could be largely ignored. But we are speaking in general terms here anyway, and you'll find quite a few transistor a.m. radios whose detector load time constants are longer than the 100 microsecond figure we arrived at in our own example."

"Are there any further types of distortion in an a.m. detector circuit?"

"There's another one, and this is given by what is usually called 'a.c. shunting' or 'a.c. loading'," replied Smyth carelessly. "However, let's get back to our game. Whose go is it next?"

"A.C. shunting, eh?" commented Dick reflectively. "That's something I've never heard of before."

Smyth ignored him.

"Who's got the next turn in this game of Battleships?" he queried sharply.

"Come on, Smyth," wheedled Dick. "It won't take you long to give me the gen on this a.c. shunting business."

"Who," thundered Smyth, "has the next go?"

Reluctantly, Dick allowed his curiosity to diminish for the moment.

"Well, it's my turn," he replied, concentrating on the paper in front of him. "I'll have a stab at F4."

Stricken, Smyth reeled back from his sheet of paper.

"Ye gods," he breathed incredulously. "You've sunk my battleship. You've gone and sunk it, just like that."

He stared unbelievably at his paper. "All right, then," he stated, a note of iron entering his voice. "I'll try A7."

"No hit."

"There must be a hit."

"I tell you, no hit."

Smyth glared at his assistant suspiciously.

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10
Tel: 01-969 3657

KT88 TRANSFORMERS

100-WATT OUTPUT

PRIMARY: 4.5k Ω A-A ULTRA
LINEAR (43% TAPS).

SECONDARY: 0-3-8-15 Ω .

THEY ARE LAYER-WOUND ON
GRAIN ORIENTATED
LAMINATIONS
WITH FREQUENCY RESPONSE
OF 20Hz-20kHz (-3dB)

ONLY £15 EACH inc. P. & P.

MASTER SOUND
56 Ashford Road, Cricklewood
London NW2 6TT.

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road
Bournemouth
Telephone 25232

"You aren't using any right-angled cruisers or things like that, are you?"

"All my vessels are of regulation size and shape," retorted Dick icily. "You wouldn't find better in Jayne's *Fighting Ships*. Anyway, it's my turn again and I'll try D3."

"D3?"

"D3," repeated Dick firmly.

"This is terrible," moaned the shattered Serviceman. "You've just knocked a great chunk out of my second cruiser. Have you got radar over there or something?"

"Of course I haven't," replied Dick airily. "I just use logical deduction, that's all. I'd much rather hear about a.c. shunting than play Battleships, though."

"I'm not," said Smithy, "going to utter another word about electronics until I've had the satisfaction of scoring at least one further hit."

A glint appeared in Dick's eye.

"Aren't you?"

"I am not," averred Smithy. "So let me have another bash at your fleet. I'm going to try B7."

"Did you," asked Dick carelessly, as he marked up his sheet of paper, "say B7?"

"I did," said Smithy. "Now don't keep me in suspense."

"You have," remarked Dick slowly, "hit a destroyer."

"Thank goodness for that! All right, you have a go now."

"E3."

"E3? Blow me, you've hit my cruiser again. Let's have another bash at that destroyer of yours. How about C7?"

Once more, Dick marked up his sheet.

"You have," he announced unemotionally, "sunk my destroyer."

"Oh good," said Smithy happily.


"Success at last."

"Well then," commented Dick, "how about this a.c. shunting effort then."


A.C. SHUNTING

"All right," replied Smithy obligingly. "I'll break off the game for a bit so that I can give you the gen on that. Now, a.c. shunting comes into the picture when you couple a further resistor via a capacitor across the diode load resistor. In practical sound radio circuits you have to do this anyway in order to prevent the mean d.c. level of the detected signal getting through to the following a.f. stage. The mean d.c. level is just the job for providing automatic gain control but, if the diode load were coupled direct to the following a.f. stage, it would upset the biasing for that stage. So the d.c. level has to be blocked off by a capacitor which has a low impedance at audio frequencies. A typical instance is given by having the capacitor couple to a second resistor which is also a volume control." (Fig. 8(a).)


"I can picture a set-up like that,"

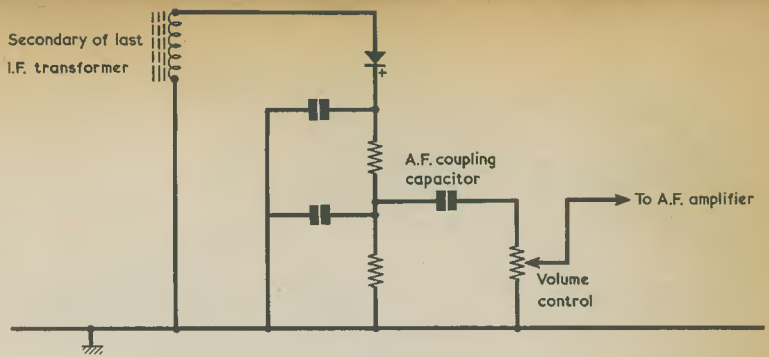

(a)

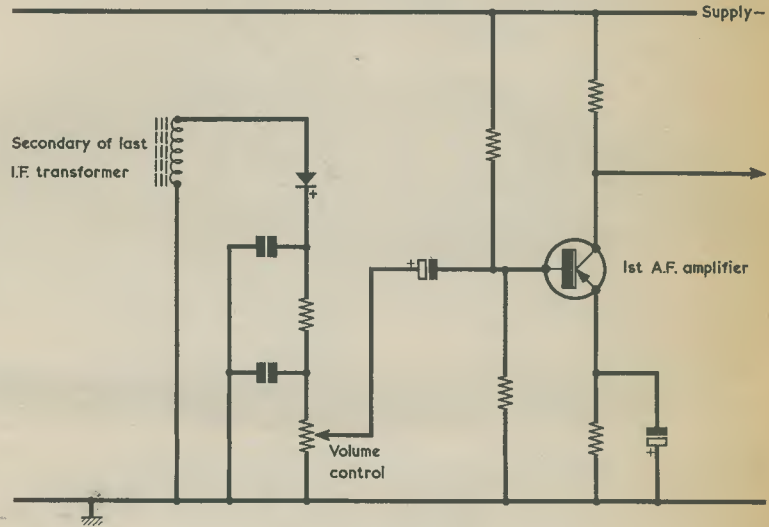

(b)

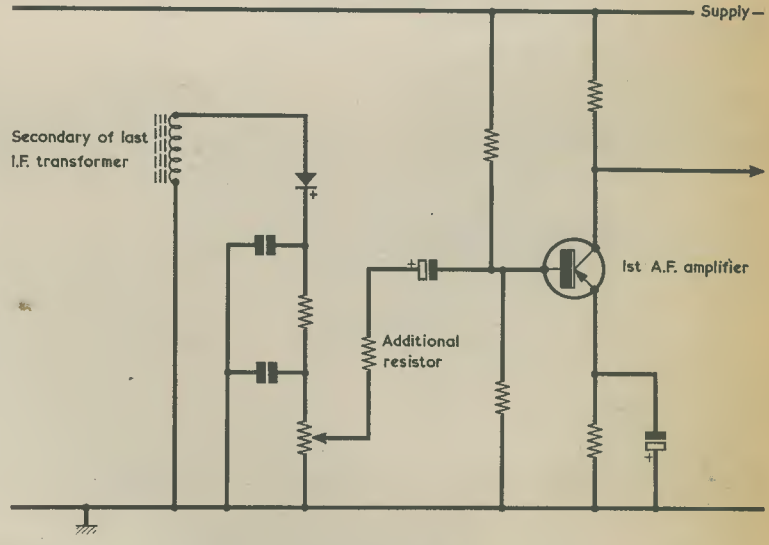

(c)

Fig. 8 (a). Adding an a.f. coupling capacitor and a volume control. This circuit helps to demonstrate a.c. shunting and it should be assumed that the slider of the volume control couples to a device having a high input impedance such as a valve or an f.e.t.

(b). In a practical transistor a.m. detector circuit the diode load is frequently the volume control for the receiver, and its slider couples direct to the base of the first a.f. amplifier

(c). An additional resistor may be inserted in the base circuit of the first a.f. transistor to reduce a.c. shunting

remarked Dick. "It used to be particularly common in the old valve receivers."

"Quite so," concurred Smithy, "and I've chosen it here because it affords a good starting-off point to explain a.c. shunting. With this latest circuit the diode now has two effective loads. One is the d.c. load and, assuming that the filter resistor has a relatively low value, can be considered as being the diode load resistor on its own. And the other is the a.c. load. Since the a.f. coupling capacitor has negligible impedance at modulation frequencies the a.c. load consists of the d.c. load and the volume control track in parallel. Obviously the a.c. load must always have a lower value than the d.c. load. Okay?"

"Yep," said Dick. "Things seem pretty reasonable up to now."

"That's good," responded Smithy. "Because we're now getting to a rather tricky bit. If an unmodulated signal is applied to the diode circuit a direct voltage is built up across the diode load in the usual manner. Also, the current flowing in the diode to keep the first capacitor which appears after it charged up on i.f. half-cycle tips will be the same regardless of whether or not the a.f. coupling capacitor and the volume control are in circuit or not. If, however, we modulate the signal, the diode will pass more current at modulation frequency into the a.c. load than it would into the d.c. load on its own when the modulation goes up; and it will pass less current at modulation frequency into the a.c. load than it would into the d.c. load on its own when the modulation goes down. If the modulation level is high, and the a.c. load is quite a lot smaller than the d.c. load, the diode can actually cut off on the lowermost tips of the modulation waveform; that is, on the parts of the modulation waveform which produce minimum carrier amplitude."

"Blimey," remarked Dick, impressed. "That should cause quite noticeable distortion."

"It will," said Smithy. "The distortion sets in when, approximately, the degree of modulation depth in the signal is greater than the value of the a.c. load divided by the value of the d.c. load. In the old valve sets, a detector of the type we're talking about would be satisfactory in practice if the volume control track had a resistance four times greater than that of the diode load. These values would result in the a.c. load being four-fifths of the d.c. load, and the circuit could cope with modulation depths of up to 80%, which is higher than that transmitted by most a.m. broadcast stations. With transistor receivers, though, it's usual to make the diode load the volume control and couple it via an a.f. coupling capacitor to the base of the first a.f. transistor." (Fig. 8(b).)

"Ah yes," commented Dick. "I know that circuit pretty well off by heart now."

MAY 1974

"It seems to work all right in practice," said Smithy. "In theory, the d.c. load for the diode is the volume control track on its own, plus the small filter resistor which immediately follows the diode. When the volume control is set to maximum the a.c. load then consists of the volume control track with the input impedance of the following transistor in parallel, and this will be considerably lower than the d.c. load. Normally, however, the volume control is only partly advanced from the minimum volume end, whereupon the a.c. shunting given by the following a.f. circuit is only applied across the lower part of the volume control track, and the overall a.c. load is not in consequence much lower than the d.c. load. Distortion on high modulation signals is then only possible when the volume control is at a high setting near the non-earthly end of its track. There are other approaches used in transistor a.m. radios towards seeing that the a.c. load is not too much smaller than the d.c. load. For example, the bypass resistor between the diode and the volume control can be given a higher value, of the order of that of the volume control itself. This ensures that the a.c. shunting is not too great even when the volume control is set to a high level. Again, a high value resistor can be inserted between the volume control slider and the base of the first a.f. transistor. This resistor can have a value which is about the same as that of the volume control." (Fig. 8(c).)

"Couldn't the input impedance of the first a.f. stage be increased?"

"It could," confirmed Smithy. "The input impedance can be increased by negative feedback."

VISION DETECTOR

"Well," said Dick, visibly pleased with the knowledge he had acquired. "I must keep my eyes open for these d.c. and a.c. diode loads in the future. Hang on a minute, I've just had a thought!"

"Oh dear," remarked Smithy unhappily. "I hope you aren't going to open up a whole new discussion."

"I don't think I shall be," said Dick quickly. "What's happened is that it's just occurred to me that the vision i.f. signal in a TV set is also amplitude modulated. Do you have trouble with a.c. and d.c. loads at the vision detector?"

Smithy grinned.

"You don't get any trouble in present-day transistor TV circuits," he chuckled, "because the a.c. and d.c. diode loads are virtually the same! The usual practice is to couple the d.c. diode load direct to the base of the vision emitter follower with no coupling capacitors at all. You then have a delightfully simple arrangement in which there are no problems with the different loads whatsoever." (Fig. 9.)

"That seems to tidy up that ques-

Your Local Supplier

SURREY

WITWORTH TRANSFORMERS

TV Line out-put transformers
Manufacturers of the largest range in the country. All makes supplied.

Modern
BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.
For "By-return" service, contact
London 01-948 3702
Tidman Mail Order Ltd., Dept. R.C.
236 Sandycombe Road,
Richmond, Surrey TW9 2EQ
Callers welcome.

SUSSEX

E. JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

WARWICKSHIRE

Norman H. Field

HI-FIDELITY

Large demonstration room, Sony, Trio, KEF, B & O,
Sanyo, BSR, Toshiba, Goldring, National etc.

TAPE RECORDERS

Sony, Revox, Tandberg, B & O
specialists. Cassette and 8-track

ELECTRONICS

All component parts, cartridges,
stills, radios, Self Build Kits, Disco-
Group and P.A. Equipment.

Norman H. Field

ALBANY HOUSE, HURST STREET,
BHAM B54BJ Tel: 021-622 2323
Specialist Repair Service

EIRE

PEATS for PARTS ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply
Radio & Electronics
Constructor
Data Books and
Panel-Signs Transfers
Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

**NEW PRACTICAL
PAPERBACKS
FROM
FOULSHAM-TAB**

**125 Typical Electronic
Circuits Analysed and
Repaired**

by Art Margolis £1.45

**Understanding and using the
Oscilloscope**

by Clayton Hallmark £1.70

**Pictorial Guide to Colour TV
Circuit Troubles**

by Forest Belt £1.60

**How to Repair Small Petrol
Engines**

by Paul Dempsey £1.75

**Troubleshooting Solid State
Amplifiers**

by Ben Gaddis £1.60

Fun with Electricity

by Tom Kennedy Jr. £1.30

**Transistors — How to Test —
How to Build**

by Tab Editorial £1.20

**How to Fix Radios and
Printed Circuits**

by Leonard C. Lane £1.60

**Handbook of Magnetic
Recording**

by Finn Jorgensen £1.45

**Landsailing from RC Models
to Big Ones**

by George Sipposs £1.45

Small Appliance Repair Guide

by Lemons & Montgomery £1.50

Basic Colour TV Course

by Stan Prentiss £2.20

**Electronics Hobbyist IC
Project Handbook**

by Robert M. Brown £1.40

Radio Communication

Transceiver Servicing

by Burns & Sands £1.45

99 Ways to Use the

Oscilloscope

by Albert Saunders £1.45

On the Colour TV Service

Bench

by Jay Shane £1.45

Basic Radio Course

by John T. Fry £1.50

How to Repair Home and

Car Air Conditioners

by Lemons & Price £1.45

Complete Mini Bike Handbook

by Paul Dempsey £1.85



**FOULSHAM-TAB LTD.
YEOVIL ROAD, SLOUGH, BUCKS.**

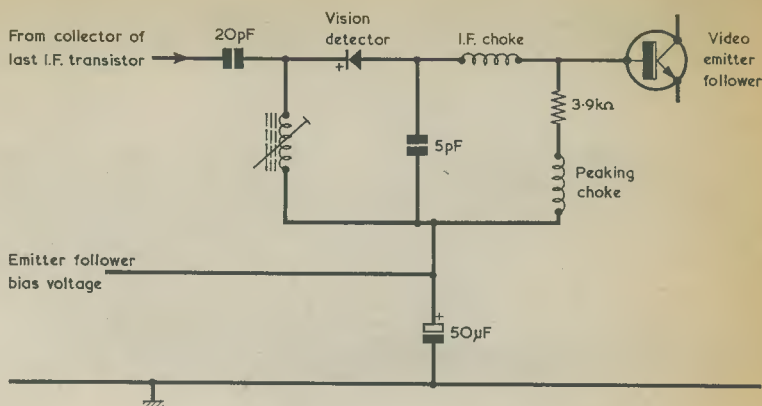


Fig. 9. A basic 625 line vision detector circuit with representative component values. The direct coupling to the emitter follower eliminates a.c. shunting problems

tion," commented Dick. "And it also seems to have cleared up all the queries I had about a.m. diode circuits."

"Thank goodness for that," remarked Smithy, glancing at his watch. "Well, we've still got five minutes left to finish off this game of ours, so let's get back to it. Your go!"

"Is it? Okay then, I'll have a bash at C3."
"Well, stap me," said Smithy delightedly. "For the first time in this game you haven't hit anything. I'll try D4."

"Nothing there."

"Are you sure?"

"Positive."

"I don't believe it," said Smithy, rising from his stool.

He walked quickly over to his assistant's bench and, before the latter could stop him, snatched up Dick's paper.

"Why, you rotten cheat," he expostulated. "You didn't fill in any of your ships at the start at all. You're filling them in now, after I've called out my numbers!"

"And why not?" replied Dick defensively. "Any silly twirp can fill in the ships before the game starts. But it takes a man of skill to enter them after it gets going, because you've then got to bear in mind how many squares are available for the ships as each square gets cancelled off. I've still got room for all my ships in spite of the number of goes you've already had."

"But," protested Smithy, "if we both did that, we'd both call out a lot of meaningless numbers until we got to the inevitable bit at the end where practically every number would result in a hit. There's no point in playing if you don't stick to the rules."

"Mine," replied Dick, "is the 1974 version of the game. Nobody sticks to the rules."

"And you know," stated Smithy grimly, "what the outcome of that is, don't you?"

"No, what is the outcome?"

"Nobody wins."



"It was a snip at £75 — one careful owner and its own distinctive TV programme!"

TWO - WIRE TWO - WAY BUZZERS



**Directional signalling
over two wires.**


By Barrie Gilbert

IT IS OFTEN NECESSARY TO SIGNAL FOR ATTENTION AT either one of two points separated by appreciable distance. For example, a telephone extension in a home can be a nuisance if a call is taken on the wrong receiver - no way is usually available to alert the person for whom the call was intended. Of course, a simple buzzer circuit can be employed, but since signalling is required in both directions a three-wire circuit is sometimes used.

TWO-WIRE SYSTEM

There is a very simple way this requirement can be met with just two wires. The diagram shows how. Diodes across each of the push-buttons allow the circuit to be completed even if only one button is pressed. If, for instance, button A is pressed the diode across button B allows negative half-cycles to pass to the two buzzers. Buzzer B sounds but buzzer A is silent because it is effectively short-circuited by diode D3.

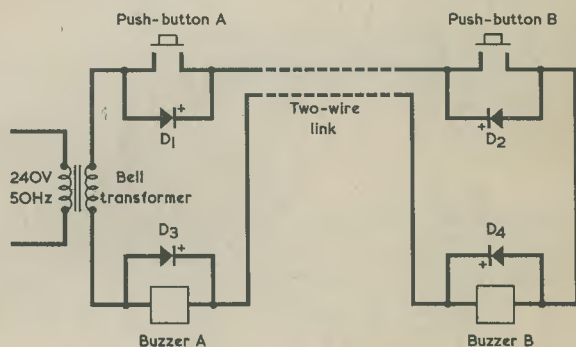Similarly, if button B is pressed, D1 allows positive half-cycles to pass to the buzzers. In this case buzzer B is effectively short-circuited by diode D4 and does not sound.



A two-way signalling system which requires only two inter-connecting wires.

The diodes can be any silicon rectifiers having a forward current rating of 1 amp and a peak inverse voltage rating of 100 volts or more. A high p.i.v. is desirable because some buzzers can produce a high back e.m.f. on operation or on the cessation of current. A suitable type would be the 1N4002. It would also, of course, be possible to employ bells instead of buzzers. ■

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two year old. The cost is the cover price stated on the issue, plus 6p postage.


Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

RADIO MODELLER



ELECTRONIC BOOKS

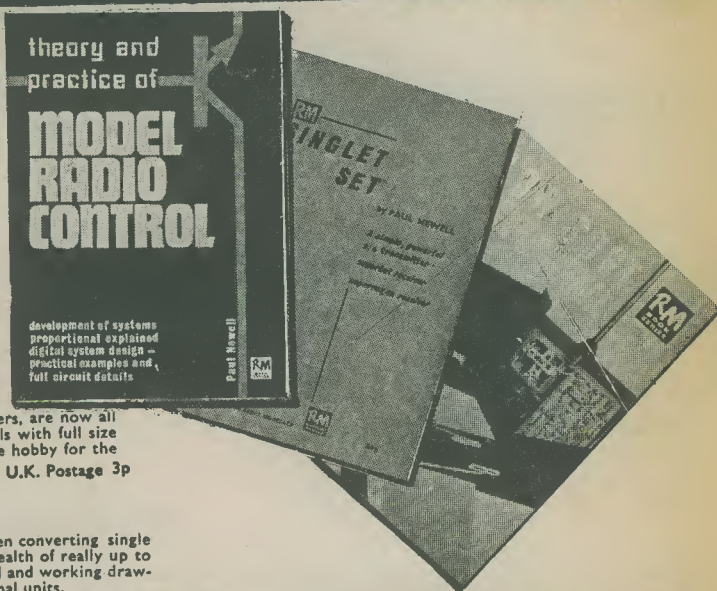

● MODEL RADIO CONTROL

Detailing both Theory and Practice, this book, by leading authority Paul Newell, will become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.

134 pages. Price £2.25 U.K. Postage 13p

● SINGLET SET

The Singlet Transmitter, Superhet and Super-regen receivers, are now all three available in one book. Complete construction details with full size p.c. layout, components list etc. Ideal introduction to the hobby for the home constructor. 20 pages. Price 30p. U.K. Postage 3p

● LOW COST PROPORTIONAL

Modellers who want to save money buy this volume when converting single channel equipment to simple proportional. They find a wealth of really up to date information in the clear descriptions, full size practical and working drawings, plus over a dozen circuit modules for pulse proportional units.

118 pages. Price £1.05 U.K. Postage 11p

ON SALE NOW at all leading shops or direct from:-

RADIO MODELLER, BOOK SALES, 64 Wellington Road, Hampton Hill, Middx.

Simple Short-Wave Receivers

by F. A. Baldwin

140 Pages



★ FOUR BASIC DESIGNS

1, 2 and 3 Valves. In total, six design variations are described, all have been thoroughly air-tested. Fifteen photographs and thirty-nine working diagrams illustrate the construction of the 'Saxon', 'Voyager', 'Explorer' and 'Sentinel' receivers.

★ INTRODUCTION TO SHORTWAVE LISTENING

Radio Wave Propagation Conditions; Aerial and Earth Systems; Broadcast Bands Operating; Identifying Broadcast Stations; Using a Tape Recorder; Reception Reports (Broadcast); Reporting Codes (Broadcast); Specialising; Amateur Band Operating; Reception Reports (Amateur); Reporting Codes (Amateur); CW or Phone?; Clubs and Societies; Receiver Calibration; Operating a Short Wave Receiver; Addresses. Six Tables, two photographs and ten diagrams.

★ WORKSHOP PRACTICE ★ SOLDERING NOTES

★ GENERAL PURPOSE POWER SUPPLY

May be used as a bench supply or for use with two of the basic receiver designs. Two photographs, four working diagrams, Test Table.

80p

P. & P. 6p

TO DATA PUBLICATIONS LTD 57 Maida Vale London W9 1SN

Please supplycopy(ies) of 'Simple Short-Wave Receivers', Data Book No. 19.
I enclose cheque/crossed postal order for

NAME

ADDRESS

BLOCK LETTERS PLEASE

TELEVISION TRANSMISSION FREQUENCIES I


The Table lists vision and sound carrier frequencies for television transmissions in Bands I and III (v.h.f. and 405 lines) and Band IV (u.h.f. and 625 lines). Band I consists of Channels 1 to 5 and Band III of channels 6 to 13. The next Data Sheet will give transmission frequencies in Band V.

Channel	Bands I and III		Band IV		
	Vision Carrier (MHz)	Sound Carrier (MHz)	Channel	Vision Carrier (MHz)	Sound Carrier (MHz)
1	45.0	41.5	21	471.25	477.25
2	51.75	48.25	22	479.25	485.25
3	56.75	53.25	23	487.25	493.25
4	61.75	58.25	24	495.25	501.25
5	66.75	63.25	25	503.25	509.25
6	179.75	176.25	26	511.25	517.25
7	184.75	181.25	27	519.25	525.25
8	189.75	186.25	28	527.25	533.25
9	194.75	191.25	29	535.25	541.25
10	199.75	196.25	30	543.25	549.25
11	204.75	201.25	31	551.25	557.25
12	209.75	206.25	32	559.25	565.25
13	214.75	211.25	33	567.25	573.25
			34	575.25	581.25

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi Fi and Transistors - Up to date
Brochures on request

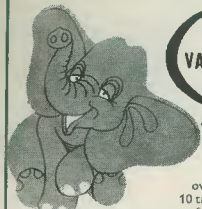
**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept. 1974.



You pay less
VAT with Henry's
Low Prices


BUILD THE TEXAN

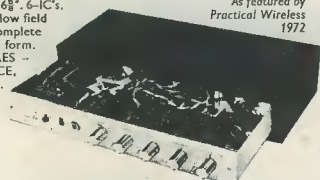**20 + 20 WATT IC
STEREO AMPLIFIER**
As featured by
Practical Wireless
1972



BUILD THE HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators. Tuning meter, AFC, easy to construct and use. Mainly operated. Slim modern design with fibre glass PC, Teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p.) Henry's are sole distributors UK and Europe

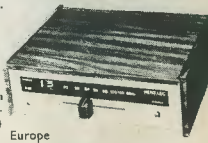

or built and tested
KIT PRICE £21.00 (+ VAT) £24.95 (+ VAT)

Now built and used by thousands of satisfied customers. Features slim design overall size: in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6-IC's, 10 transistors, 2 amplifiers. Gardeners low field transformer. Fibre Glass PC panel, complete chassis work. Now available built and tested as well as in kit form.
HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE - RELIABILITY AND EASE OF CONSTRUCTION FACILITIES.
On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U. Radio Tuner. Aux. Can be altered for Mic., Tape, Tape-head etc. Constructional details Ref. No. 21 30p. Distributed by Henry's throughout UK. **FREE** - Teak cabinet with complete kit.


KIT PRICE £28.50 (+ VAT 50p carr. packing) or built and tested £35.00 (+ VAT 50p carr. packing) as illustrated

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI** A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98-50**
- As above but with Slider Controls **£118.50**
- 100 watt amplifier for above **£49-50**
- SDLS** 100 watt mixer/amplifier with slider controls **£69-00**
- RS 50** watt mixer/amplifier **£49-50**
- R100** 100 watt mixer/amplifier **£57-50**
- DISCO AMP** 100 watt mixer/amplifier **£73-00**
- Northcourt**
- 400 400 watt mixer amp **£37-50**
- 800 80 watt mixer amp **£45-00**
- DISCO MIXER/PREAMPLIFIERS** (OP for up to 6-100 watt amplifiers)
- SDLI** (rotary controls) **£49-50**
- SDLII** (slider controls) **£58-50**
- DISCO VOX** (slider controls) the complete disco pre-amp **£72-00**
- DJ100** 100 watt power amplifier for above **£49-50**
- DJ30L MKII** 3 channel 3kw sound to light **£41-25**
- DJ30L MKII** Slider Controls **£45-50**
- DJ DISCLITE** As 30L/II + variable speed flashes **£54-00**

EXCLUSIVE DECCA KELLY SPEAKERS

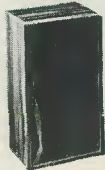12 watt speaker Tweeter systems. 8" Bass Midrange and Melinex Domed HF radiator plus crossover **£12.50** per pair of systems (carr./packg. 40p) or built into veneered cabinets, size 18 x 12 x 6 1/2" **£19-50** pair (carr. £1).



HI FI TAPE EQUIPMENT
U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17). Phone 01-402-4736 for Barclay/Access Card. Direct orders and latest prices.

TRANSISTORS/SEMI-CONDUCTORS
U.K.'s largest range for every application. Small quantity discounts. Also Trade, Export and industrial enquiries invited. Latest stock list (Ref. No. 36) including valves on request.

ELECTRONICS SUPPLIES
Specialists in electronics for more than 30 years. Trade and industry supplies—every type of component and equipment.

Barclaycard/Access, call, write or phone, your order 01-402 4736
EASY TERMS FOR CALLERS

- Carlsbro Reverberation Unit **£44-00**
- Disco anti-feedback microphone **£11-95**
- Cote 150 watt liquid wheel projector **£23-50**
- 150 watt Q1 liquid wheel projector **£50-00**
- 150 watt Q1 and Liquid cassette wheel projector **£50-00**
- Spare Effects cassettes large range of patterns **£6-00**
- 6" Liquid wheels **£5-00** Various cassettes
- Mini spot bank fitted 3 lamps **£12-95**
- Auto Trilite (mini with flashers) **£17-00**
- Bubblemaker with liquid **£22-50**
- Mixer/Mics/Speakers/Lighting UK's largest range U.K.'s largest range of Disco lighting
FREE stock list ref. No. 18 on request.

AKG RESLO DJ CARLSBRO EAGLE MICS, STANDS, MIXERS, CABINETS, CHASSIS & COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURNTABLES, PUBLIC ADDRESS COMPONENTS.




All prices carr. paid (UK) (VAT EXTRA)
Barclaycard/Access, call, write or phone your order 01-723 6963 — easy terms for callers.

FREE LISTS
36 TRANSISTORS IC's
14 100 KITS TO BUILD
17 HI FI TAPE GEAR
2 TRANSISTOR RADIO TO BUILD

LOW COST HI-FI SPEAKERS

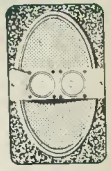SPECIAL OFFERS
EMI 13" x 8" — full range speakers (post 20p each or 30p pair)
*150TC — 8 ohms Twin Cone 10 watt **£2-20** each or **£4-00** pair.
*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms **£3-85** each.
EW 15 watt 8 ohms C/o Tweeter **£5-25** each.
350 20 watt C/o Tweeters, 8 or 15 ohms **£7-80** each.
* Polished wood cabinet **£4-80** post 35p.



SPEAKER KITS (carr. etc. 35p)

20-2	30 watt	£24-50 pair
20-3	40 watt	£35-95 pair
LINTON 2	20 watt	£18-30 pair
GLENDALE 3	30 watt	£32-95 pair
DOVEDALE 3	50 watt	£51-50 pair
KEF KK2		£55-00 pair
KEF KK3		£78-00 pair

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble — that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs. Tangents. Sines etc.



PRICE £19.95 + VAT
Also available assembled **£22.50 + VAT** ready for use

SUPER TESTER 680R— The complete testing system

Volts AC — 11 ranges from 2V to 2500V
Volts DC — 13 ranges from 100mV to 2KV
Amp DC — 12 ranges from 500A to 2KV
Amp AC — 10 ranges from 200A to 5A
Ohms — 6 ranges from one tenth of Ohm to 100MΩ
Reactance — 1 range from 0 to 10MΩ
Capacity — 6 ranges from 0 to 500pF and from 0 to 0.5µF and from 0 to 50,000pF
Frequency — 2 ranges from 0 to 500Hz and from 0 to 5000Hz
Output Voltage — 9 ranges 10V to 2500V
Decibels — 10 ranges from —24 to +70dB

price £18.50

Accessories

Transistor tester	£11.00
Electronic Voltmeter	£18.00
Amplamp	£11.95
Temperature probe	£11.95
Gauss meter	£11.95
Signal Injector	£5.95
Phase Sequence	£5.95
EHT Probe	£5.95
Shunts	
25/50/100A	£4.50

10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E & O E.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404 406 Electronic Components and Equipment 01-402 8381
354 356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA Disco Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open - 9 am - 6 pm
6 days a week
(309 closed
Thursday)
All stores open
all day Saturday