

RADIO ELECTRONICS CONSTRUCTOR

OCTOBER 1980
60p

GO-NO GO TRANSISTOR TESTER



TWO 20dB AMPLIFIERS


Personal MEDIUM WAVE RADIO



ALSO
FEATURED HI-FI P.C.M.

DIRECT SUPPLY SERVICE TO READERS

TOWERS INTERNATIONAL FET SELECTOR

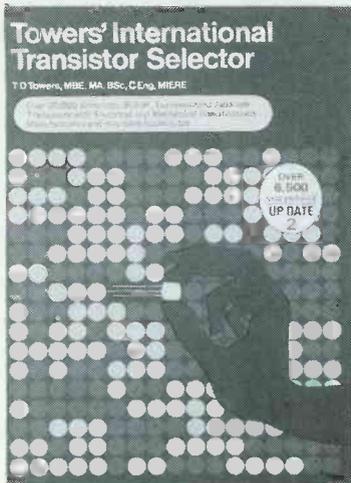

This is dead!



Would this replace it?



If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest!

In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price **£10.35 inc P&P**



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price **£4.00 inc P&P**

(Please allow 21 days for delivery)

**Tower's
International
Transistor
Selector**

by **T. D. Towers**
MBE, MA, BSc, C Eng, MIERE
£10.35
inc. post and packing

To:—**DATA PUBLICATIONS LTD.**
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

(Block capitals)

**Tower's
International
FET
Selector**

by **T. D. TOWERS**
MBE, MA, BSc, C Eng, MIERE
£4.00
inc. post and packing

To:—**DATA PUBLICATIONS LTD.**
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

(Block capitals)

RADIO & ELECTRONICS CONSTRUCTOR

OCTOBER 1980
Volume 34 No.2

Published Monthly

First published in 1947

Incorporating The Radio
Amateur

Editorial and Advertising Offices
57, MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

© Data Publications Ltd., 1980. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$25.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production – Web Offset.

NEWS AND COMMENT

78

CAPACITANCE COMBINATION LOCK
– Suggested Circuit by G. A. French

80

HI-FI P.C.M. – An introduction to pulse code modulation techniques by J. R. Davies

83

TRADE NEWS

87

PERSONAL MEDIUM WAVE RADIO
by R. A. Penfold

88

TWO 20dB AMPLIFIERS – Precise Voltage Gain of 10 Times – Part 1 (2 parts)
by M. V. Hastings

92

GO – NO GO TRANSISTOR TESTER
by A. P. Roberts

96

The INSTRUCTOR – A Practical Introduction to Microprocessors – Part 3 by Ian Sinclair

100

'LISA' 2-BAND PORTABLE. Part 2 (Conclusion) by Sir Douglas Hall, Bt., K.C.M.G.

104

SHORT WAVE NEWS – For DX Listeners
by Frank A. Baldwin

106

AIRING CUPBOARD WARMER
by Owen Bishop

108

SAFETY IN QUARRIES – Trade Note

111

DIGITAL OHMMETER – Product Review

112

IN NEXT MONTH'S ISSUE

113

CROWBAR PROTECTION CIRCUIT
– In Your Workshop

114

RADIO TOPICS by Recorder

120

STRAY AND SELF-CAPACITANCE
Electronics Data No. 62

iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE
WILL BE PUBLISHED
IN LATTER PART
OF OCTOBER

AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS

TBA120S	1.00	KB4113	1.95
L200	1.95	KB4417	1.80
U237B	1.28	TD4420	2.25
U247B	1.28	KB4420B	1.09
U257B	1.28	KB4423	2.30
U267B	1.28	KB4424	1.65
LM301H	0.67	KB4431	1.95
LM301N	0.30	KB4432	1.95
LM308H	0.96	KB4433	1.52
LM308N	0.65	KB4436	2.53
LM339N	0.66	KB4437	1.75
LM348N	1.86	KB4438	2.22
LF351N	0.38	KB4441	1.35
LF353N	0.76	KB4445	1.29
LM374N	3.75	KB4446	2.75
LM380N-14	1.00	KB4448	1.65
LM380N-8	1.00	NE504AN	2.26
LM381N	1.81	NE5532N	1.85
2N419CE	1.95	SD6000	3.75
NE544N	1.80	SL6270	2.03
NE555N	0.30	SL6310	2.03
NE556N	0.30	SL6600	3.75
NE560N	0.50	SL6640	2.75
NE562N	4.05	SL6690	3.20
NE564N	4.29	SL6700	2.35
NE565N	1.00	ICL8038CC	4.50
NE566N	1.60	MSL9362	1.75
NE570N	3.85	MSL9363	1.75
SL624	3.28	HALL1211	1.95
TBA651	1.81	HALL1223	2.15
uA709HC	0.64	HALL1225	1.45
uA709PC	0.36	HALL2002	1.45
uA710HC	0.65	HALL2017	0.80
uA710PC	0.59	HALL2402	1.95
uA741CN	0.66	HALL2411	1.20
uA741CN	0.27	HALL2412	1.55
uA747CN	0.70	LF13741	0.33
uA748CN	0.36	SNT7666CN	0.80
uA753	2.44		
uA758	2.35		
TBA810A	1.09		
TBA820M	0.75		
TCA940E	1.80		
TDA1028	2.11	SAA1056	3.75
TDA1029	2.11	SAA1058	3.35
TDA1054	1.45	11C90DC	14.00
TDA1062	1.95	LM1232	19.00
TDA1072	2.69	LM1242	19.00
TDA1074A	5.04	MSL2318	3.84
TDA1083	1.95	MSM5523	11.30
TDA1090	3.05	MSM5524	11.30
HALL137	1.20	MSM5525	7.85
HALL196	2.00	MSM5526	7.85
HALL197	1.00	MSM5527	9.75
LM1220	1.40	MSM5527A	9.75
TD1303	0.99	ICM7106CP	9.55
LM1307	1.55	ICM7107CP	9.55
MC1310P	1.90	ICM7216B	19.25
MC1330	1.20	ICM7217A	9.50
MC1350	1.20	SP8629	3.85
HALL370	1.90	SP8647	6.00
HALL388	2.75	95H90PC	6.00
TDA1490	1.86	HD10551	2.45
MC1496P	1.25	HD4015	4.45
SL1610P	1.60	HD12009	6.00
SL1611P	1.60	HD44752	8.00
SL1612P	1.60		
SL1613P	1.89		
SL1620P	2.17		
SL1621P	2.17		
SL1623P	2.24		
SL624C	3.28		
SL1625P	2.17		
SL1626P	2.44		
SL1630P	1.62		
SL1640P	1.89		
SL1641P	1.89		
TDA2002	1.25		
TDA2020	3.00		
ULN2242A	3.05		
ULN2823B	1.00		
CA3080E	0.70		
CA3089E	1.84		
CA3090A	3.35		
CA3123E	1.40		
CA3130E	0.80		
CA3130T	0.90		
CA3140E	0.46		
CA3189E	2.20		
MC3357P	2.35		
LM3900N	0.60		
LM3914N	0.68		
LM3915N	2.80		
KB4400	2.80		
KB4406	0.60		
KB4412	1.95		

TTL N and LSN

7400N	0.13	7444N	1.15
74LS00	0.20	7444N-1	1.12
7401N	0.13	7445N	0.94
74LS01	0.20	7445N-1	0.94
7402N	0.14	7448N	0.56
74LS02	0.20	7448N-1	0.56
7403N	0.14	7448S	0.99
74LS03	0.20	7448S-1	0.99
7404N	0.14	7451N	0.17
74LS04	0.24	7451N-1	0.17
7405N	0.18	7451S	0.24
74LS05	0.26	7451S-1	0.24
7406N	0.28	7453N	0.17
7407N	0.38	7453N-1	0.17
7408N	0.17	7454N	0.17
74LS08	0.24	7454N-1	0.17
7409N	0.17	7455N	0.24
74LS09	0.24	7455N-1	0.24
7410N	0.15	7456N	0.17
74LS10	0.24	7456N-1	0.17
7411N	0.20	7457N	0.38
74LS11	0.24	7457N-1	0.38
7412N	0.17	7457S	0.38
7413N	0.30	7457S-1	0.38
7414N	0.51	7458N	0.48
74LS15	0.24	7458N-1	0.48
7416N	0.30	7459N	0.69
7417N	0.30	7459N-1	0.69
7420N	0.16	7459S	1.04
74LS20	0.24	7459S-1	1.04
7421N	0.29	7459S	0.99
7422N	0.27	7459S-1	0.99
7423N	0.27	7459S	0.40
7424N	0.27	7459S-1	0.40
7425N	0.27	7459S	0.49
7426N	0.27	7459S-1	0.49
7427N	0.27	7459S	0.49
7428N	0.44	7459S-1	0.49
7429N	0.38	7459S	0.49
7430N	0.35	7459S-1	0.49
7431N	0.32	7459S	0.49
7432N	0.32	7459S-1	0.49
7433N	0.24	7459S	0.49
7434N	0.25	7459S-1	0.49
7435N	0.24	7459S	0.49
7436N	0.40	7459S-1	0.49
7437N	0.40	7459S	0.49
7438N	0.33	7459S-1	0.49
7439N	0.24	7459S	0.49
7440N	0.17	7459S-1	0.49
7441N	0.24	7459S	0.49
7442N	0.70	7459S-1	0.49
7443N	0.99	7459S	0.49

VOLTAGE REGULATORS

4043	0.85	78Series	0.95
4044	0.80	79Series	1.00
3046	1.30	78MSeries	0.65
4047	0.99	78LSeries	0.35
4049	0.52	79LSeries	0.85
4050	0.65	78MGT2C	1.75
4051	0.65	79MGT2C	1.75
4052	0.65	LM220	0.95
4053	0.65	LM220-1	0.95
4054	0.65	LM220-2	0.95
4055	0.65	LM220-3	0.95
4056	0.26	LM220-4	0.95
4057	0.26	LM220-5	0.95
4058	0.26	LM220-6	0.95
4059	0.20	LM220-7	0.95
4060	0.20	LM220-8	0.95
4061	0.20	LM220-9	0.95
4062	0.20	LM220-10	0.95
4063	0.20	LM220-11	0.95
4064	0.20	LM220-12	0.95
4065	0.20	LM220-13	0.95
4066	0.20	LM220-14	0.95
4067	0.20	LM220-15	0.95
4068	0.20	LM220-16	0.95
4069	0.20	LM220-17	0.95
4070	0.20	LM220-18	0.95
4071	0.20	LM220-19	0.95
4072	0.20	LM220-20	0.95
4073	0.20	LM220-21	0.95
4074	0.20	LM220-22	0.95
4075	0.20	LM220-23	0.95
4076	0.90	LM220-24	0.95
4077	0.90	LM220-25	0.95
4078	0.20	LM220-26	0.95
4079	0.20	LM220-27	0.95
4080	0.20	LM220-28	0.95
4152	0.20	LM220-100	0.95

MICROMARKET

8080A/2	7.50	2C12708	7.50
8212	2.30	2C12714	6.50
8214	3.50	2C12720	5.70
8216	1.95	2C12726	1.70
8224	3.50	2C12732	3.40
8251	6.25	2C12738	7.54
8255	5.40	2C12744	4.50
6800P	7.50	2C12750	1.25
6810	5.95		
6820	7.45		
6850	4.90		
6852	4.85		

VARIACAP

74170N	2.30	74LS112	0.38
74170T	2.30	74LS113	0.38
74171N	2.00	74LS114	0.38
74171T	2.00	74LS118	0.83
74172N	1.15	74120N	1.45
74172T	1.15	74120T	1.45
74173N	0.87	74121N	0.42
74173T	0.87	74121T	0.42
74174N	0.75	74122N	

**DMM
BREAKTHROUGH**



If you want an Autoranging 3½-digit LCD DMM For only **£39.95**

(inc VAT)

We've got to hand it to you!

- * ZERO ADJUSTMENT
- * 3½-DIGIT LCD WITH 200 HRS CONTINUOUS BATTERY LIFE
- * AUTO 'BATT' WARNING
- * FULL AUTORANGING
- * AUTO UNIT DISPLAY
- * CONTINUITY TEST (6110 and 6100 only)
- * 10 AMP AC/DC (6110 and 6220 only)

Introducing the latest professional state-of-the-art 3½-digit DMM – at really old-fashioned prices! From just an unbelievable £39.95 inc. VAT, plus £1.15 p&p!

	6100	6110	6200	6220
RESOLUTION	1mV, 10µA, 0.1Ω on all models			
FULL AUTO RANGING	✓	✓	✓	✓
RANGE HOLD	✓	✓		
UNITS OF MEASUREMENT DISPLAYED	mV, V, mA	mV, V, mA, A	mV, V, mA	mV, V, mA, A
FUNCTIONS DISPLAYED	Ω, KΩ, AUTO, BATT, ADJ, LO. – and AC			
MEASURES DC VOLTAGE TO:	1000V	1000V	1000V	1000V
MEASURES AC VOLTAGE TO:	750V	750V	750V	750V
MEASURES AC/DC CURRENT TO:	200mA	10A	200mA	10A
ZERO ADJUSTMENT	Zeros out minute test-lead resistances for precise measurements			
ACCURACY	0.5%	0.5%	0.8%	0.8%
LOW POWER OHM RANGES	For in-circuit resistance measurements on all models			
BUZZER – Continuity Test	✓	✓		
BUZZER – Over Range Indicator	✓	✓		
COMPLETE WITH	Batteries, pair of Test Leads, Spare Fuse, One Year's Guarantee			
PRICE	ONLY £64.95	ONLY £74.95	ONLY £39.95	ONLY £49.95
p&p	£1.15	£1.15	£1.15	£1.15

Why such a low, low price? Because the A/D converter and display are custom built! This is a genuine top-spec DMM. Check these features for unbeatable value – you won't find a hand-held DMM with these features at these prices again!

I believe you! Please send me the DMM/s as marked.

_____ 6200 @ £41.10 each, inc. VAT, p&p. Total price £ _____
 _____ 6220 @ £51.10 each, inc. VAT, p&p. Total price £ _____
 _____ 6100 @ £66.10 each, inc. VAT, p&p. Total price £ _____
 _____ 6110 @ £76.10 each, inc. VAT, p&p. Total price £ _____

Total cash/cheque enclosed £ _____
 Cheques payable to
 Maclin-Zand Electronics Ltd., please.

Available exclusively from the company that gives you tomorrow's technology today.
 38 Mount Pleasant, London WC1X 0AP.
 Tel. 01-278 7369/01-837 1165

ACCESS orders taken. Please write card no. and signature.

ACCESS NO _____

Name _____

Address _____

Signed _____



Maclin-Zand

Making state-of-the-art affordable

To: Maclin-Zand Electronics Ltd., 38 Mount Pleasant, London WC1X 0AP.
 Despatch by return. For overseas orders, please add £5 to cost of total order package.
 Allow 4-6 weeks for delivery

2REC

CERAMIC PAK

16160 - 24 - 3 of each value - 22pf	AC107	£0.26
27pf 33pf 39pf 47pf 68pf 82pf £0.69	AC113	£0.23
16161 - 24 - 3 of each value - 100pf	AC115	£0.23
120pf 150pf 180pf 220pf 270pf 330pf	AC117	£0.36
390pf £0.69	AC117K	£0.39
16162 - 24 - 3 of each value - 470pf	AC121	£0.23
560pf 680pf 820pf 1000pf 1500pf	AC122	£0.23
2200pf 3300pf £0.69	AC125	£0.21
16163 - 24 - 3 of each value - 4700pf	AC126	£0.21
6800pf 01uf 015uf 022uf 033uf	AC127	£0.21
047uf £0.69	AC128	£0.18
	AC129	£0.18
	AC132	£0.23
	AC134	£0.23
	AC137	£0.23
	AC141	£0.24
	AC142	£0.23
	AC143	£0.23
	AC144	£0.24
	AC145	£0.23
	AC146	£0.23
	AC147	£0.23
	AC148	£0.23
	AC149	£0.23
	AC150	£0.23
	AC151	£0.23
	AC152	£0.23
	AC153	£0.23
	AC154	£0.23

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniatures

16201 - 47mFD-10mFD	£0.69
16202 - 10mFD-100mFD	£0.69
16203 - 100mFD-680mFD	£0.69

CARBON RESISTOR PAKS

16213 - 60 mixed \pm 100 ohms - 820 ohms	£0.69
16214 - 60 mixed \pm 1K ohms - 82K ohms	£0.69
16215 - 60 mixed \pm 10K ohms - 83K ohms	£0.69
16216 - 60 mixed \pm 100K ohms - 820K ohms	£0.69
16217 - 40 mixed \pm 100 ohms - 820 ohms	£0.69
16218 - 40 mixed \pm 1K ohms - 82K ohms	£0.69
16219 - 40 mixed \pm 10K ohms - 82K ohms	£0.69
16220 - 40 mixed \pm 100K ohms - 820K ohms	£0.69
16220 - 40 mixed \pm 1 Meg 10 Meg ohms	£0.69
16231 - 40 mixed \pm 1 Meg - 10 Meg ohms	£0.69

COMPONENT PAKS

16164 - 200 Resistor mixed value approx (Count by weight)	£0.69
16165 - 150 Capacitors mixed value approx (Count by weight)	£0.69
16166 - 50 Precision resistors. Mixed values	£0.69
16167 - 80 \pm resistors. Mixed values	£0.69
16168 - 5 pieces assorted ferrite rods	£0.69
16169 - 2 Tuning gangs MW LV VHF	£0.69
16170 - 1 Pack wire 50 metres assorted colours single strand	£0.69
16171 - 10 Reed switches	£0.69
16172 - 3 Micro switches	£0.69
16173 - 15 Assorted pots	£0.69
16174 - 5 metal jack sockets 3 x 3.5mm 2 x standard switch types	£0.69
16175 - 30 Paper condensers - mixed values	£0.69
16176 - 20 Electrolytics trans types	£0.69
16177 - 1 Pack assorted hardware Nuts, bolts, gromets etc	£0.69
16178 - 5 Mains slide switches, assorted	£0.69
16179 - 20 Assorted tag strips and panels	£0.69
16180 - 15 Assorted control knobs	£0.69
16181 - 3 Rotary wave change switches	£0.69
16182 - 2 Relays 6-24v operating	£0.69
16183 - 1 Pak copper laminate approx 200 sq inches	£0.69
16184 - 15 Assorted Fuses 100mA 5 amp	£0.69
16185 - 50 metres PVC sleeving assorted size and colours	£0.69

METAL FOIL CAPACITOR PAK

16204 - Containing 50 metal foil capacitor like Mullard C280 series - Mixed values ranging from 01uf-2uf. Complete with identification sheet £1.38

SLIDER PAKS

16190 - 6 slider mixed	£0.69
16191 - 6 slider 470 ohms	£0.69
16192 - 6 slider 10K ohms 1in£0.69	£0.69
16193 - 6 slider 22K ohms 1in£0.69	£0.69
16194 - 6 slider 47K ohms 1in£0.69	£0.69
16195 - 6 slider 47K ohms	£0.69

TRANSISTORS

AD162	£0.40	BC151	£0.25	BC441	£0.35	BF165	£0.85	2N1305	£0.21
AD161/162	£0.81	BC152	£0.23	BC460	£0.44	BF167	£0.28	2N1306	£0.29
AD140	£0.63	BC153	£0.29	BC461	£0.44	BF173	£0.23	2N1307	£0.29
AF124	£0.36	BC154	£0.22	BC477	£0.23	BF176	£0.44	2N1308	£0.35
AF125	£0.37	BC157	£0.12	BC478	£0.23	BF177	£0.30	2N1309	£0.35
AF126	£0.38	BC158	£0.12	BC479	£0.23	BF178	£0.32	2N1711	£0.23
AF127	£0.39	BC159	£0.12	BC547	£0.12	BF179	£0.35	2N2219	£0.23
AF128	£0.40	BC160	£0.30	BC548	£0.12	BD239A	£1.15	2N2221	£0.23
AF178	£0.88	BC161	£0.44	BC549	£0.18	240AMP	£0.15	2N2222	£0.23
AF179	£0.89	BC167	£0.14	BC550	£0.16	BF180	£0.35	2N2369	£0.16
AF180	£0.89	BC168	£0.14	BC556	£0.16	BF181	£0.35	2N2711	£0.25
AF181	£0.89	BC169	£0.10	BC557	£0.16	BF182	£0.35	2N2712	£0.25
AF186	£0.58	BC170	£0.10	BC558	£0.14	BF183	£0.35	2N2714	£0.25
AF239	£0.44	BC171	£0.10	BC559	£0.14	BF184	£0.23	2N2904	£0.21
AL102	£1.38	BC172	£0.10	BC569	£0.12	BF185	£0.23	2N2905	£0.21
AL103	£1.38	BC173	£0.10	BC570	£0.12	BF186	£0.23	2N2906	£0.18
AU104	£1.61	BC174	£0.10	BC571	£0.12	BF187	£0.23	2N2907	£0.23
AU110	£1.61	BC175	£0.10	BC572	£0.12	BF188	£0.23	2N2923	£0.17
BC107	£0.09	BC177	£0.18	BC573	£0.12	BF189	£0.23	2N2925	£0.17
BC107B	£0.09	BC178	£0.18	BC574	£0.12	BF190	£0.23	2N2926G	£0.10
BC107C	£0.12	BC179	£0.18	BC575	£0.12	BF191	£0.14	2N2927	£0.09
BC108	£0.09	BC181	£0.10	BC576	£0.12	BF192	£0.18	2N2928	£0.09
BC108A	£0.09	BC182	£0.26	BC577	£0.12	BF193	£0.18	2N2929	£0.09
BC108B	£0.10	BC183	£0.10	BC578	£0.12	BF194	£0.18	2N2930	£0.09
BC108C	£0.12	BC184	£0.10	BC579	£0.12	BF195	£0.18	2N2931	£0.09
BC109	£0.09	BC185	£0.10	BC580	£0.12	BF196	£0.18	2N2932	£0.09
BC109B	£0.12	BC186	£0.10	BC581	£0.12	BF197	£0.18	2N2933	£0.09
BC109C	£0.12	BC187	£0.10	BC582	£0.12	BF198	£0.18	2N2934	£0.09
BC113	£0.18	BC188	£0.26	BC583	£0.12	BF199	£0.18	2N2935	£0.09
BC114	£0.18	BC189	£0.26	BC584	£0.12	BF200	£0.18	2N2936	£0.09
BC115	£0.18	BC190	£0.26	BC585	£0.12	BF201	£0.18	2N2937	£0.09
BC116	£0.18	BC191	£0.26	BC586	£0.12	BF202	£0.18	2N2938	£0.09
BC117	£0.18	BC192	£0.26	BC587	£0.12	BF203	£0.18	2N2939	£0.09
BC118	£0.18	BC193	£0.26	BC588	£0.12	BF204	£0.18	2N2940	£0.09
BC119	£0.18	BC194	£0.26	BC589	£0.12	BF205	£0.18	2N2941	£0.09
BC120	£0.18	BC195	£0.26	BC590	£0.12	BF206	£0.18	2N2942	£0.09
BC121	£0.18	BC196	£0.26	BC591	£0.12	BF207	£0.18	2N2943	£0.09
BC122	£0.18	BC197	£0.26	BC592	£0.12	BF208	£0.18	2N2944	£0.09
BC123	£0.18	BC198	£0.26	BC593	£0.12	BF209	£0.18	2N2945	£0.09
BC124	£0.18	BC199	£0.26	BC594	£0.12	BF210	£0.18	2N2946	£0.09
BC125	£0.18	BC200	£0.26	BC595	£0.12	BF211	£0.18	2N2947	£0.09
BC126	£0.18	BC201	£0.26	BC596	£0.12	BF212	£0.18	2N2948	£0.09
BC127	£0.18	BC202	£0.26	BC597	£0.12	BF213	£0.18	2N2949	£0.09
BC128	£0.18	BC203	£0.26	BC598	£0.12	BF214	£0.18	2N2950	£0.09
BC129	£0.18	BC204	£0.26	BC599	£0.12	BF215	£0.18	2N2951	£0.09
BC130	£0.18	BC205	£0.26	BC600	£0.12	BF216	£0.18	2N2952	£0.09
BC131	£0.18	BC206	£0.26	BC601	£0.12	BF217	£0.18	2N2953	£0.09
BC132	£0.18	BC207	£0.26	BC602	£0.12	BF218	£0.18	2N2954	£0.09
BC133	£0.18	BC208	£0.26	BC603	£0.12	BF219	£0.18	2N2955	£0.09
BC134	£0.18	BC209	£0.26	BC604	£0.12	BF220	£0.18	2N2956	£0.09
BC135	£0.18	BC210	£0.26	BC605	£0.12	BF221	£0.18	2N2957	£0.09
BC136	£0.18	BC211	£0.26	BC606	£0.12	BF222	£0.18	2N2958	£0.09
BC137	£0.18	BC212	£0.26	BC607	£0.12	BF223	£0.18	2N2959	£0.09
BC138	£0.18	BC213	£0.26	BC608	£0.12	BF224	£0.18	2N2960	£0.09
BC139	£0.18	BC214	£0.26	BC609	£0.12	BF225	£0.18	2N2961	£0.09
BC140	£0.18	BC215	£0.26	BC610	£0.12	BF226	£0.18	2N2962	£0.09
BC141	£0.18	BC216	£0.26	BC611	£0.12	BF227	£0.18	2N2963	£0.09
BC142	£0.18	BC217	£0.26	BC612	£0.12	BF228	£0.18	2N2964	£0.09
BC143	£0.18	BC218	£0.26	BC613	£0.12	BF229	£0.18	2N2965	£0.09
BC144	£0.18	BC219	£0.26	BC614	£0.12	BF230	£0.18	2N2966	£0.09
BC145	£0.18	BC220	£0.26	BC615	£0.12	BF231	£0.18	2N2967	£0.09
BC146	£0.18	BC221	£0.26	BC616	£0.12	BF232	£0.18	2N2968	£0.09
BC147	£0.18	BC222	£0.26	BC617	£0.12	BF233	£0.18	2N2969	£0.09
BC148	£0.18	BC223	£0.26	BC618	£0.12	BF234	£0.18	2N2970	£0.09
BC149	£0.18	BC224	£0.26	BC619	£0.12	BF235	£0.18	2N2971	£0.09
BC150	£0.18	BC225	£0.26	BC620	£0.12	BF236	£0.18	2N2972	£0.09
BC151	£0.18	BC226	£0.26	BC621	£0.12	BF237	£0.18	2N2973	£0.09
BC152	£0.18	BC227	£0.26	BC622	£0.12	BF238	£0.18	2N2974	£0.09
BC153	£0.18	BC228	£0.26	BC623	£0.12	BF239	£0.18	2N2975	£0.09
BC154	£0.18	BC229	£0.26	BC624	£0.12	BF240	£0.18	2N2976	£0.09
BC155	£0.18	BC230	£0.26	BC625	£0.12	BF241	£0.18	2N2977	£0.09
BC156	£0.18	BC231	£0.26	BC626	£0.12	BF242	£0.18	2N2978	£0.09
BC157	£0.18	BC232	£0.26	BC627	£0.12	BF243	£0.18	2N2979	£0.09
BC158	£0.18	BC233	£0.26	BC628	£0.12	BF244	£0.18	2N2980	£0.09
BC159	£0.18	BC234	£0.26	BC629	£0.12	BF245	£0.18	2N2981	£0.09
BC160	£0.18	BC235	£0.26	BC630	£0.12	BF246	£0.18	2N2982	£0.09
BC161	£0.18	BC236	£0.26	BC631	£0.12	BF247	£0.18	2N2983	£0.09
BC162	£0.18	BC237	£0.26	BC632	£0.12	BF248	£0.18	2N2984	£0.09
BC163	£0.18	BC238	£0.26	BC633	£0.12	BF249	£0.18	2N2985	£0.09
BC164	£0.18	BC239	£0.26	BC634	£0.12	BF250	£0.18	2N2986	£0.09
BC165	£0.18	BC240	£0.26	BC635	£0.12	BF251	£0.18	2N2987	£0.09
BC166	£0.18	BC241	£0.26	BC636	£0.12	BF252	£0.18	2N2988	£0.09
BC167	£0.18	BC242	£0.26	BC637	£0.12	BF253	£0.18	2N2989	£0.09
BC168	£0.18	BC243	£0.26	BC638	£0.12	BF254	£0.18	2N2990	£0.09
BC169	£0.18	BC244	£0.26	BC639	£0.12	BF255	£0.18	2N2991	£0.09
BC170	£0.18	BC245	£0.26	BC640	£0.12	BF256	£0.18	2N2992	£0.09
BC171	£0.18	BC246	£0.26	BC641	£0.12	BF257	£0.18	2N2993	£0.09
BC172	£0.18	BC24							

SPECIAL OFFER BARGAIN PACKS

RESISTORS

Mixed Pack of 1/4, 1/3 and 1/2 watt Resistors; approx 500 items
Price: £2.75

ELECTROLYTICS

Mixed Pack of 150 off Radial and Axial lead Electrolytics Wide range; modern type
Price: £2.75

CAPACITORS

Mixed Pack of Ceramic, Silver Mica, Polystyrene, Mixed Dielectric, etc. capacitors, 1kg.
Price: £1.00

POLYESTERS

Mixed Pack of 100 off Radial and Axial lead Polyester capacitors.
Price: £2.25

DIODES

Mixed Pack of 50 off Diodes.
Price: £1.00

PRESETS

Mixed Pack of 50 off Sub-min Presets, Vert. and Horiz. 15 different values.
Price: £2.00

GROMMETS

Mixed Pack of 100 off Rubber Grommets.
Price: 75p

TTL IC's

Mixed Pack of 50 off TTL I.C.'s Full spec., clearly marked. 15 different types. Data sheet supplied.
Price: £3.00

TRANSISTORS

Mixed Pack of 50 off Transistors.
Price: £2.25

PC BOARD AND ETCH PENS

5 pieces bonded paper, copper clad single sided P.C. Board, approx size 2" x 8 1/2" and two etch resist pens.
Price: 85p

POTENTIOMETERS

Mixed Pack of 25 off Potentiometers.
Price: £2.50

COMPONENTS

Mixed Pack of Components including transistors, resistors, I.C.'s, diodes, capacitors, etc. Ideal for beginners. Data sheets supplied.
Price: £2.25

BITS AND PIECES

Mixed Pack of Bits and Pieces including plugs, sockets, switches, wire, terminal block, ear-piece, etc.
Price: £2.50

LOW PROFILE DIL I.C. SOCKETS

8 pin	10p
14 pin	12p
16 pin	13p
18 pin	15p
20 pin	16p
22 pin	18p
24 pin	19p
28 pin	24p
40 pin	34p

L.E.D.'s

Red .2	12p
Green .2	21p
Yellow .2	21p
Red .125	12p
Green .125	21p
Yellow .125	21p

uA 741 8 pin	26p
NE555 8 pin	32p

SWITCHES

Push to Make	16p
Push to Break	22p
SPST Toggle	44p
DPDT Toggle	49p

BATTERY CLIPS



PP3	7p
PP9	16p

HARRISON BROS.

P.O. Box 55,
 Westcliff-on-Sea, Essex

ALL PRICES INCLUDE V.A.T. AND P. & P.
 Please add £1 handling charge to all orders
OUR NEW CATALOGUE IS NOW AVAILABLE.
SEND 50p FOR YOUR COPY

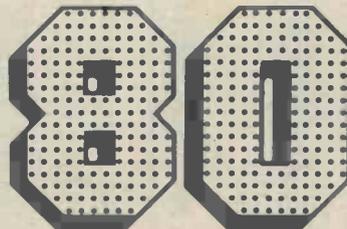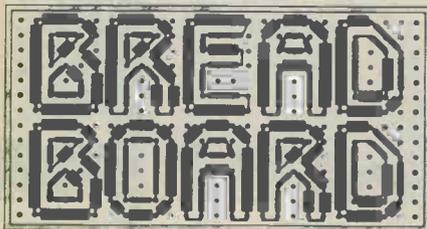COMPUTERS AUDIO RADIO MUSIC LOGIC TEST GEAR CB GAMES KITS



26th Nov — WEDNESDAY — 10am-6pm
 27th Nov — THURSDAY — 10am-8pm
 28th Nov — FRIDAY — 10am-6pm
 29th Nov — SATURDAY — 10am-6pm
 30th Nov — SUNDAY — 10am-4pm

COMPONENTS DEMONSTRATIONS SPECIAL OFFERS MAGAZINES BOOKS

Royal Horticultural Halls Elverton Street

Westminster London SW1

November 26-30 1980

It's all at Breadboard '80

This is **the** exhibition for the electronics enthusiast. From November 26-30 there is only one place in the universe for the electronics enthusiast to be — Breadboard '80, at the Royal Horticultural Hall in London. The majority of leading companies will be exhibiting, including all the top monthly magazines in the field. There will be demonstrations on most stands and many feature special offers that are **EXCLUSIVE** to Breadboard!

All aspects of this fascinating field are catered for, from CB to home computing, so whether you want to buy a soldering iron or a synthesiser — or just keep up to date with your hobby — don't miss Breadboard '80.

AVOID QUEUES — GET ADVANCE TICKETS

Send to: Advance Tickets, Modmags Ltd,
 145 Charing Cross Rd, London WC2H 0EE

Please send: tickets @ £1.50

..... tickets @ £1.00 (Student/Child/OAP)

TO:

.....

.....

.....

.....

I enclose P.O./Cheque for £

TRANSISTORS

AC126	16p	BD235	35p	MJE2371	80p	2N3054	35p
AC127	16p	BD238	25p	M 11 15 Russian	25p	2N3055RCA	68p
AC128	5p	BD239C	29p	M 11 4/A Russian	25p	2N3133	24p
AC153	11p	BD242	30p			2N3283	25p
AC176	11p	BD240	30p	MPF131 Dual	15p	2N3418	15p
AC188	10p	BD243/B 65Wt	30p	MOSFET	15p	2N3553	56p
AC198	10p	BD244C	30p	MPU131 Prog. Uni. J.	15p	2N3583	18p
AC212	20p	BD246	32p			2N3614	75p
AC228	22p	BD253	44p	MRF502 Improved		2N3645	3p
AD161/162	70p	BD375	35p	BFY90	50p	2N3703	3p
match pair		BD437	35p	16A Russian	23p	2N3704	3p
AF119	35p	BD438	28p	142A Russian	25p	2N3707	3p
AF124	27p	BD677 60v 40w	50p	NKT A49	23p	2N3711	3p
AF127	27p	BD678 Pwr. Darl.	50p	NKTAS2	20p	2N3714 80v 150w	54p
AF139	23p	BDX33B Pwr Darl.	50p	NKTBS4	30p	2N3794	14p
AF178	35p	BDX34B Pwr. Darl.	50p	NKT152	38p	2N3799	18p
AF180	35p			NKT153	24p	2N3823 FET	25p
AF181	33p			NKT154	26p	2N3906	8p
AF239	35p			NKT251	18p	2N4000	15p
ASV60	35p			NKT775	16p	2N4026	15p
ASV63	4p			NKTME2	13p	2N4031	15p
ASV73	35p			OC41	4p	2N4062	4p
ASZ21	4p			OC42	21p	2N4285	17p
AC176A/B/C	14p			OC43	23p	2N4891	30p
AU113	1.03p			OC44	4p	2N4898 40v 25w	36p
AU110	70p			OC45	13p	2N4900 80v 25w	36p
BC107A/B	6p			OC71	4p	2N4918	15p
BC108A/B/C	6p			OC72 (XK120)	4p	2N5058 (BF259)	11p
BC109B/C	6p			OC76	15p	2N5147	15p
BC125B	3p			OC77	46p	2N5247	40p
BC140	45p			OC81 (XK122)	4p	2N5293	30p
BC141	11p			OC84	30p	2N5295	30p
BC147A/B/C	5p			OC89	41p	2N5296 60v 36w	30p
BC148A/B/C	5p			OC200	66p	2N5449	3p
BC149A/B/C/S	5p			OC201	66p	2N5484	37p
BC154	7p			OC603	50p	2N5492 75v 50w	36p
BC157A/B	5p			OC710	23p	2N5494 60v 50w	36p
BC158A/B	5p			P346A	24p	2N5915 (16068)	47p
BC159B/C	5p			P7029	30p	450Mhz 6VLT R.F. 12v	56p
BC171B	4p			PXB103	25p		£2.50
BC172	6p			RCP701A/B/D	10w	2N5927	36p
BC172c	7p					2N5954 P, 80v, 40w	2.2
BC173	4p			R1039 (2010)	54p	2N6028 PUJT	3p
BC177A	10p			R2008B	£1.18	2N6124	24p
BC178A/B/C	10p			R2010B	£1.18	2N6178 100v 25w	30p
BC179B	14p			R2540	£1.70	2N6211 275v 35w	56p
BC182/AL	5p			S3017	25p	2N6254	36p
BC182L	3p			S8240	26p	2N6290 60v 16w	30p
BC183A/AL/L/LC	3p			SFT357	26p	2N6292 80v 16w	30p
BC184L	3p			SJES039	8p	2N6385 Pwr. Darl. 54p	
BC186	21p			SL102	40p	2N6486 40v 75w	36p
BC187	8p			TE896	£1	2N6488 90v 75w	36p
BC204	11p			TIP30	22p	2S701	18p
BC212L/B	5p			TIP31	22p	2SA12	42p
BC213L	5p			TIP32C	22p	2SA50	36p
BC213LA	3p			TIP48	33p	2SA83	36p
BC213LB	4p			TIS60GY	3p	2SA141	36p
BC214B	5p			TIS61	3p	2SA142	36p
BC214L	3p			TIS73L	4p	2SA234	30p
BC237A	7p			TIS91	3p	2SA235	50p
BC238	5p			TIS92GY	14p	2SA354	38p
BC238B/C	7p			TIS98	3p	2SA360	34p
BC239C	7p			TK24	20p	2SA367	56p
BC251	3p			V435	20p	2SA518	38p
BC257B	7p			U14710	20p	2SA634	80p
BC258B/C	7p			ZT403P	30p	2SB56	18p
BC259C	7p			ZT1486	£1.10	2SB75	25p
BC302	15p			ZTX300	9p	2SB77	25p
BC304	15p			ZTX327	18p	2SB135	25p
BC307	7p			ZTX341	9p	2SB136	25p
BC308B/C	7p			ZG103	33p	2SB156	60p
BC309B	7p			ZG302	12p	2SB175	20p
BC327	5p			ZG309	30p	2SB176	20p
BC328	6p			ZG329	20p	2SB187	25p
BC338	5p			ZG371	18p	2SB457	25p
BC382L	7p			2N456A	71p	2SD315D	80p
BC384B	7p			2N597	16p	40235	50p
BC386	5p			2N598	16p	40250	36p
BC347A/B	5p			2N601	£1.50	40250VI (2N3054 + Ht. sink)	40p
BC348A/B/C	5p			2N644	22p	40316 40v, 50w	36p
BC349C	5p			2N706A	10p	40372 (2N3054 + Ht. sink)	40p
BC356	5p			2N708	9p	40349v2 160v 1w	30p
BC357B	5p			2N718	9p	40394 60v 1w	30p
BC358A	5p			2N914	15p	40409 + Ht. sink 90v	180
BC359	5p			2N918	12p	3w	40p
BC612L	4p			2N929	16p	40410 + Ht. sink 90v	240
BCW71R	1p			2N984	28p	40602 VHF Mosfet	350
BCX32	10p			2N987	45p	40633 NPN 40w	36p
BCX34	10p			2N1091	16p	40816	30p
BCX36	10p			2N1132	14p	40911 (2N6261 + Ht. sink)	40p
BCY11	28p			2N1302	16p		
BCY31	10p			2N1303	16p		
BCY56	59p			2N1395	25p		
BCY70	8p			2N1484	36p		
BCY71	8p			2N1485 60v 25w	36p		
BCY72	8p			2N1487	90p		
BCY79B	15p			2N1490	30p		
BD113	32p			2N1500	30p		
BD115	35p			2N1507	18p		
BD132	45p			2N1711	13p		
BD133	28p			2N1716	15p		
BD136	22p			2N1748	28p		
BD137	14p			2N192A	15p		
BD138	28p			2N2221/A	8p		
BD137/8 mtch pr	60p			2N2222A	8p		
BD139	17p			2N2269	10p		
BD140	26p			2N2401	7p		
BD142	35p			2N2412	27p		
BD156	50p			2N2483	28p		
BD182p	70v 117w			2N2484	60p		
				2N2586	15p		
				2N2614	4p		
				2N2887	£2		
				2N2894	11p		
				2N2904	9p		
				2N2905	15p		
				2N2906	9p		
				2N2907/A	9p		
				2N2926	4p		
				2N3020	25p		
				2N3053	16p		

WIREWOUND RESISTORS

0.22Ω	8p	1 Watt	4p	IK5	10p
		0.33Ω			
		2 Watt			
1.5	10p	47	10p	390	10p
2.2	7p	120	10p	500	10p
4.7	10p	180	10p	680	10p
5.6	7p	300	10p		
		3 Watt			
0.1	10p	22	10p	150	4p
0.8	4p	25	10p	330	10p
1.8	4p	50	10p	390	10p
3.3	4p	75	10p	470	10p
		4 Watt			
1.5	10p	10	10p	3K	10p
6.8	10p	1K8	10p		
		5 Watt			
0.1	5p	75	8p	750	10p
1	7p	80	10p	820	10p
1.5	7p	92	10p	910	10p
2.7	10p	80	10p	1K	10p
3.3	10p	100	10p	1K2	10p
3.5	10p	120	10p	1K4	10p
4	10p	130	10p	1K5	10p
4.7	4p	133	7p	1K8	10p
5	10p	160	8p	2K5	10p
5.6	10p	300	10p	2K7	10p
6.8	6p	330	10p	3K	10p
7	10p	350	10p	3K3	10p
10	7p	360	10p	3K5	10p
15	7p	390	10p	4K	10p
22	10p	420	10p	4K3	10p
25	10p	450	10p	4K7	10p
30	10p	470	10p	5K6	10p
30	10p	530	10p	5K1	10p
33	10p	560	10p	10K	10p
39	7p	600	10p	18K	10p
47	7p	620	10p	22K	10p
56	10p	680	10p	68K	10p
60	10p	700	10p		
		6 Watt			
2.2	7p	500	10p	15K	10p
10	10p	620	10p	22K	10p
12	10p	680	10p	36K	10p
150	10p	4K7	10p	3K	10p
390	10p	6K8	10p	47K	10p
		7 Watt			
60	10p	470	10p	3K9	10p
90	10p	560	10p	4K7	10p
360	10p	1K5	10p	5K6	10p
		9 Watt			
33	10p	200	10p	10p	
50	10p	2K7	10p		
		10 Watt			
1	10p	430	10p	3K9	10p
1.2	10p	437	10p	4K	10p
1.5	7p	470	10p	4K3	10p
1.8	10p	500	10p	4K7	10p
2.7	10p	560	10p	5K6	10p
3	10p	620	10p	5K6	10p
38	10p	680	10p	6K	10p
40	10p	750	10p	6K8	10p
68	10p	800	10p	7K	10p
71	10p	820	10p	7K5	10p
82	10p	900	10p	15K	10p
91	10p	1K	10p	18K	10p
93	10p	1K2	10p	22K	10p
100	8p	1K5	10p	27K	10p
120	10p	1K6	10p	30K	10p
125	8p	1K8	10p	33K	10p
130	8p	2K2	10p	35K	10p
270	10p	2K5	10p	36K	10p
330	10p	3K	10p	47K	10p
350	10p	3K3	10p	56K	10p
390	10p	3K5	10p	68K	10p
400	10p	3K6	10p		
		11/12 Watt			
500	10p	800	10p		
		15/17 Watt			
0.2	10p	450	10p	2K2	10p
1.2	7p	500	10p	2K8	10p
1.5	10p	520	10p	3K5	10p
5	10p	560	10p	3K74	10p
40	10p	620	10p	4K	10p
47	10p	680	10p	4K3	10p
62	10p	750 Tapped	10p	4K5	10p
70	10p		10p	4K7	10p
82	10p	800	10p		

PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE
ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

VAT & POST PAID
 (2nd Class or Parcel)
MINIMUM ORDER £3 (excluding catalogue) OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDE 12p S.A.E.)

UK - Postal Orders for same day service. Cheques require 8 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) same day service. Foreign currency not accepted. VAT content becomes documentation charge.

OPTO ELECTRONICS
 Photo Diodes: BPX40, BPX42, BPY10, CQY77, CQY17, BPY68, BPY69, BPY77 36p.
 Wire end neon 4p.
 Photo transistors: BPX43, BP103, 2N5777 Darlington, 36p. OCP71 40p. LED's (Mullard Seimans) Red .2" 8p. .125" 9p. Green .2" 11p. .125" 12p. Micro Yellow LD481 7p.
 PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp 36p
 CA3062 Photo Detector and power amp. £1

7 SEGMENT L.E.D. DISPLAYS
 3" Red com. anode 81p
 6" Green R.S.C.A. £1.77
 5082-7650 Red com. anode
 5082-7653 Red com. cath
 5082-7600 Yellow com. anode
 H.P. Highbrilliance .43" 72p

HEWLETT PACKARD MULTIPLEXED .12" 7 SEGMENT LED DISPLAYS
 3 Digit HP 5082 7413 45p
 4 Digit HP 5082 7414 45p
 5 Digit HP 5082 7415 45p
 Infra red transmit diodes CQY11B or LD27 High power 1.6-2v or 3-3.5v Pulse 32p LD242 36p
 H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
 Data Sheet 10p
 CNY17/1 opto coupler 70p
 Cold cathode tubes I.T.T. G517A or 5870L 60p

SPECIAL OFFER
 IN4004 or IN4006. Sealed manufacturers carton of 300.
£6.75

HIGH VOLTAGE CAPACITORS
 2500 VOLT 16p
 1000 pF .01, .03, .05 30p
 3000 VOLT 470pF 2p
 150, 300, 1800pF 17p
 .012 MFD 22p
 4000 VOLT 330pF 18p 1000pF 22p
 5000 VOLT .02 MFD 45p
 10,000 VOLT 1000pF 14p
 20,000 VOLT 500pF 60p

8/12 KV PULSE TUBE
 10 2p. 68 12p. 140 12p.
 12 12p. 82 2p. 200 12p.
 47 2p. 100 2p. 300 2p.
 56 2p. 120 2p. 350 12p.

8KV LOW IONISATION DISC.
 10 15p. 15 15p. 20 15p. 27 15p. 30 15p. 33 15p. 68 15p. 75 2p. 100 16p. 150 16p. 160 - 36p pack 3. 180 16p. 210 - 36p pack 3.

2.8 Volt 200 M/A Nicad Battery Unit. Recharges direct from mains. 80p

DIODES

AA119	7p	OA5	25p
AA133	9p	OA7	25p
AAZ15	15p	OA10	7p
B1	11p	OA47	10p
BA116	30p	OA70	11p
BA128	21p	OA75	11p
BA145	21p	OA79	31p
BA148	12p	OA81	8p
BA182 Varicap	6p	OA95	21p
BAX14	21p	OA200	21p
BAX54	8p	OA202	11p
BAY36P	21p	IGP7	11p
BB103 Varicap	6p	IGP10	21p
BB104 Varicap	16p	IN662	21p
BB109 Varicap	24p	IN914	21p
BB110B Varicap	24p	IN916	21p
BB113 Triple Varicap	43p	IN935B	71p
		IN936B	71p
		IN937B	71p
BB139	£1	IN941B	71p
BY206	23p	IN942B	71p
BY207	23p	IN943B	71p
BY402	21p	IN3064	21p
BY403	21p	IN3716 Tunnel Diode	30p
Centercell CG65/3	9p	IN4009	21p
CR HG/3	10p	IN4148	1p
CSD117YLZ	40p	IN4150	21p
CV7095	21p	IN4151	21p
CV7098	21p	IN4446	21p
D3202Y Diac.	11p	IN4449	21p
DC2845 Microwave	20p	IN5456	15p
DOG53	11p	5082 2900 RF Schottky Barrier	20p
FSY28A	40p		
HG1012	10p		
HS2091	11p		
MPN3401	30p		

RECTIFIERS

Type	Volt	Amp	Price
BY127	1250	1	4p
BY212	EHT		6p
BY235	600	1 1/2	7 1/2p
BY236	900	1 1/2	7 1/2p
BY264	300	3	9p
BY265	600	3	11 1/2p
BY266	900	3	15p
BY274	300	5	14 1/2p
BY275	600	5	17 1/2p
BY277	1200	5	27p
BY299	800	2	4p
BY1202	2kV	10mA	6p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38-300R	300	2 1/2	48p
BYX38-600	600	2 1/2	52p
BYX38-900	900	2 1/2	60p
BYX38-1200	1200	2 1/2	65p
BYX42-300	300	10	36p
BYX42-600	600	10	46p
BYX42-900	900	10	92p
BYX42-1200	1200	10	£1.07
BYX46-300R	300	15	£1.19
BYX46-400R	400	15	£1.75
BYX46-500R	500	15	£2.00
BYX46-600	600	15	£2.30
BYX48-300R	300	6	47p
BYX48-600	600	6	60p
BYX48-900	900	6	70p
BYX48-1200R	1200	6	92p
BYX49-300R	300	3	35p
BYX49-600	600	3	42p
BYX49-900R	900	3	47p
BYX49-1200	1200	3	60p
BYX52-300	300	40	42p
BYX52-1200	1200	40	£2.90
BYX72-150R	150	10	42p
BYX72-300R	300	10	52p
BYX72-500R	500	10	65p
BYX94	1250	1	5p
E250C50	250	1	14p
LT102	30	2	15p
M1	68	1	5p
MR856	600	3	24p
OA210	400	5	33p
RAS3 10AF	1250	1 1/2	48p
Avalanche			
REC53A	1250	1 1/2	16p
S10BR30	1000	30	£2.00
SKE4G	200	6	30p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
IN3254	400	1	4p
IN4002	100	1	3p
IN4004	400	1	4 1/2p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5401	100	3	10p
IS138	800	1	21p
IS921	100	1	8p
25G100	100	60	£4.35
3052	200	3	11p

16 PIN DIL RESISTOR NETWORK
 8 x 33K or 8 x 10K 16p

BRIDGE RECTIFIERS

1	60V	BC30 C350	23p
1	1,600	BYX10	34p
0.6	110	EC433	20p
	50V	W005	19p
1	140	OSH01-200	25p
1	200V	W02 Ex Equip	15p
1	400V	W04	28p
1	400V	MDA104	29p
1	800V	W08	27p
1	1000	W10	36p
1 1/2	75V	IBIBY234	11 1/2p
1 1/2	150V	IBIBY235	15p
2 1/2	100	I.R.	40p
2 1/2	350V	9F2	70p
2 1/2	500V	9E4	85p
3	50	KBS005	30p
3	100	KBS01	30p
3	200	KBS02	30p
3	400	KBS04	30p
3 1/2	600	KBS06	30p
5	100	B40C 3200	58p
	400	Texas	85p
		Miniature Meter Type	34p

Thyristors

Amp	Volt	Part No.	Price	
1	240	BTX18-200	35p	
1	240	BTX30-200	35p	
1	400	BTX18-300	41p	
4	500	40506 with heatsink	58p	
4	600	2N3228	36p	
6.5	500	BT109/SCR957	71p	
2	400	S2710D with heatsink	40p	
8	100	S2800A	36p	
4	600	C106M sensitive gate	36p	
20	600	BTW92-600RM	£3.40	
15	800	BTX95-800 Pulse Modulated	£1	
0.8	50	2N5061	3p	
0.8	200	2N5064	18p	
3	600	T3N06C00	53p	
3	100	T3N1C00	36p	
110	20	72RC2A	£3	
75	800	71CG80	£6	
150	1000	151RA100	£10	
150	1200	151RA120	£11	
12	1000	CR121103-RB	£8	
10	200	S2800B	54p	
5	600	S5800M	44p	
8	600	S112M	54p	
5	400	S3700D	44p	
4	50	S2060F	36p	
7	400	S2620D	45p	
7	600	S2620M	45p	
BT 106		70p	BT 107	£1
BT 121		70p		

TRIACS

Amp	Volt	Part No.	Price
0.1	40	7W84	3p
25	100	BTX94-100	£2.25
25	1200	BTX94-1200	£5
6	200	T2500B/41014	54p
2.5	600	2N5757	44p
8	400	T2850D	72p
4	400	T2716D/40730	74p
6	400	T2500D	72p

ZENER DIODES

4/500MW. BZY88, BZX97, etc.	5p
2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.	11p
1.3/1.5WT BZX61, BZY97, etc.	13p
2v4. 2v7. 3v. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 15v. 18v. 27v. 33v.	13p
2.5WT BZX70, etc.	15p
v75. 1v. 2v4. 3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p). 20v. 22v. 24v. 26v.	15p
5WT BZY40, etc.	15p
3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 33v. 68v. 120v.	20p
10WT ZSD, ZX, etc.	20p
4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 68v. 150v.	24p
BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode	12p
20WT BZY93, etc.	44p
8v2. 12v. 39v.	

WIREWOUND RESISTORS

23/25 WATT					
15	24p	380	24p	1K5	24p
110	24p	800	24p	2K	24p
300	24p	1K2	24p	10K	24p
30 WATT					
1	10p	80	34p	940	34p
2.3	34p	100	34p	1K	34p
20	10p	190	9p	3K3	34p
25	6p	200	9p	6K8	34p
36	22p	250	34p	15K	34p
60	34p	400	34p		
75	34p	726	34p		
50/60 WATT					
47	50p	100	50p	3K	50p
50	50p	250	50p	5K	50p
62	50p	750	50p	22K	50p
100 WATT					
			15K	80p	

BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS
Cut out and keep these 3 pages. Over the months they will bring to you some of the 6,000 items stocked.

INTEGRATED CIRCUITS

542 Servo Amp	18p	74LS221 Dual Monostable M/VIB	52p	CD4077 Quad Exclusive Nor	30p	SN76023 5Wt. Amp	36p
555 Timer	20p	74LS290	47p	CD4078 8 Input Nor	19p	SN76110P	35p
702 CL	25p	74293	80p	CD4081 Quad 2 Input and Buffer	15p	SN76115N Stereo Decoder	35p
709/72709 OP Amp. (14 pin 10p)	18p	74298	£1	CD4086 4 Wide 2 Input and/or Inv.	54p	SN76131	58p
710	28p	74490	£1.30	CD4093 Quad 2 Input Nand S.T.	54p	SN76227	59p
724	20p	7905 - 5v Reg. 1 Amp	54p	CD4094	72p	SN76228N	£1.60
741 OP Amp	16p	8080A C.P.U.	£3.60	CD4096	72p	SN76396 (TBA396)	151p
747 Dual OP Amp	44p	8086MPU	£3.60	CD40100 32 bit L/R Shift Reg.	£1.78	SN76620 AN	18p
930DC	4p	82S129	£5	CD40101	£1.08	SN76650N	50p
933DC	4p	9093DC	4p	CD40162	72p	SN76660N	35p
936DC	4p	9112DC	4p	CD40181BE Quad 2 Input and	£2.12	SN76666N	35p
937DC	4p	93S10	£1	CD40182	72p	SN158093	50p
946DC	4p	9311	£1.20	CD40192	72p	SN158097	4p
949DC	4p	93L16	36p	CD40194	72p	SN158099	50p
953 - 42300 Trip. 2 Innand	4p	9370	25p	CD40208BF	£2.12	TAA263 Amp	75p
961DC	4p	930399-256 Bit Shift Register	4p	CD4502 Strobed Hex Invertor	44p	TAA300 1Wt. Amp	£1
962DC	4p	930399-480 Bit Shift Register	4p	CD4508BF	£1.78	TAA320	35p
963DC	4p	930399-500 Bit Shift Register	4p	CD4514	£1.45	TAA550 Volt Reg.	10p
1315P2	36p	AJ371-002	4p	CD4516 Binary up/down counter	54p	TAA700	£2.30
2102 Memory	73p	AY58300 Ch/Time Display	36p	CD4519/MC14519	54p	TAD100 AM Radio	£1.22
2716 Eprom	£10.35	BRCM300 Volt Reg.	£1.40	CD4520 Dual Synch. 4 Bit Binary	72p	TBA120S/CC/SB/B TV Amp	25p
3351-2DC 40 x 9 Bit FIFO 2MHZ	£1.07	BTT822	£1.25	CD4532	£1.08	TBA240	£3.90
4060 Dymamic RAM 300ns	£1.45	C500 Calculator	37p	CD4527	£1.20	TBA395Q	£1.50
7400 } Quad 2 Input	10p	CA101 Wide Band Op. Comp	36p	CD4555	72p	TBA396	36p
74H00 } Positive Nand	26p	CA139AG Quad Volt. Comp.	54p	CD4555	£1.45	TBA550Q	£1.25
74LS00 } Gates	13p	(T)CA270AE	£1	CD22100	£1.45	TBA560C	52p
74S00 } Gates	18p	(T)CA270CW/AW	35p	CDP1802 Cosmac MPU	£3.60	TBA800 Amp 5 Watt Audio	52p
7401	7p	(T)CA270CE	36p	CDP1833 Cosmac Rom 1824 x 8	£3.60	TBA810 Amp 7 Watt Audio	70p
74H01	26p	CA758 (MC1311)	36p	D3624	36p	TBA920 TV Line System	70p
7402	11p	CA920 TV Horiz. system	72p	DM8214 Interrupt (8080 support)	36p	TCA270Q/SA/AE/OS	£1
7404	11p	CA3001 RF Amp.	86p	FCH111 8 input Nand/Nor	8p	TCA270SQ	55p
54/7406	15p	CA3028A	86p	FCH201	18p	TCA440 A.M. Receiver	£1.25
74LS08	15p	CA3044	£1.20	FCJ101	50p	TCA830S Ex. Equip.	18p
7410 } Triple 3 Input	10p	CA3046 Transistor Array	40p	FQJ/MPQ3725 4 Tr. Array.	45p	TCA830S	37p
74L10 } Positive Nand	25p	CA3054	69p	FM1303N Dual Stereo Pre Amp	65p	TCA4401	£1.25
74H10 } Gates	26p	CA3060	72p	LM309 (Ex Equip.) + 5v Reg. 1.2A	60p	TCEP100	£1
7411	8p	CA3083	36p	LM326 Volt Reg.	20p	TDA/MC1327 Dual Chroma Demod	18p
7414	29p	CA3086	29p	LM340T6 6v Reg.	36p	TDA2610	71p
7417	18p	CA3089	54p	LM343 Amp	42p	TDA2680	71p
7420 } Dual 4 Input	11p	CA3090AQ	72p	LM1303N Dual Stereo Pre Amp	65p	TDA2690	71p
74S20 } Positive Nand Gates	50p	CA3093	36p	LM/MC1458N Dual OP Amp	19p	TL720	28p
74S22	18p	CA3094 Prog. Sw. Pwr. OP Amp.	36p	LM3900 Quad Op. Amp (C.B. Amp)	36p	TMS4034 Memory	£1.08
74S22	18p	CA3097	36p	MC830P	4p	TYA0171	4p
7425	16p	CA3123	73p	MC833P	4p	XR215	£2
7426	12p	CA312EM	£2.22	MC837P	4p	ZN14 AM Radio Receiver	79p
5430	11p	CA3146E	90p	MC846P	4p	ZST131A 5 Input Power NOR	8p
7430	11p	CA3183	80p	MC862P	4p		
7432	13p	CA3189	73p	MC863P	4p		
54/7437	13p	CA3401 (LM3900) Quad OP Amp	36p	MC1306P	40p		
7438	14p	CD2500E 30mA/Seg DcmI Point Dvr	90p	MC1307P	35p		
74H40	26p	CD4000 Dual 3 input Nor + Inv.	12p	MC/CA/BRC 1310P St. Dec.	35p		
7442 BCD to Decimal Decoder	26p	CD4001 Quad 2 Input Nor	14p	MC1312P Stereo Decoder	40p		
74LS42 BCD to Decimal Decoder	40p	CD4002 Dual 4 Input Nor	12p	MC1314P	35p		
7445	42p	CD4006 18 Stage Static Shift Reg.	36p	MC1315P	35p		
7450 } Expandable Dual 2	11p	CD4007 Dual Comp. Pair + Inv.	12p	MC/BRC133Q Video Detector	85p		
74H50 } Wide 2 Input and/or Inv.	26p	CD4008 4 Bit Binary Full Adder	54p	MC1350P	35p		
7451	7p	CD4010 Hex Buffers	30p	MC1357P	35p		
7454	11p	CD4011 Quad 2 Input Nand	14p	MC1358PQ	35p		
54/7472 } And Gated JK Master	17p	CD4012 Dual 4 Input Nand	13p	MC1596L	75p		
74L72 } Slave F.F. Preset + Clear	25p	CD4013 Dual D Flip Flop	36p	MC3302L	£1		
5473 } Dual JK Master	12p	CD4014 8 Bit Shift Register	36p	MC4044P	£3.50		
7473 } Slave Flip Flops	17p	CD4016 Quad Bilateral Latch	36p	MIC7	25p		
74H73 } with Clear	26p	CD4017 Decade Count/Divide	54p	MK2686	36p		
7474	13p	CD4018 Preset Divide N Count	43p	ML237B	£1		
74L74	25p	CD4019 Quad 2 Input Multiplex	25p	MM5335D M.P.U.	36p		
7475	24p	CD4020 14 Stage Binary Count	54p	MM8008 M.P.U.	36p		
54/7476	19p	CD4021 8 Bit Shift Register	54p	MPC900 10A - 4 to 30v Reg.	75p		
5480	22p	CD4022 Divide by 8 Count/Divide	36p	MT300 Volt Reg.	8p		
7482	35p	CD4023 Triple 3 Input Nand	19p	MT305 Volt Reg.	8p		
7483	45p	CD4025 Triple 3 Input Nor	14p	SA1010	36p		
74LS83	47p	CD4026 Dec. Count + 7 Seg. Out	72p	SA1025	34p		
54/7486	18p	CD4028/MC14028 BCD/Decimal	42p	SAS580	£4		
5490	25p	CD4029 Synch. Preset Bin/Dec	54p	SAS590	18p		
7493 Binary Counter 4 Bit	25p	CD4030 Quad Exclusive or	36p	SAS590 Op. Amp	4p		
54/7495	25p	CD4031	£1.20	SL403A 3Wt. Amp	38p		
74LS98	£1.25	CD4032	72p	SL442	11p		
74107	20p	CD4033 Dec. Count. 7 Seg. Output	72p	SN7528	25p		
74S112	38p	CD4035 4 Bit Par. in out Shift	54p	SN15836	50p		
74118	75p	CD4037	72p	SN15845	50p		
74121	12p	CD4038	54p	SN15846	37p		
74122	18p	CD4041 Quad True/Comp. Buffer	54p	SN15851	50p		
54/74123	35p	CD4043 Quad Nor R/S Latch	54p	SN15858N	55p		
74132	44p	CD4044 Quad Nand R/S Latch	54p	SN15862	6p		
74141	42p	CD4045 4 Bit Par. in out shift	54p	SN75107 Interface	£1.15		
74LS145	93p	CD4046 Micro Power PH. Lock Loop	36p	SN75108	46p		
74150	12p	CD4048	36p	SN75110	18p		
74151	32p	CD4049 Hex Inverter Buffers	36p	SN75235N	11p		
74154 16 Way Dist.	35p	CD4050 Hex Buffers	25p	SN75451	36p		
74155	12p	CD4051 Analogue Multi/Demulti	36p	SN76001	36p		
74157	58p	CD4053 Analogue Multi/Demulti	54p	SN76003 5Wt. Amp	36p		
74173	23p	CD4055	72p	SN76003N 5Wt. Amp	£1.10		
74176/8280	44p	CD4056	72p	SN76013 5Wt. Amp	36p		
74180	30p	CD4063	72p	SN76013N 5Wt. Amplifier	92p		
74192	12p	CD4066 Quad Bilateral Switch	27p	SN76013ND 5Wt. Amp	£1.18		
74LS192	60p	CD4067	£2.12				
74193	38p	CD4068 8 Input Nand	20p				
74196	36p	CD4069 Hex Inverter	13p				
74S196/82S90	65p	CD4076 Quad D Flip-Flop	54p				

FUSIBLE WIREWOUND RESISTORS

5 Watt					
80Ω	22p	100Ω	22p	270Ω	22p
4K7	22p				
7 Watt					
200Ω	22p				
7Ω	22p	220	22p	3K2	22p
		750	22p		
15 Watt					
750Ω	22p				
		20 Watt	2K2 22p		
5.6Ω	8p				
23 Watt					
180Ω	9p				

HISTAB POLY/CERAMIC 1% AND 2% CAPACITORS

10pF	6p	470	6p	5N75	6p
20	6p	680	6p	0.01	6p
47	6p	1N2	6p	0.0147	6p
50	6p	1N28	6p	0.015	6p
68	6p	1N75	6p	0.0285	6p
79	6p	2N	6p	0.033	6p
88	6p	2N2	6p	0.047	6p
110	6p	2N34	6p	0.068	2p
130	6p	2N5	6p	0.082	5p
140	6p	2N7	6p	0.09	6p
150	6p	2N8	6p	0.1	6p
180	6p	3N04	6p	0.22	10p
250	6p	3N3	6p	0.4	15p
270	6p	3N96	6p	0.5	15p
370	6p	4N07	6p	0.68	10p
420	6p	4N7	6p	1 MFD	30p
above are various voltages up to 500.					
750 Volt					
82pF	22p	88pF	22p	150pF	22p
2000 Volt					
390pF	48p				
600pF 48p					
1/2 0.25 MFD 125v					

LEAD THROUGH CAPACITORS

1000pF	£2.20 per 100
36p	500 or 1000pF High Volt/Current
35p	£6.20 per 100
0.05 MFD 20 Amp	
Non Capacitive Lead Through	
2p	

TRIPLE CERAMIC CAPACITOR

3 x 1000 pF in small tubular construction. Series or parallel to give various values

10 for 35p

The Logic Probes

Spend Less

Test More



LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

£31.00*



LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,


replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £11-92)

£18.00*

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

*price excluding P.&P. and 15% VAT

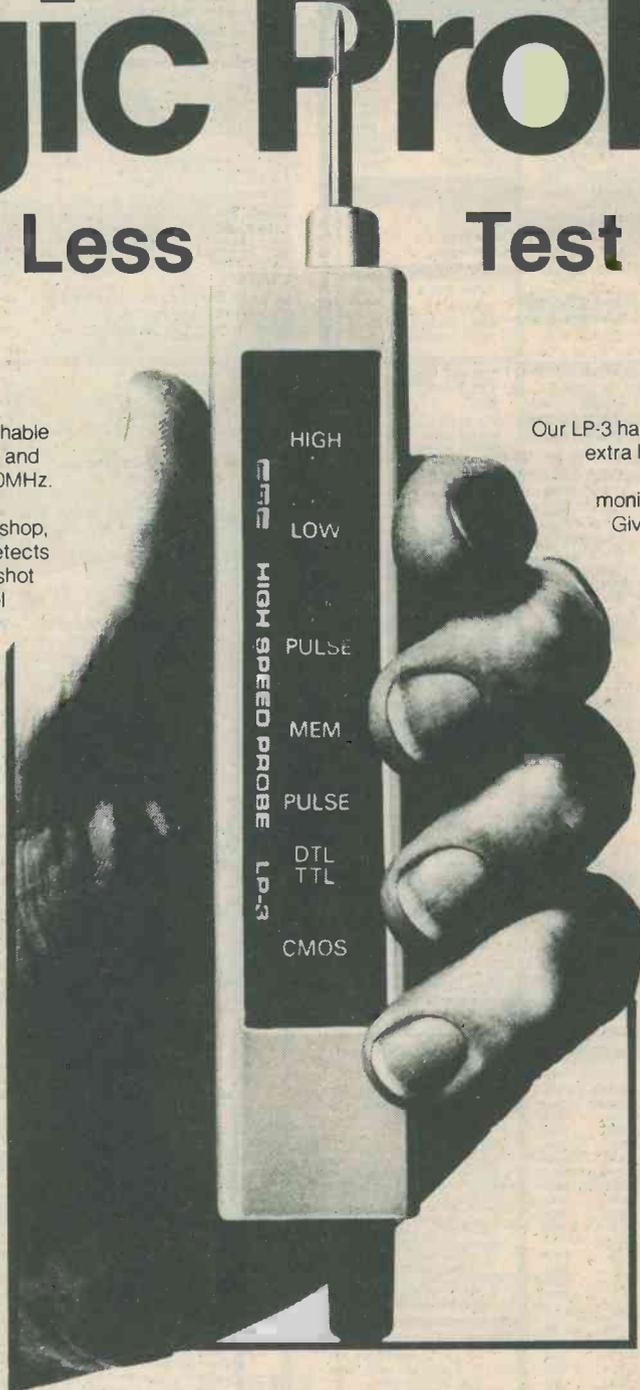

LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz.

Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

£49.00*



The New Pulser DP-1

The Digital Pulser: another new idea from C.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz.

The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

£51.00*



CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 1611, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Prices include P.&P. and 15% VAT

LP-1	£37.38	Qty	LP-2	£22.14	Qty	LP-3	£58.08	Qty	DP-1	£60.38	Qty	LPK-1	£14.86	Qty
------	--------	-----	------	--------	-----	------	--------	-----	------	--------	-----	-------	--------	-----

Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard/Access/American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION — The C.S.C. 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately.

for FREE catalogue tick box


C.S.C. (UK) Ltd. Dept. 1611, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

Telephone: Saffron Walden (0799) 21682

OCTOBER 1980

ELECTROVALUE

SUPPLIERS OF COMPONENTS THAT COUNT

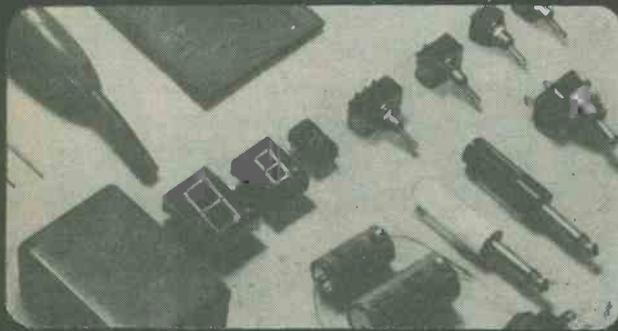

SIEMENS SEMI-CONDUCTOR CAPACITORS FERRITES	NASCOM MICRO COMPUTERS AND ANCILLARIES	VERO BOARDS CASES & KITS
ISKRA RESISTORS	RADIOHM POTENTIOMETERS OPTO-ELECTRONICS	BREADBOARDS SOLDER TOOLS SWITCHES CATALOGUE 10

OUR MINI-SELECTION POINTS THE WAY!

EXAMPLE ONE - SOLDERING IRONS

Aryx 50	£12.08 net	Antex x 25	£4.83 net
Isotip	£25.90 net	Desolder tool SR3A	£7.48 net
Antex C	£4.83 net	500 gm reel solder	£6.61 net

EXAMPLE TWO - PRINTED CIRCUIT MATERIALS

PCB's 300 x 150 mm	Etch Resist Pen	£1.14
SRBP S/S £1.38	Breadboards	
F/Glass S/S £1.96	Bimboard	£9.23
Positive resist 75cc	Eurobreadboard	£6.56 net
Ferric Chloride 500 g	T-DeC	£5.18

EXAMPLE THREE - SWITCHES

Chrome toggle	13A time switch adaptors	
Std. SPDT 65p	Smiths TS100	£14.43 net
Min. SPDT 66p	Wavechange, Lorlin, 1P12W, 2P6W, 3P4W, 4P3W	46p each
DPDT 89p		
DPDT 92p		

EXAMPLE FOUR - CAPACITORS BY SIEMENS

Polyester 7.5mm PCM
1, 1.5, 2.2, 3.3, 4.7µF, 10, 15, 22, 33, 42µF 8p each, .1µ 12p, .15µ 15p, .22µ 18p, .33µ 21p, .47µ 27p, .68µ 34p, 10mm PCM 1µ 37p.

Electrolytic, axial, (µ F/V)
1/40 24p, 1/100 15p, 2.2/25 24p, 2.2/63 15p, 4.7/16 24p, 4.7/40 15p, 10/25 15p, 10/40 18p, 22/25 18p, 22/40 18p, 22/63 19p, 47/10 18p, 47/25 18p, 47/40 16p, 47/63 20p, up to 1000/16V 36p, then 1000/25V 49p to 47/16 65p.

EXAMPLE FIVE - POTENTIOMETERS BY RADIOHM

Single gang lin or log	34p	(Twin types stereo matched)
Twin gang lin or log	93p	Slider knobs 10p each.
Mono slider lin or log	83p	Presets lin, horiz, or vert at 10p
Twin slider lin or log	136p	

EXAMPLE SIX - RESISTORS

1/3, 1/2, 2/3, 2.3p 1W 6p
Wirewound from 21p

AND AS FOR SEMI CONDUCTORS

1N914	6p	40673	99p	MU481	£1.70	T1P41A	69p
1N4007	9p	AC128	36p	MJ491	£1.88	T1P41C	74p
1N4148	9p	AC176	67p	MJ2955	97p	T1P42A	69p
1N5402	19p	AD136	£4.25	MJE2955	£1.13	T1P42C	74p
2N1599	£1.01	AD149	£1.01	MJE3055	£1.00	T1P2955	69p
2N2369A	24p	AD161	40p	MPSA12	42p	T1P3055	69p
2N3085	81p	AD162	52p	MPSA63	44p	T1S43	40p
2N3702-11	11p	AF127	43p	OA47	14p	W02	35p
2N4443	£1.78	AL102	£1.84	OA90	8p	2T x 107, 9	14p
2N4444	£2.28	BA379	29p	OA91	8p	2T x 300	14p
2N4991	98p	BB103	43p	OA202	16p	62T x 500	16p
2N5457-9	45p	BB104	70p	OC29	£1.23		
40HF40	£2.25	BB105	37p	OC36	£1.18	This list is	
40361	49p	C106D1	52p	T2800D	£1.20	but a fraction	
40362	49p	E1110	92p	T1P31A	52p	of what we	
40636	£1.69	E1210	97p	T1P32A	52p	carry.	


INFORMATION - To show everything we supply would take about seven pages of closely packed type in this journal - the range is enormous including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! IT'S ALL IN CATALOGUE 10 - OUR 120 PAGE CATALOGUE FREE FOR THE ASKING. PRICES AND V.A.T. - All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

POSTAGE - For orders up to £5.57 value (U.K.) please add 40p for p/p. If over, orders sent post free in U.K. Overseas orders sent at cost (Min. 40p).

DISCOUNTS - 5% allowed on non-net items if order value exceeds £11.50, 10% if order value exceeds £29. Quantity discount prices on most components.

ELECTROVALUE LTD. Dept. 28(A), St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 Telex 264475.
Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

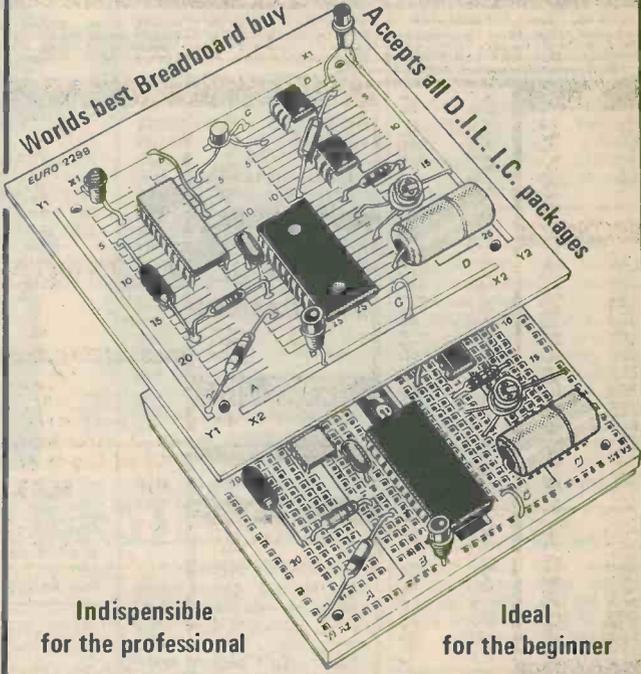First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard - Instal on a EuroSolderBoard

First the EuroBreadBoard
Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

Now the EuroSolderBoard
New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's

And don't forget the EuroSolderSucker
Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.
Please send me:-

1 EuroBreadBoard @ £ 6.20

or 2 EuroBreadBoards @ £11.70 Please

or 3 EuroSolderBoards @ £ 2.00 Tick

or 1 EuroSolderSucker @ £ 7.25

All prices are applicable from Jan. 1st 1980 and include VAT & PP but add 15% for overseas orders.

Name

Company

Address

ERC/10

Tel. No

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Cassette Motors 5-8VDC ex. equip. 70p. Geared Mains Motors (240V) 2.5 rpm 75p. 115VAC 4rpm Geared Motors 95p.

SEMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. CA3020 45p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. NE556 50p. ZN414 75p. BD238 28p. BD438 28p. CB4069 15p. TIL305 alpha numeric displays £2.50. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p.

PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

MOTOROLA PIEZO CERAMIC TWEETERS

No crossover required



2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

SWIVEL BASE VICES (with anvil)

With anvil, bench clamp, and plated parts, body smooth, lacquered finish. Jaw width 2", jaw opening 2 1/2" £5.55 + £1.20 P&P.

MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35 x 10mm 40p. GRUNDIG electric inserts with FET pre-amp, 3-6VDC operation £1.00.

LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic swich on when dark £4.50

RIBBON CABLE

8 way single strand miniature 22p per metre.

SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p (CCT supplied).

MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50



20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Rec/Sender £3.50 pair.

TELEPHONE PICK UP COIL

Sucker type with lead and 3.5mm plug 62p.

RELAYS

Plastic Encap. Reed Relay, 0.1 matrix. 1k Ω coil, 9-12VDC normally open, 35p. Miniature encapsulated reed relay 0.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. Min. sealed relay, P.C. mounting, 6-9vdc operation changeover 3 amp contacts, new 85p. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each. Magnets 1/2" long 1/8" thick with fixing hole, 10 for 40p.

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists

TMK500 MULTIMETER



TMK500 30,000 ohms per volt. 1KV AC/DC., D.C. Current to 12 amps. Resistance to 60 meg in 4 ranges, mirror scale, with built in buzzer for continuity testing £20.95

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts. 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 40 0mA, switchable £3.45. HC244R STABILISED SUPPLY. 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 63p. Carters 12 volt Minimate Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p.

DPDT (8 x 7 x 7mm) 55p.

DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

Electrolytic Caps, can type, 2,200mfd and 2,200mfd 50VDC 35p each.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90.


Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

Conquer the chip.

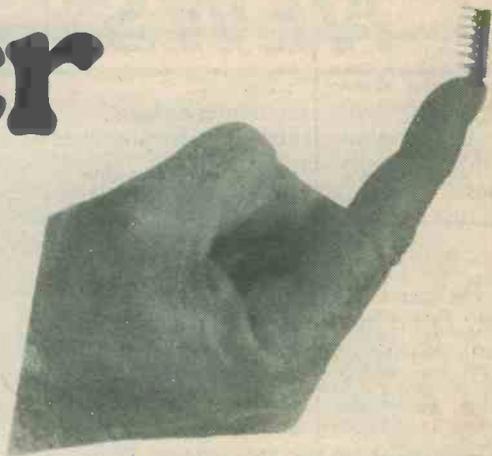

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.


MASTER ELECTRONICS



LEARN THE
PRACTICAL WAY BY
SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

MASTER COMPUTERS

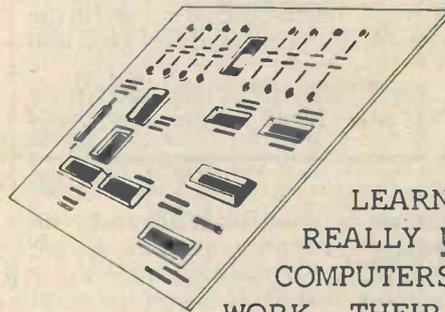

LEARN HOW TO
REALLY UNDERSTAND
COMPUTERS, HOW THEY
WORK - THEIR 'LANGUAGE'
AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.

FREE

Please send your **FREE** brochure without obligation to:-

REC/10/811

Name

Address

BLOCK CAPS PLEASE

I am interested in :-

PRACTICAL ELECTRONICS

COMPUTER TECHNOLOGY

OTHER SUBJECTS
(please state your interest)

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

At the very least, an incorrectly wired socket can damage valuable electrical equipment; at its worst it can be physically dangerous.

Martindale, the Neasden-based company that specialises in industrial safety equipment and electrical test instruments, has now introduced its simple Ring Main Tester for use by householders etc.

No larger than a conventional plug, the Tester is simply fitted into a standard 13 amp socket to give instant visual identification of the polarity of the wiring. Correct wiring, faulty earth connections, faulty neutral and reversed live/neutral connections are immediately shown by combinations of the carefully selected neons on the face of the Tester adjacent to explanatory diagrams. A fault in the live connection or supply is indicated when no neons are lit.

The Martindale Ring Main Tester, constructed from flame retardant plastic is virtually indestructible and, weighing less than 4 ounces, can be carried in the pocket or toolbox or can be permanently plugged into an extension lead.

Available from local electrical retail outlets at a recommended retail price of £4.70 plus VAT. Any



The Martindale Ring Main Tester that is simply fitted into a standard 13 amp socket to give instant visual identification of the polarity of the wiring

difficulty in obtaining supplies should be reported to Martindale Electric Company Ltd., Neasden Lane, London. NW10 1RN,

AMATEUR RADIO IN HOSPITAL

Providing permission is obtained in advance, there is usually no objection to the use of amateur radio transmitting equipment by licenced operators during a spell in hospital. However, there are certain rules that must be observed aside from obtaining permission in the first place. Small 2 metre equipment is the obvious choice except in cases where the stay in hospital may be for a very considerable time e.g., in a hospital or home for the handicapped.

Permission for use of radio or indeed any electrical equipment should be obtained as much in advance as possible from the Unit Administrator and/or District Works Officer c/o the hospital concerned.

This is important in hospitals where sensitive electronic equipment is in use for example, operating theatre life support systems and in intensive care units etc. It is vital that radiation, however low, cannot cause interference. Tests with respect to this are absolutely essential and hospital staff will normally be willing to co-operate. It is also essential that any equipment connected directly to a mains socket (usually available at bedsides) meets electrical standard safety regulations. This aspect can be checked by an appropriate member of the hospital staff. Providing such equipment takes negligible power from the mains e.g., a small charger unit for a portable battery operated 2 metre hand-held or low power mains operated TX/RX there may be no charge for electricity consumed. Check on this.


The following conditions concerned with actual operation are recommended:-

Use lowest transmitting power possible. Your hospital may not be too far from a repeater station.

Have regard for other patients by using an earphone for listening (or mic/earphone) and keep voice level to a minimum when talking.

Close down immediately if asked to do so.

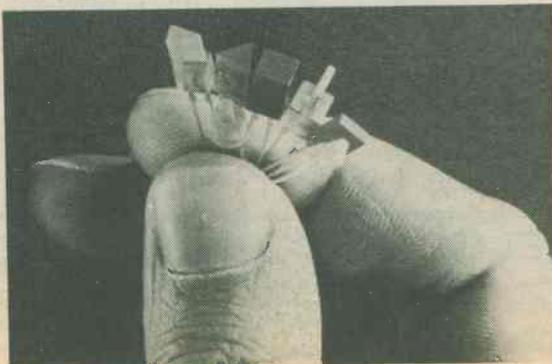The writer is indebted to Senior Staff Members of the Norfolk and Norwich Hospital, Norwich for guidance on the above, and we, in turn are indebted to F. C. Judd, the well known radio amateur and technical author, for this information.



SHAPED L.E.D. LAMPS

In addition to conventional tubular L.E.D. lamps, Sharp Corporation offer a range of special shapes.

Designed for flush fitting in front panels, the shapes presently offered include round 'point' indicators, equilateral and isosceles triangles, square and flat sections in three different sizes (basically 3, 4 and 5 mm) and colours (red, yellow and green).

Prices are very attractive, for 1,000 pieces these are in the region of 5p. to 10p. each, depending on size, shape and colour.

For further details contact: C. R. P. Electronics Ltd., 13 Hazelbury Crescent, Luton LU1 1DF.

... COMMENT

TELETEXT GOING "GREAT GUNS"

BBC CEEFAX Editor, Colin McIntyre, told a Radio Industries' Club luncheon in London recently that teletext was going great guns in Britain, but that British manufacturers still needed to 'look lively' or their two-year lead would be overtaken overseas.

"Britain has made all the running throughout the 1970's, and is streets ahead of the rest of the world in establishing a public service of teletext. But those elsewhere who have sat on the sidelines during the pioneering days were now beginning to make all sorts of claims and were muddying the issues. It is up to British manufacturers to get out and sell the necessary transmission and receiving equipment outside the United Kingdom - to ensure that trade followed the efforts of the broadcasting missionaries."

Colin McIntyre reported some 80,000 to 90,000 teletext in Britain, which were now selling or renting at about 5,000 to 6,000 a month. With a little boom at Christmas this could mean 150,000 by the end of 1980, and a quarter-of-a-million by the end of 1981.

CEEFAX and the ITV's service Oracle were now fully established in Britain, but it was very encouraging to see U.K. standards succeeding abroad. Austria and Australia were probably the furthest ahead, which gave a nice alphabetical fillip to other teletext activity in Belgium, Denmark, Germany, Holland and Sweden.

"The most exciting and exhilarating thing about teletext (Colin McIntyre said) is that it is on the move on an almost daily basis."

TANDY MOVES INTO SCOTLAND

Tandy, the international retail and manufacturing electronics group, have opened their first store in Scotland. The store, at 28 Jamaica Street, Glasgow, is the first of a number due to be opened in Scotland.

Tandy Corporation (Branch UK), an off-shoot of the Tandy Corporation in Fort Worth, Texas, USA, with 7,600 stores worldwide, was set up in 1973 and already has a network of nearly 200 retail outlets in England and Wales. In addition to a huge range of over 2,000 electronic products, Tandy manufacture and sell the world's leading microcomputer, the TRS-80.

The opening of the Glasgow shop will be followed in September by the opening of a store in Edinburgh. It is planned that a total of 12 stores will be opened throughout Scotland in the near future.

We regret that with this issue our cover price has had to be increased by 5p to 60p. The reason is, of course, the continuing rising costs due to inflation. Annual subscriptions have also had to be increased to £9.50 for UK subscribers and to £10.50 for readers in Eire and overseas.

A glance at our contents list will confirm that we continue to give excellent value for money and we have many first class articles in the pipe line.

We are continuing to publish at shorter than monthly intervals, following the hiatus caused by our previous printers ceasing to trade. Therefore readers should keep a sharp lookout at newsagents to make sure they do not miss an issue.

POWER SCREWDRIVER




A powerful new screwdriver, the DMS2, has been introduced by Klippon.

This hand tool offers the very latest in design, enabling it to be used easily in confined and awkward spaces. Its high technical specification offers a preset automatic torque limitation; variable speed from 350 to 700 RPM; automatic switch-on possible only when pressure is applied to the screwdriver bit; increased speed through increasing pressure on the bit; ON-OFF switch for isolation; forward and reverse switch and a chuck for standard 5.5mm hexagonal socket to DIN3126 suitable for use with other tool inserts.

The DMS2 is a light weight tool, quiet in operation, with full electronic control. It will continue to maintain its high accuracy even in repetitive production work and meets Safety Classification 11 to DIN 57740, VDE 0740 and CEE. Operating voltage is 220/240V a.c. 50Hz. Power consumption is 45W and current consumption is just 0.20A. A 110V version will be available in due course.

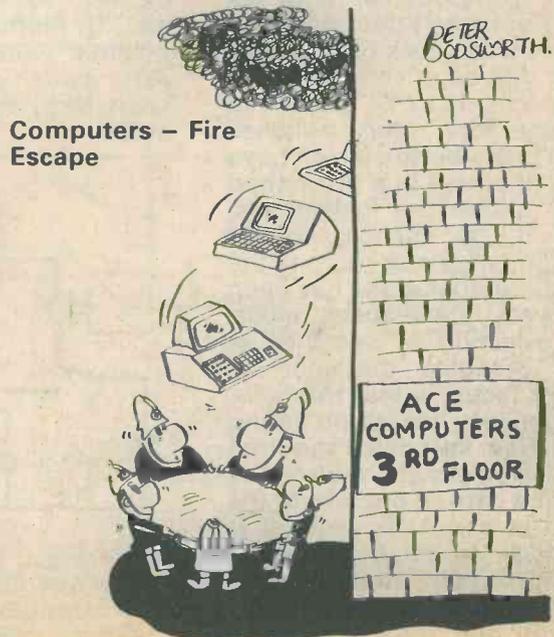For further details contact: Klippon, Power Station Road, Sheerness, Kent, ME12 3AB.





CAPACITANCE COMBINATION LOCK

By G. A. French

In these times, when one's thoughts tend to concentrate more and more on the question of security, a wide field of application is open for the design of electronic intruder alarms, proximity detectors and similar equipment. One particularly challenging sector is concerned with the construction of combination lock switches which, when operated in the correct sequence, cause a solenoid to unlock a door or the lid of a box. Such combination locks can employ press-buttons, rotary switches and a number of relatively inexpensive electronic components, and are much less costly than would be a mechanical lock offering the same degree of complexity.

The circuit to be described employs four rotary switches and a press-button which have to be operated in a prescribed order before the lock opens. Even if, by chance, correct selection of one or more of the switching operations has been achieved, subsequent incorrect selection of switches at once disables the lock. A further factor is that the combination lock has inbuilt timing protection. Part of the required succession of switch selections must be carried out within the space of about six seconds if the lock is to be opened. Finally, even after all the switches have been taken through the right sequence,

there is still a further time delay before the lock opens.

How, the question may be asked, can anybody not knowing the combination open the lock? The answer is: with great difficulty!

BASIC CIRCUIT

As an introduction to the functioning of the lock, a simplified version of the basic circuit is given in Fig. 1. Here, S1 and S2 are two "ways" of a 12-way rotary switch, whilst S3 is a single "way" of a third such switch. The latch after S3 can be triggered from the "lock closed" to the "lock open" state by momentarily passing a positive voltage to its input. After switch-on of power, the latch is in the "lock closed" state.

To trigger the latch, the press-button in Fig. 1 is pushed whilst S1 is in the upper position. This causes capacitor C1 to charge to the supply potential of 9 volts. S1 is then moved to its lower position, whereupon C1 is connected in parallel with C2 via S2 in its upper position. The charge in C1 is shared between the two capacitors. If S2 is now moved to its lower position the positive voltage on the upper terminal of C2 is applied, through S3, to the input terminal of the latch, which is then triggered to the "lock open" state.

Before proceeding further, it is necessary to consider the values required in C1 and C2. When a single capacitor with no connections made to its terminals is charged, the relationship between the

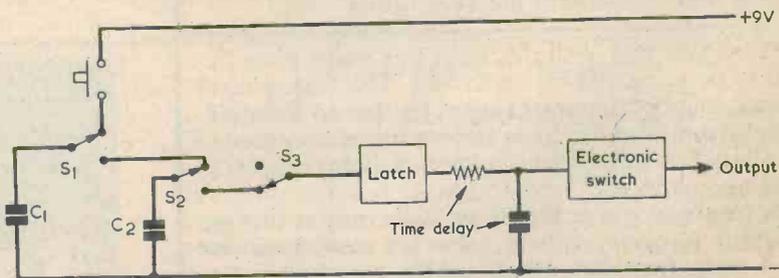


Fig. 1. Simplified circuit illustrating the sequential operation required in S1 and S2, and the time delay components between the latch and electronic switching sections of the combination lock.

ples the input of the latch to position 9 of S2. Note that diode D1 is now interposed between S2 and S3. This diode enables a positive voltage from C2 to trigger the latch and prevents the latch from reverting to its previous state when C2 discharges. All switch contacts which do not contribute to the lock opening process are returned to the negative rail, either directly, or by 10Ω current limiting resistors. Thus C1 is effectively short-circuited when S1 is at any position other than positions 1 and 2, and C2 is short-circuited if S2 is set to any position except positions 10 and 9. Even if either of these capacitors has been charged, an incorrect setting of S1 or S2 will discharge it again. Further protection is given by the new switch, S4, which ensures that C2 is always discharged unless it is in position 7.

The latch of Fig.1 is given by the two NAND gates of IC1 which are associated with pins 1 to 6. After the Reset button has been pressed, or S3 set to

an incorrect position, this latches with a low input at pins 1 and 2, and a low output at pin 4. When it latches to its alternate "lock open" state, pin 4 goes high and C3 charges slowly via R8. The electronic switch in Fig.1 consists of the remaining two NAND gates of IC1. When C3 has charged sufficiently, after a time delay of around 12 seconds, the output at pin 11 goes high and turns on TR1 which energises the relay. The relay contacts complete the lock opening circuit. If press-button S7 is pushed, capacitor C3 is short-circuited via R7 and the lock closes quickly.

The fixed resistors which ensure a quick discharge in C1 and C2 are R1 and R3 respectively. These resistors make it necessary to operate S1 and S2 within a maximum of around 6 seconds if a positive voltage of sufficient magnitude is to be applied to the latch. This allows 3 seconds for the operation of each switch.

OPENING THE LOCK

We can now examine the procedure needed for opening the lock.

First, S3 has to be set to position 8 to ensure that the input to the latch is connected to D1 and not to the negative rail. Second, S4 must be in position 7, so that there is no short-circuit across C2. Next, S1 is put to position 1 and S2 to position 10. S5 is then pressed, to charge C1, after which S1 is quickly moved to position 2 to cause C2 to be charged via S2 at position 10. S2 is next quickly changed to position 9, causing the positive voltage from C2 to be applied via D1 and S3 to the input of the latch. There is then a 12 second delay before TR1 turns on and the lock opens. If, during that delay period, either S3 is adjusted or S6 is pushed, the latch returns to the "lock closed" state, with C3 discharging slowly through R8.

Thus the total process of breaking the combination consists of the following sequence: S3 at position 8, S4 at position 7, S1 at position 1, S2 at position 10, S5 pressed, S1 to position 2, S2 to position 9, 12 second wait,

CONSTRUCTION

The method of assembly is left to the constructor but there will obviously need to be a front panel of some kind, on which are mounted the four rotary switches and the three press-buttons. The rotary switches can of course be wired so that contact positions other than those shown in Fig. 2 need to be selected, although with S1 and S2 the two positions should be adjacent to each other. All the switches can be positioned on the panel with any layout preferred.

The switches may all be miniature 12-way rotary and they will need to be fitted with pointer knobs, and have numbers from "1" to "12" marked out on the panel behind them. The relay employed with the prototype circuit was an "Open Relay" with a 410Ω coil and changeover contacts which is available from Maplin Electronic Supplies and other mail-order retailers. The three electrolytic capacitors should have working voltages of 10 or more. All the resistors are ½ watt 5%.

If desired, a simplification can be achieved by omitting S4 and R5, and this will result in having one less number in the combination to remember. The Reset button could also be omitted since its function is carried out by setting S3 to any contact other than 8. However, S6 provides a small extra safeguard insofar that, if the latch has been triggered, it will return to its previous state if S6 is inadvertently pressed.

The current drawn from the 9 volt supply by the circuit in the quiescent state is too small to be indicated by a multimeter switched to a 50μA range. The current rises to some 3mA in the switching NAND gates about 10 seconds after the latch has been triggered and then remains steady at approximately 20mA when the relay energises. ■

APOLOGY

We regret that in our last issue pages numbered 24 and 30 were transposed during the course of production. It appears that readers soon realised what had happened, nevertheless we apologise for the inconvenience caused.

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL SUBSCRIPTIONS

to this magazine may
be obtained through
your newsagent or
direct from the
publishers

INLAND £9.50
OVERSEAS . . £10.50
(including Eire)
per year, post free

*please send remittance with
name and address and
commencing issue required to:*

DATA PUBLICATIONS
LTD
57 Maida Vale, London
W9 1SN

HI-FI P.C.M.

By J. R. Davies

An introduction to pulse code modulation techniques, as currently employed in the transmission and reception of high quality stereophonic sound signals.

We are all familiar with the analogue method of handling audio frequency signals, for the simple reason that this is the only method with which such signals can be dealt with using simple equipment. Sound picked up by a microphone is converted to its electrical analogue and this analogue signal is then passed through the a.f. chain to the reproducing loudspeaker. Links in the chain can consist of a tape recording head, tape and tape replay head; a record cutter, disc and pick-up; a land line; or a radio transmitter and receiver. All these links introduce distortion and noise. With all its varied frequencies, and its amplitudes and phase relationships, the analogue a.f. signal can suffer partial degradation at any stage between the input microphone and the reproducing loudspeaker.

PULSE CODE MODULATION

Considerable interest in the high fidelity world is now centred on pulse code modulation as an alternative process for the handling of audio frequency signals. At an early stage in the signal path between audio input and the output loudspeaker the signal is changed to a pulse code modulation equivalent by an analogue-to-digital converter (a.d.c.), and at a late stage in

the signal path it is changed back to its original form by a digital-to-analogue converter (d.a.c.). The p.c.m. signal is purely digital in nature and consists of a series of binary digits (bits) which contain signal information by the presentation of 1 (bit pulse present) or 0 (bit pulse absent). The p.c.m. signal is extremely robust and is capable of being converted back faithfully to the analogue original even when accompanied by noise levels which would make the analogue signal worthless. The p.c.m. signal can pass through suitable tape and disc links in the signal path without degradation. When properly encoded and decoded, the p.c.m. process introduces negligible distortion. It does cause the formation of a low noise level but this can be held at an extremely small level.

On the debit side is the fact that the circuits and links carrying a p.c.m. audio signal must have a bandwidth considerably wider than would be required by the signal in its analogue form. Also, the a.d.c. coding circuits and the d.a.c. decoding circuits are fairly complex. However, the wide bandwidth required by a p.c.m. audio channel presents few serious difficulties. Transmission, reception, recording and replay facilities intended for

video signals are readily available and these offer more than adequate bandwidth for p.c.m. audio signals. Similarly, the coding and decoding processes, although not simple, are well within the capabilities of present-day logic components and techniques.



An engineer setting up a test procedure on the BBC p.c.m. system. (Courtesy BBC).

The use of p.c.m. channels for high quality audio signals has been established in the UK for a number of years now, and is employed internally by the BBC for the distribution of high quality stereophonic sound from studio centres to sound transmitters. The p.c.m. signals are passed over conventional 5.5MHz television microwave links, which replace earlier analogue "music lines" provided by the British Post Office. To give an idea of the bandwidth required by a p.c.m. audio signal, each BBC 5.5MHz microwave link carries 13 audio channels, these consisting of 3 stereo programmes plus seven mono channels. The 13 channels are time multiplexed, i.e. successive signals are "interleaved" in terms of time, but we will not deal with multiplexing in this short article. Instead, and at the expense of some simplification, we shall deal with the basic elements of pulse code modulation when employed with a single mono audio signal. In passing, nevertheless, it is worth observing that if 13 audio channels can be accommodated in a signal path having a bandwidth of 5.5MHz, it becomes quite feasible to

pass a 2 channel high fidelity p.c.m. stereo programme through a system having the bandwidth available with current video recording and reproducing equipment.

CODING

To convert an analogue signal to its p.c.m. equivalent, the amplitude of the analogue signal has to be sampled at regular intervals. In Fig. 1(a) we have a short part of an analogue signal, this being sampled at the points indicated. The result of the sampling process is the series of pulses shown in Fig. 1(b), the height of each pulse corresponding to the amplitude of the analogue signal at the time of sampling. The pulses constitute a pulse amplitude modulation (p.a.m.) version of the analogue signal.

In Fig. 2(a) the height of each pulse in the p.a.m. signal is assessed against an arbitrarily derived series of equally spaced amplitude levels calibrated in binary numbers from 0000 to 1111 (15 in decimal). The pulse tips will either coincide with a binary amplitude level or, much more probably, lie between two amplitude

levels. Each pulse is then assigned the binary number for the level with which its tip is coincident or, according to the coding system employed, is assigned a binary number corresponding to the level immediately below it or that immediately above it. Assuming that the first of the two coding systems is used, the pulse train can then be represented by the binary numbers shown in the diagram below the pulses. In Fig. 2(b) the binary numbers are presented as a new series of pulses. All the pulses have the same amplitude and they represent the binary levels by having a pulse present for digit 1 and a pulse absent for digit 0.

The signal shown in Fig. 2(b) is the p.c.m. version of the analogue signal of Fig. 1(a).

The process of assessing the height of each p.a.m. pulse in terms of pre-determined discrete levels is known as quantising or quantisation. In Fig. 2(a) there are only 16 quantising levels (taking into account the 0000 level) whereupon the p.c.m. version of the analogue signal has very poor accuracy. It will be obvious that we can increase the accuracy of the p.c.m. signal by providing more quantising levels. An improvement would be given by going up to 32 quantising levels, these consisting of binary 00000 to 11111 (31 in decimal), and a further improvement by using 64 levels, given by 000000 to 111111 (63 in decimal). Note that to obtain maximum advantage of the binary coding each increase in quantising levels is from one power of 2 to the next power of 2. 32 is 2 to the power of 5 and 64 is 2 to the power of 6. 32 levels can be represented by 5 binary digits and 64 levels by 6 binary digits.

When we start dealing with high quality audio signals we need very many quantising levels. As the number of quantising levels increases the levels become more closely spaced and each binary assessment of analogue signal amplitude represents more accurately the actual analogue amplitude at the time of sampling. If, in practice, we use 1,024 (2 to the power of 10) quantising levels we are just below the

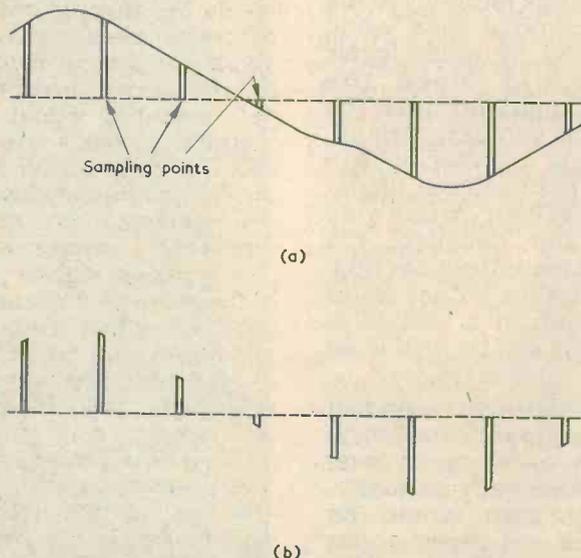


Fig. 1(a). The amplitude of an analogue signal is sampled at regular intervals. (b). Each sampling operation produces a pulse whose amplitude is equal to the amplitude of the analogue signal at the time of sampling. This is a pulse amplitude modulation version of the analogue signal.

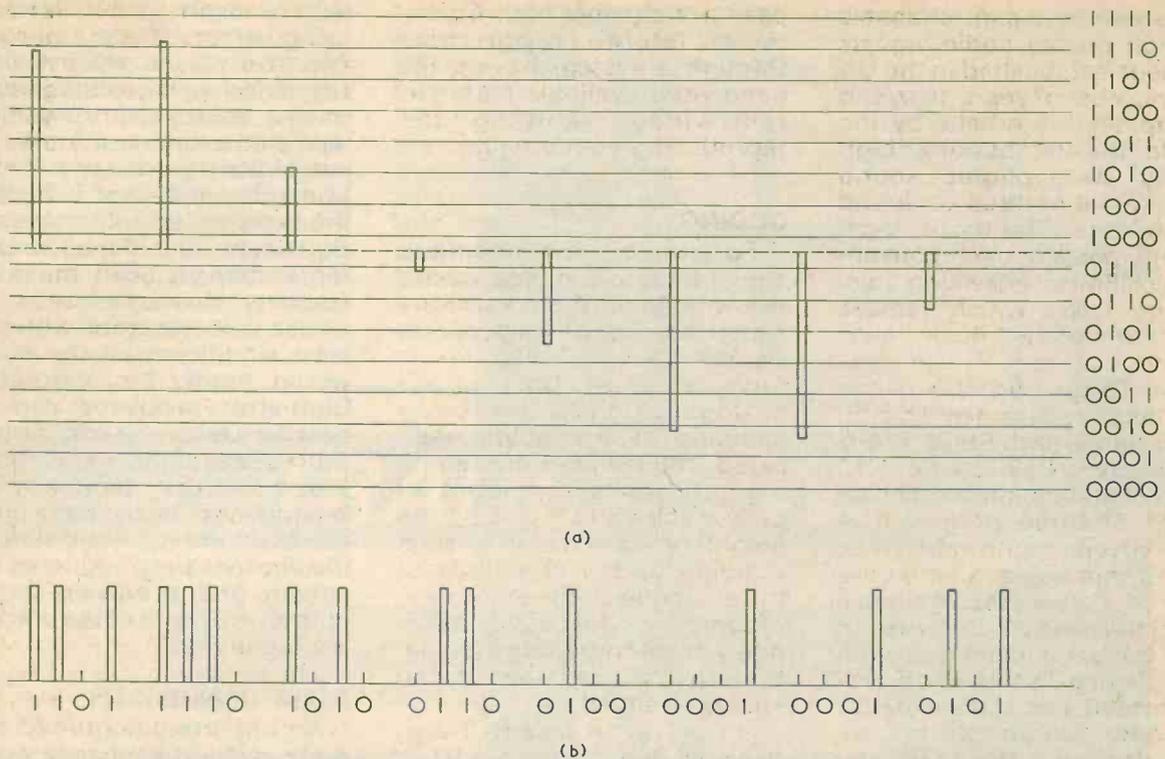


Fig. 2(a). The height of each pulse in the p.a.m. signal of Fig. 1(b) is assigned a binary number corresponding to the quantising level at or near the pulse tip. **(b).** The quantising numbers constitute the p.c.m. equivalent of the original analogue signal, and are passed along the signal chain in the form of bit streams. The 16 quantising levels employed here give a 4-bit p.c.m. system.

situation at which high quality audio can be handled in p.c.m. form without noticeable distortion. The situation improves with 2,048 quantising levels, and at 4,096 quantising levels the distortion introduced by the p.c.m. processing is virtually negligible. A further improvement, barely perceptible subjectively, is given by going up to the next step of 8,192 (2 to the power of 13) levels. With this number of levels each sample p.a.m. pulse is converted to a pulse bit stream of 13 bits. 13 bit quantising is employed in the BBC p.c.m. system.

SAMPLING RATE


Intuition tells us that the rate in time at which amplitude samples of the analogue signal are taken must be at some frequency which is higher than the highest frequency in the analogue signal. If, for instance, the sampling rate were only 10kHz, the p.c.m. signal could not possibly represent with any accuracy the

successive amplitude states of the higher frequencies in a high quality audio signal. The situation here is governed by a well-known waveform sampling theorem due to Nyquist. The Nyquist sampling theorem states that if any analogue signal, however complex, has its highest frequency limited to FHz, it can be reproduced truly and in its entirety by sampling at a frequency of 2FHz. Sampling must not be carried out at less than 2FHz but it can, of course, be carried out at more than 2FHz. In the BBC p.c.m. system the maximum analogue frequency passed to the a.d.c. is 15kHz, and sampling is carried out at 32kHz. (Another reason for choosing this particular sampling frequency is applicable to BBC requirements. 32kHz is 4 times the sampling frequency used in BPO telephony p.c.m. circuits, and synchronising problems would be eased if, in the future, BPO lines were used by the BBC for carrying high quality p.c.m. audio.)

QUANTISING NOISE

Even with 8,192 quantising levels there must still be tiny discrepancies between the actual heights of most p.a.m. pulses derived from the original analogue signal and the quantising levels assigned to them. Provided that there are enough quantising levels these discrepancies do not make themselves evident as distortion but they appear, instead, in the form of a random background noise. Subjectively, this quantising noise is similar to random "white noise", although the frequencies which appear in it are governed by a different probability function. Quantising noise reduces as the number of quantising levels increases, because the discrepancies are then made smaller. With 1,024 levels the peak signal to r.m.s. quantising noise ratio is 65dB, with 4,096 levels it is 77dB, and with 8,192 quantising levels it is 83dB.

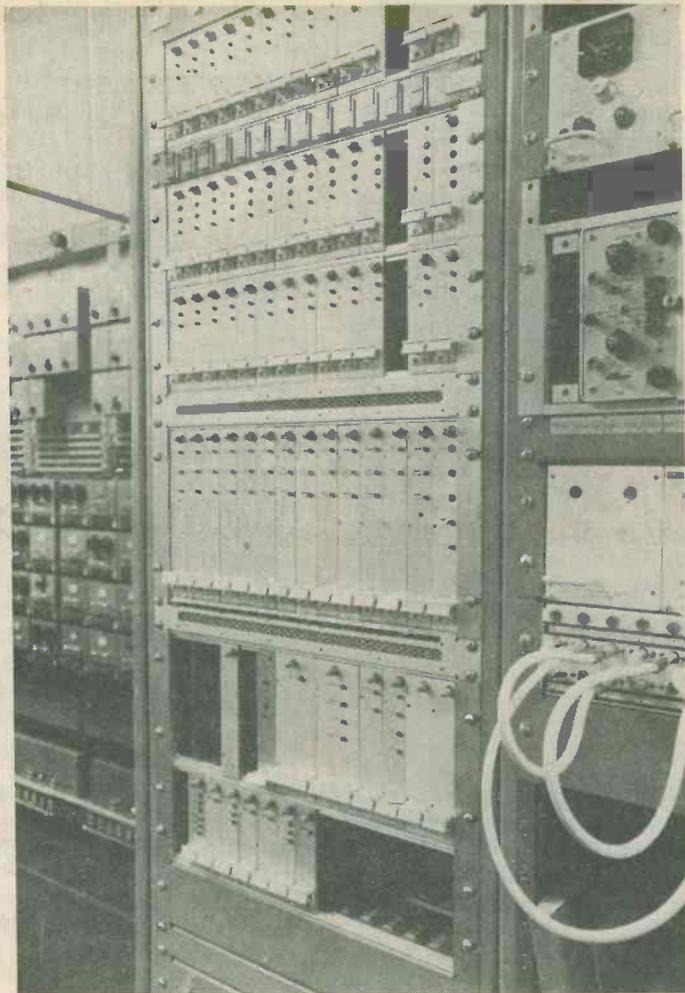Several precautions have to be undertaken before the



A close-up of one of the bays of equipment in the BBC p.c.m. system. (Courtesy BBC).

analogue signal is presented to the a.d.c. for conversion to p.c.m. First, the analogue signal must be filtered so that its maximum frequency does not exceed half the sampling frequency. Second, its amplitude must be limited so that it does not exceed the highest quantising level. If it did, the result would be clipping distortion similar to the clipping distortion given in overloaded totem pole audio amplifier output stages.

Another problem arises when the analogue signal has an extremely low amplitude, as can occur during a very quiet passage in a broadcast programme. If signal excursion is then too small to bring about a change from one quantising level to the next with successive p.a.m. pulses, there is no sound signal from the decoding circuit. Should this effect take place as part of a

waveform which is also at a low level, it will produce a discontinuity and consequent heavy distortion. There is an analogous "granular effect" in telephony with carbon microphones, with which very low audible signal levels may be unable to overcome mechanical inertia in the carbon granules and thereby alter the contact resistance which they offer. The BBC solution is to add a "dither" signal to the analogue signal before coding, this consisting of a signal, at half sampling frequency, which has an amplitude of half a quantising step. To this is added a smaller level of random white noise. By this artifice the analogue signal must always keep shifting from one quantising level to another, even if only between two neighbouring quantising levels, and decoded signal discontinuities at very quiet prog-

ramme levels are eradicated.

Digit-error effects are possible in a p.c.m. system. Due, say, to fading or static in a microwave link, or to drop-out in a tape transcription, a 1 may be lost at the decoder or a 0 may be represented as a 1. Should the error occur with the most significant bit in the bit stream representing a p.a.m. pulse the result would be a loud click, whilst if it occurred with the least significant bit the effect would hardly be noticeable. Digit-error problems can be eased by adding a parity bit to each signal bit stream. When, at the decoder, the parity bit indicates that there is an incorrect bit in the signal bit stream, the decoder simply ignores the stream and produces, in its output, the result of the preceding bit stream.

P.C.M. BANDWIDTH

An important feature of any p.c.m. system is the bandwidth needed in the channel which carries the p.c.m. signal. In this article we shall look upon bandwidth requirements in a simplified manner.

Taking the p.c.m. signal as so far described, we may visualise it as consisting of 14 bit streams (13 bits plus a parity bit) produced at a sampling frequency of 32kHz. If each 14 bit stream were immediately followed by the next 14 bit stream, there would then be 14 times 32,000, or 448,000 signal information bits per second. This signal can be passed through a channel having a bandwidth of 224kHz. The bandwidth must not be less than 224kHz, and it would be desirable in practice to have it greater than this figure. At first sight it may be surprising to find that the minimum channel bandwidth in Hertz is equal to half the number of bits per second, but this finding is another expression of the Nyquist sampling theorem.

It must be emphasised that the last paragraph represents a simplified state of affairs, because it would be impracticable to work with a p.c.m. signal made up in the manner described. In the BBC 13 channel system, for instance, the channels are time multiplexed and the signal includes not only 13 bit and parity bit

streams but also synchronising bits to keep the d.a.c. decoder in step with the a.d.c. coder. Included, too, are auxiliary bits for other purposes. In our simplified approach of the last paragraph we referred to 448,000 signal information bits per second for a channel and if we multiply this by 13 (for 13 channels) we arrive at a megabit per second figure of 5.824. This figure applies only

to our simplified version of the signal, and the bit rate of the BBC 13 channel p.c.m. signal, taking into account multiplexing, synchronising and auxiliary bits, is actually 6.336 megabits per second. The sampling theorem states that this could pass through a channel having a minimum bandwidth of 3.168MHz. The 5.5MHz bandwidth of a television signal link is comfortably

above the minimum required.

ACKNOWLEDGMENT

The author is grateful to the Engineering Information Department of the British Broadcasting Corporation, who have provided extensive details of the BBC p.c.m. system for the preparation of this article. ■

TRADE NEWS

P.C.M. AUDIO DISC STANDARD

The mutual co-operation between N.V. Philips' Gloeilampenfabrieken of the Netherlands and Sony Corporation of Japan has led to further improvements in the optical Digital Compact Disc system which was announced by Philips in March 1979. These further improvements are in the field of modulation and error correction.

The Digital Compact Disc system permits the recording and reproduction of sound as discontinuous pulse signals and allows wider frequency response with a much greater dynamic range and greatly improved sound quality. Although the disc diameter is only 12cm (4.72in.) the system, with improved modulation and error correction, permits 60 minutes of high-density recording on one side of the disc.

The main characteristics of the system are:

1. It is optical. Due to the non-contact pick-up system a long life for disc and player is ensured.
2. It is a 16 bit system. The distortion and errors

which are inherent in the conventional analogue recording system are eliminated by the use of pulse code modulation.

3. It is compact. The compactness of the player offers wide application possibilities in various consumer products, while the handling and storing of discs is much easier when compared with conventional audio records.

The world-wide Polygram group, one of the world's leading record manufacturers, has announced that they will release their music programmes in this format. CBS/Sony (Japan) will also be releasing both CBS and CBS/Sony repertoires on the Digital Compact Disc. CBS Incorporated has announced that it will work closely with Sony and Philips on future developments of the new system. It is anticipated that the Digital Compact Disc will become a future international standard for disc recording and reproduction.

SEMICONDUCTOR REORGANISATION

All the semiconductor activities of GEC-Marconi Electronics Limited are being combined under the aegis of a single company, Marconi Electronic Devices Limited. This will incorporate AEI Semiconductors Limited, GEC Semiconductors Limited and the Microelectronics Division of Marconi Space and Defence Systems Limited.

Marconi Electronic Devices will design, develop and manufacture integrated circuits, hybrid microelectronics, microwave semiconductor devices and assemblies, and power semiconductor devices and assemblies.

The breadth of semiconductor technology available to Marconi Electronic Devices now puts the

company in a unique position to tackle wide-ranging solid-state systems requirements from in-house capabilities. These can involve silicon power, r.f. and microwave device and component expertise, thick film custom design microcircuitry and specialised design for large scale integration in MOS technology.

An agreement has been signed with Mitel Corporation of Canada to obtain their advanced ISO-CMOS integrated circuit technology which has been very successfully applied in the telecommunications industry. Further research and development of this process will be undertaken jointly by the GPO and GEC with the object of keeping the U.K. ahead in the area of large scale integration applied to telecommunications.

PERSONAL MEDIUM WAVE RADIO

By
R. A. Penfold

- Full medium wave coverage.
- Particularly suited to the beginner.
- Low battery current consumption.

This very simple medium wave receiver has been specifically designed for ease of construction and is therefore ideal as a beginner's project. The circuit is of the t.r.f. (tuned radio frequency) type and the completed set requires no alignment. Only one adjustment has to be made to the finished receiver, this merely consisting of setting up a pre-set potentiometer for optimum sensitivity. In some instances, it may be necessary also to adjust the position of the ferrite aerial coil.

The receiver's internal ferrite rod aerial provides good reception of the three national BBC medium wave networks, plus local medium wave stations where these are in operation. A few Continental stations, including Radio Luxembourg, should be received in most parts of the U.K. after dark and at reasonable volume. The output is suitable for a crystal earpiece, high impedance magnetic headphones or a high impedance magnetic earphone. These last two should have impedances of $1k\Omega$ or more. The set cannot be used with a low impedance earphone or headphones. Power is obtained from a PP3 9 volt battery. This will have an extended life as the current consumption is only about 1.5mA.


THE CIRCUIT

As can be seen from the circuit diagram of Fig.1, the receiver requires few components. There are only two transistors. TR1 is a junction gate field effect transistor (Jfet) which functions as a regenerative detector, whilst TR2 is a high gain silicon transistor acting as an audio amplifier.

L1 is the tuned winding of the ferrite rod aerial, and this is tuned over the entire medium wave band by the variable capacitor, VC1. The tuned circuit can be coupled directly to the gate of TR1, which has a very high input impedance. So far as bias is concerned, the gate is held by L1 at the same potential as the negative rail, and the source is taken positive of the gate by the voltage dropped across R3. C2 functions as a bypass capacitor at radio frequencies.

TR1 detects the signal tuned in by L1 and VC1 due to non-linearity in its characteristic, and the detected a.f. signal appears at its source. This is passed via C3 to the base of TR2. An amplified r.f. signal is present at the drain of TR1, and this is fed back via R1, C1 and coupling winding L2 to the tuned winding, L1. There is a reversal of phase

Fig.1. The circuit of the medium wave personal receiver. This is very simple and requires few components.

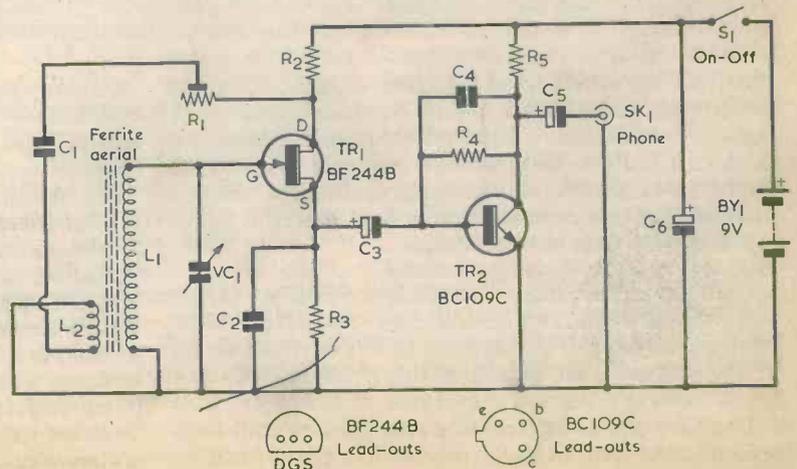



To ensure that the ferrite rod aerial is not screened the receiver is housed in a plastic case.

between the gate and drain of TR1, and a further reversal of phase in the coupling between L2 and L1. As a result, the r.f. feedback is positive. R1 is adjusted so that the feedback is slightly below the level at which oscillation occurs, and the feedback gives a considerable boost to both sensitivity and selectivity.

TR2 is a standard high gain common emitter amplifier, and the amplified signal at its collector is passed by way of d.c. blocking capacitor C5 to the output jack socket, SK1. C4 provides negative feedback at radio frequencies and assists in maintaining stability. S1 is the on-off switch and C6 is the supply bypass capacitor.

COMPONENTS

The prototype receiver is housed in a plastic box with approximate dimensions of 155 by 90 by 50mm. This is a Teko case type TEK P3P, and is available from West Hyde Developments Ltd., Unit 9, Park Street Industrial Estate, Aylesbury, Bucks, HP20 1ET. Any other all-plastic case of about the same dimensions which can take the components, including the 5in. ferrite aerial rod, could be used instead. A metal case cannot be employed as this would screen the ferrite aerial.

The transistor specified for TR1 is available from several suppliers including Greenweld, 443 Millbrook Road, Southampton, SO1 0HX. If difficulty is experienced in obtaining the ferrite rod aerial, it may be purchased direct from the manufacturer at Denco (Clacton) Ltd., 357/9 Old Road, Clacton-on-Sea, Essex, CO15 3RH. The 300pF Dilecon variable capacitor listed for VC1 can be obtained from Maplin Electronic Supplies. In the prototype, on-off switch S1 was one pole of a 4-pole 2-way rotary switch with no connections made to the unused poles. Any other type of switch, such as a toggle or slide component, could be used instead.

The ferrite rod has to be secured to the Veroboard panel by two non-metallic clamps. The author used two nylon cable clamps, described as "Cable 'P' Clips", which are available from Maplin Electronic Supplies. The clamps should be the size which is suitable for cables of diameter 9.5 to 12mm. The two 1 μ F electrolytic capacitors in the Components List are specified as 10 volts working. In practice it will be found difficult to

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5% unless otherwise stated)

- R1 10k Ω pre-set potentiometer, 0.1 watt horizontal
- R2 560 Ω
- R3 2.7k Ω
- R4 1.8M Ω 10%
- R5 4.7k Ω

Capacitors

- C1 100pF ceramic plate
- C2 0.047 μ F polyester type C280
- C3 1 μ F electrolytic, 10V. Wkg. (see text)
- C4 47pF ceramic plate
- C5 1 μ F electrolytic, 10V. Wkg.
- C6 100 μ F electrolytic, 10V. Wkg.
- VC1 300pF variable, Dilecon (Jackson)

Inductor

- L1, L2 medium wave ferrite aerial type MW.5FR (Denco)

Transistors

- TR1 BF244B
- TR2 BC109C

Socket

- SK1 3.5mm. jack socket

Switch

- S1 s.p.s.t., rotary (see text)


Battery

- BY1 9-volt battery type PP3

Miscellaneous

- Plastic case (see text)
- Veroboard, 0.1 in. matrix
- 2 control knobs
- Battery connector
- 2 cable clips (see text)
- Crystal or high impedance magnetic earphone with 3.5mm. jack plug (see text)
- Wire, solder, etc.

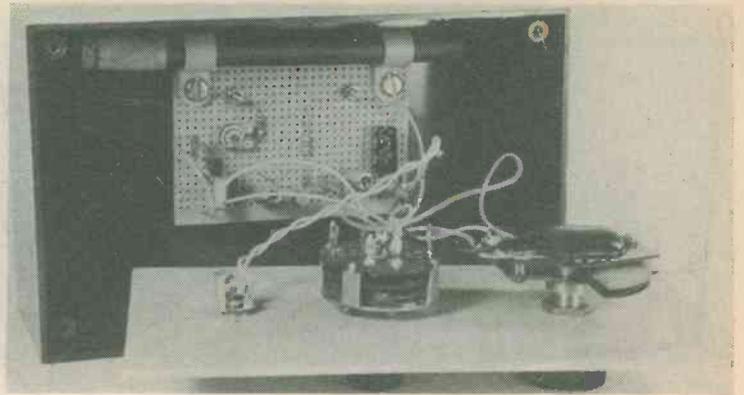Most of the parts are assembled on a Vero board panel. This connects to the front panel components by way of short flexible leads.



obtain these capacitors with a working voltage as low as this, and it will be quite in order to use $1\mu\text{F}$ capacitors with a much higher working voltage, such as 63 volts. The $100\mu\text{F}$ capacitor may also have a higher working voltage, such as 16, if this is found more convenient to obtain. The fixed resistors are listed as $\frac{1}{2}$ watt. If desired, $\frac{1}{3}$ watt resistors may alternatively be employed.

CONSTRUCTION

As can be seen from the photographs, the output jack socket, the on-off switch and the tuning capacitor are all mounted on the front panel of the

case. SK1 is to the left, VC1 to the right and S1 is between these two components. Apart from the battery, all the remaining components are fitted to a Veroboard panel of 0.1in. matrix having 18 copper strips by 30 holes. The layout is shown in Fig.2. The panel is not a standard size and has to be cut from a larger Veroboard by means of a small hacksaw. If necessary, the cut edges of the panel are then cleaned up to give a neat appearance with the aid of a file. The two 3.3mm. mounting holes are next drilled, these being clearance size for M3 (or 6BA) screws. After this, the two 4.5mm. holes (clearance for M4 screws) are drilled to take the ferrite aerial mounting clamp sec-

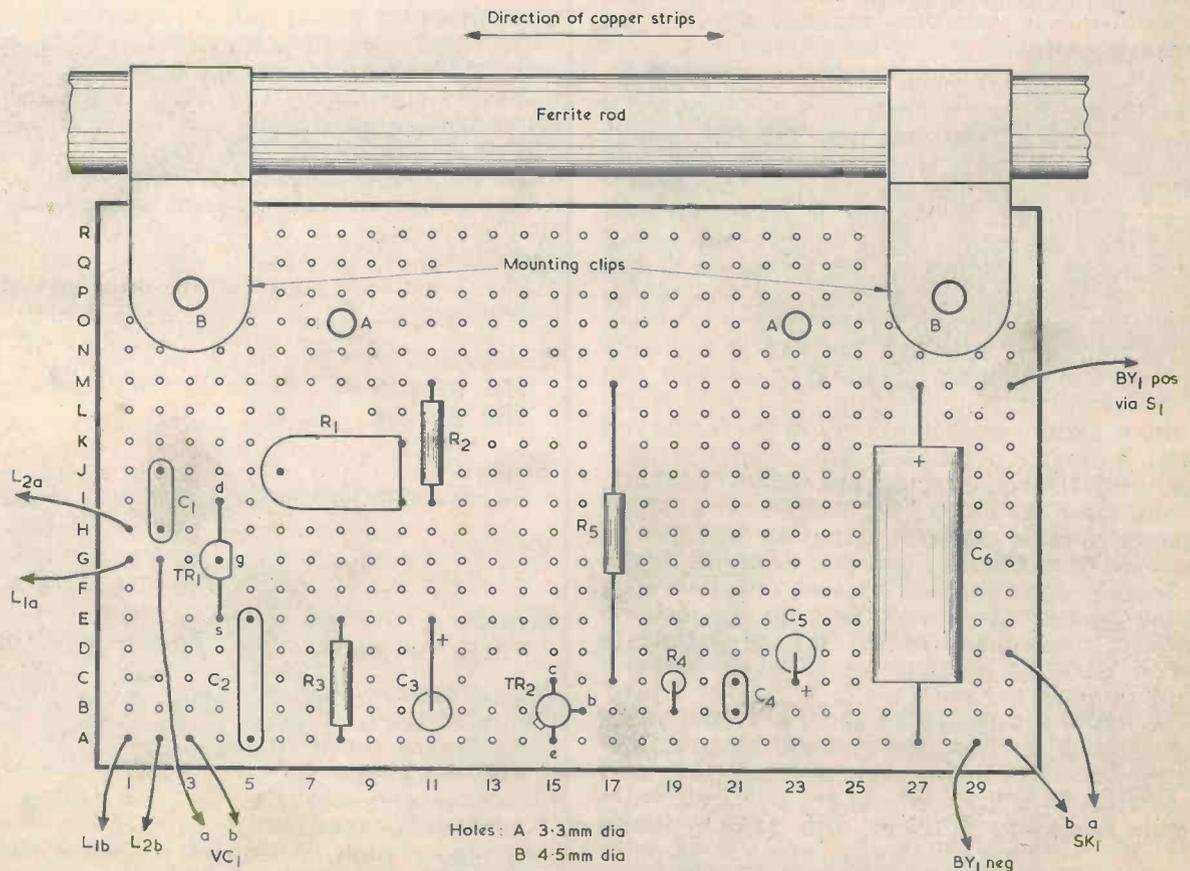


Fig.2. How the components are assembled on the Veroboard panel. There are no breaks in the copper strips.

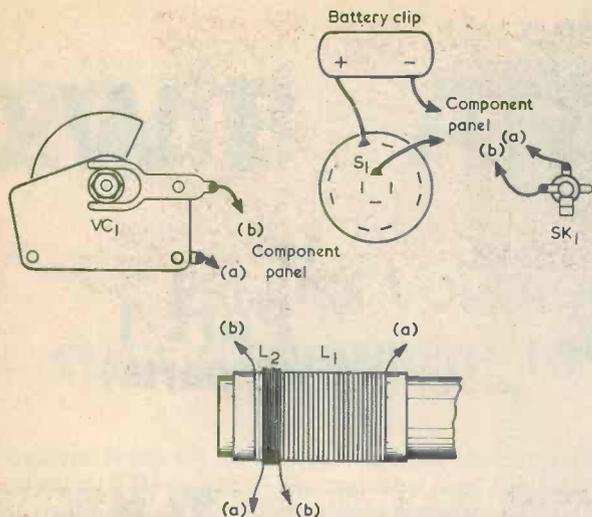



Fig. 3. The connections to VC1, S1, SK1 and the ferrite aerial windings.

uring bolts. No further board preparation is required, as there are no breaks in the copper strips.


The ferrite aerial is next mounted to the Veroboard, using two short M4 bolts with nuts. The end of the aerial coil former should be roughly flush with the end of the ferrite rod, and the coil should be to the left of the Veroboard, as seen in the view of Fig. 2. The coupling winding, L2, should be nearer the end of the rod. Mount the ferrite aerial such that the coil can be moved slightly further onto the rod, should this prove necessary later.

Next, wire up the components, as in Fig. 2. Flexible wires pass from the board to S1, VC1 and SK1, and these should be kept reasonably short. The connections at S1, VC1 and SK1 are illustrated in Fig. 3, as also are the ferrite aerial connections. It is not difficult to identify the ferrite aerial lead-out wires due to the fact that the two windings can be clearly seen and are wound with wire of different colours. The ends of the lead-out wires are tinned with solder by the manufacturer. Do *not* trim these wires as the coils are wound with multi-strand Litz wire, which can be very difficult to solder.

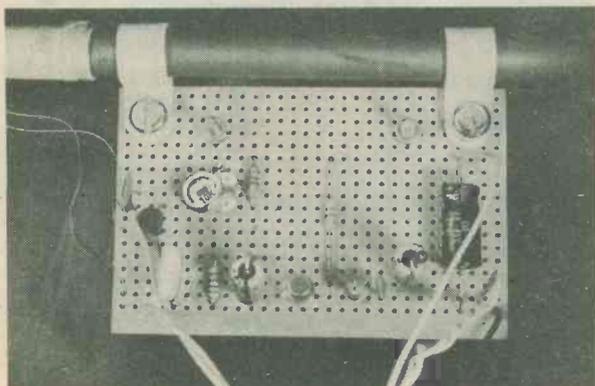The finished component panel is fixed to the



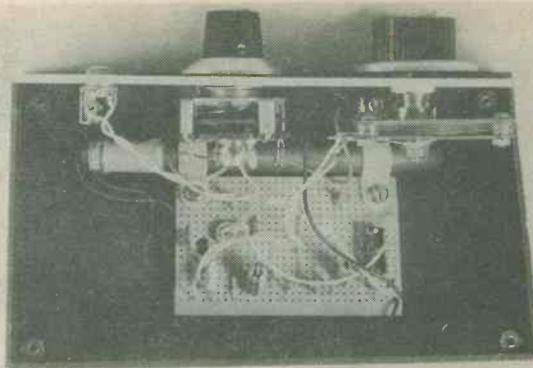A closer look at the Veroboard assembly. The ferrite rod is secured to this with two plastic clamps.



Another view of the receiver with the front panel removed.

back of the case using M3 or 6BA screws and nuts. Spacing washers are needed between the panel underside and the inside surface of the case to prevent strain on the panel when the nuts and bolts are tightened up. The ferrite aerial should be towards the top of the case as, otherwise, the performance of the set might be seriously degraded if it is placed on a metal surface. The positions of the two holes required in the back of the case can be marked out with the aid of the component panel.

There is plenty of space for the battery, and some plastic foam material can be used to keep it in place when the front panel of the case is fitted. Alternatively, a simple home-made clamp can be made up to secure it.

ADJUSTMENT

After completion of the receiver, R1 should be adjusted to insert maximum resistance into circuit. This is fully clockwise as illustrated in Fig. 2. It should then be possible to tune in a few stations, although probably at fairly low volume only. Sensitivity will increase if the slider of R1 is slowly advanced to insert less resistance. A setting will be reached at which the receiver goes into oscillation, causing whistles of varying pitch to be heard as stations are tuned through on part or nearly all of the band. Optimum sensitivity and selectivity are given with R1 backed off just enough to prevent oscillation occurring at any setting of VC1.


It should be found that the set tunes over the full medium wave band. If there is an obvious lack of coverage at the low frequency end of the band (the end where VC1 vanes are fully enmeshed) the situation can be corrected by moving the aerial coil further onto the rod. Any obvious lack of coverage at the other end of the band can be corrected by moving the aerial closer to the end of the ferrite rod. The position of the aerial coil on the rod is not especially critical as VC1 gives a tuning range which is slightly greater than is needed to cover the medium wave band. It will be necessary to re-adjust R1 if the aerial coil is moved along the ferrite rod to alter the coverage.

In practice, it may be found that tuning is so sharp that accurate adjustment becomes difficult. Should this occur, R1 may be backed off a little further from the setting which is just short of the oscillation point. Tuning will be easier if VC1 is fitted with a large control knob. ■

TWO

Part 1 (2 parts)

By
M. V. Hastings

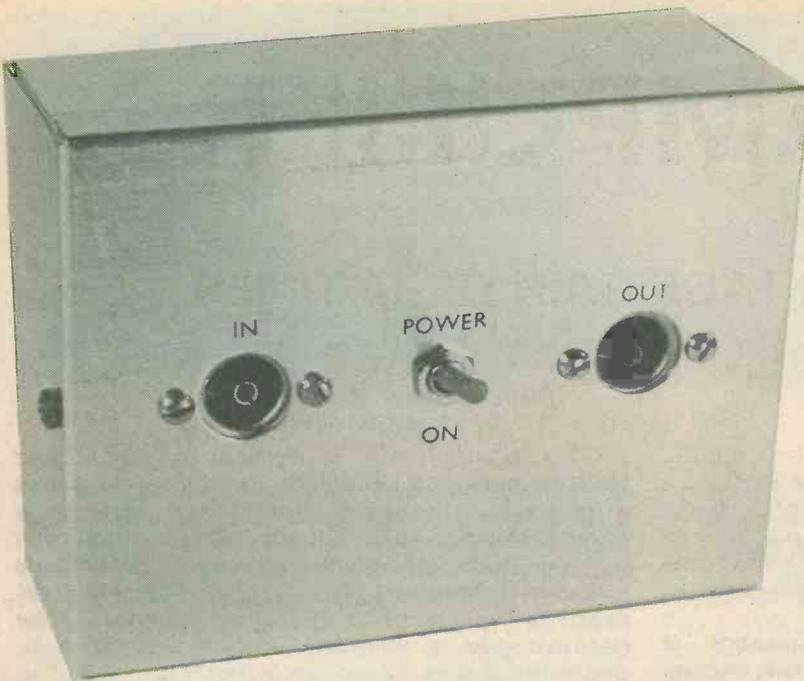

The a.c. coupled 20dB amplifier is fitted in an aluminium box which provides complete screen.

This 2-part article describes two amplifiers, each of which has a voltage gain of 20 dB, or 10 times. The first of the amplifiers employs a simple a.c. coupled circuit incorporating two transistors. The second amplifier, to be described next month, has a more complex circuit, uses a CMOS operational amplifier and is d.c. coupled throughout.

WIDEBAND CIRCUIT

The amplifier which is dealt with in this month's issue has a wideband circuit offering a frequency response which is flat up to at least 20MHz. This figure is actually the maximum at which the author's test equipment permits accurate gain measurements to be made, and the response almost certainly extends well beyond 20MHz. At the other end of the frequency spectrum the response has a -6 dB point at approximately 17Hz. The input impedance is of the order of 8k Ω although, as with any normal amplifier, this reduces somewhat at high frequencies due to a certain amount of input capacitance. The output impedance is a little under 100 Ω and, again as normal, this alters slightly at high frequencies.

The main use for an amplifier of this type is as a pre-amplifier for an oscilloscope when measuring or displaying low level high frequency or wide bandwidth signals. As the upper frequency response of the amplifier extends well beyond that of most workshop oscilloscopes, adding the amplifier does not have a detrimental effect on the frequency response of the equipment. Since it provides a voltage gain of 10 times, any oscilloscope calibration is still functional and readings merely have to be multiplied by 10 to arrive at the correct figure.

The amplifier has other applications, of course, and it can for example be used as a pre-amplifier for a digital frequency meter or an r.f. voltmeter. This unit has not been designed to function as an untuned

pre-amplifier for a receiver, and is not recommended for this application in which its noise performance may be inadequate.

THE CIRCUIT

The circuit of the amplifier is shown in Fig. 1 and is basically a conventional 2-stage directly coupled common emitter arrangement of the type often employed in audio pre-amplifiers. The first transistor, TR1, has R1 as its collector load resistance. R2 provides local negative feedback and enables overall

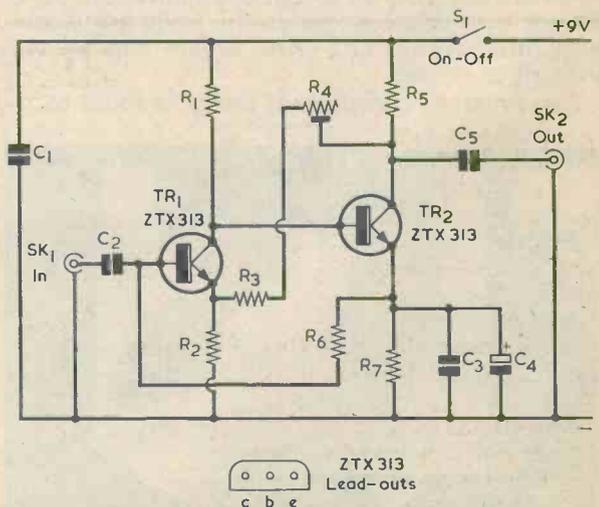


Fig. 1. The circuit of the a.c. coupled 20dB amplifier. Both transistors are high speed devices, giving a bandwidth extending to at least 20MHz.

20dB AMPLIFIERS

**PRECISE VOLTAGE GAIN OF 10 TIMES.
FLAT BANDWIDTH UP TO AT LEAST 20 MHz.**

negative feedback to be applied from the amplifier output to TR1 emitter. The collector load for TR2 is R5, with R7 as the emitter bias resistor. C4 is the emitter bypass capacitor, C3 being connected across it to improve the bypass performance at high frequencies. R6 biases TR1, and TR2 is biased by the collector voltage of TR1.

Overall negative feedback is given by R4 and R3. If the amplifier had a very high open loop voltage gain, the amplifier gain would be equal to the sum of R4 and R3 divided by R2. However, the open loop of TR1 and TR2 is only about 100 times and the gain given in practice when R4, R3 and R2 have values calculated for 10 times would be of the order of 9 times only. In this circuit, R4 is made variable so that the actual voltage gain of the amplifier can be trimmed to 10 times.

The high frequency performance of the amplifier is due to the use of high speed transistors for TR1 and TR2. The ZTX313 transistors specified (which are available from Maplin Electronic Supplies) have an fT rating of 500MHz. In order to obtain this fT figure it is necessary to run the transistors at a reasonably high collector current, and TR1 operates at a little over 5mA whilst TR2 has a quiescent collector current of just over 14mA. The use of local and overall negative feedback also helps to give a wide and flat frequency response.

C1 is the supply decoupling capacitor, and C2 and C5 are input and output d.c. blocking capacitors respectively. The total current consumption is approximately 20mA. The PP3 battery employed with the author's prototype has a reasonable life if the amplifier is not used frequently, but a larger battery such as a PP6 or even a PP9 is recommended if the amplifier is to be operated over long periods.

CONSTRUCTION

The amplifier should be housed in an all-metal box to provide screening, and the author employed an aluminium box measuring 4 by 3 by 1½in. which is available from Harrison Bros., P.O. Box 55, Westcliff-on-Sea, Essex, SS0 7LQ. A somewhat larger box will be required if a PP6 or PP9 battery is employed, and aluminium boxes with a wide range of dimensions are available from many mail-order retail suppliers. The metal box ensures that the amplifier is screened from radio signals and other possible sources of interference.

Flush mounting coaxial sockets are used for input and output connections and, in company with the on-off switch, these are mounted on the lid of the box, which is used as the front panel. A solder tag is fitted under one of the securing nuts for each socket. The printed board is connected to these sockets by way of

COMPONENTS

Semiconductors

TR1 ZTX313.
TR2 ZTX313.

Switch

S1 s.p.s.t. toggle.

Sockets

SK1 coaxial socket, flush mounting.
SK2 coaxial socket, flush mounting.

Miscellaneous

Aluminium box (see text).
Printed circuit board.
9-volt battery type PP3 (see text).
Battery connector.
Coaxial cable.
Nuts, bolts, wire, etc.


Resistors

(All fixed values ¼ watt 5%)


R1 1kΩ.
R2 100Ω.
R3 470Ω.
R4 1kΩ pre-set potentiometer, 0.25 watt horizontal.
R5 270Ω.
R6 12kΩ.
R7 270Ω.

Capacitors

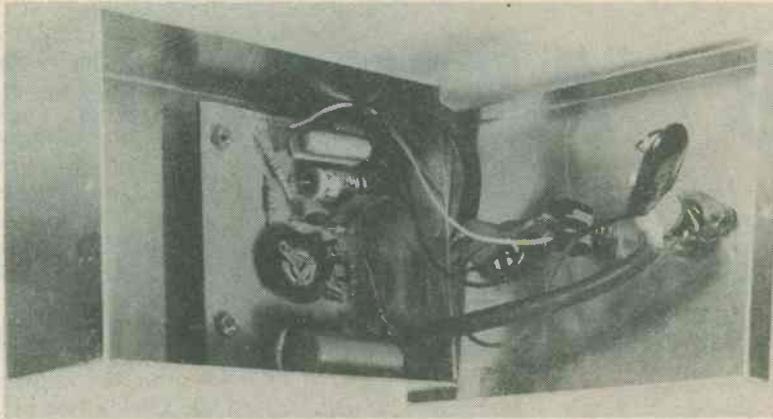
C1 0.1μF polyester type C280.
C2 2.2μF polyester type C280.
C3 0.01μF ceramic.
C4 100μF electrolytic, 10V. Wkg.
C5 0.47μF polyester type C280.



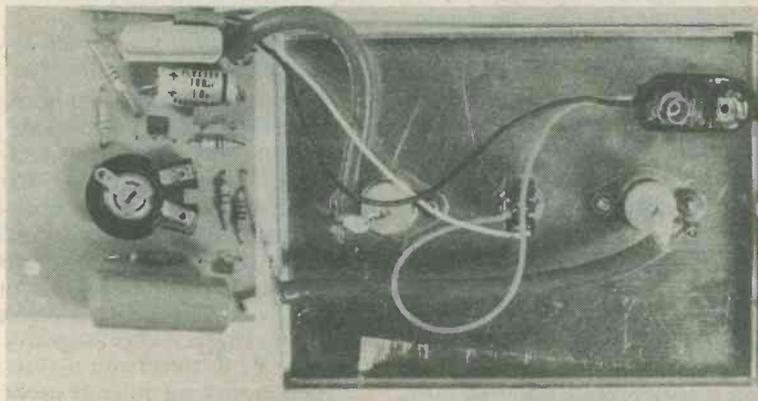The printed circuit board is secured inside the case with two 6BA bolts and nuts with spacing washers.



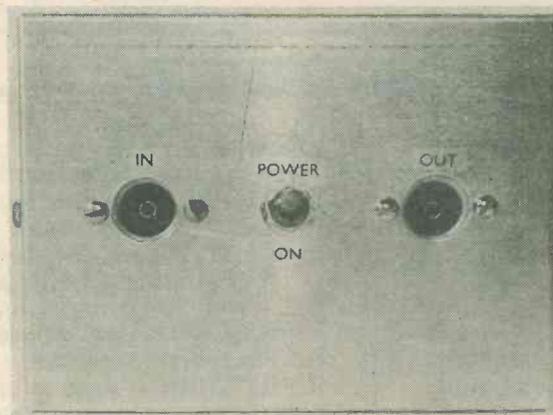The front panel and board removed from the case.



On the front panel the input socket is to the left and the output socket to the right. The on-off switch is mounted centrally.

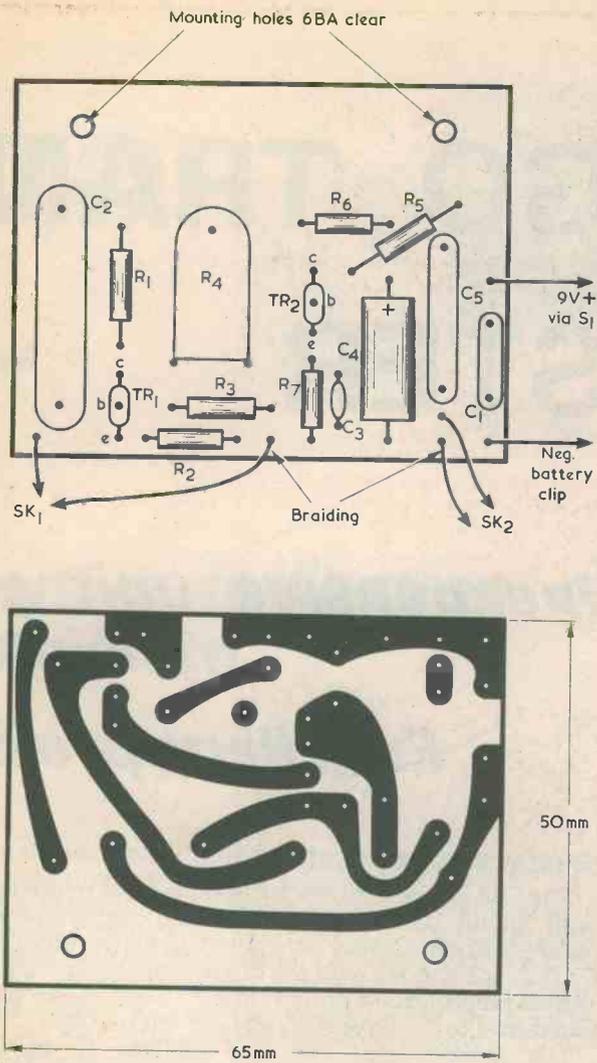


Fig. 2. The layout of the amplifier is rather critical. A suitable printed circuit board is shown here, reproduced full size.

short lengths of coaxial cable, the braiding of which is soldered to the solder tags at the sockets.

The remaining components are assembled on the printed circuit board, which is shown full size in Fig. 2. It is not recommended that any other form of construction be employed as component layout is rather critical due to the wide bandwidth of the amplifier. Another factor is that the input and output are in phase, so that any significant stray feedback is likely to cause instability. The braiding of the input and output coaxial cables is connected to the printed board at the points indicated. The holes in the board will be too small to take the braiding itself and this is connected to the board by way of pins at the board holes or via short lengths of tinned copper wire.

The board is mounted at the right hand side of the case, behind SK2, using two 6BA bolts and nuts with spacing washers to keep the underside of the board clear of the inside surface of the case. The battery is then fitted inside the case to the left of the board.

ADJUSTMENT

To set up the voltage gain of the amplifier it is necessary to have a signal generator and an amplitude measuring instrument such as an a.f. voltmeter or an oscilloscope. A signal of known amplitude is applied to the input of the amplifier. Its amplitude should be measured whilst connected to the amplifier in case the loading given by the amplifier input circuit changes it by any significant amount. R4 is then adjusted to give an output amplitude which is 10 times the input level. The input signal should be between 100Hz and 20MHz and should not produce an output greater than about 1 volt r.m.s., which is the maximum unclipped level the amplifier can provide.

If the amplifier is to be used as a pre-amplifier for a digital frequency meter, or in any other application where its precise voltage gain is of no importance, R4 can simply be adjusted to insert into circuit slightly more than half its maximum resistance. The amplifier gain will then be roughly 10 times.

NEXT MONTH

In part 2 of this article, to be published next month, the second 20dB amplifier will be described.

(To be concluded)

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who fail to supply goods or refund money and who have become the subject of liquidation or bankruptcy proceedings. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

“Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered.”

Classified and catalogue mail order advertising are excluded.

GO-NO GO TRANSISTOR TESTER

By A. P.

This inexpensive project is a very useful item of test equipment to have around the electronics workshop as it provides a quick and reliable check of bipolar transistors. It is merely necessary to switch the unit to n.p.n. or p.n.p. as applicable, and then connect the device to be tested. If the test transistor is operational a tone is heard in a crystal earphone; the absence of the tone means that the test transistor is a dud.

Inexpensive unit gives transistor test
Excellent project


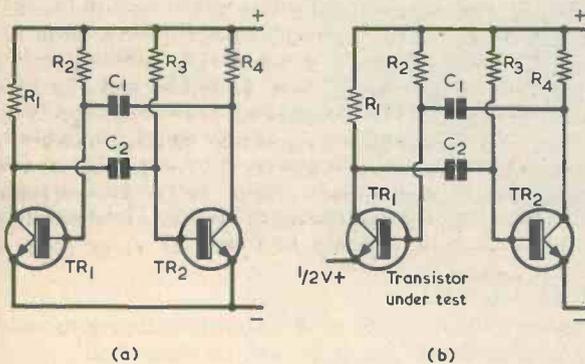


Fig.1(a). Basic astable multivibrator with n.p.n. transistors.

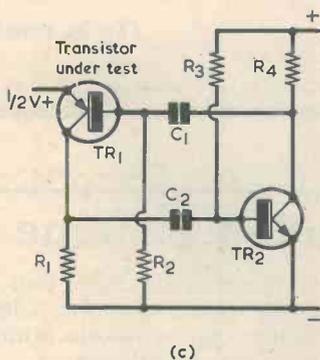(b). To simplify polarity switching requirements in the transistor tester, the emitter of TR1 (which becomes the transistor under test) is returned to a supply voltage midway between the positive and negative rails.



(c). A p.n.p. transistor can be catered for by returning R1 and R2 to the negative rail. This produces a different mode of oscillation.

OPERATING PRINCIPLE

The unit is based on the standard astable multivibrator circuit shown in Fig.1(a). The multivibrator oscillates at a frequency dependent upon the values of C1, C2, R2 and R3, and the cross-coupling and high mutual amplification present in the circuit causes the transistors to be turned on and off alternately.

The multivibrator will also oscillate if, as in Fig.1(b), the emitter of the left-hand transistor, which can now be looked on as the transistor under test, is connected to a voltage midway between the supply rails instead of directly to the negative rail. This altered method of connection allows a simple n.p.n. - p.n.p. switching circuit to be used in the transistor tester.

The circuits of Figs. 1(a) and (b) apply to an n.p.n. test transistor. The configuration shown in Fig.1(c) is set up if the test transistor is p.n.p. The collector and base resistors, R1 and R2, are now returned to the negative rail, giving the required supply polarity for a p.n.p. transistor. Also, the mode of oscillation is different. Both transistors are on at the same time and then turn off at the same time during the oscillation cycle.

At switch-on of the power supply in Fig.1(c) both C1 and C2 are discharged. R4 and C1 hold the base of TR1 positive of its emitter and R1 and C2 hold TR2 base at the same potential as the negative rail. The two transistors are thus turned off. C1 now charges via R2 and C2 charges via R3. The base of TR2 is soon taken 0.6 volt positive of its emitter and TR2 starts to turn on. Its collector goes negative, taking TR1 base negative by way of C1, whereupon TR1 collector then takes TR2 base positive by way of C2. Both transistors are turned hard on at this instant.

C1 and C2 start to take up charges corresponding to this new situation with the result that, after a period, the base of one of the transistors is biased only

ISTOR

Roberts

positive indication of serviceability.

for the newcomer.



The Go-No Go Transistor Tester. The only control is the 3-way switch in the centre of the front panel, and this selects "Off", "N.P.N." and "P.N.P." The test transistor connects to the DIN socket on the right of the panel.

by the current flowing through its base bias resistor. Neither transistor is now saturated and both are capable of linear amplification, with a very high degree of mutual amplification between the two. The very small reduction in the base current of the transistor whose base capacitor has charged results in a very rapid changeover with both transistors turned off. C1 now holds TR1 base positive of its emitter and C2 holds TR2 base negative of its emitter. The capacitors charge as before, causing both transistors to turn on again after a period. The cycles then proceed.

The frequency of oscillation with the circuit of Fig.1(c) differs slightly from that given by the circuit of Fig.1(b). If the resistors and capacitors in both circuits have the same values, the oscillator of Fig.1(c) runs at a higher frequency.

FULL CIRCUIT

The full circuit of the transistor checker appears in Fig.2. The right hand transistor in the circuits of Fig.1 is now TR1, with R5 as its base resistor and R6 as its collector resistor. The two cross-coupling capacitors are C3 and C4. R1 and R2 provide the half-voltage supply point of Figs. 1(b) and (c), with C2 functioning as bypass capacitor. R3 and R4 are the base and collector resistors respectively for the test transistor, and S1(a) returns these to the positive rail for n.p.n. transistors and to the negative rail for p.n.p. transistors. S1(b) provides on-off switching. These two switches are two sections of a 4-pole 3-way rotary switch, with no connections being made to the unused sections. This switch is the only control in the unit. C1 is a supply bypass component. The current consumption of the circuit is about 7mA, both with no test transistor connected and when the astable is oscillating.

Oscillation is at an audio frequency and the signal amplitude at TR1 collector is about 9 volts peak-to-peak. This is too high for comfortable listening with a crystal earphone and R7 is included in series to provide attenuation. The crystal earphone is plugged into socket SK1. An output tone is only produced when a serviceable transistor is correctly connected to the unit and the function switch is set to the proper position. Open-circuit, short-circuit and very low gain test transistors will not oscillate to give the audio tone in the earphone.


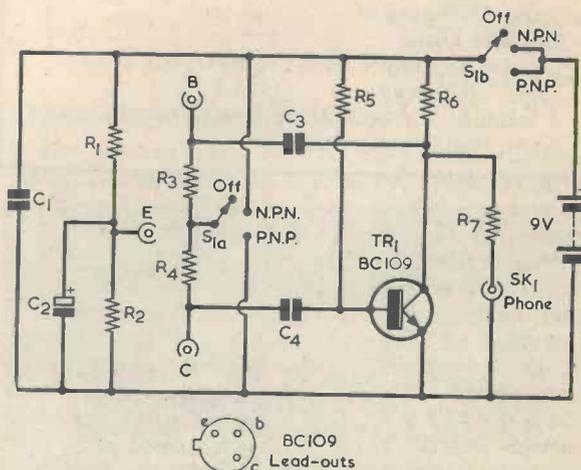


Fig.2. The circuit of the Go-No Go Transistor Tester. The transistor under test connects to the points indicated as "E", "B" and "C".

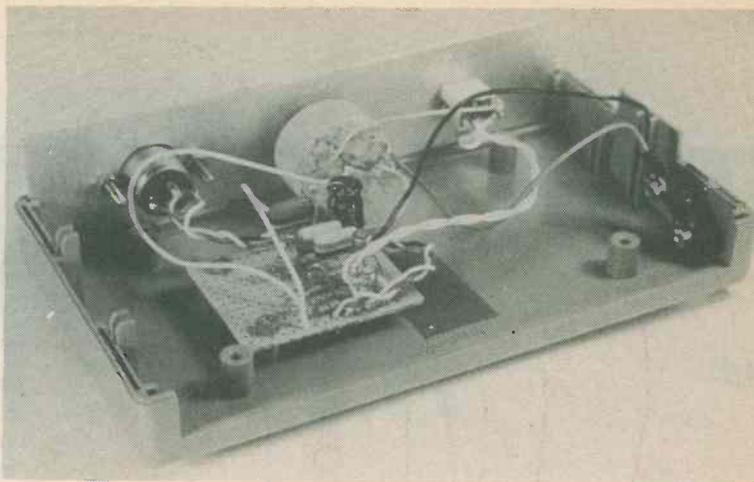The transistor tester with its top cover removed. A phone jack socket different to the more common "open" type shown in Fig.3 was used in the prototype.



COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5%)

- R1 820 Ω
- R2 820 Ω
- R3 27k Ω
- R4 4.7k Ω
- R5 47k Ω
- R6 4.7k Ω
- R7 560k Ω

Capacitors

- C1 0.1 μ F polyester, type C280
- C2 100 μ F electrolytic, 10V. Wkg.
- C3 0.047 μ F polyester, type C280
- C4 0.047 μ F polyester, type C280

Semiconductor

- TR1 BC109

Switch

- S1(a) (b) 4 pole 3 way, rotary

Socket

- SK1 3.5mm. jack socket

Miscellaneous


- Verocase type 75-1237J
- 9-volt battery type PP3
- Battery connector
- Veroboard, 0.1 in matrix
- 3-pin DIN socket
- Control knob
- Crystal earphone with 3.5mm. jack plug
- 3-pin DIN plug
- 3 miniature crocodile clips with vinyl sleeves
- Nuts, bolts, wire, etc.

CONSTRUCTION

The prototype is housed in a Verocase type 75-1237J, which has dimensions of 153 by 84 by 39.5mm. As can be seen from the photographs, S1(a) (b) is mounted in the centre of the front panel, with output socket SK1, to its left and a 3-pin DIN socket to its right. Connections to the test transistor are made by way of this socket.

All the remaining components, apart from the battery, are assembled on a 0.1in. matrix Veroboard panel having 15 copper strips by 13 holes. There are no breaks in the copper strips, and the component wiring layout is shown in Fig.3. Also shown in this diagram are the connections from the board to the front panel components. The Veroboard panel is secured to the base of the case with 6BA or M3 bolts and nuts, using spacing washers to keep the board underside clear of the case bottom. The board is positioned to the rear of S1(a) (b) and the DIN socket, as shown in the photograph of the case interior, with strip "O" towards the centre of the case. This leaves plenty of space for the PP3 battery.

A close-up view of the Veroboard assembly. This is bolted, with spacing washers, to the bottom of the case.

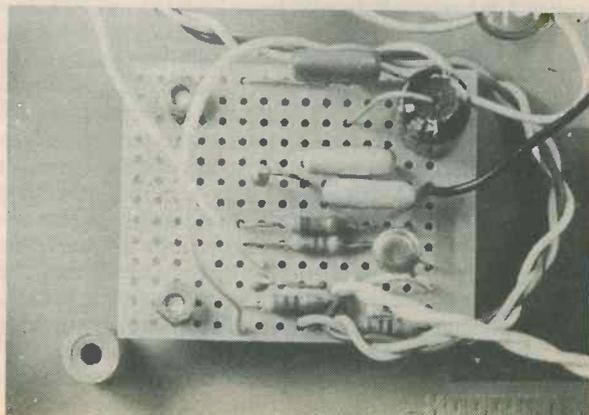


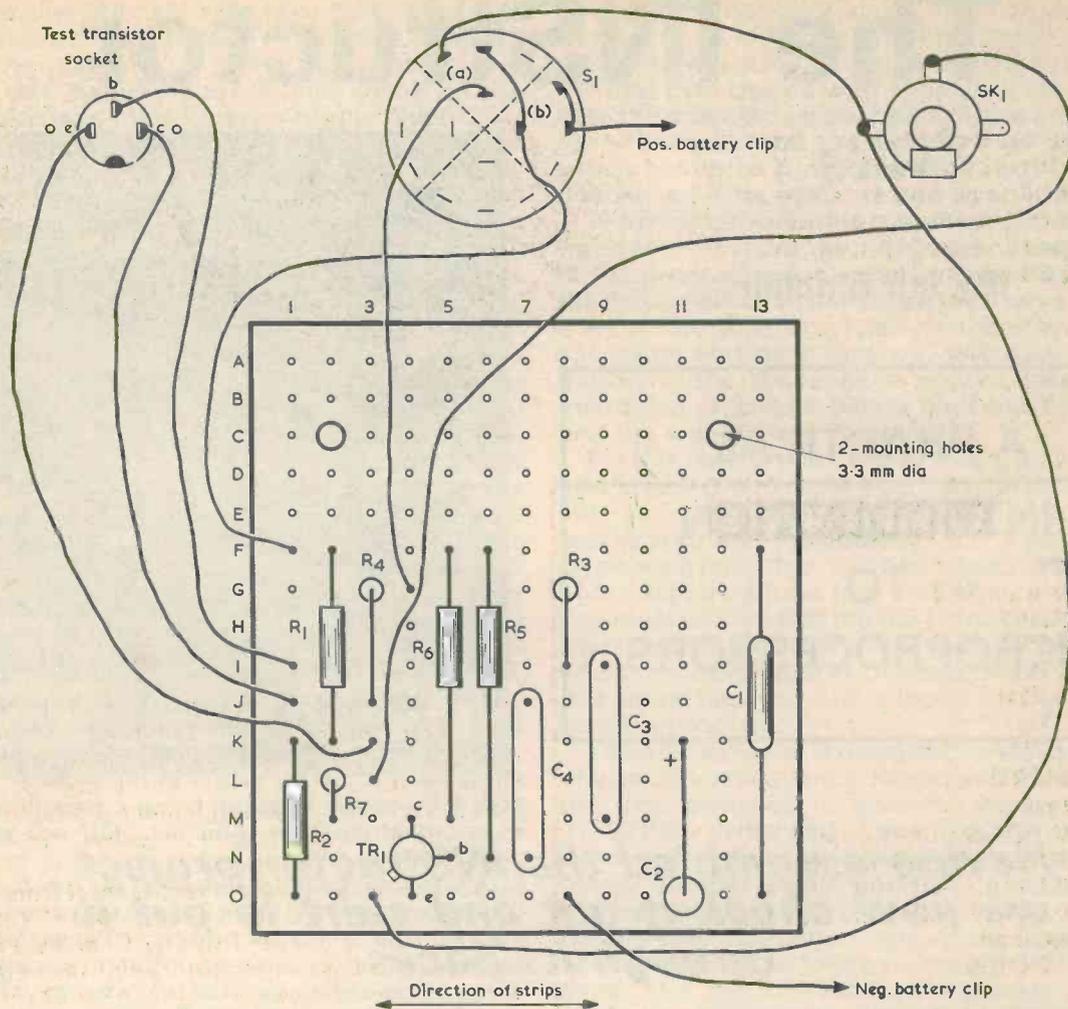


Fig.3. Wiring up the transistor tester. There are no breaks in the copper strips of the Veroboard. Before wiring to S1(a) (b) confirm the corresponding inner and outer tags with a continuity tester in case the switch employed has a different tag layout to that shown here.

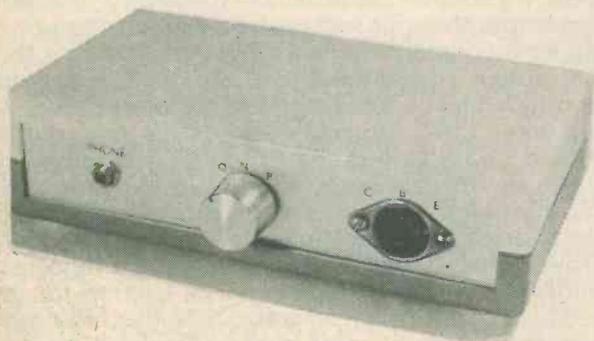

The use of a readily available manufactured case simplifies construction and gives the completed transistor tester a neat and professional appearance.

USING THE UNIT

The leads of many TO-18, TO-5 and plastic encapsulated transistors will be found to plug into the DIN socket without difficulty. Take care to ensure that the test transistor is connected correctly and that the function switch is at the proper setting, so that misleading results are avoided.

Some transistors, particularly power types, cannot connect directly to the socket, and a test lead assembly is made to cater for these. The assembly consists of a 3-pin DIN plug with three short flexible p.v.c. covered leads of different colours connected to it. The free ends of the leads are terminated in miniature crocodile clips with vinyl sleeves.


It should be noted that the unit is only suitable for use with a crystal earphone. The tone is hardly perceptible if a low impedance magnetic type is employed. ■

The INSTRUCTOR

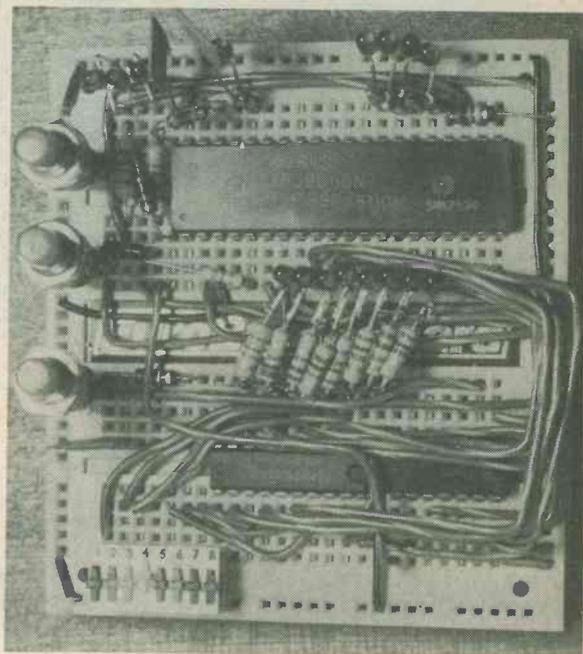Part 3

By Ian Sinclair

A PRACTICAL INTRODUCTION TO MICROPROCESSORS



Having assembled the INSTRUCTOR project we now check it out and start to put it through its paces.

Now the INSTRUCTOR assembly is all ready to go, but we've got a few odds and ends to sort out first. First of all, remove the shorting link you fitted before inserting the 8060 – it's not good for power supplies to have positive and negative shorted. Next make sure that you know what each l.e.d. signal and what each switch is for. Keep last month's article opened out at its Fig.3, and this will act as a reminder about these points.

POWER SUPPLY

Connect up the board to the power supply. The negative supply goes to either of the Y lines and the positive to one of the holes along line X1. With a 4.5 volt battery, this simply means making the two connections. Mains power supplies often have an earth connection which is separate from the positive and negative terminals. If you're using such a supply connect the earth to one of the Y lines, then connect the negative and finally connect the positive. By this time you've checked the board often enough – I hope – and all you need to do is to make sure that you've removed the shorting link, and plugged in the supplies correctly. Remember that the voltage of a mains supply, unless it's a regulated 5 volt supply, should be checked before plugging in – it's no use switching on and only then remembering that you had set it to 12 volts, your microprocessor will have gone long before you reach for the switch again.

If all is well switch on, and look at the l.e.d.'s. When any digital circuit is switched on, every flip-flop comes on at random, so that some store 1's and others store 0's. The microprocessor is no exception, so you'll find that various l.e.d.'s come on. If nothing comes on, it's probably because there's no supply voltage or because the oscillator isn't oscillating. The time constants we've used, in the form of the capacitors between A17, A21 and the Y1 line, are on the long side for the 8060 and though all of mine oscillated happily, yours might not. If you're *sure* that everything else is OK, try smaller capacitors in these portions, but remember that this will probably mean changing the time constant at the GO switch. Now for the real crunch – press the RESET button. This should extinguish all l.e.d.'s while the button is pressed, and when the button is released only two l.e.d.'s should be lit. One is the READ l.e.d., indicating that the microprocessor is waiting for some information to go in, the other is the first l.e.d. of the address group at the top of the board, which shows address 0001. These two l.e.d.'s together tell us that the microprocessor is waiting for its first byte of data from address 0001. In a full-scale system this would come out of a read-only memory, and the whole action would take only a few microseconds. In our system, the data comes from the data switch, and the action takes as long as you like!

Having checked that the reset action is working

satisfactorily, the next step is to make sure that the system will go smoothly from one program step to the next, with no "bouncing" problem. We can do this by setting up an instruction on the data switches – the binary number 00001000, which on our switches means switch 5 up and the rest down. When you set this you'll see the data l.e.d.'s displaying the same number unless there's a data wire crossed somewhere. That's because the microprocessor is waiting at the "read" part of its cycle, so that the buffer i.c. is allowing the data switches to affect the l.e.d.'s. The data *isn't actually read into* the microprocessor at this point. With the INS8060 the data is read in at the *back* edge of the pulse from the NRDS pin and that happens just at the instant when you press the GO button. Press RESET and release, and you should have the address 0001. Now ignore the eight data l.e.d.'s and look at the address l.e.d.'s only. Press GO and you should see the address change to 0010 (binary 2). Press again, and you should get 0011 (binary 3). Each push of the GO button should increase the binary count by 1 until you reach 1111. The next count will extinguish the four l.e.d.'s because the following number is 10000, and we have no l.e.d. on the next address line, AD4. Yes, I know it's the fifth address line, but both data and address pins are numbered starting from 0, so that the sequence is AD0, AD1, AD2 and so on. It may seem odd but there's a good logical reason – the AD0 line like the data D0 line, represents the zero power of 2, which is 1. The AD1 and D1 lines represent the 1st power of 2, which is 2, the AD2 and D2 lines represent 2 squared (=4) and so on.

We digress. The important thing is to be sure that there are no numbers skipped on the address count. Try resetting at various stages of the count and starting again. Every now and again, you may find that the address doesn't shift. That's not too important so long as it doesn't happen too often, but what we don't want is, for example the address 0010 to jump to 0100 on a single push of the GO button. If this happens the remedy is to reduce the value of the 0.1µF GO button capacitor, so making the pulse on the NHOLD pin a little shorter. (The push button switch itself can also cause multiple triggering, as we found when we used one with a noticeably "rough" mechanical operation – Editor.)

INSTRUCTION

The input byte 00001000 which we've been using is one of the single byte instructions of the INS8060, and it signals NO OPERATION, shortened to NOP. A single byte instruction means one which is not followed by another byte of data, so that the microprocessor will treat this as an instruction *and will also treat the next byte as an instruction*. This is one of the points which worry newcomers to microprocessing, and which never seem to be explained in textbooks, because beginners always ask how the microprocessor "knows" which group of 8 bits is an instruction and which is a number. The answer is that the microprocessor sets up gates and counters to identify the bytes. The first byte in after resetting is *always* treated as an instruction. What happens after that depends on what this first byte was. For example, if the first instruction byte starts with 0,

as the NOP instruction does, the microprocessor treats this as a single byte instruction, and the next byte will also be treated as an instruction. If the first byte begins with 1, as we'll see shortly, then the microprocessor treats this as an instruction – but will treat the *next* byte as a number which has to be processed. The next byte after that will be once again treated as an instruction.

The microprocessor is a strict-sequence device – you can't interchange numbers and instructions in the program because everything has to be in the correct order. In this series we'll work through a lot of instructions to see how the microprocessor treats numbers, and you will have to keep exactly to the sequence as shown, resetting as instructed. Just one binary digit out anywhere, and the whole thing "crashes"!

For this reason you need to keep a watch on the address l.e.d.'s to make sure that the address has changed at each press of the GO button. Once you're sure that the address l.e.d.'s step up one bit on each push then you don't need to keep track of the actual address (not until later, at least) but you must be sure that the GO button has operated by checking that there is a change of address when the GO button is pressed. Make a note of this point because one slipped instruction will wreck a program.

The next exercise is designed to rub in this idea of instruction sequence. Reset, and then arrange the data switches to give the binary number 11000100 – switches 1, 2 and 6 up, the rest down. Once again, the led.'s should show the same binary number unless you have a crossed wire somewhere. This instruction starts with 1, so it's a double byte instruction, one which needs a second byte of data to follow it. Press the GO button, once, and the address l.e.d.'s change to 0010. What has happened? The microprocessor has been instructed to load. Load what? The next byte that you put in right now. To save a lot of switch operation, reset switch 1 only so that the number that is left set up is 01000100 (68 in decimal). Push the GO button again and the address changes to 0011, with this number loaded into the accumulator of the microprocessor.

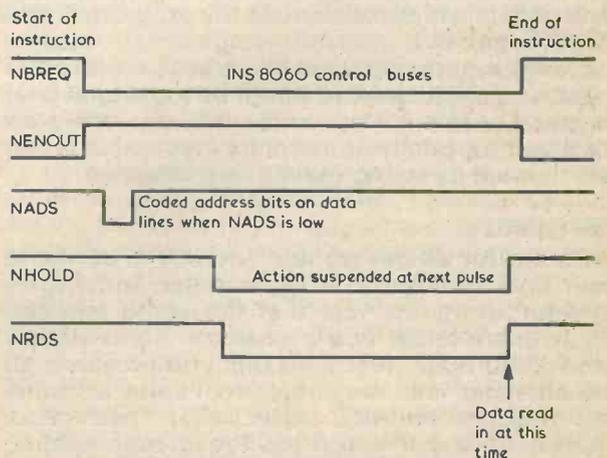


Fig.1. The pulse sequence of outputs from the 8060. This shows only command pulses, not the address pulses nor any data outputs.

The accumulator is, as its name suggests, the main store of the microprocessor, where all numbers that are to be operated on are loaded into or taken from. How do we know that this number is loaded in? We can check by asking the microprocessor to "write" it out again, but we'll need to see what has to be done to write data out first.

Reading, incidentally, ALWAYS means that data is going INTO the microprocessor, and writing ALWAYS means that data is coming out of the microprocessor. Keeping to this convention avoids confusion and we'll use it throughout.

Now, at the moment the data l.e.d.'s are displaying the number 01000100. That's only because the data switches are set up to this number, though. Remember that whenever the microprocessor is *holding* (with the READ l.e.d. on) the data l.e.d.'s will show the same number as the switches are set to. We can check that the number was loaded in by another procedure. Set the data switches to 11001000 and push the GO button *twice*. At the first push the address l.e.d.'s advance to the next address, 100, but at the second push several interesting things happen. For one thing, the READ l.e.d. goes out. That shows that the microprocessor is not reading, and the data l.e.d.'s are displaying a number which is stored in the accumulator, rather than the number set up on the data switch. A quick look at the data l.e.d.'s shows that they are displaying 01000100. That's the number we fed into the accumulator, not the number set up on the switches (which is 11001000). The other odd thing is the address – it's skipped to 1100 on the four low-order l.e.d.'s, and the AD11 l.e.d. is on as well! We'll deal with these address jumps later, but there's nothing wrong when the number skips like this. The important point is that by setting up 11001000 and pressing GO *twice*, we can cause the l.e.d.'s to display a number which was in the accumulator. From now on we will refer to that procedure as DISPLAY, and each time this occurs you'll know that we mean the steps 11001000, GO, GO.

The instruction we started with, 11000100, is called LOAD IMMEDIATE, shortened to LDI, and it has the effect of loading into the accumulator the byte of data which follows it in the program. If you forget to put in a byte following the LDI instruction, the program crashes! There are several other LOAD instructions which we'll be looking at later in part 6, when we deal with memory reference instructions, but the immediate instruction is one which we'll be using mainly in this series.

ARITHMETIC

So far, for all our trouble and effort, all we've been able to do is to load in a number, and display it. Apart from the fact that the same exercise might have taken you a week on some widely advertised units, it's not exactly impressive, so the next step is in the direction of some arithmetic. There is an ADD IMMEDIATE instruction, shortened to ADI, which has the effect of adding the next byte (after the ADI code) to the accumulator. We can demonstrate this by setting up a small number in the accumulator, adding another one to it and then displaying.

The sequence after resetting is shown in Fig.2.

```

RESET
11000100 LDI
00000100 4
11110100 ADI
00010100 20
11001000 Display
11001000
  
```

(PRESS GO AFTER EACH
BYTE SHOWN)

Fig.2. A binary addition program.

The byte 11000100 is LDI, instructing the 8060 to load in the *next* number, which is 00000100. That gives us binary 100 (decimal 4) loaded into the accumulator. The next byte 11110100 is ADI, which has to be followed by a number. We've used 00010100 (decimal 20) to minimise switch-juggling, and the press of GO after setting this up performs the addition. To see the answer, use the DISPLAY steps, and the answer which appears on the data l.e.d.'s is 00011000 (decimal 24) which is correct. We'd be a bit worried if it turned out to be wrong, but it's nice to see that it all actually happens.

DECIMAL ADDITION

There's another type of addition on offer in the 8060's instruction set, decimal addition. This is, as the name suggests, addition of decimal numbers but, because the microprocessor can use only binary numbers, the decimal number is BCD coded and the results are not the same as the binary equivalent of the decimal number. The decimal number 36 for example is BCD coded as 0011 (that's 3) 0110 (that's 6), making 00110110 in all. In pure binary, 36 is 00100100 – quite a different byte. Because of this, BCD numbers don't add up in the same way as binary numbers, as Fig.3 shows. The rules for addition are not terribly complicated, but there's no point in going

2	4	Decimal	3	8
0010	0100		0011	1000

So that, in BCD, 24 is 00100100
and 38 is 00111000

Addition: Binary	00100100
	00111000
	01011100

BCD result is 01100010 (decimal 62).

Fig.3. BCD arithmetic. The answers from a BCD addition are quite different from those of a binary addition, even though the same bits are used.

```

RESET
11000100 LDI
00100111 BCD27
11101100 DAI
00111000 BCD38
Display

```

Fig.4. A BCD arithmetic program for the 8060.

```

1 1 0 0 0 0 0 0 192
1 1 1 1 0 0 0 0 240

```

```

1 1 0 1 1 0 0 0 0
Carry bit Byte in accumulator

```

Fig.6. The "carry" illustrated.

through them, because we can do the addition in decimal numbers, and the microprocessor is already programmed to deal with BCD.

A decimal addition program is shown in Fig.4. We start, as usual, by resetting so as to clear the microprocessor of any data in store. The first instruction is LDI, followed by the BCD number, in this example 27 (00100111). Decimal add immediate (DAI) is 11101100, and we've followed it with 38 (00111000). As usual, the answer is worked out when the GO button is pushed after setting up the decimal-add number, and we can display in the usual way, getting 01100101 (decimal 65).

Want to try a few for yourself? Just use the same instruction sequence as has been shown, but substitute your own 8-bit numbers for the data bytes in the examples.

These two immediate instructions cover two important operations, but we haven't learned all the secrets of the INS8060 by a long way. Just to underline this, try the sequence which is shown in Fig.5. This starts off by loading a binary number 11000000 (decimal 192) and then adding to it the number 11110000 (decimal 240). The answer which pops out of the display is 10110000 (decimal 176) which is obviously wrong. Why? We can see why when we try it out on paper (Fig.6). The numbers we are adding are of eight bits each, but the answer to the addition should have nine bits. In arithmetical language, there's a carry to the next place. This carry is not stored in the accumulator, so where is it? The answer comes later. After the NOP step which simply allows the microprocessor to get back to its normal address numbers, we load 00000001

```

RESET
11000100 LDI
11000000 192
11110100 ADI
11110000 240
Display
00001000 NOP
11000100 LDI
00000001 1
11110100 ADI
00000010 2
Display

```

Fig.5. More binary addition, using larger numbers.

```

RESET
11000100 LDI
11000000 192
11110100 ADI
11110000 240
Display
00001000 NOP
00000010 CCL
11000100 LDI
00000001 1
11110100 ADI
00000010 2
Display

```

Fig.7. The same addition as was done in Fig.5, but with the carry cleared.

(decimal 1) and add (immediate) 00000010 (decimal 2). This should, of course, give 00000011 (decimal 3), but we get 00000100 (decimal 4) when we display this time. That's part of the answer to the question – the carry bit is added into the next addition. It's stored in a flip-flop which forms part of what's called the status register of the 8060, and is automatically added into the next addition.


Why should this be done? The reason is simple. If we're adding large numbers which need more than eight bits, we can add only eight bits at a time, because that's all the accumulator can hold. What we do then is to add the lower eight bits, store the carry and then add it into the next addition, which will be of the upper eight bits of a sixteen bit number. We don't have to worry about the carry when we're operating with sixteen bit numbers, then, because the microprocessor attends to all this for us. Suppose we don't want the carry added in? We may not be interested in sixteen bit addition, so that the next sum isn't of the higher eight bits of the first one. In that case, we have an instruction, shortened to CCL, which clears the carry/link. This one is a single byte instruction, coded 00000010. To see it at work, try the instruction set in Fig.7. This repeats the same loadings and additions as we used in Fig.5, but this time with the carry cleared so that the carry is not added into the second sum. Just to complete the set, there's also an instruction which sets the carry link (to 1) – we'll see why in the next Part.

(To be continued)

'LISA' 2-BAND PORTABLE

Part 2 (Conclusion)

By Sir Douglas Hall,
Bt., K.C.M.G.

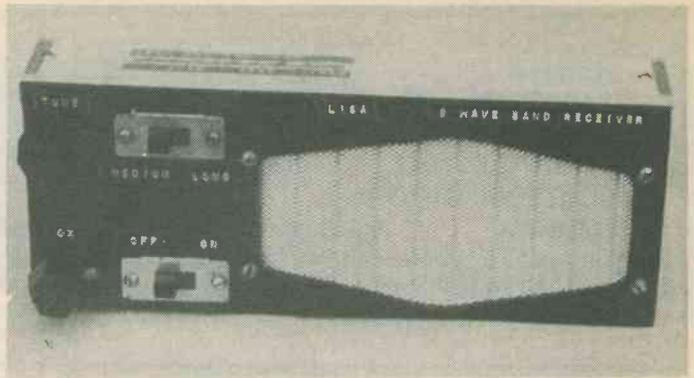

The assembled receiver in its home-constructed case.

Wiring and setting up this ingenious 3 transistor reflex design.

In last month's article we completed the mechanical assembly of the receiver, ending with the construction of the permeability tuning drive. We deal next with the wiring.

WIRING

The wiring is carried out as shown in Fig.6. Note that the end mounting lugs of T1 and T2 are soldered to tags on the 19-way tagstrip and that the transformer mounting clamps complete some of the negative supply rail circuitry. For clarity, many of the tagstrip components are shown spread out. In practice, components should be connected with short direct leads

and all parts should be kept within the edges of the Fig.2(a) panel. C9 lies immediately over S2. When VR3 is fitted, make sure that it does not foul the ferrite rod as the tuning control is operated. Connections to the two transformers follow the lead layouts shown inset.

When wiring has been completed, set VC1 to minimum capacitance, VR1 to a central setting and VR3 fully anticlockwise as shown in Fig.6. Switch on. There may be oscillation or distortion which is unaffected by the setting of VR2. Should this occur, reverse the connections to leads 3 and 4 of T1. Put S1(a) (b) to the medium wave position, whereupon it should be possible to receive many stations after

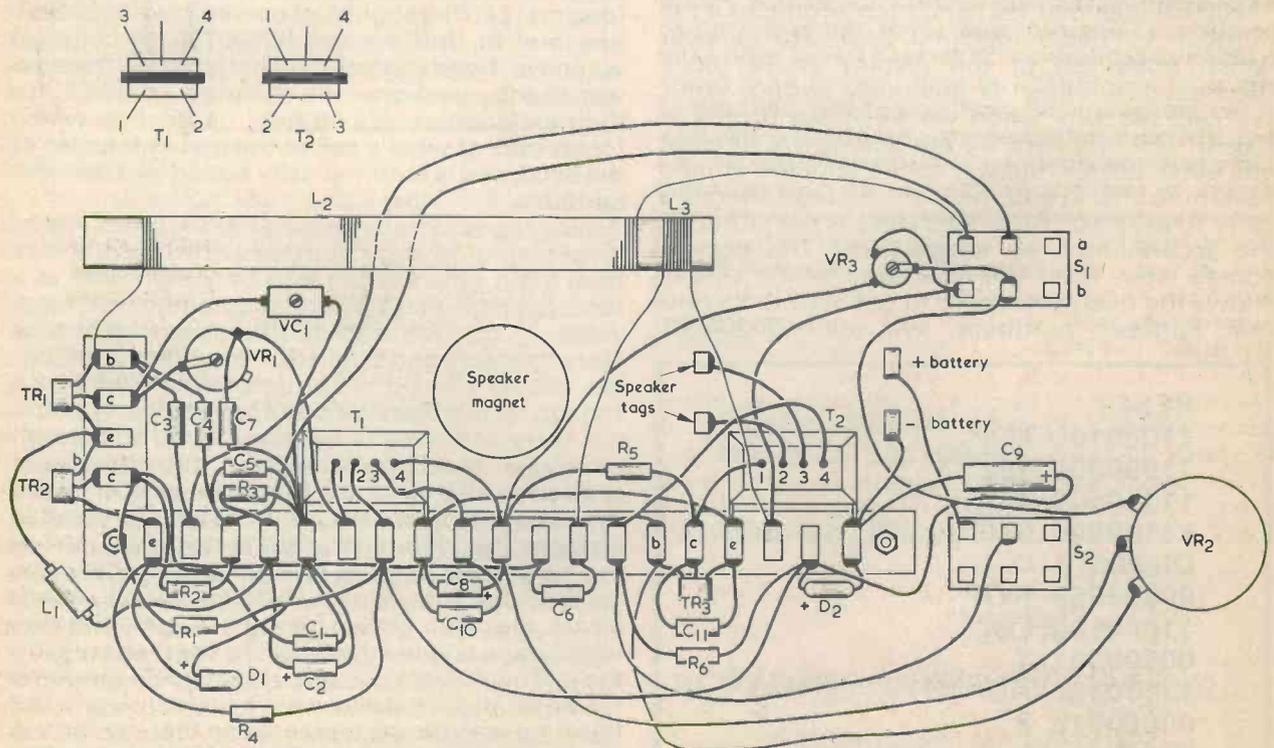


Fig.6. Wiring up the receiver. The cathode end of zener diode D2 is indicated by a plus sign. Components are shown spread out for clarity but in practice should be kept within the outside edges of the receiver front panel.

During wiring, all components should be kept inside the edges of the front panel.


dark, and quite a number during daylight hours, by adjusting the tuning control. The receiver should be kept at full sensitivity, whilst tuning, by setting VR2 so that the receiver is almost, but not quite, oscillating. When all is proved well adjust VR1 until a setting is found where the least possible adjustment is needed in VR2 to maintain maximum sensitivity over the tuning range from about 250 to 450 metres. After this adjustment has been carried out, the need will still arise to set VR2 back for stations of lower wavelength than about 250 metres. Adjust VC1 until the effect disappears. This may necessitate a slight re-adjustment in VR1 to maintain as constant a setting as possible in VR2 for critical reaction over the range, now, of about 200 to 450 metres. When these adjustments are completed it will probably be found that VR2 has to be advanced a little further for stations with wavelengths greater than 450 metres, and that oscillation may tend to occur a little more readily around 350 metres than at other tuning settings. However, in general, very little re-adjustment of VR2 should be necessary for critical reaction throughout the medium wave band.

LONG WAVES

Set S1 to the long wave position and tune in Radio 4 on 1,500 metres. VR2 will need to be well advanced for optimum reaction at this wavelength. Switch back to medium waves and adjust VR3 so that critical reaction is obtained with about the same setting which was employed with the long wave 1,500 metre signal.

Setting up is now complete and the top panel of Fig.2(b) may be secured to the panel of Fig.2(a), using thin countersunk wood screws. The top panel should be positioned so that the 6BA screw tuning pointer appears within, but does not pass through, the slot provided for it. Either long edge of the top panel may be secured to the front panel; choose the edge which allows the most free travel of the 6BA tuning pointer. The front panel will now stand proud of the top panel by a little less than 1/8 in., leaving room for a piece of thin Perspex to cover it later.

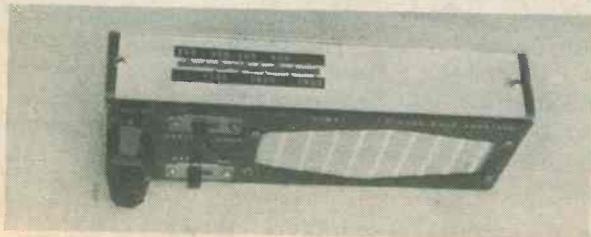Cut out a piece of thin white card to the dimensions shown for the top panel of Fig.2(b) and glue this to the panel. Draw out a tuning scale on this calibrated in wavelength or frequency, using the large number of stations available after dark to facilitate the calibration. Cover the top panel and card with a sheet of thin



A calibrated tuning scale is provided at the slot in the top panel.

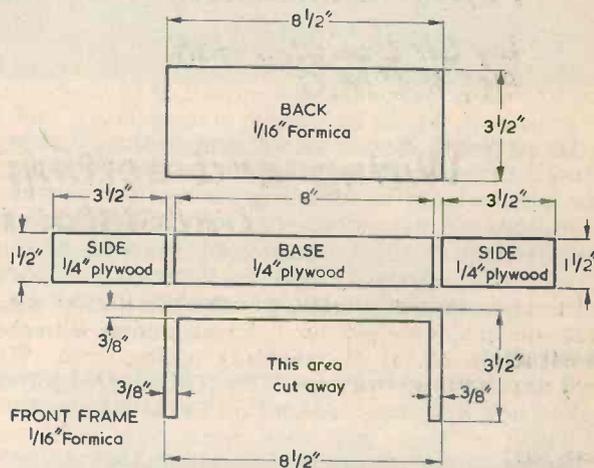
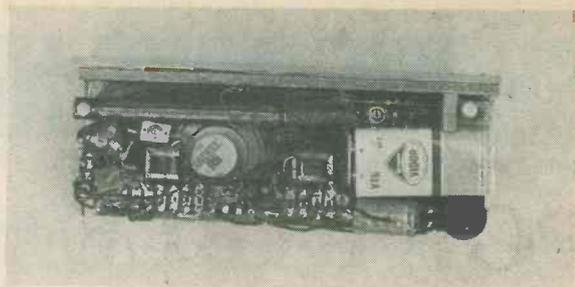


Fig.7. A suitable case for the receiver may be made up with the items shown here.

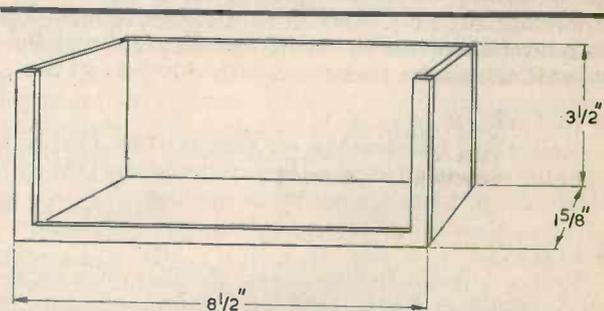


Fig.8. The pieces of Fig.7 made up to form the case, into which the receiver assembly slides. The dimensions shown here and in Fig.7 are for guidance only, and the case should be made, in practice, to take the receiver assembly as constructed.


Perspex measuring 8 in. by 1 3/8 in. Two small woodscrews are used to hold the Perspex in place.

A suitable case with suggested dimensions is illustrated in Figs. 7 and 8. The five pieces of the case are cut out and screwed together as shown, and are then covered with Fablon or Contact of a colour favoured by the constructor. The receiver assembly will then slide in from the top. Note that the dimensions given in Figs. 7 and 8 are for guidance only, and assume that the receiver assembly has been made precisely to the dimensions given last month. In practice the dimensions should be amended to take the receiver assembly as constructed, with small clearances being given where necessary.

(Concluded)

SHORT WAVE NEWS

FOR DX LISTENERS

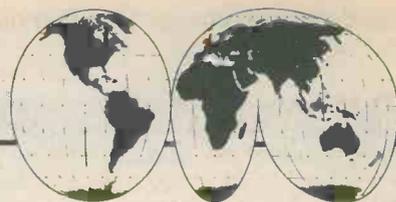

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Dxing South American stations on the 90 metre band is never an easy matter but just now and then one may be lucky by switching the receiver on when conditions are reasonable – or even good – for reception of some of these transmitters. As with all our loggings presented in this article, these are published for the guidance of readers who wish to ‘have a go’.

● BRAZIL

Radio Riberao Preto on **3205** at 0055, OM with a ballad in Portuguese, OM with station identification at 0100.

Radio Aruana, Barra do Garcas, on **3245** at 0105, OM with announcements in Portuguese, OM with ballad.

Radio Cultura, Araraquara, on **3365** at 0111, OM with songs in Portuguese – rather staid songs at that!

Radio Clube do Dourados on **3375** at 0115, OM with local announcements, light music, OM with ballad in Portuguese.

● ECUADOR

Radio Iris, Esmeraldas, on **3380** at 0120, OM with announcements of local interest followed by OM with a talk about local affairs, all in Spanish.

● BOLIVIA

Radio Alfonso Padilla Vega, Padilla, on a measured **3480.5** at 0128, OM with announcements in Spanish, military music, more announcements, more military music! Out of band perhaps, but this frequency is occasionally worth a visit.

● FINLAND

Helsinki on **21475** at 1449, OM (Old Man = Male Announcer) with station identification followed by a programme of Finnish pops and groups on records in the English transmission for Europe and North America, scheduled from 1430 to 1500 on this channel.

● TURKEY

Ankara on **15185** at 1340, local-type music, some with songs by OM in the Turkish programme for Turks living overseas, scheduled from 1300 to 1500 on this frequency.

Ankara on **17860** at 1346, YL (Young Lady = Female Announcer) with a talk about the music of various Turkish localities in an English programme which ended at 1430.

● ALBANIA

Tirana on **9500** at 1412, OM with a talk about

foreign affairs from the Albanian point of view in the English programme for South East Asia and Australia, scheduled here from 1400 to 1430.

● SWITZERLAND

Berne on **9535** at 1335, OM with a talk about Zimbabwe, the present problems and the future aspirations, in an English programme for Europe, Asia and the Far East, scheduled from 1315 to 1345 at the dial reading shown.

● EAST GERMANY

Berlin International on **9730** at 1350, YL with a talk about social achievements in the “Socialist World” during an English programme intended for Arabia and scheduled from 1315 to 1400 according to announcements. Off after identification and announcements at 1359.

● HUNGARY

Budapest on **9835** at 1415, OM with station identification and announcements at the commencement of the English programme for Dxers intended for Europe, scheduled from 1415 to 1430 on Tuesdays and Fridays only (afternoon sessions).

● NETHERLANDS

Hilversum on **9895** at 1445, OM with a programme in French intended for African and European consumption, scheduled from 1430 to 1520.

● AUSTRIA

Vienna on **12015** at 1439, OM with identification in several languages, including English, followed by light orchestral music during the German programme for Europe, scheduled here from 1330 to 1500.

● USSR

Moscow on **9450** at 1430, OM with a newscast in English in the English-linguaged World Service. This service is scheduled almost around the clock on many differing channels and is in itself an unconscious tribute to the English.

● EGYPT

Cairo on **9850** at 1435, OM with a political talk during the Arabic-linguaged Domestic Service. Also logged in parallel on **12050**.

● ITALY

Rome on **15330** at 0535, interval signal, OM with station identification and announcements at the

commencement of the Arabic programme for Arabia which ended at 0555.

● **PORTUGAL**

Lisbon on 15125 at 1840, OM with a talk about classical guitar music, Portuguese style, in the Portuguese programme to Europe, scheduled from 1800 to 2000 on this frequency.

● **BULGARIA**

Sofia on 15310 at 1850, YL with a talk about students and the higher grade educational system in Bulgaria in an announced English programme for Africa from 1830 to 1900.

● **CZECHOSLOVAKIA**

Prague on 7345 at 1856, OM with announcements in Spanish, interval signal, OM station identification followed by announcements about the various English transmissions of Radio Prague, this one being to Europe from 1900 to 1930. Another English programme for Europe on this channel is from 2000 to 2030. All this followed by YL with a newcast of both local and world events – the latter from the Czechoslovakian viewpoint.

● **NETHERLANDS – 2**

Hilversum on 17605 at 1904, OM's with a discussion about tea – both the growing and the drinking – in an announced English programme for Africa from 1830 to 1920 on this channel.

● **GREECE**

Athens on 11860 at 1920, OM with station identification followed by a newcast of both Greek and world events. All in English to Europe and scheduled from 1920 to 1930.

● **ROMANIA**

Bucharest on 11940 at 1930, OM with station identification in the "European Service", followed by a newcast in an English programme, scheduled from 1930 to 2030 at this point of the dial.

● **BULGARIA – 2**

Sofia on 11720 at 1930, interval signal then YL with station identification followed by a news reading of both Bulgarian and world events in the English programme for the U.K., scheduled from 1930 to 2000.

● **FINLAND – 2**

Helsinki on 15265 at 1934, OM with news about Finnish affairs in an English programme for Europe, scheduled from 1930 to 2000 on this frequency.

● **SOUTH AFRICA**

Meyerton on 3250 at 1940, YL with a pop song in English in the "Radio Five" programme scheduled from 0300 (Sundays 0400) to 0545 and from 1535 to 2400. The All Night Service is from 0000 to 0300 (Sundays 0400) and the power is 100kW.

Johannesburg on 21535 at 1455, OM with an English programme about South African exports to both the U.K. and Europe in the English transmission to Africa and Europe, scheduled from 1300 to 1550 on this frequency.

● **KUWAIT**

KBS Kuwait on 21545 at 0526, YL with a talk

about Islamic Law and its present administration within Kuwait. All in an English transmission.

● **MOROCCO**

VOA (Voice of America) Tangier on 15245 at 0600, OM with station identification followed by a newcast in English. Also logged in parallel on 15160.

● **SOUTH KOREA**

Seoul on 15570 at 1358, YL in Korean followed by OM with identification and an announced French programme to Africa at 1400.

● **VIETNAM**

Hanoi on 10040 at 1836, YL with songs in Vietnamese, local-style music, all in an English transmission directed to Europe and scheduled from 1800 to 1900. Also logged in parallel on 15010. According to announcements there is also a further English programme for Europe timed from 2030 to 2130.

● **NIGERIA**

Kaduna on 4770 at 0504, YL with the news in English, both local and world events, then an interview with a visiting Canadian newspaper reporter. Schedule unknown.

● **EQUATORIAL GUINEA**

Bata, Rio Muni, on 5005 at 0515, OM in vernacular, local type music with folk songs by OM's in chorus. The schedule of this one is from 0430 to 0655, 0955 to 1355 and from 1700 to 2200. The power is thought to be 100kW and this channel would seem to be an alternative to 4926.

● **COLOMBIA**

Emisora Kennedy ("La Voz de Maria"), Bogata, on 4775 at 0150, OM with local announcements in Spanish then OM and YL with more announcements alternately. This one has a schedule from 1100 to 0400 and the power is 5kW.

● **ECUADOR**

Radio Nacional Progreso, Loja, on 5060 at 0206, light music Palm Court style, OM ballad in Spanish. The schedule is from 1000 to 0415 but has been reported signing on at various times up to 1100 and signing-off as late as 0648. The power is 5kW.

● **BOLIVIA**

Radio Riberalta, Riberalta, on a measured 4697 at 0140, OM's with a discussion in Spanish about local affairs. The schedule is from 1100 to 0400 (Saturdays until 0500) and the power is 3kW.



AIRING CUPBOARD WARMER

By
Owen Bishop

**Inexpensive outlay and running costs.
Schmitt trigger thermostat switching.**

When we decided to economise by reducing the temperature and the length of time for which we ran the central heating, we soon discovered one snag. The airing cupboard became too cool to air the clothes properly. Our airing cupboard measures about 3ft. wide by 2ft. deep and 8ft. high and is heated, when the central heating is on, by three 2in. pipes that pass through the cupboard from top to bottom. These pipes are unlagged and are part of the system which circulates water to the radiators. The cupboard does not contain the hot water tank for the house.

The solution to our problem is the simple thermostat heater which is described in this article. The heater has proved completely successful and has been in constant use for many months.

Another application for the heater will appeal to those who make their own wine or beer at home. The heater can be placed in a large cupboard or wooden crate where it will keep fermenting wine or beer up to the correct temperature during winter months. The fermentation will not then become "stuck" because of low temperature; also wine will be ready at an earlier date. With the popular 2-week and 3-week wines a relatively high temperature is essential, and the thermostat heater will readily supply this.

CIRCUIT OPERATION

The circuit is shown in Fig.1. The heat is provided by two 100 watt mains lamps connected in series and which are turned on and off by the contacts of relay RLA. In keeping with the spirit of economy that led to the development of the heater, the power for the thermostat circuit is provided without the use of a transformer. Instead, the mains voltage is rectified by D1 and passed via dropping resistors R1 and R2 to the smoothing capacitor C1 and the zener diode ZD1. A relatively steady voltage of approximately 6.2 volts appears across these last two components.

The temperature inside the airing cupboard is sensed by the thermistor TH1. This is a disc thermistor type VA1038, which is available from several sources including Maplin Electronic Supplies. It has a nominal resistance of 1.5k Ω at 25deg. C, and this resistance decreases as its temperature rises.

When, due to a high temperature in the airing cupboard, TH1 exhibits a low resistance, sufficient current flows in the base of TR1 to turn this transistor hard on. The low voltage between its emitter and

collector keeps TR2 turned off and the relay is de-energised. About 6mA flows through R4 and R6, causing a voltage of about 0.06 volt to appear across R6. As the temperature falls the resistance of TH1 increases, causing the base current for TR1 to decrease, and a point is reached where this transistor begins to turn off. Its collector voltage rises and base current flows into TR2 by way of R4. The emitter current of TR2 passing through R6 causes an increased voltage drop across this resistor with the result that TR1 turns off rapidly whilst TR2 just as rapidly turns fully on and energises the relay. The relay contact arm moves over to the normally open contact and the two lamps are turned on.

The voltage across R6 has now increased to about 0.12 volt and the temperature in the cupboard must

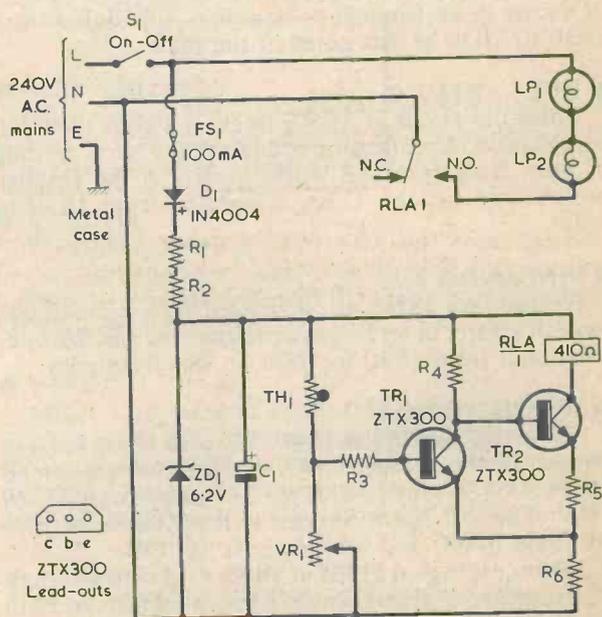


Fig.1. The circuit of the airing cupboard warmer. Thermistor TH1 is the temperature sensor, and the lamps are controlled by the contacts of relay RLA.

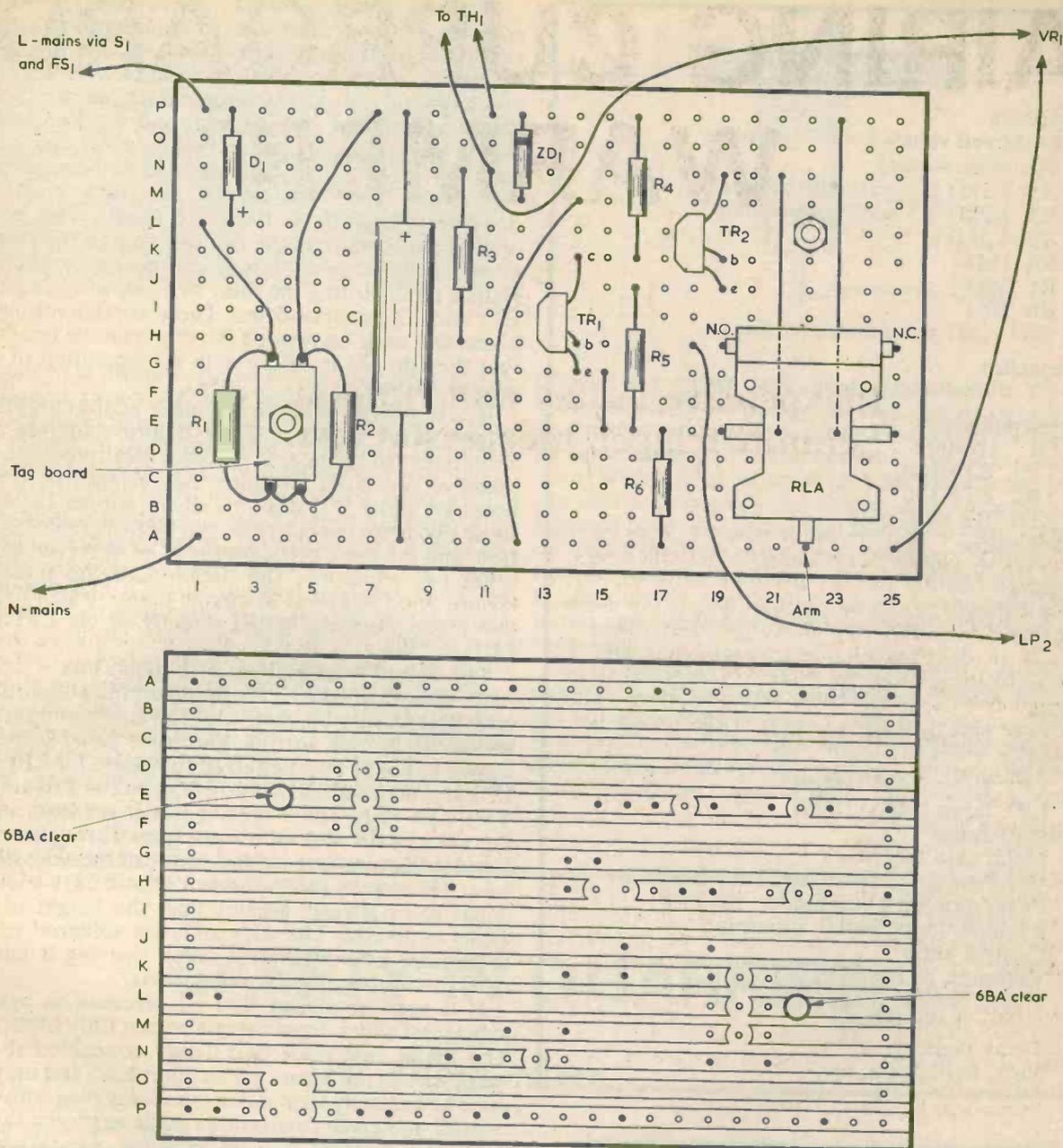


Fig.2. The relay is soldered directly to the Veroboard panel, as also are most of the other components. Veropins suitable for 0.15in. Veroboard are employed at the connection points to parts external to the board. Fig.1 should be followed for circuit details not shown here.

rise appreciably before falling resistance in TH1 causes TR1 to turn on again. The simple Schmitt trigger employed ensures that there is a "snap" action both when the relay energises and when it de-energises, and the resultant hysteresis caters for relatively small changes in temperature without incessant switching on and off around the required level. The average temperature at which the thermostat operates is controlled by adjusting VR1. Increasing the resistance inserted into circuit by this component causes triggering to occur at a lower average temperature.

CONSTRUCTION

Most of the components can be assembled on a piece of 0.15in. Veroboard with the standard size of 3.75 by 2.5in. This has 16 copper strips by 25 holes. The layout is shown in Fig.2. The board has two 6BA clear holes drilled in it and the screw passing through one of these also holds a tagboard which is spaced away from the Veroboard. R1 and R2 are connected to this tagboard. These two resistors dissipate an appreciable amount of heat and they are raised above the board to allow air to circulate around them.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

- R1 2.2k Ω 2.5 watt wire-wound
- R2 2.2k Ω 2.5 watt wire-wound
- R3 4.7k Ω
- R4 1k Ω
- R5 68 Ω
- R6 10 Ω
- VR1 1k Ω potentiometer, linear

Capacitor

- C1 470 μ F electrolytic, 10V. Wkg.

Semiconductors

- D1 1N4004
- TR1 ZTX300
- TR2 ZTX300
- ZD1 BZY88C6V2

Thermistor

- TH1 VA1038

Switch

- S1 s.p.s.t. toggle, 2A at 250 V.A.C.

Relay

- RLA "Open Relay" with 410 Ω coil and changeover contacts.

Fuse

- FS1 100mA cartridge fuse, $1\frac{1}{4}$ in.

Lamps

- LP1 lamp, 240V 100W
- LP2 lamp, 240V 100W

Miscellaneous

- Metal case (see text)
- Veroboard, 0.15in. Matrix, 2.5 x 3.75in.
- Panel-mounting fuseholder, for FS1
- 2 lampholders, batten mounting
- Control knob
- Veropins, as required
- 3-core flexible lead
- 2-core flexible lead
- 4-way tagboard
- Nuts, bolts, wire, etc.

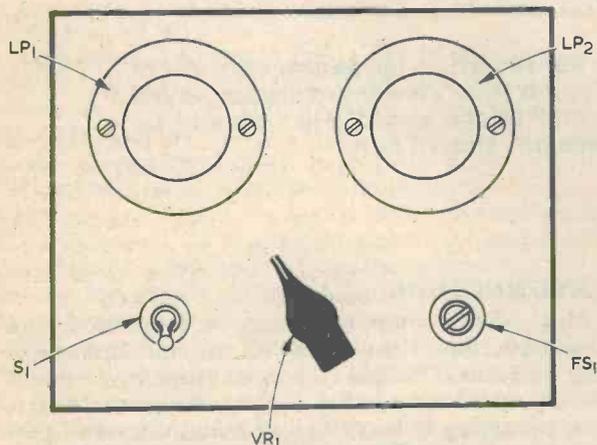


Fig.3. Apart from the thermistor and the lamps, the components are all enclosed in a metal case. The two lampholders, S1, VR1 and the fuseholder are fitted to the top panel.

The relay employed is an "Open" type with 410 Ω coil and is intended for direct mounting to a printed circuit board. If it is held over the Veroboard with its armature downwards it will be found that its tags are approximately at the Veroboard holes shown in the diagram. The tags may be bent and the Veroboard holes enlarged as required so that the relay then seats onto the board with its tags soldered to the appropriate strips. The bending of the tags must be done very carefully as these are fragile. This point applies particularly to the two coil tags, as the plastic in which they are anchored can be easily broken. Before finally fitting the relay two link wires to holes E21 and E23 must be fitted. These are thin insulated wires, and must be pressed flat down on the board so that they do not interfere with the operation of the relay armature.

It is, of course, necessary to make all the cuts in the copper strips shown in Fig.2 before soldering any component to the board. At three locations, cuts are made at two adjacent holes. An instance occurs at holes P4 and P5. If desired, all the copper between these two holes may be removed to give greater isolation, and the same procedure may be observed at the other two locations. The double cuts are made to ensure good isolation at circuit points which are at live mains potential either directly or via LP1 and LP2.

The circuit is assembled in a metal box which is large enough to take all the parts comfortably with no crowding. A suitable case would be an aluminium box measuring 8 by 6 by 3in. The front panel layout is shown in Fig.3. Two batten lampholders for LP1 and LP2 are mounted on the top of the box as also are S1, VR1 and FS1. The 3-core mains input lead and a 2-core wire to the thermistor pass through holes, fitted with grommets, drilled in one of the sides of the case. The wire to the thermistor should have a length equal to or slightly greater than the height of the airing cupboard. The wire ends are soldered to the thermistor lead-outs, after which sleeving is passed over the solder joints and lead-outs.


It is very important that all precautions against accidental shock from the mains are fully observed. The metal case *must* be reliably connected to the earth wire of the 3-core mains input lead, and the lead *must* be correctly terminated in a 3-way plug with live, neutral and earth connections made as shown in Figs 1 and 2. The earth connection at the case should be given by a solder tag secured to the case by a nut and bolt. The fuseholder should be wired in the manner shown in Fig.4, so that there is less risk of shock when the fuse is unscrewed. Apart from the thermistor there should be no access to any circuit point which is at mains potential when the lid of the box is in place, and that lid should be secured by at least two screws. All the exposed circuit points at the thermistor must be fully covered with insulating tape.

A further point to remember is that the metal framework of the relay is common with its contact arm and is, therefore, at mains potential. Resistors R1 and R2 run warm and care must be taken to ensure that plastic covered insulated wires are kept well away from these two components when the lid of the box is fitted in place.

INSTALLATION

The two 100 watt lamps in series dissipate roughly 50 watts between them, and this has been found

Fig.4. The fuseholder should be wired up in the manner shown here. This reduces the risk of shock when the fuse is removed.

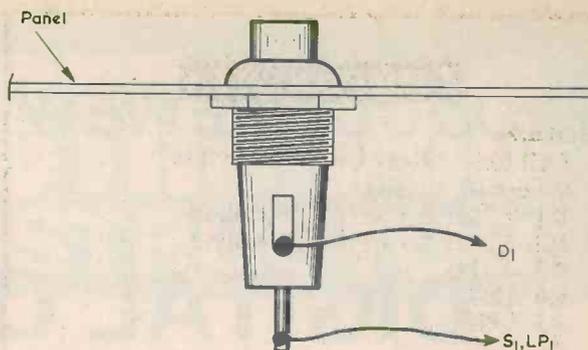

adequate for airing a cupboard of the size already mentioned. Generally, plain glass lamps are cheaper than the pearl types, so these are the type preferred. One reason for using two lamps in series is that they are under-run and their life considerably extended. Also, the heating affect is spread over a larger area.

The unit is placed at the bottom of the cupboard with the lamps uppermost. Take care that nothing can fall on it, especially clothing or other items which might interfere with the thermal feedback between lamps and thermistor and so cause local overheating. People using the cupboard must always ensure that items are stacked so that they cannot fall. The thermistor is positioned at, or near, the top of the cupboard. This, too, should be kept well away from clothing or other items which could interfere with the correct operation of the circuit.

The use of dropper resistors instead of a mains

transformer might, in some applications, be considered wasteful of power. In this circuit, which is designed to produce heat, the fact that some 3 watts of power is dissipated in the resistors is of no consequence. With a total rating of around 50 watts the unit can run continuously for 20 hours to consume 1 kilowatt-hour. Assuming that the lamps were turned on for all the time, which with VR1 correctly set up they are *not*, the monthly cost of running the heater would only be a little over £1.10. It thus makes a useful and convenient contribution to the "Save It" campaign.

As a final point it may be noted that no protective diode is connected across the relay coil. Such a diode has not been found necessary with the present circuit, with which the relay has been energised and de-energised a considerable number of times during many months of constant use. ■

SAFETY IN QUARRIES

TRADE NOTE

Marconi Avionics Limited state that orders are now being received for a specially developed rearward viewing television system intended for mounting on large capacity dump trucks of the type used in opencast sites and quarries. The company's Electro-Optical Products Division at Basildon, which supplies the system, has developed it as a private venture working in close co-operation with leading companies in the mining and construction industry.

The closed circuit television system, costing approximately £1,400, can be fitted to new vehicles or to existing fleets for greater safety. Systems have been ordered, for instance, by Orenstein and Koppel Limited

for installation on their enormous new Giant Wabco 170 ton trucks. These are the largest rear dump trucks used in Europe. The new TV system comprises a rearward pointing television camera, in a rugged weatherproof housing, mounted on the vehicle and connected to a monitor in the driver's cab.

As bigger dumper trucks are introduced into mines and quarries, in the interests of efficiency, the difficulties of rearward vision become increasingly acute. Accidents can occur in which trucks are backed over tips or into high walls, other vehicles and working personnel. The idea of using television as a safety aid originated from H.M. Inspecto-

rate of Mines and Quarries, which has thoroughly analysed the known hazards and various potential solutions.

The camera employed in the system gives a 90 degree rearward viewing angle. A single multi-core cable leaves its housing via a standard quick-release connector and terminates in the driver's cab at an interface unit coupling to the driver's monitor. The interface unit also provides power to the system from the standard 24 volt battery source and incorporates suppression filters to eliminate interference from the vehicle's electrical systems. ■

PRODUCT REVIEW . . .

DIGITAL OHMMETER

The name "Megger" has, since 1908, marked a series of resistance measuring instruments of very robust construction and high accuracy. Old hands will remember the cranked Megger, with which a handle was turned to actuate an internal generator. The MEGGER Instruments Division (of Evershed & Vignoles Limited, Archcliffe Road, Dover, Kent, CT17 9EN) now announce the introduction of the first digital electronic instrument in the Megger range, this being the D201 DUCTER Digital Ohmmeter.

The D201 is a portable battery operated test set with five measuring ranges covering 1 microhm to 20 ohms. Range selection is achieved by a single rotary control on the


front panel. Test current is up to 10 amps d.c. depending on the range in use. The instrument is especially useful for measuring earth bonding and continuity, as well as switch and circuit breaker contact resistance. It may be used for resistance measurements of fuses, lightning conductors, transformer windings, armatures, busbar joints, welded connections and rail-bonds.

The instrument employs a 4-terminal measuring system, the sample under test being connected by wing-nut terminals. The measured value is presented as a direct reading on a $3\frac{1}{2}$ digit I.e.d. display. The characters are large and easy to read, being 12mm. high, and there is automatic indication of the decimal point.

Power is given by internal rechargeable batteries. A separate battery charger unit is available, and this operates from a mains supply of 240 volts, 50 or 60Hz. Two battery test positions ensure that a check can be made at any time on the battery powering the digital electronics and also on the batteries which supply the measuring current.


The D201 is housed in a robust ABS plastic case with a carrying handle and a detachable lid, which also acts as a light shield for the digital display under bright sunlight conditions. The charger unit is supplied in a similar case and space is provided for the storage of test leads. Both items are shown in the photograph, the charger unit being on the right.

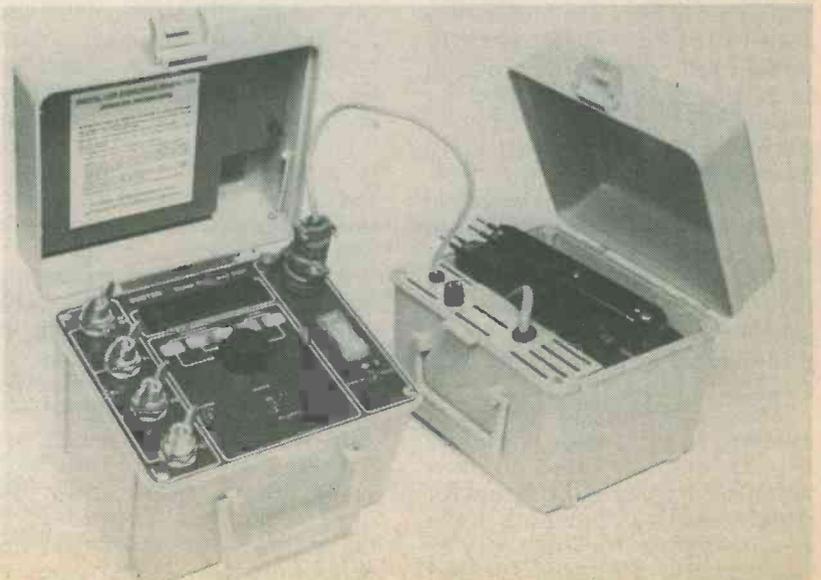Possessor of a proud name, the portable instrument on the left is the Megger digital ohmmeter type D201, with a measuring range from 1 microhm to 20 ohms. The internal batteries may be charged at any time from the special mains charger unit, which is shown on the right.



RADIO & ELECTRONICS CONSTRUCTOR

IN NEXT MONTH'S ISSUE

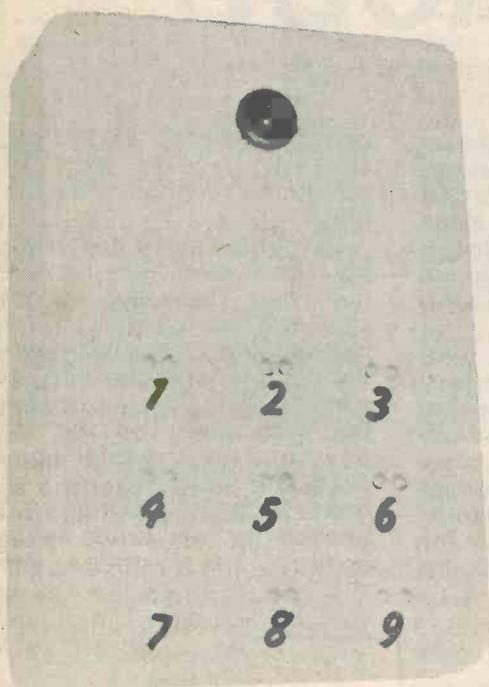

CMOS COMBINATION SWITCH

- Negligibly low standby current
- Automatic inhibit on selection of incorrect contacts
- Finger-tip operation.

LINEAR SCALE OHMMETER

Suggested Circuit

RADIO DISTRIBUTION FAULT

In Your Workshop


TREMOLO MODULATION UNIT

Easily made circuit adds brilliance to guitars, organs and electronic music. Opto coupling gives smooth modulation.

COIL-COUPLED S.W. CONVERTER

Inductive coupling to M.W. radio – no wires. 19-67 metres. Full Superhet Selectivity

PLUS MANY OTHER ARTICLES

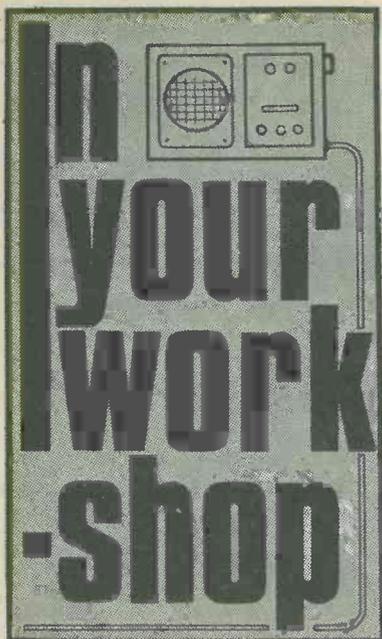

CROWBAR PROTECTION CIRCUIT

"Output power: 30 watts per channel into 8Ω, 40 watts per channel into 4Ω."

Impressed, Dick raised his eyes from the specification in the service manual. He glanced again at the manual's title, which described the equipment on his bench. "Hi-Fi Stereo Tuner Amplifier and Turntable Unit." The equipment certainly gave every indication of offering what, for domestic purposes, was a more than adequate power output. On its top was the gram turntable and on the front panel were an output meter, a tuning meter, comprehensive bass and treble tone controls, volume and balance controls, a set of function switches, a pilot light and a row of touch tuning contacts. Whoever had brought the unit in for servicing had been thoughtful enough to include the two speakers in their cabinets. And those cabinets were good and large.

Dick set up the speakers on the floor on either side of his bench, ensured that they were plugged into the correct DIN sockets on the rear panel of the unit and connected its mains lead to one of the sockets at the back of his bench. He switched on.

BLOWN FUSE

Nothing happened.

There was no sound from the

speakers and the pilot light on the front panel remained extinguished. To all intents and purposes the unit was completely dead. Dick turned to the circuit diagram in the service manual and examined the power supply section. The mains transformer had two secondary windings, one providing high current positive and negative supply rails at 29 volts each for the power amplifiers in both channels, whilst the other provided a lower current single positive supply for the tuner circuits, the audio

pre-amplifiers, the touch tuning circuits and the remaining sections of the unit. (Fig.1.)

Dick gazed at the power supply circuit and then his eyes narrowed. There was a 1 amp cartridge fuse in series with the mains input to the primary of the mains transformer. He switched off the unit, located the fuse-holder on the rear panel and unscrewed the fuse. Next, he switched his test-meter to an ohms range and applied its test prods to the ends of the cartridge fuse.

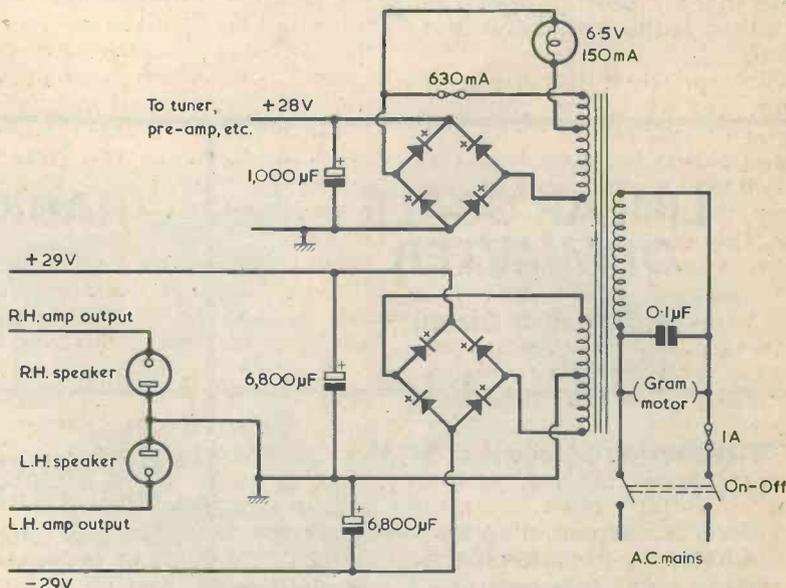


Fig.1. Power supply circuit in the hi-fi unit serviced by Dick. The two 29 volt rails supply the right and left hand power output amplifiers. The pilot lamp connects to a 6 volt tap in the upper mains transformer secondary.

There was no continuity: the fuse had blown. Dick studied the service manual once again.

"Hey, Smithy!"

"Hullo."

"I've got a hi-fi unit here with a blown mains input fuse."

"So?"

"Well, the service manual says you're supposed to replace the fuse only with one which has been approved by the manufacturer of the unit."

"Oh."

Smithy put down his soldering iron and walked over to Dick's bench. Bending over, he looked at the hi-fi unit and then at the service manual circuit.

"We're in luck here," he announced. "I've got a few 1 amp fuses of the recommended type in the spares cupboard. Hang on a jiffy and I'll see if I can find them for you."

After a little searching, Smithy produced a small cardboard box and returned with it to Dick's side.

"You'd better be careful with these fuses," he warned. "I've only got three left. If you blow these you'll have to wait until I can get some more ordered in."

"Well, shall I fit one of them right now and see what happens when I switch the unit on?"

"All right," conceded Smithy. "But if it goes, you'll have to start looking for shorts or other faults inside the unit itself."

Dick quickly fitted the new fuse into its spring cap and screwed the latter into the fuse-holder. He switched on. There was a noticeable thump from the right hand speaker and the pilot lamp came on. Then, after a brief moment, it extinguished again and the unit became dead once more. Dick switched off, unscrewed the fuse and checked it with his testmeter. The new fuse had blown.

"There's another fuse in this power supply circuit," stated Smithy as he looked down at the service manual diagram. "It's a 630mA job and it's in the supply circuit for the pre-amplifier and tuner part of the unit. Check that fuse."

Obediently, Dick located the 630mA fuse and unscrewed it. As he applied the testmeter prods to its ends the meter

needle swung over to indicate zero ohms.

"That one's all right."

"Fair enough," said Smithy.

"Well, at the expense of one fuse we've already learned enough to make a few inspired guesses as to what's wrong here."

"Already?"

"Of course," retorted Smithy. "For a start that pilot lamp came on. This makes it probable, although not entirely certain I'll admit, that there are no shorts in the mains transformer or the circuits immediately connecting to the mains transformer. If there had been it's doubtful whether the lamp would have lit up, and the fuse would have almost certainly blown as soon as the on-off switch contacts closed. Secondly, the 630mA fuse you've just checked is okay. So that rules out possible shorts in the sections of the unit which that fuse supplies."

"Well, I'll agree with what you've said up to now."

"Good. Let's next look at the supply circuit for the power amplifier section of the unit. The mains transformer secondary is centre-tapped, with the centre-tap connecting to chassis. The result is that it gives two supply rails, one being positive of chassis and the other negative of chassis. The important thing here is that there are no fuses in the rectifier circuit or in either of these supply rails, which means that the unit has almost certainly been designed so that if there are any faults in the power amplifiers it will be the 1 amp mains input fuse which blows. Okay?"

"In other words," said Dick slowly, "We can fully expect the fault to be in the power amplifier section of the unit."

"Everything points that way," replied Smithy cheerfully. "I should start looking for obvious shorts or other faults in the right hand channel power amplifier."

"Come on, Smithy! You can't locate the fault as closely as that with just one fuse blowing!"

"That right hand channel idea is only a suggestion," stated Smithy mildly. "I'm almost certain I heard a thump in the right hand channel

Z TECHNICAL BOOKS

by popular authors and publishers
ELECTRONICS - AUDIO - CB RADIO -
AMATEUR RADIO - COMPUTERS -
PROJECTS.

British and American publications.

Send 12p stamp (not sae) with your name and address for lists and prices.

In stock books despatched same day as order received.

Z. L. COMMUNICATIONS

35, Burnt House Road, Cantley,
Nr. Norwich Norfolk, NR13 3RT.
Tel: Freethorpe 821.

THE MODERN BOOK CO.

*Largest selection of English &
American radio and technical
books in the country.*

19-21 PRAED STREET

LONDON W2 1NP

Tel: 01-402 9176

ELECTRONIC TUTOR KITS

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

RXG ELECTRONICS LTD.

15 Walnut Tree Crescent,

Sawbridgeworth, Herts, CM21 9EB.

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

*For the convenience of Irish
enthusiasts we supply:*

Radio & Electronics
Constructor Data Books
Panel Signs Transfers

Also a postal service

peats

the world of electronics

25 Parnell Street, Dublin 1. Tel 749972

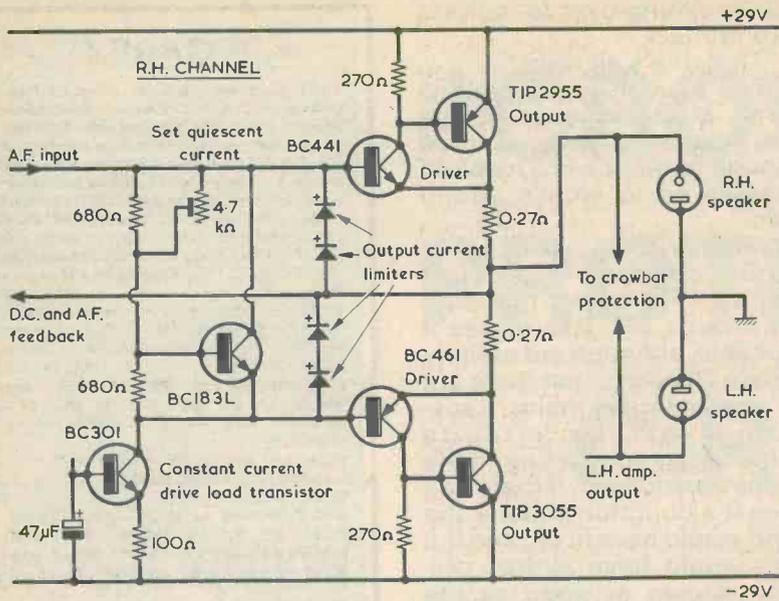


Fig.2. The driver and output transistors of the right hand channel amplifier appear in the circuit shown here, with connection to the right hand speaker being made via a DIN socket. The left hand amplifier stages are identical.

speaker when you switched on the unit just now. If they were working properly, both the left hand and right hand power amplifiers should be giving an output voltage which is midway between the supply rails or, in other words, is at about the same potential as chassis. The two speakers connect between the amplifier outputs and chassis, and it was only the right hand speaker which gave the thump. Start looking for trouble in the right hand section, or for any other thing which could cause the right hand output to be at an incorrect voltage. It could be something quite simple like a short in the output or driver transistors."

CIRCUIT TESTING

With these words, Smithy left his assistant and proceeded to his own bench.

Dick removed the mains plug of the hi-fi unit and turned his attention to the circuit of the power amplifier section as shown in the service manual. It was certainly far more complex than the simple a.f. amplifiers he was used to, but the two output transistors and their driver transistors could be

easily identified. His eyes faltered momentarily as he noticed a part of the circuit following the amplifier which was designated "Crowbar Protection". (Fig.2.)

Dick frowned. Crowbar protection? What in heck was crowbar protection? He shrugged his shoulders. He had enough mysteries to contend with as it was without adding crowbar protection to the list. A lunatic image arose in his mind of a circuit which blew out warning puffs of smoke if anyone tried to break into the hi-fi unit with a crowbar, and he dismissed it irritably. Like electronics is getting too involved, man.

He started to dismantle the unit and was soon able to reach the power amplifier board with his test prods. His meter was still switched to the ohms range and he happily started to check through the power amplifier section for obvious short-circuits. Now, this was something he could do any time of the day...

"Hey, Smithy!"

"What is it now?"

"You were right. There was a short in the right hand power amplifier section."

"Was there?"

Smithy sounded pleased.

"It was in the BC441 driver transistor. There's a 100% dead short between its base and collector." (Fig.3.)

Smithy walked over once more to look at the circuit diagram of the hi-fi unit.

"It's nice," he remarked in a gratified tone, "to know that one of my guesses has turned out right. That short in the driver transistor would certainly cause the output voltage to be well away from its proper potential, which should be midway between the supply rails."

"It will also," remarked Dick, "explain the thump in the right hand speaker when I switched on. But I don't see how the short in the transistor could have caused the 1 amp input fuse to blow."

"That bit's obvious," replied Smithy. "The unbalance at the right hand amplifier output would have triggered off the crowbar protection circuit."

Dick sighed.

"I've been trying to keep that crowbar protection business out of my mind ever since I started looking at the circuit of this power amplifier. What on earth is a crowbar protection circuit?"

"It's a circuit which puts a dead short-circuit across the supply rails when there's a fault condition," explained Smithy. "It acts as though you put an imaginary crowbar across the rails. When the crowbar circuit is triggered the consequent short across the

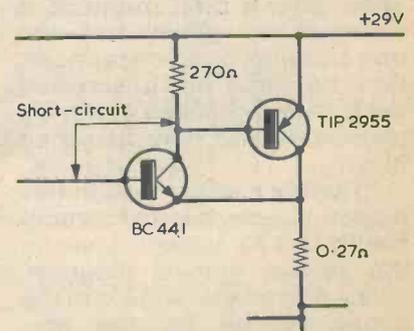


Fig.3. Simple ohmmeter checks led Dick to a base-collector short-circuit in the BC441 driver transistor.

rails causes the mains input fuse to blow."

"But why have a crowbar protection circuit in the first place?"

"Because," said Smithy, "there are a number of faults in the power amplifier circuit which could cause damage to components but which do not result in the supply current consumption rising to a fuse-blowing level. The crowbar protection section detects these faults and then proceeds to blow the fuse for you!"

CROWBAR OPERATION

Dick sat back on his stool.

"This," he said, "you'll have to explain to me."

Smithy glanced at his watch. "All right," he said equably, "the crowbar protection in this hi-fi unit is very simple and it won't take long to show you how it works. If you look at the circuit in the service manual you'll see that it has four transistors and a silicon controlled rectifier, or thyristor."

Smithy pointed to the circuit in the manual. (Fig.4.)

"Now there's a 22 μ F electrolytic," he resumed, "which acts as an input reservoir capacitor. The output of the right hand channel amplifier couples to it via an 820k Ω resistor, and the output of the left

hand amplifier couples to it via another 820k Ω resistor. Under quiescent conditions, the outputs of both amplifiers should be at, or very close to, chassis potential so that either zero voltage or a very low voltage appears across the capacitor."

"What about when the two amplifiers are handling a signal?"

"In that case the average voltage from each amplifier output should still be zero. Now in our case we had a fault which caused the right hand output to be other than zero with respect to chassis under quiescent conditions. But there are other faults which could make themselves shown when the left and right hand amplifiers are handling a signal, and these could cause an amplifier to give more amplification to positive half-cycles than to negative half-cycles, or more amplification to negative half-cycles than to positive half-cycles. The first of these effects would cause the non-earthly plate of the 22 μ F capacitor to go slowly positive, and the second would cause it to go slowly negative."

"But," protested Dick, "that 22 μ F capacitor is an *electrolytic*! It's non-earthly plate *can't* go negative!"

"Yes it can," replied Smithy. "For the moment forget about

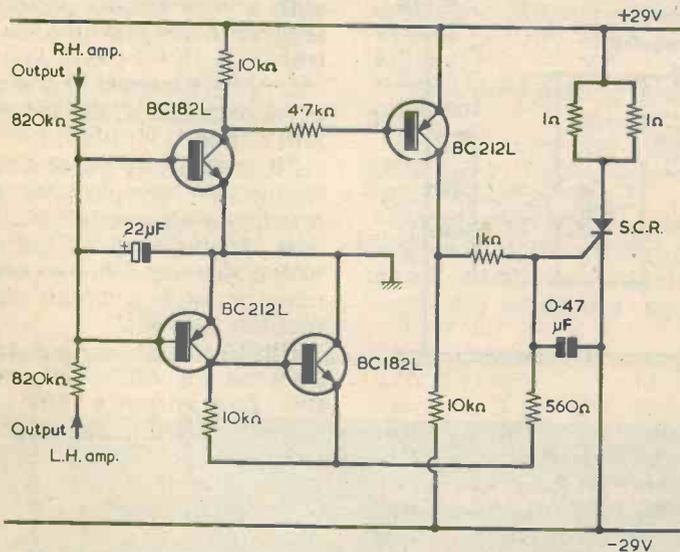


Fig.4. The crowbar protection circuit. The two 1 Ω resistors in parallel limit the short-circuit current which flows when the silicon controlled rectifier, or thyristor, is fired. This circuit, and those of Figs.1 and 2, are slightly simplified versions of the corresponding circuits in the Ferguson 3987 Hi-Fi Unit.

GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 inc. VAT. Crystals, if required: £2.60 each. All popular 2m. channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8 Ω) input and output for extn. speaker amplification, with circuit £2.75.

Neons min wire end 70p/10: £4.50/100

Slide switches min DPDT 20p ea; 5 plus: 16p

Resistor Kits E12 series, 22 Ω to 1M Ω 57 values, 5% carbon film, 1/4W or 1/2W Starter pack, 5 each, value (285) £3.10

Mixed pack, 5 each 1/4W plus 1/2W (570) £5.55

Standard pack, 10 each (570) £5.55

Giant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50 Ω 25p; 5 plus: 20p;

PL259 UHF Plug and Reducer 75p; 5 plus: 67p;

SO239 UHF Socket panel mtd. 60p; 5 plus: 50p;

Nicad rechargeables physically equiv. to zinc-carbon types: AAA (016) £1.80; AA(U7) £1.30; C(U11) £3.35; PP3 £5.55. Any 5 plus: less 10%. Any 10 plus less 20%.

We stock V.H.F. & U.H.F. mobile aerials s.a.e. details.

Access - Barclaycard


PRICES INCLUDE UK POST, PACKING & VAT

Mail order only

Sole Address

GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH.
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 668684

MORSE MADE EASY

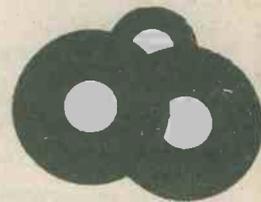

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.
Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750gram). Details only s.a.e.

THE G3HSC MORSE CENTRE
S. Bennett, (Box 8), 45 Green Lane,
Purley, Surrey.

Name

Address

it being an electrolytic and assume that it's a non-electrolytic component. Let's next see what happens when the non-earthly plate goes positive. As soon as the voltage across the capacitor reaches about 0.6 volt the upper pair of transistors will be turned on. Base current will flow into the BC182L and its amplified collector current will flow in the base of the BC212L. The BC212L collector current then flows into the gate of the thyristor via a 1kΩ resistor whereupon this thyristor turns on, short circuits the power rails and – wham – there goes the main fuse!" (Fig.5(a).)

"Gosh," spluttered Dick, "this really is something new to me. Let's see if I can trace out what happens when the non-earthly plate of that 22μF capacitor goes negative."

"Go on," said Smithy encouragingly.

"Well," stated Dick, "the voltage on that plate will go more and more negative until it reaches around 0.6 volt. This time it is the two lower transistors which will turn on. There'll be base current in the BC212L

and its collector current will then be the base current for the BC182L. The BC182L acts as an emitter follower and its emitter current flows into the gate of the thyristor." (Fig.5(b).)

"Whereupon the thyristor is fired and – wham again – the main fuse blows!"

REVERSE POLARITY

Dick looked pleased with himself.

"This crowbar protection business isn't so difficult after all. Does it turn up in other circuits?"

"Oh yes," confirmed Smithy. "You may find it for instance in some colour TV supply circuits. The transistors and other components coupled to the gate of a thyristor detect fault conditions which, of themselves, would not cause sufficient current to flow to blow an input fuse. When the fault appears the protection circuit triggers on the crowbar thyristor and it is that which blows the fuse."

"There's one thing you haven't explained."

"What's that?"

"How, in the circuit we've got here, the 22μF electrolytic

acts as a reservoir capacitor even when its positive plate goes negative."

"Well, to understand that you have to remember how an aluminium electrolytic is made up. One plate is an aluminium sheet, usually etched to increase its surface area, and the other plate is the electrolyte itself which is in intimate contact with all the surface of the aluminium sheet. The dielectric between the sheet and the electrolyte is a film of oxide on the surface of the aluminium sheet. This film is very thin, which explains why electrolytic capacitors have such high values."

"And that film," stated Dick with conviction, "breaks down if you apply a reverse voltage to the electrolytic."

"It doesn't break down," Smithy corrected him, "if the reverse voltage is very low. In the circuit we've been looking at, the reverse voltage is limited to about 0.6 volt by the base-emitter junction of the BC212L."

"This," wailed Dick, "goes against everything I've been taught! Never, but never, I've been told, apply a reverse voltage to an electrolytic capacitor!"

"In general you shouldn't," stated Smithy, "and especially if it's a tantalum electrolytic. However, you can get away with a very small reverse voltage with an aluminium electrolytic."

Smithy glanced at the stubborn expression on his assistant's face.

"It looks," he went on, "as though I'll have to give you a practical demonstration. See if you can hunt up a 22μF electrolytic for me. Oh, and a 4.7kΩ resistor and a small silicon rectifier as well."

Smithy walked over to his own bench whilst Dick found the components and then returned with a few crocodile clip leads and a PP9 battery.

"Here we are, Smithy," said Dick, handing the components over to him.

"Right. Well, I'll start off by wiring up the resistor and rectifier to give us a voltage across the rectifier of 0.6 volt."

Smithy soon connected the two components together and to the battery. (Fig.6(a).)

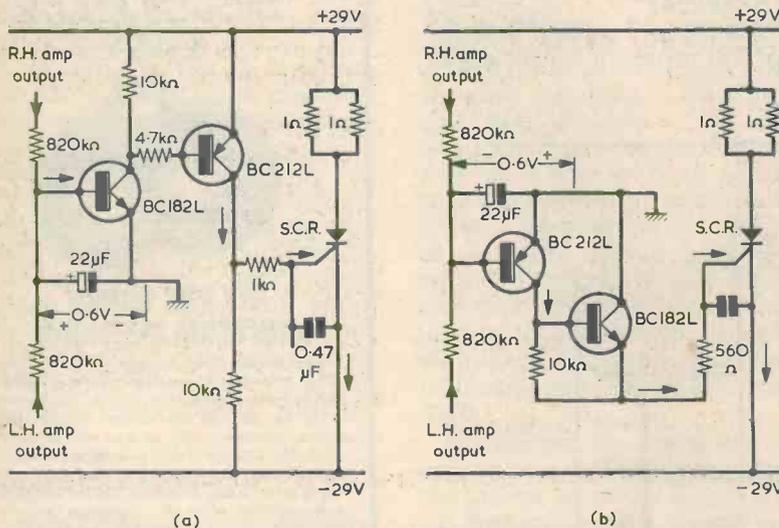


Fig.5(a). If the non-earthly terminal of the 22μF reservoir capacitor is taken about 0.6 volt positive of chassis the upper two transistors turn on and trigger the thyristor. The arrows show current flow (assumed to be from positive to negative).

(b). Taking the non-earthly terminal of the reservoir capacitor about 0.6 volt negative of chassis turns on the lower two transistors. The crowbar protection circuit monitors the outputs of both the right and the left hand amplifiers.

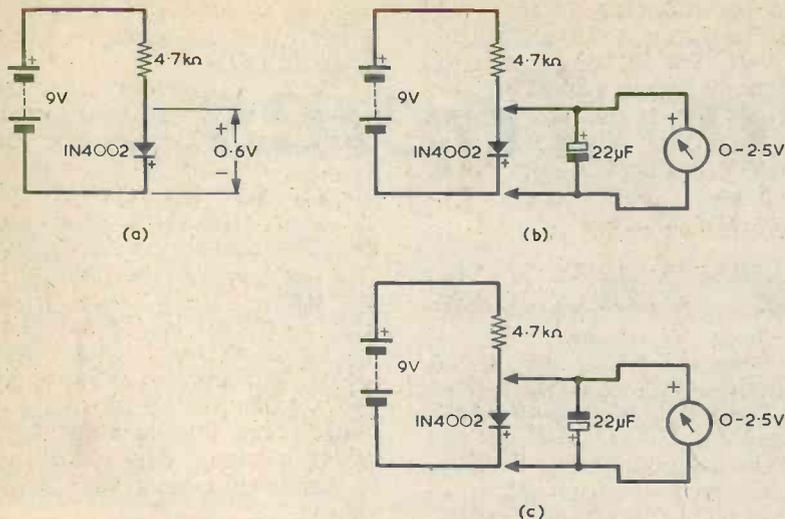


Fig.6(a). A simple circuit which offers about 0.6 volt across the silicon rectifier.
(b). Smithy connected a high resistance voltmeter across a 22 μ F electrolytic capacitor and temporarily applied its leads across the silicon rectifier.
(c). Smithy then repeated the process with the electrolytic capacitor connected the other way round.

"I next," he said, "want a fairly sensitive voltmeter. An electronic voltmeter would be ideal but a sensitive analogue moving-coil voltmeter will prove my point just as well. Your testmeter has got a resistance of 20,000 ohms per volt and it also has a low d.c. volts range of 2.5 volts, which I'll now select. This means that the resistance between the test leads is 50,000 ohms. I'll clip the leads to the capacitor right way round and I'll then touch the capacitor leads with correct polarity across the silicon rectifier." (Fig.6(b).)

"The meter," said Dick, "is reading 0.6 volt, which of course is what you'd expect."

"Good. I'll now take the capacitor away from the rectifier."

"The voltage reading falls fairly slowly," announced Dick, gazing at the meter, "Until it falls to zero."

"That's fair enough. The time constant of 50,000 ohms and 22 μ F is about 1 second, and so the fall in voltmeter reading will be slow enough to be observable. I'll now reverse the testmeter connections to the capacitor and also apply it across the silicon rectifier with reverse polarity. Here we go!" (Fig.6(c).)

"We are getting 0.6 volt again."

Smithy took the capacitor leads away from the rectifier. "And now?"

"Why, stap me," exclaimed Dick incredulously, "the voltage is falling slowly again, just like it did when the capacitor

was connected with correct polarity!"

"There you are then," said Smithy triumphantly. "Are you now convinced that an aluminium electrolytic will hold a reverse charge provided that the reverse voltage is kept small?"

"Gosh, yes. But I wouldn't have believed it if I hadn't seen it with my own eyes!"

NEW TRANSISTOR

A replacement transistor for the faulty BC441 was not available, even from Smithy's capacious spares cupboard, and so it *had* to be ordered. Smithy took advantage of the situation to include an order for several dozen 1 amp fuses as well, so that he was well stocked up for the future. Cartridge fuses are neat and unobtrusive little components but, during their lifetime, they are only allowed one self-destructive bite at the cherry.

As always with Dick and Smithy, the story has a happy ending. The replacement transistor, when it arrived, completely cured the fault in the hi-fi unit, and this was able to push out all its 40 watts per channel into 4 Ω loads without the crowbar thyristor even giving a hint that it intended to bring proceedings to a sudden and cataclysmic conclusion.

EDITOR'S NOTE

Smithy slipped up slightly in his description of the 6MHz sound trap shown in Fig.2 of "In your Workshop" in the April 1980 issue. The trap is a bridged-T filter offering a higher degree of rejection than does an acceptor tuned circuit. We are trying to keep this news away from Dick.

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 73p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

Radio Topics



By Recorder

Some imaginative words are coined in the discipline of electronics and they continue to appear in a truly rich profusion. In the older days, inventors of new electronic devices used to append quite stylish names to their creations, whereupon there were indignant letters to *Wireless World* if these terms happened to derive from a mixture of Latin and Greek. Nowadays, nobody bothers one little bit about the etymology of technical terms, which can so far as anyone cares stem from Latin, Greek, Chaucerian English or Outer Mongolese. Forcefulness in meaning is the essence of technical word production.

PINOUT

Take the 6-letter word "pin-out".

To the uninitiated this could be a miniature version of "stake out", conjuring up a scene in which diminutive mineral prospectors mark out their own tiny areas of terrain. But in practice "pinout" merely refers to the manner in which the pins, or "leads", of an integrated circuit appear about its body. It can also apply to the lead-out layout of a transistor, a voltage regulator, a multiple varicap diode unit, or even a multi-pin relay unit intended for p.c.b. mounting. Come to think of it, the word could refer to the pin connections of those marvellously long-running Denco miniature Dual Purpose coils which plug into B9A valveholders. The first Denco Dual

Purpose coils to hit the amateur market, incidentally, were designed to plug into much larger 8-pin octal valveholders, and nobody dreamed of employing such a term as "pinout" in those days.

Some conventions have arisen with pinout presentations in drawings and diagrams. So far as *Radio & Electronics Constructor* is concerned we always, with a few exceptions, present transistor pinouts, or lead-out layouts, with the pins pointing towards the reader. The exceptions occur with the occasional device which has to be drawn with its lead-outs pointing sideways, in the plane of the paper on which they are printed.

INTEGRATED CIRCUITS

Integrated circuits, on the other hand, are always presented as a top view, with the pins pointing away from the reader. You then locate pin No. 1, which usually has a dot alongside it on the i.c. housing when this is rectangular, and count the pins in order working in an anti-clockwise direction. With a round i.c. case having a locating lug, the lug normally indicates the pin having the highest number, so that pin No. 1 is the next one to the lug, working in the anti-clockwise direction.

Why should transistor and i.c. lead layouts be presented in completely opposite ways? The only answer to that is that it is one of those things which

just happen. When transistors first came on the scene the manufacturers showed them in their literature with pins pointing towards the reader. And when i.c.'s settled down to their current dual-in-line housings, manufacturers' literature showed them with their pins pointing in the other direction.

It must be fun being in at the birth of an electronic device.

"Hey boss, this new device they've dreamed up in the labs is really something."

"What is it, Joe?"

"Well, nobody's quite sure, but the lab boys reckon it simulates human thought."

"Great news, Joe! How do you connect to it?"

"That's one problem to be cleared up. It uses three dimensional instead of lateral logic, and the best we can do is have its connection pins laid out in two counter-directional helices. But we don't know how to identify them."

"That's easy, Joe. Identify the pins in one helix with numbers starting from 1, and the pins in the other helix with letters starting from A."

"Hey boss, you've just created an industrial standard!"

And so is electronic history made.

MICROPROCESSOR-BASED OSCILLOSCOPE

As can be seen in the accompanying photograph, the new Tektronix Model 7854 oscillo-

scope presents a truly futuristic appearance. And so it should, since it combines the analogue features of a conventional oscilloscope with a micro-processor, the latter providing extensive digital storage and signal processing facilities. The fully programmable Model 7854 allows most waveform measurements to be carried out at the touch of a button, offers improved measurement quality in the presence of noise, and can be combined with a Tektronix desk-top graphics computer to form a complete signal processing system capable of carrying out a wide variety of operations on the basic waveform data.

The conventional analogue features of the oscilloscope include a bandwidth of d.c. to 400MHz at 10mV per division, calibrated sweep rates of up to 500 picasecond per division, and the ability to be used with more than thirty compatible plug-in units in the Tektronix 7000 Series.

The waveform is displayed as on a conventional oscilloscope, but it can also be digitised, stored and recalled for comparison. Digital storage of repetitive waveforms can take place at up to 400MHz, and single-shot events can be stored at sweep speeds of up to 50 microseconds per division. A plug-in unit enables pre-trigger information from zero to 100% of sweep to be dis-

played, and an optional memory allows up to 40 separate waveforms to be digitised and stored.

The oscilloscope is pre-programmed so that most of the normal waveform measurements (rise time, fall time, pulse width, etc.) and more complex waveform comparisons can be carried out by touching a button on the instrument's calculator-type keyboard, giving faster, more accurate and repeatable measurements. In addition, the Model 7854 can be programmed by the user to calculate specific answers. Key-stroke programs of up to 1,000 lines can be written for repetitive testing requirements, and the instrument can be set to monitor signals in the operator's absence or to automate and organise a long series of measurements.

SIGNAL AVERAGING

The digital storage system allows signal averaging to be carried out, so that signals buried in noise can be recovered and measurement quality can be improved. The maximum vertical and horizontal resolution of the stored data is 0.01 of a division, and the operator has a choice of 128, 256, 512 or 1,024 horizontal points per waveform. Using the storage system, the operator can make


the same measurement on a one-division signal which normally takes six divisions on a conventional oscilloscope.

The Model 7854 has a GPIB (General Purpose Interface Bus) interface for users requiring additional processing, data storage or co-ordination of the oscilloscope with other instruments. Waveform data or measurement results, as well as external programming instructions, can be sent over the interface.

Tektronix also supply a signal processing system, designated WP1310, which is a combination of the Model 7854 oscilloscope and a Model 4052 graphics computing system. The computer provides flexible data communications, an easy-to-learn extended BASIC software language and high resolution graphics capabilities.

The WP1310 includes special signal processing memory packs which tailor the system for waveform processing. Among the features included are extended graphic capability, program storage and control, data storage, a hard-copy option for documentation, and the ability to interface with other computers. Further details on this oscilloscope breakthrough can be obtained from Tektronix U.K. Ltd., Beaverton House, P.O. Box 69, Harpenden, Herts.

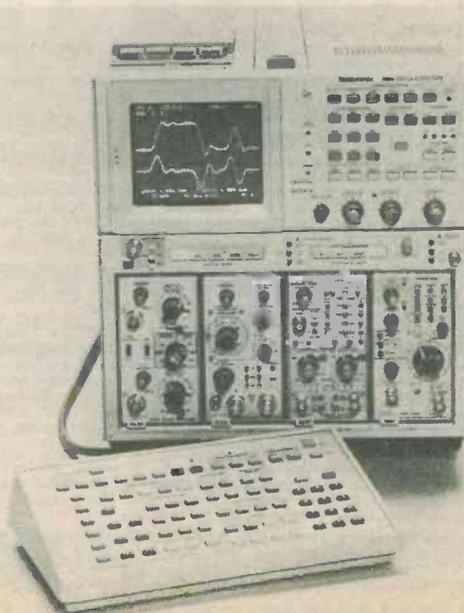The Tektronix Model 7854 oscilloscope system. This combines the features of a high resolution oscilloscope with the special storage facilities and operations provided by a microprocessor.



UNDERSTANDING MICROPROCESSORS Texas Ins. £4.25

For the newcomer to Microprocessors. An in-depth look at the magic of the solid-state chips that are affecting our lives. Written in everyday language. Ideal for self-paced individualised learning.

ELECTRONIC FAULT DIAGNOSIS By I. R. Sinclair Price £3.50	AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR by I. R. Sinclair Price £3.50	UNDERSTANDING ELECTRONIC CIRCUITS by I. R. Sinclair Price £4.50
ELECTRONIC PROJECTS IN AUDIO by R. A. Penfold Price £2.50	REPAIRING POCKET TRANSISTOR RADIOS by I. R. Sinclair Price £2.55	UNDERSTANDING ELECTRONIC COMPONENTS by I. R. Sinclair Price £4.50
OP-AMPS THEIR PRINCIPLES & APPL. by J. B. Dance Price £2.50	MAKING & REPAIRING TRANSISTOR RADIOS by W. Oliver Price £2.30	UNDERSTANDING SOLID-STATE ELECTRONICS by Texas Inst. Price £3.95
PRINTED CIRCUIT ASSEMBLY by M. J. Hughes Price £2.10	WORLD RADIO TV HANDBOOK by J. M. Frost Price £9.25	A SIMPLE GUIDE TO HOME COMPUTERS by S. Ditlea Price £4.00
ELECTRONIC SECURITY DEVICES by R. A. Penfold Price £1.65	PROJECTS IN RADIO & ELECTRONICS by I. R. Sinclair Price £2.50	HOW TO BUILD A COMPUTER-CONTROLLED ROBOT by T. Loofbourrow Price £5.30
UNDERSTANDING DIGITAL ELECTRONICS by Texas Inst. Price £4.00	ELECTRONIC PROJECTS IN THE HOME by O. Bishop Price £2.50	THE CATHODE-RAY OSCILLOSCOPE & ITS USE by G. N. Patchett Price £4.00
UNDERSTANDING MICRO-PROCESSORS by Motorola Price £4.30	SIMPLE CIRCUIT BUILDING by P. C. Graham Price £2.20	A GUIDE TO AMATEUR RADIO by P. Hawker Price £1.70
THE FIRST BK OF MICROCOMPUTERS by R. Moody Price £3.35	110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price £3.20	MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE by R. H. Warring Price £2.90
HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE by F. G. Rayer Price £1.70	HAM RADIO by K. Uilyett Price £5.00	
THE OSCILLOSCOPE IN USE by I. R. Sinclair Price £3.50		

We have the Finest Selection of English and American Radio Books in the Country

PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176

SWITCHVANCE LTD.

49 Wadeson Street, London E2 9DP.
Tel: 01-980 1028/1029

All items brand new and fully guaranteed. Prices Inclusive of VAT. Minimum order value £5. Terms: Cash/Cheque/P.O. with order. Please add 40p P&P to all orders except where otherwise marked.

ELECTROLYTIC CAPACITORS - Wire ended.

Mfd/Volt	4p	10/350	10p	47/50	7p	470/16	9p
4.7/50	5p	15/40	6p	68/40	7p	470/25	12p
6.8/63	5p	22/16	5p	100/16	7p	1000/10	12p
10/16	5p	22/63	6p	100/25	7p	1000/16	16p
10/25	5p	47/16	5p	100/50	9p	1000/40	20p
10/50	6p	47/25	6p	220/25	8p	2200/40	40p
						4700/25	52p
						6800/16	30p

CANS: 1500/63 — 35p. 3300/40 — 52p. 4700/40 — 60p. 6800/40 — 80p.

POLYESTER CAPACITORS - Radial leads.

63V: .15, .22, .33, .47, .68 8p. 1.0 12p. 1.5 18p. 250V: .01, .022, .033, .047, .068 5p. .1, .22, .47 7p. 1.0 18p. 1.5 23p.

POTENTIOMETERS. Rotary. Carbon track. 0.25W log. 0.5W 1in.

Spindle 1/4 x 1/4 in.
Single gang: 1K log, 5K log, 250K log, 1M log, 25p. Single gang D/P switch: 2K5 1in, 5K 1in, 5K log, 10K log, 25K log, 50K 1in, 50K log, 100K 1in, 100K log, 250K 1in, 500K 1in, 500K log, 46p. Dual gang: 1K 1in, 5K 1in, 5K log, 10K 1in, 10K log, 25K 1in, 25K log, 50K log, 100K 1in, 100K log, 250K 1in, 250K log, 500K 1in, 1M log, 60p.

Wirewound 1W (1in). Spindle size 1 x 2in. 10R, 30R, 220R, 500R, 1K, 3K3, 5K. 50p. Wirewound 3W (1in). Spindle 1 x 1 or 1 1/2in. 10K, 50K. 95p. Presets. 0.1W and 0.15W Vertical or horizontal mtg. 100R — 1M. 6p.

SWITCHES: Rotary. 1 pole 12 way, 3 pole 4 way, 4 pole 3 way. 45p. Mains Rockerswitch with built-in neon. DPST. 10A contacts. 80p. 3 gang DP latching pushswitch with knobs. 40p. DIL switches: standard DIL package incorporating 1 — 10 single pole switches. 1 way 35p. 3 way 46p. 5 way 65p. 6 way 70p. 7 way 70p. 8 way 82p. 9 way 82p. 10 way 95p. Also 1 way DP 35p. 2 way DP 46p. 5 way DP 80p. Standard toggle switch 3A 250V Single pole. Plastic dolly. 32p. Microswitches: All SPDT. Standard V3 size button operated 28p. Subminiature button operated 32p. Subminiature lever operated 35p.

KNOBS: Black pointer type with metal inlay, screw fix. 25mm dia. 20p. Plain brushed aluminium type on black base. Push on for D spindle. 30mm. 14p. Slider control knob. Black with metal inlay. 14p. Button knob for pushbutton switches. Black body metal cap. 14p.

ANTISURGE FUSES: 20mm. 160mA 15p. 500mA, 4A, 10A. 12p. 32MM. 200mA, 500mA, 800mA, 1.5A, 2A, 2.5A. 14p.

ALL PRICES ARE INCLUSIVE OF VAT. WE ARE A MAILORDER COMPANY — CALLERS BY APPOINTMENT ONLY PLEASE

HIGH CAPACITANCE ELECTROLYTICS. Ideal for P.S.U.'s, Smoothing etc. Voltages 10-25v.d.c. Values 1000-4700uf. Pack of 10 assorted for £2.25. Pack of 25 for £4.25. Sorry no special selections.

CABLES: Single stranded connecting wire. Various colours. 4p metre. Figure 8 twin flex 0.5mm for speaker leads, etc. White only. 7p metre. 3 core mains flex 0.5mm (3A) in white. 15p metre. 4 core flex 7/02mm (1.5A) for telephones, alarms, etc. White. 15p metre. 8 core flex 7/02mm (1.5A) overall dia. 10mm. Grey. 30p metre. 10 way ribbon cable. U.S. equiv 7/02mm. Colour coded. 30p metre. U.H.F. Low loss co-axial cable 75 ohm. White only. 20p metre.

Liquid Crystal Displays. Field effect, low power requirement. 12.7mm high digits. 7 segment format plus decimal points and colon. 40 pin DIL package. 4-17V operating. Available 3; digit (inc. polarity and overrange) or 4 digit. £7.50. Miniature enclosed relays. 24V 1250 ohm D.P. changeover solder tags. £1.70. 24V (operating range 11-37V) 700 ohm 4 pole changeover. P.C. mounting. £1.95. Standard car radio suppressors 1 uf. 150V. Fit on condensers. £1.25. Speaker motors 12V. d.c. with variable speed control and pulley. £1.25. Speaker cabinets. Teak effect finish with black front. Dims. 15 x 9 1/2 x 6 1/2 in. Fitted with 8 x 5 in. 8 ohm speaker. Complete with lead and plug. £16.95 pair. P&P £2.50 pair. Chassis loudspeakers 8in. 8 ohm 15W. Dual-cone Mag. weight 15oz approx. £6.75. 6 x 4 in. 4 or 15 ohm 6W. Mag weight 6oz. approx. £2.60.

SEMICONDUCTORS:

IN 4001	5p	BC 108C	12p	BF 594	26p
BZY88 4.3	7p	BC 148	7p	BSX 20	20p
BZY88 4.7	7p	BC 177A	15p	BSY 95A	17p
BZY88 6.8	7p	BC 178	14p	BZX61C15	10p
BZY88 12	7p	BC 178A	14p	BZY91C75	11p
BA316 10V	5p	BC 182	11p	TIS 90	18p
BAX 13	7p	BC 183L	11p	2N 2484	21p
BC 107	10p	BC 239C	11p	2N 3707	10p
BC 107A	10p	BC 549	11p	2N 3704	10p
BC 107B	12p	BCY 70	14p	741 (8 pin)	18p
BC 107C	12p	BCY 71	14p	74L54	17p
BC 108	10p	BF 180	30p	SN 76023N	175p
BC 108A	10p	BF 195	11p	MC 3401P	46p
BC 108B	12p	BF 451	22p	S01 (2A 100V)	40p

CONNECTORS:

Professional quality stereo jackplugs 1/2in. Metal body and cable grip. 42p. Stereo jack sockets. Open type 3 contact 20p. Headphone type 8 tag 35p. Chassis DIN sockets. 2 pin 8p. 5 pin 13p. Cannon locking 3 pin DIN plug 65p. Belling Lee 3 pole mains connector 10A 250V. Cable plug and chassis socket 65p pair. Television coax plugs all aluminium body. 77p. BNC free socket 50 ohm 60p. U.H.F. Elbow plugs 150p. U.H.F. 'T' adaptor (2 sockets to 1 plug) 175p. 12 way polythene terminal blocks. 5A 380V. Easily subdivided. 24p.

MINIATURE BULBS: M.E.S 6.5V, 0.3A round and 0.15A tubular. 10p.

L.E.S. 6.5V 1W. and 14V 0.75W 10p.

PANEL NEON INDICATOR. Amber lens, chromed body 10mm dia. 250V. 35p.

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge
£2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers.

Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, Radio and Electronics Constructor, 57 Maida Vale, London, W9 1SN.

BIGGEST RANGE SERVICE SHEETS/MANUALS. Any published sheet £1. plus s.a.e. Repair data any named TV £5.50 (with circuit set £7). S.A.E. newsletter, quotations, bargains. G.T., 76 Church Street, Larkhall, Lanarkshire.

THE BRITISH AMATEUR ELECTRONICS CLUB for all interested in electronics. Four Newsletters a year. Library of technical books and magazines. Help for members by experts. U.K. & Eire £4.50. Europe £6. Airmail £7.50—Sterling per year. Details from Hon. Sec., J. G. Margetts, 3 Bishopstone Close, Golden Valley, Cheltenham, Glos.

COLLECTORS' ITEMS. Nearly 50 copies of RADIO Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

25 MIXED I.C.'S £1.50. 100 mixed transistors £3.50. Valves. Early radios. Electronic bargains. Interesting lists 15p. Sole Electronics, REC, 37 Stanley Street, Ormskirk, Lancs, L39 2DH.

£5 OSCILLOSCOPE. Standard junk box components plus approx. another £5 (Total components approx £12). This unit plugs into TV aerial socket and converts TV to oscilloscope. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

BOOKS FOR SALE: *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Digital I.C. Equivalents & Pin Connections*, by Adrian Michaels, £1.20. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Understanding & Using Modern Signal Generators* by Charles Gilmore. £1.20. *Electronics Unravalled* by Kyle, £1. *How to Use your VOM VTVM Oscilloscope*, by Clifford, £1. *Modern Radio Repair Techniques*, by Art Margolis, £1. Box No. 394.

BOOKS AND TECHNICAL MANUALS. Electrical/electronic interest. 1930's to present. About 50. £15 for the lot. Collect Seaford. Telephone: 01-789-1629.

(Continued on page 125)

RADIO & ELECTRONICS Constructor Projects

80 METRE AMATEUR BAND RECEIVER	July	£21.75
CAPACITANCE MEASURING ADAPTER	July	£8.75
REMOTE VOLUME ATTENUATOR	August	£3.00
WIEN BRIDGE A.F. SIGNAL GENERATOR	June 1980	£8.60
DUSK-TO-DAWN SWITCH	June 1980	£8.50
PASSIVE LOGIC PROBE	June 1980	£2.50
MODULATED ALARM GENERATOR	June 1980	£4.50
RING OF LEDS PRINT TIMER	January 1980	£7.80
LOGIC TESTER	February 1980	£3.05
LABORATORY POWER SUPPLY	May 1980	£12.80
DUAL POLARITY VOLTMETER	May 1980	£9.60
STEREO MIXER UNIT	March 1980	£7.60
INFRA-RED INTRUDER ALARM	March 1980 (Relay 2p 2w £3.20 extra).	£6.10
TELEPHONE BELL REPEATER	February 1980 (Excludes screened cable which is supplied as required).	£5.80
GENERAL PURPOSE 8 WATT AMPLIFIER	May 1980 (Excludes etched p.c.b.)	£12.75

All kits include parts as specified in the article except where indicated. Batteries and solder are not supplied with any kit. Prices include VAT. Postage is 50p per kit. Please allow 10 days for delivery. Send 30p in stamps for our full lists. Mail order only.

T & J ELECTRONIC COMPONENTS
98 Burrow Road, Chigwell, Essex. IG7 4HB

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for *you*.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'
MPT Radio Communications Cert
**EXAMINATION STUDENTS —
GUARANTEED COACHING
UNTIL SUCCESSFUL**

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering
& Servicing
Electrical Engineering Installations
& Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

..... Occupation

ICS

Accredited
by CACC
Member of
ABCC

To
International Correspondence Schools
Dept Z278, Intertext House, LONDON
SW8 4UJ or phone 01-622 9911 (anytime)



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS &
 WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO DEPT REC
 SWAN WORKS, BANK SQUARE, WILMSLOW
 CHESHIRE SK9 1HF

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,

Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536



PRICED FROM £148.75

Stereomicroscope
This microscope's working distance and field of view is relatively large; this feature ensures convenience to the operator who works with both hands while assembling precision mechanisms.

IDEAL FOR PRINTED CIRCUITS AND OTHER DELICATE WORK.

COMES COMPLETE WITH

built-in x 10 Mag. Objectives x 20 Objectives x 35 At extra cost

We stock one of the largest selections of second hand microscopes and optical magnifiers, on and off stands. Please phone for details.

LATEST BOUND VOLUME No. 32



of "Radio & Electronics Constructor"

Comprising 776 pages inc. index

SEPTEMBER 1978 to AUGUST 1979

PRICE £5.50 P&P £1.30

BOUND VOLUME No. 27 (August 1973 to July 1974)
 BOUND VOLUME No. 28 (August 1974 to July 1975)
 BOUND VOLUME No. 29 (August 1975 to July 1976)
 BOUND VOLUME No. 30 (August 1976 to July 1977)
 BOUND VOLUME No. 31 (August 1977 to August 1978)

PRICE £3.00 p&p £1.30
 PRICE £3.20 p&p £1.30
 PRICE £3.50 p&p £1.30
 PRICE £3.70 p&p £1.30
 PRICE £5.20 p&p £1.30

We regret all other volumes are now completely sold out.

Available only from:

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 123)

JOIN THE INTERNATIONAL S.W. LEAGUE.

Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

PEN TYPE SIGNAL INJECTOR available for £2.50 including air freight. Business Promotion Bureau, 376 Lajpat Rai Market, Delhi 110006, India.

FOR SALE: Wide angle 9.5mm cine equipment: camera, projector, screen, etc. Also several other 9.5mm cine cameras. S.A.E. for details Box No. G388.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

WANTED: Service manual - Ekco car-portable type CP 920. To buy or borrow. Box No. G398.

WANTED: Service Manual, circuit diagram of Telequipment Serviscope Type S51A. To buy or borrow copy. Expenses refunded plus small remuneration. 35 Stanhope Road, Swanscombe, Kent, DA10 0AN.

ELECTRICAL/ELECTRONICS WORKSHOP.

Remains. Many motors, transformers, variable condensers, meters (including 2 multimeters, large microammeters, CR bridge), switches, relays, etc., etc. Some obsolete and some modern. Offers around £70 for the lot. To be collected from Seaford, Sussex. Telephone 01-789-1629.

AMATEUR REORGANIZING WORKSHOP

has the following items for sale in working order. Avo 8 £35. Advance audio signal generator £18. Cossor 1052 D.B. 'scope £20. Cossor 2½ inch miniscope £16. Triplet a.m. signal generator 100kHz - 25MHz £20. BC221 frequency meter £20. Also variacs, auto transformers and meggers. State wants. S.A.E. enquiries. Carriage extra. Box No. G395.

HEATHKIT DIGITAL DISPLAY shelf clock with Westminster chimes. Used one month only. £80. (Cost £160). Telephone:- Southend (0702) 711181.

FOR SALE: A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

(Continued on page 126)

ELECTRONICS

A NEW AND EXCITING HOBBY!!

BIG, WELL ILLUSTRATED BOOK

Ideal for beginners - gives lots of general information - explains how to build lots of projects: Intercom, Rain Alarm, Radios, Organ, Parking Light etc. All parts supplied and can be re-used on special deck provided, so **NO SOLDERING** is required. Just needs 4½V battery.



£17.50 inc. VAT & Post

Also

ADVENTURES WITH MICROELECTRONICS


- Explore the world of silicon chips -

All components & Deck, £27.95 inc VAT & Post.

Component Catalogue & Bargain List 75p

GREENWELD

443G Millbrook Road, Southampton SO1 0HX

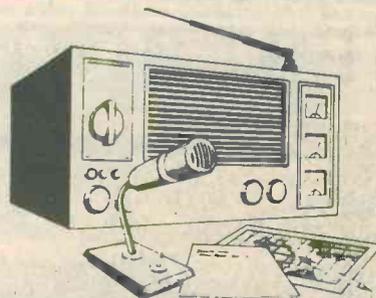

BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-

British National Radio & Electronic School

4 Cleveland Road, Jersey, Channel Islands.

Name

Address

REC/10/815

BLOCK CAPS PLEASE

AMATEUR RADIO EQUIPMENT & ACCESSORIES

YAESU FT-202R 2 METER HAND-HELD
FM TRANSCEIVER
"THE HANDIE"

£101 INC. POSTAGE

FT-207R
CPU CONTROLLED
SYNTHESIZED HANDIE
WITH CHARGER

£209 INC. POSTAGE

SEND CWO OR ACCESS CARD NUMBER

for our latest
catalogue
plus **£3.60 VOUCHER!**

SEND 36p IN STAMPS -
(STATING INTEREST)

TO: **Amateur
Electronics
East Ruston
Norfolk. NR12 0RU**



FT207

**YAESU
The radio.**

MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

400m/w ZENOR DIODES

Low Price

3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2,
6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V,
13V, 13V5, 15V, 16V, 18V, 20V,
22V, 24V, 27V, 30V, 33V
Price: 8p each 100 any mix £6.00

RESISTORS

1/4W at 40°C 5% tol., 2.2 Ω
to 2MΩ, E12 2p each.
Resistor Pack - 2.2 Ω - 2MΩ, 10
each, value (730 resistors) £6.00

1 watt

ZENER DIODES

3V3 to 200V Full range
Price 15p each 100 any mix £12.50
8 DIL 10p 22 DIL 23p
14 DIL 13p 24 DIL 24p
16 DIL 15p 28 DIL 28p
18 DIL 18p 40 DIL 40p
20 DIL 22p

VEROBOARD (Copper Clad)

Size Inch 0-1" 0.15
2.5 x 1 20p N/A
2.5 x 5 55p 56p
2.5 x 3.75 46p 50p

Vero Wiring Pen (including spool
of wire) £2.84

CONNECTING CABLE

Black, Blue, Green, Grey, Orange,
Pink, Red, White, Violet, Yellow,
Brown. Singles 5p per metre
7/0.2mm 5p per metre
16/0.2mm 8p per metre

SPECIAL OFFERS

BRAND NEW METAL SLIDER POTENTIOMETERS

60mm TRACK	1+	100+	BZY96 ZENERS (21W) - 6VZ
500 ohm Lin. Mono	35p	28p	1+ 20p each
50K Log. Stereo	40p	30p	100+ 12p each
100K Lin. Stereo	40p	30p	
1 Meg Log. Stereo	40p	30p	

Other values available in 45mm track - send for list.

Send your orders to:

DEPT DP12, MARCO TRADING, THE OLD SCHOOL,
EDSTASTON, Nr. WEM, SHROPSHIRE SY4 5RJ

Tel: Whixall (094872) 464/465

Please add 30p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage. Air/Sea at cost

SMALL ADVERTISEMENTS

(Continued from page 125)

COMPONENTS, Items, Bargains. Various lists
15p or s.a.e. Sole Electronics (REC), 37 Stanley
Street, Ormskirk, Lancs., L39 2DH.

**THE RADIO AMATEUR INVALID & BLIND
CLUB** is a well established Society providing
facilities for the physically handicapped to enjoy
the hobby of Amateur Radio. Please become a
supporter of this worthy cause. Details from the
Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch
Court, Adelaide Road, Surbiton, Surrey, KT6
4TE.

INTERESTED IN OSCAR? Then join
AMSAT-UK. Newsletters, OSCAR NEWS
Journal, prediction charts, etc. Details of mem-
bership from: Ron Broadbent, G3AAJ, 94
Herongate Road, Wanstead Park, London, E12
5EQ.

FOR SALE: Photographic enlarging equipment:
Vivitar enlarger. Model E.36 with 50mm f. 3.5
and 75mm f.3.5 lenses. Kodak safety light.
Kodak contrast filter set. 11 in. x 14 in. printing
frame with copying facilities. Measuring flask.
Three trays, three tweezers. Three plastic bot-
tles. Clips. Printing paper. Antistatic brush for
cleaning negatives. Kodak Photoguide Booklet.
Man's protective apron. £75 o.n.o. Pair of
Goodman's speakers 8 ohms, 15 watts, £50
o.n.o. R. L. Gee, 3 Longfellow Drive, Hutton,
Essex, CM13 2QQ.

BOOKS FOR SALE: *Amateur Radio Antennas* by
Harry Hooton, £1. *Ham Antenna Construction
Projects* by J. A. Stanley, 75p. *All about Cubical
Quad Antennas* by W6SAI, £1. *Radio
Astronomy for the Amateur* by Dave Heiser-
man, £2. *HAM-RTTY* by W2NSD, 50p. All plus
postage. Box No. G397.

POSTAL ADVERTISING? This is the Holborn
Service. Mailing lists, addressing, enclosing,
wrapping, facsimile letters, automatic typing,
copy service, campaign planning, design and
artwork, printing and stationery. Please ask for
price list. - The Holborn Direct Mail Company,
Capacity House, 2-6 Rothsay Street, Tower
Bridge Road, London, S.E.1. Telephone:
01-407 6444.

INTERESTED IN RTTY? You should find the
"RTTY Journal" of interest. Published in
California, U.S.A., it gives a wide outlook on the
current RTTY scene; RTTY-DX; DXCC Hon-
our Roll; VHF RTTY news; and up to date
technical articles are included. Specimen copies
35p from: The Subscription Manager, RTTY
Journal, 21 Romany Road, Oulton Broad,
Lowestoft, Suffolk, NR32 3PJ.

(Continued on page 127)

SMALL ADVERTISEMENTS

(Continued from page 126)

RADIO/RADIO & ELECTRONICS CONSTRUCTOR. 1950 - 1979 bound volumes. Also *Wireless World* 1955-1975 bound and some *Practical Electronics*. Collect Seaford. Telephone: 01-789-1629.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

Give for those who Gave

WINGS APPEAL



During September



"TWO 20dB AMPLIFIERS" - PART 1. PRINTED CIRCUITS There is no need to make up and print your own circuit board for this project - we can supply the board fully printed, prepared and ready for use. The board is glass fibre, roller tinned and drilled - just fit components and solder! Price for each board 68p plus 25p post and packing by mail order from BRB PRINTED CIRCUITS, 109 Potter Street, Worksop, Notts., S80 0BY.

COMMUNICATIONS RECEIVERS part of Navy CAS equipment made by Murphy Radio 5 band Rx covers 60 to 550Kc two bands and 1.5Mc/s to 30Mc/s three bands. The Rx uses a total of 13 B7g valves as two RF stages, Sep L.O. 3x IF stages at 800Kc Det, Noise Lim, 2x AF stages, BFO, Crystal Cal at 800Kc, the O/P stage matches to 100 ohm phones and a 600 ohm 2 watt speaker line. Controls main tune, band sel, RF gain, LF gain, Phone gain, AGC on/off, Selectivity at 8.3, 1Kc and 200c/s the 1Kc position uses a bandpass crystal filter, the 200c/s uses crystal plus Audio filter, BFO this swt selects upper or lower beat or tune also selects 800Kc crystal cal, there are two O/P jacks for phones and one for speaker on front panel, provision for 75 ohm Ae I/P or long wire. Complete in steel case size 13 x 14" front 14" deep these Rx req ext power supplies of 250v HT and 150v Stab total load 100Ma 6.3v AC at 4 amps. Their is room inside the case to build internal P.U. Rx supplied Tested with copy of Circuit and 40 page handbook, more details on request. £115. VIDEO RECORDERS Philips type LDL100 portable monochrome 625 line recorder reel to reel 1/2" tape 75 ohm I/P 1v sig. 4v sync 75 ohm O/P ext size 42 x 34 x 20 Cm weight 12Kg we also have a few /2 models these are table case version, both 240v 50c I/P these are supplied in good cond with 80 page handbook and tested, fuller spec on request. £185.

ARMY RADIO station 128 small low power T/Rx covers 2 to 8Mc/s tunable Rx with crystal controlled Tx normally operates from dry batteries 135v and 1.5v supplied with haversack, battery holder, Morse key, aerial wire, headphones and circ. £25.

MAINS INVERTORS small 12v DC I/P 240v O/P at 20 watts square wave at 50c/s in case size 6 1/2 x 4 1/2 x 3" stab freq from UJT, okay for Soldering irons or AC/DC razors with rect O/P tested £15.

PANEL VARIAC small type 200/250v O/P 0 to 240 at 700Ma max ex new equip with knob 9.50.

Above prices include Postage & Vat goods
ex equipment unless stated new, 2 x 10p
stamps for list 25/1.

A. H. SUPPLIES

122, Handsworth Road, Sheffield. S9.4AE.
Phone 444278 (0742).

BUILD YOUR OWN

P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING

5 Swan Street, Wilmslow, Cheshire

NEW ELECTRONIC BOOKS

Build Your Own Transistor Radio	£2.25
TV Trouble Diagnosis Made Easy	£2.75
Electronic Musical Projects	£2.30
Electronic Gadgets for You	£2.25
Transistor Circuits & Servicing	£2.25
555 Timer & Its Applications	£2.40
Electronic Hobby Circuits	£2.25
Simple Crystal Diode Circuits	£2.25
Fascinating I.C. Projects	£2.30
Transistor Receivers Self-Constructor	£3.10
Build Your Own Digital Clock	£2.75
Cassette Recorders: How They Work, Care & Repair	£5.95
Build a 2-Band Silicon Transistor Radio	£2.30
Pictorial Guide to Colour TV Circuit Problems	£5.95

Books postpaid from:

FINBARR'S LTD.,

16 Turketel Road, Folkestone, Kent.

MAIL ORDER ONLY

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 60p each, p&p 18p
Issue(s) required

Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)
post free, commence with issue

Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.30
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.30
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.30
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.30
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.30
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.30

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only Price £2.25, post & pkg 50p
With no title on spine, maroon Price £2.25, post & pkg 50p
With no title on spine, green Price £2.25, post & pkg 50p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages	Price £1.20, P.&P. 27p
DB6 Radio Amateur Operator's Handbook, New edition in course of preparation	
DB17 Understanding Television, 504 pages	Price £3.95, P. & P. £1.00
DB19 Simple Short Wave Receivers 140 pages	Price 80p, P. & P. 27p

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording - White	- 6 sheets	Price £1.50, P. & P. 11p
Set 4: Wording - Black	- 6 sheets	Price £1.50, P. & P. 11p
Set 5: Dials	- 6 sheets	Price £1.50, P. & P. 11p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

*Overseas customers please pay by International Money Order.
All publications are obtainable through your local bookseller*

Data Publications Ltd., 57 Maida Vale, London W9 1SN


PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

STRAY AND SELF-CAPACITANCE

A stray capacitance exists between two adjacent wires, as in (a), this reducing as the spacing between the wires increases and as the diameter of one or both wires reduces. The stray capacitive coupling disappears when an earthed screen is interposed, as in (b), and each wire then has a stray capacitance to the screen.

In (c) a stray capacitance appears between an amplifier output and non-inverting input. Should the consequent positive feedback be high enough it can modify the frequency response if there are frequency-conscious components at either terminal or in the amplifier, or cause instability. Feedback problems tend to increase with increasing amplifier gain, bandwidth and input terminal impedance.

Stray capacitance in the tuned circuit wiring of (d) reduces the resonant frequency. To the wiring stray capacitance should be added the self-capacitance of the coil, see (e), which is a summation of all the capacitances between the turns of the coil. It is found that the self-capacitance of a single layer close-wound coil increases almost directly as coil diameter increases, whilst coil length has little effect on self-capacitance. The enlarged section in (f) shows a few of the very many capacitances between coil turns, the most important being those between adjacent turns. Because of the distribution of these capacitances, a coil resonant with its own self-capacitance may not exhibit as sharp a resonant peak as it will if a low value external capacitor is connected across it. The self-capacitance of a coil requiring a large number of turns may be reduced by wave-winding it, (g), and also by winding it, as in (h), with two or three sections connected in series.

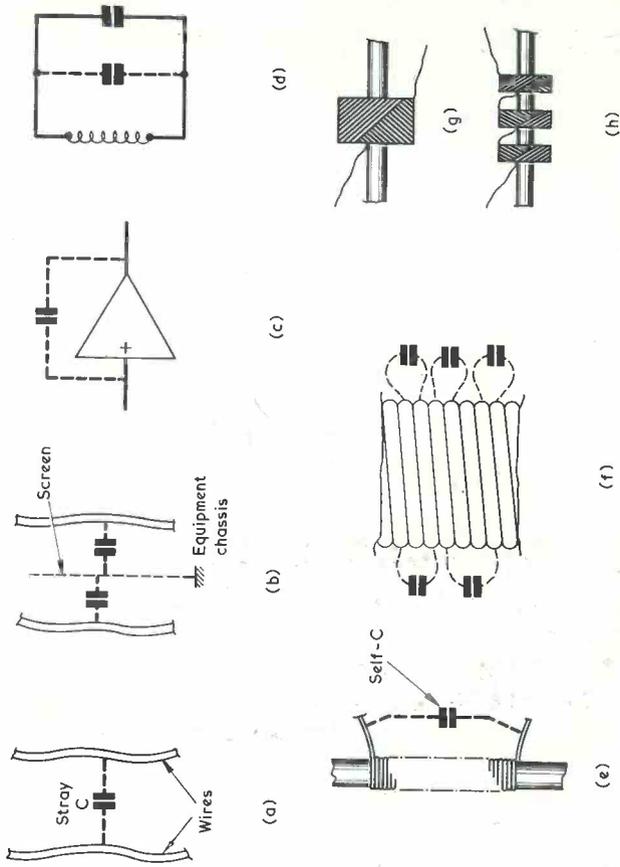

MAPLIN

announce the opening of their new LONDON shop

259-261
King St.
Hammersmith
London W6
01-748 0926



- * Excellent metered parking
- * Close to Hammersmith Underground Station for Piccadilly, District & Metropolitan Lines
- * Bus no's 260 · 266 · 704 · 27 · 91 267 · 290 stop outside



Opens Tuesday 16th September, 1980

Opening Hours 9.45 am to 5.30 pm Tuesday to Saturday (Closed Monday)

Maplin mail-order –
Now better than ever!

- * Up to 8% discount for use with next order
- * All prices include VAT
- * Same day service on in-stock lines
- * Over 95% of our stock lines in stock
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components – no rejects – no re-marks
- * Competitive prices
- * Your money is safe with a reputable Company

On price, service, stock, quality and security, it makes sense now more than ever to make **Maplin** – your first choice for components every time!

Post this coupon now for your copy of our 1979-80 Catalogue price 70p


Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46 p.p.p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

Name _____

Address _____

REC 10/80

Stereo Cassette Tape Deck

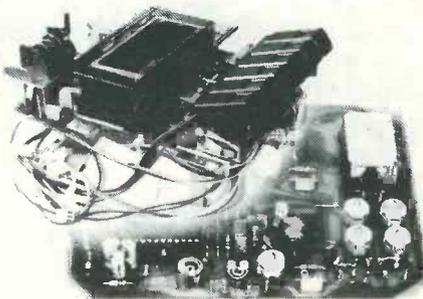

Utilising the superb JVC deck made for Tandberg and a ready-made pre-aligned, tested and guaranteed module, this cassette deck has a superb sound and a high quality specification. We've got everything you need (except cabinet) including full instruction leaflet for only £39.95. Order as XY36P (Cassette Recorder Kit)

Space Invaders

Fight the space invaders, be a polaris captain or a spaceship commander. Full colour action on your own TV set and over 450 games to play.

Basic console with Combat cartridge (AC00A) £99.50 + £2.50 carriage

All cartridges available including:

Space Invaders (AC26D)	£29.95	Adventure (AC22Y)	£23.95
Indy 500 (AC24B)	£34.50	Skydiver (AC13P)	£16.95
Chess (8 levels) (AC28F)	£34.50	Breakout (AC05F)	£16.95
Golf (9 holes) (AC18U)	£16.95	Slot Racers (AC19V)	£16.95
Air Sea Battle (AC01B)	£16.95	Programming (AC27E)	£34.50
Space War (AC02C)	£16.95	Olympics (AC04E)	£16.95
Brain Games (AC16S)	£16.95	Street Racer (AC14Q)	£16.95
Outlaw (AC03D)	£16.95	Keyboards per pair (AC29G)	£11.95

All prices include VAT and carriage except where shown.

MAPLIN

Maplin Electronic Supplies Ltd

All mail to: - P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea,
Essex. (Closed on Monday)
Telephone: Southend (0702) 554000.



Catalogue now available in all branches of WHSMITH Price £1.00