

RADIO & ELECTRONICS CONSTRUCTOR


JULY 1981

60p

SCANNING NBFM RECEIVER

CAN BE BUILT TO
COVER ANY
TWO BANDS*
FROM
25MHz TO
200 MHz

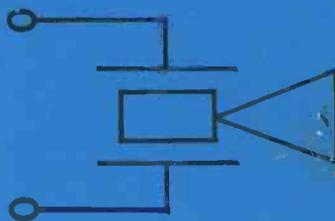- * MODEL AERO
- * 4M
- * 2M
- * PMR etc.



DESIGN IDEAS —
USING PIEZO ACOUSTIC
RESONATORS

STARTING IN
THIS ISSUE

COMPULINK —
LINKING MPU'S TO
THE REAL WORLD



- IR REMOTE CONTROL
- DIGITAL STOPWATCH

CB — LATEST NEWS

R&EC'S NEW PROJECT TEAM GETS UNDERWAY
PROFESSIONALLY DESIGNED AND
DEVELOPED CONSTRUCTIONAL
FEATURES — VERIFIED
IN OUR NEW
£50,000 LAB.

RADIO & ELECTRONICS CONSTRUCTOR

JULY 1981
Volume 34 No. 11

Published Monthly

First published in 1947

*Incorporating The Radio
Amateur*

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

©Data Publications Ltd., 1981. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$30.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production – Web Offset.

SPECIAL BOOK SECTION	642
READER'S OFFER – Electric Headphones	655
NEWS AND COMMENT	656
PIEZO ACOUSTIC TRANSDUCERS Design Ideas No. 1 by Jonathan Charles Burchell	658
IN NEXT MONTH'S ISSUE	661
INFRA-RED REMOTE CONTROL SYSTEM Part 1 by I.M. Attrill	662
CB CB CB CB.....	666
A SCANNING MONITOR RECEIVER SYSTEM Part 1 by L. Power	670
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	677
TRADE NEWS	679
RADIO SWITCH-OFF TIMER by John Baker	680
COMPULINK SERIES – No. 1	684
UNIVERSAL 12v 5W AMPLIFIER	686
KNOW YOUR RF CONNECTORS – Part 1 Electronics Data – No. 71	689
LCD DIGITAL STOPWATCH/CLOCK by J. L. Mills	690
FURTHER THOUGHTS ON OHM'S LAW Smithy straightens out non-linear resistors – In Your Workshop	692
NEW PRODUCTS	697

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE
WILL BE PUBLISHED
15th JULY

The R&EW Book Service

By way of an introduction to part of the philosophy behind the forthcoming *Radio and Electronics World*, we are introducing some of the vastly expanded range of titles on electronics, radio and computing that we are now able to offer in conjunction with *International Book Distributors*.

Unlike many magazine book services, *R&EW* is actually stocking the titles for direct despatch, and thus we are basically offering only those titles which we feel are really worthwhile. The editorial eye has been cast over the titles listed here, and we have weeded out those which we feel are not particularly appropriate or apposite.

In case you think this must be the same range as you have seen elsewhere - wait a moment, since *IBC* has *not* previously engaged in such an exercise with a monthly magazine, you will find a plethora of new material herein.

New titles are introduced at the rate of 3-4 a month, and we will be reviewing and stocking all those which have a contribution to make to the prime *R&EW* aim, which is to improve both the quantity and quality of the information that is available to the electronics enthusiast - be he/she an 'amateur' or 'professional'.

You will see that we have introduced a couple of title from the famous *Howard Sams* series. The *Sams'* photofact series are widely appreciated in the USA as being the standard service engineer's 'bible' on subjects ranging from washing machines to CB. In view of the nature of the equipment and the varying standards that apply both sides of the Atlantic - we will probably only be stocking the CB and scanner-monitor series for UK consumption.

Books BOOKS Books



Z-80 Microcomputer Design Projects

by William Barden, Jr.

208 pages; 8½ x 11; softbound. © 1980
(ISBN: 0-672-21682-5) £8.40

Even a beginner in electronics will enjoy constructing and operating the EZ-80 microcomputer, a project that requires surprisingly little time and money. The book is a solid introduction to the Z-80 microcomputer and the remarkable chip, EZ-80. Several EZ-80 applications programs are included.

Microcomputer Interfacing With the 8255 PPI Chip

by Paul F. Goldsbrough

224 pages; 5½ x 8½; softbound. © 1979
(ISBN: 0-672-21614-0) £5.80

This self-instructional text is designed to introduce the reader to the Intel 8255 Programmable Peripheral Interface (PPI) through discussion and experiments. Much of the material is applicable to PPIs in general and tells what the 8255 is, where it fits in a microcomputer system, why it is used, and how it is used.

One Evening Electronic Projects

by Calvin R. Graf

128 pages; 5½ x 8½; softbound. © 1980
(ISBN: 0-672-21699-X) £3.20

Even beginners will discover the pleasure of building their own electronic projects with this book as a guide. Simple tools found in the home workshop and readily available components can result in an evening of fun and a useful project for the house, garage, workshop, or office.

Programming & Interfacing the 6502, With Experiments

by Marvin L. De Jong

416 pages; 5½ x 8½; softbound. © 1980
(ISBN: 0-672-21651-5) £10.35

Dr. De Jong has compiled 14 interesting chapters of information and programs that will be useful to anyone interested in using 6502-based microcomputer systems. Experiments and examples are written so that a KIM, AIM or SYM system may be used to reinforce the material presented in each chapter.

6502 Software Design

by Leo Scanlon

272 pages; 5½ x 8½; softbound. © 1980
(ISBN: 0-672-21656-6) £7.50



The 6502 integrated circuit is a very popular microprocessor that is currently being used in general-purpose microcomputers, video games, and personal computers. This material is presented to increase the reader's understanding of the 6502 integrated circuit. Fundamentals are first explained then more complex topics are gradually introduced in the nine information-packed chapters.

Active Filter Cookbook

by Don Lancaster

240 pages; 5½ x 8½; softbound. © 1975
(ISBN: 0-672-21168-8) £9.70

A practical, user-oriented treatment of active filters. Explains what active filters are and how they work, and gives detailed information on design, analysis, and synthesis techniques. Explores some interesting applications for active filters in brainwave research, electronic music, quadrature art, and psychedelic lighting.

Design of Op-Amp Circuits, With Experiments

by Howard M. Berlin

224 pages; 5½ x 8½; softbound. © 1977
(ISBN: 0-672-21537-3) £5.80



Covers the fundamentals of operational amplifier devices in linear amplifiers, differentiators, filters, and nonlinear amplifiers. Use of the readily available 741 and 3900 devices is stressed with many practical circuits and 35 experiments.

Practical Low-Cost IC Projects (2nd Edition)

by Herbert Friedman

96 pages; 5½ x 8½; softbound. © 1979
(ISBN: 0-672-21599-3) £2.95

Presents complete parts lists and schematic diagrams for 38 different integrated-circuit projects, most of which can be inexpensively built in a few hours by either the inexperienced or the experienced project builder. Proj-

ects include a walkie-talkie power pack, hi level mixer, scope calibrator, head-phone amplifier, LED power blinker, and fuzzer for electric guitars.

555 Timer Applications Sourcebook, With Experiments

by Howard M. Berlin

160 pages; 5½ x 8½; softbound. © 1976
(ISBN: 0-672-21538-1) £4.50



Deals with the many applications of the popular 555 timer "chip." Uses for voltage regulation, control, sequencing are covered as well as the more usual timing and signal generating functions. With many useful circuits and 15 detailed experiments.


Computer Language Reference Guide with Keyword Dictionary.

by Harry L. Helms, Jr.

112 pages; 5½ x 8½; softbound
© 1980
(ISBN: 0-672-21786-4) £4.50

If you're working with computers and find yourself confronted with programs written in languages you normally don't use or even know, then this new book is exactly what you need.

Seven chapters explain the computer languages—BASIC, ALGOL, LISP, Pascal, PL/1, COBOL and FORTRAN. Each chapter follows the same pattern—introduction, program format, variables and constants, etc.—to give you a clear distinction of the differences in each language. A helpful Resource work list is included in most chapters, while Chapter 8 contains a complete keyword dictionary. You can depend on this quick, easy-to-follow reference for a better understanding of today's computer languages.

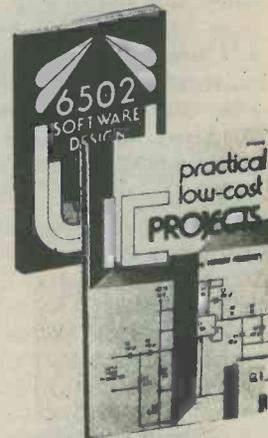

TRS-80 Interfacing — Book 1

by Jonathan A. Titus

192 pages; 5½ x 8½; softbound. © 1979
(ISBN: 0-672-21633-7) £5.80

If you have a fairly good understanding of the commands in Level II BASIC, this book will appeal to you. The book introduces you to the signals available within the TRS-80 computer and to show you how they can be used to control external devices. You will have an opportunity to construct and test a number of interesting interface circuits that will be used in the experiments.

TRS-80 Interfacing — Book 2

by Jonathan A. Titus, Christopher A. Titus, and David G. Larsen

256 pages; 5½ x 8½; softbound. © 1980
(ISBN: 0-672-21739-2) £7.10

Introduces you to more advanced interfacing techniques that allow you to do real things with your TRS-80 computer. You learn how to drive high current and high voltage loads, how to generate voltage and current signals used in a variety of control applications, how to measure unknown voltages and currents with your computer, and how to use remote control circuits that allow you to control Universal Asynchronous Receiver/Transmitter Chips, analog-to-digital and digital-to-analog converters, and other devices located some distance from your computer. Contains complete software examples.

How to Program and Interface the 6800

by Andrew C. Staugaard, Jr.

416 pages; 5½ x 8½; softbound. © 1980
(ISBN: 0-672-21684-1) £10.35

An in-depth introduction to microprocessors and microcomputers in general and the Motorola 6800 microprocessor family in particular. Covers 6800-based microcomputers-learning systems. Over 30 "real-world" experiments demonstrate applications as the concepts are being explained. Includes detailed discussions of the internal structure, instruction set, and programming techniques for the 6800. Input/output techniques, memory interfacing, the 6820/6821 peripheral interface adapter, and system interfacing are all covered.

Design of VMOS Circuits, With Experiments

by Robert T. Stone & Howard M. Berlin

176 pages; 5½ x 8½; softbound. © 1980
(ISBN: 0-672-21686-8) £7.10

The vertical metal oxide semiconductor, or VMOS, is a new and exciting device that may be a giant step towards the ideal active circuit element. This book written to whet your appetite, features 11 chapters on the VMOS and its characteristics. Chapter 11 presents a series of experiments that demonstrate a number of the concepts discussed in earlier chapters.

DEBUG: An 8080 Interpretive Debugger

by Jonathan A. Titus and Christopher A. Titus

112 pages; 5½ x 8½; softbound. © 1977
(ISBN: 0-672-21536-5) £3.20

This text describes DEBUG, a software debugging package for 8080-based microcomputers. It describes the operation of the program and how it can be applied to program development and testing. Complete with documented hexadecimal and octal listings of programs.

TV Antennas and Signal Distribution Systems

by M. J. Salvati

256 pages; 5½ x 8½; softbound. © 1979
(ISBN: 0-672-21584-5) £6.45

An invaluable guide to selecting and installing tv antennas and signal distribution systems, this book is packed with easy-to-understand information on using these systems to produce high quality tv reception. Many of the antennas described have been personally tested by the author.

Design of Phase-Locked Loop Circuits, With Experiments

by Howard M. Berlin

256 pages; 5½ x 8½; softbound. © 1978
(ISBN: 0-672-21545-4) £6.45

The design of the basic PLL circuits is described; detector, phase comparator, and voltage-controlled oscillator circuits are detailed. Contains many practical circuits using the 560-series devices and the CMOS 4046 chip. With over 15 experiments.





The Howard W. Sams Crash Course in Microcomputers

by Louis E. Frenzel, Jr.
264 pages; 8½ x 11; wirebound. © 1980
(ISBN: 0-672-21634-5) £11.40

Because of its content and unique form of presentation, the reader is provided with a solid background in microcomputers quickly and effectively. This course, arranged as a series of lessons in a self-teaching format, features 14 units and 2 appendices that will teach the average consumer as effectively as the scientist with a PhD to deal with complete microcomputer systems. Each unit includes self-test review questions and answers.

Practical RF Communications Data for Engineers and Technicians

by M. F. "Doug" DeMaw
256 pages; 5½ x 8½; softbound. © 1978
(ISBN: 0-672-21557-8) £5.80

Communications engineers and technicians who need a practical reference of rf circuit design data will find that these five chapters of vital information have been compiled specifically for them. Subjects include ferromagnetic devices, networks for semiconductor circuits, transistor design basics, receiver design basics, and practical communications antennas. Each chapter contains an extensive bibliography.

other books currently available

General Titles

ABCs Integrated Circuits	2.55
Ferromagnetic Core Design Handbook	12.95
How to Build your own Stereo Speakers	4.50
Integrated Circuit Projects	3.60
99 Practical Electronic Projects	3.85
Practical Hardware Details	14.25
Unique Electronic Weather Projects	5.15

Radio Books

CB Radio Construction Projects	2.55
Ham & CB Antenna Dimensions	1.65
Intro Microcomputers/Ham Shack	3.20
Microwave Devices & Circuits	19.45
Microwave Theory & Applications	14.25
Practical RF Communications Data	5.80
Q & A about CB Operations	2.45

Computer Books

Architecture of Concurrent Programmes	16.20
CP/M Primer	7.75
Mostly Basic; Apple II	7.10
Mostly Basic; PET	7.10
Mostly Basic; TRS-80	7.10

Watch these pages for more new titles in this exciting series.

Post your completed Order Form to:

RADIO & ELECTRONICS WORLD

Book Department,

200, North Service Road,

Brentwood, Essex CM14 4SG

Please supply the following books:

No. of price £ p
copies

-----	-----	-----
-----	-----	-----
-----	-----	-----
-----	-----	-----

POSTAGE & PACKING 75p for the first book of any order, thereafter 25p per book.
Orders over £50 - Free Delivery.

Total

I herewith enclose a cheque/P.O. no.....
value £* made payable to RADIO
and ELECTRONICS CONSTRUCTOR:

Please debit my Access/Barclaycard

No.*



* please delete as applicable.

Allow up to 21 days for delivery.

name-----

address-----

postcode-----

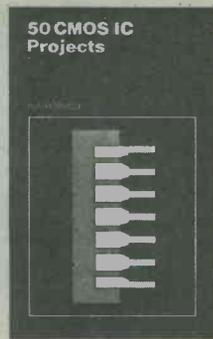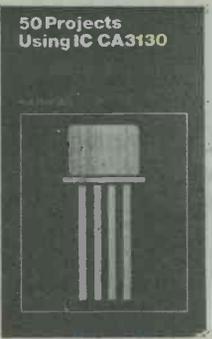

DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

18. 50 Projects Using IC CA3130	£1.25	47. Practical Electronic Calculations and Formulae	£2.25
19. 50 CMOS IC Projects	£1.25	48. Radio Stations Guide	£1.45
20. A Practical Introduction to Digital IC's	95p	49. Electronic Security Devices	£1.45
22. Beginners Guide to Building Electronic Projects	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
23. Essential Theory for the Electronics Hobbyist	£1.25	51. 50 Circuits Using 7400 Series IC's	£1.45
26. 52 Projects Using IC741	95p	52. Second Book of CMOS IC Projects	£1.50
28. Two Transistor Electronic Projects	85p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
29. How to Build Your Own Metal and Treasure Locators	£1.00	54. Beginners Guide to Digital Techniques	95p
30. Electronic Calculator Users Handbook	95p	55. 28 Tested Transistor Projects	£1.25
31. Practical Repair and Renovation of Colour TVs	£1.25	56. Digital IC Equivalents and Pin Connections	£2.50
32. Handbook of IC Audio Preamplifier and Power Amplifier Construction	£1.25	57. Linear IC Equivalents and Pin Connections	£2.75
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	58. Electronic Household Projects	£1.75
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	59. Microprocessor Primer	£1.75
35. Fun and Games with your Electronic Calculator	75p	60. Remote control projects	£1.95
36. 50 (FET) Field Effect Transistor Projects	£1.25	61. Electronic Music Projects	£1.75
37. 50 Simple L.E.D. Circuits	75p	62. Electronic Test Equipment Construction	£1.75
38. How to Make Walkie-Talkies	£1.25	63. Power Supply Projects	£1.75
39. IC 555 Projects	£1.75	64. Elements of Electronics Book 4	£2.95
40. Projects in Opto-Electronics	£1.25	65. Practical Computer Experiments	£1.75
41. Radio Circuits Using IC's	£1.35	66. Radio Control for Beginners	£1.75
42. Mobile Discotheque Handbook	£1.35	67. Popular Electronic Circuits Book 1	£1.95
43. Electronic Projects for Beginners	£1.35	68. Electronics synthesiser Projects	£1.75
44. Popular Electronic Projects	£1.45	69. VMOS Projects	£1.95
45. IC LM3900 Projects	£1.35	70. Digital I.C. Projects	£1.95
46. Electronic Music and Creative Tape Recording	£1.25	71. International Transistor Equivalents Guide	£2.95

POSTAGE 30p PER BOOK, and 15p THEREAFTER FOR EACH BOOK ORDERED

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies

Book Nos:

.

.

I enclose Postal Order/Cheque for £

Name

Address

.

.


(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

DIRECT SUPPLY SERVICE TO READERS

TOWERS INTERNATIONAL TRANSISTOR SELECTOR

(NEW REVISED EDITION)

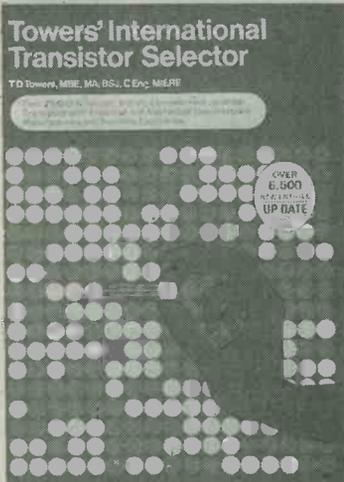

This is dead! 

Would this replace it?




If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest! In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price **£10-70** inc P&P

TOWERS INTERNATIONAL FET SELECTOR

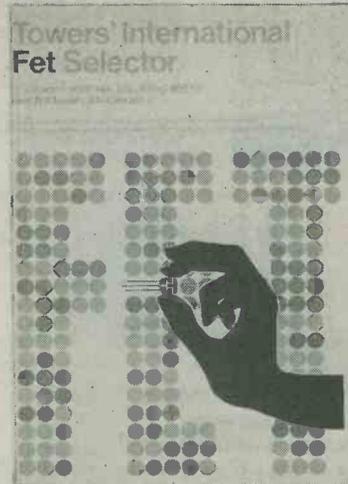

If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price **£4-60** inc P&P

(Please allow 21 days for delivery)

Tower's International Transistor Selector by T. D. Towers MBE, MA, BSc, C Eng, MIERE **£10-70** inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies to the address shown below

NAME

ADDRESS

(Block capitals)

Tower's International FET Selector by T. D. TOWERS MBE, MA, BSc, C Eng, MIERE **£4-60** inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies to the address shown below

NAME

ADDRESS

(Block capitals)


Chokes, block filters, ceramic filters, resonators, IFTs, oscillator coils, audio filter blocks etc.

LOW PASS FILTERS

Now from 10kHz to 20MHz TOKO's recently expanded LPF series covers from the audio spectrum through to 20MHz in a series of LPFs for mpX, video, radio etc.



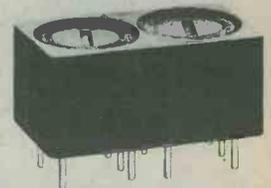The LPFs are based on 7&10mm formats with up to 4 LC tuned elements per block. Many stock types available.




HELICAL FILTERS for VHF and UHF:

2 & 3 elements available. Featuring low insertion losses, -80dB at the +/- 21.4MHz points. Ask for details.




CERAMIC RESONATORS & PIEZO SOUNDERS

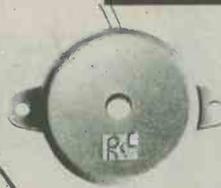Audio buzzers now down to 1kHz - low cost 400-600kHz crystal replacements for MPUs, RCs etc. Low cost - wide range.



VIDEO FRAME STORES

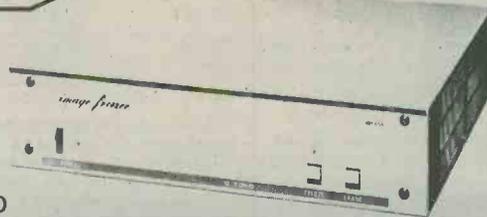- ★ 525/625 operation
- ★ 512 pixell/line
- ★ Local or remote control
- ★ Top/bottom & L/R reverse
- ★ Models available with digitized I/O



Video frame stores are a new addition to TOKO's memory product range. They permit easy analysis of low dose X-Ray pictures, digital processing of picture information (including the VFM10D with 8" disk drive) with much better resolution than available from VTR

AMBIT international TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
200 North Service Road, Brentwood, Essex

THE MODERN BOOK CO

WORLD RADIO T.V. HANDBOOK 1981 EDITION £10.50p

REPAIRING POCKET TRANSISTOR RADIOS

by I. R. Sinclair Price £2.55

TEST GEAR PROJECTS

by T. Dixon Price £4.50

ELECTRONICS - BUILD & LEARN

by R. A. Penfold Price £3.20

AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR

by I. R. Sinclair Price £3.00

BEGINNER'S GUIDE TO INTEGRATED CIRCUITS

by I. R. Sinclair Price £3.50

BEGINNER'S GUIDE TO RADIO

by G. J. King Price £3.50

ELECTRONIC PROJECTS IN THE WORKSHOP

by R. A. Penfold Price £2.75

110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR

by R. M. Marston Price £4.35

UNDERSTANDING MICROPROCESSORS

by Texas Ins. Price £4.00

AMATEUR RADIO OPERATING MANUAL

by R. J. Eckersley Price £4.70

THE OSCILLOSCOPE IN USE

by I. R. Sinclair Price £3.50

PROJECTS FOR THE CAR & GARAGE

by G. Bishop Price £4.00

SIMPLE CIRCUIT BUILDING

by P. C. Graham Price £2.75

UNDERSTANDING HI FI SPECIFICATIONS

by John Earl Price £3.40

BEGINNER'S GUIDE TO DIGITAL ELECTRONICS

by I. R. Sinclair Price £3.50

ELECTRONICS POCKET BOOK

by P. J. McGoldrick Price £5.00

PROJECTS IN RADIO & ELECTRONICS

by I. R. Sinclair Price £2.50

UNDERSTANDING CALCULATOR MATH

by Texas Ins. Price £4.00

UNDERSTANDING SOLID STATE ELECTRONICS

by Texas Ins. Price £4.00

AMATEUR RADIO TECHNIQUES

by P. Hawker Price £3.70

COST EFFECTIVE PROJECTS AROUND THE HOME

by J. Watson Price 4.50

AUDIO CIRCUITS & PROJECTS

by G. Bishop Price £5.35

PRINTED CIRCUIT ASSEMBLY

by M. J. Hughes Price: £2.75

MICROPHONES IN ACTION

by V. Capel Price £5.00

BEGINNER'S GUIDE TO COLOUR TELEVISION

by G. J. King Price £3.50

HOW TO BUILD ELECTRONIC KITS

by V. Capel Price £2.50

ELECTRONIC GAME PROJECTS

by F. G. Rayer Price £2.75

UNDERSTANDING DIGITAL ELECTRONICS

by Texas Ins. Price £4.00

HOW TO BUILD SPEAKER ENCLOSURES

by A. Badmaieff Price £3.50

BEGINNER'S GUIDE TO HAM RADIO

by L. Buckwalter Price £3.50

We have the Finest Selection of English and American Radio Books in the Country
ALL PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176


C.B. P.A. MICROPHONES.
Hand held with thumb switch & Curly Lead, Type 1 600Ω dynamic at £4.25.

Type 2 600Ω, noise cancelling type at £7.25
Type 3 Power type, with volume control 1KΩ Imp, £7.95

SEMICONDUCTORS
LM340 80p. BY103 10p.
2N5062 100V 800mA SCR 18p.
BX504 Opto Isolator 25p. CA3130 95p.
MC4741CP 50p. 741 22p. 741S 35p. 723 35p. NE555 24p.
2N3773 £1.70. NE556 50p. ZN414 75p. BD238 28p.
BD438 28p. CB4069 15p.
4" Red Led Displays, c.c. or c.a. 95p. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p. BY223 20p.

PROJECT BOXES
Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

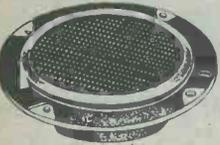MOTOROLA PIEZO CERAMIC TWEETERS
No crossover required



2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

TOOL SALE
Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

HANDY BENCH VICE
1" Jaw opening, £2.95.



Hand drill, double pinion with machine cut gears, 3/16", only £2.75p plus 50p p&p.

MORSE KEYS
Beginners practice key £1.05. All metal full adjustable type. £2.60

F.M. MICROPHONE,
Electret condenser type, tuneable 85-95Mhz. Arrival distance 50 mtrs. (Approx outdoors) Size 163 x 35 mm £10.25. (Not licensable in U.K.).

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS
All 240VAC Primary (postage per transformer is shown after price).
MINIATURE RANGE: 6-0-6V 100mA, Volts 100mA, 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 24 volt 2 Amp £2.45 (54p).


T.V. AERIAL AMPLIFIERS
Wide Band, 240 VAC operated, with two outlets, £7.75

MICROPHONES
Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. F.M. WIRELESS MICROPHONE, 88-108 MHz, Electret type £10.25. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. GRUNDIG electric inserts with FET pre amp, 3-6VDC operation £1.00.

LIGHT DIMMER
240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

C.B. 40 CHANNEL RECEIVER
For car use, operates on 12V DC., £7.95

SPECIAL OFFER TAPE HEAD DEMAGNETIZER

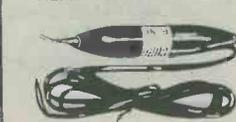

240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p

MULTIMETER BARGAINS




Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50



20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Rec/Sender £3.50 pair.

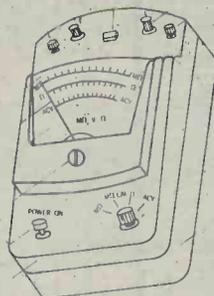TELEPHONE PICK UP COIL
Sucker type with lead and 3.5mm plug 62p.



500V electronic megger, push button operation. Ranges:- LO ohm Range 0 - 100Ω (MW scale 5Ω) 0 - 100MΩ Mid scale (5MΩ) £46.75p

Stabilized power supplies, 240V A.C. input output 13.8 volts at 3/5 amps D.C. £14.75p

TERMS:
Cash with order (Official Orders - welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.
S.A.E. for illustrated lists

MULTI-TESTER



KRT5001 50k/v range doubler multimeter, 0-1kv (125mv LO range) 0-1kv AC, 0-10amp DC, 0-20MΩ res. (LO ohm 0-2k range) 170 x 124 x 50mm £15.50.

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL
Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles. only £2.30.

SWITCHED TYPE PLUGS into 13 amp socket, 3-6-9 volts DC out at 300mA, £2.95. STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

AMPHENOL CONNECTORS
(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with Indicator bulb 95p.

BUZZERS
MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. **LOUD 12VDC BUZZER,** with, metal case. 50mm diam. x 30mm high 63p. **Carters 12 volt Minimit Alarm sirens** £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £4.45

Antex Model CX 17 watt soldering irons, 240VAC £4.45

Antex Model X25 25 watt soldering irons, 240VAC £4.45

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 69p each.
Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. **PUSH SWITCHES,** 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

TEI Mobile SWR metre, with field strength, PL259 connection, £8.35.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F. output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.
ALL ORDERS DESPATCHED BY RETURN POST

SUITABLE FOR
"CITIZEN'S BAND RADIO"

STEEL ENCLOSURES

Direct From Manufacturers

"QUINN TYPE"

Ridged Construction - Stove Enamelled
 Front, Base & Rear one piece (Satin Black)
 Wrap over cover one piece (White Gloss)



ACCESSORIES

Aluminium drop in Chassis (Blank)
 Pivot Bracket "Bright Plated"

TRADE ENQUIRIES WELCOME

Larger Enclosures, Console, Brackets,
 Chassis, Prototype or Production Runs.

"QUINN" TYPE

SIZE IN MM

TYPE	LENGTH	HEIGHT	DEPTH	PRICE	CHASSIS	PIVOT BRACKET
A	120	60	90	£4.85	95p	£1.40
B	200	60	90	£5.70	£1.30	£1.90
C	180	100	150	£8.50	£2.95	£2.30
D	250	100	150	£12.60	£3.65	£2.85

POST AND PACKAGE £1.00.

JAMES ENGINEERING

(Phillips-James Engineering (North East) Ltd.)

Precision sheet metal and press work
 Phone: Chester-le-Street 883230

Registered Office and Works:

Unit 4, Stella Gill Industrial Estate, Pelton Fell,
 Chester-le-Street Co. Durham DH2 2RG.

PLEASE SUPPLY "QUINN TYPE" ENCL.

TYPE	ENCLOSURE	QTY	CHASSIS	QTY	PIVOT BRACKET	QTY
A						
B						
C						
D						

TICK REQUIREMENTS

I ENCLOSE CHEQUE/PO

NAME

ADDRESS

.....

.....

BLOCK LETTERS PLEASE.

**LATEST
 BOUND VOLUME
 No. 33**

of

**"Radio & Electronics
 Constructor"**



SEPTEMBER 1979 to AUGUST 1980

Comprising
 752 pages
 inc. index

PRICED £6.20 P&P £1.50

**BOUND VOLUME No. 27
 (August 1973 to July 1974)
 Price £3.00 P&P £1.50**

**BOUND VOLUME No. 28
 (August 1974 to July 1975)
 Price £3.20 P&P £1.50**

**BOUND VOLUME No. 29
 (August 1975 to July 1976)
 Price £3.50 P&P £1.50**

**BOUND VOLUME No. 30
 (August 1976 to July 1977)
 Price £3.70 P&P £1.50**

**BOUND VOLUME No. 31
 (August 1977 to August 1978)
 Price £5.20 P&P £1.50**

**BOUND VOLUME No. 32
 (September 1978 to August 1979)
 Price £5.20 P&P £1.50**

Limited number of these
 volumes still available.

We regret all earlier volumes are now
 completely sold out.


Available only from

**DATA PUBLICATIONS LTD.,
 57, MAIDA VALE, LONDON, W9 1SN**

RX 80 MkII - A DIY SOLID-STATE-OF-THE-ART MODULAR DUAL CONVERSION RECEIVER SYSTEM FOR THE ENTHUSIAST

• AS DESCRIBED IN JAN/FEB/MAR 81 RADCOM BY TONY BAILEY-G3WPO : REPRINTS £1 inc

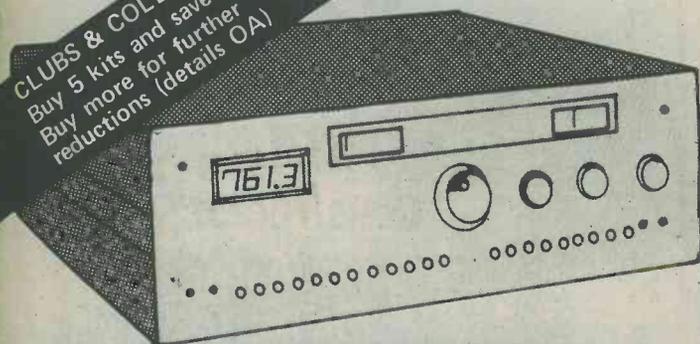CLUBS & COLLEGES:
Buy 5 kits and save 10%
Buy more for further
reductions (details OA)



- ★ LOW DRIFT VARICAP TUNING (READILY ADAPTABLE FOR SYNTHESISED/ HUFF&PUFF STABILIZATION)
- ★ DUAL CONVERSION BASED ON A 3.4 MHz SSB IF, WITH MECHANICAL IF FILTER, AUDIO DERIVED AGC, BALANCED MIXER, WITH ON-BOARD AF AMP AND VOLTAGE REGULATOR
- ★ CAPACITY FOR UP TO 12 HF/VHF/UHF 1 MHz WIDE CRYSTAL CONTROLLED CONVERTERS WITH TRACKED RF TUNING
- ★ EACH CONVERTER SELF CONTAINED - SO MORE CAN BE USED EXTERNALLY IF REQUIRED. RF PATHS ARE DC SWITCHED AT LOW IMPEDANCE

PRICES

RX 80 Mk. II tuneable 3.4MHz SSB receiver/IF with MFL series	..£42.66
2.4kHz mechanical SSB IF filter	..£32.42
A/A but with low cost 4kHz CFM2 series filter	..£9.10 ea
HF Converters, including crystal for the following bands: 1-2MHz, 7-8MHz, 10-11MHz, 14-15MHz, 18-19MHz, 21-22MHz 24-25MHz, 28-29MHz, 29-30MHz	..£25.00
Hardware: Case, meters, pots, knobs (exc. DFM)	..£132.50
Complete RX 80, 6 converters, switches, case, PSU	

CURRENT OPTIONS INCLUDE

★ LCD DFM with built in IF offset, interface PCB	..£23.75
★ HUFF/PUFF vfo stabilizer	..£9.60
★ NBFM adapter inc 8kHz multielement ceramic IF filter	..£9.95
★ Constant Z PIN diode attenuator	..£4.95
★ 12v low RF noise mains PSU	..£7.95

PLANNED ADDITIONS TO THE SYSTEM

- 3.4MHz IF frequency synthesiser
- 'UP Conversion' front end system
- AM IF adapter ■ Noise blanker
- VHF/UHF converters with helical filters



PRICES EXCLUDE VAT (15%). Postage 50p on orders under £12. Free postage on orders over £12, except please note any order including HARDWARE should be accompanied with a £2 carriage charge. General price lists are available FOC with an SAE - full AMBIT catalogues including a multitude of radio parts/components £1.80 a set - or 70p per section.

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

AMBIT international 200 North Service Road, Brentwood, Essex

The beginning of the
WORLD
is nigh

TRANSISTORS

*NPN, otherwise PNP

*AC122 30v.2w 12p
*AC126 30v.2w 12p
*AC128 36v.1wt 5p
*AC153 32v.1wt 11p
*AC176 32v.7w 11p
*AC179 20v.1.1w 40p
*AC185 25v.1w 10p
*AC210 40v.3w 30p
*AC212 40v.3w 30p
*AC218 20v.2w 22p
*AD161 20v.6wt 40p
*AD162 20v.6wt 40p
*AD164 25v.6w 40p
*AD165 25v.6w 40p
*AF119 30v.2w 35p
*AF124 32v.1w 27p
*AF126 32v.1w 27p
*AF127 32v.1w 27p
*AF139 22v.1w 23p
*AF178 25v.1w 35p
*AF180 25v.1w 35p
*AF181 30v.16w 33p
*AF239 20v.1w 35p
*AL120 50v.5w 37p
*ASV60 35p
*ASV63 26v.1w 4p
*ASV73 30v.15w 35p
*ASZ21 20v.12w 4p
*AU107 200v.30w £1.55
*AU110 160v.30w £1.43
*AU113 250v.30w £1.03

BC107A/B 7p
BC108/A/B/C 7p
BC109/B 30v.3w 7p
BC109C 30v.3w 7p
BC125 50v.3w 4p
BC125B 60v.3w 4p
BC129A/B 50v.2w 7p
BC130A/C 25v.2w 7p
BC131C 25v.2w 7p
BC139 40v.7w 11p
BC140 40v.7w 11p
BC141 60v.7w 11p
BC143 60v.8w 11p
BC147/A/B/C 5p
BC148/A/B/C 5p
BC149/A/B/C 5p
BC154 40v.2w 7p
BC157/A/50v.4w 5p
BC158/A/B 5p
BC159/B/C 5p
BC160/10 40v.3.2w 12p
BC168B 20v.3w 7p
BC171B 45v.3w 4p
BC172 25v.3w 6p
BC172C 25v.3w 6p
BC173 25v.3w 7p
BC177A 45v.4w 10p
BC178A/B/C 10p
BC179B 20v.3w 14p
BC182/AL 50v.3w 5p
BC183A/AL/LC 3p
BC184 45v.3w 5p
BC186 40v.3w 21p
BC187 30v.3w 8p
BC196A 30v.50mW 100 for £3.65p
BC197A 50v.50mW 4p
BC198B 30v.50mW 100 for £3.65p
BC199B 30v.50mW 100 for £3.65p
BC200 50v.3w 11p
BC212B 50v.3w 5p
BC213L 45v.3w 5p
BC213LA 45v.3w 3p
BC213LB 45v.3w 4p
BC214B 45v.3w 5p
BC237A 45v.3w 7p
BC237B 60v.3w 7p
BC238 20v.3w 5p
BC238B/C 7p
BC239C 20v.3w 7p
BC251 45v.3w 3p
BC257B 45v.3w 7p
BC258B/C 7p
BC259C 20v.3w 7p
BC301 90v.3w 15p
BC302 80v.3w 15p
BC304 80v.3w 15p
BC307 45v.3w 15p
BC308B/C 25v.3w 7p
BC309B 20v.3w 7p
BC327 45v.7w 5p
BC328 25v.7w 6p
BC329 45v.7w 6p
BC338 25v.7w 5p
BC382L 50v.3w 7p
BC384B 45v.3w 7p
BC546 80v.6w 5p
BC547/A/B 45v 5p
BC548/A/B/C 5p
BC549C 30v.5w 5p
BC556 80v.5w 5p
BC557/B 5p
BC558A 30v.5w 5p
BC559 30v.5w 5p

*BC612L 75v.3w 4p
*BCX32 80v.8w 80p
*BCX33 80v.75w 10p
*BCX34 40v.8w 10p
*BCX36 60v.1.5w 10p
*BCY11 60v.5w 28p
*BCY31 64v.6w 5p
*BCY56 45v.3w 10p
*BCY70 50v.35v 9p
*BCY71 45v.35v 9p
*BCY72 25v.3w 9p
*BCY78 45v.3w 15p
*BCZ11 25v.25v 32p
*BD113 60v.15w 57p
*BD115 250v.6w 35p
*BD116 80v.10w 35p
*BD131 45v.15w 15p
*BD132 45v.15w 15p
*BD133 90v.15w 28p
*BD135 45v.13w 22p
*BD136 45v.13w 22p
*BD137 60v.8w 28p
*BD138 60v.8w 28p
*BD137/8 mitch pr

*BD139 80v.12w 30p
*BD140 80v.8w 26p
*BD142 50v.117w 35p
*BD156 70v.25v 50p
*BD182 70v.117w 44p
*BD201 45v.60w 86p
*BD203 60v.60w 86p
*BD232 500v.15w 86p
*BD233 45v.25v 25p
*BD235 60v.25v 35p
*BD238 80v.25v 25p
*BD239C 115v.30w

*BD240 55v.30w 30p
*BD240B 90v.30w 36p
*BD240C 115v.30w

*BD241 45v.40w 39p
*BD242B 90v.40w 30p
*BD243 55v.65w 32p
*BD244 90v.65w 43p
*BD244C 115v.65w

*BD246 55v.80w 32p
*BD253 35v.50w 44p
*BD277 45v.70w 37p
*BD375 50v.25v 35p
*BD437 45v.36v 36p
*BD438 45v.36v 28p
*BD597 60v.55v 36p
*BD677 60v.40w 50p
*BD678 Pwr. Darl.

*BD678 60v.40w 50p
*BD678A 88v.20w 44p
*BD678B 88v.20w 44p
*BDX42 60v.3w 36p
*BDX77 80v.60w 50p
*BDY20 60v.117w 86p
*BF115 50v.2w 18p
*BF137 160v.7w 11p
*BF167 30v.15w 18p
*BF173 25v.2w 18p
*BF178 185v.6w 23p
*BF179 250v.6w 23p
*BF180 30v.2w 12p
*BF181 30v.2w 8p
*BF182 25v.12w 18p
*BF183 25v.12w 18p
*BF184 20v.15w 18p
*BF185 20v.15w 18p
*BF194A/B 5p
*BF194B 5p
*BF195C/D 5p
*BF196 40v.25w 5p
*BF197 40v.3w 5p
*BF198 30v.3w 5p
*BF200 30v.2w 13p
*BF224 45v.36w 4p
*BF244C FET 30v 7p
*BF245 FET 6p
*BF254 30v.3w 12p
*BF256FET 8p
*BF266B/LC/FET 6p
*BF287 160v.5w 20p
*BF259 see 2N5058

*BF262 30v.12w 29p
*BF263 30v.12w 29p
*BF274 25v.12w 8p
*BF324 30v.3w 3p
*BF336 185v.3w 16p
*BF355 300v.3w 15p
*BF394B 3p
*BF451 40v.3w 6p
*BF494 20v.3w 10p
*BF494B 20v.3w 10p
*BF495 20v.3w 5p
*BF595C 30v.25v 9p
*BF615 27p
*BF617 27p
*BFQ35 15p
*BFQ37 15p
*BFQ37A 12v.2w 61p
*BFQ38 40v.2w 68p
*BFQ39 120v.8w 19p
*BFS21 FET pair 13p
*BFS28 Dual M/Fet

*BFT30 70v.36w 15p
*BFT31 60v.36w 15p
*BFT39 90v.8w 15p
*BFT41 60v.8w 15p
*BFT60 80v.8w 6p
*BFT71 60v.8w 15p
*BFT70 70v.36w 15p
*BFT71 60v.8w 15p
*BFW10 FET 30v 46p
*BFW11 FET 30v 46p
*BFW30 20v.25w 15p

*BFW31 50v.5w 15p
*BFW57 80v.5w 18p
*BFW58 80v.5w 18p
*BFX12 20v.3w 23p
*BFX29 60v.6w 11p
*BFX30 60v.6w 16p
*BFX37 60v.4w 20p
*BFX84 100v.8w 20p
*BFX85 100v.8w 14p
*BFX88 40v.6w 20p
*BFX89 30v.2w 20p
*BFY39 45v.3w 20p
*BFY50 35v.1wt 15p
*BFY51 60v.1w 15p
*BFY52 40v.1w 15p
*BFY75 30v.35w 15p
*BFY90 30v.2w 59p
*BLY10 100v.115w

BR101 Prog. 20p
BRY39 Uni- 29p
BRY56 Junct 29p
BSV60 45v.8w 30p
BSV64 100v.1w 36p
BSV79 40v.4w 50p
BSV80 40v FET 50p
BSV81 Dep. Mos Fet

BSX19 40v.4w 75p
BSX20 40v.4w 7p
BSX21 120v.3w 10p
BSX78 40v.3w 8p
BSY40 25v.3w 30p
BSY95A 20v.3w 60p
BU105 1k5v 10w 14p
BU105/04 78p
BU204 1k3v 10w 75p
C1544 4p
C1601 4p
D40C4 40v.8wt 22p
D40D1 45v.7wt 22p
D40D2 45v.7wt 15p
D40D4 60v.7wt 22p
D4102 45v.7wt 22p
D43C7 70v.13wt 30p
D43C8 50v.13wt 30p
D43C9 40v.30w 50p
D45C2 40v.30w 50p
D20HF 50MHz 50p
DS70 Darl. 10wt 22p
GET102 30v.2w 46p
GET111 60v.2w 45p
GET120 30v.44w

*M103G MOSFET 30p
*MA393 32v.5w 25p
*MD7000 30v.7w dual 52p
*ME2 15v.1w 13p
*ME0412 60v.2w 14p
*ME0461 60v.3w 7p
*ME6101 70v.36w

*ME102 60v.4w 7p
*ME8003 80v.4w 20p
*MJ481 60v.9w 25p
*MJE370 30v.25w 32p
*MJE371 40v.40w 40p
*MJE201T IHigain 80p
*Mn15 Russian 25p
*Mn41 Russian 25p
*MP8113 60v.3w 25p
*MPF131 Dual 8p
*MOSFET 21p
*MPS 8513 60v.3w 31p
*MPSA13 30v.31w 21p
*MPU131 Prog. Uni J 15p
*MRF502 Improved 90p
*BFY60 100v.100w 40p
*MST 1027 80v 100w 40p
*MST1072 300v 100W 50p
*MST2007 4p
*MST2013 4p
*MST2015 4p
*MST2018 4p
n 16A Russian 25p
n 12A Russian: 25p
*NKT45 10v.1w 20p
*NKT85 10v.1w 30p
*NKT152 6v.1w 38p
*NKT153 32v.1.6w 24p
*NKT154 6v.1w 26p
*NKT251 30v.2w 18p
*NKTME2 15v.1w 13p
NSD102 45v 10wt 23p
NSD104 80v 10wt 26p
NSD129 250v 10wt 23p
NSD131 250v 10wt 30p
NSD132 250v 10wt 30p
NSD134 300v 10wt 30p
NSD151 30v 10wt 22p
Darlington 22p

NSD457 160v 10wt 23p
NSD U45 40v 10wt 30p
*NSD U51 30v 10wt 22p
*NSD U55 60v 10w 25p
*OC23 55v 16w 53p
*OC28 80v 30w 78p
*OC41 16v.1w 4p
*OC42 16v.1w 21p
*OC43 15v.1w 55p
*OC44 15v.1w 4p
*OC45 15v.1w 13p
*OC71 30v.2w 4p
*OC72 32v.2w 4p
*OC76 32v.13w 15p
*OC77 60v.13w 46p
*OC81 32v.8w 5p
*OC84 32v.6w 30p
*OC200 30v.25w 41p
*OC201 25v.25w 66p
*OC202 15v.25w 66p
*OC603 22v.1w 50p
*OC701 80v.35w 50p
ON222 23p
P77 Plastic 10wt 15p
P346A 30v.6w 24p
P7029 20p
*PXB103 30v.15w 25p
R1039 (2008B) 54p
R2008B 660v 85w 25v.2w 4p
R20302 140v.8w 4p
R20108 £1.18
*R2306 100v.40w 26p
R2540 £1.70
RCA467 Pwr. Darl. 22p
RCF701A/B/D 10wt 30p
RCF703 80v.10w 30p
*S3017 25p
*SB240 26p
*SFT357 20v.12w 26p
*SL102 26p
TE886 4p
TIP29 40v.30w 22p
TIP30 40v.30w 22p
TIP30C 100v.30w 26p
TIP31C 100v.40w 26p
TIP32A 60v.40w 22p
TIP32C 100v.40w 26p
TIP41 40v.65w 26p
TIP42C 100v.65w 15p
TIP48 300v.40w 33p
TIP110 60v.50w 45p
TIP112 100v.50w 45p
TIP115 60v.50w 45p
Darlington 30p
TIP2955 100v.90w 45p
TIP3055 100v.90w 34p
TIS44 25v.25w 9p
TIS60GY 40v.3w 3p
TIS61 40v.3w 3p
TIS73L FET .7p
TIS90 40v.65w 4p
TIS91 40v.65w 6p
TIS92GY 40v.65w 5p
TIS98 30v.25w 14p
TK24 30v.2w 20p
U14710 20p
V435 30v.6w 20p
ZT430 30v.3w 30p
ZT1486 110v.25w £1.10
MRF502 90p
ZTX341 100v.3w 9p
*G2103 15v.3w 33p
*G2102 20v.3w 32p
*G2309 20v.3w 30p
*G239A 30v.1.5w 20p
*G2G371 20v.2w 18p
*N2388 25v.15w 7p
*N256A 40v.90w 71p
*N2525 45v.3w 12p
*N2527 45v.25w 16p
*N2597 45v.25w 16p
*N2598 35v.25w 16p
*N2601 35v.75w 16p
*N2644 30v.15w 22p
*N2698 120v.8w 12p
*N2699 120v.6w 12p
*N2706/A 25v.3w 10p
N2708 40v.4w 9p
N2718 60v.4w 9p
N2720A 120v.5w 10p
N2736 80v.5w 7p
N2914 40v.4w 15p
N2918 15v.2w 12p
N2929 25v.3w 16p
N2930 45v.3w 7p
*N2984 15v.1w 28p
*N2987 40v.1w 16p
*N21091 25v.2w 16p
*N21132 50v.6w 14p
*N21302 25v.2w 16p
*N21303 30v.2w 16p
*N21395 40v.15w 25p

2N1484 100v.25w 36p
2N1485 60v.25w 36p
2N1487 60v.70w 90p
2N1490 100v.70w £3
2N1500 15v.1w 30p
2N1507 60v.6w 18p
2N1711 75v.8w 13p
2N1716 90v.15w 15p
2N1724A 118wt Rf 180v
2N1748 30v.2w £2.10
2N192A 60v.8w 28p
2N2221A 40v.5w 9p
2N2222A 40v.5w 8p
2N2369 40v.4w 10p
*2N2401 7p
*2N2412 25v.3w 27p
2N2483 60v.36w 28p
2N2484 60v.4w 15p
2N2586 60v.3w 10p
*2N2614 32v.9w 41p
2N2887 £2
*2N2894 12v.36w 11p
*2N2904 60v.6w 9p
*2N2906 60v.4w 9p
*2N2907/A 60v.4w 9p
2N2926Y 25v.2w 4p
2N2926 25v.2w 4p
2N3020 140v.8w 4p
2N3055 100v.115w 38p
2N3055RCA 100v.115wt 68p
2N3133 50v.6w 24p
2N3235 55v.117w 38p
*2N3283 25v.1w 25p
2N3375 65v.12wrf £3
2N3418 85v.1wt 15p
2N3442 160v.117w 75p
2N3583 250v.35w 18p
*2N3645 60v.3w 3p
2N3663 30v.2w 6p
*2N3702 40v.4w 4p
*2N3703 50v.4w 3p
*2N3704 50v.4w 4p
*2N3707 30v.3w 4p
*2N3711 30v.3w 8p
*2N3714 80v.150w 54p
*2N3792 80v.150w 33p
2N3794 75v.5w 14p
*2N3799 90v.36w 40p
18p
2N3823 FET 30v 25p
2N3878 120v.35w 45p
2N3904 60v.3w 7p
*2N3905 40v.3w 7p
*2N3908 40v.3w 8p
2N4000 100v.15w 15p
*2N4026 60v.5w 15p
2N4031 80v.1w 15p
2N4039 MOSFET 54p
*2N4285 5p
*2N4403 40v.3w 7p
2N4693 FET 30p
*2N4898 40v.25w 37p
*2N4900 60v.25w 37p
*2N4918 40v.3w 15p
*2N5037 70v.83w 52p
2N5058 300v.5w 11p
*2N5147 100v.7w 15p
2N5163 Fet 25v 21p

2N5191 60v.40w 40p
2N5293 80v.36w 30p
2N5294 80v.36w 30p
2N5295 60v.36w 30p
2N5296 60v.36w 30p
2N5297 80v.36w 30p
2N5298 80v.36w 30p
2N5449 30v.3w 3p
2N5484 30v FET 37p
2N5492 75v.50w 36p
2N5915 (16068) 12v
450MHz 6WT R.F. £2.50

2N6028 PUJT 6p
2N6103 45v.7w 45p
*2N6106 80v.40w 44p
*2N6109 60v.40w 44p
*2N6111 40v.40w 36p
*2N6124 45v.40w 24p
*2N6178 100v.25w 30p
*2N6180 100v.25w 30p
*2N6181 75v.25w 30p
2N6288 30v.4w 36p
2N6290 60v.40w 36p
2N6292 80v.40w 36p
2N6387 60v.40w 55p
2N6486 40v.75w 36p
2N6488 90v.75w 36p
ZS701 30v.5w 18p
*ZS712 16v.1w 42p
*ZS750 18v.1w 36p
*ZS780 20v.1w 36p
*ZS783 25v.1w 36p
*ZS784 25v.1w 36p
*ZS785 25v.1w 36p
*ZS787 25v.1w 25p
*ZS788 25v.1w 25p
*ZS789 25v.1w 25p
*ZS8136 25v.15w 25p
*ZS8156 16v.15w 25p
*ZS8175 30v.15w 60p
*ZS8176 32v.15w 20p
*ZS8457 20v.15w 25p
2SC1061 50v.25w 50p
2SD234 60v.25w 50p
2SD315D 200v 80p
353-3 40v.5wt 22p
362-4 300v.6wt/A Video Amp (BF459) 30p
868-01 Plast. 10wt 15p
1034 Plast. 10wt 15p
16120 (MPSU55/ D238) 19p
40235 40v.5w 50p
40250 50v.30w 36p
40250V1 (2N3054 + Ht. sink) 40p
40316 40v.5w 36p
40372 (2N3054 + Ht. sink) 40p
40349v2 160v.1w 40p
40394 60v.1w 30p
40409 90v.3w 32p
40633 40w 36p
40874 80v.40w 38p
40911 (2N6261 + Ht. sink) 40p

ONE TON OF POWER
Sack fulls of ex-equipment metal power devices. Mainly to 3 transistor, some TO66, some stud rectifiers 1 S.C.R.'s. From a bankrupt distributor who cleaned them up for industry. All marked. No duds found in a random test.
Lucky dip 10 for £7.75

22 pin I.C. Socket
Low Profile
Tube of 15
£1.70

2N3055RCA 100v.115wt 68p
2N3133 50v.6w 24p
2N3235 55v.117w 38p
*2N3283 25v.1w 25p
2N3375 65v.12wrf £3
2N3418 85v.1wt 15p
2N3442 160v.117w 75p
2N3583 250v.35w 18p
*2N3645 60v.3w 3p
2N3663 30v.2w 6p
*2N3702 40v.4w 4p
*2N3703 50v.4w 3p
*2N3704 50v.4w 4p
*2N3707 30v.3w 4p
*2N3711 30v.3w 8p
*2N3714 80v.150w 54p
*2N3792 80v.150w 33p
2N3794 75v.5w 14p
*2N3799 90v.36w 40p
18p
2N3823 FET 30v 25p
2N3878 120v.35w 45p
2N3904 60v.3w 7p
*2N3905 40v.3w 7p
*2N3908 40v.3w 8p
2N4000 100v.15w 15p
*2N4026 60v.5w 15p
2N4031 80v.1w 15p
2N4039 MOSFET 54p
*2N4285 5p
*2N4403 40v.3w 7p
2N4693 FET 30p
*2N4898 40v.25w 37p
*2N4900 60v.25w 37p
*2N4918 40v.3w 15p
*2N5037 70v.83w 52p
2N5058 300v.5w 11p
*2N5147 100v.7w 15p
2N5163 Fet 25v 21p

2N6028 PUJT 6p
2N6103 45v.7w 45p
*2N6106 80v.40w 44p
*2N6109 60v.40w 44p
*2N6111 40v.40w 36p
*2N6124 45v.40w 24p
*2N6178 100v.25w 30p
*2N6180 100v.25w 30p
*2N6181 75v.25w 30p
2N6288 30v.4w 36p
2N6290 60v.40w 36p
2N6292 80v.40w 36p
2N6387 60v.40w 55p
2N6486 40v.75w 36p
2N6488 90v.75w 36p
ZS701 30v.5w 18p
*ZS712 16v.1w 42p
*ZS750 18v.1w 36p
*ZS780 20v.1w 36p
*ZS783 25v.1w 36p
*ZS784 25v.1w 36p
*ZS785 25v.1w 36p
*ZS787 25v.1w 25p
*ZS788 25v.1w 25p
*ZS789 25v.1w 25p
*ZS8136 25v.15w 25p
*ZS8156 16v.15w 25p
*ZS8175 30v.15w 60p
*ZS8176 32v.15w 20p
*ZS8457 20v.15w 25p
2SC1061 50v.25w 50p
2SD234 60v.25w 50p
2SD315D 200v 80p
353-3 40v.5wt 22p
362-4 300v.6wt/A Video Amp (BF459) 30p
868-01 Plast. 10wt 15p
1034 Plast. 10wt 15p
16120 (MPSU55/ D238) 19p
40235 40v.5w 50p
40250 50v.30w 36p
40250V1 (2N3054 + Ht. sink) 40p
40316 40v.5w 36p
40372 (2N3054 + Ht. sink) 40p
40349v2

VAT & POST PAID
(UK 2nd Class or Parcel) Just include stamped addressed envelope
MINIMUM ORDER FIVE POUNDS. OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS

UK - Postal Orders for prompt service. Cheques require 9 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) prompt service. Foreign currency not accepted. VAT content becomes documentation charge. Add additional postage for overseas mail.

PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE
ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

OPTO ELECTRONICS
Photo Diodes: 30F2, 31F2, 32F2, 33F2, BPX40, BPY10, BPY68, BPY69, BPY77, CQY17, CQY77. All types 38p
Wire and neons 5p.
Photo transistor: BPX43, BP103, 2N5777, Darlington 36p; LED's (Mullard Siemens) Red 5mm 8p, 3mm 13p; Green 5mm 13p, 3mm 13p; Yellow 5mm 13p, 3mm 13p, micro LD481 8p
PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp 36p
CA3062 Photo Detector and power amp. £1.05p

7 SEGMENT L.E.D. DISPLAYS
.3" Red com. anode 81p
.6" Green C.A. £1.77
5082-7650 Red com. anode.
5082-7653 Red com. cath
5082-7600 Yellow com. anode.
H.P. Highbrilliance .43" 72p

HEWLETT PACKARD MULTIPLEXED .11" 7 SEGMENT LED DISPLAYS
3 Digit HP5082 7413 45p
4 Digit HP 5082 7414 45p
5 Digit HP 5082 7415 45p
Infra red transmit diodes CQY11B or LD271 High power 1.6-2v or 3-3.5v Pulse 32p
LD242 36p
H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
CNY17/1 opto coupler 70p
Cold cathode tubes I.T.T. G517A or 5870L 60p

SPECIAL OFFER
IN4004 or IN4006 Sealed manufacturers carton of 300. £6.85

Nuts, Bolts, Washers, Screws, Self Tappers, Spacers etc.
1kg. for £2.66p

MONO XTAL CARTRIDGE STEREO COMPATIBLE
E.R. compat X 2 £1.20p
Carrier 15p

STEREO XTAL CARTRIDGE
Garrard GCS23 £1.30p
Carrier 15p

MONO CERAMIC CARTRIDGE STEREO COMPATIBLE
Garrard GKM24T £1.20p
Carrier 15p
GKM24 + spacer £1.20p

TINNED COPPER WIRE
0.5mm/25 SWG 1KG £2.60p
24 SWG 200 GRM 95p

DIODES
*AA118 90v 50ma 4p
*AA119 30v 35ma 7p
*AA133 100v 50ma 9p
*AA144 100v 5ma 4p
*AAZ15 100v 250ma 15p
*AAZ17 50v 40ma 5p
*BA101B varicap 10p
BA116 20v 100ma 30p
BA127 60v 100ma 3p
BA128 50v 100ma 21p
BA145 350v 500ma 21p
BA148 350v 500ma 12p
BA182 Varicap 6p
BAX 13 50v 150ma 3p
BAX14 40v 350ma 21p
BAX20 25v 115ma 3p
BAX21 50v 120ma 3p
BAX22 100v 120ma 3p
BAX54 8p
BAY36P 30v 3ma 21p
BAY44 50v 250ma 4p
BAY68 25v 115ma 3p
BAY72 100v 400ma 4p
BB103 Varicap 24p
BB104 Varicap 16p
BB109 Varicap 24p
BB110B Varicap 24p
BB113 3x Varicap 43p
BB139 varicap £1
BR100 Diac. 15p
BY206 350v 600ma 71p
BY207 600v 600ma 23p
BY402 100v 1A 21p
BY403 200v 1A 21p
Centercell 3p
CG651 9p
CR HG/3 10p
CSD117V LZ 40p
CV7095 21p
CV7098 21p
D3202Y Diac. 11p
DC2845 Microwave 20p
DOG53 11p

*Germanium: rest silicon
FSY28A 40p
*HG1005 100v 45ma 3p
*HG1012 50v 50ma 10p
*MPN3401 VHF switch 30p
*OA5 100v 115ma 5p
*OA7 25v 50ma 25p
*OA10 25v 110ma 25p
*OA40 40v 50ma 4p
*OA47 30v 150ma 7p
*OA51 50v 50ma 4p
*OA70 22v 50ma 10p
*OA75 40v 50ma 11p
*OA79 45v 35ma 11p
*OA81 115v 150ma 31p
*OA90 30v 45ma 4p
*OA91 115v 150ma 6p
*OA95 115v 150ma 6p
*OA200 50v 250ma 21p
*IN63 100v 40ma 4p
*IN337 200v 200ma 4p
*IN447 40v 25ma 3p
*IN604 400v 300ma 4p
*IN662 80v 40ma 21p
*IN914 75v 225ma 11p
*IN916 100v 300ma 21p
*IN3062 75v 20ma 3p
*IN3063 (BAV10) 6p
*IN3064 75v 10ma 21p
*IN4009 25v 75ma 24p
*IN4148 100v 200ma 11p
*IN4149 100v 200ma 3p
*IN4150 50v 200ma 21p
*IN4151 50v 200ma 21p
*IN4152 40v 200ma 3p
*IN4446 100v 200ma 21p
*IN4449 100v 200ma 21p
*IN5154 25v 30ma 3p
*IN5456 Varicap 15p
*IS22 150v 200ma 4p
*IS940 30v 50ma 3p
5082 2900 RF Schotky Barrier 50p

RECTIFIERS

Type	Volt	Amp	Price
BY126	650	1	5p
BY127	1250	1	5p
BY212	15kv	500ma	6p
BY235	600	1 1/2	7 1/2p
BY236	900	1 1/2	7 1/2p
BY264	300	3	9p
BY265	600	3	11 1/2p
BY266	900	3	15n
BY275	600	5	19 1/2p
BY277	1200	5	27p
BY1202	2kv	10mA	6p
BYW55	800	2 (Oxide bead)	15p
BYW56	1000	2 (Oxide bead)	18p
BYX20-200	200	25	72p
BYX22-200	300	11	25p
BYX38 300R	300	6	48p
BYX38 600	600	6	52p
BYX38 900	900	6	60p
BYX38 1200	1200	6	65p
BYX42 300	300	12	36p
BYX42 600	600	12	46p
BYX42 900	900	12	49p
BYX42 1200	1200	12	51p
BYX46 300R	300	15	£1.07
BYX46 400R	400	15	£1.19
BYX46 500R	500	15	£1.75
BYX46 600	600	15	£2.00
BYX46 900	900	15	£2.30
BYX48 300R	300	6	47p
BYX48 600	600	6	60p
BYX48 900	900	6	70p
BYX48 1200R	1200	6	92p
BYX49 300R	300	6	35p
BYX49 600	600	6	42p
BYX49 900R	900	6	47p
BYX49 1200	1200	6	60p
BYX52 300	300	48	£2.05
BYX52 1200	1200	48	£2.90
BYX70	600	4	4p
BYX72 150R	150	10	42p
BYX72 300R	300	10	52p
BYX72 500R	500	10	65p
BYX94	1250	1	6a
DD3026	400	2 1/2	10p
E250C50	250	3	15p
KS11394	800	3	14p
LT102	30	2	23p
M1	68	1	5p
MR856	800	3	24p
MSR5	800	3	12p
OA210	400	5	33p
RAS3 10AF	1250	11 (Avalanche)	48p
RAS508AF	1250	11 (Avalanche)	50p
REC53A	1250	11	Pack of 4 66p
SKF4G	200	6	25p
SR100	100	11	9p
SR400	400	11	10p
SR1825	100	50	75p
IN3254	400	1	4p
IN4002	100	1	4p
IN4004	400	1	4p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5401	100	3	12 1/2p
IN5402	200	3	11p
IN5406	600	3	15p
IN5408	1000	3	19p
IS027	800	1 1/2	11p
IS138	800	1	21p
25G100	100	60	£4.35
3052	200	2	11p
16094P	900	2	15p
16492	700	1 1/2	9p

BRIDGE RECTIFIERS

Amp	60VOLT	B30C350	23p	
1	1600	BYX10	34p	
0.6	100	EC433	20p	
1	100V	B40C800	12p	
1	140	USH01-200	25p	
1	400V	MDA104	29p	
1 1/2	50V	W005	27p	
1 1/2	75V	IBIBY234	11 1/2p	
1 1/2	150V	IBIBY235	15p	
1 1/2	200V	W02 Ex Equip	15p	
1 1/2	400V	W04	28p	
1 1/2	400V	UE4R1	12p	
1 1/2	800V	W08	27p	
1 1/2	1000	W10	36p	
2 1/2	100	I.R.	40p	
2 1/2	350V	9F2	53p	
3	500V	9E4	85p	
3	50	KBS005	30p	
3	100	KBS01	30p	
3	200	KBS02	30p	
3	400	KBS04	30p	
3 1/2	100	B40C 3200	39p	
5	400	Texas	85p	
	Miniature	Meter	Type	34p

THYRISTORS

Amp	Volt	THYRISTORS	Price
0.8	200	2N5064	19p
1	240	BTX18-200	35p
1	240	BTX30-200	35p
1	400	BTX18-300	41p
1	700	BT 106	70p
2	400	S2710D with heatsink	40p
3	600	T3N06C00	53p
3	100	T3N1C00	36p
4	50	S107F Sensitive Gate	36p
4	50	S2060F Sensitive Gate	36p
4	400	S2060D	36p
4	400	S2061D Sensitive Gate	38p
4	500	40506 with heatsink	58p
4	500	17083	36p
4	600	C106M Sensitive Gate	37p
4	600	N23228	36p
4	600	GAK	36p
5	400	S5800D/R	36p
5	500	17047A	40p
5	600	17058	44p
5	600	S5800M	44p
5	600	BT121	70p
6	100	SCR 6/100	33p
6.5	500	BT107	£1
6.5	500	BT109/SCR957	71p
7	400	S2620D	45p
7	600	S2620M	45p
8	100	S2800A	36p
8	600	S122M	54p
12	1000	CR121103-RB	£8
15	800	BTX95-800 Pulse Modulated	£1
16	400	2N6403	82p
20	600	BTW92-600RM	£3.40
75	800	71CG80	£6
110	20	72RC2A	£3
150	1000	151RA100	£10
150	1200	151RA120	£11

ZENER DIODES

4/500MW. BZY88, BZX97, etc. 51p
2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.
BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode 12p
1.3/1.5WT BZX61, BZY97, etc. 11p
3v. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 12v. 15v. 18v. 20v. 27v. 33v.
2.5WT BZX70, etc. 13p
3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p) 20v. 22v. 26v.
5WT BZV40, etc. 15p
3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 20v. 33v. 68v. 120v.
10WT Z5D, ZX, IS50, etc. 23p
4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 10v. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 43v. 51v. 56v. 62v. 68v. 75v. 150v.
15WT BZV15C 12R 12volt 37p
20WT BZY93, etc. 44p

TEMPERATURE COMPENSATED REFERENCE
IN935B, IN936B, IN937B 9volt
IN941B, IN942B, IN943B 11.7volt

MY CATALOGUE (75p + 25p post/pack) OFFERS AT VERY LOW PRICES, THE FOLLOWING:

CAPACITORS - ELECTROLYTIC; CAN, WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR PAPER BLOCK, CAN POLY, MICA, CERAMIC LOW AND HIGH VOLTAGE, RESISTORS 1/2 WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS, FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS... SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTARY AND SLIDE, DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLI, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS AND OTHERS.

BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS
Cut out and keep these 3 pages. Over the months they will bring to you some of the 6,000 items stocked.

INTEGRATED CIRCUITS

326 HINIL 2, 2, 3, 3, Input Nand	20p	74174 Hex D/F/F and clear	55p	CD4049 Hex Inverter Buffers	36p	ML2378 (6108) 6 channel tuner	£1
332 Hex inverter, HINIL	11p	74S174 Hex D Flip Flop + clear	72p	CD4050 Hex Buffer converter	38p	MM5262 PMOS 2048 x 1 Dyn. RAM	80p
343 4 bit comparator	5p	74176/8280 Pre-set 35MHz Decode	30p	CD4051 Analogue Multi/Demulti	36p	MM8008 C.P.U.	36p
371AJ (MC684) Decade count, HINIL	5p	74180 8 bit parity gen.	12p	CD4052 Analogue Multi/Demulti	56p	MP3202 3z Digit DVM	£1.45
542 Servo Amp	18p	74181 Arith. Logic unit/funt. Gen.	56p	CD4053 Analogue Multi/Demulti	54p	MT300 Volt Regulator	8p
576-14 audio amp, 2 watt	60p	74H183 Dual full adder	36p	CD4054 4 LINE Lcd driver/count	72p	MW4050 Static Ram 200ns	£1.60
577 Mod A.F. Equaliser/Pre-amp	69p	74192 Synch. Dec. Up/Down	33p	CD4055 BCD 7SEG. Decoder/Drive.	72p	MW5510 256x4 SOS CMOS Ram	£2.60
702 CL OP Amp	25p	74LS192 Count + Dual Clock	60p	CD4056 Decoder	£1	SA4651 FM 1F Amp/Detector	36p
709/72709 OP Amp	18p	74193 reversible binary count	38p	CD4060 count 14 stage + osc.	90p	SA41010 Audio Amp, 10watt	34p
723 2V - 37v 150ma Regulator	36p	74196 Pre-set 50MHz.	36p	CD4061 256 X 1 Bit Static Ram	£5.30	SA41025 TV Remote control	£4
724 Zero Crossing A.C. Trigger	20p	74S196/82S90 Decade Count/Latch	65p	CD4062 4 bit magnitude comp.	72p	SA45012 Teletext Binary Tuner	£2.75
733 diff. wide band video amp	40p	74LS221 Dual Monostable M/VIB	52p	CD4066 Quad Bilateral Switch	72p	SL4034 3 Wt. Amp.	38p
741 OP Amp	17p	74221 dual Mono Multi. Schm. Trig.	72p	CD4067 1.16 MULTIPLEXER	£2.12	SL3203 3sec 1535	
747 Dual Op Amp	44p	74285 binary 4 x 4 mult.	47p	CD4068 8 bit I/P Nand	76p	SL60745 audio amp, 2 watt	60p
930DC Dual 4 in ext Nand	5p	74S290 Decade counter	72p	CD4069 Hex inverter	76p	SN7528 Dual Core Memory S.A.	11p
933DC Dual 4 in ext	5p	74293 4 bit binary counter	80p	CD4071 quad 2 input or buffer	16p	SN15836 Hex. Inverter	25p
936DC Hex Inverter	5p	74298 Quad 2 in multi plus store	£1	CD4072 dual 4 input or	15p	SN15845 Clocked Flip.Flop	50p
937DC Hex Inverter	5p	74490 dual decade ripple count	54p	CD4076 Quad D Flip-Flop	54p	SN15846 Quad 2 Input Nand	37p
946DC Quad 2 in Nand	5p	78M12 Pos. Reg. 12v 1A	54p	CD4077 Quad Exclusive Nor	30p	SN15851 Monostable Multivib.	50p
949DC Quad 2 in Nand. Fast	5p	7905 - 5v Reg. 1 Amp	54p	CD4078 8 Input Nor	19p	SN15858N Quad 3 input Nand	55p
961DC Dual 4in Ext Nand	5p	8080A C.P.U. 8 bit	£3.60	CD4081 Quad 2 Input and Buffer	15p	SN15862 Triple 3 input Nand	6p
963DC	5p	8284 Binary up down synch.	36p	CD4082 Dual 4 Input and	15p	SN75107 Dual line Receiver	£1.15
1315P2 Multivib. 1 shot processor	36p	82S128 256 x 4 prom	90p	CD4085 Dual 2 in. 2 wide and/or Inv.	72p	SN75108 Diff line Receiver	36p
1535 MOS decoder	50p	82S129 Trl state prom 256 x 4	90p	CD4086 4 Wide 2 Input and/or Inv.	54p	SN75110 Dual line driver	46p
1702A spon. 256 x 8	£3.10	9093DC Dual M.S.J.K. Flip Flop	4p	CD4088 2 Input Nand S.T.	54p	SN75125 7 line Rec. Interface	72p
2102 Memory 1024 static 450ns	73p	9112DC Hex TTL to DTL Inverter	4p	CD4093 4 bit ser. par. hold bus reg.	72p	SN75251 Dual Parph. driver	36p
2107B see µPD411AC		9310 4 to 16 line Decode/Demult.	£1.20	CD4095 JK Gated flip flop non Inv.	72p	SN75463 dual periph. or driver	36p
2125 1024x1 Static 95ns RAM	£1.25	9316 Binary count synch. P/Sin	35p	CD4096 gated JK flip flop	72p	SN76001 Audio Amp 5 watt	36p
2140 4 x S.P.D.T. for D/A	£1.83	9370 BCD to 7 Seg. Dec/Drive ALOC	25p	CD4097 µm/dux 8ch.	£2.90	SN76003 5Wt. Amp	36p
2472 MOS decoder	50p	16963	5p	CD4502 Strobed Hex Inverter	£1.78	SN76033 5Wt. Amp	36p
25 LS 374 Octal D edge Trig F/F 3st	£1.30	93453 Schottky prom 1024 x 4	£1.83	CD4508BF dual 4 bit latch	£1.78	SN76039 5Wt. Amp	92p
2708 Eprom 1024 x 8	£2.60	93039S 256 Bit Shift Register	5p	CD4511 BCD 7 seg. latch dec/driver	72p	SN76039 5Wt. Amp	36p
2716 Eprom 2048 x 8	£5.30	93039S 480 Bit Shift Register	5p	CD4514 decoder	£1.45	SN76039 5Wt. Amp	36p
3351-ZDC 40 x 9 Bit FIFO 2MHZ	£1.07	93039S 500 Bit Shift Register	5p	CD4515 decoder	£2.12	SN76039 5Wt. Amp	36p
3624-4 prom 512x8 90ns	£1	93039S 500 Bit Shift Register	5p	CD4517 2x64 bit Shift Register	£3.60	SN76101 FM Stereo Decoder	35p
4060 Dynamic RAM 300ns 4k BIT	£1.45	AY5-3507 3z Digit DVM	£1.65	CD4519/MC14519 4 bit and/or Sel.	54p	SN76131 Dual Pre Amp	58p
5203 see 1535		AY5-8300 3 In. Display	36p	CD4522 Dual Synch. 4 Bit Binary	72p	SN76227	59p
5224 see 2472		BRM300 Volt Regulator	£1.40	CD4527 BCD rate multiplier	£1.20	SN76228N	£1.60
7400 Quad 2 Input	11p	BT822 Tight Match mon PNP Pr.	£1.25	CD4532 8 In Priority encoder	£1.08	SN76396 (TBA396)	35p
74H00 Positive Nand	26p	C500 Calculator	39p	CD4555 decoder	72p	SN76650N 3 stage video I.F. + A.G.C. 50p	
74LS00 Gates	13p	CA101T Wide Band Op Amp	40p	CD4556 Decoder	56p	SN76650N	35p
74S00	18p	CA139AG Quad Volt Comparator	54p	CD22100 cross point switch	£1.45	SN76660N TV Sound Circuit	35p
7401 Quad 2 input positive	7p	CA239G Quad volt comparator	54p	CD40100 32 bit L/R Shift Reg.	£1.78	SN76666N View I.F. + Demod. + Driver	35p
74H01 Nand + O/C out	26p	(TICA270AE) Signal Processing	35p	CD40101 9 bit Par. Gen. check	£1.08	SN158093 Dual M.S.J.K. Flip Flop	5p
7402 quad 2 in pos nor	12p	(TICA270CE) Signal Processing	36p	CD40108 4 x 4 Multiport Reg.	£3.10	SN158099 Dual M.S.J.K. Flip Flop	5p
7403 Quad 2 in Nand O/C	12p	CA920 TV Horiz. system	72p	CD40160 Dec. Count. Async. clear	72p	SP4021 -64 VHF/UHF 5mv TTL O/P	75p
7404 Hex. Inverter	11p	CA3001 RF Amp	86p	CD40163 Bin. count synch. clear	72p	SP4022 VHF/UHF + 64 hi-speed	75p
54/7406 Hex. Inv./Buff/Drive	15p	CA3028A balanced OP. AMP.	75p	CD40182 look ahead carry block	72p	SP4030	75p
74L508 Quad 2 in pos. and.	25p	CA3044 TV AFT System	£1.20	CD40183 2 input and	£2.12	TAA263 Amp (low level)	75p
7410 Triple 3 input	19p	CA3045 Transistor Array (5)	8p	CD40184 4 bit L/R SR	72p	TAA320 Integrated most AMP.	10p
74L10 Positive Nand	18p	CA3046 Transistor Array (5) NPN	40p	CD40208BF 16 bit multi port RAM	£2.12	TAA550 Volt Reg.	35p
74H10 Gates	8p	CA3065 TV Sound I.F.	72p	CD40257 Data Selector	£1.15p	TAA700	£2.30
7411 Triple 3 In. Pos. and.	29p	CA3080 Prog. Transconduct. Amp.	59p	CD40257 Data Selector	£1.15p	TAD100 AM Radio	£1.22
7414 Hex. Schmitt trig. Inverter	29p	CA3083 NPN transistor array	65p	CDP1833 Cosmic Rom 1824 x 8	£3.60	TBA120/CQ/5B/B TV Amp	36p
7420 Dual 4 Input	19p	CA3086 NPN 5 transistor array	29p	CD40184 4 bit L/R SR	72p	TBA249	£3.90
74S20 Positive Nand Gates	19p	CA3089 FM I.F. amp plus detector	1.10p	CD40257 Data Selector	£1.15p	TBA3950 TV Chroma Circuit	£1.50
74S22 Dual 4 in. Pos. Nand o/c	18p	CA3090 Q/AQ FM decoder.	£1.72p	CDP1834 Cosmic Rom 1024 x 8	£3.60	TBA396 Luminescence and chrom.	£1.50
7425 Dual 4in nor strobe	18p	CA3094 Prog. Sw. Pwr. OP Amp.	36p	CM4116AE CMOS Quad Bilat. Switch	£2.49	TBA5500 Synch. Sep. + A.G.C.	£1.25
7428 4 x 2in + Nor Buf/CL. Drive	16p	CA3097 Thyristor - Transistor array	75p	CT1012 C Frequency synthesiser	75p	TBA5600 Lum/Chrom. control	52p
5430	12p	CA3123 AM Radio RF/IF Amp	73p	CT1112	75p	TBA800 Amp 5 Watt Audio	52p
7430 8 In. Pos. Nand	11p	CA3132EM Audio Amp. 10watt	£2.22	CT1115 Frequency Synthesiser	75p	TBA920 TV Line System	70p
74L30	11p	CA3140T Bimos op amp	40p	CT1116 Non Volatile NMOS Ram 16 x 14. Data held 30 hrs. after supply removed	£1.50	TCA2700/SA/AE/Q5 Vid. Det.	£1
54/7437 Quad 2 In. Pos. Nand. Buf.	13p	CA3146E Hi-volt 5 transistor array	90p	CT1119 NMOS 16 x 14 RAM Freq. Synth.	75p	TCA270/SB synch. demodulator	55p
7438 Quad 2 in nand buf O/P	14p	CA3160S BIMOS OP Amp	90p	DC18093 See 74125		TCA440 A.M. Receiver	£1.25
7440 Dual 4 in Nand Buffer	13p	CA3183 NPN transistor array	80p	FCH111 8 input Nand/Nor	8p	TCA830S Ex. Equip A.F. Amp.	18p
74H40 Dual 4 in. Pos. Nand. Buffer	14p	CA3189 FM receive I.F. system	£1.40	FCH201	18p	TCA4401	£1.25
7441 BCD to DEC. Decode/Drive	42p	CA3290 Comparator	58p	FCHJ01	18p	TCEP100	£1
7442 BCD to Decimal Decoder	40p	CA3401 (LM3900) Quad Op Amp	58p	FPO/MPQ3725 4 Tr. Array	50p	TDA0470 Organ, 2 tone Generator	37p
74LS42 BCD to Decimal Decoder	42p	CD4000 Dual 3 input Nor + Invert	12p	FZH151	18p	TDA1003 Pre-amp and record	£1
74LS44 BCD to Decimal Decoder	42p	CD4002 Dual 4 Input Nor	12p	FZH191	18p	TDA2020 audio amp 20 watt	£2.60
7445 BCD Decimal Decoder	42p	CD4004	56p	FZH201	18p	TDA2610 6watt audio amp	71p
Expandable Dual 2		CD4006 18 Stage Static Shift Reg.	36p	ICL7103 4z Digit DVM/DPM	£2.04	TDA2680 T.V. Signal processor	£1.83
74H50 Quad 2 Input and/or Inv.	26p	CD4007 Dual Comp. Pair + Invert	12p	IG3412 see 1535		TDI25A 16 diode array	5p
7454 4 Wide 2 In. and/or Inv.	11p	CD4008 4 Bit Binary Full Adder	54p	LM300 Volt Regulator	42p	TL441 Log-antilog amp.	36p
54/7472 Slave Fd. Preset + Clear	25p	CD4010 Hex Buffers	30p	LM377 Dual 2 wt audio amp	£1	TL µ A720 AM Radio RF/IF Amp	73p
7472 Dual JK Master	17p	CD4012 Dual 4 Input Nand	36p	LM378 Dual 2 wt audio amp	£1	TMS 7B J. Fet SPDT switch + driver	53p
5473 Slave JK Master	12p	CD4013 Dual D Flip Flop	13p	LM380 audio amp, 2 watt	60p	TMS 3409 memory 80 bit shift Reg.	£1.10p
7473 Slave Flip Flop	17p	CD4014 8 Bit Shift Register	36p	LM3407V Regulator	36p	TMS4034 Memory	£1.08
74H73 with Clear	26p	CD4016 Quad Bi-Lateral Switch	36p	LM3407V Regulator	36p	µ PD411AC 200ns Dynamic 4096 x 1 ram	£1.30
7474 Dual D. Pos. Trigger	13p	CD4017 Decode Count/Divide	54p	LM3909 (See CA3401)	5p	XR215 Hi-freq. phase lock loop	£2
74L74 FF 2/Preset + Clear	25p	CD4018 Preset Divide N Count	54p	MC8330P Dual 4 In Ext and	5p	ZN414 AM Radio Receiver	79p
7475 Quadlatch	24p	CD4019 Quad 2 Inout Multiplex	54p	MC837P Hex invert fast rise	5p	ZST131A 5 Input Power NOR	8p
54/7478 Dual JK Mas./SL Flip Flop	19p	CD4020 14 Stage Binary Counter	54p	MC849 quad 2 in Nand/Nor fast	11p		
5480 gated full adder	22p	CD4021 Shift register, 8 bit	36p	MC862P Triple 3 in Nand	5p		
7482 2 Bit Binary Full Adder	35p	CD4022 Divide by 8 Count/Divide	36p	MC863P Triple 3 in Nand Fast	5p		
7483 4 Bit Binary full	45p	CD4023 Triple 3 Input Nand	19p	MC836P Audio Amp. 6 watt	40p		
74LS83 Add + Fast carry	47p	CD4024 7-Stage Binary Counter	36p	MC1307 FM Stereo Decoder	35p		
54/7486 Quad exclusive or	18p	CD4025 Triple 3 Input Nor	14p	MC/CA/BRC 1310P St. Decoder	35p		
5490/7490 Decade Counter	25p	CD4027 Dual JK Flip Flop + RS	30p	MC1312P Stereo Decoder	40p		
7493 Binary Counter 4 Bit	25p	CD4028 Quad Bi-Lateral Switch	42p	MC1314P 4 Channel sound	35p		
7495 4 Bit Shift Reg. P.I.P.O.	35p	CD4029 Synch. Preset Bin/Decode	36p	MC1315P 4 channel sound	35p		
54/74L95 4 Bit Ser./Par. In Out	25p	CD4030 Quad exclusive. shift reg.	£1.20	MC1350P Video I.F. Amp + A.G.C.	35p		
74LS98 4 bit storage register	£1.25	CD4031 64 stage static. shift reg.	72p	MC1357P sound I.F. + Demod.	35p		
74107 Dual JK Flip Flop Clear	20p	CD4032 Trip. Ser. Add. Neg.	72p	MC1463G Neg 3.8 - 32v 200ma reg.	38p		
74S112 Dual JK N.E.T. Flip Flop	38p	CD4033 Dec. Count. 7 Seg. Output	72p	MC1469G Pos 3.8 - 32v 200ma Reg.	38p		
74118 Hex Reset latch	75p	CD4034 Static shift register	£1.48p	MC1723C Pos 2 - 37v 150ma Reg.	38p		
74121 Monostable Multivibrator.	12p	CD4035 4 Bit Par. in out Shift	54p	MC3302L Quad amp (volt comparator)	75p		
54/74123 Dual Retrigger. Multivibrator	£1.10	CD4036 Word Buff. Store, Decode	£2.00	MC4044P Phase/Frequency detector	£1		
54S124 dual volt cont. osc.	36p	CD4037 triple and/or B1 Phase pairs	72p	MC4344P Phase/Frequency Detector.	£3.50		
74125 Tristate Quad Buffer	38p	CD4038 Triple serial adder	54p	MC7C	25p		
74132 Quad 2 in nand schmitt	44p	CD4040 12 stage binary counter	80p	MK2686	36p		
74141 BCD to Decimal Dec/Drive	42p	CD4041 Quad True/Comp. Buffer	54p	MK4012 Memory Static Shift Reg	38p		
74LS145 BCD to decimal Dec/Drive	93p	CD4042 Quad clocked D type catch	54p	ML2368 (6024) 6ch. touchtone	£1		
74151 1 of 8 Data Sel/Multivibrator	32p	CD4043 Quad Nor R/S Latch	54p				
74153 Dual 4 to 1 multiplexer	36p	CD4044 Quad Nor R/S Latch	54p				
74156 16 Way Distribution	35p	CD4045 4 Bit Par. in out shift	72p				
74155 Dual 2 to 4 line decoder	12p	CD4046 Micro Power Hh. Lock Loop	72p				
74167 Quad 2 line to 1 Data	12p	CD4047 monostable	72p				
74165 8 bit shift reg. PISO	58p	CD4048 Exp 8 input gate	36p				
74167 Synch. Dec. Rate Multivibrator	23p						
74173 Quad 3 state latch	44p						

Metal Film 2% 1/2 WT Resistors 100 for 45p
120 220k 147k 215k 221k 475k 620k 8K2 150k.

Duraplugg 13 amp trailing rubber socket 85p.

AS A ONE MAN BUSINESS, I WORK 15 TO 17 HOURS A DAY, 61 DAYS A WEEK; (LUCKILY I DO NOT ENJOY OR HAVE HOLIDAYS) RE-INVESTING PROFITS, IN ORDER TO CONTINUE TO OFFER COMPONENTS AT VERY LOW PRICES. OVERHEADS AND COST OF LIVING RISE MONTHLY SO I MUST WORK FASTER AND SELL MORE AS I CANNOT STRIKE; OR GET A 'WAGE ???' RISE WITHOUT INCREASING PRICES WHICH I DO NOT WANT TO DO (EXCEPT FOR VAT AND POST WHICH COMES TO MORE THAN MY PROFITS) . . . SO I HOPE GOODS OFFERED MEET YOUR APPROVAL.

R&EC

Offer you

.....a medium wave superhet radio,
built into a pair of headphones.

Ideal for following a test match,
or generally listening to the radio
when those about you do not
share your tastes!

If you work in a noisy
environment - or simply
do not wish to be
disturbed - then here's
an entertaining
alternative solution.....



Your beloved editor gets
his 'ears' on to avoid being
disturbed whilst penning a few
more pearls at the word
processor.

If you don't need the radio
facility - then these
phones provide an excellent
basis for the development of a
'cordless' headphones set -
complete with battery compartment
and controls. R&EC will be
exploiting this aspect in
an early issue with a
project based on the
'phones'.

ELECTRIC HEADPHONES

Please send me Pairs of
R&EC Radio Headphones.

Name

Address

POSTCODE

PRICE £10

Per Pair

INCLUDES VAT & POSTAGE

DOES NOT INCLUDE BATTERY (PP3)

PLEASE ALLOW 21 days for delivery

Please remit by cheque/PO/ACCESS/BARCLAYCARD/cash

Please make payable to: Radio & Electronics Constructor

Send to:

57 Maida Vale, London W9 1SN

Please include a SAE in case this offer is
over - subscribed and we need to return
your payment.


NEWS . . . AND

Improved cutting and bending tool

Eraser International of Unit M, Portway Industrial Estate, Andover, Hants., have announced the availability of a new improved tool, the Model TP3, for component lead cutting and bending in Printed Circuit Board Assembly.

The TP3 is designed to cut the legs of electronic components subsequent to their insertion in a Printed Circuit Board. In addition to the cutting legs, it also bends them over at a right angle thus retaining the component firmly in the Printed Circuit Board for subsequent manual or automatic soldering operations. This method of cutting and bending the component lead legs after insertion into a P.C.B. eliminates the possibility of components being dislodged during wave soldering.

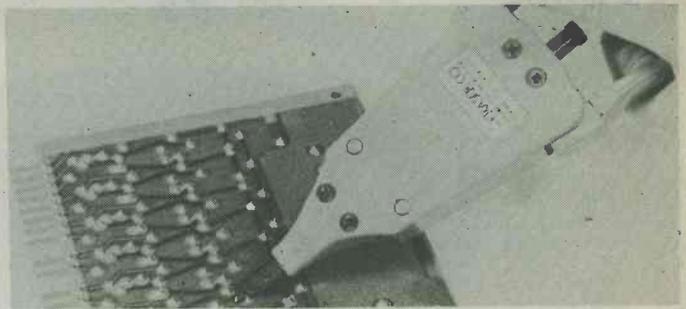The TP3 incorporates a new fixed and moving blade system giving extended blade life and ease of operator use where the angle of the tool relative to the Printed Circuit Board is not critical.



The TP3 is suitable for cutting and bending all electronic components with lead diameters of between 0.3mm and 1.5mm. The hand tool is self-adjusting to compensate for different lead diameters.

The TP3 employs hardened steel cutting blades

which are both regrindable and replaceable.

The tool is constructed from rugged diecast aluminium and is suitable for both production and prototype work.

Further information is available from Eraser International Limited.

International Year of Disabled People

The International Year of Disabled People is to be acknowledged by the Amateur Radio fraternity with an "International Weekend on the Air" for the disabled. The weekend selected is 1st - 3rd August, to coincide with the opening of the International Meeting of the Devon Sports Association for Disabled Persons at St. Loyes College, Exeter.

The Exeter Amateur Radio Society will operate stations from St. Loyes on all amateur frequencies from 80m to 10m, VHF and UHF between the hours of 0900z and 2000z using the call signs GB21YD and GB6IYD. It is hoped that disabled operators all over the world will contact each other and exchange greetings and QSL cards. It is suggested that stations should call "CQ IYDP from . . . (c/s). Further details from: G. Draper, 1 Carlyon Close, Exeter EX1 3AZ. Tel: 37170.

Marconi International Fellowship Award

Dr. Seymour A. Papert, Professor of Mathematics and Education at the Massachusetts Institute of Technology has been awarded the Seventh Marconi International Fellowship which takes the form of a \$25,000 grant which the recipient can use to originate or complete a project of his choice.

Dr Papert was honoured for his work in computer education and in particular the development of the LOGO language which he designed especially for children. A computer education system based on the LOGO language encourages a child to take an active role in the learning process. To do this the LOGO system reverses the usual computer-pupil relationship, instead of the computer teaching the pupil, the student is required to teach the computer. The system has shown itself to be particularly useful in the education of children suffering from cerebral palsy, a disability which imposes a passive role on its victims.

Low priced DFMs especially imported



Due to the difficulty of obtaining a low priced high quality digital frequency meter in the UK, Messrs. Holdings of Mincing Lane, Darwen Street, Blackburn, Lancs., have arranged to import DFMs from Japan.

A DFM is, of course, invaluable to the electronic enthusiast and the unit being imported can be used to check many types of equipment.

The basic price of the unit is £39.99, including V.A.T., and the total price including batteries, input lead, carriage and insurance is £43.58.

... COMMENT

The customer is always right

The completed survey forms (supplied in last month's issue) look like providing a very useful and comprehensive insight into the attitudes and opinions of our readers.

As far as we can tell, most respondents want more to do with radio and communication topics. And as we had guessed, there is distinct evidence of a broadening in the market for 'personal computing', and we are pleased to say that the thoughts offered by readers tend to align with those that we have put forward as our own 'platform' - namely less of the 'space invaders', and more practical examples of microprocessors at work.

Test equipment features seem to have emerged as another favourite. We have a number of articles 'booked' that both describe test equipment (including a 500MHz 8 digit multigigahertz frequency counter and capacitance meter) from the users viewpoint, and also approach the subject from a practical and constructional viewpoint.

The section covering the buying habits of 'electronic man' has obviously provided a vent for feelings ranging from satisfied to the vitriolic, so this is perhaps an opportune time to point out the advantages of careful cooperation between publishers and suppliers to ensure that featured items use parts selected from a 'standard range'. A surprisingly small number of 'standards' can be used in an extremely broad range of circuits, thereby benefitting the reader (who gets a better price due to the increased volume of the 'standards' forcing down the price), the supplier (who is not faced with an unnecessarily vast range of stock items) and the publisher, who can rest in the knowledge that he won't get endless letters and 'phone calls asking where a BC923 can be run to ground.

Next month's *Constructor* will contain the opening shot in our crusade to try and constrain 'components' into some sort of order and we look forward to useful dialogue with suppliers and readers alike until we can produce the definitive 'selection'.

Smaller Video Recorder maintenance Kit



A smaller version of the Bib Video Recorder Maintenance Kit has been marketed by Bib Hi-Fi for inclusion in their Videophile Edition range, making it particularly suitable as a gift item.

Available in blister form, this smaller Video Recorder Maintenance Kit is completely disposable, since it is recommended that it should only be used for 5 machine cleanings. Bib suggest that with the average use of video recorders, this Kit should last for about 2 years.

The Kit comprises 5 Video Tape Head Cleaning Tools, Dust-Away Air-Blast and Head Cleaning Fluid. Full instructions for use with both VHS or BETAMAX are provided and the Kit is packed in a clear container, the same size as a VHS cassette, enabling it to be stored conveniently with video tapes.

The recommended retail price is £5.47.

The Bib Video Recorder Maintenance Kit is marketed by Bib Hi-Fi Accessories Limited, Kelsey House, Wood Lane End, Hemel Hempstead, Herts.

Computer wakes the guests

In the old days of gracious hotel living, a guest used to smile at the receptionist or maid, and ask to be woken at a particular time with one's morning tea and a paper.

Now though, thanks to a computer, graciousness and human contact can be restored, but at a fraction of the cost of maintaining the old human-operated system. Millbank Electronics have worked out this new technological marvel, and integrated it with their existing hotel sound system which gives a choice of radio programmes, controls the TV, tells you whether there's a message waiting for you, and switches the lights on and off, all from a neat aluminium panel beside the bed.

When you smile at the receptionist - yes, it's that human - and ask for your call, all she does is tap out your room number and the time you request on a little calculator-like keyboard on her desk. Your room number and time are displayed on the panel, so she

can check that she's got the details right. When she confirms that she has, the call is printed on a paper roll, just as a record. Then, at just the right time, an electronic 'bleeper' raises you from your slumbers. Sadly it can't deliver tea and your choice of paper - yet - but no doubt the Millbank people are working on that. But the machine doesn't end there. If you are one of those people who seem capable of switching the alarm clock off without waking, the system catches you - for it prints out, as well as the initial call request, what time it beeped you, and what time you cancelled the bleep. And if you're capable of sleeping through earthquakes even, then after a preset time, the system warns the receptionist so she can despatch someone to wake you.

Now all we need is a computer that cleans the boots and changes the towels as well as making morning tea and delivering newspapers - so long as it isn't programmed to ask for tips!

Piezo Acoustic Transducers

Jonathan Charles Burchell

Introduction

Next time your project needs some kind of built-in tone or alarm signalling device consider using a Piezo-electric buzzer. This output device complete in its plastic encapsulation is comparable in size and cost to a 50 pence piece, yet at resonance the device is capable of producing sound levels of over 95db some 10 cm away, a volume level in excess of that obtainable from most 4 inch loudspeakers.

Because of the extremely high efficiency of the piezo-buzzer even at this high output level—the input power is only 30 milliwatts.

THE PIEZO-ELECTRIC BUZZER

The piezo-electric effect is well known and exploited in objects as diverse as Gas lighters, Record cartridges, Crystal filters, and of course Quartz crystals.

Piezo-electricity is caused by certain crystals which produce a voltage across their faces when subjected to mechanical stress. The effect is reversible, the crystal undergoing mechanical contraction when subjected to a suitably applied voltage, it is this effect which is used in the piezo-electric buzzer.

Fig. 1. illustrates the method of construction used in a piezo-sounder. A circular disc of suitable crystals (often Titanate-Zirconate) is deposited onto a slightly larger disc of thin metal, which forms one electrode, a second electrode is produced by depositing a layer of metal onto the surface of the crystals.

When a voltage is applied, the mechanical contractions of the crystals are converted into vertical flexing of the plate. If the unit is driven by an oscillating voltage, then mechanical oscillations of the same fre-


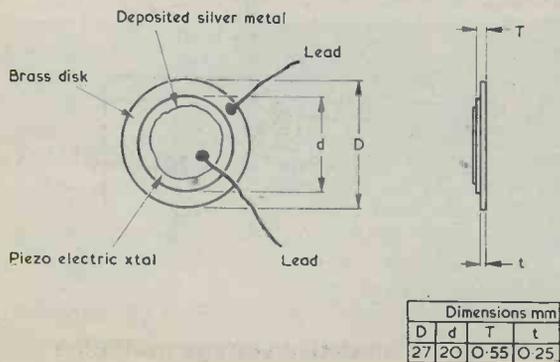



Fig. 1.

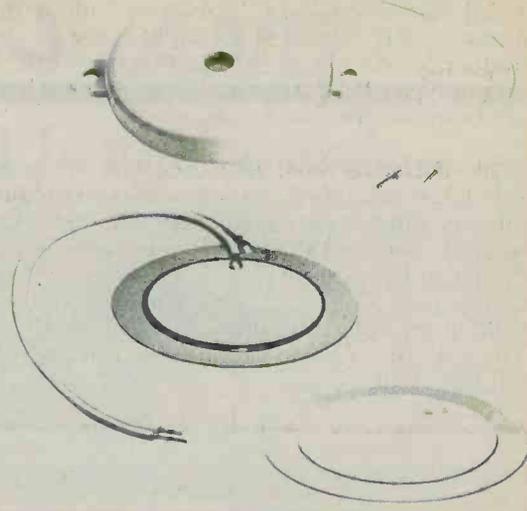

Vibrating node

Metal plate

Piezo-electric element

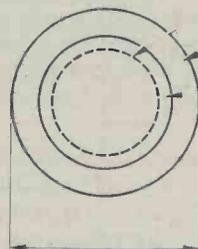

Frequency characteristics PB2720

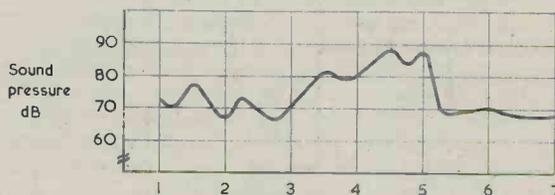


Fig. 2.

quency will be set up in the plate as shown in Fig. 2.

As the mechanical coupling from crystals to plate, and plate to media, is near perfect, combined with the high efficiency of the piezo-electric energy conversion process, the overall efficiency of the device is excellent making the device ideal for use in any application requiring high output combined with low power consumption. The metal disc provides both mechanical support for the crystals, and a lowering of the resonant frequency of the whole structure which would otherwise be in the ultrasonic region.

The designer of a digital watch would use the bare element and build it into his watch case, but to make the device easier to handle and mount (and to enable a severalfold increase in output to be obtained), they are normally supplied in some form of plastic case which acts as a resonant cavity for the element.

Although maximum output from the buzzer is only obtained at resonance, the buzzer gives a useful output over much of the Audio-spectrum – as can be seen from the Graph of Fig.2.

APPLICATION AND DRIVING CIRCUITS

All that is needed to obtain an output from the piezo-electric buzzer is an input wave of the right frequency. All these circuits use the TOKO piezo buzzer type PB-2720 which has a resonant frequency of about 3.5 KHz.

CONTINUOUS SOUND CIRCUITS

Fig.3. is possibly the simplest way to obtain a continuous output of tremendous volume. A simple single transistor LC feedback oscillator is used and the piezo buzzer connected across the coil, at resonance some 30 + volts p-p are applied to the buzzer (due to the voltage multiplication of the LC circuit). The core of L1 should be trimmed to provide maximum output.

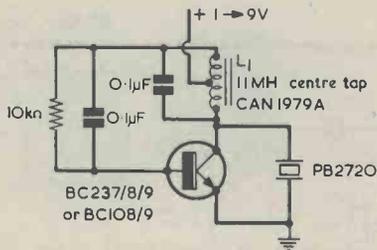


Fig. 3. Tune for resonance. Ultra high output/low consumption tuned transformer drive.

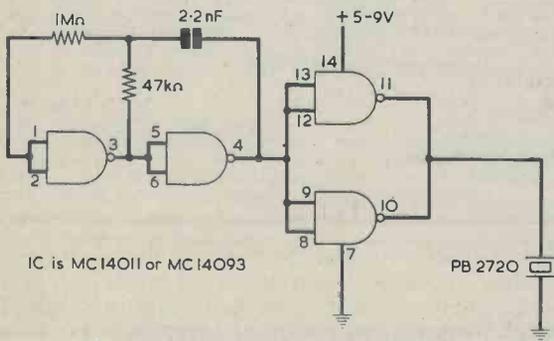


Fig. 4. Simple CMOS drive.

Fig.4: is also a continuous tone circuit but built this time from a single CMOS quad Nand gate.

Gates G1 and G2 form a simple cross coupled RC oscillator, whilst Gates G3 and G4 are coupled in parallel to increase the available output current. As the applied voltage is rather less than that of Fig.3. the output will be correspondingly less, but the output booster of Fig.6. may be added to further increase the output.

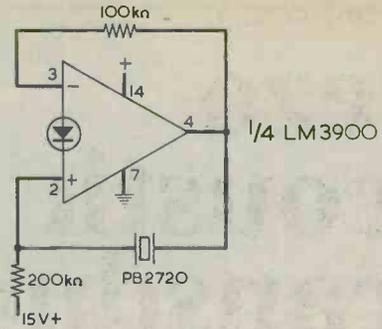


Fig. 5. Using a spare 'Op-amp' section.

Fig.5. The last circuit in this section shows a very simple oscillator built by using the piezo buzzer as the positive feedback element around a current input op-amp. The main advantage of this particular circuit is that the circuit inherently oscillates at the resonant frequency of the piezo-buzzer thus insuring maximum possible output from the device.

INTERFACE TO EXISTING OSCILLATORS

Fig.6. In many applications a suitable source of oscillations may already be available. The output of many LCD clock modules is a 1KHz or so square wave. In these applications all that is needed is some simple form of buffer/amplifier, and this circuit is just that.

The coil L2 forms the collector load of Tr2, the resulting back e.m.f. from switching Tr2 on and off is applied to the buzzer causing it to be driven from a voltage in excess of the rail voltage with a corresponding increase in output volume. A capacitor may be added as shown which creates a somewhat milder output tone, although causing a slight reduction in output volume.

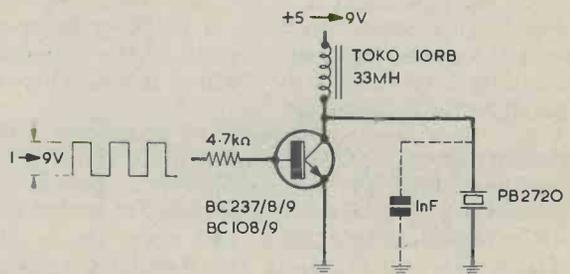


Fig. 6. An inductive voltage multiplier for increased output.

Fig. 7. Intermittent 'Bleper'.

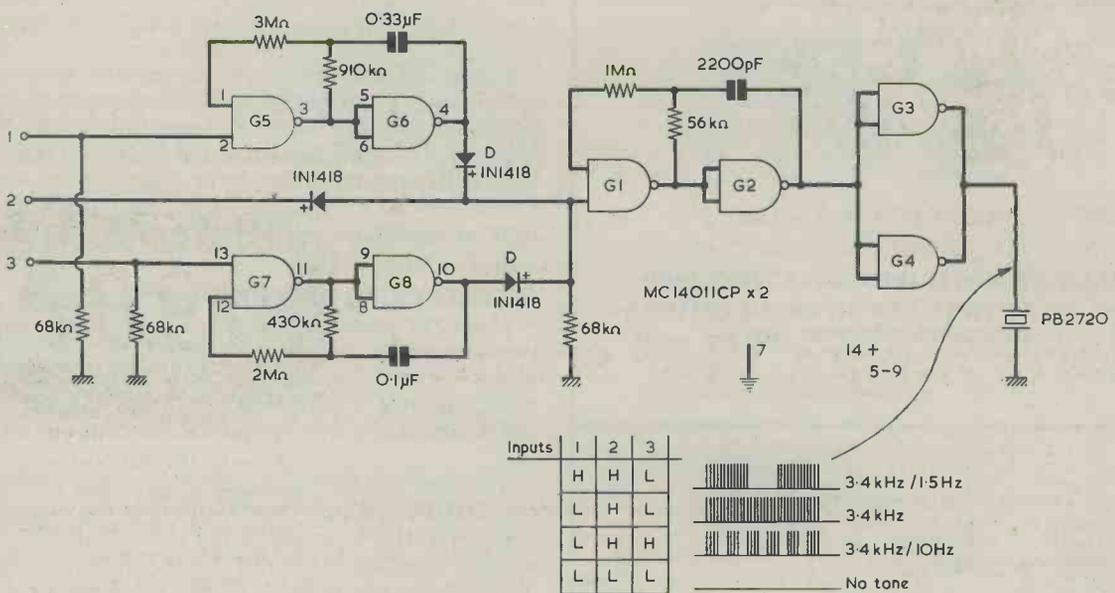
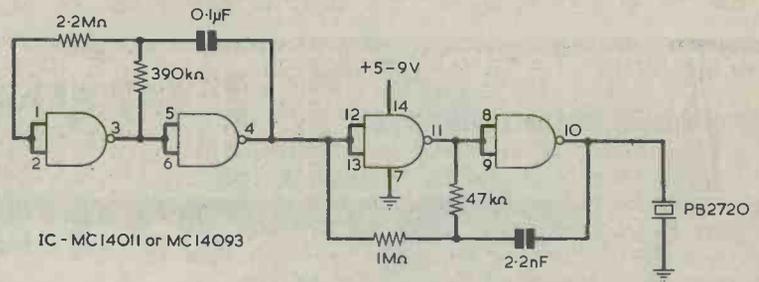


Fig.8. 3 'State' audible annunciator.

MODULATED OUTPUTS

Fig.7. This circuit produces a pleasant bleeping sound at several hertz, and consists of the RC oscillator of fig.4. modulated by a second RC oscillator at a much lower frequency.

Fig.8. This circuit is capable of producing three different tone sequences according to the states of the three input lines. The three different sequences are continuous 3.4Khz, 3.4Khz modulated at 1.5Hz, and 3.4Khz modulated at 10Hz.

Gates G1 and G2 form the 3.4Khz Oscillator, Gates G5 and G6 form the 10hz oscillator and G7 and G8 the 1.5Hz Oscillator. The input lines and control diodes allow the 3.4Khz Oscillator to remain un-modulated or to be modulated by either the 10 or 1.5Hz oscillator.

Whilst the layout of the above circuits is non-

critical, there exists a potential danger when connecting Piezo-buzzers onto CMOS devices.

Due to the piezo electric effect of the buzzer and the very high impedance between the input leads of the device, it is possible for a considerable potential to build up across the device when it is subjected to mechanical stress.

If an unconnected buzzer is tapped fairly sharply and the leads from the device then shorted together a click will be heard from the element as the built up charge is lost. So before connecting the buzzer into a circuit which already has CMOS gates plugged into it—the leads should be shorted together.


No trouble has been experienced in practice once the circuit has been connected up, but if the buzzer is going to be subjected to external shocks, a 1 to 10 Megohm resistor across the buzzer leads should prevent further problems. ■

IN NEXT MONTH'S

RADIO & ELECTRONICS

CONSTRUCTOR

5 CHANNEL RADIO CONTROL SYSTEM

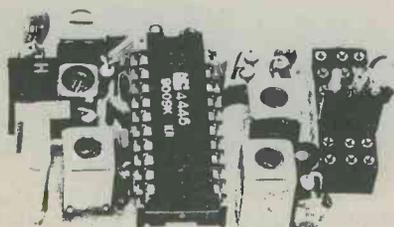


**SIMPLE TO CONSTRUCT RELIABLE
5-CHANNEL RADIO CONTROL SYSTEM
BASED ON A SINGLE CHIP SOLUTION
FOR BOTH TRANSMITTER AND RECEIVER.**

don't forget VHF scanner pt 2

```

380 N2$=STR$(N2)
390 IF LEN(F9$)=2 AND LEN(F0$)=7 THEN G4$="CANADA"
400 IF G3$<>" THEN G8$="/"+G3$ ELSE G8$=""
410 PRINT #1, #71, N2, " ", F3$,
420 IF F4$<>" THEN E1$=INT(100*(F4$-G1$)/F4$)
430 PRINT #1, TAB(11), E1$, " ", F4$,
440 IF G2$="" THEN PRINT #1, TAB(73), G8$, ELSE PRINT #1, TAB(73), G2$,
450 PRINT #1, TAB(99), F8$, TAB(115), F9$, TAB(126), F0$, TAB(135), G4$,
460 IF G5$<>" THEN PRINT #1, TAB(149), "("+G5$+" )",
470 IF G6$<>" THEN PRINT #1, TAB(155), G6$
480 L=L+1
490 L0=0
500 IF F4$<>" THEN 510 ELSE 530
510 IF G1$<>" THEN PRINT #1, TAB(11), G1$,
520 L0=L
530 IF G2$<>" THEN 540 ELSE 560
540 IF G3$<>" THEN PRINT #1, TAB(73), G3$,
550 L0=L
    
```

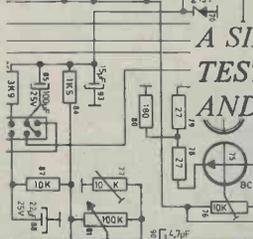Dick and Smithy battle on; will Dick save the Galaxy for the third time that Summer's afternoon? Eavesdrop once again on the popular duo to discover what tips they have for you
In Your Workshop.....



A SIMPLE LOW-COST DIGITAL TEST METER FOR DC VOLTAGE AND CURRENT.




Cast on 91 (97:103:109) sts.

Work 8cm k1 s1.
1st row k2 (k1.p1) to last stitch K1
2nd row k1 p1 to end.

..... Rib 3 (6:3:6) * inc.
7 (7;8:7) rep from* 11 times.
ib to end 104(110:116:122)
in stst until back measures
13:55)cm end p row.

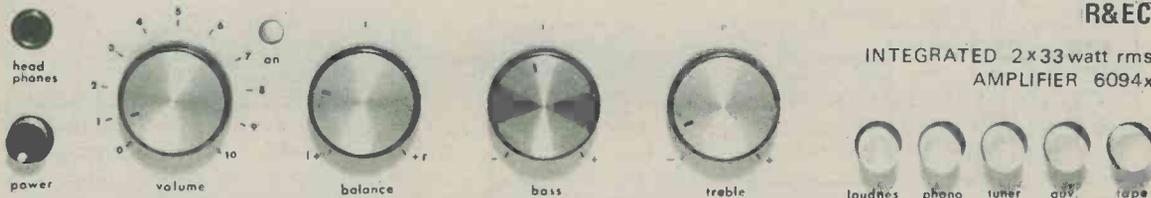COMPULINK
Programming and Program Languages—
a cohesive approach to the black art
of programming, beginning with such
familiar items as
Knitting Patterns & Washing Instructions!



THE AUDIOMASTER—A Hi - Fi Amplifier of compact construction and design developed with the finest advanced electronic technology yet not too daunting in assembly. With 30 watts per channel and very good performance in all areas this project is a 'must' — especially as the amp will be available as a complete kit (down to the last nut & bolt!) for under £65.

PLUS MUCH MUCH MORE

Infra-Red Remote Control System Part 1

I. M. Attrill

This remote control system is of the sequential type where operating a push-button on the transmitter unit causes the controlled equipment to be switched on, and operating the push button switch again causes the equipment to be switched off, and so on. Although most short distance remote control systems use ultrasonics to provide the link between the transmitter and receiver, infra-red light now offers a practical alternative for the home-constructor, and is the medium used in this system.

The system has a maximum range of only about 6 or 7 metres, which is perfectly adequate for controlling equipment in the same room as the user. The equipment could, for example, be used to provide remote on/off switching for a T.V. set or light in a bedroom.

SYSTEM OPERATION

Fig.1. shows in block diagram form the various stages of the transmitter and receiver units. The transmitter is extremely simple, and is based on a pulse generator that has an operating frequency of about 10kHz, with a mark space ratio of about 10 to 1. The brief output pulses are used to operate an infra-red L.E.D. via an amplifier which provides the high peak output currents that are required. The peak L.E.D. current is actually about 400mA; but due to the fairly high mark space ratio of the pulse generator the L.E.D. is only receiving power for about 10% of

the time. It thus receives an average current of only about 40mA. This gives strong pulses of infra-red light, but ensures that the dissipation in the L.E.D. is not excessive.

The human eye is insensitive to infra-red radiation, and as infra-red L.E.D.s do not produce significant output in the visible light spectrum, no visual changes occur to the L.E.D. when the transmitter is switched on and off.

The reason for using a pulsed beam rather than a continuous one is simply that the steady-state output from an infra-red L.E.D. is not very strong, and a continuous beam would be swamped by the ambient infra-red level at more than a few inches from the L.E.D. Even if the pulses of infra-red from the transmitter are below the ambient infra-red level, they will produce small voltage pulses at the detector, and these pulses can then be amplified to give a suitable output to operate the control logic circuitry. The use of a pulsed signal also allows the receiver to be A.C. coupled, thus avoiding problems due to D.C. and thermal drift.

Therefore, the receiver has an infra-red detector diode which has its output fed to a two stage high gain amplifier. The output from the amplifier is fed to a Schmitt trigger circuit which ensures that the rise and fall times of the signal are fast enough to operate the subsequent stage of the circuit reliably. The Schmitt trigger also effectively removes any noise from the signal that might otherwise give erratic operation.

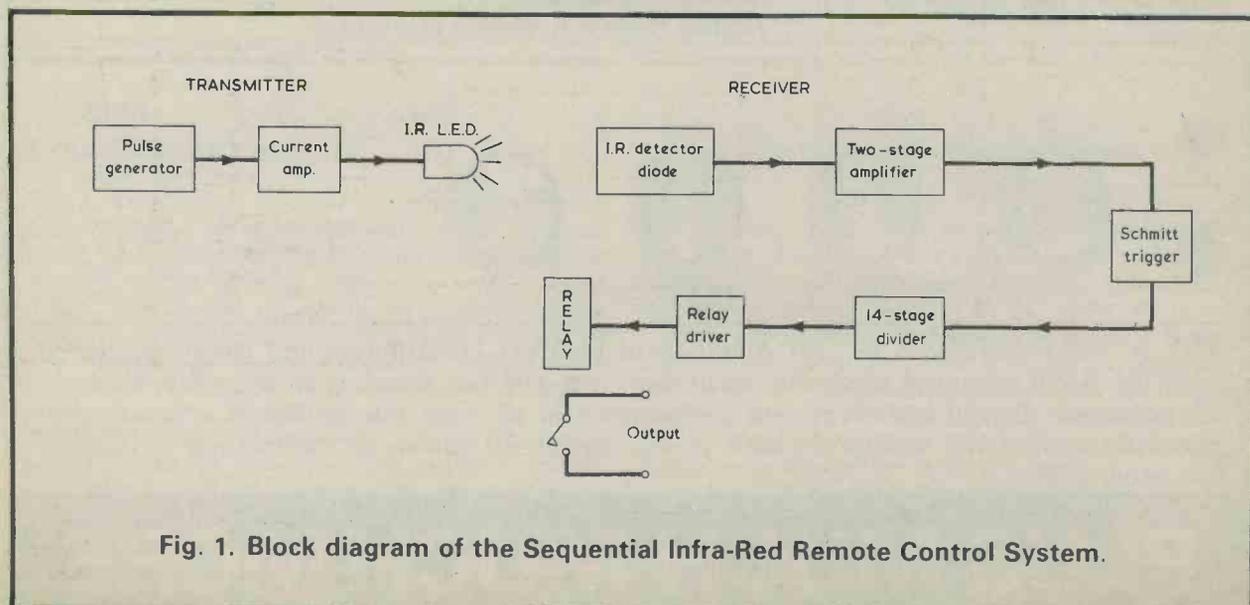


Fig. 1. Block diagram of the Sequential Infra-Red Remote Control System.

The transmitter in case.



The next stage of the circuit is a CMOS 14 stage binary divider, and this divides the input signal by 16,384. If the transmitter is run continuously, the output of the divider changes state slightly more frequently than once per second. A relay coil is driven from the output of the divider by way of an emitter follower buffer stage, and the load is controlled via a pair of normally open relay contacts. If the push button at the transmitter is depressed to make the transmitter operate non-stop, the controlled equipment will continuously switch on and off. In practice the transmitter is operated just long enough to switch the load on or off, as appropriate.

TRANSMITTER CIRCUIT



The circuit diagram of the transmitter is shown in Fig.2. This is based on a CMOS 4001 quad 2 input NOR gate I.C. In this application only two of the gates are used, and these both have their inputs connected together so that they give a simple inverter action. The two gates are connected in a CMOS ast-

able multivibrator circuit, with the timing resistor formed by two resistors (R1 and R2), and two steering diodes (D1 and D2). In effect, the timing resistance is formed by R1 and D2 when the output is in the high state, and by R2 plus D1 when it is in the low state. This gives the required short positive output pulses, as R1 is much lower in value than R2, giving a shorter time constant when the output is 'high'.


The unused inputs of IC1 are tied to the negative supply rail so that they cannot be damaged by high static voltages, or spuriously operated by stray pick-up.

IC1 provides an output at a fairly high impedance, and it is not able to supply anything approaching the peak output current needed to power the L.E.D. Tr1 is therefore used as a common source amplifier which gives the necessary current amplification. Tr1 is a VMOS device which, unlike a bipolar transistor, is voltage rather than current operated. It is not like the f.e.t.s encountered in most designs, which are *depletion* mode types. These are normally switched hard

Fig. 2. The circuit diagram of the Infra-Red Transmitter.

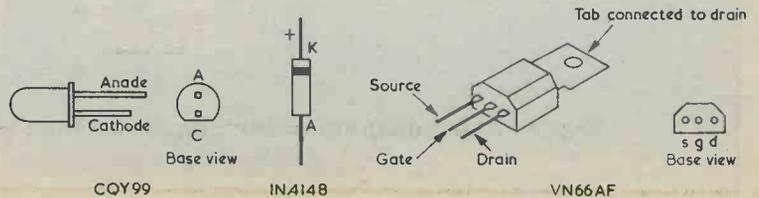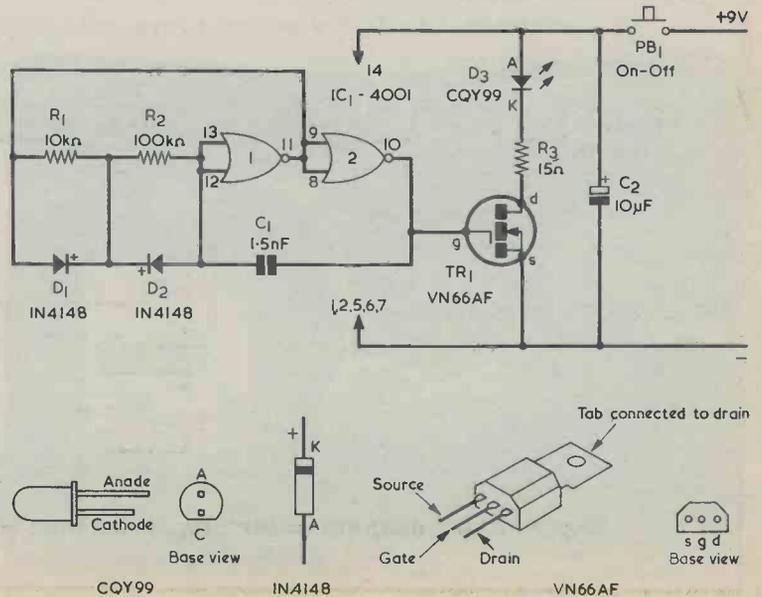

Inside of the transmitter.

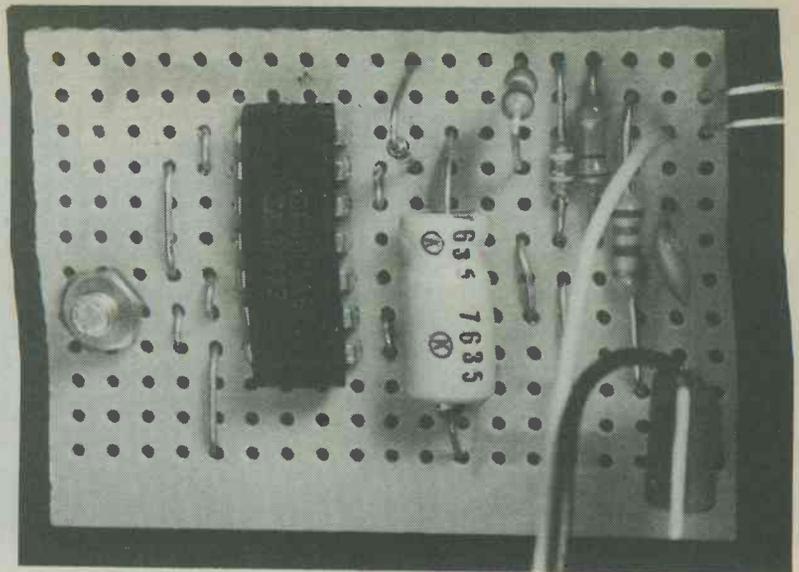

on, and must be reverse biased in order to switch them off. Tr1 is an *enhancement* mode device which, like an ordinary bipolar device, is normally in the off state and must be forward biased in order to switch it on. Thus, during the brief positive output pulses from IC1 Tr1 is biased into conduction and provides pulses of current L.E.D. D1 via current limiting "on" resistance and is capable of providing the high L.E.D. currents required.

On/off switching is provided by PB1, and C2 is a supply decoupling capacitor. The current consumption of the unit is a little over 40mA. Power is provided by a small (PP3 size) battery, and this has quite a long operational life despite the current consumption of the circuit, since the unit is only switched on very briefly each time it is used.

CONSTRUCTION

The prototype is housed in a small plastic box having approximate outside dimensions of 100 x 75 x 40mm, but it should be possible to accommodate all the components in virtually any small case, which is of a convenient size.

PB1 is mounted on the lid of the case, slightly forward of a central position. The holder for D3 is


mounted on one of the end panels of the case. This simple layout can be seen in the accompanying photographs.

Most of the components, including D3, are assembled on a 0.1in. matrix stripboard, and details of this are provided in Fig.3. After cutting out a board having 12 strips by 19 holes, drill the single 3.3mm. diameter mounting hole and make the seven breaks in the copper strips. The components and link wires are then soldered into place, with the IC1 being left until last. As this is a CMOS device it should be handled as little as possible, and should be soldered into place using a soldering iron having an earthed bit.

With D3 fitted into its panel holder, the component panel can be used as a template to locate the position of the single mounting hole in the case. After wiring PB1 and the battery clip into circuit, the panel can be bolted in place using M3 or 6BA fixings.

TESTING

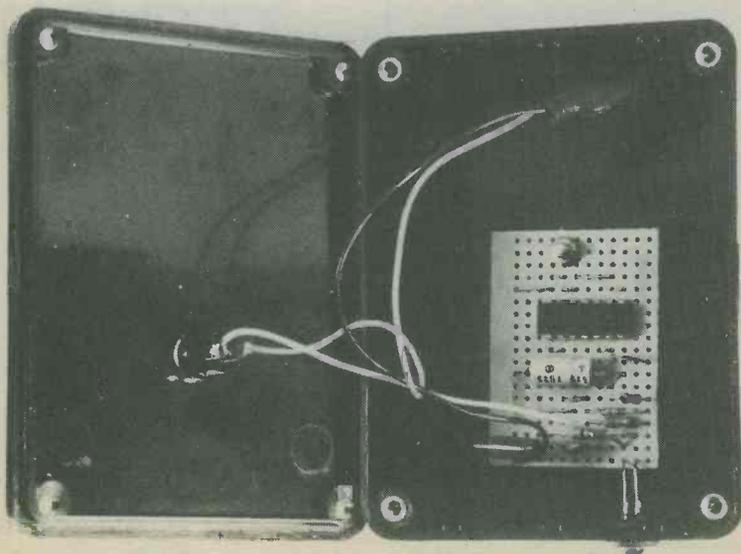With a multimeter set to read 100mA. f.s.d. (or set to some similar high D.C. current range) connected in series with the positive battery lead, depressing PB1 should give a reading of about 40mA. or so. If a greatly different reading is obtained, re-check the



The transmitter electronics in case.

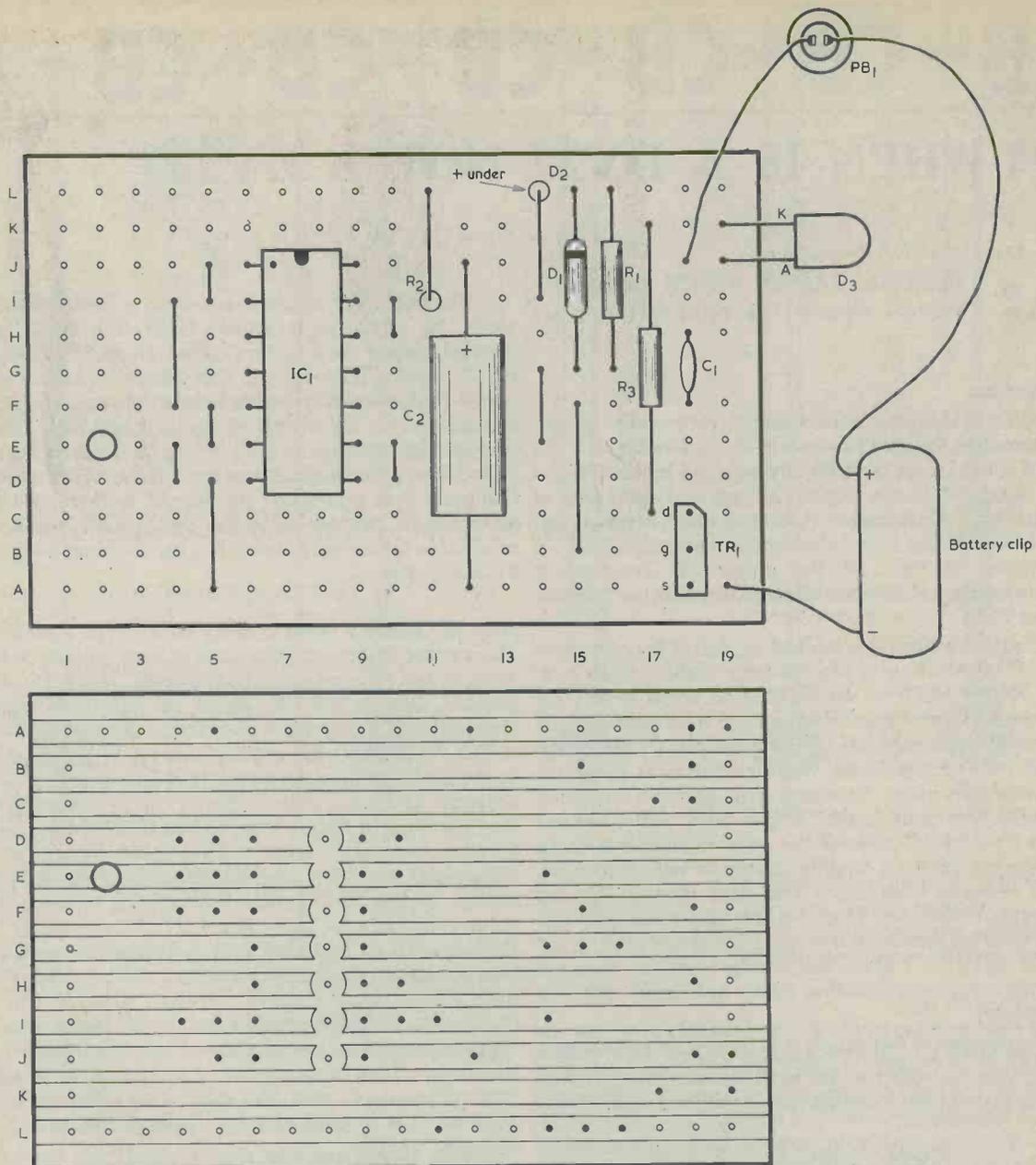


Fig. 3. The 0.1in. matrix stripboard layout for the Infra-Red Transmitter.

Transmitter Components

Resistors.

Miniature 1/3 watt 5%

R1 10K

R2 100K

R3 15 ohms

Capacitors.

C1 1.5nF ceramic plate

C2 10µF 10V

Switch

PB1 Push-to-make, non-locking type

Semiconductors

IC1 4001

Tr1 VN66AF

D1 1N4148

D2 1N4148

D3 CQY99

Miscellaneous

Small plastic case.

0.1in. matrix stripboard.

PP3 battery and connector to suit.

Wire, solder, etc.

wiring and check for accidental solder bridges between adjacent strips of the component panel. As a further check, a crystal earphone can be connected

across D3, and a fairly loud, high pitched tone should be produced when PB1 is operated.

(To be Continued)



Q: WHEN IS A DV27 NOT A DV27?

A: Read on, JAMES FINCH helps you to choose the right antenna.....

Introduction

The author of this article has recently returned to the UK after spending the past 12 years living in Sweden. For the past 10 years I have been legally engaged in the Citizens Band Business, in the buying, selling and designing of Citizens Band Accessories, Antennas and Transceivers. During this period I had the unique opportunity as an Englishman to visit all the major CB Transceiver Manufacturers and Antenna Manufacturers in the Far East and the USA.

I find it therefore very interesting, and at the same time rather disappointing to see the poor taste, and in fact, direct NON-FACTUAL advertising in some of the CB Magazines. In some magazines one can read some serious discussions about antennas, giving facts, and data, written by well informed persons, while on the next page are advertisements about Antennas with, gain-performance that make the mind boggle. If this were not a serious subject I would call some of the advertisements nothing other than a joke: i.e. mobile antennas with 6dB gain. Mobile antenna with extra 1dB gain through special treatment of whip. etc. One can only hope that once the system does become legal then the market will start to get cleaned up (with, I hope, some help from the very CB magazines that are printing some extremely dubious information).

The purpose of this article is to try and help the would be purchaser of a mobile antenna as to how to get the right antenna for the right requirement, and also from the right Antenna manufacture, into this jungle of advertisements with Companies trying to out-bid each other, using antennas as a "VOGUE" with fantastic names, colours and ridiculous claims of Antenna gains.

To try and keep this simple (there are many serious articles written about antenna gains, and radiation patterns etc. Most of them are beyond the scope of most readers, as this is quite a difficult field to explain in simple terms), I shall start off with one antenna type. The antenna I have chosen is the most well known mobile CB antenna in the whole of Europe (also the most copied) the DV27 reduced 1/4 wave glass fibre antenna. Fig. 1.

The main reasons for the popularity of the DV27 are:

1. One of the first European made CB antennas, been around 16 years.
2. Extremely efficient (good radiation efficiency).
3. Simple to mount, easy to fold over. Due to unique toggle mount (the V in the DV means 'toggle-joint' in Danish).
4. Flexibility. i.e. Many types of whips are available, from short 30cm long to full 1/4 2.6m long. All can be used on basic toggle-mount.
5. High quality parts-finish. If, of course, you select right manufacturer . . .

The first DV27 antenna was made in Denmark around 1965, by a Company called HMP (the HMP is an abbreviation of the founders name), all other subsequent DV27s were offshoots from this design for better or for worse (unfortunately worse in most cases). The actual designer of the DV27 and all the different HMP CB and professional antennas up to 1979 was an Antenna Engineer called Bjarne Sorensen. It can be said that HMP were the Company that pioneered the use of reduced 1/4 type antennas in Europe, using the toggle joint mount, and adjustable tuning pin mounted on tip of antenna whip for SWR adjustment.

How to Choose a Good Quality DV27 Type Antenna

The answer to this question is not so easy unless you know what to look for, and also what to avoid. There are, at the present time in the UK, about ten different types of standard DV27s, varying in price from approximately £3.80 to £13. WHY? Well, the original HMP type DV27 from back in the 60s soon became a standard European CB mobile antenna, and many other antenna companies jumped on the Band Wagon. Before long we had DV27, being made in Sweden, Denmark, Germany, Italy, Spain, Japan, Taiwan, Hong-Kong etc. Most of them from the outside looking similar to the HMP types. Well seeing is not always believing, that's for sure! Some DV27s, especially from Taiwan, are so bad that it is a disgrace to call them Communications antennas, let alone antennas. I am certain that some readers have already experienced the frustrations of not being able to get the SWR any way near right, or mounting bases falling apart, paint cracking on whips, glass fibre cracking, hollow soft metal tubing which bends or breaks for ever. Never buy a set with a give away antenna, it is in most cases a 'nothing' antenna, of the cheapest quality.

If you are offered a DV27 type antenna, (not a HMP or a Procom type), then ask the salesman to bend the whip double. Do not do it yourself, as he might try and make you pay for a new whip. It should bend over and spring back into position again without any bends, cracks, etc.

Another very good quality type DV27 antenna to be found on the UK market comes under the Brand name PROCOM, these antennas are also made in Denmark, and all of their antennas are to be highly recommended. One of the main reasons they have made such advances on the UK market is that these antennas are just not a mirror copy of the HMP, as the person who has designed all the PROCOM antennas is none other than Mr Bjarne Sorensen who now works from Procom Antenna Company. There are a couple of points worth mentioning for the unknowing. The PROCOM antennas are once again very similar to the HMP types, but on closer inspection you will notice, that

1. The cable plug connecting cable to mount is a different size.
2. The HMP whip will not fit a PROCOM mount, but it will the other way around.

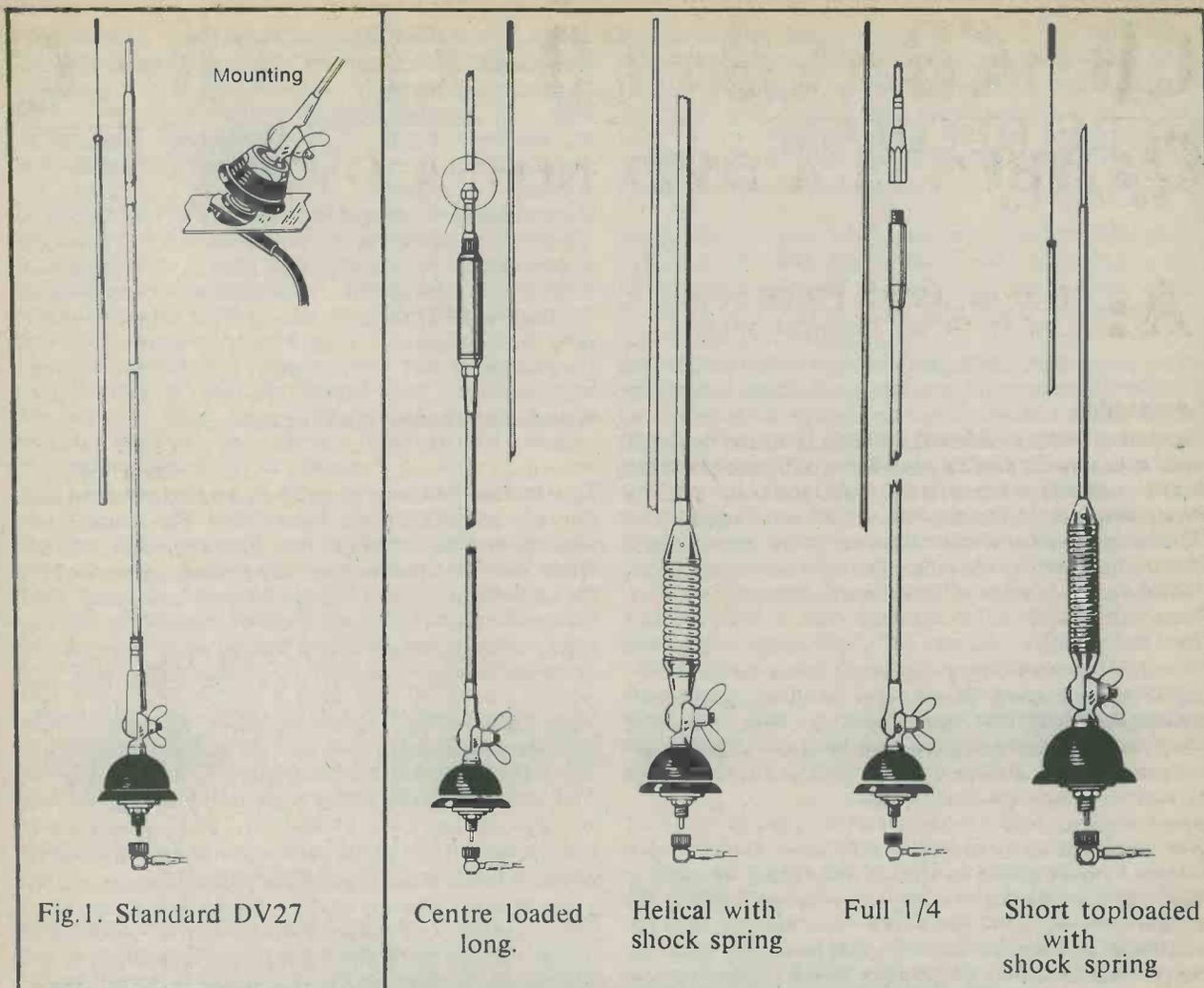


Fig. 2. Groups of Whip Antennas

Both companies offer a very wide range of whips for these mounts. Both companies have two different mounts.

- 1) Standard type with cable plug.
- 2) Low profile mount for roof mounting.

I have not tried to push any one brand antenna although I have mentioned the name of HMP many times. This is quite natural as they designed and made the first DV27, and that is what we are talking about. Having personally used many types of Citizens Band antennas in Sweden for the past years, in a climate which to say the least is pretty rough in winter, then I can only recommend the antennas that have proved, over a time, to be both mechanically and electrically of good quality, to the potential purchaser.

Most antennas from the following companies are to be highly recommended: PROCOM, HMP, ALGON, CARANT, UA, KATHREIN, HIRSCHMAN, WISI.

It is an interesting point, but a fact, that in Scandinavia approximately 99% of all the CB and professional mobile antennas, used by Police, Fire Brigades, Government Departments etc. are made in Europe. The same applies for West Germany and Holland, and the UK. It seems that in this field the Europeans can still compete successfully.

Which DV27 Model (Whip-Mounting Base) to Select?

The number of DV27 whips available is very considerable. I do not propose to list any directly, as I

am not advertising for any Antenna manufacture. I suggest you obtain a catalogue from your local dealer of DV27 type antennas, from any of the companies listed above. Basically the whips fall into the following groups. (See Fig. 2).

1. Top loaded whip (long size) (short size)
2. Centre loaded whip (long size) (short size)
3. Full length 1/4 wave
4. Helical wound whip (long size) (short size)
5. Most of the above types with or without shock spring
6. Most of the above mentioned whips, with standard mount or Low Profile mount.

Depending on what type of vehicle, van, truck, sports car, saloon car, bus, etc. so you will have to decide what length of whip you want, and where to place it on the vehicle. Depending on where you place the antenna will of course effect the radiation pattern you obtain. Normally the higher the better, and the longer the whip the better. Do not fall into the trap many advertisements would have you believe, that their 60cm long super antenna is better than a standard 1.5m length. If you mount a shortish whip on the car roof, then you can always buy an extra whip which is longer and use it when you want to make contact when you are parked for instance, or in the countryside.

Good luck with your antenna, and remember that a good copy is not always due to the pounds your putting out. It's how well your antenna is putting them out!

LET'S HAVE A LITTLE MORE DECORUM, PLEASE.

Make	Type No.	Serial No.	Location
Kenwood/Trio	TR7800	1040911	Brentwood
Sommerkamp	TS280	8300025	Glasgow
FDK	Multi700E	02259	
Yaesu	FT7B	9H040405	Lincoln
Sommerkamp	TS240	9000180	Bolton
ICOM	IC255		Lincoln
Sommerkamp	TS280FM	8300212	Romford
Yaesu	FT101E	8H351814	Brentwood
Sommerkamp	Switched power linear		Brentwood
Yaesu	FT207RB	9M20204	Brentwood
Trio	TR2400		

Quite apart from the legality (or otherwise) of CB in its present illicit form, there is a very insidious side effect, in the shape of the sudden increase in theft from, and tampering with, vehicles apparently fitted with CB radios. Mosty CB'ers don't know the difference between a CB radio and a perfectly legal piece of amateur equipment — but since these fellons imagine that anyone possessing a CB radio would not be willing to disclose its theft to the police (for obvious reasons) they feel they can indulge to their hearts content.

Not surprisingly, owners of legal radio equipment assailed by these characters are getting just a bit fed up. Very few users of amateur band equipment are willing to leave their gear in the car overnight — or even in a public car park any longer. Antennas get unscrewed (or simply hacked off), and the whole situation is very tiresome indeed.

The legalization of CB will tend to deter thefts from a couple of viewpoints — firstly the 'black market' in them will disappear overnight. In fact, after the experience of the US where the market was so saturated and overburdened — that one of the trade 'in' jokes suggested that there were dealers breaking into cars at night to fit CB radios! The second deterrent is the fact that the subject of the theft will not be illegally possessed, and thus the owner will be only too anxious to go and burden the crime statistics at his local police station.

Some observers have likened the present CB situation to that of the way in which drug takers are exploited by both the 'pushers' and any other shady elements who can use their illegal dependance to further criminal aims.

So R&EC is going to try and help to make life a little harder for these unfortunate characters, by offering rewards to anyone supplying information leading to the arrest and conviction of anyone found guilty of theft or criminal damage in connection with amateur radio and CB equipment. We are also offering free space in these pages to publicise the descriptions and serial numbers of stolen equipment.

The reward we offer is up to £100 (or 50% of the fine imposed on the guilty party, whichever is less) for any information that leads to a conviction for the theft of — or interference with — legally possessed CB and amateur radio equipment fitted to a car. If the owners of the rigs whose descriptions we give would care to add to this reward, then they are at liberty to do so.

So far, we have gathered a few names and numbers in conjunction with Arrow Electronics Ltd., but we expect to hear of many others:

We all need friends, good buddies . . .

This feature has been at pains to try and point out that the only good CB'er is a legal CB'er. The moment you step across the threshold into illegality, then you are doing your bit towards the undermining of respect for the Law and all that is implied by such behaviour. Most CB'ers would certainly not consider themselves on a par with rioters throwing petrol bombs, but where do you draw the line between the law and an illegal act?

Mass disobedience seems to have aquired a very insidious respectability — and the unfortunate truth is that a lot of the responsibility must fall on governments who have been perennially too weak to uphold the rule of law, either by stubbornly and thoughtlessly maintaining totally unworkable laws, or failing to clamp down on offenders with adequate resolve.

Not surprisingly, perhaps, some of the more influential Home Office civil servants are very uncertain as to the benefits of the legalization of CB, which is seen as the criminal's answer to the use of radio by the police. If the police cannot do anything about the currently totally illegal CB situation, how on earth are they going to be able to sort out legal and illegal users — when the only visible difference on the set is very easily copied indeed?

It would be surprising if anyone was daft enough to use the legal CB allocation for criminal purposes, since the legal band will be used and monitored to such an extent as to make the idea laughable. The reservations lie in the continued use of illegal 120/280 channel AM/SSB equipment, covered by the cloak of respectability offered to legal users.

The rather unhelpful remarks made by CB lobbyists on their view of the legal situation indicate that acquiescence to the power of reasoned argument is still not one of their social graces, and that they will continue to use whatever frequencies and powers they like until the cows come home. Naturally enough, the Home Office feel that they have been more generous than any other European authority in the specification that they have offered — so the gloves are gradually coming off, and illegal users are being rounded up at the rate of over 100 a week in the London area alone. Courts have been told to get tough, since the once apparently reasonable arguments put forward by those collared about the 'unavoidability', the civil 'rights' aspects of CB, and the fact that the rest of the world has 'it' have crystalized into a very definite situation at last.

Furthermore, the Home Office now has a simple, cheap and 100% effective device to issue to police forces that will clearly show the difference between a legal and an illegal user — both as a general monitor, and as a specific test instrument once the suspect vehicle has been apprehended.

If UK CB had merely adopted the status quo, then CB would have been a worthless mess inside 6 months. As it is, we have a very good chance of maintaining a workable service indefinitely — assuming those with pretensions to 'DXing' do the sensible thing and proceed to amateur radio — which as we have said before, is really very simple if you are at all keen. If CB'ers wish to gain the cooperation of police (and amateurs) in their emergency network groups, then it will only happen if the rules are observed and a degree of social responsibility is evident.

Finally, how you would like it if any 17 year old could pick up a set of keys and thrash down the M1 at 70 mph in a 32 ton truck? The closest parallel that actually seems to make some impact on the more hardened CBER is the very obvious one of the driving test. CB is a provisional licence if you like, or cruder still, the ability to ride a push bike on the air waves, without offering CB the potential to foul up essential emergency communications and navigational systems that is implied in the scope offered to the demonstrably more knowledgeable radio amateur operator.

On yer bike

On the occasions that confessed CBERs 'come out' and go to an amateur radio club to try and find out more about their new found fascination in communication via radio, rather too many clubs have simply 'asked' them to clear off . . . or else. Rather than try to educate the breakers in the benefits of amateur radio, and the folly of risking their necks with an illegal rig, it seems that the reception afforded to CBERs is going to create a big chasm between the two closely associated groups that is leading to some form of totally unnecessary conflict. Spiteful reactions are all too simple when there are vulnerable things like repeaters, and CB rigs labelled "2m transceivers" readily accessible to the thwarted CBER wishing to get into amateur radio.

Outraged of Chelmsford

CB is a topic that is guaranteed to extract an extreme response from anyone with an opinion on the matter. The interminable correspondence in the electronics press bears witness to this fact.

But one aspect of CB that hasn't been too closely examined is the relationship between CB and amateur radio — and if ever there was a league of opinionated fraternities, amateur radio enthusiasts would come in the top half. The Masons couldn't hold a candle to the average amateur radio club (or is it a pair of compasses? I never did understand the funny handshakes either . . .) when it comes to coded speech and 'knowing' looks.

This is not to say that such attitudes are necessarily to be condemned, but that any organisation operating along the lines of the Cosa Nostra has potential for

trouble through misinformation, and the general blanket of subversiveness that surrounds the hobby. Many is the time that the writer has been having QSO (ratchet) on the 2m band, only to find from subsequent comments and third party revelations that half the local amateur population have been eavesdropping without bothering to let their presence be known.

As far as CB goes, radio amateurs tend to polarize in favour of CB, and those who would dearly like to see all breakers whipped to death with the nearest DV27. Those in favour tend to be able to see the benefits to the amateur fraternity, as CB inevitably draws a bigger following to 'real' amateur radio. After the rather bad press image afforded to amateur radio by such infamous events as the Tony Hancock "Radio Amateur" sketch, and the general 'eccentric boffins' image retained by most members of the public, they should be grateful that CB has given amateur radio communication a relatively normal image at last — at least, as long as the jargon can be kept under control.

On the other hand, the first of these R&EC supplements was received at one amateur radio club as the next worst thing since Ghengis Khan. This information was passed second hand onto us by one of the more enlightened members who couldn't really understand what the fuss was about, since it appears the contentious bit was the publication of the table of frequencies of the 120 channel sets.

Well, we're very sorry if the fact that some of these occur in the 10m amateur band has engaged the wrath of some amateurs, but that just happens to be a fact of life. A fait accompli, and not likely to be influenced by anything we have to say. Larger powers than the amateur radio associations have been distinctly impotent when it comes to trying to sort out the basic problem of the original 40 channels.

Many breakers with these 120 channel rigs have no idea what the frequencies are, and so they have no idea that they have absolutely no hope of ever being legalized in Europe — let alone the UK. Many CBERs think that these extra channels are simply conjured out of the existing space available through some miracle of modern technology. If anything, publishing these frequencies will tend to inform CBERs that these rigs gobble up an unacceptable additional chunk of the precious spectrum.

Furthermore, there is a motto in the amateur radio world known as "use or lose". This basically refers to the lack of activity on many amateur bands, and the fact that if the bands were not more fully occupied, chunks of spectrum might be taken away for more worthy causes. It is only really since the availability of ready-made 'plug it in and switch it on' equipment for amateur radio that the hobby has got going in a big way, and also enabled the seedier elements to make their unwelcome presence felt on too many of the 144MHz repeaters.

So before there is much more sanctemoneous preaching about the evils of CB, some amateurs might reflect sheepishly on their own contribution towards the furtherance of constructive technical achievement within the hobby. A net deficit to our balance of payments more frequently results from their participation in the hobby.

A SCANNING MONITOR RECEIVER SYSTEM

Part 1

L. Power

The rapid growth of 'private' telecommunications (as opposed to the broadcast variety) has encouraged a market for receivers capable of monitoring this activity – both in the capacity of surveillance devices, and as simple receivers for listening to 'what's happening'.

Applications range from receivers for the 35MHz model aircraft band to check activity on the channels being used for model aircraft, to 144MHz (2 metre) band receivers to check propagation conditions, and general activity. This is especially useful for local repeater frequencies where most basic 'calling' is routed these days. Other uses include boat owners who need to check the local VHF frequencies for emergency and general harbour information, and anyone else with a need for checking activity in sectors of the VHF NBFM communications spectrum from 25MHz to 200MHz.

THE 'R&EC' BAND MONITOR

Commercial scanners are available from a number of sources. Many of these oriental marvels tend to be overcomplicated (but a lot of fun nevertheless) and manage to cover virtually every communications band from 30MHz to 515MHz. But many users of a scanner simply want to keep an ear open on three to ten local communication channels to see what's going on, and find the £200+ spent on one of the more comprehensive scanners is not necessary. The device described here can be built for £40 or less. In fact, as little as £25 with careful buying (excluding crystals).

The scanner described here is very versatile and lends itself to being built to cover any two bands in the range 25MHz to 200MHz, simply by selecting the correct coils for the RF and mixer stages. The bands are restricted in width by the practical consideration of the design of tuned circuits, but work out to be about 2-6% of the chosen centre frequency, depending on the RF tuned circuit coupling factors.

In other words, one band might be the 35.050 to 35.250MHz model aircraft band, and the other might

be 144-146MHz for the 2m amateur band. The choice of RF coils and the crystal frequency used in the oscillator are the only variables.

This scanner is the first in a long line of R&EC radio projects that will cover the entire spectrum of radio interest from LF to UHF (and beyond). It is to be presented in a proprietary case for visual appeal and general enhancement, since one of the major 'turn offs' for the home constructor is the relatively indifferent finish and appearance of what might otherwise be an exceedingly good project.

The scanner has been derived from a number of ideas and designs, and should offer the constructor both an opportunity to save money, and get a thorough insight into the way in which commercial equipment is designed and constructed.

Despite the apparently daunting complexity of the circuit, the availability of a PCB design greatly simplifies the construction of this project, and brings it within the scope of many enthusiasts with a basic appreciation of some of the finer points of RF construction – namely the special brand of patience available only to enthusiasts.

WHAT DOES IT DO?

The scanner provides 2x8 channels of coverage, this may be 2 separate bands in the region of 25-200MHz (NBFM) or it may cover 16 channels in a single band.

When active, the receiver clocks along a row of LEDs on the front panel to indicate which channel is 'active', and which one of the 2 blocks of 8 channels currently being scanned is indicated on a further LED lamp when the scanning process is halted.

The receiver 'squench' (interstation muting) remains shut whilst there is no signal present on any of the channels being monitored – but when a signal appears on a channel, the sequencing is stopped, and the loudspeaker is activated. The squench and volume levels are both preset by front panel controls.

The complete receiver unit built into the case supplied with the kit.



The LED remains lit above the appropriate channel indicator until the transmission ceases – and after a brief pause (determined by presettable values in the circuit) – the scanning is resumed until stopped by a signal once again.

However, there are many instances where some of the 'local' and frequently used channels may not be of interest, and so it is essential to be able to bypass them from the scanning process – or the receiver will remain permanently 'hung up'. One solution is to pull out the crystals – but this is obviously tedious in the extreme, so the circuit incorporates an electronic bypass system which can be switched in to skip unwanted channels.

BLOCK DESCRIPTION

Fig. 1 outlines the basic approach of the scanner, which will be seen to be a relatively straightforward double superhet system.

The signal from the antenna is routed to the active RF section via diode switching, according to the output of the sequencing counter. From there, the signal passes through a bandpass pair tuned circuit (using top capacity coupling) in front of the RF stage.

The RF amplifier is nothing very exotic, being a straightforward transistor amplifier using self biasing. The output is fed to a second bandpass pair before the mixer. The mixer stage converts down to 10.7MHz for the first IF, where the crystal filter provides roof-

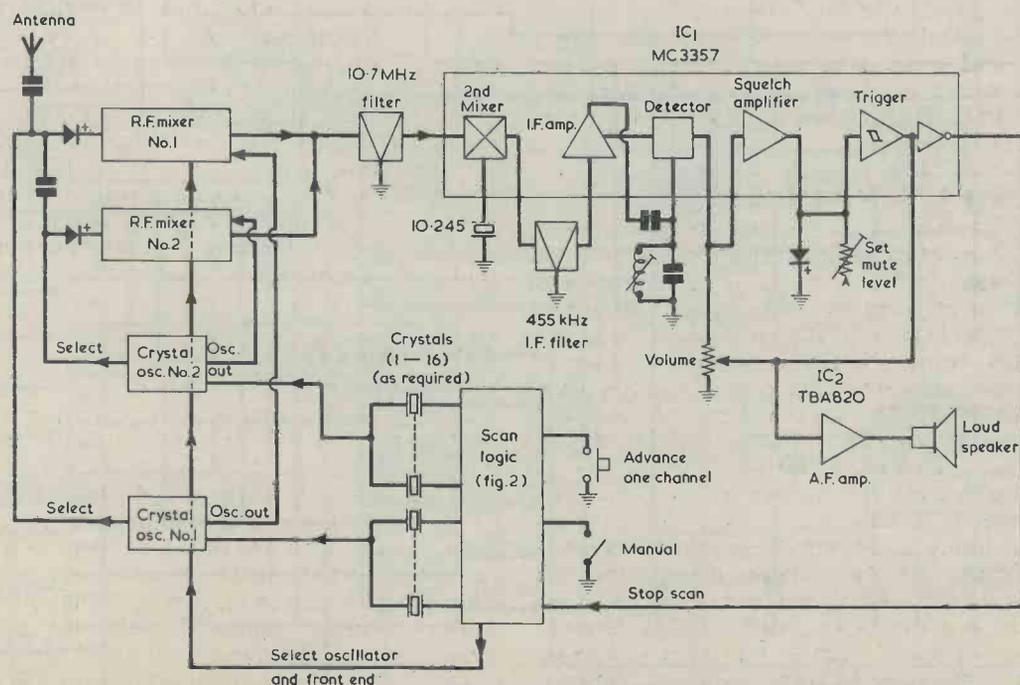


Fig. 1. Block schematic of receiver. The oscillator and mixer stages are duplicated to allow scanning over two widely separated bands.

ing selectivity to prevent unwanted image responses occurring at 10.7MHz-910kHz as a result of the second conversion to 455kHz.

The main signal processing is carried out in an MPS5071/MC3357 IC, which includes all the features necessary to accept the 10.7MHz IF input, and provide demodulated audio output with squelch amplifier, detector and 'switch'. The device includes a 10.245MHz 2nd conversion oscillator, balanced mixer, 455kHz IF amplifier, detector, noise amplifier and squelch gate with hysteresis. All that remains is the audio amplifier, which is a simple TBA820M stage to drive an internal loudspeaker. If additional volume is required for any reason (mobile applications) then a higher output amplifier may be desirable - but this should be fitted externally, and possibly

built into the extension speaker device itself. The basic receiver has been designed for minimal current consumption in applications where a switched (as opposed to automatically scanned with its relatively thirsty logic) receiver is required, the overall consumption can be as low as 9ma.

The scanning system logic is described in Fig. 2. A simple two transistor astable oscillator provides the system clock and drives a 7493 using a 3 bit binary counter connected to a 74145 one-of-ten decoder.

Switching between the two 'front ends' of the scanner is achieved by dividing the MSB of the counter by 2, and using the output to select one of the two 'front ends' in alternating sequences of eight.

The clock is stopped by the squelch line going 'low' - or by switching the same line manually.

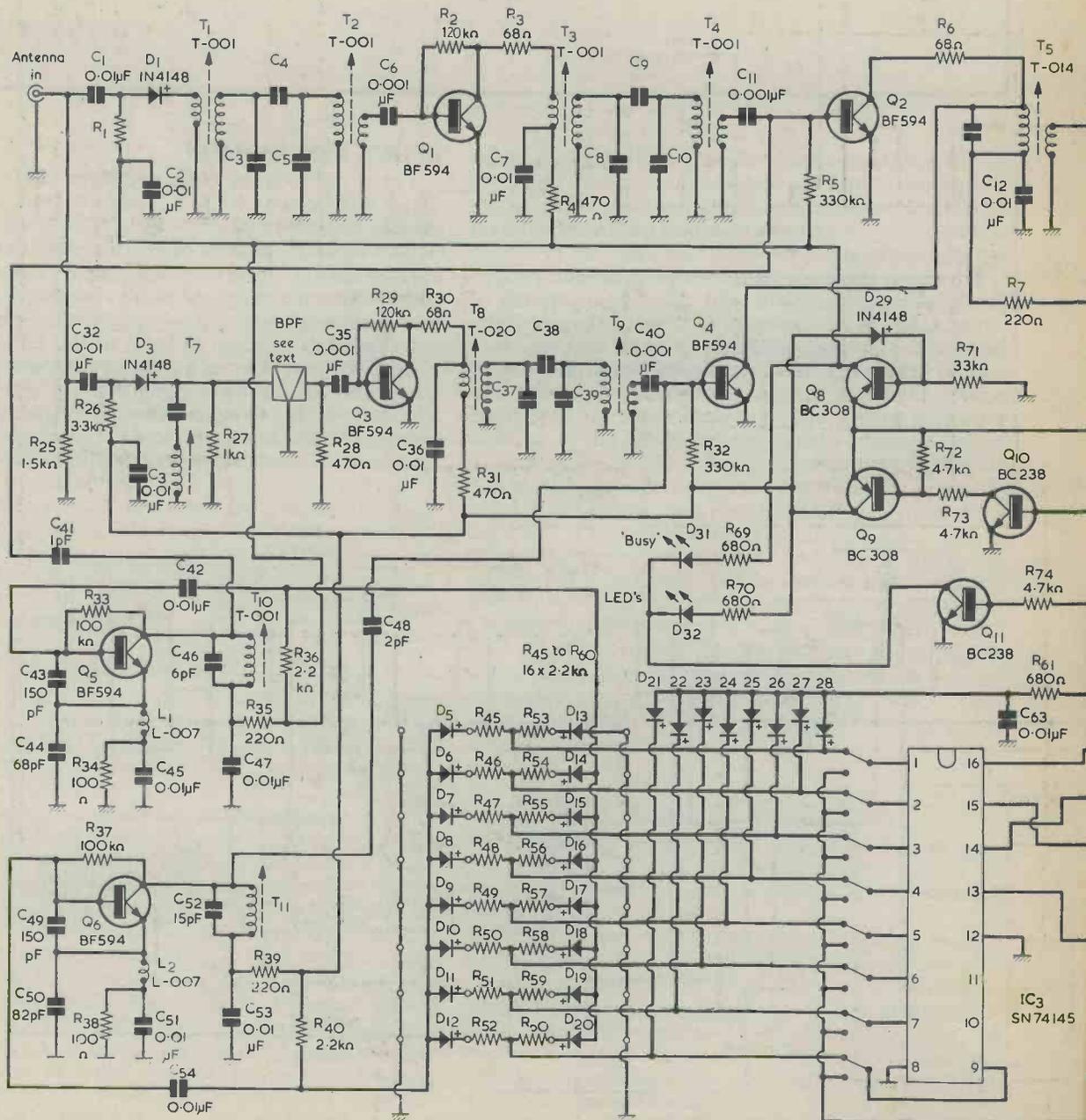


Fig. 3. Circuit of complete receiver. Details

THE CIRCUIT DESCRIPTION (Fig. 3)

The RF/IF/AF sections . . .

The antenna is connected via the switching diodes D1 or D3 to the appropriate front end as selected in the scanning circuitry. A nominal 50/75 ohms impedance is used.


Two top coupled bandpass pairs using two standard coils and capacitors selected according to the frequency range required (Table 1 in Part Two) determines the RF response on either side of the RF amplifier transistor. The RF stages are thus fixed bandwidth, and can operate over a relatively narrow range based on the centre frequency selected. The use of ganged tuning with varicaps would enable a 20%-30% range to be achieved, but this is not the

prime function of this receiver. The actual bandwidth is determined by the coupling capacitor (C4/9). Mathematical analysis of top coupled filters is available (Reference 1).

The two mixers, Q2 and Q4, are fed from the crystal oscillators (Q5 and Q6) selected by the scanning logic.

These oscillators are standard Colpitts devices, using a tuned emitter load to ensure operation on the 3rd overtone of the crystal. The crystal frequency is selected according to the formula:
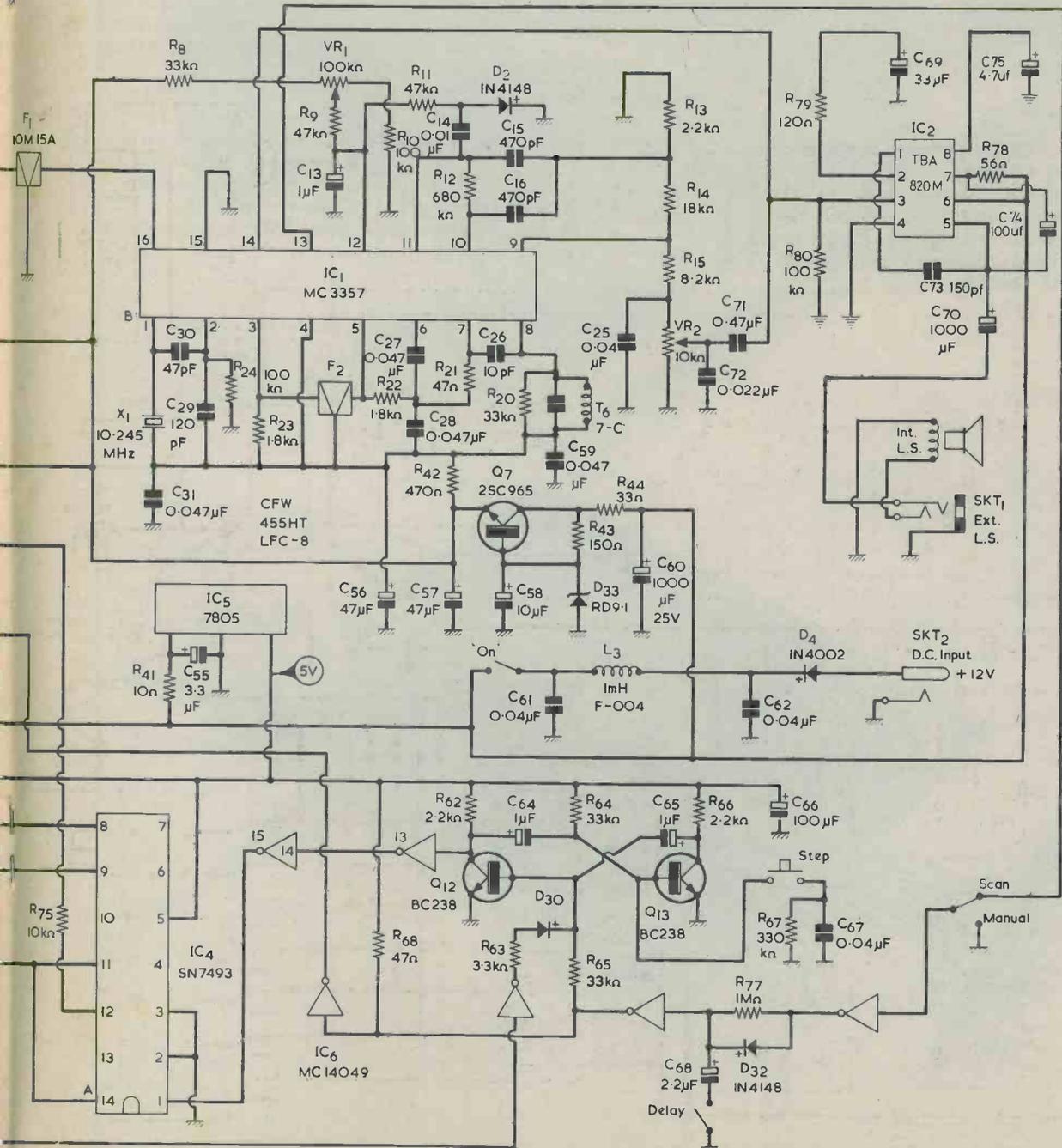
$$\frac{\text{Desired RF frequency} - 10.7\text{MHz}}{3}$$



Parts of the main IC (IC1) are shown in Fig. 4.

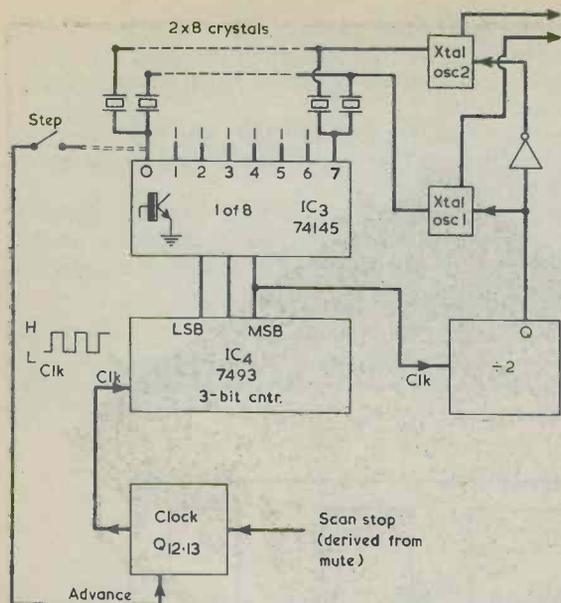


Fig. 2 . The automatic scanning logic. Sixteen channels can be scanned in two separate bands of eight. The frequency coverage of each band is determined by the choice of crystals and coils, explained in paragraph "The RF/IF/AF sections".


Crystal type should be parallel resonant, 3rd overtone cut, 20pF load (or 30pF if C44 is increased to 82pF). The injection frequency is determined by the collector circuit, which is set to 3x the crystal frequency.

The 'self-oscillating' tripler is a highly effective method of producing the necessary injection to the mixer but the level of oscillation is relatively low. Injection via the base circuit is best – but it does mean that the circuit does not readily lend itself to feeding FET or MOSFET mixers, which require at least a volt of LO for optimum operation. A separate tripler amplifier is necessary for FET/MOSFET mixers.

The two mixer transistors feed a common output IF transformer at 10.7MHz, which matches into the monolithic two pole crystal filter – used for 'roofing' selectivity, as opposed to the narrower 'channel' selectivity provided later on. The main purpose of this filter is to suppress the -910kHz images that arise from the second conversion derived from mixing 10.7MHz with 10.245MHz.

Everything from 10.7MHz IF to audio output is contained within IC1 – so it is as well to consider this device in some detail (Fig. 4). The input at pin 16 is to one half of a balanced mixer, the other half of which is fed from the Colpitts oscillator formed around pins 1 and 2, with the external conversion crystal.

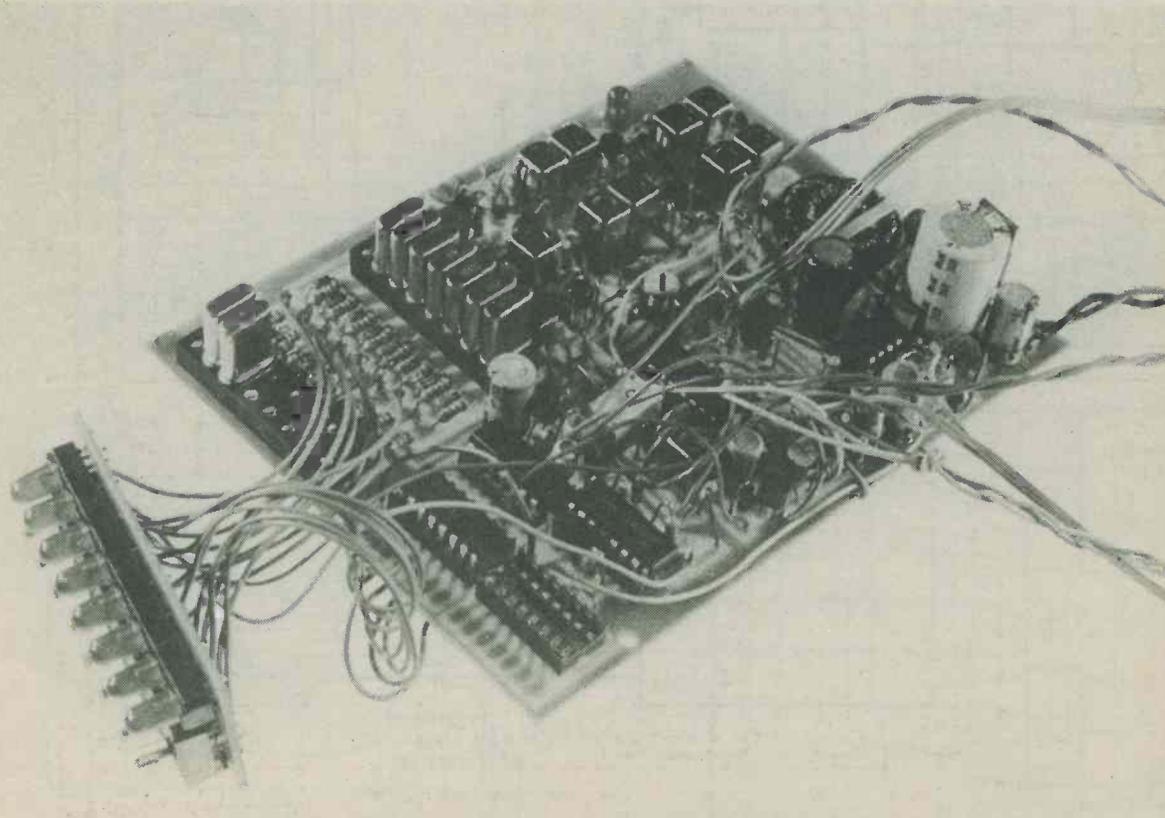The mixer output is resistively terminated at pin 3, to match the input impedance of the main channel filter – a multi element ceramic ladder filter of



The internal construction of the complete receiver.

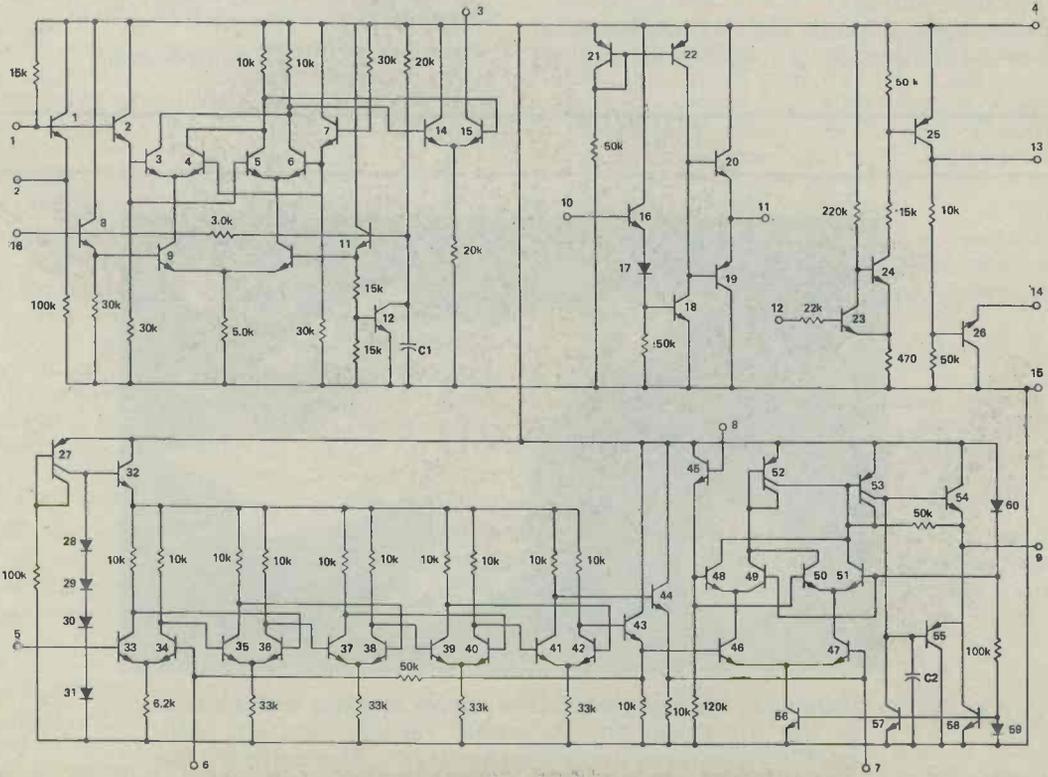
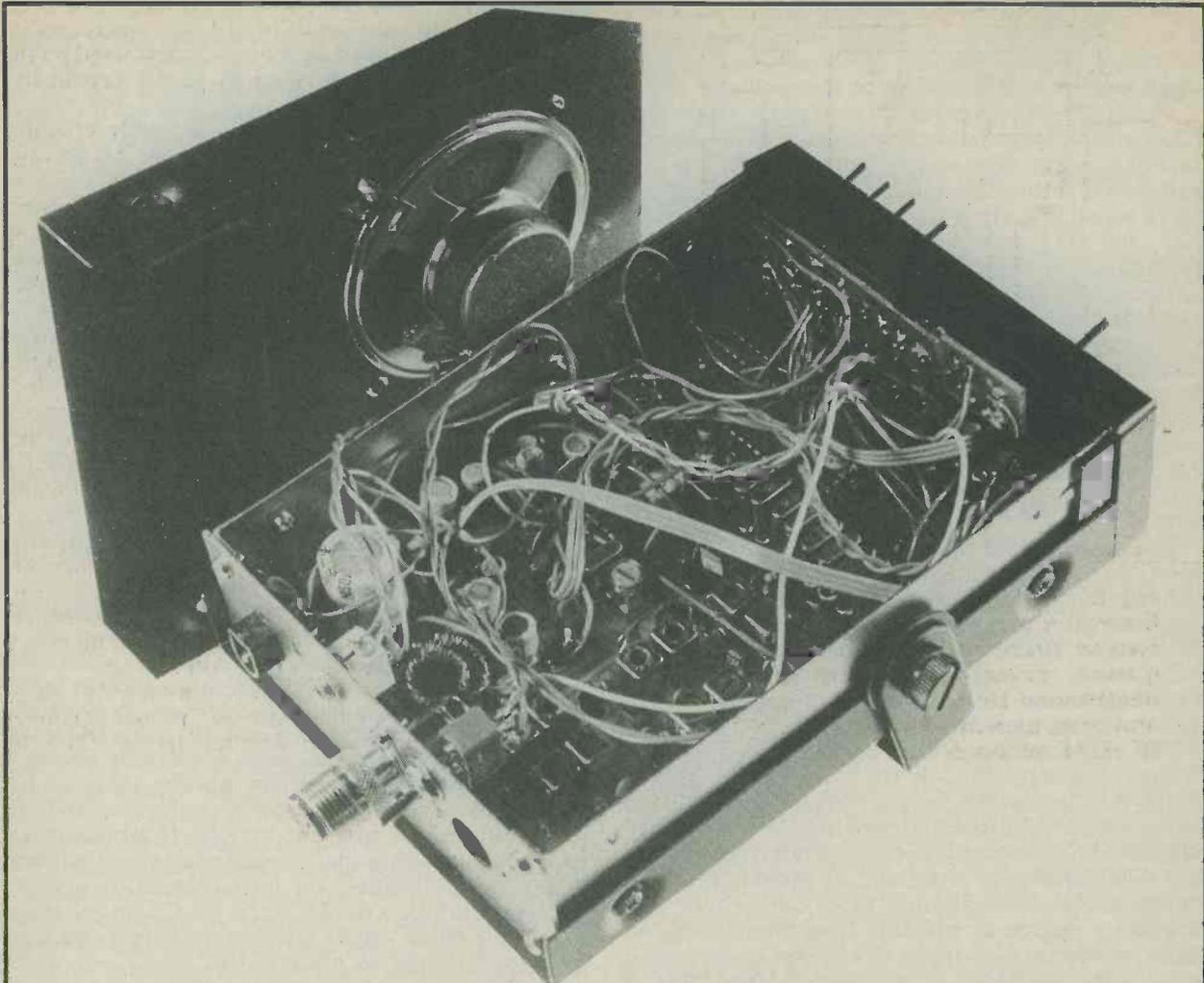


Fig. 4. Details of the internal functions of the main IC.

approximately 8kHz-12kHz bandwidth. Since there is no direct mechanism for trimming the crystal frequency, it is as well to err on the wide side here to cover some of the tolerances at the oscillator stage.

The limiting IF amplifier input at pin 5 is biased by R22, which also terminates the filter in the correct impedance. The IF amplifier output at pin 7 is also terminated at the same bias point, and so decoupling the IF signal to earth at the conjunction of C28, R22, C27, and R21 must be very effective. A low RF impedance capacitor is essential in this position.

The quadrature detector phase shift coil at pin 8 is a straightforward 455kHz IF transformer with a Q of between 100 and 150. The deviation-to-audio conversion is too efficient for this level of Q, so the coil is damped by R20 to achieve an audio level to suit the deviation in use. For the 2m amateur band, deviation levels of 5-7kHz are commonplace, but for commercial frequencies, the deviation levels are kept to 2-3kHz, allowing more scope for a higher Q component.

The audio output appears at pin 9 of IC1, and is immediately fed to the inverting input of an 'on-chip' operational amplifier active filter at pin 10 of IC1, in a bandpass filter configuration with centre frequency set at about 10kHz. In other words, well above the audio band, and only likely to be activated by the broadband noise characteristic of a limiting FM IF with no signal present.

The output of this noise amplifier appears at pin 11, and is then rectified by D2 to provide a signal to switch the input of the Schmidt trigger at pin 12. An external mute adjustment is provided by VR1, which alters the DC bias on the mute Schmidt trigger input, and thus adjusts the threshold of operation. Good voltage stability is essential here, and whilst C13 provides a degree of isolation from the spikes and audio present on the supply, an effectively decoupled series pass regulator is necessary – and this is provided by Q7 and D33.

The mute trigger output at pin 14 is connected to the input of the audio stage, IC2, so that the audio is

shorted to ground (via an internal switch of IC1) when the muting is active – and open circuit when a signal is being received.

IC2 is a simple, cheap and efficient 1W audio stage of which little more need be said. See the manufacturer's data sheet if you want to delve deeper (Reference 2).

The scanning logic . . .

Most of the description of this section is covered in the analysis of the block diagram and Fig. 2. The actual switching of the crystals is achieved by grounding the appropriate cathode of diodes D21 to D28, thus enabling the crystal whose anode is being fed from either R40 or R36, according to the status of the scanning sequence through Q8 and Q9.

Bypassed channels are simply selected by switching the appropriate output of the 74145 back to the transistor astable, causing it to prematurely reset and thus advance the 7493.


5v for the logic is provided by a cheap 5v regulator – IC5 – which also keeps the switching noise out of the rest of the circuit.

POWER SUPPLY

The unit operates from a 12v supply. Unless the sequencing logic is omitted, the consumption is too high for primary cell battery operation. A thorough RFI input filter is provided just after the DC input jack, to prevent external hash (especially useful if used in vehicles) from getting into the sensitive RF stages. D4 is the reverse polarity protection, and can save you a lot of cost and trouble. If problems are experienced with audio motorboating and general instability or 'chatter' on high volume, it may be necessary to place the DC feed to IC2 on the input side of the diode – or to increase the supply decoupling capacity close by pin 6 of IC2.

Construction and testing will be covered in Part Two . . .!


(To be Continued)

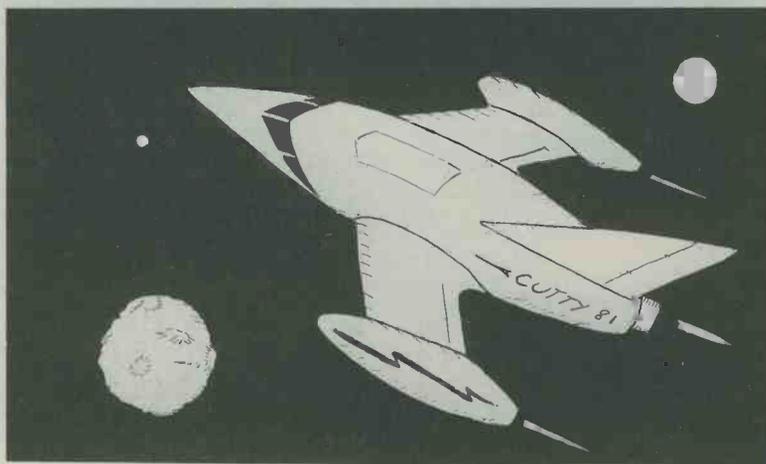

"We have a suppressed state power storage malfunction in the unilateral entertainment receiver system skipper!" "What does that mean Scotty?" "The battery's flat on the tranny Skip."

SHORT WAVE NEWS

FOR DX LISTENERS

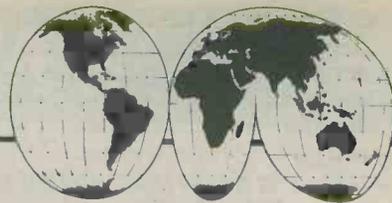

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Continuing with our review of some of the results achieved during the last far-eastern season (see the previous issue of this journal) we commence with an often reported station but on a not often reported frequency.

● NORTH KOREA

Pyongyang on a measured **7203** at 0855, OM with announcements in an Asian vernacular, sign-off after some military music. This is thought to be the termination of the Korean programme for the Near and Middle East and Africa, probably scheduled from 0800 to 0855. Information from North Korea is sparse to say the least!

● NEW CALEDONIA

Turning our attention to the Pacific area we did manage, after several attempts, to log Noumea on **7170** at 0830 one morning last January. A moderate signal on a clear channel produced a log entry from the time shown up to 0858 when Vienna opens with its tuning signal and blasts Noumea right off the air! The reception of Noumea however was unmistakable, OM with announcements and station identification in French at 0831, this being followed by music from a mandolin-type instrument. The power is 20kW.

● VANUATU

Formerly the New Hebrides, Vanuatu may be logged by listening for Port Vila operating on **7260** where we heard it at 0801 on the very last day of January.

This one has a power of just 2kW and, as one might expect, it is quite difficult to log. OM with a newscast in vernacular – several Pacific place-names mentioned – according to the schedule the language used would be Bislama. Reception was on LSB to avoid adjacent channel QRM but the signal slowly faded until lost under the noise at 0812.

AROUND THE DIAL

In which are listed some of the transmissions recently received which may interest some readers and also act as a general guide to what may be heard via the short waves.

● U.S.S.R.

Moscow on **17790** at 0837 with a relay of Orbita 1 and 2 programme for Soviet Youth. This programme is scheduled from 0815 to 0900.

Moscow on **17795** at 0832 when radiating the Standard Chinese programme to China, scheduled

from 0700 to 0900 on this channel and in parallel on **17860**.

Moscow on **17820** at 0810 with the Russian language 5th programme "Pravda Review", timed from 0800 to 0815.

Moscow on **17880** at 0840, classical music with announcements in English in the World Service, scheduled from 0200 through to 1500 on this particular channel.

● CZECHOSLAVAKIA

Prague on **17705** at 1557, male and female announcers with alternate items in the English programme for Africa, South Asia, the Far East and Europe, scheduled from 1530 to 1625.

Prague on **9605** at 1500, station identification at the commencement of the Czech programme for Africa, South Asia, the Far East and Europe, scheduled from 1500 to 1530.

● SWITZERLAND

Berne on **9535** at 1340 when radiating a talk about world affairs in the English programme to the Far East, South and South East Asia, North America and Europe, scheduled from 1315 to 1345.

Berne on **9725** at 0434 with a review of local affairs in the English programme for the West Coast of North America, scheduled from 0430 to 0500.

● NETHERLANDS

Hilversum on **9895** at 1340, a commentary on world affairs from the Dutch point of view in the English programme for Europe, scheduled from 1330 to 1420.

● VATICAN CITY

Vatican on **9645** at 1450 with a news review of internal affairs, mostly religious, in the English programme intended for the UK and Eire and timed from 1445 to 1500.

● WEST GERMANY

Cologne on **17765** at 1110, OM with a newscast of African affairs in the English programme beamed to Central and East Africa from 1045 to 1115. Into the Swahili programme at 1115.

● EAST GERMANY

"Radio Berlin International" on **9730** at 1440, OM with a talk about public libraries in the German Democratic Republic, all in the English programme for East Africa and scheduled from 1415 to 1500.

Berlin on **9665** at 1257, OM with station identification in German then into the Arabic programme for the Near East, South Arabia and North West Africa, scheduled from 1300 to 1415.

● AUSTRIA

Vienna on **9770** at 1500, station identifications in English and other European languages then into a newscast in the German programme for Europe, scheduled from 1430 to 1600.

● ITALY

Rome on **9575** at 1555, interval signal (bird-song), OM station identification followed by the Italian programme for Europe, timed from 1555 to 1635 on this channel.

● POLAND

Warsaw on **9525** at 2005, OM with a newscast in the English programme directed to Africa and scheduled from 2000 to 2030. Also logged in parallel on **9675**.

● EGYPT

Cairo on **9455** at 0426, religious chants in the Domestic Service General Programme which may be heard on this frequency from 0400 through to 0645.

● CHINA

Radio Peking on **11635** at 0854 with a review of agricultural achievements in China in the English programme intended for Australia and New Zealand and scheduled on this channel from 0830 to 0930.

Radio Peking on **17680** at 0858, female announcer with the Indonesian programme for Indonesia, scheduled from 0830 to 0930.

Radio Peking on a measured **17533** at 0859, 'East is Red' theme then OM in Chinese to South East Asia scheduled from 0900 to 1000 but heavily jammed soon after commencing the programme.

● VIETNAM

Hanoi on **9840** at 1346 with announcements in the Cambodian Programme for South East Asia scheduled from 1100 to 1200.

● PAKISTAN

Rawalpindi on **5010** at 0135, OM with religious chants, OM announcer, identification as "Radio Pakistan" at 0140. Logged on USB to clear an unmodulated carrier on channel.

Islamabad on **5060** at 0150, OM announcements in vernacular, local songs and music in typical style. A good clear signal at this time. Both these channels are 'seasonal'.

● AFGHANISTAN

Ariana Radio and TV Service, Kabul, on **4740** at 0205, OM with song in vernacular then local music on a mandolin-type instrument in the Home Service 1 programme scheduled here from 0125 to 0330 and from 1340 to 1930.

● GABON

Libreville ("Africa No. 1") on **4811** (originally heard on **4807.6** which would have effectively blotted out Sao Tome) with a programme of recorded pops and announcements in French. All part of the current French plan to 'push' the language interna-

tionally and equal, if not surpass, the BBC with its English language world coverage. They'll have a mammoth task to rival the Moscow emanated World Service in English!

● CAMEROON

Garoua on **5010** at 0504, a newscast in English of African and Middle East affairs then "More news in English at 0700". Into African songs and music at 0506. The schedule is from 0500 to 0700 and from 1700 to 2200 and the power is 100kW.

● BOTSWANA

Gaberones on **4845** at 0617, local songs and chants complete with drum beats, a good signal in the clear at this time. The schedule is from 0400 to 0630 and from 1500 to 2100 (Thursdays to Saturdays inclusive from 1430). The power is 10kW.

● CONGO

RTV Congolaise, Brazzaville on **3265** at 1838, OM in vernacular then into local music and songs. This one has a schedule from 0400 to 0700 and from 1700 to 2300. The closing time is variable as is the frequency. The power is 50kW.

● VENEZUELA

La Voz de Carabobo, Valencia on **4780** at 0125, OM with an excited commentary on futbol! The schedule is from 1000 to 0400 and the power is 1kW.

Radio Mundial, Bolivar on **4770** at 0333, OM song in Spanish, dance music Latin American style. The schedule is from 1000 to 0400 and the power is 1kW.

● NICARAGUA

La Voz de Nicaragua, Managua on **5950** at 0330, OM station identification in Spanish, many announcements with place-names. Schedule unknown. Power 50kW.

● ECUADOR

Radio Federacion, Sucua on **4960** at 0319, announcements in Spanish, folk songs and music in typical local-style. The schedule is from 1030 to 0300 (Sundays from 1100). Closing time on Saturdays is 0400 and on Sundays at 0100. The power is 5kW.

● COLOMBIA

Radio Neiva, Neiva on **4855** at 0451, OM with songs in Spanish with local-style folk music. Station identification at 0455 as "Radio Centro". The schedule is from 2300 to 0530 but on an irregular basis. The power is 1kW.

Radio Guatapuri, Valledupar on **4815** at 0438, OM station identification in Spanish, commercials, local pops on records. The schedule is around the clock and the power is 10kW.


Ondas del Meta, Villavicencio on **4885** at 0202, OM with a long political talk all about Colombian affairs. The schedule is from 1000 to 0500 but has been reported closing as early as 0410 on occasions. The power is 1kW.

● PERU

Radio Atlantida, Iquitos on **4790** at 0411, OM pop song in Spanish, OM announcer. The schedule is from 0900 to 0500 (Sundays until 0400) but sometimes radiates around the clock. The power is 1 kW.

TRADE NEWS

High specification magnetic tape heads

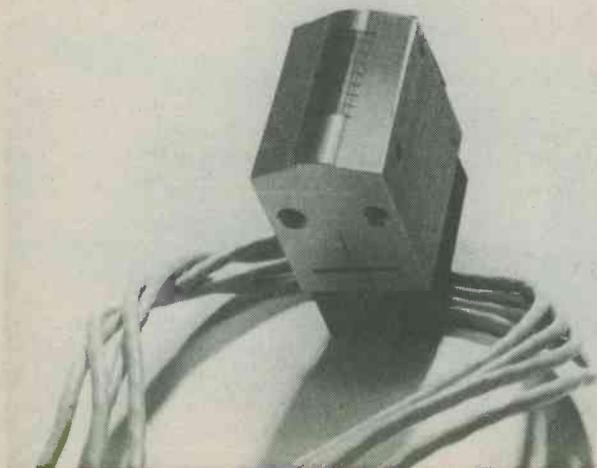

Marketed exclusively in the UK by Patrick Cole, P.O. Box 14, Sevenoaks, Kent, the new Bogen GmbH range of Magnetic Tape Heads has been specifically designed for high quality Audio, Data and Copying applications with special Hall Effect and customer specified heads also being available.

Covering tape widths of 3,81mm, 6,35mm, $\frac{1}{2}$ " and 1", the Audio Heads cover cap lengths ranging from $<1\mu\text{m}$, to several μ . Optimum sensitivity, frequency response and, in particular, long term stability, is achieved in all cases by special material selection.

In Copying Head format speed variations ranging from 1:1 to 64 times normal speed can be accepted with, dependent upon operational conditions, slave or master head core material being selected from Recovac, Sendust or ferrite material, thereby significantly increasing service life.

Bogen Data Heads, using solely Recovac core material, cover storage densities of from 800 frpi to 9000 frpi and have either flat, radial or hyperbolic face profiles, individually adapted to the requirements dictated by the operational speed and storage density. When used for instrumental purposes, wide-band 1 and wide-band 2 ranges can be covered which, in conjunction with ease of adjustment make these heads uniquely versatile. Further increase in service life is achieved by hard-chromium plating or oxide//carbide coating of the metal contact surface.

Hall Effect playback heads, as well as, for instance, individual designs for video-sound equipment, speed-independent information evaluation, and special control purposes are also available or can be designed/customised dependent upon normal commercial criteria.

Soundex crack the IEC 468-2 noise problem

The new Soundex AMM 200 Noise Meter is a small economically priced instrument exactly meeting the difficult CCIR 468-2 specification, for the measurement of audio frequency noise in broadcasting, recording systems and on sound programme circuits.

A vital feature of the AMM 200 is its overload warning light. This is imperative because amplifier stages before the weighting network may overload at frequencies attenuated by the weighting network and therefore not be apparent by the meter reading.

With a measuring range of -100dB to -8dB , (-80dB to -10dB selected by push buttons in 10dB steps and 22 dB of calibrated meter scale), the AMM 200 has a balanced P.O. jack input terminated to either 20K ohms or 600 ohms as selected by a push button.

A front panel BNC socket provides a means of looking at the measured signal on an oscilloscope, either before or after the weighting network filter.

Mains operated on a double insulated power supply, the dimensions are 175 x 113 x 67mm (7" x 4" x 2 $\frac{3}{4}$ ") and the weight 1.2Kg (2 $\frac{3}{4}$ lbs).

Produced to meet the company's concept of a range

of very portable audio instruments for the engineer, whether working in the field, the studio or on general test bench work, it comes complete and ready to use with Broadcast Weighting network as standard.

A range of plug-in alternative filters will be available in the near future.

The Soundex AMM 200, is very competitively priced at £350. Enquiries to Soundex Ltd., Park Lane, Broxbourne, Herts.



current. During the timing period it allows virtually the full 9 volts from battery BY1 to be applied to the radio connected to the output terminals. There is a voltage drop across TR1, of course, but it has a typical "on" resistance of only about 4R and the voltage drop will be insignificant when the circuit is used with any conventional 9 volt radio. Closing S2 bypasses TR1 and allows the radio to be used normally.

The length of the timing period, during which the Q output IC1 is high, is governed by a resistance connected between pins 2 and 3, and a capacitance connected between pins 1 and 3. The nominal duration of the timing period is $2.48 RC$ seconds, where R is in megohms and C is in microfarads. In this circuit the capacitance is given by C1 and C2 in series. The 4047 is not suitable for use with a plarised timing capacitance, but in the present application the very long timing periods require an electrolytic component. The well-known technique of using two electrolytic capacitors connected in series with opposing polarity has therefore been employed, and in practice this gives reliable results provided the capacitors are good quality types (which, in any case, they would have to be in any RC timer circuit incorporating a high timing resistance). It will be in order to use capacitors with a higher working voltage than 16 volts if these are more readily available.

With S1 in the "3" minute position the timing resistance is given by R3. In the "5" minute position the timing resistance is R3 plus R2, and in the "7" minutes position R3, R4 and R1 are all in series to provide the timing resistance.

It should be noted that the actual timing periods will almost certainly be longer than the nominal values ascribed to them. First, the calculated periods are a few seconds longer than the nominal periods. Second, electrolytic capacitors have values which, on average, are greater than those marked on them. This is simply because tolerances on value of electrolytic capacitors are typically -10% to +50%. The third reason for extended periods is that a small leakage current will flow in the electrolytic capacitors. The cumulative effect of all these factions is that, for instance, the timing period given with S1 at "7" may be 8 minutes or more. This effect is not of any real significance in a non-critical application such as the present one.

No on-off switch is required as the unit has a negligible current drain of only about 1 microamp under standby conditions, and this will not seriously affect battery life even if a small battery is used. Most of the standby current consumption is leakage current in TR1, and IC1 has virtually no current consumption in

The output leads pass through the rear panel of the case and are terminated in a connector (or connectors) suitable for the particular radio used.

COMPONENTS

Resistors

- (All .25 watt)
- R1 1MR 5%
- R2 1MR 5%
- R3 1.5MR 10%
- R4 10MR 10%

Capacitors

- C1 100 microfarad electrolytic, 16V. Wkg.
- C2 100 microfarad electrolytic, 16V. Wkg.

Semiconductors

- IC1 4047
- TR1 VN10KM

Switches

- S1 4-pole 3-way rotary (only 1 pole used)
- S2 s.p.s.t. miniature toggle

Miscellaneous

- Case
- Veroboard, 0.1in. matrix
- 9 volt battery
- Battery connector (see text)
- Control knob
- Nuts, bolts, wire etc.

the standby mode. Even when IC1 is triggered it still only draws a current of about 10 to 20 microamps, whilst TR1 requires no significant gate current since it is a voltage rather than a current operated device and has an input impedance of thousands of megohms. Thus, the addition of the timer should not result in any noticeable reduction in battery life. Note that even the tiny current in TR1 will be eradicated if the radio is turned off at its own on-off switch.

CONSTRUCTION

The size of the case required for the unit will depend on the battery to be employed. The author's unit is housed in a Verocase type 202 21041C, which has dimensions of 153 by 84 by 59mm, and this is large enough to accommodate a PP3 or PP6 battery. (The old Vero part number for this case was 75-1238-D).

The two touch contacts are fitted at the top panel of the case and, when these are used instead of a push-button, it is necessary to have a case with a top panel made of insulating material. The contacts consist of



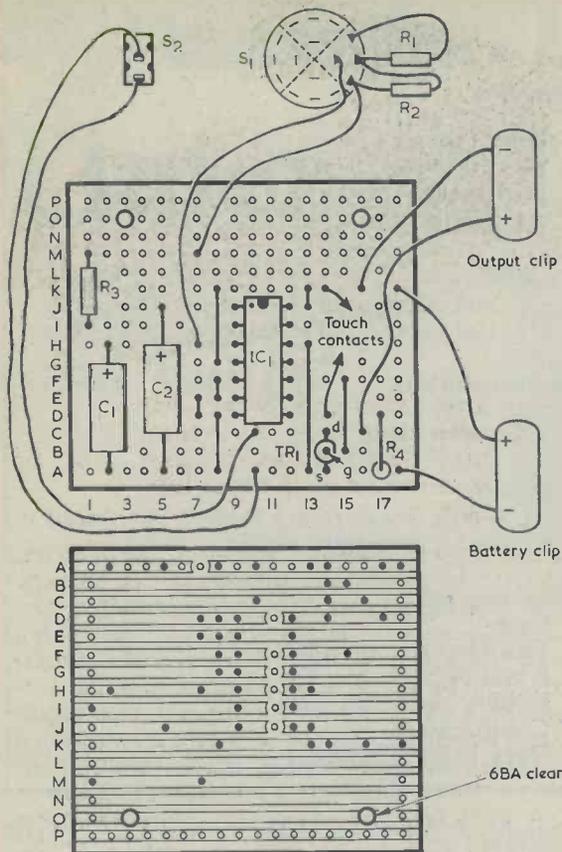


Figure 2. The component and copper sides of the Veroboard panel, on which most of the components are assembled. The output clip connects to the battery clip of the radio, hence its apparent reversed polarity.

two M4 panel-head screws with solder tags under their nuts inside the case to facilitate connection to them. The two screws should be mounted with very little space between them.

S1 and S2 are mounted on the front panel. A hole is required in the rear panel for the output lead and, if the panel is metal, this hole should have a grommet fitted to it.

Most of the components are assembled on a piece of 0.1in. Veroboard having 16 copper strips by 18 holes. Details of this board and all the other wiring of the timer are given in Fig. 2. After the board has been cut out, the two mounting holes should be drilled and the seven breaks made in the copper strips. The board is then wired up as shown. IC1 should be the last component to be soldered in place, and the soldering iron must have a reliably earthed bit. R1 and R2 are mounted on S1 and not on the board. Check the positioning of the inside and corresponding outer tags with an ohmmeter before soldering to S1, as relative positioning of the tags with some switches may differ from that shown in Fig. 2.


The two battery clips in Fig. 2. are shown as PP3 types. The output clip may appear to be connected with incorrect polarity, but this is because it mates up with the correct polarity clip in the radio. If the receiver has PP9 style clips, and if a battery with PP9 type terminals is fitted in the timer unit, individual clips at the ends of flexible wires will need to be fitted instead of the 2-way clips shown. The two output clips will again be of apparent opposite polarity. Take care to ensure that the supply to the radio is correct polarity, as damage could result if a supply of incorrect polarity is applied.

The component panel is mounted by means of two 6BA bolts and nuts at any convenient place on the bottom panel of the case, leaving sufficient room for the battery. Spacing washers on the 6BA bolts keep the board underside clear of the inside surface of the case.

If it is desired to have a push-button instead of the touch contacts this is wired up in place of the contacts. The push-button should be of the press-to-make type. A "cancel" switch can also be added, and this may consist of a press-to-make push-button wired up in series with a 1kR resistor, as shown in Fig. 3. Pressing this push-button will bring a timing period to an end.



The Veroboard module. This carries all the small components except R1 and R2.

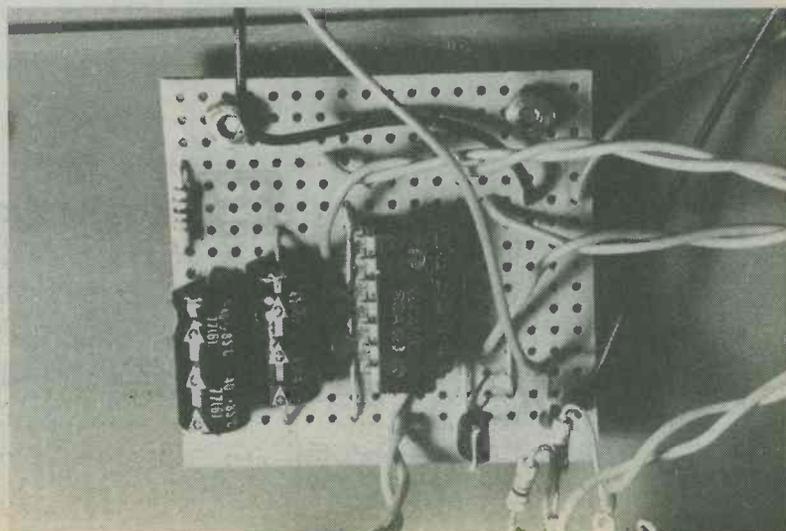


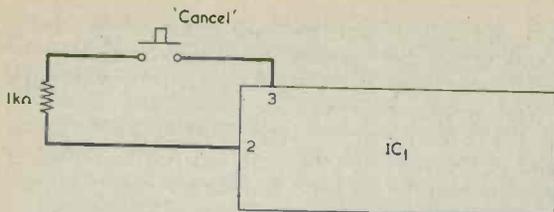


Figure 3. If desired, a "cancel" push-button can be connected to the circuit, as shown here. When pressed, this brings timing period rapidly to a close.

CONNECTING TO THE RADIO

With most radios there will be no difficulty in taking the output lead of the timer into the radio battery compartment, and it will merely be necessary to leave the battery compartment cover slightly open to provide an opening for the lead. If preferred, a small notch can be cut in the battery compartment cover to allow the lead to pass through with the cover fully closed. If there is any risk of the timer output and radio battery clips touching any metalwork or connections inside the receiver they should be covered with insulating tape. PP9 type connectors should be covered with insulating tape in any case, because of the possibility of their short-circuiting each other.

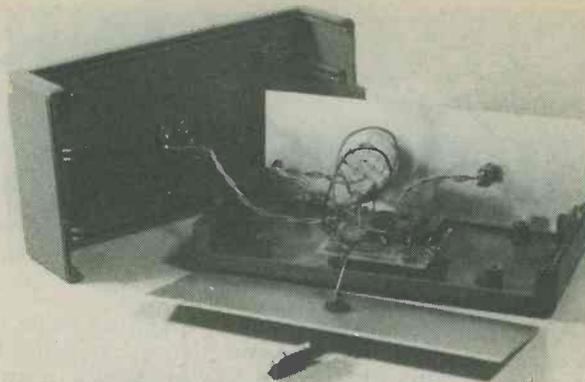When completed, the timer unit is ready for testing. It is possible that IC1 will trigger when the battery is first connected but, after that, control will be exerted



The prototype timer unit with the case disassembled. The Veroboard panel is mounted on the case bottom.

by the touch contacts only. The lengths of the timing periods for the three positions of S1 can then be checked, bearing in mind that these can differ from the nominal periods. If, as is desirable, C1 and C2 are good quality new components, the first few timing periods could be significantly different from the subsequent ones. This is merely because electrolytic capacitors which have been in stock for a long period require a short-time with voltage applied for the electrolytic to "form", and it is not a fault condition.

The VN10KM specified for TR1 is available from several retail sources, including Maplin Electronic Supplies.


New all aluminium instrument cases

Recently introduced by ZAERIX Electronics Ltd, a new series of 70mm high, all aluminium instrument cases is available in 10 sizes ranging from 150 x 150mm to 300 x 200mm deep.

Comprising a unique 4 piece construction, the top and bottom covers of these ECOBOXES can be independently removed from the 1.5mm thick front and rear panels, which incorporate pre-punched holes and deformable teeth, thereby providing integral supports for pcb's and chassis etc.

Eminently suitable for both development and OEM applications, the front and rear panels of these inexpensive cases are professionally finished in natural coloured anodised aluminium, with the covers in aesthetically contrasting matt black.

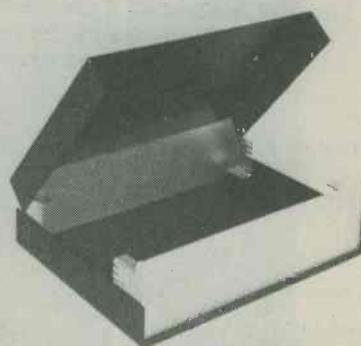Enquiries to Zerix Electronics Ltd., 46, Westbourne Grove, London.



NEW ALL ALUMINIUM INSTRUMENT CASES

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 80p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.


COMPULINK

SERIES – No. 1:

Compu-link is a new series in which we hope to provide sufficient practical and theoretical information, to enable the reader to construct micro-processor based projects which “really do something!”

Introduction

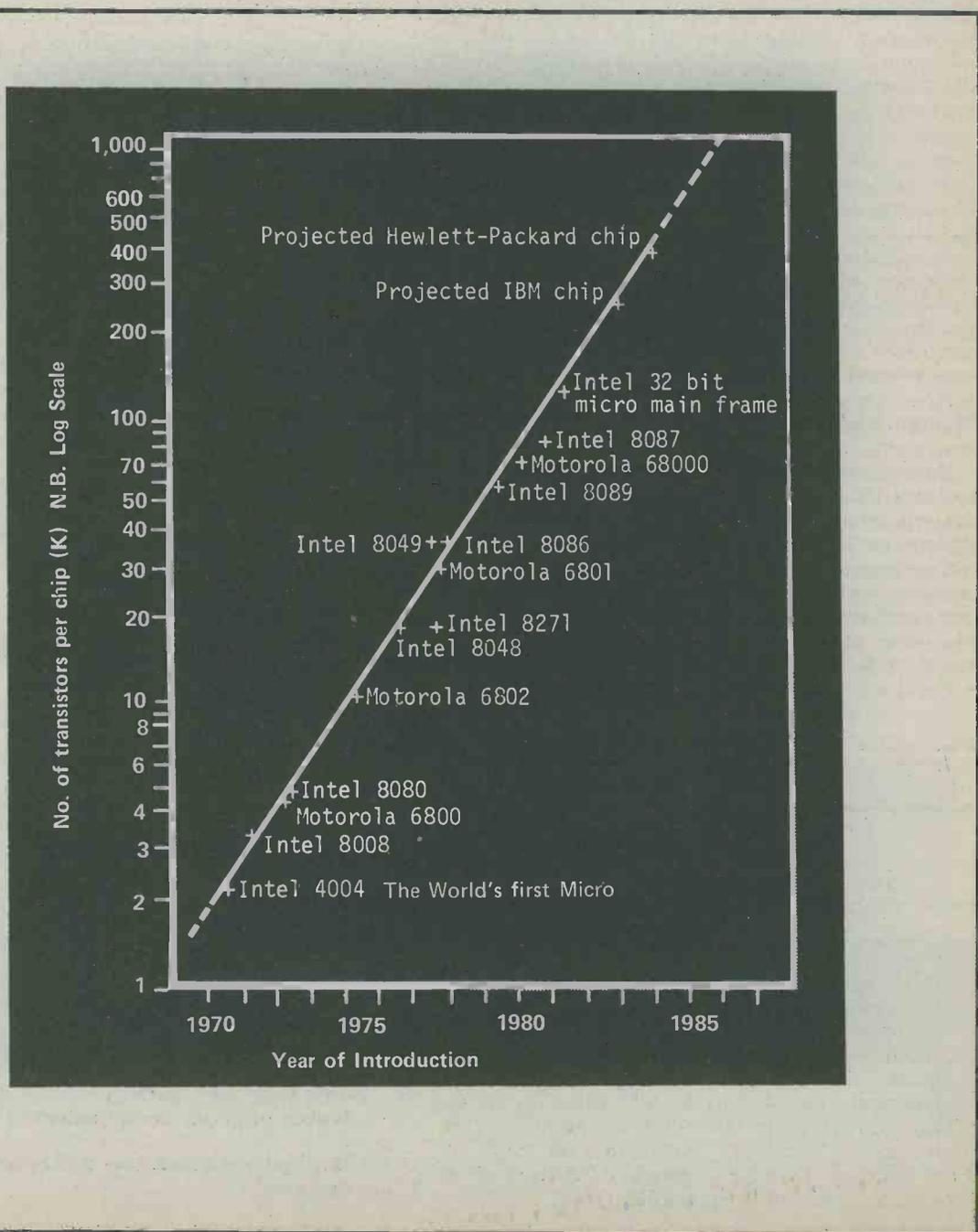Advances made in integrated circuit design during the mid seventies has meant that instead of only being able to incorporate several hundreds of active devices on a single integrated circuit die (the chip) manufac-



turers were able to build devices using tens of thousands of active devices. This technology which became known as Large Scale Integration, meant that products previously constructed from numerous Small Scale Integration parts (such as many of the standard 74xx series logic parts) could now be produced on a single custom Integrated Circuit.

This ability to shrink the size of an application from a bench-full of devices to one single integrated circuit, meant that many products which would have previously been impossible to manufacture due to the high cost of assembly or even the sheer bulk of the electronics, were now quite feasible.

The new technology was quickly put to work producing high volume consumer applications such as digital clocks/watches and simple personal calculators. However the initial cost of development was extremely high and could only be successfully amortised if the final application was to be of tremendous volume. Moreover, the resulting integrated circuit was so specific that it could only be used in that one particular application, therefore it was very susceptible to being overtaken by a new and better device from a competitor.

What was needed was a truly universal "logic" element which could be produced in high volume and then characterised or programmed for the customer's final application, thus the idea of a micro-processor was born.

The first micro-processor was produced by Intel Ltd as the basis of a scientific calculator they had been asked to design. Two design solutions were pursued, one based on the production of yet another custom integrated circuit and the other based on the production of a universal programmable controller or micro-processor, the processor solution was finally adopted and the first commercial use of micro-processors had begun.

At the time the full implications of this new device had not been fully realised and Intel were quickly overwhelmed by people wanting to use micro-processors as the basis of a new product. This tremendous commercial pressure ensured the rapid development of new and better offerings by all semiconductor 'Giants', and has accounted for the phenomenal rate at which advances have been made in the availability and application of micro-processors.

It is interesting to note that the intended applications of these new devices were not as personal computers, but rather as intelligent control elements in consumer equipment. It was probably the American computer hobbyists who first used micro-processors as personal computers, and opened the way to a whole new previously unimagined industry.

Motorola semiconductors now feel that by the end of this decade each household in America will contain some ten micro-processors in applications as diverse as washing machines, energy management and conservation. (e.g. intelligent central heating controllers and personal computers/diaries).

Already the availability of serious business/scientific computers for under £5,000 coupled with the availability of personal computers such as the Sinclair ZX81 for around £50 means that many of today's engineers and enthusiasts are already learning and developing the new technology of "personal computing".

In future issues of *R & EC* we hope to provide an 'in depth' review of the background to the development of the micro-processor coupled with an original and instructive course on the elements of programming and small computer system construction, but most importantly of all, we intend to develop a number of control applications for you to construct and use.

These applications will hopefully include such things as intelligent burglar alarms, lighting and heating controllers, waveform generators, test equipment, morse and TTY decoders and perhaps, most excitingly of all, control of complete radio/audio systems. The technology now exists to enable the enthusiast to build a fully synthesised radio offering features such as preset stations, search scanning for activity, timed recording of programme material and many other facilities that a micro-processor based unit can provide.

As we intend to devote ourselves to developing the control side of micro-processors, we will be describing a custom control unit based on a well known processor chip, and offering 8-16 programmable outputs and a similar number of programmable inputs. This unit will then be used as the basis of the constructional features. Sufficient information will be given to enable readers to programme the units themselves or if they prefer, to buy already programmed units from *R & E.C.* ■

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who have become the subject of liquidation or bankruptcy proceedings and who fail to supply goods or refund money. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

Universal 12v 5W amplifier

Most people will have come up against the problem of trying to obtain spare parts for imported consumer electrical equipment. The most frequent and troublesome part for many radios, cassette recorders, tape players, and other radio equipment is the audio output integrated circuit. A good example is the Hitachi HA1366 IC which is very widely used in many types of car radio, cassette player and CB radio, but is officially designated obsolete by the manufacturer. Whilst it would suit Hitachi very well if persons requiring spares threw the equipment away and bought a new set, this does seem a rather drastic solution when there is a cheaper alternative.

This project describes such an alternative, in the shape of a micro-sized universal audio amplifier replacement based on the TDA2002 IC, which is available from many manufacturers and widely used in European car radio and audio equipment. The rather high quiescent current consumption makes this device unsuitable for battery equipment, but as a replacement for the many obscure types of audio IC which seem to fail with monotonous regularity in Japanese and Far Eastern in-car entertainment, it is an excellent solution. The integrated circuit itself, is not a pin for pin replacement for any of the fragile Japanese devices it replaces, and so it must be fitted as a complete entity with its own peripheral circuitry.

However, from the illustrations and diagrams you will see that the complete unit requires only a minimal amount of space, and is therefore readily accommo-

dated in most types of equipment. Some care needs to be taken with regards to the earthing as far as ground potential considerations are concerned, and with the almost universal application of the negative earth for vehicles, this is not a severe problem.

As a further point in its favour, TDA2002 is a great deal less likely to fail in use than the devices it will be replacing, and so should be a once and for all substitution.

FIRST THINGS FIRST . . .

The first thing you need to do is establish that there is in fact room in your piece of equipment for the board described herein. Bearing in mind, that you may remove the existing audio IC and all components directly connected thereto to make room, and so this should not present much of a problem. The main thing is to locate the audio input and this is easily traced by following the wiper on the volume control to the audio output IC. (Fig. 1). The output should present little trouble either, since this can be traced back from the loudspeaker leads. This just leaves the positive supply, which can be located either using a multi-meter or simple visual inspection.

If you actually possess the handbook for the equipment concerned, it is very likely that a circuit diagram and parts list will enable easy identification of these features without having to resort to trial and error.


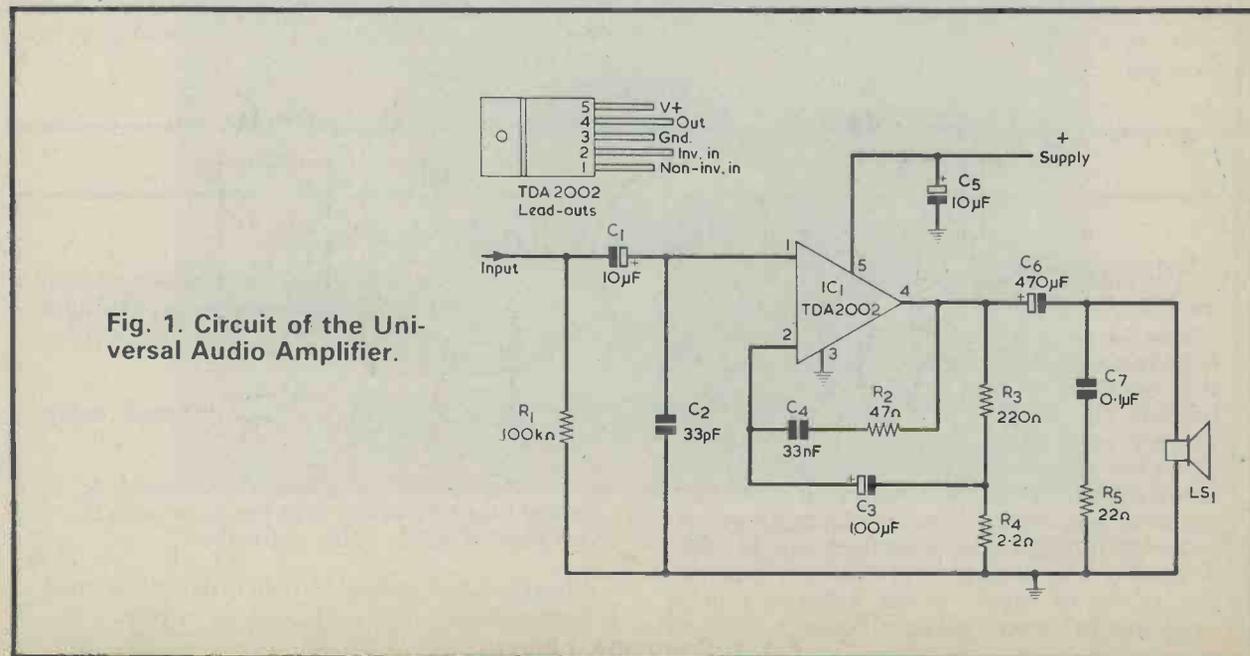


Fig. 1. Circuit of the Universal Audio Amplifier.

Photo of Universal Amplifier PCB, and when mounted in screening can.

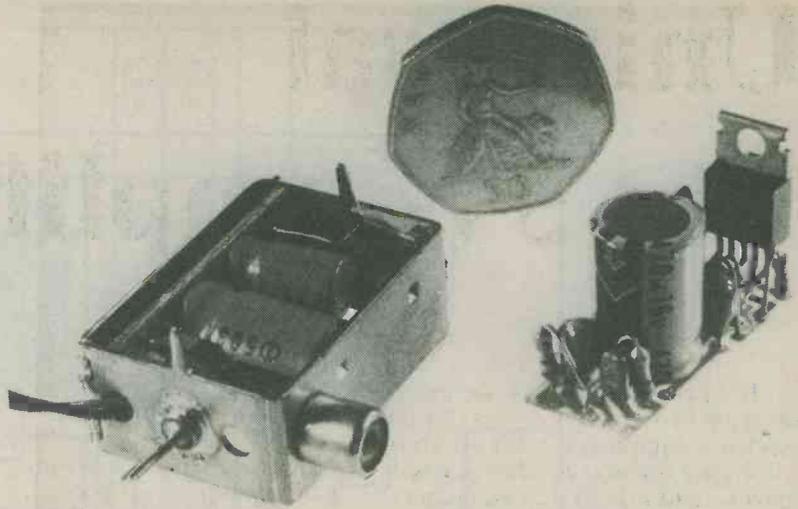

CIRCUIT DESCRIPTION

Fig. 2. demonstrates the basic circuit of the universal audio amplifier. This is a straightforward application of the TDA2002, with a few precautions to prevent low frequency instability (C2 at the input, and C7/R5 at the output). The major point to consider is the decoupling of the positive supply, since the board space available in this application only permits a 10 microfarad device for C5, on the assumption that the existing application will already be complete with at least a few hundred microfarads to decouple the heavy audio current peaks drawn from the positive supply for the existing audio output IC. If the application has inadequate decoupling, it will be apparent

very quickly as audio peaks cause the whole circuit to become unstable and start to oscillate (motorboating). The input and output are capacitively coupled, and once again these components may well be available on the existing board.

The amplifier will provide 3-5 watts RMS output for a typical car supply, which will be adequate for the vast majority of applications. The actual voltage gain of the device is determined by the external feedback components R3, and R4 – and if a more detailed analysis of the device characteristics is required, you should ask for a copy of the manufacturer's data sheet when ordering.

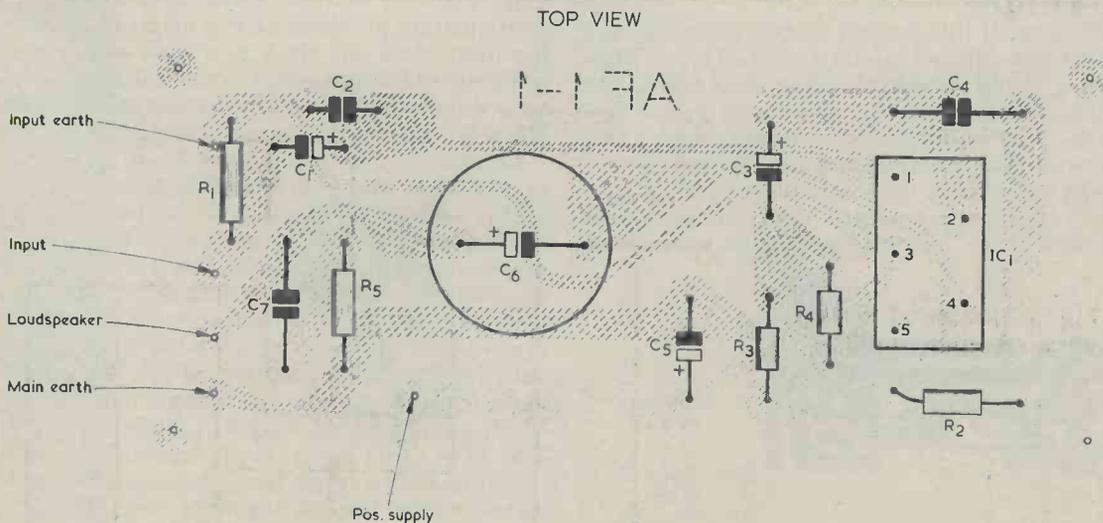


Fig. 2. Component layout.

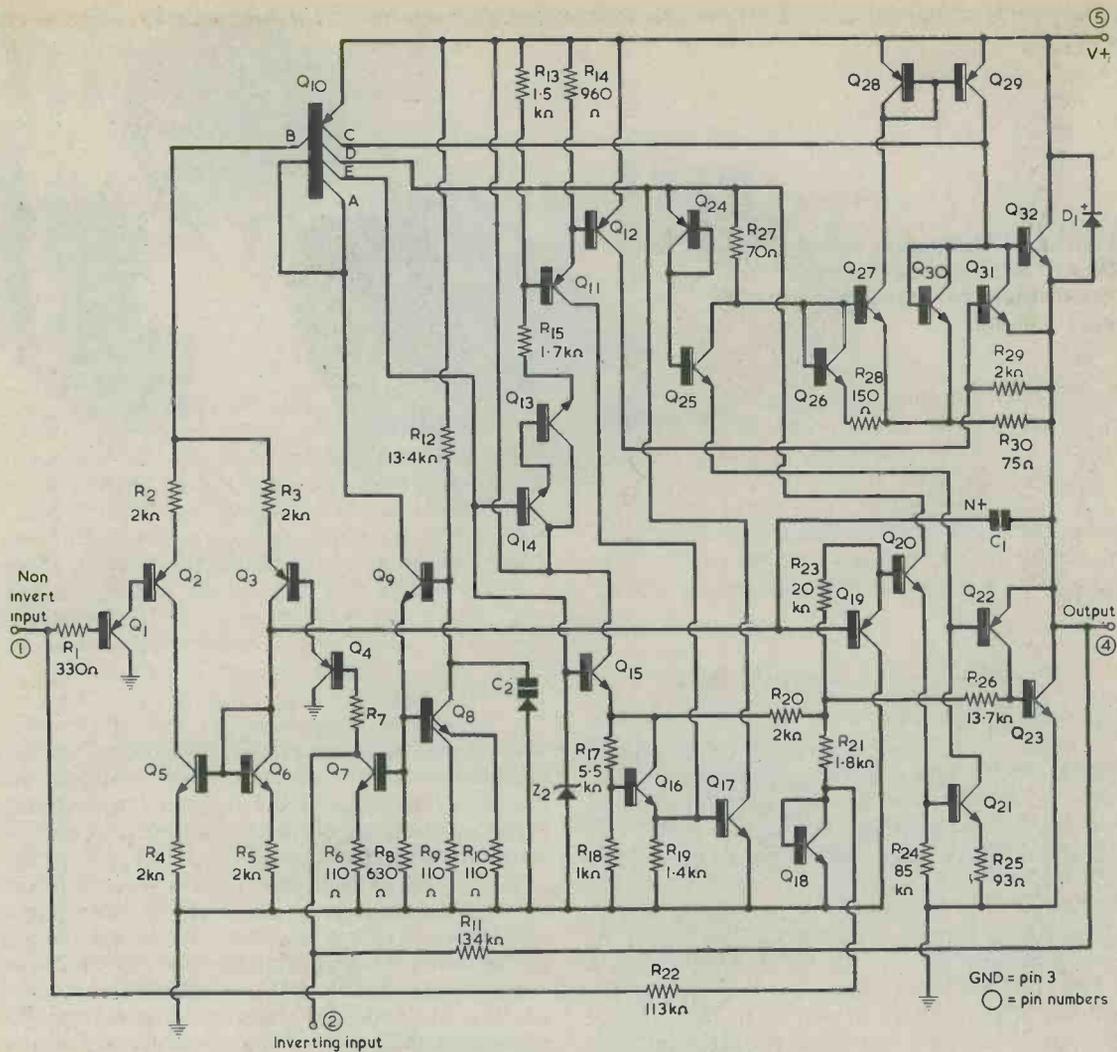


Fig. 3. TDA 2020 internal circuit diagram.

CONSTRUCTION

Construction of this project hinges around a very tightly laid out printed circuit board. This is illustrated in Fig. 3 and is available pre-etched and drilled from Ambit International for those who do not possess the nerve or skills necessary to make such a fine piece of work. The illustration is four times full-size, as opposed to the more usual same-size or twice-size, since the very compact nature of the circuit would make details of the layout (Fig.4) quite indecipher-

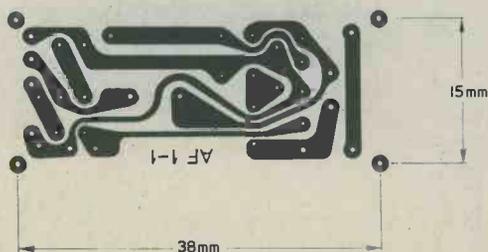


Fig. 4. PCB layout. Scale 4:1.

able. There is nothing particularly awkward about construction, provided care is taken to avoid soldering more than one track at a time and most of the difficulty in this project, will come in actually picking your way through the maze of wires inside the defunct piece of equipment you are attempting to repair.

Of course, this unit may be built for stand-alone operation as an audio amplifier for a 12v source, and is sufficiently compact to be built into a loud-speaker enclosure. Bearing in mind the nature of the power supply requirements, this device would make an excellent PA speaker amplifier, and fits easily inside the housing of most weatherproof horn speakers available today. A major point to consider is the very high input impedance, which will make long input leads susceptible to the pick up of RF and 50 cycles hum along the length of the input connection. The TDA 2020 has a simple heatsink requirement, requiring only a single fixing hole and this can either be taken from the existing audio amplifier, or drilled in convenient position on the case of the equipment. If the power requirement is relatively low, an internal heatsink, such as a piece of aluminium bracket, may be fitted.

NC-551 (PL-259) CABLE CONNECTOR
Bakelite insulation
Net weight: 22gr.




NC-555 (UG-175/U) ADAPTOR
For RG-58/U Cable
Net weight: 10gr.


NC-556 (UG-176/U) ADAPTOR
For RG-59/U Cable
Net weight: 9gr.



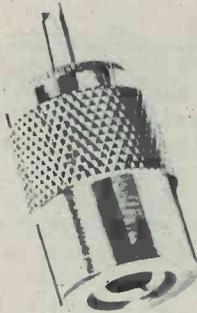NC-551/2 (PL-259/6) CABLE CONNECTOR
With Built-in Adaptor
Bakelite insulation
Net weight: 23gr.



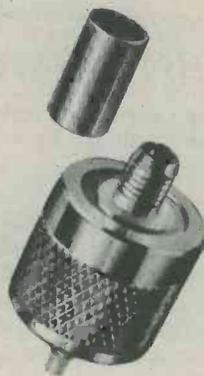
NC-572/C CRIMP TYPE CABLE CONNECTOR
For RG-58/U cable
Noryl insulation
Net weight: 16gr.



NC-573 SOLDERLESS CABLE CONNECTOR
For .RG-8/U cable
Noryl insulation
Net weight: 15gr.



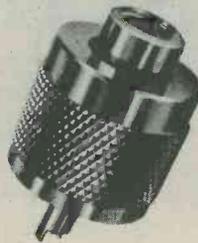NC-572 SOLDERLESS CABLE CONNECTOR
For RG-58/U cable
Noryl insulation
Net weight: 15gr.



Know your RF connectors (1)

The popular PL-259 series of RF connectors comes in a variety of guises, and the unwary frequently fall into the trap of thinking that a 'PL-259' is a totally standard designation identifying a single part. The above illustrations show the prime variations on the theme of the connector - with the NC-572 and the NC-551/NC-555 representing the most popular types in the UK. The NC572 is one of the simpler types to use, since the bared coax is simply screwed into the plug, with the inner soldered into the centre connector. Provided to correct diameter cable is used, this type of fixing is perfectly secure - and in many cases a good deal better than an imperfectly made NC-551 with adaptor.

LCD digital stopwatch/clock

J. L. Mills

LCD clock modules are fairly commonplace these days, although surprisingly few people appreciate the actual scope of the range available to the designer/constructor. One of these devices is available from PCI and is designated the CM174/5L, and apart from simple time-keeping functions, various alarms and a stopwatch facility are also available. The external components required are fairly minimal, being those required for setting the time and functions, plus the external peripheral drivers for the sleep and alarm control functions.

Once again, the versatility of "doing it yourself" allows a very large number of different approaches to be adopted when constructing this project, although the text relates to the "all up" version covering every conceivable feature that the module has to offer.

CHIEF DESCRIPTION

The diagram indicates the complete circuit of the digital stopwatch clock with the CM174 module. The actual timing device involved with the integrated circuit more closely resembles a microprocessor than a clock, it still manages to operate from a single 1.5 volt battery for a period of several years. The quiescent current drain is only 15 microamps, which means that a single AA cell will probably keep the entire system

running for three to four years. A separate power source will be required for the external functions such as a loud alarm tone and a relay for switching external loads, and this can either be a separate battery, or derived from the equipments own power supply.

The setting of the various functions and the selection of certain functions is achieved using momentary type switches for positions S1,2,3,6,7,8,9. Multiple switching is required for S4,5,10 and 11 where optional features are to be selected.


It is worth noting that the supply to the clock module is primarily a positive earth function, and thus is not easily obtained by simply tapping some power off an external circuit using a negative earth. In view of the low current consumption, it is invariably better to keep the supply for the clock module entirely independent of any other power considerations concerned with this application.

The audible alarm is derived from the output on the clock module and this is amplified by TR2 to drive a piezo electric sounder with a multiplier inductor. The purpose of the inductor L1 is to provide very large voltage spikes which will greatly increase the volume from the high impedance transducer.

TR1 provides the relay switching function for the automatic sleep timer (for example, a delayed switch



The CM17415 LCD clock module.

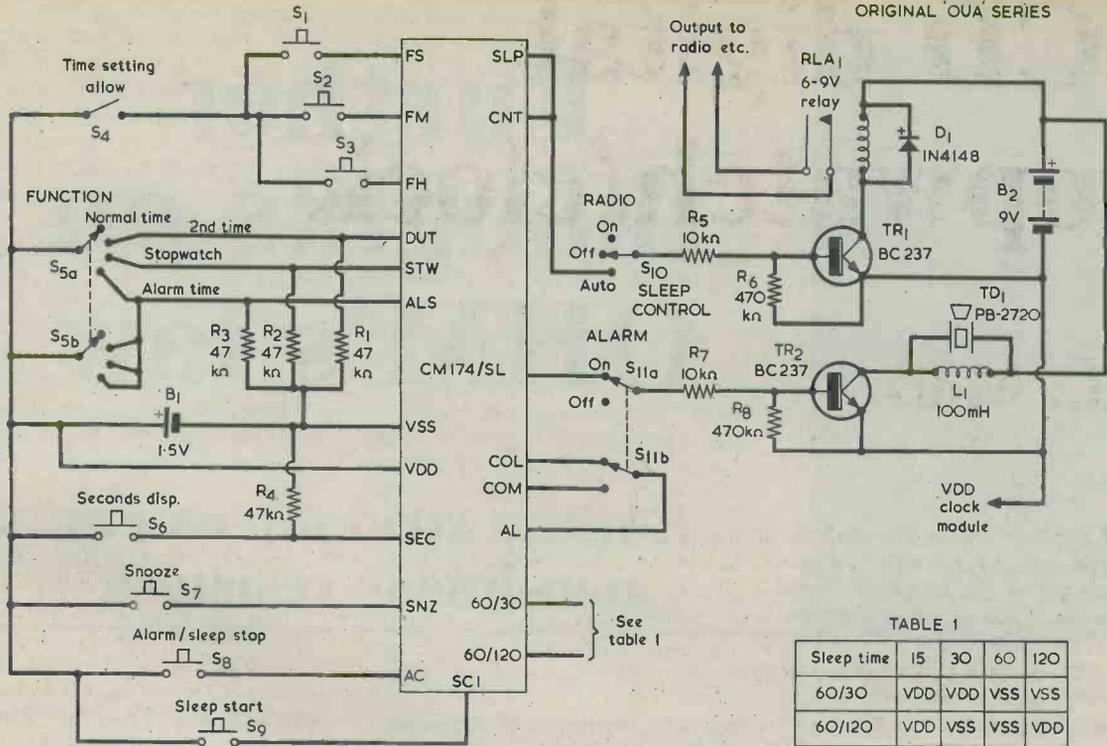

Circuit of the Digital Stop Watch/Clock.

or function for a bedside radio). The relay can be virtually any type of relay that can be driven from a DC237 and line volt supply. A prototype used an original series OUA or OUB relay, selected according to the number of poles required to be switched.

Various functions are offered by the CM174/SL and are best described by reference to the appropriate pin function.

FS During normal time operation this pin enables the clock to be set accurately to a time signal. Depressing FS on the time 'pip' will reset the seconds to '00'.

FM In normal mode is used for setting minutes, each push advancing the clock one minute. In stopwatch mode this pin resets the stopwatch to 00.0.

FH In normal mode this is used for setting hours. In stopwatch mode FH is used as a start/stop button.

DUT A second time zone is displayed when DUT and ALS are taken to +1.5v. Time setting is carried out as before using FH and FM.

STW Taking STW and ALS to +1.5v. puts the module into its stopwatch function and it displays 00 mins 0 secs.

ALS As can be seen ALS is used with STW, or DUT. Taken to +1.5v on its own however, it displays an alarm time. This is a 24 hour type, settable for any one alarm time within a 24 hour period. Again, setting is achieved by FH and FM.

It should be noted that the dual time, stopwatch and alarm cannot be used together. For example, if a dual time is set, selecting alarm or stopwatch will destroy the DUT setting.

SEC Selecting SEC simply changes the hours/mins display to read min/secs thereby providing the equivalent of a 6 digit clock.

SNZ This snooze function should be familiar to most digital alarm clock users - when the alarm sounds depressing SNZ will reset the alarm for another 4 mins, when the alarm will again sound.

ACS This function immediately cancels the alarm, control and sleep functions.

SCI This function starts the sleep/control timer. The time period selected is determined by the wiring of 6/3 and 6/12 terminals - see Table 1.

Whilst the basic clock operation should now be clear the operation of TR1 and TR2 circuits may not.


The switch S10 has three functions. In 'auto' position RLA1 will be activated when the SLP/CNT output goes high.

This will be achieved only when S9 (sleep start) is pushed, after which SLP/CNT will be 'on' for the time period set by 6/3, 6/2, see Table 1.

After this time period has elapsed SLP/CNT will go low, thereby switching off an external circuit connected to RLA1. If for example a radio is connected to RLA1 it can be switched on for any length of time by placing S10 in 'radio on' position, thus acting as an 'off/on' switch for the radio.

S11 Alarm 'on/off' simply activates TD1 via TR2 to provide an audible alarm when ALM output provides a 2kHz output. S11b activates a symbol when the alarm is 'on'. When 'off' the symbol is connected to the BP drive of the LCD (COM) thereby disabling it.

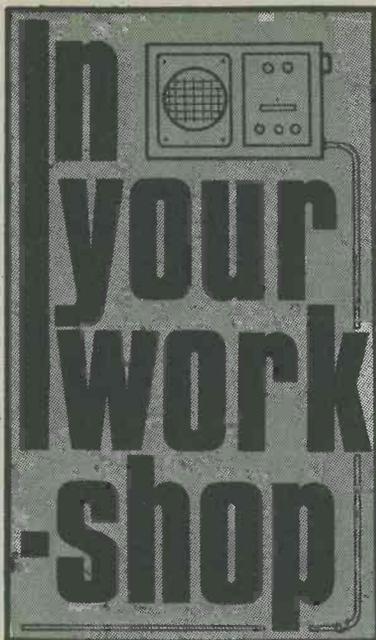Construction of the project is left up to the individual, since many people may not wish to use all the functions shown. To ease mounting, a bezel is also available, enabling the module to be affixed to a panel without any visible fixings.



Further thoughts on OHM's law

Smithy straightens out non-linear resistors

Smithy looked across at Dick's bench for the third time in as many minutes. Dick was unusually quiet and inactive and it was this strange calm which attracted Smithy's attention.

The morning had passed uneventfully with a satisfying number of repairs to show for their labours so far, but now as it was approaching teabreak time, Dick's thoughts were clearly very far from the television set on the bench in front of him. Any particularly tricky problem usually brought on a flurry of mutterings and frantic activity at Dick's bench, so Smithy found the silence somewhat unnerving.

Another minute passed and then Smithy moved over to Dick's bench, flicking the switch down for the electric kettle as he passed. But even this familiar noise which heralded their tea-break did not break Dick's reverie. Smithy's curiosity was too much.

"Penny for your thoughts Dick," he said.

Dick blinked, glanced down at the set in front of him, sighed and said "Oh I don't know Smithy, it seems you just can't rely on anything."

After their years together Smithy had seen most of Dick's moods, but he wondered if this remark was directed at the fickleness of life in general, or the

non-functioning T.V. set in particular.

So he asked cautiously "What's the problem, anything I can help with?"

"Oh, it's Ohms Law," said Dick dispiritedly and after a pause, "they keep changing it."

Smithy was bewildered. Now it was his turn also to stand silently for a moment staring into the middle distance.

"How do you mean, they keep changing it?" he queried. "Is this something you are doing at evening classes?"

Dick nodded. "Yes," he said. "Last week we did some problems on Ohms Law and it was all straightforward stuff really. You know the sort of thing, resistors in series and parallel and I thought it was all a doddle. Old Johnson who takes us for circuit theory was saying that all this Ohms Law stuff was 'linear' and I even understood that."

Dick paused and frowned as he struggled with the unfamiliar theoretical concepts.

"You see" he continued "in maths we've been doing linear functions. How one thing changes the same as another, or at least not the same, but in proportion to another. You know, Smithy, X is proportional to Y and all that stuff. Well it didn't seem to mean much at the time, but when we

did Ohms Law it sort of 'clicked' and there it was, volts and amps related to each other linearly, or as Old Johnson puts it, 'directly related' to each other. I was feeling quite chuffed at that, I thought I'd managed to tie it all together. And then this week they went and changed it all."

Clearly Dick was troubled and Smithy knew that this would take some time to sort out. So he settled himself on the stool alongside Dick's bench and probed a little deeper into the source of Dick's troubles.

"What was Old John..." Smithy corrected himself, "... Mr. Johnson's lecture about this week then?" he asked.

"Same sort of thing really," explained Dick, "but to do with non-linear resistors, you know - thermistors and things like that. I can't say I understood it all like I did the last lecture though. It was all graphical solutions and old Johnson said that we probably wouldn't get it in the exam anyway. But I was thinking about it when I found the problem on this set, or at least I thought I had found the fault."

"What was it?" asked Smithy glancing down at the set, and then, noticing the absence of a 'repaired' tag added "Or what is it?"

"It was the thermistor" said

Dick, "it had gone open-circuit. Straightforward enough, but it's still not working."

Smithy looked at the blackened thermistor lying on the bench alongside the television and then glanced over the old and dusty chassis.

"So what's wrong with Ohms Law?" he asked.

"Well, is it linear or non-linear," demanded Dick.

Smithy looked up from the chassis, paused and then said "Let's get a pencil and paper and see if we can sort this out."

A few moments later he had sketched out the familiar battery and resistor circuit which Dick had been working on the previous week at his recently started evening classes. (Fig.1).

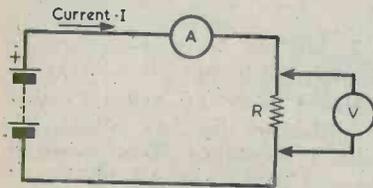


Fig. 1. Smithy's first sketch $I = \frac{V}{R}$, or Current is proportional to voltage and inversely proportional to resistance.

"I don't suppose we need go back to the usual explanations involving water tanks and all that," said Smithy, "where you compare the voltage in a circuit to water pressure and the current in the circuit to the rate of flow of water in a pipe, because it could get very confusing when you start to deal with non-linear circuits."

"Blimey," muttered Dick, "non-linear plumbing, it doesn't bear thinking about, whatever it is."

Smithy ignored Dick's interruption and pointed to the circuit he had drawn.

"This is the simplest circuit I can think of," he said. "It's got a battery and a resistor."

"And two meters," added Dick.

"Yes, but we are going to ignore the effect of the meters

and say that for our purposes the ammeter is a short circuit and the voltmeter is an open circuit."

Dick blinked. "But they won't work if they're open circuit or short circuit," he protested.

Smithy scowled. "Look," he said "if we are to get anywhere with this explanation then we are going to assume that the ammeter is just like a piece of wire and that the voltmeter is not touching the circuit at all."

"I'll go along with that," said Dick affably, "but it already seems like one of old Johnson's tricks."

Smithy ignored Dick's scepticism and continued with his explanation.

"The current flowing in the resistor is due to the voltage in the battery." Smithy paused, but there was no protest from Dick.

"And," Smithy continued, "this current is limited by the resistance of the resistor."

"Amps, volts and ohms," muttered Dick.

"Right," said Smithy "and these amps volts and ohms, as you put it, are all in the same circuit. So if we know the battery volts and we know the value of the resistor then we can say what the current will be before we connect up."

"Good thing," chuckled Dick "when the meters are open-circuit and short-circuit."

"OK, OK," snorted Smithy "so you don't need the meters. But that's the point, with Ohms Law you can calculate one of the circuit conditions if you know the other two."

"Current equals Volts divided by Resistance," he intoned as he jotted down the familiar expression:


$$I = \frac{V}{R}$$

Dick brightened. "This I understand," he said. "If the voltage is doubled, the current doubles, but if the resistance is doubled the current is halved."

"Correct," said Smithy. "And if the resistance is fixed then the relationship between the voltage and current is linear."

"Yes I know what you mean," said Dick and added

MORSE MADE EASY

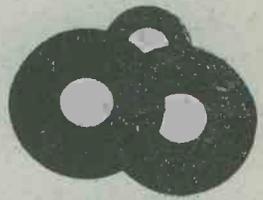

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750gms). Details only s.a.e.

THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane, Purley, Surrey.

Name

Address

GAREX

RESISTOR KITS new extended range at old prices: E12 series 10Ω to 1M, 61 values, 5% carbon film, general purpose ratings ½W or ¼W (please state).

Starter pack 5 each value (305) £3.10

Standard pack 10 each (610) £5.55

Mixed pack 5 each ½W plus ¼W (610) £5.55

Giant pack 25 each (1525) £13.60

NICAD RECHARGEABLES physically as zinc carbon: AA(U7) £1.30, C(U11) £3.35, PP3 £5.55.

Any 5+: less 10%; any 10+: less 20%.

VHF FM MONITOR RECEIVERS

HF 12 POCKET SIZE 12 channel xtal controlled. 4MHz bandwidth in range 130-174MHz. With nicad & charger. £57.95 Xtals extra, see below.

SOUNDAIR 008 PORTABLE SCANNER 8 channel xtal controlled. Nicad, charger. £59. Xtals extra.

SR-9 top selling monitor: 2m FM with 144-146MHz full coverage VFO, plus 11 xtal controlled channels, ideal for fixed or mobile listening. 12V DC operation. £47.50. Xtals extra.

MARINE BAND SR-9. 156-162MHz £47.50.

CRYSTALS FOR HF-12, NR-56, SR-9, SOUNDAIR 008, TM56B: all 2m channels in stock from Q(145.0) to 32(145.8) at £2.46 (plus 15p post). Over 40 popular marine channels at £2.85 (plus 15p post). See list.

AMPLIFIER MODULE new, fully assembled 6W IC unit, 12V DC. Low impedance (4-8:) input & output for extrn. speaker amplification, with circuit £2.75

CO-AXIAL CONNECTORS & ADAPTORS see list

PL259 UHF plug plus reducer 75p;

SO239 UHF socket panel mtd. 60p;

2xSO239 inline coupler £1

2xPL259 inline coupler £1

Co-ax fitting - any 5+: less 10%

MAINS P.S.U. 12v 1A regulated. British made by GAREX £15.95.

Main distributor of Revco aeriels and special products.

Access - Barclaycard

PRICES INCLUDE UK POST & VAT

CALLERS BY APPOINTMENT

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH.

TRING, HERTS HP23 4LS

Cheddington (STD 0296) 668684

suspiciously "but why did you say 'if' the resistance is fixed. I mean, the resistance alters the current too, doesn't it."

"Certainly," said Smithy, "but the resistance may not be fixed. That's to say it may not be an independent element in the calculation. Look at this graph."

Smithy sketched the axes of a graph and with a flourish added a nearly perfect straight diagonal line. (Fig.2).

"There we are," he said "Current plotted against volts." Then, as he added some numbers to the axes he explained, "For every voltage value along the horizontal line there is a corresponding current value on the vertical line, and each pair of voltage and current values has a single and unique point on the graph."

"And if you join the points up they form a straight line."

"Right," said Smithy "and if you had a different resistor value you'd get a different straight line."

Dick pointed to the second line which Smithy had just drawn. "How do you know which is which? he asked.

"Because the higher the resistance the lower the current, and so the slope of the line is less."

"So this lower line is for higher resistance."

"Yes," said Smithy "and there's a separate line for each value of resistance."

"But what if you use a

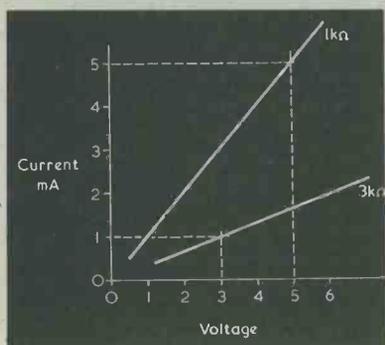


Fig.2. Smithy shows the straight line or 'linear' relationship between voltage and current for fixed values of resistance.

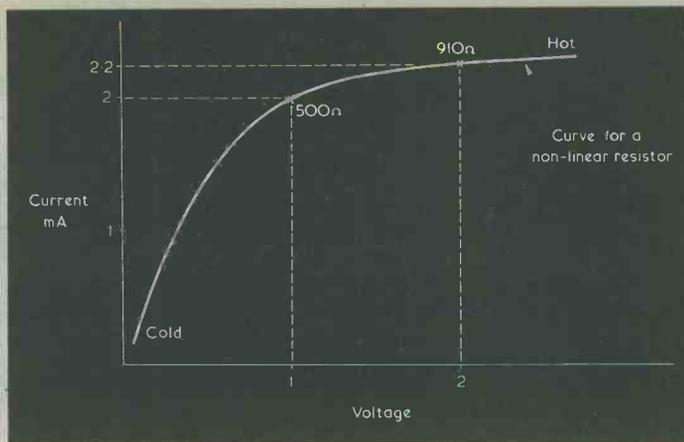


Fig. 3. Positive Temperature Coefficient. Although the resistance is different at each point of the graph, the volts, amps and ohms still obey Ohm's Law.

variable resistor?" demanded Dick.

"That's the point," said Smithy. "The graph will move from the points on a line for one value of resistance to the points on another line for another value."

Dick brightened. "And bang goes your straight line."

"Exactly, because the resistance is varying."

POSITIVE TEMPERATURE COEFFICIENT

Smithy sketched another pair of axes and with a deft flourish drew a line which rose and then flattened out. (Fig.3).

"Just a minute," protested Dick, "Old Johnson never said anything about variable resistors, only these non-linear resistors."

"Right," said Smithy, "so what happens if the resistor changes its value while you are increasing the voltage or current in the circuit?"

Dick looked puzzled. "How would it do that?"

"It might get hot," explained Smithy, and added "in which case the resistance could go higher or lower."

"That'll muck things up," muttered Dick, looking glumly at Smithy's second sketch, and thinking about Ohm's Law.

"Not always. It can be very useful to a designer," said Smithy.

"Look at what's happening here." He pointed to the start of the graph line.

"As the voltage increases, the current increases. But if

you increase the voltage across the resistor," said Smithy moving his finger up along the graph line to where it levelled out, "it gets hot and its resistance increases so that the current isn't as high as you might have thought at first. It's called Positive Temperature Coefficient because its resistance increases with temperature."

Dick was silent for a moment as he thought about the meaning of the phrase 'Positive Temperature Coefficient' then he brightened suddenly. "Oh I see, so in the end it won't let as much current through. It varies its own resistance, well I'm blown!"

"And blowed it well might be," Smithy chuckled at Dick's choice of words. "If you applied all the voltage at once, the resistor wouldn't have time to warm up and with the resistance still very low the high current could cause excessive heating at a small spot in the resistor and damage that one small spot."

Dick frowned suddenly. "I've never heard of it happening," he said, thinking of all the resistors in sets which had passed through the workshop.

"That's because the effect is very small in the usual resistors we have in circuits," explained Smithy. "In fact they are designed to have a stable value of resistance over their normal temperature range."

"So what's the problem?" asked Dick. "Why worry about

it at all if the effect is small?"

"Because some resistances, such as the heaters in valves or television tubes are meant to run hot, so there is a great deal of difference between their cold resistance and their hot resistance."

Dick pointed to the tip of Smithy's third sketch. "But surely they're meant to be hot. I mean, they're meant to be heaters aren't they?"

"Yes," agreed Smithy, "but the heater is a long thin resistance which is like a chain of small resistors in series. Now if you apply the full working voltage straight away, when the heater is cold, the high current might just vaporise one small part of the heater."

"The weakest link in the chain!" interjected Dick. "It burns out before the others have got hot and done their job. They don't stop the current, and it sorts out the weakest part and blows it to smithereens!"

Smithy winced at Dick's phrasing. "Not quite how I'd put it," he said "but that's right."

But Dick wasn't to be put down by Smithy's careful approach to this idea. "What you need is a thermal cut-out," he said, and added "no not that - something to let the current build up slowly."

Smithy looked across the workshop. "Just so," he mused. Then he scowled, slid from the stool, stepped across to the still silent kettle and stabbed a finger at the automatic thermal trip. "I don't know why we went in for this new-fangled thing," he said glaring at the stone cold kettle. He returned to Dick's bench and settled himself on the stool. "More trouble than it's worth," he grumbled, forgetting his displeasure of times past at the steam filled workshop when his able assistant's enthusiasm for some knotty problem or other had distracted him from the simple task of tea-making.

"Quite a good protection gadget, I thought," said Dick brightly.

"Which is what we need here," Smithy pointed to the neck of the tube in the set on Dick's bench, "if we're not to have heaters blowing every time we switch on the T.V."

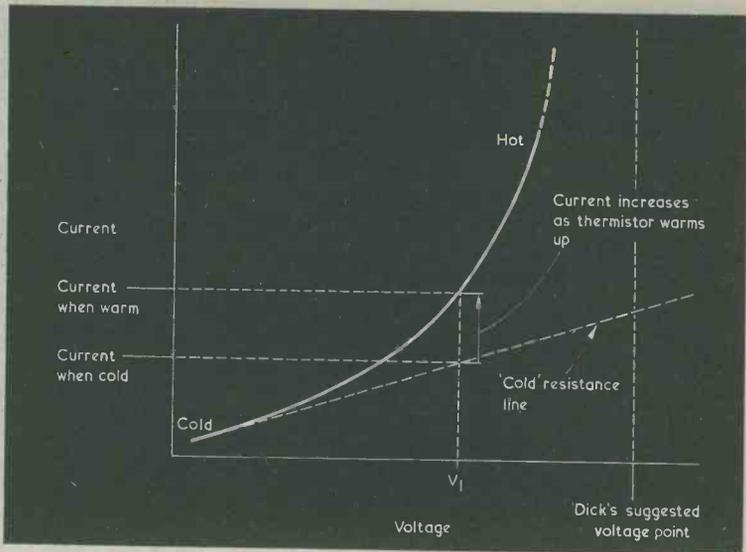


Fig. 4. Graph showing how the current through a Negative Temperature Coefficient thermistor increases as it heats up.

NEGATIVE TEMPERATURE COEFFICIENT

Smithy drew another pair of axes and this time added a line which swept upwards. (Fig.4).

"That looks familiar," said Dick. "Where have I seen that before?"

"I know what you're thinking of," said Smithy, "but first let's consider it to be a resistor whose resistance falls as it gets hot."

"Falls!" exclaimed Dick. "That's unusual isn't it?"

"Yes," agreed Smithy "but it can be very useful". Smithy added a dotted line on the graph. "This shows the resistance of the device when its cold. At voltage V_1 ," Smithy marked a point on the horizontal axis and drew a line vertically up across the dotted line and on to the curving line, "the current is low," he finished. His pencil point rested on the intersection of his new vertical line with the dotted line. "But as the device warms up the resistance falls and the current increases until we reach a final stable condition."

Dick studied the situation on the graph for a moment and said, "But what happens if we put a high voltage on it? Say just here." And he indicated a point over to the right of Smithy's point V_1 . The current

will keep rising until" he trailed off, his finger tracing a path up past the top of the graph. "There's nothing to stop it!" he protested.

"In practice there's always something to limit the current," Smithy added quickly, "look here." He drew another circuit, this time with two resistors each with its own voltmeter. (Fig.5).

"More magic meters," muttered Dick.

Smithy ignored Dick's cynic-

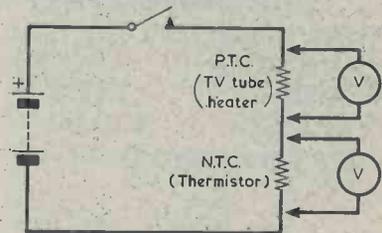


Fig. 5. When first switched on the heater and thermistor are cold. The heater is therefore low resistance, but the thermistor is high resistance and prevents any damaging current surge.

THE
MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-402 9176

PEATS for PARTS

**ELECTRONIC COMPONENTS
RADIO & TELEVISION**

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs Transfers

Also a postal service

PEATS

the world of electronics
25 Parnell Street, Dublin 1. Tel 749972.

**RADIO & ELECTRONICS
CONSTRUCTOR**

**ANNUAL
SUBSCRIPTIONS**

**to this magazine may
be obtained through
your newsagent or
direct from the
publishers**



INLAND £9.50
OVERSEAS . . £10.50
per year, post free



*Please send remittance with
name and address and
commencing issue required to:*

**DATA PUBLICATIONS
LTD**
57 Maida Vale, London
W9 1SN

ism and wrote 'PTC' alongside one resistor and 'NTC' alongside the other. "Two resistances," he said. "One a tube heater, which has a positive temperature coefficient and the other a thermistor which has a negative temperature coefficient. When we apply a working voltage to this set-up both devices are cold and so the NTC thermistor is high resistance while the tube heaters are low resistance."

"And so could be damaged by any sudden voltage," interrupted Dick.

"Exactly, but the current is limited by the NTC thermistor because most of the voltage is dropped across its high resistance. Now the thermistor will heat up, its resistance falls, and . . ."

"The voltage is transferred to the tube heater," finished Dick.

"Well, yes," Smithy agreed hesitating at Dick's graphic explanation. "I'd rather put it that the circuit conditions change so that the proportion of the voltage dropped across the heater increases while that dropped across the thermistor decreases."

"And so the heater comes on very slowly," emphasised Dick. "And doesn't blow up."

"Yes," agreed Smithy, "and all the time during this process the voltage current and resistance values for both the heater and the thermistor obey Ohms Law."

There was silence for a moment as each perused his own line of thought.

Dick spoke next. "Where have I seen that graph before?" he asked as he pointed to Smithy's third sketch with its upward curving line.

"You're probably thinking of the semiconductor diode law," explained Smithy. "That's a non-linear law, but in that case the effective resistance of the device varies with the applied voltage so the effect is instantaneous rather than the slow thermal effects of heaters and thermistors. But that's a topic for another time."

Silence settled again and Smithy returned to his own bench.

"So Ohms Law itself is always linear," mused Dick, and added, "except in special

cases where thermal effects can change things."

"Thermal effects always change things," stressed Smithy, "even in a good conductor like a piece of wire."

Dick looked puzzled. "Oh, come off it," he protested, "not enough to make any difference."

"Not necessarily," said Smithy as he settled himself firmly on his own stool at his own bench. "What happens if you pass too much current through a piece of wire?"

"It gets hot, but so what?"

"What if you increase the current further?"

"The resistance will increase?"

"Yes but if you take it beyond that?" persisted Smithy.

"The wire will burn out, and the current will stop."

"Just so," muttered Smithy as he bent over the set on his bench. "The wire goes open-circuit and the current stops."

"So Ohms Law is still satisfied," said Dick puzzled. "But so what?"

"The current definitely stops." The Serviceman fell silent.

His puzzled assistant turned back to the T.V. chassis on his bench.

There was silence for a full minute as Dick's gaze roamed the valves and other components on the dusty and very dead old chassis. And then Dick spotted it. "Well I'm"

We will protect our gentle reader's mind from the expletives used by Dick as he glared at the blackened and blown fuse set alongside the power supply components.

Smithy bent lower over his work and tried not to grin too broadly.

Dick turned to Smithy. "The fuse is blown. After all that it's just the blooming fuse. I might have known what you were driving at, it's just clicked!"

Smithy straightened and turned to face Dick, now grinning broadly. He pointed to the kettle which had long gone off the boil. "You're wrong," he said, "it clicked about five minutes ago."

"Nice one Smithy," and Dick set about making the long delayed tea.

New Products



NEW WINGED BIMDICATORS


BOSS Industrial Mouldings Ltd, 2 Herne Hill Road, London, have launched their new range of LED Filament and Neon 'Winged Bimdicators' which, where appropriate also house an integral ballast resistor.

Offering 17 round, square or arrow shape lens options in combination with 6 body sizes ranging from 9.75mm to 19.8mm dia, the unique wings moulded onto both sides of the body automatically fold in as the indicator is pushed through the panel hole, to progressively slip out behind the panel, thereby firmly locking the indicator in position.

Capable of accepting panel thicknesses of between 0.5mm and 3.5mm this new indicator is obviously eminently suitable for production line/OEM type applications, where speed of assembly is a major consideration.


MPUroBreadBoard

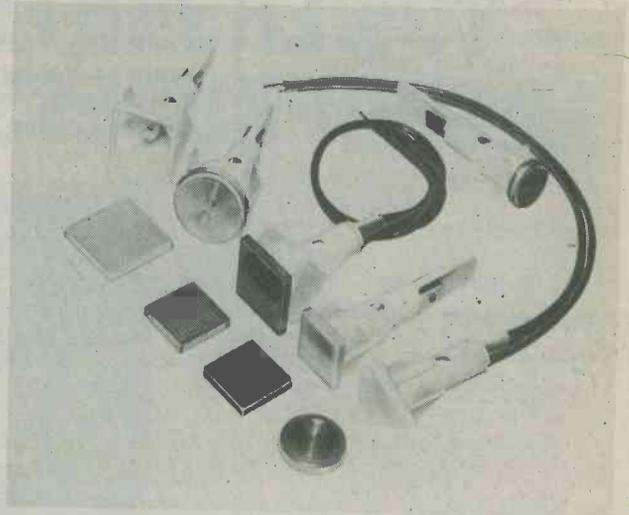Also recently launched is the MPUroBreadBoard, a new Eurocard size breadboard laid out specifically for microprocessor designs, which interlocks with all existing BOSS BIMBOARD components. Incorporating a special central microprocessor section, flanked on both sides by peripheral chip areas, this new MPUroBreadBoard has single or double bus



strips on all sides, plus 5 turret terminals for incoming power lines. Ideal for beginners and professionals alike, all rows and columns are numbered and lettered for exact contact location, this being imperative for educational use where step-by-step build up instructions are used.

MINIATURE HANDTOOLS

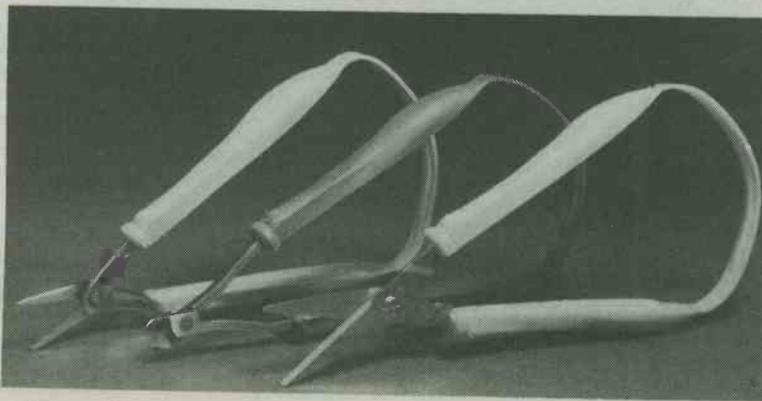

Tele-Production Tools Ltd., of Stiron House, Electric Avenue, Westcliff, Essex, manufacturer of Handtools and Production aids announces the introduction of a set of three new 'Easi-Grip' miniature handtools designed for use in electronics and fine modelling.


All are fitted with ergonomically styled self opening handles and are operated with finger tips to ensure fine control and ease of operation. This

'Easi-Grip' set consists of miniature carbon steel side cutters, fine nosed stainless steel tweezers-Pliers and a serrated stainless steel scissor/shear for cutting fine wires, boards, foil etc.

The average tool weight is only 40 gms and the cost is £3.75 each which includes Post and Packing also V.A.T. or £10.00 for the set of three.

**PLEASE MENTION THIS MAGAZINE
WHEN REPLYING TO
ADVERTISEMENTS**

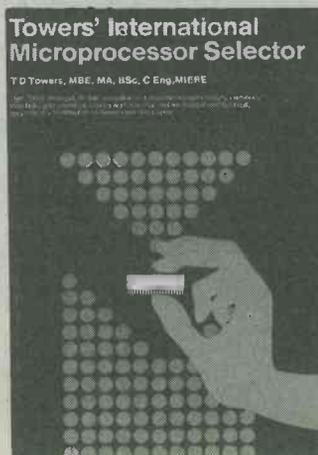NEW! JUST PUBLISHED TOWERS INTERNATIONAL MICROPROCESSOR SELECTOR



**ONLY
£16.25
POST PAID**

If you come into contact with microprocessors (whether as hobbyist, student, circuit engineer, programmer, buyer, teacher, serviceman, or just humble reader) you often find you would like data information on a specific microcircuit element. Specifications apart, you may be even more interested in where you can get the device in question. And perhaps even more important still (particularly with obsolete devices), you may be looking for guidance on a readily-available second source or possible substitute.

This microprocessor selector (working on the same basis as the TRANSISTOR, FET, and OPAMP LINEAR-IC selectors already compiled by the author) is designed to provide in one handy reference volume a comprehensive body of readily-accessible, user-slanted essential information across the field of microprocessors.

In the data tabulations will be found set out the essential basic specifications of over 7,000 commercially-available microprocessor 'chips', including not only the microprocessor elements themselves (e.g. MPUs and CPUs) but also the many other LSI 'support' circuits (e.g. ROMs, RAMs, PROMs, clocks, UARTs, I/Os) normally used in harness with the microprocessors proper to produce complete microcom-

puters or microcontrollers. For ease of reference, the descriptions and control specifications of the individual circuits are set out in the detailed data tables on separate single lines, arranged in alpha-numeric order by type number.

For the newcomer to the very new field of microprocessors, the selector includes a full introductory note on these devices before the data tables.

Besides this, the tables are supplemented by separate appendices giving additional information on: (a) Microprocessor chip applications (and codings); (b) Microprocessor 'families'; (c) Microprocessor LSI chip manufacturers (and codings); (d) Semiconductor LSI technologies (and codings); (e) Microprocessor chip packages (and codings); (f) Microprocessor trainer and development systems; (g) Microprocessor bibliography; (h) Manufacturers' house codes; (i) Glossary of microprocessor terms; (j) Explanatory notes to tabulations.

This selector is fully international in scope and covers not only microprocessors and related devices from the USA and Continental Europe, but also from the UK and the Far East (Japan).

TO:- DATA PUBLICATIONS LTD, 57 MAIDA VALE, LONDON W9 1SN

Please send me copy/copies of

**TOWERS INTERNATIONAL
MICROPROCESSOR SELECTOR**

Price: £16.25 inc P&P

NAME

ADDRESS

(BLOCK CAPITALS PLEASE)

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge
£2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the **bona fides** of Advertisers.

Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, **Radio and Electronics Constructor**, 57 Maida Vale, London, W9 1SN.

BOOKS. BOOKS. BOOKS. Large range of radio and electronic books in stock. Send s.a.e. for lists. Servio Radio, Dept. REC7, 156-158 Merton Road, Wimbledon, London SW19 1EG.

BOOKS FOR SALE: *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Electronics Unravelled* by Kyle. £1. *Auto Electronics Simplified*, by Tab Books. £1.20. Box No. G394.

SIMPLE BEGINNERS KITS: L.E.D. flasher £3.25. Crystal set £2.95. 1 transistor radio £3.25. Variable tone generator £3.25. All less case. Cheques made payable to: Elektron Kits, 51 Fairfield, Gamlingay, Sandy, Beds., SG19 3LG.

ANY SINGLE SERVICE SHEET £1 plus S.A.E. Thousands of different service/repair manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E. newsletter, price lists, quotations. (0698-883334). Ausrec, 76 Churches, Larkhall, Lanarkshire.

FOR SALE: A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

B. J.'s DICTIONARY OF CB SLANG. Quality printed. 95p + stamp. Refund if not highly delighted. Trade welcome. Bailey & Co., Tondy, Bridgend, Mid-Glam.

WIRELESS, VALVES, PRE-WAR ONWARD S.A.E. Modern bargains list 15p. Sole Electronics, (REC), 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

MINI FANS: Uses HP11 battery. Pocket Size. Ideal for hot weather. Only £1.50 or £2.75 for two, inc. P & P. To: — P.D. Electronics, 11 Bluebell Close, Orpington, Kent, BR6 8HS.

RADIO VALVES 1930 ONWARDS. Ex-equipment, guaranteed. Magazines, P.W., W.W., etc. S.A.E. list. Malnors Radio, 12 Kirkham Close, Chilton, Ferryhill, Co. Durham, DL17 ORL.

(Continued on page 700)



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO

DEPT REC
35/39 CHURCH STREET, WILMSLOW
CHESHIRE SK9 1AS.

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,
Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers



BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to —

British National Radio & Electronic School

4 Cleveland Road, Jersey, Channel Islands.

Name
Address

REC/7/815


BLOCK CAPS PLEASE

Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

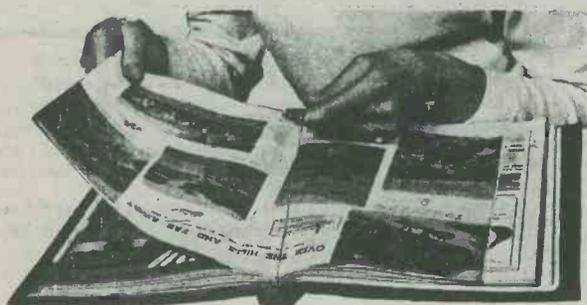

PRICE £2.25 P. & P. 60p
including V.A.T.

For your other magazines

Plain-backed in Maroon or Green
(Please state colour choice)

PRICE £2.25 P. & P. 60p
including VAT

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 699)

THE RADIO AMATEUR INVALID & BLIND CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

BOOK CLEARANCE. Bound volumes *Radio & Electronics Constructor* Nos. 27, 28 and 29, £3.00 each. *Cost Effective Projects Around the Home* by John Watson, £1.50. *Talk-Back TV: Two-Way Cable Television*, by Richard Veith, £1.00. *Solid State Short Wave Receivers for Beginners*, by R. A. Penfold, 60p. *50 Simple LED Circuits*, by R. N. Soar, 50p. All prices include postage. Box No. G399.

FOR SALE: FM Transmitter microphone – hear your own voice on radio, price £15.00. Holograms £12.50. Mini cassette recorder and 10 C60's, £20.00. LED watches £3.50. 50 2W zeners £1.00. 50 BZY88 type zeners £1.00. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

WANTED: Army wireless sets and instruction books on same. Hallicrafter receivers, and speakers. Will collect during my holidays in September. Please write to: A. Huizer (PE1 – DMN), Wilhelminasingel 16, 3135 JP Vlaardingen, Holland.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

ELECTRONIC COMPONENTS. 6 x CD4011 £1.00. Veroboard 0.1, 4" x 4" 80p. 13 x TIL 209 £1.00. 30 x C280 capacitors 95p. 130 mixed resistors £1.00. 30 assorted electrolytic capacitors 70p. 12 x BC212 £1.00. 40 mixed capacitors 80p. 12 x 2N3702 £1.00. 10 x BC108 £1.00. 7 x TIL 211 £1.00. Add 25p P. & P. Lists 35p. John E. Harris, 9 Ivybridge, Broxbourne, Herts.

JOIN THE INTERNATIONAL S.W. LEAGUE.

Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. – both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine etc., £9-00 per annum U.K. Overseas rates on request, Secretary Grove Road, Lydney, Glos., GL15 5JE.

(Continued on page 701)

SMALL ADVERTISEMENTS

(Continued from page 700)

MICRO TRANSMITTERS. Range 1 mile. Tunable 60-150MHz. Receive on VHF/FM radio. Supplied assembled and working. With sensitive microphone and data £4.75 plus 25p. P & P. P.D. Electronics, 11 Bluebell Close, Orpington, Kent, BR6 8HS.

LOOK TRANSISTORS - BC182L 9p. BC184 10p. BC212L 10p. BC214L 10p. 2N3055 35p. OA81 3p. 1N4148 2p. 1N4004 6p. P. & P. 25p. C. Pearce, 14 Launde Park, Market Harborough, Leics.

100 1N4148 £1. 150 Resistors £1. 100 Capacitors £1. P. & P. 25p. S.A.E. Lists. Dept. R, D. B. Products, P.O. Box 8, York, YO1 1FT.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

FOR SALE: LED non-working repairable watches £2.50 each. C60 cassettes 15p each plus postage 10p. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

FOR SALE: Bound Volume No. 26 **Radio & Electronics Constructor** 1972/1973. As new. £2.50 plus £1.50 Post & packing. Box No. G402.

FOR SALE: Photographic enlarging equipment: Vivitar enlarger. Model E.36 with 50mm f. 3.5 and 75mm f.3.5 lenses. Kodak safety light. Kodak contrast filter set. 11 in. x 14 in. printing frame with copying facilities. Measuring flask. Three trays, three tweezers. Three plastic bottles. Clips. Printing paper. Antistatic brush for cleaning negatives. Kodak Photoguide Booklet. Man's protective apron. £75 o.n.o. Pair of Goodman's speakers 8 ohms, 15 watts, £50 o.n.o. R. L. Gee, 9 Glanmead, Shenfield, Essex.

BREAKER, BREAK. Build your own C.B. rig. (27MHz transceiver). Circuit diagram, parts list, etc. All components available in U.K. Send £2.95 & large s.a.e. to: P. Sherwood, 8a Aylesstone Walk, Manchester, M10 9NU. I'm down and on the side.

INTERESTED IN RTTY? You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

(Continued on page 703)



68
LARGER
PAGES

The larger
Catalogue
that means
FREE POSTAGE
IN U.K.

**ADDITIONAL
DISCOUNTS**

**GUARANTEED
SATISFACTION**

**GOOD STOCKS
GOOD DELIVERY**

We pay postage.

**Semi-Conductors • I.C.s • Opto-
devices • Rs and Cs in great variety
• Pots • Switches • Knobs •
Accessories • Tools • Materials •
Connectors**

ELECTROVALUE

**FREE
FOR THE
ASKING**

ELECTROVALUE LTD., (RC7), St. Jude's Rd.,
Englefield Green, Egham, Surrey TW20 0HB.
Phone: 33603 (London 87) STD 0784. Telex 264475.

NORTHERN BRANCH (Personal shoppers Only): 680 Burnage Lane, Burnage,
Manchester M19 1NA. Phone (061) 432 4945.

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'

MPT Radio Communications Cert

EXAMINATION STUDENTS -

GUARANTEED COACHING

UNTIL SUCCESSFUL

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:

Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering
& Servicing
Electrical Engineering Installations
& Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name

Age

Address

Occupation

ICS

Accredited
by CACC
Member of
ABCC

To
International Correspondence Schools
Dept 278J, Intertext House, LONDON
SW8 4UJ or phone 01-622 8911 (anytime)

RECHARGEABLE BATTERIES

**PRIVATE & TRADE
ENQUIRIES WELCOME**

FULL RANGE AVAILABLE SEND SAE
FOR LISTS. £1.45 for Booklet Nickel
Cadmium Power" plus Catalogue.
Write or call:

*NEW SEALED
LEAD RANGE AVAILABLE*

SANDWELL PLANT LTD

2 Union Drive, Boldmere,
Sutton Coldfield, West Midlands,
021-354 9764.

INTERNATIONAL SHORT WAVE LEAGUE



Membership £9.00 per annum (Overseas rates
on request) including 12 monthly issues of
Monitor - the League journal. Including free
use of all Services, QSL Bureau etc.

**THE LARGEST S.W.L. ORGANISATION
IN THE WORLD**

For full details write to:

The Secretary,
I.S.W.L.,
1, GROVE ROAD, LYDNEY,
GLOS. GL15 5JE.

BUY THIS BEST SELLER

T.V. FAULT FINDING

MONOCHROME
405/625 LINES



REVISED & ENLARGED

Edited by J. R. Davies

132 pages

PRICE £1.20

Over 100 illustrations, including 60
photographs of a television screen after
the appropriate faults have been
deliberately introduced.

Comprehensive Fault Finding Guide
cross-referenced to methods of fault
rectification described at greater length
in the text.

Price £1.20 from your bookseller.

*or post this Coupon together
with remittance for £1.50
(to include postage) to*

DATA PUBLICATIONS LTD.
57 Maida Vale, London, W9 1SN

*Please send me the 5th revised edition of TV
Fault Finding. Data Book No. 5*

I enclose cheque/crossed postal order for . . .

NAME

ADDRESS

.

.

BLOCK LETTERS PLEASE

APRIL

SMALL ADVERTISEMENTS (Continued from page 701)

WANTED - Handbook for the 8 valve Trio 9R-59DE. Please contact P. Bradbury, 2A Colwood Road, Harpenden, Herts., Telephone: 63942.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

PERSONAL
JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

TWO'S COMPANY for friendship/marriage. Introductions with the personal touch for people of discernment. Brochure on request. TWO'S COMPANY, Dept. 1E/R, 111 High Holborn, London WC1V 6JS. Telephone: 01-242-2345.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Ick-nield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

PRINTED CIRCUIT BOARDS FOR "RADIO & ELECTRONICS CONSTRUCTOR" PROJECTS.

OCT 20dB amp. Part 1 68p plus 30p P&P
NOV. 20dB amp. Part 2 62p plus 30p P&P
NOV. Basic Med. Wave radio 69p plus 30p P&P
DEC. Volume Expander £2.25 plus 30p P&P
FEB. '81 Cricket Game £1.67 plus 30p P&P
APR. Med. & Short Wave radio £1.20 plus 30p P&P
APR. Active tone control mod. £1.25 plus 30p P&P
MAY. Crystal Calibrator £1.75 plus 30p P&P
All boards ready for use, roller tinned and drilled, glassfibre.

Trade enquiries welcome. Highly competitive prices.

Write now for quote to:

BRB PRINTED CIRCUITS (REC)

109, Potter Street, Worksop, Notts. S80 2HL.

T & J ELECTRONIC COMPONENTS

METAL BOXES

Two piece design consisting of a "U" shaped base and cover. Finished in black stelvite.
WB1 6 x 4 x 1 1/2" 165p
WB2 8 x 5 x 2" 215p
WB3 9 x 5 x 2 1/2" 230p
WB6 4 1/2 x 2 1/2 x 2 1/2" 130p

PLAIN ALUMINIUM (With lid)
AB7 5 1/2 x 2 1/2 x 1 1/2" 90p
AB8 4 x 4 x 1 1/2" 90p
AB9 4 x 2 1/2 x 1 1/2" 90p
AB10 5 1/2 x 4 x 1 1/2" 105p
AB12 3 x 2 x 1" 72p

PLASTIC BOXES

PB1 4 1/2 x 3 x 1 1/2 white 70p
O25L 2 1/2 x 1 1/2 x 1" (Vero) white 50p
Many other boxes in catalogue.

MISCELLANEOUS

P.C.B. Transfers (13 sheets) 300p
Insulated crocodile clip 9p
Telephone pick up coil 75p
2.5" x 1", 0.1" Veroboard 16p
Small cable ties 2p
PP3 battery connectors 14p
F.M. ribbon dipole aerial 45p
Spirawrap 1/4" diameter (per metre) 16p
Spirawrap 1/8" diameter (per metre) 13p
Grommets 1/4" bore 1p
Grommets 3/8" bore 1.5p
3.5mm jack plug 10p
2.5mm jack plugs 10p
2.5 and 3.5mm sockets 10p
2 pin DIN plugs 8p
2 pin DIN sockets 8p
Veropins 0.1" and 0.15" per 25 15p
s.p.s.t. toggle switches 38p

L.E.D.S.

0.125" red 12p
0.125" green or yellow 21p
0.2" red 13p
0.2" green or yellow 22p
0.2" clear, illuminates red 22p
Clips for all above types: 2p

RESISTORS

1/4W and 1/2W tolerance ± 5% 4.7Ω to 10M. E2 series. Price each 2p
Miniature presets. Tolerance ± 20%
Power rating 0.1W. E6 series 100Ω to 1M. Price each, vertical or horizontal. 9p

I.C. SOCKETS

Low profile types by Texas.
8 pin 11p. 14 pin 13p. 16 pin 13p.

SEMICONDUCTORS

BC107/8/9 11p, BC182/3/4 11p,
AC127/8 24p, 2N3702/3/4/6 11p,
BC338 16p, BC169 12p, 2N3819 25p,
1N4001/2 5p, BY127 18p, 1N5401
15p, 1N914 5p, IS44 7p, BZY88C
series 2.7V to 33V 10p.

COMPONENT KITS

All previously advertised kits still available.

Latest kit prices:

Voltmeter Sensitivity Booster £3.15
May 1981
Crystal Calibrator May 1981 £14.85

Please note that some kits exclude certain items. Full details in list, available on receipt of an s.a.e.

98 Burrow Road, Chigwell Essex. IG7 4HB.

Mail order only. Prices include VAT, overseas deduct 15%
NO minimum order charge. Postage: Components 40p
(Overseas add £1.50, airmail at cost), kits 65p. Orders are
despatched same day as received.
Full catalogue available 45p cheque or postal order.
Enquiries please enclose an s.a.e.

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536

**PRICED
FROM
£148.75**

Stereomaster

This microscope's working distance and field of view is relatively large; this feature ensures convenience to the operator who works with both hands while assembling precision mechanisms.

**IDEAL FOR
PRINTED CIRCUITS
AND OTHER
DELICATE WORK.**

**COMES
COMPLETE WITH**

built-in x 10 Mag.
Objectives x 20
Objectives x 35
At extra cost



We stock one of the largest selections of second hand microscopes and optical magnifiers, on and off stands. Please phone for details.

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 60p each, p&p 20p

Issue(s) required

Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)

post free, commence with issue

Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.50
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.50
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.50
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.50
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.50
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.50
Vol. 33	September 1979 to August 1980	Price £6.20, post & pkg. £1.50

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price £2.25, post & pkg 60p

With no title on spine, maroon

Price £2.25, post & pkg 60p

With no title on spine, green

Price £2.25, post & pkg 60p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages

Price £1.20, P.&P. 30p

DB6 Radio Amateur Operator's Handbook,

New edition in course of preparation

DB19 Simple Short Wave Receivers

Price 80p, P. & P. 30p

140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording - White

- 6 sheets

Price £1.50, P. & P. 13p

Set 4: Wording - Black

- 6 sheets

Price £1.50, P. & P. 13p

Set 5: Dials

- 6 sheets

Price £1.50, P. & P. 13p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

THE LOWEST PRICES FOR PRIME CMOS/TTL/74C IN THE UK

L INEAR ICs TRANSISTORS

TBA120S	1.00	SL1610P	1.60	HA11223	2.15	4000 series	4060	0.95	4566	1.59	7448	0.56	74125	0.40	74190	0.55	7405	0.14	7496	1.20	74190	0.60	74C CMOS	7400	0.20	BF194	18p
L200	1.95	SL1611P	1.60	HA11225	1.45	4000	4063	1.15	4568	2.18	7450	0.14	74126	0.40	74191	0.55	7408	0.14	74107	0.25	74192	0.60	7400	0.20	BF195	18p	
U237B	1.28	SL1612P	1.60	HA12002	1.45	4001	4063	0.38	4569	1.95	7451	0.14	74128	0.65	74192	0.55	7409	0.14	74107	0.25	74193	0.68	7400	0.20	BF224	22p	
U267B	1.28	SL1620P	1.89	HA12017	0.80	4002	4067	4.30	4572	0.30	7453	0.14	74132	0.50	74193	0.42	7410	0.13	74113	0.25	74194	0.68	7400	0.20	BF241	18p	
LM301H	1.28	SL1621P	2.17	HA12042	1.95	4007	4068	0.18	4572	0.30	7454	0.14	74136	0.65	74194	0.42	7408	0.20	74113	0.25	74195	0.68	7400	0.20	BF274	18p	
LM301TC	0.67	SL1623P	2.17	HA12411	1.20	4008	4070	0.18	4584	0.40	7460	0.14	74141	0.45	74195	0.55	7411	0.14	74113	0.25	74196	0.65	7400	0.20	BF440	21p	
LM308	0.65	SL1624C	3.28	HA12412	1.55	4009	4070	0.25	4584	0.40	7470	0.28	74142	0.85	74196	0.55	7410	0.14	74113	0.25	74197	0.65	7400	0.20	BF441	21p	
LM324	0.64	SL1625P	2.17	SF76660N	0.30	4011	4072	0.22	4702	4.50	7473	0.28	74143	2.50	74197	0.85	7412	0.28	74122	0.55	74200	0.65	7400	0.20	BF362	49p	
LM339N	0.66	SL1626P	2.44	FREQ. DISPLAY		4011	4074	0.22	4703	4.50	7474	0.28	74144	2.50	74198	0.85	7414	0.28	74122	0.55	74200	0.65	7400	0.20	BF395	18p	
LM348N	1.86	SL1630P	1.62	AND SYNTH.		4012	4075	0.18	4704	4.24	7475	0.35	74145	1.50	74199	1.00	7421	0.15	74126	0.29	74221	0.60	7400	0.20	BF479	66p	
LF351N	0.49	SL1640P	1.89	DEVICES		4013	4076	0.60	4705	4.24	7476	0.30	74148	1.09	74200	1.00	7421	0.15	74126	0.29	74221	0.60	7400	0.20	BF479	66p	
LF353N	0.75	SL1641P	1.89	SAAT056	3.75	4015	4077	0.23	4706	4.50	7480	0.26	74150	0.79	74201	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF691	33p	
LM330N-14	3.05	SL1642P	3.05	SAAT058	3.35	4016	4078	0.25	4720	4.00	7481	0.20	74151	0.55	74202	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF692	33p	
LM330N-8	1.00	ULN2283B	1.00	SAAT059	3.35	4017	4078	0.25	4720	4.00	7482	0.20	74152	0.55	74203	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF693	33p	
LM330N	1.81	CA3308E	0.70	1TC900C	14.00	4020	4083	0.45	4725	2.24	7483	0.60	74153	0.55	74204	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF694	33p	
LM331	1.81	CA3309E	1.84	LM123C	19.00	4021	4083	0.45	4725	2.24	7483	0.60	74154	0.55	74205	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF695	33p	
CA3309E	1.98	CA3309E	3.35	LM123C	19.00	4022	4083	0.45	4725	2.24	7483	0.60	74155	0.55	74206	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF696	33p	
CA3312E	1.80	CA3312E	3.84	MSL2318	3.84	4024	4083	0.45	4725	2.24	7483	0.60	74156	0.55	74207	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF697	33p	
CA3313E	1.80	CA3313E	3.84	MSM5523	11.30	4025	4083	0.45	4725	2.24	7483	0.60	74157	0.55	74208	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF698	33p	
CA3313E	0.90	CA3313E	0.90	MSM5524	11.30	4026	4083	0.45	4725	2.24	7483	0.60	74158	0.55	74209	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF699	33p	
CA3313E	0.90	CA3313E	0.90	MSM5525	7.85	4027	4083	0.45	4725	2.24	7483	0.60	74159	0.55	74210	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF700	33p	
CA3313E	0.90	CA3313E	0.90	MSM5526	7.85	4028	4083	0.45	4725	2.24	7483	0.60	74160	0.55	74211	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF701	33p	
CA3313E	0.90	CA3313E	0.90	MSM5527	9.75	4029	4083	0.45	4725	2.24	7483	0.60	74161	0.55	74212	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF702	33p	
CA3313E	0.90	CA3313E	0.90	MSM5528	9.75	4030	4083	0.45	4725	2.24	7483	0.60	74162	0.55	74213	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF703	33p	
CA3313E	0.90	CA3313E	0.90	MSM5529	9.75	4031	4083	0.45	4725	2.24	7483	0.60	74163	0.55	74214	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF704	33p	
CA3313E	0.90	CA3313E	0.90	MSM5530	9.75	4032	4083	0.45	4725	2.24	7483	0.60	74164	0.55	74215	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF705	33p	
CA3313E	0.90	CA3313E	0.90	MSM5531	9.75	4033	4083	0.45	4725	2.24	7483	0.60	74165	0.55	74216	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF706	33p	
CA3313E	0.90	CA3313E	0.90	MSM5532	9.75	4034	4083	0.45	4725	2.24	7483	0.60	74166	0.55	74217	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF707	33p	
CA3313E	0.90	CA3313E	0.90	MSM5533	9.75	4035	4083	0.45	4725	2.24	7483	0.60	74167	0.55	74218	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF708	33p	
CA3313E	0.90	CA3313E	0.90	MSM5534	9.75	4036	4083	0.45	4725	2.24	7483	0.60	74168	0.55	74219	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF709	33p	
CA3313E	0.90	CA3313E	0.90	MSM5535	9.75	4037	4083	0.45	4725	2.24	7483	0.60	74169	0.55	74220	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF710	33p	
CA3313E	0.90	CA3313E	0.90	MSM5536	9.75	4038	4083	0.45	4725	2.24	7483	0.60	74170	0.55	74221	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF711	33p	
CA3313E	0.90	CA3313E	0.90	MSM5537	9.75	4039	4083	0.45	4725	2.24	7483	0.60	74171	0.55	74222	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF712	33p	
CA3313E	0.90	CA3313E	0.90	MSM5538	9.75	4040	4083	0.45	4725	2.24	7483	0.60	74172	0.55	74223	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF713	33p	
CA3313E	0.90	CA3313E	0.90	MSM5539	9.75	4041	4083	0.45	4725	2.24	7483	0.60	74173	0.55	74224	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF714	33p	
CA3313E	0.90	CA3313E	0.90	MSM5540	9.75	4042	4083	0.45	4725	2.24	7483	0.60	74174	0.55	74225	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF715	33p	
CA3313E	0.90	CA3313E	0.90	MSM5541	9.75	4043	4083	0.45	4725	2.24	7483	0.60	74175	0.55	74226	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF716	33p	
CA3313E	0.90	CA3313E	0.90	MSM5542	9.75	4044	4083	0.45	4725	2.24	7483	0.60	74176	0.55	74227	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF717	33p	
CA3313E	0.90	CA3313E	0.90	MSM5543	9.75	4045	4083	0.45	4725	2.24	7483	0.60	74177	0.55	74228	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF718	33p	
CA3313E	0.90	CA3313E	0.90	MSM5544	9.75	4046	4083	0.45	4725	2.24	7483	0.60	74178	0.55	74229	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF719	33p	
CA3313E	0.90	CA3313E	0.90	MSM5545	9.75	4047	4083	0.45	4725	2.24	7483	0.60	74179	0.55	74230	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF720	33p	
CA3313E	0.90	CA3313E	0.90	MSM5546	9.75	4048	4083	0.45	4725	2.24	7483	0.60	74180	0.55	74231	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20	BF721	33p	
CA3313E	0.90	CA3313E	0.90	MSM5547	9.75	4049	4083	0.45	4725	2.24	7483	0.60	74181	0.55	74232	1.00	7422	0.15	74126	0.29	74221	0.60	7400	0.20			

MAPLIN make it easy...



in
SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



in
HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our
CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.

On sale now in all branches
WH Smith  price £1.

In case of difficulty check the coupon below.

make it easy... with MAPLIN

The
Maplin Matinée

Amazing value for only £299.95 plus £99.50 for cabinet if required

Easy to build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in Electronics & Music Maker commencing March, 1981 issue. Back numbers available.



MAPLIN ELECTRONIC SUPPLIES LTD.

by MAIL ORDER
A fast service you can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____

Address _____

REC 781

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911