

The Wireless Constructor

6^D
MONTHLY



Vol. III

NOVEMBER, 1926

No. 1

COMPLETE CONSTRUCTIONAL
ENVELOPE
WITH BLUEPRINTS


*Free
with this
issue*



HOW TO BUILD

The "MIDGET REFLEX" SET

Below the Pyrometer scale

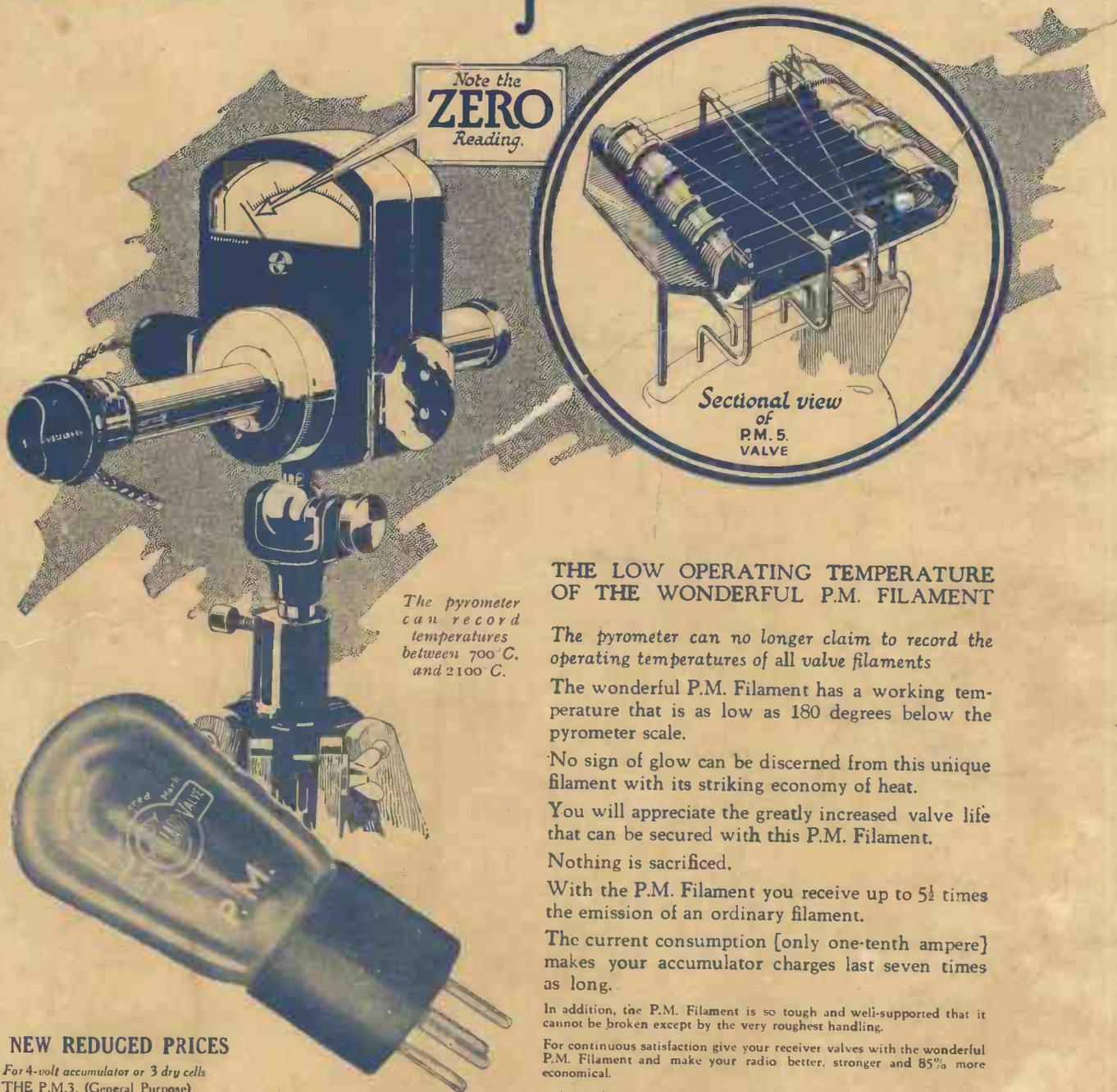

The pyrometer can record temperatures between 700° C. and 2100° C.

THE LOW OPERATING TEMPERATURE OF THE WONDERFUL P.M. FILAMENT

The pyrometer can no longer claim to record the operating temperatures of all valve filaments

The wonderful P.M. Filament has a working temperature that is as low as 180 degrees below the pyrometer scale.

No sign of glow can be discerned from this unique filament with its striking economy of heat.

You will appreciate the greatly increased valve life that can be secured with this P.M. Filament.

Nothing is sacrificed.

With the P.M. Filament you receive up to 5½ times the emission of an ordinary filament.

The current consumption [only one-tenth ampere] makes your accumulator charges last seven times as long.

In addition, the P.M. Filament is so tough and well-supported that it cannot be broken except by the very roughest handling.

For continuous satisfaction give your receiver valves with the wonderful P.M. Filament and make your radio better, stronger and 85% more economical.

ASK YOUR RADIO DEALER FOR P.M. VALVES

NEW REDUCED PRICES

For 4-volt accumulator or 3 dry cells		
THE P.M.3. (General Purpose)	0.1 amp.	14/-
THE P.M.4. (Power)	0.1 amp.	18/6
For 6-volt accumulator or 4 dry cells		
THE P.M.5. (General Purpose)	0.1 amp.	18/6
THE P.M.6. (Power)	0.1 amp.	18/6
For 2-volt accumulator		
THE P.M.1. H.F.	0.1 amp.	14/-
THE P.M.1. L.F.	0.1 amp.	14/-
THE P.M.2. (Power)	0.15 amp.	18/6

These prices do not apply in Irish Free State

British made
in a
British Factory.

Mullard

THE · MASTER · VALVE

ADVT. THE MULLARD WIRELESS SERVICE CO., LTD., MULLARD HOUSE, DENMARK STREET, LONDON, W.C.2


The WIRELESS CONSTRUCTOR

Vol. III. No. 1.

CONTENTS

NOVEMBER.

The "Span-space Three" 3	First in Europe—A Radio Press Triumph 39
By G. P. KENDALL, B.Sc. 8	Remarkable Success of the Elstree "Solodyne" 41
The Cat-astrophe 9	Getting the Best from the "Night Hawk" 43
Prepare for the Winter 11	By PERCY W. HARRIS, M.I.R.E. 47
Talks to Beginners—VIII 13	Another Radio Press Success 49
By CAPT. JACK FROST, M.I.R.E. 20	An All-Enclosed Crystal Set 58
The "Invalid's Three" 25	By A. V. D. HORT, B.A. 63
Described by J. H. REYNER, B.Sc. (Hons.), A.M.I.E.E. 29	Modern Superheterodyne Practice 69
Mr. Gumplethorpe Visits Olympia 29	Workshop Hints 77
Operating the "Distaflex Two" 33	Gearing as an Aid to Wireless 77
Seen at the Show 33	Apparatus Tested 82
A Selective One-Coil Single-Valve Set 33	Our Readers' Views 82
By D. J. S. HART, B.Sc.	

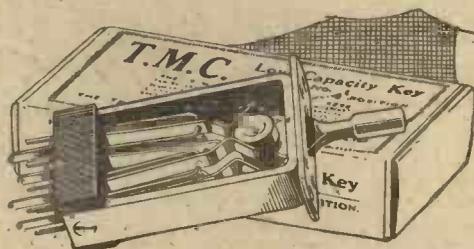

T.M.C. Low Capacity Keys

Solve the Switching Problem

MADE IN THREE MODELS.

- No. 1. 12 point, 3 position .. 7/-
 No. 2. 6 point, 2 position .. 6/-
 No. 3. 24 point, 3 position .. 15/6

Packed in attractive black, red and yellow labelled cartons.

Ask for the new T.M.C. Catalogue at your local Wireless Shop—or we will send a copy free on request. Please mention the name of your usual dealer.

ASK your dealer to show you T.M.C. Low Capacity Keys. Designed by radio engineers, their adaptability to varied switching requirements is simple.

They combine a positive locking action with rapid make and break of unvarying performance. They are of strong and accurate construction, the live parts of the key being insulated from the frame, while the gold-silver contacts will not oxidise. Escutcheon plates and levers are polished and lacquered brass or bright nickel, and give a neat and pleasing appearance.

T.M.C. Low Capacity Keys can be used for:—

- Remote Control.
- Multi-valve series parallel and battery switching.
- Change over from Head set to Loud-speaker, etc.

Telephone Manufacturing Co. Ltd.

HOLLINGSWORTH WORKS, WEST DULWICH, S.E. 21

'Phone: Sydenham 2460/1.

Telegrams: "Bubastis, Dulcros, London."

Free

with every copy

THIS useful GIFT BOOKLET presented with the next issue of WIRELESS—on sale Tuesday next, October 19th—has been written from an entirely new viewpoint. Reference to its pages will enable you to track down immediately even the most puzzling of faults, and it contains many useful tables by the use of which you are directed in a novel, methodical and systematic way to the source of trouble.

This FREE GIFT will sell this issue rapidly, so buy your copy early, when you will be able to see for yourself why WIRELESS is the most popular weekly wireless journal.



J. H. Reyner, B.Sc. (Hons.), A.M.I.E.E., who writes on the interesting subject of "Problems of Single-Dial Control."

Why not place a standing order with your Newsagent for regular delivery?

The Contents of this Issue will include:

The first of the "Wireless" Series of Star Single Dial Receivers.

"PROBLEMS OF SINGLE-DIAL CONTROL,"

By J. H. Reyner, B.Sc. (Hons.), A.M.I.E.E.


"WHY I CHOOSE RADIO." By John Henry.

WIRELESS 2^D

THE ONE-WORD WEEKLY

Obtainable from all Newsagents, Bookstalls and Booksellers, or direct from the Publishers, Radio Press, Ltd., Bush House, Strand, London, W.C.2. Subscription Rates, 13/- per annum throughout the world.

FROM YOUR NEWSAGENT

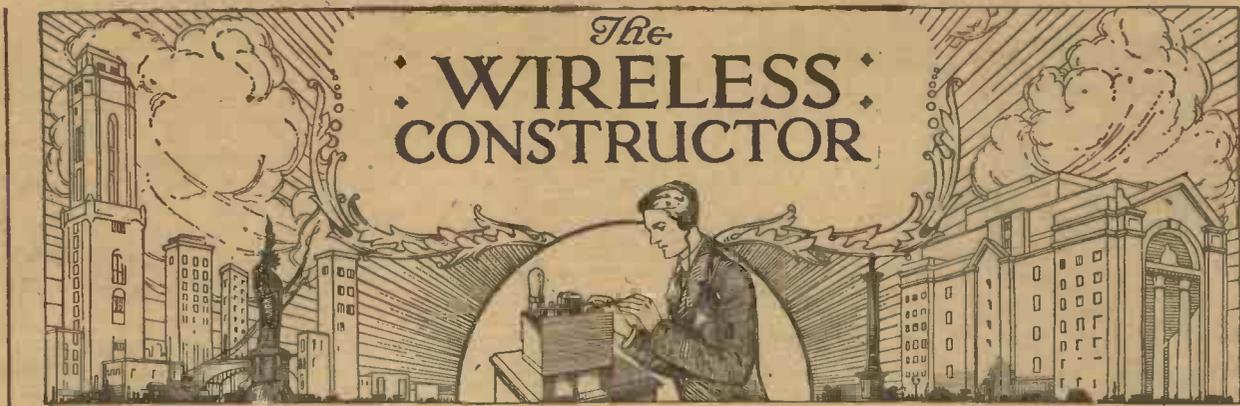


Published by Radio Press, Ltd., Bush House, Strand, W.C.2. 'Phone : City 9911.

THE "SPANSPACE THREE"

A Radio Press Star Set

AN INEXPENSIVE SET OF HIGH PERFORMANCE

By G. P. KENDALL, B.Sc.

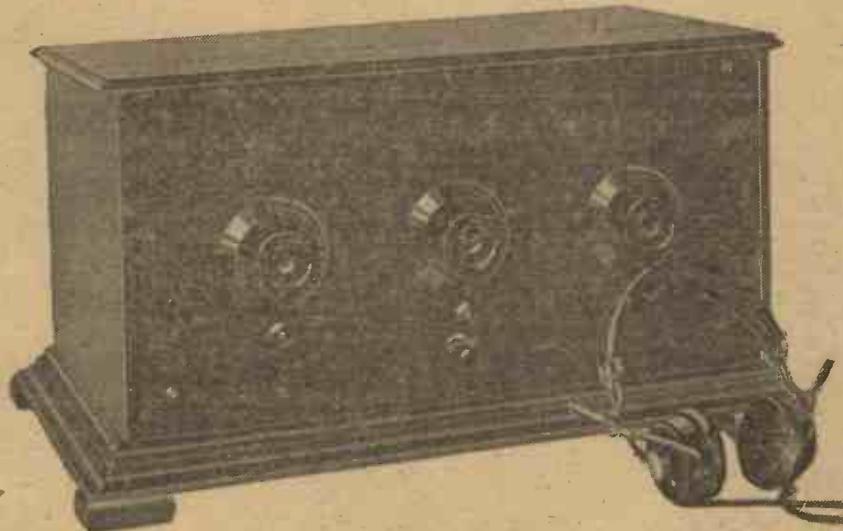

THE aim in producing the "Span-space Three" has been to provide a design giving a degree of sensitivity, selectivity, and stability at least up to the modern standard at a very moderate outlay without compelling the constructor to make any of his own components with the exception of the coils. As we shall see, the complete cost of material for building this set is only in the neighbourhood of £8, and yet the only actual constructional work which has to be done is the winding of some coil formers, and even this can be avoided if desired by purchasing the coil ready wound, which of course can be recommended to those

who lack the necessary patience for dealing with fairly fine wire.

The Circuit

The circuit of the "Span-space Three" is given in one of the diagrams accompanying this article, and it will be seen that the grid circuit of the first valve, which includes the neutralising and "anti-parasitic" arrangements, is of the same type as that which has proved so successful in the famous "El-tree Six." A centre tapping is used upon the coil, and this is connected to the centre point on a small double condenser, through a 100,000-ohms resistance.

This double condenser, it should be

explained, is not a full-size tuning condenser, but merely a small base-board-mounting balancing condenser, which has two sets of fixed plates, and only one set of moving plates, meshing more or less with either set of fixed plates. This component is included simply for the purpose of finding a centre point, which is done by setting the moving plates to engage half and half with each set of fixed plates. Tuning is done with an entirely different full-size condenser.


Intervalve Coupling

A form of tuned-anode coupling is used between the first and second valves, that is to say, between the

A Radio Press Star Set

easily as possible, the middle condenser should be removed from the panel, until practically the conclusion

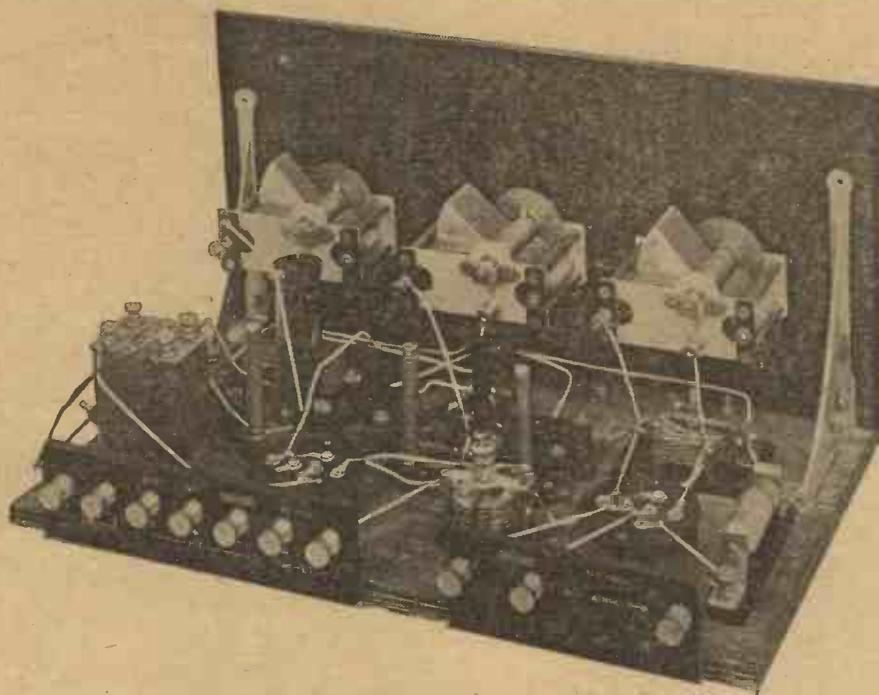soldered directly to the appropriate filament soldering tag of the valve socket, and it will be found easier to



The terminals marked GB on the left-hand strip are used for the telephones or loud-speaker.

of the wiring operations, the connections to this condenser being almost the last to be made in the set.

make this connection if it is done before the valve sockets are finally screwed down upon the baseboard,

BUILD THIS SET WITH

- One ebonite panel, 16 in. by 8 in. by 1/4 in.
- One cabinet, with baseboard, 9 in. deep.
- Two panel brackets (Peto Scott Co., Ltd.).
- Two .0005 and one .0003 geared variable condensers (Jackson Bros.).
- One "Keystone" balancing condenser (Peto-Scott Co., Ltd.).
- One baseboard mounting neutralising condenser (Burne-Jones & Co., Ltd.).
- One fixed condenser, .0003, type 610.
- One fixed condenser, .0003, type 600, with grid leak extension, and leak 2 megohms.
- One 100,000 ohm anode resistance, baseboard mounting (Dubilier).
- One H.F. Choke (Varley Magnet Co.).
- Three anti-phonics valveholders (Benjamin).
- Three holders and three suitable fixed resistors (Burndept).
- One Yaxley on-and-off switch (Rothermel Radio Corporation).
- One L.F. transformer (Brandes, Ltd.).
- Two bakelite coil formers, with standardised bases (Collinson Precision Screw Co., Ltd.).
- One ebonite strip, 5 in. by 2 in., with three terminals.
- One ebonite strip, 7 in. by 2 in., with seven terminals (Burne-Jones & Co., Ltd.).
- Glazite and a short length of flex.
- Radio Press panel transfers.

Approximate Cost - £8

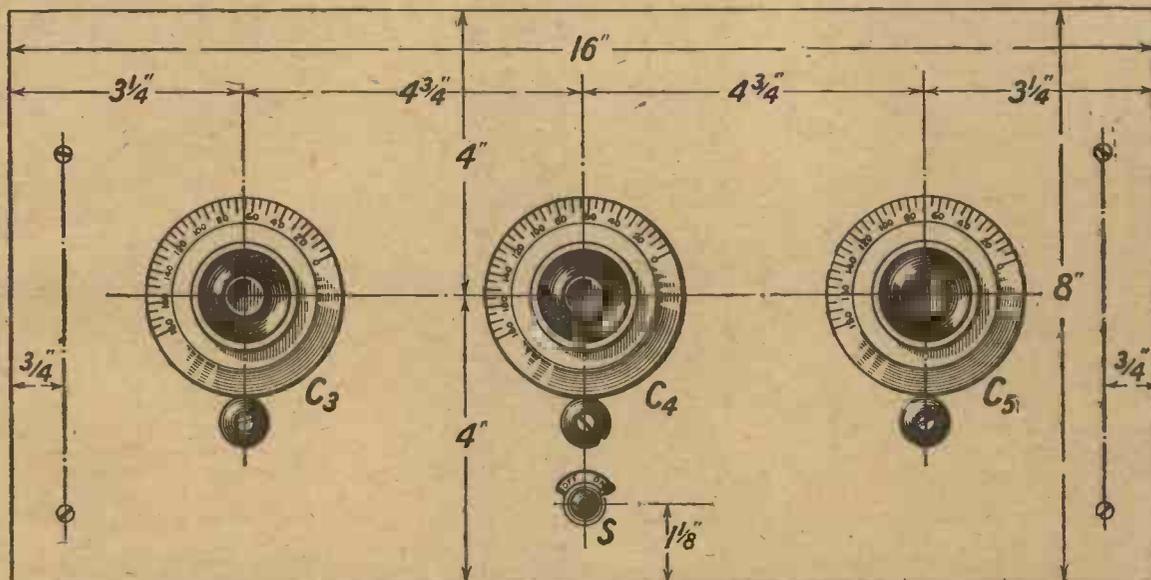


Fig. 2.—No difficulty should be experienced in laying out the panel, with the aid of this drawing. Blueprint, No. C1059A, is also obtainable.


A Soldering Tip

It will be observed that one tag of each of the fixed resistor sockets is

since if these components are operated upon separately (out of the set) the joint is quite easily made.

It will also be as well to solder one end of the wire to the lower end of the high-frequency choke, before the

THE "SPANSACE THREE"—continued

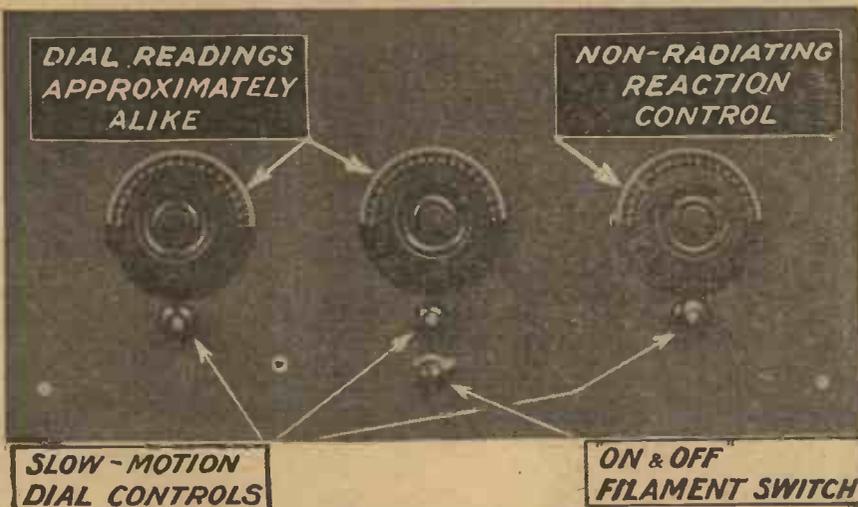

The tuning controls are simple, full non-radiating reaction is provided, and one switch brings the set into operation.

WIRING IN WORDS.

All directions are given as viewing the set from the back.

Join aerial 1 terminal to one side of condenser C.

Join other side of condenser C to aerial 2 terminal and to socket 2 of No. 1 coil base.

Join earth terminal to socket 5 of No. 1 coil base.

Join socket 3 of No. 1 coil base to one side of anode resistance R4.

Join other side of R4 to moving vanes of balancing condenser C1C2, thence to lower contact of switch S, and to one filament contact of V1, V2 and V3.

Join socket 1 of No. 1 coil base to right (C2) fixed vanes of C1C2, thence to moving vanes of variable condenser C3, and to moving vanes of neutralising condenser N.C.

Join socket 4 of No. 1 coil base to left (C1) fixed vanes of C1C2, thence to fixed vanes of variable condenser C3, and to grid contact of valve holder V1.

Join remaining filament contact of V1 to one side of fixed resistor R1.

Join other side of R1 to one side of fixed resistors R2 and R3, also to L.T.+ and H.T.— terminals, and to end of leak R5 remote from fixed condenser C6.

Join remaining side of R2 to remaining filament contact of V2.

Join remaining side of R3 to remaining filament contact of V3.

Join top contact of switch S to L.T.— terminal.

Join common contact of leak R5 and fixed condenser C6 to grid contact of V2.

Join anode contact of V1 to remaining contact of C6, also to fixed vanes of variable condenser C4, fixed vanes of neutralising condenser N.C., and socket 1 of No. 2 coil base.

Join moving vanes of variable condenser C4 to moving vanes of variable condenser C5, also to socket 4 of No. 2 coil base.

Join grid contact of V3 to G terminal of L.F. transformer T1, T2.

Join socket 3 of No. 2 coil base to H.T.+1 terminal, also to H.T.+ terminal of T1, T2.

Join H.T.+2 terminal to right telephone terminal.

Join left telephone terminal to anode contact of V3.

Join P terminal of T1, T2 to bottom end of R.F. choke.

Join top end of R.F. choke to fixed vanes of variable condenser C5, and to anode contact of V2.

Join flex leads, fitted with battery wander plugs—

- To filament negative contact of V3, for connection to grid bias positive.
- To L.T.—terminal of T1, T2, for connection to grid bias negative.

used, with perhaps 100 or 120 volts on the anode and 4½ or 6 volts grid bias.

Neutralising

The neutralising adjustment on this set can be made in the ordinary way by tuning in the local station, removing the fixed resistor which controls the first valve, and so setting the neutralising condenser that no amount of re-tuning will bring in the local station once more.

It should be noted that full details are given in this article to enable the intending constructor to build the "Spanspace Three." In the next issue of THE WIRELESS CONSTRUCTOR further notes will appear, describing the operation of the set and how to obtain the best results from it.

DETAILS OF COIL WINDINGS

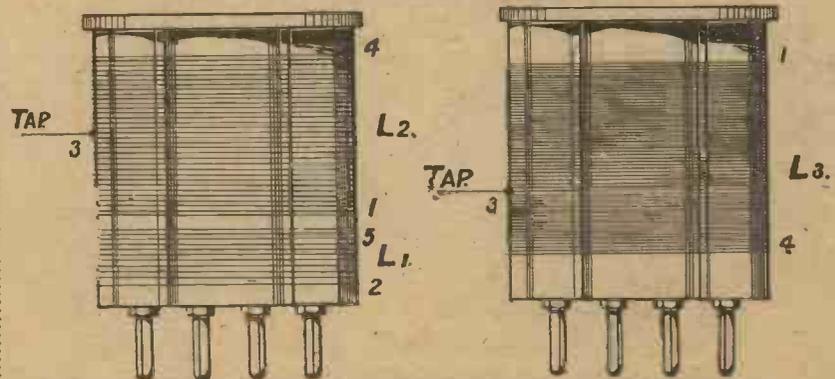


Fig. 4.—The coils are wound with No. 34 d.s.c. copper wire on the bakelite formers, turns touching.

L1—20 turns. Top end to pin 5, bottom end to pin 2.

L2—90 turns, on the same former and in the same direction as L1, tapped at 45 turns. Top end to pin 4, tapping to pin 3, bottom end to pin 1.

L3—90 turns, in the same direction on the other former, tapped at 30 turns. Top end to pin 1, tapping to pin 3, bottom end to pin 4.

NEWS IN ADVERTISEMENTS

Messrs. Telephone Manufacturing Co., Ltd., request our readers to send for the new T.M.C. catalogue.

Full particulars of the Standard and Belden products are contained in the catalogue issued by The Standard Insulator Co., Ltd.

"Makers of things more useful."—The Benjamin Electric, Ltd., describe the full range of Benjamin products in their two advertisements.

The International Radio catalogue issued by Messrs. Will Day will be sent upon request.

Full descriptions of Eddystone Radio Products will be forwarded by Messrs. Stratton and Co., Ltd.

Colvern screened coils are announced by Messrs. The Collinson Precision Screw Co., Ltd.

The Weston Pin Jack Voltmeter is the subject of an announcement by the Weston Electrical Instrument Co., Ltd.

A postcard will bring an interesting booklet from Messrs. Peto and Radford.

The Duvarileak—the new variable grid leak produced by the well-known condenser manufacturers—is featured by Messrs. The Dubilier Condenser Co., Ltd.


Experts in the solution of cross-word competitions will be interested in the advertisement of The New London Electron Co. Ltd.

Messrs. A. H. Hunt's Leaflet No. 155 will be sent upon application.

The 1926/1927 catalogue of Duodyne and Curtis' receivers can be obtained by any reader.

Messrs. Pettigrew and Merriman are offering to send the Newey catalogue of radio components.

THE CAT-ASTROPHE.

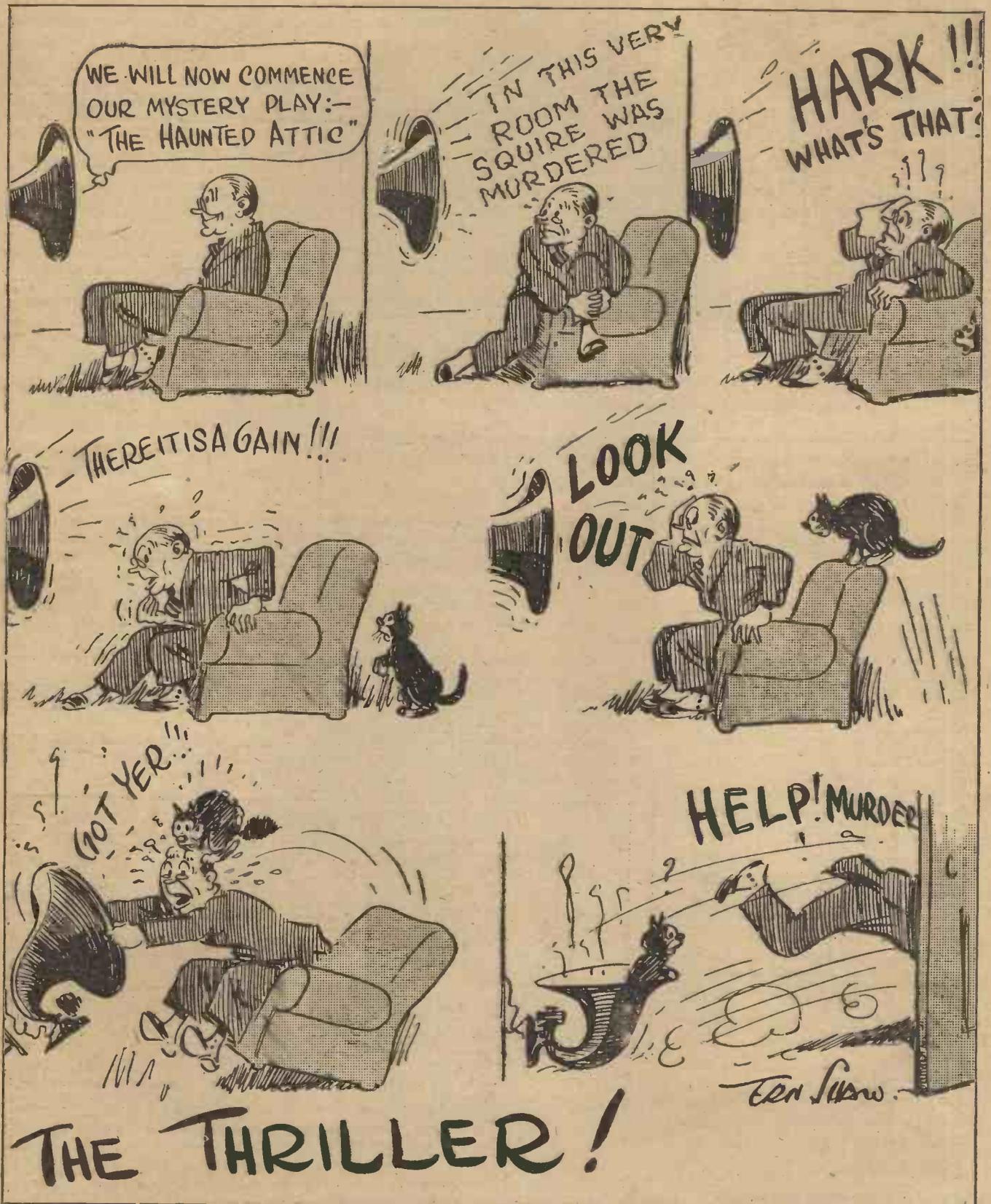



PREPARE FOR THE WINTER

The Autumn Overhaul

By Captain JACK FROST, M.I.R.E.

Has your set been laid aside during the summer? The long evenings when you will want it again are coming, so now is the time to overhaul it and see that every part is ready for service. Captain Frost tells you in this article where to look for trouble if the set has been neglected.

HOW many of my readers are folk who, for the sunny, warm weather, put the wireless set away into a cupboard, lock it up and say: "Until the dark evenings come once again, I am saying 'Good-bye' to you, my fireside friend; good though you may be during the winter months, you hold no attraction for me now that the open air is calling"? Sometimes those who think as my imaginary friend thinks do not even trouble to put the set into a cupboard and lock it up.

The Penalty of Neglect

They carefully leave it just where it is, batteries, valves, 'phones and accumulator, all exposed to the sunshine coming in through the near-by window, and all connected just as they were when last the set was used. Dust collects upon the ebonite panel, the sun robs that panel of its insulating qualities. The dry batteries deteriorate and become useless, the low-tension accumulator does something a degree or so worse than that; it commences to sulphate.

And those valves, poor expensive things, exposed to broom handles and sundry knocks when the room is being cleaned, they may well have ceased to be whole, at any rate as regards their filaments. Poor old set! Yet, that set may have to bear a great deal of blame, or perhaps 2LO will, when it fails to do as it has always done when once more you switch it on and the weakness of its voice is evident!

The Set Complains

The set, if it could speak, would say: "I am doing exceptionally well in being able to speak at all. I have had but little food to eat these many months, for my store of filament current has run low, and the high-tension volts for my valve anodes are lower still. I am choked with dust, and my interior is nearly short-circuited by it. My ebonite face is dusty and has lost its insulating qualities. My aerial—". And here speech failed the set, for it gave up with a rapid "fade" into silence.

Don't Forget the Aerial

But what about that aerial? What has happened to it during these many

weeks? The skies have rained upon it, soot has choked it, gases in the air have acted upon it, its joints have worked loose by continual swaying in the wind, and it has sagged like a candle in strong sunshine. That which the aerial can give to the set, and no more, the set is able to use. If that be little, the set cannot possibly give you a great deal. The whole game of Radio is to have a good high aerial, so that the set, providing that it is itself efficient, may receive as much energy from the ether as is reasonably possible. The set must be able to take that energy and magnify it without distortion, converting it in the process into audible sound.

Do You Do This?

But what of those of us who do not sit aside in the summer months, leaving Radio to its own devices? We may not do very much to our winter set, but may use a portable set, which

ing in this life seems ever to bide still; when things are not moving forward they are going backward. Anything which we may have done to the installation will be all to the good, but that "little more" in readiness for the "best reception in the town" reputation is necessary. It is not going to cost much either. A little time and a little care which is going to be well repaid.

What Needs Doing

Suppose that we set about it? I do hope that your aerial is as mine is, "lettable down" by a couple of pulleys? If so, then labour will be lightened. When it is down, go along the wire with an old cloth and clean it. See if there are any "kinks" in the wire, or any flaws. If they are too bad, then put in a new length of wire. Look at the insulators; are they cracked? Clean them or renew them as necessary. See that the aerial wire,

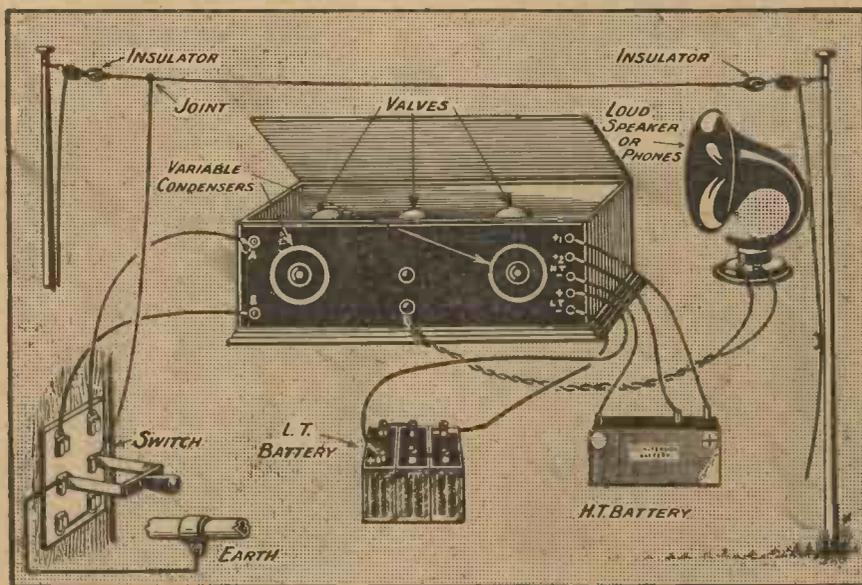


Fig. 1.—Here are the principal points in the set and its accessories which are likely to need attention.

we take away with us into the open air and there listen, or not listen, as the mood takes us. At home our set is being "corrupted" by "moth and dust," and much is happening. Noth-


ing in passing around the insulators, does not touch any anchoring wires that also pass through the porcelain holes. Unbind and examine the joint between the aerial and lead-in wires,

Prepare for the Winter—continued

Clean with a knife the strands of wire which form the joint until shining copper is exposed. Remake the joint, re-soldering it for preference. Your lead-in wire is insulated? It may be faulty beneath the insulation. Get a battery and galvanometer and test for continuity. If you cannot do that, feel along the wire for breaks. Examine the lightning switch, and tighten up screws and joints, clean the joint where the lead-in comes on to

hulls. If so, then you can leave the rest to them. That, too, will cost very little, fresh acid, perhaps, "topping up," and a recharge. If the plates have buckled or shorted, or if sulphation has started, then the proprietor will tell you. That greyish-white deposit at the terminals of an accumulator is the first sign of sulphation. Do not let it get that far, but keep the screw pillars of the terminals well greased with vaseline."

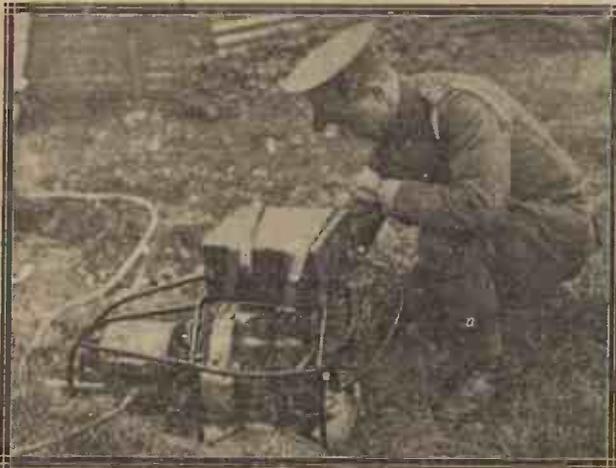of good; if that old set, overhauled, gives you satisfaction instead of annoyance, at the expense of a small sum which might save you a greater outlay for a fresh set later on.



* * *

A portable high- and low-tension generator used in the Army training "war" this year.

* * *

the switch and where the cable goes through the window frame from switch to set. Test that, too, for continuity and freedom from breaks.

Testing the Set

Deal similarly with the earth lead. If it is a water-pipe earth, disconnect it from the pipe and clean the strands till they shine again. Then remake the joint. The set comes next. Take out the valves, examine them, and see if they light? You can, for the rest, best test them in the set itself, for if they are broken you will certainly get no signals! With a fine brush, dust the set inside and out. See that it, and the batteries are where the sun cannot get at them. Revolve the condenser dials and see whether, with the set "on," you hear cracklings as you turn them round. If you do, then they may be caused by dust on the plates or by two of the plates coming into contact as they revolve.

If You Can't Do It Yourself

You cannot really do very much to the set unless you happen to be someone who knows a lot about it and can test transformers and leads. If your set is still "dud," or if you really want to have a proper overhaul carried out, then send it along to the makers. They will only charge you a shilling or two, and it will be well worth while. Send the filament lighting accumulator to your local charging depot, but first see that that station is really one qualified to do over-

haul. If so, then you can leave the rest to them. That, too, will cost very little, fresh acid, perhaps, "topping up," and a recharge. If the plates have buckled or shorted, or if sulphation has started, then the proprietor will tell you. That greyish-white deposit at the terminals of an accumulator is the first sign of sulphation. Do not let it get that far, but keep the screw pillars of the terminals well greased with vaseline."

Loud-Speaker or 'Phones

Testing of 'phones and loud-speaker comes next. The terminals on your set, to which your loud-speaker and/or 'phones are connected are marked + and -. One tag of your 'phones is bound with a little piece of red cotton. That is the +, the other being the -. You should have had the + 'phone or loud-speaker lead connected to the + terminal of the set, and the - to the -. If you have not, the odds are that your 'phones or loud-speaker have suffered what is called "demagnetisation," a long word for a run-down condition of the magnet, without which that loud-speaker or those 'phones will not operate. Even if you have had them connected correctly, a little overhaul will do no harm. So just send them to the makers whose name is stamped upon them. If they are foreign instruments, then, I am sorry! The makers will make a world of difference to them at the cost of a few pence, and within a day or so.

This is quite a sermon, and a long list of "do this's" and "do that's," but it will do your interest in wireless and in the programmes a whole lot

DRILLING LARGE HOLES

THE process of drilling holes of large diameter in ebonite or wood is not an easy one for those who do not possess a good fret-saw. The accompanying diagram shows how this may be done. First scribe the hole to be cut with a pair of sharp-pointed dividers, as shown.



Fig. 1.—When no special tool is available, a large hole may be made in the manner shown.

Next make a succession of fine drill holes around the circumference thus marked. It should be noted that in employing this method, the diameter of the circle described should be somewhat less than the full diameter of the hole required, to allow for the diameter of the drill holes and finishing. When holes have been drilled all round the circumference, a sharp knife will easily and quickly complete the work. A smooth finish is finally obtained by running first a file and then glass paper round the edges of the hole thus made.


H. B.

THE ELSTREE "SOLODYNE"

One Dial—Over 50 Stations.
Further notes on the operation of this Radio Press Star Set appear in the October issue of

"MODERN WIRELESS."

Now on Sale. Price - 1/-

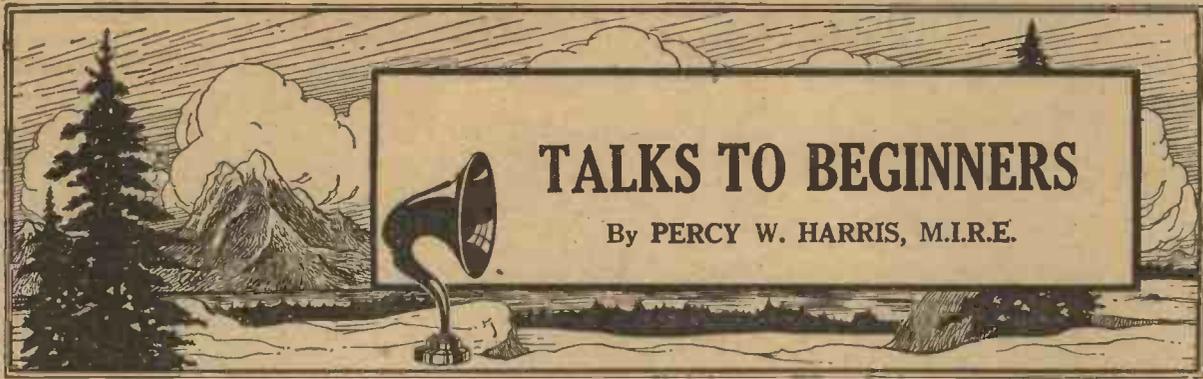

VIII.—THE WORLD ROUND US

SO far in these articles I have dealt in the main with the apparatus we use, the reasons for constructing it in certain ways and the manner in which it is operated. As by the time this issue is in your hands, the season of the dark evenings will have arrived and your wireless set will be coming once more into regular use, a talk about the etheric conditions surrounding us may not be inappropriate. And so in this article I want to tell you a few facts about range, ether conditions and what you may reasonably expect in various circumstances.

The Uncertainty of Reception

As is the case with nearly all sciences, the more one learns about radio, the less certain does one feel in making predictions. Only the most inexperienced salesman will definitely guarantee long-distance reception with the set he is trying to sell, for the more experienced investigator will know that wireless conditions vary enormously from place to place and almost from hour to hour. Do not imagine from what I have just said that long-distance reception is impossible—far from it. What I wish to impress upon you is that the fact that a particular receiver has given loud-speaker results from a station a thousand miles away on, say, September 15 in Hampstead is no proof that the same receiver will give such reception in, say, Croydon on the same date or at, perhaps, Clapham on any other date. We shall see in a few minutes why this is so.

Day and Night Variations

It was thought at one time, and the deduction was based upon relatively few experiments, that wireless waves travelled out equally in all directions from a station, and that if we drew a circle round the station up to any distance within its range, the strength of signals would be approximately equal (given identical apparatus) at all points on the circumference of the circle. Very soon it was found that day conditions were quite different from those obtaining at night, that

some wavelengths travel much better in daytime than at night, while others travel much better at night than during the day, and that a line joining all the points at which signal strength was equal would take the form, not of a circle, but of an extremely irregular figure, its shape much more resembling a large splash of ink than the circle which theorists had been led to assume.

and I am reproducing this map herewith for your guidance. You will see how different are the facts from the early elementary theory.

Directive Effect

Now there are a number of factors contributing to the modification of the perfect circle. For one thing the form of the aerial at the broadcasting station may be such that signals are

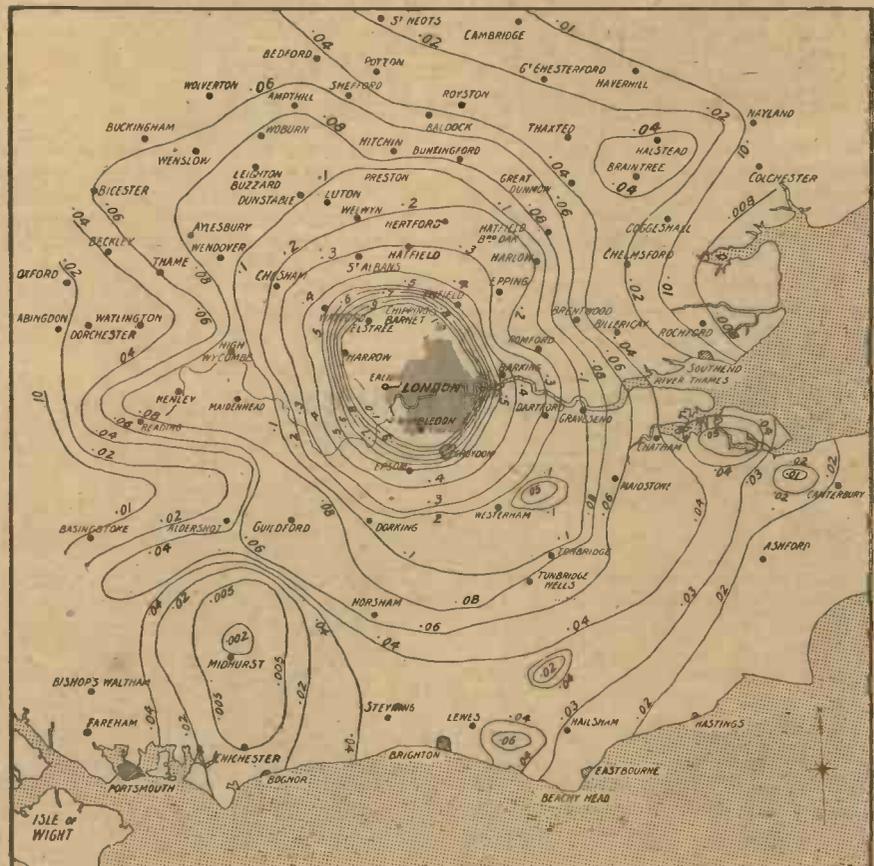


Fig. 1.—This map shows the comparative strength of signals received from the London station as observed over a considerable area.

Some weeks ago *Wireless*, the One-Word Weekly, published a map showing a series of lines joining points of equal signal strength around London,

not sent uniformly in all directions. All receiving aerials do not receive equally well in all directions, although, as a matter of fact the type of aerial

Talks to Beginners—continued

used by the average amateur, in which the top, flat portion is not much more than two or three times the length of the downlead, receives fairly equally in all directions. The 2LO aerial, I believe, radiates better in some directions than in others.

An Interesting Test

Then again, there may be screening by hills, and in the immediate locality of a receiving station by high buildings. I remember driving home in a friend's car from Bush House to Wimbledon with a portable receiver on board working a loud-speaker all the time. It was most fascinating to observe the differences in signal strength as we proceeded along the route, which incidentally followed the Embankment, King's Road, Chelsea, Putney Bridge, Putney Hill and across Putney Heath and Wimbledon Common.

Screening

Sometimes we would pass a tall building which would intervene between the London station (which was then Marconi House) and the car, and would expect signals to be reduced, but the strength would remain just the same. At other points where the land seemed quite clear and there was no obvious screening, signals would drop to practically zero. All the time they were up and down, sometimes coming intensely strong and at others dropping to a whisper. At the beginning, along the Strand and down Whitehall, signals were quite poor, and it was not until we were on the Embankment that the strength



started to rise to something approaching what one would expect. Although I have not tested it myself, I am told that on the high ground at Wimbledon Common there is at least one spot where signals are very weak, although there is nothing around to suggest screening of any kind.

Summer and Winter

Wavelengths on the broadcast band invariably carry much better at night than during the daytime. As most



This "Radio Tower," recently erected in Berlin, is 460 feet high, and is designed for use in connection with broadcasting in Germany.

wireless listeners use their sets in the evenings after dark, they may not be aware of this fact. Generally speak-

were so good that there was hardly a set made by Radio Press designers that did not during its test and in the early hours of the morning receive at least one of the American broadcasting stations. During that season I heard WGY, Schenectady, WHAZ, Troy, New York, WJZ, New York, KDKA, and many more, not once, but twenty or thirty times.

On one occasion I remember listening on a two-valve set in the early hours of the morning, hoping that I might possibly be able to hear an American station. After less than a quarter of an hour's searching I succeeded in picking up WGY so distinctly as to recognise every word the announcer spoke. Those conditions did not last long, and after about 10 minutes I could get nothing further, but the reception was achieved, and at the time was thought nothing very remarkable. On another occasion, using the Anglo-American Six, to which I referred in my last article, a piano recital from WGY, Schenectady, came over so well that it gave loud-speaker reproduction audible throughout the house as distinctly as if it had been 2LO.

Short Waves

Last winter reception conditions from America were, I think I can safely say, worse than they have been for several years past, and I do not think there was a single night as good as that to which I have just referred. KDKA, the Westinghouse Station at Pittsburg, is now working on very short waves, and as these are not affected so much by seasonal variations and by day and night conditions, they can very often be heard in the daytime, but short-wave reception of this kind needs special apparatus and does not come within the scope of this article.

Bad Conditions

Conditions on the other side of the Atlantic have also been bad, and, indeed, so many complaints have been made to wireless set manufacturers and so many sets returned to their makers as being inefficient that the Government has decided to hold an inquiry into radio conditions and to collate evidence. When I was in America last year conditions were particularly good, as I was able personally to observe, but this year they have been very bad indeed, and the manufacturers are therefore anxious for the Government to prove that it is not the fault of the sets that reception is so bad.

A Good Season Coming

All this may lead you to ask, "What are conditions going to be like this winter?" It is impossible to prophesy, but a few observations
(Concluded on page 74.)

ing, the winter months are far better for long-distance reception than the summer months, and in passing I may say that wireless conditions during the past summer have in the main been very poor. A couple of years ago we had a most remarkable winter. Long distance reception conditions

THE "INVALID'S THREE"

Described by

J. H. REYNER, B.Sc. (Hons.), A.C.G.I., D.I.C., A.M.I.E.E.

A three-valve receiver which will give good volume from the local station or Daventry, a switch bringing in either station, and no tuning being needed when once the receiver has been adjusted.



MANY people must have wanted a set which had only to be switched on to receive either the local station or Daventry at will. A receiver was recently described in these columns by W. Q. Kay (the "Davlow Three," in the August issue of THE WIRELESS CONSTRUCTOR), in which it was possible to change over from London to Daventry by a simple push-pull switch, but at the same time a re-tuning of the condensers was necessary.

Few Controls

The receiver to be described here contains two tuning circuits, one of which is tuned to the local station and the other to Daventry, and the detector and amplifying apparatus is switched from one to the other by a simple push-pull arrangement. As far as controls are concerned, therefore, there are two only. To switch on the receiver one has to insert an

Such a receiver is ideal for an invalid, and in fact a receiver of this nature was actually made up a short time ago for a friend who was temporarily confined to bed. The boon of being able to receive either programme at will without any necessity for tuning was a considerable one, and the idea will probably recommend itself to our readers.

Quality

For a receiver such as this the question of quality is of great importance.

per stage is small, and three stages at least are necessary in order to obtain an amplification comparable, say, with that given by two good transformers.

Modern Improvements

Recent developments have changed this state of affairs. The maximum amplification which is obtainable from a resistance-coupled arrangement is given by that of the valve itself. In practice the actual amplification is about 90 per cent. of the theoretical voltage amplification factor. Thus in

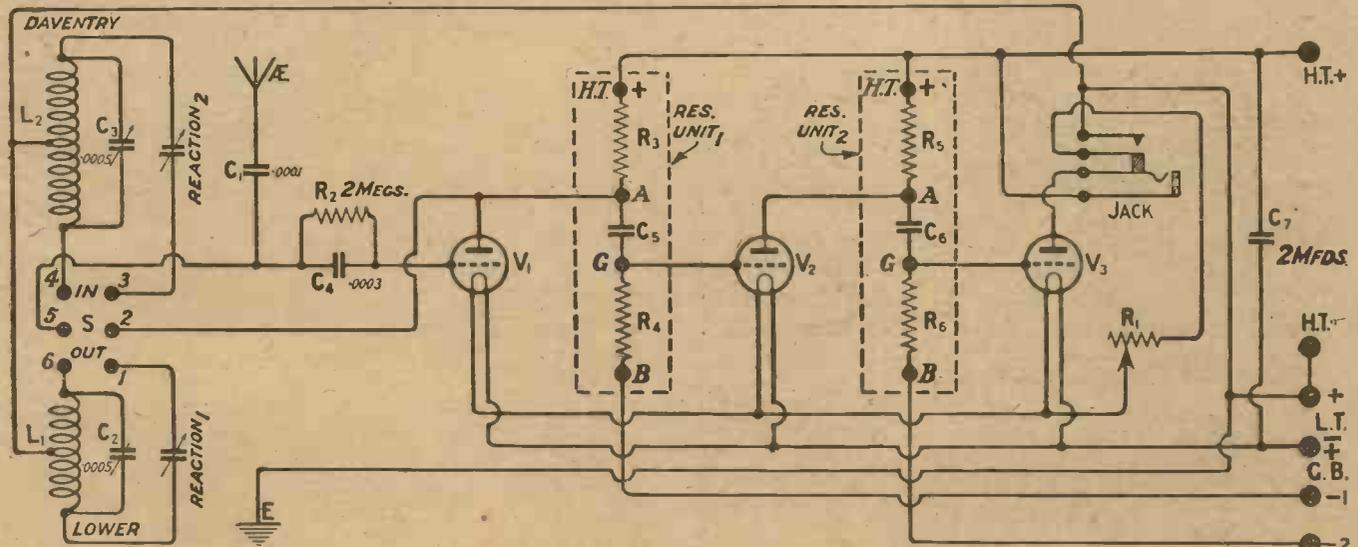


Fig. 1.—A filament switching jack is used, so that the set is brought into operation by inserting the loud-speaker plug.

ordinary telephone plug into a jack, while the programme from the local station or Daventry can be received at will without any further adjustment by a simple setting of the push-pull switch.

There can be no doubt that a really well-designed resistance-coupled amplifier is capable of giving almost perfect quality. The drawback to the usual methods of resistance amplification is that the total amplification

the ordinary high-impedance valve the limit to the amplification per stage is something of the order of 16 to 18, whereas with a transformer the nett amplification is the product of the valve amplification and the step-

The "Invalid's Three"—continued

up ratio, and this can quite easily result in an amplification per stage of between 30 and 40.

Suitable Valves

Recently, however, valves have been developed having a very high amplification factor, of the order of

of the order of 70,000 or 80,000 ohms, and it is obviously necessary to adopt slightly different constants in the circuit in order to obtain maximum efficiency from such valves.

Excellent Results

This method has been adopted in the

resistance coupling adopted, and there can be no doubt that this type of circuit opens up new possibilities in the art of resistance-coupled amplification.

Circuit

The actual circuit is shown in Fig. 1. It will be seen that there are

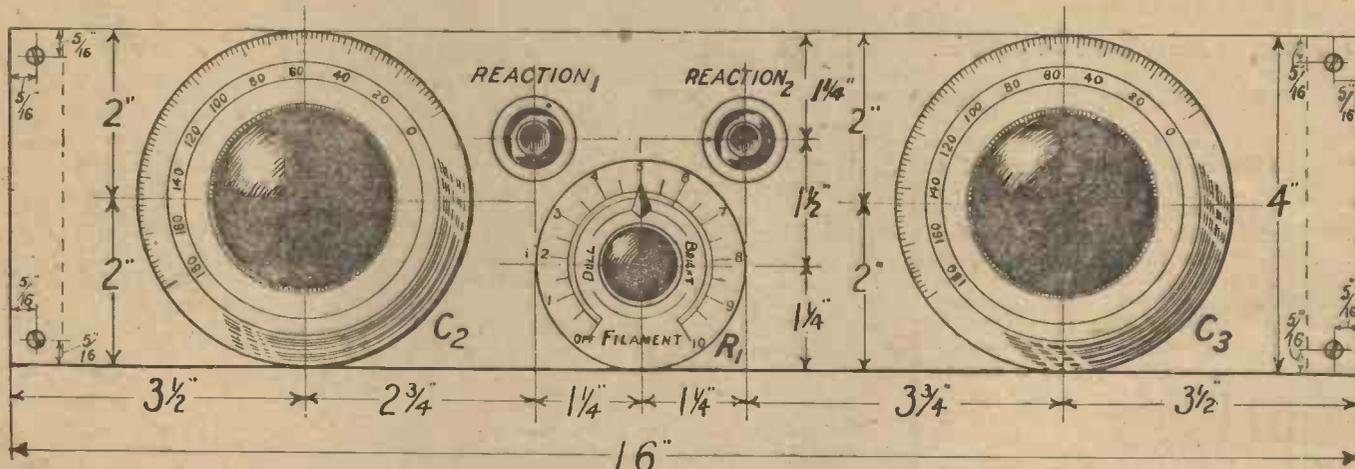


Fig. 2.—The drilling layout of the panel carrying the tuning controls is quite simple. Blueprint No. 1066A.

35 to 40, and obviously if such valves can be utilised for resistance amplification, then the discrepancy between

BUILD THIS SET WITH—

One cabinet, with wooden panel, 18 in. by 9 in., with a circular hole, 2½ in. diameter in the centre, and baseboard 9 in. deep.

Three ebonite panels, one 16 in. by 4 in. by ¼ in., one 6 in. by 3 in. and one 9 in. by 3 in., with 9 terminals.

Two .0005 "Cylton" variable condensers (S. S. Bird).

Two panel mounting neutralising condensers (Peto-Scott Co., Ltd.)

Three valve holders (Etherplus).

Two baseboard mounting coil sockets (Burne-Jones & Co., Ltd.).

One filament rheostat. In this set a dual rheostat has been used, to allow various types of valves to be employed (Burndept).

One .0003 fixed condenser, type 600, and 2-megohm leak, and one .0001 fixed condenser, type 600 (Dubilier).

One Frost filament switching jack (Rothermel Radio Corporation of Great Britain, Ltd.).

One push-pull change-over switch (Falk, Stadelmann & Co., Ltd.).

Two centre-tapped coils, one for the lower broadcast band, and one for the higher range. In this receiver Gambrell centre-tapped C and E coils were used.

Two resistance coupling units (Cosmos).

One 2-microfarad Mansbridge fixed condenser (I.C.C.).


Glazite and a short length of flex.

this method and the transformer-coupled method will not be by any means so marked. Such valves have at the same time a high impedance,

present case. The receiver is a simple three-valve one, comprising a detector and two resistance-coupled note magnifiers. The volume of signals obtainable from this is, as good as that obtainable from transformer-coupled stages, if not better. The London station at a distance of 12 miles is too

two tuned circuits, incorporating a centre-tapped coil. One end of the circuit is taken to the grid of the valve, the centre tapping taken to earth and the negative of the filament, while the other end of the coil is taken through a small neutralising condenser on to the anode of the

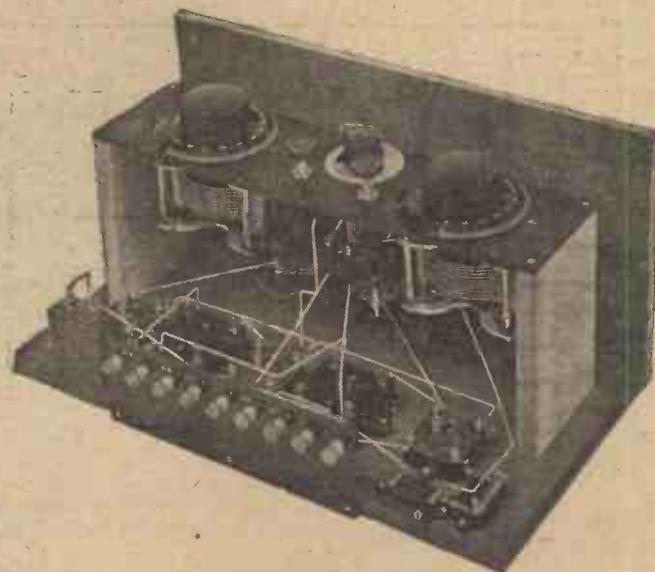The disposition of the components on the baseboard should receive careful attention.



loud for the average loud-speaker, and has to be mistuned for pleasant results, while on Daventry the volume is quite as much as the loud-speaker can handle. At the same time, provided adequate precautions are taken, the quality is excellent, owing to the

valve. This arrangement enables Hartley reaction to be obtained on the circuit if necessary. In the majority of cases it will not be necessary, but it may be useful for those living in more remote localities.

A simple change-over switch takes

The "Invalid's Three"—continued

the connections from the grid and anode from one circuit to the other, while the aerial itself is connected to a small fixed condenser direct on to the grid of the valve.

Resistance Coupling

The anode circuit of the first valve, which of course is the detector, contains a high resistance of the order of

this in practice has been found to be the case, the signal strength obtainable from the arrangement being truly astonishing.

The list of components required to construct this receiver will be found in the accompanying table.

Constructional Work

The constructional work of this

large ebonite panel just to contain these two components, so a wooden panel with a circular hole cut in it has been employed, and these two components have been mounted on a small ebonite panel 6 in. by 3 in., which is placed behind the wooden front panel.

The first operation, therefore, is to mount the push-pull change-over switch and the filament switching jack


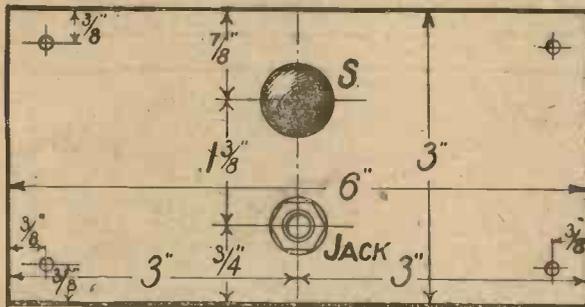


Fig. 3.—The drilling diagram for the ebonite panel which is attached behind the hole in the wooden panel. Blueprint No. 1066B.

250,000 ohms. The voltages developed across this resistance are transferred through a small fixed condenser on to the grid of the next valve, a leak being provided from this to a point on the grid bias battery, in order to stabilise the potential of the grid.

The second valve is provided with a similar form of resistance coupling, having a very high resistance in the

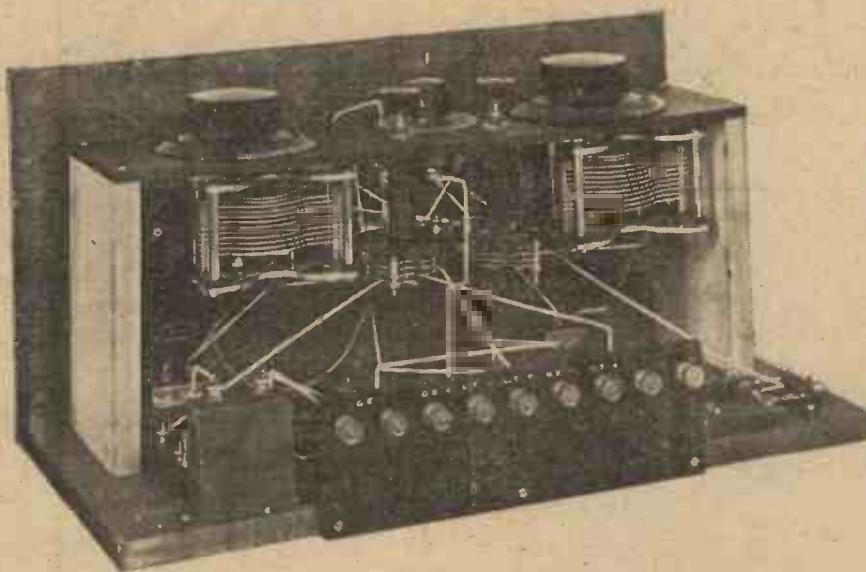receiver is not so straightforward as in many cases. The tuning controls have been placed on a sub-panel behind the main panel, so that they may be adjusted once and for all, and altered from time to time if any change of wavelengths occurs, but beyond that they are not normally touched in the operation of the receiver.



This view of the set shows clearly the disposition of the wiring to the components on the tuning control panel.

anode circuit, while the last valve, which should be a power valve, simply contains the loud-speaker in the anode circuit. As long as the resistances in circuit are large compared with the impedances of the valves, then practically full amplification is obtainable from the valves in use, and

Wooden Panel

The only controls on the front panel, therefore, as previously stated, are the change-over switch from the local station to Daventry and the jack, which at the same time switches the set on or off. It is not necessary to have a

WIRING IN WORDS

Join aerial terminal to one side of fixed condenser C1.

Join other side of C1 to one side of fixed condenser C4 and leak R2, and also to contact 5 of switch.

Join other side of C4 and R2 to grid contact of V1 valve holder.

Join earth terminal to H.T.— and L.T.+ terminals, thence to top contact of jack.

Join two flex leads to top contact of jack, for connection to centre taps of coils L1 and L2.

Join H.T.+ terminal to H.T.+ terminals of both resistance units, to one side of fixed condenser C7, and to bottom contact of jack. Join L.T.— terminal to G.B.+ terminal, to one filament contact of each of the valve holders V1, V2 and V3, and to remaining side of fixed condenser C7.

Join G.B.—1 terminal to B terminal of No. 1 resistance unit.

Join G.B.—2 terminal to B terminal of No. 2 resistance unit.

Join G terminal of No. 1 resistance unit to grid contact of V2 valve holder.

Join G terminal of No. 2 resistance unit to grid contact of V3 valve holder.

Join A contact of No. 1 resistance unit to anode contact of V1 valve holder, thence to contact 2 of switch.

Join A contact of No. 2 resistance unit to anode contact of V2 valve holder.

Join anode contact of V3 valve holder to lower right contact of jack.

Join contact 4 of switch to one side of L2 coil socket.

Join contact 6 of switch to one side of L1 coil socket.

The following connections are on the sub-panel.

Join moving vanes of variable condenser C3 to fixed vanes of No. 2 reaction condenser.

Join moving vanes of variable condenser C2 to fixed vanes of No. 1 reaction condenser.

The remaining connections go to the sub-panel.

Join contact 1 of switch to moving vanes of No. 1 reaction condenser (3).

Join contact 3 of switch to moving vanes of No. 2 reaction condenser (4).

Join wire between contact 4 of switch and L2 coil socket to fixed vanes of variable condenser C3 (2).

Join other side of L2 coil socket to moving vanes of C3 (1).

Join wire between contact 6 of switch and L1 coil socket to fixed vanes of variable condenser C2 (7).

Join other side of L1 coil socket to moving vanes of C2 (8).

Join together remaining filament contacts of V1, V2 and V3 and continue to one contact of filament rheostat R1 (6).

Join remaining contact of R1 to top left contact of jack (5).

one above the other in the manner shown in the diagram given. This panel may then be mounted in position behind the main wooden panel, so that the switch and jack show through the hole cut away in the centre.

Sub-Panel

The next operation is the mounting of the two variable condensers, the two reaction condensers, and the filament rheostat on the sub-panel. This panel is 16 in. by 4 in., and is

The "Invalid's Three"—continued


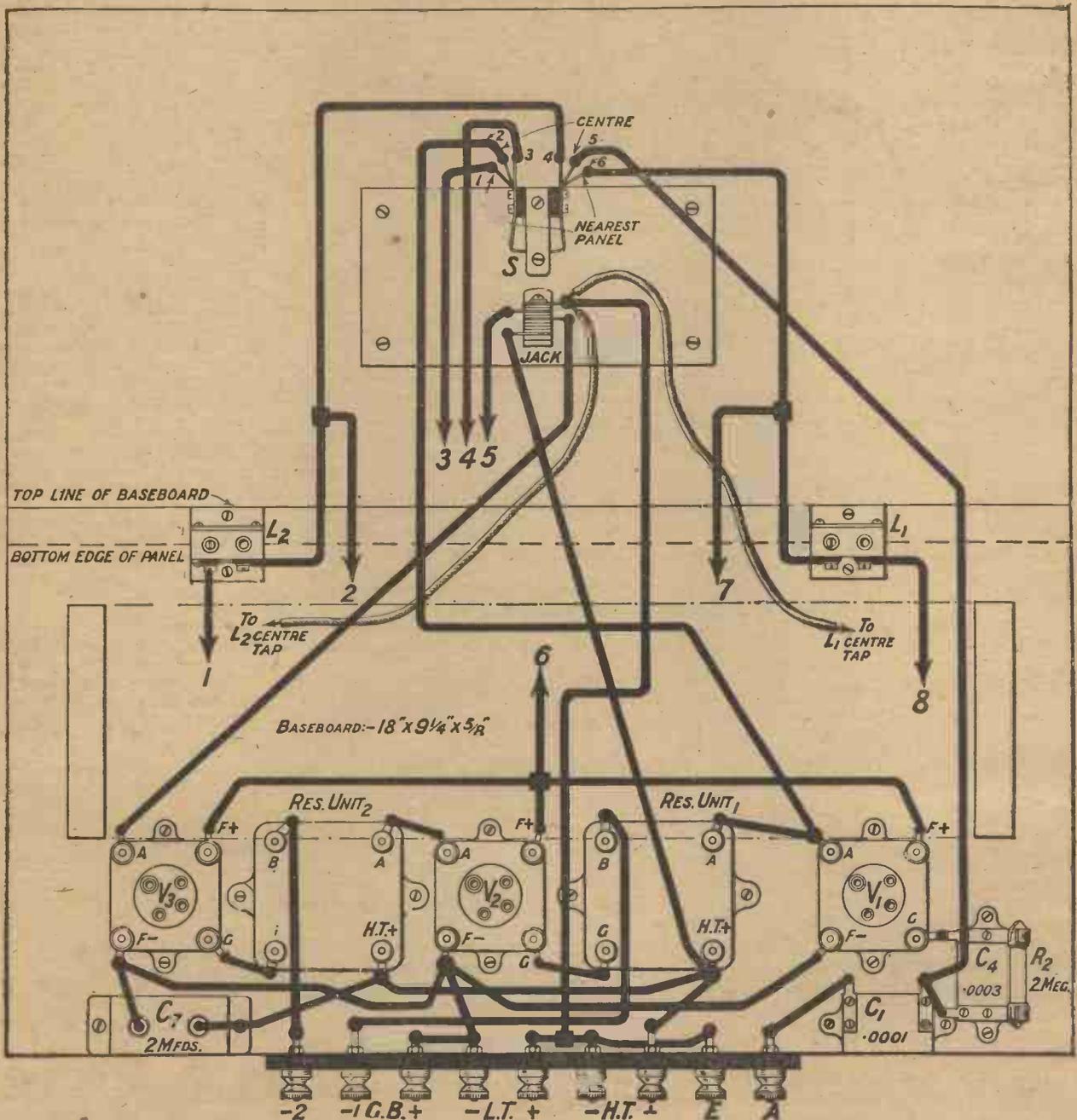
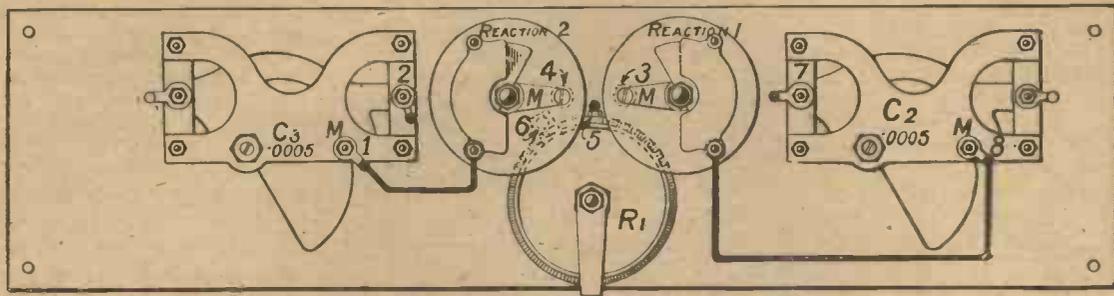


Fig. 4.—The numbered connections on the lower back-of-panel diagram go to the correspondingly numbered points on the sub-panel, shown above. Blueprints Nos. 1066C and 1066D are also available.

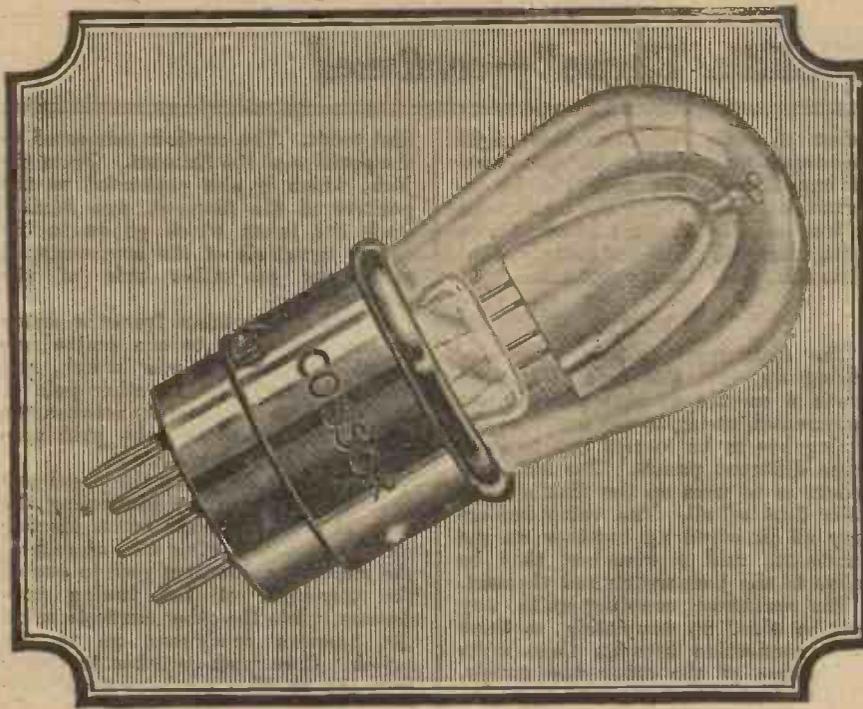

New!

from end to end

RATHER more than three years ago Cossor startled the world of Wireless by producing a valve which utilised almost the whole of the electron emission from the filament. Its unorthodox construction provoked astonishment amongst those who had accustomed themselves to the wastefulness of spiral grids and tubular anodes.

But despite the unconventional appearance of the P1 an amazingly large number of wireless enthusiasts bought it—and, in so doing, discovered an easier way to better reception, to louder signals and to a greater economy in maintenance.

The success of the first Cossor Valve was never in doubt—in fact, the famous P1 is still the standard British Bright Emitter. And during the past three years Cossor has steadily

forged ahead—winning an ever-increasing public by the sheer merit of its products.

The culmination of many years experience and determination is about to be realised in the new Cossor Point One with its revolutionary system of Co-axial Mounting and its extraordinarily low current consumption.

To the huge army of staunch Cossor enthusiasts the opportunity of acquiring a valve exhibiting such an impressive list of improvements as those shown in the adjoining column will be quickly grasped. Others—who, perhaps, have but lately succumbed to the fascination of Radio—will be glad to read about a British Valve which worthily upholds the great traditions for fine workmanship which this country has built up among the nations of the world.

New Anode

The Anode of the Cossor Point One is deeper and permits a greater length of filament being used. This in turn obviously means that a greater emission surface is available. It is electrically welded to two short, stout electrodes. Movement is absolutely impossible.

New Grid

The Grid is wound around a very stout molybdenum support. Each turn of the wire is electrically welded in no fewer than 30 positions. This method of construction ensures absolute rigidity and ability to withstand the hardest shock.

New Filament

An exceptionally long filament is used which is secured in three distinct places. When the valve is operating it is hardly possible to discern any glow. Although rated at 1.8 volts this new valve will function satisfactorily at a voltage as low as 1.2. It can therefore be used, if required, with dry batteries. No other valve has such a wide range of working voltages.

New Bulb

Its handsome new pipless glass bulb is a further safeguard against accidental damage. Only glass of the finest quality is used on all Cossor valves.

New Base

The same exclusive low loss design of base which has proved so remarkably successful on all other Cossor valves is being retained on the new Cossor Point One. A wide flange is now incorporated to enable the user to withdraw the valve from the most stubborn socket without fear of harm.

New Pins

The new pins on the Cossor Point One is a further indication of Cossor's determination to "do the job properly." Instead of a single slot, each pin is now slotted in two intersecting positions. In addition the points of the pins are tapered. Because of these improvements the valve can be inserted easily and smoothly into any socket and, once in position, perfect electrical contact is ensured.

—and new methods of construction

The Cossor Point One is the only valve to be able to utilise the new patented system of Co-axial Mounting—whereby the Filament, Grid and Anode are rigidly secured to each other in their exact relative positions in permanent alignment at the top and at the bottom. As a result, absolute uniformity of characteristics is ensured throughout the whole life of the valve, whilst the filament is fully protected against damage by shocks.

Cossor Point One

Red Band for H.F. use	1.8 volts, .1 amp.	14/-
Plain Band for Detector	1.8 volts, .1 amp.	14/-

Cossor Stentor Two

Green Band Power Valve	1.8 volts, .15 amp.	18/6
------------------------	---------------------	------

The new Cossor Point One

The "Invalid's Three"—continued

mounted on two wooden feet 6½ in. high by 4 in. wide.

Mount the two condensers on the outside positions of the panel, the two reaction condensers towards the centre and the filament rheostat in the middle. With the particular condensers shown, the layout is not perfectly symmetrical, owing to the fact that the condenser spindles are not in the centres of the condensers themselves. This applies to any of the usual types of square-law condenser.

Having mounted these components on the sub-panel, the remaining components may now be mounted on the baseboard itself. These are the three valve holders, the various resistances and condensers associated with the resistance-coupling circuits, and the C.A.T. condenser and grid condenser and leak for the rectifier valve.

Coils

Finally, the two coil mounts should be placed in the positions shown close up against the front panel. The coils are actually inserted between the front panel and the sub-panel containing the tuning arrangement. This position is a little awkward to get at when the receiver is fitted into its case, but since the coils when in position do not require to be changed

unless a fault develops, this slight inconvenience need not be considered of importance. The coils can be inserted in position when the instrument is first tested out on the bench, before being inserted into its cabinet, and thereafter no difficulty will arise.

Wiring

The instrument is now ready for wiring up, and this is a matter on which a certain amount of care will be required, owing to the fact that the wiring has to be carried out between three different panels. The best procedure is to wire up the filament circuits first of all. The valve holders may all be wired up together on the baseboard, and a wire can then be taken to the jack switch and rheostat.

The resistance coupling units may now be wired up completely, as there is no connection between these units and either of the other two panels. This part of the wiring may therefore be completed without any difficulty.

Tuning Circuits

All that now remains is the wiring up of the tuning circuits themselves. The aerial is connected through a C.A.T. condenser (.0001 capacity) to one side of the grid condenser of the

first valve. The earth is connected to the positive of the filament. From the jack, which is also connected to the positive of the filament, two flexible leads are taken which go on to the centre terminals of the centre-tapped coils, one on either side of the receiver.

A lead is now taken from the anode of the first valve to one centre terminal of the change-over switch, and a lead taken from the other pole of this switch to the junction between the C.A.T. condenser and the grid condenser of the first valve.

The wiring on the main panel can then be completed, by connecting the main tuning condensers across the two coils respectively. One side of each of the reaction condensers goes to one of the terminals of the tuning condensers, while the other connections on the reaction condensers go to the switch. Care must be taken to ensure that the reaction condensers are connected to the correct terminals on the tuning condensers, as if this is not done no reaction effect will be produced. Apart from this, little difficulty will be experienced if the wiring diagram and instructions given are followed carefully.

(Concluded on page 81.)



The "MIDGET"

An inexpensive friction tuning device giving excellent results.

The "Midget" can easily be fitted to all sets in a few moments, and it will work equally as well as many higher priced vernier controls.


All metal parts heavily nickel-plated, highly polished Bakelite knob and best quality rubber washers. It is self-adjusting. Fit one and add 100% efficiency to your set.

Complete with full instructions for fixing.

9d. Each.

Full particulars of other "STANDARD" Radio Products on application. "Belden" Battery Cord, 5, 6, and 7 way. Headphone and Loud Speaker Cords. "Belden" Loop Antenna Wire. Trade enquiries solicited.

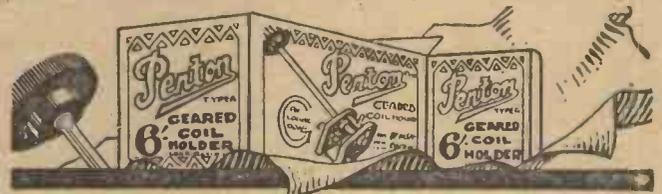THE STANDARD INSULATOR Co., Ltd.,
Winsley House, Wells Street, Oxford Street,
LONDON, W.1.
Phone: Museum 5978 and 7577.



BACKLASH—

That free-play inevitable in ordinarily geared Coil Holders and its consequent incorrect tuning and fading is

DEFINITELY BANISHED—The First Step to Perfection.

THE ECCENTRIC METAL BEARING, immediately adjustable for taking up wear (if any).

THE METAL TO METAL HELICAL GEARS (ratio 9 to 1) give a slow and even movement.

A SPECIAL LOCKING DEVICE gives a fixed security. These points together with a Finish consistent with the highest grade of workmanship throughout make

THE PENTON TYPE "A"

THE ONLY PERFECT COIL HOLDER

From your Local Dealer or Post Free. PRICE .. 6-

MOVING BLOCK CANNOT FALL.


Ebonite Strips for inside panel mounting supplied free.

Penton
TYPE "A"
GEARED
COIL HOLDER

Patent No. 193150.

For Outside Panel or Inside Baseboard Mounting.

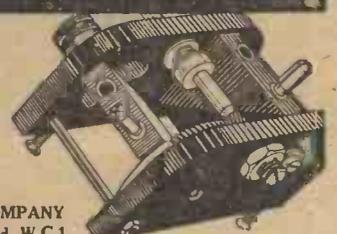THE PENTON ENGINEERING COMPANY
15, Cromer Street, Gray's Inn Road, W.C.1



**S.P. 18
RED SPOT.**

A real two-volt power valve designed specially for low frequency amplification. Should always be used in last stage for operating loud speaker. It is also suitable as a detector

Fil. Volts: 1'6.
Amps.: '3.
PRICE 14/-

**S.P. 18
GREEN SPOT.**

A high amplification valve having a moderate impedance. Designed as a high frequency amplifier and as a detector. Also suitable for resistance, choke and transformer coupling (except last stage, where an S.P. 18 Red should always be used).

Fil. Volts: 1'6.
Amps.: '3.
PRICE 14/-

**S.P. 18
BLUE SPOT.**

Extra high amplification valve. Designed for resistance capacity, choke and early stages of transformer coupling. Excellent as a detector or tuned anode H.F. amplifier.

Fil. Volts: 1'6.
Amps.: '09.
PRICE 14/-



Team work

TEAM WORK counts in Radio too. Unless valves work together harmoniously reception will never be at its best. That is why BENJAMIN Valves should be used in every stage. They have been designed as a team which, working together, will give results far surpassing those that can be obtained with any other valves, in any other way.

Anode and filament are very close together, and therefore the electrons traverse a very *short path*. This increases amplification. A specially designed filament consumes less current. Tone is improved. Ask your dealer or write for descriptive leaflet giving curves.

BENJAMIN SHORTPATH RADIO VALVES

THE BENJAMIN ELECTRIC LTD.,
Brantwood Works, Tottenham, N. 17.

D.E. 55.

A very economical general purpose valve. For high frequency, detector and low frequency (except last stage, when the S.P. 55 Red should always be used).

Fil. Volts: 5'5.
Amps.: '09.
PRICE 18/6

**S.P. 55
BLUE SPOT.**

Extra high amplification valve. Designed for resistance capacity, choke and early stage transformer coupling. Also excellent as a rectifier or high frequency amplifier.

Fil. Volts: 5'5.
Amps.: '09.
PRICE 18/6


**S.P. 55
RED SPOT.**

Super power valve specially designed as a last stage power amplifier. Will give great power without distortion. Also suitable for detector or H.F. amplifier


Fil. Volts: 5'5.
Amps.: '25.
PRICE 22/6



RV3

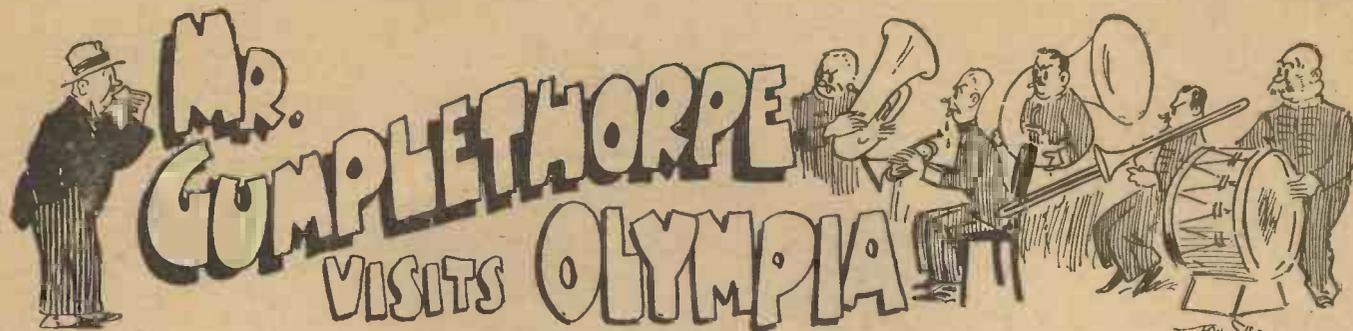

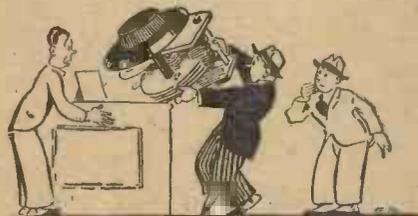MR. GUMPLETHORPE'S pockets were bursting with catalogues, and he himself with enthusiasm, when he called on me one evening last month to insist upon my accompanying him to the Exhibition at Olympia on the very next day that ever was. I had rather hoped to be able to sneak off by myself, for Mr. Gumplethorpe



Mr. Gumplethorpe fell on it with cries of rapture.

is apt to be a little trying at times, especially when he gets one of his inquisitive fits; but, as no decent excuse occurred to me, I had perforce to agree, with what grace I might. We decided to motor to Olympia in our fine L.G.O.C. car—all the knuts refer to their cars as 'buses, so I do not see why I should not refer to my 'bus as a car—which took us there without losing its way once, despite the merry-go-rounds, one-way streets, and the other little hazards and bunkers of the Metropolitan thoroughfares. Entering the main door, we found ourselves opposite a turnstile labelled "Press." Both Mr. Gumplethorpe and I pressed hard, but nothing happened. Mr. Gumplethorpe had quite a lot to say to the attendant on the subject of silly practical jokes. Not deigning to reply, he directed us to another turnstile, where we were called upon to part with eighteenpence apiece. Since I am one of the world's best fumbleers, it was actually Mr. Gumplethorpe who parted with eighteenpence twice; after all, if you have to accompany a fellow like that, I don't see why you should pay to do so.

A Man's Size in Sets

The first stand that attracted his attention was one devoted to condensers, which displayed a large-scale model of a variable instrument, a thing about as big as a rabbit hutch. Upon this Mr. Gumplethorpe fell with little cries of rapture. Always, he told the attendant, he had hated those beastly little instruments that were sold as variable condensers in wireless

shops. Here was a man's size condenser that was exactly what he wanted. He proposed to buy it on the spot, and to take it home with him.

After some discussion, he was told that he could have it after the exhibition was over, and not before. At another stand he found a similar model of a variable grid-leak with a dial about the size of a bicycle wheel. This threw Mr. Gumplethorpe into a positive ecstasy, and he entered at once into negotiations for its purchase. A stand or two away he came across a gigantic coil, which so tickled his fancy that nothing would prevent him from treating for its purchase. Having bought these things and a Weco-valve, Mr. Gumplethorpe assured me that he would shortly be turning out the finest single-valve set that had ever been seen. Personally, I am quite content to see it, so long as I am not called upon to hear it, for, having lost him for a few moments, I was horrified, on finding him again, to discover that he had purchased a loud-speaker with a horn some fifteen feet in length that decorated one of the stands. I am not quite sure whether he means to get his new components into his present house with the help of an outsize in shoehorns, or whether his intention is simply to dump them down in a field, and have a new house built round them. That, however, is his affair.

Tact

We were getting on quite nicely when Mr. Gumplethorpe put his foot slap into the middle of things. Just as we were passing one of the ebonite people's stands, he pulled out a match to light a gasper of the bespatted, or cork-tipped type that he effects, and struck it thoughtlessly upon a shining panel. Everything seemed to happen at once. Half a dozen demonstrators, speechless with rage; surrounded Mr. Gumplethorpe and myself, raising their arms to the heavens in horror, or brandishing them (with knobby-looking fists at their ends) in our faces. Luckily, my natural presence of mind enabled me to rise to the occasion and to avert bloodshed. "My friend," I said, "always strikes matches on the panels of his receiving sets. He has been sadly disappointed lately by the purchase of several large panels whose nature was such that they simply rubbed the head off the match without producing the necessary flame. Your panels appear

to be exactly what he needs, and he will be glad if you will kindly send him a dozen. My friend always pays cash down. . . ." Realising that discretion was the better part of valour, Mr. Gumplethorpe parted with the necessary Fishers, whereupon the scowls were turned miraculously into smiles. This just shows what tact can do. By exercising some more of it on



. . . he came across a gigantic coil . . .

Mr. Gumplethorpe, I am trusting to be provided with free panels for some little time to come.

The Art of Selling

"Phew!" said Mr. Gumplethorpe, mopping his brow, as we moved away. "Give me a cigarette, will you, old chap? I have not a single one left." "Sorry," I replied, "I was just going to ask you for one, for my case is also empty." "Tut, tut," said Mr. Gumplethorpe, "I must go and buy some. I wonder where the stall is where they sell them." Neither he nor I knew, but Mr. Gumplethorpe said that he would find out in two ticks. Advancing to the man in charge of the nearest stand, he began politely, "I wonder if you would be so good as to . . ." "Certainly, my dear sir, certainly," crooned the man in charge. "It is most kind of you to take such an interest in this neat little device, and I shall be charmed to show you exactly what it is for, how it works, and ——" "Look here!" protested Mr. Gumplethorpe, "what I want to know is ——" "Exactly," said the man, nipping further protests in the bud. "What you were going to say, my dear sir, is that you wish to know why it is imperative that you should fit this exceedingly neat little device to your receiving set."

The bewildered Mr. Gumplethorpe was told precisely what it did, and how and when and where and why. "Yes," said the salesman, coming to his peroration, "such is this mar-

For High Efficiency Sets

To obtain that high efficiency of an experimental set, the experimenter must ascertain that each individual component of the set will not have a deteriorating effect on the remaining parts. This efficiency can only be obtained by having guaranteed and tested components of a reputable firm. Bowyer-Lowe fulfil these qualifications and their guarantee protects you against damage by careless handling after leaving the factory, since every article bought from Bowyer-Lowe if found faulty within twelve months of purchase will be replaced free of charge.

COIL SCREENING BOXES



These Screening Boxes screw into the base and provide a perfect electrostatic screen. Sockets and terminals are to Radio Press standards. Finished in highly polished aluminium. Price 15/-

NEUTRALISING CONDENSERS



These condensers have been specially designed and provide a high class component for use in Radio Press Circuits. The minimum capacity is .00002 U.F., while the maximum capacity is .00025 U.F. Price (Board or Panel Mounting) 7/-



SUPER HETERODYNE TRANSFORMERS

Thousands of amateurs have built Super Heterodyne sets, using these transformers, with perfect success. Set of 4 transformers 24 0 0
Interchangeable Oscillator Couplers, 300-600 metres 21 0 0
Interchangeable Oscillator Couplers, 650-2000 metres 21 0 0
Base for same, 4/-

POPULAR CONDENSER



Electrically and mechanically sound in design, the Bowyer-Lowe Condensers ensure perfect results. Price with dial .0003 10/-
Price with dial .0005 10 6

JACKS



Bowyer-Lowe Jacks mark a great advance in design.

- Single Circuit open - 2/2
- " " closed - 2/7
- Double " - 3/-
- Filament single control 2/9
- " double control 3/3

ANTIPONG VALVE HOLDERS



The only valve holder with such a low capacity combined with the cushioning necessary for preventing your valves from vibrating. Universal fitting. Universal in mounting. Base board mounting. Price 3/- complete.

BOWYER-Lowe



ANNOUNCEMENT BY BOWYER-LOWE CO. LTD. LETCHWORTH, HERTS

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.

Mr. Gumplethorpe Visits Olympia—continued

vellous component whose usefulness you, my dear sir, thoroughly appreciate, as I can judge from your remarks. Was it half a dozen or a dozen that you said?" Mr. Gumplethorpe raised a feeble protesting hand, but as another torrent of words appeared to be imminent, he caved in and said that he would take half a dozen.

More Components

After some more phewing and some more mopping of his brow, Mr. Gumplethorpe suggested that I should approach a chappie at another stall. As, however, I noticed that he was dealing with aerial masts, for a dozen of which I had no use whatever, I declined emphatically to do anything of the kind.

In the end I grew so tired that I gave up following him on his frenzied excursions, and after a brief visit to one stand, sat down to wait for him to come down to earth. When he joined me an hour or so later practically a ruined man, but still cigaretteless, he gave me one awful look. "Where," he cried, pointing an accusing finger, "where did you get that cigarette?" "From the stall just behind you," I said sweetly. "I tried to tell you several times, but you were so busy buying earth tubes and things

that you would not listen to a word I said."

Refreshment

When we had rested a little, Mr. Gumplethorpe insisted upon going to the refreshment stall, where he purchased a lemon, which he had cut in half. He assured me that there is nothing like a lemon to calm one down



... struck it upon a shining panel ...

after great mental stress. His progress through the hall with his quaint fruit excited a certain amount of comment, but no great harm was done. It was only when he insisted upon visiting the B.B.O. studio that things really began to happen. We took our places in the queue, Mr. Gumplethorpe still extracting consolation from his lemon. In course of time we found ourselves before the plate-glass window

of the studio, behind which the Military Band was in full blast. This interested Mr. Gumplethorpe enormously. Despite the requests of the commissionaire to move on, he planted himself firmly in position, applying the lemon to his lips as he stood in meditation.

The Acid Test

The cornet was the first man to be affected. I noticed funny things happening to his face, and finally he threw down his instrument and shook his fist at Mr. Gumplethorpe. The euphonium and the trombone followed fairly quickly, though the bombardon and the French horn stuck it out for a time, fighting a real he-man battle against the desire to screw up their countenances. At length they, too, gave in, and no one was left but the drummer, who continued in action despite the grimaces that he was making. At this moment firm hands were laid on the shoulders of Mr. Gumplethorpe and myself, and we were conducted down the stairs to the nearest exit. "It is a good thing," remarked Mr. Gumplethorpe, turning out his empty pockets when we were in the street outside, "that one has not to pay to get out of wireless exhibitions."

A great achievement Short Wave Receiving Set

Our Short Wave Receiver received perfectly the news of the recent Dempsey-Tunney Fight. With this Receiver we will GUARANTEE RESULTS DOWN TO TWENTY METRES, or with special Coils, AS LOW AS FIVE METRES.

Full particulars of this remarkable outfit
FREE ON APPLICATION.

DO NOT FAIL TO CALL AND SEE THE NEW ILLUMINATED TUNING DIAL. Fits any condenser. Positive Hairline Tuning.

ON VIEW in our SHOWROOM WINDOWS

THE NEW SOLODYNE RECEIVING SET

the marvellous long range circuit with the single control. We have complete units for making up this set now in stock.

OUR INTERNATIONAL RADIO CATALOGUE (3rd Edition) will be sent to all enthusiasts sending 6d. to cover cost of postage and packing.


WILL DAY, LTD. (Dept. D.)
19, LISLE STREET, LEICESTER SQUARE,
LONDON, W.C.2.

Telephone:
Regent 4577.

Telegrams:
Titles, Westrand, London.

Charge your H.T. Accumulators with the NEW
"Z"

Filamentless Vacuum Tube Rectifier.

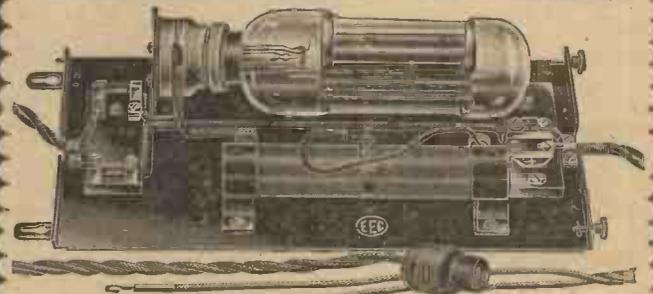

EXTRAORDINARILY EFFICIENT.
Consumption 1 unit in 50 hours!

SILENT. SAFE. SURE.

Practically Indestructible.

Operates on 200-220 volts A.C. mains of any periodicity.
D.C. output approximately 100 volts 80 milliamperes.

Price, complete, with input and output £3
leads, variable resistance, and fuses

We stock complete sets of components, valves and accessories for sets described in this and in all other Wireless Publications. Save endless delay by sending your complete order to us; we guarantee safe and prompt delivery.

Send us your name and address on a P.C. for a copy of our 44-page Radio Catalogue.

Economic Electric Ltd 10, FITZROY Sq.
LONDON W.1.



A NEW AMPLION Model

The SENIOR "DRAGON"

Model AR.65

65/-

A new member of the famous "Dragon" Series. All metal, of patent non-resonant design and finished in a pleasing chocolate shade. A new and improved light-weight unit is fitted.

Height 17". Diameter of flare 12".

AMPLION

The World's Standard Wireless Loud Speaker

Announcement of Alfred Graham & Co. (M. Graham) 25, Savile Row, London, W.1.

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.



Just as an inferior lens will create distortion so an inefficient Transformer will distort a voice



The new Eureka Concert Grand

ALMOST any kind of lens will serve to produce an image on a sensitive photographic plate. But no one expects that a simple uncorrected achromatic lens will give such faithful reproduction as an anastigmat. Exactly the same principles apply in wireless. Practically any L.F. Transformer will amplify and give some kind of results.

But if you want to hear the rippling notes of the soprano you must use a Transformer scientifically corrected against distortion. Every Eureka has been scientifically designed by specialists in the science of sound reproduction to give an even amplification throughout its entire frequency range. It does not amplify some notes at the

expense of others, but is, in fact, fully corrected against distortion.

And now, through an improved method of "stratum-winding," the efficiency of Eureka Transformers has been still further increased. At no extra cost to you there is now available greater volume and sweeter tone, whilst the possibility of breakdown has been eliminated by the use of interspaced insulation between windings.

These new and exclusive features will place the Eureka again ahead of possible competition. For your next Set, therefore, be sure to use a Eureka—"the Transformer which re-creates the living Artiste."

Types and Prices

Concert Grand	25/-
Ditto for 2nd stage	21/-
Baby Grand (1st or 2nd)	15/-
Eureka Reflex	15/-
Eureka L.F. Choke Unit	25/-

Re-creates the **EUREKA** Living Artiste

Portable Utilities Co., Ltd.,
Fisher St., W.C.I.

Gilbert Ad. 5814.



OPERATING THE "DISTAFLEX TWO"

VALVES TO USE

FULL instructions for the construction and preliminary testing of the Radio Press Star Set, the "Distaflex Two," were given in the last issue of THE WIRELESS CONSTRUCTOR. It will be assumed, therefore, that the receiver has been constructed and the wiring checked, and that tests have shown that the receiver is in order. In the photograph at the head of this article the "Distaflex Two" is shown in the special cabinet which was mentioned in the list of components in last month's issue.

Valves

As was mentioned in the previous article on the "Distaflex Two," the choice of suitable valves for use in this receiver is of importance. Valves which are capable of handling considerable volume are especially necessary when the set is used for reception from the local station. For the best results under these conditions it is essential to use a low-impedance type of power valve.

Remedy for Blasting

Such valves need not be used if no very great volume is to be handled when the set is being used for the reception of stations at a greater distance. The tendency to blasting which may be observed when the valves used are called upon to handle too great a volume may be dealt with in many cases by correct adjustment of the grid bias values, imple grid bias being generally the rule.

A list of valves which may be used in the "Distaflex Two" is given in the accompanying table.

Grid Bias

The high-tension voltage should be about 100 to 120 volts if full volume

is required; and with this voltage from 6 to 9 volts grid bias will be required. This should, however, be adjusted to suit the valves actually in use.

Neutralising

The first operation to perform on bringing the set into use is to adjust

VALVES

The following types of valves, among others, will be found suitable for use in the "Distaflex Two," the same type of valve being used in each valve holder:—

MANUFACTURER.	VALVE TYPE.
Benjamin	S.P. 55/R. (Red Spot).
B.T.H.	B. 4.
Burndep't	LL. 525. L. 525. L. 550. L. 240.
Cleartron	C.T. 15+ C.T. 25+
Cosmos (Metro-Vick) ..	S.P. 18/R. S.P. 55/R.
Cossor	Stentor Two. P. 3.
Ediswan	P.V. 5 D.E. P.V. 2.
Marconi or Osram ..	D.E. 5. D.E. 5 A. D.E. 8 L.F.
Mullard	P.M. 4. P.M. 6. D.F.A. 0. D.F.A. 1.

the neutralising condenser controlling the first valve. This condenser is the one mounted on the baseboard in the set as described. To do this the two neutralising condensers, on the baseboard and panel, are set about one-third of the way round, and the local station is tuned in with the telephones

in No. 1 jack. If there is any sign of oscillation, the neutralising condensers should be adjusted till it ceases.

Non-Radiating Reaction

The dials should then be rotated together from top to bottom of their scales, the aerial condenser being swung backwards and forwards over a few degrees on either side of the tuning point as the other two dials are moved forward. If the set oscillates at any point on the scale, this may be checked by adjustment of the neutralising condensers. When this operation is completed, the baseboard neutralising condenser should be left alone. The neutralising condenser on the panel may then be used as a reaction control, without fear of causing re-radiation of energy and annoyance to the neighbours.

Loud-Speaker Connections

It should be noted that the loud-speaker may be connected either to the terminals at the back of the set or, if preferred, by means of a plug into No. 2 jack. The insertion of a plug into No. 1 jack cuts out the low-frequency amplifying stages, so that this position is most suitable for the insertion of telephones in circuit when tuning-in distant stations.

Transformers

The three transformers required for the set are all alike, being of the split-secondary type. Before these are inserted in their places on the set, the pins should be opened out slightly with a penknife. This will obviate the possibility of poor contacts in any of the sockets on the coil bases, which might well be detrimental to the operation of the set.

Operating the "Distaflex Two"—continued

Crystal Detector


The best setting for the crystal detector should be ascertained when the set is tested on the local station.

batteries will put matters right in this respect.

Reaction

The reaction control, provided by

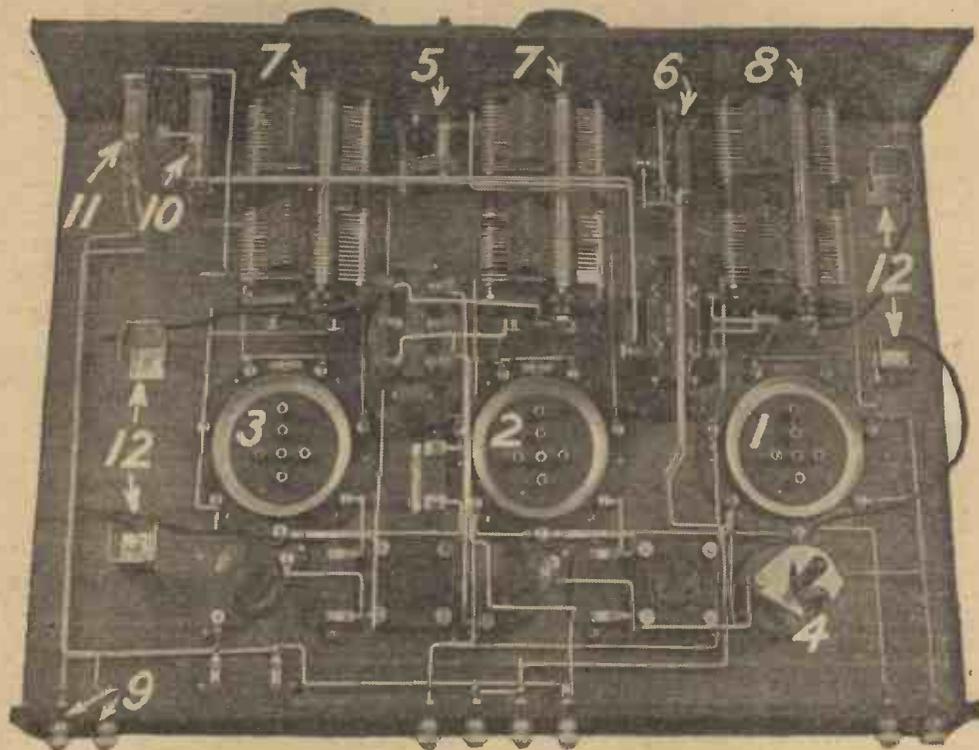wave stations received with the "Distaflex Two." Since, however, these coils are not yet generally available, these readings will be given in a future issue of this journal.



SPECIAL POINTS TO NOTE

- | | |
|--|---|
| <p>1, 2 & 3.—Insert here split-secondary transformers for the required wavelength range.</p> <p>4.—This neutralising condenser is adjusted to prevent oscillation and then left set.</p> <p>5.—This neutralising condenser provides a non-radiating reaction control.</p> <p>6.—One filament rheostat controls both valves.</p> <p>7.—The dials of these two tuning condensers read alike.</p> | <p>8.—The dial of this tuning condenser reads within a few degrees of the other two.</p> <p>9.—Connect the loud-speaker here for full volume.</p> <p>10.—Insert telephone plug in this jack. This uses two stages of H.F. amplification and the crystal detector.</p> <p>11.—Insert loud-speaker plug in this jack (alternative to terminals 9). This uses two stages of H.F. amplification, crystal detector, and two stages of L.F. amplification.</p> <p>12.—Insert grid bias batteries here, and use ample grid bias to prevent blasting and rectification by the valves.</p> |
|--|---|

When once this has been done, the operator will be well advised not to interfere with this setting while searching for more distant stations, since alterations may affect slightly the dial reading of the third tuning condenser. This dial reading may also be upset slightly, and need re-adjustment on removing the telephones from No. 1 jack and bringing the loud-speaker into circuit.

If it is observed that the tuning of the circuits is somewhat flat, it will probably be found that the grid bias values are incorrect, and that the selection of other tappings on the

means of the neutralising condenser on the panel, will be found useful in locating the settings for distant stations. It should, however, be handled with care and not advanced too far, or the set may show a tendency to howl. This control should be used very sparingly for increasing the volume of initially loud signals, owing to the distortion which will be introduced by the application of excessive reaction.

Long Wave Coils

It was the intention to give this month the dial readings for the long-


DON'T MISS IT!

The issue of "WIRELESS," the One-Word Weekly, dated October 23rd, will be a FREE GIFT issue.

PRICE 2d.

ON SALE OCTOBER 19th.

whichever way you look at it—

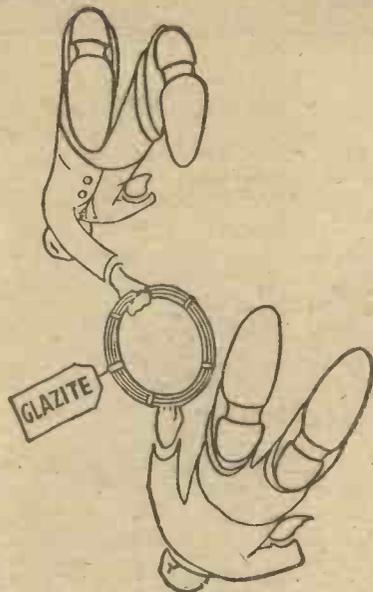

you can't beat
Glazite for wiring!

If you want ease of wiring—GLAZITE. If you want neatness—GLAZITE. If you want economy—GLAZITE. If you want perfect insulation—GLAZITE.

In every way GLAZITE is the best way to wire a set! Flameproof and damp-proof, it will not deteriorate in use. Try GLAZITE next time.

GLAZITE
BRITISH MADE REGD.

COLOURED CONNECTING WIRE
[RED · YELLOW · BLUE · BLACK · WHITE and GREEN]

Obtainable in ten-foot coils, price 1s. 2d. per coil. Or in two-foot lengths—four assorted colours—1s. per packet. Write for interesting descriptive leaflet to

The
LONDON ELECTRIC WIRE COMPANY & SMITHS, LTD.
Playhouse Yard, Golden Lane, London, E.C.1

Makers of Electric Wire

for over  40 years

JUDD

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.



WESTON
Pin Jack
VOLT METER

plugged into
High Range
Stand.

Range 6v. and
range 200v.

(750 and 25,000
ohms resistance.)

£2 10s. 0d.

WESTON Instruments
for Economy and Efficiency.

Open circuit tests are useless. With the aid of this WESTON Voltmeter you can test under normal working conditions. Thus you can protect your valves and secure the best results of which your set is capable, by correct adjustment of Filament, Plate and Grid Voltage.

WESTON ELECTRICAL INSTRUMENT Co., Ltd.,
15, Great Saffron Hill, London E.C.1.

Telephone: Holborn 2029; Telegrams: "Pitoted, Smith, London."

65

SUM IT UP

for yourself. The British Made Lustralux '06 H.F. Det. or L.F. Valves cost 9/- each. The Lustralux '34 Power Valve costs 11/-. You can get an ideal three-valve combination for 29/- and no valve calls for more than 2 volt!


Quite apart from the low initial cost, think of the current economy of arranging your accumulator cells in parallel—and the three valves together only call for '46 amps.

Quality and reproduction—well, just try! Compare the Lustralux with any valve you like quite irrespective of cost. Your own good opinion will be confirmed by your most musically inclined friend.

ASK YOUR DEALER.

Send for Catalogue G.
Lustralux Valves obtainable from Lewis's Ltd., Liverpool and Manchester, and LUSTROLUX Ltd., West Bollington, near MACCLESFIELD.

LUSTROLUX

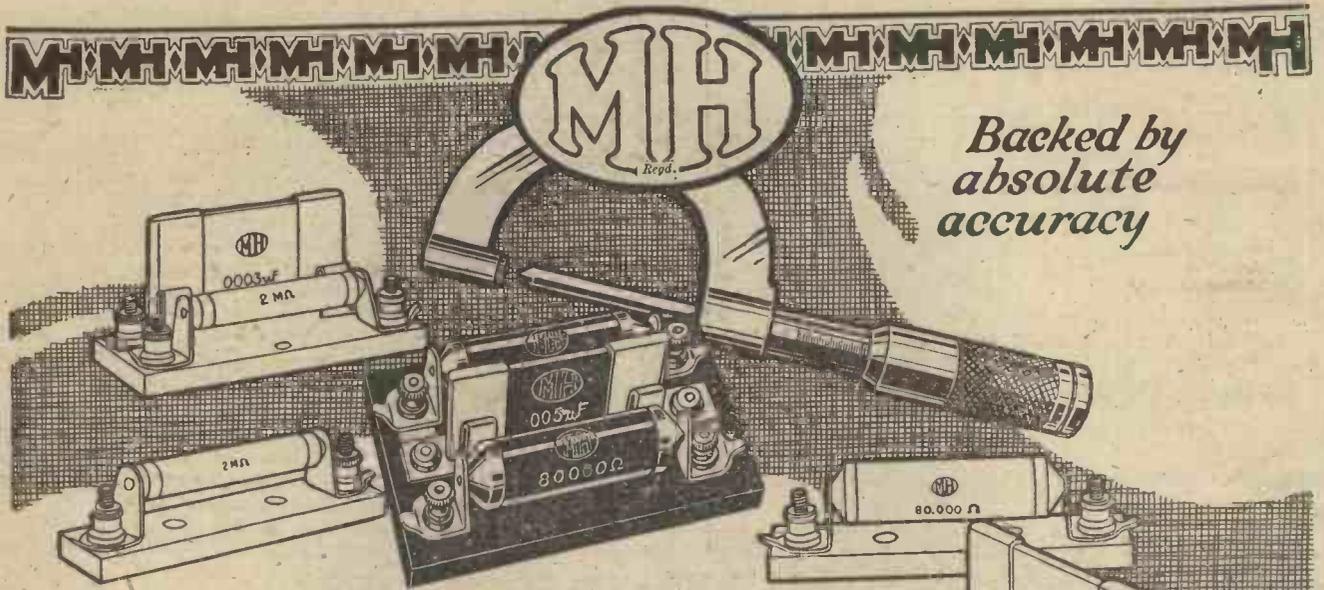

Backed by absolute accuracy

FAITHFUL TONE QUALITY

Radio Experts all agree that the Resistance Coupled Amplifier gives the most faithful reproduction of all the tones received from the Broadcast Station. In an Amplifier using the **MH** Resistance Coupling Unit, the higher or lower audible frequencies so essential for the perfect reproduction of all instruments are faithfully reproduced.

With the **MH** Resistance Coupling Unit a violin sounds like a violin, a flute like a flute, etc. The perfectly designed **MH** Resistances and Condensers forming the unit transfer the music from valve to valve with perfect fidelity. They do not age or deteriorate. Once they are in your set you can forget them.

As with the **MH** R.C. Unit, all **MH** Components are backed by the experience and resources of the **MH** experts, and are therefore absolutely reliable.

Demand of your dealer **MH** Components.

They're British.

MH GRID LEAKS.

Price (in Cartons).

All values (040) 2/6 each
(Supplied with two clips.)
Mounted on ebonite base, with terminals,
1/- extra.

MH RESISTANCE CAPACITY COUPLING.

Price (Complete as illustrated) (200) 12/6

MH MICA FIXED CONDENSERS.

(Two clips are supplied with each Condenser.)

0.0001 to 0.0005 μ F (030)	2/6 each
0.001 to 0.01 μ F (031)	3/- each
0.015 to 0.0 μ F (034)	4/- each

Mounted on ebonite base, with terminals, any value, 1/- extra.

MH GRID LEAK AND CONDENSER MOUNTED.

Price (in Cartons) (020) 5/- each
On base with terminals.

MH ANODE RESISTANCES.

Price (in Cartons).

40,000 to 100,000 ohms (041) 4/6 each
(New Type.) (Supplied with two clips.)
Mounted on ebonite base, with terminals,
1/- extra.

Prices (in Cartons), Unmounted.

NEW

MH

COMPONENTS OF EXTREME INTEREST

MH Unimic Coil.

Its special base mounting is electrically and mechanically perfect, and allows of variable coupling.

Price 5/-

Base 2/6 extra.

MH Dimic Coil. No. 1.

Taken at the Middle frequency it has a resistance of 5.25 ohms at a frequency corresponding to 40m., i.e., .026 ohms per μ H.

Price 10/-

Base 2/6 extra.

MH Balancing Condenser

The growing need for precise balancing encouraged us to produce a component which you will find essential.

Price 4/9

L.M. MICHAEL LTD

Manufacturers of Wireless and Scientific Apparatus
WEXHAM ROAD, SLOUGH, BUCKS.

Telephone:
Slough
441-442.

Telegrams:
Radiether,
Slough.



Pool's Advertising Service Co.

SEEN AT THE SHOW

An Impression of some of the Exhibits at the National Radio Exhibition.



A general view of the National Radio Exhibition in the New Hall at Olympia.

AN impression gathered at the National Radio Exhibition, held at Olympia from September 4 to 18, was that this year's exhibits have shown the development of wireless sets and accessories to be proceeding along the lines of improving the reception obtainable by the listener. Novelties

supply all over the country, there is no doubt that the prospect is attractive.

High Tension Units

Messrs. Burndopt were showing their "Ethopower" H.T. unit, an instrument employing a special rectifying valve for use on A.C. mains,


both models, the valves used being of the double-anode type.

A New Rectifier

The General Electric Co. produce a complete set of parts for the construction of an H.T. battery eliminator, which uses an Osram gas-discharge rectifier. An advantage of this type of rectifier is that it has no filament, so that it cannot be overrun.

High and Low Tension

The "Hiloten" battery eliminator is a product of the Dubilier Condenser Co., Ltd., which incorporates several interesting features. For the low-tension supply there are two accumulators, which are automatically charged alternately as they are discharged. A high-tension voltage of 200 volts for low-frequency amplifiers and a variable voltage with a maximum of 100 volts are also provided. The converter itself may be placed in any convenient position in the house,

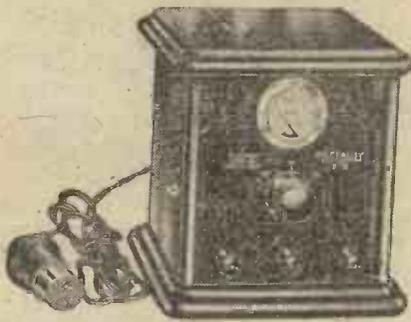


A battery charging unit shown by Rectalloy, Ltd.

and new lines which are now available to the public do not take the form of "freak" sets or components so much as solid improvements on the designs of the past.


Battery Eliminators

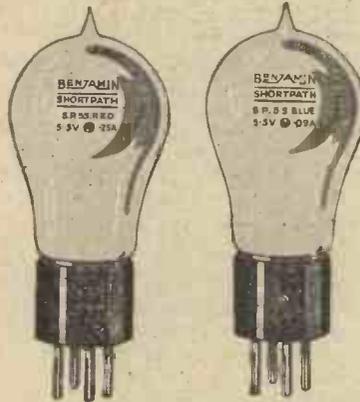The wireless needs of the home were, for example, well served by the numerous types of battery eliminators exhibited. It is prophesied in some



Two new Benjamin 6-volt valves, the S.P. 55/R and the S.P. 55/B.

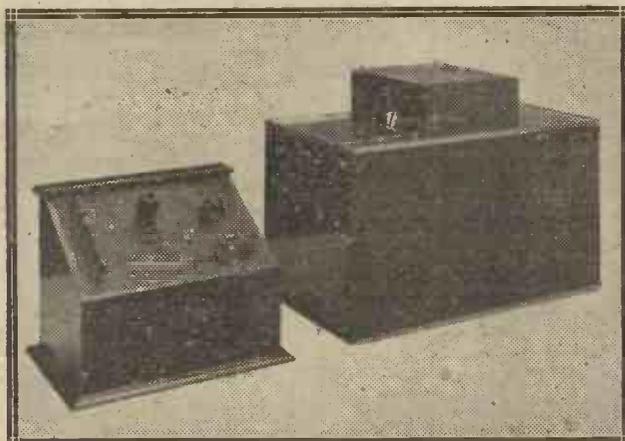and supplying to the set voltages of 40 to 60 and 120 to 160 volts, so that the needs of individual valves in the



Messrs. Dubilier's "Hiloten" battery eliminator is provided with a separate remote control unit.



The new disc loud-speaker shown by S. G. Brown, Ltd.

a control box for remote control being connected to the receiver.

Battery Chargers

With battery eliminators may be associated battery chargers of which a large variety were exhibited. A

quarters that within a few years time hardly any listener, except perhaps those in the remote country districts, will still continue to use batteries. Dependent as the alternative system is on the universal adoption of electric

set may be served. Two new converters for high-tension supply were exhibited by Messrs. Igranic Electric Co., Ltd., suitable for providing high-tension for the set from A.C. mains. Full-wave rectification is furnished on

Seen at the Show—continued.

low-tension pattern shown by Messrs. Rectalloy is suitable for 2-, 4- or 6-volt accumulators and charges at .2 or .4 amperes. Chemical full-wave rectification is employed, and simple operation is a feature of the instrument.

Messrs. Burndept's "Balkite Trickle Charger," for use with A.C. mains, contains a special rectifying cell, and delivers a current of about half an ampere to the accumulator. The latter may thus be switched over from the set to the charger when not in use,




The "Ethopower" A.C. mains battery eliminator for high-tension supply.

ensuring a constant low-tension supply.

Several "Tungar" charges were shown by the British Thomson-Houston Co., Ltd., these including an instrument supplying 12 ampères at 75 volts and a smaller model to give from .1 to 2 amperes at from 7.5 to 100 volts. These instruments are for use on A.C. mains and give a D.C. output.

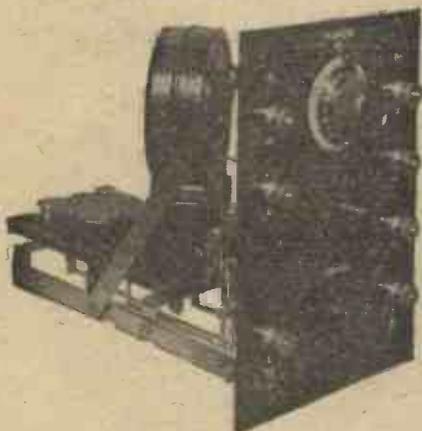Compact unit for obtaining high-tension from D.C. mains is the



A superheterodyne attachment produced by Messrs. Gambrell Bros., Ltd.

"Ekco" eliminator, produced by Messrs. E. K. Cole. Simplicity is a feature of this instrument, four terminals and a standard lamp plug being the only external fittings.

Loud-Speakers

Among the loud-speakers there were several new models to be seen, the aim

appearing in the main to be directed towards securing good reproduction.

The C.A.V. "Musicola" loud-speaker, of which a photograph was




The Darimont cell is somewhat of a novelty in primary cells.

published in last month's issue, is of the conical diaphragm type, mounted in a trunnion bearing, so that it is adjustable to any angle. Messrs. S. G. Brown, Ltd., have also turned their attention to the open-diaphragm type of loud-speaker, the diaphragm in this instance being enclosed in a metal screen, which is designed to protect the instrument from damage.

Messrs. B.S.A. Radio were showing three types of "Kone" loud-speaker, one of which, known as "Model C," is illustrated on these pages. On Messrs. Alfred Graham & Co.'s stand was a complete range of the Amplion loud-speakers, improvements in detail and finish being the most noticeable points.

Unusual Designs

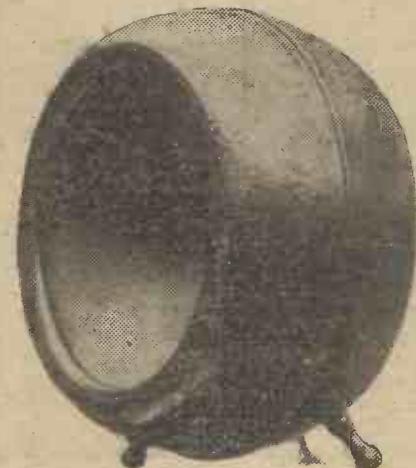Considerable claims are made for the Donotone instrument, which consists of a complete series of tuned reed mechanisms for the audible frequency range. Several firms have produced loud-speakers cleverly disguised and made to serve an additional purpose. Such are a loud-speaker with a clock




The new B.S.A. loud-speaker, Model C.

in the centre, shown by the Peto-Scott Co., Ltd., and the "Beco" rose-bowl instrument illustrated on these pages.

Valves

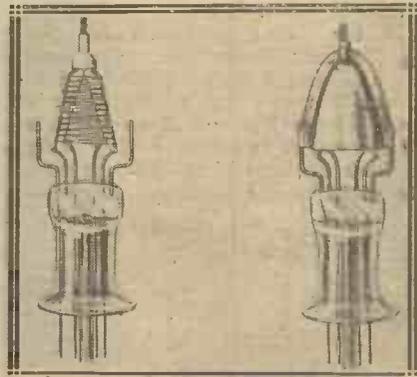Several interesting new types of valves were to be seen at the Exhibi-



Showing the disposition of the electrodes in the Cossor Point One valves,

tion, among which were the new Benjamin "Shortpath" valves. Six examples of these were shown, intended for operation from 2-volt or 6-volt accumulators, three in each category. The new Burndept valves include a "super power valve," the LL525, and the L240, a 2-volt power valve designed to operate with anode voltages up to 120 volts.

Three new Cleartron power valves are the C.T. 08+, the C.T. 15+ and the C.T. 25+. These are of the 3-volt, 2-volt and 5-6-volt types respectively. Some new 2-volt Ediswan valves have been introduced into the range of valves manufactured by this firm,



The appearance of the "Beco" rose-bowl loud-speaker gives little suggestion of its dual purpose.


these being general purpose, special detector, resistance-capacity amplification and power valves.

Variable Condensers

Low-loss construction in accordance with sound design is a feature of the variable condensers exhibited this

SEEN AT THE SHOW—continued

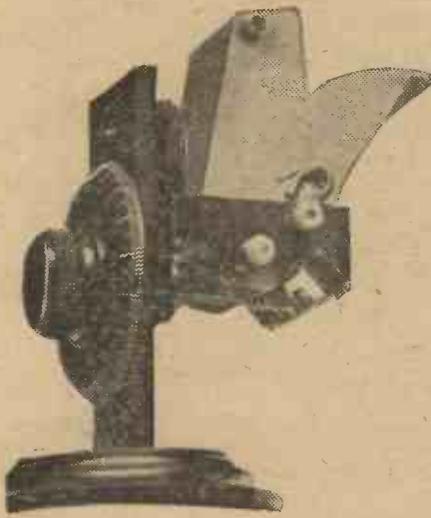year. Ball bearings are popular for providing a smooth spindle movement, and many instruments are fitted with slow-motion devices, either integral




The Bretwood variable condenser has an unusual form of movement.

with the condenser construction or separately attached in the form of vernier dials.

Special Condensers

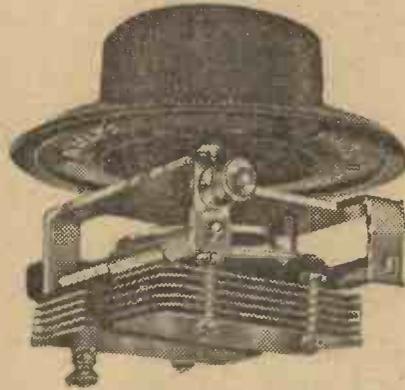Several manufacturers have now produced "gang" condensers, designed




Messrs. Ripaults' lateral action variable condenser is an interesting departure from the conventional.

for use in the Radio Press Star Set, the Elstree "Solodyne," a receiver which attracted a great deal of attention at the show. Since the moving vanes of each condenser must be capable of individual adjustment, the construction of these special instruments calls for a high standard of design and execution.

GRAHAM FARISH

GUARANTEED

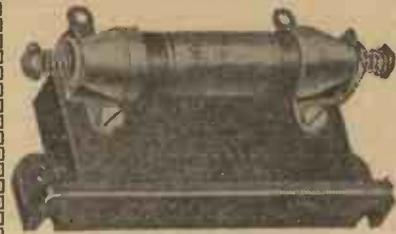

BAKELITE CONDENSERS & LEAKS

- can be attached in series or parallel.
- can be mounted upright or flat.
- are issued with a written guarantee.
- are cased in solid Bakelite.

PRICES.

.0003 mfd. Condenser and 2 megohm Leak	2/- each.
Any size Condenser up to .002 mfd. and any size Leak	2/3 "
Any size Condenser over .002 mfd. and any size Leak	2/9 "
Condensers only .0001—.002	1/- "
Grid Leaks, " .003—.01	1/6 "
Condensers, any size	1/3 "

Sent post free if you cannot obtain locally.

DEALERS WRITE FOR TERMS.

The Graham Farish Mfg. Co.,
17, Masons Hill, Bromley, Kent.

BETTER RADIO PARTS



MAGNUM VOLUME CONTROL UNIT

No. 1062.

A new Magnum Product for controlling the volume from Loud Speaker without sacrifice of quality. Wire wound. Non-inductive. One-hole fitting Price 15s.


THE SPANSPACE 3

	£	s.	d.
1 Mahogany Cabinet, with baseboard	1	5	6
1 Ebonite Panel, 16 x 8 x 1/4	..	10	6
2 J. B. Variable Geared Condensers, .0005	..	1	10 0
1 J. B. Variable Geared Condenser, .0003	..	13	6
3 Benjamin Valve Holders	..	8	3
1 Brandes L.F. Transformer, 3 to 1	..	17	6
1 Dubilier 100,000 ohm Resistance and Base	..	5	6
2 Collinson Coil Formers and Bases	..	10	0
1 Peto Scott Balancing Condenser	..	7	6
2 Magnum Angle Brackets	..	2	6
1 Magnum Baseboard Neutralising Condenser	..	5	0
1 Yaxley Switch	..	3	6
1 Dubilier Condenser, Type 610	..	4	0
1 Dubilier Condenser, .0003 and Leak, 2 meg.	..	5	0
3 Resistors	..	7	6
1 Magnum No. 1 Terminal Panel	..	4	6
1 Magnum No. 2 Terminal Panel	..	2	6
1 H.F. Choke Varley	..	9	6
Connecting Wire	..	2	9
	£8	15	0

Send stamp for latest Lists dealing with Radio Press constructional sets, and new components.

NOTE.—Where a complete set of Components, together with a drilled panel, is purchased, Royalties at the rate of 12s. 6d. per valve holder are payable.

MAGNUM SCREENED COILS

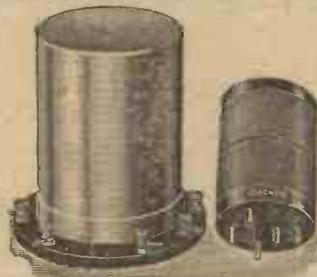

No. 1058.

NEW STANDARD COILS AND PRICES. MAGNUM Screening Box, complete with 6-Pin base (Standard spacing and cross formation) 15s.

Split Primaries.		s.	d.
Aerial Coil	.. 250/550	6	0
H.F. Transformer	.. 250/550	10	0
Aerial Coil	.. 1000/2000	6	0
H.F. Transformer	.. 1000/2000	10	0
Split Secondaries.		s.	d.
H.F. Transformer	.. 250/550	10	0
H.F. Transformer	.. 1000/2000	14	0
Reinartz Coil	.. 250/550	10	0
Reinartz Coil	.. 1000/2000	14	0

Size of Screening Box:		s.	d.
Overall height, 4 1/2 in.; Dia. of base, 4 1/2 in.		2	6
Set of 3 Screened Coils, as used in Distaflex 2	..	3	15 0
Set of 3 Screened Coils, as used in Solodyne	..	3	11 0
Set of 3 Screened Coils, as used in Magic 5	..	3	11 0

BURNE-JONES & Co., LTD.,

Manufacturing Radio Engineers,
Magnum House,
296, BOROUGH HIGH ST.,
LONDON, S.E.1.

Telephone: Hop 6237.
Telegrams: "Burjomag, Sedist, London."
Cables: "Burjomag, London."

MAGNUM RESISTORS

are suitable for all Modern Sets, including:—The Night Hawk; The Distaflex Two: The Elstree Six; The Elstree Solodyne, etc., etc.



Resistor on base	Price:	s.	d.
Resistor only	2	6
Shorting Plug	1	9
	Size:	s.	d.

Overall size of base, 2 1/2 in. by 1/2 in. Overall height, 1 1/2 in.

THE INVALIDS' THREE

	£	s.	d.
1 Mahogany Cabinet, with Baseboard and Panel	..	2	15 0
3 Panels, 16 x 4, 6 x 3, 9 x 3, with 9 terminals	..	11	4
2 Cydon Variable Condensers, .0005	..	1	15 0
2 Panel Mounting Neutralising Condensers	..	10	0
3 Etherplus Valve Holders	..	7	6
2 Magnum Coil Sockets	..	3	6
1 Burndept Dual Rheostat	..	6	0
1 Dubilier Condenser .0003 and Leak, 2 meg.	..	5	0
1 Dubilier Condenser, .0001	..	2	6
1 Flammé Switching Jack	..	2	6
1 Efesca Push-Pull C.O. Switch	..	4	0
2 Gambrell Centre Tap Coils, C. & E.	..	14	6
2 Cosmos Resistance Coupling Units	..	8	6
1 T.C.C. Condenser, 2 mfd.	..	4	8
Glazite and Flex	..	3	0
	£9	13	0

We specialise in and can supply Components for all Sets described in this and all Radio Press publications, including:—

- THE ELSTREE SIX.
- THE ELSTREE SOLODYNE.
- THE MEWFLEX.
- THE NIGHT HAWK.
- THE DISTAFLEX TWO, Etc., etc.

Lists on receipt of stamp.





THE CHOICE of EXPERTS

—and all discriminating amateurs

LOOK through your copies of the leading radio journals; notice how often IGRANIC Low Loss Variable Condensers are used.


The excellent reception enjoyed by so many amateur constructors is due to their following the example of experts and making Igranitic Condensers THEIR choice.

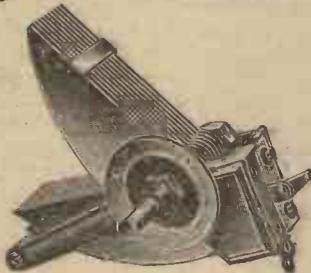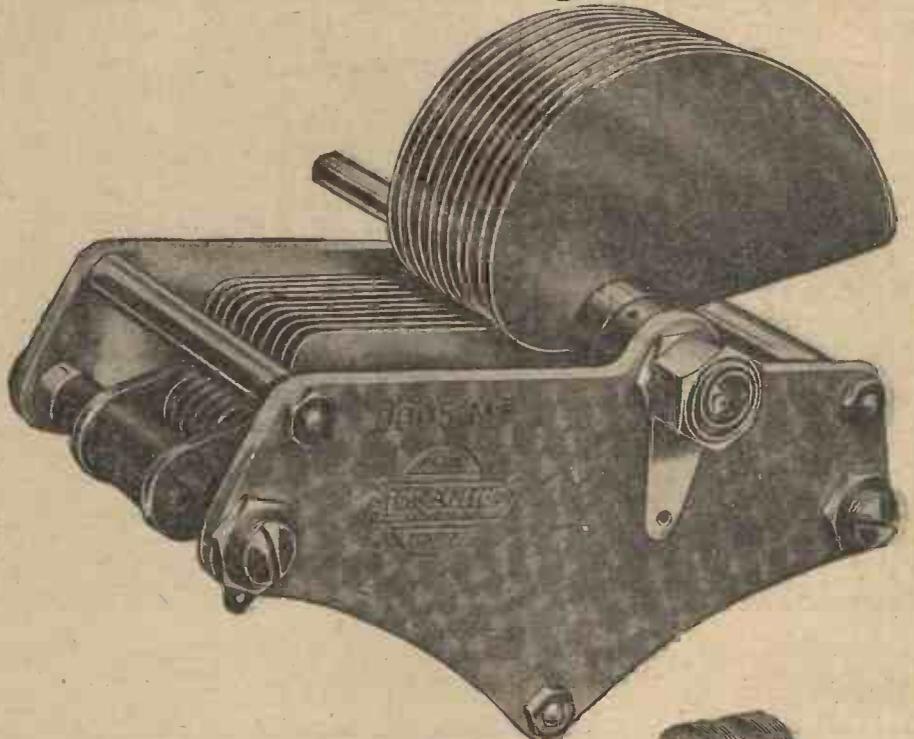BUILD IGRANIC CONDENSERS into your RECEIVERS!



IGRANIC PACENT S.L.F. CON ENSER. For accurate straight line frequency tuning.
PRICES: .00035 14/6
 .0005 18/6

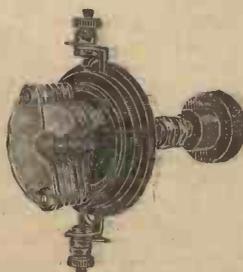TRIPLE GANG PATTERN, made up of three .0005 mfd. condensers. **PRICE £3:10s.**



IGRANIC MICRO CONDENSER. Particularly suitable for neutrodyning.


IGRANIC VERNIER BALANCING CONDENSER: For balancing two H.F. stages.
PRICE .. 5/6 each.

Features which make IGRANIC LOW LOSS SQUARE LAW CONDENSERS DISTINCTIVE

Extremely low losses; accurate square law tuning; flexible connection to moving plates; negligible minimum capacity; ball bearings giving extremely smooth turning movement; strong metal frame and stout brass plates; highest quality scientific instrument finish throughout.

PRICES:	.00015 mfd.	17/-
	.0003 "	18/6
	.0005 "	21/6
	.001 "	25/-

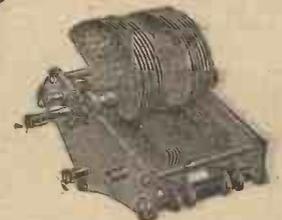Send for Catalogue No. J140 and full range of Igranitic publications.




IGRANIC DUAL CONDENSER: Of similar design and possessing all the unique features of the single pattern.
PRICES: .0003 (Dual) .. 22/6
 .0005 (Dual) .. 27/-



IGRANIC BASEBOARD BRACKET: Designed for baseboard mounting of Igranitic Micro and Vernier Balancing Condensers.
PRICE: 6d.

IGRANIC ELECTRIC CO LTD

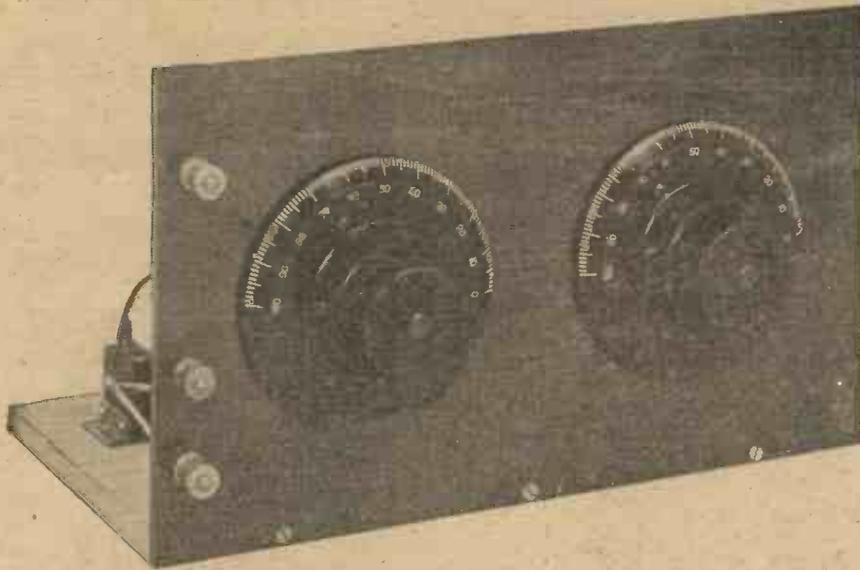149, Queen Victoria St., LONDON: Works: BEDFORD.



A SELECTIVE ONE-COIL SINGLE-VALVE SET

By D. J. S. HARTT, B.Sc.

Describing an interesting set, involving little constructional work, which gives good selectivity and the full benefits of reaction amplification with a single coil.

I CONSTRUCTED recently a single-valve receiver with the idea of obtaining a high degree of selectivity without too many controls, and I finally adopted a modification of the Reinartz circuit, using a "tight-coupled" aerial, capacity-controlled reaction, and tapped the valve only across a portion of the secondary coil. This scheme proved very effective, but had the disadvantage that it necessitated the use of three coils, one being tapped for every range. Consequently, to be able to cover the whole broadcast range satisfactorily, including the longer waves, about nine coils were required.

Utmost Simplification

It occurred to me that one might achieve the same object in a much simpler manner by the use of only one or two tapped coils for the lower broadcast range, and one for 5XX, thereby greatly reducing the cost of the complete set. This I found possible, and the circuit shown in Fig. 2 is the result, and is used in the receiver shown in the accompanying photographs.

BUILD THIS SET WITH

- One panel, 12 in. by 7 in. by 1/4 in. (American Hard Rubber Co.).
 - One suitable cabinet, with baseboard 6 3/8 in. deep.
 - One .0005 and one .0003 low loss variable condenser, with "Utility" vernier dials (Wilkins & Wright, Ltd.).
 - One Amperite, to suit the valve used (Rothermel Radio Corporation).
 - One baseboard coil socket.
 - One valve-holder (Burne-Jones & Co., Ltd.).
 - One H.F. choke.
 - One .0003 fixed condenser and 2-megohm $\lambda. k.$ (Lisser, Ltd.).
 - Two .0001 clip-in condensers, one with baseboard mounting and one with clips only.
 - Three terminals.
 - One ebonite strip, 2 in. by 2 in., with two terminals.
 - One centre-tapped No. 60 coil. Also centre-tapped No. 250 coil for Daventry, if required.
 - Glazite and about 3 yds. of rubber-covered flex. Radio Press panel transfers.
- Approximate cost, £5.

by the condenser C_1 . The circuit as shown gives results practically identical with those obtained with the Fig. 1 arrangement.

Reaction Control

Initially the circuit was tried without the fixed condensers C_1 and C_2 , but some little difficulty was experienced in obtaining the desired reaction control. It was found that without these condensers reaction was possible on the lower portion of the broadcast band, and that with normal high-tension voltage oscillation could not be controlled on the longer wavelengths.

Remedies Adopted

To reduce the reaction effect on the long wavelengths the expedient was tried of providing an alternative by-pass for the H.F. component from anode to earth by the connection of a clip-in fixed condenser between these points. Several values were tried, and it was found that a .0001 condenser made it possible to obtain the desired smooth control.


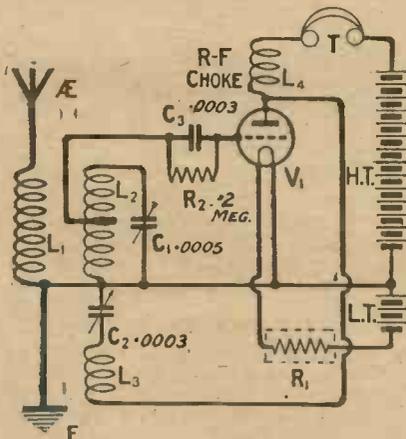


Fig. 1 (left).—This circuit was tried by the author, but was troublesome, since three coils were needed.

Fig. 2 (right).—The circuit of the set described, which will be seen to require one centre-tapped coil only.

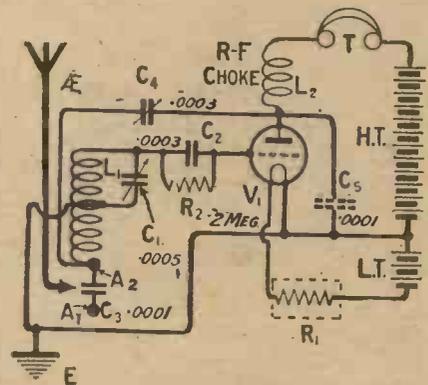

The more complicated circuit from which this was derived is given in Fig. 1.

Reference to Fig. 2 will show that

the valve is tapped across half of the coil L_1 only, that the other half is used as a combined aerial and reaction coil, and that half of the coil is tuned

In order to make reaction possible over the whole of the broadcast range, a small fixed condenser C_5 was connected as shown, so that the aerial

A Selective One-Coil Single-Valve Set—continued

could be connected to either A₂ or A₁. With the aerial taken to the latter terminal satisfactory reaction control was possible over the whole of the lower broadcast band. The clip-in by-pass condenser C₂ is, of course, removed when operating on these shorter wavelengths. Thus, although the saving in coils necessitates the use of two extra fixed condensers, the cost of the latter is usually less than the price of a single coil.

Coils Tried

In making the tests on reaction control both Lissen and Gambrell centretapped coils were used, with the same results in each case, so that the phenomena observed were not characteristic of any particular make of coil, but appeared to be rather inherent in the circuit.

The remainder of the circuit is probably quite clear; reaction is, of course, controlled by variation of the capacity of the condenser C₁, once the initial changes described above have been made, according to the wavelength range in use.

The usual variable filament resistance has been dispensed with, and one of the constant-current type fixed resistors or barreters substituted. Consequently only two dials appear on the panel, and a simple and attractive appearance is the result.

good quality. If this is your first set, however, you are advised to adhere closely to the list given.


Constructing the Set

Even an absolute novice will find very little difficulty in constructing a

properly when putting on the vernier dials, and secure these to the spindles with the set screws. Next place the baseboard in the cabinet, put the panel in position and secure it to the baseboard with three brass wood screws through countersunk holes, which

✱ ✱ ✱

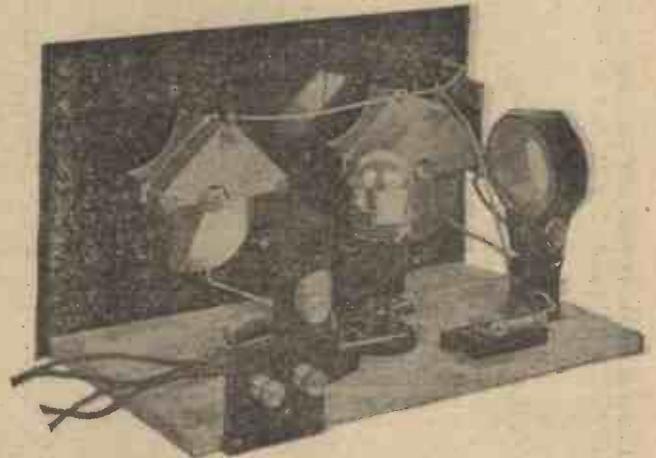Ample space is allowed for the mounting of the components, the two terminals on the baseboard being for the telephones.



✱ ✱ ✱

receiver such as this. There are only eight holes to be drilled in the panel, two of these, namely, those for the variable condensers, being 9/16th in. in diameter. If you do not happen to possess a drill of this size drill the

should be drilled in the proper positions when the other panel drilling is done.

Next mount the baseboard components in the positions indicated on the wiring diagram and photographs, and

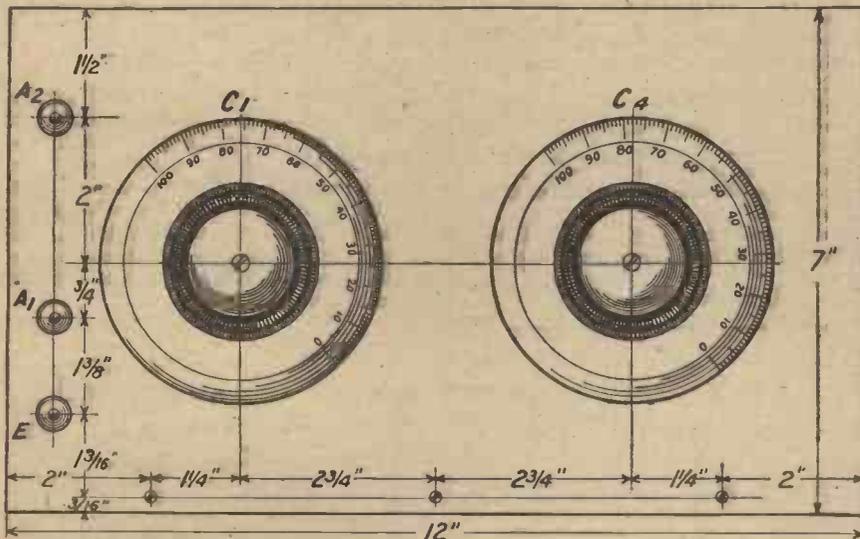


Fig. 3.—There is very little drilling to be carried out on the front panel. Blueprint No. 1667A.

For the sake of simplicity, battery terminals have been omitted, and flex leads about 2 ft. long are connected to the appropriate points.

Components

The complete list of components required to build this set is given in the accompanying table, with the usual reservation as to substituting those of other makes that these should be of

usual 3/8-in. hole and carefully enlarge it with the tang of a file or with a small penknife blade.

The condensers are mounted on the panel in the usual way, but do not forget to place the stop in position on the threaded boss before putting on the securing nut.

Vernier Dials

Make sure that the stops engage

WIRING IN WORDS

All directions are given as viewing the set from the back of the panel.

Join top aerial terminal to fixed vanes of variable condensers C₁ and C₄, and also to one side of L1 coil socket.

Join earth terminal to moving vanes of variable condenser C₁, also to one side of fixed condenser C₅, and to one filament contact of valve holder.

Join remaining side of L1 coil socket to one side of fixed condenser C₂ and leak R₂.

Join remaining side of C₂ and R₂ to grid contact of valve holder.

Join remaining filament contact of valve holder to one side of resistor R₁.

Join anode contact of valve holder to one side of R.F. choke coil, thence to remaining side of fixed condenser C₅ and to moving vanes of variable condenser C₄.

Join remaining side of R.F. choke coil to one telephone terminal.

Join flex leads to the following points:—

One to the remaining telephone terminal, for connection to H.T. +.

One to the remaining side of resistor R₁, for connection to L.T. —

Two to the earthed filament contact of the valve holder, for connection to L.T. + and H.T. —

One to the earthed end of fixed condenser C₅, for connection to the centre tap of coil L1.

you are then ready to commence the wiring.

Preferably solder all connections and give each joint a sharp tug to make sure it is sound. Finally solder the flex connections to the correct points, not forgetting the connection from earth to the centre-tapping on the coil.

Testing

Connect up the aerial, earth, telephones and L.T. battery, insert the

The Duvarileak



**The Variable
Grid Leak
that remains
variable**

No Dubilier product is placed on the market until we can be absolutely certain of its giving perfectly satisfactory results in use.

The Duvarileak has been in the experimental stage for three years.

The final result is that this Grid Leak will show a smooth and uniform variation of resistance from zero to five million ohms. More important still, by successfully discovering a resistance element of extremely hard surface and by arranging a ball-bearing contact (see inset) we have assured that the wear in operation will be negligible.

This means that the Duvarileak will, throughout its life, give a *constant resistance value for any given setting of the dial.*

Like all Dubilier products the Duvarileak can be relied upon to give the utmost efficiency in service—it is, in fact, the perfect variable Grid Leak at last.


As seen in the illustration it has one-hole fixing and a dial scale by which the resistance may be set.

The Duvoleon for Loud Speaker Volume control is the same in appearance and price as the Duvarileak, and is suitable for use with any Loud Speaker.

Price 7/6 of all Dealers.



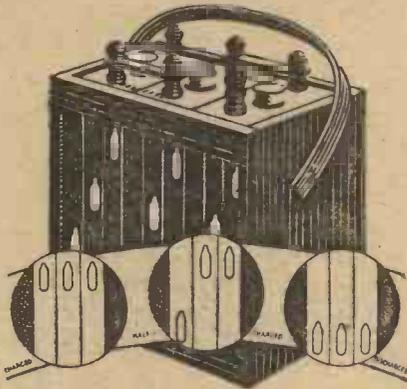ADVERTISEMENT OF THE DUBILIER CONDENSER CO. (1926), LTD., DUCON WORKS, VICTORIA ROAD, N. ACTON W.3. TELEPHONE: CHISWICK 2241-2-3. E.P.S. 223



BATH-WATER BLUES

Cheery, isn't it, when the last of the juice in the accumulator trickles gurgling away like water down the bath plug, and the loud-speaker bows its head in heart-broken silence?


Light your valves from a P. & R. Gravity Float Accumulator, and you won't be jammed that way any more. The P. & R. Gravity Float never gets run-down without telling you. Its tell-tale floats say whether its full, half-charged or nearly discharged.

Besides not being dumb, the P. & R. is a good accumulator. The capacity stated is its *capacity*: not a hypothetical and oh-so-hopeful "intermittent" rating: but real, honest-to-goodness valve-burning capacity. Extra plate area and solidity of building make it a long-life worker, too.

We should like to explain technically to you. Send a postcard for explanatory booklet to Peto & Radford, 50, Grosvenor Gardens, S.W.1.

P AND R
PETO & RADFORD
ACCUMULATORS
The beginning and the end in
POWER

D 8

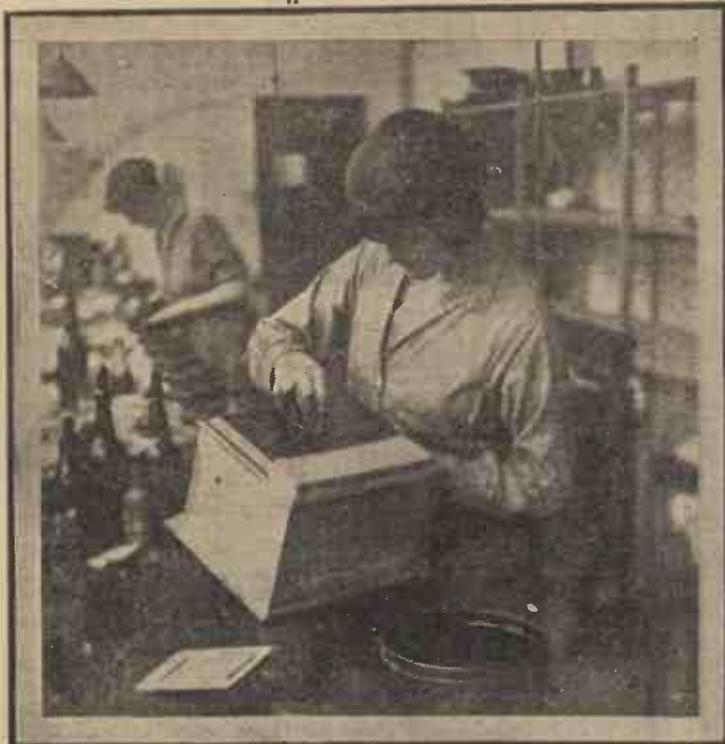

ART and Science go hand in hand in the Brown Cabinet Loud Speaker. Beautifully finished in rich Mahogany or Oak, it will harmonise with the setting of any room; while in purity of tone and adequacy of volume it stands alone among Loud Speakers of this type. In resistances of 2,000 or 4,000 ohms. £6.6.0

Conscientiously made—for you

The careful, conscientious workmanship—the almost loving care with which Brown workers tend the instruments they make is almost akin to the pride with which the Craftsmen of old fashioned their work. This pride of work is distinctly reflected in the finished product—it will be obvious to you the moment you see a Brown Loud Speaker or Headphone.

Each Brown Instrument is conscientiously made; we, its sponsors, know that in it we have designed

a Loud Speaker which will give the most faithful rendering of the Broadcast it is possible to imagine; one that, in purity of tone and adequacy of volume, sets a standard in reproduction unequalled throughout the World. Because we want to pass this on to you, we are determined that not by the slightest deviation from the high standard of workmanship, nor by a moment's relaxing in the discernment with which only the finest quality materials are chosen, shall the astounding fidelity of Brown reproduction be prejudiced.



Q

In addition to the Cabinet, there are eight other Brown Loud Speakers—a type for everyone from 30/- to £15 15 0.

Brown

S. G. BROWN, LTD., Western Avenue, North Acton, W.3

Retail Showrooms: 19, Mortimer Street, W.1; 15, Moorfields, Liverpool; 67, High Street, Southampton.
Wholesale Depots:—2, Lansdown Place West, Bath; Cross House, Westgate Road, Newcastle; 120, Wellington St., Glasgow; 5-7, Godwin St., Bradford; Howard S. Cooke & Co., 59, Caroline St., Birmingham. N. Ireland: Robert Garmany, Union Chambers, 1, Union St., Belfast.

Gilbert Ad. 5805.

A Selective One-Coil Single-Valve Set—continued

valve, and ascertain that the filament circuit is correctly wired by the fact that the valve lights. Next connect the H.T. battery, using, say, 40 to 60 volts, and finally see that you can

ing condenser adjustments fairly sharp, but when the condenser is correctly adjusted the local station should be audible at good strength, and the application of reaction, by increasing

until you have acquired a certain amount of familiarity with the operation of the set.

Results

On test at 10 miles S.W. of London

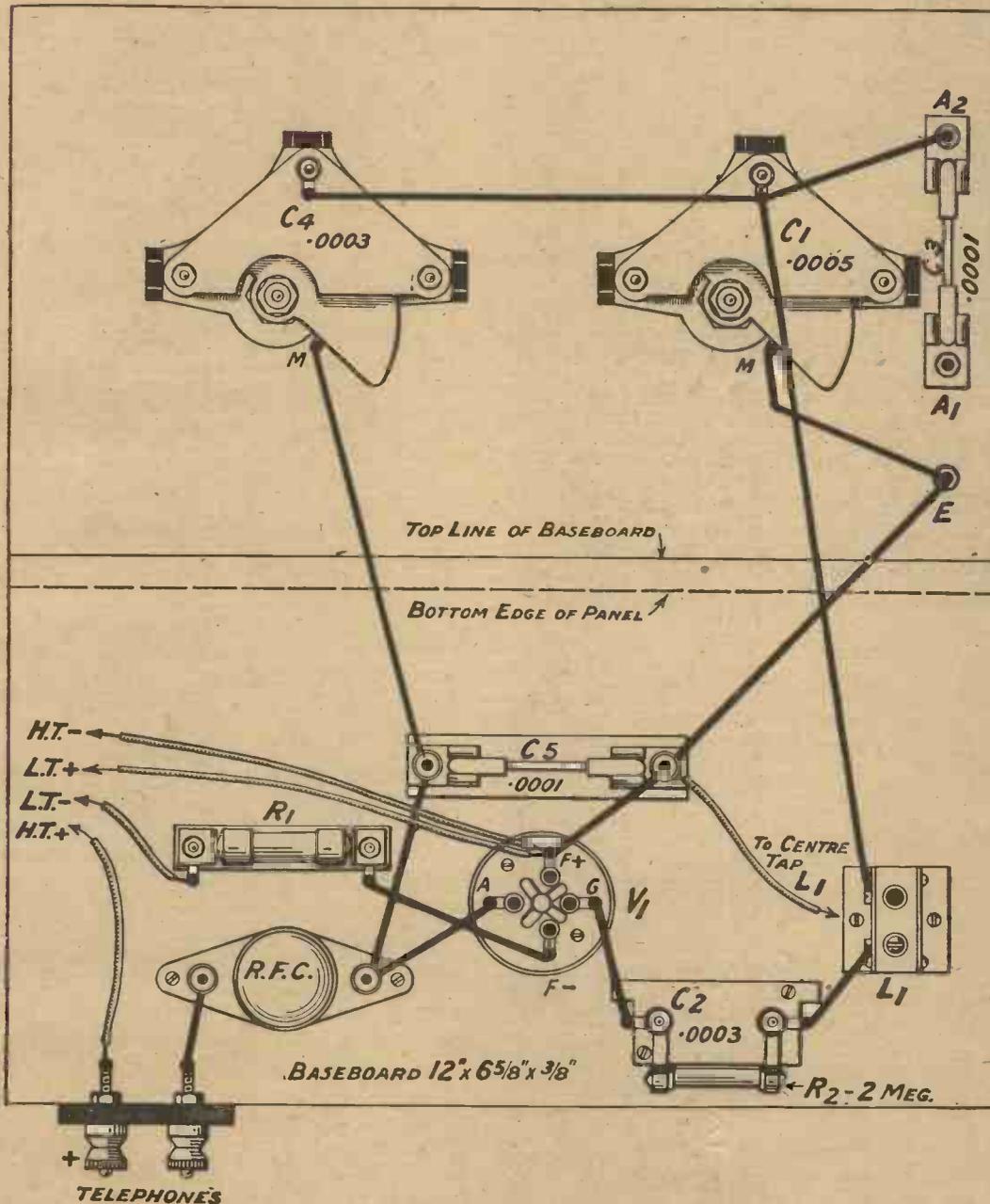


Fig. 4.—The fixed condenser, C5, is removed from its clips when working on the shorter wavelengths. Flexible leads are fitted for connection to the batteries. Blueprint No. 1067B may also be obtained.

obtain reaction smoothly over the whole of the tuning range, using both lower broadcast range and longer wave coils, and making the changes referred to previously.

Searching

If everything is satisfactory you are now in a position to search for stations. Set the reaction condenser on the right at zero, and tune in the local station. You will find the tun-

the capacity of the right-hand condenser, should give you a very useful increase in signal strength.

Searching for the more distant stations is done by slowly rotating the left-hand dial and just keeping the circuit near to the point of oscillation by careful adjustment of the reaction condenser. The vernier dials greatly facilitate these operations, but you are advised when searching not to approach too close to oscillation point

on a good average aerial, 2LO and 5XX were both heard at very good strength, as was Radio Paris.

Union Radio, Madrid, three unidentified German stations, one other Spanish station, Radio Toulouse, Berne and San Sebastian were also heard at quite good telephone strength. The British stations received were Bournemouth (when 2LO was working), Newcastle, one relay station (faint but intelligible) and Birmingham.

£1,000
MUST BE
WON

12 FEET

2/-

POST FREE

Any length obtainable.

ON SALE
EVERYWHERE



SUPERIAL

SIMPLE-STRIP

NO
ENTRANCE
FEE

SHARPER TUNING.
MORE POWERFUL
SIGNALS.

Entirely
British Manufacture.

100% EFFICIENCY.

DELIGHTFUL TO USE.

"SIMPLE-STRIP" is made of the finest hard-drawn copper—heavily tinned—perforated to take 4B.A. connections, and will stay put without solder. No need for bits and pieces. One length of "Simple-Strip" will cover several connections. And between these connections it will turn and twist as you will.

The most complicated circuit can now be wired by any amateur without difficulty and without waste. Simple-Strip may be cut with an ordinary pair of scissors, bends and twists can be made with the fingers to any angle.

Simple-Strip must be included in the kit of every wireless enthusiast. It has many uses: A spade terminal with one snip of the scissors: A battery, or accumulator connection: An excellent earth clip for gas or water pipe—and 101 other uses.



- CLUES DOWN.**
1. Hinder, to obstruct.
 2. Exclamation.
 3. Over.
 4. Large inns.
 5. Level.
 6. Cross gallows.
 7. Consumed.
 8. Help.
 9. Sharp, tapering body.
 10. Enclosure.
 15. Islands.
 17. Edge.
 18. Dye.
 21. Cease.
 23. Warbles.
 25. Turkish institution.
 27. Former Russian Parliament.
 28. Impaired by surroundings
 30. Meals.
 31. Omit.
 34. Certain.
 37. Evil.
 38. Perform.
 39. Preposition.
 41. Part of the verb to be.
 45. Spike of corn.
 47. The ocean.
 49. Abyss.
 50. To navigate.
 51. Measure.
 53. Lively.
 54. Narrow openings.
 55. Protuberance.
 56. Outlet.
 60. Small ocean.
 61. Animal.
 63. Denial.
 64. Father.
 67. Doctor (abbreviated).


WORK OUT THIS CROSS-WORD THEN

ASK YOUR WIRELESS SHOP
HOW YOU MAY WIN £500
WITH YOUR SOLUTION

or write direct to

The NEW LONDON ELECTRON WORKS Ltd.,
EAST HAM Dept. 78. LONDON, E.6

- CLUES ACROSS.**
1. Pacify.
 6. Acid.
 8. Serpent.
 11. The definite article.
 12. Open, public.
 13. Fit for use.
 14. Religious act.
 16. Fish.
 19. Violent noise.
 20. Understanding.
 22. It is.
 24. Tug.
 26. Matched.
 29. Exercises.
 32. At home.
 33. Employ.
 35. On high.
 36. Sphere of influence.
 40. Total.
 41. To feel pain.
 42. Seat.
 43. Conveyance.
 44. Colour.
 46. Scriptural pronoun.
 47. Myself.
 48. Recess.
 52. Animal.
 57. Exists.
 58. Cultivate.
 59. Custom.
 62. Conclusion.
 65. Persons.
 66. Widely, expansively.
 68. Lover of own land.
 69. Pulls along.

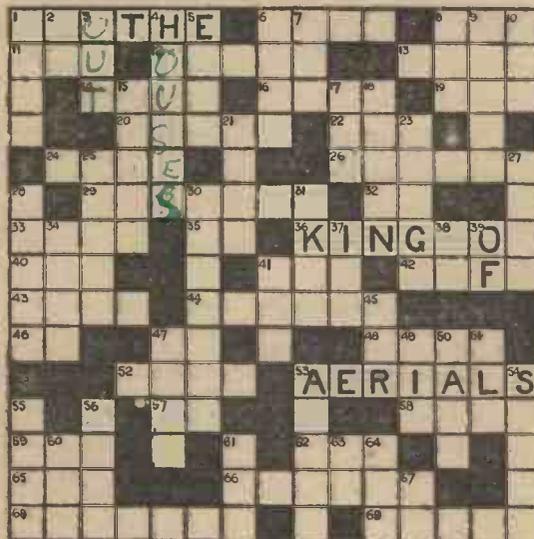

SAVE THE
2/-
DISC

ONE ENTRY
FOR EVERY
1/- SPENT



The Research behind the finest Valve behind a wire wound Anode Resistance

When one research organisation controls several products, it follows that the same standard of efficiency must be applicable to each product marketed. The costly patient research which has resulted in the finest valve, lies behind THE MULLARD WIRE WOUND ANODE RESISTANCE, and it is placed on the market with the certain knowledge that its efficiency is the efficiency of the finest valve.

A resistance wound on a textile fibre core perfectly covered, and interlaid with the same material, ensuring the elimination of all self-capacity, and also that the fine metallic wire is rendered absolutely free from every particle of mechanical shock.

The temperature co-efficient is negligible, since the resistance is not set in wax but only covered with a thin layer of wax to allow a perfect dissipation of heat.

Mullard EVER-REST Wire Wound Anode Resistance (80,000 and 100,000 ohms) ... 5/-

Complete with Holder ... 6/6

Other valves to specification.

- Mullard Grid Leaks and Condensers, ... 2/6
- Type Grid B 0.5 to 5.0 megohms
- Type Grid B combined with .0003 mfd. Condenser Type MA ... 5/-
- Type MA Condenser .0001 to .0009 mfd. ... 2/6
- Type MB Condenser .001 to .01 mfd. ... 3/-

Leaflet W.C. free on request.



WIRE WOUND ANODE RESISTANCE
The MULLARD WIRELESS SERVICE Co., Ltd.
Mullard House, Denmark St., London, W.C.2.

FIRST IN EUROPE

RADIO PRESS TRIUMPH IN INTERNATIONAL COMPETITION IN NEW YORK

"WIRELESS CONSTRUCTOR" READER TO GIVE FULL CONSTRUCTIONAL DETAILS NEXT MONTH.

A specially interesting feature of the great annual Radio World's Fair at New Madison Square Garden, New York, was the international competition for home-constructed sets of all types. The principal class, and the only one in which Radio Press readers entered, was the multi-valve (3 or more valves) category.

Entries were invited from all over the globe, and many sets were sent in by British amateurs, a truly international contest of set-builders resulting. The awards were made on a basis of "workmanship, appearance, volume, distance, selectivity and tone," a body of leading American experts, headed by Dr. Alfred Goldsmith, being the judges.

The result has proved to be a triumph for Radio Press readers, and also for Radio Press designs. The third prize in the multi-valve class in the senior competition was won by a set using the "Elstree Six" circuit, entered by Mr. H. E. Hassall, of 40, Norfolk Street, Strand, London, while in the junior equivalent competition a "Mewflex" receiver (described in "Modern Wireless"), entered by a thirteen-year-old British competitor, J. A. E. Black, of Mill Hill School, won the second prize. This set also won a special cup for general fine workmanship.

These Radio Press readers head the list of the British multi-valve entrants in the international competition — another triumph for Elstree, whose circuit and complete design respectively were used.

Mr. Hassall, who thus holds the European championship, will describe his six-valve set in the next issue of "The Wireless Constructor." While using a similar circuit to that of the "Elstree Six," the design is quite different; screened coils are used and the set is much smaller.



THIS loudspeaker is designed on quite new and original acoustic lines. It is possible on this to get the lowest bass notes and as well the highest treble notes in a perfect form of reproduction.



For distinction of design and construction it stands alone. The attractive cabinet harmonise with any furniture.

Over four feet of curving flute lies in the Touchstone Cabinet to preserve the overtones of perfect rendering.

Price in Oak - - - £6-6-0
Mahogany - - - £7-0-0

Write for full illustrated leaflet 141 giving all particulars.

LONDON:
25, Victoria St., S.W.1.




Newcastle-on-Tyne:
Tangent House, Blackett St.

GENT & CO. Ltd., Faraday Works, LEICESTER.

Don't throw your Fountain Pen away every time it runs dry!

NO fountain pen user would think of throwing his pen away whenever it ran dry. Yet that is exactly what thousands of wireless users are continually doing—whenever their H.T. Dry Battery “runs out” they are obliged to scrap it and buy a new one. But those who have discovered Oldham are more fortunate; they just charge their H.T. Accumulators whenever they run down (four times a year) and forget them! Thus has the Oldham High Tension Accumulator solved the vexed question of H.T. Supply. There are so many improvements embodied in this latest Oldham triumph that it is difficult to imagine anyone ignoring it for one of different make. The refinements which the Oldham includes have long been eagerly looked for by all who deplored the inefficiency of the old dry battery. Think what it means to have an Accumulator which gives the many following advantages:

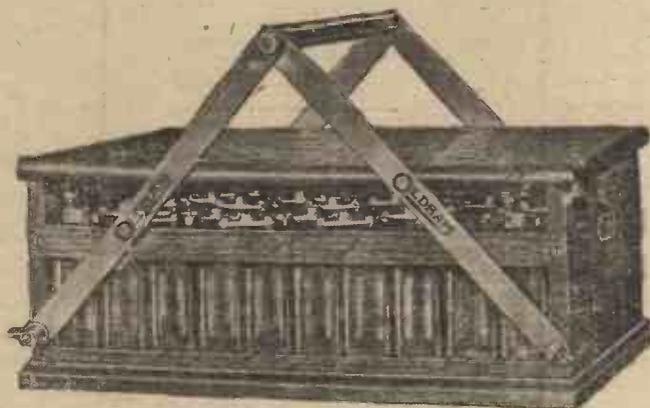A glance at the illustration will show it is built on the unit system—like an expanding bookcase. You can start with, say, 60 volts, and then add to it in 20 volt units as the need arises; 80, 100, 120 volts—just as you will.



10d. per volt
 60 volts £2 10 0, 100 volts £4 3 4
 80 volts £3 6 8, 120 volts £5 0 0
 Complete with lid and handles
 Solid Oak Base, 3/6 extra.

The Accumulator is always neat and tidy—fit to take its place in any room. Acid can't be spilt, and when it needs recharging a convenient carrying handle is available. Each of its big capacity cells is a miniature Oldham accumulator capable of holding its charge for months on end. Each plate is made under the same Special Activation Process which has made the name Oldham famous throughout the world.

Which do you prefer—the ordinary dry H.T. Battery with its consequent noises and cracklings—after some of the cells have become weak—its distortion, lack of volume and constant expense for renewals; or the Oldham H.T. Accumulator which will give a new lease of life to your set, more volume, greater sensitivity, and the utmost economy in operation? Once a man chooses this Oldham he never goes back to expensive dry batteries.

Ask your dealer to show you one of these handsome H.T. Accumulators—don't be put off with a substitute. Nothing can take its place for none other can give you the same steady flow of power—the same freedom from sulphation and the same generous length of service.

OLDHAM & SON, Ltd., Head Office & Works: Denton, MANCHESTER.
 London Office and Service Depot: 6, Eccleston Place, S.W.1. (Phone: Vict. 0286).



REMARKABLE SUCCESS OF THE ELSTREE "SOLODYNE"

Press Opinions of a Radio Press Star Set

THOSE who were able to visit the National Radio Exhibition at Olympia this year will need no introduction to the Elstree "Solodyne." Our readers, too, will remember that in the last issue of THE WIRELESS CONSTRUCTOR it was announced that Radio Press, Limited, would at an early date commence to give demonstrations of the "Solodyne" and possibly of other Radio Press Star Sets.

Full constructional details of the "Solodyne" were published in the September issue of *Modern Wireless*. It possesses only one tuning control, though two stages of tuned high-frequency amplification are used, and fifty stations have been received on the loud-speaker with its aid.

Press Demonstration

In accordance with the policy of Radio Press, Limited, quoted above, a demonstration was given on August 31 last to a gathering of Press representatives at the Radio Press Elstree Laboratories. Among those present were representatives of the following:—*Morning Post*, *Daily Express*, *Daily Telegraph*, *The Scotsman* and *Dispatch*, *Daily News*, the Press Association and the Exchange Telegraph Company.

Simple Tuning

Mr. J. H. Reyner, who was in charge of the demonstration, explained to the visitors some of the difficulties which had to be overcome in designing the "Solodyne." Subsequently the set was connected up, and numerous British and Continental stations were tuned in, the loud-speaker being employed throughout. It is significant also that the aerial system with which the set was used

PRESS OPINIONS

MORNING POST

"A set that in actual test has received 50 Continental stations by merely turning one knob instead of endless fiddling with two or more controls."

DAILY NEWS

"Universal reception made easy. . . . Last night I picked up a dozen stations in as many seconds by turning the dial a few fractions of an inch. Frankfurt, Munster, Bournemouth, San Sebastian, London, Cassel and Dresden tumbled over each other as I turned the dial slowly round."

DAILY EXPRESS

"A wireless receiver which is the last word in simplicity."



One dial—fifty stations on the loud-speaker. The remarkable achievement of the "Solodyne."

DAILY TELEGRAPH

"A remarkable wireless receiving set with an all-Europe range controlled by a single dial was demonstrated to a party of Press representatives at a demonstration at Elstree last night. . . . It is a five-valve set, and simply by the manipulation of this one dial I heard at least a dozen Continental stations as well as the main British Stations. . . . The problem of simple control has thus been practically solved, and, moreover, the set is so constructed that it can be made up by any amateur from components obtainable on the ordinary market."

was a small one of no great height, approximating to the type of aerial system available to the average listener.

When the capabilities of the "Solodyne" had been demonstrated in this way, the Press representatives were then invited to handle the set themselves, and to see how simple an operation is the tuning of it. We give on this page some of the opinions published subsequently.

Choosing Your Star Set

A number of queries have been received from readers, who ask which is the better of the two sets, the "Elstree Six" or the "Solodyne," and which we recommend them to construct. They hesitate to begin building one or other of these Radio Press Star Sets, because they have an idea that one design must be superior to the other.

Each Set the Best in its Class

The answer to these queries is that neither set is superior to the other, and that each is a Radio Press Star Set and is the best in its class.

The "Elstree Six" has three stages of high-frequency amplification, while the "Solodyne" uses two, so that the former set may be expected to give longer range. The "Solodyne," which uses screened coils, has one control, as against four on the "Elstree Six." Alterations in the degree of sensitivity and selectivity obtainable with the "Elstree Six" may be affected by the employment of different anode coils.

Numerous other examples could be taken, and it remains to say that individual preference can be the only deciding factor in determining the choice of one set or the other.



GETTING THE BEST FROM THE "NIGHT HAWK"

Dial Readings for Long-Wave Stations

By PERCY W. HARRIS, M.I.R.E.

THE "Night Hawk," which thousands of readers have already had the opportunity of inspecting at Olympia, is now being built in very large numbers all over the country. Since the article on this Radio Press Star Set was written for last month's WIRELESS CONSTRUCTOR, many further tests have been carried out, which fully justify the claims made for the receiver that it will give long-distance reception for everyone. Full constructional details were given in the last issue, and the article in question, together with the free blue print, will have enabled all who so desire to proceed with the work. I will therefore assume that you have completed building the receiver from the particulars given, and are anxious to get the best from it in adjustment and manipulation.

Filament Circuit

Assuming that you have connected up all wires, and are ready to attach the flexible leads, I would suggest that first of all you connect up positive and negative L.T. leads to your accumulator. As many modern valves, such as the Cossor Point One, give no visible glow to show that the valve is alight, it is of no use trying to see whether your L.T. circuit is correct by plugging in the valves and seeing whether the filament lights up. For this reason if you happen to have handy any valve which shows a visible glow, it is as well to use it for the preliminary test, although, of course, this is not essential. Switch on the current, if you have such a valve, and

plug it into each socket successively, having made sure first of all that your filament resistances are adjusted to allow a flow of current through the valves.

High Tension and Grid Bias

When you are sure that the filament circuit is working and that the on-and-off switch operates satisfactorily set the reaction condenser at zero, carefully unscrew the neutralising condensers

LONG-WAVE STATIONS

The dial readings for long-wave stations heard on the loud-speaker with the "Night Hawk" are as follows:

Station	Degrees
Hilversum	45
Koenigswusterhausen	50
Daventry	135
Radio Paris	146

The above dial readings apply to the second and third dials. The first (aerial circuit) dial may give slightly different readings.

to the minimum position (in the case of the McMichael condensers this will mean that the knob will be screwed upwards as far as it will go), and if you are using 2-volt valves, set the filament resistances as far as they will go in the "on" position. Connect up the high-tension negative and two positives, together with grid bias as suggested by the valve maker for the anode voltage in use. The actual position for the leads will be found on page 1051 of the October issue, under

the heading "Wiring in Words." Do not connect the aerial and earth for a moment.

Preliminary Tests

On switching on and slightly tapping the detector valve with your finger nail, you will probably hear a slight sound in the loud-speaker which will indicate to you that the batteries are properly connected up and the valves are functioning. If you have previously made a set you will know what I mean when I say that set will sound "live." Now set the three condensers at about 5 or 6 degrees in the case of the second and third dial and swing the first dial backwards and forwards. You will probably find that, on reaching a certain position, you will hear a rushing noise, indicating oscillation, and the set will pass in and out of oscillation with a click as you turn any one of the dials.

Neutralising

Now, if you have not already done so, try setting the high-tension voltage at, say, 100 or 120, if you have batteries which reach this figure, for H.T. +2 and about 60 or 70 for H.T. +1. Turn the two neutralising condensers about half-way towards the lowest position, and try swinging the condensers again. You should find a point on the two neutralising condensers where you are just off oscillation at a point where previously the set would have been oscillating. Now place the condensers at about half-way towards their upper reading, say at 90 for a 180 degrees dial, and repeat the process again, leaving the neu-

GETTING THE BEST FROM THE "NIGHT HAWK"

—continued


tralisng condensers in position as before, but trying to see whether you can make the set oscillate by manipulating the dials. Probably you will find that the set will also be stable at this position. Repeat the process once more on the upper range, and you will probably find the set is stable all through. If, however, you find it is not so, slight readjustment of the neutralising condensers will soon put you right. Generally, about half-way down will be found correct.

Reaction Control

Now try the effect of the reaction condenser. You will find it will bring

cally. When you have found your local station, make a note on a sheet of paper of the readings of all three dials, and then gradually proceed to find others. After about half an hour's work on this set, you will find the amazing sensitivity which it possesses.

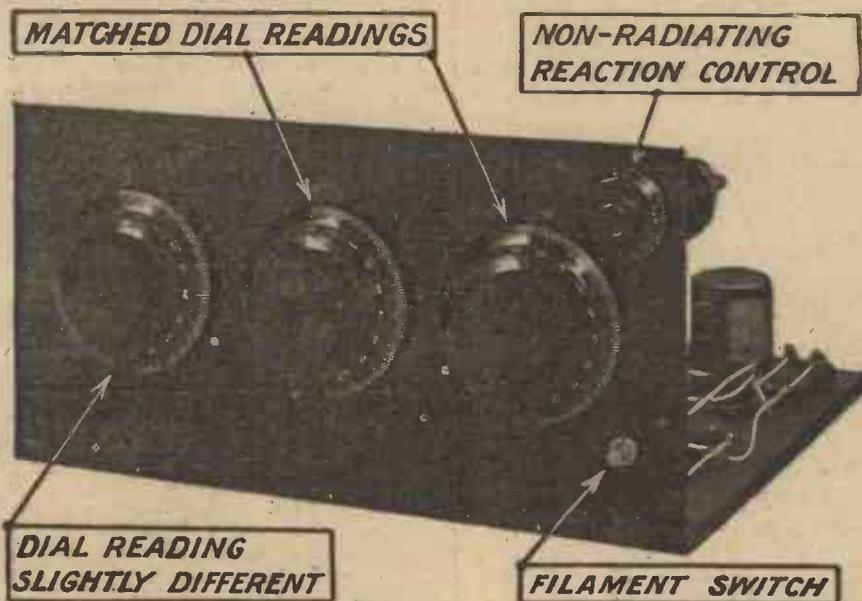If you desire to give the set every refinement, then you may care to buy one of the excellent vernier dials now available. Although not essential to the set, many people will find them very useful owing to the sharp tuning. If you purchase one of the types of dial in which you can make a note of readings, I suggest that you mark the



The operation of the "Night Hawk" is rendered simple by the small number of controls to be handled. A single switch sets all the valves on or off.

the set smoothly in and out of oscillation without what is called "backlash." Backlash means roughly that if on turning the dial oscillation begins at, say, 60 degrees, on turning back the dial the set will not pass out of oscillation again until you have gone much below the 60 point. When reaction is correctly designed in such a set as this, the set should pass smoothly in and out of oscillation without any backlash.

Matched Dials

You may now connect the aerial and earth. Do not be disappointed if you hear no station, even your local station, for the first few minutes, for the set is extraordinarily sharp in tuning, almost as sharp, in fact, as a superheterodyne. You will probably find that the second and third dials read the same for a given wavelength, while the first dial may vary slightly, although in many cases you will find that all three dials will read identi-

positions lightly in pencil. Later, when you have recorded a good number, you may care to remove the dial and carefully ink them in, thus making a really neat job.

Series Condenser

Whether or not you find it best to use the series condenser in the aerial circuit as shown in the last issue, depends entirely on your own aerial. In any case, whatever aerial you use try shorting this condenser with a coin, as indicated last month. On my own aerial I found it better to short the condenser, while others have found it very helpful to keep it in series.

Long Waves

Although the number of stations that can be picked up with one set of coils is very large, some people may prefer also to get, Radio Paris, Daventry, Hilversum, and Koenigswusterhausen on the long range. Messrs.


The latest in Jacks & Plugs



LOTUS JACK SWITCHES

This push-pull switch is designed to occupy the minimum space, being only 1 1/2 in. deep. Of the finest Bakelite, it has nickel silver springs and contacts of pure silver. Soldering contacts can be made to suit any wiring.

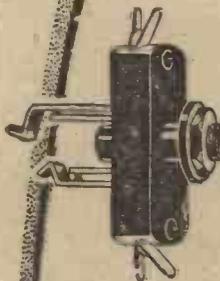
PRICES:
No. 9 as illustrated ... 4/-
Others from ... 2/9



LOTUS JACK

Designed to take up the least space, the depth back of panel being 1 1/2 in. Made from best Bakelite mouldings with nickel silver springs and pure silver contacts. One-hole fixing. Soldering contacts can be brought into any position.

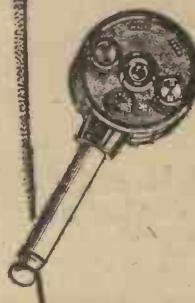PRICES:
No. 3 as illustrated ... 2/6
Others from 2/- to 3/-



LOTUS JACK PLUGS

Designed for use with Lotus Jacks. Made from best Bakelite mouldings and nickel-plated brass. To fix, the wires are placed in slots and gripped in position by a turn of the screw cams.

A spacing sleeve supplied with each Plug makes it adaptable for any make of Jack.

PRICE 2/-


From all Radio Dealers.

LOTUS

JACKS · SWITCHES · PLUGS

Garnett, Whiteley & Co., Ltd.
Lotus Works, Broadgreen Rd., LIVERPOOL

EXPERTS IN RADIO ACOUSTICS SINCE 1908

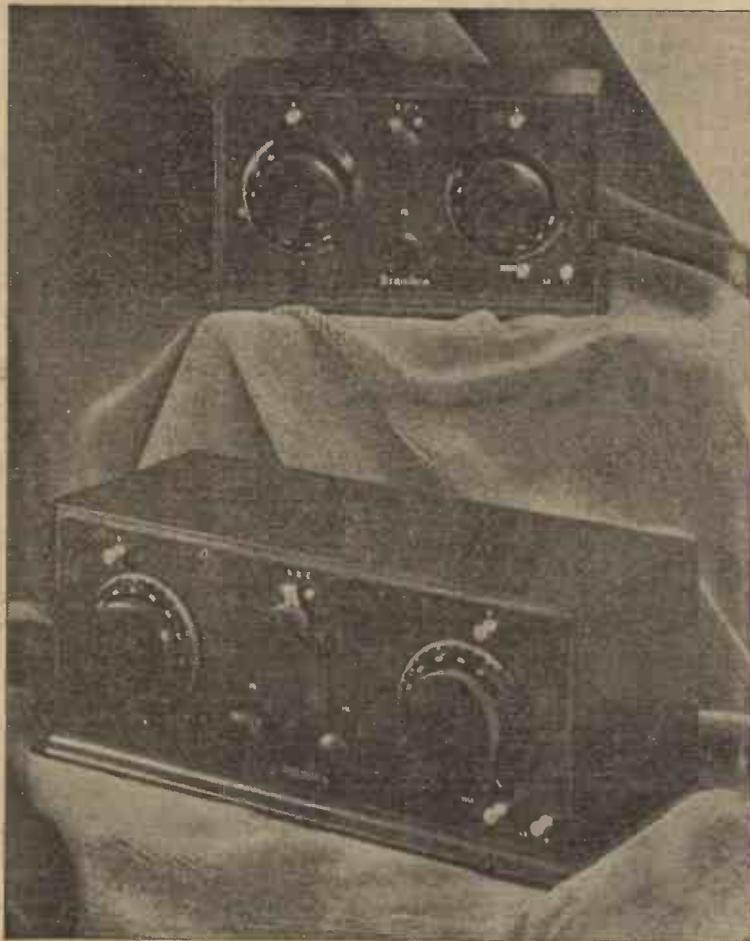

TWO NEW SETS

THE BRANDESET II

The new Brandes 2-valve set is designed for ease of operation, real compactness, and thoroughly efficient loud speaker work. It is simple to operate, and will bring most excellent results from local broadcast stations, and the high power station. It will give good loud speaker results during long range work, depending, of course, on the efficiency of your aerial and earth. It is of the same excellent quality of all Brandes' products, and is reasonably priced

£6:10

(Exclusive of Marconi Royalty and Accessories)

THE BRANDESET III

Like the 2-valve set, the new Brandes 3-valve receiver is designed for ease of operation, marvellous compactness and guaranteed efficiency. If loud-speaker results of great purity and volume are expected from a number of outlying stations, its performance in this direction is unequalled. Both sets have but three controls on the panel, and can easily be operated by a novice. The 3-valve set has, of course, a greater range, but in other respects its characteristics are as the 2-valve set

£8:10

(Exclusive of Marconi Royalty and Accessories)

Brandes

From any reputable Dealer.

BRANDES LIMITED, 296 REGENT ST., LONDON, W.1.

73

Service Advertising

GETTING THE BEST FROM THE "NIGHT HAWK"—continued

Lissens have now prepared excellent long-wave binocular coils for this set, and, having had an opportunity of trying them thoroughly, I can recommend them for use.

They, too, are very sharp in tuning, and there is not the slightest interference on the Daventry wavelength from Radio Paris, or on the Radio Paris wavelength from Daventry. Actual readings on my own set of coils are given in the table accompanying this article.

Stable Neutralisation

It is interesting to note that once the neutralising condensers have been set for the short waves, they do not need touching when the longer wave coils are plugged in. This means, of course, that once you have adjusted the set on the neutralising condensers, you do not need to touch it again; nor, for that matter, need the lid be opened, and all you have to do when starting to listen in the evening, or during the day, for that matter, is to pull out the on-and-off switch, and set your dials at the station you want to hear.

Daylight Reception


Of course, your night range will be far greater than the daytime range, as is the case with all receivers, but full loud-speaker strength in daylight is obtainable from Radio Paris, Daventry, Koenigswusterhausen, and Hilversum, as well, of course, as from a number of British stations, depending on your exact location. I am writing this in the morning, and I have just been listening to the morning news transmission from Hilversum. Although the set is working upstairs in my laboratory, it is clearly audible in the dining room. An hour ago I listened to both 5XX and Radio Paris in the same way, finding that there was not the slightest interference from either of them when listening to the other.

Note Your Readings

To give a complete list of stations audible on the loud-speaker after dark is an impossible task, owing to the fact that so many are now working, and, relatively, so few announce themselves, either comprehensively or regularly. The best thing to do is to keep a notebook, and every time you hear a station make a note of its readings, and, if you can, some kind of note which will help you to identify it again.

Readers' results from the "Night Hawk" will always be welcome, as everyone is interested in what other people get, particularly when they find that the reader who is writing about the subject is situated in their own locality.

H.T. SUPPLY UNIT

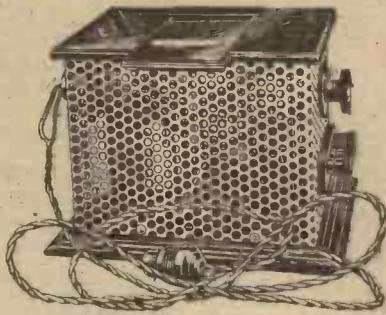

Supplies direct from A.C. mains all the high tension current needed by any wireless receiver. Weak signals are brought up clearly against a background of dead silence.

Arranged to give 3 output voltages of 40, 80 and 120 volts. Embodying double-wave valve rectifier £6 16s. (exclusive of valves).

WEARITE

COMPONENTS

WRIGHT & WEAIRE, LTD.,
740, High Road, Tottenham,
LONDON N. 17.

Telephone: Tottenham 3132. Telegrams: Inland, "Writewe", Totlane, London; Foreign, "Writewe, London."

Lancashire Agent: Alexander Sclanders, 1B, Cooper Street, Manchester.
Glasgow Agent: C. G. Tideman, 47, Carrick Street, C.2, Glasgow.

186-6

Second and third prizes in American Amateur Competition won by users of Copex Copper Coil Screens and COPEX "O.C." COILS



In the recent American Amateur Competition the Third Prize was awarded to a set using Copex "O.C." Coils and Copper Shields. This was the highest award given to any European entry. Also Second Prize awarded to the "Mewflex" (section for entrants under 16 years of age) using Copex Copper Shields and Copex Coils.

The principal advantages of Copex "O.C." Coils over all other screened coils are:

1. Oscillation is rendered perfectly under control.
2. High Amplification. These factors are due to an improved and patented method of construction.

Here are the prices of Copex Coils.

Copex Copper & Screen and 6-pin base ... **15/-**
Copex "O.C." Type Split Secondary Transformer 250/550N. ... **10/6**

Full details of Copex Coils and Screens appear in the Copex Folder W.R. Senda 2d. stamp for a copy to-day.


Patentees and Sole Manufacturers—

PETO-SCOTT Co., Ltd., 77, City Rd., E.C.1
Branches at 62, High Holborn, W.C.1, Walthamstow, Plymouth & Liverpool.

DON'T EXPERIMENT—FIT COPEX!

Increased Electronic emission.

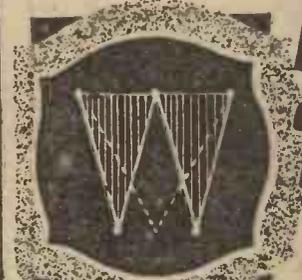length of filament about twice that in the usual type.



Duo-triangular filament suspension



Comparative Diagram SIX-SIXTY



SEEMING is believing. It is obvious from the construction of the Six-Sixty Duo-Triangular system of suspension that the length of filament employed is almost twice that in the usual type of design, represented by broken lines. Now this increased length of filament must result in a corresponding increase in electronic emission, and if in turn all this valuable electron stream is utilised, then greater efficiency must ensue.

In the early days of the radio valve, the length of filament in the old type of cylindrical construction may have been relatively great, but a very large proportion of the electron stream was lost. The design of the new Six-Sixty Point One Valves is such that the entire filament—supported at each corner of both triangles—is wholly enclosed within the grid and anode, and therefore all the electron stream is utilised.

Then, too, the stability and perfect alignment resulting from the additional supports render it unnecessary to assemble the filament in tension, and ensure a constancy of perfect reception.

And, remember, the special Six-Sixty filament itself is wonderfully economical. Its current consumption is barely 1 amp., and when operating at the rated voltage there is absolutely no sign of "glow."

The new Six-Sixty Point One Valves—embodying all the advantages of Duo-Triangular Filament Suspension—are suitable for operation in all stages of a receiver, whether the L.T. supply be 2, 4 or 6 volts.

After exacting and exhaustive tests, Messrs. A. J. Stevens (1914) Ltd., have decided to standardise SIX-SIXTY valves in their famous "Symphony" Range of Receivers.

Descriptive leaflet S.S.9—26, with particulars of complete range, free on application.

S.S.2A., H.F. and L.F. D.E., 1.8 volts, 1 amp. H.F., L.F., and Detector - - 14/-

S.S.10. D.E., 2 volts, 1.5 amp., Power Amplifier - - 18/6

S.S.7. D.E., 3.7 volts, 1 amp., Power Amplifier - - 18/6

S.S.8. D.E., 3.4 volts, 1 amp., General Purpose - - 14/-

These Prices do not apply in the Irish Free State.

SIX-SIXTY VALVES
Better by Six Times Sixty


P.S. 5822.

The Electron Co., Ltd., Triumph House, 189, Regent Street, London, W.1. 2.A.

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.

CAXTON 4-VALVE CABINET

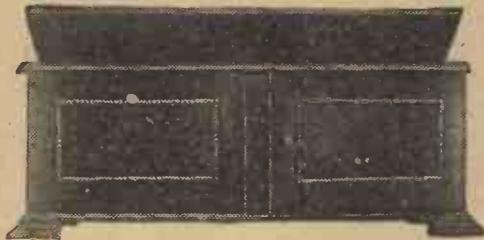Made for Sets "All Concert Receiver,"
 "Fieldless Coil Three Valve Set."
 "Any Valve Low Frequency Amplifier."
 Special Cabinets made to customer's measurements.
 Prices Quoted.



Cash with Order. Fumed Oak ... £1 5 0
 Dark or Jacobean Oak ... £1 10 0
 Real Mahogany ... £1 14 0
 Detachable 7" deep Base Board to mount 16" by 8" panel to slide out of Cabinet front.

The two beaded front doors as illustrated, placed 2 ins. in front of the enclosed panel at 10/- extra.

Ebonite or Radion Panels Supplied and perfectly Fitted at low extra cost.

All Polished with the new enamel that gives a glass hard surface that cannot be soiled or scratched. SENT FREE.—Catalogue of standard Wireless Cabinets in various sizes and woods.

Packed and delivered free in U.K. No. C2

CAXTON WOOD TURNERY CO., Market Harborough

Selling at the rate of a quarter of a million per month in the U.S.A.

HYDRA CONDENSERS



Tested on 500 volts.

Capacity	Mfd.	D.C.	A.C.
.00011 to .0011	..	1/8	..
.016 up to .10	..	1/3	..
..	..	1/2	..
.25 and .50	..	2/3	..
1-	..	2/3	..
2-	..	3/8	..
3-	..	4/5	..
4-	..	6/-	..

Obtainable from your dealer, or direct from
LOUIS HOLZMAN
 109 KINGSWAY - LONDON, W.C.2

Makes short circuit impossible



THE "Peerless" JUNIOR Rheostat

An OFF position is provided, while definite stops make short circuit impossible. Resistance element is immune from damage. Will safely carry current of two valves. Complete with nickelled dial and one-hole fixing. Three types: Size 1 1/2" diameter, 1/2" high, 6, 15 or 30 ohms. Retail Price only


2/6

From all dealers or direct:

THE BEDFORD ELECTRICAL & RADIO Co. Ltd.
 22 CAMPBELL ROAD, BEDFORD

GAMBRELL

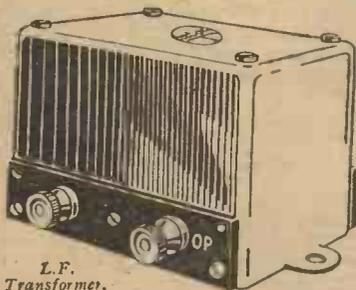Low Frequency Transformers were designed to reduce to a minimum self-capacity and other defects which cause distortion. They give you a great degree of amplification as well as constant amplification over a wide band of frequencies resulting in ample volume with perfect reproduction.



L.F. Transformer.

of approximately 2 to 38 micro micro-farads. Each revolution represents approximately 6 m. mfd's. Highly commented upon by leading Radio publications and used in many famous designs of sets.

PRICES:

Stage 1, Ratio 3 1/2 to 1.
 Stage 2, Ratio 5 to 1.
 25/6 Each.

NEUTROVERNIA CONDENSER

Only six complete revolutions of the Control Knob take you through the wide capacity range
 Price 5/6 Each.

GAMBRELL "EFFICIENCY" COILS.

Our Standard Coils are now supplied CENTRE TAPPED at an extra cost of 6d. each.

AT OLYMPIA we distributed thousands of our new illustrated folders; if you were not there send for particulars of Sets—Wavemeters—or Components that interest you. Mention the "Wireless Constructor."


GAMBRELL BROS., LTD.,
 76, VICTORIA STREET, LONDON, S.W.1



ULTRA LOW LOSS Straight Line Frequency Condenser.

Cone Bearings, Braced Vanes, Positive Collector. A Real Precision job.
 Condenser only .0003µF.—.0005µF. 9/-
 Condenser with plain Dial Standard 1/2" Dia. Shaft. 10/6

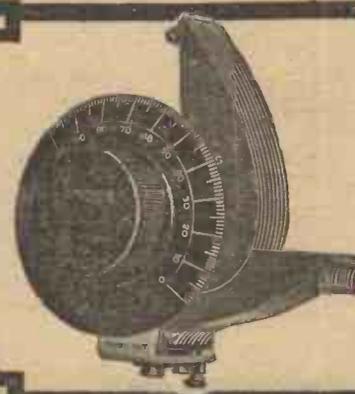SEND FOR CATALOGUE AND DESCRIPTIVE LITERATURE OF COMPLETE FORMO RANGE THE FORMO COMPANY, Crown Works, Cricklewood, N.W.2. Phone: Hamp. 1787. Manchester: Mr. J. B. Levee, 23, Hartley Street, Levenshulme. Phone: Heaton Moor 475. See page 50 for Formo Transformers.



BUSH HOUSE

The Largest Wireless House outside London
 CALL IN AND SEE US.

PARTS FOR
ELSTREE SIX; SOLODYNE
 and all other POPULAR CIRCUITS.

Do not fail to write for it—it is sure to be in stock.
 SEND FOR LIST NOW.

60 Volt SURE LIFE BATTERIES - 7/6
 100 " GRID BIAS - 12/6
 9 " - 1/-
 Guaranteed and Post Free over 5/-
 All makes of Valves in Stock.

35. SHUDEHILL, MANCHESTER

ANOTHER RADIO PRESS SUCCESS

Blue Riband of the Ether
Won at Amsterdam

“ELSTREE SIX” WINS WORLD CHAMPIONSHIP

AMATEURS of all nationalities were invited to submit wireless apparatus constructed by themselves for competition at the International Radio-Amateur Festival, held in Amsterdam between September 18 and 26. The aim of the Amsterdam Radio Society, organisers of the Festival, was to encourage the spirit of goodwill between Dutch

radio amateurs and their friends in all countries.

The result of this international competition, open to the world, has gained for a Radio Press reader and a Radio Press design the first place. The gold medal of the competition, the highest distinction possible, has been awarded to an “Elstree Six” set, entered by Mr. R. W. Emerson, of 3, St. Ann’s Terrace, St. John’s

Wood, London, N.W.8. Mr. Emerson is interested in the construction of wireless sets purely as a hobby, being engaged in the fur business.

The “Elstree Six” entered for competition was identical in layout and construction with the original “Elstree Six,” the Radio Press Star Set, of which a full description was published in the June issue of *Modern Wireless*.



EFFICIENT BECAUSE the coil is wound with a low capacity spaced winding under Burndep’t Patent No. 168249.

STRONG BECAUSE the coil is supported by a best quality ebony ring, and will not lose its shape when pulled out of the holder.


LOW-LOSS FINALLY because it is mounted on the TRIX low-loss coil mount.

PRICES:
From 2/3 (No. 35)
to 4/6 (No. 250)

Use these Coils in the TRIX COIL HOLDER.



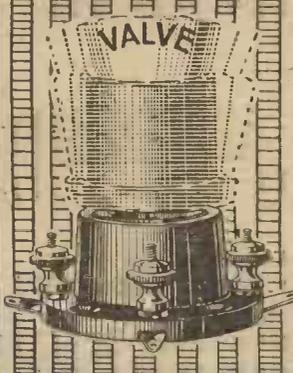ERIC J. LEVER, 33, Clerkenwell Green, London, E.C.1.
Phone: Clerk. 3014/5. And at Birmingham, Liverpool, Glasgow, etc.



FINSTON
Puratone Valve Holder

The name of this valve holder agrees with the quality of reproduction secured when using them in your set.


They eliminate all valve noises and absorb vibration interferences.

AN IDEAL HOLDER FOR PERFECTLY PURE RECEPTION.

Price 2/- each
(See Illustration).

Obtainable from all good dealers. Write for Complete Folder of all our Components.

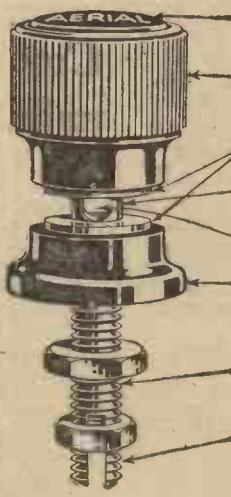FINSTON MFG. CO., LTD.
45, Horseferry Road, London, S.W.1



- Non-rotating insulated engraved top.
- Highly finished screw-action Bakelite-insulated head.
- Shielded metal clamping faces.
- Smooth stem, ensuring that strands of connecting wire will not bind up with thread.
- Cross-hole for connections, flush with clamping face.
- Highly finished Bakelite-insulated collar.
- Standard 2 B.A. stem with nut.
- Transverse slot with clamping nut, eliminating soldering.

Patent No. 248921.
Registered Design No. 715424.

*The Belling-Lee Terminal,
made with 28 different engravings.*

Standard Model (Bakelite-insulated) (Type B)... .. 9d. each.
Popular Model (non-insulated) (Type M)... .. 6d. each.

If you cannot get these at your dealer's, send your order to us enclosing his name and address.
Illustrated Catalogue free on request.

BELLING-LEE
PANEL FITTINGS

BELLING & LEE, Ltd., Queensway Works, Ponders End, Middlesex. E.P.8.13

Parrs Ad.

The World's best Radio Products



1/6

Fit Neutron and Detect the Difference in volume, range and purity.



12/6

**BRING IN MORE STATIONS
ELIMINATE INTERFERENCE**

Cut through local programmes by using NEUTRON VALVES

NEUTRON DULL EMITTER VALVES.

If you want to tune in those distant stations use Neutron D.E. Valves. Extraordinary filament emission unequalled for Crystal clarity of reproduction—absolutely Non-microphonic. BRITISH MADE. FULLY GUARANTEED.

4 volt. H.F. '06 amps. 2 volt. H.F. 0'2 amps. } 12/6 each
4 " L.F. '06 " 2 " L.F. 0'2 " }

POWER VALVE, 5-6 volt. 15/6 each.

FOR LOUDEST RECEPTION

The most sensitive series of PERMANENT DETECTORS

MAGN M or CRYSTASTAT for panel mounting. PANTECTOR, one hole fixing, under panel.

These Detectors are guaranteed and tested on actual Broadcast 130 miles from 5XX.

THE NEUTRON H.T. BATTERY.

Full 60 Volt. BRITISH MADE, Long Life. 10/6

Note new price (Sealed with special plugs to avoid tampering.)

A WONDERFUL NEW INVENTION.

NEUTRON CHEMICAL EARTH.

Signal strength increased by 50%.

Simply dissolve in hot water and pour into earth tube or around your earth connection. 3/6



5/6



3/6




4/6



Advertisement of Neutron Ltd., London

Sole Distributors for U.K. and Ireland:
NEUTRON DISTRIBUTORS, 144, Theobald's Road, London, W.C.1.

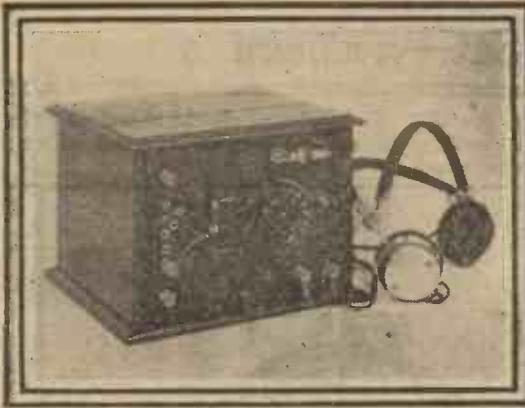All Export enquiries for Continent and Australasia to:
Pettigrew & Merriman, Ltd., 2 & 4, Bucknall Street, Oxford Street, W.1.



AN ALL-ENCLOSED CRYSTAL SET

By A. V. D. HORT, B.A.

A simply-constructed crystal set which will give reception of a station on the lower wavelength range or Daventry without change of coils. Selectivity is provided for by means of aerial and crystal tappings.

THERE is a certain attraction, both in elaborate and in simple sets, in being able to make every necessary adjustment of the set by means of controls on the panel. It is sometimes annoying, for example, to be compelled to open the cabinet, or even temporarily to remove the set from it, in order to insert or withdraw a coil.

Simplicity

In the crystal set to be described here, simplicity has been aimed at, consistent with adequate provision for adapting the set to suit different

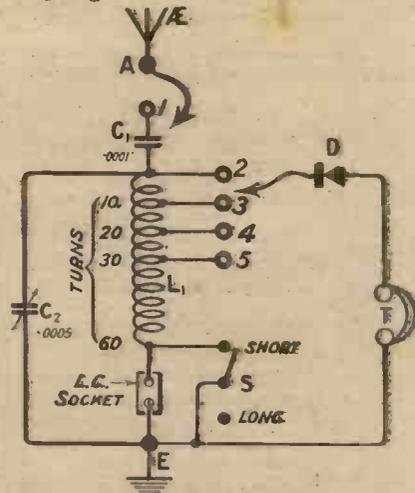


Fig. 1.—The tuning condenser, C2, is placed in parallel with both coils, the loading coil being short-circuited when not required.

aerials, while at the same time all the controls are placed on the panel. The theoretical circuit diagram is given in Fig. 1, and reference to this will show that tapping points are provided on the tuning coil, L₁, which is of a suitable size for the lower broadcast range of wavelengths.

Tappings

By means of plugs and sockets the connections to the aerial and to the crystal detector may be brought to the tappings on the coil found by experiment to give the best results. In addi-

tion, a series condenser is fitted, which may be included in the aerial circuit if necessary.

The loading coil for the reception of Daventry is housed inside the cabinet, and is left permanently in its socket, the change from long to short waves or vice versa being effected by means of a switch on the panel.

The list of components required for the construction of the set is given in the accompanying table. This list is intended as a guide for the constructor, and it is recommended that if any departures from it be made, the constructor ensures that he obtains only components of good quality.

Winding the Coil

The first constructional operation to be carried out is that of winding the tuning coil, L₁, in the circuit diagram. This is a straightforward matter, the only point worthy of special note being the method of securing the tappings.

Begin by drilling two small holes in the former close together at one end. Pass the end of the No. 26 S.W.G.


former. Wind on ten turns and then, holding the former and the winding

BUILD THIS SET WITH

- One ebonite panel, 8 in. by 6 in. by $\frac{1}{16}$ or $\frac{1}{8}$ in.
- One cabinet to suit, and baseboard 7 in. deep (Peto-Scott Co., Ltd.)
- One square law low loss variable condenser .0005 (Ormond).
- One fixed condenser .0001, type 600A. (Dubilier.)
- One permanent crystal detector. (Brownie Wireless, Ltd.)
- One baseboard mounting coil socket. (Burne-Jones & Co., Ltd.)
- One panel mounting single-pole change-over switch. (A. F. Bulgin & Co.)
- One octagonal ribbed ebonite coil former, 3 in. diameter by 3½ in. long. (Redfern's Rubber Works, Ltd.)
- One Daventry loading coil No. 150.
- Four Clix sockets and two Clix plugs. (Autoveyors.)
- Four terminals.
- Glazite, a short length of flex, and about 16 yards of No. 26 s.w.g. d.c.c. wire.
- Radio Press panel transfers.



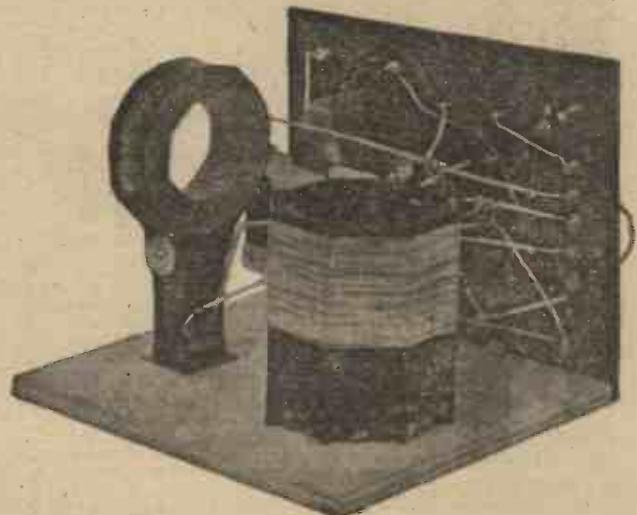Note the rigid wires from the Clix sockets to the tappings on the coil.



wire through these, so that it is quite secure, and commence winding the first turn about $\frac{1}{8}$ inch from the end of the

to prevent the latter coming loose, drill a small hole through the base of one of the ridges on the former.

An All-Enclosed Crystal Set—continued

Bend the wire back on itself 2 inches from this hole, and pass the end of the loop so formed through the hole in the direction of winding. Pull the last turn wound quite tight before continuing to wind the coil.

Tappings are made in this way at the 10th, 20th and 30th turns, the winding being then continued till 50 turns have been wound, the end of the wire being secured in a similar manner to the start of the winding.

As will be seen from the wiring diagram, the tappings are spaced round the former, so that they shall not come too close together. This arrangement makes it possible for the stiff wire leads to the tappings to be well separated, and also makes it easy to fix these leads in position.

The Panel

The next operation is to drill the necessary holes in the panel. If the components listed elsewhere are used, the drilling diagram (Fig. 2) will supply the required dimensions. When the holes have been drilled, the baseboard and panel should be placed in their proper positions in the cabinet and the four woodscrews inserted along the base of the panel to secure it to the baseboard. Since the panel is

small and does not carry any great weight, no panel brackets are used. The screws which hold the panel to

the baseboard should therefore be long enough to project into the latter for at least half an inch.


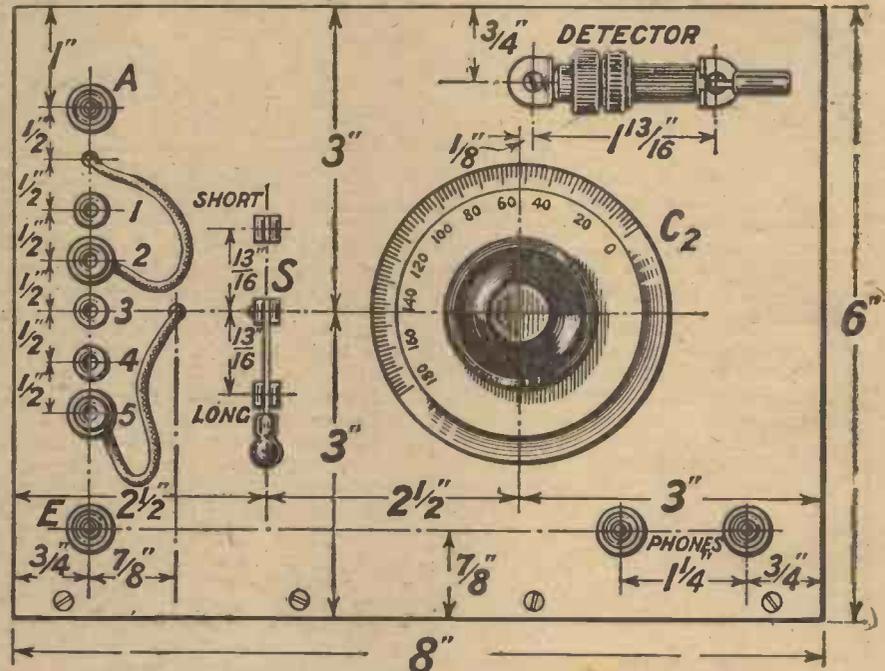


Fig. 2.—The dimensions for laying out the panel may be taken from this diagram. Blueprint No. 1068A is also obtainable.

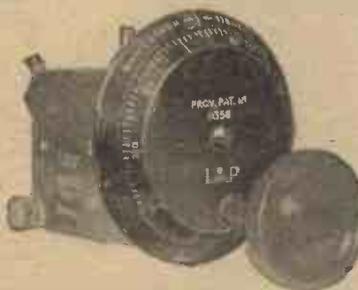

The L & P Indicating Dial

The whole wireless world knows that the "L & P" Universal Coil Holder gives the finest control of coupling ever achieved.

Thanks to the new L & P Indicating Dial you can now keep a record of the exact degree of coupling between the two coils, from 0 to 90°. The dial is easily fitted to any L & P Coil Holder—without even the need of drilling a hole. It is an accurate scientific instrument, beautifully made, and working without a trace of backlash.

L & P Indicating Dial 5/6 each
The L & P Universal Two-Coil Holder is a marvel of value at 8s. 6d.

FROM GOOD DEALERS EVERYWHERE.

Manufacturers:
LONDON & PROVINCIAL RADIO CO. LTD.,
COLNE, LANCS.

Telephone: 94. Telegrams: "Reception."



FINSTON
Filament Resistances.

Well designed and constructed. Supplied for use with any type of valve. Clearly engraved dials. Bakelite mouldings and Knob with combined pointer, Terminals and Soldering Tags, complete.

Prices:
7 ohms, 2/3; 15 and 30 ohms, 2/6 each Dual. 6 and 30 ohms, 3/3

Smooth in Action. Low in Price.

Obtainable from most Dealers. Illustrated Leaflet of all Finston Components Free.

FINSTON MFG. CO., LTD.,
45, Horseferry Road, London, S.W.1

Patrs Ad.



FORMO
A MONUMENT IN THE MARCH OF PROGRESS.

The FORMO SHROUDED Transformer is the universal favourite.

10/6 Made in Ratios 1-1, 1-2, 1-3, 1-4 & 1-5
1-3 & 1-5 for 1st & 2nd Stages.

SEND FOR CATALOGUE AND DESCRIPTIVE LITERATURE OF COMPLETE FORMO RANGE.

THE FORMO COMPANY,
CROWN WORKS, CRICKLEWOOD, N.W.2
Phone: Hamp. 1787.

Manchester: Mr. J. B. Levee, 23, Hartley St., Levenshulme. Phone: Heaton Moor, 475.
See page 46 for Formo S.L.F. Condenser.




USE A CONDENSER THAT DELIVERS ALL ITS STORED-UP ENERGY



Use LISSEN FIXED MICA CONDENSERS—made with scrupulous care—accurate to 5 per cent.—THEY NEVER LEAK—THEY NEVER VARY—THEY DELIVER ALL THEIR STORED-UP ENERGY, ALL THE TIME.

Capacities '0001 to '001. 1/- each (reduced '002 to '006. 1/6 price)
(One pair grid leak clips included free with each '0003 and '0002 capacity.)

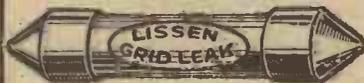LEAVING GRID-LEAKS ON OUR FACTORY ROOF TO TEST THEM



A case of LISSEN FIXED GRID LEAKS were left on the roof of the LISSEN Factory—they were soaked by rain, they were baked by the sun—then they were handed over to the LISSEN research department and carefully tested—in every grid leak the resistance was found unvaried and true to the marked value.

All capacities, previously 1/8, now 1/- each

DOUBLE PURPOSE VALVE HOLDER



Bend back springs for baseboard mounting—or put through panel for panel mounting—low loss, low capacity, meaning clearer, better signals.

LISSEN VALVE HOLDER, previously 1/8, now 1/- each.

REAL RADIO SWITCHES

There is a LISSEN switch for every switching need. Your dealer has them all, or, if any difficulty, send direct.

	Previously	Now
LISSEN 2-way switch ... 2/9	...	1/6
.. Series-parallel switch 3/9	...	2/6
.. Double Pole Double Throw 4/-	...	2/6
.. Key Switch ... 2/6	...	1/6

PARTS THAT PULL TOGETHER

When you are equipped with LISSEN Parts every vital part is pulling strongly with each other, and then you have a receiver which is the best you can ever get.

Important to the trade!

Retailers who have not already been notified of our new direct-from-factory-to-dealer distributing policy should in their own interests communicate with us without delay. All orders must now be sent to us at Richmond, and not to usual factor.

A Revolution in Transformer Value—

powerful amplifiers now within the reach of all.



Everybody will be wanting to buy this new LISSEN L.F. Transformer. There will be LISSEN home-built amplifiers everywhere, and home-built LISSENOLA loud speakers, too, because everybody can now possess themselves of a powerful LISSEN loud speaker combination that will equal anything you ever heard, and at a price within the reach of all. Telephones can be discarded by everybody and radio made to yield much greater enjoyment in consequence. By ourselves distributing direct to the retail trade from factory we cut out all wholesale profits. This new policy has been a deciding factor in enabling us to sell this new Lissen part at a remarkable low price.

There is no longer any need for you to pay higher for a first-grade transformer. So good is this new one that we have unhesitatingly withdrawn all our old previous high-priced models in its favour. Compare it against any for tone, purity, and power—it amplifies every note, every harmonic, and every overtone.

You can get it at your dealer's, or direct from factory if you have any difficulty. If you are not satisfied with it after test take it back to your dealer's or send it back to us. You will find it suits every set and every valve you will want to use.

Amplifies fully every note—every harmonic—every overtone.

Turns ratio 3 to 1.
Resistance ratio 4 to 1.

Build a better Amplifier!

Price **8/6**—and guaranteed for 12 months.


Include no postage if you send for it direct, but please send dealer's name and address.



This week-end build your own loud speaker!

First of all go to your dealer and satisfy yourself that the "Lissenola," costing only 13/6, really is fully equal in power and tone to any loud speaker on the market. Ask your Dealer to put on the best loud speaker he has in stock—then use the same horn on the "Lissenola," and see if you can notice any difference.

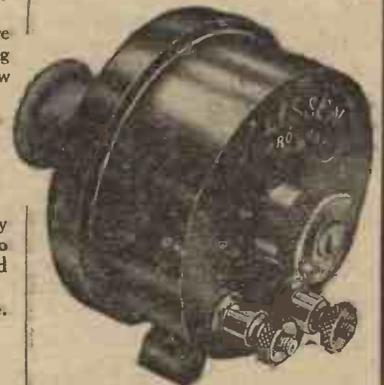When you get the "Lissenola" home you can build a horn yourself for a few pence, providing you with a powerful instrument which will compare with any expensive loud speaker you have ever heard. Or, if you prefer a cone-principle diaphragm—very simply made—you should get a Lissen Reed as well (1/- extra). If you have never heard a "Lissenola" there's a surprise in store for you.



*These diagrams and instructions will be sent post free to any address on receipt of 6d. in stamps. Send to-day.

Before buying ask your dealer to demonstrate the "LISSENOLA."

LISSEN LIMITED

Lissenium Works,
26-30, Friars Lane,
Richmond, Surrey.

Managing Director: T. N. COLE.

There is a LISSEN part for every radio need.



7 Say "Seven" and Save Money 7

THE NEW No. 7 RECUPERATING AGENT IN THE HELLESEN DRY BATTERIES GIVES YOU BETTER AND LONGER SERVICE.

To-day you demand more from your H.T. Battery in long and frequent usage and a Battery which possesses the power of recuperation to the greatest degree is absolutely necessary.

To-day you also have the opportunity of buying at a competitive price Dry Batteries which have always sold on quality—not on price—

Helleesen Batteries at Hunt's New Prices

represent the best value on the market to-day.

60 volt "WIRIN" 12/6 99 volt "WIRUP" 21/-.
Postage extra.

All types, voltages, etc., in Double and Treble Capacities, Dry Batteries for Low Tension Hand and Pocket Lamps.

With quadruple insulation and sealed cover the GENUINE HELLESEN is the GENUINE ARTICLE.

From all Radio, Electrical and General Stores, Harrods', Selfridge's, Barker's, Whiteley's, etc., or direct from:

A. H. HUNT (DEPT. 15) CROYDON, SURREY

Write for Leaflet 155a



"Silvertown"

WIRELESS ACCESSORIES

Quality guaranteed by over 50 years electrical manufacturing experience.



The SILVERVOX


The "Silvervox" Loud-speaker will reproduce both speech and music without the loss of its original tone and quality. Coils wound to either 120 or 2,000 ohms; The tone arm is a heavy aluminium casting, Total height 20 inches, Size of trumpet 12 1/2 inches diameter, Price £3:0:0 each.

B. 599.

FILAMENT RHEOSTAT ONE HOLE FIXING.

Circular pattern, on ebonite former, complete with knob, pointer, black celluloid scale engraved in white, and two terminals for connections. The resistance wire is wound on an insulating rod, thereby giving a perfectly smooth adjustment. B.599—Wound to approximately 5 ohms resistance. Price 3/- each.

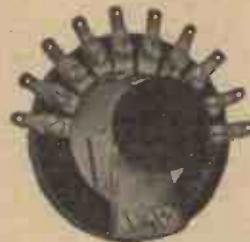B. 600—Wound to approximately 30 ohms resistance. Price 5/6 each.



B. 570.

10-WAY INDUCTANCE OR CAPACITY SWITCH.

(Patent 226245.)

This switch is of the under panel mounting type, and is fitted to the panel by means of the two countersunk head screws supplied. It enables the experimenter to build up large capacities, and is an invaluable addition to any set. Price 5/6 each.

AN AID TO ENTHUSIASTS.

We have prepared a logging chart for recording wavelengths, condenser settings, etc., of those stations which require careful calibration to tune in. A copy of this chart, printed on stiff card with hanger, can be obtained free of charge at any of our Branches or from any high-class dealer.

MAKERS :

THE SILVERTOWN COMPANY,

106, Cannon St., London, E.C.4. Works : Silvertown, E.16.

BELFAST.
BIRMINGHAM.
BRISTOL.
CARDIFF.

DUBLIN.
GLASGOW.
LEEDS.
LIVERPOOL,
LONDON.

MANCHESTER.
NEWCASTLE-ON-TYNE.
PORTSMOUTH.
SHEFFIELD.



An All-Enclosed Crystal Set—continued

Mounting Components

The components may now be mounted on the panel. In fixing the

board by means of a wooden cross-piece at the lower end of the former. A strip of wood about $\frac{1}{4}$ in. thick is required, cut to fit inside the end of

ensure that it clears the variable condenser and the back of the cabinet.

Wiring

The wiring of the set should present no difficulties if the wiring dia-

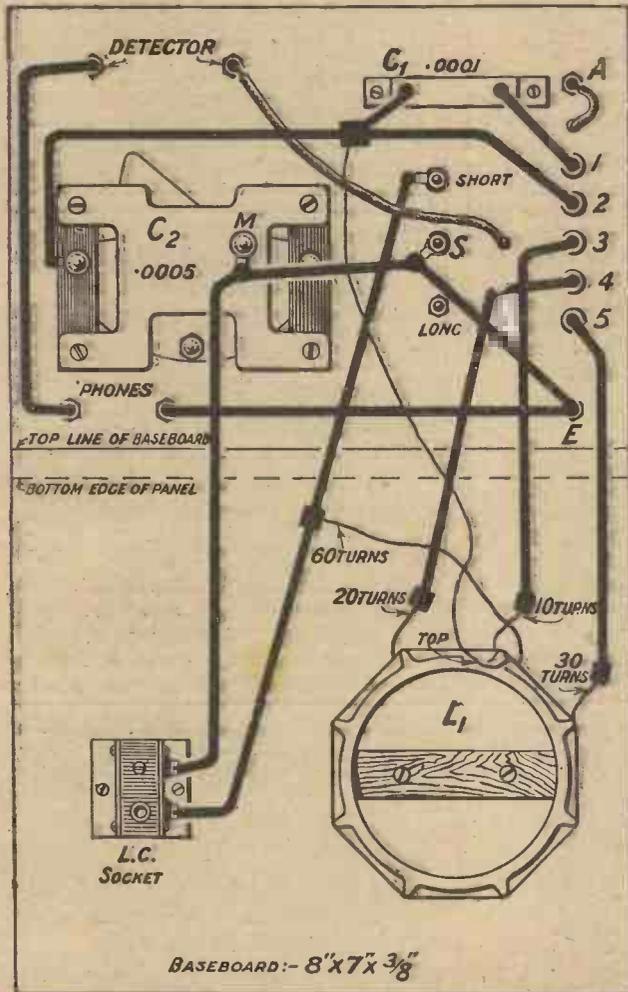


Fig. 3.—Note that stiff wire leads connect the tap-pings on the coil L1 to the Clix sockets. Blueprint No. 1068B.

WIRING IN WORDS

All directions are given as viewing the set from the back.

Join earth terminal to right telephone terminal; also to centre of knife switch, thence to moving vanes of variable condenser C2 and to one terminal of loading coil socket.

Join remaining telephone terminal to left terminal of crystal detector.

Join remaining terminal of loading coil socket to top of knife switch, and also to lower end of coil L1.

Join bottom Clix socket (No. 5) to 30-turn tapping on coil L1.

Join No. 4 Clix socket to 20-turn tapping on coil L1.

Join No. 3 Clix socket to 10-turn tapping on coil L1.

Join fixed vanes of variable condenser C2 to No. 2 Clix socket, to top end of coil L1, and to one side of fixed condenser C1.

Join remaining side of condenser C1 to top Clix socket (No. 1).

Join flex leads to remaining terminal of crystal detector and to aerial terminal, fitting the free ends with Clix plugs.

gram (Fig. 3) and the special wiring instructions are followed. The tap-pings on the coil are soldered to short lengths of Glazite; themselves soldered to the Clix sockets, this making for rigidity of these connections. The insulation is removed from the tapping loops and the bared loops are twisted round the ends of the rigid wires before soldering.

It should be noted that one of the Clix plugs should be fixed to the flex lead by gripping the latter under the nut below the insulating bush. One or other of the plugs should be treated in this way, since if both were attached to the lead down the centre it would be impossible to insert the aerial and crystal plugs in the same tapping socket.

single-pole switch, the centre clip carrying the switch blade should be secured first. Then the other two clips should be placed in position, the blade being inserted into each in turn as the nuts are tightened, to ensure correct alignment of the clips.

The variable condenser should be mounted last of the components on the panel, and it will render the operation of wiring easier if the wires from the telephone terminals to the crystal detector and the earth terminal are soldered in position before the variable condenser is mounted.

In the set illustrated here the fixed condenser, C1 in the circuit diagram, is secured to the panel by means of two 6B.A. bolts in "blind" holes tapped in the panel. If preferred; clearance holes may be drilled in the panel and countersunk bolts passed through it with nuts at the back to hold the condenser.


Fixing the Coil

The tapped coil is fixed on the base-


the former. It is secured by two screws through the walls of the former, two other screws fixing the cross-piece to the baseboard.



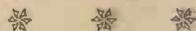The coil has here been removed to show the disposition of the wiring.



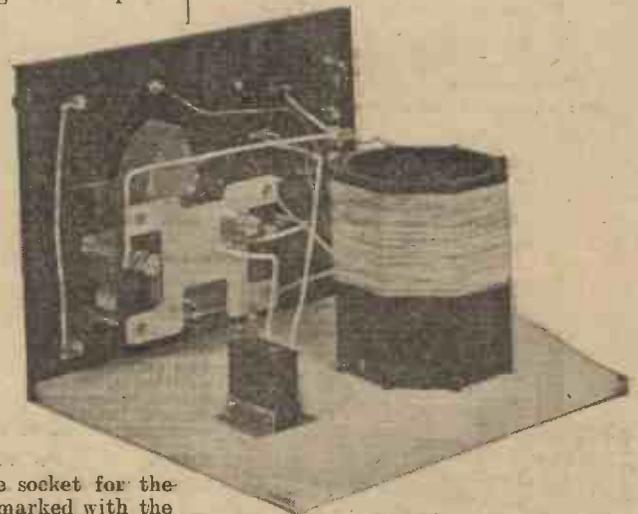The position for the socket for the loading coil should be marked with the correct size of coil in the socket, to



(Concluded on p. 54.)

CABINETS of QUALITY

Wireless Cabinets made of prime quality material. All sizes in stock for Radio Press Sets. Specials made to order. Vertical type with hinged lid moulded top and base; complete with baseboard.

Size—inside measurements. 1" PLY. OAK. MAHOG.
 12" x 8" x 8" Price 13/0 15/6 18/0
 16" x 8" x 8" Price 16/6 19/6 22/6
 Carriage Paid.

Wood supplied cut, planed, and moulded ready to assemble. Estimates free.

J. W. WALKER, Cabinet Maker,
 9, Manor Park Parade, High Rd., Lee, S.E.13

AN ALL-ENCLOSED CRYSTAL SET—concluded from page 53

Results

Tested on a low aerial of average length in the London N.W. district, at a distance of about one mile from the 2LO aerial, the set gave signals of excellent strength from the London station, with aerial plug in socket No. 1 and the crystal plug in socket No. 2. With these settings tuning was distinctly flat. The best results as far as selectivity was concerned were obtained with both aerial and crystal plugs in socket No. 5, and there was little noticeable reduction in signal strength. With this adjustment 2LO could be tuned out within a few degrees of the tuning condenser on either side of a point of marked maximum signal strength.

Daventry

While in the locality mentioned Daventry could not be picked up on the crystal set alone, the addition of an amplifier made possible the testing of the change-over switch. It was found that the change from long to short waves could be accomplished in a moment and with a minimum of trouble.

The approximate cost of the components required for building this set is £2.

A HOME FOR YOUR WIRELESS SET

OUR STANDARD CABINETS

are **DUSTPROOF** and house the whole apparatus, leaving no parts to be interfered with. All you do is **UNLOCK and TUNE IN**. Made on mass production lines, hence the low price. Provision is made to take panels from 16 x 7 up to 30 x 18 in.



Carriage paid and packed free England and Wales. Money returned if not satisfied.

MAKERIMPORT Co.

From 24 15 0
 Write to-day for descriptive pamphlet and suggestions for adapting your receiver or panel in our Standard Cabinets. Immediate Delivery. Dept. 20, Melville Chambers, 50a, Lord St., LIVERPOOL.

ACCUMULATORS ON EASY PAYMENTS

High Tension Accumulators built up from 20 Volt sections (15/- each). Example: 60 Volt H.T. 45/- CASH or 12/6 DOWN and 6 monthly payments of 6/-. Carriage Paid. Satisfaction or money back.



Write for Lists to DEPT. 13, COVENTRY DIRECT SUPPLIES LIMITED, 23, Warwick Row, COVENTRY. Any Wireless Goods supplied on easy payments.

LITTLE WIRELESS CABINETS

MAP

Small Parts to the Trade

MAP Co. 246, Gt. Lister St., Birmingham.


All communications regarding advertisements should be addressed to:

The Advertisement Manager,
"WIRELESS CONSTRUCTOR,"
 Bush House, Strand, London, W.C.2
 Telephone: City 9911.

COMPONENTS AT WHOLESALE PRICES

Send for Bargain Price List. EVERYTHING REDUCED.

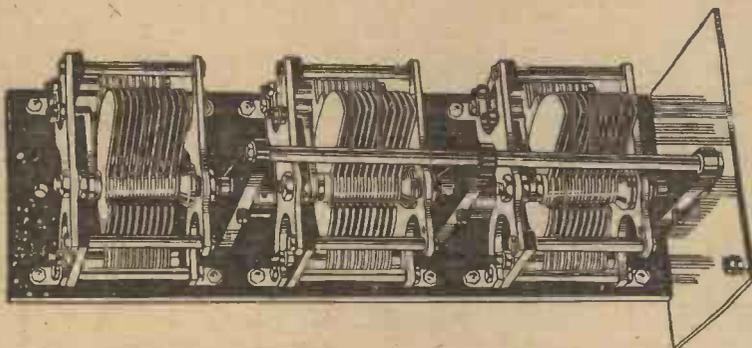Laurie & McConal Ltd., Fitzroy Street, Cambridge



The **CYLDON** (pronounced SIL-DON)
TRIPLE GANG CONDENSER

for use in the New **Five-Valve Elstree**

"SOLODYNE"

Price £3 . 10 . 0 (Without Dial)

Get full particulars of all Cyldon Products from your dealer or write direct to the makers. Other Cyldon Condensers comprise Square Law, Square Law Dual Pattern, and the S.L.F. 4 in. Knob Dial, supplied free with Square Law and Dual Models, and 2s. extra with S.L.F. or Triple Gang.

SYDNEY S. BIRD & SONS,

"Cyldon" Works, Sarnesfield Road, ENFIELD TOWN, MIDDLESEX.
 Telephone: Enfield 0672.

CONSTRUCTORS are giving this handsome new model a most enthusiastic welcome because of (1) Its absolute freedom from whip. (2) Independent adjustment of each Condenser by novel means, completely eliminating hand capacity.

OTHER attractive features are—each Condenser electrically separated. Anti-capacity plate supplied. Operation of all three condensers as "silky" as if only one was used. Whole instrument perfectly rigid. Supplied ready for immediate fitting. Construction and finish are well up to the fine Cyldon standard.

Send for particulars of the Cyldon **WAVEMETER**—it identifies unknown stations and makes searching and testing out simplicity itself.



Cyldon TEMPRYTES

The best means of valve control. British-Made and delivered from stock immediately. Can be supplied in correct resistance for any Valve. State resistance (ohms) required, when buying, or be sure to give name of Valve and voltage of Accumulator supplying current to the Valve.

Cyldon Temprytes each 2/6
 Holder mountings each 1/6



*A Name to Conjure
with in the world
of Broadcasting*

HART BATTERIES

ENSURE

*A marked increase in Volume
of tone & freedom from distortion*

says- **DE GROOT**
THE FAMOUS VIOLINIST OF THE
PICCADILLY HOTEL



There are models of "HART"
BATTERIES for all wireless
circuits. Write to-day to
Department W.C.3 for illus-
trated leaflets and full particulars.

THE PICCADILLY HOTEL,
PICCADILLY AND REGENT STREET,
LONDON. W 1.

Messrs. Hart Accumulator Co. Ltd.,
Stratford, E.15.

Dear Sirs,

I have been immensely pleased with the very excellent results of substituting a "HART" High Tension Accumulator for the dry battery previously in use with my wireless set. The reception generally has been tremendously improved, whilst I have also noticed a marked increase of volume of tone and freedom from distortion, which, in the case particularly of delicately phrased musical items, is, of course, a pronounced asset to critical listeners.

I am happy to recommend "HART" High Tension Accumulators as infinitely superior to dry batteries, the relatively short life of which, in my opinion, constitutes not the least of their many disadvantages.

Yours sincerely,

July 21st, 1926.

HART

THE BATTERY OF QUALITY

HART ACCUMULATOR CO.LTD. STRATFORD LONDON E.15

EXPERTS IN RADIO ACOUSTICS SINCE 1908



OLD FRIENDS

THE BRANDOLA

Greater volume with minimum current input. Large diaphragm gives fullness to upper and lower registers. Walnut plinth, electro-plated fittings. *Reduced from ninety shillings.*

75/-

THE TABLE-TALKER

Material used in the construction of goose-neck horn eliminates metallic harshness. Adjustable. Height 18 ins., neutral brown finish, padded base.

30/-

THE AUDIO TRANSFORMERS

Ratio 1 to 5. High amplification of applied voltage, together with straight line amplification frequency curve. Also 2nd stage, 1-3, 1-5 (Black case). 1-3 (Brown case).

17/6

MATCHED TONE HEADPHONES

The synchronised effort of both receivers discovers greater sensitivity and volume and truer tone. Light, comfortable and sturdy

20/-

Brandes

From any reputable Dealer.

BRANDES, LIMITED, 296 REGENT ST., LONDON, W.1

74

Service Advertising

SAFETY FOR YOUR VALVES


THE modern valve holder, as contrasted with the four separate sockets which were common in the past, is designed in such a way that it is difficult to insert a valve incorrectly and burn out the filament by an accidental connection across the high-tension supply. It is, of course, wisest always to disconnect the high-tension battery when moving valves in a receiver, but this is not abso-



Fig. 1.—This method of inserting a valve in its holder will prevent damage to the filament.


lutely necessary if the valves are inserted with due care.

The right way to put a valve in its holder is to grasp the bulb in the hand with the forefinger on the anode leg. The valve is then held at an angle as it is placed in the holder, as indicated in Fig. 1. The tip of the anode leg is inserted in its socket first of all. Then the valve is brought over "level" with the top of the holder, when the remaining legs will drop naturally and easily into their sockets.

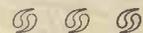

IN the handling of wireless components generally it is not unusual for familiarity to breed, if not contempt, at least a certain amount of carelessness. Coils of the standard plug-in type, for instance, should always be gripped by the plug portion when inserted in or withdrawn from a holder. Care is also needed in handling low-loss coils on "skeleton" formers, since ebonite is notoriously brittle stuff. A skeleton cylindrical former, for example, should preferably be grasped by the ends, if not too long for the span of the hand. Too firm a grip round an interchangeable coil of this type may displace the winding or may even break the former, especially if the coil is tight in its mount and tends to come away rather suddenly when withdrawn.

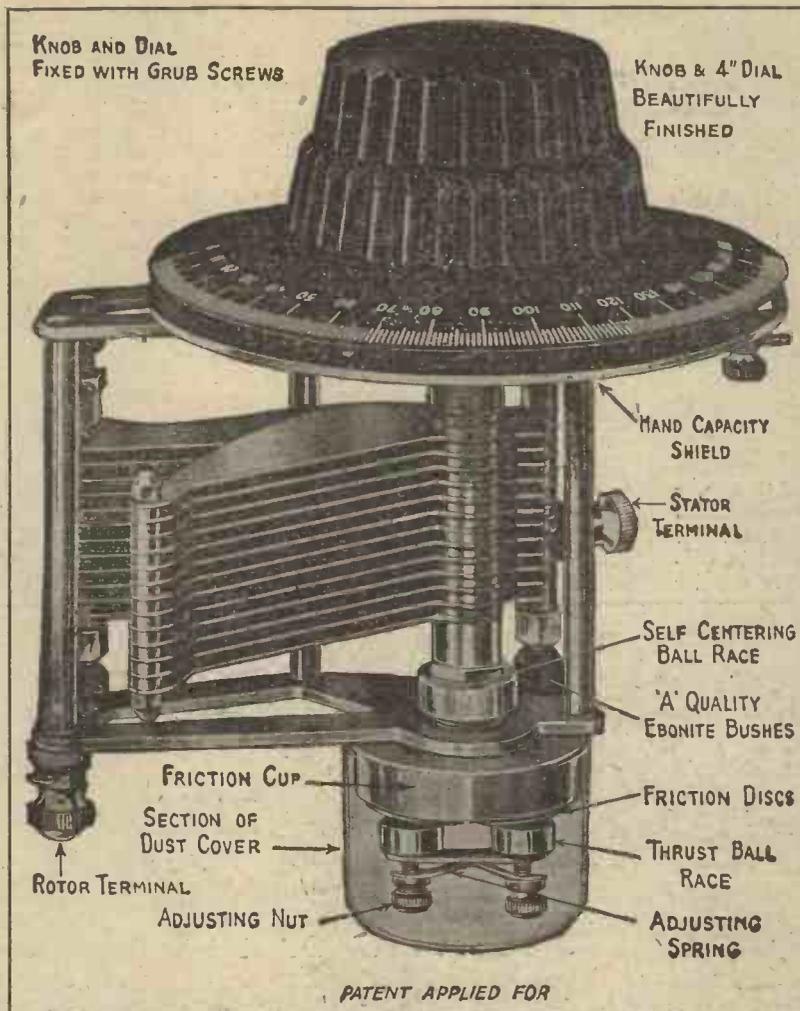Under the heading "An Improvement Worth Trying," on page 1054 of the October issue of THE WIRELESS CONSTRUCTOR, the description of the diagram should read—"The ebonite strip . . . is screwed to the inside of the cabinet."



The New Ormond S.L.F. Condenser Dial

is marked to enable you to pick up any station with the minimum of trouble and without any unnecessary calculations. Precise tuning adjustments with noiseless operation are ensured by the general sound construction of this newest ORMOND S.L.F. CONDENSER. The famous ORMOND SLOW MOTION FRICTION DRIVE (RATIO 55-1) is incorporated, and special ball bearings give liquid-

like movement to every turn of the Knob. This world-famous ORMOND component is easy to mount, having one and three holes for fixing, with both terminals and soldering tags for connections.

Ask any dealer to show you this new ORMOND S.L.F. CONDENSER. It is by far the best condenser to use under the new "Geneva Plan."

Prices:—With 4in. Bakelite Knob—

·005 microfarad	...	20/-
·00035 "	...	19/6
·00025 "	...	19/-
(RATIO 55-1.)		

Obtainable from all dealers



Prices:—With Dual Indicator Dial—

·0005 microfarad	...	21/6
·00035 "	...	21/-
·00025 "	...	20/6
(RATIO 55-1.)		

Obtainable from all dealers.

199-205, PENTONVILLE RD., KING'S CROSS, LONDON, N.1

Telephone: Clerkenwell 9344-5-6.

Telegrams: "Ormondengi, Kincross."

FACTORIES: WHISKIN STREET AND HARDWICK STREET, CLERKENWELL, E.C.1

Continental Agents: Messrs. PETTIGREW & MERRIMAN Ltd., "Phonos House," 2 and 4, Bucknall Street, New Oxford Street, W.C.1

Modern Superheterodyne Practice

WHILE the modern developments in high-frequency amplification have naturally brought before the attention of the public the great merits of neutralised "straight" and reflex circuits in properly designed receivers, the superheterodyne must still rank high in the estimation of many enthusiasts.

Screened Coils

The application of modern methods to the design of a superheterodyne is admirably exemplified in the "Screened - Coil Superheterodyne," described in the October issue of *Modern Wireless*, by Mr. G. P. Kendall. This receiver, which employs eight valves, makes use of the now well-known screening cases, which have been developed by Mr. J. H. Reyner. These cases are used in conjunction with the oscillator coupler

and the intermediate frequency transformers, with the result that interaction between the various parts of the circuit is effectively eliminated. Furthermore, a notable freedom from direct pick-up of long-wave interference is achieved.

Radio Press Star Sets

In the same issue of *Modern Wireless* will be found full operating details for the Elstree "Solodyne" and the "Mewflex," the two Radio Press Star Sets, of which complete constructional articles appeared in the previous issue of *Modern Wireless*. The Elstree "Solodyne" attracted very considerable attention at the Exhibition at Olympia, a fact which is not surprising when it is realised that this receiver has to its credit the loud-speaker reception of fifty broadcasting stations, and that one dial controls all the tuning of the receiver.

The "Mewflex"

With the "Mewflex" forty stations have been recorded on the loud-speaker. This set uses a three-valve neutralised reflex circuit, and incorporates the recently developed methods of reflexing which ensure complete stability of the receiver.

"The Design of Loud-speaker Horns" is the title of a most informative article by Captain H. J. Round, providing much useful data for the practical experimenter.

FREE GIFT WITH "WIRELESS"

With the issue of *Wireless*, the One-Word Weekly, dated October 23, which appears on October 19, a Free Gift Booklet is presented to all readers. You will be wise to secure your copy of this issue as early as possible.

RADIO PRESS STAR SETS



supplied as finished Receivers or in parts ready for home assembly.

Every finished Receiver sold by us bears the signature of **Capt. W. R. TINGEY** (late of Radio Press Research Laboratories).

£5 This is our charge for assembling, wiring, testing and guaranteeing any Radio Press Set. £5
(Any Set installed free within 50 miles of any one of our Branches.)

THE NIGHT HAWK.

Finished instrument aerial tested and guaranteed	£	s.	d.
Set of Kerstone fieldless coils 250/550 metres complete with bases	2	2	0
Other parts required to complete set	9	5	6
"Red Triangle" Ebonite Panel, matted and drilled	0	9	6
Polished Mahogany Cabinet with fall front	3	0	0

THE ELSTREE SOLODYNE.

(Illustrated above).

Finished instrument aerial tested and guaranteed	£	s.	d.
Set of Copex Screened Coils, 250/550 metres	3	11	0
Other parts required to complete the set	10	17	6
"Red Triangle" Panel matted and drilled	0	11	6
Mahogany Panel drilled	0	18	6
Polished Mahogany Cabinet as described	4	5	0

MARCONI ROYALTIES.

In all cases where a finished receiver or a complete set of parts is ordered, Marconi Royalties at the rate of 12/8 per valve holder are payable, and must be added to the prices quoted.

TRY THE ELSTREE SIX

—with Screened Coils—

you'll be delighted with the amazing results.

Finished instrument aerial tested and guaranteed	£	s.	d.
Set of Copex Screened Coils 250/550 Metres with diagram of connections	32	5	6
Other parts required to complete the set	5	0	0
Polished Mahogany Cabinet with drilled panel and baseboard	16	5	6
	6	0	0

Send for a copy of the Pilot Manual, which contains full details of a number of Radio Press sets. Much useful advice on assembling, wiring, testing, etc., is also given. Post free, 3d.

PETO-SCOTT CO., LTD.

77, City Road, LONDON, E.C.1.

BRANCHES: 62, High Holborn, London, W.C.1.
Walthamstow: 230, Wood Street.
Plymouth: 4, Bank of England Place.
Liverpool: 4, Manchester Street.

COPEX COPPER SHIELDED COILS



Copied by many—equalled by none!

The chief advantages of the Copex Copper Coil Screen and Base over the imitations now on the market are as follows:—

- (1) High grade copper is used for the screen—other metals cannot give the same degree of efficiency.
- (2) Copex Screens are sprung on to the copper base, thus ensuring perfect electrical contact.
- (3) Copex Shrouds may be revolved on the base, thus giving a self-cleaning contact.
- (4) Copex Screens are mounted on bases cut from best quality ebonite and highly polished.
- (5) In appearance alone, Copex Coil Screens excel all others. The highly polished and lacquered copper screen is untarnishable.
- (6) All Copex Coils and Transformers are matched within 1 metre, each coil being checked several times during the process of manufacture against a quartz oscillator the accuracy of which is well known.

Copex Copper Shroud and Interchangeable 6-pin base (Patent applied for) 15/-

Interchangeable Coils and Transformers (usual prices).

INTERCHANGEABLE COILS.

	B.B.C.	5XX
250/550 metres	1,000/2,000 metres	
6/- each	6/- each	

Tapped Primary Aerial Coils	10/-	10/-
H.F. Transformers (Split Primary and reaction)	10/-	10/-
Split Secondary H.F. Transformers	10/-	10/-
Reinartz Transformers	10/-	14/-

STOP PRESS

This Month's Set:

THE "SPANSACE THREE."

Finished instrument, aerial tested and guaranteed	£	s.	d.
Complete Kit of Components	13	16	6
"Red Triangle" Panel, matted and drilled	6	16	6
Polished Mahogany Cabinet with baseboard	1	10	0

All the parts for the Midget Reflex Set described in the Gift envelope given with this issue are now available. Write for prices.

SEE OUR IMPORTANT ANNOUNCEMENT ON PAGE 45.

P.S. 5822

TESTIMONIALS:

From R. Barker, Esq., Ivy-bridge, Stanley, near Woking, Yorks.

24th September, 1926. "When passing through London last Saturday, I called at your shop and bought one of your 'KAY RAY' L.F. Transformers. On placing it against two British models, one at 25/- and the other at 17/6, I am glad to report an increase in volume—moreover, the tone is equally pure.

"On showing the Transformer to friends, I am pleased to say that they were delighted and are going to put them in their own sets. I herewith enclose you order for two 5-1 ratio. "In closing, I would like to congratulate you on your Establishment. I have seen many Northern Wireless Shops, but none such as yours with such stock, Bargains, or service. I can assure you that all our further orders will go to Raymonds.

"(Signed) B. BARKER."

From J. M. Haines, M.L.E.E., 33, Retreat Road, Hackney, E.3.

24th September, 1926. "I have two of your .0005 Low Loss S.L.F. at present giving excellent results. I put them in my Set in place of two condensers of a very reputable maker and increased the selectivity 100 per cent. You may see this testimonial (entirely unsolicited) as you wish.

"(Signed) J. M. HAINES."

382, Cranbrook Road, Ilford, Essex.

"Messrs. Raymond, "I am writing to let you know the wonderful change your new type condenser has made in my one valve Straight set. "On Sunday evening (with 2LD working) I was successful in receiving Radio 10, Berlin, Durlin, Hamburg and Newcastle at excellent phone strength. All these stations had previously passed me by.

"I can only say that if there is a 100 per cent. condenser on the market, yours is it.

"HARRY L. PROCKTER."

29, Barrington Road, Brixton, S.W.9. 30th September, 1926.

"May I be allowed to congratulate you on the wonderful 2 valve set which you are selling for 43/10s. Gd. complete. "I was fortunate enough to purchase one of these sets this week, and after very thorough tests it has proved to be perfect in every detail, giving very fine clear results, and I shall be only too pleased to recommend this set to all my friends.

"Yours faithfully, "JOHN F. DREW."

TRIPLE GANG CONDENSERS CLYDON .. 70/- Dial extra.

LISSEN ALL LISSON GOODS NETT PRICES. West-End Distributor. Postage extra.

Lissenola, 13/6. L.F. Transformer, 8/6. 35 ohm Rheostat, 2/6. H.F. or L.F. Choke, 10/-.

BEFORE YOU PURCHASE ELSEWHERE: CALL AND LET ME QUOTE YOU.

SPECIAL PRICES given over the counter for sets or parts of various circuits. Any parts you have no use for entertained in exchange for purchased. Goods may be brought without obligation either side.

Place of Payment—27, LISLE STREET, W.C.2.

Sets for the Million.



Sets complete with the following accessories—Long distance 2-valve L.F. and Detector Receiver in handsome polished cabinet; includes set as shown, 1 power, 1.06 D.E. valves, tuning coils, H.T. 100 volt, L.T. 3, Aerial Equipment, H.T. and L.T. Leads, 2 pairs of 4,000 ohms 'phones, or LOUD SPEAKER (Marconi Tax Paid).

Also new circuit specially adapted for use with indoor aerials. Specification as above, 25/10s. Carriage and Packing, 6/-.

WONDERFUL 3-VALVE SETS. In handsome American cabinet; Royalty paid, all complete, including Aerial, Coils, Batteries, grand Loud Speaker, Valves .06 1 Power, ready to fit, 28/18/6. Everything of the very best. Carriage, 7/8 extra.

SEND STAMPED ENVELOPE FOR PARTICULARS OF DEFERRED PAYMENT SCHEME.

RADIO MICRO VALVES. .06, 3 v. 6/11; 25, 2 v. 6/11; Power .3, 8/6; Power 1, 9/11. (Power are 3.4 volts.) Phillips 4 Electrode, 4 pin for Unidyne, 8/11. Post, 6d. each.

ADICO BATTERIES (H.T.). Highest award. Trade Test, 60 volt, 6/11; 100 volt, 13/11. Not sent by post. The 100 volt is specially suitable for 2LD sets.

MARCONIPHONE.—Auto Series Par. Variometer, 16/-.

"J.B."—All lines stocked. S.L.F. (Brass). .0005, 11/6; .00035, 10/6; post, 6d.—set.

WATNEL PRODUCTS. .0002 or .0003 and Grid Leak, 2/6.

COIL STANDS.—Lotus 2-way, 7/-; 3-way, 10/6; (extension handles extra). Polar 2-way, 9/-; 3-way, 9/6.

WEST END DEPOT FOR "MAGNUM" (Burne Jones).

"SUPER" ONE VALVE SET works loud speaker fine; demonstration free! Set, including Tax, 49/6. Complete with valve, batteries, coils, aerial, Loud speaker, 79/6. Carriage, 5/-.


STAR COILS. Mounted centre tapped. 25, 35, 1/6 each; 50, 1/8; 75, 2/-; 100, 2/3; 150, 2/8; 200, 2/50, 3/0; 3/- each; 400, 3/3; 500, 3/6. "T" (Reinartz Circuit). B.B.C. 2/8; 5X2, 3/3. Other sizes stocked.

INDUCTANCE COILS. All wave lengths. H.P. CROCK 3/3. Post Extra.

BURNE JONES (MAGNUM) Screened coils, as delivered. Baseboard, N. Condensers, 5/-.

SETS OF PARTS. ELSTRELEX. SOLODYNE. ELSTREX SIX. MAGIC FIVE. NEWFLEX. 1927 FIVE. Two Valve Reinartz. Slight delay screened coils.

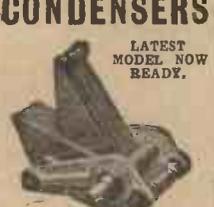KAY RAY WONDERFUL VALUE IN STRAIGHT LINE FREQUENCY CONDENSERS



WITH KNOB AND DIAL. Post 6d. Set. .0005, .0003 .. 7/11 each

THE CONDENSER OF THE FUTURE. S.L.F.



LOW LOSS, including knob and dial as sketch, Brass Vanes, Centre Rotar. .0003, 6/11 .. .0005, 7/11. Vernier 1/- extra. Post 6d. Set.

SPECIALS (ALL POST EXTRA). SCREENED COILS with base, by Burne-Jones, Magnum, and Lewcos. All Orders in Rotation.

GRAHAM-FARISH, WEST END DISTRIBUTOR OF THEIR WONDERFUL PRODUCTS.

Fixed Condensers, 1/ 1/8; .0003 and Grid Leak, 2/- for Series and parallel; Grid Leaks, 1/3 each.

Sold on Money Back Guarantee.

Detex Calibro Dials, 5/9; Detex Verno Dials, 4/6; Ecco H.T. Units, 5/5; Igranic Tone Control, 5/3; Star "T" Coils for Reinartz, B.B.C., 2/6; 5 XX, 3/6; Ormond Neutralizing, 4/- (for Base or Panel).

AMPLION. LARGE STOCKS OF LOUD SPEAKERS. 38/-, 48/-, 68/-.

BROWN'S LOUD SPEAKERS. Type H4, 30/-; Type H3, 60/-.

CLAR.TONE. The World's Best, 50/- All carriage extra.

RADIO MICRO "SAXIR," 5/8. 2,000 ohms.

PHILLIPS "TETRODE." 4 Electrode Valve, Double Grid, for one valve Loud Speaker, Sets, 8/11. Post 6d. ea.

VARIABLE CONDENSERS.—Folr Standard, 0/6. Junior, 5/8 each. Bowyer-Lowe Popular, 10/6. Igranic, 24/-, 21/-.

R.I. Multi Ratio, L.F., 27/6; Standard Model, 25/-.

FINE BRITISH VALVES: Smash High Prices!! PURATONE (RUBEN) 2 volt. .06 6/11 3-35 6/11 Post 1/- each

ACCUMULATORS.—2 v. 40, 7/11; 2 v. 60, 9/6; 2 v. 80, 12/8; 2 v. 100, 14/6; 4 v. 40, 13/11, 4 v. 60, 17/11; 4 v. 80, 26/6; 6 v. 60, 28/6; 6 v. 80, 35/6. ALSO another good make, 1/6 extra on each of above. Post 1/-

IN STOCK ALL NEWEST MAKES OF VALVES. We give you immediate benefit of makers' reductions in price.

VALVES.—Cosmos S.F.18 Red or Green, 14/-; New Blue Spot, 14/-; All Mullard, Ediswan, Osram, Marconi, Cossor stocked. Bright D.E. and Power, 8/-, 14/-, 18/6, 22/6, 24/6, 30/-, 32, Mullard P.M.4, 18/6. Do. P.M.3, 15/6. 4/11.

FIXED CONDENSERS.—Dublier, .0001 2, 3, 4, 5, each 2/6. .001, 2, 3, 4, 5, 6 each 3/-.

L.F. TRANSFORMERS.—Ferranti A.F.3, 25/-; A.F.4, 17/6; Eureka Control, 25/-; 2nd Stage 21/-; Baby 1st or 2nd, 15/-; Reflex, 15/-; Formo shrouded, 10/6. Success (Black), 21/-.

Grand Value in NON-MICROPHONIC VALVE HOLDERS. Board Mounting, 1/6.

SUNDRIES. Newey 2-way geared coil-stant, 6/8, 4-point condenser, 17/6, 15/-.

LOW LOSS SQUARE LAW This variable Condenser is simply marvelous value. It cannot be equalled in price or quality.

RECOGNISED WEST END DISTRIBUTOR of the manufactures of Edison Bell, Jackson's (JB) Polar, Igranic, Peerless, Eureka, Magnum, Burnpelt, Lotus, Dubliner, Marconi, Dorwood, Sterling, Success, B.H. Michael, Lissen, Dilly, R.I., Bowyer-Lowe, Formo, Brunet, Ormond, Newey, P. and M., T.C.C., etc., etc.

ORDERS BY POST MUST BE ACCOMPANIED BY SUFFICIENT TO PAY POSTAL CHARGES.

Ormond Products. SQUARE LAW LOW-LOSS. .0005, 9/6. .0003, 8/6 (1/8 each less vernier). FRICTION GEARED, .0005, 15/-; .0003, 14/6; .00025, 13/6. STRAIGHT LINE FREQUENCY FRICTION GEARED, .0005, 20/-; .00035, 19/6. S.L.F. .0005, 12/-; .00025, 11/-.

OUR NOTED ONE VALVE and CRYSTAL SET, in solid polished cabinet, complete with valves, 'phones, H.T. and L.T. Units, Aerial Equipment, Daventry Coil. Extraordinary value, 45/11. Carriage, 2/-.

ASTOUNDING 2 Valve AM-VALUE IN L.F. amplifier, 25/11. Amplifiers in or COMPLETE hands ome with valves, polished box, H.T. and L.T. 1 valve, 16/11. Units, 4/6. Carriage, 1/6. Carriage, 2/-.

EVERYTHING in Demand Stocked for Wireless.

IGRANIC TRIPLE - HONEY-COMB INDUCTANCE COILS. 30, 2/8; 40, 2/8; 50, 2/8; 60, 3/3; 75, 3/8; 100, 3/6; 150, 3/3; 200, 4/-; 250, 4/6; 300, 4/8; 400, 5/8; 600, 7/-; 750, 9/8; 1,250, 14/-; 1,500, 18/-.

ASHLEY PLUGS AND JACKS.—Fit panels 4 to 1/2 thick, one hole using S.C.C., 1/3; S.C.C., 1/8; D.C., 1/9; F.S.C., 1/9; F.D.C., 2/3; Phone Plugs, 1/6. Post extra.

EXIDE H.T. ACCUMULATORS. 20 v. Unit, 15/- (not sent by post).

H.T. BATTERIES. EVEREADY 60 v., 12/6; 108 v., 21/-, L.T. 3 or D.E. Valves, 7/6.

HEADPHONES All 4,000 ohms. N. & K. STANDARD PATERN 'PHONES, Super Tone 4,000 ohms. Special Price, 7/11 pair. N. & K. GENUINE New lightweight, 11/6. Extra quality do., 13/6.

BRITISH HEADPHONES. BROWN'S FEATHERWEIGHT 20-1. BROWN'S A TYPE (Red), 80/-; B.H. 20-1. STERLING, 80/-; WESTERN ELECTRIC, 20/-.

SEE K. RAYMOND'S NAME ON PREMISES, THIS WILL ASSURE YOU GETTING THE GOODS I ADVERTISE. PLEASE ASK "IS THIS RAYMOND'S?"

GALLER'S COLUMN NOT SENT BY POST.

Switch Spade Terminals for H.T., L.T., etc., 1/6 pair. Spade tags, 6 a 1d. Spade screws, 6 for 14d., 6 a 1d. Black, 3d. pair. Ins. staples, 5 a 1d. Ormond screws and nuts, 2 a 1d. Switch arms and studs, 1/-, Nickel, 1/4. Wanger plugs, 2d., 3d., 4d. pair. Plug and socket, red and black, 6d. to 1/- pair. Twin Fife, red and black, 12 yds., 1/6. Minature S.H.C., 6d., Ins. hooks or egg insulators, 2 for 1d. Aerial wire, 7/22, 100 ft., 1/11. Extra heavy weight, 2/3. Stranded aerial, 100 ft. (49 strands), 1/3. D.C.C. wire, per 1 lb. reel, 20 g., 9d., 22 g., 10d., 24 g., 11d., 26 g., 1/-, 28 g., 1/1. Tinned copper, 17/6 for 1 lb. Bus bar, 12 ft., 6d. Empty tape, 12 yds., 6d. Earth Tubes, Copper, good value, 1/1. Chimney, 2/3, 5/-.

SPECIAL OFFER in Oak American Type, hinged lid, Carbamide, with baseboard for 12 by 7 panels, 8 in. back to front, 9/6. Also 12 by 9, 10/11; 16 by 8, 16/11.

INDOOR AERIALS.—Wire 40 Stranded Length, 12 ft., width, 4 in. Ebonite Insulators, complete with rubber rings, ready to fix up, 4/6.

VARIOMETERS FOR B.B.C.—Handsome Model, Ball Rotar, Ebonite, Ferranti wound, D.C.C. Grand Value, 1/9. Both with knob.

SWITCHES.—D.P.D.T. panel 1/-; S.F.D.T. panel, 9d. On and off switch, 1/-; Double Switch, 2/6; Tumbler, 1/-; Push and Pull, 1/-.

CRYSTAL SETS.—Handsome design, for local or Daventry Station. Everything complete, ready to fix up, 18/11. Comprises Set, Coils, Head-phones, Aerial Equipment.

BATTERY BOXES. 63 v.—Metal, take 14 batteries, 3/6. Fitted Cups, Battery Testers, 4d. Bulls-eye Bulbs, 3d., 6 for 1/3.

FRONITE PANELS 3/16.—For Crystal Sets, 6 by 6 1/2; 7 by 6, 1/2; 8 by 6, 1/6; 9 by 6, 1/6.

BROWNIE NO. 2.—Latest model, 10/6. Complete with pair of high-class phones, 4,000 ohms, value 8/11. Aerial wire, lead-in, Daventry Coil, the lot, 18/11.

SUNDRIES.—Adhesive Tape (black), 41d. Set of 8 drills, 1/3. Set of 5 Spanners, 6d. Set of Taps, 1/11 (O.B.A. 2, 4, 6 B.A.). Screwdrivers, 6d. Soldering Irons, 8d. 2 B.A., Rod, 21d. Wanger Plugs, pair, 21d. Extra quality, pair, 41d. and 6d. Valve windows, 8d. Basket Holders, 10d. Extra quality, 1/-.

D.E.T. BATTERIES.—Crown Polo 60 v., 9/11; Grid Bias, 9 volts, Tapped 11 v., 1/3, 1/6. All well-known makes stocked.

L.F. TRANSFORMERS.—Standard Ormond, 13/11; "Kay Ray," 5-1, 11/8; Croix, 5-1, 4/6; Wates' Super pattern, 7/11.


BRASS PARTS, ETC.—Terminal nuts and washers, W.O. Pillar, phone, doz., 1/-, Nickel Ditto, doz., 1/4. Studs complete, 2 by 1/2, doz., 6d.

BARGAIN DEPT. Huge quantities of window-rolled and rods which have been taken in exchange for sale at ridiculous prices. Bargains not sent by post. ABOVE CALLERS ONLY.

K. RAYMOND 27 and 28a, LISLE STREET, LEICESTER SQUARE, W.C.2. OPPOSITE DALY'S GALLERY DOOR. OPEN: 9 to 8 Daily. 9 to 9 Saturday. 11 to 1 Sunday. Phone: Gerard 4637.

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.

A USEFUL HINT

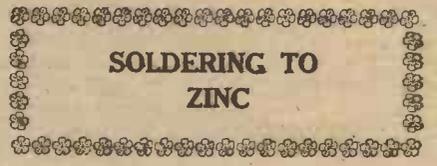

SOLDERING TO ZINC

CONSTRUCTORS who have tried to solder wires to zinc tags, as for instance when making the connections between the cells of a home-made Léclanché battery, will very likely have found that it is not at all easy to avoid melting the zinc tags. This difficulty also applies when soldering on connections to the zinc containers of dry battery cells, such as are used for grid or high-tension batteries. If the soldering iron is hot enough to do its work quickly, the least touch of it on the zinc will usually melt the latter, while if it is cooler the solder will not run.

Preparing the Zinc

Special fluxes may be obtained for soldering to zinc, but in default of these one of the usual paste fluxes, such as Fluxite, will be found quite suitable. Resin is not much use for this work.

To solder a wire to zinc without any danger of melting it, the following procedure may be adopted. Clean the surface of the zinc with a piece of emery cloth and put on it a trace of flux. Then make the soldering iron quite hot and apply the stick of solder to its tinned face until quite a large blob has run on to it.

The Point to Watch

Now bring the blob of solder on the iron into contact with the cleaned surface of the zinc, being very careful to let only the blob of solder, and not the iron itself, come into contact with the zinc. In a few seconds the solder will run on to the zinc and take. The connecting wire may then be tinned and placed in position on the zinc, when a further application of the iron in exactly the same way as before, the solder blob being the only thing to touch the zinc, will result in a good joint being made. There will be no danger of the zinc melting even if the iron is held close to it for some time, so long as it does not come into actual contact with it.

A. V. D. H.

In the table of "Drill Sizes" given on the concluding page of the Free Gift Booklet, "How to Build Your Own Wireless Set," presented with the last issue of THE WIRELESS CONSTRUCTOR, the third heading, "Tapping Size, Morse or ins.," should read "Clearing Size, Morse or ins."



Patent Nos. 238003. 223625 and pending.



Sir Oliver Lodge

LODGE
N'
CIRCUIT

IMPORTANT
NOTICE

Having acquired the World Rights for Sir Oliver Lodge's famous "N" Circuit we desire to state that we assume all responsibility under the CLEARTRON Ironclad Guarantee for the performance of all sets made by us or in accordance with the diagrams furnished with CLEARTRON-Lodge "N" Constructor Kits containing the components selected and approved by the inventors—and royalty paid. Any sets made up otherwise than in accordance with the foregoing carry no guarantee, and no authorisation of Sir Oliver Lodge. Unless the "Lodge" royalty is paid the manufacture of these Circuits constitutes an infringement of the Lodge Patents owned by "CLEARTRON."


CHIEF FEATURES:

Non-radiating,
Non-interfering.
Great volume,
Extreme purity,
Keenly selective,
Highly sensitive.

Also
Home
Constructor Kits
complete

2-Valve - £6.6.0
3-Valve - £8.8.0
plus Royalties and
Valves.

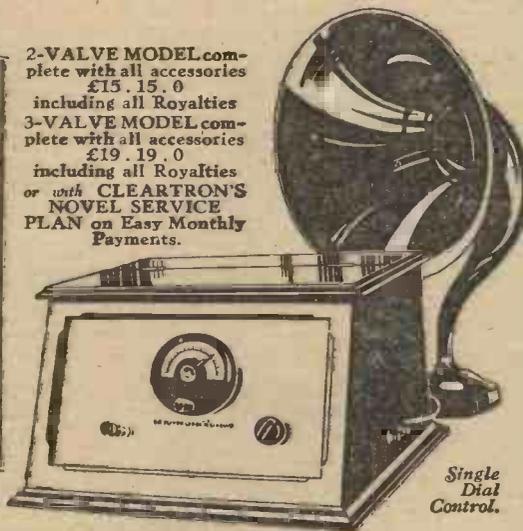2-VALVE MODEL complete with all accessories £15.15.0 including all Royalties
3-VALVE MODEL complete with all accessories £19.19.0 including all Royalties
or with CLEARTRON'S NOVEL SERVICE PLAN on Easy Monthly Payments.



Single
Dial
Control.

Send for Lodge "N" Booklet post free.

All LODGE "N" CIRCUITS are fitted with

CLEARTRON NEW MODEL VALVES
1926/27

and backed by Cleartron's Ironclad Guarantee.

CLEARTRON RADIO LTD

ONE, CHARING CROSS, LONDON, S.W.1.
Telephone: Regent 2231/2.

Works: Birmingham
Telegrams: "Cleartron, Westrand, London"

C.T.53.

The New Combination Lotus Grid Leak and Buoyancy Valve Holder



Pro. Pat. 20339
Pat. 256833

The Grid Leak is not discernible, being totally enclosed in Bakelite Valve Holder Base.

Yet Another LOTUS Triumph in Component Design

Like all other LOTUS Components, the new Combination Grid Leak and Valve Holder is guaranteed efficient in construction and design. It eliminates unnecessary wiring and soldering, and makes for economy in cost and space.

Ordinary Terminal Valve Holder, 2s. 6d. Combination Grid Leak and terminal Valve Holder, 3s. 9d.
Without terminals, 2s. 3d.

All Anti-Microphonic Type.

LOTUS


Combination GRID LEAK AND BUOYANCY VALVE HOLDER Anti-Microphonic.

From all Radio Dealers. Write for List.

Garnett, Whiteley & Co., Ltd.

Lotus Works, Broadgreen Road, Liverpool.
Makers of the famous Vernier Coil Holders.

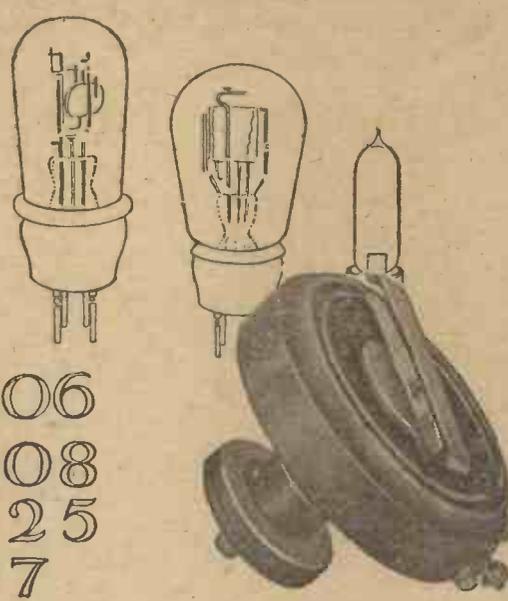Ericsson Ericsson Ericsson Ericsson Ericsson



- 06
- 08
- 25
- 7

—the Ericsson Dual Rheostat controls them all!



For wonderfully powerful amplification, fit Ericsson Transformers. Made in a handy size for convenience in constructing. Made in two ratios. 1:2, 1:4. Guaranteed free from distortion.

Don't be tied down to one type of valve—put Ericsson Dual Rheostats on your panel. Then you can use any type, any amperage with the certainty that they will at the same time get the proper amount of "juice," and yet be free from the over-running danger. A beautifully made piece of apparatus—velvety, smooth in action—complete with knob, dial pointer and fixing screws. As fitted on most up-to-date modern sets. Fit them on yours to-day. Price 8/6 at all good dealers. If unable to obtain locally write us to-day sending name of dealer.

17/6

ERICSSON TELEPHONES, Ltd.
67/73, Kingsway, London, W.C.2

Ericsson

COMPONENTS.

Ericsson Ericsson Ericsson Ericsson Ericsson


There are three kinds of Variable Condensers

—here are the results you'll get from each

No. 1 Ordinary Condenser

(Straight line capacity)

The ordinary Variable Condenser as used in the vast majority of Wireless sets jumbles together no less than 51 wavelengths (of 10 kilocycles separation) in the first 15 degrees of dial setting; while the remaining 85 degrees of the dial cover only 49 wavelengths. This might have been good enough in the early days when any sort of reception was gratefully received. But science has moved since then and there is no longer any need for your set to remain an obsolete jumble of conflicting and jamming stations.

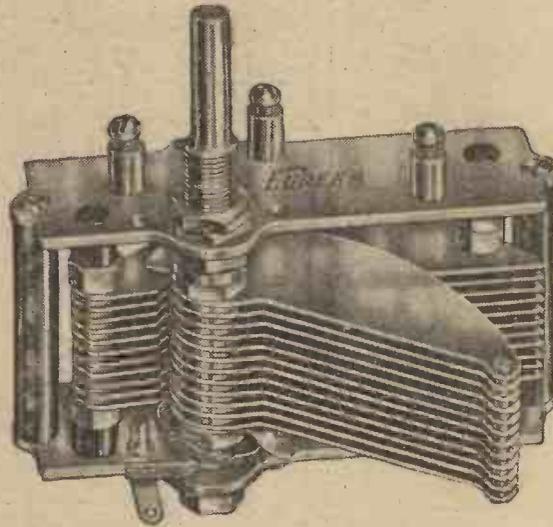

No. 2 Square Law Condenser

(Straight line Wave-length)

The square law condenser made a serious—if not very successful—attempt to overcome this aerial traffic tangle. But even this type of condenser bundles together into the first 15 degrees no less than 36 wave lengths (nearly 2½ stations to every degree of dial setting) and thus falls far short of solving the tuning riddle with which every ambitious Set user is confronted. As a proof of this it should not be forgotten that square law condensers have been available on the market for more than a year—yet selection has been just as difficult to obtain.

—and the Eureka Ortho-cyclic

NOW comes the new principle of tuning by which, with the Eureka Ortho-cyclic Condenser, a definite separation of wavelengths evenly and exactly over the whole scale is accomplished. By this new principle of design each movement of one degree of dial setting (with 100° dial)

gives a definite separation of ten kilocycles over the whole scale.

Thus, instead of 51 conflicting wavelengths in the first 15 degrees, you get exactly 15 wave lengths in 15 degrees. And so on, right through the scale, the same exactitude of station separation is maintained

In this way scrambling and crowding of stations is entirely eliminated; tuning is made easier, more regular and more certain. Vernier plates are rendered obsolete and the danger of stations heterodyning each other at the cost of purity in your reception is materially reduced.

Which kind does your Set deserve?

IF you possess a Set capable of receiving distant stations, that Set deserves Eureka Ortho-cyclics. The true pleasures of distant reception are only possible where the Ortho-cyclic principle of tuning is employed. Take out your obsolete Condensers and replace them with these beautifully made Eureka Ortho-cyclics. Owing to their compactness they require

only a panel depth of 2 inches—they can be fitted in a few minutes by either one-hole fixing or four-point mounting, whichever method you prefer. Ball-bearing—superbly finished—they represent a standard of efficiency far in advance of present-day levels. Ask your Dealer to show you one—you'll be proud to see such an outstanding example of British workmanship.

Prices:

- 0003 mfd 14/6
- 0005 mfd 15/6


EUREKA

ORTHO-CYCLIC

Equip your Set also with Eureka Transformers and Coils.

Manufactured only by Portable Utilities Co. Ltd. (Eureka Radio Products) 8 Fisher Street, W.C.1

WORKSHOP HINTS FOR THE HOME CONSTRUCTOR

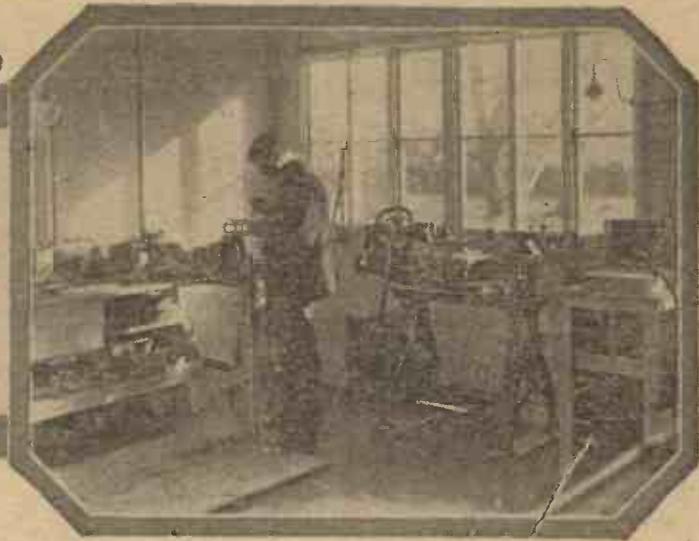

The Soldering Question—A Fine Keyhole Saw—For Slow-motion Dials—Countersinks—Useful Gauges.

THE SOLDERING QUESTION

CONSTRUCTORS of wireless gear are divided at present into two camps, one of which favours soldered joints whilst the other is strongly opposed to their use. Though I was at one time a strong supporter of the use of solder wherever possible for making joints, I must confess that my faith in this form of connection has slowly waned. Theoretically it would seem that for connections in high-frequency circuits, at any rate, where it is essential to eliminate all possible sources of resistance, the soldered joint should be superior to the screw-down connection. In the perfect soldered joint there should be an amalgamation between the surfaces of the metals and the solder itself, and a connection of very low resistance

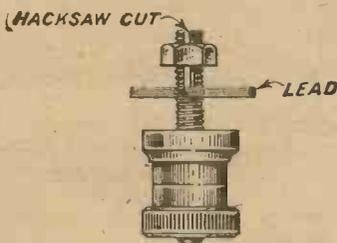


Fig. 1.—This method of adapting a terminal for connections is easiest with 2 B.A. shanks.

should result. There can be little doubt that this actually takes place when the joint is first made, but the most important question is—how long does this almost ideal state endure?

Deterioration

The other day I undertook the job of dismantling a receiving set made two or three years ago in which solder had been used throughout, resin having

been employed as a flux. One would have expected to find the joints in perfect condition, but this is far from what had happened. There was no need to use a hot soldering iron in order to disconnect leads from the tips of terminals or even from other wires; only a small amount of force was actually needed to pull them apart; there was in fact hardly a joint that could be classed as sound in the whole piece of apparatus. But I would like to emphasise the fact that the surfaces had been properly cleaned before soldering was done, that a hot iron had been used, that the flux was of the least "active" kind, and that all were originally thoroughly good joints.

Chemical Action

Yet when they were pulled apart it was clear that the majority of them were in a thoroughly unsatisfactory condition from a wireless point of view. The solder was white and powdery looking, and it was obvious that chemical action had taken place. I have no doubt that many readers must have come across instances of receiving sets falling off in their performances when they have been in use for some time. Such a falling off is often ascribed to a variety of causes, such as the deterioration of the ebonite under the influence of light, the formation on insulating surfaces of a semi-conducting coating of dust mingled with moisture and the like. When, however, a receiving set shows signs of declining sensitiveness, of a loss of selectivity and of kindred symptoms, it can often be restored to its original efficiency by the simple process of applying a hot iron to each of the soldered joints, so that the solder is made to run and afterwards allowed to set again. This seems pretty conclusive proof that the soldered joint is hardly stable enough

for use in wireless apparatus where long service is expected.

When one comes to think of it, it is not surprising that action should take place in time in a soldered joint, since so many dissimilar metals are involved. In the solder itself we have lead and tin, whilst if we fix a wire to a terminal we are dealing with copper in the wire itself and with an alloy of copper and zinc in the brass terminal. In the finished joint there are thus lead, tin, copper and zinc, all of them probably containing slight impurities and possibly traces of yet other metals.

What Can We Substitute?

If we condemn soldering for wireless purposes, what are we to substitute in its stead? My own belief is that in the near future we shall probably employ spot-welding. There is no reason why a simple little apparatus enabling the home constructor to carry

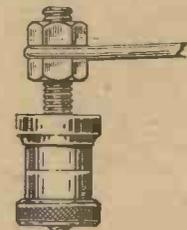


Fig. 2.—A closed loop at the end of the wire gripped tightly between two nuts makes a good connection.

out this highly efficient form of jointing should not become available, but at present it is a job that comparatively few readers will be able to undertake. Meantime, a method which I have found very satisfactory is that seen in Fig. 1. The shank of the terminal is split for about half an inch down from its point by means of a jeweller's or dentist's hacksaw. A nut is then started on the threads and the

Utility

GUARANTEED

COMPONENTS are always dependable

Although the well-known "Utility" Components have been greatly reduced in price, users can implicitly depend upon their efficiency and satisfactory service. The "Utility" Specialities on view at the recent National Radio Exhibition completely demonstrated their superiority in soundness of workmanship, quality of material, and utility of design.

And, remember, our guarantee to repair or replace defective parts free of charge still maintains.



"Utility"
Low Loss Condensers

All brass parts are nickel-plated. Pigtail connection from moving plates, terminals and soldering lugs are fitted, and the centre spindle rotates on ball bearings. The Vernier pattern is fitted with a Micro-Dial as illustrated below.

Prices from :
Vernier Pattern - - 13/-
(0002 MF) - - 7/6
Without Vernier - - 7/6
(0002 MF)



"Utility"
Push-Pull Switch

A switch of the push-pull type with the advantages of our well-known "Utility" switch. Its low capacity, smooth action, and perfect contact ensure highest efficiency. One-hole fixing, two-pole change-over.

Price 4/6



"Utility"
Micro-Dial

A handsome 4in. Dial in which is incorporated the Slow Motion mechanism for obtaining the finest tuning of the Condenser. The Dial itself gives coarse adjustment, and the gear ratio is 70:3. Backlash is entirely eliminated.

Price 7/6



"Utility"
Jack and Plug

A Jack designed on the same principles as our popular "Utility" Switch, and similar to our Push-Pull Switch in size. It has many advantages over the ordinary type of Jack. Perfect rubbing contact and low self-capacity.

Prices: Jack 4/6, Plug 2/6

All Go-Ahead Dealers stock "Utility."
Ask for particulars.

WILKINS & WRIGHT LTD

KENYON ST.



BIRMINGHAM

WHY AN AERIAL?

THE CURTIS DOUBLE SUPER HET. 8 CIRCUIT GUARANTEES

FULL LOUD SPEAKER STRENGTH WITH PERFECT TONAL REPRODUCTION FROM ALL EUROPEAN BROADCASTING STATIONS WITH
A FRAME AERIAL.

2 RECEIVERS IN ONE:—

A REGENERATIVE CIRCUIT of two or three Valves for Loud Speaker reproduction from Local Station.

A SUPER HETRODYNE CIRCUIT of 7 or 8 Valves for Loud Speaker Reproduction of long distance reception,

Either circuit brought automatically into operation by a single switch.

AUTOMATIC TUNING. NO SEARCHING.

WE GUARANTEE

Every home constructed Curtis Super Het. to operate with equal efficiency of our Standard Models, provided our chart and schedule have been adhered to—**THEN**

BUILD YOUR OWN

CURTIS DOUBLE SUPER HET. 8

WITH



The Curtis Intermediate Unit

4 VALVE, 3 IF and 1 FILTER - £7 10 0.

The Curtis Intermediate Unit is a complete component consisting of the intermediate frequency and filter transformers, with corresponding valve sockets and accessories. Wired up, boxed, tested and matched ready for use.

WE HAVE BUILT THE SUPER-HET. FOR YOU. Home Constructor's Treatise, Price 2/6

- contains :
1. Circuit Diagrams. 2. Simplified lay-out and wiring chart.
3. Instructions for operation. 4. Complete schedule of components.

1926-1927 CATALOGUES OF DUODYNE AND CURTIS RECEIVERS AND COMPONENTS FREE ON REQUEST.


PETER CURTIS, LTD.

11, RED LION SQUARE, W.C.1
Telephone—Chancery 7543-4. Telegrams—"Paracurtex."
MANCHESTER 312, DEANSGATE.
Telephone—Central 5095.

Workshop Hints—continued

lead is passed through the slot. As the nut is tightened down the edges of the slot are pinched firmly on to the lead, holding it in a grip that is literally vice-like. Where 4 B.A. terminals are used, rather a fine gauge of wire must be employed for making

connections, but with 2 B.A. terminals it is possible to make the cut with an ordinary hacksaw and to use fairly stout wire. A simpler connection consists in making at the end of the lead a loop which is a fairly tight fit for the shank of the terminal. This is placed between two nuts, which are tightly locked together. In making this connection hold the lower nut with a flat spanner and turn the upper one hard down with a box spanner.

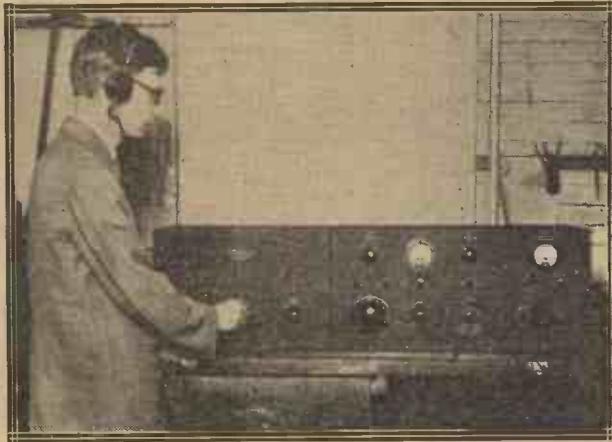

With the assistance of powerful transmitting stations in various parts of the world, longitudes may be checked with great accuracy. This photograph shows the receiver to be used for this work at San Diego, California.



An Excellent Tool

The effectiveness of the tool so made surpassed all expectations, for it

enabled the work to be done with almost incredible ease and quickness. These keen little blades go through ebonite almost like a wire through cheese. Buckling may occur if you are not careful, but a bent blade can

denser. This fact makes some of these excellent dials rather difficult to use for short-wave work. A simple method of overcoming the difficulty is that seen in Fig. 3. The knob is removed and placed boss-uppermost in the drill vice. A No. 33 drill is then carefully centred in the recess made for the spindle and is run right through. The hole so made is tapped 4 B.A. Into this is screwed a short length of 4 B.A. studding, which must not be allowed to project so far into the recess as to prevent the knob from going properly on to its spindle. The studding is locked in place by means of a nut. In one end of a piece of 1/2-inch round ebonite rod a central 4 B.A. tapped hole is made, after which the rod is screwed tightly on to the projecting end of the studding. If desired, a short piece of 2 B.A. studding may be screwed into the other end of the rod and a standard knob mounted with its aid. The only difficulty that the constructor may find in making these extension handles, which are useful for a variety of purposes other than that indicated, lies in marking the hole made in the ebonite rod truly central. So long as the rod itself is straight, this is quite a simple business, if the tip mentioned a month or two ago in these notes is adopted; the

connections, but with 2 B.A. terminals it is possible to make the cut with an ordinary hacksaw and to use fairly stout wire. A simpler connection consists in making at the end of the lead a loop which is a fairly tight fit for the shank of the terminal. This is placed between two nuts, which are tightly locked together. In making this connection hold the lower nut with a flat spanner and turn the upper one hard down with a box spanner.



A FINE KEYHOLE SAW

HAVING to tackle the other day a rather awkward little job of cutting away the superfluous ebonite from a "finned" former on which a short-wave coil was to be mounted, I found myself badly in need of a little keyhole saw with a fine blade and a sharp point. There was nothing quite suitable in the tool box, so something had to be improvised. This was done



Fig. 3.—An easily fitted extension handle for a condenser dial.

very successfully with a jeweller's hacksaw blade. Since the backs of these blades are quite soft, there is no difficulty in bringing one end to as fine a point as may be required with a pair of tin shears; if a harder blade is used, its point can be shaped with an emery wheel. This having been done, the blade was mounted in the universal tool handle—a skeleton iron

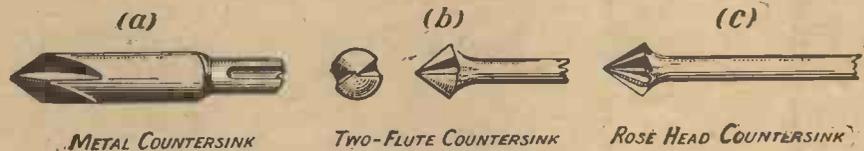


Fig. 4.—Countersinks (b) and (c) will be found most suitable for use on ebonite.


always be straightened with a hammer, whilst should the point break off it is the work of a moment to re-shape the tool. The great secret of using such an improvised keyhole saw is to start by pushing the blade as far as it will go into the handle, allowing only about 2 1/2 inches to project. If the point breaks off, you can pull out a little more of the blade, from your reserve within the handle, to allow for the loss in length when re-pointing has been done.



FOR SLOW-MOTION DIALS

IN certain types of slow-motion dial, in which a small pulley wheel actuated by the knob drives a metal disc connected to the condenser spindle, hand-capacity effects may be found rather a nuisance when certain kinds of circuit are in use. The reason is that the small spindle within the knob is in electrical contact via the pulley, the disc and the main spindle with the moving plates of the con-

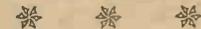work is placed in the chuck of the bench or the hand drill and spun rapidly; it is then quite easy to mark the centre with a pencil.




COUNTERSINKS

MANY constructors find it difficult to do countersinking easily and quickly. This is largely because they do not employ the best tool for the purpose. If an ordinary metal countersink, such as that seen in Fig. 4a, is used the type required is that which has a 90-degree bevel. For ebonite working, however, I find either the two-flute countersink (Fig. 4b), or the rose head, better than the tool designed for metal working, for both seem to cut ebonite more quickly and cleanly without any tendency either to polish or to tear the material. One great advantage of the two-flute type is that when it becomes blunt it can be sharpened without difficulty with a fine file. If a rose head is chosen, it should be of small size with a large

CLIX REDUCED PRICES

for Clix Taper and
Accessories

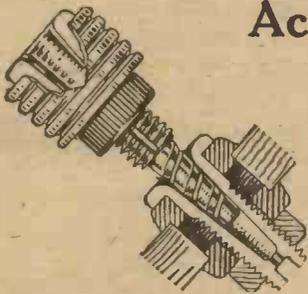


NICKEL PLATED
CLIX Plug Sockets 2d. each
CLIX Taper Adapters 1½d. each
Insulators, in six colours, ½d. each
Bushes, in six colours, ½d. per pair

A unique connector with an unlimited application. Any number of connections may be made to one point. Insulators and bushes in six distinctive colours. Terminals eliminated. Tight connections ensured.


OTHER CLIX FITMENTS



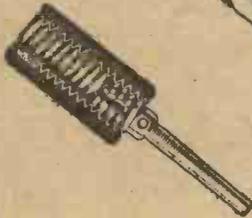CLIX
WANDER PLUGS
Always fit perfectly. They hold the leads tightly and make firm contact with the battery. Nickel plated. 2d. each.



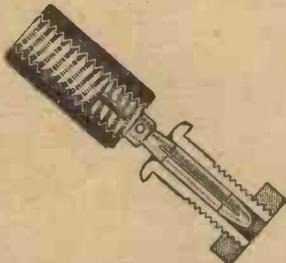CLIX
PIN TERMINALS
An exceedingly useful pin for every purpose. Nickel plated, insulated red or black. 2d. each.




CLIX PARALLEL
PLUGS
CLIX PARALLEL
SOCKETS
Present a perfect fit for use with valve sockets. Their resiliency ensures efficient contact. Nickel plated, red or black.
Plugs, 2d. each
Sockets, 1d. each

AUTOVEYORS, LIMITED,

84, VICTORIA STREET, WESTMINSTER, S.W.1.

'Phone: Victoria 309. Telegrams: "Autoveyor," Sowest, London.

EFESCA

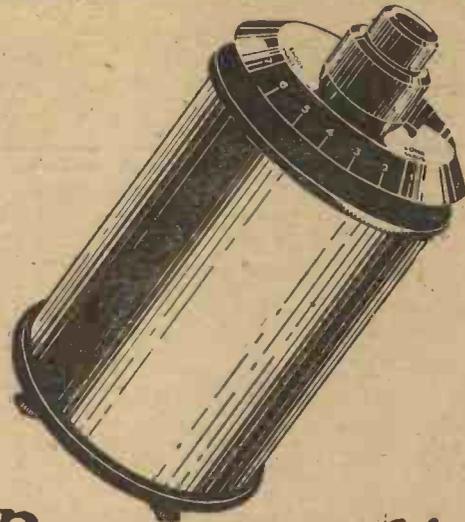

Regenerative AERIAL TUNER

THE Efesca Regenerative Aerial Tuning Coil comprises a coil wound on a cylindrical former, having an inductance equal to a whole range of plug-in type coils, from No. 30 to No. 300, and by using a .0003 Variable Condenser in parallel, all wave lengths are covered from 200 metres to 2,600 metres.

The Coil is tapped at calculated points so that the inductance, with reference to the capacity in use, may be had by a simple turn of the switch, thus enabling the desideratum of maximum inductance with minimum capacity to be far more easily secured than is possible with fixed coils.

Reaction is effected by employing a rotor, rotating within a separately wound section of the aerial coil, so that efficient and easily controlled regenerative effect is obtained over the whole wave band.

The advantages of the Efesca Regenerative Aerial Tuner. Possesses the tuning range of a whole set of coils in a single self-contained unit. A turn of the switch covers both low and high wave lengths. Obviates the bother of choosing coil combinations. Losses eliminated. Reaction under perfect control. Convenient to mount and simple to operate.

Price complete 35/-

WHOLESALE ONLY.
FALK STADELMANN & CO., LTD.,
83/93, Farringdon Road, E.C.1.




Ask your Wireless Dealer
or write for Catalogue
No. 573/1 and
Circuits employ-
ing these
components.



Tune-in with
Efesca Headphone!

Presented FREE

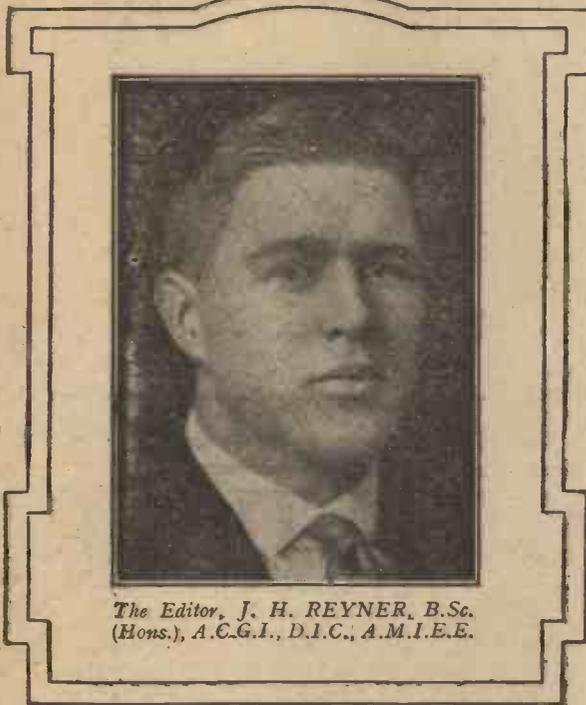

WITH ISSUE NOW ON SALE

A WONDERFUL FREE GIFT BOOKLET, THE RAPID STATION GUIDE, will be presented with every copy of the October issue of MODERN WIRELESS, now on sale at all Newsagents, Bookstalls and Booksellers to-day. The wavelength redistribution of European stations, which comes into operation on October 15th, will make this presentation booklet extremely useful to everyone.

BUY YOUR COPY TO-DAY

**1/-
MONTHLY**



- The Contents for the October issue include:*
- MORE ABOUT THE ELSTREE "SOLODYNE"**
HOW TO BUILD AN EIGHT-VALVE SCREENED-COIL SUPERHETERODYNE
By G. P. KENDALL, B.Sc.
 - MODERN DESIGN IN SIMPLE SETS**
By J. H. REYNER, B.Sc. (Hons.), A.C.G.I., D.I.C., A.M.I.E.E.
 - AN H.T. CHARGING UNIT FOR HOME USE**
By the Staff of the Elstree Laboratories.
 - FURTHER HINTS ON THE "MEWFLEX"**
REPRODUCING THE LOW TONES
By CAPT. H. J. ROUND, M.I.E.E.

MODERN WIRELESS

Obtainable from all Newsagents, Booksellers or Bookstalls, or direct from the Publishers, Radio Press, Ltd., Bush House, Strand, London, W.C.2. Subscription Rates 15/- per annum (13/6 per annum Canada and Newfoundland). Lesser periods pro rata.

From the nearest Newsagent -

GEARING AS AN AID TO WIRELESS



By C. P. ALLINSON,
A.M.I.R.E.

With the development of selective receivers needing accurate tuning, a good deal of attention is being paid to mechanical devices to assist the operator. Some of the forms which these take and their methods of application are described in this article, together with some additional hints for the constructor.

EVERYBODY knows what a gear-box is and what it does, for without it motoring would be a very different matter from what it is now. In some cars methods are applied which differ from the conventional gear-box; for instance, the ubiquitous Ford employs epicyclic gearing, while in certain older makes of car a friction reduction drive that was variable in a number of steps was used. Similar methods are made use of for helping the listener to receive music on his wireless set, and it is interesting to see in what way these principles are employed.

MOULDED WINDOW CASING

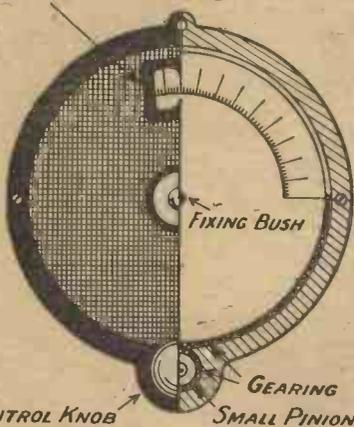


Fig. 1.—This form of geared dial is rotated by means of the small knob at the bottom, which turns a pinion engaging with the large gear wheel fixed on the spindle.

Slow-Motion Condensers

The most obvious use for these forms of reduction gear is in the slow-motion dial for controlling variable condensers. With the increased efficiency of circuits now in use, the tuning has automatically become sharper, and even the most skilled and experienced experimenters find a vernier control of some description helpful at times.

Some fine adjustment dials make use of straightforward gearing, in which a small knob used for making accurate adjustments carries a small pinion which is meshed with a large gear wheel fixed to the dial itself. In some cases the whole mechanism is cased within a moulded insulating case which is fixed to the panel, while the scale of the dial appears through a small window in this casing. This form of construction is particularly favoured by American designers. This method does not as a rule give a very large reduction, since mechanical considerations make it a rather difficult matter.

Avoiding Backlash

There is, however, a dial in which a reduction ratio of 80 to 1 is obtained by the use of straightforward gearing, and this is ingeniously arranged by means of a train of gears. In order to avoid backlash, these are carried on jockey-arms which hold the gears in constant mesh by means of small springs, so that any variation in the true running of the gears is taken up automatically.

A different method followed in several dials of British construction is the worm reduction gear. In some cases the gear with which the worm engages is fixed rigidly to the dial and provision is made for engaging and disengaging the worm, thus allowing coarse or fine adjustments to be obtained. In others the gear wheel is frictionally engaged with the dial, so that the spindle of the condenser may be rotated independently of the fine adjustment, a separate knob being provided for this purpose. With this form of reduction gear a very high ratio can easily be obtained, and this may well be in the region of 120 or even 200 to 1.

Fine Readings

In one make of dial that I have in mind the small spindle carrying the worm is provided with a scale en-

graved on the circumference of a small cylinder affixed to it, which, in conjunction with a pointer, enables fractions of a degree to be read with ease and certainty. Backlash, it is clear,

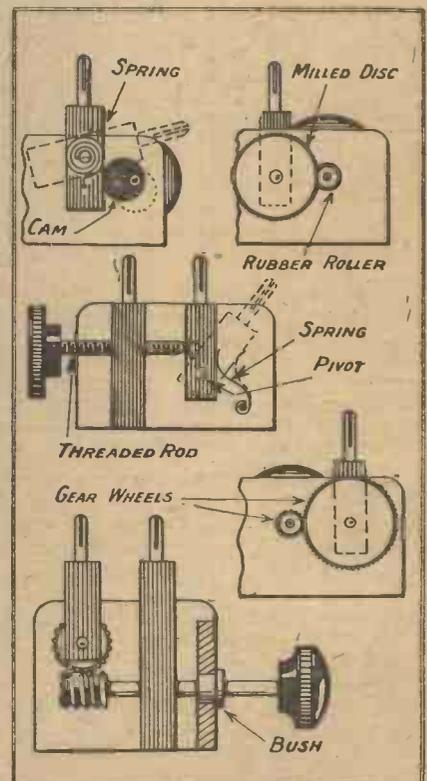


Fig. 2.—Some of the mechanical principles applied to the slow-motion control of coil holders are illustrated here

must be obviated with an arrangement of this description, and in order to do so the worm drive spindle is spring loaded so as to keep it always in tight mesh with the gear wheel.

Most of these dials show a high degree of mechanical perfection in their construction, the gear wheels

Gearing as an Aid to Wireless—continued

being correctly cut and the worms generated in the proper manner.

An Ingenious Method

Another method which is extremely ingenious is employed in an American dial and also in a British one. This is what may be termed the "wobble-plate" method. In the American dial the reduction is obtained by gearing. One set of teeth is cut on the inside of a brass ring within which a slightly smaller ring, provided with teeth on its periphery, can revolve. This latter is mounted so that it is always at an angle to the outer ring, and the teeth therefore only mesh at the one point where the two rings are in contact. A spring arm rotates on a track provided on the smaller ring, this arm being controlled by an insulated knob. As this knob is turned, the spring arm forces the skewed ring to mesh with the internal gear. Since both gears are cut so as to have a different number of teeth, the forcing into mesh of the inner ring with the outer will cause the latter to be rotated slowly at a rate equal to the difference between the pitch of the teeth.

Supposing there are a hundred teeth on the outer ring and ninety-nine on the inner one, then one revolution of

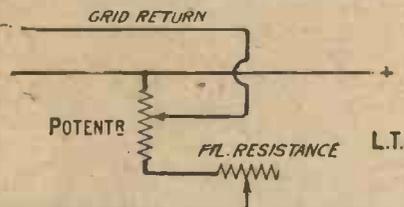


Fig. 3.—This simple addition to a potentiometer will render fine settings of this control easily possible.

the spring arm (which causes the inner gear wheel to wobble once) will cause the outer ring to move over a distance corresponding to one tooth or one-hundredth of a revolution.

The British dial employs a somewhat similar principle, except that friction drive is incorporated instead of actual gearing. This dial gives a delightfully smooth action, and backlash is, of course, entirely absent.


Friction Methods

Various forms of vernier control utilise friction entirely. In one case, for instance, the vernier knob of the dial is in frictional contact with a small rubber roller which is inclined at an angle to it and is fixed to a small shaft carrying another rubber roller. This presses against the panel on which the condenser is mounted, and a reduction ratio in the neighbourhood of 10 to 1 is obtained. The dial is simple in construction and easily fixed, while it has the advantage

that there is nothing to go wrong with it.

A number of attachments that are available make use of a rubber roller which engages with the bevel edge of the scale and are exceedingly useful where a large reduction is not required. They have the advantage of

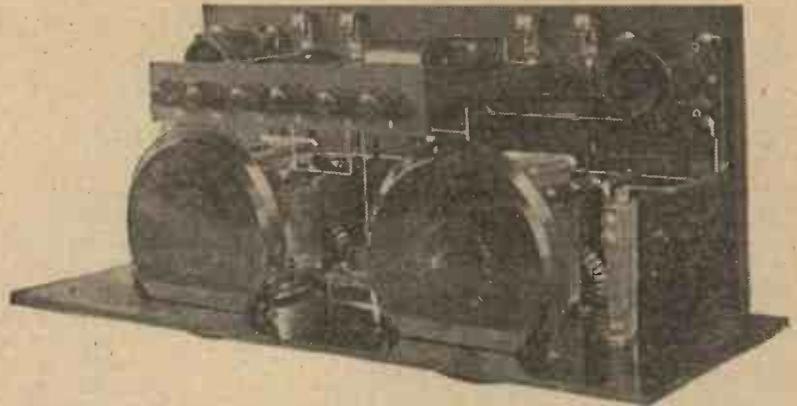ing coil is often advisable. An examination of some of the leading makes of coil holders shows that all types of gearing are employed. Straight gears, epicyclic, friction and worm drives and ingenious cam arrangements are used, all with the object of giving positive and accurate



In the American Grebe receiver a form of "reduction gearing" is provided by presenting only the edge of the dial to the hand of the operator.

being cheap to buy and easy to fit to existing apparatus with a minimum of trouble.

Integral Verniers

A number of makes of variable condensers now incorporate some form of fine adjustment in the condenser itself. The most usual form is that in which an integral vernier is used. This generally consists of one or two moving vanes with one or more fixed vanes, the moving vanes being controlled independently of the main bank of moving vanes. As the capacity range of the vernier portion of the condenser may be from 1/10th to 1/20th of the total capacity of the variable condenser a very fine adjustment is provided. Another method which is employed is to gear a spindle carrying the dial and control knob to the moving spindle of the condenser either through plain gears or through a worm reduction gear. A variation of this method is to provide a separate control for the vernier adjustment by means of a small rubber wheel which is connected to the main spindle by means of some form of friction drive. This allows a rough setting to be obtained by means of the ordinary control knob and the final setting is obtained by the vernier knob.

Application to Coil Holders

A component in which some form of vernier adjustment is of great use is in the coil holder. When magnetic reaction is used, it is necessary in order that the maximum sensitivity be obtained that the set be kept just off the oscillation point, and in order to do this a fine control of the swing-

control of the coupling between two or three coils.

Aerial Coupling

As regards the coupling between aerial and grid coils, this is by no means critical and a vernier adjustment is hardly necessary, nevertheless there are cases occasionally where it is an advantage. A very satisfactory means of getting a fine control is obtained by the use of a special cam. In this type of coil holder one socket is adjusted by the usual spindle fixed directly to the coil holder, this giving the coarse adjustment. The coil which is usually kept fixed in this case is free to move and is kept in engagement with a small eccentric or cam by means of a stiff spring. It will readily be appreciated that rotating the cam gives a very fine control and by this means the coupling between coils can be accurately adjusted.

A Variety of Methods

A very simple method of getting the desired fine adjustment is by means of a threaded rod which presses against the moving coil socket which is held up against the end of the rod by a spring. This gives a fine continuous variation of the coupling, but suffers from the disadvantage that if it is desired to swing the coil over the whole of its travel it takes some time to do so. Various forms of vernier action that are used are shown sketched in Fig. 2, and some of the methods can be applied by the home constructor who possesses the necessary skill and tools.

(Concluded on page 80.)

<p>JACKS (POINT)</p>  <p>1-ROLE FIXING 1/9</p>	<p>IZION HAND DRILL</p>  <p>Only TAKES DRILLS UP TO 5/16 in. SIX DRILLS - 1/-</p>	<p>RELIABILITY CONDENSERS</p>  <p>Mansbridge Type. 25. 1/8 1, 2, 6. 5. 1/9 2, 3/6</p>	<p>WIRELESS CABINETS</p>  <p>For Panels 7in. high Width 6" Baseboard Oak 12", 14", 14", 15"; 15", 16", 15"; Mahogany, 1/- extra</p>	<p>DEWAR SWITCH</p>  <p>12-CONTACT 2/6</p>
--	---	---	---	--

READ THIS LIST & SAVE MONEY ON COMPONENTS.

ACCUMULATORS.—Exide, D.T.O., 4/6; D.F.G., 8/6; W.J., 20 v. H.T. type, 15/-; Oldham H.T., 10d. per volt, complete; Duros 20 v., 12/-; 10 v., 6/-; Repairing Outfit, 2/6.

AERIALS.—100 ft. 1 in. Copper Tape, 1/6; 7/22s Bright, 2/3; Fanned, 3/3; Electron, 1/8; Superior, 2/8; Mars, 8/8; O.V., complete, 2/6; Ashton Spreader, 12/- per pair.

INSULATORS.—Large Shell, 8d.; Reel or Egg, 1d.; C/Imax, 6d.; Ditto, with shock absorbers, 3/- pair; Gal. Pulleys, 4d.; 100 ft. Gal. Straining Wire, 1/8; Straining Bolts, 6d.

BATTERIES.—Reliability, 90 v., 11/-; 60 v., 7/6; 36 v., 4/6; 15 v., 1/10; Ever Ready, Siemens, Hellesen, 100 volt, 21/-; 66 v., 12/6; 36 v., 7/6; 41 v. Batteries, 4d.

EBONITE.—Any size cut, Clayton brand, 1/2 in., 1d. sq. in.; 9 in. by 6 in., 2/2; 12 in. by 9 in., 4/6; 15 in. by 9 in., 5/6; 2 1/2 in., 25 1/2 test; Paxson and Radion, 1d. per sq. in.

CONDENSERS.—Low Loss, Square Law, with knob and dial, .0005, 5/-; .0003, 4/6; with Vernier Blade, 1/4 extra; Twin, .0005 for Elstree Six, unequalled value, 3/6; Cydon Twin for ditto, 2/6; Ormond, J.B., Utility, Sterling, Polar, Formo, Igranite, G.E.C. Variable.

FIXED CONDENSERS.—Dubiller, Edison-Bell, Lissen, Watmel, Mullard, McMichael, at advertised prices. Special Reliability Fallon, .0003 2-meg. Leak, 1/3; Cases only, 4d.

L.F. TRANSFORMERS.—B.L. Multi Radio, 2/6; Marconi Ideal, 30/-; Junior, 13/6; Ferranti A.P.3, 25/-; A.P.4, 17/6; Formo, 10/6; H.T.C. Empire, 7/6; Croix, 5 to 1, 4/-; Lissen New Type, 8/6; Igranite, 16/-; Eureka Concert Grand, 25/-; No. 2, 21/-; Baby Grand, 15/-; Ormond, 15/-; Royal, 20/-; Success all black, 21/-; Silvertown, 21/-; G.R.C., 16/-; Brandes, 17/6; Burndept, 16/6; Special Value, 7/6; Modulation or Telephone types, 7/6.

VALVE HOLDERS.—Antiphonic Benjamin, 2/9; Lotus, 2/3; with terminals, 2/6; Burndept, 2/9; Harris, 1/6; Reliability Unequalled, 2/-; all baseboard types, ordinary ditto, 6d.; N.P. Valve Sockets, 1/2 in. 1/6; Superior Panel Type, 6d.; all Ebonite 10d.

HEADPHONES.—B.T.H., 15/-; Brown's F. Type, 20/-; Reliability, 7/6; Adjustable, 8/-; Dr. Nesper, 12/11; T.M.C., 17/6; Western Electric, 20/-; all 4,000 ohms, Sullivan 120 ohm Double Ex-Govt. New, 4/6; 120 ohm Single 'Phone, 2/6; Long 'Phone Cord, 1/-.

DETECTORS.—R.L., 6/6 and 6/-; Liberty, 3/6; Cat's Eye, 2/6, all permanently set; also good glass enclosed, 1/-; 5 tested Crystals, 1/-; Neutron, 1/6; Hertzite, 6d.

COIL HOLDERS, 2 Way.—Lotus, 7/-; with long handle, 8/-; Denton geared, 8/-; Polar Cam Vernier, 6/-; Newey, 6/6; Woolfall, 10/6; Reliability geared, 3/6; good quality, 2/6; Unequalled Value, 2/-; 1 Hole Fixing 3/9; Geared do. 5/-; Vernier Friction Drive type, 3/6

COIL MOUNTS.—Honeycomb Type Reversible Pins, 6d.; Solid Ebonite ditto, 8d.; Basket Coilholder, 8d.; Horned Coil Plug 8d.; Narrow Ebonite, 5d.; Shorting Plug, 7d.

UNEQUALLED VALUES.—Twin Red and Black Flex, 2d. yard; 46 Pin Coilformer and instructions, 1/-; with handle, 1/3; 30 ohm Resistance, 1/6; N. Plated Valve Windows, 8d.; 1 lb. Round 1/8 in. or 1/16 in. Tinned Copper Wire, 7d.; Square 24 in. by 1/16 in. Tinned Copper Busbar, 1d.; Coil Black Tape, 6d.; 12 yards 1 in. Empire Tape, 8d.; Box assorted BA Screws and Nuts, 1/-; Ex-Govt. Standard Telephone Plugs, 1/3; 3 Coils for 5X 3/6.

EXPERIMENTERS' PARCELS.—Accessories of various types, worth 20/-, post paid, 5/6.

VALVES.—Radion All Types, Prelat 2 volt 3 amp, 4/11. All advertised makes stocked.

Send for **RELIABILITY WIRELESS GUIDE No. 2.** Free on Request.

J.H. TAYLOR & CO.
7, RADIO HOUSE, MACAULAY ST., HUDDERSFIELD.
Tel: 541. Grams: THOROUGH HUDDERSFIELD.

Orders 5/6 Value Carriage Paid. Under 5/6, 2d. per 1/- for Packing, etc.



No. 1
Things are not always what they seem.

"The Cowl does not make the Monk"

"THINGS are not always what they seem," says the old adage. A man may wear cloak and cowl, yet who can tell he is of the Monastery—until he probes beneath. Who knows but that the sacred cowl may be but the shield of an impostor? Is there a "Judas" in your Wireless Set? Those constant cracklings and that worrying weakening of your signals—where do you suspect, lies the culprit? You examine the components, check over the wiring—everything seems correct. Are you sure of the fixed Condenser? Of all the faults in a Receiver more are traceable to the fixed condenser than to any other component. Yet you buy it on faith: you may have the choice of two Condensers—alike in outward appearance, except that one bears the name "T.C.C." stamped upon its case. The unnamed condenser may be nothing but a case shielding inferior materials and bad workmanship—an impostor. To buy such is false economy.

Although to buy T.C.C. may cost a few pence more in the first place, it will assuredly save you time, money and temper, for when you buy a T.C.C. Mica or Mansbridge Condenser you obtain a product behind which is the experience of England's Condenser pioneers. Because only the finest materials available are used, by men with more-than-a-score years' experience in Condenser manufacturing, you know you are buying a Component whose capacity is guaranteed to be within an ace of accuracy, and that your set will be entirely free from leakage and all other condenser-troubles.

T. C. C. Mansbridge Condensers are priced from 2s. 0d. upwards; Mica are from 2s. 4d.

T.C.C. Condensers
[Mansbridge and Mica]



Telegraph Condenser Co. Ltd.,
Wales Farm Road, N. Acton,
London, W.3.
G.A., 5823.

SIMPLY WONDERFUL!

"The 'AF3' I have fitted is simply wonderful."
ENGINEER COMMANDER, R.N.

WONDERFULLY SIMPLE!

YOUR RADIO WILL BE IMPROVED SIMPLY BY SUBSTITUTING

FERRANTI

British Made
AUDIO FREQUENCY TRANSFORMERS TYPE AF3 FOR THE OTHERS

No better Transformer is available at any price. **25/-**

ASK YOUR DEALER FOR LEAFLET W-491.

FERRANTI LTD., HOLLINWOOD, LANCASHIRE.

PERFECT CONTACT maintained

The WATMEL GRID LEAK possesses a very attractive feature for Constructors, in the special contrivance which automatically takes up any slackness (due to wear) in the adjusting screw, and maintains effective and silent electrical contact.



WATMEL VARIABLE GRID LEAKS AND ANODE RESISTANCES

Ask your dealer or write direct for full particulars of all Watmel Products, including combined Fixed Condensers and Fixed Grid Leaks, and the Watmel Auto-Choke.

Watmel

The WATMEL WIRELESS CO., Ltd.
332a, Goswell Road, London, E.C.1.
*Phone: Clerkenwell 7990.

Lancashire, Cheshire and Yorkshire Representative:
Mr. J. B. LEVEE, 23, Hartley Street, Levenshulme,
Manchester. *Phone: Heaton Moor 475.

A READER'S APPRECIATION

THE POWERFUL THREE

Sir,—I write to you to give a few of the stations which I received on my set, the "Powerful Three-Valve," described by Percy W. Harris, M.I.R.E., in the April, 1925, issue of THE WIRELESS CONSTRUCTOR. I live in the West Riding of Yorkshire, about twelve or fourteen miles from Leeds and about forty or just over from Manchester. My aerial is screened, the pole at the opposite end from my set being 27 ft. high. My thanks to THE WIRELESS CONSTRUCTOR, and good luck in future days. The stations received were as follow:—Leeds and Bradford, Manchester, and Daventry, all on loud-speaker, and could be heard twenty yards away; three foreign stations, which I could not make out, as I could not recognise the language. Newcastle on the loud-speaker was about the same strength as is given by one valve on the 'phones.

JOSEPH W. SMITH.
Liversedge, Yorks.

Valves Repaired AS GOOD AS NEW!!

HALF
LIST
PRICE

Except Weco, S.P.'s, and low capacity types. Minimum D.E. Current 0-15 amps when repaired.
ALL BRIGHT & DULL EMITTERS Listed at less than 10/-.
MINIMUM CHARGE - - 5/-
VALCO LTD., Dept. G., Tabor Grove, Wimbledon, S.W.

2-VALVE AMPLIFIER, 35/-
1-Valve Amplifier 20/-, as new. Valves, D.E. '06 7/-.
Headphones 8/6 pair. New 4-Volt Accumulator 13/-.
New 60-Volt H.T., guaranteed, 7/-.
2-Valve All Stn. Set, 24. Approval willingly. Write for free bargain list.
C. Taylor, 57, Studley Road, Stockwell, London.

TRIUMPH

2-COIL STAND


Ref. No. C. 169
PRICE 5/9



THE LATEST SUCCESS
VELVET VERNIER ACTION.

Also
TRIUMPH VALVE-HOLDER

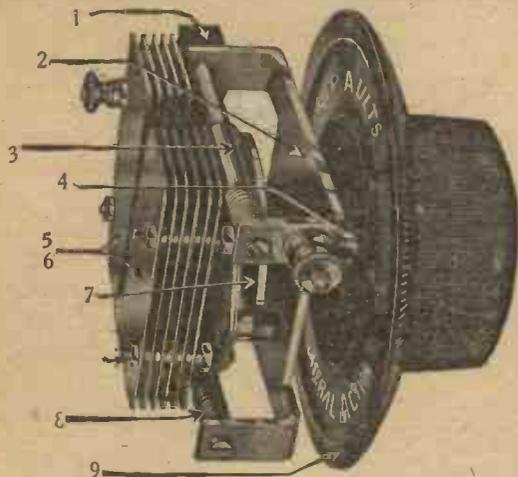(Anti-Microphonic) &
TRIUMPH RHEOSTAT.
ASK YOUR DEALER FOR ILLUSTRATED LISTS,
or send p.c., mentioning Wireless Constructor, to:
A. H. GLACKSON, LTD.,
WHITE HART WORKS, LONDON, N.22.



Special Constructional Features :

1. High-grade Ebonite Insulating Bar.
2. Rigid Heavy Gauge Main Frame, placed out of the magnetic field, avoiding eddy current losses.
3. Slider Contact, silent in action and making permanent connection to terminal.
4. One-hole Mounting.
5. Bolted Heavy Gauge Brass Plates giving true lateral action.
6. Minimum space occupied at back of panel. 4 in. dial covers whole Condenser.
7. Specially shaped Driving Cam, by which Straight-line frequency characteristic is obtained.
8. Special Compensating Springs, ensuring permanently smooth movement. Backlash cannot develop.
9. 4 in. Dial, divided into 360 degrees for most precise control and easier tuning.

Prices : .0005 - 18/6 .0025 - 17/6
(Complete with 4 in. Knob and Dial.)

Revolutionary Design of New Condenser proves Triumph of the Show!

Many advantages must necessarily result from the *revolutionary* design and construction of the Ripaults Lateral Action Condenser. How much these advantages are appreciated has been proved by the enthusiasm the Ripaults Condenser aroused at the show amongst constructors of Sets—both amateurs and manufacturers.

The excellent points of design which are so necessary for the efficient operation of a commercial Set make Ripaults Lateral Action Condensers ideal for your own purposes.

So study the unique constructional features listed—and ask yourself whether you can really afford to leave the tuning circuits of your Set *minus* the efficiency given by this *triumph* in Condenser design.

Ripaults

LATERAL ACTION CONDENSER

(PATENT APPLIED FOR)


MANUFACTURED AND GUARANTEED BY RIPAUTS, LTD., 1, KING'S ROAD, ST. PANCRAS, LONDON, N.W.1.

FIT BENJAMIN COMPONENTS

BENJAMIN VALVE HOLDER

complete with Dublier Fixe Condenser (0003) and Dumetohm Grid Leak (2 megohms)—series or parallel.

Price 7/- each

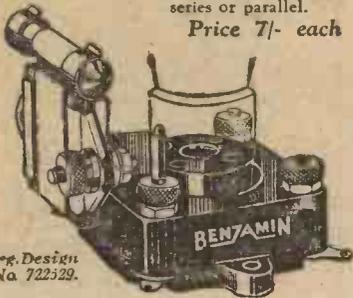

Reg. Design No. 722529.




BENJAMIN Clearer-Tone Anti-Microphonic VALVE HOLDER

Price 2/9 each

BENJAMIN VALVE HOLDER

complete with Dumetohm Grid Leak (2 megohms).

Price 5/3 each

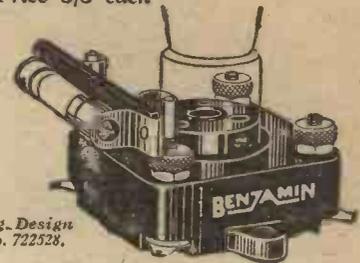

Reg. Design No. 722528.

FIVE EXCLUSIVE FEATURES:—

- (1) Valve sockets and springs are made in one piece, with no joints or rivets to work loose and cause faulty connections.
- (2) Valves are free to float in every direction.
- (3) Valves can be inserted and removed easily and safely.
- (4) Valve legs cannot possibly foul the base-board.
- (5) Both terminals and soldering tags are provided.

Patent Nos. 222086—1923, 250431—1925. Registered Design No. 714847.




BENJAMIN Self-Contained RHEOSTAT

The resistance is *inside* the dial. Nothing behind the panel except lock-nut and soldering tags. Panel space saved, wiring and mounting simplified and the appearance of the panel improved.

Made of genuine Bakelite. Three windings as standard—6, 15 and 30 ohms.


Price 2/9 each

Patent No. 246435.

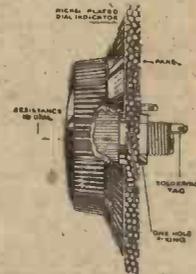

BENJAMIN BATTERY SWITCH

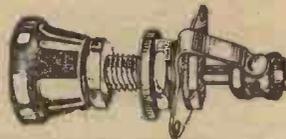A sturdy, positive action switch for high or low tension. It's OFF when it's IN, thus preventing the accidental turning



on of current. Single contact, one-hole fixing.

Price 1/3 each

Ask your dealer or write for particulars.


THE BENJAMIN ELECTRIC LIMITED

Brantwood Works, Tottenham, London, N.17

MAKERS OF THINGS MORE USEFUL

The Varley

Bi-duplex winding

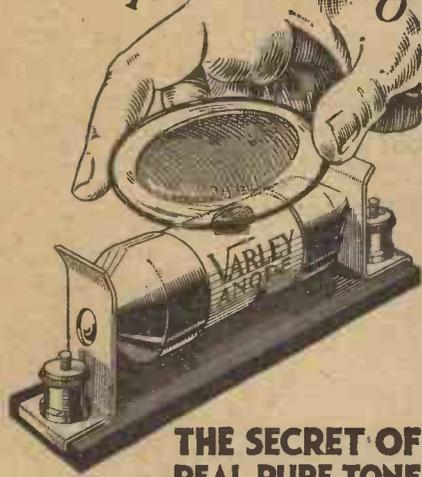

THE SECRET OF REAL PURE TONE

It's the Varley Bi-duplex winding that makes all the difference. Revealed by the magnifying glass, the secret of that real pure tone is seen in the perfect winding, where every turn of bare wire is separated by pure silk, thereby preventing all possibility of shorting between turns, and ensuring that remarkable constancy of perfect reception for which the Varley is so famous.

Varley Anode Resistances have figured in all the big sets of 1926, including the "Elstree Six."

Made in a complete range of sizes up to 250,000 ohms. Descriptive leaflet giving full particulars of sizes, prices, etc. on application.



The Varley Multi-cellular High Frequency Choke.

Wonderfully efficient! Absolutely in a class by itself. This is the universal opinion of the Varley H.F. Choke. This new product has been chosen for "The Night Hawk," the "Spanspace Three," and the Screened Coil Superheterodyne (Modern Wireless).

Readers will be interested to know that Varley H.F. Chokes are ideal for the "Elstree Six," the "Elstree Solodyne" and the "Davlow Three."

PRICE, complete 9/6.

Descriptive Leaflet on application.



THE VARLEY MAGNET CO.
 (Proprietors Oliver Pell Control Ltd.),
 Granville House, Arundel Street, London W.C.2.
 Telephone: City 3393.

TALKS TO BEGINNERS

(Concluded from page 12)

recently tend to suggest that they will be much better than we have had them. I have noticed that they are tending to be "freaky." On one night they will be exceedingly good and the next night very bad, variations sometimes taking place during the evening to a very marked degree. Previous experience has taught me that a good season is usually preceded by a good deal of "freaking," so that I should not be surprised to find that we have a very good season this winter. If so, reception conditions in this country will be very remarkable, for we now have available receivers far more efficient and sensitive than any available during the previous good seasons.

Don't Blame the Set

Do not be disappointed, then, if your new set, when tried the first night, does not bring in as many stations as you have been led to anticipate, or if you find that the wonderful results you got on the first night cannot be repeated a week later for the benefit of a friend.

A Curious Phenomenon

There is another phenomenon which is only just beginning to be observed, but which is of great interest to the listener who is keen on long-distance reception. For some reason or other—probably reflection from some other strata in the atmosphere—stations 500 and 600 miles away, or even further, will come in much better than stations perhaps 200 miles away. I noticed in America that listening in the neighbourhood of New York one could always very easily hear the Chicago station after dark. If you look upon a map you will see that Chicago is some 700 or 800 miles at least from New York, taking a direct line, but at the same time stations much nearer were not audible or, if audible, were much weaker.

Useful Comparisons

I put this down at the time to some exceptionally freak conditions pertaining to the American ether, but on discussing the matter with Capt. Round on my return to this country, he suggested that if I were to draw a circle round London of a radius equal to the distance from New York to Chicago, and if any stations fell on the circumference of the circle, they would probably be found to come in very well indeed. I did make a number of observations of this kind, and then noticed that Madrid, Rome, Prague and a number of other stations at a considerable distance from London came in extraordinarily well considering their power. Madrid, for example, can be received almost any night after dark on the most simple receivers.

Cheaper and Better Jacks

Ashley Radio Jacks are made of nickel silver springs, with pure silver contact and Bakelite insulation throughout. Tags are tinned and spread fan wise for easy soldering.




SHOWING HOW TAGS ARE FANNED.


Note the Prices below:




JACK No. 1. SINGLE CIRCUIT (OPEN). 1/3

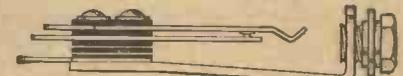


JACK No. 2. SINGLE CIRCUIT (CLOSED). 1/6

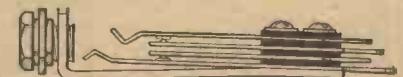

JACK No. 3. DOUBLE CIRCUIT. 1/9

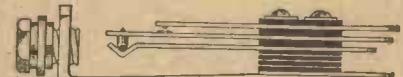

JACK No. 4. FILAMENT SINGLE CONTROL. 1/9

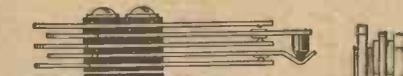

JACK No. 5. FILAMENT DOUBLE CONTROL? 2/3

Telephone Plug



Price 1/6

Occupies less space than any other plug. Metal parts highly nickelled and polished. Bakelite insulation throughout, suitable for spade or pin tags, and any type of flexible or solid wire connection.

Ashley Radio

Ashley Wireless Telephone Co. (1925), Ltd.
 Finch Place, London Road, Liverpool.



**Make your
Dream of
Success
Come True**

Some day, you hope, you will occupy a good position—draw

a handsome salary or have a prosperous business of your own. You dream of the comforts, the privileges, the broad and happy life that success can generally command.

Don't forget that success has to be fought for. You have to qualify for it by making yourself more efficient, more resourceful than your fellows of the rank and file. That calls for patient effort along carefully planned lines.

Get out of the rut by taking an I.C.S. Course. It will provide you with a sound and practical training in your own home and at your own time, all by correspondence and at a cost well within your means. There are no real difficulties and no heavy demands upon your time. The I.C.S. method is simple and practical. Let us tell you just how you can use it to your own great advantage.

Write to-day for full information as to how the I.C.S. can help you in your chosen vocation. There are 300 I.C.S. Courses, of which the following are the most important groups:—

The I.C.S. is the oldest and largest correspondence school in the world

WIRELESS ENGINEERING (an entirely new Course)

- | | | |
|---------------------|----------------------------|---------------------|
| Advertising | Engineering (all branches) | Professional Exams. |
| Architecture | French and Spanish | Salesmanship |
| Building | General Education | Showcard Writing |
| Commercial Art | Market Gardening | Textiles |
| Commercial Training | Plumbing | Window Dressing |
| Draughtsmanship | | Woodworking |

International Correspondence Schools, Ltd.
172, International Buildings, Kingsway, London, W.C.2

**COLVERN
SCREENED COIL
LOW LOSS INDUCTANCE FORMER**



ENABLES the set builder to construct coils, H.F. Transformers, oscillator couplers, etc., of the highest efficiency, conforming to the new standard windings and six-pin base. Constructed of the highest quality bakelite, the former is provided with six ribs which support the windings giving the maximum "Wound on air" effect.

- Copper Screen with Standard 6-pin Base 8/6
- Screen complete with Base and unwound Coil . . . 12/6
- Former and Base, unwound 5/- As used in the "Spanspace Three." Former only 4/-

Collinson Precision Screw Co., Ltd.
Walthamstow, London, E.17.
Provost Works, Macdonald Road.

Telephone—Walthamstow 532.
ALSO AT 150, KING'S CROSS ROAD, N.W.1

As will be seen from the above illustration the Colvern low loss former conforms to the standard six-pin base. Coils when wound are 2 1/2" in diameter, the height of the former is 2 1/4" only.



5/-

5/- down and 12 monthly payments of five shillings.

SECURES

**"BULLPHONE NIGHTINGALE"
LOUD SPEAKER**

CLEAR TONE.

POST your deposit of 5/- now and get by return the famous "Bullphone Nightingale" Loud Speaker.

Individually tested and guaranteed to be superior to any other Loud Speaker, regardless of price, for finish, purity and strength of tone and value. Cash Price 60/-, post free United Kingdom.

GREAT VOLUME.

SPECIFICATION. Height 21". Bell Mouth 14" Nickel Arm and stand. Black crystal bell head, as photo. Also de luxe model, mahogany finish bell, same size, 65/- cash or 10/- deposit. List free.

W. BULLEN Dept. 38, HOLYWELL LANE, W.C.1. LONDON, E.C.2.



Patent No. 244,251

- PRICES:**
- Two Types:
 - For outside panel mounting:
 - Two-way 7/-
 - Three-way 10/6
 - For inside baseboard mounting, with 6-in. handle:
 - Two-way 8/-
 - Three-way 12/6

The Moving Block Cannot Fall

The vernier movement comprises three sets of enclosed precision machine-cut gears, and reduces the speed of the moving block by eight times. Side plates, coil blocks and knobs in artistic bakelite mouldings. All metal parts heavily nickel plated. Made for left as well as right hand.

**LOTUS
VERNIER
COIL HOLDERS**

Made by the makers of the famous Lotus Buoyancy Valve Holder.

GARNETT, WHITELEY & CO., LTD.
Lotus Works, Broadgreen Rd., Liverpool.

THE Newey "4 Point" Condenser

"The finest engineering production of the year"—an unsolicited testimonial. We reproduce below one of the numerous letters we have had from users of the Newey 4-Point Condenser: in every case there is the same enthusiasm regarding the perfect design and workmanship of this famous Condenser.

May I (as an engineer) congratulate you upon the production of what I consider absolutely the finest piece of wireless engineering that I have ever seen, & that too at a modest price. The Newey Four point condensers will go far yours Truly
S.M.


What the Wireless Technical Press thinks of the Newey 4-Point Condenser.

"Amateur Wireless." "In construction it is of the ultra low-loss type, and in this respect it is one of the finest examples we have seen."

"The Broadcaster." "A noticeable feature is the high-class workmanship throughout, and that all rubbing contacts from vanes to connecting terminals are avoided by the use of soldered flexible wire connections."

"On test we found the maximum capacity very close to the nominal (.0005 mfd.), while the minimum was lower than that of the usual vane type of condenser. Testing in critical oscillating circuits, no losses were apparent, while on practical test in a valve receiver tuning the aerial inductance, the actual performance was highly satisfactory."

THE NEWEY VERNIER COIL HOLDER.

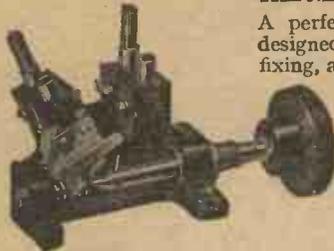

A perfectly constructed coil holder, designed for Back of Panel One-hole fixing, and in addition provided with lugs for fixing in any position on panel. Bakelite moulding throughout. Worm geared by means of metal segment and worm, and fitted with patent stop plate to prevent over winding in extreme positions—gearing ratio 8-1 giving fine critical tuning and permitting the use of the heaviest coil.

PRICE 7/6

NEWEY SNAP TERMINALS

The Terminal with 1,000 uses.


No set complete without them. The use of these Snap Terminals, which have been reduced in price and are now only

1d. each (nickel-plated 1½d.)

ensures Convenience, Simplicity, Multi-Purpose, Certain Contact, Finish.

Experimental sets in boxes.

Brass 1/6 Nickel plated 2/-

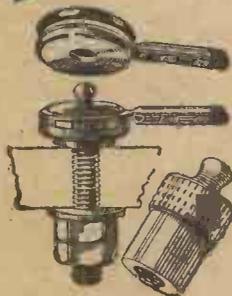


Adapters are supplied in sizes No. 2 and No. 4 B.A.

Ask your nearest dealer for the Newey Catalogue of Radio Components. If you have any difficulty, write direct.

Sole Distributors.

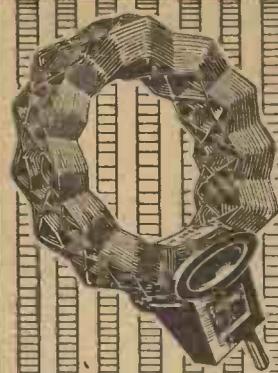PETTIGREW & MERRIMAN (1925) Ltd., PHONOS HOUSE, 2 & 4, Bucknall, St., New Oxford St., London, W.C.2 (and Branches), Telephone: Gerrard 4248-49. Telegrams: Merrigrew, Westcent, London.



FINSTON
Lo-Loss Coils

Combine Efficiency in action with Strength in construction.

Note the Thumb Grip moulded into Bakelite base. This means long life, as it prevents all damage to windings when plugging in or changing coils.

Coil No.	Prices	Coil No.	Prices
25	1/3	150	2/9
35	1/6	175	3/3
50	1/9	200	3/6
75	2/-	250	3/9
100	2/5	300	4/-

There are other Finston Components as reliable and economical to buy. Write for Complete Illustrated Leaflet.

FINSTON MFG. CO., LTD.
45, Horseferry Road, London, S.W.1

Parrs Ad.



STEEL PLATE ACCUMULATORS

FOR

HIGH TENSION

Only 1/- per volt.

Absolutely Noiseless.
No Acid. No Fumes.
Last a Lifetime.

BATTERIES, LTD., REDDITCH

LONDON OFFICE:—220, Shaftesbury Avenue, W.C.2.

PERFECT CONTACT



The Etherplus + V.C. Rheostat gives Velvet Contact! There is no other Rheostat on the market with such a smooth noiseless movement.

Handsome Pointer Knob fits flush with engraved dial. Specially designed spring ensures perfect contact. One hole fixing.

PRICE

6 ohms or } 2/3 each
30 ohms

From dealers or from

M. & A. WOLFF,
9-15, Whitecross St., London, E.C.1



ETHERPLUS

RADIO ACCESSORIES
— ENSURE — PERFECT RECEPTION

CUT THIS OUT FOR CABINETS

and post to us for FREE list illustrating Cabinets as shown in "Wireless Constructor," etc., etc.

NAME.....

ADDRESS.....





(Write in block letters please.)

CARRINGTON MFG. CO., Ltd.
18/20, Normans Buildings,
Mitchell St., Central St., E.C.1
Trade enquiries especially invited.
Telephone: Clerkenwell 6903.



For "The Wireless Constructor" at our Elstree Laboratories.

P.M.3 Valves


WE have received from Messrs. The Mullard Radio Valve Co. three P.M.3 valves. These valves are similar in appearance and construction to the P.M.4 valve, and are designed to work with a filament potential of 3 to 3.7 volts, with a filament current of .1 volt. As in the case of the P.M.4 valve, the filament does not glow visibly when working.

On test, these valves were found to be quite satisfactorily uniform, taking a filament current of .1 of an ampere at a filament potential of 3 to 3.5 volts, which is well within the maker's rating.

When measured at an anode potential of 80 volts, the impedance was found to be 17,000 ohms in two cases, and 18,000 in the other, while an average amplification of 11.6 was obtained.

C.E. Precision Rheostat

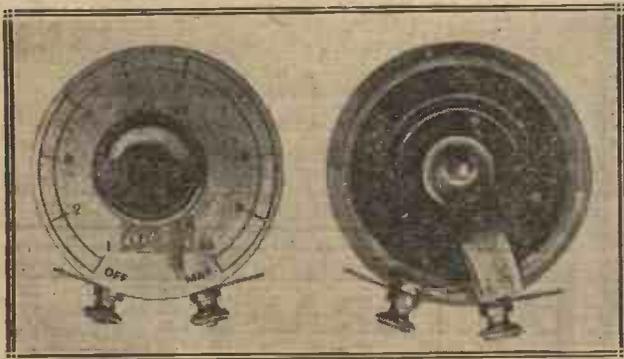WE have received from Messrs. C. Ede & Co. several of their rheostats for test and report. The samples submitted are improved models in which several detailed refinements have been incorporated. All these components are constructed on the



same lines. The resistance winding is carried on a fibre former which is bent around a circular insulating moulding. There is a positive stop both for on and off positions, and connections are provided for by means of terminals and soldering tags. One-hole fixing is employed and a graduated metal scale is provided with each instrument. A small knob and pointer control the movement of the slider, which was found to be exceedingly smooth in action.

When placed on test, the bright-

emitter rheostat was found to have a resistance of 5.5 ohms, while it would pass a current of .7 amps. without any appreciable heating. The 30 ohms resistance was found to have an actual value of 32 ohms, and this, again, would pass .5 amps. without overheating.

All these rheostats were found to be silent in operation, and gave smooth control.

L.F. Transformer

WE have received one of their L.F. transformers from Messrs. Brandes for test and report.

This transformer is of the shrouded type, ratio 5 to 1, being about 2½ in. by 1½ in. and just over 3 in. high. Four terminals are provided, together with soldering tags for making connections, while the terminals are marked giving the actual connections to be employed, which is a useful feature.

When placed on test on our standard transformer test panel it was found that a degree of amplification somewhat about the average was obtained in the first stage, the quality of reproduction being very good. Used in the second stage, the amplification obtained was equal to that given by

This battery is contained in a polished mahogany box, the cells being carried in a wooden cradle, which can be lifted out intact for inspecting and examining the cells. The cells are tubular in form, each containing a single positive and negative plate separated by a corrugated separator.



Messrs. Brandes low-frequency transformer is unconventional in appearance.

The whole assembly makes a rigid workmanlike job.

This H.T. accumulator can be tapped off at every 2 volts, and it is possible to obtain two separate H.T. positive voltages from this battery, by means of the plugs provided.

This battery is rated by the makers as having a capacity of 2,000 milli-ampere hours. The capacity obtained under severe test conditions was found to be 1,800 milliampere hours before the voltage had dropped to below a satisfactory working value. Even then the plates were found to be of a good colour, and the cells appeared to be in an excellent condition. This high-tension battery is excellently constructed, and highly satisfactory in operation, and we can thoroughly recommend it for use.

"M.L." L.F. Transformer

MESSRS. S. A. SMITH, LTD., have sent us one of their "M.L." L.F. Transformers for test and report. This instrument, which is partly shrouded, is of an unconventional design. The core is of very substantial dimensions, being circular in form. The upper part of the instrument consists of black moulded insulating material carrying four ter-

the standard transformer which is actually of a higher step up ratio than the transformer under test. The quality in the second stage was also very good. The insulation resistance between primary and secondary was found to be infinity, and this transformer can be thoroughly recommended.

High Tension Accumulator

MESSRS. The General Electric Co. have submitted to us for test and report one of their high-tension accumulators.

Apparatus Tested—continued

minals at the top, each of which is marked for connections. The whole instrument is well finished.

When placed on test in our standard transformer test panel, the amplification obtained in the first stage following a valve detector was found to be a little below average. The quality was of quite a good order, but its tone was a trifle thin, though clear, and with no signs of roughness.

The insulation resistance between primary and secondary was found to be infinity, and this component is soundly constructed.

Radion Valves

WE have received a number of valves from Messrs. Radions, Ltd. The D.E. .06 type are 3-volt valves, consuming .06 of an ampere, while the anode potential is rated at 30 to 90 volts. When tested with 80 volts on the anode, an average impedance of 25,000 ohms was obtained for several of these valves, with an amplification factor of 6.3, a very satisfactory degree of uniformity being noticed.

When tested in a three-valve set employing one stage of neutralised high-frequency amplification, detector and one stage of low frequency, the results obtained were quite satisfac-

tory for a low-consumption valve of this type. Both as detector and low-frequency amplifier these valves gave quite a commendable performance.

D.E. .34 Type

The D.E. .34 type are designed to take a filament current of .34 at a



The "M.L." low-frequency transformer sent for test by Messrs. S. A. Smith, Ltd.

filament potential of 1.6 to 2 volts. Under test it was found that 2 volts were required to pass the rated filament current while, with 70 volts on

the plate, one of these valves gave an impedance of 25,000 with a maximum amplification factor of 6.3, while the other gave an impedance of 20,000 ohms with an amplification factor of 2.

When tested in a three-valve receiver used for the previous test, these valves were found to function satisfactorily as H.F. and detector, the best results being obtained with a fairly low value of grid-leak.

Power Valve


Another valve produced by this firm is the Radion Pyramid power valve. This is of the 5.5-volt type, consuming a filament current of .34 amperes. It was actually found that a filament potential of 5.2 volts was required to pass the rated current. With an anode potential of 80 volts an impedance of 11,000 and an amplification factor of 6.1 was obtained, while the valves showed a satisfactory degree of uniformity.

Tested in the receiver previously used, excellent results were obtained with these valves, a degree somewhat above the average for H.F. amplification, being obtained. As a rectifier these valves gave results up to the standard whilst for low-frequency amplification they can certainly be recommended.

This New Bretwood Component

(STRAIGHT LINE FREQUENCY CONDENSER)

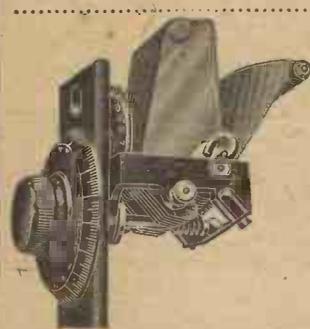has all the essentials of a real Low Loss, Slow Motion, Straight Line Frequency Condenser.



LOW LOSS—Losses minimised, the supports between the fixed and moving plates being two only and as short as possible with very small area surface of round design.

STRAIGHT LINE FREQUENCY—Fixed and moving plates specially designed to give straight line frequency.

VERNIER—Noiseless adjustment with a reduction of 40 to 1, with dial giving 360 degrees registering in all 3,600 degrees between minimum and maximum capacity.

CONSTANCY—This is obtained through unique and rigid design.

HAND and Body Capacities—These are completely eliminated by insulation and the special setting of vanes.

CALIBRATION of Vernier—Calibration over the whole vernier by the automatic indication of numbers and degrees.

High Class workmanship and finish.

All parts guaranteed dead true to within one thousandth of an inch.

Easy to Mount and Connect.

PRICE
17/6

British throughout and carries the Bretwood Guarantee. Obtainable from most Dealers or from Sole Manufacturers

BRETWOOD LTD.,

12, London Mews, Maple Street, London, W.1.

Parr's Ad.

Use

Trelleborgs Guaranteed Genuine Ebonite Panels IN STANDARD SIZES

Highly Polished Surface

Write for Price List and Copy of N.P.L. Report.

Trade Orders to—

TRELLEBORGS EBONITE WORKS LTD.
AUDREY HOUSE, ELY PLACE, LONDON, E.C.1

ARTCRAFT Cabinets, "Popular Type"

Oak or Mahogany Cabinets of Artcraft design and construction are a credit to the set you build

Sizes of "Artcraft Popular Type" Cabinets

Panel Size	Depth	Price in Oak	Price in Mahog.
9 x 6	6 x 6	6/0	10/0
10 x 8	6 x 6	8/0	12/0
12 x 10	8 x 8	12/0	16/0
14 x 10	8 x 8	14/0	19/0
16 x 8	8 x 8	14/0	19/0
18 x 12	9 x 9	21/0	29/0

Baseboards Free. Hinged Lids 1/6 extra

CARRIAGE PAID England & Wales. Illustrated Catalogue Post Free.

The ARTCRAFT Co.

156, CHERRY ORCHARD RD., CROYDON

All Radio Press Cabinets

Parr's Ad.

SUCCESS

RADIO PRODUCTS

For Perfect Radio Reception.

FAMOUS "SUCCESS" SUPER CHOKE



High Impedance Value. Price 18/6

"SUCCESS" SUPER TAPPED CHOKE (4 Tappings)

List No. 132 .. Price 22/6

"SUCCESS" H.F. CHOKE

List No. 126 .. Price 10/6

"SUCCESS" STANDARD L.F. CHOKE

List No. 111 .. Price 10/6


MANUFACTURED BY

Beard & Fitch, Ltd.

34-36, Aylesbury Street, LONDON, E.C.1

Phone—Clerkenwell 8941.

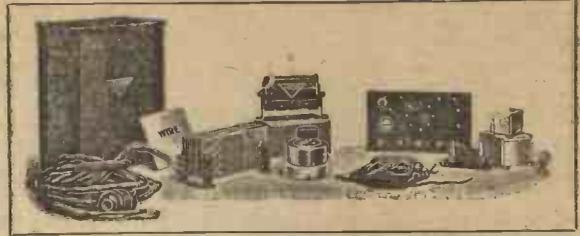BUILD YOUR OWN HIGH TENSION BATTERY ELIMINATOR



"GOLSTONE" CONSTRUCTIONAL KITS.

(Regd.)

At the request of innumerable Radio Constructors we are now offering "Constructional Kits" to build the finest H.T. Battery Eliminators.

The "Kits" are complete with all components ready for wiring and connecting.

Easily fitted with exceptionally efficient results.

DIRECT CURRENT MOI EL

Approx. Voltage Tappings 30, 50, 75, 90 & 130 volts. 5 separate Tappings, Complete "Kit" with full wiring instructions.

£2/5/8

ALTERNATING CURRENT MODEL

Approx. voltage tappings 30, 60, 90 and 130 volts. Dual tappings are taken from each voltage thus providing 8 separate tappings, Complete "Kit" with full wiring instructions.

£4/3/8

Valve extra - 18/6.

Please state voltage of lighting circuit when ordering.

See Catalogue No. R/115 for full particulars.



Extract from "POPULAR WIRELESS" Aug. 21st 1926. "Laboratory Test Report."


"We have had one of these instruments (Golstone A.C. Eliminators) for some time and it has given perfectly satisfactory service.

Running costs are almost negligible and results equal those given by battery supplies."

Large 48-page Catalogue on request. Traders should enclose Business Card for Trade Terms. "Golstone" Products are stocked by the leading Radio Stores. Refuse Substitutes.

RADIAX H.F. COUPLINGS for all Modern Circuits

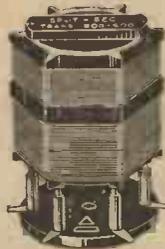These splendid new coils are made in 8 series with 4 wave-length ranges to cover practically all circuits up to date. The T.A. TRANSFORMER AND A.A. AERIAL coils are special for ELSTREE SIX with split secondaries and dual condenser tuning. The separate coil is thus avoided and a neat efficient unit results.



- T.A. Transformer (3 required) each 10/6
- A.A. Aerial Transformer (1 required) 10/6
- 6 Leg Bases for above ... 2/6
- Dual Condenser, .0005 ... 17/0

SPLIT SINGLE COILS for Anode tuning, etc., this is an almost universal type and will be in large demand this season whenever a single split low loss coil is needed.


150/400 6/9. 200/600 6/9. 600/1200 8/3. 1200/3000 9/0
H.F. CHOKE 150/4000 metres ... 8/0

Send 1d. stamp for lists of above, or 3d. for full illustrated catalogue of Modern Radio Components.

RADIAX Ltd., 44, Accessory House, Palmer Place, Holloway, LONDON, N.7.

Parre Ad.

EDDYSTONE SHORT-WAVE UNIT

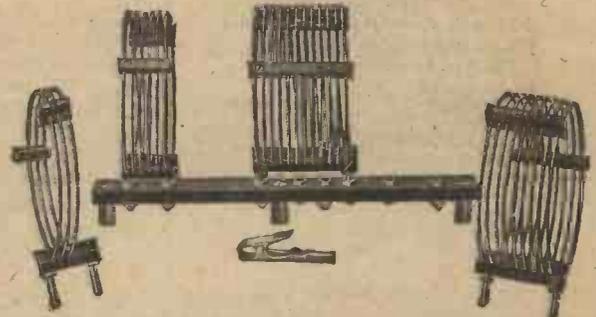


This unit is designed for building into a short-wave receiver as the inductance portion. By combinations of the coils the entire waveband from 15-00 metres can be covered with full efficiency on each stage of wavebands. The coils themselves are rigid and well finished, have a minimum of insulation and each turn is entirely air-spaced.

PRICE 15/6 COMPLETE.

Obtainable from all high-class dealers.

Full instructions and circuit diagram with each unit. Send for catalogue of this and other "Eddystone" radio products.

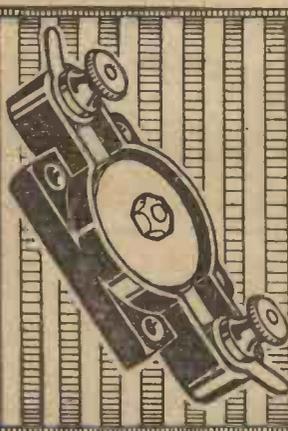STRATTON & CO., LTD., BROMSGROVE ST., BIRMINGHAM.



FINSTON

Fixed Condensers

This season's improved model is worthy of replacing any you may have in your set.

Ruby Mica and Copper Foil Bakelite moulding. Quality Terminals and Sensible Soldering Tags.

Prices:

'0001-2-3-4-5-6 and '001 1/- each

'002-3-4-5 and '003 - 1/9 each

Get them from your Dealer and write us for Complete Illustrated Folder of all Finston Components.

FINSTON MFG. CO., LTD.
45, Horseferry Road, London, S.W.1

Parre Ad.


**STERLING RECEIVERS
SENSATIONAL OFFER!**

Having purchased a large number of Sterling 2 Valve Loud Speaker Sets, we are offering them to the public on unprecedented terms. A genuine Sterling 2 Valve Loud Speaker Set complete, ready for immediate use with D.E. '06 Valves, H.T. and L.T. accumulator, Ariel Equipment and one of our World Famed De Luxe Excellent Loud Speakers. Price £16 15s. 0d., royalties paid. Terms 15/- Deposit and 15 Monthly Payments of 20/-



15/- Deposit.

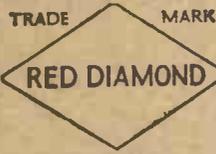Send for one of these Superb sets at once as the number for sale is limited, and when sold cannot be repeated under double the price.
Free Catalogue on Application
The Wireless Distributing Co., Ltd., (Dept. A.C.),
Wireless House, Stoke Newington, N.16



**FINEST
QUALITY
RADIO
COMPONENTS.**
EVERY COMPONENT IS
PERFECT.

R.D.40. Perm. Detector 2/- each.



Of all High-Class Radio Dealers or Sole Makers:
JEWEL PEN Co. Ltd. Radio Dept. 41,
21/22 Gt. Sutton St., E.C.1



**AERMONIC
VALVE 1/9 HOLDER
DON'T PAY MORE**

AERMONIC cost a shilling less—and they're better. Air-spaced. Anti-phonetic. Beautifully sprung. High insulation. Splendid new design. So don't pay more than 1/9. List free

If your dealer does not stock, apply to:—
JAMES CHRISTIE & SONS, LTD.
246, West Street, SHEFFIELD.
London Agents:
**A. F. Bulgin & Co., 10, Cursitor
Street, LONDON, E. C.4**

CABINETS

IN THIS ISSUE:

The Spanspace Three, Oak, 20/-; Mahogany, 23/-
Midget Reflex Rec. Oak, 13/-; Mahogany, 15/6
The Invalids Three
(folding doors), Oak, 35/-; Mahogany, 33/6
BASEBOARDS AND CARRIAGE INCLUDED.
Paragon guaranteed panels supplied.
H. CATTERMOLLE, 227, ANLABY ROAD, HULL.

BUILD YOUR OWN LOUDSPEAKER

WITH A LISSENOLA OR BROWN A and our COMPONENTS. You can construct yourself a handsome CONE type LOUDSPEAKER, or any other approved type, for less than it would cost you for the ordinary cheap horn type. You will obtain VOLUME, CLARITY, and unsurpassed tonal quality. Prices, particulars and illustrations for stamp.
TRADE inquiries invited. Tell your dealer.
Goodman's, 27, Farringdon St., E.C.4
(Tel.: City 4472.)
Also obtainable from Spencer's Stores, 4-5, Mason's Ave., E.C.

Gearing as an Aid to Wireless
(Concluded from page 70)

Filament Control

In certain critical circuits there is need for a vernier control of the filament current. Such circuits are the Ultraudion and Mr. A. D. Cowper's Negadyne. In both these circuits reaction is controlled by the filament temperature and it is extremely important if distant reception is to be successfully carried out that it be possible to bring the set just up to the oscillation point (though without actually letting it oscillate) and hold it there.

The usual vernier adjustment on a filament resistance consists of a single turn of resistance wire over which a separate sliding contact can be moved independently of the main contact. The adjustment is obtained as a rule by means of a small knob concentric with the main control thus allowing the filament temperature to be adjusted with great accuracy.

In one ingenious design only one knob is provided for both coarse and fine adjustment. Through a certain angle the knob varies the resistance over a short length of wire connected in series with the main resistance winding, while on either side of this degree of travel the rheostat slider is moved over the main winding in the usual manner.

A Useful Hint

Another form of control that may occasionally require fine adjustment is the potentiometer. An easy method of obtaining a vernier control is by connecting a 30-ohm filament resistance in series with the potentiometer winding. The method is shown diagrammatically in Fig. 3, from which it will be seen that when the value of the filament resistance is decreased it has the effect of bringing the slider of the potentiometer nearer to the negative end of the potentiometer. Since the resistance of every turn of the filament resistance is probably about 1/5th of that of the potentiometer an adjustment is obtained that is five times as accurate.

Good Control

I have used this scheme with success in a superheterodyne receiver and it gave a delightfully smooth and certain control of oscillation on the long wave side. It is seldom, however, that such careful setting of a potentiometer is required, and it is only necessary in cases such as that mentioned above that this device need be made use of.


Since the whole art of obtaining the best from a receiver lies in making such adjustments as are required with exactness, the beginner who has not yet acquired the skill to do so without adventitious aid is enabled to call to his help the resources of mechanical engineering so that he may, without difficulty, tune in those elusive distant stations.

**SOLDERING SUPERSEDED
"KRISCROS" CONNECTORS**



Prices from 1/- per doz. Send for List.
KRISCROS COMPANY, 50, GRAY'S INN ROAD, LONDON, W.C.1

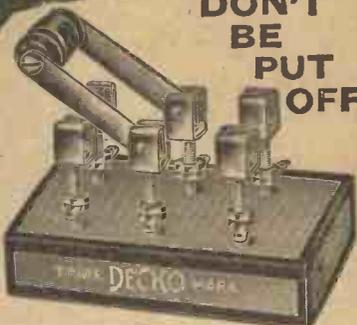DECKOREM BRITISH MADE
RADIO PRODUCTS
REGD TRADE MARK



**DON'T
BE
PUT
OFF!**


ASK TO SEE OUR
S.P.C.O. Price 9d. each.
D.P.C.O. Price 1/6 each.
SEND FOR OUR NEW CATALOGUES,
OBTAINABLE FROM ALL DEALERS OR

A.F. BULGIN & CO.
9-H. CURSITOR STREET
TEL HOLBORN 2072 CHANCERY LANE E.C.6. WORKS CHISWICK
TRADE DECKO MARK

REPAIRS

By specialists skilled in every form of accurate and intricate coil winding.
Headphones, Loud Speakers and Transformers rewound, remagnetised, and reconditioned
EQUAL TO NEW
Owing to the rapid growth of business in our REPAIRS Department, we regret that we find it temporarily impossible to maintain our 24-hours service. Pending extension and reorganisation, a delay of a few days may be unavoidable.

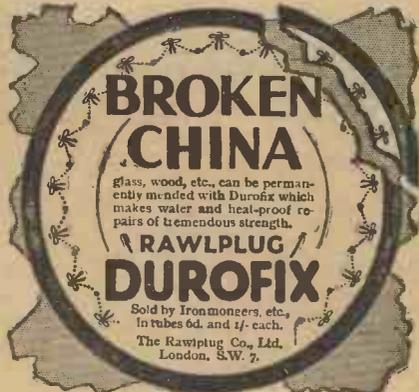VARLEY Magnet Co.
Coil Dept.: Woolwich, S.E.18.
Proprietors: Oliver Pell Control Ltd.



THE "INVALID'S THREE"

—concluded from page 18

Operation

This receiver requires for its operation the use of very high-impedance valves. The detector valve should be a Benjamin S.P.18 Blue, the Cosmos Shortpath Blue Spot, the Ediswan R.C.2, or a similar valve. These valves all have very high impedances of the order of 70,000 to 100,000 ohms, and amplification factors of between 35 and 40.

Valves

A similar valve may be used in the second stage, but in the particular case of the receiver under test it was found that if this was done the second valve was overloaded. It was necessary, therefore, to utilise a valve having a slightly lower impedance, and a Benjamin S.P.18 Green or a Cosmos Green Spot was found to give better results in this stage. The amplification obtained from such an arrangement was naturally a little less than would be obtained if the Blue Spot valve had been used in the second stage, but since the amplification was more than was desired, this sacrifice of signal strength could well be afforded.

The last valve should be any suitable power valve.

High Tension

The H.T. voltage need not be excessive, and excellent results were obtained with only 90 volts high tension. Only one high-tension tapping is employed, so that the battery is uniformly discharged. A particularly interesting point about this receiver is that the consumption of high-tension current with all three valves in use, including a power valve in the last stage, is only 5 or 6 milliamps, when the correct values of grid bias are used. The grid bias used was 1½ volts on the second valve and 9 volts on the last. Of this amount the power valve is responsible for the greater part, since the first two valves both take .7 or .8 of a milliamp. only.

Easy Control

The operation of the receiver is simplicity itself. When the switch is pushed in the receiver is connected to Daventry, and when the switch is pulled out the local station is received.

To tune in to Daventry, therefore, push the switch in and turn the right-hand dial until Daventry is received. If necessary, increase the strength a little with the reaction adjustment, which is the right hand of the two reaction condensers. This is all that is necessary. Now pull the switch out and tune into the local station on the left-hand dial, utilising reaction again if necessary.

The lid of the cabinet may then be closed, the receiver being subsequently controlled with the jack and switch only. The approximate cost of the components for this set is £8.

EXPERTS IN RADIO ACOUSTICS SINCE 1908



TWO NEW CONES
THE ELLIPTICON **THE TABLE CONE**

(Registered Trade-mark)

(Trade-mark)

The handsome cabinet is finished in dark walnut and will admirably harmonise with any decorative scheme or furnishings. The elliptical concavity of this casing reflects the full body of sound with wonderful depth and sweetness. The large vibrating area of the cone, together with a driving unit of special design, brings pleasing and natural tone with plenty of power. The magnets in the cone unit are very large. There is no diaphragm, but a small amature which, reacting to the faintest impulse, faithfully reproduces extremely low and high tones.
 Height 12½ ins., depth 7½ ins., width 10½ ins.

£5:10

The cone is housed in an attractive cabinet of unique design, which has a walnut finish. The circular diaphragm has an extremely sensitive driving unit which brings a wealth of volume with pure and effortless ease. The magnet in the cone unit is unusually large. The instrument is supplied complete with cord connection, and is a proposition of excellent value. It has a genuine claim to be better than any similar instrument at the price.
 Height 10 inches,
 breadth 11½ ins. at
 base, depth 9½ ins.

£2:15

Brandes

From any reputable Dealer.

BRANDES LIMITED, 296 REGENT ST., LONDON, W.1

72.

Service Advertising.

A Genuine Spare-time Business

PATENT-PROTECTED ARTICLES YOU CAN MAKE AT HOME.

Good Profits Guaranteed!

IF you are interested in any way in Wireless, here is a wonderfully interesting way of making money in your spare time. Simply write for particulars, and by return you will be given full details how to make at home a most marvellously improved article which reduces the upkeep costs of all valve sets, gives splendidly efficient service, contains no harmful ingredients whatever, and which is in enthusiastic demand all over the country.



Is your spare time wasted time? Why not turn it to good account and change the whole of your future life for something better and bigger?

There are any inconvenient demand on space. A spare room, an outhouse, or even your kitchen table can be used as your "factory"—a factory without machinery or plant or electric current. The few simple tools needed you are shown how to make yourself, or buy for a shilling or two.

Output Easily Sold.

Each article you make is protected by Royal Letters Patent so that your rights cannot be infringed. The market is immense and only one person per 50,000 of the population is granted a licence to manufacture, thus giving you a huge field for sales at a very big profit. The articles you can produce without any mechanical skill or talent are manifestly superior in quality and value for money to anything on the market, and if you have the least difficulty in disposing of your output to friends, private owners of wireless sets, wireless or electrical dealers in your district, arrangements will be made to take it off your hands, thus guaranteeing your profits!

Think of what you could do with pounds extra per week! Think of the delightful hobby you can pursue instead of finding time hang heavily on your hands! Think of the new and most interesting field opened to you as a responsible "master man"!—and do not delay a single moment in sending the coupon below!

Send this form now for full particulars.

"MAKE-MONEY-AT-HOME" COUPON.

To the ENGLAND-RICHARDS CO., 11-K, King's Lynn, Norfolk.

Sign.—Please send me at once, and FREE, full details of how I can Make Money at Home in my spare time. I enclose 2d. stamps for postage.

Print your name and address boldly in capital letters on a plain sheet of paper and pin this coupon to it.

Wireless Constructor, 15/10/26.

Our Readers' Views

"SINGERS" BY WIRELESS

SIR,—Now that wireless speakers have been drilled in the niceties of pronunciation, what of the sins of the singers?

When a speaker used one of two alternative pronunciations for a word the listener-in did at least know what he meant. Can the same be said of the impression left by certain singer's songs?

It may appear incredible, but it is a fact that there are wireless singers to-day who actually do not trouble about the words of the songs they sing. They think of the voice, of how they

NO "PLANT" NEEDED.
—The Kitchen Table or Any Small Out-building Can Be Your "Factory."

The work is fascinating. You can put in just as many or just as few hours work per week as you desire. The children can help. There is no mess, no smell, nothing disagreeable whatever, nor is

there any inconvenient demand on space. A spare room, an outhouse, or even your kitchen table can be used as your "factory"—a factory without machinery or plant or electric current. The few simple tools needed you are shown how to make yourself, or buy for a shilling or two.



Why not make money this easy, fascinating way? Remember that profits are guaranteed, and that the coupon below brings you FULL particulars FREE!



Mr. S. Hedgeland has designed a loud-speaker on ingenious lines, concealing the mechanism in a picture.

can arrange for a particular effect, and the result of all this posturing is quite disastrous for the unhappy listener-in.

"Nerves" are another frequent cause of failure. I myself do not broadcast, but in my gramophone work I sing into a microphone, and I am never nervous there unless I have been away for a time, and then I take perhaps an hour before I get into my stride.

Many wireless singers, on the other hand, do get a fit of nerves when they remember the millions who are listening to them, and that makes them go for the song with too much voice. Now, economy in voice is the greatest asset of a wireless artist. A whisper is heard where a shout would become a blur, and the singer from whom the listener-in hears every word is the one

(Continued on page 83.)

GLASS TUBES FOR WET H.T. BATTERIES

Best English Make at Lowest Prices

I. ISAACS & CO.,
North London Glass Bottle Works,
106, Midland Road, N.W.1.

Phone: Museum, 4209
Telegrams: Isaglasbot, Kinross, London. Established 100 years.

WIRELESS

Capable, trustworthy men with spare time who wish to substantially increase income required where we are not fully represented. Applicants must have practical knowledge of installation of Set and Aerial, be a Householder or live with parents, and be able to give references; state age and experience. Address Dept. 22, GENERAL RADIO COMPANY LIMITED, Radio House, Regent Street, LONDON, W.1.

SOLODYNE built for 12/6

We construct any Radio Press set at the price of the components plus 2/6 per valve only. First-class workmanship.—LONDON RADIO SUPPLY CO., 11, Oat Lane, London, E.C.2. Phone: City 1977.

AGENTS to sell cheapest and safest non-pumping petrolgas lamp; good income earned converting paraffin lamps into 150 c.p. Titus Light. **TITUS, Kingston, BRIGHTON.**

FROM 1/6 TO £5

CABINETS!

Highly Polished. Trade Marked and Guaranteed. Sending ON APPROVAL at our entire risk in safe delivery. From Stock or Hand-made to Customers' sizes.

Estimates per return. LISTS FREE.

PICKETTS,
(W. Co.),
Cabinet Works, Bexleyheath

TRIUMPH

CUSHION ANTI-MICROPHONIC VALVE-HOLDER

TEST this new holder alongside any other, and you will agree with experts in pronouncing it best.

NO METAL SPRINGS VIBRATIONS QUICKLY DAMPED

Ask your Dealer for free list of **TRIUMPH GUARANTEED COMPONENTS & SETS** or send P.C. mentioning "Wireless Constructor" to:

A. H. CLACKSON, LTD., WHITE HART WORKS, LONDON, N.22

who sings quietly at the microphone mouth.

Surely a little gentle supervision here would be at least as welcome to listeners-in as the selection of the more correct of two correct pronunciations of "idyll"?

Yours faithfully,
PETER DAWSON.

Ealing, W.5.

**A LOUD-SPEAKER
HINT**

SIR,—With regard to the hissing sound caused by overloading a loud-speaker, mentioned by the writer of "Notes and Jottings" in the September WIRELESS CONSTRUCTOR, I have



The diaphragm control of the "picture" loud-speaker shown opposite is accessible from the back of the picture.

found that a by-pass condenser across the primary of the last L.F. transformer (of the order of .001) will cure this without producing the muffling effect too often caused by shunting the loud-speaker itself with a condenser.

Yours faithfully,
M. K. O'DWYER.

Plymouth.

**A SHORT-WAVE
SUCCESS**

SIR,—I have the two-valve set, "Australia on Two Valves," described by Percy W. Harris, M.I.R.E., in the August issue, and at midnight a few weeks ago I tried it for the first time. Will you believe me? At 12.5 p.m. I got W.G.Y., Schenectady, New York, clearly—dance music, then sports news, then time, 6.31 Eastern standard time, and closing down. I use P.M.1 and P.M.2 valves (two-volt). There was not the slightest hand capacity present, so I am delighted.

Yours faithfully,
W. C. SANSON.
Dorchester, Dorset.



Columbia

DRY BATTERIES FOR ECONOMY

DEPRECIATION of cell life and power is actually much less on sets operated and maintained by COLUMBIA Batteries. Initial cost on dry batteries is moderate, they give long service and eliminate the expense of frequent and troublesome accumulator renewals. There is a Columbia Battery for every purpose—use them for every radio battery need. Safe, clean and easily handled, long and inexpensive service and amazing efficiency.

The right battery in the right place naturally means a great deal to your reception. Therefore "How to get the most out of your radio batteries" is a little book which will be most useful to you. It is packed full of really practical and interesting information. These booklets are sent free on request.



Send for "How to get the most out of your radio batteries" and "Choosing and using the right radio batteries." It is astonishing what will result in marked economy in operation and improved quality of reception when you have a little definite knowledge as to the correct use of your radio batteries.

Ask your dealer for Columbia High Tension Battery No. 4780 60 volts, a special size with extra large radio cells. Or Columbia High Tension Battery No. 4770 45 volts (extra heavy duty), for long service and economy. Columbia "A" Dry Cell Battery for Dull Emitter valves will meet heavy current demands and give much longer service than other batteries. All Columbias are fitted with spring clip terminals to ensure quick and secure connections.

ASK ANY GOOD DEALER FOR COLUMBIA.

J. R. MORRIS,

15-19, KINGSWAY, LONDON, W.C.2.

Telegrams: Colcarprod, London.

Telephone: Gerrard, 3038.

Scottish Representative:

John T. Cartwright, 3, Cadogan Street, GLASGOW.

No. 4

In replying to advertisers, please mention THE WIRELESS CONSTRUCTOR.

INDEX TO ADVERTISERS.

	PAGE		PAGE		PAGE
American Hard Rubber Co.	84	Falk, Stadelmann & Co., Ltd.	67	Neutron, Ltd.	48
Aircraft Company (The)	78	Ferranti, Ltd.	71	New London Electron Wks., Ltd.	38
Ashley Wireless Telephone Co., Ltd.	74	Finston Mfg. Co., Ltd.	47, 50, 76, 79	Oldham & Son, Ltd.	40
Autoveyors, Ltd.	67	Formo Co.	46, 50	Ormond Engineering Co., Ltd.	57
Batteries, Ltd.	76	Gambrell Bros., Ltd.	46	Penton Engineering Co.	18
Beard & Fitch	79	Garnett, Whiteley & Co., Ltd.	43, 61, 75	Peto & Radford	35
Bedford Electrical & Radio Co., Ltd.	46	General Radio Co., Ltd.	82	Peto-Scott Co., Ltd.	45, 58
Belling & Lee, Ltd.	47	Gent & Co., Ltd.	39	Pettigrew & Merriman (1925), Ltd.	66, 76
Benjamin Electric Co.	19, 73	Goodman's	80	Picketts Cabinet Works	82
Bird (Sydney S.)	54	Graham (Alfred) & Co.	23	Portable Utilities Co., Ltd.	24, 62
Bowyer-Lowe Co., Ltd.	21	Graham-Farish Mfg. Co.	31	Radiax, Ltd.	79
Brandes, Ltd.	44, 56, 81	Hart Accumulator Co., Ltd.	55	Radio Instruments, Ltd.	Cover iv
Bretwood, Ltd.	78	Hunt (A. H.), Ltd.	52	Rawplug Co., Ltd.	80
British L.M. Ericsson Mfg. Co.	61	Holzman (Louis)	46	Raymond (K.)	59
Brown (S. G.), Ltd.	36	Igranic Electric Co., Ltd.	32	Ripaults, Ltd.	72
Bulgin (A. F.) & Co.	30	International Correspondence Schools, Ltd.	75	Silvertown Co., The	52
Bullen (W.)	75	Isaacs & Co.	82	Smith Farmer & Co.	84
Burne-Jones & Co., Ltd.	31	Jackson Bros.	66	Standard Insulator Co., Ltd.	18
Bush House	46	Jewel Pen Co.	80	Stratton & Co.	79
Carrington Mfg. Co., Ltd.	74	Kriseros Co.	80	Taylor (C.)	72
Cattermole (H.)	80	Laurie & McConnell	56	Taylor (J. H.) & Co.	71
Caxton Wood Turnery Co.	46	Lever (Eric J.)	47	Telegraph Condenser Co., Ltd.	71
Christie (Jas.) & Son	80	Lisson, Ltd.	51	Telephone Mfg. Co., Ltd.	1
Clackson (A. H.)	72, 82	London Electric Wire Co. and Smiths, Ltd.	27	Titus	82
Cleartron Radio, Ltd.	60	London & Provincial Radio Co., Ltd.	50	Trelleborg's Ebonite Works	78
Collinson Precision Screw Co.	75	London Radio Supply Co., Ltd.	82	Valco, Ltd.	72
Cossor (A. C.), Ltd.	17	Lustrolux, Ltd.	27	Varley Magnet Co.	74, 80
Coventry Direct Supplies, Ltd.	54	McMichael (L.), Ltd.	28	Walker (J. M.)	66
Curtis (Peter), Ltd.	64	Makerimport Co.	54	Ward & Goldstone	75
Day (Will)	22	M.A.P. Co.	54	Watmel Wireless Co., Ltd.	72
Dubilier Condenser Co. (1925), Ltd.	35	Morris (J. R.)	83	Weston Elec. Instrument Co.	27
Eastick (J. J.) & Sons	66	Mullard Wireless Serv. Co., Ltd.	Cover ii, 39	Wilkins & Wright, Ltd.	64
Economic Electric, Ltd.	22			Wireless Distributing Co.	80
Electron Co., Ltd.	45			Wolf (M. & A.)	76
England-Richards Co.	82			Wright & Weaire	45
Eton Glass Battery Co.	66				

Panel Talks: No. 1.

Should a panel be a looking-glass?

IS a mirror-like finish desirable on a panel? This is a question which has troubled the minds of most constructors. Here, then, is the answer: It is common knowledge that, after ebonite has been vulcanized, a metallic deposit is left on the panel's surface. This would cause serious leakage and the ebonite is, therefore, sandpapered to remove it. The rough "Matt" surface thus left is well known to ebonite-users. Look at such a panel under a microscope and it will be seen that there are in-

numerable tiny valleys and crevices—each one a "pocket" ready for a dust particle or speck of moisture, so making leakage an easy matter. It is on this account that the new Resiston Panels (like the famous Radion) are supplied ready for use with a highly polished, mirror-like surface, not produced by metallic rolling, but by an exclusive process which seals up the pores of the ebonite and thus provides a hundred-per-cent. insulating material. It's necessary to handle a Resiston panel to appreciate its superfine finish.



Look for the name



on every panel

Made by American Hard Rubber Co., Ltd., 132, Fore St., E.C. 2

Made by the Makers of Radion Panels

G.A. 5988

COUPON QUESTIONS AND ANSWERS.

This Coupon must be accompanied with a 2/6 P.O. and Stamped Addressed Envelope.

"Wireless Constructor," NOVEMBER, 1926.

FREE BLUEPRINT SERVICE COUPON


Wireless Constructor, Vol. III, No. 1, Nov., 1926.

This coupon entitles the reader to one back-of-panel blueprint of any set described in the above issue, and must accompany each postal application.

9d. "FLOR" The World's finest H.T. Accumulators

- 40v—£1 16 8
 - 60v—£2 12 6
 - 80v—£3 6 8
 - 120v—£4 10 0
- In handsome Oak Cabinets with carrying handle.

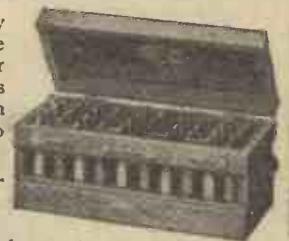Leakage positively eliminated. The patented tubular plate connections reduces evaporation of the electrolyte to the minimum. 1½ amp. hour capacity.



Send to-day for illustrated Brochure dealing with "Flor" H.T. Accumulators.

Smith Farmer & Co. 6, Broad St. Place, E.C. 2.

Dealers send at once for generous trade terms.



Wider scope—greater power from this acquisition

This is to inform you that in accordance with the policy of consolidating this business, we have acquired the "RADIO TRADE JOURNAL" after negotiations covering the last six months.

The "RADIO TRADE JOURNAL" is now merged into "THE WIRELESS DEALER" which will henceforth use the title of the weekly paper as a sub-title.

SUBSCRIPTION RATES:


7/6 per annum (abroad 10/-). Available to the Trade only. Trade card or business heading should accompany every subscription to the SALES MANAGER, Radio Press, Ltd., Bush House, Strand, London, W.C.2.

This is an acquisition, the effect of which will be to enlarge the already wide scope and usefulness of "THE WIRELESS DEALER," giving it an even more powerful and prominent position in wireless trade journalism.

"THE WIRELESS DEALER and Radio Trade Journal" will be published as usual on the 15th of every month. Now is a suitable time to add your name to the growing list of subscribers.

The Contents of the October issue include:
Important Speeches at the Opening of the Exhibition; The Anniversary Dinner; Reviews of: Berlin, New York, Birmingham and Ulster Exhibitions; The forthcoming Manchester Exhibition.

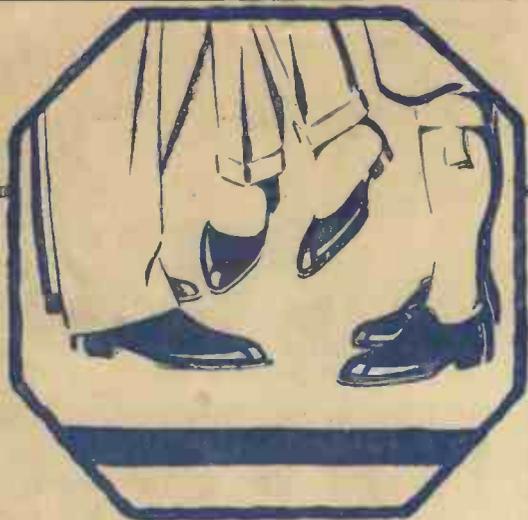The Wireless Dealer
AND
Radio Trade Journal



A Coincidence

BROWN having built his 3-Valve Reinartz, the only set that would satisfy Jones was a Super-het. So the spirit of competition exhausted, Smith had to content himself with a simple "straight" 2-valver.

The sets duly completed and each delighting its respective owner with an unique and previously unheard-of perfection of tone, the three friends ran into one another just outside the recharging station.

The topic of conversation is, of course, obvious. And the coincidence is perhaps just as obvious. All three had used R.I. Multi-Ratio Transformers in their L.F. stages. All three were getting the same perfect L.F. amplification, although the circuits were entirely different, and various types of valves were being used.

That sort of treatment, however, doesn't trouble the R.I. Multi-Ratio Transformer, which is built for all such varying conditions. It is the one transformer to solve all L.F. amplifying difficulties in any set from a 2-valve to a super-heterodyne.

Try it yourself, you'll notice at once the increased volume and purity of tone that other transformers always seem to lose. It certainly costs a little more but to a discriminating listener that little more is a very sound investment.

PRICE 27/6

Write for the new R.I. Catalogue.

THE MARK OF



BETTER RADIO



THE REASON WHY

Because the R.I. Multi-Ratio Transformer offers a choice of seven different ratios and nine impedance values you can rest assured when you fit it in your set, no matter what circuit or valves you are using, that the reproduction will be of the maximum power and purity. The R.I. Multi-Ratio Transformer gives perfect L.F. amplification with any valve in any circuit.



CRYSTAL DETECTION PERFECTED

The R.I. Permanent Mineral Detector is now manufactured with a special device which completely protects the sensitive crystals during adjustment.

With this last improvement we can honestly say that the present model is unsurpassed in any way for crystal rectification.

For good rectification a crystal detector cannot be excelled, for perfect rectification you'll need the R.I. Permanent Mineral Detector.



Clip Mounting type 6/-
Panel " " with ebonite cap 6/6



Advt. R.I., Ltd., 12, Hyde Street, New Oxford Street, London, W.C.1.

HOW TO MAKE THE MIDGET REFLEX RECEIVER

PRICE 1/6

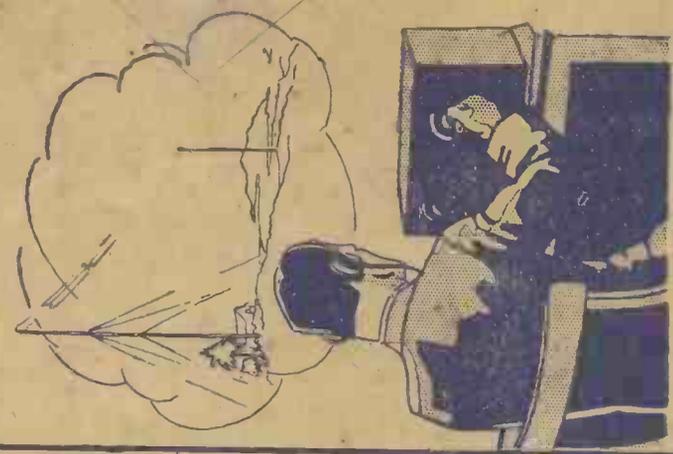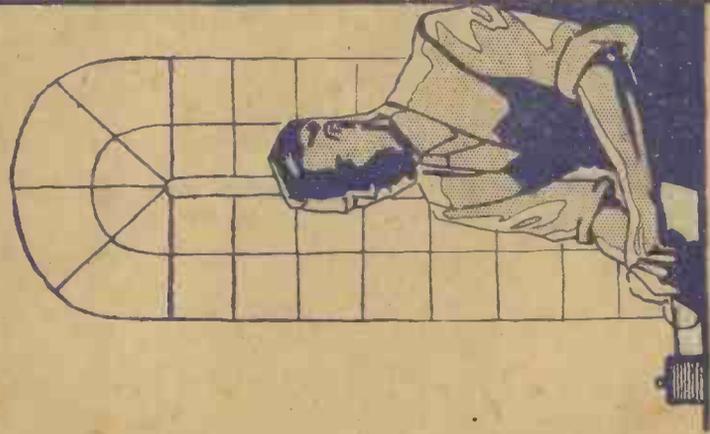



The Midget Single-Valve Reflex Receiver

By A. S. CLARK

COMPLETE CONSTRUCTIONAL DETAILS


This receiver is particularly easy to operate, since there is only one tuning control and a reaction adjustment, and even the novice can build it. Full size blue-prints, detailed instructions, reproductions of photographs, etc., are given.

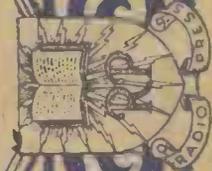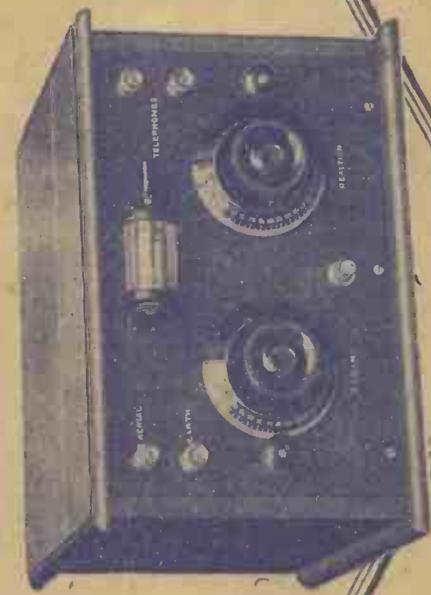
Presented as a Free Gift Supplement to "The Wireless Constructor" for November, 1926. Published by Radio Press, Ltd., Bish House, Strand, London, W.C.2.



THE MIDGET REFLEX RECEIVER.

RADIO PRESS LTD

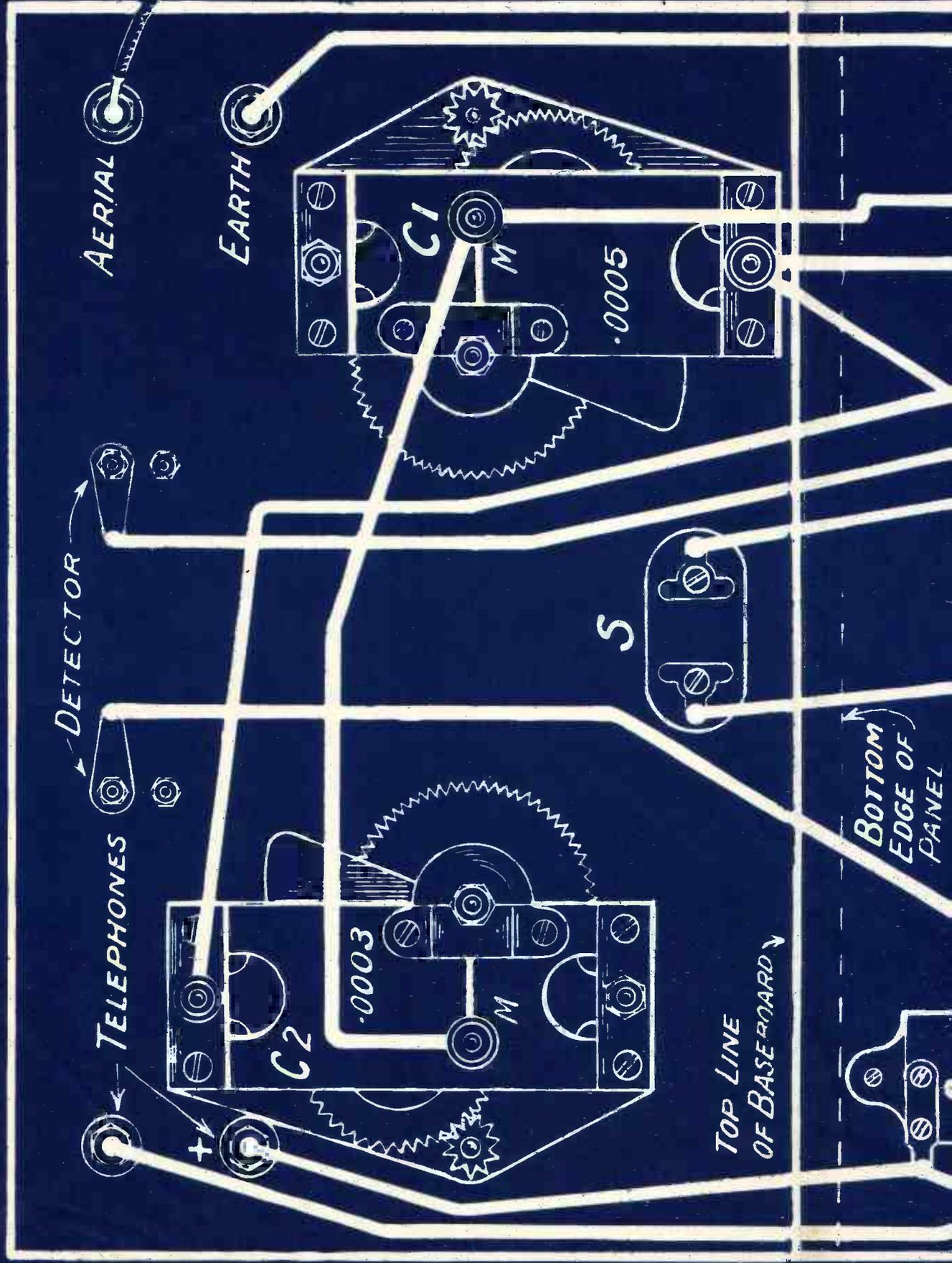



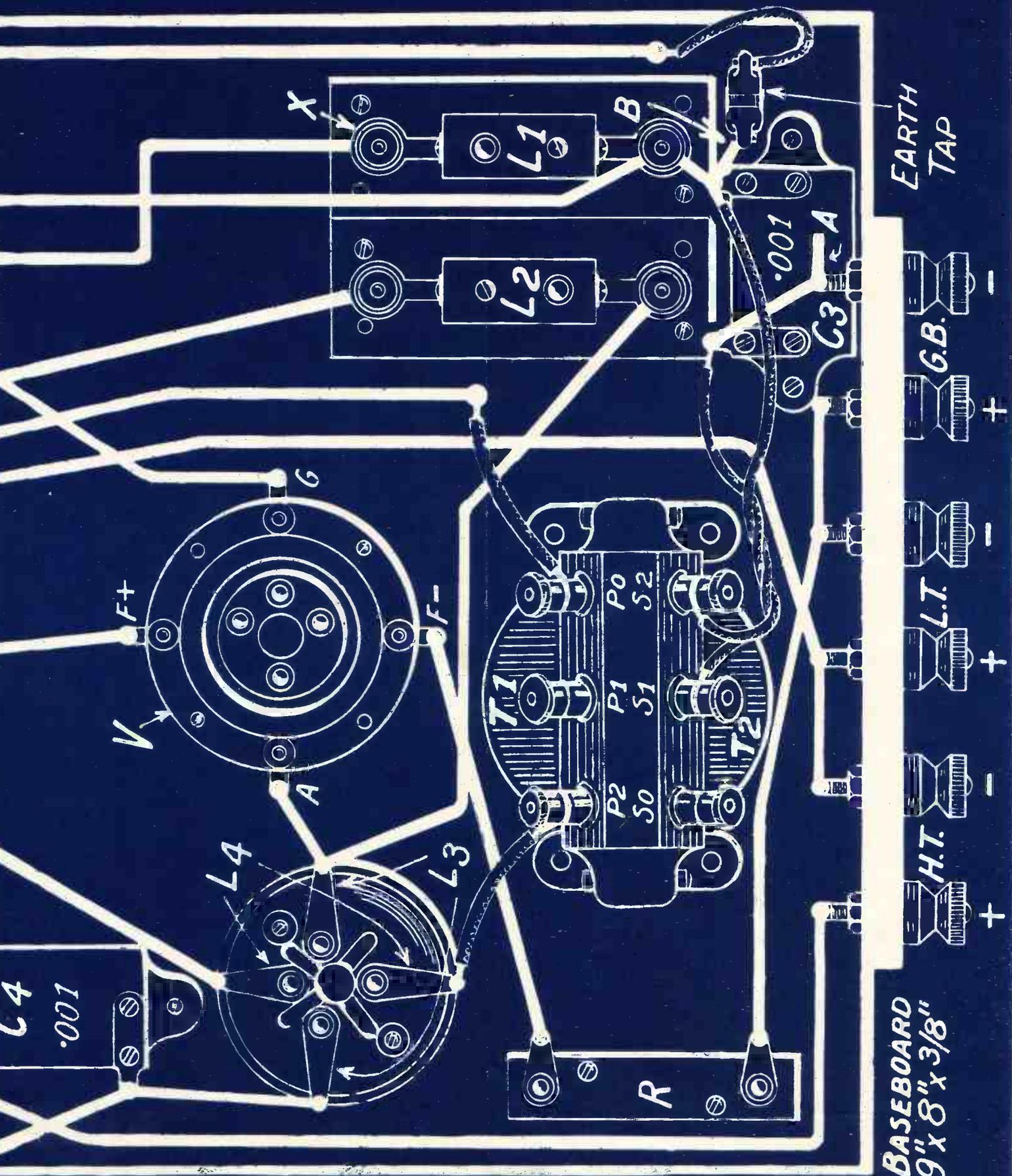


EARTH
TAP

- G.B. -
- + -
- L.T. -
- + -
- H.T. -
- + -

BASEBOARD
9" x 8" x 3/8"

L4
.001

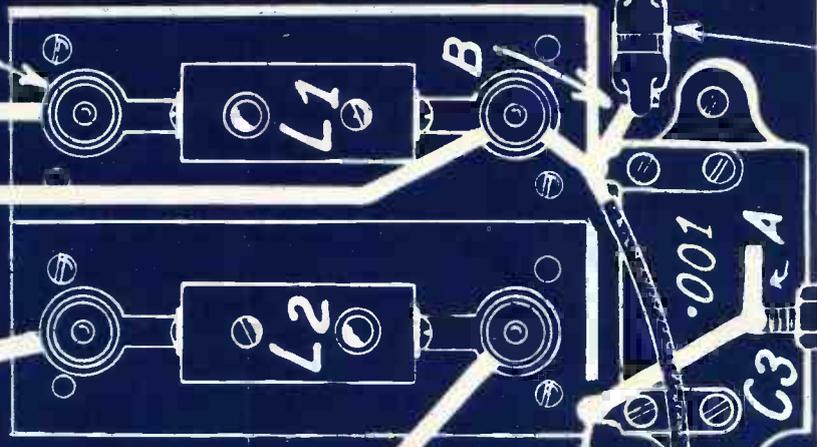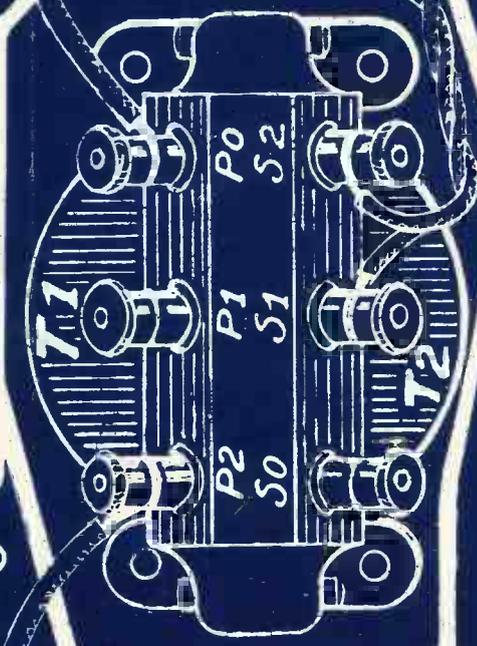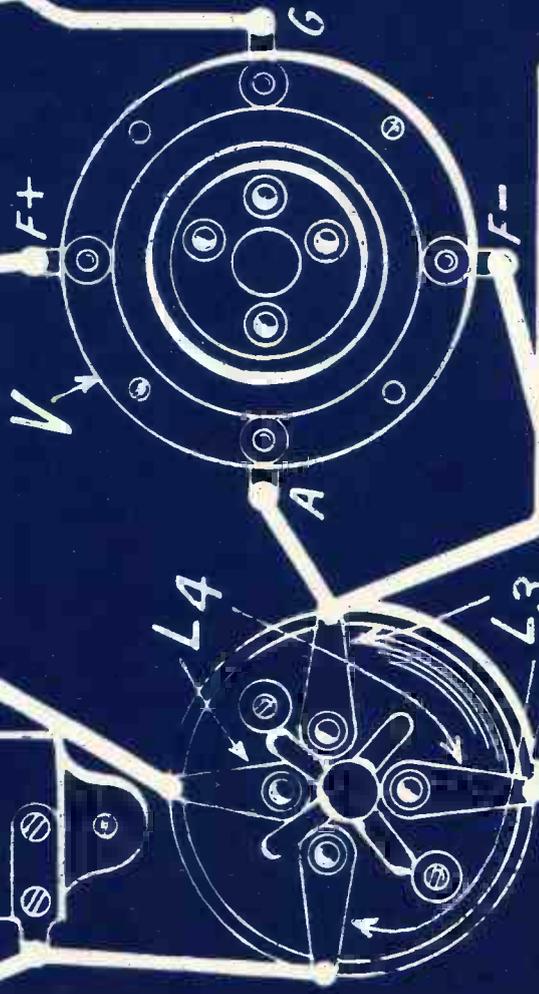

.001
G3
A

R

L1

L2

L4

L3

V
F+

F-

A

X

B

P0

P1

P2

S2

S1

S0

T1

T2

H.T.


L.T.

G.B.

BASEBOARD
9" x 8" x 3/8"

THE MIDGET REFLEX RECEIVER.

RADIO PRESS LTD

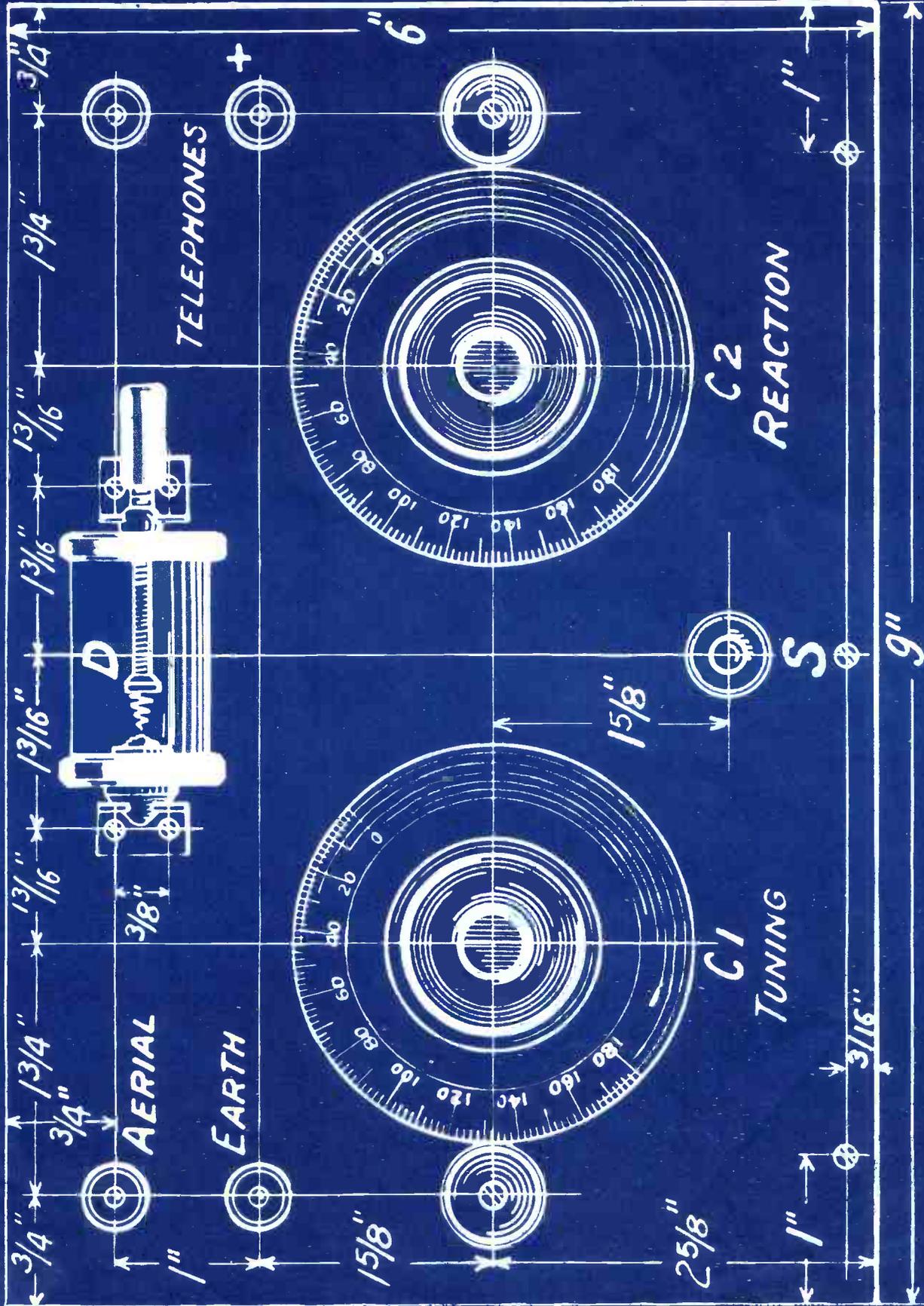

Supplement to "The Wireless Constructor," November Issue, 1926.

HOW TO MAKE THE MIDGET REFLEX RECEIVER



By A. S. CLARK.

RADIO PRESS LTD., BUSH HOUSE,
STRAND, LONDON, W.C.2.

400 P.M. filaments will lift a man!



The life of a valve is not one minute longer than the life of its filament.

Therefore, for real value, see that your valves have **STRONG FILAMENTS.**


The wonderful P.M. Filament offers you three times more for your money. It is so tough that even after 1,000 hours' life it can be tied in knots and cannot be broken except by the very roughest handling—*result, safety against accidents.*

There is more than strength in the P.M. Filament. It has up to 3 times greater length and up to 5½ times greater emission than an ordinary filament. *This is where the P.M. Filament gives you real value.*

Another big point, the P.M. Filament requires only one-tenth ampere giving 7 times the life to each of your accumulator charges.

For great economy, great life and great results secure the valves with

THE WONDERFUL P.M. FILAMENT

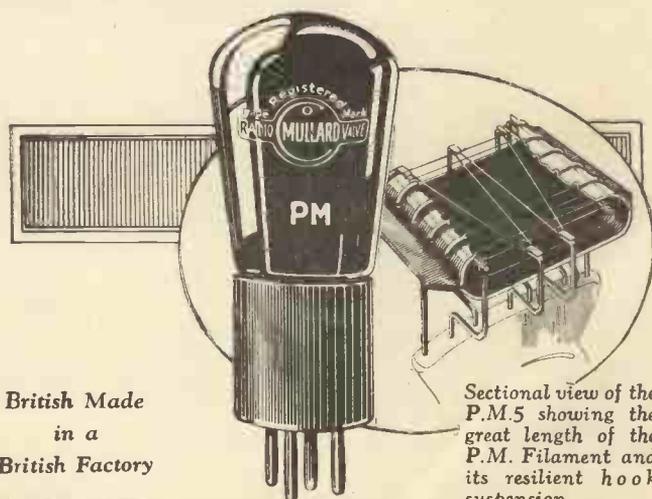

**British Made
in a
British Factory**

Sectional view of the P.M.5 showing the great length of the P.M. Filament and its resilient hook suspension.

- For 4-volt accumulator or 3 dry cells
- THE P.M.3 (General Purpose) 0'1 amp. 14/-
- THE P.M.4 (Power) 0'1 amp. 18/6
- For 6-volt accumulator or 4 dry cells
- THE P.M.5 (General Purpose) 0'1 amp. 18/6
- THE P.M.6 (Power) 0'1 amp. 18/6
- For 2-volt accumulator
- THE P.M.1 H.F. 0'1 amp. 14/-
- THE P.M.1 L.F. 0'1 amp. 14/-
- THE P.M.2 (Power) 0'15 amp. 18/6

These prices do not apply in Irish Free State

Mullard

THE · MASTER · VALVE

THE MULLARD WIRELESS SERVICE CO., LTD., MULLARD HOUSE, DENMARK ST., LONDON, W.C.2.

THE MIDGET SINGLE VALVE REFLEX RECEIVER.

Reflex receivers are by no means so dead as some people would have us believe. It is true the old circuits are more or less obsolete, but their place is being taken by new ones. The early reflex circuits suffered from several disadvantages, which are disappearing in the modern designs. The circuit used in the set described in this envelope has been so arranged that nearly all the disadvantages usually found in a single valve reflex receiver are absent. Apart from the adjustment of the crystal detector, there are only two controls, thus making it much easier to tune in distant stations than if there had been the usual three. A form of Reinartz reaction has been employed, which gives very smooth control, and is vastly superior to coupling the grid coil to a tuned plate circuit.

SELECTIVITY.

Another great advantage of the set is sharp tuning. With some reflex receivers it is impossible to cut out the local station, it being heard all round the dial, but with the Midget reflex it is possible to enjoy listening to other broadcast stations on a wavelength near to that of the local station, while the latter is working.

THE APPEARANCE.

On looking at the photograph of the front of the set, it will be seen that it is very neat and has a symmetrical layout. The panel is small, and the general compactness of the set makes it well worthy of its name. The valve and coils are enclosed inside the cabinet, the only external accessories being the telephones and the batteries. Terminals for the aerial, earth and telephones will be seen on the front panel; those for the batteries are carried on a strip of ebonite at the back of the set. Condensers with a slow-motion control are used to facilitate fine tuning, the small knobs at the sides of the variable condenser dials being for this purpose. A fixed resistor has been employed to remove one of the variable controls, and a switch on the panel enables the set to be turned on and off.

THE CIRCUIT.

Reference to the theoretical diagram will help to make clear the working of the circuit. It will be seen that in order to obtain good selectivity a tapped coil is used for the tuned circuit

of the valve. The aerial is connected to one of the taps on this, which may be an X coil, and so produces an "aperiodic" aerial circuit. As far as the H.F. currents are concerned the secondary of the L.F. transformer has no effect due to the by-pass condenser across it.

In the plate circuit is connected one winding of a semi-aperiodic transformer, across the other winding of which are the crystal detector and primary of the L.F. transformer. This semi-aperiodic transformer does not need tuning, and thus one control is dispensed with.

HOW IT WORKS.

The H.F. currents which are applied by the tuned circuit L1 C1 across the grid and filament of the valve, appear in an amplified form at the plate of the valve. The transformer L3 L4 passes them on to the crystal detector for rectification. After this the currents pass through the primary of the L.F. transformer T1 T2 and the resulting secondary potentials are applied across the grid and filament of the valve for audio amplification. Finally the varying currents reach the telephones where they are converted into sound waves.

Grid bias is employed to make certain that the valve is worked on the best part of its characteristic for amplification, namely the straight part to the left of the "zero" line and also to avoid rectification by the valve taking place.

COMPONENTS REQUIRED.

A list of all the parts required to build this set is given, together with the names of the manufacturers who made the actual ones used in the original set. It is not, however, imperative that these makes should be adhered to, since any other suitable components of good quality may be substituted, and should give as good results. As far as the L.F. transformer is concerned, it is as well to keep to the same make, as this is tapped, and makes it possible to find the best ratio for any valve.

The components are as follows ;-

One ebonite panel 9 in. x 6 in. x $\frac{3}{16}$ in. (Peto-Scott Co. Ltd.)
One cabinet for same with baseboard 9 in. x 8 in. x $\frac{3}{8}$ in. (Peto-Scott Co. Ltd.)
One ebonite strip 6 in. x 2 in. x $\frac{1}{4}$ in. (Peto-Scott Co. Ltd.)
One .0005 variable condenser with slow-motion control, low-loss type (Jackson Bros.)

One .0003 variable condenser, the same as before (Jackson Bros.)
One crystal detector (Burndept Wireless Ltd.)
One "push-pull" on and off switch (Igranic Electric Co. Ltd.)
Ten terminals.
One multi-ratio L.F. transformer (Radio Instruments Ltd.)
One Lotus base-board mounting anti-vibratory valve holder (Garnett Whiteley & Co. Ltd.)
One ordinary base-board mounting valve holder (Burne-Jones & Co. Ltd.)
One Magnum aperiodic H.F. transformer 300-600 metres (Burne-Jones & Co. Ltd.)

If it is desired to use the set on the long waves another transformer covering the required wavelength should be purchased.

One fixed resistor base and fixed resistor to suit valve to be used. (Burne-Jones & Co. Ltd.)
Two single coil mounts (Beard & Fitch Ltd.)
Two .001 fixed condensers (Dubilier Condenser Co. Ltd.)
Glazite wire.
Packet Radio Press panel transfers.
One small spring clip.

It is as well before commencing any of the constructional work to collect all the necessary components together so that there will be no delay once the work has been started.

CONSTRUCTION.

The constructional work involved in making this set is not difficult and does not require great skill. If the instructions are carefully followed it is possible for an absolute novice to turn out a set which will work well and give him satisfaction.

First take the blueprint of the front of the panel, which will be found in this envelope, and with this as a guide mark the points at which holes have to be drilled in the panel. This may be done in one of two ways. First, the blueprint may be laid on the panel and the hole positions pricked through with a sharp instrument such as a scribe or secondly, the panel may be marked out with a square and scribe according to the dimensions shown on the blueprint. If this latter method is followed, there is no need to reverse the positions of the holes, since the panel is symmetrical about the vertical centre line. The blueprint is drawn looking at the front of the set, and, of course, the panel has to be marked out on its back.

DRILLING.

Having ascertained the positions for the holes, all points should be centre punched before drilling. Clearance size drills are used in all cases, and in making the three large holes for the two variable condensers and the switch, a small size drill should first be used so as to make a small hole to guide the large drill. No difficulty will be found in the drilling, so we can pass on to the next step, that is, mounting the components.

MOUNTING THE COMPONENTS.

Before any components are mounted, it is as well to tin all points on them to which soldered connections are to be made. This does not, of course, apply to terminals, which should be fixed in place before tinning, although it is as well to do this before the other parts are mounted.

Mount the components on the panel first. Then with the base-board in the cabinet, screw the panel and terminal strip to it. This will ensure that the set will fit into its cabinet when it has been completed. The remaining components can now be screwed to the baseboard. Follow the layout on the back of panel blueprint so that you are sure to allow room for the valve and coils when these are put in. Also take care to put the coil mounts the same way round as shown or trouble may result from more than one source.

WIRING.

Attention can now be turned to the wiring. It is as well to take plenty of time over this, since neat wiring not only enhances the appearance of a set greatly, but also adds to its efficiency. Glazite wire is used, and since this is covered with an insulating material, trouble which might be caused by two wires touching is obviated. A list of connections to be made is given under wiring instructions. These are arranged in the order in which it is best to make the connections and should be followed in conjunction with the wiring shown on the back-of-panel blueprint. The two flexible wires which run to the secondary of the transformer are twisted together for neatness. Be careful in arranging the wires, that they do not run in positions which may foul the valve, H.F. transformer or coils. To avoid this it is best to have these in place when bending the wires into shape. When the wiring is complete, the panel transfers may be affixed, and the lettering required is shown on the blueprints.

VALVES TO USE.

This receiver will work with any general purpose valve, such as a bright emitter, one of the .06 type or one with a different rating altogether. Of course the right type of resistor must be used, and when ordering it is best to specify the type of valve to be used, and the voltage of the accumulator which will be employed. A valve of the small power type is very effective and gives extremely good volume on the local station, but sometimes is not quite so good for distant reception. In all cases it is necessary that the valve is worked properly otherwise it may partially rectify. This can be avoided by using sufficient H.T. and grid bias. How to tell whether the valve is working properly is explained later. Different transformer ratios should be tried to find the one which best suits the valve in use. This is easily accomplished by means of the flexible leads provided as connections to the L.F. transformer.

TYPES OF COILS.

Any type of plug-in coil may be used when direct coupling is employed. The flex lead from the aerial being placed under the terminal nearest the panel on the aerial coil holder and marked X. If selectivity is not great enough when direct coupling is employed, an X coil or a centre tapped coil may be tried for the aerial circuit. In this case the aerial lead is taken to one of the X coil taps or the centre tap. It will be as well to try all three since in some cases it is possible that a loss of signal strength might result. This, of course, depends on local conditions entirely, especially on the particular aerial which is being used.

TESTING THE SET.

When the set is first used, it will be found best to start with a general purpose valve with a high-tension voltage of from 60 to 80 volts. Direct coupling should also be used, and a No. 35 or No. 50 coil inserted in the aerial socket. The value of the reaction coil varies under different conditions, but a No. 25 or No. 35 should be found suitable.

ADJUSTING THE GRID BIAS.

The grid bias terminals are temporarily shorted. With the reaction condenser at its zero position and with the catwhisker touching the crystal detector, tune in the local station. Now remove the

catwhisker from the crystal. You will probably still be able to hear the local station at some strength. Now connect up the grid bias and adjust it to such a value that signals are weakened as much as possible. The catwhisker can now be replaced and the effect of the reaction condenser tried.

REACTION ADJUSTMENTS.

The control of reaction will be found very smooth and to build up strength very well. If you are very near to your local station, it is possible that you will not notice much improvement on that station by increasing reaction.

Always use the reaction control judiciously, increasing and decreasing slowly in conjunction with the tuning condenser ; otherwise you may cause interference, because once past the useful point of reaction, the set soon gets into self oscillation.

RESULTS.

Loud-speaker results may be expected up to about 6 miles with the average aerial, or up to about 8 miles with an extra good one. It is possible to receive a few other broadcast stations at very good telephone strength while the local station is working.

As many as 10 stations on one coil have been tuned-in easily and at very good strength when the local station was closed down.

These include Birmingham, Bournemouth, Barcelona, Hamburg, and Ecole Superieure, but all were not identified since no wavemeter was used at the time.

DAVENTRY.

Long wave broadcasting stations may be received, appropriate coils being used and, of course, a long wave H.F. transformer. With a No. 150 coil in the aerial circuit and a No. 75 as reaction, Daventry was received at very good headphone strength.

EARTH CONNECTION.

So far no mention has been made about the earth clip. As will be gathered from the wiring blueprint, this may be attached to either side of the secondary of the L.F. transformer. Not much difference

will be noticed between the two sides, but where there are electric light mains in the house and interference is experienced in the form of a hum, it will often be found best to connect the earth so that the secondary of the transformer is not in the aerial circuit. To do this the clip is put on to the "B" connection.

WIRING INSTRUCTIONS.

Join GB + to LT- ; LT- to one side of R; join other side of R to F- of V.

Join F+ of V to one side of S. Join other side of S to LT+; LT+ to H.T.-.

Join one side of L4 to one side of Detector. Join other side of Detector to length of Glazite with flex wire on end for one side of TI.

Join flex lead to remaining side of L4 for connection to remaining side of TI.

Join P of V to one side of L3; same side of L3 to socket of holder for L2.

Join G of V to fixed plates of C1; fixed plates of C1 to socket of holder for L1.

Join fixed plates of C2 to pin of holder for L2.

Join moving plates of C2 to moving plates of C1; moving plates of C1 to pin of holder for L1; pin of holder for L1 to one side of C3, and leave wire projecting from here for earth clip.

Join remaining side of C3 to GB-, and leave wire projecting from here for earth clip.


Join flex leads to both sides of C3 for connection to T2.

Join Earth to length of Glazite with flex lead on end for earth clip.

Join flex lead to Aerial for connection to L1.

Join telephone+ terminal to one side of C4; same side of C4 to H.T.+.

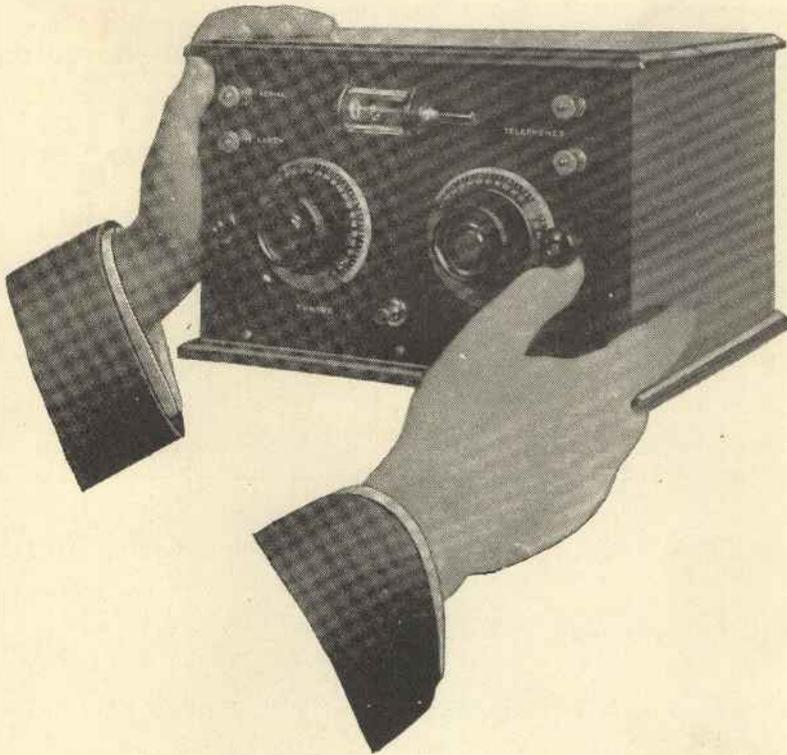Join remaining telephone terminal to remaining side of C4; same side of C4 to remaining side of L3.




THE
COMPLETED
SET:


The Midget Receiver certainly justifies its name, being smaller than many forms of hand camera.

Its proportions are also very pleasing to the eye.

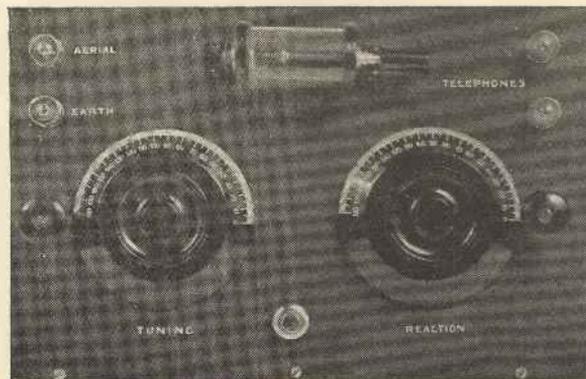A plan view of the panel layout, showing the symmetrical disposition of the components. Notice the perfect balance, which simplifies the task of panel drilling.



It's Right in every base!

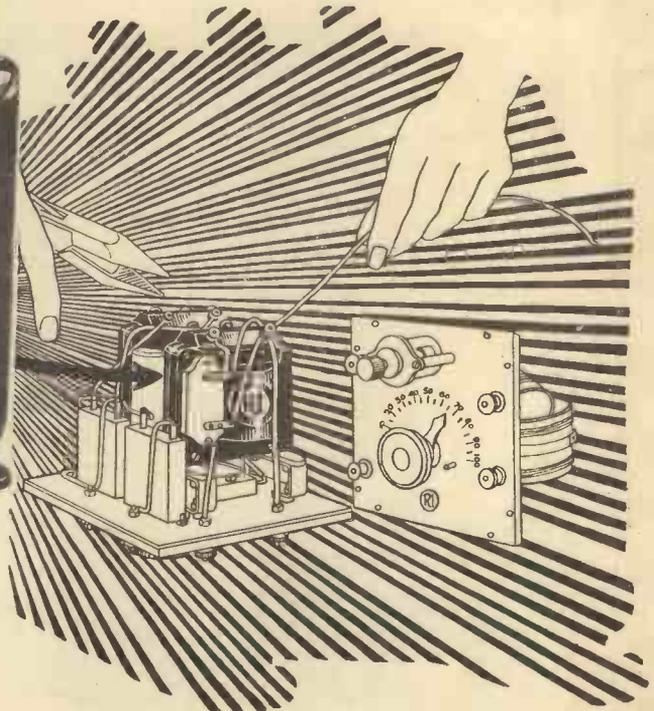


You can rest assured when you fit the R.I. Multi-Ratio Transformer in your set, no matter what circuit or valves you are using, that the amplification will be of the maximum power and purity obtainable.

You need have no hesitation because the R.I. Multi-Ratio Transformer is designed to meet all requirements—7 ratios to give perfect amplification in any stage in any circuit—3 Impedence values to operate correctly in conjunction with any valve—all facts to give you complete confidence in the success of your set.

Further than these you have the knowledge that this instrument is an R.I. Product, that its design and execution are the finest examples of British craftsmanship.

PRICE 27/6

Write for new R.I. Catalogue.

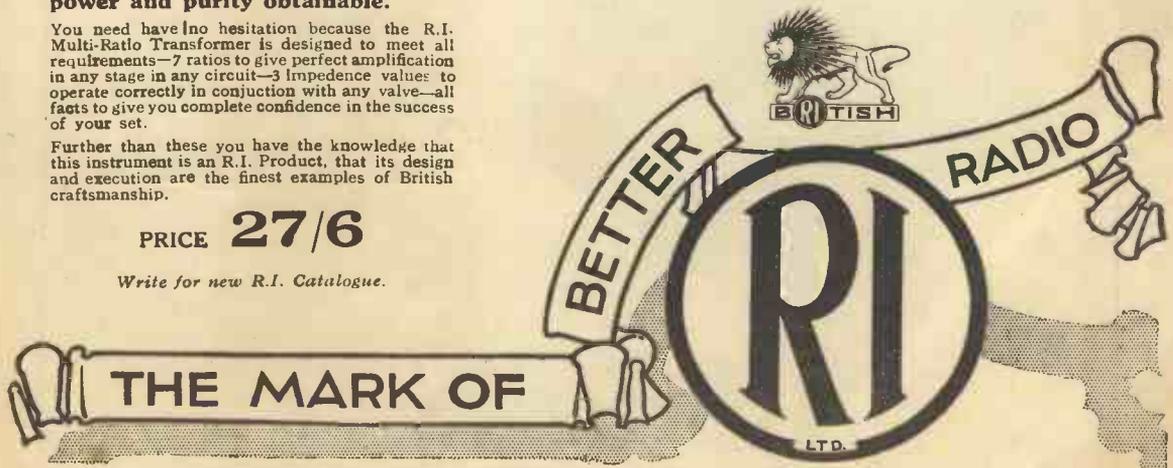

Advt. R.I. Ltd., 12, Hyde Street, New Oxford Street, London, W.C.1.