

Design competition - 3 prizes worth £900 in total

ELECTRONICS WORLD



MARCH 2001 £2.80

Free gift with this issue:
555 timer that runs off 1.5V

Circuit ideas:

PIC frame check for PPP

Road ice warning

Automatic antenna
attenuator

Dry cell charger

Prog. voltage reference

Crystal ref. sinewave

Simple theft alarm

Power chopper

Planar resistor design

Wireless 32-channel voltmeter

Telnet

Tel: 02476 650702

Quality second-user test & measurement equipment

NEW PHONE CODE FOR COVENTRY 02476

Hewlett Packard	
8642A – high performance R/F synthesiser (0.1-1050MHz)	£4750
3335A – synthesiser (200Hz-81MHz)	£2400
Hewlett Packard	
436A power meter and sensor (various)	from £750
437B power meter and sensor (various)	from £1100
Hewlett Packard	
Wandel & Goltermann	
SPECIAL OFFER	
PCM-4 PCM Channel measurement set (various options available)	from £5500
Marconi 6310 – programmable sweep generator (2 to 20GHz) – new	
	£3250
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£4000
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£6250
Hewlett Packard	
5370B – universal time interval counter	£1500
Hewlett Packard 8662A synth. sig. gen. (10kHz to 1280MHz)	£8250
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	
	£2,500

OSCILLOSCOPES

Gould 400 20MHz - DSO - 2 channel	£800
Gould 1421 20MHz - DSO - 2 channel	£600
Gould 4068 150MHz 4 channel DSO	£1500
Gould 4074 100MHz - 400 Ms/s - 4 channel	£1350
Hewlett Packard 54201A - 300MHz Digitizing	£995
Hewlett Packard 54600A - 100MHz - 2 channel	£750
Hewlett Packard 54610A - 500MHz - 2 channel	£1850
Hewlett Packard 54502A - 400MHz-400 MS/s - 2 channel	£1800
Hitachi V162/V12/V222/V302B/V302F/V353F/V550B/V650F	from £125
Hitachi V1100A - 100MHz - 4 channel	£900
Intron 2020 - 20MHz - Dual channel D.S.O. (new)	£450
Iwatsu SS 5710/SS 5702 -	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lecroy 9354M 500MHz - 2 Gs/s - 4 channel	£6000
Lecroy 9314L 300MHz - 4 channels	£3000
Meguro MSO 1270A - 20MHz - D.S.O. (new)	£450
Philips PM3094 - 200MHz - 4 channel	£1750
Philips 3295A - 400MHz - Dual channel	£1600
Philips PM3392 - 200MHz - 200Ms/s - 4 channel	£1995
Philips PM3070 - 100MHz - 2 channel - cursor readout	£750
Tektronix 465 - 100MHz - Dual channel	£350
Tektronix 464/466 - 100MHz - (with AN. storage)	£350
Tektronix 475/475A - 200MHz/250MHz -	from £450
Tektronix 468 - 100MHz - D.S.O.	£650
Tektronix 2213/2215 - 60MHz - Dual channel	£350
Tektronix 2220 - 60MHz - Dual channel D.S.O.	£995
Tektronix 2235 - 100MHz - Dual channel	£600
Tektronix 2221 - 60MHz - Dual channel D.S.O.	£995
Tektronix 2245A - 100MHz - 4 channel	£900
Tektronix 2440 - 300MHz/500 MS/s D.S.O.	£2450
Tektronix 2445A/2445B - 150MHz - 4 channel	£1000
Tektronix 2445 - 150MHz - 4 channel + DMM	£1200
Tektronix TAS 475 - 100MHz - 4 channel	£995
Tektronix 7000 Series (100MHz to 500MHz)	from £200
Tektronix 7104 - 1GHz Real Time - with 7A29 x2, 7B10 and 7B15	from £2500
Tektronix 2465/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2467B - 400MHz - 4 channel high writing speed	£4750
Tektronix TDS 310 50MHz DSO - 2 channel	£750
Tektronix TDS 320 100MHz 2 channel	£850
Tektronix TDS 340A 100MHz DSO - 2 channel	£1250
Tektronix 544A 500MHz 4 channel	£4950

SPECTRUM ANALYSERS

Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£850
Anritsu MS 610B 10KHz - 2GHz - as new	£3500
Advantest/TAKEDA RIKEN - 4132 - 100KHz - 1000MHz	£1500
Hewlett Packard 8756A/8757A Scaler Network Analyser	from £1000
Hewlett Packard 853A Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2750
Hewlett Packard 182T Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2250
Hewlett Packard 8568A (100Hz - 1500MHz) Spectrum Analyser	£3500
Hewlett Packard 8568B - 100Hz - 1500MHz	£5250
Hewlett Packard 8567A - 100Hz - 1500MHz	£3995
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£5995
Hewlett Packard 8754A - Network Analyser (4MHz-1300MHz)	£1900
Hewlett Packard 8591E 9KHz-1.8GHz	£4250
Hewlett Packard 3561A Dynamic signal analyser	£3995
Hewlett Packard 35660A Dynamic signal analyser	£3250
IFR A7550 - 10KHz-1GHz - Portable	£1950
Meguro - MSA 4901 - 30MHz - Spec.Analyser	£700
Meguro - MSA 4912 - 1 MHz - 1GHz Spec. Analyser	£995
Tektronix 2712 Spec. Analyser (9KHz - 1.8GHz)	£3950
Wandel & Goltermann TSA-1 system analyser (100Hz-180MHz)	£2750
Wiltron 6409 - 10-2000MHz R/F Analyser	£1750

Radio Communications Test Sets

Marconi 2955	£2000
Marconi 2955B	£4500
Anritsu MS555A2	£1200
Hewlett Packard 8922B (GSM)	£6950
Schlumberger Stabilock 4031	£3500
Schlumberger Stabilock 4040	£1500
Racal 6111 (GSM)	£1750
Racal 6115 (GSM)	£3995
Rhode & Schwarz CMTA 94 (GSM)	£4995



Fax 02476 650 773

MISCELLANEOUS

Eaton 2075-2A - Noise Gain Analyser	at £2750
Fluke 5100A/5100B/5200A - Calibration Units (various available)	from £1000
Fluke 2620 Data Buckets	£500
Hewlett Packard 339A Distortion measuring set	£1200
Hewlett Packard 435A + 435B Power meters	from £100
Hewlett Packard 778D Dual-Directional Couplers	£650
Hewlett Packard 3488A - Switch/Control unit	£475
Hewlett Packard 3457A multi meter 6 1/2 digit	£950
Hewlett Packard 3784A - Digital Transmission Analyser	£4500
Hewlett Packard 3785A - Jitter Generator & Receiver	£1250
Hewlett Packard 5385A - 1 GHz Frequency counter	£950
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6622A - Dual O/P system p.s.u.	£1250
Hewlett Packard 6624A - Quad Output Power Supply	£2000
Hewlett Packard 6632A - System Power Supply (20v-5A)	£800
Hewlett Packard 811A Pulse/Function Generator (1Hz-20MHz)	£1250
Hewlett Packard 8112A - 50MHz Pulse Generator	£2250
Hewlett Packard 8350B - Sweep Generator Mainframe	£2000
Hewlett Packard 8656A Synthesised signal generator	£850
Hewlett Packard 8656B Synthesised signal generator	£1450
Hewlett Packard 8657A Synth. sig. gen. (0.1-1040MHz)	£1750
Hewlett Packard 8660D - Synth'd Sig. Gen (10 KHz-2600MHz)	£3250
Hewlett Packard 8801B - Modulation Analyser	£2750
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1250
Hewlett Packard 16500A + B - Logic Analyser Mainframes	from £1000
Hewlett Packard 16500C - Logic Analyser Mainframe	£3250
Hewlett Packard 16501A/B & C - Logic Analyser System Expander Frame	from £2000
Hewlett Packard 37900D - Signalling test set	£3750
Hewlett Packard 5350B - 20Hz Frequency Counter	£1950
Hewlett Packard 8320A DCS/PCS test sets	£3000
Hewlett Packard 8657B - 100KHz-2060 MHz Sig Gen	£3995
Hewlett Packard 8657D - XX DQPSK Sig Gen	£4500
Hewlett Packard 8130A - 300 MHz High speed pulse generator	£5250
Hewlett Packard 8116A - 50MHz Pulse/Function generator	£2250
Marconi 1066B - Demultiplexer & Frame Alignment Monitor (140MBIT to 64KBIT)	NEW
Marconi 2305 - modulation meter	£1750
Marconi 2610 True RMS Voltmeter	£999
Marconi 6950/6960/6960B Power Meters & Sensors	£550
Philips 5515 - TN - Colour TV pattern generator	from £1400
Philips PM 5193 - 50MHz Function generator	£400
Leader 3216 Signal generator 100KHz - 140MHz - AM/FM/CW with built in FM stereo modulator (as new) a snip at	£1500
Racal 1992 - 1.3GHz Frequency Counter	£795
Rohde & Schwarz NRV dual channel power meter & NAV Z2 Sensor	£500
Rohde & Schwarz SMG (B1/B2) sig. Gen. 1GHz	£1250
Systron Donner 6030 - 26.5GHz Microwave Freq Counter	£3250
Tektronix ASG100 - Audio Signal Generator	£1995
Wavetek 178 Function generator (50 MHz)	£750
Wayne Kerr 3245 - Precision Inductance Analyser	£950
Wayne Kerr 6245 - Precision Component Analyser	£1995
	£2500

All equipment is used - with 30 days guarantee and 90 days in some cases

Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate, Coventry CV3 2SF.

CIRCLE NO. 101 ON REPLY CARD

Tel: 02476 650 702
Fax: 02476 650 773

163 COMMENT

Analysts rush in...

164 NEWS

- Magnetic memory closer to reality
- £7m funding for mobile hazard research
- Bluetooth gets a five-fold boost
- Ultra-fast transistors
- UK joins in MEDEA+ research
- Transistor gate just three atoms thick

170 WIRELESS 32-CHANNEL VOLTMETER

Read up 32 analogue voltages to 12 bit accuracy via four remote modules using **Pei An** and **Ping Hua Xie's** wireless data logger. Its central controller links to a PC.

180 HARD-DRIVE HAVOC

Your hard drive just took a dive and you haven't backed it up for months. Is there any hope of recovering your information? **Andrew Emmerson** reports.

184 NEW FILTER/MIXER CHIP

Zetex's new versatile high-Q bandpass filter chip operates to 150kHz and its integral mixer extends operation to 700kHz. This device is the subject of our design competition on page 187.

DESIGN COMPETITION

Turn to page 187 to find out how to enter our design competition. You could win one of three prizes worth £900 in total.

188 BEGINNERS' CORNER: BALANCED CIRCUITS

Balanced circuits play an important role in communications and in many other applications from audio to microwave frequencies. **Ian Hickman** explains why.



194 BEAUTIFUL RESISTORS

Les Green looks at the rarely discussed topic of the effects of stress in planar resistors and explains how to reduce it.

199 NEW PRODUCTS

New product outlines, edited by **Richard Wilson**

211 SOUND REINFORCEMENT AMPLIFIER

Needing a sound-reinforcement system for use in a medium size hall, **Ben Sullivan** came up with this unusual and versatile design.

214 CIRCUIT IDEAS

- Ice alert
- Battery-operated alarm
- Precision programmable reference
- PIC frame-check code for PPP
- Sinewave with crystal accuracy
- Auto input attenuator for radio
- Versatile power switcher

224 PHONE FEAR

The only thing scientists agree about on the mobile phone health question is that you cannot rule out the risk factor. So where does that leave the worried consumer? **Melanie Reynolds** reports.

227 CABLE FAULT LOCATOR

David Huddart's simple reflectometer is used with a reasonably fast scope to find faults in cables. It can test cables up to




200m long and resolve to 100mm yet it comprises only one IC and three transistors.

232 WEB DIRECTIONS

Useful web addresses for the electronics engineer.

236 LETTERS

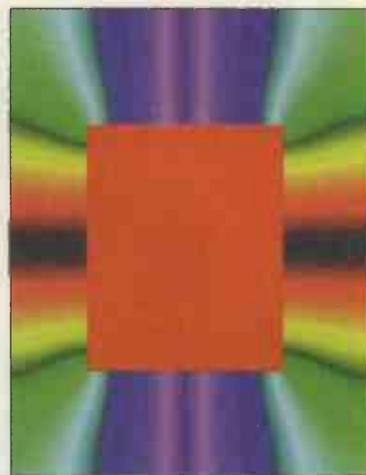B-class Class B, LF communications, Radio interference generator? E, fancy that, Speaker performance, Remote satisfaction, Amplifier for electrostatics? What is sky-scattered sunlight?




Collage created from **Les Green's** resistor stress patterns



Hard-drive havoc – **Andy Emmerson** reports on what you can do to recover the data from your crashed hard drive – page 180.



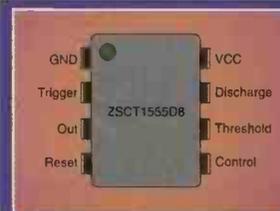Health hazards from mobile phone – when will we have the facts? **Melanie Reynolds' reports** on page 224.



FREE WITH THIS ISSUE

555 timer with guaranteed 0.9V operation (UK magazines and subscribers only). Turn to page 230 to find out more about it.

Sinking fast with poor tech support?
Expensive maintenance fees?
costly upgrades?
old fashioned software?

Realise your potential & break free with EDS!

electronic design STUDIO

Introducing EDS Advance the new modular electronics design system that includes simulation, schematic, PCB, autorouting and CAD/CAM modules as standard.

Our powerful integrated development environment brings powerful management to your projects and now features 3D style PCB footprints, Viper rip up and retry autorouter, shape based design rule checking, full copper pour support with unlimited automatic zones and split power planes, cross probing between schematic/pcb/netlist, netlist navigator, wizards to automate key features, DTP quality feature rich schematics, 2000 look and feel, and a wide range of import/export options.

If you are struggling with your existing system and feel its time for a change, why not give us a call and we will send you our free information pack. Or visit our web site and download a free trial copy of EDS.

Try before you Buy at www.quickroute.co.uk



Quickroute Systems Ltd,
Regent House, Heaton Lane,
Stockport SK4 1BS UK
Tel 0161 476 0202 Fax 0161 476 0505
Email info@quicksys.demon.co.uk




CIRCLE NO.104 ON REPLY CARD

Standalone Data Loggers

Low-cost standalone data capture solution



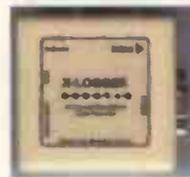T-Logger **44.99 +Vat**
Micro power standalone single channel temperature logger



X-Logger **69.99 +Vat**
Micro power standalone voltage logger with 1 temperature and 3 voltages channels

- ◆ Initialised by a PC via a RS232 port
- ◆ Catch data and store the values into its on-board memory for future retrieval
- ◆ Data can be downloaded into a PC and viewed through Excel or other spreadsheet packages
- ◆ Win 95/98 driver for initialisation and download
- ◆ Ultra-low power consumption
- ◆ Sensors available for X-logger: temperature, humidity, light intensity, etc.

Other Standalone Loggers

- ✦ Standalone Event Loggers (record occurrence of events)
- ✦ Standalone Data Loggers with memory up to 8 Mega byte.
- ✦ Intec designs standalone data loggers to your specification

Intec Associates Limited www.intec-group.co.uk
11 Sandpiper Drive, Stockport, Cheshire, SK3 8UL, UK
Tel: +44 (0)161 477 5855 Fax: +44 (0)161 477 5755
E-mail: mail@intec-group.co.uk

CIRCLE NO.105 ON REPLY CARD



WWW.PCB-POOL.COM

Prototype PCBs
from your usual manufacturer for a
fraction of the cost

1 Eurocard ds / pth
+ TOOLING
+ PHOTO PLOTS
+ VAT
= **£49**

FREE Layout Software
FREE Digital-Multimeter
FREE PHONE 0800 389 8560



☎ +353 (0)61 701170
FAX 701164

CIRCLE NO.106 ON REPLY CARD

Analysts rush in...

EDITOR

Martin Eccles
020 8652 3614

CONSULTANTS

Ian Hickman
Philip Darrington
Frank Ogden

EDITORIAL ADMINISTRATION

Jackie Lowe
020 8652 3614

EDITORIAL E-MAILS

jackie.lowe@rbi.co.uk

GROUP SALES EXECUTIVE

Pat Bunce
020 8652 8339

ADVERTISEMENT E-MAILS

pat.bunce@rbi.co.uk

ADVERTISING PRODUCTION

020 8652 8339

PUBLISHER

Mick Elliott

EDITORIAL FAX

020 8652 8111

CLASSIFIED FAX

020 8652 8938

NEWSTRADE ENQUIRIES

020 7907 7777

ISSN 0959-8332

For a full listing of
RBI magazines:
<http://www.reedbusiness.com>

No group of people made themselves look more foolish in 2000 than the financial analysts. At the beginning of the year they valued high-tech companies so extravagantly that organisations like ARM and Bookham were propelled into the FTSE 100 of the UK's most valuable companies.

By the end of the year, these values had been decimated. Yet the companies involved were doing very nicely, thank you, in executing their business plans. It wasn't the businesses that had changed – it was the analysts' views of them. The analysts were fools in Q1 or fools in Q4 – they can take their pick.

To an extent, the hysterical nature of the analysts can be blamed on the attitude of their employers – stockbrokers, investment banks and the like – who require them to produce recommendations which 'churn' stock i.e. which make people want to buy or sell stock, so that the employers can make a commission on the deal.

On the other hand there's also the inexperience – and sometimes even the stupidity – of the people involved. As one CEO puts it: "As long as 23 year-old analysts spit out bad stuff, there's a problem with market perceptions – if they only realised the explosion happening in electronics!"

Some analysts are confused because they are employed to study the industrial world in sectors, and assume that the trends in a sector apply to every company within it, whereas different companies within a sector can operate in different markets, and perform in accordance with different industrial and technological cycles.

So it could be that the '23 year-olds' look at bad figures from Intel, Apple, Dell and Microsoft and think: 'High-tech's a bummer,' when what they should be concluding is: 'The PC business is a bummer'.

But the PC business should not be seen as an indicator of the state of the electronics industry. The commoditisation of the PC, with fewer people willing to upgrade regularly, while mainstream PC prices are dropping in line with Moore's Law, spells the end of the PC's role as

the main driver of growth for the electronics industry.

"People seem to be surprised that Intel, which is tied to the PC industry, puts out these warnings about reduced growth", says Malcolm Penn, chairman of Future Horizons, "but it's obviously going to grow slower than the rest of the industry. The PC industry is growing at half the rate of the semiconductor industry".

Dataquest not only predicts slowing growth in the value of semiconductors going into PCs, but forecasts an actual decline in the market for semiconductors for PCs starting in 2002.

In 2000, for the first time since the 1980s, the main chip types which go into PCs – CPUs and DRAMs – grew by less than the industry average

By contrast, chips for applications such as mobile phones, digital consumer, car multimedia, storage, smart card and networking are growing so fast that they will represent 40 per cent of the chip market in 2004.

So the PC industry's problems should not be taken as symptomatic of the state of the electronics industry as a whole. The only thing that can save the Intel PC business model of constant upgrading via more powerful processors, extra DRAM and more elaborate software, is the rapid deployment of inexpensive xDSL and cable modem installations giving the opportunity for more services to be offered to users.

However, despite EU regulations opening up all European markets to local loop unbundling in 2001, Dataquest is pessimistic about domestic adoption of DSL and cable modems, estimating that, in 2005, only 8 per cent of Internet PC connections will be broadband through xDSL or cable modems

Instead, mass market broadband connectivity may come to the mass market via the TV using low-cost, or free, 'Internet Appliances' bundled with attractive entertainment, new services and interactivity.

Such appliances could prove to be the deathknell of the PC's aspirations to be the central device in a connected world. ■

David Manners

SUBSCRIPTION HOTLINE

Tel (0) 1444 475662
Fax (0) 1444 445447

SUBSCRIPTION QUERIES

rbp.subscriptions@rbi.co.uk
Tel (0) 1444 445666
Fax (0) 1444 445447

Electronics World is published monthly. By post, current issue £2.65, back issues, if available, £3.00. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tlx:892984 REED BP G. Make cheques payable to Reed Business Information Ltd
Newstrade: Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0207 261 5108.
Subscriptions: Quadrant Subscription Services, Oakfield House Perrymount Road, Haywards Heath, Sussex RH16 3DH. Phone 01444 445566. Please notify change of address.
Subscription, 1 year UK £36.00 2 years £58.00 3 years £72.00.
Europe/Eu 1 year £51.00 2 years £82.00 3 years £103.00
ROW 1 year £61.00 2 years £98.00 3 years £123

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Colchester) Ltd, **Filmsetting by** JJ Typographics Ltd, Unit 4 Baron Court, Chondlers Way, Southend-on-Sea, Essex SS2 5SE.

© Reed Business Information Ltd 1997 ISSN 0959 8332

£7m funding for independent research into mobile phone hazards

The UK's biggest ever investigation into the possible health effects of mobile phone use will see the Government and industry ploughing £7m into an independent research programme.

Industry will provide 50 per cent of the funding for the independent programme over the next three years.

There is still no proven scientific link between mobile phone use and potential health problems but the amount of research being done around the world is growing.

Speaking at the 'Mobile phones – is there a health risk?' conference last week was Dr Sheila Johnston, neuroscience consultant to the UK mobile phone industry. "There is a lot

of research but the problem is a lot of people don't understand it. The gap right now is in human research," said Johnston who believes this is where the latest programme will be concentrated.

"There is no question that microwave radiation can be hazardous to human health," said James Lin, professor of Bioengineering at the University of Illinois. "The question is how hazardous is it?"

Concerns about negative results from the investigation being quashed, as happened with the BSE mad cow saga, were dismissed by Michael Repacholi of the World Health Organisation. He believes the lessons

have been learnt: "The UK Government is BSE sensitive which may even cause an over reaction in the EMF (radiation) situation."

Leaflets setting out advice on the use of mobile phones will also now be included with every new phone as recommended by the independent Stewart report in May.

The advice includes keeping calls short, especially for those under 16, not using a phone while driving, and considering the SAR (specific absorption rate) value of phones when choosing a model. However, the standard method of measuring SAR is not expected to be set until the middle of next year.

Melanie Reynolds

UK-based mobile phone start-up warns rivals that it's "not just another wannabe"

UK-based start-up Sendo is set to take on the big mobile phone manufacturers in the European market by targeting the network operators.

"The operator is the key purchaser, the key decision maker, in what gets to market," said Hugh Brogan, CEO. "The operators are looking to retain customers, they're looking to differentiate themselves."

Brogan believes the company is ideally placed to meet this need by offering unique physical designs and customised software. Its manufacturing technique also means it can ship products within 48 to 72 hours.

A basic electronics module is manufactured in China and shipped to

the Netherlands. On receipt of a customer order the module is programmed and the casing is fitted to completely enclose the module.

The first product, announced in Italy last week, is "technologically advanced" according to Brogan: "We want to show we're not just another wannabe."

The company is aiming to sell a "few million" phones in the first year and said sales of less than 500 000 would be enough to break even. In the UK, the first products should be offered through Virgin Mobile.

Sendo was founded in August 1999 with an initial \$10m of funding from Hong Kong telecoms company CCT. Since then CCT has invested a further



Sendo is aiming to sell a "few million" phones in the first year and said sales of less than 500 000 would be enough to break even.

\$25m and owns 35 per cent of the company. Brogan said its present plans did not require further investors but if it "bagged a big deal" then more cash will be needed.

Bluetooth gets a five-fold boost

TDK Systems has announced a Bluetooth product that operates at a distance up to five times greater than required by the specification.

The mobile communications specialist's Bluetooth PC Card can connect to another Bluetooth device up to 50m away while the specification requires operation at 10m. TDK said this performance is achieved by using new ceramic antenna and input

technology.

The card is expected to ship in the first quarter of next year.

The company is also developing a next generation Bluetooth /10/100 Ethernet PC card to combine fixed LAN connection and wireless Bluetooth in one PC card slot.

It has been working in partnership with UK-based Cambridge Silicon Radio.

A reprieve for Moore's law?

Researchers from Purdue University in the US have developed a transistor they claim could keep Moore's Law running until 2025.

A simulation tool showed that the double-gate transistor works as well as a conventional device down to a tenth of the channel length. A gate would function easily down to 10nm. "If we could learn how to manufacture a device like this we could extend Moore's Law to the year 2025," said Professor Mark Lundstrom from purdue.



**Unique reader offer:
x1, x10 switchable
oscilloscope probes,
only £21.74 a pair,
fully inclusive***

*Additional pairs as part of the same order, only £19.24 each pair.

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (please circle)

Cheques should be made payable to Reed Business

Information

Access/Mastercard/Visa/Cheque/PO

Credit card no _____

Card expiry date

Signed

Please allow up to 28 days for delivery

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to Probe Offer, Electronics World Editorial, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Readers outside Europe, please add £2.50 to your order.

Specifications

Switch position 1

Bandwidth	DC to 10MHz
Input resistance	1MΩ – i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC

Switch position 2

Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10MΩ ±1% if oscilloscope i/p is 1MΩ
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC

Switch position 'Ref'

Probe tip grounded via 9MΩ, scope i/p grounded

UK is set to participate in European MEDEA+ research plan

Britain is to join MEDEA+, the Europe-wide research programme which starts in January, extending the existing scheme by eight years.

A spokesperson from the Department for Trade and Industry said: "The UK will formally join MEDEA+ this January, and it's our intention to fund suitable projects."

European companies such as Philips and STMicroelectronics have benefited significantly over the last decade from MEDEA and its predecessors.

Of the 9400 man-years of research in the original MEDEA programme, only 16 came from UK firms.

While companies based in the UK were eligible, no applications for funding were made, the DTI said. This was probably due to restrictive Eureka rules.

In addition, the DTI cited limited demand for MEDEA in the UK: "The UK has a substantial semiconductor manufacturing industry, but most of the large companies are inward investors who do R&D in their own

countries."

As inward investors change their attitude and opt to carry out research in the UK, they may choose to apply for funding.

"We are in negotiation with a number of companies including large ones," the DTI said.

The Government will also encourage small and medium sized firms to enter the programme, which will be worth a total of £4bn over the next eight years.

Richard Ball

Magnetic memory comes closer to reality as IBM and Infineon agree collaboration

Magnetic memory has taken a step closer with a joint development agreement between IBM and Infineon.

The two firms are to take MRAM research and develop it for production. IBM will combine its well-developed MRAM technology with Infineon's ability to manufacture high density memory.

Commercially available products – both embedded memory and stand-alone chips – are expected by 2004. MRAM, with the desirable traits of being fast, small, having a non-destructive read, being non-volatile and easy to integrate, sounds like the ideal technology.

IBM has offered glimpses of its MRAM technology over the past year at various technical conferences. At ISSCC earlier this year the firm detailed its core technology.

IBM is using a magnetic tunnelling junction (MTJ) to store data. Two electrodes of magnetic material, such as nickel/iron or cobalt/iron, sandwich a thin aluminium-oxide tunnelling layer.

Information is stored as magnetic polarisation – not as a charge. When the two magnetic electrodes have the same polarisation, there is more chance of electrons tunnelling through the aluminium oxide layer, so its resistance is reduced by 20 to 30%.

By changing the magnetic polarisation of one layer, resistance is increased. This resistance is sensed using a FET.

"For 15 years or so people have been trying to use magneto-resistive materials," Roy Scheuerlein, a researcher at IBM, said earlier this year. But previous MRAMs used serially-linked MR blocks which reduced sensitivity.

"The MTJ, and the way we use it in the cell, is dramatically better," said Scheuerlein. "The power required to read is 10^5 times better than GMR [used in hard disk drives]." Resistance of the cell is around 2.5k Ω compared with about 10 Ω for a GMR head.

"We can build this on standard CMOS. It looks somewhat like a DRAM cell," Scheuerlein said.


Which is where Infineon comes in to the picture. It will apply its

expertise in building large memory arrays – as it does with DRAM today.

IBM has already produced a 1Kbit test chip made using a standard 0.25 μ m CMOS. It claims to have achieved 10ns access time from address input to data output. Using higher performance sense amplifiers, IBM has brought this down to 3ns. At the cell level, writing bits takes a time of less than 2.5ns.

However, MRAM is not the perfect memory. It is not as small as DRAM, but is a lot smaller than SRAM, it's not as fast as SRAM, but is quicker than both DRAM and flash.

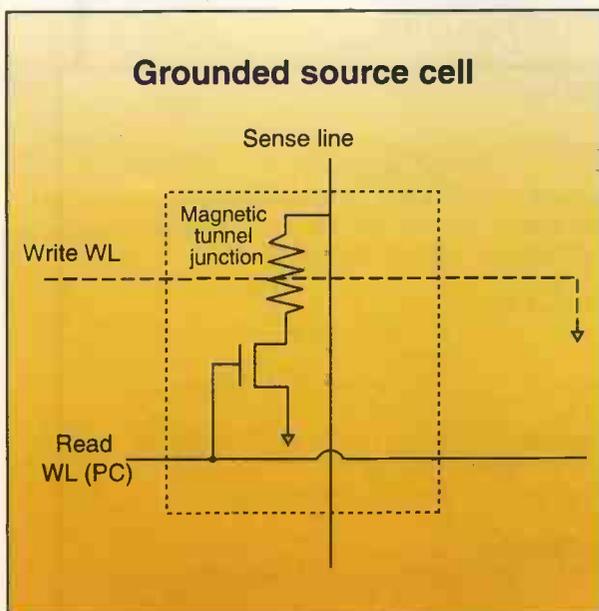IBM and Infineon are sure to come up against some significant hurdles in moving to production. MRAM's non-volatility may well be the attribute that forces it through to volume production.



PCB buyers hit by material shortfalls

Material shortages are causing serious problems for electronic equipment manufacturers, according to analysts Purcon-iPro. The shortages, combined with rising prices and lengthening lead times means that buyers of PCBs face a shortage. Purcon-iPro said there are all the signs that it is currently a sellers market.

The Headphone Amplifier Box

Balanced or unbalanced microphone or line input to headphone output.

Professional portable units operating from an internal PP3 battery or external mains adaptor



- * Precision transformerless balanced input
- * Bridged headphones output drive
- * Sensitivity selectable over a wide range of input levels
- * Low noise and distortion
- * High common mode rejection
- * Loop through facility
- * Extensive RFI protection

The Balance Box (precision mic/line amplifier) –
The Phantom Power Box – **The OneStop** DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines.

Conford Electronics Conford Liphook Hants GU30 7QW

Information line 01428 751469 Fax 751223

E-mail contact@confordelec.co.uk

Web <http://www.confordelec.co.uk/>

CIRCLE NO.107 ON REPLY CARD

Ramco

GENUINE GOVERNMENT SURPLUS

We currently have in stock a selection of MOD surplus electrical equipment. All items are untested and sold as seen. Please ring for more details.

Tektronics 466 Storage Oscilloscope	£99.00
Tektronics 2445a Oscilloscope 150mhz	£399.00
Phillips 3217 Oscilloscope 50mhz	£99.00
Goold OS300 Oscilloscope 20mhz as new, boxed	£99.00
Goold DS 4072 Oscilloscope 100mhz	£50.00
Racal 9009 Modulation Meter	£69.99
Static Sine Wave Inverter 8242 as new, boxed	£89.00
Megger Pat.2 Portable Appliance Tester	£39.99
Marconi 2019A Signal Generator 80khz-1040mhz	£249.00

Take a look at our next
TENDER SALE
FEBRUARY 5th -7th
 You may just find what
 you are looking for! (Details on our web site)

From May 2001
 we will be able to offer
 tested equipment via our
 refurbishment cell

FIND OUT MORE ABOUT US ON OUR WEBSITE

www.ramco.co.uk

CHURCH LANE, CROFT, SKEGNESS, Lincs (JUST OFF THE A52)


01754 880880

EW 1/01

CIRCLE NO.108 ON REPLY CARD

b² Spice 2000

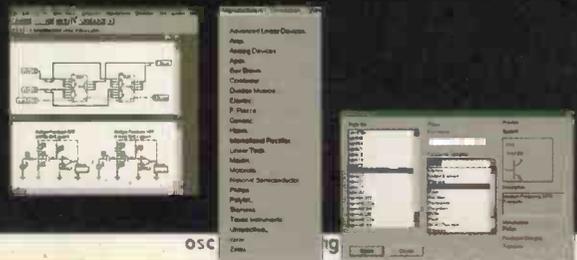Analogue and digital circuit design for the PC



Design and test circuits quickly and easily

Packed with new features:

- Uses the latest **xspice** engine for guaranteed accurate mixed mode simulation
- Parameterised ac sweep
- Monte carlo analyses
- Parameterised transient sweep
- New **xspice** simulations
- New noise and distortion analyses
- Improved features for processing plot families as units
- New menu items to show local maxima, minima, and zero crossings **and much more!**

Accurate results that can be relied on

ONLY £199 ex VAT*
 (UPGRADES FOR EXISTING USERS)
FREE
 30 DAY EVALUATION



RD Research, Research House, Norwich Road, Eastgate, Norwich NR10 4HA
 Tel: 01603 872331 Email: rd.research@paston.co.uk www.looking.co.uk/spice

*Please add £5.00 postage and packing. *applies to users of B² Spice & B² Logic. All trademarks acknowledged



+45 344m
 0.0

CIRCLE NO.109 ON REPLY CARD

Government announces dramatic shake-up plans for comms regulation

The Government has announced in a White Paper the biggest shake-up of communications and broadcast regulation for a decade.

A single regulator for the entire industry will be created including the current responsibilities of OfTel to be called the Office of Communications (Ofcom).

The White Paper also holds out the prospect of Government cash being used to accelerate the introduction of

broadband technology like ADSL. It suggests there may be a case to require higher bandwidth services to be made universally available in an attack on the slow pace of change in unbundling the local telephone network.


"We will promote the availability of widespread access to higher bandwidth services and we will look for ways to build on the public investment that is already being

made in broadband and consider whether public support is needed to help research and develop new high-speed networks," said the White Paper.

In a joint statement Culture Media and Sport Secretary Chris Smith and Trade and Industry Secretary Stephen Byers said: "Our goal is to make the UK the safest and most reliable place to use the new communications services."

Transistor has a gate just three atoms thick

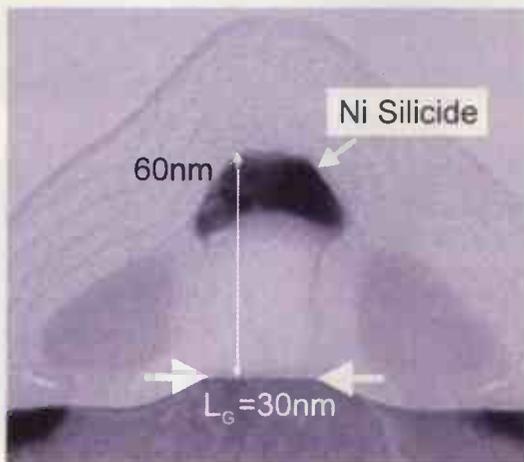Intel researchers have made transistors with gate lengths of 30nm and using a gate dielectric just three atomic layers thick. The firm expects to be using these devices in as little as



five years.

Clock speeds will reach 10GHz operating from a sub-1V supply. Moreover the transistor's design is compatible with current IC techniques.

"Many experts thought it would be impossible to build CMOS transistors this small because of electrical leakage problems. Our research has proven that these smaller transistors behave in the same way as today's devices and shows there are no fundamental barriers to putting them into high volume in the future," said Intel's Dr Gerald Marcyk.

The company reckons Moore's Law has at least ten years of life. "As our researchers venture into uncharted areas beyond the previously expected limits of silicon scaling, they find Moore's Law still intact," said Intel v-p Dr Sunlin Chou.

£128m for science fund

Photonics and communications technology research at universities will benefit from an injection of Government cash into scientific research.

A total of 28 research projects at universities across the country will get a share of £128m, which will be managed jointly by the Department of Trade and Industry and the Wellcome Trust.

Inevitably biochemistry, DNA and medical research dominate the project list but there is also room for some projects related to microelectronics, photonics and multimedia.

Semiconductor analyst predicts downturn in 2001

The semiconductor industry will turn down next year, according to IC Insights, the Arizona semiconductor industry analyst.

"Over the past 30 years, the IC industry has encountered six boom-bust cycles," said the analyst's report, "the downturn portion of an IC industry cycle is usually triggered by global economic recession, IC industry overcapacity, or IC inventory corrections. In 2001, IC Insights believes that the IC industry will be affected by all three 'triggers'."

For this year, the company is predicting 35 per cent growth for the semiconductor industry and 79 per cent growth in the semiconductor production equipment industry.

In the UK, Malcolm Penn, chairman of analysts Future Horizons, attributed

the Q4 downturn to over-expectations by PC makers leading to inventory sell-offs. "The PC industry is growing at half the rate of the semiconductor industry," said Penn, "people seem to be surprised that Intel, which is tied to the PC industry, puts out these warnings about reduced growth. But it's obviously going to grow slower than the rest of the industry."

Dataquest not only predicts slowing growth in the value of semiconductors going into PCs, but forecasts an actual decline in the market for semiconductors for PCs starting in 2002.

IC Insights reckons semiconductor production capacity will grow 24 per cent this year but less than 10 per cent next year. It reckons the 'inventory burn' – the selling off of

semiconductors surplus to requirements – will continue until mid-2001.

"Worldwide GDP is forecast to slow from 4.8 per cent growth in 2000 to 3.5 per cent or less in 2001," says IC Insights, "although not a worldwide recession, the reduction in growth will negatively impact electronic system sales in 2001."

The result of that is over-stocking of components which, says the company, usually results in pricing weaknesses which are expected to persist throughout the first half of 2001.

The report ends optimistically: "After modest growth in 2001 and 2002, IC Insights expects the IC market to increase 20 per cent or more beginning in 2003."

David Manners

TEST EQUIPMENT SOLUTIONS

Quality second user test equipment bought and sold
All purchases backed with full one-year warranty and technical support

AMPLIFIERS

Amplifier Research 1W1000 1GHz 1W Amplifier	1850
HP 70621A /H50 100KHz to 2.9GHz Pre-Amp Module	1500

COMPONENT ANALYSERS

HP 4084B Switching Matrix Controller	3500
HP 4085M Switching Matrix	4500
Tek 370A Curve Tracer	16500



DATA COMMS

Fluke DSP-100 Cat 5 Cable Tester	1650
Fluke DSP-FOM Fibre Optic Meter For DSP Series	350
Fluke DSP-SR Smart Remote Injector for DSP-100	350
HP J2300A /002 64KBPS Protocol Analyser	3000
Microtest MT340 Cat 5 Tester	950
Microtest PentaScanner+ CAT 5 Cable Tester	1650

ELECTRICAL NOISE

Eaton 2075 Noise Analyzer	3250
HP 8970B 1.6GHz Noise Meter	7950

EMC

HP 84110B Pre Production EMC Test System	24500
R&S EB 100 1GHz Miniport Receiver	3750
R&S EPZ 100 Mini Panoramic Display	1250
R&S HE100 1GHz Active Antenna	1150

FREQUENCY COUNTERS

HP 5371A 500MHz Frequency / TI Analyser	3950
Marconi CPM46 Counter Power Meter	4950
Philips PM6654C/526 1.5GHz/2ns Counter Timer	1250

FUNCTION GENERATORS

HP 33120A/001 15MHz Func/Arb Wave Generator	975
HP 8116A 50MHz Function Generator	2000
HP 8165A Function Generator	1250
Philips PM5193 50MHz Function Generator	1750



LOGIC ANALYSERS

HP 16500B Logic Analyser Mainframe	1150
HP 1650A 80 Channel Logic Analyser	1000
HP 16550A Timing Analysis Module	1950
HP 1672A 68 Channel Logic Analyser	4500

MULTIMETERS

HP 3466A 4.5 Digit Digital Multimeter	350
---------------------------------------	-----

NETWORK ANALYSERS

HP 8510C 50GHz Microwave Network Analyser	22500
HP 8720C/006/010 20GHz Vector Network Analyser	35000
HP 8753C 3GHz Vector Network Analyser	13500
Marconi 6200A 10MHz-20GHz Microwave Test Set	14500

OPTICAL FIBRE TEST

Anritsu MN9610B Optical Power Meter	1500
Anritsu MS9710B Optical Spectrum Analyser	21500

OSCILLOSCOPES

HP 54111D 500MHz Digitising Scope	2950
HP 54602A 4 Channel 150MHz Digital Storage Scope	1250
HP 54603B 2 Channel 60MHz Digital Storage Scope	1150
HP 70700A /H25 20MS/S Digitiser Module	1000

Philips PM3295 2 Channel 350MHz Scope	1250
Philips PM3295A/40 2 Channel 400MHz Scope	1500
Philips PM3394 4 Channel 200MHz Combi-Scope	3200
Tek 2445A 200MHz 4 Channel Analogue Scope	1500
Tek 2465A/10 350MHz Analog Scope	1950
Tek 2465B 400MHz 4 Channel Analogue Scope	2500
Tek Current Probe Set with Amplifier	1750
Tek TAS465 2 Channel 100MHz Analogue Scope	695
Tek TDS380 400MHz 2 Channel Digitising Scope	2500
Tek TDS380P As Above But With Integral Printer	2950

POWER METERS

HP 436A/022 RF Power Meter With GPIB	750
HP 438A /002 Dual Channel RF Power Meter	1950
Various HP 848x Power Sensors (from)	400
Marconi 6960 RF Power Meter	650
Various Marconi 699x Power Sensors (from)	350



POWER SUPPLIES

HP 6282A/005/028 10V/10A DC Power Supply	150
HP 6284A 005/028 20V/3A DC Power Supply	150
HP 6632A 20V/5A Power Supply	1250
HP6652A 20V/25A DC Power Supply	795
HP E3615A 20V/3A DC Power Supply	195
HP E3631A 25V/5A DC PSU	650
Hunting Hivolt Series 250 50kV/5mA Power Supply	895
Kikusui PLZ300W 300w Electronic Load	950
Philips PE1539 20V/6A DC PSU	100
Philips PE1541 75V/1.6A DC PSU	100
Thandar PL330 32V/3A DC Power Supply	195
Weir 732 60V/1A 30W DC PSU	75
Weir 761 30V/4A 60W DC PSU	75

RF SWEEP GENERATORS

HP 8340A 26.5GHz Synthesized Sweep Generator	15500
Marconi 6311 20GHz Sweep Generator	4950

SIGNAL & SPECTRUM ANALYSERS

Advantest R3265 8GHz Spectrum Analyser	8500
Advantest R3361A Spectrum Analyser	7500
Advantest R3465 8GHz Spectrum Analyser	11950
Advantest R4131B 3.5GHz Spectrum Analyser	3950
Advantest R4131D 3.5GHz Spectrum Analyser	4500
Advantest R9211A 100KHz 2 Channel FFT Analyser	3950
Anritsu MS2601B 2.2GHz Spectrum Analyser	5500
Anritsu MS610B Spectrum Analyser	2650
Anritsu MS612A 50Hz to 5.5GHz Spectrum Analyser	6500
Anritsu MS710F 23GHz Spectrum Analyser	6950
HP 3561A 100KHz Dynamic Signal Analyser	3250
HP 3562A 2 Channel 100KHz FFT Analyser	4250
HP 35660A 102.5KHz Dynamic Signal Analyser	2950
HP 70000 2.9GHz Spectrum Analyser System	9000
HP 8560A 2.9GHz Spectrum Analyser	9950
HP 8591A / 021 1.8GHz Spectrum Analyser	4500
HP 8592B 22GHz Spectrum Analyser	9500
HP 8593A 22GHz Spectrum Analyser	13500
HP 8594A / 010/021 2.9GHz Spectrum Analyser	7950
HP 8901A 1.3GHz Modulation Analyser	1250
HP 8903B 20Hz TO 100KHz Audio Analyser	2750
HP8970B 1.6GHz Noise Figure Meter	7950
Lindos LA100 Audio Analyser (LA101 & LA102)	2750
Marconi 2305 2.3GHz Modulation Analyser	950
Tek 492 /02 21GHz Spectrum Analyser	3950
Tek WM780V 50-75GHz Mixer Set	900

TV & VIDEO

Mitsubishi CA-100 CRT Colour Analyser	2650
Tek VM700A Video Measurement Set (various from)	12000

SIGNAL GENERATORS

Advantest R4262/ 023 4.5GHz Signal Generator	12500
HP 8642A 1GHz Synthesised Signal Generator	2500
HP 8656B /001 1GHz Synthesised Signal Generator	1150
HP 8657B 2GHz Signal Generator	4250
HP 8662A 1.28GHz Synthesised Signal Generator	8900
HP 8672A 18GHz Synthesised Signal Generator	6950
HP 8683D 2.3-13GHz Signal Generator	6950
Marconi 2017 1GHz Low Noise Signal Generator	1000
Marconi 2019A 1GHz Signal Generator	1000
Marconi 2022 1GHz Signal Generator	650
Marconi 2024 10KHz To 2.4GHz Signal Generator	4950
R&S SME06 / B1/B11 6GHz Signal Generator	21500
R&S SMG 1GHz Signal Generator	1950
R&S SMH 2GHz Signal Generator	6950
R&S SMHU 4.32GHz Synthesised Signal Generator	13500
R&S SMIQ03 3.3GHz Vector Signal Generator	21500



SWITCHES & MULTIPLEXERS

HP 3488A Switch / Control Unit	400
Various HP 444xx Switch Modules (from)	150
Racal 1250 Switching System Mainframe	450
Various Racal 1250 Switch Cards (from)	350

TELECOMS

Anritsu MD6420A Data Transmission Analyser	5950
Anritsu MP1656A / 02 STM16 Analyser	13500
Anritsu MS371A PCM Frame Analyser	4500
HP 3788A/001 2MBPS Error Performance Analyser	1950
Marconi 2840A Analyser	1950
Marconi Triton Signalling Test set	2500
Trend Aurora Duet Handheld ISDN Tester	2150
TTC Firebird 6000 Opts 6007/6008	5500
Various Firebird Interface Modules (from)	395
W&G PFA-35 2MBPS Communications Tester	4950
W&G DST-1 Handheld E&M Signalling Tester	1250
W&G PCM23 Voice Frequency PCM Tester	2750
W&G PF-4 Bit Error Measuring Set	4500
W&G PMP20 20KHz Digital Level Meter	650



WIRELESS

HP 83220A /022 PCS/DCS1800 Test Set	3950
HP 83220E PCS/DCS1800 MS Test Set	3500
HP 8902A 1.3GHz Measuring Receiver	12500
HP 8920A 1GHz Radio Test Set (various from)	4950
HP 8922M GSM Test Set	8500
Marconi 2945A /001/003/023 Radio Comms Test Set	7500
Marconi 2955B Radio Comms Test Set	3500
Racal 6103/001/002 GSM/DCS Test Set	7750
R&S CMS52 1GHz Radio Comms Test Set	5500
R&S CMT54 B1/B4/B5/B6/B9 Radio Comms Test Set	4500
R&S CMT56/B1/4/6/9/11/13/U1/9 Radio Test Set	2250
R&S CMT84 B1/B5/B6/B9 Radio Comms Test Set	4500
R&S CMTA84 /B5/B6/B8 Radio Comms Test Set	4950
Schlumberger 4015 1GHz Radio Comms Test Set	4500
Schlumberger 4031 1GHz Radio Comms Test Set	3250
Schlumberger 4039 960MHz Radio Comms Test Set	1250
Schlumberger 4040 1GHz Radio Comms Test Set	1950
Schlumberger 4922 Radio Code Analyser	250

See our extensive online catalogue at www.TestEquipmentHQ.com Flexible commercial solutions available on all products.

Prices shown are in £UK and are exclusive of VAT. Free carriage to UK mainland addresses. This is just a selection of equipment we have available. If you don't see what you want, please call. All items supplied fully tested and refurbished with one year warranty. All manuals & accessories required for normal operation included. Certificate of Conformance supplied as standard, Certificate of calibration available at additional cost. Test Equipment Solutions terms apply. E&OE.

01753 59 6000
fax: 01753 59 6001

www.TestEquipmentHQ.com
 e-mail info@TestEquipmentHQ.com

FREE

Free Palm m100 shipped with every order over £10k



Wireless

32-channel voltmeter

You can read up to 32 analogue voltages accurately via four individual remote a-to-d converter modules using Pei An and Ping Hua Xie's wireless data logger system. The central control station links to a PC via its COM port and each channel is read with 12-bit resolution.

This system allows a computer to measure up to 32 voltages remotely via a 433MHz radio link. It consists of a central station connected to the RS232 port of a computer and up to four wireless remote data loggers having different addresses.

Each logger has eight analogue input channels with an analogue-to-digital conversion accuracy of 12 bit. The measuring range is 0 to 2.5V.

Within buildings, the radio can operate at up to 30m, or 120m over open ground, Fig. 1.

Main elements of the system

The central station connects to a PC's RS232 port. Its function is to receive commands from the computer, to broadcast the message to remote data loggers, to receive data sent back by remote loggers and finally to send the data back to the computer.

A Microchip PIC16F84 is at the heart of the central station. An RS232 transceiver and a Radiometrix radio packet controller take care of the wireless interfacing, Fig. 2a).

Each remote data logger is a stand-alone device located within the radio range of the central station. Up to four loggers can be used, each with a unique address of 0, 1, 2 or 3.

A PIC16F84 controls the logger. An eight-channel MAX147 a-to-d converter is used for measuring analogue voltages. This converter has 12-bit resolution. Further radio packet controllers handle the wireless data transfer, Fig. 2b).

How it works

At power-up, the central station reads data from its RS232 interface to see if the computer has sent a command. At this stage, its radio transmitter is switched off.

To read eight analogue voltages from a particular remote data logger, the computer first sends a stream of commands to the central station. These commands incorporate an address byte specifying which remote logger will receive them. Then the central station broadcasts the message. Next, the central station listens to a reply from the addressed data logger.

Immediately after power-up, all the remote data loggers are in listening mode, waiting for a valid radio-frequency signal. Once the message broadcast by the central station is received by the RPC, the PIC on the data logger checks whether the current data logger is addressed by comparing the received address with its own.

If the logger is not addressed, it just goes back to listening mode. If the logger is addressed, the PIC reads data from the eight-channel a-to-d converter. It then writes data to

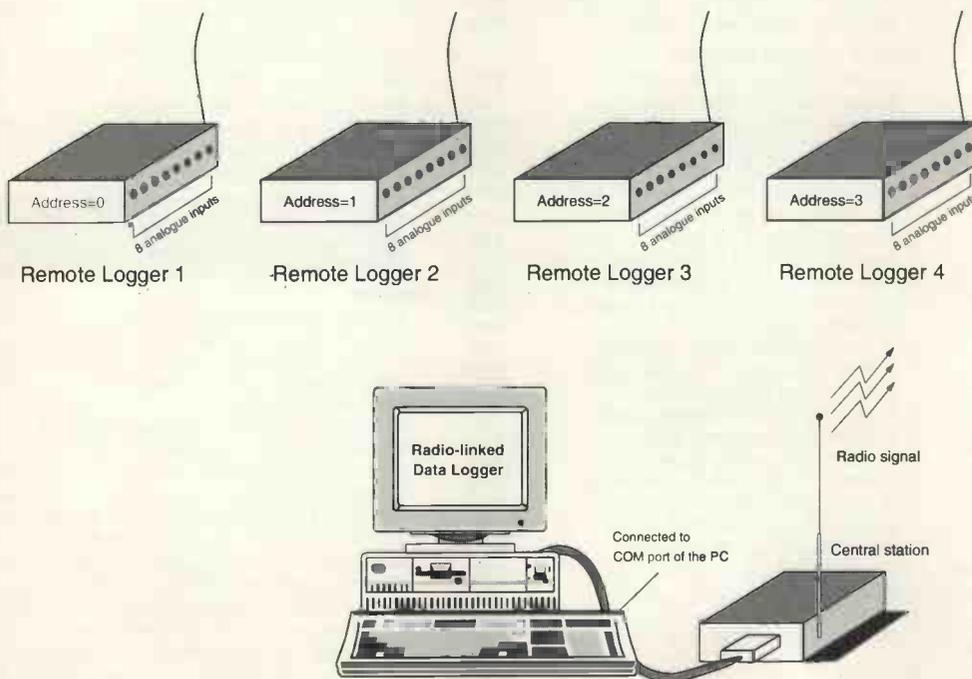


Fig. 1. Wireless remote data acquisition system comprising a central station and up to four remote data loggers. Each data logger has eight 12-bit analogue inputs. The central station connects to the RS232 port of a computer. In total, the computer can read 32 voltages remotely. Communication distance is 30 metres in building, 120 metres over open ground.

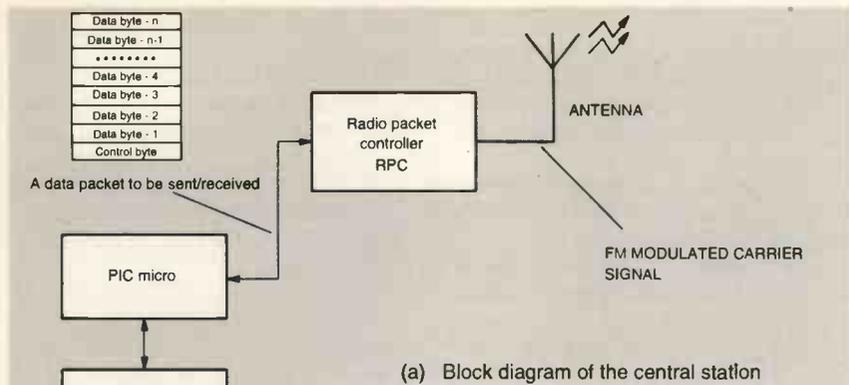


Fig. 2. Block diagram of the central station and remote data logger.

the RPC, which broadcasts the data.

After the central station receives data from the addressed logger, it sends data to the computer via the RS232 port. Inside the computer, the information can be stored in a file for future retrieval, or it may be displayed on the screen. This completes a data read cycle.

Radio packet controller


The RPC is a SAW-controlled FM transmitter and superhet receiver. It is designed to comply with ETSi 300-220 regulations.

There are two versions of the RPC. One works at 418MHz for UK use and the other at 433MHz for European use. Their respective part numbers are RPC-418-A and RPC-433-A.

These RPCs are self-contained plug-in devices that require a whip type

antenna, a 5V power supply and a byte-wide I/O port on a host microcontroller. Logic levels on the i/o port are 5V CMOS compatible.


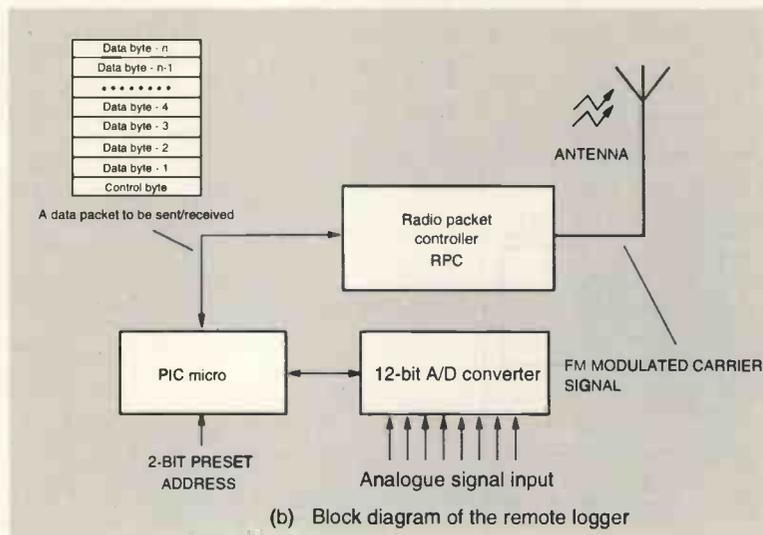
All the necessary rf circuitry is contained within the RPC, as are the low-level packet formatting and packet recovery functions required to interconnect a number RPCs to a single radio-linked network.



Details of the RPC presented here are limited to those relevant to the design. More information can be found in the manufacturer's data sheet¹.

Figure 3a) shows the pin-out of the RPC while 3b) illustrates how it is applied. This device has a four-bit bi-directional data bus – D0-D3 – and four handshake lines. Its pin-functions are:

Fig. 3. Lines D0 to D3 form a bi-directional data bus. There are four handshake lines, namely -RXA, RXR, TXA and RXR. Two LEDs provided on the module indicate operating modes. Data bus and handshake lines are used to connect the RPC to a host microcontroller.

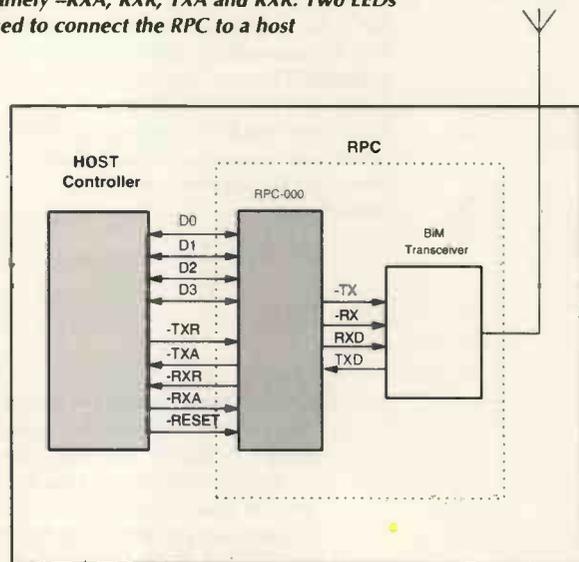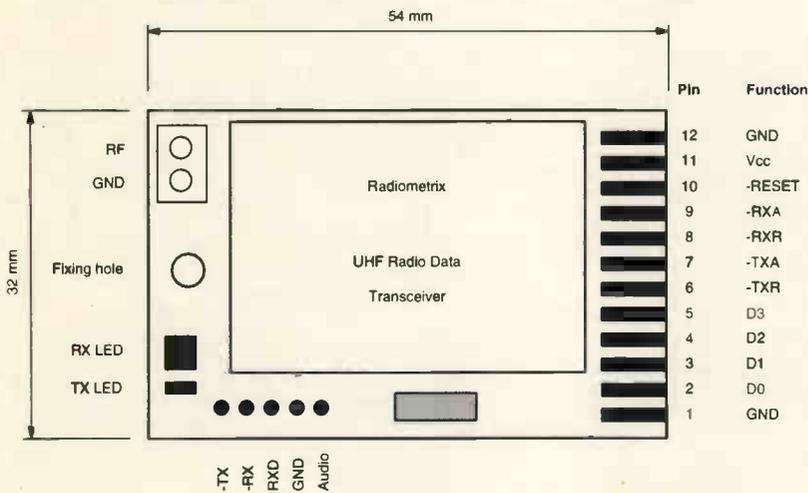

Pin Function

- | | | | | | |
|---|--|---|--|----|--|
| 1 | Ground | 6 | -TXR, host requests to transfer data into the RPC. Input to RPC. +5V CMOS logic. | 9 | -RXA, host acknowledge request to RPC. Input to RPC. +5V CMOS logic. |
| 2 | D0, bi-directional data bus. Input or output of RPC. +5V CMOS logic. | 7 | -TXA, RPC acknowledges request to the host. Output from RPC. +5V CMOS logic. | 10 | -RESET, HOST reset the RPC. Input to RPC. +5V CMOS logic. |
| 3 | D1, bi-directional data bus. Input or output of RPC. +5V CMOS logic. | 8 | -RXR, RPC requests to transfer data to host. Output from RPC. | 11 | V _{cc} , +5V supply. |
| 4 | D2, bi-directional data bus. Input or output of RPC. +5V CMOS logic. | | | 12 | Ground. |
| 5 | D3, bi-directional data bus. Input or | | | | |


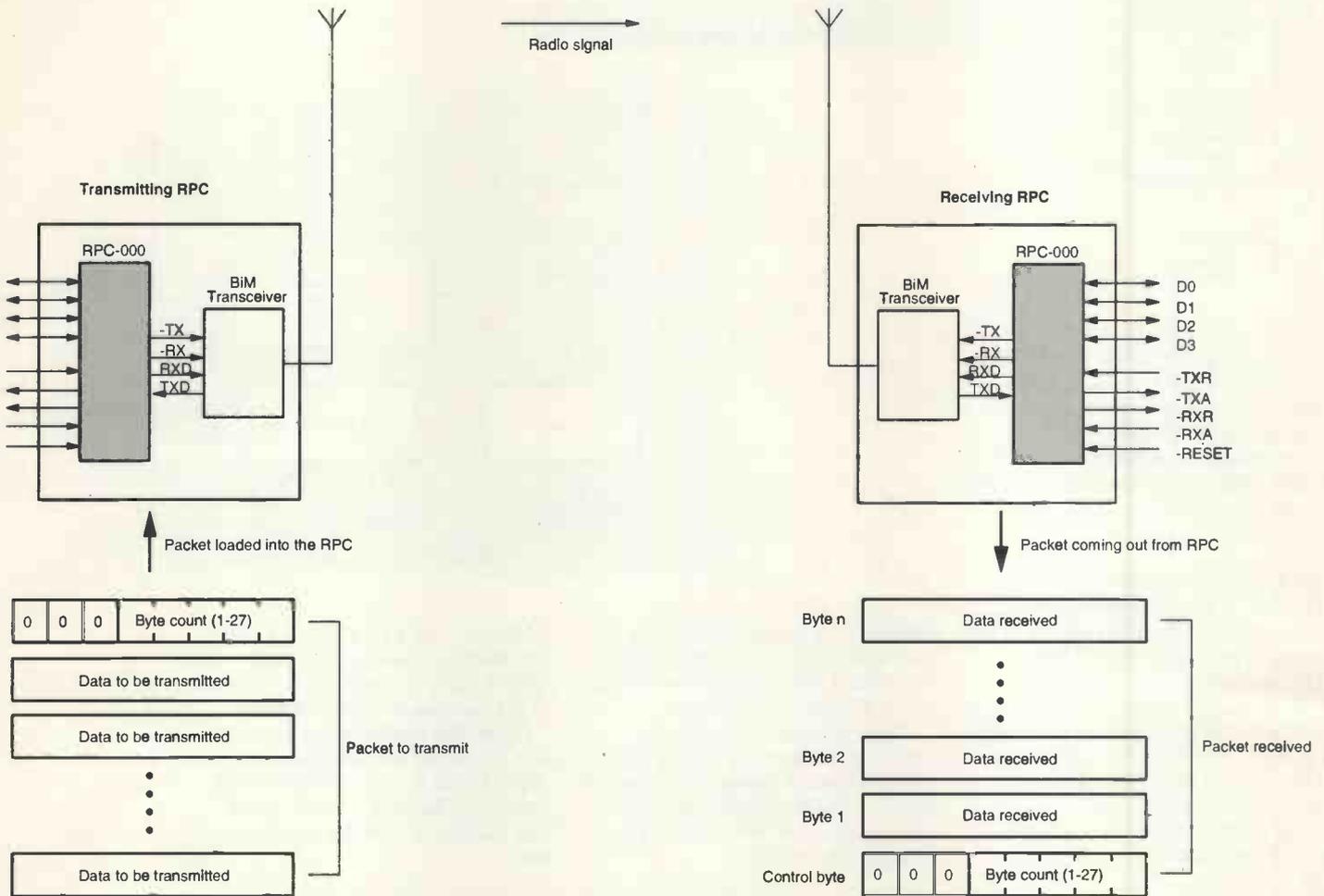


Fig. 4. Up to 27 bytes can be downloaded into the transmitting radio packet controller's buffers. These bytes can be transmitted to receiving RPCs and appear in the receiving RPC's buffers. The RPCs perform all necessary low-level data formatting for reliable radio digital transmission.

Fig. 5. Timing waveforms for writing data into the RPC's buffer and for reading data from it. The handshake between the host and the RPC secures data transfer between the host and the RPC. Note that a complete byte (8 bits) is transferred in two consecutive nibble (4 bits) transfers.

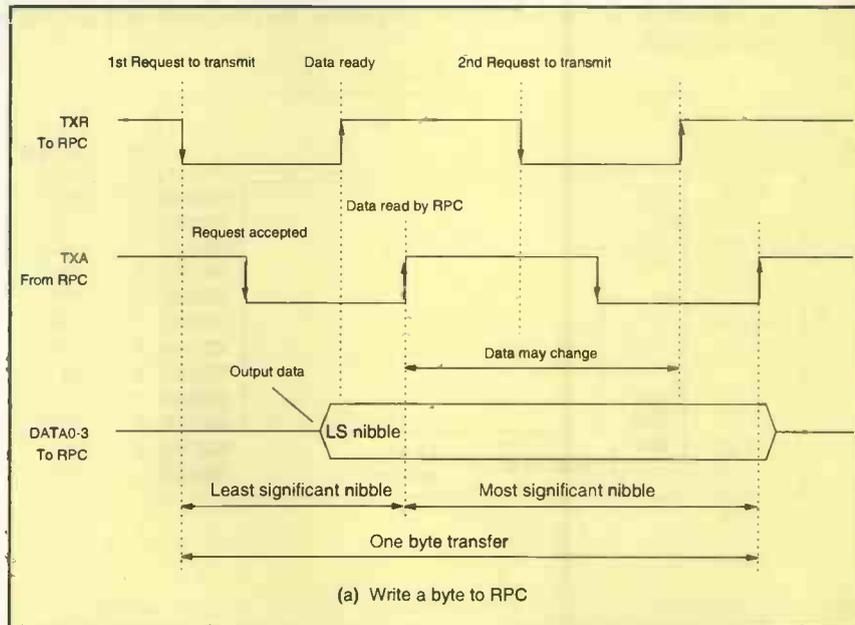

The host can be a micro-controller or a computer. It needs to be able to write a data packet consisting of 1 to 27 bytes into the RPC's data buffers. The packet is then sent out by the transmitting RPC to other RPCs.

The exact data packet appears in the receive buffers of all RPCs within the radio range. Once data is written into its buffers, the RPC takes care of the radio data transmission to other RPCs without any

further intervention Fig. 4.

More details on how data are transferred between RPCs is given in the module's data sheet.

How the packet controller works

The packet controller has four operating modes: idle/sleep, host-RPC data transfer, radio-data transmission and radio-data receive.

In idle/sleep mode, the receiver is enabled continuously or intermittently, depending on the set-up, to search for valid message preambles. Programming the RPC to search intermittently minimises power consumption. In this mode, the RPC also monitors the TXR line. The host requests to send data using an active-low signal.

In the host-RPC data-transfer mode, if the host is to transfer data into the RPC, the TXR


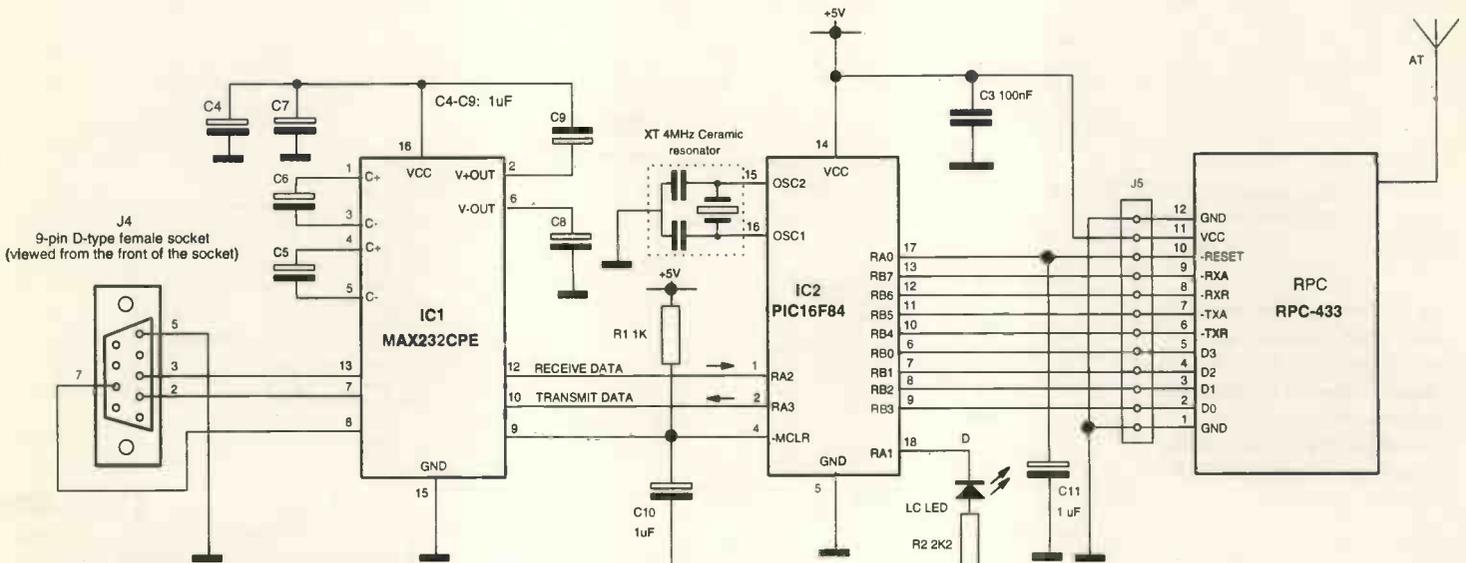


Fig. 6. Circuit of the central station consists of an RS232 line transceiver, a PIC micro-controller and a Radiometrix radio packet controller, or RPC. It is possible to build the circuit on a single-sided PCB.

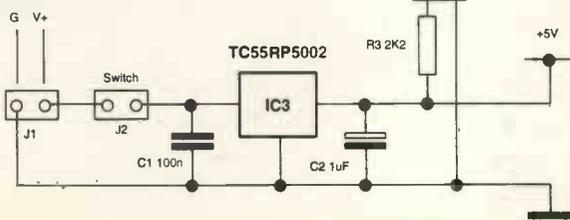

line is taken low by the host. If the RPC is to transfer data into the host, the RXR line is taken low by the RPC. In this mode, the radio receiver of the RPC is disabled.

To transfer a full 27-byte packet between the RPC and the host takes less than a millisecond. Details of writing data into the RPC or reading data from it are described later.

Once a complete data packet is transferred into the RPC, it first manipulates data for proper radio transmission and then transmits the message. A full 27 bytes takes 13.8ms to transmit with a 5ms preamble.


Listen-before-transmit collision avoidance schemes are applied to prevent loss of data. The length of the preamble period can be also varied to increase the reliability of data reception.

On detection of a preamble, the receiving RPC carries out a number of actions in order to get the data packet correctly. Then the received packet is placed in data buffers.

To tell the host that a data packet has been received successfully, and is awaiting downloading, the RXR line is pulled low by the RPC. The data packet in the receiver RPC has the same contents as those in the transmitting RPC.

Transfer between host and RPC

Figure 5a) shows how data bytes are written into the RPC. Firstly, the host pulls the TXR line low to tell the RPC that the host is about to send data. Then the host waits for the RPC to low its TXA line as an indication that the

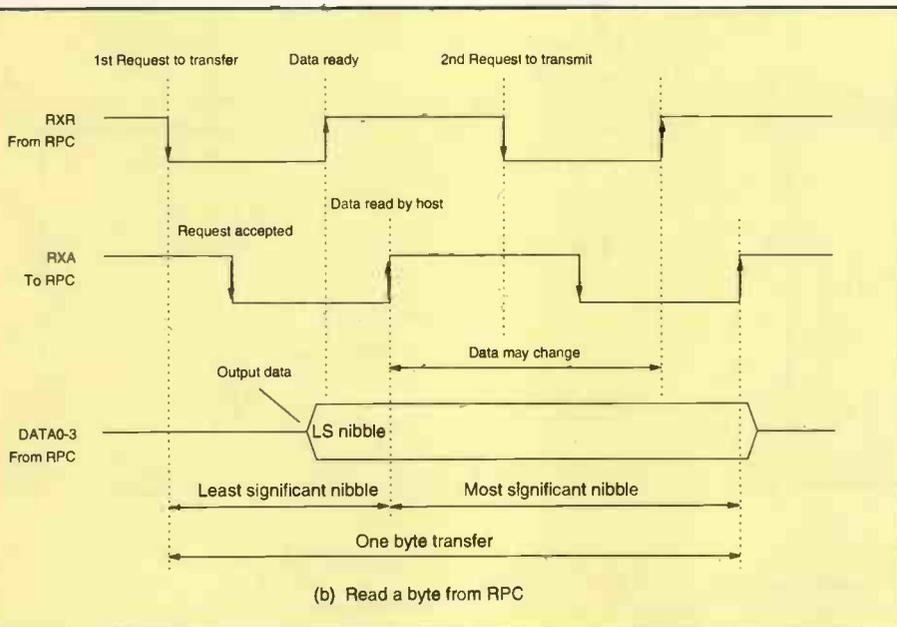

operating modes. These commands are to be written into RPC's memory.

There are 63 on-board memory locations within each RPC, 01_{16} to $3F_{16}$. The first 15 bytes contain parameters to control the RPC. The rest of the memory is free for user-defined data. Functions of the locations are detailed in the manufacturer's data sheet.

For a data packet, the first byte is always the control byte. Bit 7 of the byte is always 0. Bits 6 and 5 are the preamble control bits. For normal preamble, which is the case in this design, bits 6 and 5 are both zero. Bits 4 and 0 indicate the number of bytes in the present packet – including the control byte itself. The maximum number of data bytes is 28, including the control byte.

To read a byte from an RPC's memory location, the byte sent to the RPC by the host has bit 7 set to one and bit 6 to zero. Bits 5 to

0 define the address of a memory location.

The RPC responds with two bytes, the first of which is a control byte itself – i.e. an echo. The second byte is the memory contents.

To write a byte to the RPC's memory, the host issues two bytes: a control byte and the byte to be written into the location. The control byte has bits 6 and 7 set to one. Bits 5 to 0 define the address of a memory location. The RPC does not give any response.

Circuit of the central controller

The central station consists of a MAX232CPE RS232 transceiver, a PIC16F84 and an RPC, Fig. 6. The station connects to a computer via an RS232 port.

Line PA2 of the PIC receives data from an RS232 port while PA3 transmits data to the RS232 port. Port B controls the RPC. Line PA1 connects to a low-current LED that gives

a visual indication.

The power supply to the central station is a DC at 5.5V to 10V. A low-power TC55RP5002 regulator produces the +5V rail. Component layout and connections of the board are shown in Fig 8a).

The communication protocol is rather simple. First, the computer sends a command byte 88_{16} to the central station. The byte is followed by a byte that specifies a remote logger address of 0, 1, 2 or 3.

After the PIC receives these two bytes from the computer, it writes a data packet into the RPC. The packet consists of a control byte 02_{16} and the address byte of 0 to 3. The RPC then broadcasts the data packet.

After the RPC completes the broadcasting, it goes into listening mode to catch the reply from the addressed remote logger.

PIC object code for the remote module

```
:020000001028C6
:1000200083166F30860003308500831200308B000A
:1000300085110516762105116C2105158617061602
:10004000030AF00051826282F1027282F148518F8
:100050002B28AF102C28AF143D20F32002300E02C5
:10006000031D2D28F3200E082F02031D2D288511B6
:1000700043207121E02085152D28762185117621D8
:10008000851576210800103084008E308F00962070
:100090000C088000840A0D088000840A7121CE308B
:1000A0008F0096200C088000840A0D088000840AC6
:1000B00071219E308F0096200C088000840A0D0864
:1000C0008000840A7121DE308F0096200C088000A9
:1000D000840A0D088000840A7121AE308F009620BA
:1000E0000C088000840A0D088000840A7121EE301B
:1000F0008F0096200C088000840A0D088000840A76
:100100007121BE308F0096200C088000840A0D08F3
:100110008000840A7121FE308F0096200C08800038
:10012000840A0D088000840A7121080086170616CB
:100130007121831663308600831286110611051221
:100140007121AE018F1BA6280611A728061567216D
:1001500086156721861107302E020319B228AE0AD0
:100160008F0DA228672167216721AE0186156721BF
:10017000861167210618BE280C10BF280C14073002
:100180002E020319C628AE0A8C0DB628AE018615BC
:100190006721861167210618CF280D1D0D280D146D
:1001A00007302E020319D728AE0A8D0DC728051671
:1001B000762183166F308600831206168617080094
:1001C00005116C2105156C2111308E002821110308D
:1001D000840000088E0028211F3004020319F22831
:1001E000840AE9280800861AF3280612861EF628D3
:1001F0008619FC288E11FD288E15061901290E116D
:1002000002290E15861806298E1007298E14061845
:100210000B290E100C290E140616861A0D2906122B
:10022000861E1029861916298E1317298E1706196E
:100230001B290E131C290E17861820298E1221291E
:100240008E16061825290E1226290E1606160800E7
:10025000712183166030860083128E193129861130
:10026000322986150E1936290611372906158E18DA
:100270003B2986103C2986140E1840290610412976
:1002800006148613061B42298617061F45298E1B56
:100290004B2986114C2986150E1B50290611512910
:1002A00006158E1A55298610562986140E1A5A29B3
:1002B00006105B2906148613061B5C298617061F89
:1002C0005F29712183166F30860083120800123077
:1002D000AD0AD0B692908000F30AD0AD0B6E29E4
:1002E00008003630AD0AD0B732908005030AE0069
:0802F0006C21AE0B7829080017
:00000001FF
```

PIC object code for the central station.

```
:020000001028C6
:1000200083166F30860014308500831200308B00F9
:10003000851085158617061605100C2105142F202E
:10004000D92055300C0203193428AA300C020319A8
:10005000382888300C0203193C282F202D2816211F
:100060008510162185140800AA308C00EC20202869
:1000700055308C00EC202028432011214C201121E8
:10008000592011213C28D920112102308D006520F2
:100090000C088D0065200800A42010308400A420E6
:1000A0000D0880001F30040203195828840A4F28C5
:1000B000800103084000088C00EC201F3004027F
:1000C00003196428840A5B28080011218316603014
:1000D000860083128D196E2806106F2806140D19DC
:1000E00073288610742886148D18782806117928AC
:1000F00006150D187D2886117E2886150612861A8B
:100100007F280616861E82288D1B882806108928BF
:1001100006140D1B8D2886108E2886148D1A9228A1
:100120000611932806150D1A97288611982886150A
:100130000612861A99280616861E9C2811218316F7
:100140006F30860083120800061BA4288613061F42
:10015000A7288619AD280D10AE280D140619B2284F
:100160008D10B3288D148618B7280D11B8280D15D9
:100170000618BC288D11BD288D158617061BBE28B4
:100180008613061FC1288619C7280D12C8280D1608
:100190000619CC288D12CD288D168618D1280D135E
:1001A000D2280D170618D6288D13D7288D17861735
:1001B00008000519D928072102218F010519E22815
:1001C0008C13E3288C17022107300F020319EB2848
:1001D0008C0C8F0ADE280800851102218F010C1C6F
:1001E000F3288515F4288511022107300F02031921
:1001F000FC288C0C8F0AEF28851502210221022190
:10020000022108001C308E008E0B042908001030DB
:100210008E008E0B09290800FF308E008E0B0E29F0
:1002200080036308E008E0B1329080010308F0026
:080230000C218F0B18290800B6
:00000001FF
```

Technical support

Designers' kits, PIC and VB4 source codes are available from the authors. The kit includes PCB boards, all components, programmed PIC and VB5 software. Please direct your enquiry to Dr Pei An, 11 Sandpiper Drive, Stockport, Manchester SK3 8UL.

Tel/fax/answer: +44 (0)161-477-9583.
E-mail: pan@intec-group.co.uk

Visual Basic program list for running the remote data logger on a PC

```

Dim Rsport As Boolean
Dim Data(16) As Byte
Dim Filename, UsePort, UseNolog As String
Dim dummy As Double
Dim i As Integer
Dim TimeStart As Long
Dim Inputdata As String
Dim Overrun As Boolean
Dim Start_time As Long

Sub Delay(ByVal Interval As Integer)
Dim start As Long
    start = Timer
    Do While Timer < start + Interval
    Loop
End Sub

Private Sub Log_data()
If cmbPort.Text = "COM1" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 1
        MSComm1.PortOpen = True
    Else
        MSComm1.CommPort = 1
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
        MSComm1.PortOpen = True
    End If
    Rsport = True

ElseIf cmbPort.Text = "COM2" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 2
        MSComm1.PortOpen = True
    Else
        MSComm1.CommPort = 2
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
        MSComm1.PortOpen = True
    End If
    Rsport = True

ElseIf cmbPort.Text = "COM3" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 3
        MSComm1.PortOpen = True
    Else
        MSComm1.CommPort = 3
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
        MSComm1.PortOpen = True
    End If
    Rsport = True

ElseIf cmbPort.Text = "COM4" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 4
        MSComm1.PortOpen = True
    Else
        MSComm1.CommPort = 4
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
    End If
End Sub

MSComm1.PortOpen = True
End If
Rsport = True
End If
UsePort = cmbPort.Text
UseNolog = CmbNolog.Text
Label1.Caption = "COM port:" + cmbPort + "
Logger No.: " + UseNolog
DoEvents
MSComm1.OutBufferCount = 0
MSComm1.InputLen = 16
MSComm1.Output = Chr$(8 * 16 + 8) +
Chr$(UseNolog)
Start_time = Timer
Overrun = False
Do
    DoEvents
    Label1.Caption = "Communicating with
logger..."
    Overrun = (Timer > Start_time + 2)
    Loop Until (MSComm1.InBufferCount = 16) Or
Overrun
    If Not Overrun Then Label1.Caption = "Data
received logger No. " + UseNolog Else
Label1.Caption = "Communication failed. Try again"
    Inputdata = MSComm1.Input
    If Not Overrun Then
        For i = 0 To 15
            Data(i) = Asc(Right(Inputdata, 16 -
i))
        Next
        For i = 0 To 7
            dummy = (Data(2 * i) * 16# + Data(2 * i + 1) /
16#) / 4096 * 2.508
            lblChD(i).Caption = "& " + Format(dummy,
"0.0000")
        Next i
    End If
End Sub

Private Sub cmdRead_Click()
Dim dummy As Double
Dim i As Integer
Dim TimeStart As Long
Dim Inputdata As String

If cmbPort.Text = "COM1" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 1
        MSComm1.PortOpen = True
    Else
        MSComm1.CommPort = 1
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
        MSComm1.PortOpen = True
    End If
    Rsport = True

ElseIf cmbPort.Text = "COM2" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 2
        MSComm1.PortOpen = True
    Else
    End Sub

```

```

        MSComm1.CommPort = 2
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
        MSComm1.PortOpen = True
    End If
    Rsport = True
    'MSComm1.PortOpen = True

ElseIf cmbPort.Text = "COM3" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 3
        MSComm1.PortOpen = True
    Else
        MSComm1.CommPort = 3
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
        MSComm1.PortOpen = True
    End If
    Rsport = True

ElseIf cmbPort.Text = "COM4" Then
    If Rsport = True Then
        MSComm1.PortOpen = False
        MSComm1.CommPort = 4
        MSComm1.PortOpen = True
    Else
        MSComm1.CommPort = 4
        MSComm1.PortOpen = True
        MSComm1.PortOpen = False
        MSComm1.PortOpen = True
    End If
    Rsport = True
End If

Delay (1)
UsePort = cmbPort.Text
UseNolog = CmbNolog.Text
Label1.Caption = "COM port:" + cmbPort + "
Logger No.: " + UseNolog
DoEvents
MSComm1.OutBufferCount = 0
MSComm1.InputLen = 16
MSComm1.Output = Chr$(8 * 16 + 8) +
Chr$(UseNolog)

Do
    DoEvents
    Label1.Caption = "Communicating with
the logger..."
    Loop Until MSComm1.InBufferCount = 16

Label1.Caption = "Data received logger
No. " + UseNolog

Inputdata = MSComm1.Input

For i = 0 To 15
    Data(i) = Asc(Right(Inputdata, 16 -
i))

    Debug.Print Data(i);
Next

For i = 0 To 7
    dummy = (Data(2 * i) * 16# + Data(2 * i + 1) /
16#) / 4096 * 2.5
    lblChD(i).Caption = " " + Format(dummy,
"0.0000")

```

```

Next I

F:   Filename = "c:\rlg.ini"
    Open Filename For Output As #1
        Print #1, UsePort
        Print #1, UseNolog
    Close #1
    Filename = ""
End Sub

Private Sub CmbNolog_GotFocus()
    Label6.Caption = "Remote Logger No. " +
UseNolog
End Sub

Private Sub cmbPort_GotFocus()
    Command1.Enabled = True
End Sub

Private Sub Command1_Click()
    Log_data
End Sub

Private Sub Command2_Click()
End
End Sub

Private Sub Command3_Click()
    Timer1.Enabled = True
    Command1.Enabled = False
End Sub

Private Sub Command4_Click()
    Timer1.Enabled = False
    Command1.Enabled = True
End Sub

Private Sub Form_Load()
    Timer1.Enabled = False
End Sub


Private Sub Form_MouseMove(Button As Integer, Shift As
Integer, X As Single, Y As Single)
    Label5.Caption = "Com port selected: " + cmbPort.Text
    Label6.Caption = "Remote Logger No. " + CmbNolog.Text
End Sub

Private Sub Timer1_Timer()
    Log_data
End Sub

```

Here's a list of sensors that should interface with the remote data logger with little signal conditioning circuitry.

Sensor type	Part ID	Source
Temperature sensors, °C	LM35	Available from most stockists
Temperature sensors, K	LM135, AD590KH	Available from most stockists
Infrared thermometer	Calex T sensor	RS3299326
Humidity sensors	Mercator RHU217-AT	Farnell 540997
Pressure sensors	PTE5000 series	Sensor Technics
Force sensor	Honeywell	Farnell 7216671
Light intensity sensors	TSL250	Available from most stockists
Human eye light detector	IS474	RS2678447
Acceleration	ADXL05	Available from most stockists
Angular velocity	Murata Gyrostar	Farnell 731985
Magnetic field	Honeywell HMC2003	Farnell 7220121
Ultrasonic distance sensor	UNDK 30U6103	Baumer electric

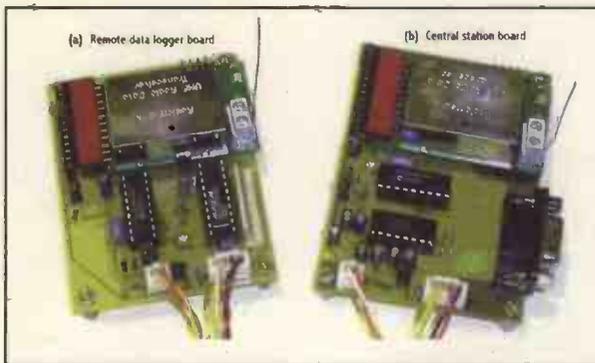

Central station board, right, and remote data logger board, left.

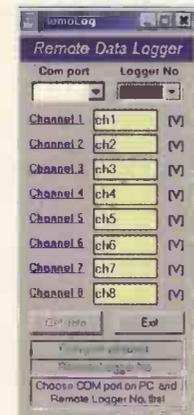


Fig. 9. Screen dump of the Visual Basic 4 control software.

Circuit of the remote data logger

The remote logger is built around a PIC16F84, a MAX147 a-to-d converter and an RPC, Fig. 7. Lines PA0 and PA1 of the PIC set the local address of the logger to 0, 1, 2 or 3.

The MAX147 is a 12-bit 8-channel a-to-d converter. The 2.5V reference is supplied by a TLE2425CPL IC.

Port B of the PIC controls the RPC as well as the MAX147. The power supply to the central station is again 5.5V to 10V DC. A low-power TC55RP5002 regulator produces the 5V rail. Component layout and connections of the board are shown in Fig. 8b).

The flow of the PIC software is as

follows. After a power reset, the RPC is in listening mode. Once a two-byte packet – as broadcast by the central station – is received by the RPC, the PIC checks whether the address byte matches its own address. If they match, the PIC reads eight voltages from the a-to-d converter.

As the conversion result is 12-bit, two bytes are used to present one voltage. Next a data packet is written into the RPC for radio transmission. The packet has 17 bytes – one control byte and 16 data bytes for eight 12-bit data words.

The PIC program also ensures that a remote logger only responds to the message sent by the central station, not to the message sent by remote loggers. This is done by checking the content of the control byte. The control byte sent by the station is 02₁₆, whereas it is 11₁₆ for the remote loggers.

PIC software

The PIC software for the central station and the remote data logger are developed using the PIC assembly language in the MPLAB environment. Both programs are lengthy. They are available from authors. Please see details in the technical support section.

PC software for the central station

The software drive for the central station is written in Visual Basic 4.

Figure 6 shows the screen of the driver. In the window, you should first select a COM port to be used and the address of the remote logger.

Next, click the 'Get Data' button.

If data logging is successful, measured voltage from a remote data logger will appear on the screen. On-line messages are shown at the bottom of the screen.

Application ideas

The analogue input channels require that the input voltage is within 0 to 2.5V. Any sensors having that voltage output level can be connected directly to the logger.

Sensors with other types of outputs require signal conditioning circuitry. A list of sensors that can be used easily with the remote logger is given separately.

Finally, I would like to thank Mr. Kangyan from Radiometrix Ltd for his help and advice on this project. ■

References

1. Data sheets on Radio Packet Controller available from Radiometrix's website www.radiometrix.co.uk. Telephone +44 (0)208 428 1220

Communication between RPCs

RPC encoder. Data bytes to be transmitted by the RPC are converted into a packet before being transmitted. This is to ensure a reliable radio digital data transmission. A packet consists of four parts: preamble, frame synchronisation, data and check sum.

Preamble. The preamble is a 20kHz square wave. The number of cycles can be defined by the user. The initial 3ms portion of the preamble is used to allow the receiving circuitry of the remote RPCs to settle. The remaining 15-cycle portion of the preamble is used by the remote RPCs to phase lock onto the incoming signal. The preamble may be extended to wake-up remote RPCs that are in power-saving mode.

Frame sync

A 7-bit Barker sequence is used to identify the start of the data. An eighth balancing bit is added after the Barker sequence.

Data. Each byte in the RPC's buffer is expanded into a 12-bit symbol prior to sending. The symbol coding has the following properties:

- Perfect 50:50 balance – always 6 zeros and 6 ones
- There are never more than 4 consecutive ones or zeros in a byte.
- Each code is different from any other codes by a minimum of 2 bits.
- Only 256 of 4096 (6.25%) possible codes are valid. This means a 93.75% probability of trapping a byte error.
- Preamble and the frame sync codes are not part of the

symbols. A clash signal will cause immediate termination of the current decoding process.

Check sum. An eight-bit check sum is used to test for overall packet integrity. This is also coded into a 12-bit symbol prior to transmission.

RPC decoder. Radio-signal decoding consists of four steps:

Search. First, the RPC searches for valid preamble comprising a 20kHz square wave. The search is performed by a 16-times over-sampling detector which computes the spectral level of 20kHz in 240 samples of the incoming signal.

Lock-in. The 240 samples are also used to compute the phase of the incoming preamble and synchronise the internal recovery clock to an accuracy of ±2µs. When the frame sync is detected the decoder attains full synchronisation and will move the next stage.

Decode. Data is taken in 12 bits at a time, decoded into the original byte and placed in the buffer. The symbol decoder verifies each received symbol as valid (only 256 out of a possible 4096 are valid) and will abort the decoding process on a symbol failure. The first byte contains the byte count and is used to determine the end of message.

Check sum

The last byte is the received check sum. If the check sum matches the locally calculated one, the RXR line becomes low to inform the host that a packet is ready for downloading.

SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

Ring for Latest Reduced Prices on this advert

HP8444A Tracking Generator • 5-1300Mc/s - £450.
 HP8444A OPT 059 Tracking Gen • 5-1500Mc/s - £650.
 HP35601A Spectrum Anz Interface - £300.
 HP4953A Protocol Anz - 3400.
 HP8970A Noise Figure Meter + 346B Noise Head - £3k.
 HP8755A+B+C Scalar Network Anz PI - £250 + MF 180C - Heads 11664 Extra - £150 each.
 HP3709B Constellation ANZ £1,000.
 FARNELL TVS70MKII PU 0-70V 10 amps - £150.
 MARCONI 6500 Network Scaler Anz - £500. Heads available to 40GHz many types in stock.
 Mixers are available for ANZs to 60GHz.
 Marconi TF2374 Zero Loss Probe - £200.
 Rascal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards and other types.
 Rascal/Dana 9303 True RMS Levelmeter + Head - £450.
 TEKA6902A also A6902B Isolator - £300-£400.
 TEK CT-5 High Current Transformer Probe - £250.
 HP Frequency comb generator type 8406 - £400.
 HP Sweep Oscillators type 8690 A+B + plug-ins from 20Mc/s to 18GHz also 18-40GHz.
 HP Network Analyser type 8407A + 8412A + 8601A - 100Kc/s - 110Mc/s - £500 - £1000.
 HP 8410-A-B-C Network Analyser 110Mc/s to 12 GHz or 18 GHz - plus most other units and displays used in this set-up - 8411a-8412-8413-8414-8418-8740-8741-8742-8743-8746-8650. From £1k.
 Rascal/Dana 9301A-9302 RF millivoltmeter - 1 - 2GHz - qty in stock £250-£400.
 Rascal/Dana Modulation Meter Type 9003-9008 - 40amps - 1.5GHz - £150/£250 - 9009A £250.
 Marconi Microwave 6600A 1 sweep osc., mainframe with 6650PI - 18-26.5 GHz - 151PI - 26.5 - 40GHz-£750 or PI only £600. MF only £250.
 Gould J38 test oscillator - manual - £150.
 Barr & Stroud Variable filter EF3 0.1Hz-100Kc/s - high pass - low pass - £150, other makes in stock.
 Rascal/Dana 9300 RMS voltmeter - £250.
 HP 8750A storage normalizer - £400 with lead + S.A. or N.
 Marconi mod meters type TF2304 - £250 - TF2305 - £1,000.
 Rascal/Dana counters-99904-9905-9906-9915-9916-9917-9921-50Mc/s-3GHz - £100 - £400 - all fitted with PK standards.
 HP180TR, HP181T, HP182T mainframes £300 - £300.
 HP432A-435A or B-436A vector meters + powerheads to 60GHz - £150 - £1750, spare heads available.
 HP3586A or C selective levelmeter - £400.
 HP8622A+B Sweep Pl. 0.1-2.4GHz - ATT £1000-£1250.
 HP86290A+B Sweep Pl-2 - 18GHz - £1000 - £1250.
 HP8620C Mainframe - £250. IEEE £350.
 HP8165A Programmable signal source - 1MHz - 50Mc/s - £1k.
 HP3455/3456A Digital voltmeter - £400.
 HP5370A Universal time interval counter - £1k.
 HP5335A Universal counter - 200Mc/s-£1000.
 TEKTRONIX 577 Curve tracer + adaptors - £900.
 TEKTRONIX 1502/1503 TDR cable test set - £400.
 HP8699B Sweep PI YIG oscillator .01-4GHz - £100, 8699A MF-£250. Both £500.
 Dummy Loads & Power att up to 2.5 kilowatt FX up to 18GHz - microwave parts new and ex equip. relays - attenuators - switches - waveguides - Yigs - SMA - APC7 plugs - adaptors etc. qty. in stock.
 B&K items in stock - ask for list.
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Rascal etc. Ask for list. Large quantity in stock, all types to 400 amp - 100Kv.
 HP8405A Vector voltmeter - late colour - £400.
 HP8508A Vector voltmeter - £2500.

LIGHT AND OPTICAL EQUIPMENT
 Anritsu ML93A & Optical Lead Power Meter - £250.
 Anritsu ML93B & Optical Lead Power Meter - £350.
 Power Sensors for above MASA - MA96A - MA913A.
 Battery Pack MZ95A.
 Anritsu MW97A Pulse Echo Tester.
 PI available - MH914C 1.3 - MH914B 1.3 - MH913B 0.85 - MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM - £500 + one PI.
 Anritsu MW98A Time Domain Reflector.
 PI available - MH914C 1.3 - MH915B 1.3 - MH913B 0.85 - MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM - £500 + one PI.
 Anritsu MZ100A E/O Converter.
 + MG912B (LD 1.35) Light Source + MG92B (LD 0.85) Light Source £350.
 Anritsu MZ118A O/E Converter.
 +MH922A 0.8 O/E unit + MH923 A1.3 O/E unit £350.
 Anritsu ML96B Power Meter & Charger £450.

Anritsu MN95B Variable Att. 1300 £100.
 Photo Dyne 1950 XR Continuous Att. 1300 - 1500 £100.
 Photo Dyne 1800 FA Att £100.
 Cossor-Raytheon 108L Optical Cable Fault Locator 0-1000M 0-10KM £200.
 TEK P6701 Optical Converter 700 MC/S-850 £250.
 TEK OF150 Fibre Optic TDR - £750.
 HP81512A Head 150MC/S 950-1700 £250.
 HP84801A Fibre Power Sensor 600-1200 £250.
 HP8158B ATT OPT 002+011 1300-1550 £300.
 HP81519A RX DC-400MC/S 550-950 £250.
 STC OFR10 Reflexometer - £250.
 STC OFSK15 Machine jointing + eye magnifier - £250.

MISCELLANEOUS ITEMS
 HP 4261 LCR meter - £650.
 HP 4274 FX LCR meter - £1,500.
 HP 3488 Switch Control Unit + PI Boards - £500.
 HP 75000 VXI Bus Controllers - £13268 DVM-quantity.
 HP 83220A GSM DQS POS 1805-1990MC/S generator for use with 8922A - £2,000.
 HP 1630-1631-1650 Logic ANZ's in stock.
 HP 8754A Network ANZ 4-1300MC/S + 8502A + cables - £1,500.
 HP 8754A Network ANZ HZ 4-1300MC/S + 8502A + Cables - £2,000.
 HP 8350A Sweeper MF - 8350A PI 2-8.4GHz - 8354A PI 5.9-12.4GHz all 3 - £3,500.
 HP MICROWAVE TWT AMPLIFIER 489A 1-2GHz-300W - £1,400.
 HP PREAMPLIFIER 8447A 0.1-400MC/S - £200. Dual - £300.
 HP PREAMPLIFIER 8447D 0.01-1.3GHz - £400.
 HP POWER AMPLIFIER 8447E 0.01-1.3GHz - £400.
 HP PRE + POWER AMPLIFIER 8447F 0.01-1.3GHz - £500.
 HP 3574 Gain-Phase Meter 1Hz-13MC/S OPT 001 Dual - £400.
 MARCONI 2305 Modulation Meter-50kHz-2.3 GHz - £1,000.
 MARCONI 2610 True RMS Meter - £450.
 MARCONI 893B AF Power Meter (opt Sinad filter) - £250-£350.
 MARCONI 6950-6960B Power Meters + Heads - £400-£600.
 MARCONI SIGNAL SOURCE 6055-6056-6057-6058-6059-6060-6061-6062-6063-6064-6065-6066-6067-6068-6069-6070-6071-6072-6073-6074-6075-6076-6077-6078-6079-6080-6081-6082-6083-6084-6085-6086-6087-6088-6089-6090-6091-6092-6093-6094-6095-6096-6097-6098-6099-6100-6101-6102-6103-6104-6105-6106-6107-6108-6109-6110-6111-6112-6113-6114-6115-6116-6117-6118-6119-6120-6121-6122-6123-6124-6125-6126-6127-6128-6129-6130-6131-6132-6133-6134-6135-6136-6137-6138-6139-6140-6141-6142-6143-6144-6145-6146-6147-6148-6149-6150-6151-6152-6153-6154-6155-6156-6157-6158-6159-6160-6161-6162-6163-6164-6165-6166-6167-6168-6169-6170-6171-6172-6173-6174-6175-6176-6177-6178-6179-6180-6181-6182-6183-6184-6185-6186-6187-6188-6189-6190-6191-6192-6193-6194-6195-6196-6197-6198-6199-6200-6201-6202-6203-6204-6205-6206-6207-6208-6209-6210-6211-6212-6213-6214-6215-6216-6217-6218-6219-6220-6221-6222-6223-6224-6225-6226-6227-6228-6229-6230-6231-6232-6233-6234-6235-6236-6237-6238-6239-6240-6241-6242-6243-6244-6245-6246-6247-6248-6249-6250-6251-6252-6253-6254-6255-6256-6257-6258-6259-6260-6261-6262-6263-6264-6265-6266-6267-6268-6269-6270-6271-6272-6273-6274-6275-6276-6277-6278-6279-6280-6281-6282-6283-6284-6285-6286-6287-6288-6289-6290-6291-6292-6293-6294-6295-6296-6297-6298-6299-6300-6301-6302-6303-6304-6305-6306-6307-6308-6309-6310-6311-6312-6313-6314-6315-6316-6317-6318-6319-6320-6321-6322-6323-6324-6325-6326-6327-6328-6329-6330-6331-6332-6333-6334-6335-6336-6337-6338-6339-6340-6341-6342-6343-6344-6345-6346-6347-6348-6349-6350-6351-6352-6353-6354-6355-6356-6357-6358-6359-6360-6361-6362-6363-6364-6365-6366-6367-6368-6369-6370-6371-6372-6373-6374-6375-6376-6377-6378-6379-6380-6381-6382-6383-6384-6385-6386-6387-6388-6389-6390-6391-6392-6393-6394-6395-6396-6397-6398-6399-6400-6401-6402-6403-6404-6405-6406-6407-6408-6409-6410-6411-6412-6413-6414-6415-6416-6417-6418-6419-6420-6421-6422-6423-6424-6425-6426-6427-6428-6429-6430-6431-6432-6433-6434-6435-6436-6437-6438-6439-6440-6441-6442-6443-6444-6445-6446-6447-6448-6449-6450-6451-6452-6453-6454-6455-6456-6457-6458-6459-6460-6461-6462-6463-6464-6465-6466-6467-6468-6469-6470-6471-6472-6473-6474-6475-6476-6477-6478-6479-6480-6481-6482-6483-6484-6485-6486-6487-6488-6489-6490-6491-6492-6493-6494-6495-6496-6497-6498-6499-6500-6501-6502-6503-6504-6505-6506-6507-6508-6509-6510-6511-6512-6513-6514-6515-6516-6517-6518-6519-6520-6521-6522-6523-6524-6525-6526-6527-6528-6529-6530-6531-6532-6533-6534-6535-6536-6537-6538-6539-6540-6541-6542-6543-6544-6545-6546-6547-6548-6549-6550-6551-6552-6553-6554-6555-6556-6557-6558-6559-6560-6561-6562-6563-6564-6565-6566-6567-6568-6569-6570-6571-6572-6573-6574-6575-6576-6577-6578-6579-6580-6581-6582-6583-6584-6585-6586-6587-6588-6589-6590-6591-6592-6593-6594-6595-6596-6597-6598-6599-6600-6601-6602-6603-6604-6605-6606-6607-6608-6609-6610-6611-6612-6613-6614-6615-6616-6617-6618-6619-6620-6621-6622-6623-6624-6625-6626-6627-6628-6629-6630-6631-6632-6633-6634-6635-6636-6637-6638-6639-6640-6641-6642-6643-6644-6645-6646-6647-6648-6649-6650-6651-6652-6653-6654-6655-6656-6657-6658-6659-6660-6661-6662-6663-6664-6665-6666-6667-6668-6669-6670-6671-6672-6673-6674-6675-6676-6677-6678-6679-6680-6681-6682-6683-6684-6685-6686-6687-6688-6689-6690-6691-6692-6693-6694-6695-6696-6697-6698-6699-6700-6701-6702-6703-6704-6705-6706-6707-6708-6709-6710-6711-6712-6713-6714-6715-6716-6717-6718-6719-6720-6721-6722-6723-6724-6725-6726-6727-6728-6729-6730-6731-6732-6733-6734-6735-6736-6737-6738-6739-6740-6741-6742-6743-6744-6745-6746-6747-6748-6749-6750-6751-6752-6753-6754-6755-6756-6757-6758-6759-6760-6761-6762-6763-6764-6765-6766-6767-6768-6769-6770-6771-6772-6773-6774-6775-6776-6777-6778-6779-6780-6781-6782-6783-6784-6785-6786-6787-6788-6789-6790-6791-6792-6793-6794-6795-6796-6797-6798-6799-6800-6801-6802-6803-6804-6805-6806-6807-6808-6809-6810-6811-6812-6813-6814-6815-6816-6817-6818-6819-6820-6821-6822-6823-6824-6825-6826-6827-6828-6829-6830-6831-6832-6833-6834-6835-6836-6837-6838-6839-6840-6841-6842-6843-6844-6845-6846-6847-6848-6849-6850-6851-6852-6853-6854-6855-6856-6857-6858-6859-6860-6861-6862-6863-6864-6865-6866-6867-6868-6869-6870-6871-6872-6873-6874-6875-6876-6877-6878-6879-6880-6881-6882-6883-6884-6885-6886-6887-6888-6889-6890-6891-6892-6893-6894-6895-6896-6897-6898-6899-6900-6901-6902-6903-6904-6905-6906-6907-6908-6909-6910-6911-6912-6913-6914-6915-6916-6917-6918-6919-6920-6921-6922-6923-6924-6925-6926-6927-6928-6929-6930-6931-6932-6933-6934-6935-6936-6937-6938-6939-6940-6941-6942-6943-6944-6945-6946-6947-6948-6949-6950-6951-6952-6953-6954-6955-6956-6957-6958-6959-6960-6961-6962-6963-6964-6965-6966-6967-6968-6969-6970-6971-6972-6973-6974-6975-6976-6977-6978-6979-6980-6981-6982-6983-6984-6985-6986-6987-6988-6989-6990-6991-6992-6993-6994-6995-6996-6997-6998-6999-7000-7001-7002-7003-7004-7005-7006-7007-7008-7009-7010-7011-7012-7013-7014-7015-7016-7017-7018-7019-7020-7021-7022-7023-7024-7025-7026-7027-7028-7029-7030-7031-7032-7033-7034-7035-7036-7037-7038-7039-7040-7041-7042-7043-7044-7045-7046-7047-7048-7049-7050-7051-7052-7053-7054-7055-7056-7057-7058-7059-7060-7061-7062-7063-7064-7065-7066-7067-7068-7069-7070-7071-7072-7073-7074-7075-7076-7077-7078-7079-7080-7081-7082-7083-7084-7085-7086-7087-7088-7089-7090-7091-7092-7093-7094-7095-7096-7097-7098-7099-7100-7101-7102-7103-7104-7105-7106-7107-7108-7109-7110-7111-7112-7113-7114-7115-7116-7117-7118-7119-7120-7121-7122-7123-7124-7125-7126-7127-7128-7129-7130-7131-7132-7133-7134-7135-7136-7137-7138-7139-7140-7141-7142-7143-7144-7145-7146-7147-7148-7149-7150-7151-7152-7153-7154-7155-7156-7157-7158-7159-7160-7161-7162-7163-7164-7165-7166-7167-7168-7169-7170-7171-7172-7173-7174-7175-7176-7177-7178-7179-7180-7181-7182-7183-7184-7185-7186-7187-7188-7189-7190-7191-7192-7193-7194-7195-7196-7197-7198-7199-7200-7201-7202-7203-7204-7205-7206-7207-7208-7209-7210-7211-7212-7213-7214-7215-7216-7217-7218-7219-7220-7221-7222-7223-7224-7225-7226-7227-7228-7229-7230-7231-7232-7233-7234-7235-7236-7237-7238-7239-7240-7241-7242-7243-7244-7245-7246-7247-7248-7249-7250-7251-7252-7253-7254-7255-7256-7257-7258-7259-7260-7261-7262-7263-7264-7265-7266-7267-7268-7269-7270-7271-7272-7273-7274-7275-7276-7277-7278-7279-7280-7281-7282-7283-7284-7285-7286-7287-7288-7289-7290-7291-7292-7293-7294-7295-7296-7297-7298-7299-7300-7301-7302-7303-7304-7305-7306-7307-7308-7309-7310-7311-7312-7313-7314-7315-7316-7317-7318-7319-7320-7321-7322-7323-7324-7325-7326-7327-7328-7329-7330-7331-7332-7333-7334-7335-7336-7337-7338-7339-7340-7341-7342-7343-7344-7345-7346-7347-7348-7349-7350-7351-7352-7353-7354-7355-7356-7357-7358-7359-7360-7361-7362-7363-7364-7365-7366-7367-7368-7369-7370-7371-7372-7373-7374-7375-7376-7377-7378-7379-7380-7381-7382-7383-7384-7385-7386-7387-7388-7389-7390-7391-7392-7393-7394-7395-7396-7397-7398-7399-7400-7401-7402-7403-7404-7405-7406-7407-7408-7409-7410-7411-7412-7413-7414-7415-7416-7417-7418-7419-7420-7421-7422-7423-7424-7425-7426-7427-7428-7429-7430-7431-7432-7433-7434-7435-7436-7437-7438-7439-7440-7441-7442-7443-7444-7445-7446-7447-7448-7449-7450-7451-7452-7453-7454-7455-7456-7457-7458-7459-7460-7461-7462-7463-7464-7465-7466-7467-7468-7469-7470-7471-7472-7473-7474-7475-7476-7477-7478-7479-7480-7481-7482-7483-7484-7485-7486-7487-7488-7489-7490-7491-7492-7493-7494-7495-7496-7497-7498-7499-7500-7501-7502-7503-7504-7505-7506-7507-7508-7509-7510-7511-7512-7513-7514-7515-7516-7517-7518-7519-7520-7521-7522-7523-7524-7525-7526-7527-7528-7529-7530-7531-7532-7533-7534-7535-7536-7537-7538-7539-7540-7541-7542-7543-7544-7545-7546-7547-7548-7549-7550-7551-7552-7553-7554-7555-7556-7557-7558-7559-7560-7561-7562-7563-7564-7565-7566-7567-7568-7569-7570-7571-7572-7573-7574-7575-7576-7577-7578-7579-7580-7581-7582-7583-7584-7585-7586-7587-7588-7589-7590-7591-7592-7593-7594-7595-7596-7597-7598-7599-7600-7601-7602-7603-7604-7605-7606-7607-7608-7609-7610-7611-7612-7613-7614-7615-7616-7617-7618-7619-7620-7621-7622-7623-7624-7625-7626-7627-7628-7629-7630-7631-7632-7633-7634-7635-7636-7637-7638-7639-7640-7641-7642-7643-7644-7645-7646-7647-7648-7649-7650-7651-7652-7653-7654-7655-7656-7657-7658-7659-7660-7661-7662-7663-7664-7665-7666-7667-7668-7669-7670-7671-7672-7673-7674-7675-7676-7677-7678-7679-7680-7681-7682-7683-7684-7685-7686-7687-7688-7689-7690-7691-7692-7693-7694-7695-7696-7697-7698-7699-7700-7701-7702-7703-7704-7705-7706-7707-7708-7709-7710-7711-7712-7713-7714-7715-7716-7717-7718-7719-7720-7721-7722-7723-7724-7725-7726-7727-7728-7729-7730-7731-7732-7733-7734-7735-7736-7737-7738-7739-7740-7741-7742-7743-7744-7745-7746-7747-7748-7749-7750-7751-7752-7753-7754-7755-7756-7757-7758-7759-7760-7761-7762-7763-7764-7765-7766-7767-7768-7769-7770-7771-7772-7773-7774-7775-7776-7777-7778-7779-7780-7781-7782-7783-7784-7785-7786-7787-7788-7789-7790-7791-7792-7793-7794-7795-7796-7797-7798-7799-7800-7801-7802-7803-7804-7805-7806-7807-7808-7809-7810-7811-7812-7813-7814-7815-7816-7817-7818-7819-7820-7821-7822-7823-7824-7825-7826-7827-7828-7829-7830-7831-7832-7833-7834-7835-7836-7837-7838-7839-7840-7841-7842-7843-7844-7845-7846-7847-7848-7849-7850-7851-7852-7853-7854-7855-7856-7857-7858-7859-7860-7861-7862-7863-7864-7865-7866-7867-7868-7869-7870-7871-7872-7873-7874-7875-7876-7877-7878-7879-7880-7881-7882-7883-7884-7885-7886-7887-7888-7



Hard drive havoc

Once bitten, twice shy, that's me. Learning the hard way is the only real way of finding out what a data loss really means and boy, do I know now! That gut-wrenching feeling as your hard drive stops and a reboot brings up the message, "primary device failure," followed by the realisation that the back-up you meant to do last month never happened.

Having not practised what I preached, I had to come to terms with the loss of 15 years' accumulated data – my contact details, my accounts records, the text files including a complete book I was working on. All gone, or so I thought.

In fact I had a month-old partial backup so I could re-create most of my appointments and accounting data. But all my current writing assignments, half-started articles, related notes and briefs for new jobs had vanished. And all because I hadn't backed up.

But what about you? Forget about my problem now; are you backed up? Do you rely on your PC for your livelihood? If it went into meltdown mode could you laugh it off and start again? Would insurance help? How long would it take to re-create the lost data and what would this cost in lost earnings? Or should you be thinking of taking the frazzled drive to a data recovery specialist in the hope it can be fixed?

What to do

To begin, start backing up regularly if you're not already doing so. But if you do have the misfortune to suffer hard-disk failure, don't try and fix it yourself. There's nothing useful that keen users or PC

Your hard drive just took a dive and you haven't backed it up for months. Is there any hope of recovering your information, or is everything lost?

Andrew Emmerson reports.

technicians can do to mend hard drives; any tinkering will only do harm. All you can do is replace the hard drive, reload the operating system

and application software and start over again.

If you're intending to use a data recovery service, save the drive and pack it carefully with the original documentation. But don't investigate it yourself.*

How drives fail...

Hard drives are remarkably reliable in the main; until my recent escapade I suffered no failure in 15 years and most other users are equally fortunate. But that's purely a statistic, just as the mean time between failure (MTBF) quoted in hard-drive specifications is purely an average.

In fact malfunctions of this kind can come at any time and make up the prime cause of data loss according to data recovery specialists Ontrack, as the chart shows. What's more, as storage capacities and density get ever higher, the impact of data loss problems can only increase. You have been warned!

Hard-drive failures are classed as either physical or logical. Of course I had to have both kinds of failure simultaneously, which is

most unusual and typical bad luck!

Physical failure implies some kind of physical destruction; it can be electronic (one of the control chips may have given up the ghost) or else mechanical, such as the dreaded head crash.

The read/write heads float above the magnetic platter on a cushion of air narrower than a human hair, so it doesn't take much disturbance to cause the most almighty ploughing up of data. The fact that grief is so rare is a tribute to the engineering standards and the hermetically sealed container in which the heads and platter reside.

Logical failure is less catastrophic; in this case the data is not actually destroyed but still effectively lost because something has wiped the disk's file allocation table (FAT) or partition information, thus erasing the directory that catalogues your data. Imagine, if you like, dropping a ring binder of 10000 un-numbered data sheets written in Chinese. You could gather up every piece of paper but without page numbers you'd never assemble them in the right order again.

...and why they fail

Accidents don't happen; they are caused. Power surges, malicious disk activity and supply interruptions are the chief sources of disk failure.


* If the data on your corrupted hard drive isn't that dear to you, try using Norton Utilities or a similar rescue package to recover it. Such software usually allows you to make a rescue floppy disk while your system is working properly. This disk is supposed to increase your chances of recovering data on the next crash.

Before you give up on a corrupted hard drive, try low-level formatting it. The only low-level formatter that I've found that wipes a drive clean enough to allow the OEM version of Windows 98 to load is SGATFMT from Seagate. It is only supposed to work with Seagate drives but I've used the 'custom' option many times on many different makes up to 5Gbyte.

I have read that low-level formatting can render a hard drive unusable though, and it will no doubt void any warranties, so be warned. Let the drive run for half an hour before formatting.

This software can be made to write a test pattern in each location then read it and report any errors. I believe that it also locks out any bad sectors. If the software finds catastrophic errors, it aborts the format. You will need to run it from a system floppy. A search using SGATFMT4 via Google should turn up Seagate's web site.

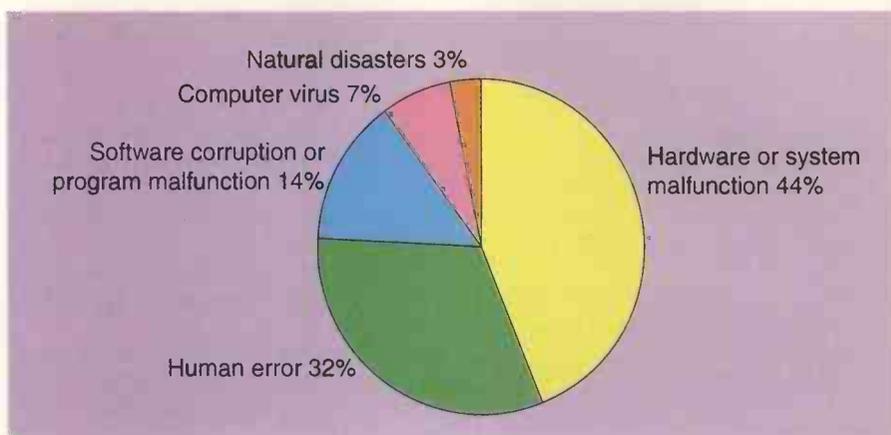Windows' Scandisk utility can be set to check your hard drive's integrity using the 'thorough' option. According to its description, a package called Spinrite constantly monitors your hard drive for impending failures. It is available from the GRC site whose address is in the contacts panel. Ed.



Leading causes of data loss, information courtesy Ontrack.

Surge filters and anti-virus software will go a long way to curing the first two evils and these are both low-cost solutions. Uninterruptible power supplies (UPS devices) will sort out supply fluctuations at a higher (but not outrageous) price.

Sometimes impending disk failure gives warning signs; very sluggish disk activity and ominous clicking sounds – both caused by repeated read/write attempts – are a clue. By this time the damage is probably done, however. Bad news.

Mission impossible?

Data recovery from dead disk drives is not impossible. Specialist firms boast of 95 per

cent success rates, but the rates they charge may put you off. In most cases you can expect little change out of £1000 and only you can decide if the lost data is worth this price. If, as in my case, your livelihood genuinely depends on it, then the cost is irrelevant. For what you get it's not bad value really.

Physical failures demand repair in a clean-room atmosphere with skills approaching those of a brain surgeon. They also involve the procurement of an identical drive for replacement parts. Finding old-production disk drives can be acutely difficult.

The work may be done on a 'no fix, no fee' basis and since the difference of just

Tips from the professionals

- Successful data recovery takes time, no matter how high its priority. There are no magic machines or instant utilities that can do the job; it's a highly specialised skill.
- There are occasions when data is damaged beyond any kind of recovery but it's a rare case when absolutely no data is retrievable. Most companies claim a data recovery success rate of around 85%.
- More data is lost every year to failed recovery attempts, than to actual breakdown or malfunction. Frequently there is no second chance so don't even think of tinkering!
- Hard disks are sealed units and just disturbing screws on the mechanical casing can destroy a drive.
- Despite a rash of new companies, there are still only a handful of legitimate, professional recovery services. Ask for references and make your choice carefully! Would you trust your valuable data to un-named individuals on an anonymous web site?
- Where the recovery company is located is irrelevant; your choice should be based on what they can do not where they are. Whether they are five or 500 miles away will make no difference in the time it takes to evaluate and recover your information.
- Maybe you do have backups but have you considered keeping them off-site, where they may be safer?
- Your problem may not be the media you've stored your data on at all. Are the drives connectors all seated properly? Is your hardware or driver configuration correct?

Useful contacts

This is not an exhaustive list nor to be taken as endorsement or recommendation. Other firms can be found on the WWW by using a search engine and the phrase 'data recovery'.

- CBL Data Recovery Technologies Limited. 0800 028 2069, <http://www.cbltech.co.uk>
- MjM Data Recovery Ltd. 01462 680 733 <http://www.mjm.co.uk>
- Vogon International. 01869 355255 vogoninternational.com
- Data recovery problem solver wizard: <http://www.ontrack.com/help-wizard/index.asp>
- The (in)famous Click of death resource page – essential reading for Zip and Jaz drive users: <http://www.grc.com/clickdeath.htm>

one month in manufacturing date can render a potential donor unit useless, the repair process can be a slow and expensive task.

No mechanical skills are needed for repairing logical failures but the work is just as involved. Hours of patient bit twiddling may be needed to recreate the file structure of a confused hard drive, the more so if the data had not been defragmented recently.

Last words

By now you should be dashing to make a backup. Either that or you're smiling because your backups are fully up to date. Pride goes before a fall, though; backups assume that your hardware and storage media are in working order; that the data is not corrupted, and that your backup is recent enough to provide full recovery. In reality, hardware and software do fail and backups don't always contain current enough data. Maybe it's time to make sure!

Put it in the fridge then tap it...

Just in case you didn't see it in the August 2000 issue, Ed Dell's letter advises owners of failed hard drives to try putting the drive in the refrigerator for an hour. Take it out, then tap it lightly and re-install. This works most of the time for Ed. A follow-up letter from Chris Eccles in the September issue explains why this trick might work.

Fatalists will argue it's all inevitable and that data loss happens to us all sooner or later. No matter how fastidious we are about backing up there will always be a crucial file created after the backup and thus lost to Silicon Heaven.

What's more, every cloud has a silver lining; as a result of my mishap I bought a new, faster, larger drive and now my PC loads far quicker and runs more efficiently. I also bought a second drive and 'mirroring' software by DataKeeper so that all work created on Drive C: is copied automatically to the D: drive as a back-up.

I'm still out of pocket though, and a lot of data that I carefully saved over the years is gone forever. It's a crying shame but a useful lesson!

How a UPS can help

An uninterruptible power supply, or UPS, is a kind of power station in miniature, using battery-powered electronics to produce a limited quantity of mains electricity as and when needed. It cuts in when there's a total outage (black-out), temporary hiccup (drop-out) or voltage reduction (brown-out).

A UPS also buffers the supply by filtering out the excess voltage surges that can destroy chips and data. It won't hold for long, but it will keep your computer running long enough to save data held in memory and shut down the computer gracefully.

Some UPS models come with power-save software that handles these back-up and shut-down procedures automatically if there's a power failure in your absence.

With a UPS, the more you pay, the better you get. Simple 'standby' systems monitor the mains and switch over to battery power when a problem is detected. Even if this is only a millisecond or two, this delay may be too long.

'On-line' models eliminate even momentary power cuts. They do this by providing power constantly from their own battery, even when the mains supply is normal. The battery is constantly under charge. On-line UPSs are superior but more expensive.

Would insurance help?

Data that has taken a lot of time to assemble can have a very high value, whether it's a

Eurocard interface design, the accounts database of your business or your twenty-volume family history. Consequently an insurance policy is no substitute for proper back-ups. Moreover you'll find that many home and small business insurance policies specifically exclude computer hardware failure too.

In some cases the insurers will pay the cost of manually recreating lost data and of replacing hardware destroyed by fire or lightning. In my own case, in which the hard drives were zapped by a power surge, the company was prepared to treat this as lightning and paid up the replacement cost – minus a standard 'excess' of £100. They also paid for the services of a data recovery expert, which made me mightily pleased I had taken out cover.

What will it cost?

Some data recovery firms work on a 'no fix, no fee' basis, while others charge an initial diagnosis fee of around £150. It is most likely that you will end up paying the same overall if recovery is possible.

Repairing a logical failure could cost between £350 and £500, while curing physical damage could easily double that cost. Worse still, work may be delayed while the contractor finds a suitable donor drive; because of constant firmware revisions and design improvements the precise characteristics of hard drives change over time. Consequently, if your drive was made in February 1998, parts from an August 1999 model may be totally unsuitable. Only an expert can tell, and finding NOS (new old stock) drives can be an expensive and very time-consuming task.

Add VAT to all these prices of course.

What if it still doesn't work?

You may have some problems when your data is recovered, but don't despair. Some DIY tasks remain even after the data recovery firm has handed you a fistful of CD-Rs containing what they have found for you.

Assuming you're using Windows Explorer, the folder names will probably show the ~ symbol (swung dash, tilde or 'twiddle') as their first character. The rest of the folder name will give you a good clue to the real name.

Most programs should now work, although you may find that document files refuse to load. The trick is to bypass Word or whatever and use Wordpad or a file viewer such as Quick View Plus. You'll find your text inside the files plus a load of garbage that was preventing it loading. Select the meaningful parts you want, then copy this into a brand new file and save it. ■

New filter/mixer chip

A versatile high-Q bandpass filter chip with integral mixer has recently been launched by UK semiconductor manufacturer **Zetex**. The subject of our design competition on page 187, this filter operates to 150kHz and its mixer extends operation to 700kHz.

The new ZXF36L01 is a versatile analogue high-Q filter chip. In addition to its variable-Q bandpass or bandstop filter, the device also contains a mixer block, extending its range of applications.

To set the centre frequency, the basic filter section requires two resistors and two capacitors. Filter Q is controlled by two external resistors and can be varied up to about 50, Fig. 1.

While the filter operates up to 150kHz, the mixer extends the useful frequency range up to 700kHz and allows the frequency to be tuned. The local oscillator can be any waveform, making microprocessor control convenient.

The device is expected to be useful in audio gear and instrumentation for bandpass, notch and adaptive filtering. As the waveform at the local oscillator's input is irrelevant, a microcontroller can be used to produce a low-cost and variable frequency input.

Combining the filter and mixer functions in one low-cost chip makes the device interesting for sonar and ultrasonics, as you will see from the application outlined in the separate panel.

Typical operating current of this 5V device is 3.4mA and there's a shutdown mode reducing current to just 160µA. Devices are easily cascaded.

Filter circuits

From Figs 2, 3 & 4, you can see how easy it is to implement various notch filters. Centre frequency, f_c , is given by,

$$f_c = \frac{1}{2\pi RC}$$

while Q is,

$$Q \propto \frac{R_f}{R_i}$$

Here R , R_i and $R_f \geq 10k\Omega$ and $C \geq 50pF$.

There's more on designing for a value of Q in the device data sheet.

Figure 5 shows how the device's frequency range can be extended using the mixer block.

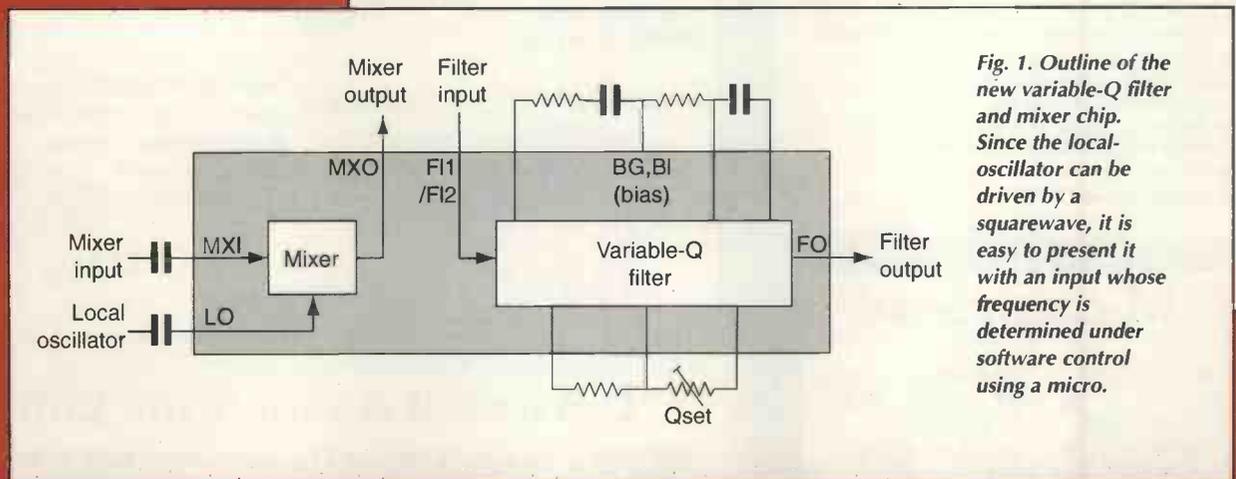


Fig. 1. Outline of the new variable-Q filter and mixer chip. Since the local-oscillator can be driven by a squarewave, it is easy to present it with an input whose frequency is determined under software control using a micro.

Fig. 2. Circuit for a notch band-stop filter using the ZXF36L01, together with its gain and phase response graphs.

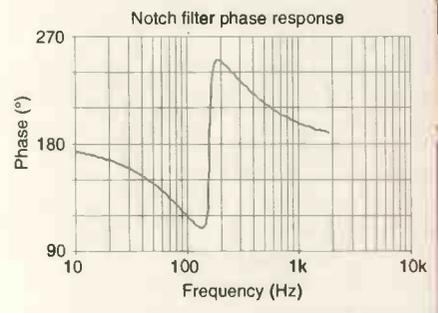
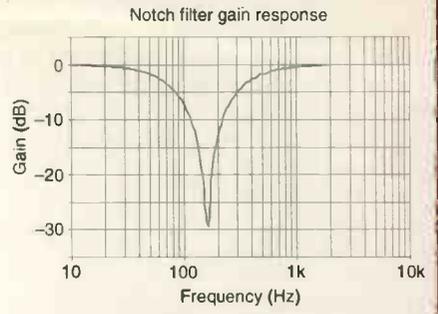
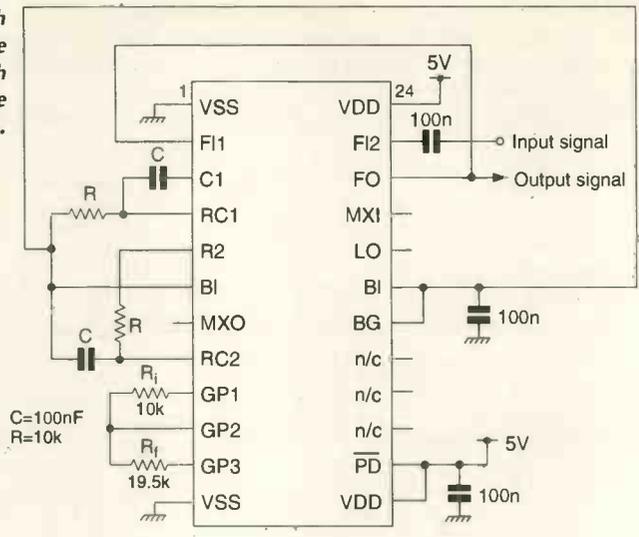


Fig. 3. Circuit for a band-pass filter with 0dB stop level.


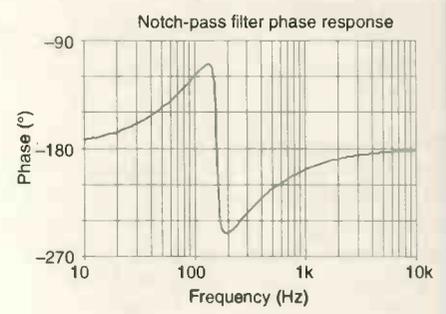
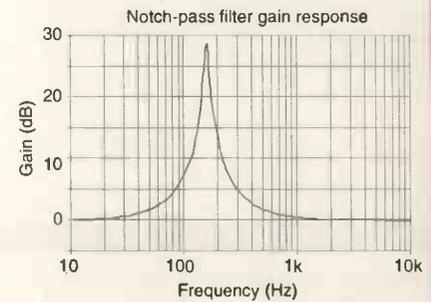
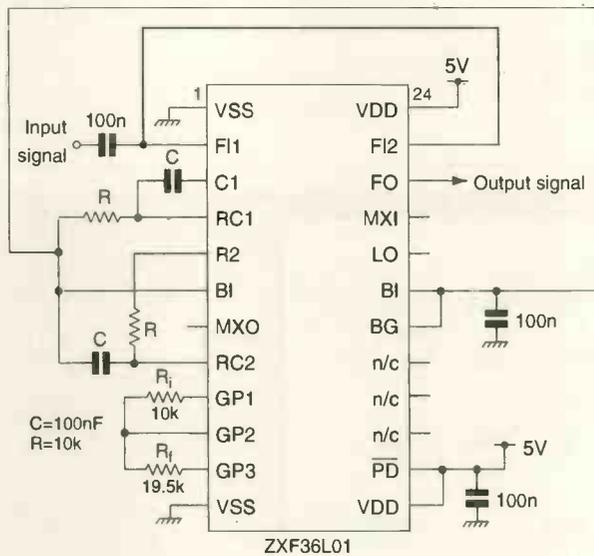
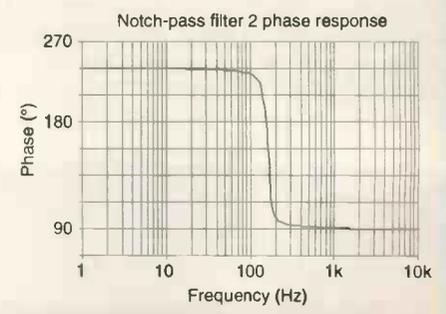
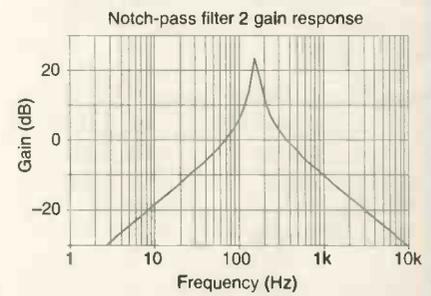


Fig. 4. Notch filter with attenuating skirts. Skirt 'roll-off' away from the peak is -20dB/decade, regardless of Q.

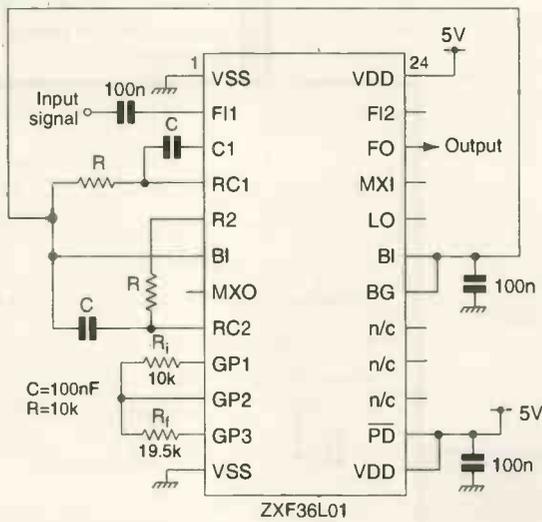

Design example - using the ZXF36L01 in a sonar application

In a typical sonar system, the transducer is pulsed at its resonant frequency and the reflection is received after a period proportional to distance. The ZXF36L01 variable-Q filter is used to maximise the sensitivity at the required frequency and reduce noise. The on-chip mixer allows the received frequency to be tuned to accommodate different transducer frequencies.


The diagram shows how the ZXF36L01 provides a tuning and filtering solution for a sonar system. The received signal is first processed by an amplifier. This amplifier's gain increases with time to compensate for the reduction in reflected signal with time. At the same time, this amplifier reduces problems due to input overload.

From here, the signal is mixed with a local oscillator generated by a micro-controller. The filter then selects the appropriate signal.

In this example for a

200kHz transducer, the filter is set at 75kHz and the local oscillator at 275kHz. The mixer output contains the sum at 475kHz and the difference at 75kHz and the filter selects the 75kHz signal.

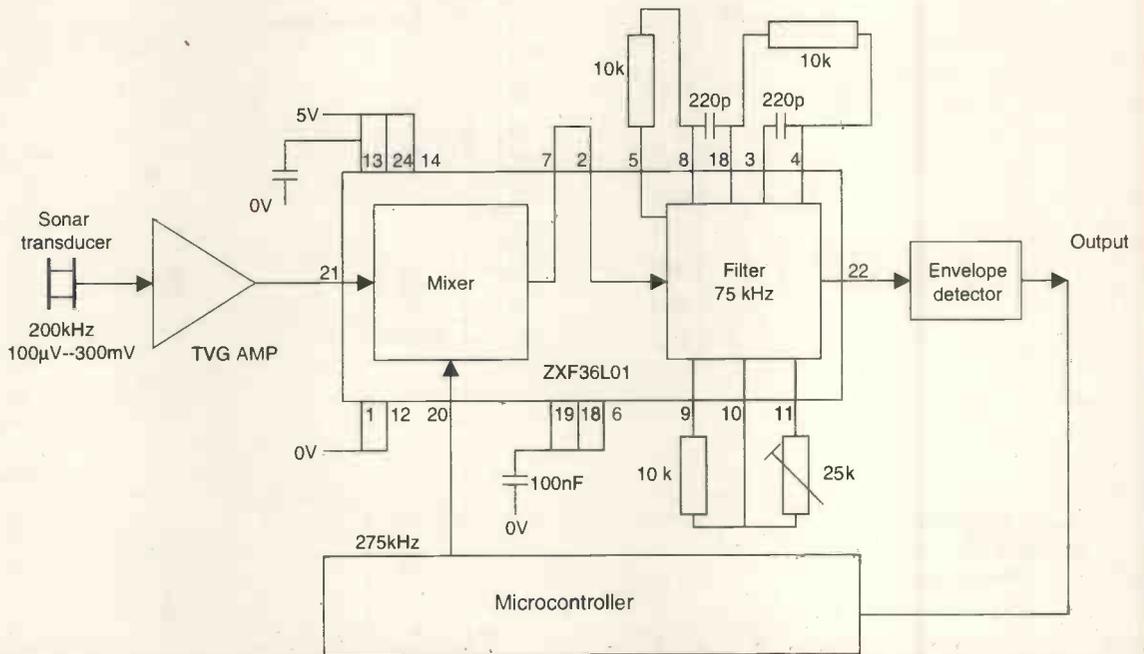An envelope detector follows the filter to provide a voltage proportional to the received signal. A microcontroller can now be used to process the time delay and signal strength to provide distance information.



Electrical characteristics of the ZXF36L01

Supply current

Parameter	Conditions	Min.	Typ.	Max.	Units
Operating	Filter	2.2	3.4	4.5	mA
Shutdown			160	300	µA

Filter characteristics

Parameter	Conditions	Min.	Typ.	Max.	Units
Max. operating frequency				150	kHz
Q usable range		0.5		50	
Centre frequency temp. co.	Q=30, $f_0=1\text{kHz}$		2000		ppm/°C
Q temp. co.	Q=30, $f_0=1\text{kHz}$		0.7		%/°C
Voltage Noise	1-100kHz		20		nV/√Hz
Input Impedance		30		50	kΩ
Linear output range	10kΩ load		1.6		V p-p
Sink current			150		µA
Source current			150		µA


Typical mixer characteristics

Max. operating frequency	700kHz
Maximum signal input	300mV p-p
Maximum LO input	100mV p-p
Minimum LO input	5mV p-p
LO input impedance	60Ω

Absolute maximum ratings

Voltage on any pin	7.0V relative to V_{SS}
Operating temperature range	0 to 70°C, derated for -40 to 85°C
Storage temperature	-55 to 125°C
Test conditions: temperature	25°C, $V_{DD} = 5.00$, $V_{SS} = 0V$

Fig. 5. Filtering higher frequencies using the mixer. The signal to be filtered is mixed with the LO, whose frequency is chosen so that the difference, or intermediate, frequency equals the filter's centre frequency.

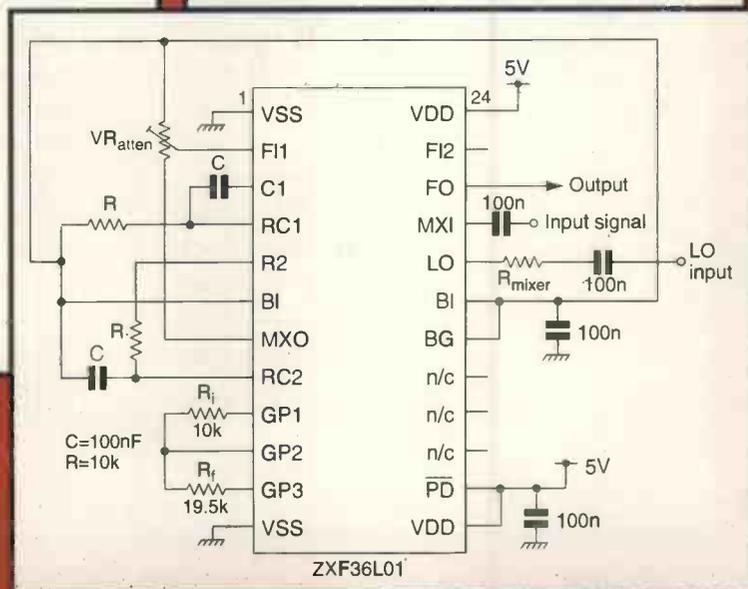

Design competition

Devise a useful and/or ingenious application for the ZXF36L01 versatile high-Q bandpass filter with integral mixer and you could win a £500 voucher to spend with Farnell. There's two runner up prizes of £100 vouchers too.

Rules

- Electronics World reserves the right to publish submitted entries. All designs published will be attributed to their designers. A minimum payment of £50 will be made for each design published.
- Submission of an entry does not remove your right to exploit your design, but it does give Zetex the right to use the entry as an application note, or as the basis thereof, effectively making the design public domain.
- Winners will be chosen jointly by technical experts from Zetex, Farnell and the editor of Electronics World. The judges' choice will be final and no correspondence will be entered into regarding the choice of winner.
- No employee of Reed Business Information, Zetex and Farnell, or any of their associated companies, may enter this competition, nor may members of their families.
- No entry will win more than one prize, but multiple entries may be submitted.
- Prizes are as stated here and not negotiable.
- Entries arriving after the closing date will be void.
- No purchase is necessary to enter this competition.
- Winners will be notified by post, and the results may be publicised.
- For a list of winning entries, send an SAE to the editorial offices.
- Submitting an entry for the competition implies acceptance of these rules.

Launched this year, the ZXF36L01 is a versatile high-Q bandpass filter requiring a minimum of external components. In addition to the variable-Q analogue filter there is also a mixer block, making the device suitable for a wide range of applications.

All you have to do to enter the competition is send a design idea incorporating the ZXF36L01 to the address below. Entries will be judged on ingenuity, originality and usefulness. All entries are subject to the rules set out below.



A designer's kit is available from Farnell and you can find full data on the device on Zetex's web site <http://www.zetex.com/pdf/ics/zxf36101.pdf>.

It is not necessary for you to prove your design, and buying the kit is not a condition of entry into the competition. The design you submit has to work in practice but you will not be penalised for not having built a prototype.

If you do submit a design that meets the competition criteria and you have bought the kit, then you will receive a Farnell voucher for £15, courtesy of Zetex.

Send your entry to Filter Design, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Note that it is not necessary to send your prototype! Simply send the circuit diagram and a clear, concise description of the circuit. It will help if you describe why you think that your circuit should be among the winners. You can also e-mail your entry to jackie.lowe@rbi.co.uk, but unless the e-mail has a subject heading that reads 'Filter Design' it will not be eligible. Please attach diagrams and text separately and include a daytime phone number with your entry if possible.

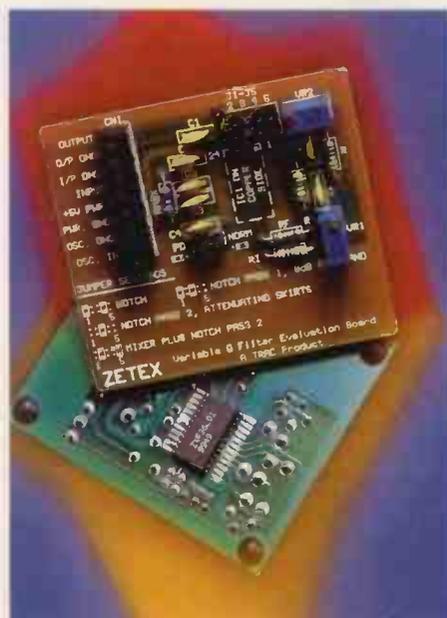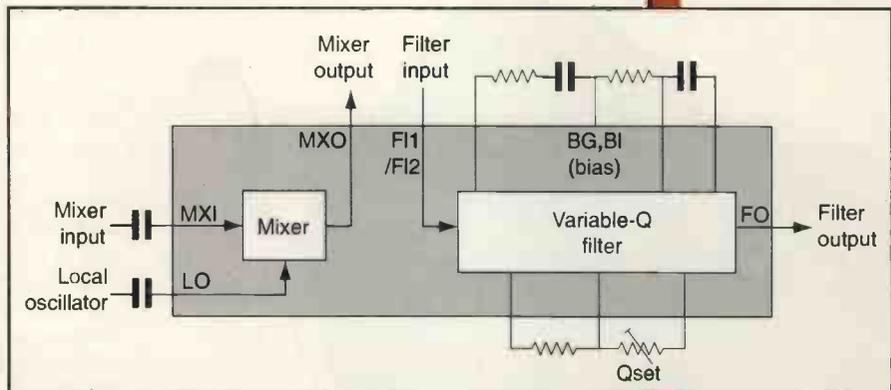The closing date for the competition is 30 April.



You don't need to buy this new development board for the ZXF36L01 in order to enter the competition, but if you do, and your entry meets the competition requirements, you will receive a Farnell voucher for £15 to help cover its cost.

**Win a £500
voucher
redeemable
at Farnell.**

For more information...

Visit <http://www.farnell.co> for details of the ZXF36L01 development kit or <http://www.zetex.com/pdf/ics/zxf36101.pdf> for more data on the filter chip.

This *Electronics World* competition is sponsored by UK semiconductor manufacturer Zetex and distributor Farnell Electronics Components.


Beginners' corner

Balanced circuits

Balanced circuits play an important role in communications and in many other applications from audio to microwave frequencies. Ian Hickman explains why they are so widely used.

Balanced circuits have played an important part in communications, since before the days of 'electronics' as a recognisable branch of engineering. They continue to do so today.

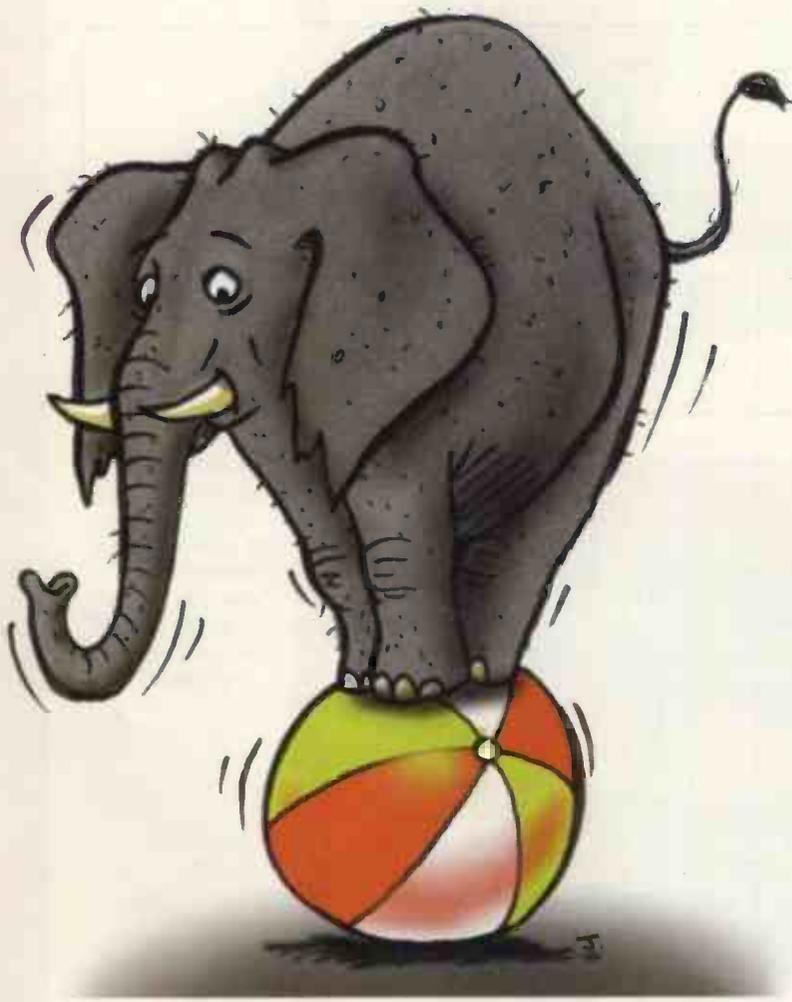Many circuits, such as a 75Ω coaxial television feeder cable for example, are unbalanced. That means that the signal is conveyed on one conductor, while the other remains at zero or ground potential – at least nominally.



Typically, unbalanced circuits are physically asymmetrical; in the case of coaxial cable, one conductor completely surrounds the other, hopefully screening it from any outside interference.

Balanced circuits, on the other hand, are both physically and electrically symmetrical. For audio-frequency signals, a typical arrangement consists of two wires side by side, spaced several inches apart.

Such wire pairs carrying telephone signals and supported on telegraph poles used to be a common sight alongside railway tracks. You can still see them in some rural areas of the country, and in many places throughout the world.

Depending on the gauge of the wire and the spacing, such circuits have a nominal characteristic impedance of 600Ω, 900Ω or 1200Ω. The latter two are more common abroad than in the United Kingdom.

If you were to climb a telegraph pole with a portable battery-operated oscilloscope, and view the signal on one wire with a high impedance probe, you would find it looked much the same as the signal on the other. But if you viewed them both at once, using a dual channel scope, you would see that the signal on one wire was the same as on the other, but inverted.

The telephone on the far end of the line responds to the voltage *difference* between the wires, i.e. the voltage on one with respect to the other. Any interference induced in the wires will produce the same voltage with respect to ground, on both lines. Such interference might be caused by electrostatic or electromagnetic coupling between the pair of wires and an overhead power transmission line for example.

In UK telephone engineers' parlance, this type of signal is called a 'longitudinal voltage'. In the US, it would be referred to as a 'voltage to ground'. It is also called a common-mode or 'push-push' signal.

The differential voltage – the voltage on one wire with respect to the other – is called the 'transverse' or 'metallic' signal by UK or US telephone engineers, or the normal-mode or push-pull voltage.

Although the circuitry within a telephone handset is not itself balanced, it responds to the transverse voltage while largely ignoring any longitudinal voltage. This is because it is 'floating', i.e. no part of it is ground referenced.

The handset also of course has to transmit outgoing speech to the line – a function traditionally performed with the aid of a specially wound transformer or 'hybrid'.

Nowadays, an electronic hybrid avoids the use of a costly, bulky wound component; various circuit arrangements can be used, such as those in reference 1.

Balanced circuits abound

That basic building block of analogue electronics, the op-amp, is equipped with a balanced floating input. This means that the output voltage should depend only upon the voltage of one input with respect to the other, regardless of whether their average potential is 0V or some other value.

Manufacturers' data sheets always quote the degree of balance or 'common-mode rejection ratio', which is frequently shortened to CMRR.

For example, the popular and long established TL081 op-amp typically provides a CMRR of 86dB, with a minimum of 70dB for the commercial TL081C, 75dB minimum for premium types. The differential input voltage amplification of the device is 200V/mV typical - 25V/mV or 50V/mV minimum, depending on version.

The typical figure corresponds to 106dB and the common-mode input voltage amplification should therefore typically be 86dB less than this, or just 20dB. In principle, you could measure the common-mode gain using the circuit of Figure 1a). With no negative feedback around the op-amp though, the offset voltage adjustment needed to set the mean output voltage level to 0V ground would be very critical.

There is a way around this problem. Instead of returning the wiper of the offset adjustment potentiometer via 1.5kΩ to the negative rail, it can be returned through a high resistance to the op-amp's output, although this back door negative feedback will of course affect the gain. I once used this scheme to make a CA3130 provide a very high impedance balanced floating input, for use as the null detector in an AC bridge.

In practice, an op-amp is always used with negative feedback applied, to define the gain to the desired value. Figure 1b) shows inverting and non-inverting amplifiers, each with an unbalanced input.

Although the input terminals themselves provide a balanced input, applying negative feedback causes unbalanced operation. Balance can be restored by a modification to the circuit, shown in Fig. 2. Here, the device inputs connect to a bridge of resistors, providing a balanced input and a gain of 20dB, if $R_2 = 10 \times R_1$.

If a common mode input of say +1V is applied, the non-inverting input rises to $10 \div 11 = 0.909V$. If the output stays at zero volts, the inverting input will rise to the same voltage, provided that the resistor values are accurate. Thus there is no change in the differential input voltage. Hence, due to the device's common-mode rejection, there is no change in output voltage.

But while the Fig. 2 circuit provides a balanced input, i.e. one with common-mode rejection, it is not ideal. In the case of the TL081, the op-amp's input pins are virtual open circuits, each looking like a resistance of $10^{12}\Omega$. So assuming that R_1 is 10kΩ and R_2 is 100kΩ, the circuit's input resistance at the non-inverting input terminal is just 110kΩ.

However, if you work it out for the inverting input, you will find that with a balanced input signal, it comes to 5.238kΩ. Thus the circuit will unbalance the output of a balanced source with a finite output resistance. This could be a problem when making 'bridging' measurements, i.e. tapping across a line in service.

Of course if the source were truly floating, there would not be a problem, but then a truly floating source could equally well use either of the Figure 1b) circuits.

There are several ways round this. For example, the LT1193 high slew-rate video difference amplifier from Linear Technology features two identical parallel input stages. These have closely defined gain, and both of them control the output. Thus one pair of input terminals can be used to set the gain, leaving the other pair floating free².

Alternatively, three op-amps can be harnessed together to provide an 'instrumentation amplifier', as in Fig. 3a). This provides a very high input impedance at both input terminals, converting the signal to an unbalanced output.

Note that the two input op-amps provide no common-mode rejection. It is all obtained from the second stage. This has the same configuration as Fig. 2, and as noted above, it

has an unbalanced input resistance. But it is driven from the output impedance of the first stage, which is near zero due to the negative feedback around the input op-amps.

The arrangement is so useful that the three op-amps together with their various resistors are available from most semiconductor manufacturers, integrated into a single IC. A typical example is the AD624 from Analog Devices, providing pin-programmable gains from $\times 1$ to $\times 1000$, a gain bandwidth product of 25MHz, low noise, high linearity and low input-offset voltage. In addition, its CMRR is 130dB minimum at gains of $\times 500$ or above.

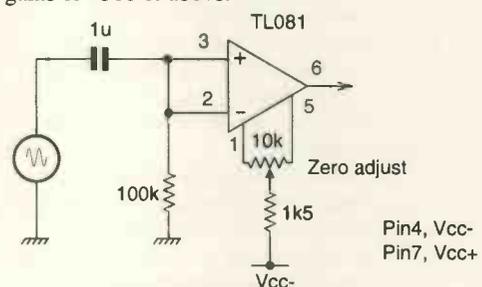


Fig. 1a). Illustrating common-mode rejection. Applying an identical signal to both inputs of an ideal op-amp would result in zero output.


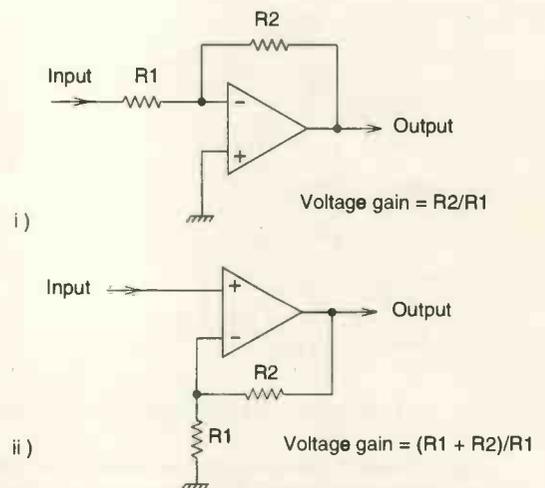


Fig. 1b). Adding negative feedback to define the gain accurately converts the op-amp to an unbalanced input circuit, either inverting with an input resistance R_1 (i), or non-inverting with a high input resistance (ii).

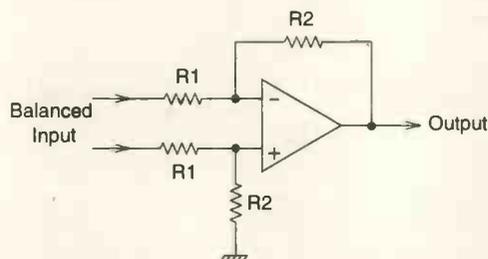

Voltage gain = R_2/R_1 = unbalanced output voltage / balanced input voltage

Fig. 2. This circuit provides a balanced input and converts the signal to a single-ended output.

An alternative circuit arrangement can provide the floating high input impedance of an instrumentation amplifier with just two op-amps, Fig. 3b).

Applications for balanced circuits

Balanced circuits are widely used. A common example is the 300Ω balanced feeder often used for the run between a dipole antenna and a VHF broadcast receiver. Any interference picked up on the feeder is a common-mode signal, which is ignored by the balanced floating input of the receiver.

At much lower frequencies, instrumentation amplifiers are used in situations where it is required to accurately record or process small signals that may be contaminated with much larger unwanted common mode voltages.

Many instances occur in manufacturing process-control, with sensors measuring strain, temperature, pH, etc. At one time I was involved with measuring the performance of telephone transmission circuits. I have already mentioned 600Ω balanced open wire lines, but many a

subscriber's 'local loop', or connection to their local exchange, is via a multi-cored twisted-pair cable for most of its length. Such twisted pairs have a lower characteristic impedance than open-wire lines. Values of 135Ω, 140Ω (standard in UK) and 150Ω are common.

On both types of line, quite large longitudinal voltages may be experienced from time to time, so telephone transmission test equipment is designed to be very well balanced. This applies particularly to a psophometer, which must meet the stringent requirements laid down in the relevant CCITT specification.

A psophometer is an instrument for measuring the perceived level of noise on a telephone circuit, using a true rms meter circuit. It includes a 'telephone weighting filter' (CCITT Rec. P53, 1970), which takes into account the variation of efficiency of a telephone earpiece with frequency, and the acuity of the ear likewise.

A 'broadcast filter' is also supplied for use on the higher bandwidth lines working at 50Hz to 15kHz. These are provided for linking studios. The filter also has a 'flat' position.

The CCITT-specified degree of

balance or rejection of longitudinal (common-mode) signals is not a unique figure, but varies according to the frequency. At 50Hz, the requirement is that when 200V rms is applied between the instrument's input and its case, the reading shall not exceed 100µV, i.e. a CMRR of 126dB. For this test, the two input terminals are strapped together.

In an instrument I designed, subsequently bought in quantity by the then GPO, roughly half the required rejection was obtained in an input transformer with a balanced floating primary. The other half was obtained from a modified version of the circuit in Fig. 2.

For signal level adjustments and measurement purposes, balanced systems need balanced attenuators. Figure 4a) shows a switched 0 or 60dB balanced 600Ω attenuator stage. Together with a bridged balanced-tee 0-50dB stage with 10dB steps and a similar 0-1dB stage with 1dB steps, it was used in another GPO contract, for a balanced attenuator covering 0-121dB in 1dB steps.

The original specification demanded a very high degree of balance – 60dB – at any attenuation setting up to the maximum, over the audio band. This was tested by applying an input between the input terminals, which were strapped together, and the case. The output was measured at various frequencies with a balanced instrument, such as a psophometer.

With careful design, the required performance can be met at low and medium values of attenuation. But if the measuring instrument's input is balanced floating, whether 'bridging' (high impedance) or 'terminating' (600Ω), the attenuator in Fig. 4a) provides no attenuation of the longitudinal signal. So one is in effect measuring the balance of the measuring instrument, rather than that of the attenuator.

The situation is little changed if the measuring instrument's input is bridging, centre tapped to ground. It is rather better if the measuring instrument's input is also set to terminating. Thus at the maximum attenuation, the degree of balance demanded could be around 180dB – which is clearly impracticable.

So the customer agreed to change the specification, and the pad was redesigned as a balanced-tee pad, with a centre tap brought out to a terminal on the front panel, Fig. 4b).

When using high attenuations of 60dB and above, the pad centre tap could be earthed, making the attenuation of longitudinal components equal


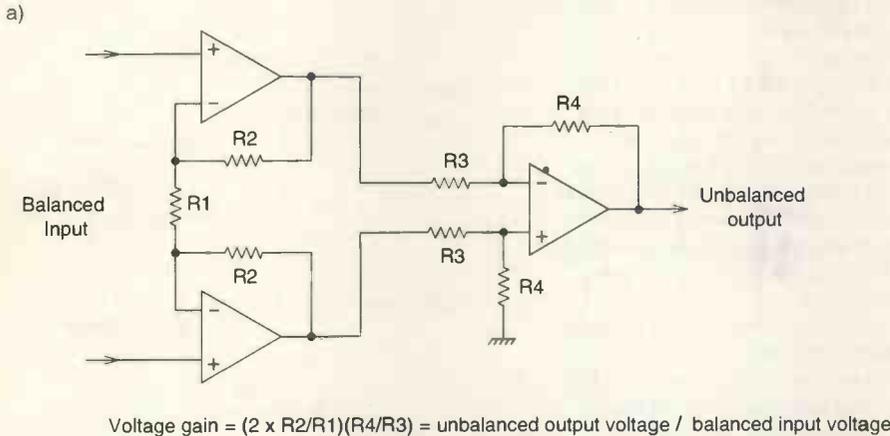


Fig. 3. Circuit a) provides a high impedance balanced floating input and converts the signal to a single-ended output. Fig. 3b) is similar to a) but uses only two op-amps.

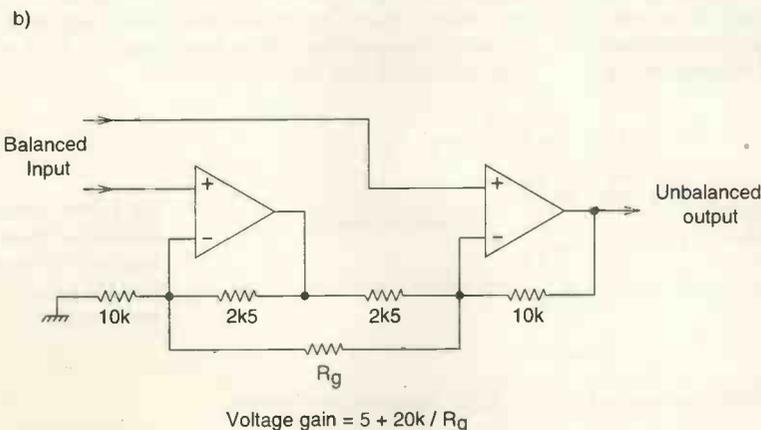

to that of transverse. Evidently, when considering a balanced transmission system, it is necessary to know if the receive end is floating or centre-tapped to ground, and whether terminated or bridging.

Balanced circuits are also used on printed circuit boards, where very high frequency emitter-coupled logic (ECL) signals must be routed from one place to another without corruption by cross-talk, etc.

Rise times of the signals concerned are of the order of a nanosecond, so correspondingly fast test signals are required. Testing of unbalanced transmission lines for data is usually carried out using time domain reflectometer (TDR) measurements.

A voltage step with a very short rise time is applied to the input of the line from a matched generator. The line input voltage is monitored by a sampling oscilloscope, and if the line is good, and correctly terminated in its characteristic impedance, 50Ω say, then the step is undistorted. But if the line is short circuited, the input voltage will collapse again to zero after a time equal to the round trip time from the input to the short and back again.

Similarly, any impedance variations at any point along the line will cause a reflection of some magnitude and sign. A measurement of the time between the step and the returned echo gives the distance to the fault.

For such measurements on a balanced line, two step generators and line input voltage monitors are necessary, one for each line. The Tektronix 11801C oscilloscope, with option SD-24, is designed for just this purpose.

With one step positive-going and the other negative-going, the performance of the balanced line as such can be determined. The effective rise time of the instrument, taking into account the rise time of the step and the rise time of the line voltage monitor section, is 35ps or less.

Further tests are possible – and desirable – given that any induced crosstalk may be a common mode component. So there is provision to reverse the polarity of the negative-going step. With both steps positive-going, the characteristics of the line to ground, as an unbalanced system can be investigated, as can its response to common-mode signals. ■

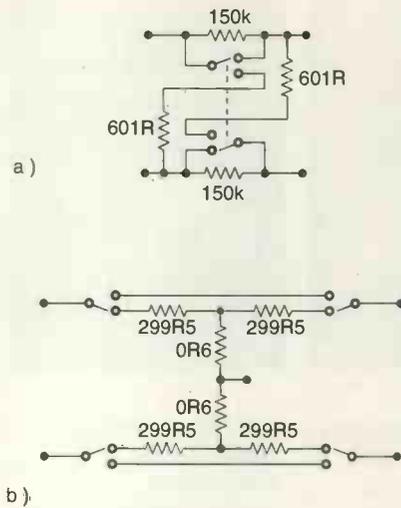


Fig. 4a). A switched 0 or 60dB 600Ω balanced π or 'box' attenuator pad. In Fig. 4b), the balanced tee or 'H' version is provided with an optionally grounded centre tap.

References

1. Hickman, Ian, 'Phantom data', *Electronics World*, August 1998 pp. 650-655.
2. Hickman, Ian, 'Four op-amp inputs are better than two,' *Electronics World*, May 1992 pp. 399-401.

How to order
(PC Interfacing and data acquisition)

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

PC Interfacing and data acquisition

A practical guide to programming for data acquisition and measurement - must-have info in just the right amount of depth for engineers who are not programming specialists. This book offers a complete guide to the programming and interfacing techniques involved in data collection and the subsequent measurement and control systems using an IBM compatible PC. It is an essential guide for electronics engineers and technicians involved in measurement and instrumentation, DA&C programmers and students aiming to gain a working knowledge of the industrial applications of computer interfacing.

Contents: Preface; The PC as a platform for data acquisition; Software considerations; Sensors and interfacing; Sampling, noise and filtering; The interrupt system; Data transfer; Parallel busses; Serial communications; Scaling and linearisation; Basic control techniques; Example projects; Appendix A: Adaptor installation reference; Appendix B: Character codes; Appendix C: References; Index.


Readership: Electronic engineers/technicians using PCs for measurement and instrumentation applications (process control, testing, etc.) Data acquisition and control programmers in industry. PC interfacing - university and advanced hobbyist projects.

Post your order to:- Jackie Lowe, Room 514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS
Or Fax 020 8652 8111



Price: UK £32.00 Europe £33.50
ROW £35.00

BOOKS TO BUY

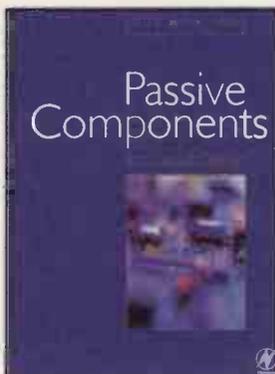


PASSIVE COMPONENTS FOR CIRCUIT DESIGN

Passive Components for Circuit Design is a unique introduction to this key area of analog electronics designed for technician engineers and anyone involved in circuit design. The coverage encompasses all component types capable of power amplification: resistors, capacitors, transformers, solenoids, motors and transducers. The behaviour of the components is explored along with the different types available and the principles of circuit design. Tolerances, stability, variation with temperature, reliability and manufacturing standards are all covered. Reading this book will improve your skills in component selection and analog circuit design. These are essential skills not only for the analog designer, but for all circuit designers, professional or amateur.

Contents: Preface; Fundamentals; Fixed resistors; Variable resistors, potentiometers and diodes; Capacitors; Inductors and inductive components; Inductive devices; Transducing components; SMT; Hardware; Index

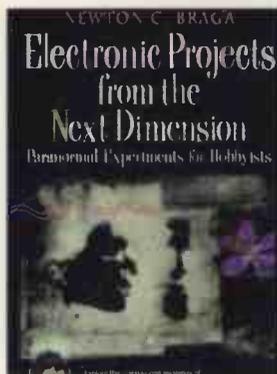Readership: Technician engineers, circuit designers, advanced hobbyists
 Pages: 304pp
Price: UK £22.00
Europe £24.00
ROW £26.00




ELECTRONIC PROJECTS FROM THE NEXT DIMENSION

For years paranormal scientists have explored the detection and documentation of spirits, auras, ESP, hypnosis, and many more phenomena through electronics. Electronic Projects from the Next Dimension provides useful information on building practical circuits and projects, and applying the knowledge to unique experiments in the paranormal field. The author writes about dozens of inexpensive projects to help electronics hobbyists search for and document their own answers about instrumental transcommunication (ITC), the electronic voice phenomenon (EVP), and paranormal experiments involving ESP, auras, and Kirlian photography.

Although paranormal studies are considered esoteric, Electronic Projects from the Next Dimension teaches the technical skills needed to make devices that can be used in many different kinds of experiments. Each section indicates how the circuit can be used in paranormal experiments with suggestions about procedures and how to analyze the results.

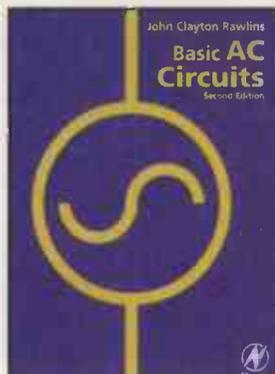Contents: White noise generators for use in instrumental transcommunication (ITC) and electronic voice phenomenon (EVP) experiments; Practical circuits for image experimentation, such as a



BASIC AC CIRCUITS

This is the step-by-step approach for beginners. This self-paced individualized learning tool covers concepts, terms, and the mathematics required to understand AC circuit problems. It has been designed to improve analysis techniques for prediction and control development.

Readership: Beginners meeting AC circuits for the first time; students; technicians
 Pages: 921pp
Price: UK £27.00
Europe £29.00
ROW £31.00

wireless sparkling image generator, horizontal bar generator, brontophic sound, magnetic field generator, high-voltage generators (Kirlian Machine's I & II); Paranormal skills experiments with temperature change, polygraph, electro-shock, random number generation, UFO detection, and ghost-finding.

Readership: Hobbyists, Electronics Enthusiasts
 Pages: 256pp
Price: UK £22.00
Europe £24.00
ROW £26.00

Post your completed order form to:-
 Jackie Lowe, Room L514, Quadrant House,
 The Quadrant, Sutton, Surrey, SM2 5AS

Fax your order form to 020 8652 8111

How to order

Book Title _____

I enclose a cheque/bank draft for £ _____
 (payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____

Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____

Tel: _____

from
£60 (inc)
 Shareware Version
 Download & Order Online!

PROTEUS VSM

Virtual System Modelling


Build It In Cyberspace

www.labcenter.co.uk

CIRCLE NO. 113 ON REPLY CARD

*Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time.**

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.

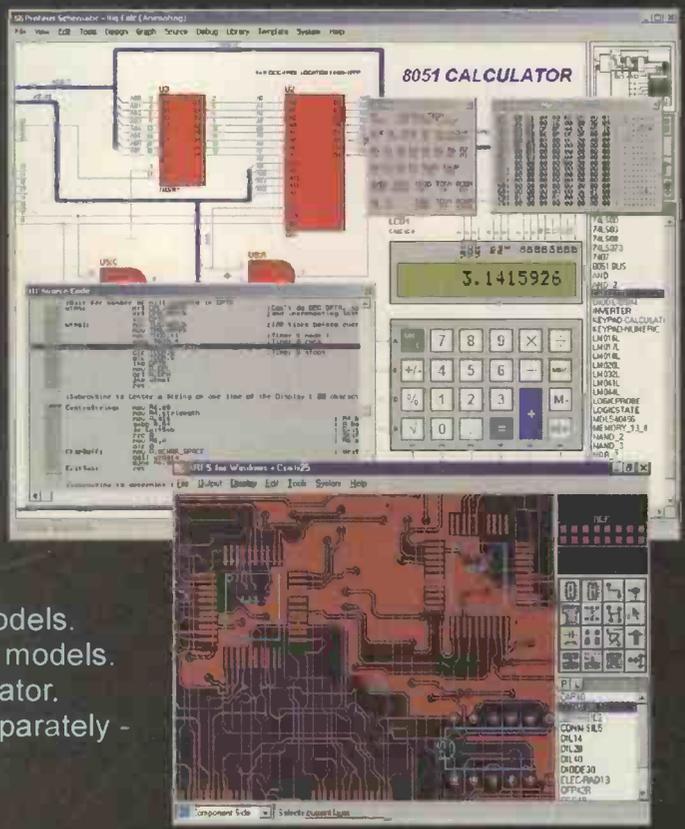

*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II.

Write, phone or fax for your free demo CD - or email info@labcenter.co.uk.
 Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

labcenter
 Electronics

Beautiful resistors

Les Green looks at the rarely discussed topic of the effects of stress in planar resistors, and he explains how to reduce it.

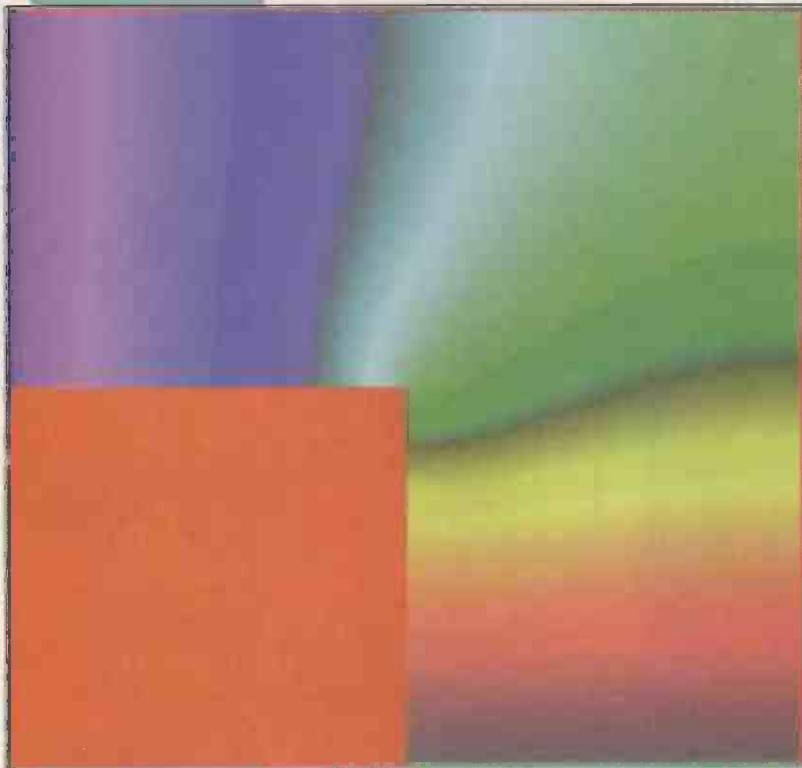


Fig. 1. Equipotential plot of a square-corner turn. Orange is insulator. The blue and green lines, left and bottom respectively, are electrodes.

*Technically, thick film usually refers to a screen-printed resistor, while thin film refers to a vacuum deposited resistor. Here I mean 'thin' in the usual English sense, rather than the specialist sense.

You may never get the chance to design your own custom resistor network. In fact you may not think there is anything interesting involved in resistor design, but every electronics designer should be able to appreciate the beauty of a well designed resistor.

The subject of resistor design is seldom taught in electronics courses, possibly because most of the techniques are computer based rather than mathematically biased. In fact it is the development of computer graphics which has really made the subject come alive.

A brief history

Early electrical research was not restricted to one or two experimenters; a great many researchers contributed along the way. The short list of discoveries shown in the panel fits the history of resistance into its proper historical perspective.

Resistors were originally coils of thin wire. As this construction method is bulky and expensive, it is now only used on laboratory standard resistors and power wire-wound resistors.

For some time, ordinary resistors were made of a mixture of carbon and insulating binding material, forming the 'carbon composition' construction. These were horribly unstable, noisy and inaccurate by modern standards.

The modern form of resistors is always a thin film*

Resistance-related discoveries

1785 **Coulomb**, discovered that electric charges exert forces on each other.

1800 **Volta**, invented the primary battery.

1820 **Oersted**, discovered that an electric current deflected a magnetic compass needle.

1820 **Ampère**, discovered that electric currents exert forces on each other.

1826 **Ohm**, identified the relationship between electric current, potential difference and resistance

1831 **Faraday**, discovered electromagnetic induction.

1845 **Kirchhoff**, formulated the basic laws of electrical networks.

of conducting material on an insulating substrate; either in tubular form or as a flat film (planar). It is this planar form that is the chief target of this article.

Rectangular film resistance

The resistance, R , of a block of conductive material is given by the formula:

$$R = \frac{\rho \times L}{T \times W}$$

Here, L is the length, T is the thickness, W is the width and ρ is the resistivity. Since R has units of ohms, it should be clear that the units of ρ are $\Omega \times \text{metre}$, often written as $\Omega \cdot \text{m}$.

For a thin film it is convenient to consider a new formula, where the resistivity and the thickness are combined into one term:

$$R = R_{sq} \times \frac{L}{W}$$

It is evident that if the length of the film and the width of the film are equal, forming a square of resistive material, the resistance is a constant value of R_{sq} . This is therefore known as the 'ohm per square', or Ω/sq for short, which is more formally called the sheet resistivity. It is not ohms per square metre or ohms per square foot; it is just ohms per geometric square.

This resistive film may be screen printed ('thick film') or vacuum deposited ('thin film'), but its primary characteristic is its Ω/sq . To make a resistor of a particular value, the aspect ratio, i.e. the ratio of the length to the width, is designed along with the Ω/sq parameter. Thus resistors are made short and fat, or long and thin, according to whether the desired resistance is greater or lesser than the Ω/sq for that film.

Resistor shape options

There is obviously a problem with high value resistors in relatively low resistance films; you need lots of squares in series. Therefore you either have to have a long resistor or a very thin resistor.

Given that the width of the resistor is governed by the manufacturing tolerances, there is obviously a limit as to how narrow you can make the resistive path. In order to make a long path in a small size, there is a need to go around corners.

Our nice simple formula now falls to pieces in the face of this geometrically simple rectangular corner. We have gone from simple geometry to a two-dimensional field pattern.

The resistance is no longer calculable without advanced mathematical formulae. We now enter the domain of finite element analysis by computer.

In Fig. 1, the orange area represents insulator. The blue line on the left is one electrode and the other electrode is below the bottom of the plot. This equipotential field plot clearly shows how the current flows around the corner. This shape has a resistance of 2.57 squares. In other words, if the sheet resistivity were $100\Omega/\text{sq}$, the resistance would be 257Ω .

By inspection we could have known that the resistance would be somewhere between 2 and 3 squares. Getting a more accurate answer would not have been possible without some sort of field plot. In fact manually produced field plots have been used for at least 100 years, as they

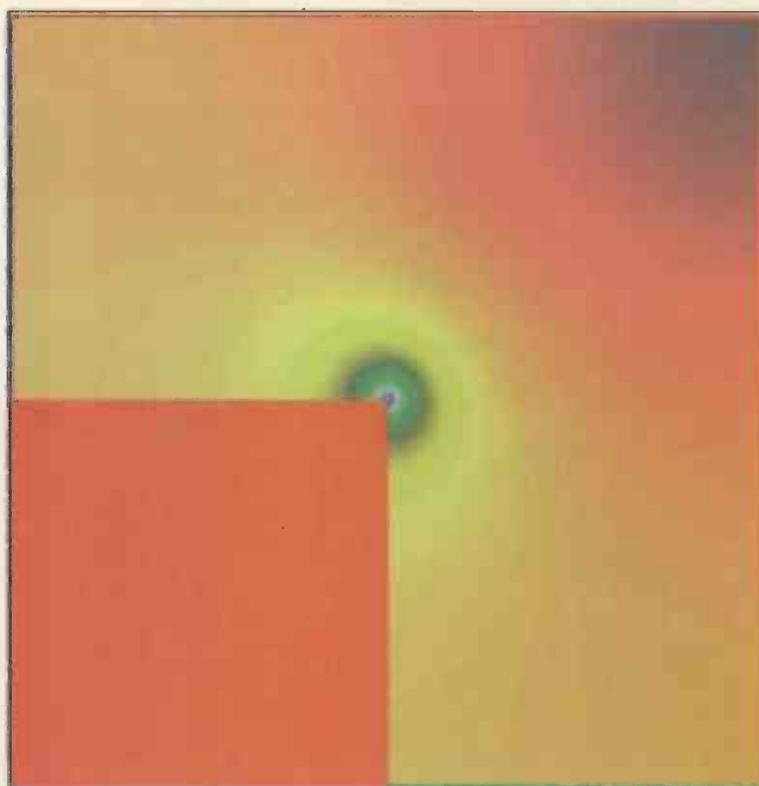


Fig. 2. Gradient field plot of the square corner turn.

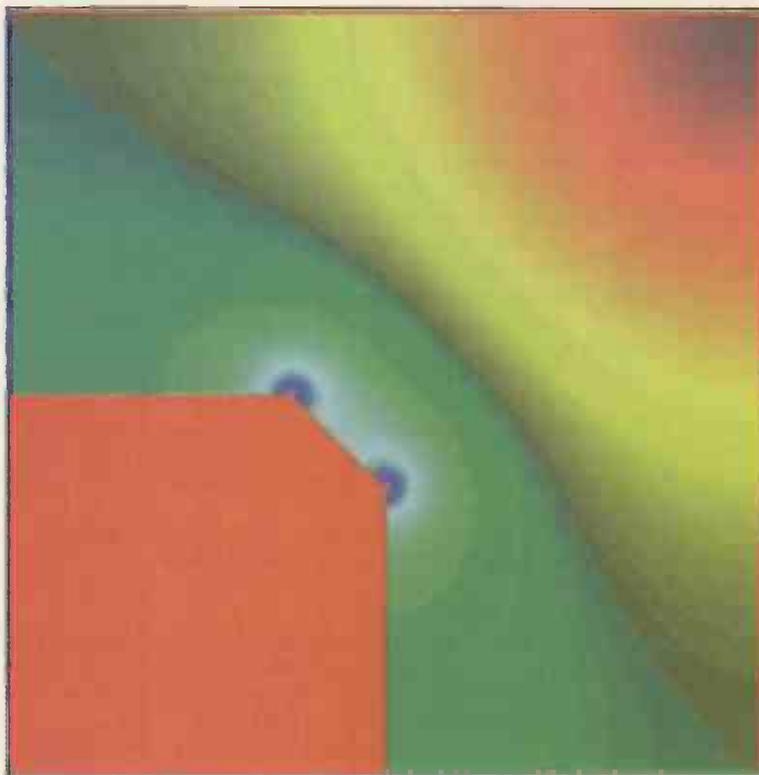


Fig. 3. Gradient plot of a bevelled corner turn.

appear in Maxwell's treatise¹.

Another way of looking at the field plot is in terms of the electric field intensity. This is the voltage gradient within the resistive film and represents electric stress on the film.

You can see from Fig. 2 that there is a lot of stress at the corner. On this simulation the electric field is around 38 units near the electrodes, but rises to 175 units at the corner.

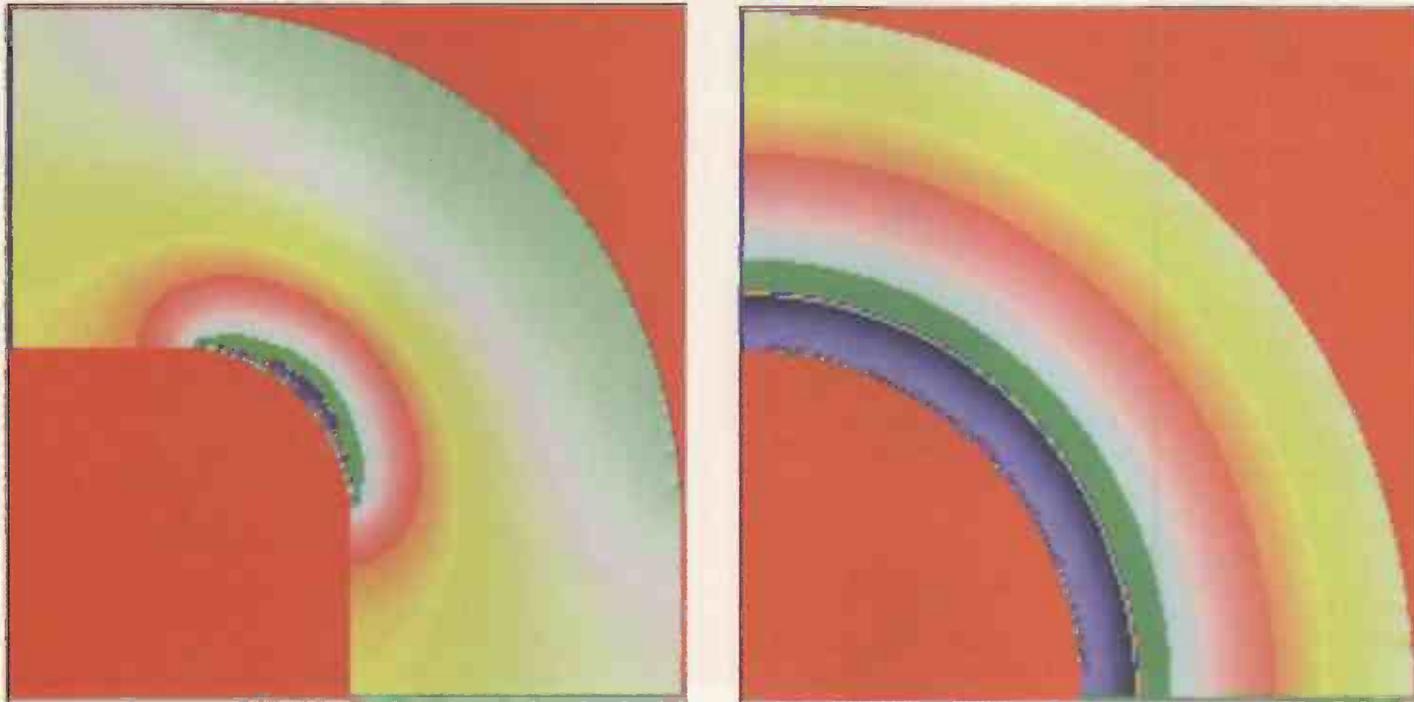


Fig. 4. Plot a) is the gradient of a half-width inner radius turn. In b) is a gradient plot of a full-width inner radius turn and in c) a gradient plot of the new style improved corner turn.

The current is taking a 'short-cut' around the corner and bunching up. This high stress point is a weakness in the design, as it will be damaged by over-voltage events more readily.

You should also realise that the power dissipated in a small element is proportional to the square of the voltage across it. Thus an element that has 5 times the electric stress across it, will actually be generating 25 times the heat. This is not a good way of making a stable resistor!

These points of stress also have a disproportionately large effect on the overall resistance compared to the rest of the pattern. This is another factor limiting the long term stability of the resistor.

The resistor is the wrong shape for accuracy and stability. What is needed is a smoother transition. Just bevelling the inside corner slightly has a useful effect, Fig. 3. The resistance has reduced to 2.4 squares, but the peak stress has reduced to 106 units at the corners, with 40 units near the conductors.

The other point about having stress in the resistive film is that current noise (1/f noise) is increased².

Stress ratio

The ratio of the peak electric field strength to some sort of average field strength is obviously important. Up to this point I have been using a fairly imprecise measure, as the field around the electrodes is not constant. What is desirable is a more definitive measure with which to make quantitative comparisons between resistor shapes.

$$\text{Stress ratio} = \frac{\text{Peak electric field strength}}{\text{Mean active field strength}}$$

The term 'mean active field strength' needs defining and explaining. If an extra resistive area is added on to any field pattern, it is possible that there will be little or no voltage gradient in that area. In this sense the area is inactive.

If we average this new area in with all the rest, the stress

ratio would get worse although the resistor would not actually be under any more stress. The inactive area would have skewed the stress ratio and given a misleading result.

A simple way to overcome this problem is to define an active area as one where the voltage gradient is greater than 5% of the peak gradient. The inactive areas are then neglected when calculating the mean electric field strength and the stress ratio.

Using this new measure the 'square corner turn' has a stress ratio of 4.94. The bevelled corner turn has a stress ratio of 2.99. This is a considerable improvement for little effort.

A radius on the inside corner of half the resistor width, with the outer radius $1\frac{1}{2}$ widths, both on the same centre, reduces the stress ratio to 2.05, Fig. 4a).

Increasing the inner radius to equal the resistor width, and making the outer radius double the resistor width, gives a slight improvement to a stress ratio of 1.71, Fig. 4b).

There is a law of diminishing returns here. The best possible stress ratio is of course 1. The half-width-radius bend achieves a stress ratio of 2.05 with a resistance of 2.515 squares. The full width radius gives a stress ratio of 1.71 and a resistance of 2.323.

We want a maximum amount of resistance in a given space, but without putting the resistor under too much stress.

An interesting compromise is to deliberately make the short-cut around the corner less 'attractive' to the current flow. By pushing the inner corner out into the flow, the path length, and therefore the path resistance, is increased, Fig. 4c).

This new shape has a stress ratio of 1.9 and a resistance of 2.87 squares. As it gives more resistance with less stress in the same space, it is undeniably preferable to the half-radius bend.


No hard and fast rule can be made about what stress ratio is acceptable for a resistor in general, because the design

environment and required specification for the resistor have not been stated. If pushed, I would say that a stress ratio of above 3 would give a poor resistor and that a stress ratio below 2 is desirable.

So far in this article, a quantitative measure of the stress in a resistive pattern has been presented. This then gives a quantitative way of saying which is a good pattern and which is a bad pattern.

In a second article on this topic, I will be discussing the subject of trimming. This is vitally important because poor trimming causes increased stress and therefore worse stability. The amount of trimming necessary on a thick film resistor is around $\pm 19\%$ so the subject is not trivial.

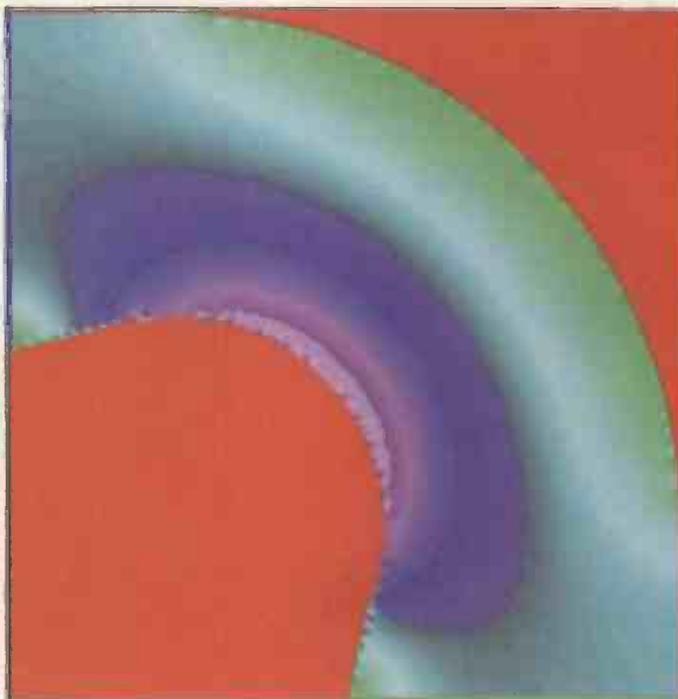The reason why this is important to the non-specialist is that because of the large trimming range, one batch of resistors can work whilst the next batch can be utterly useless. This is of considerable importance to any designer! ■



References

1. Maxwell, J.C., 'A Treatise on Electricity & Magnetism', Volume 2, 3rd edition 1891. (1954 reprint.)
2. Yoshida, H, 'The Effect of Resistor Geometry on Current Noise', IEEE Transactions on Components, Hybrids and Manufacturing Technology: Vol. 16, No 3; May 1993, pp. 344-349.

How to pay

(VCR Fault Finding Guide) paperback

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____

Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

Television magazine's VCR Clinic column is a unique forum for practical servicing tips, with the UK's leading service engineers and servicing writers contributing their observations and recommendations month by month. But try finding those faults reports for the Amstrad XYZ123 that's on your bench. Even with an index you will be chasing through a pile of magazines... until now. Peter Marlow's VCR Fault Finding Guide is a distillation of the most used fault reports from 11 years of Television magazine. Arranged by make and model the information is extremely easy to access, and the book is a convenient size for the bench or to carry with you. This will undoubtedly become one of the service engineer's most useful tools. Unlike other fault guides, this one is based on top quality information from leading authorities, and genuine repair case studies. This is real-life servicing information, not just a compilation of manufacturers' manuals.

Approximately 2,000 reports on 193 models from 35 different manufacturers. Instant on-the-spot diagnosis and repair advice. Television magazine's leading writers' wit and wisdom available for the first time in book form

Post your completed order to:-

Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS




VCR Fault Finding Guide

Peter Marlow
This book is an essential repair tool, not just another volume for the shelf

Pages: 464pp

Price: £22.50

BOOK TO BUY

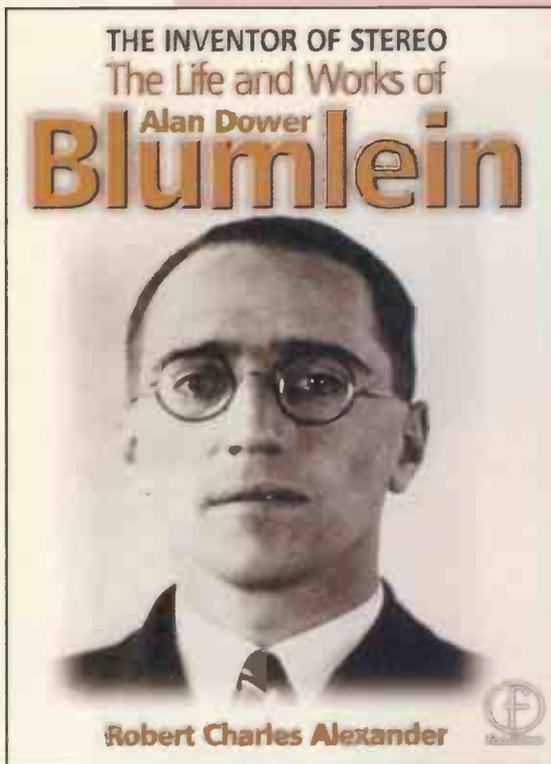

Post your completed order form to:-

Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS

Phone your credit card order: 020 8652 3614

Fax your completed order form to 020 8652 8111

UK Price: £17.50 Europe £20.00 ROW £22.00

Paperback price includes delivery

How to pay

(Blumlein) paperback

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____

Expirey Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

This book is the definitive study of the life and works of one of Britain's most important inventors who, due to a cruel set of circumstances, has all but been overlooked by history.

Alan Dower Blumlein led an extraordinary life in which his inventive output rate easily surpassed that of Edison, but whose early death during the darkest days of World War Two led to a shroud of secrecy which has covered his life and achievements ever since.

His 1931 Patent for a Binaural Recording System was so revolutionary that most of his contemporaries regarded it as more than 20 years ahead of its time. Even years after his death, the full magnitude of its detail had not been fully utilized. Among his 128 patents are the principal electronic circuits critical to the development of the world's first electronic television system. During his short working life, Blumlein produced patent after patent breaking entirely new ground in electronic and audio engineering.

During the Second World War, Alan Blumlein was deeply engaged in the very secret work of radar development and contributed enormously to the system eventually to become 'H2S' - blind-bombing radar. Tragically, during an experimental H2S flight in June 1942, the Halifax bomber in which Blumlein and several colleagues were flying, crashed and all aboard were killed. He was just days short of his thirty-ninth birthday.

For many years there have been rumours about a biography of Alan Blumlein, yet none has been forthcoming. This is the world's first study of a man whose achievements should rank among those of the greatest Britain has produced. This book provides detailed knowledge of every one of his patents and the process behind them, while giving an in-depth study of the life and times of this quite extraordinary man.

Contents


Earliest days
Telegraphy and telephony
The audio patents
Television
EMI and the Television Commission
The high- definition television period
From television to radar
The story of radar development
H2S - The coming of centimetric radar
The loss of Halifax V9977
Legacy
To Goodrich Castle and beyond

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Triple-output converter

With outputs of 3.3V at 6.2A and $\pm 12V$ at 530mA, this Elec & Eltek DC-to-DC converter is designed for telecom applications where a 3.3V DC feed is needed. Every output has over-voltage protection and the converter achieves 3.3V from 12V or 24V. With an input range of 40.5 to 60V DC this 34W unit features at least 80 per cent efficiency and operates without an additional heatsink over a temperature range of 0°C to 70°C. The specification includes 1kV DC isolation, and line and load regulation better than five per cent. Switching at

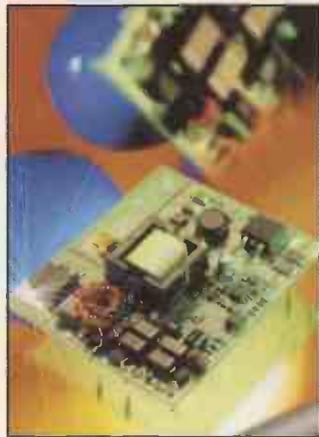

300kHz keeps dimensions down to 71 x 65mm with a height of 13mm and the footprint is compatible with industry standard models. The converter is designed to meet UL1950 and EN60950.

DT Electronics
Tel: 024 7643 7400
Web: www.dtelectronics.com

32Mbit synchronous SRAM in 119 BGA

White Electronic Designs is offering three 32Mbit synchronous SRAMs, the WED2ZL361MS-BC and the WED2ZL361MV-BC are 2.5V and 3.3V versions, respectively, of 1M x 36-bit NBL (no bus latency) synchronous SRAM. Each integrates two 1M x 18 SRAMs into a single 17mm x 23mm, 119 BGA package. The WED2ZL2365 12S-BC, also a 119 BGA, is a 2.5V version configured as two banks of 512K x 36. All three products are available in speed ranges from 100MHz to 166MHz, making them suitable for high-end networking applications such as Gigabit/Terabit Ethernet, ATM Switches, Add/Drop Multiplexers and Optical Switches. The NBL

Synchronous SRAMs are designed to sustain 100 per cent bus bandwidth by eliminating turnaround cycles when there is a transition from read to write, or *vice versa*. All inputs are synchronised to rising clock edges with the exception of output enable and linear burst order. Asynchronous inputs include sleep mode enable. Write cycles are internally self-timed and initiated by the rising edge of the clock input. This feature eliminates complex off-chip write pulse generation and provides increased timing flexibility for incoming signals. *White Electronic Designs*
Tel: 001 508 366 5151
Web: www.whitedc.com

SuperH processors run up to 200MHz

Hitachi has announced two microprocessors in the SuperH 32-bit Risc family, the SH7729R and SH7709S. Based on the SH3-DSP and SH-3 cores respectively, each device offers a high performance of 217/260Mips at operating frequencies of 167MHz/200MHz. The SH7709S achieves low power consumption with the SH-3 as



its CPU core, making it suitable for use in portable information devices such as hand-held PCs and PDAs. The SH7729R in particular, with its on-chip DSP, can handle high-speed processing of voice recorder and image data in portable information devices. This allows for the high-speed execution of middleware, for example VoIP, in products such as voice codecs. The SH7729R is also capable of simultaneously executing browser display and voice codec processing, for instance in Windows CE, which has been difficult with previous products. *Hitachi*
Tel: 01628 585163
Web: www.global.hitachi.com

Mobile phone driver IC generates 128 colours

Rohm has expanded its family of miniature LED driver ICs with a surface mount device that allows 128 different colours to be generated from a single tri-colour LED. Designed for portable, battery-powered applications such as mobile phones, the BU8770FV LED driver can be used to optimise LED colours dependent on certain operating conditions. The BU8770FV integrates an oscillator, a CPU interface block, a DC/DC converter for driving the LED and three PWM controllers for red, green and blue output respectively. The PWM circuitry allows the LED to generate up to 128 different colour shades. Device input is via a serial interface. Supplied in an SSOP 16-pin package with dimensions of 5 x 4.4 x 1.5mm, the device will operate from a 3.3V supply and incorporates a standby mode that minimises power consumption when driver operation is not required.

Rohm Electronics
Tel: 01908 282666



Please quote *Electronics World* when seeking further information

Single-cell lithium-ion battery charger IC

TelCom Semiconductor's first battery charger IC, the TC3827, is a controller designed to carry out safe and fast charging of a single lithium-ion cell. The device's accuracy is ± 1 per cent and shutdown current is $1\mu\text{A}$. With an overall system accuracy of 1 per cent, the company says this device ensures the cell capacity is fully utilised without life cycle degradation.

TelCom Semiconductor
Tel: 001 650 968 9241
Web: www.telcom-semi.com

Circular connectors are very small

Flint is offering Hirose's miniature circular connector range, the HR25 which provides up to 20 contacts in an outside diameter of 12.5mm. Designers have a choice of 4, 6, 8, 12, 16 or 20 contacts, and a variety of wiring options including crimp-



style and direct board mounting as well as soldered wiring types. The HR25 is available in screw-lock or push-type mating. Their construction ensures that pins cannot bend if the male pins are inserted incorrectly, even if the two pieces are engaged, safe positioning of male contacts prevents any possibility of collision, says the supplier. A combination of watertight coupling and gold-plated contacts comes as standard.

Flint
Tel: 01530 510 333
Web: www.flint.co.uk

200W modules output at 30, 40 and 50kV

Applied Kilovolts has introduced a range of 200W modules with output voltages of 30kV, 40kV & 50kV at 200W. The supplies use an energy recovery circuit to achieve high oscillator conversion efficiency and as a result are small in size for such high voltage power supplies, said the supplier. Operation is from 24V DC and uses a high frequency (50kHz) switch mode FET oscillator with the energy recovery circuits. All high voltage components are generously de-rated to give a design life of ten years or more and are vacuum encapsulated in silicone rubber. The modules are high stability with a load and line regulation of better than 0.1 per cent and a

temperature co-efficient of better than 300ppm/ $^{\circ}\text{C}$. Output ripple is better than one per cent peak to peak.

Applied Kilovolts
Tel: 01273 439440
www.appliedkilovolts.com

Vandal resistant keyboard is sensitive

Using high frequency touch sensitive technology, Sussex-based EAO has produced a rugged PC compatible 105-key keyboard. For Larger volume applications, touch sensitive keyboards or keypads may be customised to customers' specific needs regarding the number of keys, design, shape, colour and functionality. The keyboards are PCB based and designed to be used through a glass or polycarbonate front plate. This makes them completely sealed and resistant to chemical attack as well as vandal resistant and easy to clean.




They can also be operated using gloved hands. Available either as a stand-alone desktop unit, or a PCB version for mounting behind the customer front panel, the series 75 keyboard comprises an oscillator, a detection cell per key and an output signal processor. The keys are activated by dampening the oscillator's high frequency signal with a finger.

EAO
Tel: 01444 236000
www.eao-group.com

Hybrid IC switches varying loads

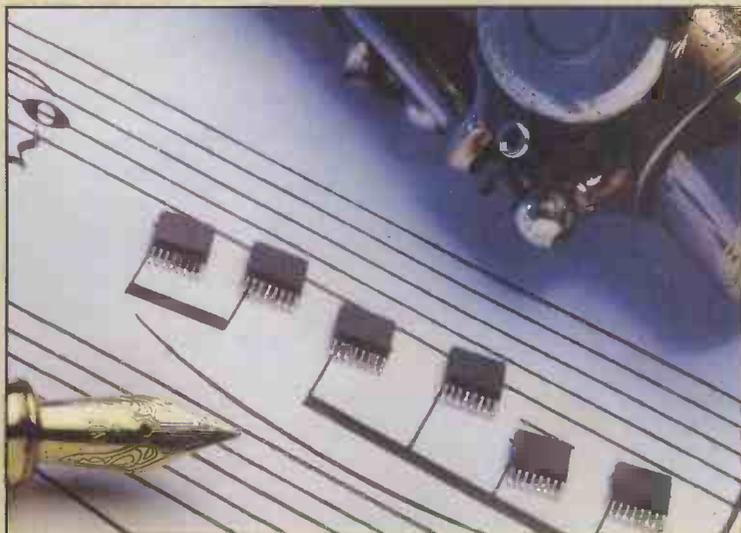The STR-G6551 is an off-line switching IC from Ultimate Renaissance which operates in 'fixed off-time' mode with a maximum frequency of 60kHz. The device features a 3.9Ω $R_{DS(on)}$ avalanche rated 650V, 158mJ FET and includes over voltage protection (OVP), under voltage lockout (UVLO) and



Class-D audio amplifier gives a virtuoso performance

Zetex has announced the first product in its Class-D audio amplifier family. The ZXCD1000 switching amplifier controller offers efficiency greater than 90 per cent, claims the supplier. This allows the amplifier to be offered in a compact package, and to generate much less heat than a comparable Class A/B linear amplifier - which would typically have an efficiency of around 65 per cent. It offers THD + N (total harmonic distortion and noise) of typically 0.2 per cent open loop, or typically less than 0.1 per cent with a 10dB feedback loop (measurements are taken at 90 per cent power, full band). Depending on the choice of output filter, the ZXCD1000 provides true high fidelity performance at an output of 25W or 50W and can drive either a 4 Ω or 8 Ω load, says the firm.

Zetex
Tel: 0161 622 4422
Web: www.zetex.com

Please quote *Electronics World* when seeking further information

thermal shutdown (TSD) circuitry. Available in a 5-pin isolated TO-220 package the STR-G6551 operates up to 60W on a European input voltage range and 30W on a world-wide input voltage range. Ambient operating temperature range is -20°C to $+125^{\circ}\text{C}$.

Ultimate Renaissance

Tel: 01793 439310

www.ur-home.com

SM LEDs protect against discharge

Lumex's latest family of surface mount technology LEDs are designed to offer protection from electrostatic discharge (ESD). Applications include right-angle panel or fault



indicators, where the light source is exposed to an end user. The SMF-HM1340XD-L series of LED indicators are available in right-angle or straight-up packaging. They can be equipped with any of the supplier's off-the-shelf lensed T-3mm (T-1) light emitting diodes. Typical choices include standard low-current ($I_f=2\text{mA}$) LEDs in red, green, yellow or amber, with blue and white also available. An ESD-safe lens snaps over the LED to complete the package. The base unit is designed as a mate-able unit.

Lumex

Tel: 001 800 278 5666

www.lumex.com

DC supplies range from 13.3 to 30kW

The Magna-Power SQ Series of DC supplies range from 13.3kW to 30kW. They are sold by Kingshill in the UK. Developed from the established PQ series, these current-fed units combine high and medium frequency power processing technologies to


Boundary scan controller supports compactpci/pxi

JTAG Technologies has extended its line of high-performance boundary-scan controllers with an addition to the JTAGTAPS family, the JT3710/PXI DataBlaster. The controller supports the CompactPCI/PXI format and its software structure is identical to the previous ISA, PCI, VXI and USB versions of the DataBlaster. The PXI-based controller offers 32-bit operation with data transfer speeds up to 25MHz. To accommodate the high data rates and lengthy vectors demanded by boundary-scan applications, such as flash memory In-System Programming, the JT3710/PXI uses a unique boundary scan implementation. This includes the firm's chipset for real-time data decompression, high-speed TAP (test access port) drivers and AutoWrite used to boost boundary-scan-based flash ISP performance. A high capacity memory is also incorporated onboard for local ISP data storage.

JTAG Technologies

Tel: 01234 272226

www.jtag.com

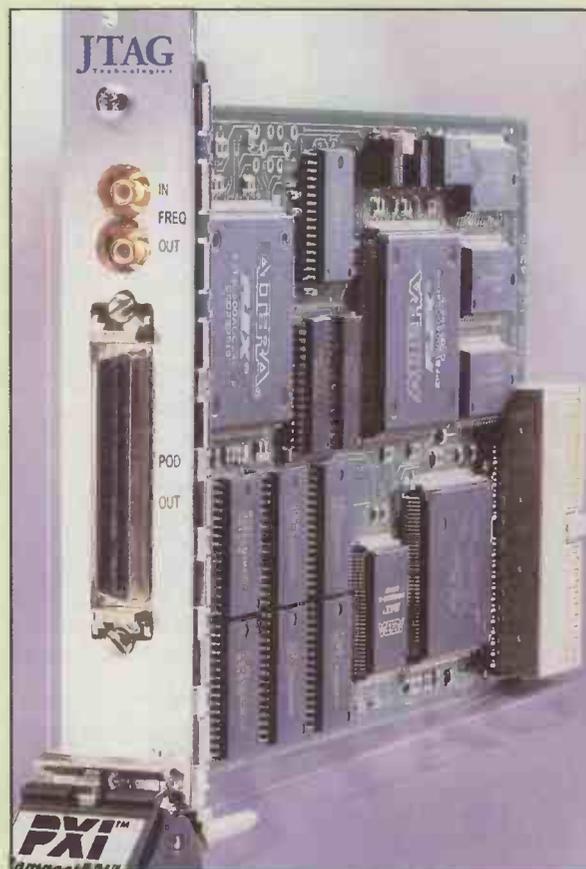

reduce package size. There are 50 models with outputs from 16-625V, DC, 21-1800A, DC. They are fully programmable through resistance, voltage, current or optional JEEE-488/R5232. Over-voltage and over-current are also programmable. Constant monitoring ensures shutdown if a line opens or a programmed input is exceeded. Units function as voltage or current sources, depending on control settings and load conditions. As a voltage source, if the load increases beyond the current command setting, the unit automatically crosses over to current mode. Diagnostics are embodied within the control loop, while proprietary circuitry identifies whether voltage, current or a fault condition has control. If the fault condition demands user intervention, mains power is disconnected and the diagnostic status latched into memory.

Kingshill

Tel: 01634 821200

www.kingshill.com

Adapter board connects CompactPCI supplies

Schroff's latest adapter board is a CompactPCI connection system using the power supply's M-connectors. It is intended to allow a user to carry out prototyping and small scale production work without having to manufacture an application specific backplane with integral power supply connections. It is based on a two layer intermediate board, which is used as an adapter between the power supplies and

the backplane of a 19in. subrack. Available in heights of 3U and 6U, these boards like the backplane itself can be mounted onto the rear horizontal rails. All signals including drive supply, sense line and current share bus signals are fed from the DIN-M24/8 connector of the CompactPCI by cable to the intermediate board and then to the backplane.

Schroff

Tel: 01442 240471

www.schroff.co.uk



Please quote *Electronics World* when seeking further information



Custom voltmeter for under £15

Lascar has launched a custom-scaled addition to its EM series of drill mountable panel meters - the EMV 1025S-XX. This new 3-wire, 3 1/2 digit LCD volt-meter has 'factory set' scaling. According to the supplier, the user orders a 10-wire evaluation unit, confirming preferred scaling and decimal point options. All subsequent meters ordered

in quantities over 50 pcs will be provided in the particular configuration chosen for only £14.94 per unit, says the firm. As with each of the modules in the EM Series, the EMV 1025S-XX is fitted with a threaded stud, mountable through a 5.5mm hole, is 43.5mm by 21.4mm in size and has a low profile finish of 5mm. *Lascar Electronics*
Tel: 01794 884616
www.lascarelectronics.com

1.4MHz buck converter offers 95% efficiency

Linear Technology's LTC3404, 1.4MHz current mode monolithic synchronous step-down DC/DC is capable of delivering up to 600mA of output current. The buck converter has an operating quiescent current for less than 1MHz operation of 10µA with

no load and less than 1µA in shutdown. Efficiency is rated at 95 per cent. *Linear Technology*
Tel: 01276 677676
www.linear.com

Comms modules for industrial PCs

Xycom Automation has extended its range of Industry Pack (IP) industrial PC communications modules. The module can be used on processor boards with IP sites, on XVME-9660 6U carrier cards (four per card) or XVME-9630 3U carrier cards (two per card). The XIP-4520 offers 8 channels of RS-232 communications with 64 bytes each of transmit and receive FIFO buffers and bit rate programmable up to 230kbit/s. *Xycom Automation*
Tel: 01604 790767
www.xycomautomation.com

32-bit configurable chip

Triscend has introduced a 32-bit configurable device which integrates an ARM7TDMI processor core with programmable logic, representing over 3000 flip-flops and 300 programmable I/O. The A7 configurable system-on-chip device includes a dedicated system bus with a transfer rate of 264Mbit/s and system features such as a four-channel DMA controller, an external memory interface unit, full power management utilities and JTAG debug interface. Additional peripherals include timers, UARTs, interrupt and watchdog. Alongside the ARM core is an SRAM-based configurable logic matrix with over 3000 flip-flops and 300 programmable I/O. The system interconnect bus combines 32-bit addressing with 32-bit data

The Distributor with 20,000 hard-to-find lines EX STOCK!!!

Semiconductors

We have one of the largest ranges of discrete parts in the UK, both new and obsolete types and, if we do not have it in stock, we can usually source it for you.

Call or fax for our latest Semiconductor stock list.

Computer products

We carry in stock everything to make a Personal Computer. CPUs - Memory - Motherboards - Cards - Scanners - Modems - Sound Cards - Speakers - All types of Drives - Cases - PSUs - Monitors etc

Components & equipment

Call or fax for our latest Semiconductor stock list.

Capacitors - Resistors - Connectors - Potentiometers - Cables - Batteries - Speakers - Amplifiers - Lamps - Microphones - Fans - Power supplies - Transformers - Buzzers - Sirens - Fuses and Holders - LEDs - LCDs - Relays - PA Systems - Tools - Test Equipment - etc

See our web site. Non-trade customers, send £9.80 to the sales office for a complete suite of catalogues.




Semiconductor Supplies International Ltd

Dawson House, 128 - 130 Carshalton Road, Sutton, Surrey, England, UK. SM1 4TW
020-8643 1126 (Sales and Technical Queries)
Fax: 020-8643 3937 (For International use +4420)
e-mail: sales@ssl-uk.com Web: ssl-uk.com

Clock generators for digital set-top boxes

AMI has introduced a family of single phase-lock loop (PLL) clock generator ICs that support a variety of platforms. Each device contains an on-chip voltage-controlled crystal oscillator (VCXO) that develops the PLL reference frequency when combined with a crystal resonator. The VCXO allows designers to adjust the timing in systems that have frequency matching requirements, such as digital satellite receivers. The AMI devices also feature a phase-locked loop (PLL) that drives one or more clock outputs. The clock outputs are phase- and frequency-locked to the VCXO reference frequency. This locking of the output frequencies to the reference tackles unpredictable artifacts in video systems and reduces electromagnetic interference (EMI) caused by harmonic frequency stacking. Individual device pin-outs vary, but all packaging features a small circuit board footprint to contribute to reduced end-product size. Both 3.3V and 5V versions are available.

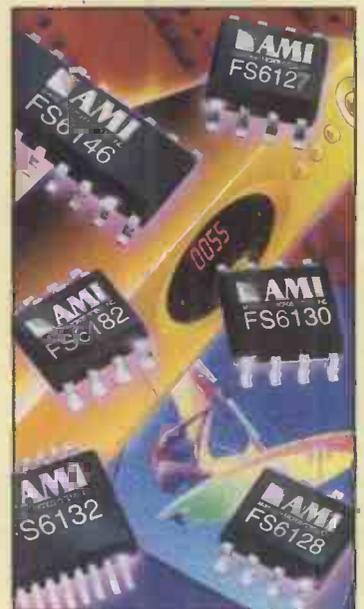

AMI
Tel: 000 49 351 530 331


Please quote *Electronics World* when seeking further information

carriage. The first device available, the TA7S20, offers 2048 configurable logic cells, 16K RAM and 251 programmable I/O. It is packaged in 128LQFP, 208QFP and 484BGA styles.

Triscend
Tel: 01628 681565
www.triscend.com

SM connector is metric

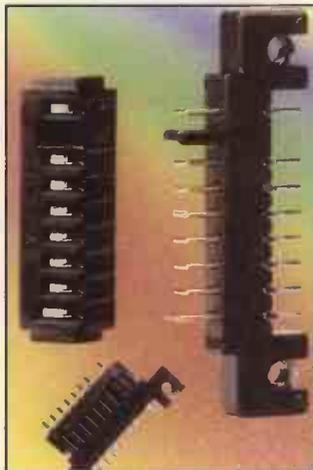The BP2 2mm contact pitch connector is an eight contact, surface mounting connector capable of handling up to 3A DC on two contacts and 0.5A on the remainder. The UL-rated insulator is high temperature and



the operating range of the connector is -55°C to +85°C. The sideways mounted copper alloy blade contacts can endure 5000 mating cycles and all are gold plated. When mated the connector provides a co-planar (end to end) style board mating. Packaging options include embossed tape or semi-hard tray for auto placement.
Robinson Nugent
Tel: 01227 794495
www.robinsonnugent.com

LED Indicators for low or mains voltage

Hero Electronics is stocking a range of 22mm LED Indicators from German manufacturer Signal Constructs. The range includes products suitable for 130 and 230V AC mains operation as well as 20-28V AC or DC operation. The indicators are sealed to meet IP67 standards, overall diameter of



Media platform in single pci slot

RadiSys' next generation family of Spirit-6000 media processing platforms is claimed to offer four-times the performance of its predecessor, the Spirit-6020, in a single PCI slot. Delivering up to 128 compressed voice or fax channels, the platform is intended for medium to high-end enterprise and media gateways including voice/fax over packet, CTI/IVR, audio conferencing, voice record and playback and other voice, fax and telephony signal processing applications. With the ability to packetise voice

and send the data over a LAN using on-board 10/100Base-T network interfaces, the board is both PCI and H.100 bus compliant. Each of the board's eight TI DSPs runs at an internal clock speed of 300MHz providing a total of 2400Mcycles/s per PCI slot. The system is available with a choice of voice coders and telephony algorithms.
RadiSys
Tel: 01793 411200
www.radisys.com



the lens is 30mm and mounting hole diameter is 22mm + 0.5mm. Designed for front panel mounting, the devices are secured with a circular fixing nut that is supplied along with an O-ring seal. A feature of the range is a 180° viewing angle. Five different LED colours are available as well as a bi-colour version. Luminous intensities range from 160 to 350mcd at 20mA operating current.
Hero Electronics
Tel: 01525 405015
www.heroelec.co.uk

In-circuit emulation support for STAR12

iSYSTEM has in-circuit emulation support for the Star12 micro controller family from Motorola. The system

supports the Star12's 25MHz bus clock (50MHz clock). Based on the firm's ActivePOD technology, a high-speed probe for real time in-circuit emulation was developed and tested with Motorola. It supports the 68HC9S12DP256 microcontroller with 256Kbyte of flash memory and can be used with all iC3000 and iC4000 systems. There is an adapter for Star12's 112-pin QFP package. The overlay RAM is on-board to provide the fast access times. The integrated trace buffer offers 16K x 160-bit capture at an upload speed of 100Msample/s. In addition to complete in-circuit emulation, iSYSTEM also provides serial debug (BDM - background debug mode) support for the STAR12 family.
iSYSTEM
Tel: 01280 700262
www.directinsight.co.uk

Emergency stop switch is foolproof

EAO's series 04 and 61 ranges of panel mounting switches now include a selection of emergency stop switches that have a foolproof actuation



method. The term foolproof means that the switch contacts cannot be accidentally operated without fully actuating the mushroom head. Available in both twist-to-release and key-to-release options, both series of emergency stop switches conform to the latest approvals and machinery directives and are environmentally protected to IP65. Available in both 16 and 22.5mm mounting dimensions and 27 and 37mm front dimensions.
EAO
Tel: 01444 236000
www.eao-group.com

TiePieScope HS801 PORTABLE MOST



ARBITRARY WAVEFORM GENERATOR-
STORAGE OSCILLOSCOPE-
SPECTRUM ANALYZER-
MULTIMETER-
TRANSIENT RECORDER-

Reliability

- The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (arbitrary waveform generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.
- The versatile software has a user-defined toolbar with which over 50 instrument settings quick and easy can be accessed. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.
- When a quick indication of the input signal is required, a simple click on the auto setup button will immediately give a good overview of the signal. The auto setup function ensures a proper setup of the time base, the trigger levels and the input sensitivities.
- The sophisticated cursor read outs have 21 possible read outs. Besides the usual read outs, like voltage and time, also quantities like rise time and frequency are displayed.
- Measured signals and instrument settings can be saved on disk. This enables the creation of a library of measured signals. Text balloons can be added to a signal, for special comments. The (colour) print outs can be supplied with three common text lines (e.g. company info) on three lines with measurement specific information.
- The HS801 has an 8 bit resolution and a maximum sampling speed of 100 MHz. The input range is 0.1 volt full scale to 80 volt full scale. The record length is 32K/64K samples. The AWG has a 10 bit resolution and a sample speed of 25 MHz. The HS801 is connected to the parallel printer port of a computer.
- The minimum system requirement is a PC with a 486 processor and 8 Mbyte RAM available. The software runs in Windows 3.xx / 95 / 98 or Windows NT and DOS 3.3 or higher.
- TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 4WJ, UK
Tel: 01480-460028; Fax: 01480-460340

TiePie engineering (NL),
Koperslagersstraat 37, 8601 WL SNEEK
The Netherlands
Tel: +31 515 415 416; Fax +31 515 418 819

Web: <http://www.tiepie.nl>



CIRCLE NO. 116 ON REPLY CARD.

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

RF amplifiers operate at Bluetooth frequencies

NEC has introduced three monolithic integrated amplifiers (μ PC8178TB, μ PC8179TB and μ PC8182TB) covering the 0.1 to 2.9GHz frequency range which makes them suitable for Bluetooth designs as well as CATV and wideband-CDMA applications. Supplied in a six-pin super minimould package (SOT-363) in tape and reel format with 3k pieces per reel, the μ PC8178/79 are manufactured using the firm's 30GHz silicon bipolar process which uses direct silicon nitride passivation



film and gold electrodes, enabling a bandwidth of 0.1 to 2.4GHz. Power consumption is 4mA or less at 3V, power gain is between 11.5 and 15.5dB at 2.4GHz for the two devices and typical signal isolation is 44dB at 1GHz. It is suggested that the devices are suitable for designing buffer amplifiers in the final stages of Bluetooth receivers. For applications where a higher frequency response is required, the μ PC8182TB has a range of 0.9 to 2.9GHz, with a power gain of 20.5dB at 2.4GHz.

NEC

Tel: 01908 691133

www.nec.de

Single latching relay in small footprint

The subminiature G6KU, DPDT single pole latching relay from Omron is suitable for high

density mounting, with its compact dimensions of 5.2mm x 6.5mm x 10mm and weight of 0.7g. Operating at less than 100mW, the relay also conforms to UL and CSA standards and is plastic sealed for use in most soldering and washing processes. Also available is the G6KU-Y version which conforms to Bellcore specifications offering an impulse withstand voltage of 2500V for 2 x 10 μ s. Models offering outside-L SM terminals, inside-L SM terminals and PCB terminal shape options are available, with surface mount terminals incorporating a specially developed terminal structure with high infrared irradiation efficiency, allowing terminal temperature to rise easily when mounting the IRS, thereby ensuring excellent soldering. Mechanical life expectancy is in excess of 50

million operations and an electrical life expectancy of 100 000 operations minimum.

Omron

Tel: 0208 450 4646

www.eu.omron.com

Desktop robot solders and assembles

A desktop robot available from Townsend Coates is suitable for applications such as screw-



BOOK TO BUY

Servicing Audio and Hi-Fi Equipment

Return to Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Servicing Audio and Hi-fi Equipment

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Information

Credit card no _____

Card expiry date _____

Signed _____

'Its readers will benefit from its wealth of easily assimilated information, and repairs hitherto thought impossible will speedily become routine. And the first may well cover its purchase price. Congratulations on a comprehensive, well-written and lucid work' *Electronics Informer*.

'Interesting, entertaining and useful for both practitioners and teachers. All round a satisfying book which deserves to be considered as a tool rather than an ornament collecting dust on the shelf.' *Skillset Newsletter*


Service engineers and technicians have come to regard this book as essential to their work. As a bench-side companion and guide it has no equal. Its purpose is to ease and speed up the processes of fault diagnosis, repair and testing of all classes of home audio equipment: receivers, amplifiers, recorders and playback machines. The mechanics and electronics of domestic audio are examined by Nick Beer in a down-to-earth and practical way, concentrating on what goes wrong, how to track down problems, and how to solve them.

A symptom index and comprehensive manufacturer and supplier guide allow quick access to specific advice and suggestions.

The third edition is bang up to date with the latest technology-DVD, CD Recordable, PC audio systems. There is also new material on PA equipment.

UK Price: £32.00 Europe £34.00 ROW £64.50

Price includes delivery and packing

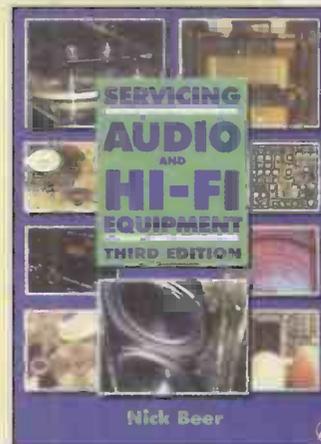

* Essential bench companion for all service engineers.

* New technology such as DVD and expanded material on MiniDisk will ensure another successful launch to this new edition

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!

TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite TV pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture + full details

FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are **BRAND NEW** or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non Laptop £18.95(B)
- 5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE £18.95(B)
- 5 1/4" Teac FD-55-03-U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy / HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS **Hi Brand New** £195.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 doubles sided **NEW** £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline **NEW** £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) **NEW** £79.95
 - 2 1/2" TOSHIBA MK2101MAN 2.16 Gb laptop (19 mm H) **NEW** £89.50
 - 2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H) **NEW** £105.00
 - 2 1/2" TOSHIBAMK6409MAT 3.1Gb laptop (12.7 mm H) **NEW** £190.00
 - 2 1/2" to 3 1/2" conversion kit for Pc's, complete with connectors £14.95
 - 3 1/2" FUJII FK-309-26 20mb MFM I/F RFE £59.95
 - 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
 - 3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00
 - 3 1/2" QUANTUM 40S Prodriv 4e 42mb SCSI I/F, New RFE £49.00
 - 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb £69.95
 - 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested £69.95
 - 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 8" NEC D2246 85 Mb SMD interface. **NEW** £199.00
 - 8" FUJITSU M322K 160Mb SMD I/F RFE tested £195.00
 - 8" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (C1)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MIT'S FA3445ETKL 14" Industrial spec SVGA monitors £245
- FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
- FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
- 1kW to 400 kW - 400 Hz 3 phase power sources - ex stock £POA
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM 53F5501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360, 11805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(2M) 64 i/o £POA
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £6500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New £4995
- HP1650B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector £POA
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set £POA
- HP6130A opt 020 300 MHz pulse generator, GPIB etc £7900
- HP A1, A0 8 pen HPGL high speed drum plotters - from £550
- HP DRAFTERMASTER 18 pen high speed plotter £750
- EG+G Brookdeal 95035C Precision lock in amp £1800
- View Eng. Mod 1200 computerised inspection system £POA
- Sony DXC-3000A High quality CCD colour TV camera £995
- Kethley 590 CV capacitor / voltage analyser £POA
- Racal ICR40 dual 40 channel video recorder system £3750
- Fiskers 45KVA 3 ph On Line UPS - New batteries £9500
- Emerson AP130 2.5KVA industrial spec UPS £2100
- Mann Tally Mt645 High speed line printer £2200
- Intel SBC 486/1335E Multibus 486 system. 8Mb Ram £945
- Siemens K4400 64Kb to 140Mb demux analyser £2950

IC's - TRANSISTORS - DIODES


OBSOLETE - SHORT SUPPLY - BULK
10,000,000 Items EX STOCK

For MAJOR SAVINGS
CALL OR SEE OUR WEB SITE www.distel.co.uk

VIDEO MONITOR SPECIALS

One of the highest specification
monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little

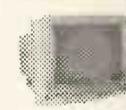

used condition. Order as MTS-SVGA
Tilt & Swivel Base £4.75 Only £119 (E)
VGA cable for IBM PC included.

External cables for other types of computers available - CALL

Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc. Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x 15 1/2" D. Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered. Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 KHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/4" x 12" x 11". Good used condition. Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call or see our web site.

- HP6030A 0-200V DC @ 17 Amps bench power supply £1950
- Intel SBC 486/125C08 Enhanced Multibus (MSA) New £1150
- Nikon HFV-11 (Ephlphot) exposure control unit £1450
- PHILIPS PM5518 Pro. TV signal generator £1250
- Motorola VME Bus boards & Components List. SAE / CALL £POA
- Trio 0-18vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM high speed band printer £1950
- Fujitsu M3041D 600 LPM printer with network interface £1250
- Perkin Elmer 299B Infrared spectrophotometer £3500
- Perkin Elmer 597 Infrared spectrophotometer £3250
- VG Electronics 1035 TELETEXT Decoding Margin Meter £495
- LightBand 60 output high spec 2u rack mount video VDA's £1995
- Seikon SD 150H 18 channel digital Hybrid chart recorder £300
- B&K 2633 Microphone pre amp £750
- Taylor Hobson Tallysur amplifier / recorder £1450
- ADC S5200 Carbon dioxide gas detector / monitor £75
- BBC AM20/3 PPM Meter (Ernest Turner) + drive electronics £675
- ANRITSU 9654A Optical DC-2.5G/b waveform monitor £5650
- ANRITSU MS9001B1 0.6-1.7 uM optical spectrum analyser £POA
- ANRITSU ML93A optical power meter £990
- ANRITSU Fibre optic characteristic test set £POA
- R&S FTD3 Dual sound unit £6650
- R&S SBUF-E1 Vision modulator £775
- WILTRON 6630B 12.4 / 20GHz RF sweep generator £5750
- TEK 2445 150 MHz 4 trace oscilloscope £1250
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1955
- TEK TDS380 400MHz digital realtime + disk drive, FFT etc £2900
- TEK TDS524A 500MHz digital realtime + colour display etc £5100
- HP3585A Opt 907 20Hz to 40 MHz spectrum analyser £3950
- PHILIPS PW1730/10 60KV XRAY generator & accessories £POA
- CLAUDE LYONS 12A 240V single phase auto. volt. regs £325
- CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs £2900

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we

have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels. £345.00 (G)
OPT Rack 2 Rack Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage' nuts. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)



Sold at LESS than a third of makers price !!

A superb buy at only £245.00 (G)
42U version of the above only £345 - CALL

12V BATTERY SCOOP - 60% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each **Our Price £35 each (C) or 4 for £99 (E)**

RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

COLOUR CCD CAMERAS

BIG £ SAVER

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available.

Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.

Web ref = LK33 ONLY £99.00 or 2 for £180.00 (B)

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95
Windows for Workgroups 3.11+ Dos 6.22 on 3 1/2" disks £55.00
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
shipping charges for software is code B

DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk

Display
- ELECTRONICS -

ALL MAIL TO
Dept ww, 29/35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5.30

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Selhurst Park SR Rail Stations

NEW
DISTEL ©
Visit our web site
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.50, (E)=£18.00, (F)=£20.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1999. E & O.E. 07/99.

CIRCLE NO. 117 ON REPLY CARD

Valve Radio and Audio Repair Handbook

* A practical manual for collectors, owners, dealers and service engineers * Essential information for all radio and audio enthusiasts * Valve technology is a hot topic

This book is not only an essential read for every professional working with antique radio and gramophone equipment, but also dealers, collectors and valve technology enthusiasts the world over. The emphasis is firmly on the practicalities of repairing and restoring, so technical content is kept to a minimum, and always explained in a way that can be followed by readers with no background in electronics. Those who have a good grounding in electronics, but wish to learn more about the practical aspects, will benefit from the emphasis given to hands-on repair work, covering mechanical as well as electrical aspects of servicing. Repair techniques are also illustrated throughout.

This book is an expanded and updated version of Chas Miller's classic Practical Handbook of Valve Radio Repair. Full coverage of valve amplifiers will add to its appeal to all audio enthusiasts who appreciate the sound quality of valve equipment.

Contents: INCLUDES: Electricity and magnetism; Voltage, current, resistance and Ohm's Law; Real life resistors; Condensers; Tuning; Valves; Principles of transmission and reception; Practical receiver design; Mains valves and power supplies; Special features of superhets; Battery and mains battery portable receivers; Automobile receivers; Frequency modulation; Tools for servicing radio receivers; Safety precautions; Fault finding; Repairing power supply stages; Finding faults on output stages; Faults on detector/AVC/AF amplifier stages; Finding faults on IF amplifiers; Faults on frequency-changer circuits; Repairing American 'midget' receivers; Repairing faults on automobile radios; Repairing battery operated receivers; Repairing FM and AM/FM receivers; Public address and high fidelity amplifiers.



UK Price: £22.50 Europe £25.00 ROW £27.00

** Price includes delivery and packing **

Return to Jackie Lowe, Room L333, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Valve Radio and Audio Repair Handbook

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Access/Mastercard/Visa/Cheque/PO

**Cheques should be made payable to
Reed Business Information**

Credit card no _____

Card expiry date _____

Signed _____

NEW PRODUCTS

Please quote *Electronics World* when seeking further information


tightening, dispensing, soldering and impulse welding. Using an L-type body structure, and an aluminium-alloy, die cast single-structure base, the Janome JR200 mini desktop robot offers positional repeatability of ± 0.01 mm. It can also support a portable work weight of 3.5kg (max.) for the Z-axis and 7kg for the X/Yaxes.

Data capacity is up to 6000 points and 100 programs and for storage the robot uses a flash memory card which needs no battery. The product is supplied as standard with two serial (RS232) interfaces (one for the teaching pendant, the other for PC connection), and a third - for external I/O - is available as an option. A simple sequencer is built into the robot, and operates independently. No further hardware is necessary, because the I/O uses part of the robot's main external I/O port. With speeds up to 500mm/s (X/Y), and 250mm/s (Z), the robot is driven by a 5-phase stepping motor operating from a 90-132VAC/180-250VAC supply, with a current consumption of 200VA.

Townsend Coates
Tel: 0116 274 4488
www.townsendcoates.com

Sealed packaging for frequency converters

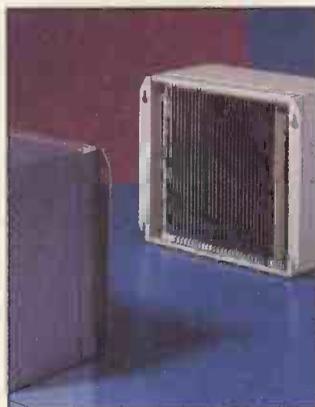Rittal's range of compact AE enclosures are now available with integrated aluminium heat sink and are designed for the installation of standard-design frequency converters, together with their corresponding protective devices and power contactors. Designed as a



passive heat sink with cooling ribs on the rear of the enclosure, the mounting plate provides space for the mounting of frequency converters, motor circuit breakers, power contactors or terminal strips. Three different sizes of heat sink permit individual adaptation of the cooling capacity and the thermal conductivity of aluminium guarantees reliable dissipation of the generated heat, says the supplier.

Rittal
Tel: 01709 704000
www.rittal.co.uk

PC power supplies can be customised

A range of PC power supplies with a number of options offering customisation is now available from Powerline. Designed for use in industrial and critical business PC applications, the units are available with continuous output ratings of up to 400W from a standard ATX package. Options available include power-factor correction to meet the requirements of forthcoming legislation, auto-ranging inputs and approvals for worldwide use, and hot-swap units for mission-critical applications.



Custom capabilities that can be factory-fitted include modified cable leads with different lengths and connector styles, fan reversal, and internal voltage trimming. In addition to the standard ATX packaged products, a range of low-profile units suitable for 1U rack mounting is available with output ratings of 150-200W. ■

Powerline
Tel: 01494 753800
www.powerline.co.uk

Self on Audio

Douglas Self

The cream of 20 years of Electronics World articles (focusing on recent material)

A unique collection of design insights and projects - essential for all audio designers, amateur and professional alike.

Scientific electronics based on empirical data

Douglas Self has been writing for Electronics World and Wireless World over the past 20 years, offering cutting-edge insights into scientific methods of electronics design.

This book is a collection of the essential Electronics World articles, covering twenty years of amplifier technology but with a very strong bias towards more recent material. The articles include self-build projects as well as design ideas and guidance for the professional audio designer. The result is a unique collection of design insights and projects - essential for all audio designers, whether amateur or professional.

Contents: Introduction; PRE-AMPLIFIERS: An advanced preamplifier MRPI; High-performance preamp MRP4; Precision preamp MRP10; Moving-coil head amp; Preamp '96 I; Preamp '96 II; "Overload Matters" (RIAA overload); Balanced line inputs and outputs, part 1; Balanced line inputs and outputs, part 2; POWER AMPLIFIERS: FETs less linear than BJTs; Distortion in power amplifiers 1-8; Distortion residuals; Trimodal part 1, 2; Load-invariant power amp INVAR.DOC; Common-emitter amps; Two-stage amplifiers; SPEAKERS: Excess speaker currents; Class distinction (amp classification); Relay control; Power partition diagrams; Audio power analysis.



Self
on
Audio
DOUGLAS SELF

Douglas Self has dedicated himself to demystifying amplifier design and establishing empirical design techniques based on electronic design principles and experimental data. His rigorous and thoroughly practical approach has established him as a leading authority on amplifier design.

Readership: Audio electronics enthusiasts;
Professional amplifier designers;
Power amp users
Paperback
Pages: 416pp

UK Price: £26.50 Europe £27.50 ROW £28.50

**Return to Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS**

Please supply the following title:

SELF AUDIO

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (*please circle*)

Mastercard/Visa/Cheque/PO

**Cheques should be made payable to
Reed Business Information**

Credit card no _____


Card expiry date _____

Signed _____

RANGER XL

The Complete Integrated Schematic PCB Layout Package

Too good for words

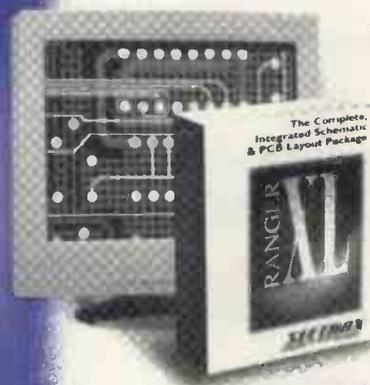

The New Ranger XL Series

Ranger 2 for Windows £170
NEW Ranger 2XL £500
NEW Ranger XL from £950
FREE Website Download Demo



Advanced Systems & Technology for PCB Manufacturers

Old Buriton Lime Works, Buriton, Petersfield, Hants. UK GU31 5SJ
 Tel: (44) 01730 260062 Fax: (44) 01730 267273

CIRCLE NO.118 ON REPLY CARD



Quality Alphanumeric backlit LCDs in 4x40, 2x40, 4x20, 2x20 and 2x16 formats


Supplied either bare or pre-fitted with one of our Eze-Use, Serial interface boards with options such as software buzzer control, backlight control, operator interface, start-up message, big character generation, and PC-AT Keypad /mouse interface - all at very competitive pricing.

We also stock Serial Interface Graphic modules and front panel bezels for all our LCDs. Please call (01977 683665) or check our web site (www.milinst.com) for full details and pricing.

Milford Instruments - your total LCD solution



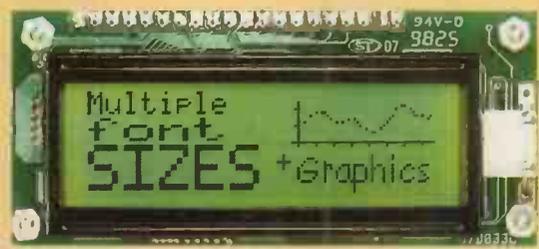Milford Instruments
 Milford House, 120 High St
 South Milford
 LEEDS LS25 5AQ
 Tel 01977 683665
 Fax 01977 681465
www.milinst.com



CIRCLE NO.119 ON REPLY CARD

Sound-reinforcement amplifier

Needing a sound-reinforcement system for use in a medium size hall, Ben Sullivan came up with this unusual and versatile design. Its pre-amp/mixer stage has three mono channels, each of which can take a variety of input options, and it caters for a wide range of input levels.

Meetings of a local society, of which I am a committee member, are due to move to a new location that does not have a sound reinforcement system. So in readiness, I designed the system presented here. Versatility was to be a key design criterion, both as far as amplifier inputs were concerned, and also for connecting different loudspeakers.

For public address, or PA, systems operating in the open air, an amplifier driving a 100V line with multiple horn speakers is the norm. But for this application, a modest maximum output power of something in excess of 15W was deemed sufficient. The equipment is intended solely for indoor use, with conventional loudspeakers.

A pair of surplus-to-requirements sizeable loudspeakers, each including a 10 inch 15Ω WB cambric cone loudspeaker, tweeter and crossover, were donated by a colleague. A suitable microphone was already to hand, so it only remained to produce an amplifier.

The requirement

In addition to using the microphone, some presenters bring along illustrations to their talks, either on cassette or CD, so more than one input channel would be required.

To allow for any contingency, three input channels would be provided. Each would have its own level control and there would be a master overall level control.

For a sound reinforcement system,

stereo operation is not appropriate. With one loudspeaker at each side of the hall near the front, most of the audience would not hear any stereo effect, while those near one loudspeaker or the other would receive just the left or right channel alone. So

the amplifier was designed to drive the approximately 8Ω load of the two loudspeakers in parallel.

Power-amplifier configuration

Figure 1 shows the configuration usually used for a hi-fi amplifier in

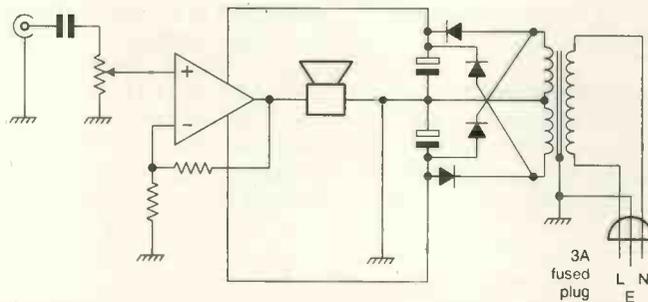


Fig. 1. Skeleton diagram of common hi-fi power-amplifier circuit with direct-coupled loudspeaker. Here, a centre-tapped transformer makes producing the necessary positive and negative rails easy.

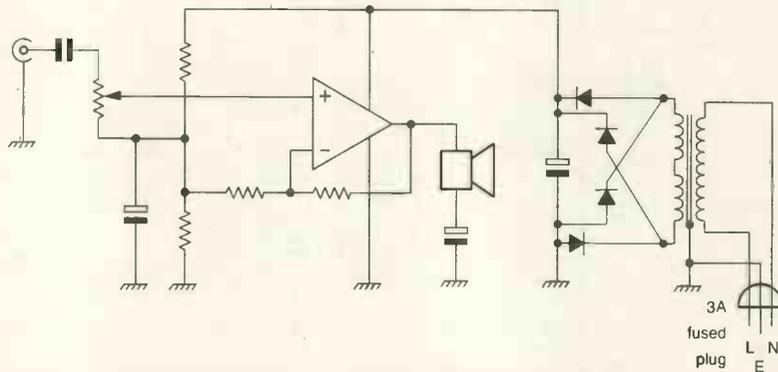


Fig. 2. Power-amplifier circuit using a single rail-supply. Because ground is no longer the same potential as the static voltage at the output of the power amplifier, the speaker has to be connected via a large electrolytic coupling capacitor.

simplified form. A mains transformer with two identical secondary windings, or a centre tapped winding, is used in conjunction with a bridge rectifier to produce plus and minus voltage rails. The arrangement requires two main smoothing capacitors, and has the advantage that the rails can also be stepped down to $\pm 15V$ to supply a preamplifier design using op-amps.

A high-quality toroidal mains transformer of suitable secondary voltage and VA rating was available from stock. On the face of it though, it was not suitable as its two secondary windings had different voltages.

As the overall voltage of the windings in series was just what was needed, the PA arrangement of Fig. 2 was viewed as a possible alternative. This needs only a single main smoothing capacitor, though of twice the voltage rating of those in Fig. 1. It is quite convenient if the input signal is large enough to drive the PA to full output, but not so useful if a preamplifier/mixer stage using op-amps is needed.

In the event, the circuit designed circumvented this difficulty.

Power amplifier design

A TDA2050V was chosen as the power amplifier. It proved to be capable of providing over 15W into a dummy load from the nominal 40V

supply provided by the transformer. The dummy load consisted of two 15Ω wirewound resistors in parallel.

After some thought and experimentation, it was incorporated into the PA circuit of Fig. 3. This can be seen as a cross between the Figure 1 and Figure 2 arrangements.

The circuit design was taken directly from the power amplifier's data sheet as far as component values are concerned. Usefully, the device includes over-temperature and over-current protection, and it provides a massive 90dB of open loop gain. With the 30dB of demanded gain set by R_7/R_6 , the 60dB of negative feedback within the loop results in a distortion figure of around 0.02%

The chassis earth symbols shown at R_3 and elsewhere indicate not only the circuit's nominal 0V rail, but also the case metalwork and mains earth. This means that effectively, the power supply provides both positive and negative voltages.

These voltages are used also, suitably stepped down, to supply the earlier preamplifier/mixer stages. This circuit arrangement means that neither side of the loudspeakers is earthed, and both poles of the loudspeaker output sockets must be isolated from ground.

As mentioned, the amplifier is designed to drive two 15Ω loudspeakers in parallel. For versatility, $1/4$ in jack sockets, two-pin DIN

loudspeaker sockets and phono (RCA) sockets were provided. All six sockets were connected in parallel.

As the power supply section was mounted at the opposite end of the case from the PA board, C_7 and C_8 were fitted close to the TDA2050V on its 0.1in matrix strip-board circuit, as local decoupling in accordance with good practice.

The TDA2050V was mounted at one end of the stripboard, with its pins twisted to fit a 0.1 inch spacing. The body of the device was bolted to a substantial L shaped bracket, using a mica insulator and silicone mounting grease. This would not have been necessary in the circuit of Fig. 2, as the device's metal heat-sink tab is connected to the negative supply rail.

In turn, the bracket was bolted to the base of the case to provide additional heat-sinking. On soak test, driving 30V peak-to-peak into the 7.5Ω resistive dummy load, the device case temperature eventually just reached $50^\circ C$, in a room ambient of $20^\circ C$.

Preamplifier and mixer stages

The three input channels and mixer stage are shown in Fig. 4. Each channel is provided with an input for a stereo signal, these being resistively combined into a mono signal.

There are also three inputs for mono signals per channel. The sockets are so distributed across the


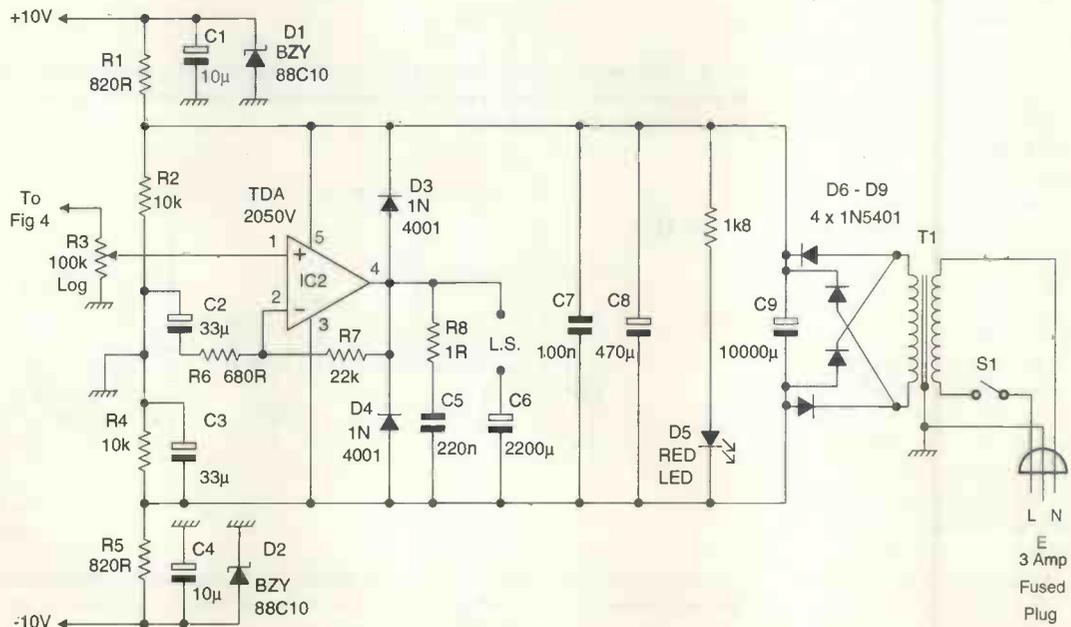


Fig. 3. Circuit of sound reinforcement amplifier using a modified single rail supply.

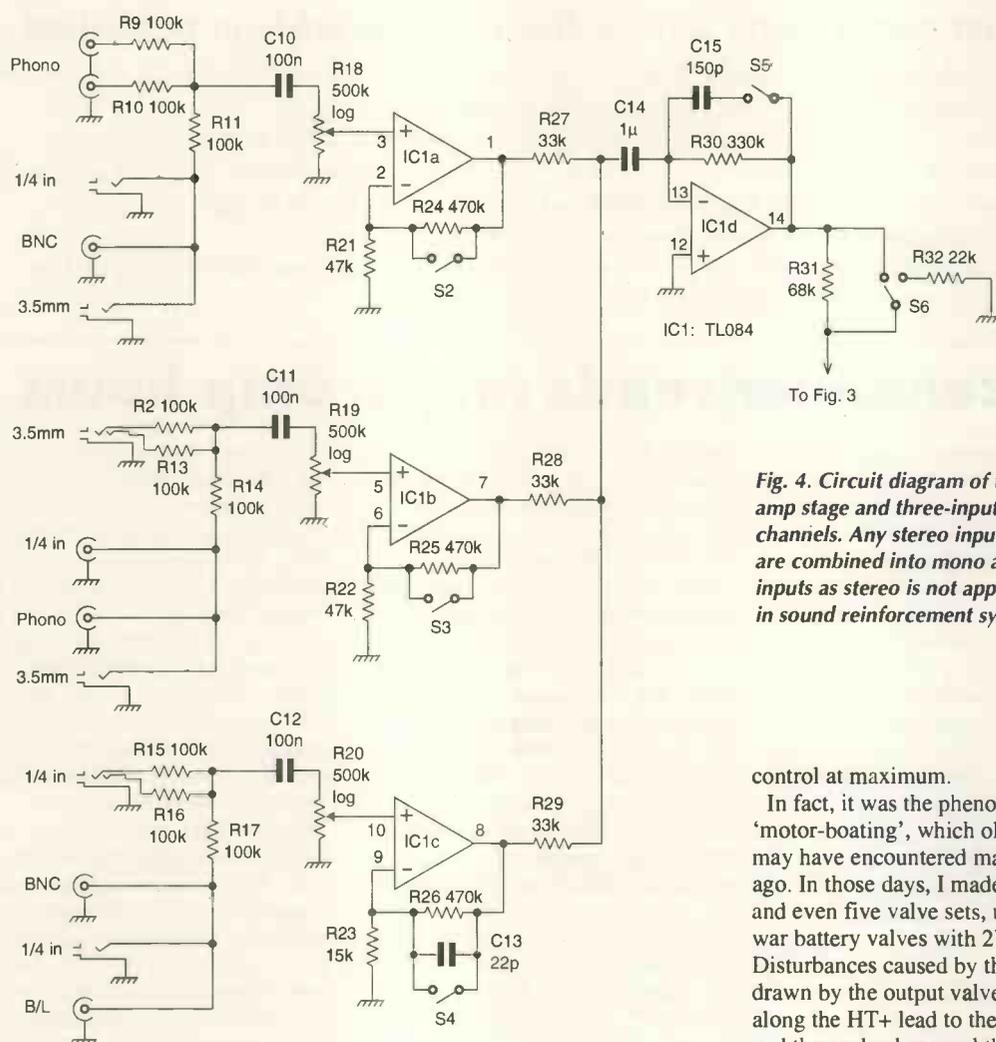

To Fig. 3

Fig. 4. Circuit diagram of the pre-amp stage and three-input mixer channels. Any stereo input signals are combined into mono at the inputs as stereo is not appropriate in sound reinforcement systems.

channels that almost any conceivable type of input can be accommodated, with the exception of the bulky XLR audio connector. A 1/4 in jack plug/XLR socket BSA (between series adapter) will cope with this eventuality, should it arise.

Each input signal is routed directly to a volume control. This is not of course good practice in a hi-fi system, but there the amplitude of the inputs is known. The arrangement used here permits the amplifier to accept any conceivable amplitude input.

Output from the pre-amp/mixer feeds the power amplifier stage via a switchable 0 or 10dB attenuator, S₆. Channels 1 and 2 are switchable between a nominal +20dB gain and unity gain. Channel 3 provides the option of unity gain or +30dB.

Capacitor C₁₃ was found necessary to ensure stability when both the channel 3 and master level controls

were at maximum, S₄ at the +30dB and S₆ at the 0dB settings. Under these conditions, a 1mV rms input will provide around 15W output.

Naturally, with such high gain, there is a little background hiss and the level of this proved to be precisely what should be expected, given the quoted 10Hz to 10kHz voltage noise of the TL084 of 4μV. The treble roll-off available with S₅ could then be useful. It is debatable if the full channel 3 gain will ever be needed, but it is available just in case.

Design anomalies

While the amplifier design described performs perfectly the function required, one or two surprises surfaced during development.

The first concerned a very low frequency instability. This set in as any of the channel level controls was advanced, with the master level

control at maximum.

In fact, it was the phenomenon of 'motor-boating', which old timers may have encountered many years ago. In those days, I made three, four and even five valve sets, using pre-war battery valves with 2V filaments. Disturbances caused by the current drawn by the output valve fed back along the HT+ lead to the first stage, and thence back around the loop. Increased decoupling served only to reduce the frequency of the oscillation. So D₁ and D₂ were added, extending the effectiveness of the decoupling down to 0Hz, and completely curing the problem.

The other oddball surfaced during frequency response testing. The bass roll-off set in at a higher frequency than expected, so C₁₄ was increased to 1μF. In conjunction with R₂₇, R₂₈ or R₂₉ – 33kΩ – one might then expect a –3dB point of 4.8Hz, but it was much higher than this.

The reason is that, once the reactance of C₁₄ becomes significant, R₂₇, R₂₈ or R₂₉ no longer look into a virtual earth. So the output of IC_{1a} via R₂₇, for example, is subject to attenuation by R₂₈ and R₂₉ in parallel before being applied to C₁₄.

It is running across points like these, and working out the reasons, that keeps circuit design a constant challenge and joy. ■

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.

Bike computer reads amps, amp.hours

A bicycle computer counts wheel revolutions, and displays speed and distance travelled. Depending on the model, it may also show the maximum and average speeds achieved.

The user has to program the computer with the wheel circumference C in metres, since velocity v in km/h is related to the frequency of wheel

rotation, F_{rps} , by $(v \div 3.6) / C = F$. Usually, a magnet attached to a wheel operates a reed relay to provide the count pulses, but in this application, a transistor switch is used.

Such a bicycle computer can be used for other purposes, such as measuring the charge rate and total charge stored in a solar panel accumulator charging set-up, Fig. 1. To achieve this, the charging current is monitored by a current shunt R_s , controlling a voltage-controlled oscillator.

The voltage controlled oscillator produces an output frequency such that a bicycle computer velocity reading of 120km/h indicates a current

of 12A, and a trip reading of 2998.9 km indicates a charge of 299.89Ah.

The programmable value of C on the computer used was up to 2.999m. The VCO was designed to produce an output frequency of up to 13.7Hz for a 140mV input, corresponding to a 14A charging current. With this design of oscillator, Fig. 2, a circumference setting C of 2.671m worked well.

This application is limited by the lowest and highest frequencies that the bicycle computer can count, and by VCO offset and linearity errors.

A minimum output frequency of 0.1Hz is produced by the VCO, even when the drop across R_s is zero. But linearity errors up to the designed maximum, checked with a DVM and DSO, proved to be generally insignificant. There is a slight increase in error at the high frequency end of the range, due to the finite discharge time of C_1 .

Heinz Zanke
GR-24002 Messenias
Greece
E10

Winner!

Overall winner of our 2000 circuit ideas competition – sponsored by National Instruments – is Heinz Zanke's ingenious amp.hour meter. Heinz wins a National Instruments LabVIEW graphical programming environment package worth over £700.

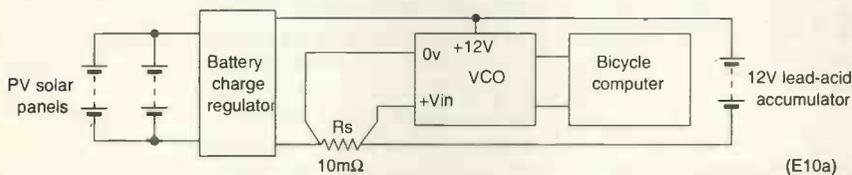


Fig. 1. Block diagram of charger metering system in a solar-energy system, using a bicycle computer to monitor amps and Ah.

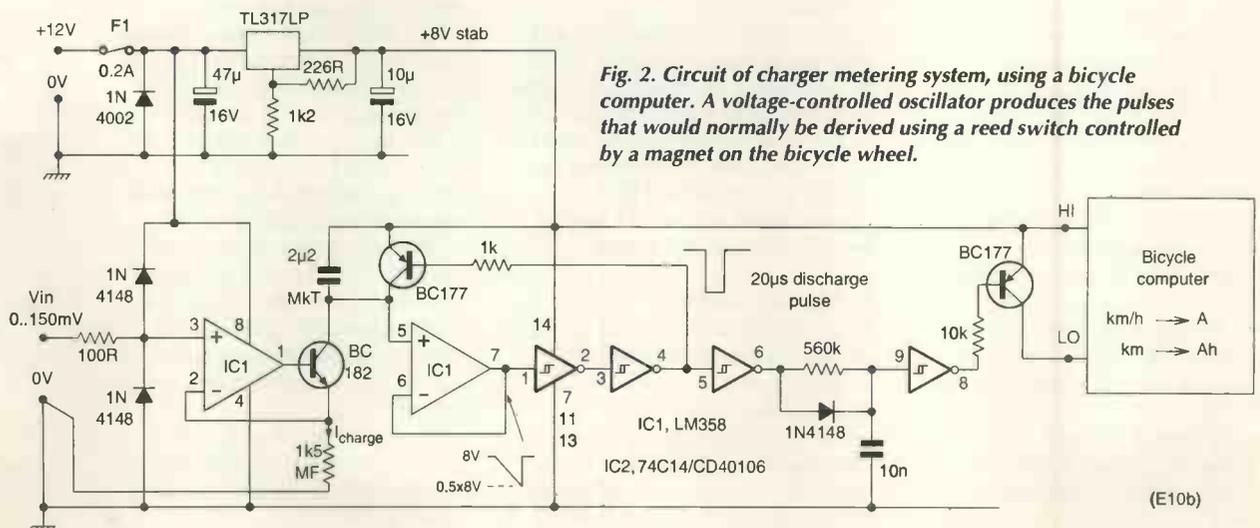


Fig. 2. Circuit of charger metering system, using a bicycle computer. A voltage-controlled oscillator produces the pulses that would normally be derived using a reed switch controlled by a magnet on the bicycle wheel.

Ice alert!

The recent cold weather reminded me of a simple ice alert warning circuit I built in 1974, long before such circuits became available as standard fittings in some cars.

My present car has a factory fitted ice warning which simply lights an orange LED for temperatures below 5°C or red LED below 0°C. This suffers from two problems. When driving in bright winter sunlight, these indicator lights do not easily attract attention, also there is no indication of temperature changes except when it passes the above limits.


My ice alert differs in that for temperatures above some 5°C the green LED glows continuously, to indicate normal function.

As temperature reduces the red LED pulses on and the green LED pulses off, approximately once each

second. The duty cycle increases as the temperature falls. Ultimately at 0°C and at lower temperatures, the green LED remains off and the


LED glows continuously.

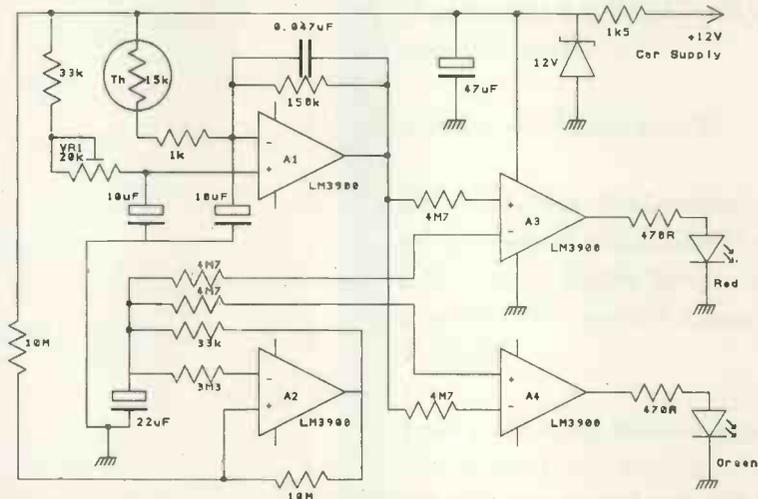I find this most beneficial in bright sunshine, because the brief initial pulses of the red LED as temperature



This ice indicator gives more useful information than a car's simple factory fitted warning indicator.

Ten year index: new update

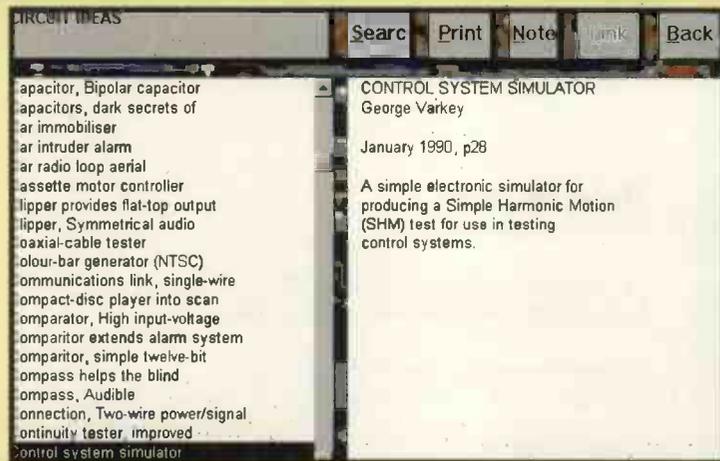

Hard copies and floppy-disk databases both available

Whether as a PC data base or as a hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications - including a synopsis for each.

The *EW* index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format.

Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Ordering details

The *EW* index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders.

Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquires about photocopies etc please send an sae to SoftCopy Ltd. **Send your orders to SoftCopy Ltd, 1 Vineries Close, Cheltenham GL53 0NU.**

Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

www.softcopy.co.uk

Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* index Indexes on paper for volumes 100, 101, and 102 are available at £2 each, excluding postage.

BOOK TO BUY

The definitive biography of the century's godfather of invention—from the pre-eminent Edison scholar "Israel's meticulous research and refusal to shy away from the dodgier aspects of Edison's personality offers a fresh glimpse into the life of the inventor."—*New Scientist*

"Remarkable."—*Nature*


"An authoritative look into Edison's working methods, here leavened by enough personal detail to give the achievements shape."—*Publishers Weekly*

"Israel's book should go a long way toward taking Edison out of the shadows and placing him in the proper light."—*Atlanta Journal-Constitution*

"Exhaustively researched, with strong emphasis on Edison's methods and achievements."—*Kirkus Reviews*

The conventional story of Thomas Edison reads more like myth than history: With only three months of formal education, a hardworking young man overcomes the odds and becomes one of the greatest inventors in history.

But the portrait that emerges from *Edison: A Life of Invention* reveals a man of genius and astonishing foresight whose career was actually a product of his fast-changing era. In this peerless biography, Paul Israel exposes for the first time the man behind the inventions, expertly situating his subject within a thoroughly realized portrait of a burgeoning country on the brink of massive change. Informed by Israel's unprecedented access to workshop diaries, notebooks, letters, and more than five million pages of archives, this definitive biography brings fresh insights to a singularly influential and triumphant career in science.

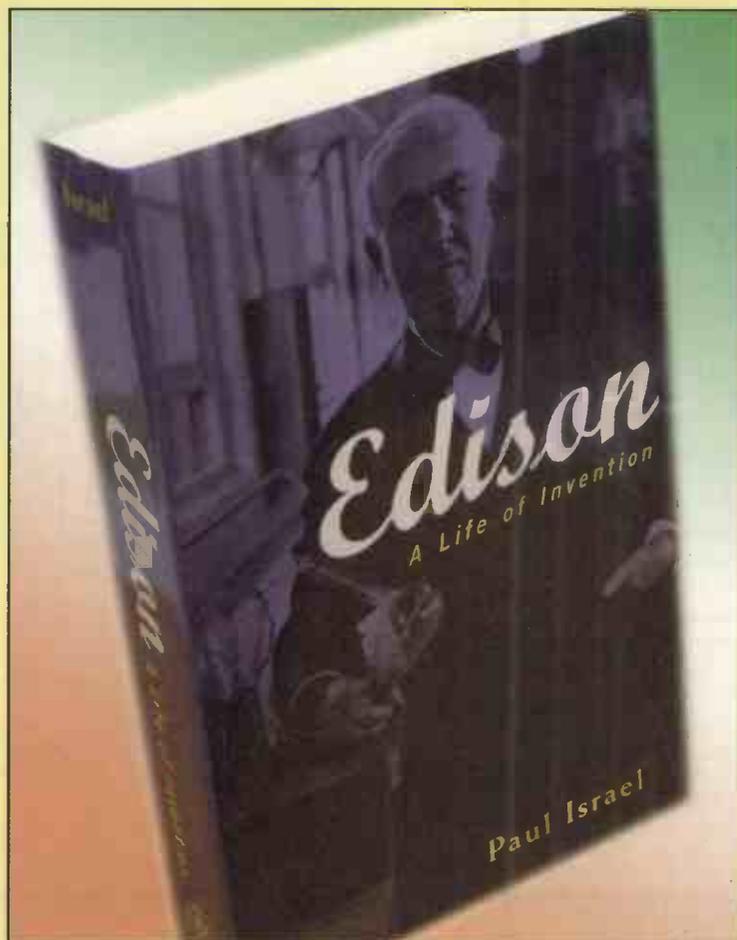

**Post your completed order form to:-
Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS**

**Fax your completed order form to 020 8652 8111
UK Price: £15.00 Europe £17.00 ROW £19.00
Price includes delivery**

How to pay (Edison) paperback

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card
 Mastercard American Express Visa Diners Club

Credit Card No: _____ Expirey Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

drops below 5°C attracts attention and the change in duty cycle indicates whether the temperature is rising or it is becoming colder. The LEDs can even be located below your line of sight, so as not to interfere with normal driving, yet still attract your attention when needed.

Using only one IC, the circuit is low cost and easily built. The thermistor should be mounted in a closed housing located behind the front bumper. While I used a thermistor of 15kΩ at 25°C, other values can be accommodated simply by amending the calibration and feedback resistors at A₁.

The LM3900 IC responds to current

ratios at its inputs, not voltage as is more usual. Hence it is insensitive to change in battery voltages. The zener is included to clip supply voltage transients caused by load shedding of the alternator.

Amplifier A₁ simply compares the resistance of the thermistor with the series combination of VR₁ and 33kΩ, changing from 0.3 V_{battery} above 5°C to 0.6 V_{battery} at 0°C.

Amplifier A₂ is configured as a free running multivibrator with a repetition rate of approximately one pulse each second and output varying between 0.3 V_{battery} and 0.6 V_{battery}.

Outputs of A₁ and A₂ are compared in the remaining amplifiers A₃ and

A₄. When the A₂ output is lower than A₁ output the red LED lights. When the A₂ output is higher than A₁, the green LED lights. Since A₃ and A₄ inputs are wired in opposition both LEDs cannot simultaneously be lit.

Calibration at 0°C is simply obtained by immersing the thermistor probe in an ice water mixture, adjusting VR₁, prior to installing in your car.

This now elderly circuit has performed well for many years in a number of different vehicles.

Cyril Bateman

Acle
Norfolk

Battery operated theft alarm

This circuit can be used as either a loop alarm or with a pressure sensor/switch to give a treasured/expensive item 24-hour alarm protection while you are on the premises with your building's burglar alarm switched off. It is simple and cheap enough to build several, with each protected item possibly using a different sounding alarm for identification purposes. Running on a single PP3 battery, it is portable and allows over 12 months use while waiting for action, less if the unit is triggered often.

The unit is built around a 4001 quad CMOS NOR gate with two gates, 1a and 1b, forming a bistable and the remaining two, 1c and 1d, forming an inverting buffer. The main on/off switch S_{1a} is ganged with S_{1b} and is a double-pole double-throw device,

which can be key operated for added security. It is wired such that when the alarm is switched on C₂ is open circuit and when the unit is switched off C₂ is shorted out.

At switch on, and assuming that the wire loop/switch is closed and hence holding pin 1 low, a brief high pulse via C₁ at pin 6 causes the bistable to set and its output to go high. As C₂ was initially discharged, via S_{1b} when the unit was off, it charges via R₃ and hence takes a little while before the inverting buffer, 1c and 1d outputs an high. During this time – approximately 1 second – Tr₁ is switched on and the sounder energised. This allows the battery condition to be assessed at switch on. After this delay Tr₁ switches off and the alarm is ready to be triggered.


To trigger the alarm, either the loop

must be broken or the sensor switch opened. This sends pin 1 of IC₁ high and resets the bistable. Its output goes low and due to D₁ the capacitor discharges very quickly sending the input to the buffer low, its output high and hence switching Tr₁ and the sounder on rapidly. To reset the unit the power must now be switched off and back on again.

Several items could be protected by a single unit if extra sensor switches are wired in series, avoiding the need to build extra circuits. The maximum current that the sounder can take is limited to 200mA by Tr₁'s maximum collector current. Upgrading this device would allow a louder unit to be used.

Lee Archer

Ashton-in-Makerfield,
Lancashire
E48

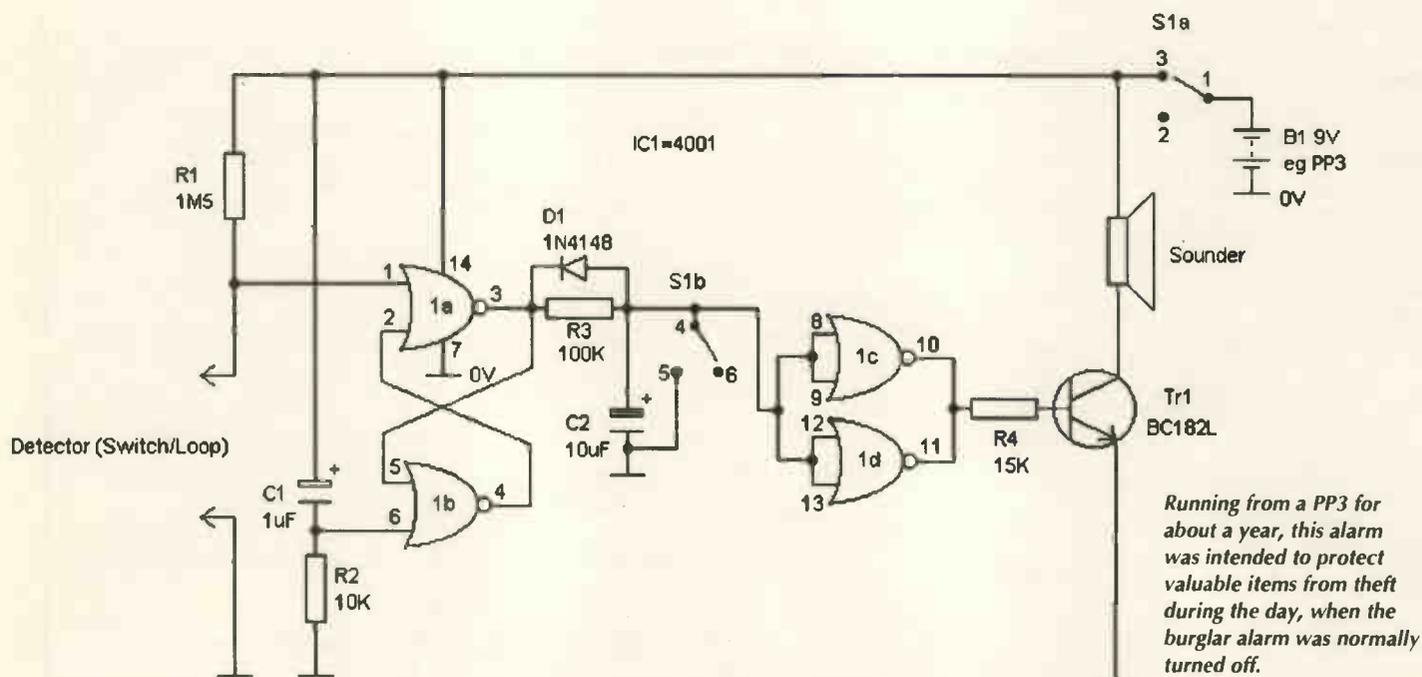

£70 WINNER

Portable precision programmable reference generator

A battery powered programmable voltage reference generator is shown here. Its output range is between 0 and 4.0955V. By pushing

up and down buttons, more than 8000 voltages can be selected.


The selected voltage is maintained in non-volatile memory when the power

is turned off. A MAX5130 13-bit serial d-to-a converter generates the reference voltage. This device has an internal reference and an operational amplifier so no external components are required to send precision voltage out.

A PIC16C84 microcontroller is used to accept input commands and control the output voltage by sending data into MAX5130 through three wires. This PIC has built-in EEPROMs to store the output data without power supply.

Four buttons control the output voltage up or down. Switches S_2 and S_4 make a step change in 0.5mV increments. Switches S_3 and S_5 change 100 steps (50mV) to make output voltage reach the desired level quickly.

*Yongping Xia
Torrence
USA
E49*

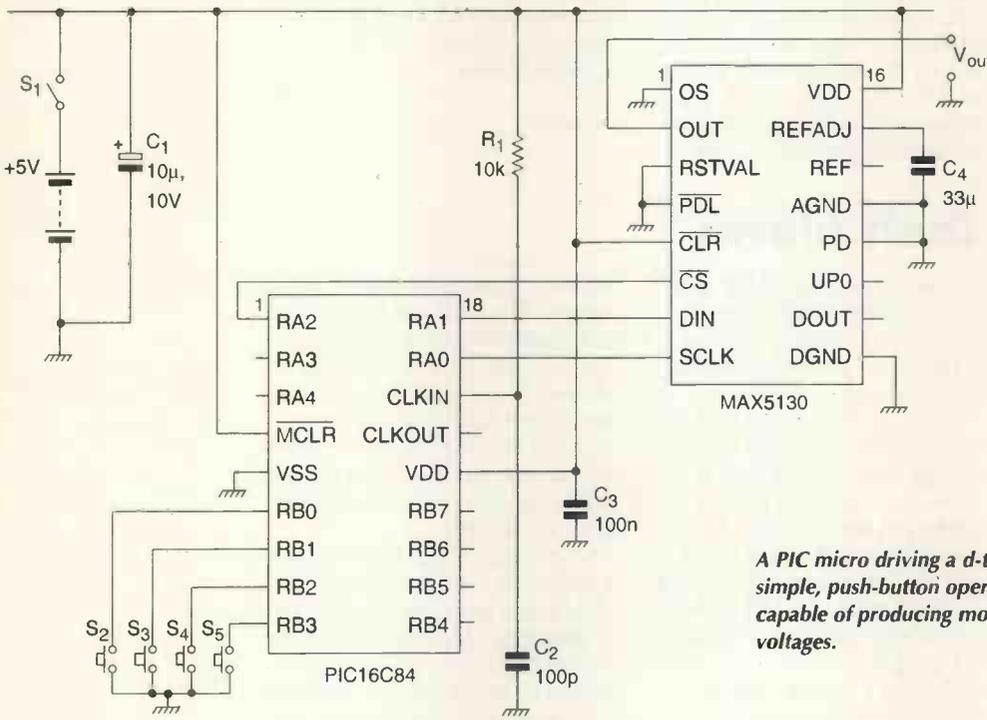

A PIC micro driving a d-to-a converter makes a very simple, push-button operated voltage reference capable of producing more than 8000 different voltages.

PIC assembler for a very simple reference circuit that can produce more than 8000 voltages between 0 and 4.0955V.

LIST p=16C84

```
TMR0 equ 0x01
PCL equ 0x02
STATUS equ 0x03
PORTA equ 0x05
PORTB equ 0x06
EEDATA equ 0x08
EEDR equ 0x09
INTCON equ 0x0b
OPT equ 0x81
TRISA equ 0x85
TRISB equ 0x86
EECON1 equ 0x88
EECON2 equ 0x89
```

```
Z equ 2
C equ 0
W equ 0
F equ 1
RP0 equ 5
RD equ -0
WR equ 1
WREN equ 2
data_1 equ 0x0c ;
```

```
data_2 equ 0x0d ;
cnt_1 equ 0x0e ;
cnt_2 equ 0x0f ;
temp_1 equ 0x10 ;
temp_2 equ 0x11 ;

org 0x0 ;
main
    clrf PORTA ;initialization
    clrf PORTB
    bsf STATUS, RP0 ;bank 1
    movlw 0x7f ;
    option
    movlw 0x00 ;
    movwf TRISA ;set PORTA output
    movlw 0x0f ;
    movwf TRISB ;set PB0-PB3 input, PB4-PB7 output
    bcf STATUS, RP0 ;bank 0
    bsf PORTA, 2 ;
    ;
    clrf EEDR ;read from eeprom
    bsf STATUS, RP0 ;bank 1
    bsf EECON1, RD ;
    bcf STATUS, RP0 ;bank 0
    movf EEDATA, W ;read data_1 from eeprom
    movwf data_1 ;
    incf EEDR, F ;
    bsf STATUS, RP0 ;bank 1
```

```

    bsf    EECON1, RD    ;
    bcf    STATUS, RP0  ;bank 0
    movwf EEDATA, W    ;read data_2 from eeprom
    movwf data_2 ;
    call   send_data   ;
;
read_button
    btfs  PORTB, 0     ;test +1 button
    goto  up_1 ;
    btfs  PORTB, 1     ;test +100 button
    goto  up_100 ;
    btfs  PORTB, 2     ;test -1 button
    goto  down_1 ;
    btfs  PORTB, 3     ;test -100 button
    goto  down_100 ;
    goto  read_button ;
;
up_1
    incfsz data_1, F ;
    goto  up_date ;
    incf  data_2, F ;
    btfs  data_2, 5 ;
    goto  up_date ;
    decf  data_1, F ;
    decf  data_2, F ;
    goto  up_date ;
;
up_100
    movlw 0x64 ;
    addwf data_1, F ;
    btfs  STATUS, C ;
    goto  up_date ;
    incf  data_2, F ;
    btfs  data_2, 5 ;
    goto  up_date ;
    movlw 0xff ;
    movwf data_1 ;
    movlw 0x1f ;
    movwf data_2 ;
    goto  up_date ;
;
down_1
    decf  data_1, F ;
    movf  data_1, W ;
    sublw 0xff ;
    btfs  STATUS, Z ;
    goto  up_date ;
    decf  data_2, F ;
    btfs  data_2, 7 ;
    goto  up_date ;
    clrf  data_1 ;
    clrf  data_2 ;
    goto  up_date ;
;
down_100
    movlw 0x64 ;
    subwf data_1, F ;
    btfs  STATUS, C ;
    goto  up_date ;
    decf  data_2, F ;
    btfs  data_2, 7 ;
    goto  up_date ;
    clrf  data_1 ;
    clrf  data_2 ;
;
up_date
    call  send_data ;
    call  write_data ;
    call  dly_1 ;
    goto  read_button ;
;
send_data
    movf  data_1, W ;
    movwf temp_1 ;
    movf  data_2, W ;
    movwf temp_2 ;
    movlw 0x40 ;
    addwf temp_2, f ;
    bcf   PORTA, 2 ;cs low
    movlw 0x08 ;
    movwf cnt_1 ;
;
lp_1
    ;send high byte
    bcf   PORTA, 1 ;
    rlf   temp_2, F ;move 1 bit
    btfs  STATUS, C ;
    bsf   PORTA, 1 ;
    bsf   PORTA, 0 ;sclk high
    bcf   PORTA, 0 ;sclk low
    decfsz cnt_1, F ;
    goto  lp_1 ;
    movlw 0x08 ;
    movwf cnt_1 ;
;
lp_2
    ;send low byte
    bcf   PORTA, 1 ;
    rlf   temp_1, F ;
    btfs  STATUS, C ;
    bsf   PORTA, 1 ;
    bsf   PORTA, 0 ;sclk high
    bcf   PORTA, 0 ;sclk low
    decfsz cnt_1, F ;
    goto  lp_2 ;
    bsf   PORTA, 2 ;cs high
    return ;
;
write_data
    movf  data_1, W ;
    movwf EEDATA ;
    clrf  EEADR ;
    call  write_eeprom ;
    movf  data_2, W ;
    movwf EEDATA ;
    incf  EEADR, F ;
    call  write_eeprom ;
    return ;
;
dly_1
    ;delay 0.2 seconds
    clrf  cnt_1 ;
    movlw 0x20 ;
    movwf cnt_2 ;
    decfsz cnt_1, F ;
    goto  lp_3 ;
    decfsz cnt_2, F ;
    goto  lp_3 ;
    return ;
;
lp_3
    return ;
;
write_eeprom
    bsf   STATUS, RP0 ;bank 1
    bsf   EECON1, WREN ;enable to write eeprom
    movlw 0x55 ;
    movwf EECON2 ;
    movlw 0xaa ;
    movwf EECON2 ;
    bsf   EECON1, WR ;start write
;
write_dly
    btfs  EECON1, WR ;
    goto  write_dly ;
    bcf   STATUS, RP0 ;bank 0
    return ;
;
end

```

£50 WINNER

PIC-based frame-check sequence for point-to-point protocol

One of this year's growth areas is likely to be internet-friendly control using the 'point-to-point protocol', or PPP for short, with the popular PIC devices from Microchip likely to lead the way. Although the minimum protocol is relatively straightforward, the generation and verification of the frame check sequence, or FCS, may not be. Here it is as a subroutine in assembler. It is based upon the original 6502 routine¹ and a tidy-up may be in order.

The required 16-bit polynomial is 8408^{2,3}. To transmit, remms and

remls are initially set to all ones (FFFF₁₆) with the 8-bit data byte at 'dat1'. At the end of transmit data, the FCS is ones complemented (inverted) and transmitted remls first, lsb first. For example (one data byte only in case you want to wade through the ones and zeros!):

	remms	remls	dat1	
	FF	FF	79	
	->	EI	C1	
Invert	1E	3E	79	-> transmit this way

To receive, preload remms/lr with

FFFF, and include the FCS bytes in the routine. The remainders remms and remls will be FOB8₁₆ for no detected error.

Graham Stephens
Plymouth
E43

References

1. 'The What and How of CRCs' *Electronics & Wireless World*, Sep 1989
2. 'RFC 1662' - Network Working Group
3. 'X.25' - CCITT Blue Book

Frame-check code for PPP in PIC assembler.

```


**** REGISTER DEFINITIONS*****
cnt1 equ h'10' ;bit per byte
tmp equ cnt1+1 ;was A in 6502
remls equ tmp+1 ;check byte ls
remms equ remls+1 ;ms
polyls equ remms+1 ;polynomial ls
polym equ polyls+1 ;ms
dat1 equ polym+1 ;data byte for crc
;polym/ls could be in-line
;literals 84 & 08 respectively
*****
;Actual Subroutine for one 8-bit byte
crc1:
    movlw h'08' ; 8 bits
    movwf cnt1
    goto crc2
crc2:
    movlw h'00' ; clear
    movwf tmp
    rrf dat1,1 ; lsb into c
    rlf tmp,1 ; and into tmp
    movf tmp,w

```

```

xorwf remls,w
movwf tmp
rrf remms,1
bcf remms,7
rrf tmp,1
btfs status,c
goto crc4
movf tmp,w
xorwf polyls,w
movwf remls
movf remms,w
xorwf polym,w
movwf remms
crc3:
    decfsz cnt1,1
    goto crc2
    return ;stop, get next data
byte
crc4:
    movf tmp,w
    movwf remls
    goto crc3

```

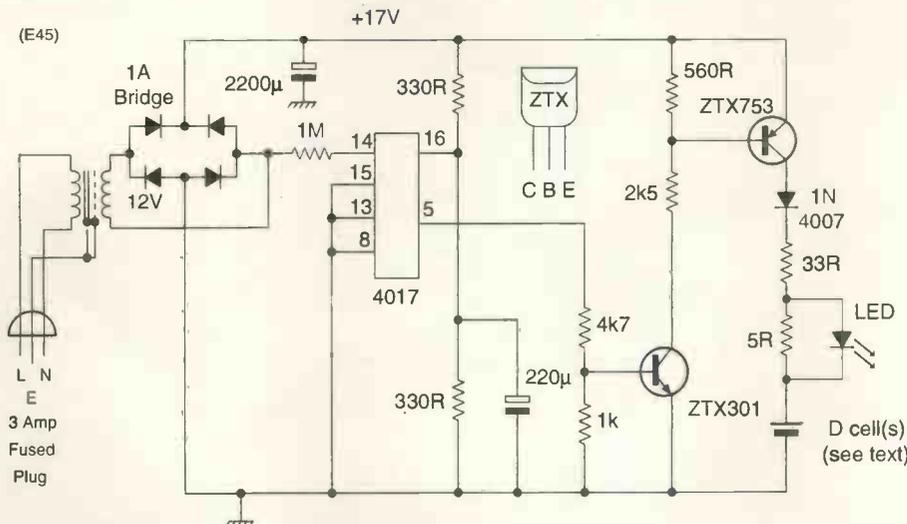

Using a 10:1 duty cycle, this circuit gives new life to tired dry cells.

Pulsed dry-cell charger

This circuit produces a charging current in short bursts with a 10% duty cycle. The average charging current is C/100 where C is the cell capacity. Typical average charge currents of 36mA and 18mA are used for the D-size and the AA-sized cells respectively.

A zinc-carbon cell may be considered as being made up of many smaller parallel connected elements. The pulses of current give each element an increased charging voltage, allowing time for all elements to stabilise.

The CMOS counter 4017 is clocked by the AC supply pulses and

produces one 20 (or 16) ms pulse for each ten AC input cycles at 50 (or 60) hertz. This establishes the duty cycle ratio of 1 to 9. The AC drive at the counter is rectified by the internal IC protection diodes.

The output pulse operates a transistor switch, which connects the cell or battery to the charging supply via the current limiting resistor and indicating LED. The limiting resistor is chosen to give the appropriate average charge current. The ballast resistor is chosen so that the LED flashes to indicate this current.

For D cells a current limiting

resistor of 33Ω and a ballast resistor of 5Ω are used. For AA sized cells 56Ω and 10Ω are used. With a modified current limiting resistor, two or more similar cells can be connected in series, so that a battery can be charged.

I have found that a pulsed charge of twelve to twenty four hours duration or 25% of the original cell's capacity, will greatly rejuvenate weak cycle lamp and personal stereo batteries.

Alkaline cells also benefit, however the total charge given should not be significantly increased,

Warning

Zinc-carbon and alkaline cells can explode due to inappropriate charging, with the potential to cause bodily harm. They may also leak. Take precautions against both of these possible eventualities.

as they tend to be more susceptible to deterioration through over charging.

Michael Mucklow

Newport Pagnell

Buckinghamshire

E45

Simple circuit delivers sinewave with crystal frequency accuracy

This circuit uses a digital clock signal up to 20kHz to produce a sinewave with exactly the same frequency. There are no critical components.

Transistor Tr_1 is switched on and off by the clock signal, see schematic, creating a square wave at node A. The amplitude of the square wave at A is determined by the voltage at point B. The square wave at A is filtered by the band-pass filter built around op-amp IC_1 , this band pass reduces the harmonics of the square wave to a level such that a very usable sinewave is the result.

To counter variation of the amplitude of the resulting sinewave with the component tolerances of the filter network a simple but effective amplitude stabilisation circuit, built around Tr_2 , is used.

When the sinewave's amplitude is small, Tr_2 is permanently off, and the

voltage at node B rises until the amplitude of the square wave at A reaches the designed value. Transistor Tr_2 then periodically draws current out of node B, keeping the sinewave's amplitude constant. At the designed amplitude – a few volts – the influence of temperature on the amplitude is very small.

The clock signal must have a 50% duty-cycle. A low cost divide-by-two IC such as the 74HC74 may be necessary to achieve this.

In many applications a microcontroller can generate the clock signal directly, using a timer function.

Alternatively, a divider with built-in crystal oscillator such as the CMOS 4060 may be used. The band-pass filter has a Q value of 5.


Component values in the schematic give a frequency of 1kHz. For other frequencies, the resistor or capacitor values may be simply scaled. The op-amp must have adequate gain-bandwidth product and slew rate; the LF356 works well up to 20kHz and beyond.

Ivan Moerman

Nazareth

Belgium

E44

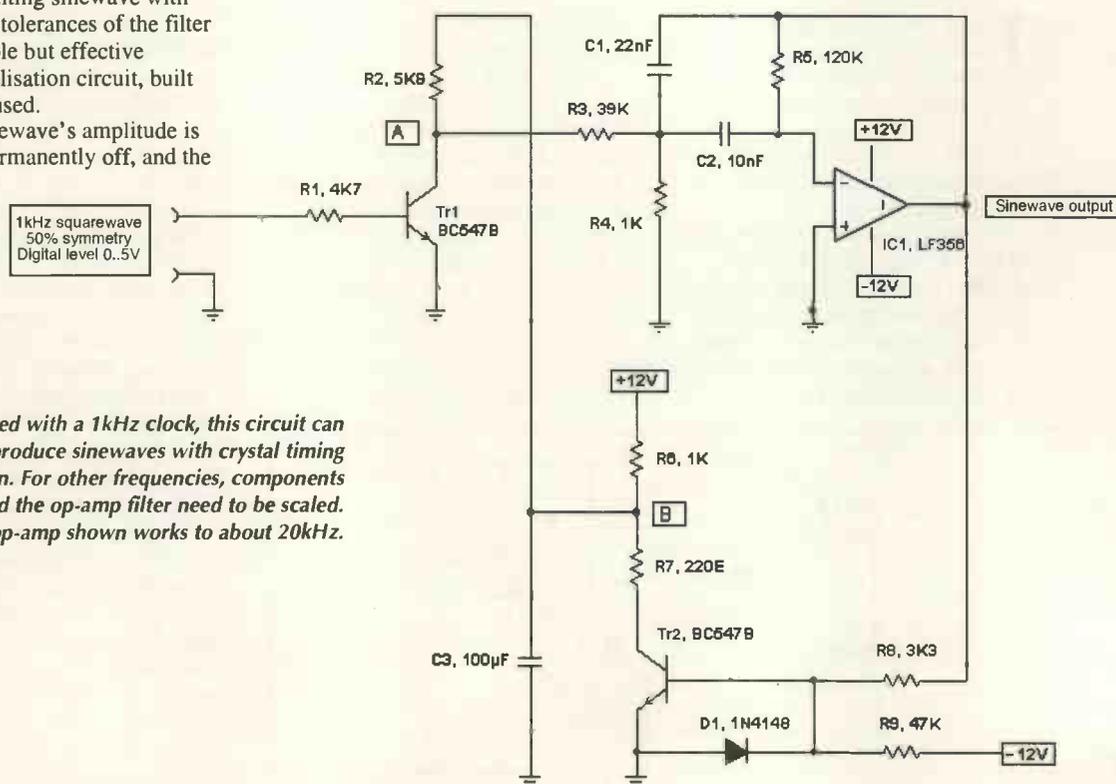

Fed with a 1kHz clock, this circuit can produce sinewaves with crystal timing precision. For other frequencies, components around the op-amp filter need to be scaled. The op-amp shown works to about 20kHz.

£70 WINNER

Automatic input attenuator for radio receiver antennas

An attenuator, located at the aerial input, can greatly reduce cross modulation in communications receivers.

Laurence Cachia has devised a simple magnetic system in which a variable resistor across a tertiary winding on a toroidal core controls the coupling between two signal windings. Subsequent developments involve the use of a FET as a voltage variable resistor to facilitate automatic control.

Attenuating an over-strong signal at the antenna greatly reduces cross modulation in comms receivers. This circuit does the job automatically.

Unless provision is made to minimise drain/source resistance, the amount of attenuation is limited. By driving the FET's gate positive with respect to its source, residual drain/source

resistance can be significantly lowered and performance comes much closer to that achieved with Cachia's original manual control.

In this circuit, the FET is connected across the arms of a bridge formed by Tr_1 , R_1 , and VR_3 . A rising agc voltage of 0V to +0.6V on the base of Tr_1 swings the gate/source voltage of Tr_2 from -2.5V to +2V, thereby maximising the resistance change.

For negative going AGC, the connections to the gate and source of Tr_2 should be reversed, and VR_1 set to increase the bias on the base of Tr_1 . The pre-set resistors can be adjusted to introduce delay and to accommodate different agc


voltage swings.

A ferrite toroid must be used, but its size is not critical. For general coverage receivers, signal windings of six turns on a core with a permeability of 850 will minimise losses at medium and low frequencies.

Turns can be reduced to three for HF receivers, and a lower permeability core could be used. Control windings should have twice the number of turns of the individual signal windings.

Insertion losses are minimal.

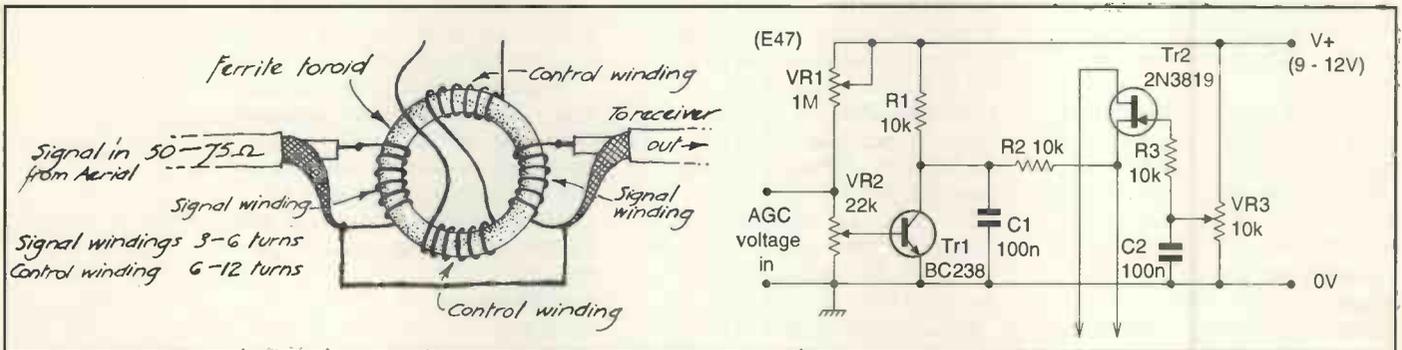Raymond Haigh
Doncaster
South Yorkshire
E4



Versatile power switching circuit

This is a simple circuit that can be used for a wide range of switching or control applications. The purpose of the original circuit was to reduce rotational speed of a small DC motor. The motor drove a 'mirror ball' and was required to turn the ball at 2rev/min.

The same basic circuit can be used to flash a LED or incandescent filament lamp or even dim a filament lamp. All these applications can be realised with two transistors, three resistors, and one capacitor. An added benefit is that the current

consumption can also be made to be extremely small.

The circuit works as a simple proportional control circuit where the ratio of 'on' to 'off' time determines the speed and the effective voltage across the load. Components C_1 and R_2 define the 'on' time while the 'OFF' time is defined by C_1 and R_1 .

The load is connected in the collector of Tr_2 . In the example given, this load is the 10Ω coil resistance of the motor. When 'on', Tr_2 saturates and when 'off', the circuit consumes very little current,


so efficiency is high. This makes the circuit ideal for battery operation with any supply voltage from a single 1.2V NiCd cell up to 24V. Maximum voltage is only limited by the choice of Tr_1 and Tr_2 and of course the motor.

All components are non-critical; in the original application Tr_2 was a small 1A device. Capacitor C_1 should be non-polar. Optimum performance in a given application may require adjustment of the timing by modifying the values of R_1 and R_2 .

If a variable speed drive is required, a potentiometer can be used instead of R_1 . In this case a fixed resistor must be placed in series, to limit the maximum Tr_1 base current.

For microprocessor control, R_1 could be a digital potentiometer IC. For other applications, alarms, beacons, etc., one or more LEDs may replace the motor.

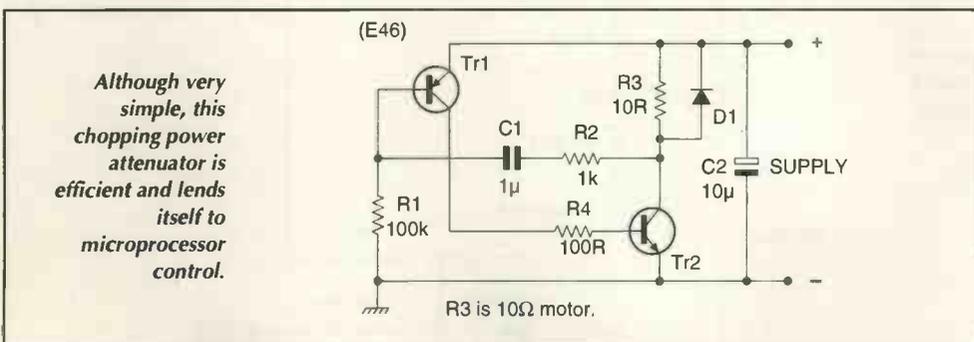Alan Jones
Newcastle-under-Lyme
Staffordshire
E46



Although very simple, this chopping power attenuator is efficient and lends itself to microprocessor control.

LANGREX SUPPLIES LTD

PHONE
020 8684
1166

DISTRIBUTORS OF ELECTRONIC VALVES
TUBES AND SEMICONDUCTORS AND I.C.S.
1 MAYO ROAD • CROYDON • SURREY CR0 2QP
24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS
email: langrex@aol.com

FAX
020 8684
3056

AZ31	£ p	KT66 Special	20.00	5Z4GT	3.00	6U8A	1.50
CL33	15.00	KT88 Special	20.00	6AQ5	2.00	6V6GT	10.00
E88CC	8.50	N78	8.00	6AR5	6.00	6X4	3.00
E180F	3.50	OA2	3.00	6AS7G	7.50	6X5GT	3.00
E610F	20.00	OB2	3.00	6AU5GT	4.00	12A7	3.00
EABC80	4.00	OC3	3.00	6AU6	2.00	12AU7	3.50
EP91	1.50	OD3	3.00	6AW8A	4.00	12AX7	5.00
EBF80	1.50	PCF80	2.00	6B4G	22.00	12AX7A	7.50
EBF89	1.50	PCL82	2.00	6BA6	1.50	12AX7M	6.00
EBL31	25.00	PCL85/805	2.50	6BE6	1.50	12BA6	2.00
ECC33	12.00	PCL86	2.50	6BH6	2.00	12BE6	2.00
ECC35	12.00	PD500	8.00	6BQ7A	2.00	12BH7	10.00
ECC81	3.00	PL36	3.00	6BR7	4.00	12B7A	7.00
ECC82	5.00	PL81	2.00	6BR8	4.00	12DW7	15.00
ECC83	3.00	PL504	3.00	6BW6	4.00	12E1	10.00
ECC85	5.00	PL508	3.00	6BW7	3.00	13E1	85.00
ECC88	6.00	PL509/519	10.00	6BX7GT	7.50	572B	27.50
ECC808	15.00	PL802	4.00	6BZ6	3.00	805	45.00
ECF80	1.50	PY500A	3.00	6C4	2.00	807	7.50
ECH35	3.50	PY800/801	1.50	6C8BA	3.00	811A	10.00
ECH42	3.50	QQV02-6	12.00	6DC6G	5.00	812A	55.00
ECH81	3.00	QQV03-10	5.00	6CL6	3.00	813	27.50
ECL82	5.00	QQV03-20A	10.00	6CG7	7.50	833A	85.00
ECL86	5.00	QQV06-40A	12.00	6CH6	3.00	866A	20.00
ECL1800	25.00	U19	8.00	6CW4	6.00	872A	20.00
EF37A	3.50	UABC80	1.60	6DQ5	17.50	931A	25.00
EF39	2.75	UCL82	2.00	6DQ6B	10.00	2050A	12.50
EF40	4.00	UCL83	2.00	6FQ7	7.50	5687WB	6.00
EF86	5.00	UF89	4.00	6GK6	4.00	5751	6.00
EF91	2.00	UL41	12.00	6J5G	6.00	5763	8.00
EF183/4	2.00	UL84	3.00	6J5M	4.00	5814A	5.00
EL33	15.00	UY41	4.00	6J7	3.00	5842	12.00
EL34	5.00	UY85	2.00	6JB6A	27.50	6072A	6.00
EL34G	5.00	VR105/30	3.00	6JEB6	27.50	6080	6.00
EL36	5.00	VR150/30	3.00	6JS8C	27.50	6146B	15.00
EL41	3.50	Z759	10.00	6K6GT	4.00	6201	8.50
EL84	2.25	Z803U	15.00	6L6G	15.00	6336A	35.00
EL95	2.00	2D21	3.50	6L6GC	17.50	6550A	25.00
EL360	15.00	3B28	12.00	6L6WGB	10.00	6883B	15.00
EL509/519	7.50	4CX250B	45.00	6Q7	3.00	7025	7.50
EM34	25.00	5R4GY	7.50	6SA7	3.00	7027A	26.00
EM81/4/7	5.00	5U4G	10.00	6SC7	3.00	7360	26.00
EN91	7.50	5U4GB	10.00	6SG7	3.00	7581A	15.00
EZ80/EZ81	5.00	5V4G	5.00	6SJ7	3.00	7586	15.00
GZ32	8.50	5Y3GT	2.50	6SK7	3.00	7587	20.00
GZ33/37	15.00	5Z3	5.00	6SL7GT	5.00		
KT61	15.00	5Z4G	6.00	6SN7GT	7.50		

OPEN TO CALLERS MON-FRI 9AM-4PM. CLOSED SATURDAY

This is a selection from our stock of over 6,000 types. Please enquire for types not listed. Obsolete items are our speciality. Valves are new mainly original British or American brands.

Terms CWO/min order £10 for credit cards.

P&P 1-3 valves £2.00, 4-5 valves £3.00

Add 17.5% VAT to total including P&P



CIRCLE NO.120 ON REPLY CARD

WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES (using a video capture card)



"Liesgang diatr" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatr.co.uk

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye).....£37.00 + vat = £43.48

30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole.....£35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses.....£32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle.....£15.97 + vat = £18.76

VSL4022F 4mm F1.22 63x47 degrees viewing angle.....£17.65 + vat = £20.74

VSL6022F 6mm F1.22 42x32 degrees viewing angle.....£19.05 + vat = £22.38

VSL8020F 8mm F1.22 32x24 degrees viewing angle.....£19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle.....£26.43 + vat = £31.06

VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle.....£77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat

1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily.....£7.46+vat = £8.77



Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS

276-278 Chatsworth Road, Chesterfield, S40 2BH.

Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch


Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

CIRCLE NO.121 ON REPLY CARD

FRUSTRATED!

Looking for ICs TRANSISTORS?

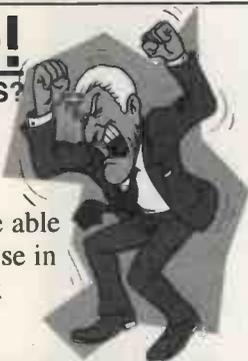A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV
BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
MC MDA J MJE MJF MM MN MPS MPSA MP5H MPSU
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
ZTX + many others

We can also offer equivalents (at customers' risk).

We also stock a full range of other electronic components.

Mail, phone, Fax, Credit Card orders & callers welcome.




Cricklewood Electronics Ltd

40-42 Cricklewood Broadway, London NW2 3ET

Tel:020 8452 0161 Fax: 020 8208 1441

CIRCLE NO.122 ON REPLY CARD

FREQUENCY SHIFTER FOR HOWL REDUCTION

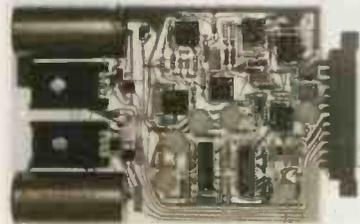

- For public address and sound reinforcement.
- Provides more gain and greater stability.
- 5Hz Fixed Shift Board with mains supply.

- Broadcast Monitor Receiver 150kHz-30MHz.
- Advanced Active Aerial 4kHz-30MHz.
- Stereo Variable Emphasis Limiter 3.
- PPM10 In-vision PPM and chart recorder.
- Twin PPM rack and Box Units.
- PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and movements.

SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh GU6 7BG

Telephone: 01483 275997 Fax: 01483 276477

The only thing scientists agree about on the mobile phone health question is that you cannot rule out the risk factor.

So where does that leave the worried consumer? In limbo for a while yet, says Melanie Reynolds



The fear

Are mobile phones detrimental to human health? This question is likely to trouble us for a very long time. It may be a question we carry on asking forever. For despite numerous studies on the subject, only one aspect of the testing is agreed upon. "One of the things about science is you cannot prove there isn't risk," says Gerd Friedrich, MD of communications industry organisation Forschungsgemeinschaft Funk in Germany.

This means tests that do not show any ill effects are doomed to be repeated to demonstrate there is still no danger. So the message remains that 'the balance of scientific evidence does not suggest that any harm is caused by mobile phone technologies'.

Of course, there have been various reports of studies that do show ill effects, but the scientific community has its rules on research, which have so far meant these studies have been set to one side. The rules mean that before a study is accepted as scientific fact, it must be repeated, with the same results, in other laboratories. To date this has not happened.

"One point we need to bear in mind is that we are dealing with biological organisms and they are notoriously unreliable," explains James Lin, professor of bioengineering at the University of Illinois. "You have to be very cautious and aware of biological variability."

Lin says consistent, dependable and scientific conclusions cannot be drawn yet. He believes that there is no immediate cause for concern. But, "this is the first time in human history that millions of

When do we get the numbers?

It is all very well being told to consider SAR (specific absorption rate) values when choosing a phone, but in Europe they are not available yet. The problem is the standards for testing SARs have not been agreed and are not expected to be available until the middle of this year.

Any SAR values quoted now could have been achieved using one of several test set-ups, all of which can provide vastly different answers.

A CENELEC standard is due this month while an apparently

similar IEEE standard is going through internal voting. But the one to wait for is the IEC document, due early 2001, which draws on both these standards.

"For the first time it looks good that we may have a harmonised standard," comments Camelia Gabriel, director of UK-based Microwave Consultants. "It's very important we get there but it's not an easy task."

Of course once the standard has been agreed the phones must be tested to it. It could be a long time before we see SAR figures which we can legitimately compare.

factor

humans have been exposed to a source of radiation close to the head," continues Lin. "There is no question that microwave radiation can be hazardous to human health. The question is, how hazardous is it?"

The speakers at IBC's 'Mobile phones - is there a health risk?' conference were all keen to illustrate how much time and money is being put into this question on a global basis.

"There is a lot of research. The problem is that a lot of people don't understand the research out there, but it is very well planned," explains Sheila Johnston, neuroscience consultant to the UK mobile phone industry. Sheila illustrated her point with an extremely long list of all the research.

Johnston feels the gap right now is in human research, but believes this area will be addressed by the UK Government's £7m research project announced at the end of last year (see news on 164).

Despite this large amount of money there remains scepticism over the issue of public health and cover-ups. You only need to look at recent history to see why. The tobacco companies are a fine example of an industry cover up, while the UK's handling of BSE (mad cow disease) illustrates political inadequacies all too well.

But Michael Repacholi of the World Health Organisation is convinced this will not happen with mobile phones.

Despite the fact a lot of research is industry funded he says there is a "firewall" which keeps industry at

arms length from the researchers.

"It won't be the tobacco problem," states Repacholi. "The UK Government is more BSE sensitive which may even cause an over reaction in the EMF situation. They might see it as another situation which could get out of control."

Repacholi also believes adopting a precautionary approach to fixing exposure levels is a mistake. In the UK levels fixed by the National Radiological Protection Board were shifted by the Government simply to bring them in line with other countries. According to Repacholi this, "undermines hundreds of millions of dollars of research for no apparent benefit to health".

"It doesn't matter how far politicians reduce levels. It doesn't reduce anxiety. It needs to be based on scientific fact," says Repacholi who believes public confidence will be increased if governments and scientists agree on the health risks. And after all, the alleviation of public concern is what all this is about. ■

EMFacts
Consultancy

EMFacts Consultancy has been in existence since 1994 and has produced over 21 publications/papers dealing with various health issues related to human exposure to Electromagnetic Radiation.

This website was established in 1997 as an independent source of information on the possible health and safety issues arising from human exposure to Electromagnetic Energy (EME).

This consists of both 50 and 60 Hertz (Hz) Electromagnetic Fields (EMF) from our use of electricity and Radio-frequency/Microwave (RF/MW) Electromagnetic Radiation (EMR) from telecommunications.

This site is designed to be utilized as a resource by individuals, groups, organisations and communities who are trying to empower themselves by gaining a better understanding of the complex issues involved with this important environmental issue.

"That which is looked upon by one generation as the apex of human knowledge is often considered an absurdity by the next, and that which is regarded as a superstition in one century, may form the basis of science for the following one." - Paracelsus

Online Resource Information:

● **Mobile Phone Health Hazards:** Over 20 research paper abstracts, articles & press releases on the possible adverse affects of mobile phone use. (Changed 6th June 2000)

There's plenty of background information on mobile phone health hazards at <http://www.tassie.net.au/emfacts/mobiles/iegroup.html>.

Advice on using mobile phones

As a result of the Stewart report on mobile phone health issues in May 2000, the Government agreed a leaflet setting out its advice would be handed out with every mobile phone sold.

The leaflet says there is some evidence that changes in brain activity can occur at levels below the guidelines set internationally for exposure to radio waves, but says it is not clear why. As a result it is taking a

precautionary approach to the use of mobile phones. Its recommendations include:

- Keep your calls short
- Consider relative SAR values when buying a mobile phone
- Do not use a mobile phone when driving, not even if you have a hands-free kit
- Under 16s should use mobile phones only for essential purposes and keep all calls short

Personal voice communications without a licence over a two mile radius for £75, exclusive.

Reader offer

A pair of two-way PMR radios for just £75*

RS 446 personal mobile radio...

To celebrate its launch, new test and instrumentation company Tecstar is offering *Electronics World* readers two RS446 personal mobile radios for just £75 excluding VAT and carriage.

Capable of transmitting and receiving voice over a distance of up to two miles, depending on terrain, the PMR 446 needs no licence. It offers eight channels, scanning – and with CTCSS up to 304 channel combinations.

A backlit liquid-crystal display shows volume level, channel number, sub-channel number, battery level and transmit/receive or channel busy. A unique call feature enables the user to alert the person they wish to contact.

Transmission distance is up to 2 miles. The radio has an accessory socket for an external headphone, earpiece or vox-microphone/headphone combination. A keypad lock and battery save feature are also standard.

The unit measures only 120 by 50 by 20mm and weighs less than 150 grams – including batteries. It is supplied complete with instructions and belt/mounting clip.

Compact, lightweight and low cost, the RS446 wireless personal-communications' hand set has a wide range of applications. These include fetes, events and rallies. Builders on building sites could benefit from these radios, as could exhibitors at exhibitions and staff at warehouses, winter activities, sports events, maintenance departments, schools and care homes. Of course you can also use the RS446 just to keep contact with someone locally. The uses are almost limitless.

Send a cheque or postal orders to Tecstar Electronics Limited, 1 Nuffield Road, St Ives, Huntingdon Cambridgeshire PE27 3LX.
Tel 01480 399499, fax 01480 399503, e mail sales@tecstar.co.uk

Order coupon

Please send me RS446 personal mobile radios, for which I enclose:

For ___ pairs of RS446 radios at £75 per pair _____

Plus VAT at 17.5%, or £13.13 per pair _____

Plus £6 UK postage per order, or £14 overseas _____

Total _____

Fill in your name and address and post this coupon together with a cheque for the total amount above payable to Tecstar to the address below.

Name _____

Address _____

Post code _____

Signature _____

Send cheques, postal orders etc to Tecstar Electronics Limited, 1 Nuffield Road, St Ives, Huntingdon Cambridgeshire PE27 3LX.
Tel 01480 399499, fax 01480 399503, e mail sales@tecstar.co.uk

*excludes carriage and VAT



RS446 key features...

- Up to 2 mile coverage radius
- Scans main and subchannels
- Eight channels, each with 38 sub channels
- Backlit display for night time use
- Unique call function
- Headphone and mic sockets allow discrete use
- Battery status indicator
- Auto battery save feature
- Keypad lock-out

What is CTCSS

CTCSS – or 'continuous-tone controlled squelch system' – allows sub channels of the main channels to be used. There are 38 sub channels to each main channel. Using subchannels decreases the likelihood that someone else will be using the same frequency.

David Huddart's simple time-domain reflectometer is used with a reasonably fast oscilloscope to find faults in cables by transmitting a pulse and analysing its echo. It has been tested with cable lengths up to 200m and can resolve down to 100mm yet it comprises only one IC and a three transistors.

CABLE FAULT LOCATOR

This design was developed for locating faults in coaxial cables. A 'time-domain reflectometer', or TDR for short, sends a brief, very fast edged pulse into a cable and then looks for reflections. If the cable is open or short circuit, a return echo that is twice the transit time of the cable will be observed – a so-called 'go and return' echo. This unit generates the fast

pulses needed and uses any reasonably fast oscilloscope to monitor the activity on the line.

How the circuit works
Schmitt trigger IC_{1A} forms a simple 50kHz oscillator. This is a 74HC part. Output from this oscillator triggers an avalanche pulse generator.

The pulse generator, and its associated voltage clamp, is based

on a previous article about sampling oscilloscopes¹. Pulse transistor Tr₁ is not designed specifically for use in avalanche mode, I found that but several samples of 2N2369, BSX20, and BFR91 all worked reliably in this sort of circuit configuration.

Other transistors such as BC107, BFY50 would not function. I put this down to the fact that the 2N2369, BSX19/20 are all high-

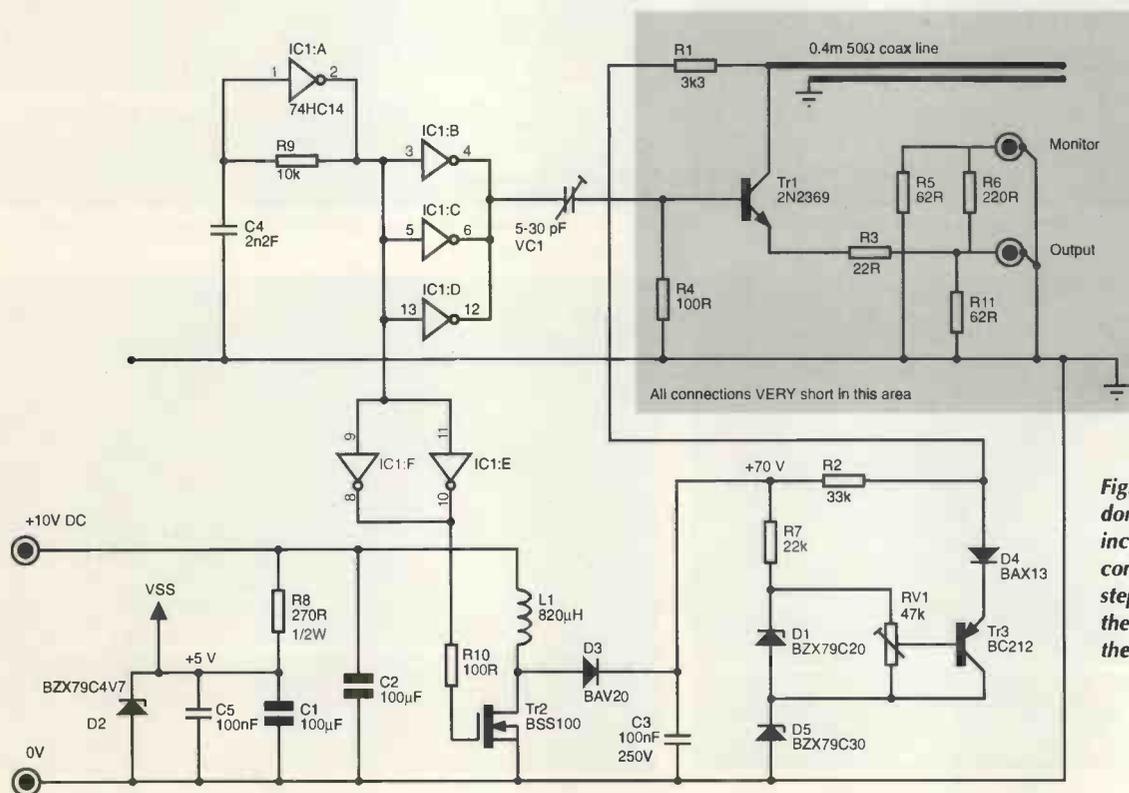


Fig. 1. Circuit of the time-domain reflectometer includes a fly-back converter around Tr₂ to step the 10V supply up to the 70V or so needed for the pulse generator.

speed switching transistors with low V_{ce0} . Ian Hickman's article mentioned in the reference details the operation of the pulse generator but I made a few minor changes:

- The open circuit 50Ω coaxial line is longer so that a pulse of approximately 6ns is generated.
- The trigger pulse feeds Tr_1 via an adjustable capacitor to fine tune the pulse waveform.
- The line charge voltage clamp is modified slightly to allow for the high-voltage supply.

The pulse generator needs at least 70V. Partly because I did not have a suitable bench supply available, I decided to build in a switch mode supply to boost the 10V input to 70V.

This simple power supply is based on the fly-back principle and uses the 50kHz signal

available from IC_{1A} , via $IC_{1E,F}$ to drive a MOSFET, Tr_2 .

During the on-time of Tr_2 , current in L_1 builds to approximately 50mA. When Tr_2 turns off the voltage at the junction of Tr_2, D_3, L_1 'flies' up to be caught by D_3 at the voltage across C_3 . All the energy in L_1 is then dumped into C_3 in about 1μs.

Because the load across C_3 is several tens of kilo-ohms, and the energy being delivered is fixed, the voltage across C_3 rises until all the energy is consumed. Expect between 60 and 100V across C_3 . The actual value is not critical.

Transistor Tr_3 and its associated components form a variable voltage clamp. This stabilises the charge voltage of the line. Adjustment from 30 to 50V is provided by RV_1 .

In operation the open circuit 50Ω line is charged to the preset clamp voltage via R_2 and R_1 . On

the rising edge of the signal feeding VC_1 , current flows into Tr_1 base and starts conduction. The avalanche effect causes Tr_1 to turn on very rapidly and the energy stored in the line is discharged via Tr_1 into R_3 and on to the output.

Resistors R_5 and R_6 form a simple attenuator so that the voltage at the output may be monitored.

Implementing the design
I built the TDR into a small die-cast box and fitted two BNC sockets for the outputs and simple flying leads for the DC power supply.

You can use Veroboard, as I did, but take care to ensure that connections are as short as possible and that decoupling capacitors are close to the source of surge currents. Capacitor C_5 must be a ceramic type and

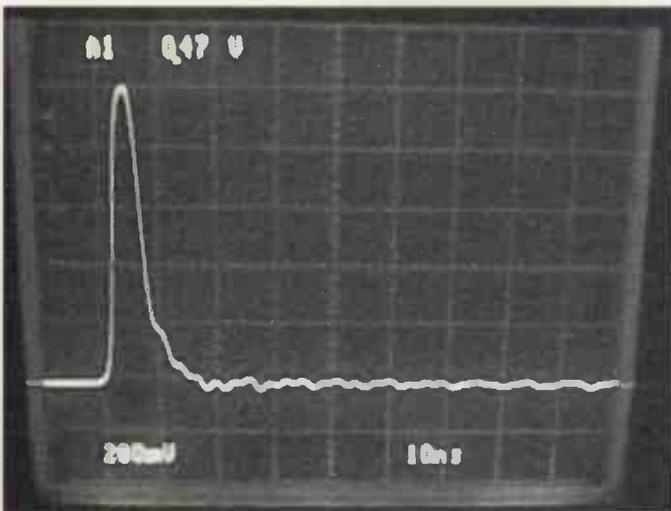


Fig. 2. Output pulse of the instrument with no cable under test connected.

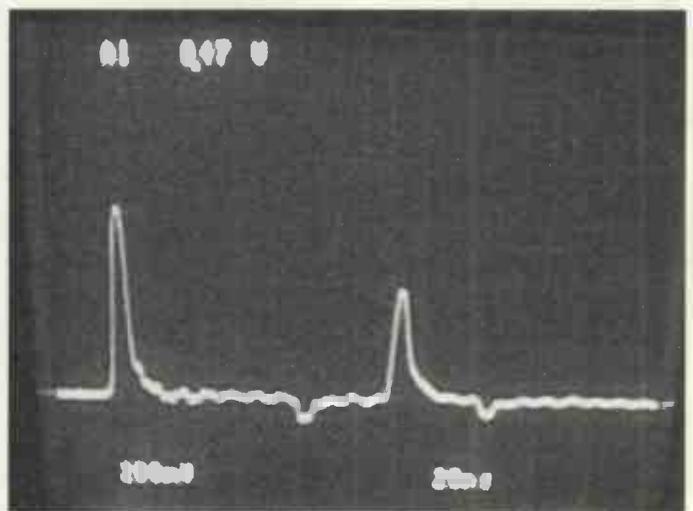


Fig. 4. Reflections from 9m of open-circuit coaxial cable and faulty BNC connector at 6m.

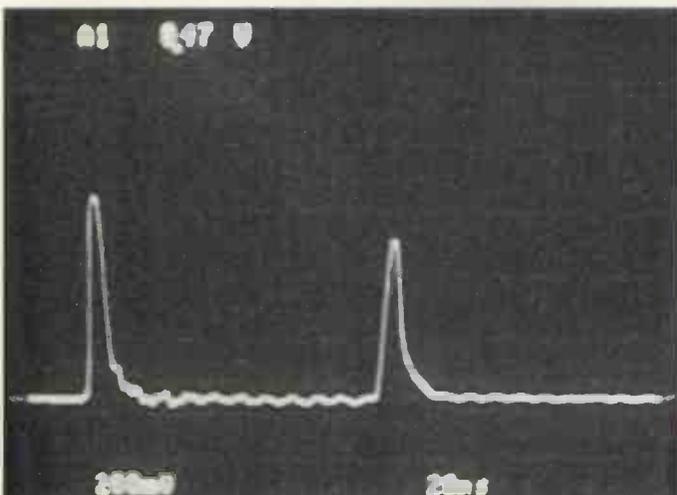


Fig. 3. Reflection from 9m open-circuit coaxial cable.

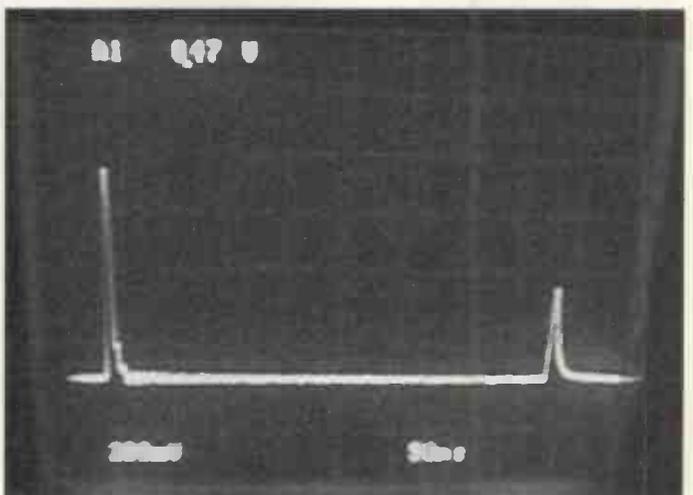


Fig. 5. Reflections from approximately 40m of open-circuit coaxial cable.

connected directly between pins 7 and 14 of IC_1 . Capacitor C_2 should be reasonably close to L_1 and Tr_2 .

Components shown in the dotted area are the heart of the device and must have very short leads – less than 10mm – to minimise inductance. If they haven't, the rise time of the pulse will be affected. I soldered them to the BNC connectors, providing support for Tr_1 on small, insulated, terminals.

The stub line is a length of RG174 miniature 50Ω coaxial cable coiled to fit inside the box. The far end is open circuit.

Setting up

Apply voltage slowly, watching for excessive current flow. Typical consumption is 40mA at 10V. Monitor Tr_2 for activity and the voltage across C_3 . It should be 110V maximum.

Next monitor the output and the collector of Tr_1 . Set VC_1 to maximum and RV_1 to give 30V at Tr_3 's emitter. Now increase RV_1 until the fall time of the voltage at Tr_1 collector suddenly becomes very sharp.

The output waveform is shown in Fig. 2. This is the point where avalanche starts. Increase RV_1 about 4V more and remove the scope probe from Tr_1 's collector.

Now the output should show a very fast rising pulse about 6ns long. Adjust VC_1 to reduce the drive current into Tr_1 's base. This should clean up the falling edge a little reducing the base current after Tr_1 has triggered.


If the output stops altogether, back off the adjustment a little to give reliable operation. This completes the set-up.

Using the meter

For good results, an oscilloscope with a bandwidth of at least 50MHz is required, otherwise the resolution is limited. My scope has a 150MHz bandwidth and 2.3ns rise time. It is easy to resolve length to 100mm.

In operation the oscilloscope is connected to the monitor output using 50Ω coax and terminated at the input to the scope. The cable under test connects to the output.

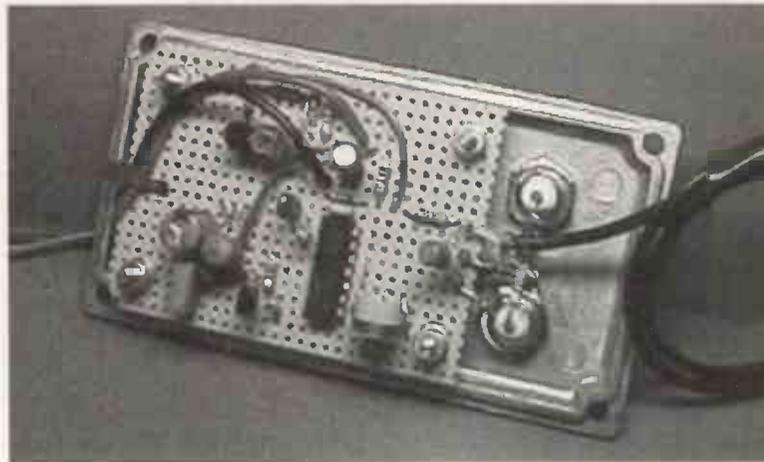The scope should display the transmit pulse and later any returned echo Fig. 3. There will be echoes from any point along the test cable where its impedance changes. Typically this would be



Note short leads around avalanche transistor near the two BNC connectors.

an open or short circuit.

It is surprising how sensitive this TDR is. For example a reflection can be obtained from the change in impedance that 5mm of stub cable connected to a tee causes, Fig. 4. Cable lengths of up to 200m have been tested and reflections easily measured. Figure 5 shows results from a 40m cable.

The polarity of the echo indicates open or short circuit ($>Z_0$ or $<Z_0$) in the cable. Positive echoes indicate high impedance and *vice versa*.

The time delay can be used to estimate the distance down the cable where a fault is,

$$l = \frac{t \times V_c \times C}{2}$$

Where l is the length of cable in metres, t is the time from transmit pulse to echo in seconds, C is the speed of light, at 3×10^8 m/s, and V_c is the velocity coefficient for cable under test.

The velocity coefficient is the ratio of the speed of signals through cable to the speed of light. It varies depending on the exact type of cable but is usually between 0.6 and 0.8. If this coefficient is not known it may be simply calculated using a known length of cable from,

$$V_c = \frac{2l}{t \times C}$$

Measure the round trip delay of a known physical length of cable and calculate V_c .

The TDR has given good service in locating faults in coaxial cable runs, detecting dubious coaxial connections and even measuring the characteristic impedance of an unknown line by adjusting the termination impedance of a length until minimum reflections are

Components

Resistors

1 off R_1	3k3
1 off R_2	33k
1 off R_3	22R
2 off $R_{4,10}$	100R
2 off $R_{5,11}$	62R
1 off R_6	220R
1 off R_7	22k
1 off R_8	270R, 1/2W
1 off R_9	10k

Capacitors

2 off $C_{1,2}$	100μF, 16V
1 off C_3	100nF, 250V
1 off C_4	2n2F
1 off C_5	100nF

Integrated circuits

1 off IC_1	74HC14
--------------	--------

Transistors

1 off Tr_1	2N2369
1 off Tr_2	BSS100
1 off Tr_3	BC212

Diodes

1 off D_1	BZX79C20
1 off D_2	BZX79C4V7
1 off D_3	BAV20
1 off D_4	BAX13
1 off D_5	BZX79C30

Miscellaneous

1 off L_1	820μH
1 off RV_1	47k
1 off VC_1	5-30pF

observed. It is surprising how useful it has become in the workshop ■

Reference

1. Hickman, Ian, 'Towards a 500MHz scope add-on', *Electronics World*, March 2000.

*UK readers and overseas subscribers only

A low-power 555 timer guaranteed to run from supplies down to 0.9V.

Sponsored by UK semiconductor manufacturer Zetex, this month's cover mount is a state-of-the-art version of one of the most successful ICs ever made – the 555 timer. The device is housed in a dual-in-line package and its pin designations are the same as those of the standard 555.

Featuring a very low quiescent current of 74µA, the ZSCT1555 can be powered by any DC supply from 0.9V up to its absolute maximum rating of 6V.

For more applications information and a data sheet, visit

www.zetex.com



This is the DIL version of Zetex's low-power 555 timer. The device is also available in SOIC with the same pin configuration.

Single-cell boost converter

Relative to similar CMOS 555 timers the ZSCT1555 has a lower operating voltage. But more importantly, it can offer a longer battery life.

The circuit shown in Fig. 1 generates a 5V output using a boost topology combined with pulse width modulation to regulate the output voltage to 5V. The ZSCT1555 generates the required 150kHz signal for the PWM circuit.

Inductor L₁, with D₂ and Q₂, allow operation up to very high switching frequency. This speed-up circuit uses active base drive, which minimises switching losses. Schottky diode, D3, used for charge steering is unique. In SOT23 the DC rating of the ZHCS750 at 750mA is exceptional.

The circuit features a ZR431 adjustable shunt regulator in the feedback control loop. This device again offers power economy as its quiescent current is only 35µA – ten times lower than other similar parts.

Extremely low saturation voltage, equating to an on-resistance of only 30mΩ at 300mA, of the FMMT617 switching transistor, Q3, further optimises circuit efficiency.

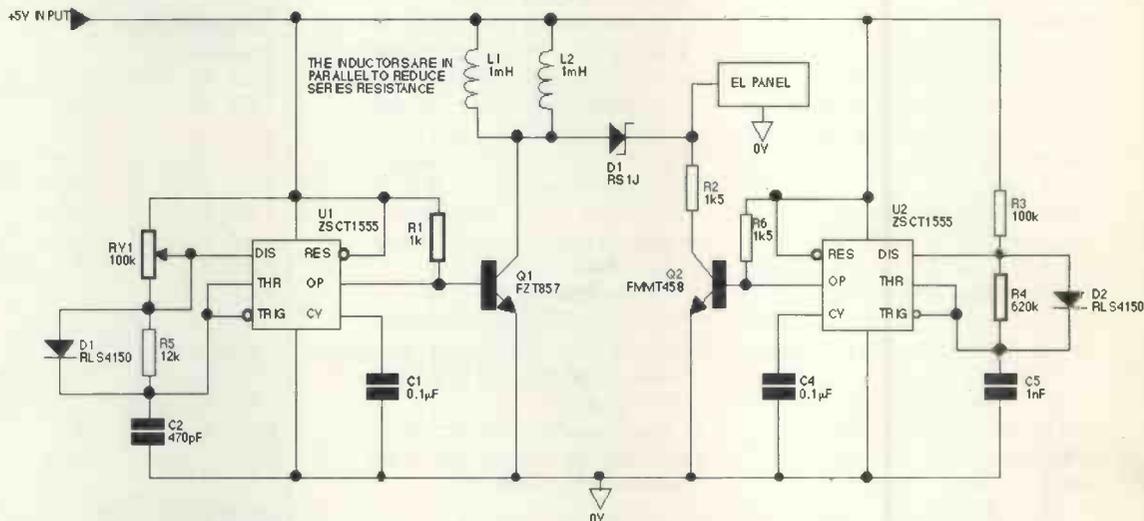


Fig. 2. Electroluminescent display drivers normally need a bulky and heavy transformer. This alternative eliminates the transformer without compromising on efficiency.

Electroluminescent driver

Traditional electroluminescent display driver circuits feature a flyback transformer topology to generate the high AC voltage required to energise the panel. This is expensive – the cost of the transformer and its size, together with a larger PCB area, increases the overall equipment cost.

Eliminating the need for a transformer, the circuit in Fig 2 is more cost-effective. To add to this, the ZSCT1555's low power consumption and the capabilities of the switching transistors make

for a highly efficient solution.

The innovative design uses two combined switching circuits. The first generates a high voltage, approximately 200V, using a 'boost' topology. This voltage is chosen, according to EL-Panel size and brightness, by varying the frequency. Effectively the EL panel behaves like a capacitor. The second circuit converts the high voltage to an 800Hz AC signal to drive the EL-Panel.

The two ZSCT1555 timers form clocks for the switching

transistors. High efficiency is ensured by the switching capabilities of the Zetex bipolar transistors. Advanced transistor design gives the lowest saturation voltage in the switch for the lowest dissipation.

These two application examples highlight the specific advantages of the ZSCT1555 for high-efficiency circuits – namely low supply voltage and low power consumption. This Zetex timer offers advantages to many of the thousands of traditional applications for the 555. ■

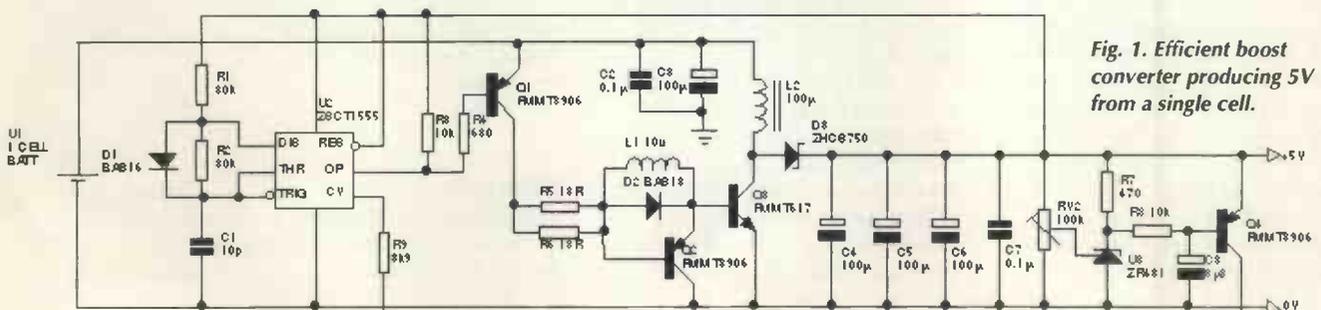



Fig. 1. Efficient boost converter producing 5V from a single cell.

BOOK TO BUY

Completely updated, this comprehensive dictionary contains over 28,000 electronic terms, phrases, acronyms, and abbreviations from the ever-expanding worlds of consumer electronics, optics, microelectronics, computers, communications, and medical electronics. This dictionary is a valuable resource for professionals in the field, hobbyists, students, or anyone interested in electronics.' - Poptronics

Included in this fully revised classic are well over 28,000 terms, phrases, acronyms, and abbreviations from the ever-expanding worlds of consumer electronics, optics, microelectronics, computers, communications, and medical electronics. From the basic elements of theory to the most cutting-edge circuit technology, this book explains it all in both words and pictures. For easy reference, the author has provided definitions for standard abbreviations and equations as well as tables of SI (International System of Units) units, measurements, and schematic symbols.

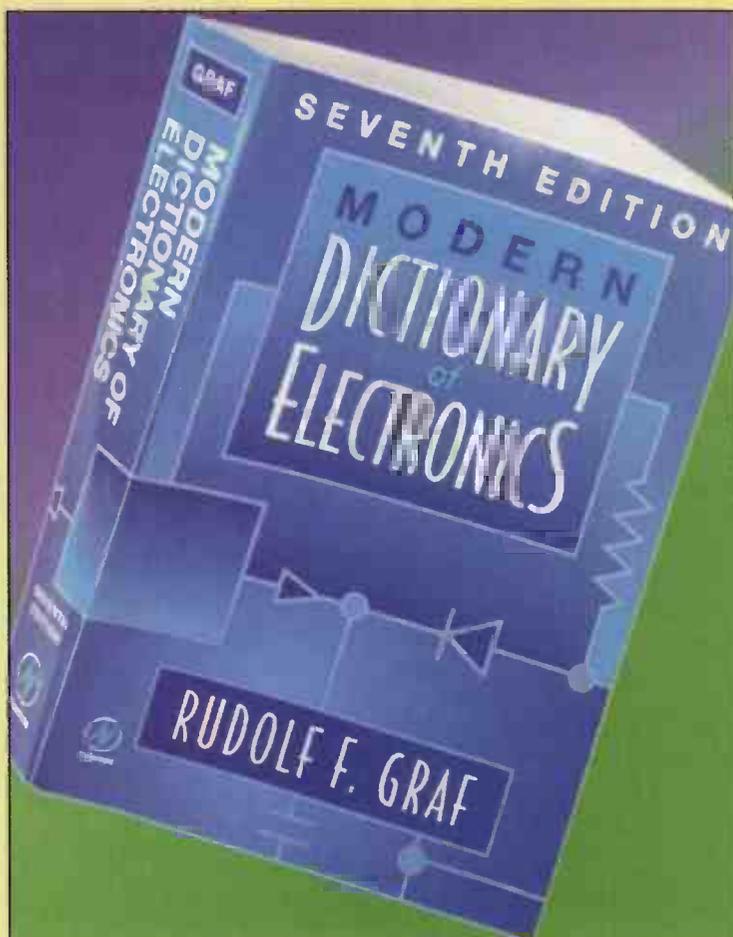Modern Dictionary of Electronics is the bible of technology reference for readers around the world. Now fully updated by the original author, this essential, comprehensive reference book should be in the library of every engineer, technician, technical writer, hobbyist, and student.



Post your completed order form to:-
Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS

Fax your completed order form to 020 8652 8111
UK Price: £42.50 Europe £45.00 ROW £47.50
Price includes delivery

How to pay

Modern Dictionary of Electronics

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____

Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

WEB DIRECTIONS

ACQUIVISION

<http://www.acquivision.com>

AcquiVision solutions, including XY-Plotting, Oscilloscopes (with FFT), Data Logging and Custom Software, have been getting the most from computers since 1994. Download software. Telephone (01903)830502.

AQUILA VISION

<http://www.aquila-vision.co.uk>



Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general interest CD-ROM's.

ALCATEL COMPONENTS

<http://www.components@alcatel.de>

ASHWELL ELECTRONICS

<http://www.ashwell-hq.com>

Ashwell provide technical support for Apex Microtechnology op-amps and DC/DC'S; Aeroflex; EMP filtered connectors; M S Kennedy; Mintech obsolescence; NSC Mil/Aero; Teledyne Relays and isocom mil/optocouplers.

ARCOM

<http://www.arcomcontrols.com/ew/>



A leading international supplier of communication and control technology to industry, Arcom provides leading edge solutions through a comprehensive range of market leading products.

BROADCASTING COMMUNICATIONS SYSTEMS

www.broadercasting.co.uk

WINRADIO now brings you a complete choice in personnel computer controlled

radio scanning and reception solutions ● Broadcast ● Media ● Monitoring ● Professional Amateur Radio communications

BEDFORD OPTO TECHNOLOGY LTD

<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and custom, LED bargraphs, circuit board Indicators, stand offs, transmissive/reflective switches, baseefa optocouplers tubular and surface mount, pannel mount LED assemblies.

CONCEPT ELECTRONICS

<http://www.conceptkey.co.uk>

Concept Keyboards are specialists in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

CONTROL SOLUTIONS

www.controlsolutions.co.uk

Data acquisition and control for beginners, hobbyists, and professionals. Perform mathematical and logical operations on data in real time. Email: info@controlsolutions.co.uk.

COOKE INTERNATIONAL

<http://www.cooke-int.com>
e-mail: info@cooke-int.com



Stockists of Quality Used Electronic Test Instruments and Operating & Service Manuals.

CROWNHILL ASSOCIATES LTD

<http://www.crownhill.co.uk>

Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.



DANIEL MCBREARTY

<http://www.danmcb.demon.co.uk/eng.html>

Experienced engineer based in London, specialist in audio and control systems. Available for design, project engineering or general consultancy. Background of high-quality work.

DESIGNER SYSTEMS CO.


<http://www.designersystems.co.uk>



Electronic product design company with over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.

ECM SELECTION

<http://www.ecmsel.co.uk>

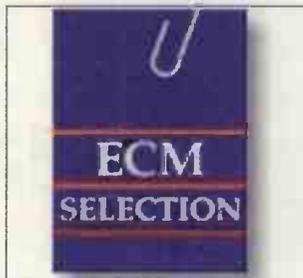

For the pick of the UK's Top High-Tech Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager - £22,000 - £70,000

EDWIN PCB DESIGN SOFTWARE

<http://www.swifteurotech.co.uk>

Swift Eurotech supply the best-selling EDWin CAD/CAE system for PCB design, including schematics, simulation and PCB design. Discounts up to 60% for non-commercial users.

ELECTRONICS AND COMPUTING PRINCIPLES

<http://www.eptsoft.com>

Studying electronics or computing or just want to keep up-to-date in an easy and enjoyable way, then this fully interactive software is for you.

EQUINOX TECHNOLOGIES UK LTD

<http://www.equinox-tech.com>



Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

FLASH DESIGNS LTD

<http://www.flash.co.uk>

Flash supply low cost AVR ISP programmers (£39), MINI-ICE starter kits (from £69), Portable Easy-ICE emulators (from £199), ICE Adapters & 'C' compilers for any ATMEL AVR, MCS51, Dallas, Hitachi H8 microcontroller. Download FLASH NEWS now, Watch out for Special Offers'. ARE YOU developing code in a Flash?

GOOT PRODUCTS

<http://www.kieagoot.co.uk>



Kiea Trading Company is the sole agent of Goot products, We specialise in supplying the soldering and desoldering product range manufactured by Goot Japan for the UK market. Goot uses advanced production technology to manufacture high quality soldering iron products for industrial, professional and general purpose use.

HSPS LTD

<http://dSPACE.dial.pipex.com/hsp/>

FILTER DESIGNER - Advanced analog and digital filter design software for the PC. - Standard and Professional versions. - Free download of Evaluation version.

To reserve your web site space contact Pat Bunce

Tel: 020 8652 8339 Fax: 020 8652 3981

HTB ELEKTRONIK

<http://www.htb-elektronik.com>

We are selling second-hand test & measurement equipment and accessories for over 10 years, from all leading manufactures.

LEVY/LATHAM GLOBAL

<http://www.levylatham.com>

U.S. Military Surplus meters, plug-ins, test sets, oscilloscopes, power supplies, signal generators, spectrum analyzers and radio components from Tektronix, Hewlett Packard, Sony, Phillips and more!

LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

MATTHEY MICROFILTERS

<http://www.microfilters.net>



30 years experience in the design and manufacture of high quality passive filters and delay lines. Used in Broadcast, Telecommunications, Medical, Multimedia, and Computer industries.

MATRIX MULTIMEDIA LTD


www.matrixmultimedia.co.uk



Matrix Multimedia publishes a number of highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

NEWNES - BOOKS FOR THE ELECTRONICS WORLD
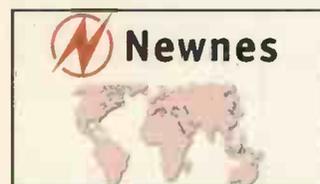
<http://www.newnespress.com>
Over 300 books and information packages



for those working with electronics and engineering technology. Visit our site for a free catalogue and downloads.

NORCALL

<http://www.norcall.co.uk>

Suppliers and repairers of MOBILE RADIO equipment
SALES
HIRE
REPAIR
Huge stocks of used radios and spares
Pye Philips Simoco Icom Kenwood
Standard Clearstone Maxon Yaesu Key Midland.
WE CAN PROGRAM ANYTHING
24hr Service

OMEGA RESEARCH LTD

<http://www.omega-research.co.uk>

"SMD prototyping adapters. Unique, flexible, low cost adapters to allow bench working with SMD devices. Range suits most devices down to 0.5mm pitch."

PCA:PHILIP COLLINS & ASSOCIATES PTY. LTD

<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transceivers from any tone phone.

POLY-FLEX CIRCUITS LTD

<http://www.polyflex.com>

Design, manufacture and population of printed polyester flexible circuits, including Flip Chip on Flex providing practical, low cost, reliable solutions for today's small lightweight products.

QUASAR ELECTRONICS

www.quasarelectronics.com



Over 250 electronic kits, projects and ready built units for hobby, educational & industrial applications.
TEL: 01279 306504, FAX: 07092 203496
or EMAIL: ewsales@quasarelectronics.com

QUILLER ELECTRONICS

<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

RADIOMETRIX

<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use.

RADIO-TECH LIMITED

<http://www.radio-tech.co.uk>

Radio modules, modems, telemetry, audio transmitters, pagers, antenna, remote controls and much more. All UK designed and manufactured.


RALFE ELECTRONICS



professional test & measurement
www.ralfe-electronics.co.uk

RD RESEARCH

<http://www.looking.co.uk/spice>

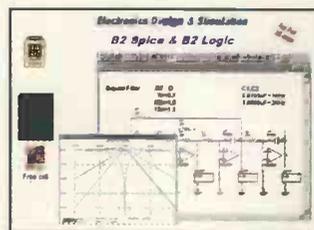

Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.

RS COMPONENTS LTD

<http://rswww.com>



The award winning on-line service from RS
- 110,000+ products available
- Technical data library
- Stock availability check
- Integrated on-line purchasing
- Order by 8pm - with you tomorrow.

SOFTCOPY

<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.



SESCOM, INC.

<http://www.sescom.com>

SESCOM, INC. is a 30-year manufacturer of audio "problem solvers" and transformers. We also offer easily-fabricated aluminum enclosures for small production runs and prototypes.

STAFFORDSHIRE WIRELESS COMPANY


<http://www.staffs-wireless.com>

Wireless, communication, test equipment, bought and sold for very competitive prices visit our web site or telephone John on 01889 569928 or 0973 296461.

SUPRA AUDIO CABLES

<http://www.jenving.se>

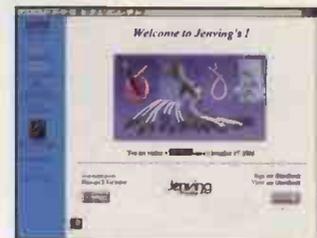Jenving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.



TEMWELL CORPORATION

<http://www.temwell.com.tw>

Manufacturer & Exporter of Heical BPF Filter, 30 Watts BPF Power Filter and Handset/Base Station Duplexers

TEST EQUIPMENT SOLUTIONS

<http://www.TestEquipmentHQ.com>

Quality second user test equipment with full warranty and support. All types of equipment from all leading manufacturers Including general purpose, communications and industrial test.



WEB DIRECTIONS



THOSE ENGINEERS LTD

<http://www.spiceage.com>

Working evaluations of SpiceAge mixed-mode simulator, Spicecycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

THERMOSPEED

<http://www.thermospeed.co.uk>



Temperature and pressure, control and instrumentation. Full on-line purchasing.
 * Overnight ex-stock delivery
 * Create your own hotlist
 * Download datasheets
 * Full technical support

TRIDENT MICROSYSTEMS LTD


<http://www.trident-uk.co.uk>

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

TOWER HILL TECHNICAL SERVICES

<http://www.towerhillaerials.com>

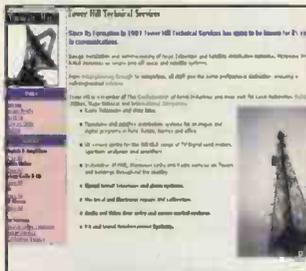Everything you need for DIY Satellite & TV aerial installation. The one stop



shop for TV, FM, Satellite, Amateur Radio PMR Aerials, Distribution Equipment, Cable & Accessories.

TECHNICAL AND SCIENTIFIC SUPPLIES

<http://www.technicalscientific.com>

Suppliers of pre-1985 equipment and components.

- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

VANN DRAPER ELECTRONICS LTD

<http://www.vanndraper.co.uk>

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>

VUTRAX electronic schematic and pcb design system for Windows 95, 98 and NT. Limited Capacity FREE version



downloads available, all upgradeable to various customised levels.

WOOD & DOUGLAS

<http://www.woodanddouglas.co.uk>

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for international telemetry, data, voice & video wireless communications.

UK ELECTRICAL DIRECT

<http://www.uked.com>

For a comprehensive on-line directory, buyers guide and resource locator for the UK Electrical Industry look at this site. Many of the companies listed have links to their own web sites, making this a one-stop shop for a huge amount of information.

UK MAILING LIST GROUP


<http://www.egroups.com/list/uktvrepair>

Following on from the newsgroup discussion last month there is a UK Email group for TV technicians where you can send an Email to everyone in the group. There's just over 30 people in the group at present. For more details and how to register look at the egroup home page. Just a general comment though - you do have to be careful who you give your Email address to so that you can avoid 'spamming' - that is getting lots of unwanted Email about dubious Russian site (amongst others).

REED CONNECT

<http://www.reedconnect.net/>

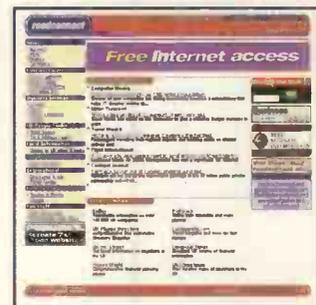Another free internet access site, this time from Reed Business Information. However the site possesses a useful UK



People and Business Finder, with an e-mail search. There's also business news and local information, and some good links to directory sites.

REPAIRWORLD

<http://www.repairworld.com>

Repairworld is a sophisticated US based fault report database which is updated bi-weekly. It operates on a subscription basis and describes itself as an "affordable solution for all technicians". You can see some samples of the material for free, monitors, VCR, DVD and Camcorders being of particular relevance to UK users. The site also provides a "chat room".

To reserve your web site space contact

Pat Bunce

Tel: 020 8652 8339

Fax: 020 8652 398

Put your web address in front of 21 000 electronics enthusiasts and experts. *Electronics World* acknowledges your company's need to promote its web site, which is why we are now dedicating pages in every issue to announce your WEB ADDRESS. This gives other readers the opportunity to look up your company's name, to find your web address and to browse the magazine page to find new sites.

We understand that cost is an important factor, as web sites are an added drain on budgets. But we are sure you will agree that the following rates make all the difference:

FOR 12 ISSUES:
 Lineage only will cost £150 for a full year just £12.50 per month.
 This includes your company's name, web address and a 25-word description.
 Lineage with colour screen shot costs £350 for

a full year, which equates to just £29.17 per month. This price includes the above mentioned information, plus a 3cm screen shot of your site, which we can produce if required.

To take up this offer or for more information ring:

Pat Bunce on 020 8652 8339 or fax on 020 8652 3981. or e-mail: pat.bunce@rbi.co.uk

Company name	Web address


Save 15% Pico ADC42

Virtual oscilloscope

£98
inclusive of VAT
and postage*

*UK only. Overseas readers please fax or e-mail for a quote including delivery charges.

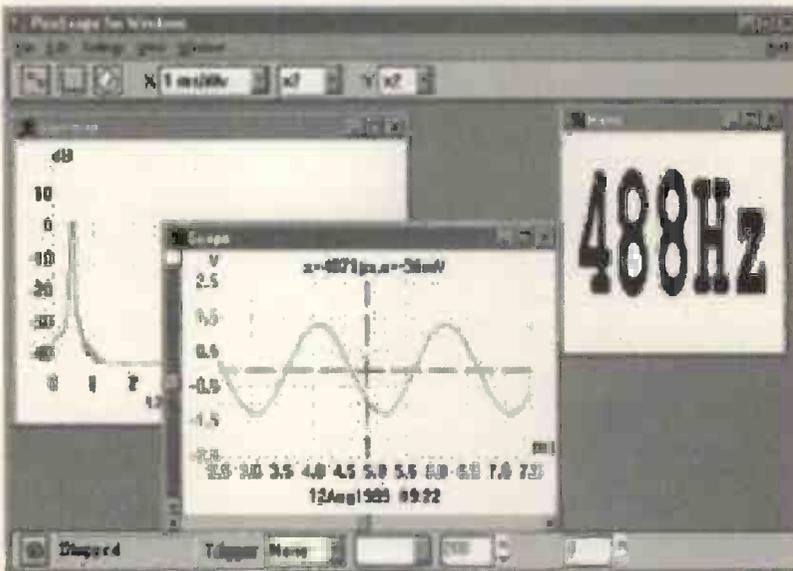Featuring 12-bit resolution and 1MΩ input impedance, the ADC42 samples at up to 15kS/s and includes software for spectrum analysis, oscilloscope functions and frequency display. Plugging into a PC's LPT port, the unit provides large, colourful displays and all the usual timebases and trigger options – all in a case slightly larger than a matchbox.



ADC42 single channel oscilloscope

- Low cost and easy to use
- No power supply required
- Ultra compact design
- Oscilloscope and data logging software included
- Write-to-disk on trigger function standard

The ADC42 is a single-channel pc based virtual instrument. Simply plug the unit into the parallel port of your pc and run the software. Designed for analysing low-frequency signals, it provide all the functionality of a conventional scope at a fraction of the price.

The ADC42 has 12-bit resolution making it suitable for applications where detection of small signal changes is needed.

Specifications

Scope timebases	500µs/div to 50s/div
Spectrum analysis	100Hz to 10kHz
Max sampling	15ksample/s
Voltage range	±5V
Resolution	12 bit
Channels	1 BNC
I/P impedance	1MΩ, dc coupled
Accuracy	1%
PC connection	D25 to PC parallel port
Power supply	Not required

Use this coupon to order your ADC42

Please send me ADC-42(s) at the special offer price of £98 fully inclusive of VAT and recorded UK delivery, normal selling price £111.63 excluding postage.

Name _____

Address _____

Phone number/fax _____

Total amount £.....

I enclose a cheque _____

Please charge to my credit/debit card.

Card type (Master/Visa/Switch etc)

Card No _____

Expiry date ____ / ____

Please mail this coupon to *Electronics World*, together with payment. Alternatively fax credit card details with order on **0181 652 8111**. Address orders and all correspondence relating to this order to Pico Offer, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. email jackie.lowe@rbi.co.uk
Make cheques payable to Reed Business Information Group.

Letters to the editor

Letters to "Electronics World" Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS
e-mail jackie.lowe@rbi.co.uk using subject heading 'Letters'.

B-class Class B

In reply to James Bongiorno's in the February 2001 issue's Letters section, I must admit that I was not aware that the problem of crossover distortion in Class-B output stages had been completely solved thirty-five years ago. Looks like we're all out of step except Jim.

If Mr Bongiorno feels he has solved a problem that has defeated thousands of engineers, I think we might expect some details, perhaps even a circuit diagram and some test results.

Since I am not quite so ignorant about diodes in output stages as Mr Bongiorno seems to think, I would like to go

straight for the jugular and ask what quiescent current is required to make his scheme work properly? Linearity is easy to achieve with amperes of current flowing – but this does not constitute solving the Class-B problem.

I am also unmoved by a THD figure of less than 0.01% at 20kHz, as most versions of the Blameless amplifier can achieve this: many of them do much better. The 'load-invariant' version gives 0.004% at 20 kHz while driving 3Ω.

What exactly are the advantages of a dual-differential input stage? The normal pair gives a differential input, and

you cannot make an input more differential than differential can you?

I am perfectly aware that complementary amplifier topologies exist, and given the time, it would be interesting to analyse them properly.

However, the disincentive is that they look unpromising in two areas: maintaining exact I_c balance of the input pair, and maintaining a well-defined current through the output stage bias generator. Both are absolute requirements for good linearity. Perhaps Mr Bongiorno has solutions to these problems.
Douglas Self
London

that it spreads the values as uniformly as possible logarithmically across the decade.

If you calculate the error in the ratio of each value to its neighbour compared with the ideal 12th root of 10, you will find that any other sequence is worse. In fact, the biggest error is 1.5, not 3.3, and changing 3.3 to 3.2 is too close to 2.7 and too far from 3.9.

Hence I suggest that whoever devised the sequence really did a very good job.

Kenneth Gundry
San Francisco

Speaker performance

Speaking as an engineer who has devoted all his working life to the misguided notion that loudspeakers could be improved by careful design, innovation and

the application of new technologies, I have to take issue with at least one of John Watkinson's statements in his article 'Baffling the speaker buyer'.

In particular, I take issue with the statement referring to the low value of drive units; "...built down to a cost like this, the performance is not going to be special". The cost of manufacturing any object is fundamentally based on four things; the value of raw materials, the ease of manufacture, the cost of labour and number of objects produced. 'Special performance' does not figure in this calculation.

Although good design costs a little more than bad design, cost is of no more relevance to the sound quality of a loudspeaker drive unit than it is to the writing ability of a ball-point pen.

How John can be saddened by purchasers of expensive audiophile cables I just don't understand. He clearly applies their criteria to his selection of drive units.

John's comment that, "CAD reduces costs, but does little for

LF communications

It is with some pleasure that I see real 'wireless' making a return to *Electronics World*, in the article entitled 'Comms at 136kHz' on page 16 of the January issue.

As it happens, the UK is a relatively active region in this area of the amateur radio spectrum. Much of the contact between the widely-spread adherents is conducted via the RSGB's LF Group reflector on the Internet.

Unfortunately, much of the comment in the article about the band is a little dated. There is a growing band of enthusiasts in Europe, Canada, the USA, Australia and New Zealand who are investigating this fascinating region of the radio spectrum again.

While a lot of our initial work was based on guidance from early books like the pre-war Admiralty Handbook, we have progressed rapidly and are probing some of the forgotten corners of technology. Litz wire, and basket weave coils, not considered by your contributors, have proved to still have advantages.

Several UK stations have constructed and operate stations running several hundred watts

output. This has enabled the Atlantic to be spanned for the first time on this frequency by an amateur signal in September this year. It was done using an ERP of just less than 1W.

Skywave or ionospheric propagation is not only available at night and there are regular instances of contacts over 1200km during daylight hours. Fortunately, as amateurs we do not have to maintain a commercial quality channel, so the exploitation of sporadic events at these frequencies adds greatly to the interest.

The UK 73kHz band has not been closed, as was stated in the article. The licence variation holders have been awarded a further three years use of this band.

Alan Melia G3NYK
Ipswich
Suffolk

Radio interference generator?

I stared with disbelief at your recent presentation of the Circuit Ideas prize to a 'radio interference generator' (p. 892 November 2000 issue), using a technique that does not work, to circumvent the EMC regulations.

Moving the frequency of a

poorly designed switching regulator around so that it does not stay in the spectrum analyser bandwidth long enough to register, does not make the amplitude of the interference any less. It merely spreads to misery.

Alan Melia

E, fancy that

Referring to Letters in the December 2000 issue, I suggest that Mr Wells has not thought about the issue of resistor E ranges enough.

I don't know who devised the system, but presumably the object was to find a series of resistor values with nominally 10% tolerance such that the ranges of adjacent values just touched. A moment's calculation indicates that this will involve 12 or 13 per decade, and 12 was chosen.

We would therefore like each value in the series to be related to the previous one by the 12th root of 10. We would also like each value to be readily expressed. In practice, this means to only two significant figures.

If you try to devise a series meeting these criteria, I think you will soon conclude that the present one is the least bad, in

performance," is just a little absurd. Try it out on Ron Dennis and he'll give you the same answer that I would.

A few caveats wouldn't have gone a miss in the article. Some of us really are trying quite hard to improve things.

Stuart Poort
Brighton

Remote satisfaction

The article 'Remote control the easy way' in the December 2000 issue immediately caught my attention because of the simplicity of the hardware. I already had a Sony remote control for my video, a spare infra-red receiver and an 8051 development board.

I connected the IR receiver to the 8051 board. Because of the broad header pulse and the convenient frame rate, I was able to view the waveform on my oscilloscope using TV frame triggering. The waveform did not match the published diagram though. But after some head scratching, I realised that the published waveform was a mirror image of the oscilloscope's display.

After I began to write the software, I had to do a lot more head scratching before I discovered that my oscilloscope had been set to 'invert', which was why the polarity of my CRO display appeared to agree

with the diagram in the article. The output of the IR detector is normally high.

After solving those problems, it didn't take too long to finish a program to select one of two LEDs as in the article. I then modified it to control the volume on my 20 year old TV set, and loaded it into an Atmel AT89C2051, which I mounted on a small piece of Veroboard.

The project was very satisfying. Thank you for the article. Interested readers can view the source code on my web site:

<http://www.users.bigpond.com/alphaelectronics>.

Ross Willson
Sydney
Australia

Amplifier for electrostatics?

High-voltage, high-power transistors, such as CRT deflection transistors, exist. Two examples are the MJL16218 and S2000AF.

Can anyone tell me if a high-voltage, low-distortion transistor amplifier capable of driving electrostatic loudspeakers directly has ever been designed? If not, does anyone think that such an amplifier would be feasible using such transistors?

Ged Landon
via e-mail

An unskilled generation

With regard to Simon Wright's article 'Exploiting Third World skills', in the January issue, the problem is not a shortage of electronics graduates. The problem is that British companies don't train people.

I have had a degree in Communication and Electronics since 1993 and I am still unemployed. I have only been able to find short-term temporary work from time to time. Of course, reading newspaper jobs sections will reveal many jobs for electronics engineers, but they all require five years experience.

There are very few training positions. The few that do exist usually want recent graduates with a 2.1 or above.

The real problem is not immigration policy. It is that two generations of school and university leavers have grown up unemployed and we have finally run out of skilled workers.

Malcolm Lisle
Gateshead

Is crossover not over?

I was surprised that cross-over distortion can still generate a heated exchange in your columns. I refer to 'Better buffers rebuffed' in February 2001 issue.

For me the problem was largely solved for me by L M Shaw's article in *Wireless World*, June 1969, and the refinement proposed by Peter Baxandall in *Wireless World* for the following September.

Then came the very elegant 'current-dumping' configuration used in the Quad 401. I think this design also originated from Baxandall.

I think the editor should not be afraid to use his blue pencil on comments about correspondents' life styles, and whether they choose to be troglodytes or not. A lot of internet material, mostly from the USA, shows how low things can sink if not moderated.

As cross-over is rather old-hat, perhaps Mr Bongiorno would like to turn his talents to help America find means to reduce its green-house gas production without too much pain for its population?

Justin Underwood
Much Marcle
Herefordshire

Justin, when contributors to the letters pages make unnecessarily harsh or derogatory criticisms, I remove them. However, if I feel that derogatory criticisms are justified, or might give readers a flavour of their author's character, thus adding information to the message being conveyed, I leave them in. Did you notice how Dave Kimber didn't respond in kind? Ed.

What is sky-scattered sunlight?

I have a couple of questions that I would like to put to your readers.

Colour television, based on the British PAL system, started in Australia in 1975. The bible of TV, recommended to all the technicians was 'Colour Television: The PAL System', by G N Pratchett. It was first published 1967 by Norman Price, London.

My question has to do with the colour of TV white, normally called 'illuminant D', which has a colour temperature 6500 kelvin. Pratchett says this is the colour temperature of "sky-scattered sunlight" and/or "sky-scattered daylight".

What do these terms mean and are they the same thing? Does it mean the light reflected off a white sheet of paper

placed in the open shade?

Where in Britain was it measured? I've heard Scotland or Wales mentioned.

Gary Yates
Sydney
Australia

Boobs


Two errors appeared in redrawn circuit diagrams in the February 2001 issue. Apologies to you, and to the authors concerned.

On page 134, in the digital metal detector circuit, the device marked IC₃ should be a 7490 – not a 555.

In the CMOS frequency tripler on page 140, the 47pF capacitor should be in the series path to the left of the shunt branch containing the 1μH inductor rather than to the right of it. The circuit will not work as shown. ■



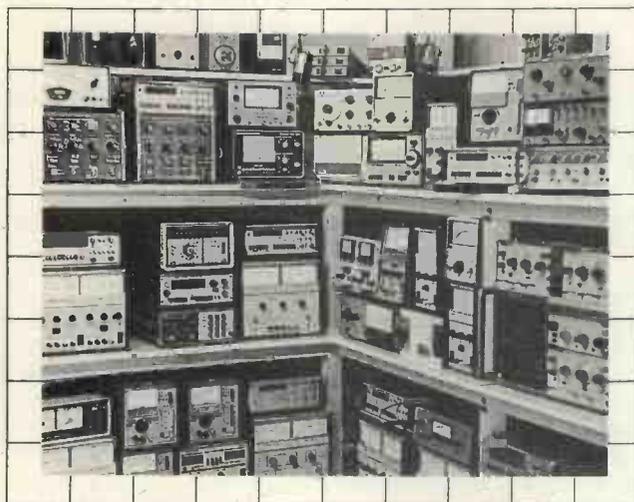SUPPLIER OF QUALITY USED TEST INSTRUMENTS



Cooke International

Unit Four, Fordingbridge Site, Barnham,
Bognor Regis, West Sussex, PO22 0HD, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>


E-mail: info@cooke-int.com

catalogue available

CIRCLE NO. 123 ON REPLY CARD



OPERATING & SERVICE MANUALS

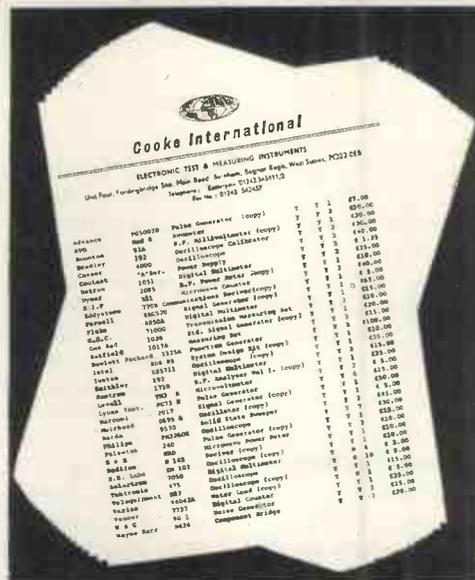

Cooke International

Unit Four, Fordingbridge Site, Barnham,
Bognor Regis, West Sussex, PO22 0HD, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457

Web: <http://www.cooke-int.com>

E-mail: info@cooke-int.com

catalogue available

CIRCLE NO. 124 ON REPLY CARD

ADVERTISERS' INDEX

BETA.....	162	LANGREX.....	223
CONFORD.....	167	PICO.....	203
COOKE INTERNATIONAL.....	238	QUICKROUTE.....	162
CRICKLEWOOD.....	223	MILFORD INST.....	210
CROWNHILL.....	183	RAMCO.....	167
DISPLAY ELECTRONICS.....	207	RD RESEARCH.....	167
DATAMAN.....	OBC	SEETRAX.....	210
EPTSOFT.....	IBC	SIGHTMAGIC.....	203
INTEC ASSOCIATES.....	162	SURREY ELECTRONICS.....	223
JOHNS RADIO.....	179	TELNET.....	IFC
JPG ELECTRONICS.....	223	TEST EQUIP SOLUTIONS.....	169
KOMPASS.....	240	TIE PIE.....	205
LABCENTER ELECTRONICS.....	193	WEB PAGES.....	232, 233, 234

As an advertiser you can be certain that your sales message is going to be read by decision-making electronics professionals with the power to purchase your products.

Service

Link

The pre-paid rate for semi-display setting is £17 per single column centimetre (maximum 4cm). Box number £22 extra. All prices plus 17½% VAT. All cheques, postal orders etc to be made payable to Reed Business Information. Advertisements together with remittance should be sent to Electronics World Classified, 12th Floor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Fax: 0208 652 3981. Tel: 0208 652 8339

ARTICLES WANTED

Rack Enclosures

New and Used most sizes
16U to 50U side and rear panels
mains distribution 19" Panel mounts
optima eurocraft. Prices from £45 +vat

M&B Radio

86 Bishopsgate Street Leeds LS1 4BB
Tel. 0113 2702114 Fax. 0113 2426881

BEST CASH PRICES PAID

For valves KT88, EL37, DA100,
PX25 and complete collections.
Please ask for our wanted list.
**WIDE RANGE OF VALVES &
OBSOLETE CRT STOCKED**

E-mail: sales@BEL-Tubes.co.uk

Tel: 01403 784961 Fax: 01403 783519
Billington Export Ltd., Sussex RH14 9EZ
Visitors by appointment please

TOP PRICES PAID

For all your valves,
tubes, semi conductors
and ICs.

Langrex Supplies Limited

1 Mayo Road, Croydon, Surrey CR0 2QP
TEL: 020 8684 1166 FAX: 020 8684 3056

SERVICES

POWER SUPPLY DESIGN

Switched Mode PSU
Power Factor Correction
designed to your specification

Tel/Fax: 01243 842520

e-mail: eugen_kus@cix.co.uk

Lomond Electronic Services

FOR SALE

RF DESIGN SERVICES

All aspects of RF
hardware development
considered from
concept to production.

WATERBEACH ELECTRONICS

www.rlaver.dial.pipex.com

TEL: 01223 862550

FAX: 01223 440853

**Do you have a
web site?**

**Then why not let
our readers
know about it.**

**See our web
section on pages
232, 233, 234**

From Concept To Production

Electronic design and engineering services
for the new millennium

- Embedded control
- Telecommunication products
- Datacommunication products
- SM PSU and battery management
- Wireless transmission systems
- Audio and Video processing
- DVD control systems
- Internet site and graphics authoring
- PCB design
- Schematic layout and re-drawing
- Technical documentation & translation

Tel/Fax: +44 (0) 1872 223306
Email: sales@designersystems.co.uk



LINEAGE

FREE to collector, two carphones, Motorola 4800X and NEC TR5E1320-11A with handsets but no leads. Phone David Martin 01279 506212.

WIRELESS WORLD magazines for sale, 1976 to 1999, please telephone/fax S. Jacovides 020-7272 7139 or e-mail: jacovides@btinternet.com

QTY Electronic Equipment, Components, Data Books etc. £550 ono. Tel/Fax 01280 848626.

APPOINTMENTS

SOFTWARE AND SYSTEMS ENGINEERS (Two Posts)

Daresbury Laboratory, Warrington, Cheshire

The Council for the Central Laboratory of the Research Councils (CLRC) at its Daresbury Laboratory, in North Cheshire, operates the UK National Synchrotron Radiation Source (the SRS). Based around a complex of three particle accelerators (Linac, Booster Synchrotron and Storage Ring) it provides world-class research facilities to a large user community from academic institutions and industry.

The Electronics and Controls Group provides design, development and operational support to maintain the SRS as a world-class facility. This includes an extensive programme of development on the SRS Control System, which is based on PC clients and embedded servers. In addition there are ongoing developments in distributed control system design, control of power converters and digital signal processing of beam position detectors.

Two vacancies exist in the Electronics and Controls Group; one as a Software Engineer and the second as a Systems Engineer. The Software Engineer will have responsibilities for application software development in C, Visual Basic and Object Orientated languages, development of databases and web page generation. The System Engineer will have responsibilities for the design of embedded systems, software and hardware, system design and interfacing to equipment.

Candidates should have a good honours degree in physics, computer science, electronic engineering or a related discipline. Knowledge of software design and experience in programming is essential while exposure to real time OSs, Linux, Microsoft Windows development, Visual Basic or C is desirable. Previous experience with VME systems, embedded systems, network protocols or Unix would be advantageous. The ability to work effectively within a team is essential. Further information about this post is available from Mark Heron. Tel: (01925) 603210 or email m.t.heron@dl.ac.uk

The salary range is between £18,620 and £26,600. Further progression is dependent upon performance. A non-contributory pension scheme, flexible working hours and a generous leave allowance are also offered.

Application forms can be obtained from: Recruitment Office, Human Resources Division, Daresbury Laboratory, Daresbury, Warrington, Cheshire, WA4 4AD. Telephone (01925) 603864 quoting reference VND047/01. More information about CLRC is available on the worldwide web at <http://www.clrc.ac.uk>

All applications must be returned by 14 February 2001.

The CLRC is committed to Equal Opportunities and to achieving the Investors In People standard.

A no smoking policy is in operation.



CLRC

COUNCIL FOR THE CENTRAL LABORATORY
OF THE RESEARCH COUNCILS

**Please Mention Electronics World
When Replying to advertisements**

Need directing to filters...


cables, connectors or sockets?

Whatever your business needs find it on kompass.com.

WWW.KOMPASS.COM

1.5 million companies worldwide at your fingertips.

Telephone: +44(0)1342 335876.

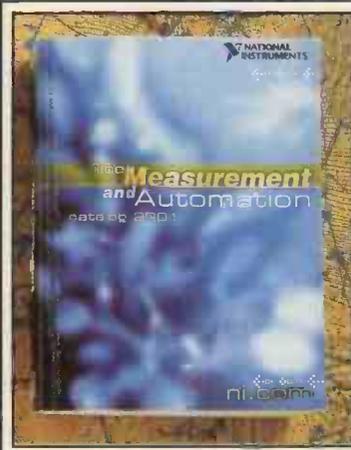

The National Instruments Measurement and Automation Catalogue 2001 is the leading resource for engineers and scientists seeking the most effective customer-defined measurement and automation solutions. The catalogue details the complete line of NI products with comprehensive tutorials, product specifications and selection advice - all designed to help engineers and scientists develop integrated networked measurement and automation applications.

Tel: 01635 523545

Fax: 01635 524395

E-mail: info.uk@ni.com

Web: www.ni.com/uk

CIRCLE NO.125 ON REPLY CARD

Hioki's New 8807/8808 Memory Recorder

These compact, light recorders have 2 or 4 analogue channels with isolated inputs, PC card slot, fax/modem communication function, versatile trigger functions and 3-way power. They are ideal for a variety of applications requiring long memory lengths and high transient speed capability.

Telonic Instruments Ltd
Tel: 0118 978 6911
Fax: 0118 979 2388

CIRCLE NO.126 ON REPLY CARD

ELECTRONICS WORLD is the longest established magazine in the industry, with a history of over 80 years.

The editorial is the most respected in the industry, presenting ideas to innovate and improve products.

For all your advertising needs

Call Pat 0208 652 8339

E-mail: Patbunce@rbi.co.uk

CIRCLE NO.127 ON REPLY CARD

How would you like to advertise in a marketplace where your products and services will be seen by the right people?

Then why not be seen in Electronics Weekly's classified section, ARENA?

If you would like further information, contact Denise Stupart on:

020 8652 3034

CIRCLE NO.128 ON REPLY CARD

'Electronics and Computing Principles V7'

'95, '98, NT or 2000 Principles V7'

Studying electronics or computing or just want to keep up-to-date in a easy and enjoyable way, then this fully interactive software is for you.

visit eptsoft.com or telephone for full details of more than a thousand menu items.

Electronics:-

Atomic Structures, DC Current flow, Basic Electronics, Simple DC Circuits, Types of Switching, Variable Voltages, Ohm's Law, DC Voltage, DC Current, Series/Parallel Resistors, AC Measurements, AC Voltage and Current, AC Theory, RCL Series/Parallel Circuits, Capacitance, Capacitors, Inductance, Inductors, Impedance, Communication System, Signals, Attenuators, Passive/Active Filters, Tuned Circuits, Coupling and Selectivity, Oscillators, Circuit Theorems, Diode Theory, Diode Applications, Transistor Theory, Bipolar Transistor, Transistor Configurations, Transistor Circuits, Field Effect Transistors, Operational Amplifier Theory and Applications, Sum and Difference Amplifiers.

Electrical:-

DC and AC Power, SCR, Power Supplies, Voltage Regulators, Magnetism, Motors/Generators, Transformers, Three Phase Systems.

Digital Techniques:-

Logic Gates, Flip Flops, Combinational Logic, Counters, Counting, Shift Registers, Logic Interfacing, Timers, Boolean Algebra and DeMorgan's Theorems.

Microprocessors and PIC Microcontrollers:-

Basic Micro-Computer, Busses, A.L.U, Clock and Reset, Instructions and Control, Memory Cells, ROM and RAM, Memory Addressing, Instructions, PIC Introduction, PIC16F84 Architecture, PIC16C71 A/D, Byte, Bit, Literal and Control Instructions.

Personal user £99.95 +VAT
Education £299.95 +VAT
(Includes unlimited multi-user site licence.)

Measurement and Component Testing:-

Analogue multi-meter, Measurement, Component Testing.

Mathematics:-

Simple Numbers, Number Types, Roots, Triangle Ratios, Triangle Angles, Area, Surface Area and Symmetry, Volume, Percentages, Ratio's, Fractions, Vectors, Circle Angles, Laws, Algebra Rule, Powers, Simplifying, Equations, Graphing, Slope and Translation, Physics, Angles, Complex Numbers, Statistics, Lottery Number Prediction, Physical Science.

Computer Science:-

Hardware Devices, Data Structures, Data Files, Binary Numbers, Binary Arithmetic.

Toolbox:-

DC Calculations, AC Calculations, Numbers, Applications.

Self-Assessment Questions:-

DC, AC, Power, Semi-Conductors, Op-Amps, Digital, Mathematics.

Components and Equipment Picture Dictionary:-

High quality digital camera images and explanatory text.

ELECTRONICS LAB (Optional add-on hardware).

eptsoft limited. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.


Tel: +44 (0)1376 514008. Fax: +44 (0)870 0509660. Email: info@eptsoft.com.

Switch, Delta, Visa and MasterCard accepted.

No additional postage or airmail charges.

STILL THE WORLD'S MOST POWERFUL PORTABLE PROGRAMMERS?

£495+VAT

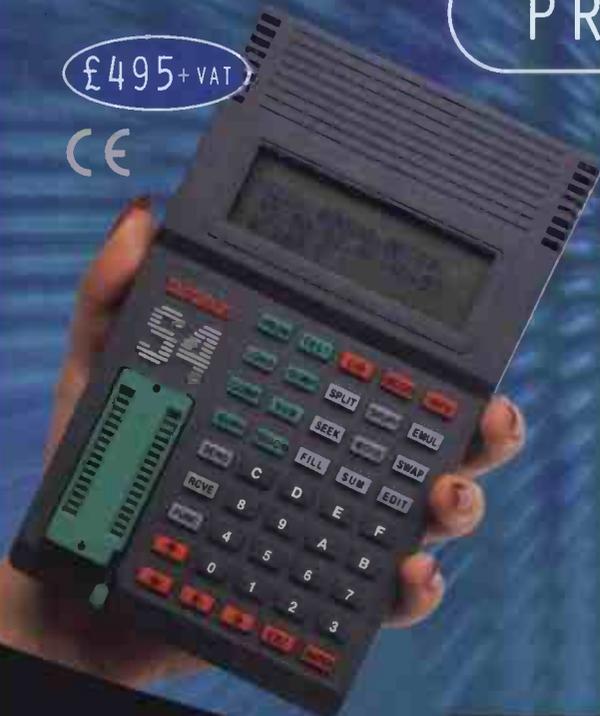

CIRCLE NO. 103 ON REPLY CARD

NEW MODEL



£795+VAT

SURELY NOT.
SURELY SOMEONE SOMEWHERE HAS
DEVELOPED A PORTABLE PROGRAMMER
THAT HAS EVEN MORE FEATURES, EVEN
GREATER FLEXIBILITY AND IS EVEN
BETTER VALUE FOR MONEY.

ACTUALLY, NO. BUT DON'T TAKE OUR
WORD FOR IT. USE THE FEATURE
SUMMARY BELOW TO SEE HOW OTHER
MANUFACTURERS' PRODUCTS COMPARE.

DATAMAN - 48LV

- Plugs straight into parallel port of PC or laptop
- Programs and verifies at 2, 2.7, 3.3 & 5V
- True no-adaptor programming up to 48 pin DIL devices
- Free universal 44 pin PLCC adaptor
- Built-in world standard PSU - for go-anywhere programming
- Package adaptors available for TSOP, PSOP, QFP, SOIC and PLCC
- Optional EPROM emulator

DATAMAN S4

- Programs 8 and 16 bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 microcontrollers and more
- EPROM emulation as standard
- Rechargeable battery power for total portability
- All-in-one price includes emulation leads, AC charger, PC software, spare library ROM, user-friendly manual
- Supplied fully charged and ready to use

S4 GAL MODULE

- Programs wide range of 20 and 24 pin logic devices from the major GAL vendors
- Supports JEDEC files from all popular compilers

SUPPORT

- 3 year parts and labour guarantee
- Windows/DOS software included
- Free technical support for life
- Next day delivery - always in stock
- Dedicated UK supplier, established 1978

Still as unbeatable as ever. Beware of cheap imitations. Beware of false promises. Beware of hidden extras. If you want the best, there's still only one choice - Dataman.

Order via credit card hotline - phone today, use tomorrow.

Alternatively, request more detailed information on these and other market-leading programming solutions.

MONEY-BACK 30 DAY TRIAL

If you do not agree that these truly are the most powerful portable programmers you can buy, simply return your Dataman product within 30 days for a full refund

hotline
01300 320719



Orders received by 4pm will normally be despatched same day.
Order today, get it tomorrow!

DATAMAN

Dataman Programmers Ltd, Station Rd,
Maiden Newton, Dorchester,
Dorset, DT2 0AE, UK
Telephone +44/0 1300 320719
Fax +44/0 1300 321012
BBS +44/0 1300 321095 (24hr)
Modem V.34/V.FC/V.32bis
Home page: <http://www.dataman.com>
FTP: [ftp.dataman.com](ftp://ftp.dataman.com)
Email: sales@dataman.com