

OFFER! – low-cost versatile oscilloscope

ELECTRONICS WORLD



MAY 2001 £2.80

**Chip capacitors
investigated**

**/O via
Ethernet**

Fuel cells


Biosensors

**New thoughts
on EMC**

**DSP hardware
design**

Circuit ideas:

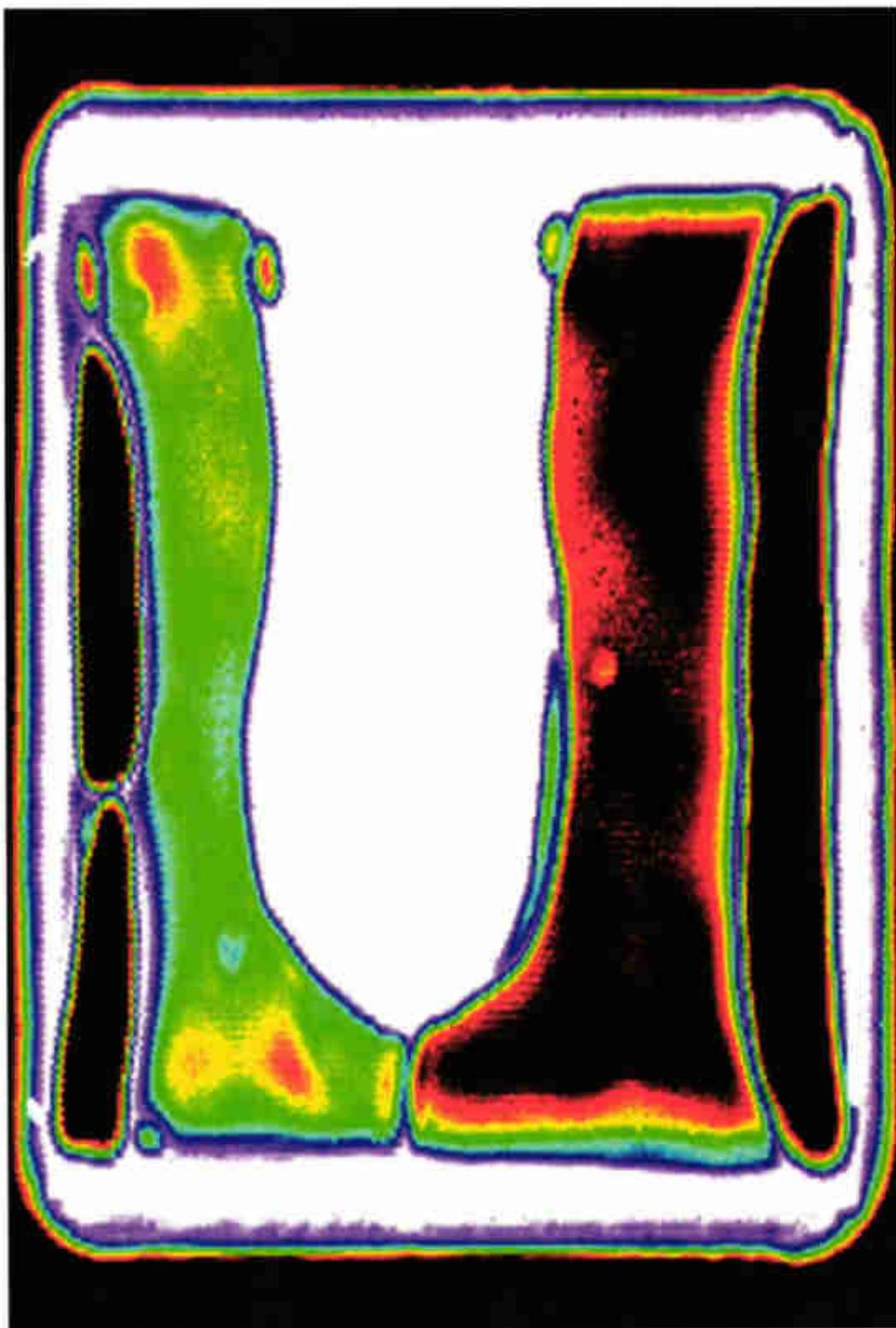- battery short protector
- LED as photodiode
- digital signal generator
- DR stabilised oscillator
- log control from linear pot.
- base-line clamp



Telnet

Tel: 02476 650702

Quality second-user test & measurement equipment

NEW PHONE CODE FOR COVENTRY 02476

Hewlett Packard	
8642A - high performance R/F synthesiser (0.1-1050MHz)	£4750
3335A - synthesiser (200Hz-81MHz)	£2200
Hewlett Packard	
436A power meter and sensor (various)	from £750
437B power meter and sensor (various)	from £1100
Hewlett Packard	
Marconi 6310 - programmable sweep generator (2 to 20GHz) - new	£2750
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£3500
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£5750
Hewlett Packard	
5370B - universal time interval counter	£1500
Hewlett Packard 8662A synth. sig. gen. (10kHz to 1280MHz)	£8250
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	£2500
Hewlett Packard 3314A Function Generator 20MHz	£1250
Hewlett Packard	
8904A Multifunction Synthesiser (opt 2+4)	£1950
R&S SMG (0.1-1GHz) Sig. Generator (opts B1+2)	£2950

OSCILLOSCOPES


Gould 400 20MHz - DSO - 2 channel	£800
Gould 1421 20MHz - DSO - 2 channel	£600
Gould 4068 150MHz 4 channel DSO	£1500
Gould 4074 100MHz - 400 Ms/s - 4 channel	£1350
Hewlett Packard 54201A - 300MHz Digitizing	£995
Hewlett Packard 54500A - 100MHz - 2 channel	£750
Hewlett Packard 54502A - 400MHz-400 MS/s 2 channel	£1600
Hewlett Packard 54810A 'Infinium' 500MHz 2ch	£4000
Hewlett Packard 54520A 500MHz 2ch	£3000
Hameg 205-2 20MHz DSO	£550
Hitachi V152/V212/V222/V302B/V302F/V353F/V550B/V650F	from £125
Hitachi V1 100A - 100MHz - 4 channel	£900
Intron 2020 - 20MHz. Dual channel D.S.O. (new)	£450
Iwatsu SS 5710/SS 5702 -	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lecroy 9314L 300MHz - 4 channels	£3000
Meguro M50 1270A - 20MHz - D.S.O. (new)	£450
Philips PM3094 - 200MHz - 4 channel	£1750
Philips 3295A - 400MHz - Dual channel	£1600
Philips PM3392 - 200MHz - 200Ms/s - 4 channel	£1995
Philips PM3070 - 100MHz - 2 channel - cursor readout	£750
Tektronix 465 - 100MHz - Dual channel	£350
Tektronix 464/466 - 100MHz - (with AN. storage)	£350
Tektronix 475/475A - 200MHz/250MHz -	from £450
Tektronix 468 - 100MHz - D.S.O.	£650
Tektronix 2213/2215 - 60MHz - Dual channel	£350
Tektronix 2220 - 60MHz - Dual channel D.S.O.	£995
Tektronix 2235 - 100MHz - Dual channel	£600
Tektronix 2221 - 60MHz - Dual channel D.S.O.	£995
Tektronix 2245A - 100MHz - 4 channel	£900
Tektronix 2440 - 300MHz/500 MS/s D.S.O.	£2450
Tektronix 2445A/2445B - 150MHz - 4 channel	£1000
Tektronix 2445 - 150MHz - 4 channel + DMM	£1200
Tektronix TAS 475 - 100MHz - 4 channel	£995
Tektronix 7000 Series (100MHz to 500MHz)	from £200
Tektronix 7104 - 1GHz Real Time - with 7A29 x2, 7B10 and 7B15	from £2500
Tektronix 2465/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix TDS 310 50MHz DSO - 2 channel	£750
Tektronix TDS 320 100MHz 2 channel	£850
Tektronix TDS 340A 100MHz DSO - 2 channel	£1250

SPECTRUM ANALYSERS

Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£850
Anritsu MS 610B 10KHz - 2GHz - as new	£3500
Anritsu MS3606B (10KHz-1GHz) network Analyser	£3500
Advantest/TAKEDA RIKEN - 4132 - 100KHz - 1000MHz	£1500
Hewlett Packard 8756A/8757A Scaler Network Analyser	from £1000
Hewlett Packard 853A Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2750
Hewlett Packard 182T Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2250
Hewlett Packard 8568A (100Hz - 1500MHz) Spectrum Analyser	£3500
Hewlett Packard 8567A - 100Hz - 1500MHz	£3995
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£5995
Hewlett Packard 8754A - Network Analyser 4MHz-1300MHz	£1500
Hewlett Packard 3561A Dynamic signal analyser	£3995
Hewlett Packard 35660A Dynamic signal analyser	£3250
Hewlett Packard 8753A (3000KHz-3GHz) Network An.	£3500
IFR A7550 - 10KHz-1GHz - Portable	£1950
Meguro - MSA 4901 - 30MHz - Spec. Analyser	£700
Meguro - MSA 4912 - 1MHz - 1GHz Spec. Analyser	£995
Tektronix 2712 Spec. Analyser (9kHz - 1.8GHz)	£3750
Wandel & Göttermann TSA-1 system analyser (100Hz-180MHz)	£2750
Wiltron 6409 - 10-2000MHz R/F Analyser	£1750

Radio Communications Test Sets

Marconi 2955	£1500
Marconi 2955B/60B	£3995
Marconi 2955A	£2000
Marconi 2955R	£2200
Marconi 2945 Comms service monitor	£4500
Anritsu MS55A2	£1200
Hewlett Packard 8922B (GSM)	£4000
Hewlett Packard 8920A (opts 1,2,3,4,5,11)	£5250
Hewlett Packard 8920B (opts 1,4,7,11,12)	£7250
Hewlett Packard 8922M	£6000
Schlumberger Stablock 4031	£3500
Schlumberger Stablock 4040	£1500
Racal 6111 (GSM)	£1750
Racal 6115 (GSM)	£3995
Rhode & Schwarz CMTA 94 (GSM)	£4995
Rhode & Schwarz CMT 55 (2GHz)	£8000
Rhode & Schwarz CMT 90 (2GHz) DECT	£4995
Wavetek 4103 (GSM 900) Mobile phone tester	£1500
Wavetek 4106 (GSM 900, 1800, 1900) Mob. Phone tester	£2200

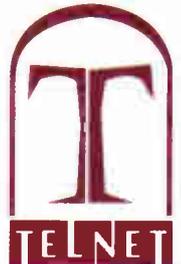

Fax 02476 650 773

MISCELLANEOUS

Eaton 2075-2A - Noise Gain Analyser	at £2750
EIP 548A 26.5GHz Frequency Counter	£1995
ENI 440LA (150KHz-300MHz) 35 Watt Power Amp	£2500
ENI 1040 (10KHz-500KHz) 400 Watt Power Amp	£2750
Fuke 5100A/5100B/5200A - Calibration Units (various available)	from £1000
Fuke 2620 Data Buckets	£500
Fuke 45 Dual Display M/meter (IEEE)	£550
Hewlett Packard 339A Distortion measuring set	£1200
Hewlett Packard 778D Dual-Directional Couplers	£650
Hewlett Packard 3488A - Switch/Control unit	£250
Hewlett Packard 3457A multi meter 6 1/2 digit	£950
Hewlett Packard 3784A - Digital Transmission Analyser	£4500
Hewlett Packard 3785A - Jitter Generator & Receiver	£1250
Hewlett Packard 5385A - 1 GHz Frequency counter	£650
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6622A - Dual O/P system p.s.u.	£1250
Hewlett Packard 6624A - Quad Output Power Supply	£2000
Hewlett Packard 6632A - System Power Supply (20v-5A)	£800
Hewlett Packard 8350B - Sweep Generator Mainframe	£1500
Hewlett Packard 8656A Synthesised signal generator	£850
Hewlett Packard 8656B Synthesised signal generator	£1250
Hewlett Packard 8657A Synth. sig. gen. (0.1-1040MHz)	£1750
Hewlett Packard 8901B - Modulation Analyser	£2750
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1250
Hewlett Packard 16500A + B - Logic Analyser Mainframes	from £1000
Hewlett Packard 16501A/B + C - Logic Analyser System Expander Frame	from £2000
Hewlett Packard 37900D - Signalling test set	£3750
Hewlett Packard 83220A DCS/PCS test sets	£3000
Hewlett Packard 8657B - 100KHz-2060 MHz Sig Gen	£3995
Hewlett Packard 8657D - XX DQPSK Sig Gen	£4500
Hewlett Packard 8130A - 300 MHz High speed pulse generator	£5250
Hewlett Packard 4275A LCR Meter (10KHz-10MHz)	£3250
Hewlett Packard 4276A LCZ Meter (100Hz-20KHz)	£1500
Marconi 1066B - Demultiplexer & Frame Alignment Monitor (140MBIT to 64KBIT)	
NEW	
Marconi 2305 - modulation meter	£1750
Marconi 2610 True RMS Voltmeter	£999
Marconi 6950/6960/6960B Power Meters & Sensors	£550
Marconi 2840A 2Mbit/s Transmission Analyser	from £400
Philips 5515 - TN - Colour TV pattern generator	P.O.A.
Philips PM 5193 - 50MHz Function generator	£1400
Leader 3216 Signal generator 100KHz - 140MHz - AM/FM/CW with built in FM stereo modulator (as new) a snip at	£1500
Racal 1992 - 1.3GHz Frequency Counter	£795
Rohde & Schwarz NRV dual channel power meter & NAV Z2 Sensor	£500
Systron Donner 6030 - 26.5GHz Microwave Freq Counter	£1250
Tektronix ASG100 - Audio Signal Generator	£1995
Wavetek 178 Function generator (50 MHz)	£750
Wayne Kerr 3245 - Precision Inductance Analyser	£950
Wayne Kerr 6245 - Precision Component Analyser	£1995
	£2500

All equipment is used - with 30 days guarantee and 90 days in some cases
Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate,
Coventry CV3 2SF.

CIRCLE NO. 101 ON REPLY CARD

Tel: 02476 650 70
Fax: 02476 650 77

323 COMMENT

Killing fields – recognition at last

324 NEWS

- Electronics skills shortages
- Cambridge firm in optical disk link up
- Firms team up to make superchip
- Amstrad profits plummet
- Patent bounty hunters pay \$40 000
- New CO sensor made in UK
- Technology halves mobile antennas
- Metallic superconductor
- Ford cars to have electronic telematics
- New 1kHz to 30MHz oscillator IC

330 CHIP CAPACITOR FLAWS INVESTIGATED

Ralph Carbone and **Tom Adams** provide a unique insight into the failure modes of ceramic chip capacitors.

334 DESIGN COMPETITION

Time to get your entries in! Our design competition – with £900 worth of prizes – closes 30 April.

336 PC INTERFACE VIA ETHERNET

Connecting external devices to your PC via a local-area network card is not as difficult as it may seem. **Eddy Insam** explains how it all works and what you need to know.

350 QUENCHING PROCESSOR THIRST

The quest for performance in today's mobile world means that high power consumption is the curse of chip designers. But plenty of solutions exist. **Richard Ball** reports.

354 SPEAKERS' CORNER

Moving-coil loudspeakers are invariably driven by a voltage amplifier. Here, **John Watkinson** explores the alternative – current drive.

356 PHONO-PREAMP FOR THE CD ERA

Power supply problems and solutions are the subjects of this second article describing **Norman Thagard's** high-performance, pick-up preamp.

362 FUEL CELLS

Chris Evans-Pughe investigates fuel cell technology and its implications.

367 NEW PRODUCTS

New product outlines, edited by **Richard Wilson**

378 CURRENT CONVEYORS III

In this third and final article on low-voltage current-conveyors and their applications, **Giuseppe Ferri et al** describe how to implement capacitance multipliers.

382 CIRCUIT IDEAS

- Battery pack short-circuit protector
- Voltage-controlled μ C-based sig. gen.
- 12V battery level detector
- LDR stabilised Wien bridge oscillator
- Use an LED as a photodetector
- Baseline clamp
- Log control from a linear pot

389 LETTERS

EMC, Skill and training, More choice on FM, Valve substitute, A true dome tweeter, Phono preamp debate

391 NEW THOUGHTS ON EMC



Ian Darney presents a new approach to EMC with a view to demystifying the subject.

395 BIOSENSORS: ELECTRONICS MEETS BIOLOGY

Biological materials combined with traditional transducers allow substances to be analysed much more rapidly than is possible using conventional laboratory techniques. **David Clark** reports.

400 WEB DIRECTIONS

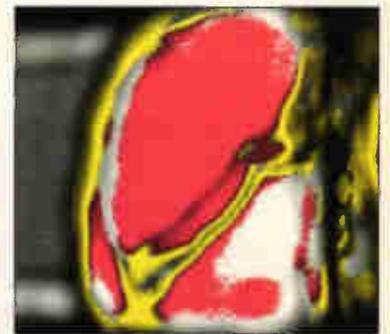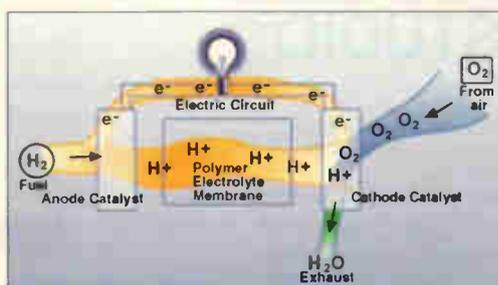
Useful web addresses for the electronics engineer.



Acoustic imaging provides a unique insight into chip capacitor failure mechanisms – page 330.



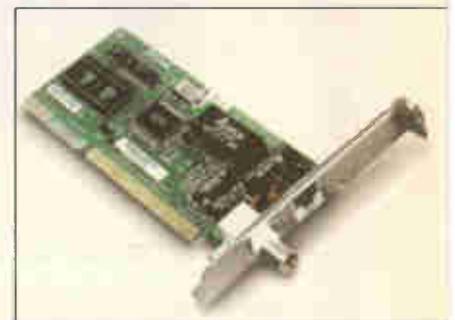Reader offer – 10MHz single-trace oscilloscope. Turn to page 353 for details.



Ethernet – 10Mbit/s over a long length of coaxial cable and very cheap to implement. Wouldn't it be nice to use it for i/o? See page 336.

New generation power sources – a fuel cell can power a mobile phone for 20 days and it takes only seconds to recharge. See page 362.

June issue on sale 3 May

b² Spice 2000

Analogue and digital circuit design for the PC



Design and test circuits quickly and easily

Packed with new features:

- Uses the latest **xspice** engine for guaranteed accurate mixed mode simulation
- Parameterised ac sweep • Monte carlo analyses
- Parameterised transient sweep
- New **xspice** simulations • New noise and distortion analyses
- Improved features for processing plot families as units
- New menu items to show local maxima, minima, and zero crossings **and much more!**



ONLY £199 ex VAT* (UPGRADES FOR EXISTING USERS) FREE 30 DAY EVALUATION

Accurate results that can be relied on




RD Research, Research House, Norwich Road, Eastgate, Norwich NR10 4HA
Tel: 01603 872331 Email: rd.research@paston.co.uk www.looking.co.uk/spice
 *Please add £5.00 postage and packing. *applies to users of B² Spice & B² Logic. All trademarks acknowledged



CIRCLE NO.104 ON REPLY CARD

Next Generation Electronics CAD

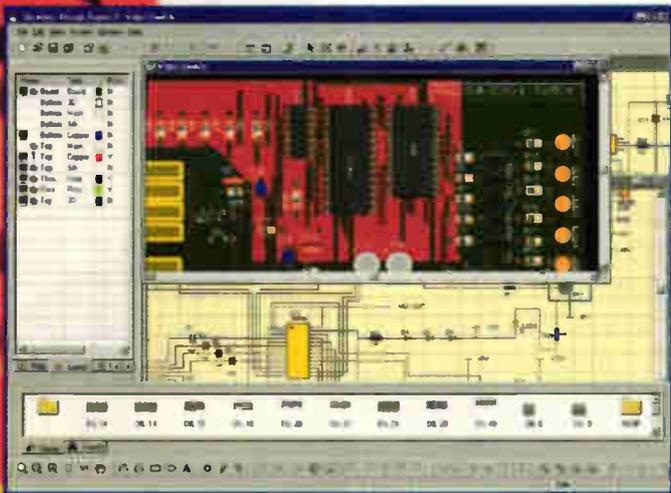

Introducing Electronic Design Studio 2, the new modular electronics design system that includes simulation, schematic, PCB, autorouting and CAD/CAM modules as standard.

Our state of the art integrated design environment brings powerful management to your projects and now features expanded libraries with 3D style PCB footprints, and the new Viper autorouter. EDS 2 Advance also includes rip up and retry routing, net styles, shape based realtime design rule checking (DRC), full copper pour support with unlimited automatic zones, split power planes with router support, cross probing, netlist navigation, DTP quality feature rich schematics and a wide range of import/export options.

EDS 2 is fully compatible with the latest TINA Pro 5.5 with support for FAST TINA net import using the Project Wizard.

	Standard	Advance
Schematic, Simulation, PCB & CAD/CAM Modules	Yes	Yes
Viper Autorouter	Single Pass	Ripup/Retry
Multiple copper pour, thermal relief, power planes		Yes
Cross probing & Net Styles		Yes
Shape based Design Rule Check		Yes
	Price*	£199 £349

electronic design STUDIO 2



Quickroute Systems Ltd
 Regent House, Heaton Lane,
 Stockport SK4 1BS UK
Tel/Fax 0161 476 0202/0505
 Email sales@dotqr.com
 *Price excludes P&P and VAT.
 (c) 2001 Quickroute Systems. E & O. E.

www.dotqr.com

CIRCLE NO.105 ON REPLY CARD

Killing fields – recognition at last

The NRPB's recently published report on 'ELF Electromagnetic Fields and the Risk of Cancer' confirms a weak association between power line electromagnetic fields and childhood leukemia. This should be no surprise to readers of *Electronics World* who may recall a series of 'Killing Fields' features in the 1990s by independent researchers investigating the effects of power lines on those living and working nearby.

What is important is that over the intervening years the NRPB has slowly shifted from outright denial of any possible link to a grudging recognition that further research is needed to determine the exact mechanism linking power lines and cancer processes.

As one of those researchers and an *EW* feature writer, I'm pleased that the door to further research has creaked slightly ajar. Nevertheless, there's still a mountain to climb to make sure that future research is directed into those areas where it is likely to shed most light.

The main problem is one of definition. The eminent research group chaired by Sir Richard Doll was only briefed to investigate the effects of non-ionising ELF radiation emanating from electric power systems. This led to an obsessional concentration on the electromagnetic fields emanating from power lines.


There has been no interest in extending power line electrostatic and electromagnetic field research to interactions with other known harmful radiations, involving natural charged particles and background ionising cosmic radiation.

In some ways it's remarkable that the Committee found any link at all, bearing in mind that over a century of domestic and industrial electric power has more or less proved that power system magnetic fields *per se* are unlikely to be directly harmful.

The problem facing regulators like the NRPB is a reluctance to range across the EM spectrum to actively research interactions that may be harmful. This is partly due to NRPB resources being hijacked to allay public disquiet about siting mobile phone masts near schools, while ignoring broadcast transmitters generating far higher field strengths in the same bands and areas.

As I write, Vatican Radio faces shutdown by the Italian Government for massively exceeding HF field safety limits in urban areas near its short wave transmitters. If threatened by local TV transmitter shutdown and loss of soaps, public concern about transmitter safety is likely to wane in the UK!

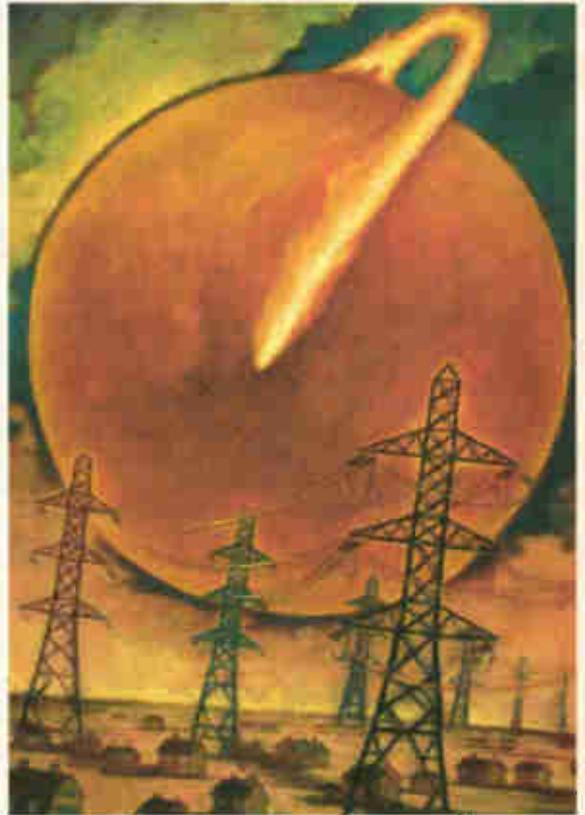The same goes for ionising radiation. Nuclear paranoia has ensured that radiation risk assessment



has failed to grasp the nettle that there may be no lower safe limit for human ionising radiation exposure, and that some public risk has to be accepted, as it is with road traffic accidents.

While the scientific jury is out, the precautionary principle has led to power companies in the USA buying up properties close to power lines deemed unsaleable, and planning codes and guidelines advising against domestic housing close to overhead lines.

In the meantime, the likelihood of a link between electrodynamic fields and human disease through background ionising radiation interactions is strengthened by the numbers of papers reporting solar cycle disease curves for cancers at high magnetic latitudes and high altitude urban locations where natural background radiation flux is intensified by location.

The NRPB must get away from its comfortable preoccupation with ELF non-ionising fields, and actively investigate ionising radiation interactions with all electrodynamic fields.

Anthony Hopwood

EDITOR

Martin Eccles
020 8652 3614

CONSULTANTS

Ian Hickman
Philip Darrington
Frank Ogden

EDITORIAL ADMINISTRATION

Jackie Lowe
020 8652 3614

EDITORIAL E-MAILS

jackie.lowe@rbi.co.uk

GROUP SALES EXECUTIVE

Pat Bunce
020 8652 8339

ADVERTISEMENT E-MAILS

pat.bunce@rbi.co.uk

ADVERTISING PRODUCTION

020 8652 8339

PUBLISHER

Mick Elliott

EDITORIAL FAX

020 8652 8111

CLASSIFIED FAX

020 8652 8938

NEWSTRADE ENQUIRIES

020 7907 7777

ISSN 0959-8332

For a full listing of
RBI magazines:
<http://www.reedbusiness.com>

SUBSCRIPTION HOTLINE

Tel (0) 1444 475662
Fax (0) 1444 445447

SUBSCRIPTION QUERIES

rpb.subscriptions@rbi.co.uk
Tel (0) 1444 445566
Fax (0) 1444 445447

Electronics World is published monthly. By post, current issue £2.65, back issues (if available) £3.00. Orders, payments and general correspondence to **L333, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**. Tel: 892984 REED BP G. Cheques should be made payable to Reed Business Information Ltd. **Newstrade:** Distributed by Marketforce (UK) Ltd, 247 Tottenham Court Road London W1P 0AU 0171 261-5108.

Subscriptions: Quadrant Subscription Services, Oakfield House Perryman Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year UK £36.00 2 years £58.00 3 years £72.00. Europe/Eu 1 year £51.00 2 years £82.00 3 years £103.00 ROW 1 year £61.00 2 years £98.00 3 years £123

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Roy Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rohwoy NJ Postmaster. Send address changes to above.

Printed by Polestar (Colchester) Ltd. **Filmsetting by** JJ Typographical Ltd, Unit 4 Baron Court, Chondlers Way, Southend-on-Sea, Essex SS2 5SE.

© Reed Business Information Ltd 1997 ISSN 0959 8332

Poll reveals serious concern over electronics skills shortages

A survey of electronics executives by City consultancy KPMG shows there is serious concern over skills shortages in the industry in the UK.

In a survey of executives from firms such as ARM, BT Cellnet, IBM and Motorola, 98 per cent of respondents in the survey said their major concern was over skills shortages.

"Much more active investment is needed in centres of learning," said KPMG's head of electronics, Crispin O'Brien. "If you compare what we

have with partnerships in Cambridge, for example, we're a long way behind other countries."

According to O'Brien, a recent IDC report says that the shortage of skilled labour in Europe could reach 3.8m by 2003. "You could probably say that just under one million of those could be in the UK," he said.

However, he stressed that KPMG's report did not try to blame any one party for the situation and insisted that the industry must also do more.

"The Government is listening, we just have to wait and see how effective their measures will be," said O'Brien, commenting on the recent publication of the enterprise, skills and innovation white paper.

The report by KPMG, announced mid February, also highlights the lack of R&D funding and the industry's relationship with Government and education as key areas that need to be addressed.

Countries where R&D funding is high have a healthier industry and economy, said O'Brien. Competition in Europe for inward investment is much higher now, he said, and only five per cent of the UK electronics industry is actually UK owned, so

the manufacturing base is not tied to Britain.

"Tax incentives are needed to keep them here. But although these incentives certainly help, the main reason that people invest in a country is the skills base," said O'Brien. "And right now, the biggest constraint is good quality people and access to a research base."

Firms team up to make superchip

IBM, Sony and Toshiba are to develop jointly a "super-computer on a chip". With a 300-person design centre in Texas, the three firms will invest \$400m on the project over the next five years.

Called 'Cell', the sub-0.1µm chip will combine technologies such as copper interconnect, silicon-on-insulator transistors and low-k dielectric material.

Cell will be more powerful than IBM's Deep Blue supercomputer, the firms claim. Providing teraflops of processing power, it will be aimed at broadband consumer products.

IT in school not hitting right spot

The effectiveness of tackling the shortage of science and engineering graduates by boosting investment on PCs and IT in schools has been questioned by a director of one of the UK's science and technology regional organisations (SATRO).

According to John Hindhaugh, director of Staffordshire SATRO, most of the Government's proposed £400m investment in new technology for schools will go on supporting IT in English, business studies, leisure & tourism, geography and every other subject area.

"This of course is no bad thing but these areas of the curriculum have little to do with electronic design. Design & technology in schools is not often seen as a priority for IT support," said Hindhaugh.

Cambridge firm wins multilayer optical disk link up

Constellation-3D, the firm developing high capacity optical disks, has partnered with Plasmon to co-develop manufacturing processes.



Cambridge-based Plasmon will use its experience in recordable optical media to set up a prototype production line for fluorescent multilayer disks (FMDs), most probably in the UK.

"Our collaboration will focus on industrialisation of the production processes, to provide future manufacturers of FMD disks with efficient, low cost and durable mass production techniques," said Nigel Street, CEO of Plasmon.

FMDs use fluorescence, rather than reflection, to sense data. Dye placed in the pits of the disk fluoresces when a laser is focused on it.

Because the CD-sized FMD is

essentially transparent, multiple layers can be formed. A 20 layer disk is capable of storing up to 100Gbyte of data, the firm claimed.

"C-3D has demonstrated multilayer read-out using their unique FMD technology at a level that is significantly greater than the two layers achievable with current reflective recording layers," added Street.


In January C-3D signed a deal with Lite-On to manufacture drives for the disks. Last November it signed a similar deal with optical disc equipment supplier Steag Hamatech.

Richard Ball

The Balance Box

Microphone or line level amplifier for balanced or unbalanced signal lines

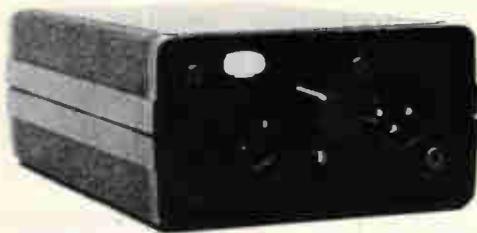Professional portable units operating from an internal PP3 battery or external mains adaptor



- ★ Precision true floating transformerless balanced input and output at microphone or line level
- ★ Simple interfacing and conversion between balanced and unbalanced signal lines
- ★ Low noise and distortion
- ★ High common mode rejection
- ★ Switchable gain selection
- ★ Extensive RFI protection

The Phantom Power Box – The Headphone Amplifier Box - The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW
 Information line 01428 751469 Fax 751223
 E-mail contact@confordelec.co.uk
 Web: www.confordelec.co.uk/

CIRCLE NO.106 ON REPLY CARD

Ramco

GENUINE GOVERNMENT SURPLUS

As an MOD Contractor we offer genuine government surplus equipment now tested and with a 120 day guarantee.



TESTING!
TESTING!

All equipment is now supplied fully tested via our refurbishment cell

BEST VALUE DEALS...

Tektronix 2440 300MHz Digital Scope	£1950
Tektronix 2445A 150MHz Analogue Scope	£800
Philips 3264 100MHz Analogue Scope	£450
Gould OS300 20MHz Analogue Scope	£180
Marconi 2370 110MHz Spectrum Analyzer	£1100
Racal 9914 Counter/Timer	£150
Philips PM2521 Bench Meter	£150
Philips PM6671 Counter/Timer	£150

Please call for more information on these and other products available

CHURCH LANE, CROFT, SKEGNESS, LINCS (JUST OFF THE A52)

01754 880880

FIND OUT MORE ABOUT US ON OUR WEBSITE

www.ramco.co.uk

CIRCLE NO.107 ON REPLY CARD

Professional PCB Layout for Windows at Computer Store Prices!

Easy-PC For Windows 4.0

now reads Ultiboard designs/libraries*

Suddenly, a professional level PCB layout product is available at a realistic price. Just check the specification and see what excellent value you get with Easy-PC For Windows. Then test before you buy with a demo version - you will be simply amazed with Easy-PC For Windows.

- True Windows 32 bit product
- Integrated Schematics and Layout as standard
- Windows drag & drop throughout
- Multiple documents open within display
- Technology files for fast start-up
- Tiled display - Cascade, Vertical, Horizontal
- Multi-level Undo/Redo
- Integrated standard AutoPlace
- Optional shape based AutoRouter
- Full Copper Pour
- Split powerplanes
- Unlimited signal/powerplane layers
- Unlimited non-electrical/doc layers
- Keep out/keep in areas for routing
- R/H mouse menu support
- Pan across design to cursor position
- Cross probing between Schematics and PCB
- Full forward & backward annotation Schematics /PCB
- Modeless driven operation, no menu selection required

Over 7,000 users must be right!

Consistently, one of Europe's most popular PCB Layout products for Windows 95/98/NT/2000, Easy-PC has won praise from users for the wealth of features within each new release. Many of these new features are normally only found in the world's most expensive PCB Layout software packages.

Now try Easy-PC For Windows for yourself !

*Ultiboard is a trademark of Ultimate Technology

Number One Systems

Call +44 1684 773662 or Fax +44 1684 773664

E-mail info@numberone.com

call us for a demonstration copy or download from

www.numberone.com

Number One Systems, Oak Lane, Bredon, Tewkesbury, Glos, GL20 7LR. UK

CIRCLE NO.108 ON REPLY CARD

Amstrad profits plummet due to e-m@iler losses

Amstrad's telephone with e-mail capability – the e-m@iler – is continuing to lose money for the company, which saw interim pre-tax profits fall by over 80 per cent to £1.5m.

The consumer electronics manufacturer's e-m@iler business is operated through a joint venture with Dixons known as Amserve. As the majority shareholder, Amstrad incurred a pre-tax loss of £3.9m in its Amserve business.

Around 77 000 e-m@ilers have been installed since the launch last March. These are being sold at a loss in order to quickly build up a user base. It is hoped that they will then generate revenues through advertising and call charges.

"With over nine months

experience, e-mail usage is currently generating an income for Amserve which equates to £20 per phone per year or £1.5m per annum on the current installed base of 77 000 units," said Amstrad chairman Sir Alan Sugar.

Sugar said that first advertising revenues were expected to start later this year when the installed base tops 120 000 units.

"We are looking for growth of the installed base and as more e-m@ilers are sold losses from the Amserve business will continue but the future profit potential of the Amserve business will increase," said Sugar.


Amstrad, which is one of five suppliers to satellite broadcaster BSkyB, also saw weakness in the digital TV set-top market.



Last week Amstrad also announced plans to license its first GSM mobile phone product to Chinese manufacturer Haier CCT.

Turnover for the six months was 27 per cent down from £60.8m to £44.1m.

Richard Wilson

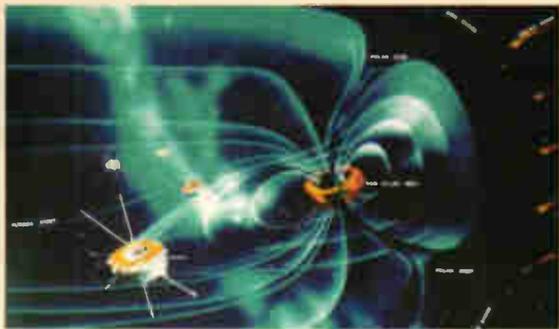

Satellite mission investigates solar storm effects

The first results have been published from the four satellite Cluster mission which is measuring the Earth's magnetosphere. The bow shockwave, where the solar wind interacts with the magnetosphere, has been measured in detail for the first time. Findings from the mission may enable designers to increase the ruggedness of communication satellites which have been destroyed by solar storms in the past.

Patent bounty hunters pay out \$40 000

BountyQuest has paid out \$10 000 each to four people who may have found 'prior art' to break patents.

The company was set up last year to make money by putting bounties on the patents that other companies do not want to exist.

"Patents are a double-edged sword. While they encourage creativity and the introduction of new products that improve lives, they can also stifle competition – particularly when they don't represent genuine innovation," said Charles Cella, founder and CEO of BountyQuest when it was set up.

Patents are awarded only if there is no evidence that an idea has been thought of before. A search for evidence, or prior art as it is called, is made before granting the patent, but this search may not be exhaustive. Finding prior art can cause a patent to be withdrawn.

"BountyQuest taps into the world's knowledge market to uncover this hard-to-find information, which can be used not only to weed out bad patents, but also to validate good ones," Cella said.

BountyQuest rewards start at \$10 000 and could go higher than \$1m, depending on the value of the information to the client searching for it, said the company.

Prior art, claims BountyQuest, has been found that challenges the following patents: a method for on-line music sampling, held by Intouch Group; a method controlling access to an event venue through alterable tickets, held by Walker Digital; a technology for database copying, held by Oracle; and a technology for single-chip network routers, held by Cisco Systems.

Steve Bush

New CO sensor stands to benefit from tighter gas laws

Fuel-cell sensor technology developed by Scipher spin-off firm Monox stands to benefit from possible changes to EPA (Environmental Protection Agency) regulations in the US.

The Swindon-based firm, a spinout from the Scipher intellectual property group, has developed a hermetic plastic carbon monoxide sensor – the subject of 27 patents.

It uses conductive plastic to

transfer the output signal to conventional solder pins while an internal platinum/ruthenium electrode system deposited directly onto plastic minimises precious metal use. Test gas passes into a sulphuric acid electrolyte via a semi-permeable membrane/wick system.

The company has already received a \$1m order for the new sensor, with more promised.

A ruling in the US, although

currently suspended, requires that all public buildings must have carbon monoxide (CO) detection alongside smoke and other fire detection systems.

An attempt was made to enforce the regulation several years ago but, following a massive spate of false alarms from the sensor technology then available, the requirement for CO detection was put on ice.

However, recent technology

developments producing better sensors has caused legislators in Canada and the European Union to set much tighter limits on CO detection – and the US is under pressure to follow suit.

New Canadian and European legislation requires reliable detection at gas concentrations down to 10ppm, a sensitivity which, until recently, could only be achieved with bulk semiconductor heated wire transducers.

Frank Ogden

New technology will halve mobile antenna numbers

Quintel S4, the company that emerged from a deal between DERA, the research arm of the Ministry of Defence, and UK landlord, Rotch Group, was launched this week.

The company is combining technology from DERA with properties owned by Rotch to halve the number of mobile phone antennas across the UK and Europe.

Radio masts are often shared but

several antennas are attached to them. DERA said its technology let each antenna receive up to five radio signals at once.

This means the services of all five 3G licence holders could be combined on one roof-top or mast antenna.

Quintel reckons that each operator will need up to 20000 sites to complete the roll out of third generation mobile services.

"Personal communications are transforming all our lives and the pace is hotting up," said Andrew Middleton, director of knowledge, information systems at DERA. "Not all change is good and it is important to offer socially responsible choices."

Rotch's part in the deal means making its £3bn portfolio of around 130 000 possible sites available to Quintel.

Interactive audio plan


Broadcaster Capital Radio has teamed up with US digital radio technology firm, Command Audio to launch on-demand interactive audio through the UK's digital audio broadcasting (DAB) network.

A joint venture company also including UBC Media, Command Audio-UK (CA-UK) will produce on-demand interactive programmes and license other programmers and service providers.


According to the firms, when deployed in the UK this will allow listeners to choose from a range of programmes and listen to them whenever and wherever they want.

Software boost for WAP developers. Nokia's WAP Toolkit 2.1 is a free software tool that provides a PC-based environment in which developers can write, test and de-bug WAP applications. For this version, the company has added simulators for its 6200 and 7100 series phones. It also includes a June 2000 WAP Forum specification reference implementation simulator,

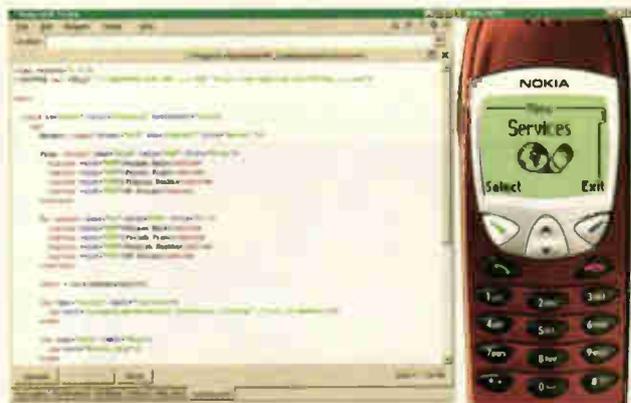which supports multipart push among other new features. The simulator enables the prototyping of next-generation WAP services that will be supported in hand-sets coming to the market later this year and next.



Orange unveils the house of the future. A detached house in Hertfordshire is being used as a research centre to test, monitor and evaluate advanced services and products for the home. Dubbed 'Orange at home' the project is being led by mobile operator Orange. The house was adapted at a cost of £2m to include a range of services that can be controlled using 'wire-free' technology such as lighting, heating, security, curtains and baths.

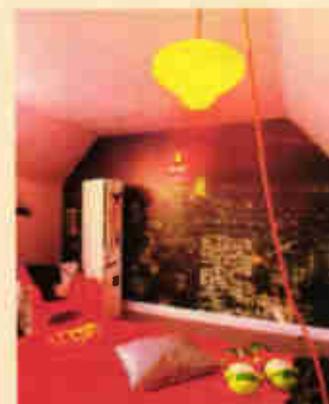

Metallic superconductor works at 39K

Japanese researchers have found a simple metallic compound that superconducts at twice the temperature of previous materials.

Magnesium diboride (MgB_2) superconducts at 39K, claims Tokyo's Aoyama Gakuin University, twice that of the previous best metallic material.

"It's certainly a new type of semiconductor," said Dr Mark Blamire, a materials scientist researching superconductivity at

Cambridge University. "But it doesn't really compete with high temperature superconductors."

Blamire's group at Cambridge has already repeated the Tokyo experiments, creating 99.99 per cent pure MgB_2 , with a T_c of 39.5K.

Ceramic and other intermetallic compounds remain much better superconductors, working at over 100K, but they are potentially harder to manufacture than metallic varieties.

The Tokyo work may open up new avenues of research, using less exotic and expensive elements than niobium, the current favourite.

At Cambridge and other research centres, scientists are at the stage of making bulk materials by sintering powders, said Blamire.

Work is under way to make useful electronic components which would involve laying down thin films on substrates.



LEDtronics has unveiled a set of incandescent replacement lamps based on clusters of high intensity LEDs. The DecorLED range uses a standard Edison-screw base and outputs in six colours from the 18 LEDs. Lifetime is claimed to be 11 years. Light output ranges from 3000mcd for a blue bulb, to 10 000mcd for green. Power consumption is just 1.0 to 1.7W, for lamps equivalent to a 15W incandescent bulb, the company said. Depending on the colour, the LEDs are made from either InGaAlP or SiC/GaN technology.

All new European Ford cars to have electronic telematics within 5 years

Ford aims to put electronic telematic systems in all its European cars within five years.

The car maker has stepped up its plans for in-car electronic systems through a partnership with mobile communications operator Vodafone with the intention of bringing in-car security and information services to its range of European vehicles by 2006.

The first production Ford Focus cars with telematics will appear in Germany next week. A UK launch using Vodafone's mobile network will follow shortly after, said a company spokesman.

"We anticipate that within five years nearly all new Ford vehicles will be fitted with some type of telematics system," said David Thursfield, president and CEO of Ford Europe.

The in-car communications links


supporting GPS-based location, security and information services will be provided by Vodafone's UK mobile network and its D2 subsidiary in Germany.

Services are expected to include providing emergency and roadside assistance, traffic information and dynamic re-routing as well as an operator and voice controlled service.

For example, the driver will be connected with the emergency services, who will also be automatically alerted if the airbag is deployed. Also, the vehicle's position will be calculated using the GPS location system.

"Telematics is an integral part of our strategy," commented Vodafone's Thomas Geitner.

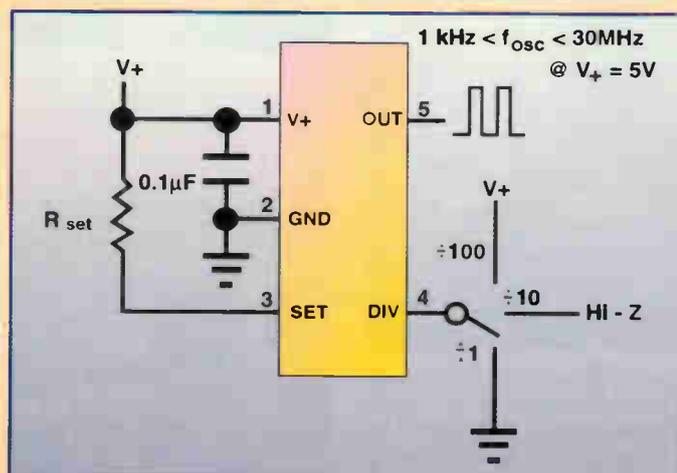Typical additional cost to the first Ford Focus' being fitted in Germany will be £845. ■



1kHz to 30MHz oscillator IC

Linear Technology has produced the LTC1799, a handy 1kHz to 30MHz oscillator in an five-pin SOT-23 package.

Frequency is set between 100kHz and 30MHz with a single resistor (f has a linear relationship to R), and an output divide ratio of 1, 10 or 100 is selected with a single external pin.

Claimed frequency error is two per cent or under between 5kHz and 20MHz (0°C to 70°C) with ± 40 ppm/°C temperature and 0.05%/V supply stabilities.

The chip operates from 2.7 to 5.5V, although it will not reach 30MHz on lower voltages.

Typical supply current is 1mA and output impedance is 100Ω. Linear sees the chip driving charge pumps, clocking switched capacitor filters and replacing crystal and ceramic oscillators.

THE OSCILLOSCOPE IS MOVING ON...

Features:

- ▲ A fraction of the cost of benchtop scopes
- ▲ Save multiple setups, for ease of use
- ▲ Save, print and e-mail your traces
- ▲ FREE software and upgrades
- ▲ Automated measurements
- ▲ Large colour displays
- ▲ Scope, spectrum analyser & meter functions

Ask for a **FREE** catalogue and demo software, or visit:

www.picotech.com



pico
Technology Limited

...DON'T GET LEFT BEHIND

Tel: +44 (0) 1480 396395, Fax: +44 (0) 1480 396296, E-mail: post@picotech.com

CIRCLE NO. 109 ON REPLY CARD

PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

- Prototypes at a fraction of the cost
- Tooling and setup included
- Any contour
- Fr4 1.6mm, 35µm Cu
- Industry standard quality
- Follow up series runs
- CAM / CAD consulting

PRICE EXAMPLE
1 EUROCARD 05/PTH

+ Tooling
+ Photoplots
+ VAT

= £ 29.89*

*Sterling rates may vary. Price = € 49

€49

FREE



Freephone
0800-389 8560

Tel: +353 (0)61 701170
Fax: +353 (0)61 701164
E-Mail: info@pcb-pool.com

Simply send your files and order ONLINE

WWW.PCB-POOL.COM

Protel orcad EDWIN GraphiCode

CIRCLE NO. 110 ON REPLY CARD

Customised design services from Intec Associates Limited

INTEC look for interdisciplinary collaborations with experts who work in other fields. We supply creative and cost-effective solutions.

Key expertise

- PC interfacing applications
- Implementation of PIC micro-controllers and PC-104
- Implementation of radio linkers
- Implementation of sensors
- Analogue and digital circuit design
- PC software development using VB, VC, Java, Turbo Pascal and Delphi

Applied areas

- Standalone data logger using PIC micro-controller
- Standalone devices using PIC micro-controller
- Data logging/control system using PCs or PC-104
- Remote data logging/control via radio link
- Remote data logging/control via telephone line

Intec instant solutions

- PC-based data loggers controllers
- Standalone data loggers
- Sound loggers
- Remote control and telemetry applications

www.intec-group.co.uk

11 Sandpiper Drive, Stockport, Cheshire, SK3 8UL, UK
Tel: +44 (0)161 477 5855 Fax: +44 (0)161 477 5755

E-mail: mail@intec-group.co.uk

CIRCLE NO. 111 ON REPLY CARD

Ralph Carbone and Tom Adams provide a unique insight into the failure modes of ceramic chip capacitors.



Above Fig. 1. Nondestructive acoustic image looking down into a ceramic chip capacitor shows overlapping delaminations (green, red, black) between layers. Acoustic image courtesy Sonoscan.

Ralph A. Carbone is a Reliability Physicist in the Failure Analysis of Components (FAC) Laboratory of Hewlett-Packard Co., Roseville CA USA. Tom Adams is a Consultant with Sonoscan Inc., Elk Grove Village IL USA.

If a ceramic chip capacitor fails, don't automatically blame the assembly process. The mechanism of failure may have been built in at the factory.

Ceramic chip capacitors are among the least expensive of electronic components, and among the simplest in design. A ceramic chip capacitor consists of alternating layers of metal plates, or electrodes, and ceramic insulating layers.

At each end of the capacitor, one set of plates – positive or negative – joins together in a termination. Properly built and installed, a ceramic chip capacitor will store and release a charge thousands or millions of times per second without incident.

The primary function of a capacitor is to block DC voltages, while passing AC signals. As such they are often used in a variety of circuit designs.

By volume, they are most often used as 'bypass' components on voltage supply or bus line circuits,

where they filter out unwanted high-frequency noise. In these applications, random circuit "glitches" are shunted to ground, thus preventing inadvertent errors from being generated.

However, the most common failure mode for a ceramic capacitor is the development of a resistive short. This causes DC signals to also be shunted to ground – i.e., a short circuit condition – resulting in the failure of the product.

Most ceramic chip capacitors sell for relatively low prices. If they were made and tested to the exacting standards of, say, a high-speed microprocessor, they would be more reliable, but they would also be exorbitantly expensive. Still, a failed ceramic chip capacitor can be an annoyance at the very least.

For example, it is typical for automotive air bags to contain a test circuit. If a capacitor in the test circuit becomes defective, a leakage current may flow around it. What

should be a closed circuit is now open, and the driver will be looking at an erroneous 'Air Bag Failure' message.

On a given printed circuit board, it's usually not difficult to tell that a ceramic chip capacitor has failed – there may be a spike in the power supply for example. It may be more difficult to tell by electrical testing which of many capacitors has failed.

Without resorting to relatively heroic measures, it is nearly impossible to tell why the capacitor failed. Examining a capacitor visually doesn't give you much information unless the capacitor has sustained gross damage that is visible on the exterior.

Often – but not always – the failure is the result of an internal manufacturing defect that eventually reached a critical state. The most common internal defects are voids in the dielectric layers.

A void is a bubble of air – or possibly another gas – that became

Fig. 2. Optical view of sectioned capacitor shows a delamination that, in this case, ran nearly the entire length of the capacitor. Photo courtesy Hewlett-Packard.


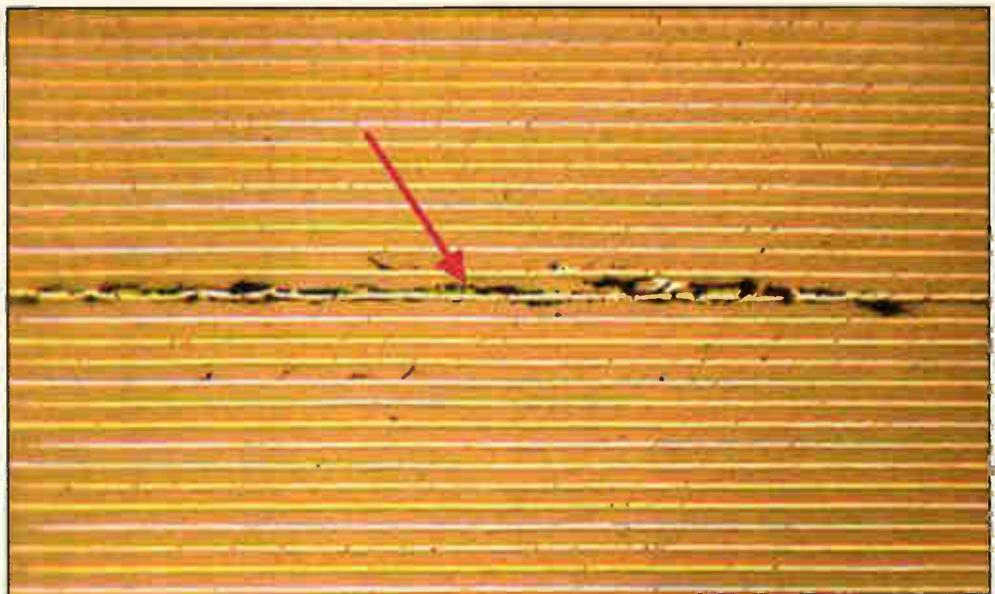


Fig. 3. Acoustic image showing damage – one or more delaminations, and probably cracks – in a ceramic chip capacitor. Acoustic image courtesy Hewlett-Packard.

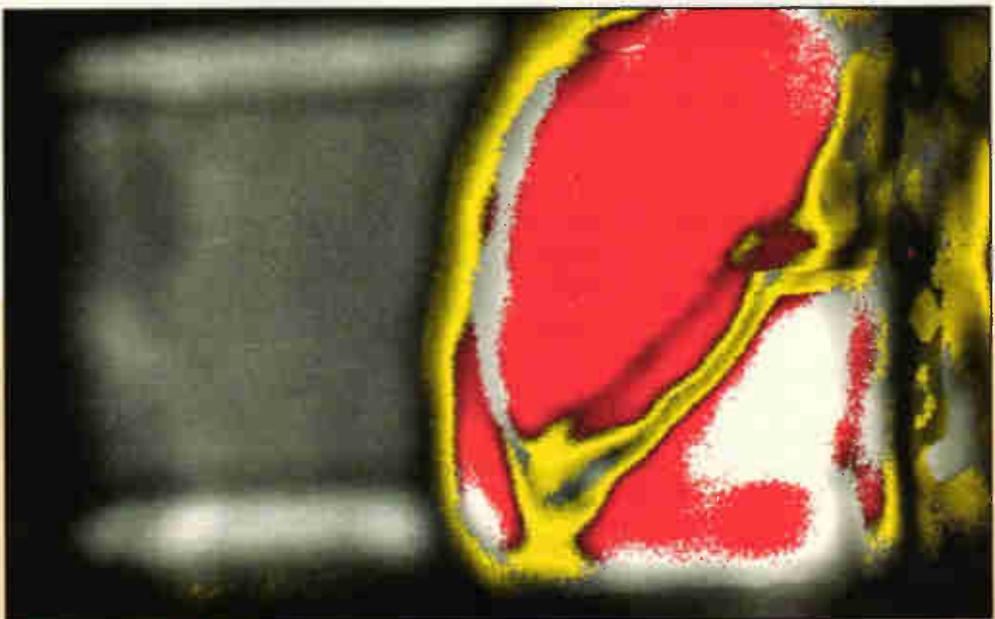

trapped in the fluid ceramic before the capacitor was fired. If you sliced a capacitor open at just the right point, the void would look like a tiny flattened bubble. It might lie entirely within one layer of ceramic, or it might be in contact with one or both of the adjacent plates.

Sawing open a capacitor to examine a void is something not often done, because of the labour and time involved. In most applications, the condition of a single ceramic chip capacitor isn't truly critical. But in some systems – those that go into earth-orbiting satellites or marine buoys, for example – every capacitor has to be flawless. For these applications, capacitors are often inspected by acoustic micro imaging, which sees internal defects nondestructively. Voids and the other frequent defects, cracks and delaminations, are usually too small to be imaged by x-ray.

Detecting flaws via acoustic imaging

Acoustic micro imaging uses an ultrasound-pulsing transducer that scans over the capacitor. Several thousand times a second, the transducer switches between pulsing

ultrasound and receiving the return echoes from the interior of the capacitor.

The return echoes are used to make data points. The whole collection of data points from a capacitor shows its internal structure, including defects.

Ultrasound is reflected only by interfaces between different materials. The stack of electrodes and dielectrics in a capacitor presents a great many material interfaces, but these are basically low-contrast interfaces, at least when compared to defects.

The three common defects – voids, cracks, and delaminations – amount to an interface between a solid material and the air or other gas inside the defect. Technically, what occurs is a difference in acoustic impedance, which is the density of a material multiplied by the speed of ultrasound through that material.

Since the density of a gas is extremely low compared to the density of a solid, the difference in acoustic impedance between either a metal or a ceramic and air is huge, and results in a very high-contrast data point.

In the completed acoustic image, defects are very easy to spot. The ordinary acoustic view, looking straight down into the acoustically transparent capacitor, shows the x-y outline of defects, but there are other kinds of acoustic views, including a nondestructive cross-section that shows feature depth.

Cracks in ceramic chip capacitors usually extend more or less vertically through several layers of ceramic and metal. Since they provide a direct pathway between plates, cracks create dead shorts. Voids can also cause shorts, by a slightly more indirect route.

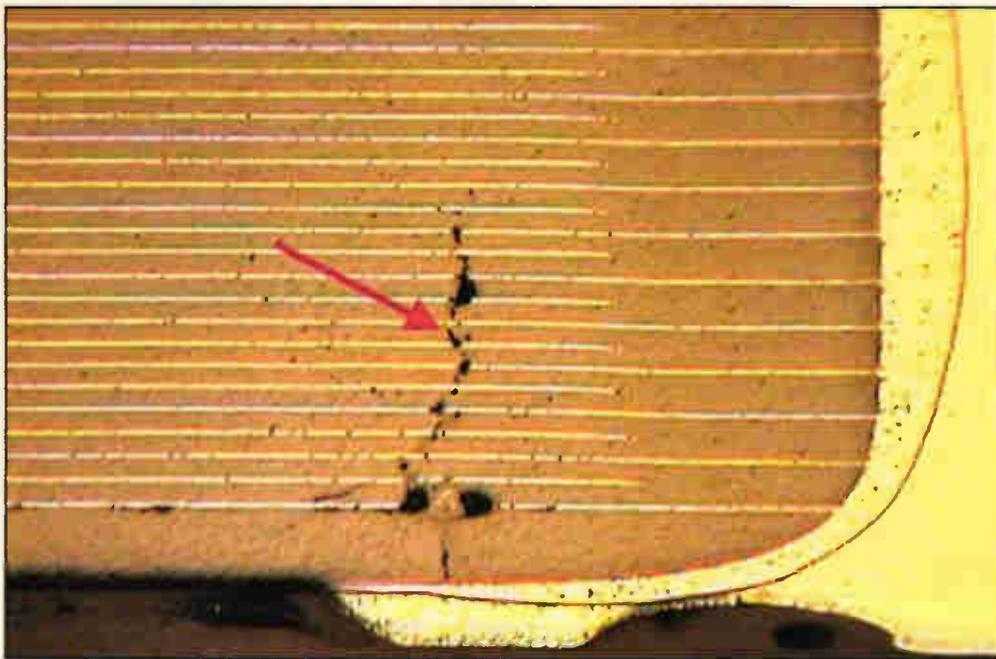


Fig. 4. Optical view of a nearly vertical firing crack first detected acoustically. The dimensional accuracy of the acoustic image simplifies and speeds up accurate physical sectioning. Photo courtesy Hewlett-Packard.

If a void lies entirely within a ceramic layer, it still encourages metal migration between the two adjacent plates. Eventually enough metal coats the inside of the void so that a short occurs between the two plates.

Delaminations are horizontal separations between layers. Capacitors having one delamination are likely to have several more delaminations at various layers, since delaminations are the result of a lack of bonding between layers.

Companies involved in high-reliability applications send around a million ceramic chip capacitors a year to the applications laboratory at Sonoscan [www.sonoscan.com] for acoustic inspection. The lab's acoustic imaging screens the capacitors into good and bad categories; for expensive high-reliability uses, this is far cheaper than having a system become impaired or fail outright in an inconvenient or impossible location.

The lab sometimes sees capacitors open too, chiefly so that customers can see defects optically. Sawing in exactly the right place is a simple

business because the acoustic image has already shown exactly where the defects are.


Because acoustic micro imaging primarily operates in the reflection mode – pulse the ultrasound, receive the return echoes – ceramic chip capacitors can be imaged acoustically equally well when they are still mounted on a board. This became important recently at Hewlett-Packard, where a circuit board used in a medical product began to experience field failures.

The problem was identified electrically as a single ceramic chip capacitor on the board. The lab could have removed the capacitor from the board for acoustic imaging, but this would have created the possibility that the removal process had caused whatever defect was present – at least in the eyes of the capacitor manufacturer. Instead, capacitors on failed assemblies were imaged right on the boards.

The results show two types of defect – large delaminations between layers, and cracks resulting from the firing process. No voids were found, suggesting that manufacturing flaws were related to firing, and did not involve the fluid ceramic material. The board assembler was then able to set up a screening process for incoming capacitors, and the capacitor manufacturer was able to adjust his processes to make delaminations and cracks less frequent. ■

Contact information

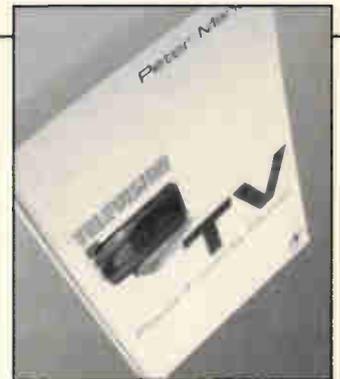Sonoscan Inc., 2149 East Pratt Blvd, Elk Grove Village IL, USA 60007. Phone: 847 437-6400, fax: 847 437-1550, e-mail: info@sonoscan.com, website: www.sonoscan.com



Peter Marlow
Contents: Introduction; A-Z of manufacturers and models
Readership: Professional service engineers, some college courses.
Pages: 400pp
Price: £22.50

TV Fault Finding Guide

Unique expert authorship and trusted Television magazine identity. Real repair and troubleshooting info – not just cribs from manufacturers' data sheets. Ease of reference – this book is an essential repair tool, not just another volume for the shelf, Television magazine's TV Fault Finding column is a unique forum for practical servicing tips, with the UK's leading service engineers and servicing writers contributing their observations and recommendations month by month. But try finding those faults reports for the Amstrad CTV2200 that's on your bench. Even with an index you will be chasing through a pile of magazines... until now. Peter Marlow's TV Fault Finding Guide is a distillation of the most used fault reports from 11 years of Television magazine. Arranged by make and model the information is extremely easy to access, and the book is a convenient size for the bench or to carry with you. This will undoubtedly become one of the service engineer's most useful tools. Unlike other fault guides, this one is based on top quality information from leading authorities, and genuine repair case studies. This is real-life servicing information, not just a compilation of manufacturers' manuals.

Over 2,000 reports covering over 300 models. Instant on-the-spot diagnosis and repair advice. Television magazine's leading writers' wit and wisdom available for the first time in book form.

To Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

5-in-1 digital multi-tester


Reader offer price £49.99 – fully inclusive

Complete with batteries, holster, test leads and temperature probe

Now you can record measurements together with readings of environmental conditions – temperature, humidity, light level and even sound pressure – using just one meter, the DT21. This 3.5-digit multi-tester even checks transistors.

Sound level readings in decibels are taken via the meter's inbuilt microphone. The **light** function relies on a very stable long-life diode – also built in – and is fully cosine corrected for the angular incidence of light. Relative **humidity** sensing – with direct reading in percentage – is taken using an inbuilt sensor, as is ambient temperature in °C. A probe is also supplied for making localised **temperature** readings. Alternatively, you can use any K-type thermocouple.

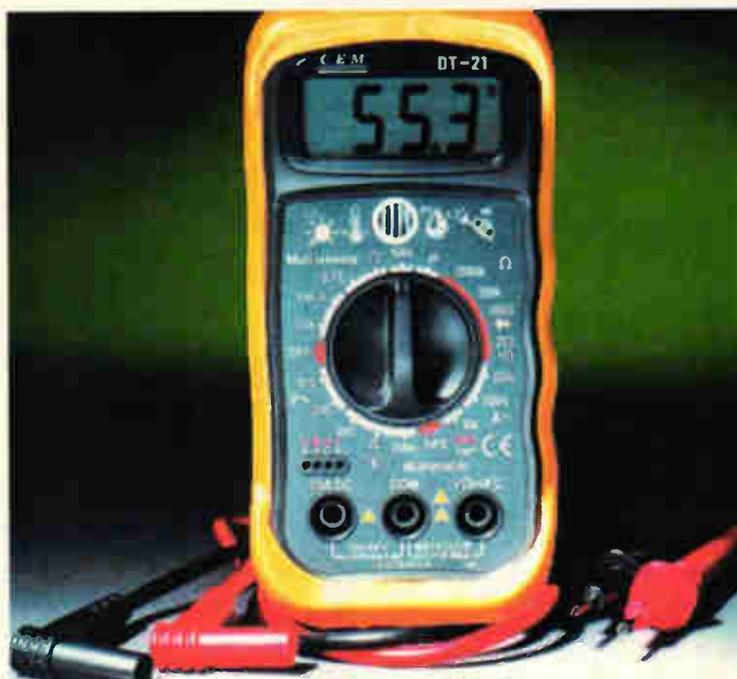The digital multimeter performs AC/DC voltage, DC current, resistance measurement and audible continuity, diode, transistor h_{FE} test.



For a PDF file of the meter's manual, e-mail eworld.orders@rbi.co.uk with the subject heading 'Meter manual'.

Features

- 11 functions: measures sound level, light, humidity, temperature, DC voltage, AC voltage, DC current, resistance, transistor, diode and continuity test.
- $3\frac{1}{2}$ large LCD with indications for lux, °C, %RH and dB.
- Sound level: from 35dB to 100dB with C weighting, 0.1dB resolution.
- Light: levels ranging from 0.1lux to 20000lux.
- Humidity: from 25%RH to 95%RH with 0.1%RH resolution and fast time response.
- Temperature: -20 to 200°C and -20 to 1200°C ranges
- Transistor h_{FE} , 0-1000 with 10µA base current
- Diode test current 1.4mA
- Separate jack for 10A current measurement
- 1MΩ input impedance
- 220V DC or RMS AC maximum overload for 200mV DC range, 600V RMS AC on other DC ranges

Voltage and current and resistance

DC volts

Range	Resolution	Accuracy
200.0mV	0.1mV	
20.00V	10mV	±0.5% of rdg, ±2dig.
600V	1V	±1% of rdg, ±2dig.

AC volts

200.0V	100mV	±1.2% of rdg, ±10dig.
600V	1V	±1.2% of rdg, ±10dig.

DC current

200.0µA	0.1µA	±1% of rdg, ±2dig.
200.0mA	100µA	±1.2% of rdg, ±2dig.
10A	10mA	±2% of rdg, ±5dig.

Resistance

200.0Ω	0.1Ω	±0.8% of rdg, ±4dig.
2.000kΩ	1Ω	
200.0kΩ	100Ω	±0.8% of rdg, ±2dig.
2.000MΩ	1kΩ	±1% of rdg, ±2dig.

Use this coupon to order your DT21 multimeter

Please send me DT21(s) at the special offer price of £49.99 each. Note that the price includes VAT and recorded UK delivery. Please add £5 for overseas orders.

Name

Company (if any)

Address

Phone number/fax

Total amount

£.....

Make cheques payable to Reed Business Information Group.
Or, please debit my credit card.

Card type (Switch/Master/Visa etc.)

Card No

Expiry date

Issue no

Please mail this coupon to *Electronics World*, together with payment. Alternatively fax credit card details with order on 020 8652 8111. You can also telephone your order on 020 8652 3614
Address orders and all correspondence relating to this order to DT21Offer, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Design competition

Devise a useful and/or ingenious application for the ZXF36L01 versatile high-Q bandpass filter with integral mixer and you could win a £500 voucher to spend with Farnell. There's two runner up prizes of £100 vouchers too.

Rules

- Electronics World reserves the right to publish submitted entries. All designs published will be attributed to their designers. A minimum payment of £50 will be made for each design published.
- Submission of an entry does not remove your right to exploit your design, but it does give Zetex the right to use the entry as an application note, or as the basis thereof, effectively making the design public domain.
- Winners will be chosen jointly by technical experts from Zetex, Farnell and the editor of Electronics World. The judges' choice will be final and no correspondence will be entered into regarding the choice of winner.
- No employee of Reed Business Information, Zetex and Farnell, or any of their associated companies, may enter this competition, nor may members of their families.
- No entry will win more than one prize, but multiple entries may be submitted.
- Prizes are as stated here and not negotiable.
- Entries arriving after the closing date will be void.
- No purchase is necessary to enter this competition.
- Winners will be notified by post, and the results may be publicised.
- For a list of winning entries, send an SAE to the editorial offices.
- Submitting an entry for the competition implies acceptance of these rules.

Launched this year, the ZXF36L01 is a versatile high-Q bandpass filter requiring a minimum of external components. In addition to the variable-Q analogue filter there is also a mixer block, making the device suitable for a wide range of applications.

All you have to do to enter the competition is send a design idea incorporating the ZXF36L01 to the address below. Entries will be judged on ingenuity, originality and usefulness. All entries are subject to the rules set out below.



A designer's kit is available from Farnell and you can find full data on the device on Zetex's web site <http://www.zetex.com/pdf/ics/zxf36101.pdf>.

It is not necessary for you to prove your design, and buying the kit is not a condition of entry into the competition. The design you submit has to work in practice but you will not be penalised for not having built a prototype.

If you do submit a design that meets the competition criteria and you have bought the kit, then you will receive a Farnell voucher for £15, courtesy of Zetex.

Send your entry to Filter Design, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Note that it is not necessary to send your prototype! Simply send the circuit diagram and a clear, concise description of the circuit. It will help if you describe why you think that your circuit should be among the winners. You can also e-mail your entry to jackie.lowe@rbi.co.uk, but unless the e-mail has a subject heading that reads 'Filter Design' it will not be eligible. Please attach diagrams and text separately and include a daytime phone number with your entry if possible.

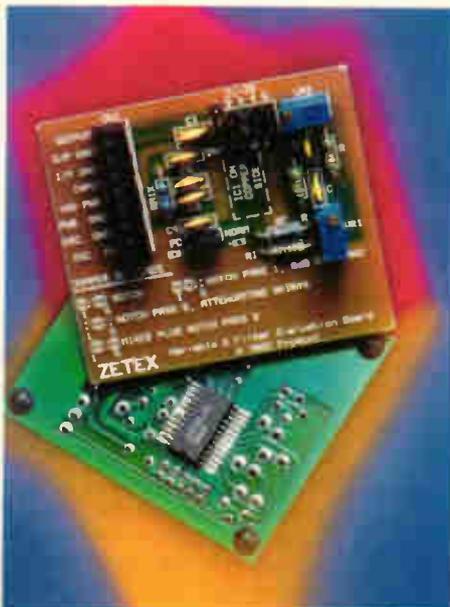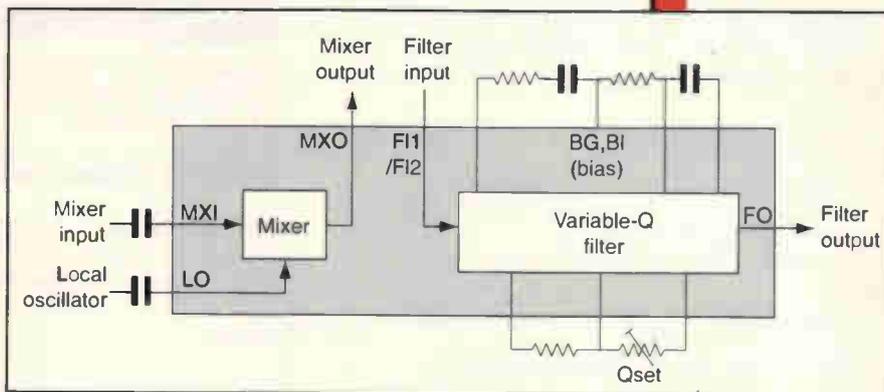The closing date for the competition is 30 April.



You don't need to buy this this new development board for the ZXF36L01 in order to enter the competition, but if you do, and your entry meets the competition requirements, you will receive a Farnell voucher for £15 to help cover its cost.




**Win a £500
voucher
redeemable
at Farnell.**

**For more
information...**

Visit <http://www.farnell.co> for details of the ZXF36L01 development kit or <http://www.zetex.com/pdf/ics/zxf36101.pdf> for more data on the filter chip.

This *Electronics World* competition is sponsored by UK semiconductor manufacturer Zetex and distributor Farnell Electronics Components.

BOOKS TO BUY

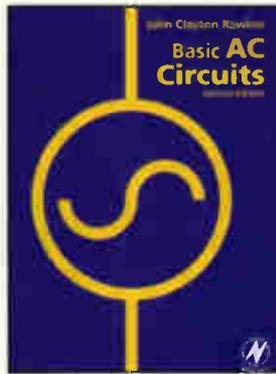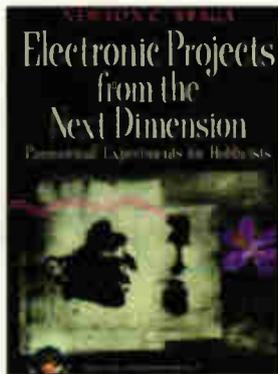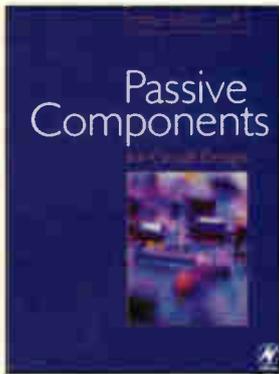

PASSIVE COMPONENTS FOR CIRCUIT DESIGN

Passive Components for Circuit Design is a unique introduction to this key area of analog electronics designed for technician engineers and anyone involved in circuit design. The coverage encompasses all component types capable of power amplification: resistors, capacitors, transformers, solenoids, motors and transducers. The behaviour of the components is explored along with the different types available and the principles of circuit design. Tolerances, stability, variation with temperature, reliability and manufacturing standards are all covered. Reading this book will improve your skills in component selection and analog circuit design. These are essential skills not only for the analog designer, but for all circuit designers, professional or amateur.

Contents: Preface; Fundamentals; Fixed resistors; Variable resistors, potentiometers and diodes; Capacitors; Inductors and inductive components; Inductive devices; Transducing components; SMT; Hardware; Index

Readership: Technician engineers, circuit designers, advanced hobbyists
Pages: 304pp
Price: UK £22.00
Europe £24.00
ROW £26.00

ELECTRONIC PROJECTS FROM THE NEXT DIMENSION

For years paranormal scientists have explored the detection and documentation of spirits, auras, ESP, hypnosis, and many more phenomena through electronics. Electronic Projects from the Next Dimension provides useful information on building practical circuits and projects, and applying the knowledge to unique experiments in the paranormal field. The author writes about dozens of inexpensive projects to help electronics hobbyists search for and document their own answers about instrumental transcommunication (ITC), the electronic voice phenomenon (EVP), and paranormal experiments involving ESP, auras, and Kirlian photography.

Although paranormal studies are considered esoteric, Electronic Projects from the Next Dimension teaches the technical skills needed to make devices that can be used in many different kinds of experiments. Each section indicates how the circuit can be used in paranormal experiments with suggestions about procedures and how to analyze the results.

Contents: White noise generators for use in instrumental transcommunication (ITC) and electronic voice phenomenon (EVP) experiments; Practical circuits for image experimentation, such as a

wireless sparkling image generator, horizontal bar generator, brontophic sound, magnetic field generator, high-voltage generators (Kirlian Machine's I & II); Paranormal skills experiments with temperature change, polygraph, electro-shock, random number generation, UFO detection, and ghost-finding.

Readership: Hobbyists, Electronics Enthusiasts
Pages: 256pp
Price: UK £22.00
Europe £24.00
ROW £26.00

BASIC AC CIRCUITS

This is the step-by-step approach for beginners. This self-paced individualized learning tool covers concepts, terms, and the mathematics required to understand AC circuit problems. It has been designed to improve analysis techniques for prediction and control development.

Readership: Beginners meeting AC circuits for the first time; students; technicians
Pages: 921pp
Price: UK £27.00
Europe £29.00
ROW £31.00

Post your completed order form to:-
Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS

Fax your order form to 020 8652 8111

How to order Book Title _____

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____

Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____

Tel: _____

PC via

Connecting external devices to your PC via a local-area network card is not as difficult as it may seem.

Eddy Insam explains how it all works and what you need to know. In a second article, Eddy will describe a development device that can get you going in no time at all.

Interactive publishing!

Interfacing via Ethernet is a complex topic involving new concepts for those of you used to RS232 and the like. If you have any queries regarding interfacing with Ethernet, e-mail martin.eccles@rbi.co.uk using the subject heading 'Ethernet interfacing'.

Any queries that are of general interest will be published in next month's article, together with their replies. We'll do our best to answer all your questions, but as the time available to prepare answers is finite, we cannot guarantee you a reply. Ed.

interfacing Ethernet

You are browsing the Internet looking at you car's own web page. The screen is full of messages and indicators telling you all about your car, but an orange flag tells you there is something that requires your attention.

You look at the various gauges: clutch, brake fluid, they seem OK. Oil looks a bit low though, so you place a tick under one of the oil brands in the 'garage reminder' memo pad.

You wonder how people did this in the past; did people actually open the bonnets and look inside their own cars? Then the door bell rings, the washing machine repairman is at your doorstep... "Your dishwasher just e-mailed us to say its drive belt is just about to go."

Whether you think the concept of networking your possessions is a good thing or not, it may be of some use knowing how it all works. In any case, this article is for you because it will at least put you on the first step of the "I am not afraid of the technology," ladder.

On the other hand, you may have already thought of network-enabling your own product or application, but been put off by the apparent complexities involved. This article will give you an insight into the expertise and effort involved. What's more, a readily available preprogrammed chip to be described in the next article will give you a head start on the prototyping stage.

Why use Ethernet?

As a consultant, I am sometimes asked about the Internet and its

potential extended uses. Boring as the subject may be, the conversation sometimes ends in opinionated discussions about the need for Internet fridges and microwaves that e-mail you when the noodles are ready.

Nevertheless, there are some interesting possibilities for considering the use of a local-area network as a serious interface between a personal computer and external input/output devices. For one, it means the two can be as remote from each other as need be – anywhere in the world in theory.

You can also share a device among several users, say a rooftop web camera or weather monitoring station accessed by all users in a building or school – or even from home.

There are benefits at the practical level too. Remote data logging and controlling equipment becomes much easier when it can all be interfaced using standard and well-tested networking components, cabling and connectors.

New network models such as 'Real Time Publish Subscribe', or RTPS for short, are also making Ethernet more suitable for real time systems, data logging and control. Interesting possibilities arise too when interfacing to other proprietary networks such as Home Automation, X10, CEBus or LON.

But then, it can all sound very complicated: the protocols, the stacks, and so little information published. But is it? The answer is not really, and it is certainly not out of reach.

Embedding is the word

Internet-enabled hardware products are slowly becoming commonplace. From vending machines dialling up to report their stock, to pinball machines publishing their high scores on the Internet for all to see.

Internet appliances – the term used for browsers that do not use a computer – are predicted to overtake PCs for Internet use within the next four years. A new addressing scheme for the Internet (version 6) allows for a staggering 2^{96} times the number of addresses currently available. The address field used is 128 bits. Each nut and bolt in your washing machine will be able to have its own unique Internet address.

Many modern products are driven by internal microprocessors. These small devices are quite powerful, but one generally omitted fact is that in order to implement the functionality required for Internet and network access, a lot of program code space is required.

Gone are the days of simple ASCII dial-up interfaces, simple ZMODEM or Kermit protocols. Nowadays your processor has to deal with PPP, ARP, IP, ICMP, TCP and a host of others. More on this later.

Of PCs and interfaces

PCs are well known for their lack of suitable interfaces into the real world. They were not originally designed with many facilities for driving external equipment, or to act as data gathering stations.

Many alternatives using the parallel and serial port have been on offer, but this approach is becoming less practical nowadays – especially with NT and Windows 2000 where special low-level software system drivers are required.

Worse still, parallel and serial ports are now called 'legacy' devices, which is computer jargon for obsolete. The newest machines from the shops just do not have these ports any more. These are all being replaced by USB.

Eventually, USB devices may be accepted as the standard method for general-purpose direct, local interfacing to a PC.

The advantage of using a network, as opposed to a direct connection, is distance. Most PCs will have a local network connection. Low cost Ethernet cards are readily available and easy to install – even in older

and non-PC machines.

From this point of view, using Ethernet for I/O external access is an attractive, cheap alternative. Furthermore, different brand, newer and older machines with different operating systems can access the devices. Macs, Linux, Unix and portable hand-held devices can all be used, Figs. 1&2.

Software at the PC end

If you develop a piece of network hardware, you will need to think about how to drive it from the PC.

You may not need to write any software at the PC end at all. Your device could for example emulate a web page, and be accessed as if it

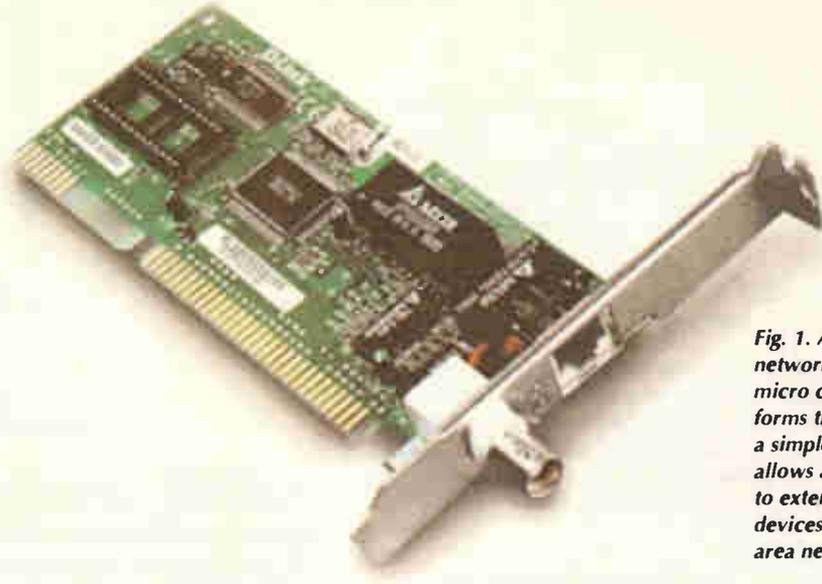


Fig. 1. A cheap PC network card plus micro controller forms the basis for a simple unit that allows a PC access to external I/O devices via a local area network.


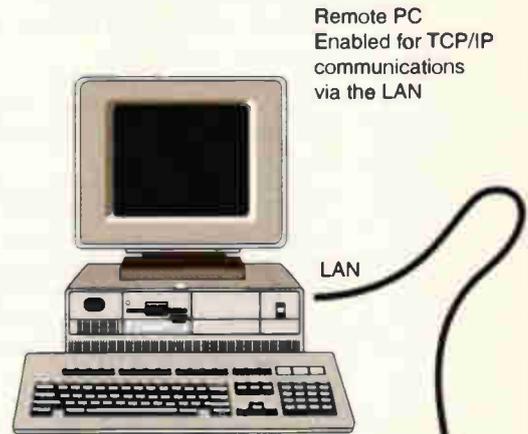


Fig. 2. It is possible to buy Network cards for well under £10 now so interfacing via Ethernet is convenient, fast and reasonably cheap. 10base2 Ethernet cards interconnect via coaxial cables. Many cards can be daisy-chained, each end of the chain being terminated with a 50Ω terminator.

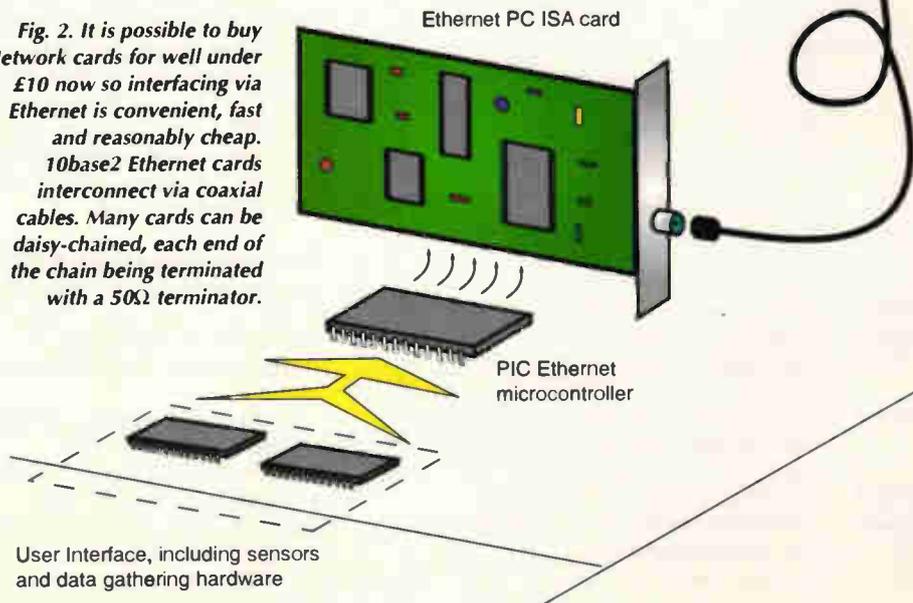

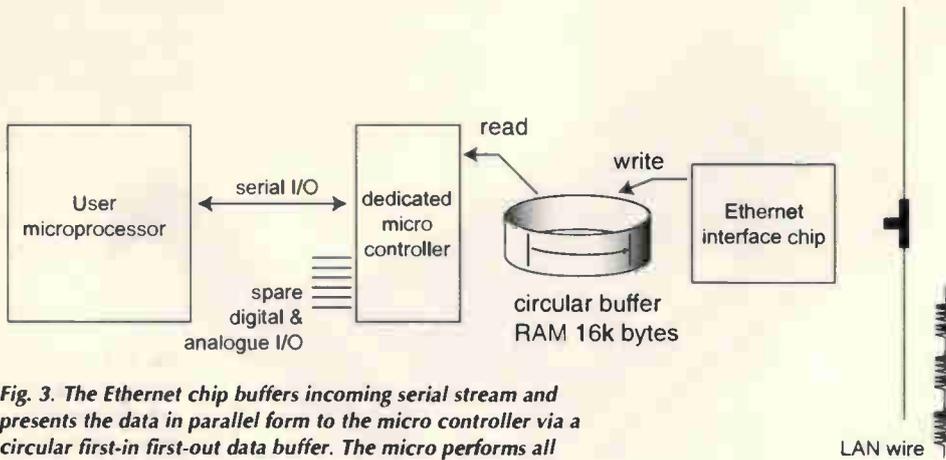


Fig. 3. The Ethernet chip buffers incoming serial stream and presents the data in parallel form to the micro controller via a circular first-in first-out data buffer. The micro performs all necessary high level addressing and decoding. Clean data is then transferred to the user application, which can be embedded in another microprocessor.

were a normal Internet page.

If you need more dedicated control, standard API libraries are available for network communications. The one in Windows is called Winsock, which is a family of API calls contained in a DLL file.

There is also higher level support in the form of ready made OCX components, add-ons for Visual Basic and C. List 1 shows a simple 'C' demonstration program showing how Winsock calls can be used to send and receive data from a remote on the network.

How do they do that?

Figure 3 shows a block diagram of the business end of a simple Ethernet embedded device. It consists of a small dedicated microprocessor connected to a

custom Ethernet interface chip, which is in turn connected to the local area network via suitable electrical isolation transformers.

The Ethernet interface chip acts like a sophisticated serial-to-parallel converter. Its job is to read serial packets of data from the wire, check their header bytes with an internal address, perform checksum calculations, and push the block into a user accessible first-in, first-out data buffer. This 'FIFO' queues the data blocks for processing by the application.

The job of the microprocessor is to retrieve the blocks, and according to the information within, perform a few more data calculations and checksums, then pass the 'clean' data on to another device or system. The micro must be quick enough to retrieve frames from the FIFO buffer before it overruns. If it isn't, packets may be lost.

During transmission, the opposite takes effect. The microprocessor places data blocks in a buffer, the Ethernet chip then adds any required headers and checksums, perform the parallel-to-serial conversion and then push the serial stream into the wire. At the same time, it checks for possible collisions. More or less, that is all there is to it. The rest is all done in the software.

What does the micro do?

The microprocessor's job looks simple. Take data from a buffer, do some conversions and then do whatever with it. Easy? Well, not quite.

A fair bit of housekeeping needs to be done along the way. Functionality needs to be included to communicate packets in the background with other users to let them know who and where we are for example. There are various established 'protocols' that describe exactly when and how this should

be done.

Protocols, as camels designed by committees, are by definition complex. The following values give a rough idea of the amount of program code required to implement an average Ethernet enabled application. Values are for a PIC 16F877 using assembler: ARP, 1.5Kb, IP and ICMP, another 1.5Kb, TCP another 2.5Kb, PPP (for modem access) 3.5Kb.

So if you want to Ethernet enable your project, you may need to dedicate quite a bit of program space to handling the protocols.

But do you need to use these complex established protocols? Isn't it possible to just talk directly to other workstations using your own simple private encoding system?

The answer is yes. Each Ethernet packet carries a frame identifier that describes the protocol format used by its payload. Pick a number of your choosing and send any data format you like.

The rest of the network will just ignore your privately encoded packets – but first check with www.isi.edu/in-notes/iana/assignments/ethernet-numbers/ to ensure the number you have chosen has not been already allocated!

Of course, you will need to program your PC to talk directly to the Ethernet card, and your packets will not be able to get past a router onto another network or the Internet. There may be real advantages in using alternative network models, for example to maintain speed and response times. There isn't that much software available at present out there. Expect little support from software vendors.

For real flexibility, you will need to use Internet protocols, and until dedicated TCP/IP interfaces are built in to the micros in hardware, you will need to live with the complexities of handling the protocol in software.

There's already a number of products in the market offering different levels of functionality. The best way to find out about these is to look at the web sites mentioned in the separate panel. What follows is just a simple summary.

The most common offerings come in the form of complete PCB cards with built-in micro, RAM, PROM and usually a built-in Ethernet interface driver chip. Units range in size from the smaller 8051 core-based, to larger, 386 embedded Linux-based cards.

Networking glossary

API	Application program interface
ARP	Addressing resolution protocol
DLL	Dynamic link library
FIFO	First in, first out
FTP	File-transfer protocol
HTTP	Hypertext transfer protocol
ICMP	Internet control message protocol
MAC	Media access control
PPP	Point-to-point protocol
RTPS	Real-time publish subscribe
SMTP	Simple mail transfer protocol
TCP/IP	Transmission-control protocol/Internet protocol
Telnet	Protocol within TCP that allows a remote terminal on the network to appear as a local one.
10baseT	Twisted-pair 10Mbit/s Ethernet
10base2	Coaxial-connected 10Mbit/s Ethernet
UDP	User datagram protocol
USB	Universal serial bus

TEST EQUIPMENT SOLUTIONS

Quality second user test equipment bought and sold

All purchases backed with full one-year warranty and technical support

AMPLIFIERS


	GBP
Amplifier Research 1W1000 1GHz 1W Amplifier	1850
HP 8449A 22GHz Pre-amplifier	4950
Kalmus AS0204-17R 2-4GHz 17 Watt Amplifier	4950
Kalmus AS0822-30R 0.8-2.2GHz 30 Watt Amplifier	6950

CALIBRATORS

Fluke 5220A Transconductance Amplifier	2400
Fluke 5200A DMM Calibrator	1950

COMPONENT ANALYSERS

HP 4084B Switching Matrix Controller	4500
HP 4085A Switching Matrix	4500
HP 4085M Switching Matrix	5500
HP 4275A 10MHz Impedance Analyser	2950

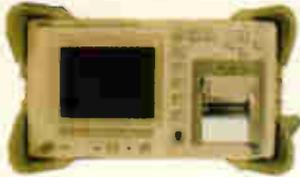

DATA COMMS

Fluke DSP-100 Cat 5 Cable Tester	1450
Fluke DSP-FDM Fibre Optic Meter For Fluke DSP Series	350
Microtest MT340 Cat 5 Tester	950
Microtest PentaScanner+ Cat 5 Cable Tester	1450

ELECTRICAL NOISE

HP 8970B 1.6GHz Noise Meter	8500
HP 346B 18GHz APC-3.5 Noise Source	1250

EMC

R & S EB 100 Miniport Receiver 20-1000MHz	3750
R & S EP2 100 Mini Panoramic Display	1250

FREQUENCY COUNTERS

HP 5342A 18GHz Frequency Counter	1750
HP 5343A 26.5GHz Frequency Counter	2950
HP 5372A 500 MHz Frequency / Time Interval Analyser	7950
Marconi CPM46 Counter Power Meter	5000
Philips PM6654C/S26 1.5GHz/2ns Counter Timer	1250
Philips PM6666 1.3GHz Counter Timer with MTCKO	750
Racal 1992 / 55 1.3GHz Frequency Counter	1250



FUNCTION GENERATORS

HP 3314A 20MHz Function Generator	1950
HP 3325B/002 21MHz Function Generator	3750
HP 8165A Function Generator	1250
Philips PMS193 50MHz Function Generator	1450

LOGIC ANALYSERS

HP 16500C Logic Analyser Mainframe	4950
HP 16515A 16 Channel Logic Analyser Card	1200
HP 16550A Timing Analysis Module	2950
HP 1650A 80 Channel Logic Analyser	1000
HP 1661C Logic Analyser	3500

NETWORK ANALYSERS

Anritsu S251A 2.5GHz 2 Port Scalar Network Analyser	7950
Anritsu S331A 3.3GHz Scalar Network Analyser	5750
HP 8510C 50GHz Microwave Network Analyser	25000
HP 8514B 20GHz S Parameter Test Set	16400
HP8711A 1.3GHz Network Analyser	5500
HP 8714C 300MHz-3GHz Vector Network Analyser	11950
HP8752A/003 3GHz Network Analyser	10950
HP 8753B 3GHz Vector Network Analyser	8950
HP8753B/006 6GHz Network Analyser	11500

GBP

HP 8753C 3GHz Vector Network Analyser	13950
HP 85046A 3GHz S Parameter Test Set	3950
HP 85047A 6GHz S Parameter Test Set (50 Ohm)	6500
HP 8757B 20GHz Scalar Network Analyser	5500

OPTICAL FIBRE TEST

HP E6000A/E6003A 1310/1550 Single Mode Mini OTDR	5500
--------------------------------------------------	------

OSCILLOSCOPES

HP 54111D 2 Channel 500MHz Digitising Scope	2950
HP 54120T 4 Channel 20GHz Digitising Scope	9700
HP 54121T 4 Channel 20GHz Digitising Scope	13500
HP 54122T 4 Channel 12.4GHz Digitising Scope	11500
HP 54602A 4 Channel 150MHz 20MS/S DSO	1250
HP 54603B 2 Channel 60MHz Digitising Scope	1150
Philips PM3295A/40 2 Channel 400MHz Scope	1500
Philips PM3394B 4 Channel 200MHz CombiScope	4250
Tek 2445A 200MHz 4 Channel Analogue Scope	1500
Tek 2465B 400MHz 4 Channel Analogue Scope	2500
Tek AMS03/A6302/TMS01 Current Probe System	1850
Tek TAS465 2 Channel 100MHz Analogue Scope	695
Tek TDS350 200MHz 2 Channel Digitising Scope	1850
Tek TDS380 400MHz 2 Channel Digitising Scope	2500
Tek TDS380P 400MHz 2 Ch Digitising Scope inc Printer	2950
Tek TDS540 4 Channel 500MHz Digitising Scope	4950
Tek TDS540A 4 Channel 500MHz Digitising Scope	5750



POWER METERS

Gigatronics 80401A Power Sensor	395
Gigatronics 8542C Dual Channel RF Power Meter	2500
HP 436A/022 RF Power Meter With GPIB	750
HP 438A/002 Dual Channel RF Power Meter	1950
Various HP 848x Power Sensors (From)	300
HP EPM441A/003 (E4418A) RF Power Meter	2150
HP E4419A Dual Channel Power Meter	2850
HP ECPE18A (E4412A) 18GHz Power Sensor	750
Marconi 6960 / GPIB RF Power Meter	695
Various Marconi 69xx Power Sensors (From)	350
Rohde & Schwarz NWD Dual Channel RF Power Meter	2500

POWER SUPPLIES

HP 6623A 50V 0.8A Triple Power Supply	2300
HP 6632A 20V 5A Power Supply	1250
HP 6652A 20V 25A PSU	795
HP E3610A 15V 3A DC PSU	150
HP E3615A 20V 3A DC Power Supply	195
HP E3631A 25V 5A DC PSU	650
Hunting Hivolt Series 250 50kV, 5mA Power Supply	850

RF SWEEP GENERATORS

HP 8341B 20GHz Synthesized Signal Generator	17500
---------------------------------------------	-------



SIGNAL & SPECTRUM ANALYSERS

Advantest R3361A 2.6GHz Spec Analyser inc T/Gen	7500
Advantest R4131C 3.5GHz Spectrum Analyser	3950
Advantest R4131D 3.5GHz Spectrum Analyser	4500
Advantest R9211A 100MHz Dual Channel FFT Analyser	3950
Anritsu MS2601B 2.2GHz Spectrum Analyser	5500
Anritsu MS2663A 8GHz Spectrum Analyser	8950
HP 3561A 100MHz Dynamic Signal Analyser	3250
HP 35660A 102.5MHz Dynamic Signal Analyser	2950
HP 3585A 40MHz Spectrum Analyser	4500
HP 70000 2.9GHz Spectrum Analyser	10000
HP 85024A 3GHz Zero Loss Probe	1350
HP 8560A 2.9GHz Spectrum Analyser	9950

GBP

HP 8562A 9KHz-22GHz Spectrum Analyser	13950
HP 8590A 1.5GHz Spectrum Analyser	2750
HP 8591A / 021 1.8GHz Spectrum Analyser	5500
HP8594E/041/101/105 2.9GHz Spectrum Analyser	9950
HP8596E 12.8GHz Spectrum Analyser	16950
HP 8901A 1.3GHz Modulation Analyser	1250
Tek WM780V 50-75GHz Mixer Set	900

SIGNAL GENERATORS

Advantest R4262/ 023 4.5GHz Signal Generator	12500
HP 8642A/01 1GHz High Performance Signal Generator	2500
HP 8656B /001 1GHz Synthesised Signal Generator	1150
HP 8657B 2GHz Signal Generator	5500
HP 8672S 0.1-18GHz Synthesised Signal Generator	9950
HP 8673B 2-26GHz Synthesised Signal Generator	11950
HP 8683D 2.3-13GHz Signal Generator	6950
Marconi 2017 1GHz Low Noise Signal Generator	1000
Marconi 2019A 1GHz Signal Generator	1000
Marconi 2022 1GHz Signal Generator	650
Marconi 2031 2.7GHz Signal Generator	7250
R & S SMH 2GHz Signal Generator	6950
R & S SMU 4.3GHz Signal Generator	13500
R & S SMUS8/B2 Signal generator with GMSK Coder	15500
R & S SMIQ03/B10/B11 3.3GHz Signal Generator	16500
R & S SMY02 9KHz-2GHz Signal Generator	4950

SWITCHES & MULTIPLEXERS

HP 3488A Switch / Control Unit	295
Various HP 444xx Switch Cards (From)	150



TELECOMS

Anritsu MD6420A Data Transmission Analyser	2500
Anritsu MD0623C 2MBPS CEPT Interface	1500
Anritsu MS371A PCM Frame Analyser	3500
GM Metttest LITE 3000	2250
HP 33722A/004/006 Digital Telecom Analyser	4950
HP 3788A/001 2MBPS Error Performance Analyser	1950
Marconi 2840A 2MBPS BERT Tester	1950
Marconi Tricon Signalling Test set	2500
Sunrise Telecom SUNSET E10 Communication Analyser	3900
Trend Aurora Duet (Basic rate only) ISDN Tester	2250
Trend Aurora Plus Handheld Basic Rate ISDN Tester	350
Trend Aurora 30 Handheld Primary Rate ISDN Tester	1500
TTC Fireberd 6000 Optis 6007/6008	5500
Various TTC Interfaces (From)	400
W&G PCM-4 Channel Measuring Set (Configs From)	9000
W&G PFA-35 2MBPS Communications Tester	4950
W & G DST-1 Handheld E&M Signalling Tester	950
W & G PA-20 PCM Performance Analyser	1950
W & G PCM23 Voice Frequency PCM Tester	1950

WIRELESS

HP 3708A Noise And Interference Test Set	15000
HP 83220A/022 PCS/DCS1800 Test Set	3950
HP 8920A 1GHz Radio Comms Test Set (Configs From)	5950
HP 8922H GSM Test Set	8500
Marconi 2945A /001/003/023 Radio Comms Test Set	7500
Marconi 2955 Radio Comms Test Set	1950
Marconi 2955B Radio Comms Test Set	3500
Racal 6103/001/002 GSM/DCS Test Set	7500
R & S CMS52/B1 Radio Comms Test Set	4850
R & S CMT54 B1/B4/B5/B6/B9 Radio Comms Test Set	4500
R & S CMT56/B1/4/6/9/11/13/17/19 Radio Comms Test Set	2250
R & S CMT84 B1/B5/B6/B9 Radio Comms Test Set	4950
R & S CMT84/B5/B6/B8 Radio Comms Test Set	4500
R & S TS120/0 / B1/3/4/6/41/61/62 DECT Protocol Tester	49500
Schlumberger Stablock 4039 Radio Comms Test Set	1250
Stablock 4015 with Duplex and IEEE Radio Comms Test Set	4500

See our extensive online catalogue at www.TestEquipmentHQ.com Flexible commercial solutions available on all products.

Prices shown are in £UK and are exclusive of VAT. Free carriage to UK mainland addresses. This is just a selection of the equipment we have available - if you don't see what you want, please call. All items supplied fully tested and refurbished with one year warranty. All manuals and accessories required for normal operation included. Certificate of Conformance supplied as standard; Certificate of Calibration available at additional cost. Most items delivered in 1-2 weeks. Test Equipment Solutions Terms Apply. E&OE.

01753 59 6000
fax: 01753 59 6001

www.TestEquipmentHQ.com
 email: info@TestEquipmentHQ.com

CIRCLE NO. 112 ON REPLY CARD

FREE

Free Palm m100 shipped with every order over £10K

Network functionality is usually supplied in the form of a 'C' software library or module that the user compiles or links with their existing code. This is sometimes a cut down, but workable, version of the standard sockets library.

If you do not want to use a ready-made card, there is nothing much available at the single chip level. Notable exceptions are the iChip systems from ConnectOne and Seiko. Originally offered as a set of software/firmware licences implemented in ASIC form, this is now available in single-chip form (the Seiko part number is 7600). A US company, Ipsil, has just announced another single chip device. More devices are expected to appear in the future.

I have found some of the claims made for these products are in the 'flexible with the truth' class. This is reflected in the unnecessarily long times taken to get the software to work properly and reliably. These difficulties are possibly due to the newness of the technology, but it is a hard way for you to learn.

Roll your own or boil in the bag?

If you want to network your application, depending on how complex it is, you will need to decide whether to go for the ready-made route, i.e. buy cards, modules or components in, or roll your own.

If you are starting from scratch, the initial learning curve is pretty steep. Using a ready-made solution may be your only option. It is pointless to re-invent the wheel.

If you are considering quantities or reliability, a deeper knowledge of the product and its performance may be important. In practice, this means that you could spend as much time trying to get an external offering to work properly and reliably –

especially one that doesn't perform as well as advertised – as you would developing your own from scratch.

Again, depending on your requirements, you will need to evaluate how many functions are necessary for your application. It is pointless to include the full TCP stack into a product that would be happy to communicate using simple UDP packets. This is a waste of code space, components and resources. Is speed of access important? Is your field of work in real-time systems? If so, you should consider alternative network models.

As I mentioned earlier, the ready-made controller described in the next article may help you a little bit with this decision process. It will allow you to evaluate and try possibilities and use it in prototypes.

Because the controller provides access to the data stream at various levels, it can also be used as a teaching tool, and as a component in a more advanced network tester or server. It was originally designed as a tool for evaluating network stress.

I have used two processors for the controller. One handles the protocol interactions and another, supplied and written by the user, handles the application.

Data transfer between the two processors is via simple serial commands. The boring overheads such as checksums and framing are completely handled by the main controller.

Still confused?

If you have managed to get this far, and still you think you have not understood networks, don't despair. The next few sections will unravel some of the theory, and explain what you need to know.

No article on Internet basics can do without a guided tour of the

technology, from the bit-shifting protocols to the higher level scripts. I am not going to cover this in any detail, as there is plenty of information around in books and magazines. What I have done is a quick tour of the basic concepts involved, with special relevance to a microcontroller-based implementation.

References mentioned later in this article contain all the extra detail you may ever need. The main sources for detailed specifications are 'RFCs' or 'requests for comments'. The text contains the reference number that relates to the topic. You can find RFCs on the Internet by searching under 'RFC'.

Ethernet

You may already have a network connector on the back of your computer. Look for a BNC socket with a coaxial cable (remember RG-58U?), or a flat cable ending in something looking like a plastic telephone connector.

In most offices, these wires just disappear down the back of the desk only to reappear at some obscure room at the end of the corridor.

Ethernet is one of the main survivors among a number of similar technologies developed in the 1970s and 80s, possibly because of its 'low tech' simple and reliable approach. The coaxial cable 'thin-wire' version – also known as 10Base2 – is widely used in low-end applications.

Thin-wire Ethernet is simplicity itself; all workstations are connected together in daisy-chain fashion with a 50Ω terminator at each end of the chain. Data packets are just bursts of current fed into the impedance of the wire, and are read as voltages by the receivers.

Transmitters fire bursts more or less without the knowledge of any other transmitters. Collisions – i.e. when two generators feed the wire at the same time – are detected by an abnormal rise in the voltage on the wire as two or more currents superimpose. Each transmitter then waits for a certain random time before attempting to transmit again.

The flat, or twisted, cable variation – known as 10BaseT – uses separate wires for transmit and receive; this gives better error immunity and simpler driver circuitry at each end. However, workstations cannot just be

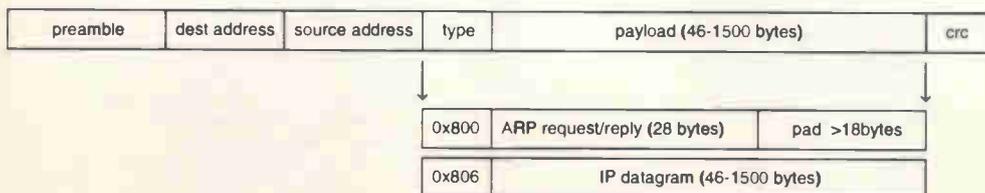


Fig. 4. Ethernet frames comprise a 6-byte destination and source addresses, plus a field word indicating the type of payload carried. The two most common payloads relevant to the TCP/IP world are shown in the figure. The preamble is a string of 62 bits used to synchronise the internal clock generator. A 4-byte CRC word terminates the packet. The Ethernet interface chip strips the headers, performs address comparison and checks for CRC validity before placing the data block in the RAM buffer.

connected to each other. Rather, they need to be connected to a central 'hub', which acts more or less like a repeater or distributor. Other methods are available, working on similar electrical principles.

In terms of speed, two main flavours are available, 10MHz and 100MHz. In many small office and home environments, 10MHz is the most popular. It is easy to install, and the cables are easily cut and crimped. I will only be considering the 10MHz version from now on.

How fast will it go?

A speed of 10MHz sounds appealing when considering using a LAN for interfacing to external I/O devices. Reality is different though; you have to consider the inefficiencies of any start-stop burst protocol, plus gridlock effect caused by collisions and other users sharing the network.

There are many good and bad statistics around showing relationships between usage and throughput. Just as on today's motorways, you can experience hold-ups at the most obscure times and for no apparent reason. Anybody designing equipment using a network for data transfer must be well aware of this.

As a conservative estimate, just one PC with one interface and no other users should be able to exchange data at between 70% and 90% of the full advertised speed.

Throughput decays drastically when more users are on the network at the same time. The 'sensormag' article in the reference includes some charts and calculations plus a pointer to an Excel program for estimating these delays.

In terms of hardware support, there are dedicated Ethernet interface chips available from various manufacturers. Most are compatible with a standard generic architecture, known as NE2000. They have a standard 8 or 16-bit data bus interface, compatible with most CPU addressing schemes.

Access to the chip is done via a number of internally paged registers, usually arranged as sixteen I/O or memory locations. Most chips can be directly connected to a CPU memory bus, or even directly to a PC-bus edge connector. The blocks of data being transferred are stored in FIFO memory, as a buffer

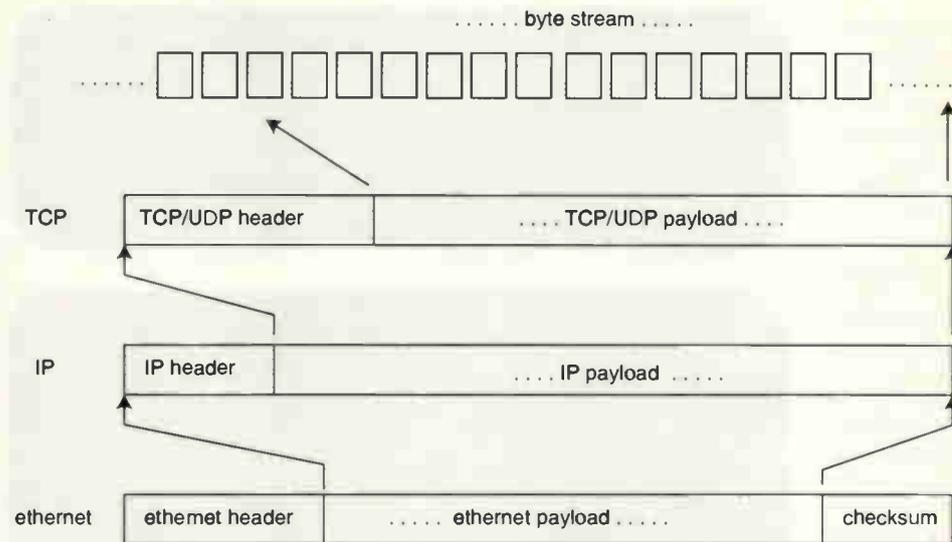


Fig. 5. Russian dolls: each protocol packet contains inside another packet of a higher level protocol. Each layer contributes something to the end result: addressing, routing fragmentation, transport, error control and error correction. The end result, in the case of TCP, is a continuous, reliable data byte stream.

area for the different speeds between the LAN and the rest of the system.

Using the chip involves first initialising a number of registers to set the various operating modes to determine, for example, whether transfers are 8 or 16-bit. Then, using a loop or interrupt routine, the chip waits for a data register ready flag, denoting that so many bytes of received data are present on the FIFO buffer.

On transmission the system places its data in another part of the RAM buffer, and sets a flag, which is usually reset at the end of transmission.

More detailed information on the workings of Ethernet interface chips can be found in manufacturers' data sheets. Unfortunately, there doesn't seem to be much information available on the Internet apart from some National Semiconductor data sheets, as mentioned in the panel.

Protocols, addressing and payloads

Ethernet data packets – better known as frames – cannot be of just any size. If you were to do some simple calculations involving the maximum distance between workstations, the speed of light in coaxial cable and various other timing considerations about collision detection, you would work out that frames cannot contain fewer than 46, or more than 1500 payload bytes each, Fig. 4.

Every Ethernet frame has a header consisting of a 6-byte source address, a 6-byte destination address, and a 2-byte protocol identifier. This is then followed by the payload, which as mentioned before, can only have between 46 and 1500 bytes.

On receipt of a frame without errors, this payload is 'peeled off' and passed on to the rest of the system. The protocol identifier field specifies which type of protocol the payload is carrying. For example, 0x806 denotes an Internet protocol, or 'IP' message.

The payload will have its own header and payload part, which are dealt with by the next layer in the chain. This is the concept of protocol 'layers', Fig. 5.

It is important to know that Ethernet data bursts or frames are completely independent of each other. Frames are fired like bullets out of a gun, and, apart from a collision detection mechanism during transmission, what happens to them afterwards is of no further concern to the transmitter. In other words, the Ethernet network layer does not provide for any global form of flow control or error protection.

At the other end, received frames are checked for consistency by calculating their CRC. Frames arriving with errors are simply dropped or ignored. It is up to the higher layers to provide for any form of flow control and error

Fig. 6. Commands are available from the DOS prompt that allow you to check your network interfaces. A PC workstation maintains a local cache of other workstation addresses, which is updated every two minutes or so. Network stations regularly transmit ARP packets to each other to maintain their caches up to date. The DOS command arp is used to display and/or update your local cache.

```
C:\>arp -a
Interface: 192.168.0.1 on Interface 0x2
Internet Address      Physical Address      Type
192.168.0.2           00-c0-d2-ee-83-5c    dynamic
192.168.0.15          45-54-40-50-49-43    dynamic
C:\>
```

```
C:\>ping 192.168.0.15
Pinging 192.168.0.15 with 32 bytes of data:

Reply from 192.168.0.15: bytes=32 time<10ms TTL=128

Ping statistics for 192.168.0.15:
    Packets: sent = 4, Received = 4, Lost = 0 (0% loss),
    Approximate round trip times in milli-seconds:
        Minimum = 0ms, Maximum = 0ms, Average = 0ms
C:\>
```

Fig. 7. Ping sends a probe packet to a remote IP destination, which just echoes the packet back. The sender can use the information collected on the way to deduce aspects of the path, delays, users, route taken, etc. The name ping is derived from submarine echo sounders. Ping is a very useful facility for advanced network support. The controller described in this article can be used to generate custom ping type packets.

protection.

It is also relevant to note that the source and destination addresses are 'hardware' addresses. Known as media access control, or 'MAC', numbers, they refer to 6-byte patterns uniquely associated with each Ethernet card and usually assigned at manufacture.

In practice, the address is stored in a separate serial EEPROM on the PC card. Blocks of addresses are assigned by the IEEE to each manufacturer, so when you buy your PC card, it will have its own unique number stored in it.

You can change this number if you want to. Apart from some simple restrictions, such as that the first byte in the sequence must have a '1' and a '0' as its least-significant bits, any number can be used as long as there are no clashes with other cards in your network.

It is not practicable to rely on fixed hardware addresses when managing a real computer network. Therefore, a more flexible form of addressing is used. This addressing scheme consists of four byte sequences, known as 'IP' addresses. They are displayed for human consumption as four decimal

numbers, e.g. '192.168.0.1'.

In a computer network, each workstation is allocated its own IP address, maybe once only by the network manager, or dynamically at various times by a program in the network server. Each workstation with an Ethernet card will also have its own hardware MAC address.

The four-byte IP address means nothing to the Ethernet card. Ethernet frames contain only MAC addresses as destinations. Sending a packet of data to a remote location requires knowing its MAC address.

If you connect a black box into a network containing a controller and data logger for example, you must allocate it an IP address, and notify everybody else of it. But how does the rest of the network know what our hardware MAC address is, and how to access the controller? You need to know about ARP to answer this one. For more on Ethernet and IP, see RFC894.

ARP

As I mentioned earlier, the payload in an Ethernet frame can carry formats other than IP. One such format is ARP, which is a simple query-response packet protocol used

to match workstations hardware addresses and IP addresses. ARP stands for address-resolution protocol.

In a typical network, computers spend a small part of their time sniffing each other, that is, sending short probe packets to see who else is around. This is usually done on a regular, or on a 'need to know' basis. The ARP protocol is used for just that. It makes use of a special MAC 'broadcast' destination address (0xFFFFFFFF).

All Ethernet stations on the network accept broadcast messages. The broadcast message basically says, "Hey out there, anybody with IP address 192.168.0.15?" The one and only station having this IP address allocated will then reply with a packet stating its hardware MAC address.

In a Windows network each workstation builds up and maintains a local table of IP versus MAC address pairs. Before sending a message to another station, the table is consulted. If there is no entry, an ARP query message is sent out. The table is dynamically maintained, flushed and refreshed every few minutes.

Windows provides a number of tools and facilities, mainly supplied as DOS console programs, which you can use to see this in action. Open an MS-DOS command box in your computer and enter "c:>ARP(if the program is not available in your machine, try installing these components from the New programs/communications tools Wizard). The program arp will display the current IP/MAC address pairs for all the local machines in your network. You may see nothing, especially if there was no recent network activity. Remember that the tables are dynamic and flushed every few minutes.

Next, enter "C:>ping 192.168.0.15" – or the address of any other station on your network – and wait to see any replies, then try "C:>arp -a" again. Assuming that your prototype controller is connected to the network, the screen will show '192.168.0.15 4E-54-54-50-49-43,' Figs 6, 7.

Any embedded Ethernet controller must include some form of ARP reply processing in order to respond to 'who are you?'-type requests made by other stations on the network. The controller also needs

New Version 2001 out now!



"multiSIM could very well herald the next step forward in PCB design methodology, because it can co-simulate both HDL and SPICE components... at a very affordable price"

SIMPLY THE BEST

Schematic Capture, Simulation & Programmable Logic

multisIM - the professional solution from Electronics Workbench.

Schematic capture, SPICE/VHDL/Verilog co-simulation of analogue and digital parts, built-in analyses and virtual instruments, and a huge library of parts in a single, affordable package.

Call **01462 480055** today for your FREE product guide or visit www.adeptscience.co.uk



Adept Scientific plc, Amor Way, Letchworth, Herts SG6 1ZA
Tel: 01462 480055 • Fax: 01462 480213
Email: ewb@adeptscience.co.uk
WebStore: www.adeptstore.co.uk



Electronics
multisIM

CIRCLE NO.113 ON REPLY CARD

MARCONI 2019A



AM/FM synthesised signal generator 80KHz-1040KHz

NOW ONLY £400

- H.P. 3312A Fun Gen 0.1Hz-13MHz.....£300
- AM/FM Sweep/Tri/Gate/Burst etc. H.P. 3310A Fun Gen 0.005Hz-5MHz.....£125
- Sine/Sq/Tri/Ramp/Pulse FARNELL LFM4 Sine/Sq Oscillator 10Hz-1MHz.....£125
- Low distortion, TTL Output, Amplitude Meter H.P. 545A Logic Probe with 546A Logic Pulsar.....£90 and 547A Current Tracer
- FLUKE 77 Multimeter 3 1/2 digit Handheld.....£60
- FLUKE 77 Series 11.....£70
- HEME 1000 LCD Clamp Meter 0-1000A In Carrying Case.....£60

RACAL 900B AUTOMATIC MODULATION METER AM/FM 1.5MHz-2GHz



ONLY £95

- H.P. 8494A Attenuator DC-4GHz 0-11dB N/SMA.....£250
- H.P. 8492A Attenuator DC-18GHz 0-6dB APC.....£95
- MANY OTHER ATTENUATORS, LOADS, COUPLERS etc AVAILABLE

DATRON 1061 HIGH QUALITY 5 1/2 DIGIT BENCH MULTIMETER True RMS/4 wire Res/Current Converter/IEEE

£150

- MARCONI TF2015 AM/FM sig gen. 10-520MHz.....£175
- RACAL 980B Auto Mod Meter. 1.5MHz-2GHz.....£200
- LEVELL TG2000MP PC Oscillator. 1Hz-1MHz.....£50
- Sine/Sq. Metr. battery operated (batts not supplied)
- FARNELL LF1 Sine Sq. Oscillator, 10Hz-1MHz.....£75
- RACAL/AM 9343M LCR Databridge. Digital Auto.....£200

STILL AVAILABLE • PREVIOUSLY ADVERTISED WITH PHOTOS

- MARCONI 893C AF Power Meter. Sinad Measurement Unused.....£100
- Others: Avion from £50
- GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused.....£75
- GOODWILL GVT427 Dual Ch AC Millivoltmeter. £100-£125
- 10mV-300V in 12 Ranges Freq 10Hz-1MHz
- SOLARTRON 7150 OMM 6 1/2 digit True RMS - IEEE £95-£150
- GOULD J3B Sine/Sq Osc. 10Hz-100KHz. Low distortion £75-£125

AVO 8MK8 in Ever Ready Case, with leads etc. £80

Others: Avion from £50

GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused.....£75

GOODWILL GVT427 Dual Ch AC Millivoltmeter. £100-£125

10mV-300V in 12 Ranges Freq 10Hz-1MHz

SOLARTRON 7150 OMM 6 1/2 digit True RMS - IEEE £95-£150

GOULD J3B Sine/Sq Osc. 10Hz-100KHz. Low distortion £75-£125

AVO 8MK8 in Ever Ready Case, with leads etc. £80

Others: Avion from £50

GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused.....£75

GOODWILL GVT427 Dual Ch AC Millivoltmeter. £100-£125

10mV-300V in 12 Ranges Freq 10Hz-1MHz

SOLARTRON 7150 Plus

RACAL TRUE RMS VOLTMETERS

9380 5Hz-20MHz usable to 60MHz, 10V-316V.....£95

9309B Version.....£150

9301/9302 RF Version to 1.5GHz from.....£200-£300

HIGH QUALITY RACAL COUNTERS

9804 Universal Timer Counter. £250

9916 Counter, 10Hz-500MHz.....£75

9918 Counter, 10Hz-500MHz, 9-digit.....£50

FARNELL AMM255 Automatic Mod Meter 1.5MHz-2GHz Unused.....£400

Others: Avion from £50

GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused.....£75

GOODWILL GVT427 Dual Ch AC Millivoltmeter. £100-£125

10mV-300V in 12 Ranges Freq 10Hz-1MHz

SOLARTRON 7150 Plus

RACAL TRUE RMS VOLTMETERS

9380 5Hz-20MHz usable to 60MHz, 10V-316V.....£95

9309B Version.....£150

9301/9302 RF Version to 1.5GHz from.....£200-£300

HIGH QUALITY RACAL COUNTERS

9804 Universal Timer Counter. £250

9916 Counter, 10Hz-500MHz.....£75

9918 Counter, 10Hz-500MHz, 9-digit.....£50

FARNELL AMM255 Automatic Mod Meter 1.5MHz-2GHz Unused.....£400

Others: Avion from £50

GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused.....£75

GOODWILL GVT427 Dual Ch AC Millivoltmeter. £100-£125

10mV-300V in 12 Ranges Freq 10Hz-1MHz

SOLARTRON 7150 Plus

RACAL TRUE RMS VOLTMETERS

9380 5Hz-20MHz usable to 60MHz, 10V-316V.....£95

9309B Version.....£150

9301/9302 RF Version to 1.5GHz from.....£200-£300

HIGH QUALITY RACAL COUNTERS

9804 Universal Timer Counter. £250

9916 Counter, 10Hz-500MHz.....£75

9918 Counter, 10Hz-500MHz, 9-digit.....£50

FARNELL AMM255 Automatic Mod Meter 1.5MHz-2GHz Unused.....£400

Others: Avion from £50

GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused.....£75

GOODWILL GVT427 Dual Ch AC Millivoltmeter. £100-£125

10mV-300V in 12 Ranges Freq 10Hz-1MHz

SOLARTRON 7150 Plus

RACAL TRUE RMS VOLTMETERS

9380 5Hz-20MHz usable to 60MHz, 10V-316V.....£95

9309B Version.....£150

9301/9302 RF Version to 1.5GHz from.....£200-£300

HIGH QUALITY RACAL COUNTERS

9804 Universal Timer Counter. £250

9916 Counter, 10Hz-500MHz.....£75

9918 Counter, 10Hz-500MHz, 9-digit.....£50

FARNELL AMM255 Automatic Mod Meter 1.5MHz-2GHz Unused.....£400

Others: Avion from £50

GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused.....£7

to include methods for querying other workstations in the network for their MAC addresses using ARP requests. This is one of a number of necessary overheads that push up the amount of code required in the controller, but they are essential for the proper operation in a shared network.

More on ARP can be found in RFC 826. The next topic of interest is IP, the 'other' relevant format carried by Ethernet frames, Fig. 4.

Internet Protocol

Internet protocol, IP for short, forms the backbone of all TCP and UDP messaging. Like the rest, each IP packet – better known as datagrams – has itself a header and a payload component. RFC 791 is the basic document describing IP.

Within the IP header, the most important items of information are the source and destination IP addresses. For local communications between two stations in a local loop, the IP address in the IP header and the MAC address in the Ethernet frame header just preceding it will correspond to the same workstation computer. This may sound like unnecessary repetition, but this pairing is required for routers, where the fields may be different.

There are other various fields including a checksum, a fragmentation pointer, a protocol code for the payload, and the payload itself.

Like Ethernet frames, IP datagrams are independent of each other and contain no in-built error protection or recovery. So why is IP necessary? Well, IP is the common layer above all hardware-dependent transport mechanisms. Irrespective of how the devices are electrically connected together – be it via fibre, radio or phone lines – all data blocks end up as compatible IP datagrams.

The job of IP is to get the data block to its destination. Its main contributions are addressing, routing and fragmentation. Remember how Ethernet frames had a limited byte size range? Similar limitations also apply to other transport mechanisms: optical fibre, satellite links, etc. Internet protocol allows datagrams to be chopped (fragmented) into shorter sections of the right size for transmission and *vice versa*: short sections packed into single, longer datagrams.

The method employed for fragmentation is relevant for embedded systems. Fragmented datagrams include a 'pointer' indexing the position of the first byte of their data payload in an imaginary 64kb data buffer. Therefore, each IP datagram contains exact information about the position and size of their payload within this imaginary buffer. This allows for fragmented datagrams to be received out of

sequence. A receiver accumulates datagrams until they all neatly fit into a contiguous block.

It follows that fragmented IP datagrams are not really independent of each other. This will introduce a time element in any system. A receiver for example, has to consider when to give up waiting for missing out of order packets, and dump any previously stored.

Fragmented datagrams cause problems with small embedded systems. In theory, a receiver needs to allocate a 64kb buffer for every first out of sequence datagram received. This means one buffer for every different open socket (or channel) being serviced. This is impractical for small RAM limited systems.

One practical solution is to disallow or ignore fragmented IP datagrams. This may not be much of a problem if the transactions involved are small, e.g. for a small data logger. However, there may be problems for systems dealing with long streams of block-encoded data such as voice or video. Fragmentation is not much of a problem with TCP (see later on) as TCP can be engineered to use small segments to start with.

In a typical situation, an embedded system may need to deal with many sources or originators. Datagrams may be arriving from more than one source at the same time. The microcontroller will need to keep track of all, keeping state variables for each contact, to ensure the right replies are sent back to the right originators. In a PC this is easily handled using concurrent threads. But small microcontrollers do not have such niceties.

Three types of IP payloads are of interest here: ICMP, UDP and TCP.

ICMP

ICMP stands for 'Internet control-message protocol'. This is not a protocol used to transfer messages, but rather to provide a kind of internal maintenance messaging service.

One of the most common uses for ICMP is a service known as 'pinging'. This is a method where a workstation can query another by transmitting a special short 'ping' message and wait for an echo response, Fig. 7.

Any embedded implementation

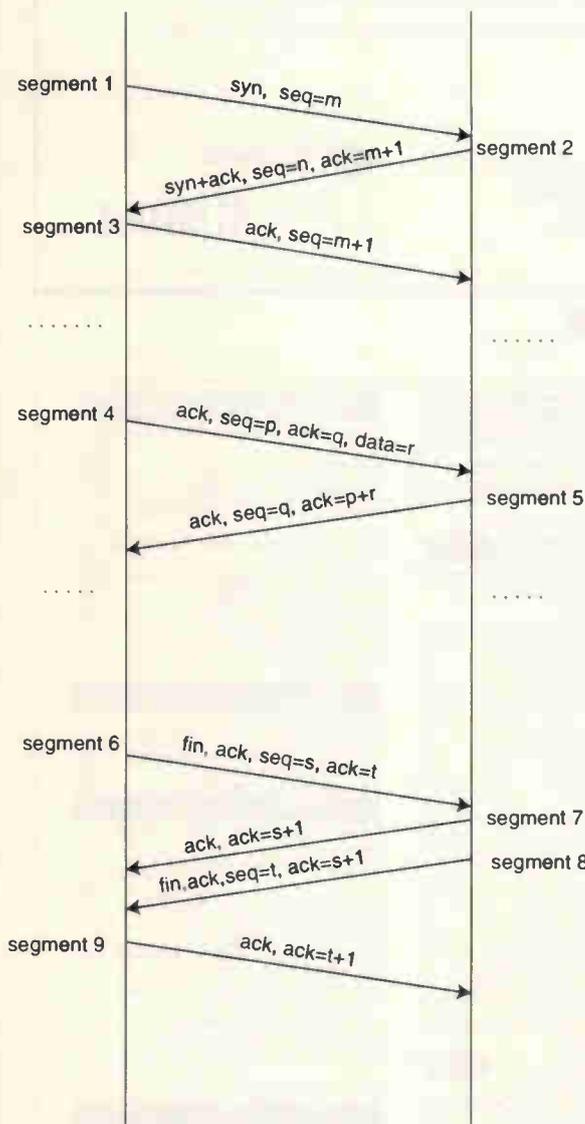


Fig. 8. Simplified diagram of a TCP conversation. Three stages are essential: setting up the channel, the actual data transfer process, and closing down the conversation. State transition tables are generally used in the software to implement the overall process. One set of tables and data memory buffers will be required for every open channel. This is not practical for small microcontroller memory limited applications.

should incorporate facilities for echoing any 'ping' commands received. There's more on this later.

Replies in ICMP are also commonly sent in response to failed UDP datagrams. An embedded application should also incorporate simple facilities for dealing with ICMP 'unobtainable' messages.

ICMP is documented in RFC 792, 950, 1812, 1122, 1191 and 1256.

Datagrams and UDP

User-datagram protocol, or UDP for short, is a simple transport-layer protocol. It is a connectionless, unreliable protocol with no error or flow control mechanisms.

In effect, UDP is nothing more sophisticated than an IP datagram with an extra addressing field: a port number. A port number is an interesting concept. If a workstation has an IP number allocated to it, how can different processes or programs in the workstation communicate at the same time? The answer is using ports.

Workstation "192.168.0.31" can use port 21 to talk to another workstation, use port 80 for web access and use port 27 for file transfers. Think of telephone extensions working off a main private exchange number.

Document RFC 768 fully describes UDP. Sending a UDP message is somewhat like sending a postcard to a friend, a simple 'shoot and forget'-type protocol. It can be very reliable in networks that are reliable to start with such as LANs.

This method is normally used for simple file transfers and remote booting of PCs. It is also used anywhere where a failure to receive is not a disastrous issue, or one that can be simply compensated by a repeat transmission later on.

Because of this simplicity, UDP is a simple protocol to implement in an embedded application. Simple error recovery can be implemented at the user level. This can take the form of mindless repetition to a simple 'ACK'-based datagram response. Writing the software at the PC end is also easy, as the program in List 1 shows.

The controller described here uses UDP to demonstrate simple read and write to a parallel and the analogue port. It also uses UDP for simple data connection to and from the user serial port. UDP is an effective protocol for developing special user applications.

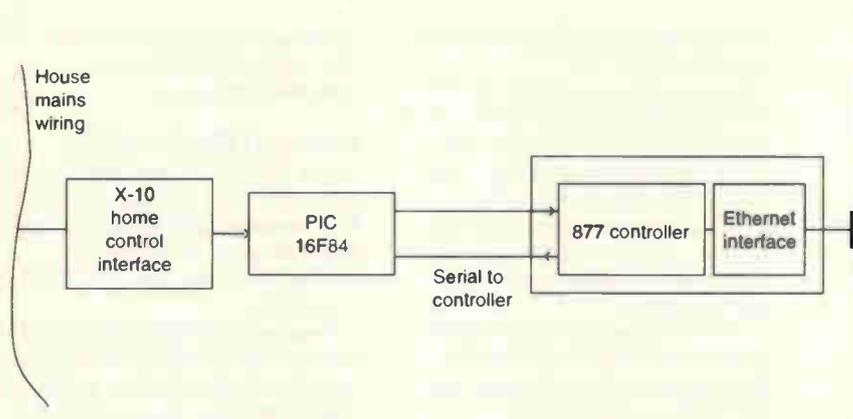


Fig. 9. X10 Home Control Interface: a separate PIC forms the basis of a simple interface between X10 home automation and the local area network. No interface standards exist at present for this kind of interactivity.

Transmission control protocol, TCP

Transmission control protocol, or TCP, is very different from UDP or to any of the protocols described previously. It is a point-to-point oriented, reliable, byte-stream service.

All error protection and flow control is carried out in TCP. The main document for this protocol is RFC 793. You will find additional information in RFC 896, 1122, 1323 and 2018.

Traditionally, error and flow control in telecommunications were handled at the lower layers. It was recently discovered that low-layer error handling is not as effective as higher layer handling. This is one of the reasons why the layers below TCP do not need to provide any form of error or flow management.

In UDP, stations just shoot packets at each other. TCP requires the two stations to establish a 'connection' first. Once the connection is established, data can flow from one station to the other.

Opening a connection is done by sending specially flagged segments – in TCP, a packet or unit of information is called a segment – that are used to synchronise counters and timers at either end, Fig. 8.

Transmission control protocol requires all data to be acknowledged. Rather than acknowledging each segment individually, TCP uses a pointer scheme where the receiver acknowledges the position of the index or pointer of the last reliable block of data received. Each segment thus carries a block of data plus an index pointer into an imaginary array of bytes, that is,

where the data block belongs in the array.

This scheme is very convenient as it allows segments to arrive out of order. There is no need to acknowledge every segment received, a single ack can be sent for more than one transmission segment received.

Both transmitter and receiver also operate a 'data window' scheme telling a transmitter how many more bytes the receiver is willing to accept. This provides a form of data flow control.

By constant adjustment of the windows and delays, TCP can be honed to provide an efficient flow mechanism tuned to a particular channel's characteristics. In such a channel, the transmission line is nearly constantly active all the time, with very few ACKs sent back.

You could see efficient and inefficient TCP in action by observing the TX and RX lights on a modem. Inefficient TCP is when both TX and RX flash or flicker in opposition, with periods of no activity in between. Efficient TCP is when the RX light is nearly constantly on, denoting a nearly constant flow, with the occasional flicker of the TX 'ACK' light.

Implementing TCP requires the use of a state transition table, linking 'actions' with 'states' and 'events', plus a data control block to store all variables for each particular connection – also known as a socket.

In normal practice a server, or listener, opens a new thread for every open connection request received from a client. This thread is maintained until the connection is

closed. The state table is described in detail in RFC 793.

Implementing the full set of TCP requirements in an embedded system is not trivial. Including each and every combination of events, states and actions will readily inflate a micro's valuable program and data memory space. In addition, threads are not easily implemented in the smaller devices.

Fortunately, some simplifications can be made if the connection has been coherent for a long time, and it is resilient to repeated and/or missing data. Depending on the use it is put to, it is possible to

Useful web sites

National Semiconductors Ethernet Chip data sheet

www.national.com/ds/DP/dp83905.pdf

General X-10 Home Control Information:

www.x10.com

More information on embedded Ethernet controllers:

www.embedded.com, www.chipcenter.com,

www.connectone.com, www.ipsil.com

RFC papers are available from various websites in different formats. Try one of the search engines such as www.google.com and enter the search word "RFC".

Useful article on Ethernet throughput and RTPS

www.sensormag.com/articles/1100/22/main.shtml

Further reading

TCP/IP Illustrated, Vol. 1, W. Richard Stevens, Addison Wesley, 2000. A very comprehensive guide for all aspects of TCP/IP. This is one of the best known books in the subject.

Windows 2000 TCP/IP Protocols and Services, Technical Reference, T. Lee and J. Davies, Microsoft Press, 2000. This book contains a CD with all published RFCs to date.

Network Programming for Windows, A. Jones and J. Ohlund, Microsoft Press, 1999. A must for anybody involved in network and Winsock programming. Many examples are included.

Interfacing Tini, Les Hughes, *Electronics World*, July 2000. A description of the Dallas Java-based web controller.

The author

Dr Eddy Insam is a consultant in innovative applications of telecommunications and specialises in graphics and signal processing. He can be reached on edinsam@eix.co.uk.

If you are considering a serious application for this device, Eddy will endeavour to answer your queries via e-mail.

implement a perfectly workable 'lite' version of TCP in an embedded processor.

Telnet, HTTP, FTP SMTP...

Telnet, HTTP, FTP and SMTP are higher level application protocols. They were designed for specific end-to-end purposes – FTP for file transfer, SMTP for mail, HTTP for web access.

These protocols have one thing in common. They work by sending and receiving streams of bytes, usually ASCII characters, down an already opened TCP connection.

In terms of implementation, these are relatively simple. One just needs to generate the right sequence of characters. As long as there is an existing TCP open channel to convey the characters, you could even use a BASIC-like program.

Implementing a simple web server involves nothing more than writing a program that receives an ASCII serial stream, senses for special character sequences, and sends back another sequence of characters.

RTPS – real-time networking

A number of alternative network models exists. Most are designed for particular applications such as stream voice, video, and real time control.

An abbreviation for 'real-time publish subscribe', RTPS is a good example of a recent innovation in networking models. Nodes 'publish' data onto a network or 'subscribe' to any data they need from the network. Subscriptions eliminate the need for request traffic.

The model is aimed at real-time control systems using the Ethernet, where speed of response and reaction has to be tightly controlled. A number of companies, among them General Motors, have evaluated the use of Ethernet in such schemes, and have found it a very reliable real-time transport medium.

RTPS technology is very recent, and typical of a number of similar developments to move away from the limitations of TCP. Companies such as RTI (www.rti.com) are offering components and toolkits under a \$10k licence.

For some small real-time applications, a subset of the technology is all that may be necessary. I have been looking at some implementation possibilities, and can see that this is an area that will see a lot more development in the future.

On telephones and modems...

I have limited the description to operation over a local area network. This may or may not be connected to the Internet via a router or server.

Most of you will be using a dial-up Internet service provider. The link between you and the ISP is via a modem. Generally, the protocol used on this link is called PPP (or the older variant SLIP).

The main purpose of PPP is to encapsulate IP datagrams into a form more suitable for modem communications; this is done by using special escape sequences to avoid transmitting characters such as ETX, which can produce odd effects on some modem links.

Extra PPP messaging sequences are used at the beginning of the transaction to negotiate details on the transmission methods used, types of compression, to exchange passwords and to allocate a dynamic IP address. Point-to-point protocol is not implemented in the present version of the controller. Even a simple version of PPP would take at least 2k of program space.

Implementing PPP is not trivial. 'Lite' versions of the protocol may not be very reliable, and can be very ISP dependent. PPP is a negotiated protocol; a negotiation can sporadically fail, say by a client requesting facilities that a server may refuse to provide at that time.

And home networks

The idea of intelligent buildings and home automation has been with us for a long time. Many proprietary standards and protocols for interfacing and control now exist; many are under development. These systems have found a slow uptake and difficult marketing, maybe because of the high cost of the interfaces and sensors.

The introduction of low-cost IP technology may influence future decisions on this subject. **Figure 9** shows a way a PC LAN could be linked to an X10 home-automation network. There are not many common or emerging protocols for such interfaces at present. ■

In the next article, Eddy discusses ways of implementing a simple controller based on a PIC 16F877 and a standard LAN PC card. This controller can be used for demonstrations or as the basis for an embedded prototype interface project.



Innovative ideas



New product news



Updates on research



Circuit diagrams

For your eyes only

Subscribe *NOW* and get your
own copy of **Electronics World**

See reverse for details...

Yes I'd like to subscribe to **Electronics World Today!**

Please enter my subscription for one of the following terms. When I subscribe for three years, I pay the price for just two years.

- | | UK | Europe | Rest of World |
|----------------------------------------------|------------------------------|-------------------------------|-------------------------------|
| <input type="checkbox"/> 3 years (36 issues) | <input type="checkbox"/> £72 | <input type="checkbox"/> £103 | <input type="checkbox"/> £123 |
| <input type="checkbox"/> 1 year (12 issues) | <input type="checkbox"/> £36 | <input type="checkbox"/> £51 | <input type="checkbox"/> £61 |

In every issue:

- Detailed circuit diagrams
- New product news
- Informative design-orientated explanations
- CAE software

...all this delivered direct to your door each month!

Full money back guarantee

If you're not completely satisfied with **Electronics World** within the first 60 days we'll refund your money in full - no questions asked.

Please allow 28 days for delivery of your first issue.

Reed Business Information Limited may use this information for direct marketing purposes, from ourselves or other companies. If you do not wish to receive direct marketing visit our data protection web page at www.reedbusiness.com/dataprotection or write to us at RBI, Freepost RCC2619, Haywards Heath RH16 3BR, UK



Reed Business Information Limited, Quadrant House,
The Quadrant, Sutton,
Surrey, SM2 5AS, UK. (Registered number 151537)

Three ways to pay

- 1 I enclose a cheque for £_____ made payable to **Electronics World**.
- 2 Please charge my Visa/Mastercard/American Express/Diners Club/Switch/Delta (Please delete as appropriate)

Card number

(Switch/Delta only)

Expiry date / / Valid from / / Issue no.

Signed _____ Date _____

3 Please invoice me/my company. Purchase Order No. _____

Name _____

Job title _____

Company _____

Address _____

Tel No. _____ Fax No. _____

E-mail address _____

Company VAT registration number _____

Return your completed form to:

Electronics World Subscriptions, FREEPOST RCC 2619,
PO BOX 302, HAYWARDS HEATH, UK, RH16 3BR

Fax: +44 (0)1444 445447 E-mail: rbi.subscriptions@rbi.co.uk

Credit Card Orders – (quoting code 158)

Tel: +44(0)1444 475662

List 1. Simple C code for the PC showing how to use the Winsock API to communicate with an external I/O device. Refer to the literature for more examples. This demonstration program shows how Winsock can be used for communicating between a PC and an embedded ethernet device. This is a Windows console application. To run, open a MSDOS box, and enter the name of the program followed by optional arguments.

Programming notes: If using Microsoft Visual C, open as a Windows console application, and copy this file to the directory.

Program must be linked with the Winsock 2 library "WS2_32.lib".

The Winsock DLL file "WS2_32.DLL" must be present in your system, usually already present in W95(SP2), W98, NT and W2K.

In order to reduce listing clutter and improve readability the code is kept as simple as possible with many parameters hard-coded in. For the same reason, error handling is implemented with simple "goto" type statements.

A useful reference (with samples) for winsock programming is A. Jones & J. Ohlund, 1999. "Network Programming for Windows", Microsoft Press.

```

//*****
//      Copyright (c) 2001, EIX ltd
//*****
//Command Line options:
//c:> exename [ipaddress]
//where ipaddress is destination address, e.g. 192.168.0.15
//*****
#include <winsock2.h>
#include "stdio.h"
#include "stdlib.h"
/** main entry point to the program
int main(int argc, char* argv[])
(
/** First, initialise any global variables to their default
char zIPadd[32];
strcpy(zIPadd, "192.168.0.15"); // default
destination IP address
/** Next, deal with any user input provided in Command Line
for (int i=1; i<argc; i++)
( if (argv[i][0]>'0') strcpy(zIPadd, argv[i][0]);
)
/** Initialise Winsock 2...
//Loads or increments DLL usage count.
//Must call WSACleanup() on exit!
WSADATA wsadata;
if (WSAStartup(0x202, &wsadata) != 0)
( printf ("Winsock 2 cannot be loaded, error %d",
GetLastError());
return -1;
)
/** Create our socket...
// Socket is initialised for UDP datagram transactions
SOCKET hSocket=socket(AF_INET, SOCK_DGRAM, 0);
if (hSocket == INVALID_SOCKET)
( printf ("Socket creation failed, error %d",
GetLastError());
goto Exit; //simple abort avoids listing clutter
)
/** Define destination as a socket structure...
//Note the use of the standard Winsock functions htons and
inet_addr
// htons() reverses byte endian order, needed for IP packets
// inet_addr() converts IP strings such as "190.0.0.1" into
IP DWORD
SOCKADDR_IN Sdest;
Sdest.sin_family= AF_INET;
Sdest.sin_port= htons(0x5001); //hard-coded
dest port
Sdest.sin_addr.s_addr= inet_addr(zIPadd); //dest IP
address
/** Now transmit the data...
//Winsock will send the UDP datagram to the socket specified
//in Sdest. The function also generates a local receive"
//port number for replies.
(
//Create some useful data to transmit. We shall be

```

```

//hardcoding the message for this demonstration.
char pTx[8];
pTx[0]=0x01; pTx[1]=rand(); //set the LEDs to some
random
pattern
pTx[2]=0x03; pTx[3]=0; //read data port in A
int nTx=4; // tot of 4 bytes in tx
packet

// The actual TX call
SOCKET stx=sendto(hSocket, pTx, nTx, 0,
(SOCKADDR*)&Sdest, sizeof(Sdest));
if (stx== SOCKET_ERROR)
( printf("Sendto() failed, error %d",GetLastError());
goto Exit;
)
)
//Having sent the data packet, we now need to wait for a
//response. Before calling the receive function, we
//could install a receiver timeout, this can be useful for
//avoiding call from blocking forever if no data received
( int to=3000; // hardcode a 3 second timeout
int
nr=setsockopt(hSocket, SOL_SOCKET, SO_RCVTIMEO, (char*)&to, size
of(to));
if (nr == SOCKET_ERROR)
( printf("setsockopt(SO_RCVTIMEO) failed, error: %d",
GetLastError());
goto Exit;
)
)
/** Waste one second...
//No need to include this in your program. This is only
//here to let the reply packet enough time to arrive before
//next function is called.
Sleep(1000);

/** Check nr of bytes in rx buffer...
// Again, no need to include this function in your
program.
// This is only here to show a possible way of sensing
if there are
// any bytes left in the receive buffer before calling
recvfom().
( DWORD nb;
int e=ioctlsocket(hSocket, FIONREAD, &nb);
if(e==SOCKET_ERROR) ( printf("Ioctl
error:%d",GetLastError());
goto Exit;
)
printf("Rx buffer has %d characters\r\n",nb);
)
/** Call the receive function...
//This function may block until whole datagram is received
//or until a defined timeout occurs, if set as above).
( SOCKADDR Sremot;
Sremot.sa_family= AF_INET;
int nremot=sizeof(SOCKADDR);
char pRx[256]; int nRx=256; // rx data goes here
SOCKET srx=recvfom
(hSocket, pRx, nRx, 0, (SOCKADDR*)&Sremot, &nremot);
if (srx== SOCKET_ERROR)
( // handle the specific "error" case of a timeout
int ee=GetLastError();
if (ee==10060) printf("Receiver timed out, no data
received");
else printf("recvfom() failed, error
%d", ee);
goto Exit;
)
)
// If we get this far, data was received OK, so do something
with it!
printf("Received OK, first 4 bytes of data: ");
for (int i=0; i<4; i++) printf("%02X ", (BYTE)pRx[i]);
printf("\r\n");
)
/** Lastly, close socket, unload Winsock. and exit...
Exit:
closesocket(hSocket);
WSACleanup();
return 0;
)

```

Personal voice communications without a licence over a two mile radius for £75, exclusive.

Reader offer

A pair of two-way PMR radios for just £75*

RS 446 personal mobile radio...

To celebrate its launch, new test and instrumentation company Tecstar is offering *Electronics World* readers two RS446 personal mobile radios for just £75 excluding VAT and carriage.

Capable of transmitting and receiving voice over a distance of up to two miles, depending on terrain, the PMR 446 needs no licence. It offers eight channels, scanning – and with CTCSS up to 304 channel combinations.

A backlit liquid-crystal display shows volume level, channel number, sub-channel number, battery level and transmit/receive or channel busy. A unique call feature enables the user to alert the person they wish to contact.

Transmission distance is up to 2 miles. The radio has an accessory socket for an external headphone, earpiece or vox-microphone/headphone combination. A keypad lock and battery save feature are also standard.

The unit measures only 120 by 50 by 20mm and weighs less than 150 grams – including batteries. It is supplied complete with instructions and belt/mounting clip.

Compact, lightweight and low cost, the RS446 wireless personal-communications hand set has a wide range of applications. These include fetes, events and rallies. Builders on building sites could benefit from these radios, as could exhibitors at exhibitions and staff at warehouses, winter activities, sports events, maintenance departments, schools and care homes. Of course you can also use the RS446 just to keep contact with someone locally. The uses are almost limitless.

Send a cheque or postal orders to Tecstar Electronics Limited, 1 Nuffield Road, St Ives, Huntingdon Cambridgeshire PE27 3LX.

Tel 01480 399499, fax 01480 399503, e mail sales@tecstar.co.uk

Order coupon

Please send me RS446 personal mobile radios, for which I enclose:

For ___ pairs of RS446 radios at £75 per pair _____

Plus VAT at 17.5%, or £13.13 per pair _____

Plus £6 UK postage per order, or £14 overseas _____

Total _____

Fill in your name and address and post this coupon together with a cheque for the total amount above payable to Tecstar to the address below.

Name _____

Address _____

Post code _____

Signature _____

Send cheques, postal orders etc to Tecstar Electronics Limited, 1 Nuffield Road, St Ives, Huntingdon Cambridgeshire PE27 3LX.
Tel 01480 399499, fax 01480 399503, e mail sales@tecstar.co.uk

*excludes carriage and VAT

RS446 key features...

- Up to 2 mile coverage radius
- Scans main and subchannels
- Eight channels, each with 38 sub channels
- Backlit display for night time use
- Unique call function
- Headphone and mic sockets allow discrete use
- Battery status indicator
- Auto battery save feature
- Keypad lock-out

What is CTCSS

CTCSS – or 'continuous-tone controlled squelch system' – allows sub channels of the main channels to be used. There are 38 sub channels to each main channel. Using subchannels decreases the likelihood that someone else will be using the same frequency.

PIC Basic Pro

The Professionals Choice

Write your PIC programs in BASIC! - No STAMP REQUIRED!

PIC Basic - £59.95

Quicker and easier than 'C' or assembler. PIC BASIC is a true compiler providing faster execution and shorter programs than BASIC stamp interpreters, built in I2C routines and serial comms upto 115K Baud and full BASIC STAMP compatibility make writing for the Microchip PICmicro's easy! PIC BASIC compiles your basic language programs to Microchip Hex format for use with In-circuit emulators or for programming directly into the PIC CHIP. Supports PIC12C67x, PIC14Cxxx, PIC16C55x, 6xx, 8xx, 84, 92 and 16F87x. Full documentation with syntax examples are provided in the 168 page user manual. A technical support mailing list is provided for life time support.

PIC Basic Pro - £169.95 the professionals choice

The PIC BASIC Pro compiler instruction set is compatible with the Basic Stamp II providing additional functionality over PIC BASIC, feature like LCD, ADCin, I2CRead, I2CWrite customisable Serial In / out. (Create a serial LCD display driver in minutes). Full de-bug facilities, compile with debug to produce assembly commented with your Basic commands PIC BASIC and PIC BASIC PRO compile tight efficient code without the use of a basic interpreter. Supplied with a 168Page manual, explaining each command and worked examples FREE PIC Macro compiler, FREE Programmers File Editor, FREE Windows Front End. PIC BASIC PRO includes samples programs and code to support Smart card read&write.

Download the full 168 page PIC BASIC MANUAL and more

<http://www.picbasic.co.uk>

Order Online via our secure server

<http://www.crownhill.co.uk>

- ◆ Low cost programmer for PIC12Cxxx, PIC12CExxx, PIC14Cxxx, PIC16C505, 55x, 6xx, 7xx, 84, 9xx PIC 16CE62x and PIC16F87x
- ◆ ZIF adaptors are available for 8/18 In 40/28Pin DIL, 8, 18 and 28 SOIC, 44 Pin MQFP, 44 and 68 Pin PLCC
- ◆ Powered by 2x 9V batteries or AC adapter.
- ◆ Connects to PC parallel port
- ◆ Upgradable software is supplied for future PIC Micro's
- ◆ FREE 8051 style PIC Macro compiler



£35 When purchased with PIC BASIC

- Parallel port extension cable - £5.95
- 40Pin ZIF socket - £22.50
- 8/ 18Pin ZIF Socket - £22.50
- PIC8 Prototype board - £4.50
- PIC18 Prototype board - £5.50
- PIC64 Prototype board - £8.50

All prices are subject to VAT @ 17.5%

A comprehensive guide to using PIC BASIC

EXPERIMENTING
with the
PICBASIC PRO
COMPILER



By Les Johnson


A COLLECTION OF BUILDING BLOCKS
AND WORKING APPLICATIONS
USING MELABS
SIMPLE TO USE
YET POWERFUL COMPILER

A CROWNHILL PUBLICATION

- Section 1 Displays
- Section 2 Interfacing with Keypads
- Section 3 Serial Eeproms
- Section 4 Analogue to Digital Converters
- Section 5 Digital to Analogue Converters
- Section 6 Remote Control
- Section 7 Temperature Measurement
- Section 8 Robotics
- Section 9 Audio Control
- Section 10 Programming Techniques
- Section 11 Powering Up the PIC

Free Download: Section 3 from www.picbasic.co.uk
Available NOW! £24.95 +P&P

SMARTCARD DEVELOPMENT SYSTEM

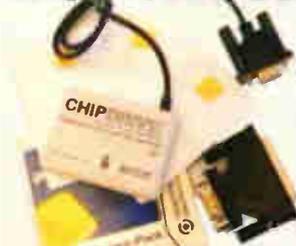

ChipDrive StarterKit + Windows Software
Read and Write data on Smart Cards and Memory cards
Microsoft PCSC compatible!
Package Includes:
Professional card Reader/Writer (ChipDrive Micro),
Assorted Smart Cards (3 pairs),
Samples of source code in VB3.4.5+6, C and Delphi.
Examples Apps to Read and Write to Smart Cards and GSM cards
Documentation and detailed Windows DLL description.

£69.95

Visit our web site for Smart Cards, Programmers and Smart Card applications.
The UK's largest stockist of Smart Card and Smart Card Technology
www.crownhill.co.uk/itm00047.htm

PIC Real-time 'Emulator' and Programmer

NEW LOW PRICE!

£119.95
PIC 16F877 In Circuit Programmer



- ☑ For PIC16F87X (emulates most PIC16C6X/7X devices)
 - ☑ In-Circuit run time debugging
 - ☑ Real Time code execution 32kHz to 20MHz real time operation
 - ☑ High Speed Parallel port interface
 - ☑ 2.5V to 6.0V operating range
 - ☑ Built in device programmer
 - ☑ Run, Stop, Run to Cursor etc
 - ☑ Conditional Animation Break
 - ☑ Software animation trace captures 3 user defined variables
- In addition to opcode, W, Status, FSR registers and corresponding instructions.
- ☑ Source Level and symbolic debugging
 - ☑ Runs under PICICD IDE (win95/98 or NT) or MPLAB
 - ☑ Supplied with ICD debug module, Proto board, 40Pin and 20Pin emulator headers, Cables IDE software and user guide

All prices are subject to VAT @ 17.5%

Call for other PIC and Memory prices PIC PROGRAMMERS and Universal Device Programmers

LabProg 48LV

Low Cost - High Performance
Intelligent Universal Device Programmer

£356.00



- Includes:
- Connection Cable
 - Diagnostic POD
 - User Manual
 - PC Software Driver
 - 240VAC/12V adaptor

CE certified

Plugs into parallel port of your PC
Adaptors for TSOP, PSOP, QFP, SOIC, PLCC
True No Adapter Programming upto 48 Pins
Programs and Verifies 2.2, 7.3, 3.3 & 5V devices
FREE software updates 3 Year Warranty

Universal Serial EEPROM programmer



£55.00

All prices are subject to VAT @ 17.5%

PreProm UNIVERSAL Eeprom Programmer
Adaptors for TSOP, PSOP, QFP, SOIC, PLCC
Adaptors for Microprocessors
Adaptors for Eeprom
Emulator adaptor

£135.00



- | | |
|--------------------------|---------------------|
| PIC 16F84 / 04p - £1.90 | PIC 12C508A - £0.63 |
| PIC 16F84 / 04so - £2.00 | PIC 12C509A - £0.63 |
| PIC 16F84 / 10p - £3.95 | 24LC16 - £0.95 |
| PIC 16C622 / 04p - £2.50 | 24LC16 so - £0.95 |
| PIC 16F877 / 04p - £5.50 | 24LC32 - £1.50 |
| PIC 16F877 / 20p - £6.00 | 24LC64 - £1.50 |
| PIC 16F876 / 04p - £4.50 | 24LC65 - £1.50 |
| PIC 16F874 / 04p - £4.50 | |
| PIC 16F873 / 04p - £4.50 | |

All prices are subject to VAT @ 17.5%

Crownhill Associates Limited



32 Broad Street Ely Cambridge Cb7 4PW
Tel: 01353 666709 Fax: 01353 666710



ORDER ON-LINE www.crownhill.co.uk

All prices are subject to a delivery charge + VAT @ 17.5%

CIRCLE NO. 115 ON REPLY CARD

Quenching

The quest for performance in today's mobile world means that high power consumption is the curse of chip designers, but plenty of solutions exist. **Richard Ball** explains the traditional approach and looks at the latest attempts to keep pace with clock speeds

If today's trends continue, by 2015 we'll all be carrying small nuclear power sources to keep our laptops going. Why? Because microprocessors will be consuming more juice than a V8 dragster and spewing out more heat than a rocket nozzle. So claims Pat Gelsinger, CTO of Intel's architecture group.

Mind you, such comments are a bit rich coming from the company that's done more than most in the race to push up clock speeds.

So why are we heading towards nuclear-powered laptops, and what are chip designers doing about it?


The quest for performance has often been at the expense of power consumption – witness Compaq's latest Alpha processor which runs at 1200MHz (1.2GHz), producing 125W. Mind you, it does have 130 million transistors.

One of the traditional routes to higher performance is increasing the number of pipeline stages in the processor. As each stage has less to do, the clock speed can increase.

Increasing the pipeline depth might increase the clock speed, but it's a dubious method of improving overall performance and is definitely bad for power consumption. Pentium 4 and its 20-stage pipeline, for example, processes fewer instructions per clock than Pentium III on conditional code, and hence its power/performance ratio is worse.

An IBM paper at this year's ISSCC conference nicely sums up pipelining: "A deeper pipeline could have yielded even higher frequencies, but at the expense of reduced instructions per clock (IPC). Processor performance is not proportional to frequency but rather the product of frequency and IPC."

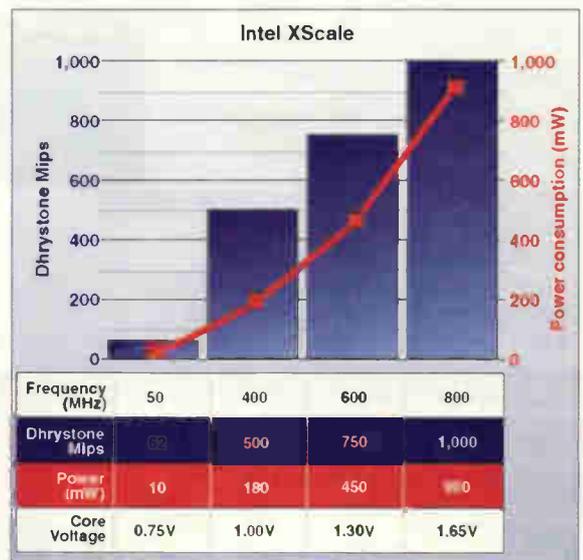Another well trodden route to performance is



Intel's XScale processor can dynamically adjust voltage, frequency and hence power.

parallelism in the processor – placing two, four or more arithmetic units in parallel to do more work in a single clock cycle.

The problem with these superscalar designs is that if the program code can't be written or reordered to take full account of the processing resources, then performance is wasted. And this happens a lot in systems with parallel

Power consumption runs wild

According to Patrick Gelsinger, chief technology officer of the Intel architecture group, increasing the absolute performance from the x86 processor series has resulted in less and less performance per gate per megahertz.

The law of diminishing returns has taken over and increasing power consumption is the result. Despite reduced supply rails, according to

Gelsinger, if current Intel trends continue chip power density will reach that of a nuclear reactor in 2007 and dissipation will be the same as the surface of the sun, 10,000W/cm², in 2015.

His solution is less brute force – so smarter branch prediction and pipelines – and processors designed for specific tasks.

Perhaps Intel is waking up and breaking out of the Windows-PC mould.



processor thirst

architectures. The end result is more heat for less useful work.

Plenty of solutions exist to the problem of high power consumption in processors and hence, to a certain extent, any system-on-chip. However, different solutions fit different markets and applications.

Dynamic clock and voltage management

Power consumption in a circuit is proportional to frequency, but it is also proportional to the square of the voltage. Therefore, the easiest way to cut power is to reduce the voltage.

This does mean a reduction in frequency, but if the loss in performance can be absorbed, then the reduction in current and power is well worth the effort.

Intel has certainly taken this approach with XScale, its second generation successor to StrongARM. At one end the chip can run from 1.65V, hitting 800MHz and consuming 900mW. Throttling back the voltage to 1.0V, however, sees the clock halved to 400MHz while power plummets to 180mW. At the extreme end power reaches just 10mW at 0.75V and 50MHz.

Intel has still gone down the "let's get maximum performance" route, but in this case that performance might not always be used. Sometimes it's sacrificed for much lower power.

A similar scheme is being applied by Transmeta to its Crusoe processors. Its LongRun technology uses subroutines in the software to determine the processor's loading and adjust the voltage and frequency settings. However, LongRun is not accessible to the programmer - XScale's power tricks are, and XScale has a wider voltage scaling range.

Obviously this technique applies well to the handheld consumer device market.

Semiconductor process

Improving the semiconductor process is the simplest trick in the book for reducing power consumption. As the geometry size reduces, voltage is forced down - most of the time - and so power drops quickly.

Today the work-horse process is 0.18 μ m, but in R&D labs, firms are building circuits on 0.13 μ m or smaller. At this level some significant problems are beginning to surface.

As gate lengths decrease, then the gate oxide thickness must also reduce, and this defines the maximum voltage of the transistors. But for high performance devices, a thin gate oxide will result in high leakage current. For low power, a thicker gate oxide will impact performance.

Therefore many firms, such as Toshiba, IBM and Motorola, are using different flavours of transistors in a single device.

Motorola's 0.13 μ m (130nm) process detailed at last year's IEDM conference has gate lengths from 80 to 110nm, and gate oxide thicknesses of 1.8nm, 2.5nm for low power, 5nm for 2.5V I/O and 7nm for 3.3V I/O.

Another way to reduce leakage current and parasitics is to use silicon-on-insulator. Driven by IBM, this technology may well be used by AMD in its mobile PC processors.

Simultaneous multi-threading

SMT is not a new idea - it was first used by Cray in one of its chips over 30 years ago. However, the idea is only just appearing in mainstream devices, and it promises much, especially in the server or telecoms markets.

In a superscalar processor - even with the greatest compiler in the world - a single thread is hard pushed to keep all the execution units active. In deeply pipelined devices, a cache miss or mis-predicted branch causes

Power restrictions in 'system-on-a-chip' devices

Hitachi has taken a fresh look at power restrictions in system-on-chip-based appliances and come up with a hardware-based on-chip power management system called ChipOS, writes Steve Bush.

Processors tend to draw power in bursts. Inconveniently, power supplies have to be sized to match the power peaks, or include chunky capacitors to meet peak demands.

This problem is particularly bad in battery-powered devices where a high peak draw can bring a pair of AA cells to their knees and cause a system reset.

ChipOS tackles this by allowing the system designer to specify a maximum power draw from a system-on-chip.

The same chip, running the same software, can be allowed to run free in a mains-powered application, and peak-limited when battery powered.

And this peak limit is accurate, rather than just the average reduction which comes from processor clock speed switching.

Hitachi claims that a die with ChipOS could be used in a low cost 1W system or a 10W high-performance system.

When multi-tasking, one task can be given priority and allowed to have all the processor's capacity up to the imposed power limit during an activity burst. The other tasks will be slowed or stalled until power becomes available again.

Power limiting clamps the overall

performance of the system, but Hitachi's figures (for an undisclosed single-processor application) show a 48 per cent reduction in peak power only results in 10 per cent slower system speed.

With four processors under the same ChipOS controller, an 81 per cent reduction in peak power was available with 10 per cent slowing.

The penalty with ChipOS is additional hardware. Logic blocks have their clocks gated and their power rails switched.

Associated with each block is a block-specific power driver, which controls clock gating, and rail switching. Running above this is a power scheduler that uses knowledge of block power requirements to allocate blocks to tasks.



Alchemy is a name to be reckoned with in the chip design world, having its ancestry in the original StrongARM team. Its first chip, the Au1000 (above), is back from the fab and undergoing testing. Like Xscale, clock frequency and hence power can be dynamically scaled. Initial figures indicate that running at 1.25V and 200MHz, the chip dissipates 200mW, while at 1.5V and 400MHz power is up to 500mW.

large chunks of data to be flushed – wasting a considerable amount of power.

Multi-threaded processors can fill slots in the instruction issue with waiting threads. So the whole thing runs faster, or to look at it another way, the same amount of work is done with less wasted power.

However, SMT doesn't come for free – it adds around ten per cent extra hardware.

SMT may be about to become mainstream, especially if, as is rumoured, Intel puts it in Foster, the next spin of Pentium 4. It's already in the latest Alpha, described earlier.

Clock distribution

Better clock distribution design is also an avenue to reducing power dissipation, as a processor's clock tree can have a massive overall impact.

For example, another IBM paper from ISSCC describes its POWER4 chip. This dual microprocessor device contains a staggering 170 million transistors. At 1.1GHz it consumes around 115W.

"Approximately 70 per cent of the power is burned in the clock distribution and latches," the firm says. ■

Electromagnetic gun fires a pellet 20km in a second

Sandia Labs' Z machine electromagnetic pellet accelerator has boosted a projectile to 20km/s – i.e. 45 000mile/h. Inside Z machine, 20 million amps produces a magnetic field that expands in around 200ns and generates "several million

atmospheres pressure" on the pellet, according to Sandia. When fired up to 13km/s, the aluminium pellets are neither distorted or melted, but with the wick turned up to achieve 20km/s the aluminium reaches 2500K and liquifies. Research over the last year

has been to keep this temperature down as the pellet can no longer be accelerated once it vapourises. The picture shows researcher Mark Knudson holding two pellets in his right hand and the chambers of Z machine on his left.



Reader offer


10MHz single-trace oscilloscope for under £200

The Tecstar CS1010 oscilloscope is easy to operate and highly reliable. It is an ideal instrument for research, production, education and development work. This is a compact and portable oscilloscope with a frequency bandwidth of 10MHz and sensitivity of 5mV/div to 5V/div. It is equipped as standard with a switchable $\times 10:1$ probe, extending the sensitivity up to 50V/div. The horizontal timebase is 0.1s/div to 0.1 μ s/div.

Features

- 10MHz bandwidth
- High brightness
- Calibration output
- Variable-Y attenuation
- AC DC and Ground
- Auto, Normal and TV triggering
- Variable trigger level
- +ve or -ve Ext trigger modes
- Internal, External or Line trigger
- Complete with $\times 1/\times 10$ probes
- Low cost

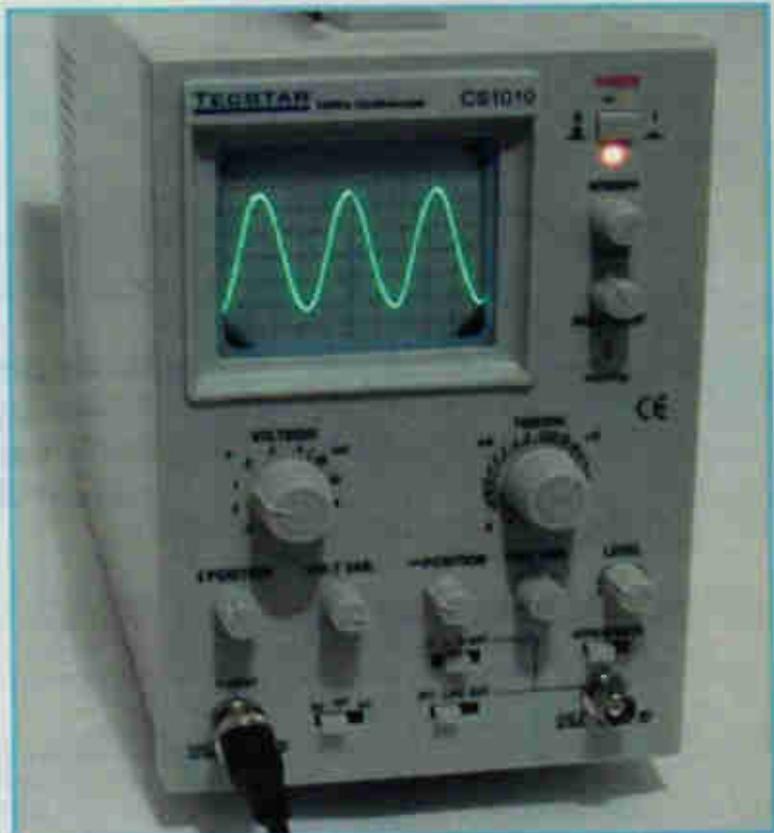- Simple operation
- Portable, small and lightweight
- Excellent Triggering



Vertical system

Sensitivity	5mV/div-5V/div $\pm 3\%$
Trimming ratio	2.5:1
Rise time	35ns
Bandwidth (-3B)	DC:0-10MHz AC:10Hz

Trigger system

Int trigger sensitivity	1 div
Ext trigger sensitivity	0.3V
Ext. trig. input impedance	1M Ω , 30pF
Ext. trig. max. input	400V pk
Trigger sources	Int, Line, Ext
Trigger mode	Norm, AUTO, TV

Horizontal system

Sweep time	0.1s/div-0.1ms/div, $\pm 3\%$
Trimming ratio	$\geq 2.5:1$

X-Y mode

Sensitivity	0.2V/div-0.5V/div
Bandwidth (-3dB)	DC: 0-1MHz AC: 10Hz-1MHz

Calibration signal

Waveform	Symmetric square wave
Amplitude	0.5V $\pm 2\%$
Frequency	1kHz $\pm 2\%$

CRT

Display area	8 x 10div (1div=6mm)
Accelerating voltage	1200V
Display colour	Green

Power source

Voltage range	220V $\pm 10\%$
Frequency	50Hz ± 2 Hz
Power consumption	25W

Physical features

Weight	3kg
Dimensions (H x W x D)	190 x 130 x 270mm

Working environment

Working temperature	5°C to 40°C
Storage environment	-30°C to 60°C, 10-80%RH
Working altitude	2000m

Use this coupon to order your 10MHz CS1010 oscilloscope

Please send me 10MHz oscilloscopes at the special offer price of £193.88 each – including VAT and UK carriage*.

Name _____

Company (if any) _____

Address _____

Phone number/fax _____

Total amount £ _____ - _____

Make cheques payable to Tecstar Electronics Ltd

Or, please debit my Master/Visa card.


Card type (Master/Visa) _____

Card No _____

Expiry date _____

*£159.00 ex. VAT, £6 UK carriage, £14 overseas.

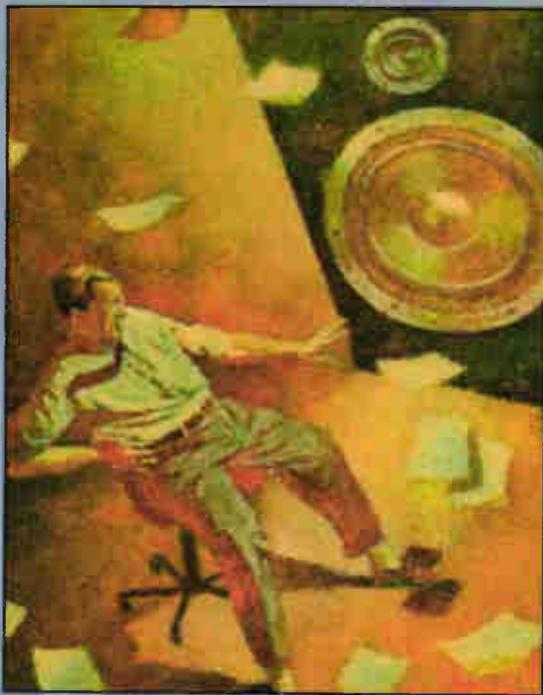Please mail this coupon to EW offer, TECSTAR Electronics Ltd, Unit 1 Nuffield Road, St Ives, Huntingdon, Cambs. PE27 3LX, Tel 01480 399 499, Fax 01480 399 503. email: sales@tecstar.co.uk



SPEAKERS' CORNER

Voltage or current drive?

Moving-coil loudspeakers are invariably driven by a voltage amplifier. Here, John Watkinson explores the alternative – current drive.

Traditionally, the moving coil loudspeaker drive unit has been connected to a voltage amplifier. **Figure 1a**) shows that an ideal voltage amplifier has zero output impedance such that the voltage at the output terminals is independent of the load impedance.

In reputable amplifiers this requirement is typically met with negative feedback, which simply compares the output voltage waveform with the input signal waveform.

Figure 1a) also shows that an ideal drive unit would have zero resistance and zero inductance. The only factor controlling the coil current is the back EMF. Any difference between the amplifier output voltage and the back EMF would result in an infinite current, so the coil velocity would

have to be proportional to the amplifier voltage.

This is a desirable condition, in which the cone velocity follows the audio waveform.

If only...

In the real world though, this doesn't happen. **Figure 1b)** shows that the tight connection between input waveform and cone velocity is lost because the drive unit has finite resistance as well as inductance.

The result is that the cone velocity no longer follows the input waveform. In any other control discipline, this would be regarded as a major shortcoming and something would be done about it. Imagine an aircraft in which the control surfaces didn't follow the stick, but were blown about by the slipstream.


Generally the audio industry does nothing about this problem, even though the cone velocity becomes anti-phase to the input below resonance, making the output waveform a travesty of the input. Instead, new clothes continue to be made for the Emperor long after his death.

With voltage drive, a number of other factors can affect the cone velocity and potentially cause distortion. These include suspension non-linearity and coil inductance.

If the coil inductance were constant, the result would just be an HF roll-off. Unfortunately, coil inductance changes with the cone position as different amounts of the pole structure are within the coil. The impedance of the drive unit is also a function of coil temperature, which itself is a function of the power dissipated.

Figure 2a) shows an ideal current source driving a loudspeaker. An ideal current source has an infinite output impedance. The output current is proportional to the input voltage and is independent of load impedance.

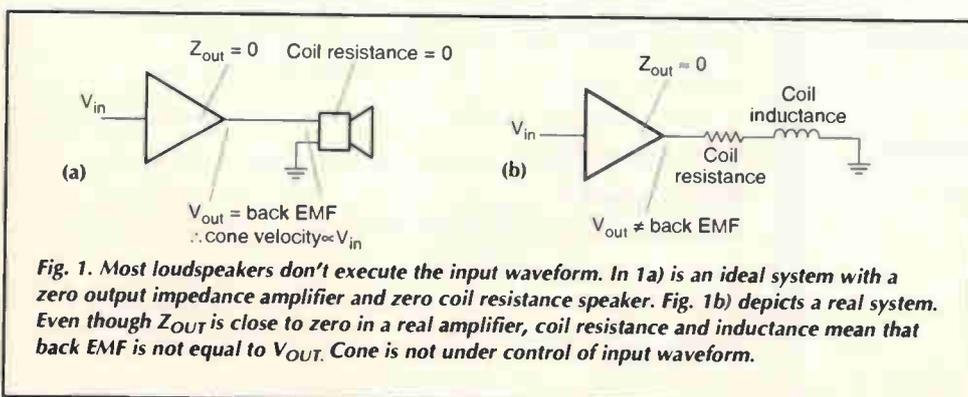Implementing current drive
Effectively, the power amplifier has become a transconductance amplifier. **Figure 2b)** shows that current drive can be achieved by providing a sense



resistor in the coil current path. Amplifier negative feedback is then used to compare the voltage across the sense resistor with the input. When the two are identical the current in the coil must be proportional to the input voltage.

The current drive amplifier can be implemented with almost any amplification technology used for voltage drive – including switched-mode, error-correcting, Class-A or vacuum-tubes.

The operating principle is now different from that of voltage drive. The force produced by the coil is proportional to the current, so the coil operates in constant-force mode. As the cone mass is also constant, the drive unit operates in mass-control mode. In this mode the amplitude falls at 6dB/octave as required for constant velocity and flat frequency response.

A desirable result of current drive is that the effects of coil inductance and inductance modulation are eliminated, along with changes in sensitivity due to coil heating. This will reduce HF distortion and extend the frequency response while eliminating thermal compression effects. Both of these benefits are well worth having.

Infinite output impedance

However, the down side of current drive is that the infinite output

impedance of the amplifier means that there is no electrical damping of the drive unit's fundamental resonance at all. The only damping is due to the drive unit's own structure, with a tiny amount due to sound radiation.

The strong resonance is audible and the drive unit can easily over-travel. Consequently the designer is forced into making some active compensation for the driver fundamental resonance in the shape of an analogue computer/op-amp circuit or DSP. In fact this is no great drawback, because this has to be done with voltage drive if any degree of precision is required. The difference is that with voltage drive it is possible to dispense with resonance compensation if a lower quality is acceptable.

At low frequencies the drive unit becomes compliance controlled. Non-linearities in the suspension, and modulation of the *Bl* product with coil position, will cause distortion whether voltage or current drive is used. In fact given good engineering and a correctly designed resonance-compensation mechanism, voltage and current drive would give exactly the same effect at low frequencies; the sound quality would be limited by the drive unit.

Inductance modulation is negligible at LF. The distortion there is dominated by magnet and suspension

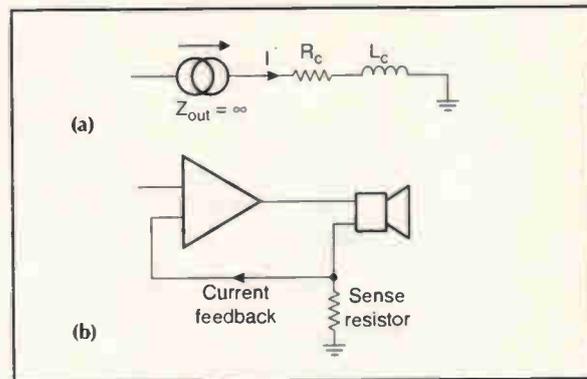


Fig. 2. Current drive principles. In a), with infinite output impedance, current is independent of coil resistance and inductance (and back EMF). Figure 2b) shows how current drive can be achieved using a load-current sense resistor.

design, which amplifier topologies can't affect.

The main advantage of current drive would appear to be in tweeters, where the elimination of the effects of coil inductance can give a useful improvement in frequency response and linearity. Tweeters tend to be used well above their fundamental resonance, so the lack of damping there may not be an issue.

At low frequencies, the use of current drive is less compelling because the problem comes down to one of precision drive unit design. If the suspension is non-linear, or if the *Bl* product changes as the coil moves because of an asymmetrical flux pattern, the choice of drive topology is irrelevant.

As has been stated countless times, to make a fine loudspeaker it is necessary to have fine drive units. ■

VCR Fault Finding Guide

This book is an essential repair tool, not just another volume for the shelf

Pages: 464pp Price: £22.50

Television magazine's VCR Clinic column is a unique forum for practical servicing tips, with the UK's leading service engineers and servicing writers contributing their observations and recommendations month by month. But try finding those faults reports for the Amstrad XYZ123 that's on your bench. Even with an index you will be chasing through a pile of magazines... until now. Peter Marlow's VCR Fault Finding Guide is a distillation of the most used fault reports from 11 years of Television magazine. Arranged by make and model the information is extremely easy to access, and the book is a convenient size for the bench or to carry with you. This will undoubtedly become one of the service engineer's most useful tools. Unlike other fault guides, this one is based on top quality information from leading authorities, and genuine repair case studies. This is real-life servicing information, not just a compilation of manufacturers' manuals. Approximately 2000 reports on 193 models from 35 different manufacturers. Instant on-the-spot diagnosis and repair advice. Television magazine's leading writers' wit and wisdom available for the first time in book form



Post to Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

How to pay

(VCR Fault Finding Guide) paperback

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

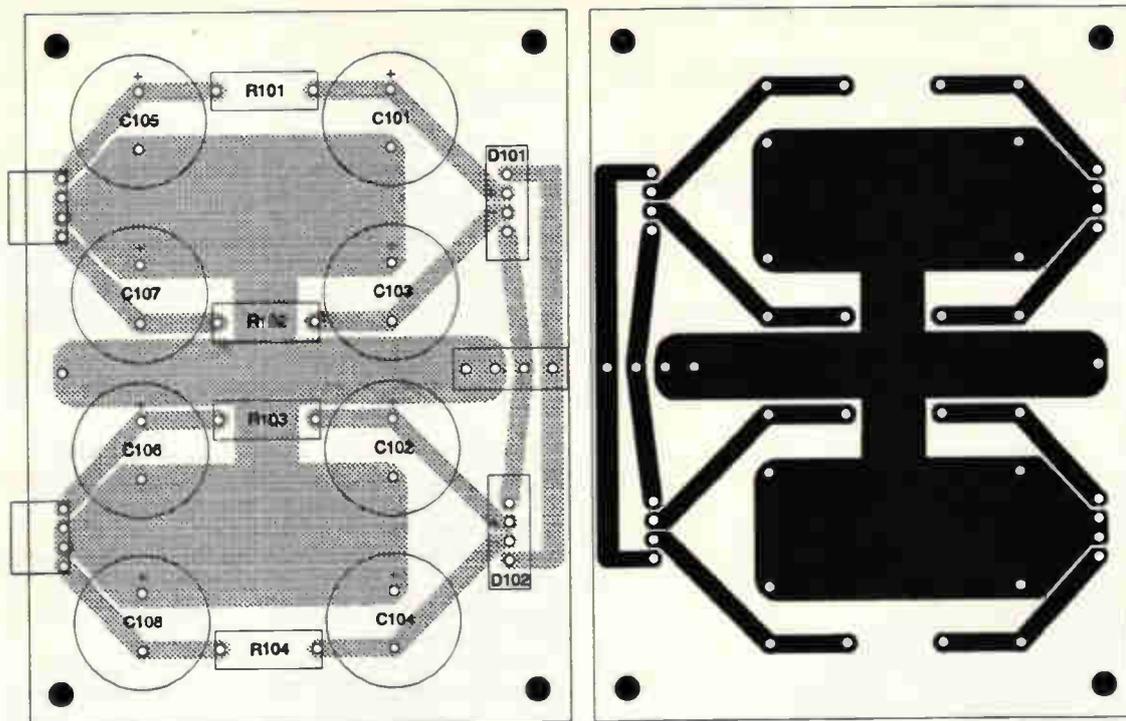


Fig. 2. Power supply board parts placement (left) and PCB pattern (right).

Filter design

With such a small current requirement, it makes sense to try for additional ripple reduction by using two stages of filtering. This takes advantage of very large, but still very compact, electrolytic capacitors, where the usual capacitor-input power-supply filter is followed by an RC low-pass filter.

My criterion for the capacitor values was the size of those most readily available to me – four at 2200µF, 50V and four at 4700µF, 35V. The smaller capacitors are positioned as conventional capacitor-input filters, with one each in the positive and negative power supplies for each channel.

Four 220Ω resistors connect the four 2200µF capacitors to the four 4700µF capacitors. In this way, each positive and negative power supply of each channel follows the raw DC output across the 2200µF capacitors with an RC filter of 1.034s time constant. This corresponds to a filter cut-off frequency of $(2\pi RC)^{-1} = 0.154\text{MHz}$. Capacitors of 470µF would be perfectly acceptable.

The total amount of ripple attenuation provided by the filter circuitry depends on whether you use half- or full-wave rectification. I know that this is almost always full-wave in high-end equipment. However, the amount of ripple attenuation is so high that either type is acceptable in this application. It may be that the 60Hz hum from residual ripple in a half-wave supply is less objectionable than any 120Hz hum from full-wave rectification.²

The idea is, of course, that no audible hum be present no matter which rectification scheme you use. There is no audible hum produced by residual ripple in this preamp with the power supply described here – a supply that uses half-wave rectifiers.

Since ripple is attenuated by a factor of ten (20dB) for each decade that the ripple frequency lies above the filter cut-off frequency, the second stage of filtering here provides, $20\text{dB/decade} \times 2.6\text{ decades} = 52\text{dB}$ of additional reduction where,

$$\frac{60\text{Hz}}{0.154\text{Hz}} = 390$$

number of decades is x , where $10^x = 390$;

$$\log 10^x = x = \log 390 = 2.6$$

For this application, I chose 220Ω for the filter resistors. I

assumed that the unregulated, but heavily filtered, output voltage delivered to the preamplifier circuit board would be no less than about 18V under worst-case conditions.

The above relationships show that if you select the full-wave rectifier, you will obtain 6dB more ripple attenuation from the RC filter.

Ripple blips

At 2mV/division, the ripple on an oscilloscope is barely visible, appearing almost as a pulse train of small 'blips.' The blips are probably due to the heavy current flow during the short period during which charging current flows through the rectifier diodes to the 2200µF capacitors of the capacitor-input filter.

A small resistor between the diodes and the capacitors would reduce the amplitude of the blips, but there is already heavy overkill here.

As a matter of interest, if ripple were to be reduced to 10mV with a capacitor input filter alone, the charging current through the rectifier diode would be about 5A – even though load current is a mere 25mA. Charge is the product of current and time. The charge removed from the filter capacitor during the 16.7ms cycle time ($T = 8.3\text{ms}$ in a full-wave rectified supply) must be restored to the capacitor during the short (in a well-designed supply) recharge period, Δt .

If recharge (diode) current is considered constant (it is not, but the approximate answer so obtained is sufficient), then,

$$I_{\text{LOAD}} \times T = I_{\text{RECHARGE}} \times \Delta t$$

Solving this expression for charging current yields,

$$I_{\text{RECHARGE}} = \frac{T}{\Delta t} \times I_{\text{LOAD}}$$

This formula already suggests that charging current will be much greater than load current³ because the small charging interval Δt is so short in comparison to the relatively long cycle period T .

Although diode conduction actually continues past the peak capacitor voltage V_{peak} , if you assume that conduction begins at time Δt before it ceases at V_{peak} , then voltage magnitude at the onset of conduction is $V_{\text{peak}} \cos \omega \Delta t$.

The quantity $\omega \Delta t$ is the diode conduction angle, and for a

half-wave rectifier the ripple frequency is $\omega=377s^{-1}$. The peak-to-peak ripple voltage is therefore,

$$V_{ripple} = V_{peak} - V_{peak} \cos \omega \Delta t.$$


Remember that $\omega \Delta t$ is intentionally made small to reduce ripple so that the trigonometric approximation,

$$\cos \omega \Delta t \approx 1 - \frac{1}{2} (\omega \Delta t)^2$$

is valid. If the output voltage of the supply is to be about 21V, then you can solve for,

$$\Delta t \approx \frac{[2V_{ripple} / V_{peak}]^{1/2}}{\omega} = \frac{[2(0.01) / 21]^{1/2}}{377} \approx 82 \mu s$$

Fig. 3. Preamp-enclosure construction pictorial.

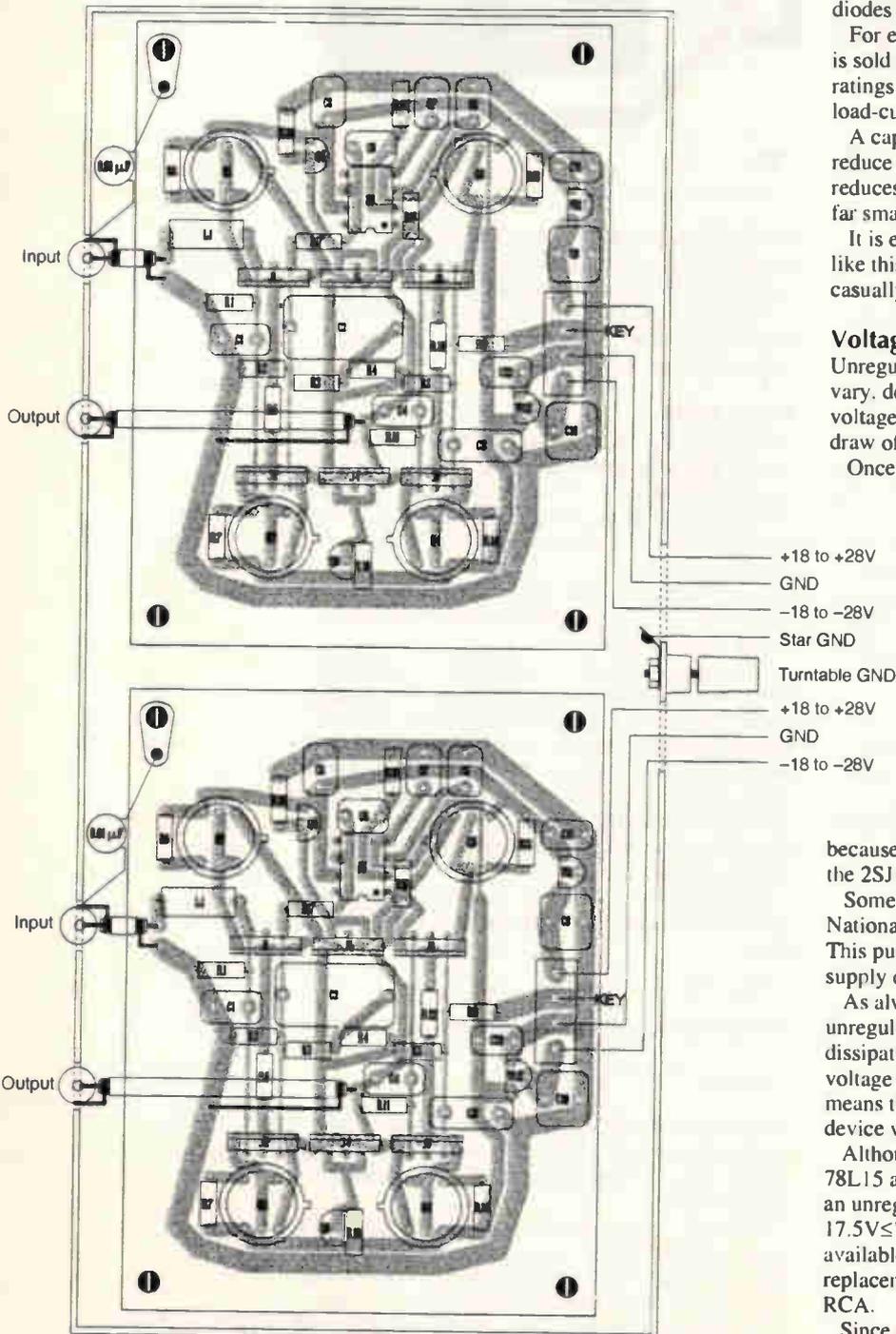

From this, it follows immediately that,

$$I_{RECHARGE} \approx \frac{0.0167}{0.000082} \times 0.025A = 5.09A$$

A pretty impressive number.

Current I_{LOAD} is constant at about 25mA and the capacitor discharges for almost the entire 16.7ms period T . The formula for the discharge of a capacitor at a constant current leads to $V_{ripple} = I_{LOAD} T / C$. For the 2200 μF filter capacitors then,

$$V_{ripple} \approx \frac{0.025 \times 0.0167}{0.0022} \approx 0.189V$$

Surge current through the diode in the preamp power supply is of the order of 1.2A. This is still a pretty startling number, but the surge ratings on even small rectifier diodes are well in excess of this.

For example, a 1N4002 diode has a 30A surge rating, but is sold as a 1A rectifier. It should be clear why surge ratings need to be so much higher than the average DC load-current rating.

A capacitor of almost 42000 μF would be required to reduce the ripple to 10mV. Using the additional RC filter reduces the almost 200mV ripple to less than 0.5mV with far smaller capacitors.

It is enlightening – even eye opening – to look at things like this. Many designers treat power supply design very casually. I used to, too, until it bit me.

Voltage regulators

Unregulated output voltage from the rectifier/filter will vary, depending on the power transformer secondary voltage under load. Measured voltage was 24V at a current draw of 25mA with the transformer that I used.

Once you've selected the actual transformer, you could simply increase the resistor value in the RC filter. Better still, you could add yet another stage of RC filter so that approximately 15V would be presented to the preamplifier under load. In either case, it would require no voltage regulator.

While you are certainly free to use other schemes, the one chosen here was to use 78L15 and 79L15 IC voltage regulators on the preamplifier circuit boards to supply the needed $\pm 15V$ power rails. The regulators are part of the main preamplifier circuit shown in last month's issue. Voltages from the regulators were limited to a 15V magnitude because of the 30V drain-to-source voltage limitation of the 2SJ109 JFETs.

Some features of on-card regulation are discussed in National Semiconductor's Voltage Regulator Handbook.⁴ This publication is a good general reference for power-supply design.

As always, there are constraints you must consider. If the unregulated voltage is too high, the voltage and/or power-dissipation limits of the regulators will be exceeded. If this voltage is too low, then the regulator will 'drop out.' This means that it will cease to regulate because some active device within it is no longer in its active operating region.

Although these limitations are slightly different for the 78L15 and 79L15 regulators, the worst-case limits require an unregulated voltage magnitude in the range $17.5V \leq V_{in-unreg} \leq 28V$. These regulators are widely available from several manufacturers, including the replacement series manufacturers such as ECG, NTE, and RCA.

Since parts numbers will vary, be careful to select

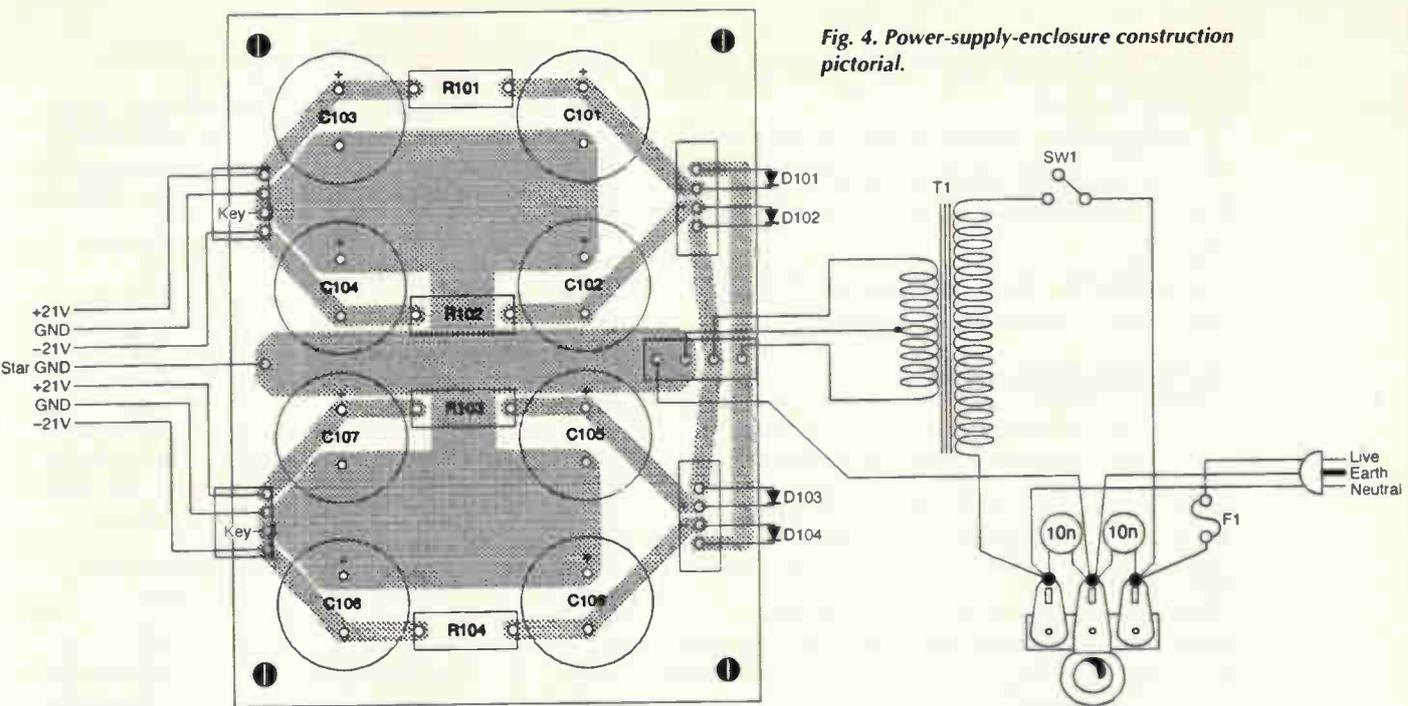


Fig. 4. Power-supply-enclosure construction pictorial.

regulators whose output-voltage tolerances are guaranteed to be within $\pm 5\%$. There are even tighter-tolerance devices available if you wish to go to the trouble and expense of finding them, but it really isn't necessary to do so.

In the interests of stability, each regulator will require the input capacitor shown, unless you place the regulator immediately at the output of the unregulated supply.

With the recommended value for the 79L15's input capacitor, there was an intermittent, low-amplitude, high-frequency oscillation. This I tamed by increasing the capacitor value to $1\mu\text{F}$. For consistency, I also used $1\mu\text{F}$ input capacitors for the 78L15 regulators.

A case could be made for deriving first-stage supplies from the output of the 78L15/79L15 regulators by using yet another RC filter, or perhaps a zener. This would mean that the first stage would operate at some lower voltage. This should be no problem, however, given that the output swing demanded from the first stage is significantly less than that required from the second.

Putting it together

Layout and construction details are reasonably well described in Figs 2-4. Nonetheless, I should elaborate on a few of the details.

As a designer, I always think about the possibility of modification or repair of the device, especially for the prototype version. For that reason, I liberally employ quick-disconnects (QDs) as well as transistor and IC sockets. The JFETs are not socketed here though because of their unusual pin-out.

The power cable between power supply and preamplifier enclosure has QDs at both ends. If you use QDs on this cable, be sure that it has male connectors at the power-supply end and female connectors at the preamp end. In this way, even if you use Molex header-type connectors, the 'hot' connector pins are not exposed.

I have serious reservations about claims of sonic effects of QD metals. Even so, I favour gold connectors because of past experience with other types' reliability problems due to corrosion.

I mounted chassis-mount RCA jacks to the edge of the PC board, and used uninsulated wire to both strap and ground the sleeve (outer portion) of each jack to the board.

Parts for the power supply

Resistors

R_{101,102} 220 Ω , 2W, 2% metal

Capacitors

C_{101,102} 2200 μF , 50V aluminum electrolytic

C_{103,104} 4700 μF , 35V aluminum electrolytic

Transformer

T₁ 48V ct at 150mA (see text)

The mating portion of the jacks extend out beyond the board's edge. This arrangement allows unimpeded connection to the jack of the RCA plug from the tonearm.

I soldered a $0.01\mu\text{F}$ ceramic-disc capacitor to the ground trace immediately adjacent to the ground trace connection of the input jack, and soldered the other end of the capacitor to a solder lug. In turn, I grounded this lug to the chassis via the screw attaching the PC board to the nearby metal stand-off.

A stand-off under each corner of the board provides its secure mounting to the chassis while ensuring that the bottom of the board does not contact the chassis. All four stand-offs should obviously be of the same height. You can make them either of metal or insulating material, except that, as described earlier, the one to which the solder lug is attached must be made of conducting material.

I made the connection between the inner-conductor (centre) connector lug of the input jack and the board trace to inductor L_1 with a very short piece of uninsulated wire, since the jack was mounted immediately adjacent to L_1 . Similarly, I strapped and grounded the output RCA jack at the board's edge, but made the connection between its inner-conductor connector lug and the appropriate board trace with small-gauge shielded cable because of the distance involved. The shield of this cable is only grounded at the phono-jack end.

With this mounting arrangement of the jacks, it was necessary to drill holes only in the front panel of the preamp enclosure, allowing the RCA jacks to protrude

almost completely outside the enclosure. To do this, the front edge of the PC board must contact the inner side of the front panel of the enclosure.

The front-panel holes for the jacks must be sufficiently large that neither the jack nor the shield connector portion of any connected RCA plug contacts the front panel. Also be sure that no other PC board component or trace contacts the front panel.

You could achieve the same effect more easily by using PC-mount RCA jacks. If you use such jacks, you must modify the board's trace pattern accordingly.

Avoiding grounding problems

Some attention to the grounding scheme is required. For one thing, there are differences among various turntables, tonearms, and even cartridges in the way grounding is handled. For that reason, the actual interconnections may be different, depending upon the builder's specific system and its components. It will probably be true that most builders will be very familiar with the schemes that work best in their systems.

I emphasise again that the RCA input and output connectors are insulated from the enclosure. It is important that the input connectors be grounded to chassis only through the 10nF capacitors as shown.

While I understand that isolating the input connector ground from the chassis avoids a ground loop, I have never seen a reason given for the capacitors. I assume they are for RF bypass, given the small capacitance value.

These capacitors may be disc-ceramic types. Voltage rating is probably not critical, but since 10n, 1kV disc-ceramic capacitors are used as AC-line filters for the power supply, it is convenient to make all of these capacitors the same and perhaps save on quantity purchases.

A ground loop can occur anyway if the cartridge or tonearm cable connects both channel grounds at the turntable end. If a continuity check indicates this situation, then break the potential loop by opening the shield connection at the turntable end for one channel only.⁶ If that is not possible, you can try omitting one shield connection to the PC board at the preamplifier end for one channel only.

I am not sure whether this, of itself, will give satisfactory results, because signal ground for that channel then comes circuitously from the other channel to the power supply and back to the first channel. I have seen amplifiers oscillate with such circuitous ground paths.

As an alternative, after breaking one shield connection for the PC-board RCA input jack, connect the ground trace of both channels' PC boards together and break the ground return to the power supply for one channel only.

Some turntable/tonearm combinations offer an optional ground lead for connection to the preamplifier chassis. Accommodation of this option is the reason for the binding post labelled 'Turntable GND' on Fig. 3. The decision whether or not to connect this optional ground lead is based empirically on the situation that results in the least hum.

For my system, the SME3009 tonearm cable provides this optional ground lead, which, at the tonearm end, is connected to the turntable platform of a Thorens TD125. Connection of the optional ground to the preamplifier binding post is the preferred configuration in my case, since this reduces hum below the audible level.

At the power supply, only one chassis interconnection point should exist. This is nicely illustrated in Fig. 4, which also indicates what is meant by such terms as 'Star GND.'

Setup and adjustment

No adjustments are required. It is a good idea, as mentioned in the text, to verify the differential amplifier currents by measuring the voltage across current source resistors R_5 and

R_{12} . Unless you used severely mismatched BJTs in the current mirrors, cascode current should be OK.

I always check the power-supply voltages before I connect the rails to the circuit. I also use current-limited bench power supplies for breadboard work, and a Variac[®] for initial power up and check-out of the prototype version of a new design or after repairs.

The presence of the 220 Ω resistors in the power supply affords short-term protection against short circuits downstream, but in the long term, their resulting power dissipation would exceed their rating. The IC voltage regulators are internally protected against short circuits.

In summary

I think that this pretty well covers the whys and wherefores of this design. It is a satisfying approach from the standpoint of precision in a relatively simple discrete design. The THD was only about 0.006% up to several kilohertz, rising to 0.026% at 20kHz with a 0.5V RMS output.

Obviously, it is possible to achieve significantly lower levels of THD with higher open-loop gain and therefore more feedback. It is difficult to do so, however, with the precise active-passive equalisation scheme realised through just two one-stage op-amps, as I did here. The proponents of 'less is better' – and especially those sceptical of the benefits of negative feedback – will appreciate this trade-off.

As for listening attributes, the sound is open and dynamic. You hear no stridency, even on massed strings. The bass is awesome, and I have no explanation for this. I do not know about the Adcom or Marantz preamps, but otherwise it is true that there are no coupling capacitors in the signal path – even at the input of the power amplifier currently in my system. This was possible because the servo limited DC offset at around 600 μ V. Still, there should be no perceptible difference in bass, even with coupling capacitors, as long as the low-frequency cut-off is well below the lower limit of hearing.

It is simply amazing how many good recordings there were in the days of vinyl. The ambience in the few Mercury Living Presence records that I have is remarkable. I am sceptical of many 'golden ear' claims of magical qualities of amplifiers and preamplifiers and I attribute none to this design. I simply assert that this phono preamp is good enough to accurately reproduce the information that is in the recording medium.

I believe you will thoroughly enjoy its use, provided that other components in the stereo system are equally good. I continue to be impressed with the sound even after several weeks. The more usual case is to be very impressed initially, with the enthusiasm fading after the first few listenings.

I am listening at higher volume levels than before. This may be a sign of lower apparent distortion, since there is a tendency to adjust volume to a level just below that at which distortion begins to be objectionable. ■

References

1. Manny Horowitz, 'How to Build Solid-State Audio Circuits', Tab Books/No. 606, 1972, (pp. 311-12).
2. Manny Horowitz, 'How to Build Solid-State Audio Circuits', Tab Books/No. 606, 1972, (p. 297).
3. Mark N. Horenstein, 'Microelectronic Circuits and Devices', Second Edition, Prentice Hall, 1996, (Problem 4.79, p. 225).
4. Voltage Regulator Handbook, National Semiconductor Corporation, 1975, (p. 1-1).
5. The ARRL Handbook for Radio Amateurs, The American Radio Relay League, 1997, (p. 11.24).
6. Manny Horowitz, 'How to Build Solid-State Audio Circuits', Tab Books/No 606, 1972, (pp. 314-15)



Quality Alphanumeric backlit LCDs in 4x40, 2x40, 4x20, 2x20 and 2x16 formats


Supplied either bare or pre-fitted with one of our Eze-Use, Serial interface boards with options such as software buzzer control, backlight control, operator interface, start-up message, big character generation, and PC-AT Keypad /mouse interface - all at very competitive pricing.

We also stock Serial Interface Graphic modules and front panel bezels for all our LCDs. Please call (01977 683665) or check our web site (www.milinst.com) for full details and pricing.

Milford Instruments - your total LCD solution



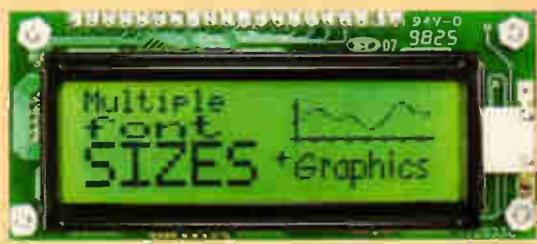Milford Instruments
 Milford House, 120 High St
 South Milford
 LEEDS LS25 5AQ
 Tel 01977 683665
 Fax 01977 681465
www.milinst.com



CIRCLE NO.116 ON REPLY CARD

LANGREX SUPPLIES LTD
 PHONE 020 8684 1166
 DISTRIBUTORS OF ELECTRONIC VALVES TUBES AND SEMICONDUCTORS AND I.C.S.
 1 MAYO ROAD • CROYDON • SURREY CR0 2QP
 24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS
 email: langrex@aol.com
 FAX 020 8684 3056

Part No.	Price	Part No.	Price	Part No.	Price
AZ31	8.00	KT66 Special	20.00	524GT	3.00
CL33	15.00	KT88 Special	20.00	6A05	2.00
E88CC	8.50	N78	8.00	6AR5	6.00
E180F	3.50	OA2	3.00	6AS7G	7.50
E810F	20.00	OB2	3.00	6A5GT	4.00
EABC80	4.00	OC3	3.00	6AU6	2.00
EB91	1.50	OD3	3.00	6AW8A	4.00
EBF80	1.50	PCF80	2.00	6B4G	22.00
EBF81	1.50	PCL82	2.00	6A6	1.50
EBL31	25.00	PCL85/805	2.50	6BE6	1.50
ECC33	12.00	PCL86	2.50	6BH6	2.00
ECC35	12.00	PD500	8.00	6BR7	4.00
ECC81	3.00	PL36	3.00	6BQ7A	2.00
ECC82	5.00	PL81	2.00	6BR8	4.00
ECC83	3.00	PL504	3.00	6BW6	4.00
ECC85	5.00	PL508	3.00	6BW7	3.00
ECC88	6.00	PL509/519	10.00	6BX7GT	7.50
ECC808	15.00	PL802	4.00	6BZ8	3.00
ECH35	3.50	PY500A	3.00	6C4	2.00
ECH42	3.50	PY800/801	1.50	6CB8A	3.00
ECH81	3.00	QOV02-6	12.00	6DC6G	5.00
ECL82	5.00	QOV03-10	5.00	6DE6	3.00
ECL86	5.00	QOV03-20A	10.00	6CG7	7.50
ECLL800	25.00	QOV06-40A	12.00	6CH6	3.00
EF37A	3.50	U19	8.00	6CW4	6.00
EF39	2.75	UABC80	1.60	6D05	17.50
EF40	4.00	UCH42	5.50	6D06B	10.00
EF86	5.00	UCL82	2.00	6F6G	8.00
EF91	2.00	UCL83	2.00	6F07	7.50
EF183/4	2.00	UF89	4.00	6GK6	4.00
EL33	15.00	UL41	12.00	6J5G	6.00
EL34	5.00	UL84	3.00	6J5M	4.00
EL34G	5.00	UY41	4.00	6J7	3.00
EL36	5.00	UY85	2.00	6JB6A	27.50
EL41	3.50	VR105/30	3.00	6JEC	27.50
EL84	3.00	VR150/30	3.00	6JS8C	27.50
EL85	2.00	Z75H	10.00	6K6GT	4.00
EL360	15.00	Z803U	15.00	6L6G	15.00
EL509/519	7.50	2D21	3.50	6L6GC	17.50
EM34	25.00	3B28	12.00	6L6WGB	10.00
EM81/47	5.00	4CX250B	45.00	6O7	3.00
EN91	7.50	5R4GY	7.50	6SA7	3.00
EZ80/EZ81	5.00	6U4G	10.00	6SC7	3.00
GZ32	8.50	6U4GB	10.00	6SG7	3.00
GZ33/37	15.00	6V4G	5.00	6SJ7	3.00
KT61	15.00	6Y3GT	2.50	6SK7	3.00
		6Z3	5.00	6SL7GT	5.00
		6Z4G	6.00	6SN7GT	7.50

Prices correct when going to press

OPEN TO CALLERS MON-FRI 9AM-4PM. CLOSED SATURDAY
 This is a selection from our stock of over 6,000 types. Please enquire for types not listed.
 Obsolete items are our speciality. Valves are new mainly original British or American brands.
 Terms CWO/min order £10 for credit cards.
 P&P 1-3 valves £2.00. 4-5 valves £3.00
 Add 17.5% VAT to total including P&P

CIRCLE NO.117 ON REPLY CARD

WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES

(using a video capture card)



"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + vat = £43.48
 30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole..... £35.00 + vat = £41.13
 40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses..... £32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle..... £15.97 + vat = £18.76
 VSL4022F 4mm F1.22 63x47 degrees viewing angle..... £17.65 + vat = £20.74
 VSL6022F 6mm F1.22 42x32 degrees viewing angle..... £19.05 + vat = £22.38
 VSL8020F 8mm F1.22 32x24 degrees viewing angle..... £19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle..... £26.43 + vat = £31.06
 VVWL813M 8mm F1.3 with iris 56x42 degrees viewing angle..... £77.45 + vat = £91.00
 1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat
 1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbitec mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily..... £7.46+vat = £8.77



Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS
 276-278 Chatsworth Road, Chesterfield, S40 2BH.
 Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch
 Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

CIRCLE NO.118 ON REPLY CARD

Power for the

Sources of energy can have massive implications for all sectors of life, from the environment to lifestyles, but one alternative energy source is making waves. **Chris Evans-Pughe** looks at fuel cells

Delve into the subject of renewable energy sources and you may end up in a series of windmill-strewn, solar-panelled alternative websites populated by noble eco-types who apparently have the patience to wait half a day to cook dinner in a box of hay. Someone should tell them about pizza delivery... I'm kidding. Alternative energy ideas are great, but not suitable for most

everyday mass-market needs. But surf a little further and you'll find fuel cells – probably the most commercially promising renewable energy technology, and one of growing interest to the electronics industry.

At the heavy-duty end of the energy market, governments, utility companies and car firms are embracing fuel cell technology. Their zeal is mainly due to pressure to cut emissions prompted by concerns about climate change.

The US Department of Energy projects that if 10 per cent of cars in the US were powered by fuel cells, regulated air pollutants would be cut by one million tons per year and carbon dioxide by 60 million tons.


The companies developing fuel cells for portable electronics applications have different motivations. They're interested in the technical advantages of a significantly longer operating time than today's batteries, cheap fuel and a re-fuel time of seconds. According to Motorola Energy Systems, fuel cells would be able to power a mobile phone for over 30 days and keep a laptop running for 20 hours. Consequently, fuel cells may be ideal for handling the increased power needs of multifunction mobile applications such as 3G that will support video and Internet surfing.

A fuel cell is a cross between an engine and a battery. Like an engine, a fuel cell will run as long as fuel (hydrogen) is supplied. Like a battery, it produces electricity by electrochemical reactions.

A fuel cell comprises two electrodes and an electrolyte. Hydrogen is fed into the anode and oxygen – or air – enters through the cathode. Encouraged by a catalyst, the hydrogen atom splits into a proton and an electron, which take different paths to the cathode. The proton passes through the electrolyte. The electrons create a separate current that can be used before they return to the cathode, to be reunited with the hydrogen and oxygen to form water.

The first fuel cell was built in

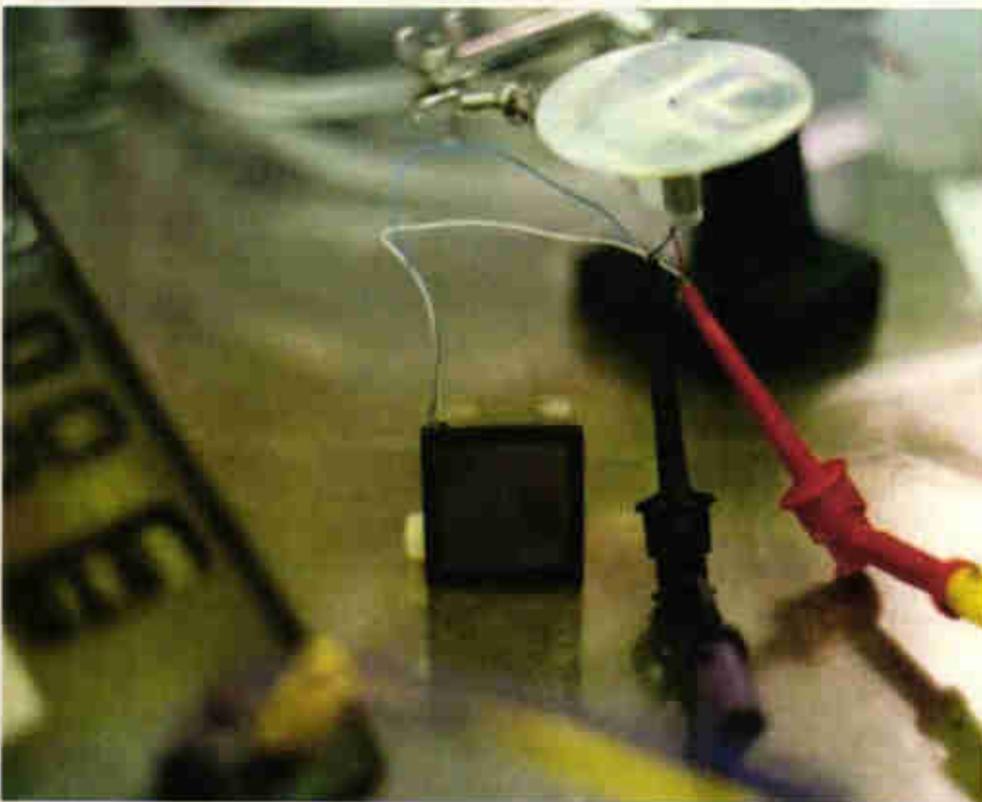This image shows Energy Related Devices' methanol powered fuel cell.



new generation

1839 by a Welsh judge called Sir William Grove, but the technology wasn't really used until the sixties, when the US space program chose fuel cells for the Gemini and Apollo spacecraft.


Nowadays there are many varieties of fuel cell around. At the high end are industrial systems using phosphoric acid and molten carbonate. At the very alternative end are entertaining concepts such as University of South Florida's microbial fuel cell. This can be powered by food, preferably meat because of its higher energy density. Within the fuel cell are bacteria that speed the breakdown of its food-fuel, releasing electrons that charge a battery.

The systems of most interest for electronics are proton exchange membrane (PEM) – the technology being used by firms such as Ballard for cars – and direct methanol fuel cells (DMFC). Both systems can operate at relatively low temperatures – from 40 to 80°C – have high power densities and can vary their output quickly to meet shifts in power demand.

PEM systems include a fuel reformer so they can use the hydrogen from any hydrocarbon fuel. DMFCs are less efficient but have the advantage that the anode catalyst draws the hydrogen directly from methanol, eliminating the need for a reformer.

Development work going on in Los Alamos, New Mexico looks to be the most significant for portable applications. Companies including Motorola Labs and recently Mechanical Technology are working with Los Alamos National Laboratory to develop miniature DMFC devices to replace batteries in laptop computers and mobile phones.

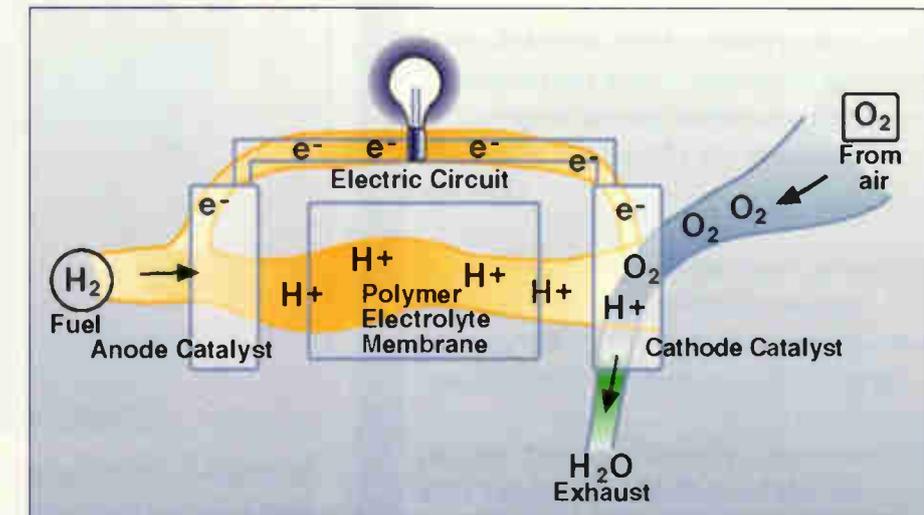Motorola's fuel cells are two to four years away from a market launch, but the company says its liquid methanol-powered cell will be



able to last up to ten times longer than existing rechargeable batteries. Fuel cell powered cell phones could be fuelled by a small methanol reservoir about the size of an ink-pen cartridge.

Energy Related Devices – ERD for short – is another Los Alamos-based firm working on miniature DMFCs for cell phone power supplies. ERD's micro fuel cell is made with multiple layers of thin films. The alcohol side of the film contains a catalyst that breaks the alcohol down into hydrogen ions and carbon dioxide.

The firm says its fuel cells can be made inexpensively using a printing process similar to the manufacture of ICs. It hopes to have production prototypes this year.

ERD is funded by New York-based Manhattan Scientifics that also owns NovArs – a German company in Passau developing PEM fuel cells to provide small external power supplies for products such as DVD players and laptop computers.

NovArs is also looking at domestic appliance applications and recently announced a joint agreement with Electrolux to develop an evaluation prototype of

a fuel cell powered domestic vacuum cleaner.

The NovArs approach to fuel cell design uses composite materials and sealing technology to minimise size and weight. According to founder Dr Arthur Koschany, PEM systems have an energy density of nearly 100 times that of DMFCs making them less bulky for higher power applications.

Koschany sees two main challenges to commercialising the technology for electronics. The first is price. The second is more technical. "The price can be low only if we can make them in high enough quantities and this will involve considerable investment," he says.

"Technically, we need a source of hydrogen because compressed gases are not appropriate for using with electronics. We are developing hydrogen generating chemical hydrides for this purpose and these then need to be integrated into the fuel cell."

NovArs plans to have a pilot production line running in 2002 to produce quantities in the order of thousands. Full commercialisation is three to four years away reckons Koschany. ■

A PEM cell uses a catalyst to split hydrogen into H⁺ ions and electrons. They recombine with oxygen to form water. Diagram courtesy of Breakthrough Technologies Institute/Fuel Cells 2000.

BOOK TO BUY

The definitive biography of the century's godfather of invention—from the pre-eminent Edison scholar "Israel's meticulous research and refusal to shy away from the dodgier aspects of Edison's personality offers a fresh glimpse into the life of the inventor."—*New Scientist*

"Remarkable."—*Nature*


"An authoritative look into Edison's working methods, here leavened by enough personal detail to give the achievements shape."—*Publishers Weekly*

"Israel's book should go a long way toward taking Edison out of the shadows and placing him in the proper light."—*Atlanta Journal-Constitution*

"Exhaustively researched, with strong emphasis on Edison's methods and achievements."—*Kirkus Reviews*

The conventional story of Thomas Edison reads more like myth than history: With only three months of formal education, a hardworking young man overcomes the odds and becomes one of the greatest inventors in history.

But the portrait that emerges from Edison: *A Life of Invention* reveals a man of genius and astonishing foresight whose career was actually a product of his fast-changing era. In this peerless biography, Paul Israel exposes for the first time the man behind the inventions, expertly situating his subject within a thoroughly realized portrait of a burgeoning country on the brink of massive change. Informed by Israel's unprecedented access to workshop diaries, notebooks, letters, and more than five million pages of archives, this definitive biography brings fresh insights to a singularly influential and triumphant career in science.

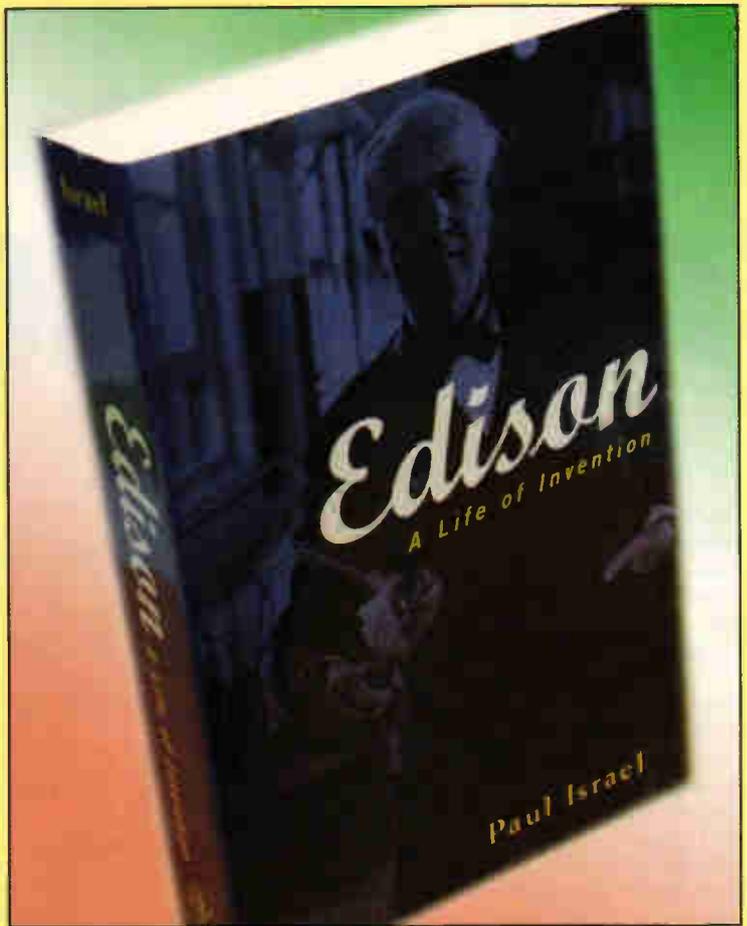

**Post your completed order form to:-
Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS**

**Fax your completed order form to 020 8652 8111
UK Price: £15.00 Europe £17.00 ROW £19.00
Price includes delivery**

How to pay (Edison) paperback

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____

Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

Ring for Latest Reduced Prices on this advert

HP8444A Tracking Generator • 5-1300Mc/s - £450.
 HP8444A OPT 059 Tracking Gen • 5-1500Mc/s - £650.
 HP35601A Spectrum Anz Interface - £300.
 HP4953A Protocol Anz - 3400.
 HP8970A Noise Figure Meter + 346B Noise Head - £3k.
 HP8755A+B+C Scalar Network Anz PI - £250 + MF 180C - Heads 11664 Extra - £150 each.
 HP3709B Constellation ANZ £1,000.
 FARNELL TVS70MKII PU 0-70V 10 amps - £150.
 MARCONI 6500 Network Scalar Anz - £500. Heads available to 40GHz many types in stock.
 Mixers are available for ANZs to 60GHz.
 Marconi TF2374 Zero Loss Probe - £200.
 Rascal/Dana 1250-1261 Universal Switch Controller + 200Mc/s PI Cards and other types.
 Rascal/Dana 9303 True RMS Levelmeter + Head - £450.
 TEKA6902A also A6902B Isolator - £300-£400.
 TEK CT-5 High Current Transformer Probe - £250.
 HP Frequency comb generator type 8406 - £400.
 HP Sweep Oscillators type 8690 A+B + plug-ins from 20Mc/s to 18GHz also 18-40GHz.
 HP Network Analyser type 8407A + 8412A + 8601A - 100Mc/s - 110Mc/s - £500 - £1000.
 HP 8410-A-B-C Network Analyser 110Mc/s to 12 GHz or 18 GHz - plus most other units and displays used in this ad - 8411A-8412-8413-8414-8418-8740-8741-8742-8743-8746-8650. From £1k.
 Rascal/Dana 9301A-9302 RF millivoltmeter - 1.5-20GHz - qty in stock £250-£400.
 Rascal/Dana Modulation Meter Type 90 - 3008 - 6Mc/s - 1.5GHz - £150-£250 - 9000A £300.
 Marconi Microwave 6600A 150Mc/s mainframe with 6650PI - 18-26.5GHz or 6650PI - 26.5-100GHz-£750 or P only £600. MF only £240.
 Gould J30 test oscillator - manual - £150.
 Barr & Stroud Variable Inter EF3 0.1Hz-100Kc/s w/ high pass - 300 pass - £150 other makes in stock.
 Rascal/Dana 9300 RMS voltmeter - £250.
 HP 8115A storage normalizer - £400 with lead + S.A. or N.A. Marconi mod meters type TF2304 - £250 - TF2305 - £1,000.
 Rascal/Dana counters-9990A-9905-9906-9915-16-9917, 9921-50Mc/s-3GHz - £100 - £400 - all fitted with FX standards.
 HP180TR, HP181T, HP182T mainframes £400 - £500.
 HP432A-435A or B-436A power meter - powerheads to 60GHz - £150 - £1750 - spare heads available.
 HP3586A or C selective level meter - £300.
 HP86222A+B Sweep PI-0.1-2.4GHz + ATT £1000-£1250.
 HP86290A+B Sweep PI-2 - 18GHz - £1000 - £1250.
 HP8620C Mainframe - £250. IEEE £350.
 HP8165A Programmable signal source - 1MHz - 50Mc/s - £1k.
 HP3455/3456A Digital voltmeter - £400.
 HP5370A Universal time interval counter - £1k.
 HP5335A Universal counter - 200Mc/s-£1000.
 TEKTRONIX 577 Curve tracer + adaptors - £900 - £1000.
 TEKTRONIX 1502/1503 TDR cable test set - £400.
 HP8699B Sweep PI YIG oscillator .01 - 40GHz - £200-£800 MF-£250. Both £500.
 Dummy Loads + Power att up to 2.5 kWatts FX up to 18GHz - microwave parts new and ex stock - relays - attenuators - switches - waveguides - Yigs - SMA - APC7 plugs - adaptors etc. qty. in stock.
 B&K items in stock - ask for list.
 Power Supplies Heavy duty + bench in stock - Farnell - HP - Weir - Thurlby - Rascal etc. Ask for list. Large quantity in stock, all types to 400 amp - 100kV.
 HP8405A Vector voltmeter - late colour - £400.
 HP8508A Vector voltmeter - £2500.

LIGHT AND OPTICAL EQUIPMENT
 Anritsu ML93A & Optical Lead Power Meter - £260.
 Anritsu ML93B & Optical Lead Power Meter - £300.
 Power Sensors for above MA96A - MA98A - MA913A - Battery Pack MZ95A.
 Anritsu MW97A Pulse Edm Tester.
 PI available - MH914C 1.3 - MH915B 1.3 - MH913B 0.85 - MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM - £500 + one PI.
 Anritsu MW98A Time Domain Reflector.
 PI available - MH914C 1.3 - MH915B 1.3 - MH913B 0.85 - MH925A 1.3 - MH929A 1.55 - MH925A 1.3GI - MH914C 1.3SM - £500 + one PI.
 Anritsu MZ100A E/O Converter.
 + MG912B (LD 1.35) Light Source + MG92B (LD 0.85) Light Source £350.
 Anritsu MZ118A O/E Converter.
 +MH922A 0.8 O/E unit + MH923 A1.3 O/E unit £350.
 Anritsu ML96B Power Meter & Charger £450.

Anritsu MN95B Variable Att. 1300 £100.
 Photo Dyne 1950 XR Continuous Att. 1300 - 1500 £100.
 Photo Dyne 1800 FA. Att £100.
 Cossor-Raytheon 108L Optical Cable Fault Locator 0-1000M 0-10KM £200.
 TEK P6701 Optical Converter 700 MC/S-850 £250.
 TEK OF150 Fibre Optic TDR - £750.
 HP81512A Head 150MC/S 950-1700 £250.
 HP84801A Fibre Power Sensor 600-1200 £250.
 HP8158B ATT OPT 002+011 1300-1550 £300.
 HP81519A RX DC-400MC/S 550-950 £250.
 STC OFR10 Reflectometer - £250.
 STC OFSK15 Machine jointing + eye magnifier - £250.

MISCELLANEOUS ITEMS
 HP 4261 LCR meter - £650.
 HP 4274 FX LCR meter - £750.
 HP 3488 Switch Control Unit + PI B-ans - £500.
 HP 75000 VXI Bus Computers - £13200-DVM quantity.
 HP 83220A GSW LDC P.C.T. 1065/1990MC/S converter for use with 8922A - £1,000.
 HP 1630 1631 1650 Logic ANZ's in stock.
 HP 8754A Network ANZ 4-1300MC/S - £250 + cables - £1,500.
 HP 8754A Network ANZ HSB 4-2000MC/S - £502A + Cables - £7,000.
 HP 8350A Sweeper, 1.5 to 5.4GHz PI-2-8.4GHz + 8354A PI 5.9-12.4GHz PI-3 - £3,800.
 HP MICROWAVE TWT AMPLIFIER 489A 1-2GHz 300B - £400.
 HP PREAMPLIFIER 8447A 0.1-400MHz - £2000 total - £300.
 HP PWR AMPLIFIER 8447D 0.01-1.3GHz - £400.
 HP POWER AMPLIFIER 8447E 0.01-1.3GHz - £400.
 HP PRE + PWR AMPLIFIER 8447F 0.01-1.3GHz - £400.
 HP 3574 Cable Loss Meter 1Hz-13MC/S OPT 001 Dura - £400.
 MARCONI 233A Modulation Meter-50kHz-2.3 GHz - £1,000.
 MARCONI 2610 True RMS Meter - £450.
 MARCONI 833B AF Power Meter - Opt Sinad filter - £250-£350.

MARCONI 6950-6960B Power Meters - Heads - £400-£800.
 MARCONI SIGNAL SOURCE-6055-6056-6057-6058-6059 FX Range 4-10GHz - £250-£400.
 RACAL 1792 COMMUNICATION RX - £500 early - £1,000 - late models in back lighting and base test.
 RACAL 1772 COMMUNICATION RX - £400-£500.
 TEK MODULE MAINFRAMES - T8015-502-503-504-506-508-509-5006.
 TEK PI 5010-M1 Prog Mtr Interface - £250. FG Prog 20MC/S Function Gen - £400. ST Prog Scanner - £100 - DM Prog LHM - £400.
 TEK YU00 OSCILLOSCOPE MAINFRAMES - 7603-7623-7633-7634-7644-7644-7694A-7104 - £150-£1,000.
 TER 1000 P's - 7A11-7A12-7A13 - 7A18-7A19-7A22-7A24-7A26-7A29-7A42-7B11-7B15-7B54-7B58-7B85-7B92A-7D15-7D20.
 TEK 7000 - ZS1 - S1 - 7S14-7W11-S1-S2-S3A-S4-S5-S6-S51-S53-921.
 HP POWER SUPPLIES - 8621A-6623A-6624A-8632A-8652A. Other available. Also 6000 types EPO.

WE KEEP IN STOCK HP and other makes' EITF Frequency dividers which when fitted to the RF output socket of a S/Generator double the output frequency EG.50-1300MC/S to 50-2600MC/S price from £250 - £450 each.

SPECTRUM ANALYZERS
 HP 3160A 5Hz-50kHz - £750.
 HP 3162A Dual 0.2Hz-25.5kHz - £1,500.
 HP 3163A 10Hz-40MC/S - £3,000.
 HP 3168A 10Hz-150MC/S - £7,500.
 HP 8598A 100Hz-1.5GHz - £3,000.
 HP 8568B 100Hz-1.5GHz - £3,000.
 HP 8590B 100Hz-1.5GHz - £4,500.
 HP 8598B 1.1MC/S - 0.1-92GHz - £3,500.
 HP 3511A Signal Analyzer 15Hz-50kHz - £1,000.
 YLK492 2kHz-21GHz OPT 2 - £2,500.
 TEL492P 2kHz-21GHz OPT 1-2-3 - £3,000.
 TEK492AP 50kHz-21GHz OPT 1-2-3 - £4,000.
 TEK492BP 50kHz-21GHz - £3,000-£4,000.
 TEK495 100Hz-1.8GHz - £2,000.
 HP 8557A 0.01MC/S-350MC/S - £500 + MF180T or 180C - £150 - 182T - £500.
 HP 8558B 0.01-1500MC/S - £750 - MF180T or 180C - £150 - 182T - £500.
 HP 8559A 0.01-21GHz - £1,000 - MF180T or 180C - £150 - 182T - £500.
 HP 8901A AM FM Modulation ANZ Meter - £800.
 HP 8901B AM FM Modulation ANZ Meter - £1,750.
 HP 8903A Audio Analyzer - £1,000.
 HP 8903B Audio Analyzer - £1,500.

MARCONI 2370 SPECTRUM ANALYZERS - HIGH QUALITY - DIGITAL STORAGE - 30Hz-1100MC/S large qty to clear as received from Gov - all sold as is from complete or add £100 for basic testing and adjustment - callers preferred - pick your own from over sixty units - discount on qty's of five.
 A EARLY MODEL GREY - horizontal alloy cooling fins - £250.
 B LATE MODEL GREY - vertical alloy cooling fins - £300.
 C LATE MODEL BROWN - as above (few only) - £500.

OSCILLOSCOPES
 TEK 465-465B 100MC/S + 2 probes - £250-£300.
 TEK 466 100MC/S storage + 2 probes - £200.
 TEK 475-475A 200MC/S-250MC/S + 2 probes - £300-£350.
 TEK 2213-2213A-2215-2215A-2224-2225-2235-2236-2245-60-100MC/S - £250-£400.
 TEK 2445 4ch 150MC/S + 2 probes - £450.
 TEK 2445A 4ch 150MC/S + 2 probes - £600.
 TEK 2445B 4ch 150MC/S + 2 probes - £750.
 TEK 468 2ch 300MC/S + 2 probes - £500.
 TEK 465 95MC/S + 2 probes - £550.
 TEK 2445 4ch 150MC/S - £1,150.
 TEK 2445A 4ch 150MC/S - £1,550.
 TEK D.S.O. 2430A -150MC/S + 2 probes - £1,750.
 TEK D.S.O. 2440 -300MC/S + 2 probes - £2,000.
 TEK TAS 475-485 -100MC/S-20MC/S 4 ch + 2 probes - £900-£1,1K.
 HP1740A - 100MC/S + 2 probes - £250.
 HP1741A - 100MC/S storage + 2 probes - £200.
 HP1742A - 1722A - 1725A - 200MC/S + 2 probes - £300-£400.
 HP1744A - 100MC/S storage large screen - £250.
 HP1745A - 1746 - 200MC/S large screen - £350.
 HP54100A 1.5Hz probe - £300.
 HP54700A 150MC/S triggering - £500.
 HP5401A 100MHz digitizing - £500.
 HP54100A 150MHz digitizing - £1,000.

MICROWAVE SOURCES - ALL LED READOUT
 EIP 351D Autohet 20Hz-18GHz - £750.
 EIP 371 Micro Source Locking - 20Hz-18GHz - £850.
 EIP 451 Micro Pulse Counter - 300MC/S-110MHz - £1,000.
 EIP 585 Microwave Frequency Counter - 10Hz-18GHz - £110.
 EIP 548A Microwave Frequency Counter - 10Hz-18GHz - £110.
 EIP 675 Microwave Source Locking - 10Hz-18GHz - £1,2K.
 EIP 588 Microwave Pulse Counter - 100MC/S-26.5GHz - £1,4K.
 SD 6054B Micro Counter 20Hz-24GHz - SMA Socket - £800.
 SD 6054D Micro Counter 20Hz-18GHz - N Socket - £700.
 SD 6054D Micro Counter 800MC/S 18GHz - £190.
 SD 6246A Micro Counter 20Hz-26GHz - £1,2K.
 SD 6244A Micro Counter 20Hz-4.5GHz - £400.
 HP5352B Micro Counter OPT 010-005-46GHz - new in box - £1,000.
 HP5340A Micro Counter 10Hz-18GHz - Nixey - £500.
 HP5342A Micro Counter 10Hz-18-24GHz - £800-£1K - OPTS 001-003-003-011 available.
 HP5342A + 5344S Source Synchronizer - £1,5K.
 HP5344A 500Hz - S 11 Digit LED Readout - £400.
 HP5345A + 5355A Plugin - 4GHz - £700.
 HP5345A + 5355A Plugin with 5356A 18GHz Head - £1K.
 HP5385A 1GHz 5386A-5386A 3GHz Counter - £1K-£2K.
 Rascal/Dana Counter 1991-160MC/S - £200.
 Rascal/Dana Counter 1992-1.3GHz - £600.
 Rascal/Dana Counter 9921-3GHz - £350.

SIGNAL GENERATORS
 HP8640A - AM-FM 0.5-512-1024MC/S - £200-£400.
 HP8640B - Phase Locked - AM-FM 0.5-512-1024MC/S - £500-£1,2K. Opts 1-2-3 available.
 HP8654A - B AM-FM 10MC/S-520MC/S - £300.
 HP8656A SYN AM-FM 0.1-990MC/S - £900.
 HP8656B SYN AM-FM 0.1-990MC/S - £1,5K.
 HP8657A SYN AM-FM 0.1-1040MC/S - £2K.
 HP8660C SYN AM-FM-PM-0.01-1300MC/S-2600MC/S - £2K.
 HP8660D SYN AM-FM-PM-0.01-1300MC/S-2600MC/S - £2K.
 HP8673D SYN AM-FM-PM-0.01-26.5 GHz - £12K.
 HP3312A Function Generator AM-FM 13MC/S-Dual - £300.
 HP3314A Function Generator AM-FM-VCO-20MC/S - £600.
 HP3325A SYN Function Generator 21MC/S - £800.
 HP3326A SYN 2CH Function Generator 13MC/S IEEE - £1,4K.
 HP3336A-B-C SYN Func/Level Gen 21MC/S - £400-£300-£500.
 Rascal/Dana 9081 SYN S/G AM-FM-PH-5-520MC/S - £300.
 Rascal/Dana 9082 SYN S/G AM-FM-PH-1.5-520MC/S - £400.
 Rascal/Dana 9084 SYN S/G AM-FM-PH-0.01-104MC/S - £300.

MARCONI 2019A SYNTHESIZED SIGNAL GENERATORS - 80KC/S-1040MC/S - AM-FM - £400 inc. instruction book - tested.
 MARCONI 2022E SYNTHESIZED SIGNAL GENERATOR - 10KC/S-1.01GHz AM-FM - £500 inc. instruction book - tested.
 R&S APN 62 LF Sig Gen 0.1Hz - 260 kHz c/w book - £250.

MARCONI 2383 S.ANZ 100Hz - 4.2 GHz. £2K.
 H.P. RF AMP 8349A 2-20 GHz microwave. £2K.
 H.P. RF AMP 8347A 100 kHz - 3GHz £1,500.
 H.P. 8922 radio communication test sets.
 G - H - M. models various. £2,000 - £3,000 each.
 H.P. 4193A VECTOR IMPEDANCE METER + probe kit. 400 kHz. To 110 M/L/S. £3,500.

H.P. 83220A - E GMS UNITS for above. £1,000 - £1,500.
 WAVETEK SCUMBERGER 4031 RADIO COMMUNICATION TEST SET. Internal Spectrum ANZ. £1,800 - £2,000.
 ANRITSU MS555A2 RADIO COMM ANZ. To 1000MC/S. No C.R. tube in this model. £450.
 TEK 2445A - 4CH - 150ML/S SCOPE + New X1 + X10-probe. Instruction book. £500 each.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. SAE FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA. ITEMS MARKED TESTED HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-SYNCRS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

Johns Road, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel: (01274) 684007. Fax: 651160

CIRCLE NO. 119 ON REPLY CARD

Available exclusively from
Electronics World



Amazing music

21 tracks – 72 minutes of recordings made between 1900 and 1929. These electronically derived reproductions are no worse than – and in many cases better than – reproductions of early 78rev/min recordings – some are stunning...

All tracks on this CD were recorded on DAT from cylinders produced in the early 1900s. Considering the age of the cylinders, and the recording techniques available at the time, these tracks are of remarkable quality, having been carefully replayed using modern electronic technology by historian Joe Pengelly.

Pandora's drums

Unique and atmospheric music recorded in the early 1900s – the days *before* 78s.

Use this coupon to order your copy of Pandora's drums

Please send me CD(s) at **£11.99** each including VAT plus **£1.50** carriage per order UK, or **£3.00** overseas for which I enclose:

Cheque

Credit card details tick as appropriate

Name

Address

Phone number

Total amount **£.....**

Make cheques payable to Reed Business Information Group.
Or, please debit my credit card.

Card type (Master/Visa)

Card No

Expiry date

Please mail this coupon to *Electronics World*, together with payment. Alternatively fax credit card details with order on 0208 652 8111. Address orders and all correspondence relating to this order to Pandora's drums, Room 514, Electronics World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Track

- 1 **Washington Post March**, Band, 1909
- 2 **Good Old Summertime**, The American Quartet 1904
- 3 **Marriage Bells**, Bells & xylophone duet, Burckhardt & Daab with orchestra, 1913
4. **The Volunteer Organist**, Peter Dawson, 1913
5. **Dialogue For Three**, Flute, Oboe and Clarinet, 1913
6. **The Toymaker's Dream**, Foxtrot, vocal, B.A. Rolfe and his orchestra, 1929
- 7 **As I Sat Upon My Dear Old Mother's Knee**, Will Oakland, 1913
- 8 **Light As A Feather**, Bells solo, Charles Daab with orchestra, 1912
- 9 **On Her Pic-Pic-Piccolo**, Billy Williams, 1913
- 10 **Polka Des English's**, Artist unknown, 1900
- 11 **Somebody's Coming To My House**, Walter Van Brunt, 1913
- 12 **Bonny Scotland Medley**, Xylophone solo, Charles Daab with orchestra, 1914
- 13 **Doin' the Raccoon**, Billy Murray, 1929
- 14 **Luce Mia!** Francesco Daddi, 1913
- 15 **The Olio Minstrel**, 2nd part, 1913
- 16 **Peg O' My Heart**, Walter Van Brunt, 1913
- 17 **Auf Dem Mississippi**, Johann Strauss orchestra, 1913
- 18 **I'm Looking For A Sweetheart And I Think You'll Do**, Ada Jones & Billy Murray, 1913
- 19 **Intermezzo**, Violin solo, Stroud Haxton, 1910
- 20 **A Juanita**, Abrego and Picazo, 1913
- 21 **All Alone**, Ada Jones, 1911

Total playing time 72.09

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

64-tap pots with four 6-bit E²PROM registers

Xicor has introduced the X9421 and X9429 64-tap, single supply, non-volatile digital potentiometer ICs. The devices are for applications in which a variable resistance value must be maintained during the system manufacturing process. They have four 6-bit EEPROM registers per potentiometer for storage of tap settings and system parameters. This lets the

system designer automatically save resistance values during power down and preset values to suit system demands. The X9421 communicates via a serial port supporting the SPI interface, while the X9429 uses a two-wire interface. Both operate from a 2.7V single supply voltage and each has four non-volatile registers that can be individually programmed. Applications include fibre optic modules, RF amplifier biasing, LCD brightness control, power supply calibration, battery operated applications and vending machines. They can recover their last position after a power down cycle and suit manufacturing applications that use preset analogue system values. Standby current is 200nA typical and 5µA maximum.

Xicor
Tel: 01993 700544
www.xicor.com

RF channel emulator with modelling feature

Telecom Analysis Systems has added a dynamic channel modelling feature to its 4500 Flex5 RF channel emulator. Available from Sematron, the 3G power-delay-profile emulation mode can be programmed to provide time-varying RF channel profiles that let it meet and exceed CDMA2000 and W-CDMA test specifications. It implements a dynamic, mobile propagation environment for time-sensitive algorithms such as rake finger management and wide band channel estimation. It also implements moving-propagation and birth-death channel models in accordance with 3G specifications. These two classes of channel models emulate the temporal variations in the propagation channel by changing delay spread characteristics versus time. A diversity technique lets the



receiver pick up multiple signal paths over time and select the strongest rather than the average, which may be several decibels less than the strongest. This is for testing smart antennas that are proposed for 3G networks where up to four TAS4500 units can be combined. It also provides the ability to go beyond two-path dynamic models by letting all its paths be independently varied over time.

Sematron
Tel: 01256 81222
www.sematron.com

32-bit micros based on v850E Risc architecture

NEC has introduced 32-bit microcontrollers based on V850E Risc architecture with programmable CAN gateway engines. The Atomic and CarGate devices have a hardware-based CAN that lets them serve as gateways for communication between networks within the vehicle. This function lets them manage multiple tasks simultaneously from up to five automotive networks, such as the power train, navigation system or comfort control system. By implementing the CAN bridge in hardware, the microcontroller relieves the CPU of routine tasks, such as data transfer from one message buffer to another. Time triggered functionality lets signals be delivered based on time slots rather than arbitrary external events. Time out monitoring lets the microcontrollers anticipate the receipt of critical messages in a defined time frame. For example, an air bag system can be programmed to communicate with the microcontroller regularly, and then the microcontroller will investigate if no message is received. The Atomic controller supports three CAN interfaces and includes 256kbit on chip ROM and peripherals such as LCD controller, 12 channel A/D converter and various 16 and 32-bit timers. The CarGate has 128kbit ROM and supports five CAN interfaces. Flash memory versions of both are also available to support secure self-programming of the memory.

NEC Electronics
Tel: 01908 691133
www.nec.com



Please quote *Electronics World* when seeking further information



Solid-state relays for DC switching

Crydom has introduced its D06D chassis-mounting solid-state relays for DC switching applications. Rated at up to 100A DC at up to 60V DC, the devices are for DC motor control, solenoid switching, DC lamp switching and battery isolation. They can be operated by an input of 3.2 to 32V DC, typically drawing 10mA. Mosfet output technology provides on-state resistance of 10mΩ or less at full rated current, and simplifies paralleling of devices. Dielectric strength at 60Hz is 2.5kV rms and minimum insulation resistance at 500V DC is 1000MΩ. Maximum input-output capacitance is 50pF. They can operate in harsh environments regardless of orientation and there are no moving parts. UL and CSA approved, they are supplied in a panel-mount package weighing 87g.

Crydom
Tel: 01202 857300
www.crydom.com

Digital baseband for Eureka DAB radios

Texas Instruments has unveiled a reference design and single-chip digital baseband for Eureka DAB radios to help make products such as integrated digital radios and Internet audio players for automotive, portable and home applications. The TMS320DRE200 digital baseband includes programmable DSP technology and Radioscape software. The reference design contains components necessary to design a receiver including the DRE200 baseband, analogue parts and RF circuitry. The baseband consumes less than 200mW. The software lets users add applications on top of the baseband, such as integrating MP3 decoding with digital radio on one chip.

Texas Instruments
Tel: 01604 663000
www.ti.com

Power relay module is customisable

A power relay module that can be customised for automotive requirements has been introduced by Tyco Electronics. Applications include power windows, fuel pumps, power sunroofs, wiper control, vehicle lighting and cooling fans. With a footprint of 26.2 by 26.2mm and a height of 25.2mm, the F4/7 can be supplied with plug-in terminals positioned to ISO7558 or terminals preprepared for soldering to an integrated PCB. Terminals one, two, six, seven, eight and nine

are optional, while terminals three, four and five are fixed. Pin assignment is according to ISO7880. Limiting continuous current is up to 70A at 23°C or 50A at 85°C. Nominal voltages are 12 and 24V; a 24V version with a contact gap more than 0.8mm can be supplied. Nominal unsuppressed power consumption is 1.6W at the nominal voltage, typical operating time 7ms and release time 2ms.

Tyco Electronics
Tel: 08706 080 208
www.tycoelectronics.com

Inlet filters rated at 16 and 20A

Schaffner EMC has introduced EN9222 IEC inlet filters rated at 16 and 20A for applications from industrial machinery to vending machines. They use the IEC320C20 connector and are safety rated for IEC950 applications. Other approvals include VDE, UL, CSA and Semko. The 20A version has dual 0.4mH inductors, with twin Y capacitors on the load side and one X capacitor on the line side.

Schaffner
Tel: 0118 977 0070
www.schaffner.com

Electrolytics come in laminated cases

The RU electrolytic capacitors from Nichicon come in laminated cases and have operating temperatures of -40 to +85°C at 6.3 to 400V and -25 to +85°C at 450V. Working voltage is 6.3 to 450V, capacitance 6.8 to 6800µF,

tolerance 20 per cent and allowable ripple 190 to 930mA depending on capacitance and working voltage. The radial lead capacitors measure 12.5 or 25mm diameter by 12.5mm high and are available with trimmed or formed leads.

Nichicon
Tel: 01276 685531
www.nichicon-us.com

USB connectors take an eighth of the space

The Mini-BTM USB connectors from Molex take up about an eighth of the space of standard USB-B connectors. They are for portable applications such as digital cameras, cell phones and PDAs and comply with USB 2.0, which enables speeds up to 480Mbit/s. The design includes five circuits, with one reserved for future use. Features of the 0.8mm pitch unit include metal shielding and grounding fingers for EMI protection and a lock for secure mating. The



connector is rated at 30V and 1.0A. There are through-hole and surface-mount versions, both with an above-board height of 3.95mm. The SMT version includes four solder tabs for PCB retention, and is available with cover tape for pick-and-place equipment. The cable plug has a standard length of 1.0m in Mini-B-to-USB-A construction, with other lengths available. The plug side can be ordered as a tested cable assembly or plug component kit.

Molex
Tel: 01252 720751
www.molex.com

Two feed signal splitter

The Faraday passive splitter provides two SDI or AES feeds from one source. For short runs of cable, it can replace digital distribution amplifiers. From a good SDI signal source it will support up to about 40m of Belden 8281 cable. Typical uses are in small studios, edit suites and multiple displays in offices. The device is fitted with BNC connectors and does not require a power supply. It may be hung on the cable or, where multiple units are required, fitted into a 1U high 19in rack, which can be supplied.

Faraday Technology
Tel: 01782 661501
www.faradaytech.co.uk



Please quote *Electronics World* when seeking further information

SM capacitors extend to 100V DC rating

The VS surface mount aluminium electrolytic capacitors from Panasonic have capacitance values from 0.1 to 1500 μ F. Rated working voltage options are 4, 6.3, 10, 16, 25, 35, 50, 63 and 100V DC. Case diameters are 10mm for the highest capacitance parts, falling to 3mm for devices with lower values. All capacitors with case diameters of 6.3mm or lower have heights of 5.4mm, while the maximum board mounting height is 10.2mm. For operation



between -40 and $+85^{\circ}\text{C}$, they have maximum DC leakage currents between 3 and 6 μ A and ripple currents at 120Hz and 85°C are 1mA rms for 0.1 μ F devices and 700mA rms for the 1500 μ F parts.

Panasonic Industrial
Tel: 01344 853667
www.piel.co.uk

SBC for Pentium III or Celeron applications

The Robo 678 single board computer from Portwell provides Intel Celeron or Pentium III processing power up to 600 or 850MHz



Rectifier is efficient to 86 per cent

International Rectifier has introduced topology-specific Hexfet power Mosfets for isolated and buck DC-to-DC converters. As DC-to-DC converter output voltages approach 1V, the Mosfets increase efficiency by up to one per cent. The 100V IRF7473 in an SO-8 package is for the primary stage of two-stage isolated converters with 48V input, 1.6V output at 60A. Peak efficiency ratings up to 90 per cent can be achieved when it is matched with the IRF7822 synchronous rectification Mosfet. The IRF7473 can also be used in a full bridge configuration. The 40V Mosfets in SO-8 packages work with a 28V bus in notebook

computers. There is a choice between two control parts, the IRF7468 and IRF7469, and two synchronous Mosfets, the IRF7470 and IRF7471. Synchronous buck topologies using the IRW7468 and IRF7470 reach an efficiency of 82 per cent in 28V input, 1.3V output converters running at 300kHz. Four additional Mosfets (IRF7453, IRF7450, IRF7451 and IRF5801) have reduced on-resistance and gate charge and are for 48V input, active and passive reset, primary-side isolated DC/DC converters below 30W.

International Rectifier
Tel: 0208 645 8003



respectively. It supports up to 512Mbyte of SDram and is based on the Intel 815E chipset. Onboard features include dual 10/100baseT Ethernet, FSB up to 133MHz and an integrated 3D graphic controller with DVMT and 4Mbyte display cache. It is PICMG compliant and has two UDMA dma 33, 66 or 100 IDE ports, one disk-on-chip socket that supports up to 288Mbyte of flash memory and a PCI connector for expansion. An optional Ultra-160 SCSI

daughter board is available. Built in system monitoring and a watchdog timer are included.
Portwell
Tel: 01202 813816
www.portwell.co.uk

Micro reset circuit is radiation-hardened

Intersil has introduced a radiation-hardened power-up microprocessor reset circuit. The Star Power IS705RH can monitor power supply voltage levels and interface with satellite control units to ensure proper device operation during power-up. It sends a reset pulse to the microprocessor when the supply reaches a nominal operating voltage of 4.65V. This prevents code execution errors that occur when signals are present on microprocessor inputs during power-up. Features include a watchdog circuit that verifies proper reset has occurred and power-fail circuit for monitoring other supply voltages. Single

event latch-up immunity is 83MeV/(mg/cm²) and single event upset capability is 38MeV/(mg/cm²). It is available in an eight-lead flatpack package, either as QML class V or Q.
Intersil
Tel: 01344 350250
www.intersil.com

Simulator software for high-speed networking

Ansoft has announced version 8.0 of its HFSS structure simulator software. It is a full-wave finite element electromagnetic simulator that lets engineers design three-dimensional structures such as connectors, IC packages and antennas in cellular telephones, broadband communications systems and microwave circuits. Models can be generated for physical layer transient simulations of Gigabit Ethernet IC packages, boards and connectors, optoelectronic

Please quote *Electronics World* when seeking further information

devices for broadband fibre modulators, receivers and routers, and electronic devices for signal conversion in hybrid fibre-coaxial systems. With the full-wave Spice add-on module, users can generate frequency-dependent Spice models automatically from full-wave electromagnetic field simulation.

Ansoft
Tel: 0208 891 6106
www.ansoft.com

Wafer-scale package saves on space


The USP-6 plastic moulded package from Torex is about two-thirds the size of an SOT-25 package. Doing away with the conventional lead frame, it measures 1.8 by 2.0 by 0.65mm and has a 0.5mm pin pitch.

Torex Semiconductor
Tel: 01509 211992
www.torex.co.jp

VDSL filters in a single package

APC's APC77110 and APC77112 are integrated hybrid filters for use with VDSL and 10baseS applications. Compatible with the Infineon PEB22810, 22811 and 22812 chipset, the components combine common mode choke, hybrid and transmit and receive filters. Samples are available to let users evaluate central office and user modem designs and for field trials. A Pots ISDN low pass filter (APC77101) is available to support designs using either product. In system tests over category five cable, the components connected at a symmetric data rate of 12Mbit/s to a distance of 1.2km, supporting telephony applications.

APC
Tel: 01634 290588
www.apc-pic.co.uk

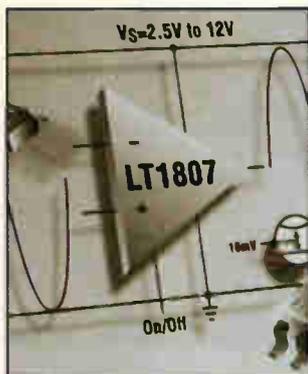

Op-amp operates on supplies down to 2.5V

Linear Technology has introduced the LT1807 dual 3.5nV/√Hz, rail-to-rail single supply amplifier. Gain bandwidth product is 325MHz and THD -80dBc at 5MHz. Input common mode range includes both rails. The output stage swings within 12mV of each rail for supplies down to 2.5V. Maximum offset voltage is less than 0.5mV, CMRR is 106dB and signal voltage gain 300V/mV. Applications include broadband digital communications, data acquisition and video. Slew rate is 140V/μs, supply range 2.5 to 12.6V and output current 85mA. For operation over the industrial and commercial temperature ranges, it is available in eight-pin SOIC and MSOP packages.

Linear Technology
Tel: 01276 677676
www.ansoft.com

CCD products have 325MHz bandwidth

Marconi is launching products based on its L3Vision CCD technology, including scientific sensors, modules, digital and analogue cameras and camera subassemblies. Applications include night surveillance, industrial monitoring, dynamic bio-sciences, machine vision and astronomy. The sensors use an output amplifier circuit to improve vision at low light levels. Scientific and TV rate sensor formats, including 512 and 1024 pixels, are being developed. Drive circuitry comes in two compatible formats. The HV clock module provides all the inputs required

for driving the sensors. A camera control module consists of a buffer and bias board with a video logic board and interfaces directly with the HV clock module allowing complete control of the CCD sensor. The camera subassembly is a circuit assembly where there is no case or lens mount. The incident light is converted directly into signal electrons and read out through a port at normal video frame rates allowing customer control of functional modes.

Marconi
Tel: 01245 493493
www.marconitech.com

Multiplexer IC with three DS3 framers

Vitesse Semiconductor has introduced the Timestream VSC9675 IC with three integrated DS3 framers, M13 multiplexers and 84 T1 and J1

framers. Applications in the access and switching infrastructure include access concentrators, routers, and switches. It supports a combination of channelised and unchannelised DS3 signals. Supported channelised formats include M23 and C-bit mode and supported T1 and J1 formats include SF and ESF. Features include performance monitoring and diagnostics such as network and local loopback. It is packaged in a 304-pin HBGA with power dissipations of 1.0, 1.5 or 2.0W.

Vitesse
Tel: 001 805 388 3700
www.vitesse.com

Accelerometer cuts monitoring costs

Endevco has introduced the Piezopak 56 accelerometer for commercial and industrial OEM engineering. The device is



PC/104 board with Elan-400 CPU


The PC/104 Microspace MSM4865V module from Digital-Logic is an embedded board based on an AMD 66MHz Elan-400 486SX CPU. Standard interfaces include a PS/2 keyboard, mouse, printer, floppy disk drive, EIDE hard disc and four com ports. A clock-controlled 5 to 3.3V DC-to-DC converter has more than 90% efficiency. Power saving functions make it possible to control power consumption in the 50 to 710mA range. It operates within a temperature range of -25 to +70°C and does not require active cooling. A version for -40 to +85°C is also available. Dram can be extended from 4 to 32Mbyte. Two flash technologies are available - program memory with capacities of 0.5 to 8Mbyte with a flash file system or an IDE hard disk-compatible flash drive that can be directly attached to the module. Features include an eight by 16 key matrix decoder, watchdog and E²PROM for saving the setup settings. Graphics support is provided by a Chips & Technologies 65548 and 65550 SVGA controller with 1Mbyte of video memory.

Digital Logic
Tel: 00 41 32 681 5800
www.digitallogic.com

RANGER XL

The Complete Integrated Schematic PCB Layout Package

Too good for words

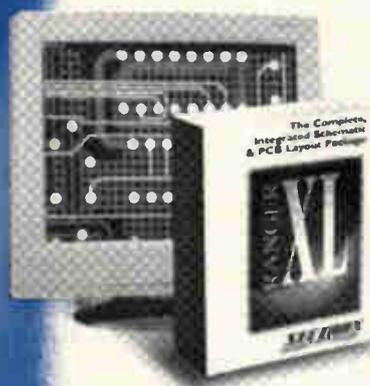

The New Ranger XL Series

Ranger 2 for Windows £60
NEW Ranger 2XL £500
NEW Ranger XL from £950
FREE Website Download Demo



Old Buriton Lime Works, Buriton, Petersfield, Hants. UK GU31 5SJ
 Tel: (44) 01730 260062 Fax: (44) 01730 267273

CIRCLE NO.120 ON REPLY CARD

ADVANCED ACTIVE AERIAL



The aerial consists of an outdoor head unit with a control and power unit and offers exceptional intermodulation performance: SOIP +90dBm, TOIP +55dBm. For the first time this permits full use of an active system around the lf and mf broadcast bands where products found are only those radiated from transmitter sites

- General purpose professional reception 4kHz-30MHz.
- -10dB gain, field strength in volts/metre to 50 Ohms.
- Preselector and attenuators allow full dynamic range to be realised on practical receivers and spectrum analysers.
- Noise - 150dBm in 1Hz. Clipping 16 volts/metre. Also 50 volts/metre version.
- ★ Broadcast Monitor Receiver 150kHz-30MHz. ★ Frequency Shifters for Howl Reduction ★ Stereo Variable Emphasis Limiter 3 ★ PPM10 In-vision PPM and chart recorder ★ Twin PPM Rack and Box Units. ★ PPM5 hybrid, PPM9 microprocessor and PPM8 IEC/DIN -50/+6dB drives and meter movements

SURREY ELECTRONICS LTD

The Forge, Lucks Green, Cranleigh GU6 7BG
 Telephone: 01483 275997 Fax: 01483 276477

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
 ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
 BFR BFS BFT BFW BFX BFY BLX BS BR BRX BRY BS
 BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUW
 BUW BUX BUZ CA CD DX CXA DAC DG DM DS
 DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
 KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
 MC MDA J MJE MJF MM MN MPS MPSA MP5H MPSU
 MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
 SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
 STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
 TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
 UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
 ZTX + many others

We can also offer equivalents (at customers' risk).

We also stock a full range of other electronic components.

Mail, phone, Fax, Credit Card orders & callers welcome.




Cricklewood Electronics Ltd

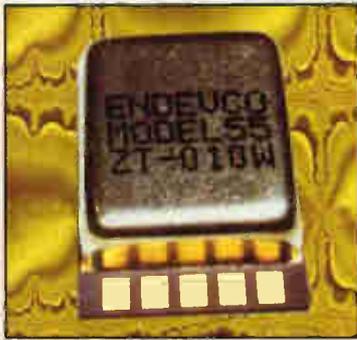40-42 Cricklewood Broadway, London NW2 3ET
 Tel:020 8452 0161 Fax: 020 8208 1441

CIRCLE NO.121 ON REPLY CARD

Please quote *Electronics World* when seeking further information



sealed against environmental contamination, shielded, ground isolated and configured with five solder pads for power and signal connection. It measures 20.3 by 15.2 by 5.3mm and can be packaged in custom housings. The model is powered by 2 to 10mA constant current, requiring a compliance voltage of +10 to +20V DC. Sensitivities of 10 and 100mV/g are available providing full-scale measurement ranges of 200 and 20g respectively. An optional temperature sensor with a linear output of 10mV/°C is available, requiring a separate supply from 4.5 to 10V DC.

Endevco
Tel: 01438 739020
www.endevco.com


Packet processing engine for comms

Blue Wave Systems has extended its family of Construct communications processing building blocks with a packet processing hardware platform. The CPCI/C5441 provides OEMs with up to 672 channels, each of which can provide compressed voice or fax relay over IP or ATM, in a CompactPCI slot. It provides telecoms equipment makers with a platform for applications such as softswitches and IP-enabled services for wireline and 3G wireless networks. It uses the programmable TMS320VC5441 DSP from Texas Instruments and Tology Software. The ATM interface makes the device a suitable building block for developing and deploying voice over ATM for DSL applications in the local loop. The device provides direct termination of multiple T1, E1, T3 and E3 and can use the H.110 interface for in-chassis call distribution and to

Firewire controller with debug indicators

From BVM is the PMC-FW2 three-port PMC Firewire controller module. Using the Texas TSB12LV26 IEEE1394 OHCI compliant host controller and the TSB41AB3 three-port transceiver and arbiter, the module complies with IEEE1394a-2000. LED indicators for cable connected, transmit and receive, and throughput speed are on the back of the module. The module supplies cable power from an on-board converter powered from the host processor's +12V line, sufficient to power up the remote phy ICs on powered-off modules. It enables a hot swap plug-and-play capability for the attached peripherals, allowing, for instance, a faulty hard drive to be swapped out without powering down the host system. Each front panel mounted independent port supports transfer speeds of 100, 200 or 400Mbits/s, providing an interface from industrial workstations or servers to mass storage devices, video equipment, scanners and other equipment.

BVM
Tel: 01489 780144
www.bvmltd.co.uk

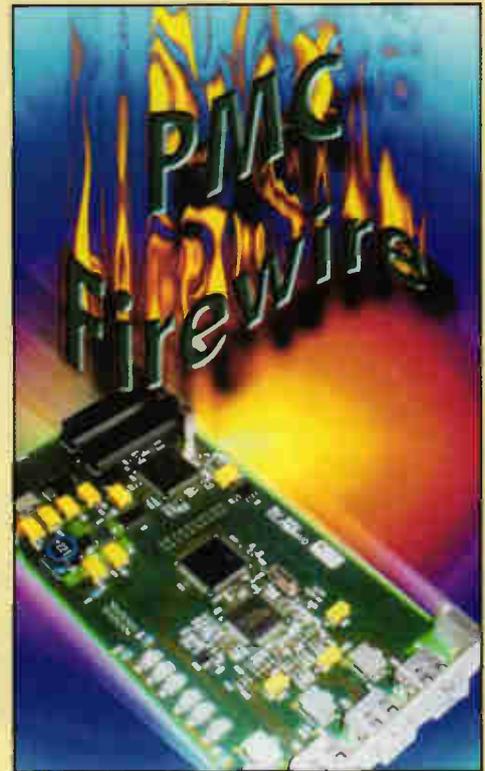


support external line termination, such as OC/3. Features include HA drivers, an IPMI interface, SNMP management interface and hot swap capability. A redundant 100baseT Ethernet interface gives the board a multipath redundant architecture. It will initially run under the Solaris 2.8 64-bit operating system and Linux.

Blue Wave
Tel: 01509 654444
www.bluews.com

Ceramic capacitors have no polarity

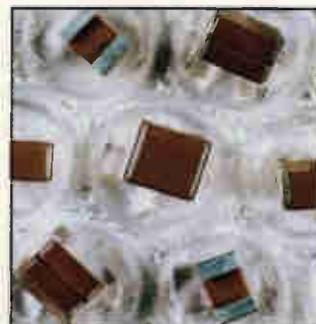Flint's Mega Cap ceramic capacitors in the TDK CGK series have no polarity, so can be mounted in either direction. There are two case sizes –



model 57D measures 5.5 by 5.5 by 7.0mm and model 45D 5.5 by 5.5 by 6.0mm. They can absorb stress from thermal and mechanical shocks even on metal substrates such as aluminium. Applications include smoothing circuits, temperature variable systems, maintenance free power supplies, vehicles and DC to DC converters. The Y5U and X7R models are constructed from slightly different materials to provide ratings of 16 to 100V and 16 to 630V respectively.

Flint
Tel: 01530 510333
www.flint.co.uk

High-speed matched impedance interfaces

Samtec can supply surface mount, micro pitch interfaces for matched impedance applications. Options include edge-mount designs and elevated designs with 16, 19 and 22mm board spacings. These interfaces in the QTE series terminate on 0.8mm pitch and have an integral ground plane. From 40 to 200 I/Os are available. They are tested for 50 and 70Ω systems for impedance, VSWR, attenuation,

crosstalk, propagation delay and rise time at frequencies from 10MHz to 1GHz.

Samtec
Tel: 01236 739292
www.samtec.com

Enclosure houses Vme64x open system architecture

A VME64x compatible 19in subrack is being introduced by Schroff. The unit has built in EMC shielding and an integrated chassis monitoring module to control system parameters. Applications include industrial automation, measurement and control. Integrated modules provide power, thermal management and system monitoring. The 1kW DC power supply tray plugs directly into the backplane from the rear and can be installed and removed using IET handles. Two fan trays that are accessed from the front of the subrack each give 500m³/hr airflow. Thermal management includes speed control and failure supervision. The 6U high boards fitted from the front of the enclosure plug into a 7U high backplane that uses SMT technology to provide 21 slots.

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX ST as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture + full details

FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are **BRAND NEW** or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GR 1.2 Meg (for IBM pc's) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for HH 5 1/4" Floppy / HD £29.95(B)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Shugart 810 8" SS HH Brand New £190.00(E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) New £79.95
 - 2 1/2" TOSHIBA MK2101MAN 2.16 Gb laptop (19 mm H) New £89.50
 - 2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H) New £105.00
 - 2 1/2" TOSHIBAMK6409MAV 3.1Gb laptop (12.7 mm H) New £190.00
 - 2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £14.95
 - 3 1/2" FUJII FK-309-26 20mb MFM I/F RFE £59.95
 - 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
 - 3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00
 - 3 1/2" QUANTUM 40S Prodriv 4e 42mb SCSI I/F, New RFE £49.00
 - 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 mb RL I/F RFE £69.95
 - 5 1/4" CDC 94205-51 40mb HH MFM I/F Refurb £69.95
 - 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 8" NEC D2246 85 Mb SMD interface. New £199.00
 - 8" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00
 - 8" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (C1)

IC's - TRANSISTORS - DIODES

OBSELETE - SHORT SUPPLY - BULK
10,000,000 Items EX STOCK

For MAJOR SAVINGS
CALL OR SEE OUR WEB SITE www.distel.co.uk

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPP specification. Fully guaranteed, in EXCELLENT little

used condition.
Tilt & Swivel Base £4.75
VGA cable for IBM PC included.

Only £119 (E) MITS-SVGA

External cables for other types of computers available - CALL

Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc.
Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors.
Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x D15 1/2" D.
Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 1 3/4". D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive test style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call or see our web site.

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245
- FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
- FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
- 1KW to 400 kW - 400 Hz 3 phase power sources - ex stock £760
- IBM 8230 Type 1, Token ring base unit driver £2500
- Wayne Kerr RA200 Audio frequency response analyser £750
- IBM 53F501 Token Ring ICS 20 port lobe modules £95
- IBM MAU Token ring distribution panel 8228-23-5050N £550
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IECE £250
- ALLGON 8360, 11805-1880 MHz hybrid power combiners £6500
- Trend DSA 274 Data Analyser with G703(2M) 64 vO £1550
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £4995
- Marconi 2022C 10KHz-1GHz RF signal generator £3750
- Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New HP1650B Logic Analyser £1800
- HP3781A Pattern generator & HP3782A Error Detector £675
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £675
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £7900
- HP54121A DC to 22 GHz four channel test set £550
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £750
- HP A1, A0 8 pen HPGL high speed drum plotters - from HP DRAFTMASTER 1 8 pen high speed plotter £1800
- EG+G Brookdeal 95035C Precision lock in amp £995
- Vony Eng. Mod 1200 computerised inspection system £995
- Siew DXC-3000A High quality CCD colour TV camera £3750
- Kelthley 590 CV capacitor / voltage analyser £9500
- Racal ICR40 dual 40 channel voice recorder system £2100
- Fiskers 45KVA 3 ph On Line UPS - New batteries £2200
- Emerson AP130 2.5KVA industrial spec UPS £945
- Mann Tally M7465 High speed line printer £2950
- Intel SBC 486/133ES Multibus 486 system, 8Mb Ram £2950
- Siemens K4400 64Kb to 140Mb demux analyser

- HP6030A 0-200V DC @ 17 Amps bench power supply £1150
- Intel SBC 486/125C08 Enhanced Multibus (MSA) New £1450
- Nikon HF-X11 (Ephiphot) exposure control unit £1250
- PHILIPS PM5518 pro. TV signal generator £550
- Motorola VME Bus Boards & Components List. SAE / CALL £1250
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £1950
- Fujitsu M3041R 600 LPM high speed band printer £1250
- Fujitsu M3041D 600 LPM printer with network interface £500
- Perkin Elmer 299B Infrared spectrophotometer £3500
- Perkin Elmer 597 Infrared spectrophotometer £3250
- VG Electronics 1035 TELETEXT Decoding Margin Meter £495
- LightBand 60 output high spec 2u rack mount Video VDA's £1995
- Sekonic SD 150H 18 channel digital Hybrid chart recorder £300
- B&K 2633 Microphone pre amp £750
- Taylor Hobson Tallysur amplifier / recorder £1450
- ADC SS200 Carbon dioxide gas detector / monitor £75
- BBC AM20/3 PPM Meter (Ernest Turner) & drive electronics £5650
- ANRITSU 9654A Optical DC-2.5Gb/w waveform monitor £990
- ANRITSU MS9001B1 0.6-1.7 uM optical spectrum analyser £650
- ANRITSU ML93A optical power meter £650
- ANRITSU Fibre optic characteristic test set £775
- R&S FTDZ-Dual sound unit £5750
- WILTRON 6630B 12.4 / 20GHz RF sweep generator £1250
- TEK 2445 150 MHz 4 trace oscilloscope £1955
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £2900
- TEK TDS380A 400MHz digital realtime + disk drive, FFT etc £5100
- TEK TDS524A 500MHz digital realtime + colour display etc £3950
- HP3585A Opt 907 20Hz to 40 Mhz spectrum analyser £325
- PHILIPS PW1730V10 60KV XRAY generator & accessories £2900
- CLAUDE LYONS 12A 240V single phase auto. volt. regs £2900
- CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we

have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays.

Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels. £345.00 (G)
OPT Rack 2 Rack. Less side panels. £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)



Sold at LESS than a third of makers price !!

A superb buy at only £245.00 (G)

42U version of the above only £345 - CALL

12V BATTERY SCOOP - 60% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12V DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each
Our Price £35 each (C) or 4 for £99 (E)

RELAYS - 200,000 FROM STOCK

Save ££££ by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Relay, Relay, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££

COLOUR CCD CAMERAS

BIG £ SAVER

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available.

Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc. etc.

Web ref = LK33 ONLY £99.00 or 2 for £180.00 (B)

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95
Windows for Workgroups 3.11a - Dos 6.22 on 3 1/2" disks £55.00
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
shipping charges for software is code B

DISTEL on the web !! - Over 16,000,000 Items from stock - www.distel.co.uk



ALL MAIL TO
Dept ww, 29/35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5:30

LONDON SHOP
Open Mon - Sat 9:00 - 5:30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Selhurst Park RR Rail Stations

NEW DISTEL ©
Visit our web site
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (B)=£4.00, (C)=£5.00, (D)=£6.00, (E)=£7.00, (F)=£8.00, (G)=£9.00, (H)=£10.00, (I)=£11.00, (J)=£12.00, (K)=£13.00, (L)=£14.00, (M)=£15.00, (N)=£16.00, (O)=£17.00, (P)=£18.00, (Q)=£19.00, (R)=£20.00, (S)=£21.00, (T)=£22.00, (U)=£23.00, (V)=£24.00, (W)=£25.00, (X)=£26.00, (Y)=£27.00, (Z)=£28.00. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged © Display Electronics 1999. E & O 07/99.

CIRCLE NO. 122 ON REPLY CARD

NEW PRODUCTS

Please quote **Electronics World** when seeking further information

I/O transition 80mm PCBs can be fitted from the rear of the enclosure. The integration of boards corresponds to IEEE1101.10 and IEEE1101.11. Front panel mounted LEDs indicate status. The subrack has a height of 10U and a depth of 460mm. Extensions include adding a 1U disk drive tray for HD, FD and CD-ROM. This is fitted to the base of the system by removing the bottom cover.

Schroff
Tel: 01442 240471
www.schroff.co.uk

0.16µm NAND flash offers up to 1Gbit in TSOP package

As well as being available as discrete components. Toshiba's single-chip 512Mbit and 1Gbit



NAND flash memory ICs can provide the storage for 64 and 128Mbyte Smartmedia cards. Based on a 0.16µm process, the 512Mbit chip was developed with Sandisk. The 1Gbit device has two 512Mbit ICs stacked on top of each other. Both can be supplied in 48-pin TSOPs. Smartmedia card applications include PDAs, portable audio players and digital cameras.

They operate from a 3.3V (±0.3V) supply and have a programming time of 200µs per page. Access times are 50ns serial and erasing time is 2ms per block. The packages measure 12.0 by 20.0 by 1.2mm.
Toshiba Electronics
Tel: 00 49 211 52960
www.toshiba-europe.com



Power amplifier handles 300A inrush

The Harmonics 1000 power amplifier from EMC Partner complies with EN61000-3-2, amendment 14 and EN61000-3-3. It can handle inrush currents above 300A and comes with Windows Harcs software. Simultaneous and real time input and output voltage

BOOK TO BUY

Servicing Audio and Hi-Fi Equipment

Return to Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:
Servicing Audio and Hi-fi Equipment

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Mastercard/Visa/Cheque/PO

Cheques should be made payable to Reed Business Information

Credit card no. _____

Card expiry date _____

Signed _____

'Its readers will benefit from its wealth of easily assimilated information, and repairs hitherto thought impossible will speedily become routine. And the first may well cover its purchase price. Congratulations on a comprehensive, well-written and lucid work' *Electronics Informer*.

'Interesting, entertaining and useful for both practitioners and teachers. All round a satisfying book which deserves to be considered as a tool rather than an ornament collecting dust on the shelf.' *Skillset Newsletter*


Service engineers and technicians have come to regard this book as essential to their work. As a bench-side companion and guide it has no equal. Its purpose is to ease and speed up the processes of fault diagnosis, repair and testing of all classes of home audio equipment: receivers, amplifiers, recorders and playback machines. The mechanics and electronics of domestic audio are examined by Nick Beer in a down-to-earth and practical way, concentrating on what goes wrong, how to track down problems, and how to solve them.

A symptom index and comprehensive manufacturer and supplier guide allow quick access to specific advice and suggestions.

The third edition is bang up to date with the latest technology - DVD, CD Recordable, PC audio systems. There is also new material on PA equipment.

UK Price: £32.00 Europe £34.00 ROW £64.50

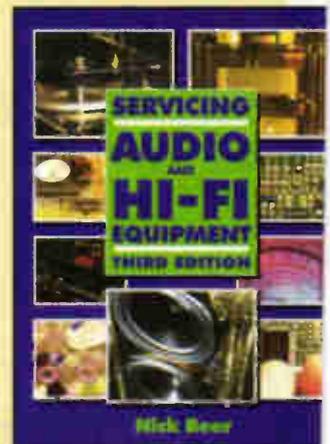****Price includes delivery and packing****



* Essential bench companion for all service engineers.

* New technology such as DVD and expanded material on MiniDisk will ensure another successful launch to this new edition

Now
Supports the
MC68HC11
and
PIC16F877

PROTEUS

VSM

Virtual System Modelling


Build It In Cyberspace

www.labcenter.co.uk

CIRCLE NO. 123 ON REPLY CARD

Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time. *

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.

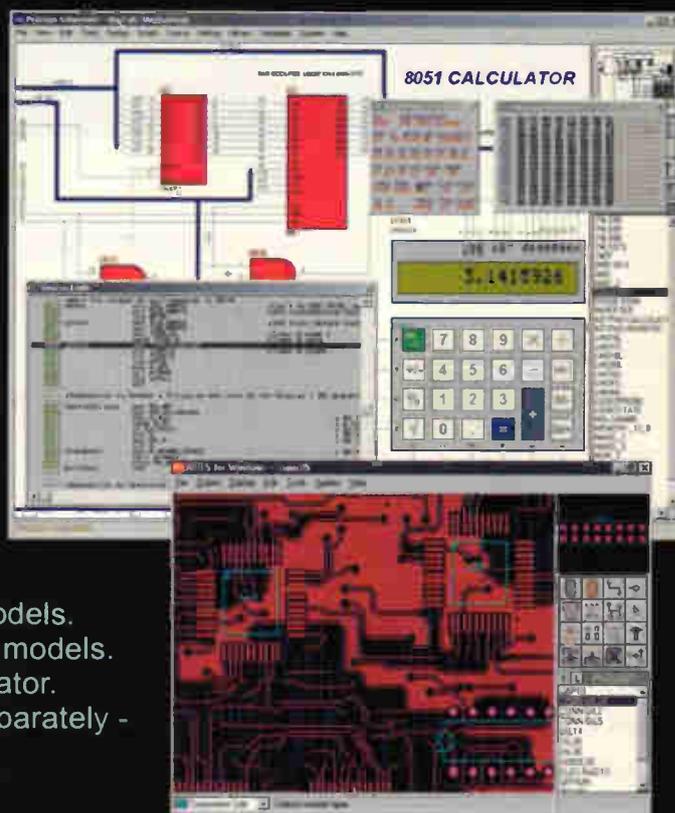

labcenter
Electronics

*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II.

Write, phone or fax for your free demo CD - or email info@labcenter.co.uk.
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

BOOK TO BUY


Valve Radio and Audio Repair Handbook

* A practical manual for collectors, owners, dealers and service engineers * Essential information for all radio and audio enthusiasts * Valve technology is a hot topic

This book is not only an essential read for every professional working with antique radio and gramophone equipment, but also dealers, collectors and valve technology enthusiasts the world over. The emphasis is firmly on the practicalities of repairing and restoring, so technical content is kept to a minimum, and always explained in a way that can be followed by readers with no background in electronics. Those who have a good grounding in electronics, but wish to learn more about the practical aspects, will benefit from the emphasis given to hands-on repair work, covering mechanical as well as electrical aspects of servicing. Repair techniques are also illustrated throughout.

This book is an expanded and updated version of Chas Miller's classic Practical Handbook of Valve Radio Repair. Full coverage of valve amplifiers will add to its appeal to all audio enthusiasts who appreciate the sound quality of valve equipment.

Contents: INCLUDES: Electricity and magnetism; Voltage, current, resistance and Ohm's Law; Real life resistors; Condensers; Tuning; Valves; Principles of transmission and reception; Practical receiver design; Mains valves and power supplies; Special features of superhets; Battery and mains battery portable receivers; Automobile receivers; Frequency modulation; Tools for servicing radio receivers; Safety precautions; Fault finding; Repairing power supply stages; Finding faults on output stages; Faults on detector/AVC/AF amplifier stages; Finding faults on IF amplifiers; Faults on frequency-changer circuits; Repairing American 'midget' receivers; Repairing faults on automobile radios; Repairing battery operated receivers; Repairing FM and AM/FM receivers; Public address and high fidelity amplifiers.

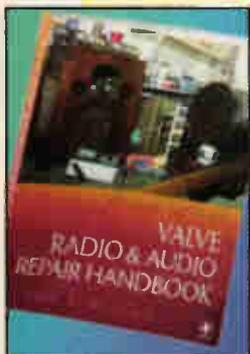

UK Price: £22.50 Europe £25.00 ROW £27.00

** Price includes delivery and packing **

Return to Jackie Lowe, Room L333, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS

Please supply the following title:

Valve Radio and Audio Repair Handbook

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Mastercard/Visa/Cheque/PO

**Cheques should be made payable to
Reed Business Information**

Credit card no _____

Card expiry date _____

Signed _____

NEW PRODUCTS

Please quote *Electronics World*
when seeking further information

and current analysis can be measured visually via an external PC letting diagnostics be interpreted in relation to the operating conditions. The integrated amplifier can handle 16A per phase 230 or 115V 50 to 60Hz. It measures 48 by 10cm and weighs 24kg.

EMC Partner

Tel: 01494 444255

www.emcpartner.co.uk

Protocol analyser for Tetra radio tests

IFR Systems has added the Tetralog protocol analyser to its 2968 Tetra radio test set. The PC-based application enables capture and detailed analysis of mobile protocol transactions.

As well as Tetra radios, it can also be used as a verification and evaluation tool for Tetra mobile developers who are not developing software in-house, but purchase protocol stacks from third parties. The application acquires data, analysing and displaying it graphically in the form of message sequence charts. The acquired messages are decoded to produce text files of the information elements contained in the messages for display, storage or printing. It can help evaluate and verify operation of a given radio type to be used on a system. Data capture is performed by connecting the mobile to the test set via its RF connection.

IFR Systems

Tel: 01438 772087

www.ifrsys.com

Serial cards download software to mobiles

QM Systems has announced multi-port PCI and PXI serial cards for downloading software to mobile phones. Using the

card, a PC can program and control over 16 phones at once at up to 12.5Mbaud per phone. Programmable output levels and optional TTL or open drain outputs provide the flexibility to control and program different phone types. Available in four, eight, 12 and 16 port versions, each port provides output levels programmable between 0.5 and 10V. The unit incorporates RS232, RS485 and RS422 and the option of adding digital I/O for interfacing to input signal lines and output indicators and actuators.

QM Systems

Tel: 01252 336612

www.qmsystems.com

Smartcard reader software goes public

Applied Card Technologies has developed software for an intelligent dual-sided smartcard reader with Taiko Electronics and Oki. The technology will work with most public access devices such as vending machines, printers, PCs, photocopiers and set-top boxes. It will let large organisations, libraries and universities offer a cashless service. The reader is also suitable for secure entry systems and employee verification across multiple locations. The software lets the chipset interact with mainstream smartcards. The reader hardware includes a dual-sided smartcard connector, which lets a card be read either way up. A separate satellite reader connects to the main PCB containing the ACT coded Oki chip and extra peripheral ports, so operators can replace just the satellite reader unit in the event of vandalism or breakage.

Applied Card Technologies

Tel: 01249 751037

www.card.co.uk





Self on Audio

DOUGLAS SELF

Self on Audio

Douglas Self

The cream of 20 years of Electronics World articles (focusing on recent material)

A unique collection of design insights and projects - essential for all audio designers, amateur and professional alike.

Scientific electronics based on empirical data

Douglas Self has been writing for Electronics World and Wireless World over the past 20 years, offering cutting-edge insights into scientific methods of electronics design.

This book is a collection of the essential Electronics World articles, covering twenty years of amplifier technology but with a very strong bias towards more recent material. The articles include self-built projects as well as design ideas and guidance for the professional audio designer. The result is a unique collection of design insights and projects - essential for all audio designers, whether amateur or professional.

Contents: Introduction; PRE-AMPLIFIERS: An advanced preamplifier MRPI; High-performance preamp MRP4; Precision preamp MRP10; Moving-coil head amp; Preamp '96 I; Preamp '96 II; "Overload Matters" (RIAA overload); Balanced line inputs and outputs, part 1; Balanced line inputs and outputs, part 2; POWER AMPLIFIERS: FETs less linear than BJTs; Distortion in power amplifiers 1-8; Distortion residuals; Trimodal part 1, 2; Load-invariant power amp INVAR.DOC; Common-emitter amps; Two-stage amplifiers; SPEAKERS: Excess speaker currents; Class distinction (amp classification); Relay control; Power partition diagrams; Audio power analysis.

Douglas Self has dedicated himself to demystifying amplifier design and establishing empirical design techniques based on electronic design principles and experimental data. His rigorous and thoroughly practical approach has established him as a leading authority on amplifier design.

Readership: Audio electronics enthusiasts;
Professional amplifier designers;
Power amp users
Paperback
Pages: 416pp

UK Price: £26.50 Europe £27.50 ROW £28.50

**Return to Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS**

Please supply the following title:

SELF AUDIO

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (*please circle*)

Mastercard/Visa/Cheque/PO

**Cheques should be made payable to
Reed Business Information**

Credit card no. _____

Card expiry date _____

Signed _____

Current-conveyors III

In this third and final article on low-voltage current conveyors and their applications, Giuseppe Ferri *et al* describe how easy it is to implement capacitance multipliers using conveyors, and how such multipliers can benefit filter designs.

In the following, we describe how capacitance can be multiplied using current conveyors.¹⁻⁷ Figure 1 outlines such a multiplier. It comprises a current conveyor followed by a current amplifier A_I .

Ideal input equivalent capacitance is,

$$C_{EQ} = A_I C_S \quad (1)$$

This shows that an equivalent capacitance is obtained that is A_I times greater than C_S . Deviations from this ideal behaviour are mainly due to:

- Voltage and current-transfer inaccuracies in the conveyor and the conveyor's finite output resistance at terminal X.
- Bandwidth limitation of the current amplifier and its finite output resistance.

Equivalent input impedance is,

$$Z_{EQ} = \frac{V_{in}}{I_{in}} = \left[\frac{1}{\alpha\beta A_I} \left(r_X \frac{1}{sC_S} \right) \right] // r_o \quad (2)$$

Here, r_X is resistance at X and r_o is resistance at the amplifier output. Voltage and current transfer errors of the

CCII- are,

$$\frac{V_X}{V_Y} = \alpha$$

and,

$$\frac{I_Y}{I_X} = \beta$$

respectively. Figure 2 is the equivalent circuit.

Equation 2 shows that the impedance Z_{EQ} is the parallel of two terms. The first term is due to capacitance C_S . This is multiplied by a factor equal to $\alpha\beta A_I$ and a series resistance equal to,

$$\frac{1}{\alpha\beta A_I}$$

times the output resistance at X terminal. Therefore, this contribution decreases for high values of the current gain A_I .

The second term is due to the output resistance of the current amplifier. This contribution can be dominant at low frequencies.

It turns out that, in order to have an ideal capacitance, as multiplied by A_I , r_X must be low and r_o high. This last condition is more important because r_X is divided by the gain A_I .⁸⁻¹⁰

Now we will describe some configurations implementing both the CCII and the current amplifier.

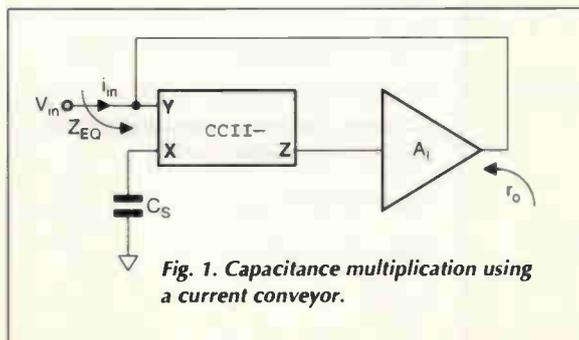


Fig. 1. Capacitance multiplication using a current conveyor.

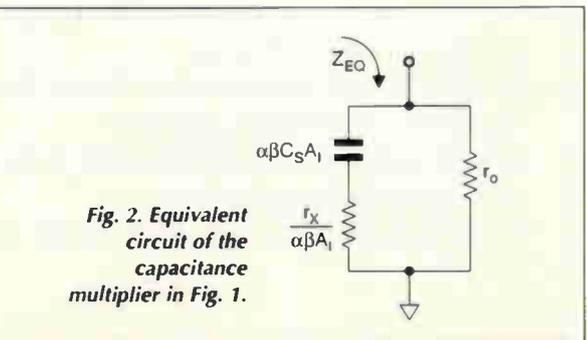


Fig. 2. Equivalent circuit of the capacitance multiplier in Fig. 1.

Conveyor and current-amp solution

Figure 3 shows a capacitance multiplier made up using a second-generation 'inverting' current conveyor, commonly called a CCII-, and a current-based operational amplifier, or COA. Figure 4 is a simplified schematic of the COA used in simulations, while Table 1 outlines its performance.

Capacitance C_s is the grounded capacitance that has to be multiplied. Resistances R_1 and R_2 accurately set the closed-loop current gain of the amplifier as given by,

$$A_f = \frac{I_z}{I_x} = 1 + \frac{R_2}{R_1} \tag{3}$$

With this solution, high capacitance gain factors can be readily achieved by simply setting the resistance ratio $R_2:R_1$.

In addition, the gain factor can be further increased by exploiting the current-gain capabilities of the CCII. For example, if you choose a COA current gain, A_f , of 10^2 and set the current gain of the CCII, β , to 10, an overall multiplication factor of 10^3 is achieved with a limited increase in power dissipation.

Usually, the current gain of a CCII is determined either by controlling the aspect ratio of the output current mirror, or by using techniques that allow electronic control of the current gain. With these solutions, the quiescent current is proportional to the multiplication factor. This means that there's a trade-off between power dissipation and gain.

Standby current at the conveyor's Z terminal limits the amount of capacitance gain that can be obtained. This current, associated with R_2 , produces an offset voltage that can saturate the op-amp's output. For this reason, the CCII needs an accurate offset control.¹¹⁻¹⁸

C multiplier using two conveyors

In order to obtain high and controlled capacitance gain factors, the second topology shown in Fig. 5 has been developed. It is made up of two CCII's and two resistors. These resistors determine the multiplication factor.

For ideal CCII's, the following expression gives the input equivalent capacitance:

$$C_{EQ} = \frac{R_2}{R_1} C_s \tag{4}$$

This equation shows that an equivalent capacitance $R_2 \div R_1$ times greater than C_s can be obtained.

For real CCII's, the following expression for the input equivalent voltage can be deduced:

$$Z_{EQ} = \frac{V_Y}{I_Y} = \left[\frac{1}{\gamma} \frac{R_1 + r_{X1}}{R_2 // r_{Z1}} \left(r_{X2} + \frac{1}{sC_s} \right) \right] // r_{Z2} \tag{5}$$

Here, γ is $\alpha_1 \beta_1 \alpha_2 \beta_2$ and α_i and β_i are the voltage and current gains for the i th CCII, respectively. All gains are nominally equally to 1.

This solution allows high gain factors. However, some limits on the values of R_1 and R_2 have to be considered.

The lower limit of R_1 is related to the output resistance at X_1 terminal, while the upper limit for R_2 is related to the output resistance at Z_1 terminal.

Multiplier using a single conveyor


This final multiplier is simple because it does not make use of a current amplifier. It uses only a current conveyor with a β current gain of greater than 1, as in Fig. 6.

In this case, taking into account the finite output resistance at X and Z terminals, r_x and r_z , and the voltage transfer gain, $V_X/V_Y = \alpha$, you can evaluate the equivalent input impedance as follows:

$$Z_{EQ} = \frac{V_Y}{I_{IN}} = \left(\frac{r_x}{\alpha\beta} + \frac{1}{s\alpha\beta C_s} \right) // r_z \tag{7}$$

where the parasitic capacitances at terminals Y and Z of the CCII have been neglected.

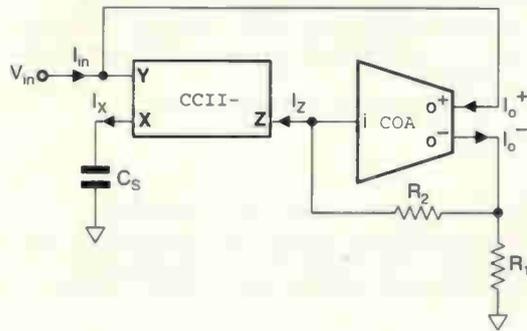Equation 7 shows that impedance Z_{EQ} is the parallel of two terms. The first term is due to the capacitance C_s , which is multiplied by a factor equal to $\alpha\beta$, with a series



Parameter	Value
Loop gain	62dB
GBW	100MHz
PM	64°

Fig. 3. Capacitance multiplier using a current conveyor followed by a current-based op-amp.

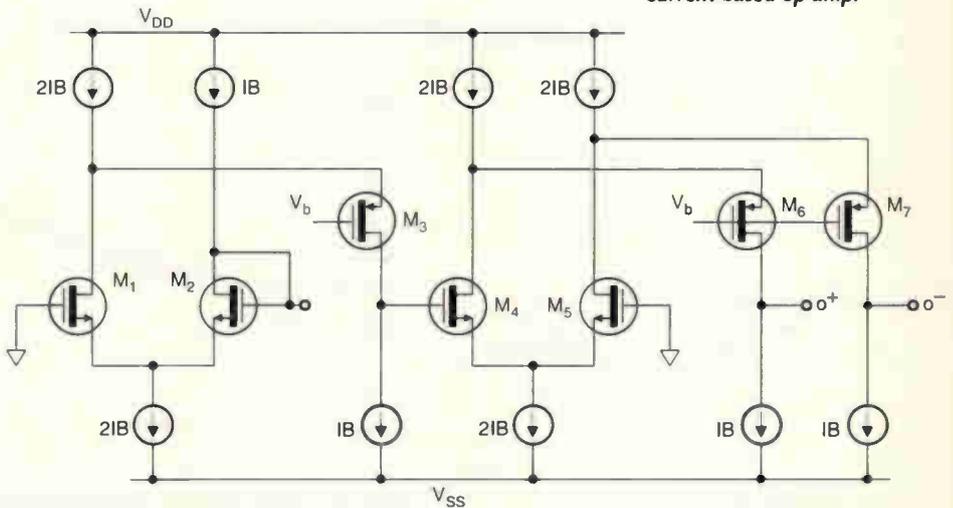


Fig. 4. Simplified schematic of the low-voltage COA used to simulate the performance of the circuit in Fig. 3.

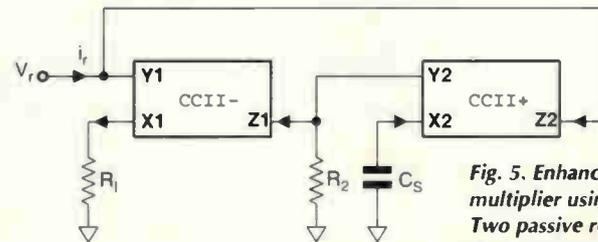


Fig. 5. Enhanced capacitance multiplier using two conveyors. Two passive resistances determine the capacitance gain.

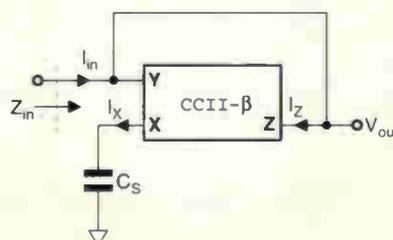


Fig. 6. The third multiplier topology uses a single current conveyor.

resistance equal to $1/\alpha\beta$ times the output resistance at X terminal. This term is predominant at high frequencies and decreases for high values of the current gain β .

The second term is due to the resistance at the Z terminal. This term is important at low frequencies. Its contribution can be made negligible by choosing CCII implementations with high values of r_z .

Non ideal situations due to X and Z node resistances limit the circuit's capacitance multiplication range, as shown in Fig. 7.

Using CCII's for low cut-off filters

Here we present a low-pass filter design based on a capacitance multiplier using current conveyors. This is a first-order low-pass filter with a low cut-off frequency, of below 10Hz, Fig. 8.¹⁹⁻²²

This filter uses a CCII- with current gain,

$$\frac{i_z}{i_x} = \beta > 1$$

In Fig. 8, C_s is the capacitance to be multiplied. Resistance R is set to 160k Ω in order to achieve a cut-off frequency of 1Hz. Figure 9 shows the magnitude response of the filter. The cut-off frequency is 0.96Hz,

which is in good agreement with what you would expect.

The DC gain of the active filter is -1.1dB instead of 0dB. This is due to the partition effect caused by the finite value of r_z .

In summary

Current conveyors are versatile building blocks suitable for many applications.

Many complex analogue functions are easily implemented using current-conveyors. The current conveyor can give better performance than traditional operational amplifiers. This is particularly so in terms of speed and bandwidth, due to the local feedback of the follower-based structure of the device.

Commercial current conveyors are easily realised in CMOS technology, and at low cost. In the first two articles of this review, we proposed some novel low supply voltage current conveyors for use in portable instrumentation application. In this final article, we have also shown how capacitance multipliers are easy to implement using current conveyors. Such multipliers make it possible to produce fully integrated filters that can work at very low frequencies. ■

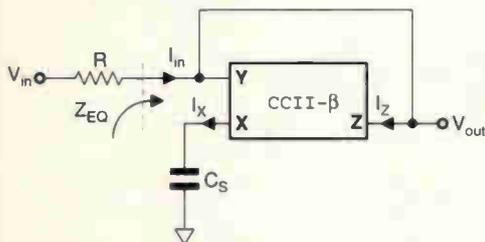


Fig. 8. Schematic of a low cut-off frequency low-pass filter implemented using current-conveyor technology.


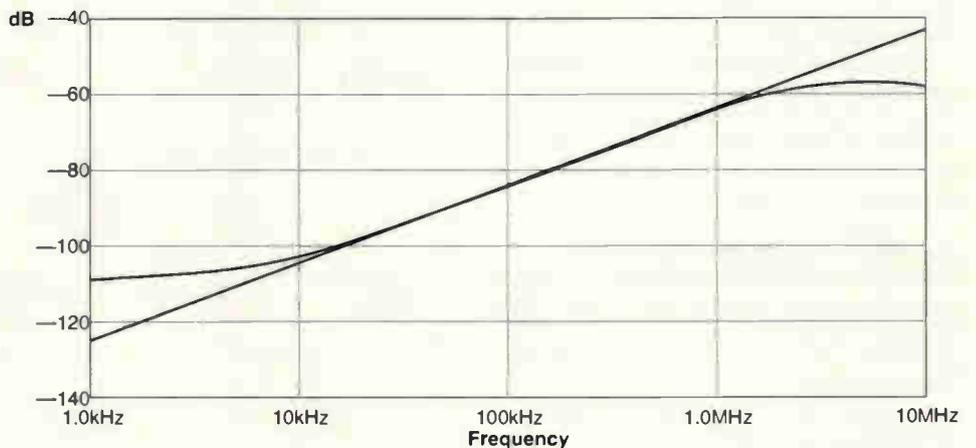


Fig. 7. Input admittance of the circuit of Fig. 6 for $C_s=1pF$ and a capacitive gain of 10^2 .

Fig. 9. Magnitude responses for an ideal RC filter and the one proposed in Fig. 8.

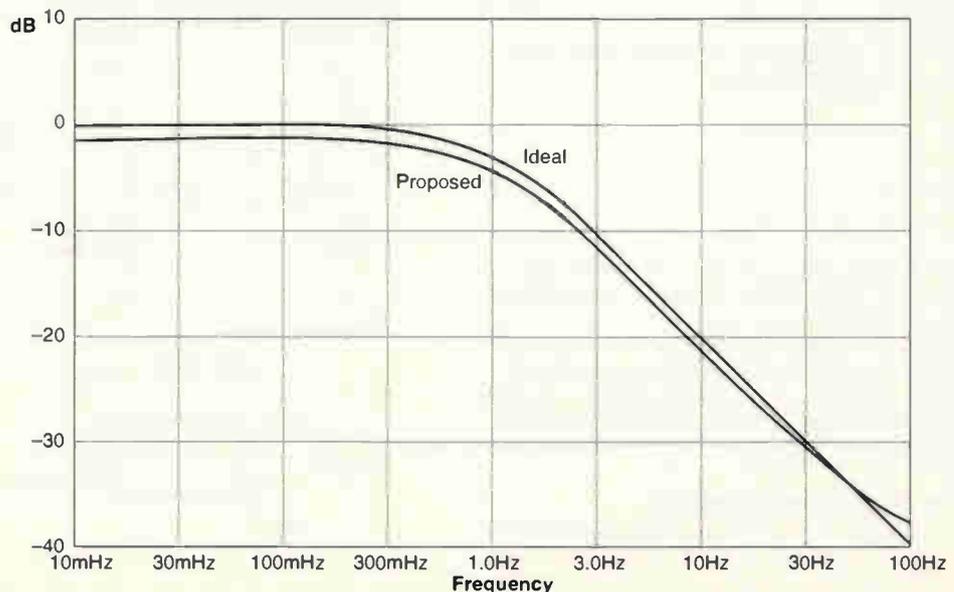

References

1. C.Kim, K.D.Wise, 'Low-voltage electronics for the stimulation of biological neural networks using fully complementary BiCMOS circuits', *IEEE Journal of Solid-State Circuits*, Vol. 32, No 10, Oct. 1997, pp. 238-236.
2. G.Weil, W.Engl, A.Renz, 'Integrated pacemakers', *IEEE Journal of Solid-State Circuits*, Vol. SC-5, pp. 67-73. 1970.
3. W.Sansen, 'On the integration of an internal human conditioning system', *IEEE Transactions on Journal of Solid-State Circuits*, Vol. SC-17, pp. 472-479, 1982.
4. G.Ferri, 'An Operational Transconductance Amplifier for Capacitive Sensor Applications', Sensors and Microsystems - Proc. Second Italian Conference of Sensors and Microsystems, Roma, Feb. 1997.
5. T.Smith, J.Bardyn, B.DeGeeter, O.Nys, 'Low power capacitive sensor interfaces', Proc. AACD 1997, Baveno, 1-3 April 1997.
6. P.Wouters, M.De Cooman, R.Puers, 'A multipurpose CMOS sensor interface for low power applications', *IEEE Journal of Solid State Circuits*, Vol. SC-29 No 8, Aug.1994, pp. 952-956.
7. A.D'Amico, C.Di Natale, M.Mariucci, G.Baccarani, M.Faccio, G.Ferri, F.Maloberti, P.Malcovati, G.Stochino, 'Active capacitance multiplication for sensor application' - Sensors and Microsystems - Proc. Second Italian Conference of Sensors and Microsystems, Roma, Feb. 1997.
8. E.Vittoz, 'Limits to LV/LP analog circuit design', Advance Course on LV LP Analog CMOS IC design - Lausanne, June 1998.
9. Y.Sun, J.K.Fidler, 'Analysis of current-conveyor error effects in signal processing circuits', *International Journal of Circuit Theory and Applications*, Vol. 24 No 4, pp. 479-488, July-Aug. 1996
10. N.Tarim, B.Yenen, H.Kuntman, 'Simple and accurate non-linear current conveyor macromodel suitable for simulation of active filters using CCII's', *International Journal of Circuit Theory and Applications*, Vol. 26 No 1, pp. 27-38, Jan-Feb. 1998.
11. O.Toshio : 'Switched-capacitor impedance simulation circuits realized with current conveyors', 'ISCAS'98, Monterey, May 1998.
12. G.Di Cataldo, G.Ferri, S.Pennisi, 'Active capacitance multiplication by current conveyors' - ISCAS'98, Monterey.
13. G.Ferri, S.Pennisi, 'A 1.5 V current-mode capacitance multiplier' - IEEE Proc. ICM98 Conference, Monastir, Tunisia, 1998.
14. T. Kaulberg, 'A CMOS Current-Mode Operational Amplifier', *IEEE Jour. of Solid-State Circ.*, Vol.28, No. 7, pp. 849-852, July 1993.
15. G. Palmisano, G. Palumbo, S. Pennisi, 'High-Drive CMOS Current Amplifier', *IEEE Jour. of Solid-State Circ.*, Vol. 33 No 2, pp. 238-236.
16. E. Bruun, 'A High-Speed CMOS Current Opamp for Very Low Supply Voltage Operation,' IEEE Proc. Iscas '94, London, 1994.
17. P. J. Crawley, G. W. Roberts, 'High-Swing MOS Current Mirror with Arbitrarily High Output Resistance,' *Electronics Letters*, Vol. 28 No. 4, pp. 362-363, Feb. 1992.
18. Y.Sun, J.K.Fielder, 'Current-mode multiple-loop feedback filters using dual output OTAs and grounded capacitors', *International Journal of Circuit Theory and Applications*, Vol. 25 No 2, pp. 69-80, March-April 1997.
19. P. Kinget, M. Steyaert, J. Van Der Spiegel, 'Full Analog CMOS Integration of Very Large Time Constants for Synaptic Transfer in Neural Networks', *Analog Integrated Circuits and Signal Proc.*, Vol. 2, pp. 281-295, 1992.
20. WHG, Deguelle, 'Limitations on the Integration of Analog Filters for Frequencies Below 10Hz', IEEE Proc. ESSCIRC 1988, pp. 131-134.
21. S. Solis-Bustos, J. Silva-Martinez, 'A 4Hz Low-Pass Continuous-Time Filter,' IEEE Proc. ICECS'98, Lisbon, Sept. 1998, pp. 169-172.
22. G.Ferri, S.Pennisi, S.Sperandii, 'A low voltage CMOS 1-Hz low pass filter' - IEEE Proc. ICECS 99 Conference, Cipro, 1999.



TV Fault Finding Guide

Peter Marlow

Contents: Introduction; A-Z of manufacturers and models
Readership: Professional service engineers, some college courses.

Pages: 400pp

Price: £22.50

Unique expert authorship and trusted Television magazine identity Real repair and troubleshooting info - not just cribs from manufacturers' data sheets. Ease of reference - this book is an essential repair tool, not just another volume for the shelf, Television magazine's TV Fault Finding column is a unique forum for practical servicing tips, with the UK's leading service engineers and servicing writers contributing their observations and recommendations month by month. But try finding those faults reports for the Amstrad CTV2200 that's on your bench. Even with an index you will be chasing through a pile of magazines... until now. Peter Marlow's TV Fault Finding Guide is a distillation of the most used fault reports from 11 years of Television magazine. Arranged by make and model the information is extremely easy to access, and the book is a convenient size for the bench or to carry with you. This will undoubtedly become one of the service engineer's most useful tools. Unlike other fault guides, this one is based on top quality information from leading authorities, and genuine repair case studies. This is real-life servicing information, not just a compilation of manufacturers' manuals.

Over 2,000 reports covering over 300 models Instant on-the-spot diagnosis and repair advice Television magazine's leading writers' wit and wisdom available for the first time in book form.
To Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

How to pay

(TV Fault Finding Guide) paperback

I enclose a cheque/bank draft for £ _____
 (payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.

Send your ideas to: Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Battery pack short-circuit protector

This circuit provides short circuit protection to a removable battery pack of up to 11V. It could be fitted in the battery pack as stand-alone protection. Or it could be included as part of the electronics if gas gauging or SMBus charging control circuit is embedded.

The circuit can be used with a working battery terminal voltage range between 2.5V and 11V. It is suitable for NiCd or NiMh batteries from 3 cells (where the lowest working limit of 0.9V per cell gives 2.7V) to 6 or 7 cells, depending on the worst case fast charge terminal voltage. It is also suitable for one or two Lithium Ion cells.

As drawn, the circuit trips at 2.7A current, but this limit can be easily

changed by adjusting the value of R_{sense} . Quiescent current consumption on a 3.6V battery is 5pA maximum for the MAX835EUK, plus 0.4µA to 2.8µA – roughly proportional to current load – for current sensor Q_1 .


The core element is the tiny 5-pin SOT-23 MAX835EUK latching voltage monitor. It has a rail-to-rail output at pin 5, which is normally high, turning on the N-channel MOSFET Q_2 and so allowing load current to pass from the battery to the external load.

Transistor Q_2 is a Temic TSSOP packaged transistor, chosen because it has a maximum $r_{ds(on)}$ of 40mΩ with a V_{GS} of 2.7V. When the input signal to pin 4 drops below the internal reference voltage of 1.2V, an internal latch is set

which takes the output low. This turns off Q_2 , thereby disconnecting the battery from its load. The latch can only be cleared by a pulse taking the CLR input (pin 1) above 2V for at least 1µs.

The reset pulse is provided by a push switch – typically, membrane type – which is AC coupled into the CLR input. The AC coupling prevents the user from disabling the protection by keeping the switch permanently pressed!

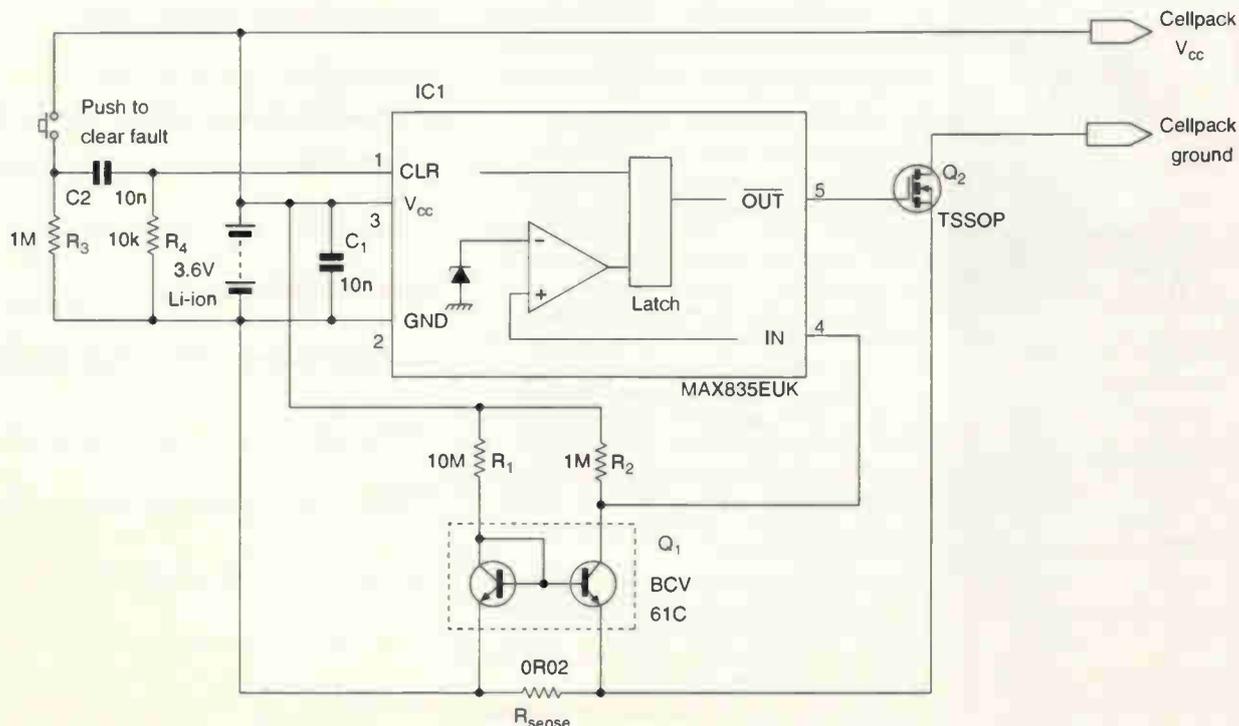The value of R_1 (10kΩ) is deliberately quite low to give high noise immunity to the switch input. Resistor R_3 (1MΩ) can be high resistance because its purpose is just to discharge C_2 after the switch is released, and noise pickup at this point



cannot reset the latch.

The intrinsic body diode of Q_2 (cathode to drain, anode to source) is used to advantage. If the battery is totally flat, then Q_2 cannot be turned on. However the pack can still be charged because the body diode allows reverse (charging) current to flow.

When the pack is charged sufficiently, the protection latch can be cleared and the battery pack used in the normal way.

Dual transistor Q_1 , a Siemens BCV61, amplifies the very small current sense voltage of 60mV up to IC's trip threshold of 1.2V. A transistor pair was selected because it is low cost and small, in a SOT-143 package. The transistors are monolithic, so thermal coupling and V_{be} matching is intrinsically good.

To understand the current sense amplifier's operation, first consider the case where no current is flowing through R_{sense} . The V_{be} voltages of the two transistors are the same in this

condition. Now Q_{1B} (diode connected) has $10M\Omega R_1$ in its collector, whereas Q_{1A} has a $1M\Omega R_2$ load.

Transistor Q_{1B} 's emitter current is lower than that of Q_{1A} by virtue of this collector load disparity, and so its working V_{be} is lower than the working V_{be} of Q_{1A} . Hence Q_{1B} is essentially turned off when no battery load current is flowing.

Now consider an increasing load current through R_{sense} . This resistor will incur an increasing voltage drop, which has the effect of taking Q_{1A} 's emitter negative with respect to Q_{1B} 's emitter. This in turn increases the V_{be} of Q_{1A} , and at some point of increasing load current through R_{sense} , Q_{1A} 's V_{be} will be large enough for the collector voltages of Q_{1A} and Q_{2A} to equate.

Voltage across R_{sense} at which this occurs is $0.026 \times \log(R_2/R_1) = 60mV$ at room temperature. The IC will actually switch when the collector of Q_{1A} drops to 1.2V, so there is a small inaccuracy in the switch point calculation – the circuit will actually

switch at a slightly lower current than calculated.

The higher the supply voltage, the smaller the error is because the difference between a V_{be} and 1.2V as a fraction of the supply voltage reduces. The table shows the latching currents for several supply voltages:

Supply voltage	Switching current
5.0V	2.88A
3.6V	2.75A
3.3V	2.69A
2.7V	2.56A

Also, the switch point varies with temperature because absolute temperature, T , is in the equation. This isn't as bad as it first appears. The working temperature range of a pack may be from as low as -20°C up to $+40^\circ\text{C}$, which is a variation of $\pm 30\text{K}$ around a mean of $+10^\circ\text{C}$ or 283K. So the variation in trip point is about $\pm 10\%$ with temperature.

Tim Herklots and Dave Watson
MAXIM Integrated Products UK Ltd
D82

Ten year index: new update

TABLE OF CONTENTS

- Applications
 - Applications by description
 - Applications by part numbers
 - Company addresses
- Books
 - Circuit Ideas
 - Information
 - Subject Index
 - Analogue Design
 - Audio
 - Avionics
 - Broadcast
 - Communications
 - Components
 - Computing
 - Consumer Electronics
 - Control Electronics
 - Digital & DSP Design
 - History

The Electronics World SoftIndex runs from January 1988 to May 1996 and contains references to 1300 articles and 800 circuit ideas. There is a separate author index with full cross references. Reprints can be obtained for all the articles in this index - see the Information section for more details. For up to date information about Electronics World see our website at <http://www.softcopy.co.uk>

Search Copy Note About Exit

www.softcopy.co.uk

Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* index
Indexes on paper for volumes 100, 101, and 102 are available at £2 each, excluding postage.

Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications - including a synopsis for each.

The EW index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format.

Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Ordering details

The EW index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders

Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide. For enquires about photocopies etc please send an s.a.e. to SoftCopy Ltd. **Send your orders to SoftCopy Ltd, 1 Vineries Close, Cheltenham GL53 0NU.**

Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

A microcontroller-based signal generator with

The circuit of Fig. 1 uses a Microchip 8-pin PIC12C671 as a voltage-controlled audio-frequency oscillator. Since the 12C671 has an internal 4MHz oscillator, 4-channel 8-bit a-to-d

converters and a built-in power-reset circuitry, no extra components are required to form the signal generator.

The PIC12C671 reads two analogue inputs through AN0 and

AN1. The conversion reference voltage is the controller's power supply V_{dd} . Voltage V_f controls the output frequency while V_d determines the duty cycle of the output signal. Frequency and duty

```

LIST    P-12C671

TMRO    equ    0X01
STATUS equ    0x03
GPIO    equ    0X05
INTCON  equ    0x0b
PIR1    equ    0x0c
ADRES   equ    0x1e
ADCON0  equ    0x1f
ADCON1  equ    0x9f
OPT      equ    0X81
port-dir equ    0x85
period  equ    0x21
cnt-I   equ    0x22
cnt - 2 equ    0x23
temp    equ    0x24

w      equ    0
F      equ    1
c      equ    0
z      equ    2

        org    0xo
        goto . main
        org    0x4
        decfsz cnt_1, F
        goto  send-out

get_range
    movlw 0x20
    movwf cnt_1
    movf  GPIO, W
    movwf temp
    rrf  temp, F
    rrf  temp, F
    rrf  temp, F
    movf temp, W
    andlw 0x07
    addlw

get-duty-cycle

        movlw 0x49 ;A/D input from AN1
        movwf 0x80 ;
        option ADCON0 ;
        call delay ;data
acquisition
    bsf  ADCON0, 2 ;start A/D
conversion
    loop_1 btfsc ADCON0,2 ;
    =goto loop_1 ;
    movf ADRES, 0 ;
    movwf period ;
    rrf  period, F ;
    rrf  period, F ;
    rrf  period, F ;
    movlw 0x1f ;
    andwf period, F ;
    incfsz period, F ;
    bcf  GPIO, 2 ;output low
get_frequency
    movlw 0x41 ;A/D input from AN0
    movwf ADCON0 ;
    call delay ;data acquisition
    bsf  ADCON0, 2 ;start A/D
conversion
    loop_2 btfsc ADCON0, 2 ;
    goto loop_2 ;
    movf ADRES, 0 ;
    movwf cnt_2 ;
    bcf  STATUS, C ;
    rrf  cnt _2, F ;
    movlw 0x7c ;
    addwf cnt _2, F ;
    movf cnt _2, W ;
    movwf TMRO ;
    Bcf  INTCON, 2 ;clear TMRO
interrupt flag
    retfie ;
    ;
send_out
    movf cnt _2, W ;

```

£75 winner

voltage-controlled frequency and duty cycle

cycle are independent: changing the frequency will not affect the duty cycle and *vice versa*.

Output frequency can be further controlled by 3-bit input A-C. These 3 bits set a pre-scaler between the

controller's clock and timer 0. When A=B=C='0', the measured frequency is from 114Hz to 1.41kHz. When A=B=C='1', output frequency range is between 0.9Hz and 11Hz. See Tables 1 and 2 below.

Yongping Xia
Torrance
California
USA
E72

```

movwf TMR0S      ;
movf  cnt_1, W   ;
subwf period, W ;
btfsc STATUS, C ;
bsf  GPIO, 2    ;output high
bcf  INTCON, 2  ;clear TMR0 interrupt

flag
retfie           ;
delay           ;

        movlw 0x03 ;
        movwf temp ;
dly_lp decfsz temp, 1 ;
        goto dly_lp ;
        return ;

main
        clrf GPIO ;
        movlw 0x01 ;
        movwf cnt_1 ;
        clrf cnt_2 ;
        decf cnt_2, F ;
        movlw 0x80 ;
        movwf period ;
        bsf STATUS, 5 ;bank I
        movlw 0x80 ;
        option ;
        movlw 0x1b ;
        movwf port_dir ;
        movlw 0x04 ;
        movwf ADCON1 ;
        bcf STATUS, 5;bank 0
        movlw 0xa0 ;
        movwf INTCON ;

loop
        goto loop ;endless loop

end

```

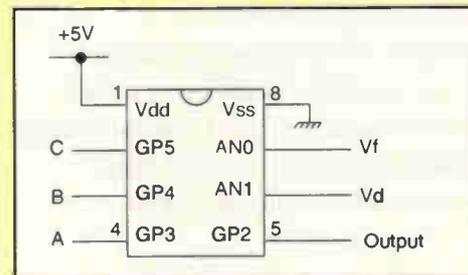


Fig. 1.

Table 1 (A=B=C=0)

Vf	Vd	0V	1V	2V	3V	4V	5V
	0V	114Hz	114Hz	114Hz	114Hz	114Hz	114Hz
0V	3.7%	22%	41%	62%	92%	96%	
	139Hz						
1V	3.8%	22%	45%	63%	81%	96%	
	179Hz						
2V	4%	23%	41%	62%	79%	96%	
	257Hz	257Hz	257Hz	256Hz	256Hz	256Hz	256Hz
3V	4%	23%	41%	62%	80%	96%	
	413Hz	413Hz	413Hz	413Hz	412Hz	412Hz	412Hz
4V	5.1%	23%	44%	63%	81%	95%	
	1.41kHz						
5V	10%	26%	42%	61%	77%	90%	

Table 2

C	B	A	Output frequency
0	0	0	f/1
0	0	1	f/2
0	1	0	f/4
0	1	1	f/8
1	0	0	f/16
1	0	1	f/32
1	1	0	f/64
1	1	1	f/128

Antennas and propagation for wireless communication systems

This will be a vital source of information on the basic concepts and specific applications of antennas and propagation to wireless systems, covering terrestrial and satellite radio systems in both mobile and fixed contexts. Antennas and propagation are the key factors influencing the robustness and quality of the wireless communication channel and this book includes:

- Illustrations of the significance and effect of the wireless propagation channel
- Overview of the fundamental electromagnetic principles underlying propagation and antennas
- Basic concepts of antennas and their application to specific wireless systems
- Propagation measurement, modelling and prediction for fixed links, macrocells, microcells, picocells and megacells

- Narrowband and wideband channel modelling and the effect of the channel on communication system performance
- Methods that overcome and transform channel impairments to enhance performance using diversity, adaptive antennas and equalisers

It will be essential reading for wireless communication engineers as well as for students at postgraduate or senior undergraduate levels.

Distinctive features of this book are:

- Examples of real world practical system problems of communication system design and operation
- Extensive worked examples
- End of chapter questions
- Topical and relevant information for and about the wireless communication industry

Post your completed order form to:-

Jackie Lowe, Room L514, Quadrant House,
The Quadrant, Sutton, Surrey, SM2 5AS

**Fax your completed order form to
020 8652 8111**

**UK Price: £42.50 Europe £45.00 ROW £47.50
Price includes delivery**

ANTENNAS AND PROPAGATION FOR WIRELESS COMMUNICATION SYSTEMS

SIMON R. SAUNDERS

How to pay

Antennas and propagation for wireless communication systems

I enclose a cheque/bank draft for £ _____
(payable to Reed Business Information)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

12V battery voltage level detector



This circuit was designed for a Peltier-effect cold box on a sailing boat but could have other applications, for example, in a caravan. Load current of the cold box is about 4A and this is a large burden when sailing, but it can easily be met from the engine's alternator when under power.

The circuit detects the rise in the 12V supply when the battery is being charged. When this is about 14.2V (set by VR1) RL1 closes and connects the load. When the supply falls (to about 12.7V) on stopping the engine, RL1 opens and the load is removed. The threshold between the two voltages prevents 'hunting' and can be changed by adjusting R7 (see graph).

The normally closed contact on RL1 connects an external 12V supply. This is for use in harbour when a mains connection is available. The external 12V supply also opens RL2 and inhibits the detector. As the mains supply also feeds a separate battery charger, without RL2 the detector will operate whenever the battery charger brings the battery voltage up to the threshold level and thus switch away from the external supply. The need for this relay was discovered in practice!

The detector should be installed as near to the battery as possible, to avoid the voltage drop in the cables to the cold box causing malfunction.

Tony Meacock
Norwich
Norfolk

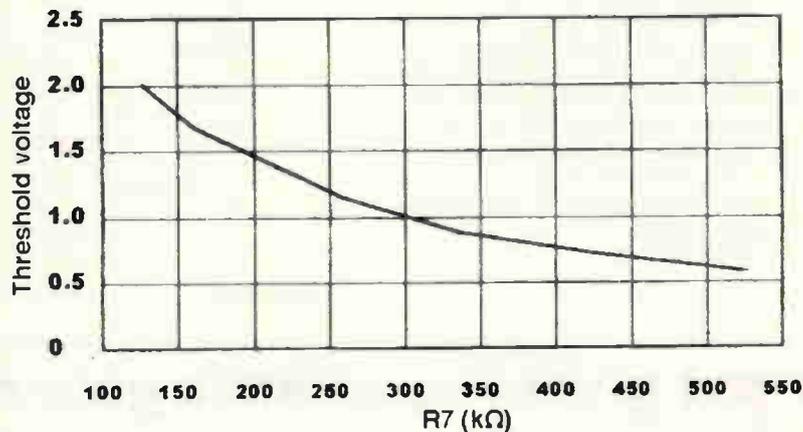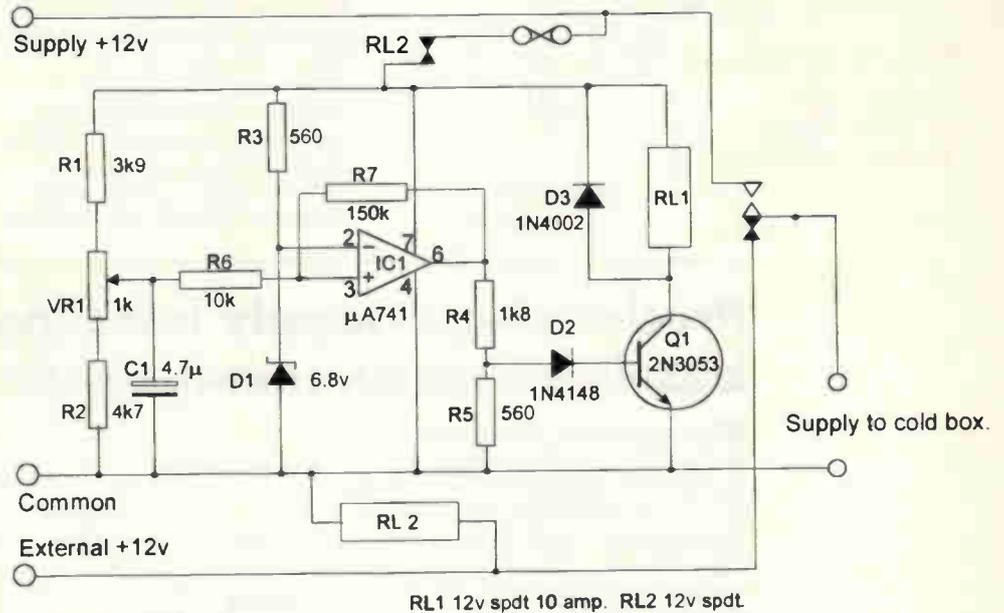

LDR-stabilised Wien-bridge oscillator


This sine wave oscillator uses feedback via an LDR to stabilise the output amplitude. The circuit arrangement of IC1 should be familiar: if $R_1=R_2=R$ and $C_1=C_2=C$ then $f=1/(2 \times \pi \times R \times C)$. With values shown, the frequency will be 1.59kHz.


Op-amp IC2 provides current to the LEDs according to output amplitude thus modifying the resistance of the LDR. Resistor R3 should be just greater than twice the value of R4. Adjust amplitude by modifying the value of R5. The circuit will work from 0Hz to 10kHz with 358 op-amps and values shown. Using rail-to-rail output amps and low voltage red LEDs, the circuit will work from a 5V supply.

The LEDs and LDR should be put in a light proof box such as a black pill bottle cap. No claims are made for a perfect sine wave but it is adequate for exciting a transducer etc.

Some LDRs have a very slow response, which helps with distortion, especially at low frequencies.

Andy Little
Penzance
Cornwall

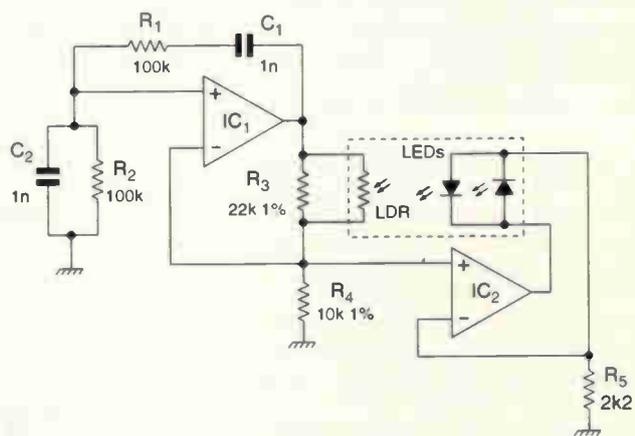

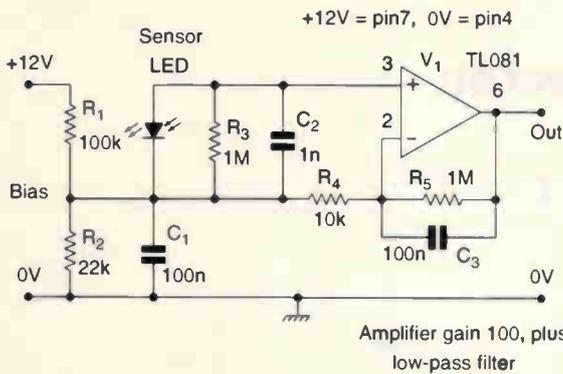

Use LED as photo-diode

Light emitting diodes are cheap and readily available. They can also act as photo-diodes, an example being in the circuit shown.

Some sixty LEDs, of various colours, were tested in the photo-voltaic mode, and all acted as photo-diodes. Testing was done using a 2.4V 0.5A lamp over-run on 3V. Yellow/orange LEDs worked best,

producing about 50mV into 1MΩ. It is reasonable to suppose that LEDs would also operate on the current-mode, which provides a wide dynamic range with response linearly related to intensity of illumination.


Colin Pye
Coventry
E67

Precise single-supply baseline clamp and baseline measurement circuit

The circuit shown, right, accurately clamps the baseline incoming waveform to within a couple of millivolts of zero volts. Subtraction of the clamped signal from the original measures the low point of the incoming waveform. Using two series analogue switches reduces baseline ripple to almost zero.

Boostrapping the switches with the output signal reduces the switches' off-state leakage and keeps the DC component stored on C_{in} from drooping between cycles. Capacitor C_{in} was chosen to allow processing of signals from 1kHz down to 0.1Hz. For higher minimum frequencies, a lower capacitance value can be chosen.

Alex Birkett
London
E68

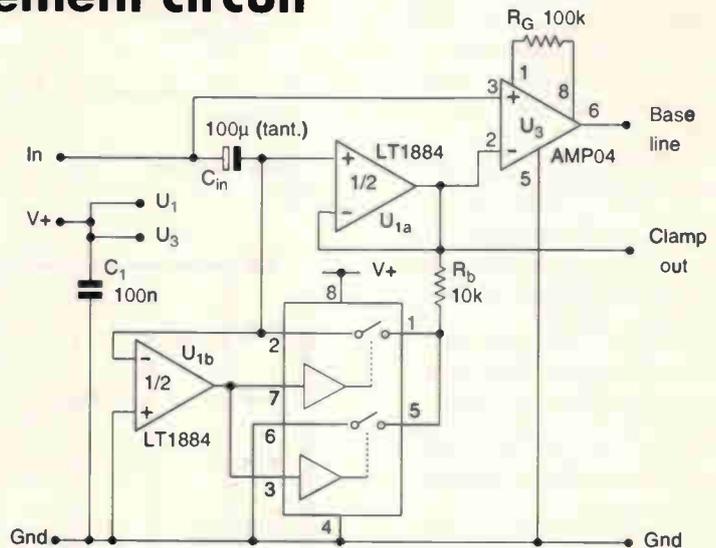

Linear pot gives logarithmic gain control

The volume control of an amplifier is generally logarithmic and sets the output to about 12% in its position. Apart from expensive models though, the tracking of these potentiometers is far from ideal.

There are good linear potentiometers with 1% or better accuracy, but in general they are not suitable as volume controls. However the circuit of Fig. 1 will give you a calibrated output signal with a gain depending on the value of the resistors used.

The input has a voltage divider R_1 and R_2 ; if $R_1=R_2$ the 0dB signal of a CD player will give 1V ac to the + input of Q_{1a} . With 10kΩ potentiometer R_4 at mid position and resistors R_3 and R_5 of 1.1kΩ, the gain of Q_{1a} is $(5+1.1) \div 1.1$. But there is an equal signal attenuation to buffer Q_{1b} , hence the output signal will be 1V ac or 0dBV also.

With R_4 fully clockwise the gain of Q_{1a} is $(10+1.1) \div 1.1 = \times 10$ or +20dB. This is connected directly to Q_{1b} ; hence the output signal is +20dB also.

However with R_4 fully counter clockwise,

gain of Q_{1a} is $\times 1$ but attenuation to Q_{1b} is now $1.1 \div (10+1.1)$ or -20dB. The potentiometer scale will be almost linear in decibels, covering -20 through 0 to +20dB. This is accurate enough for audio applications.

Increasing $R_{3,5}$ to 4.7kΩ will give a range of -10 to 0 to +10dB. In fact you can set the zero dB point anywhere, e.g. at 3 o'clock to give a range of -15 to 0 to +5dB.

Instead of this op-amp, a current conveyor like the OPA660 will do an even better job. Here, $V_{out} = V_{in} \times R_2/P_1$, so $(R_3+R_4) \div R_5$ for clockwise and $R_3 \div (R_4+R_5)$ for counter clockwise, hence the circuit of Fig. 2 performs as Fig. 1.

J van Doorn
Amersfoort
The Netherlands
E66

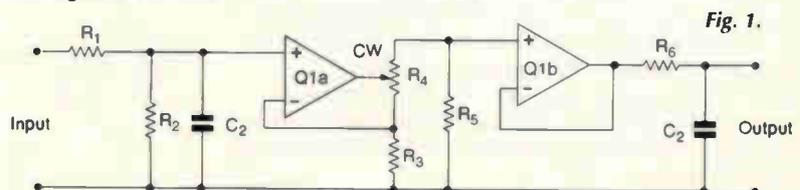


Fig. 1.

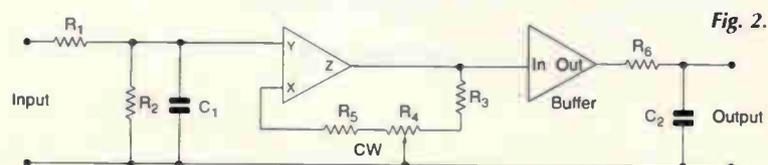


Fig. 2.

£75 winner

Letters to the editor

Letters to "Electronics World" Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS
e-mail jackie.lowe@rbi.co.uk using subject heading 'Letters'.

High-voltage power amp

I am writing in response to a letter from Ged Landon in the march issue on high-voltage amplifiers for electrostatic loudspeakers.

Back in 1985, I designed and built a push-pull transistor amplifier with a 5kV HT supply as my master thesis while I was at Chalmers University of Technology in Gothenburg. I did not use CRT deflection transistors, as a typical beta specification of the devices available at the time was >2!

I used video transistors instead, with a voltage rating of 350V and a beta of greater than 40. Some 18 Darlingtons connected pairs were used for each leg.

Arni Ingvarsson
Linköping
Sweden

On skill and training

I was very interested to read Malcolm Lisle's letter in the March issue - 'An Unskilled Generation' - on the lack of training in the electronics industry.

I'm under the impression that all the graduates get jobs in the software sector or in electronics design.

I work in the field of automated functional test of populated circuit cards and I'm keen to employ some intelligent, motivated trainees - not necessarily graduates.

How do I find them?

I've tried Job Agencies, Job Centres and the local Tec with no results.

It occurs to me that some of readers of *Electronics World* probably fit the bill, having a good knowledge of electronic circuitry, experience of software writing - possibly as a hobby - and who are addicted to electronics.

Alistair Gee
Worthing

More choice on FM

As the audio broadcast FM band is so much bigger than the AM MW and LW bands, it seems a pity that it has so few stations - especially as Radio 1 decided to have a narrower appeal.

Digital radio doesn't seem much use. Presumably this is because it takes a lot of processor power to decode and hence digital personal radios will not sip batteries like conventional AM/FM personal radios.

I read that 30kHz AM was considered for the FM band before 200kHz wideband FM was chosen: I wondered if narrow-band FM could be used to squeeze in extra channels - and could it be backwards compatible? Could narrowband FM be combined with a digital helper signal? Even if in mono, extra stations would be good.

Alan Bradley
Via e-mail

EMC and the individual

In the April 2001 issue, Leslie Green commented on EMC standards and spread spectrum. While I agree with most of his comments, his statement that an individual can make a PC without CE certification is incorrect.

All electronic equipment built and put 'into use' must comply with the EMC directive. The maker is responsible, and there's no distinction between individuals or companies.

In theory, all equipment should be tested or have a Technical Construction File - even one offs that are used in house and not sold.

With Trading Standards enforcing the regulations, it is difficult to see how anyone could be caught unless they actually caused interference and a complaint resulted. The only exception to this rule is that radio amateurs - one presumes licenced ones - may construct equipment as long as it is not sold commercially.

Every time I have taken a system for EMC testing that included a ready built CE-approved PC, the PC has required work before it would pass on its own.

Lower cost monitors also tend to fail emissions tests. Enquires or complaints to the PC suppliers just get responses such as "well

all the parts are CE marked" and a copy of a certificate (2 years old) for the monitor from an untracable Korean test house.

Robert Atkinson, G8RPI
Via e-mail

Mr Green is somewhat wide of the mark with his response to Mr Melia's undue anxiety over a 'dithered' switch-mode power supply.

As far as Britain is concerned, no proposals have been made to change the CISPR receiver and the emission requirements, in order to bear down on dithered devices. The reason that is that the subject has been investigated by the Radiocommunications Agency.

A voluminous report concludes that there is no need for a change. This is because the results of the existing tests are a fair measure of the threat posed by such devices to the reception of radio signals.

Mr Green is quite right in saying that a modification to the CISPR receiver specification might well be costly for every owner. The FCC may have decided on that ground, but in Britain, the subject has been investigated in some depth.

John Woodgate
Via e-mail

Valve substitute

I read with interest Dave Allen's article on his MOSFET replacement for a 6V6.

His idea was certainly ingenious, but I disagree that spare valves are difficult to get hold of, or very expensive. For example, Langrex Supplies Ltd, which advertise in this magazine, seems able to supply just about anything at very reasonable prices. Maplin has a much more limited range, but this includes the 6V6

More generally, there are some good web sites to interest the vintage wireless enthusiast. For instance, try <http://www.vintage-radio.com>.

Incidentally, I seem to remember that solid-state valve replacements were made commercially in the early seventies. Does anyone know anything about them?

Ranulph Poole
Via e-mail

A true dome tweeter

John Watkinson's interesting treatise on dome tweeters was flawed on one minor point. A pulsating hemispheric tweeter has been developed and has been available commercially for several years. I refer to the fascinating Audax HD-3P - a novel and unique application of piezo polymers.

Trevor Wilson
Via e-mail

Phono preamp

Norman Thagard is not the first person to use a two-stage preamplifier design in order to avoid calculating the full RIAA network. This seems an extraordinarily negative approach to circuit design.

He does not draw attention to the massive loss of headroom caused by his amplify-then-attenuate structure. This loss starts at 1dB at 1kHz, and rises to 20dB at 20kHz.

The unwanted zero produced by the single-amp version, because the gain cannot drop below unity, is easily cancelled out by placing a passive HF pole after the amplifier, as I have pointed out many times.

It did indeed come as a surprise to learn that most of the noise comes from the resistive part of the cartridge impedance - because it is not true. RIAA inputs can be made with JFET op-amps, bipolar op-amps, discrete FETs or discrete bipolars, but in every case the major noise contribution is either the amplifier or the 47k Ω input resistor.

Mr Thagard overlooks that the modest resistive component of a typical moving-magnet cartridge is completely dominated by its huge inductance. To this he adds a 10mH choke in series with the input: this seems like a very high value for EMC purposes.

For a Shure M75ED II, the relevant values are

610Ω and 0.47H. Over most of the audio spectrum, the total cartridge impedance is much higher than the resistive part. So the noise generated by the 47kΩ input resistor is not shunted away, but goes into the amplifier input.

For the best noise performance it is necessary to design for a much higher impedance than the cartridge resistance; 10kΩ to 20kΩ is about right.

It is a great pity that no information was given on noise and distortion performance.

Douglas Self
Huntingdon
Cambs

Dr Thagard replies...

I made no claim for originality of the two-stage concept. To the contrary, I wrote that I used a National Semiconductor abstract as the basis of the design. The only new feature was the single-stage op amp, but this was also based on a text book example.

The 10mH choke was per 'The Art of Electronics' recommendation. I went so far as to explain the effect of adding the choke. Reduce the choke to 2.5 or 5mH or eliminate it entirely, if it offends your sensibilities. I prefer to keep it because the reception of radio stations through a phono preamp is less desirable than the negligible alteration in frequency response.

Anyhow, the original articles for all three of these references were appropriately cited in the footnotes.

I ran the article circuit on PSpice along with circuits such as the inverter that places the 47kΩ resistor in series with the input rather than in shunt. I did not overlook the "huge inductance" (of the cartridge). I went so far as to model balanced phono preamps, but could never get rid of the input resistor noise, as the 23.5kΩ (1/2 47kΩ) gate resistors are in series with the inputs.

The Shure V15xMR 1kΩ dc resistance and 425mH inductance were modelled as well. I also had and used the PSpice models for the input JFETs, types 2SK389 and 2SJ109. The only devices in the model that differed from the prototype devices were the current mirror BJTs. Even there, I edited their instance models to more closely conform to the dual ITS transistors of the prototype.

Unless PSpice is wrong, the cartridge resistance is the greatest source of noise throughout the audio band. The preamp, as I stated in the article, contributed little additional noise. I wrote the disclaimer in the article that, "If the model is correct, the preamp, itself, adds little to the total noise output." Obviously, I acknowledged the basis of my claim for good noise performance.

I don't believe that I am even the first author to cite the cartridge dc resistance as the biggest source of noise, but admittedly, I cannot recall the citation.

For an inverting input stage, most of the noise comes from the 47kΩ resistor. I don't pretend to understand everything about PSpice, but in general it gives similar results to the breadboard circuits based on the computer-modelled circuits.

In any event, since no noise is audible from

the actual preamp operating in my system (Martin-Logan ReQuest loudspeakers), I can't imagine why this is worth much discussion on any but the theoretical plane. Too many designers spend too much time and money chasing the ultimate when much less would give the same subjective, if not objective performance in audio. In commercial work, over design is almost as heinous as under design.

If this argument is insufficient, I quote from AN-346: "In contrast (to the inverting op amp-my words), the 47kΩ damping resistor in figure 2(a) is in parallel with the source, and is a significant noise contributor only when the source impedance is high. This will occur near resonance, when the source is a moving magnet cartridge."

Resonance, according to the author, will occur between 15 kHz and 20 kHz. I was, therefore, not unaware of the point that Mr Self makes. However, I do dispute the significance since the application-note author goes on to say that the shunt location of the 47kΩ resistor has a 13-18 dB noise advantage over the series placement. Now I have to choose whether to believe Mr Self or Kerry Lacanette, the author of the application note. PSpice favours the application note author.

I don't have an ac voltmeter sufficiently sensitive for noise measurements. Noise measurement results were published for the application note circuit, which used LM833 op-amps in lieu of my "single-stage" op amps. Unweighted signal/noise referred to a 1 kHz, 5mV input was 82dB while 'A'-weighted S/N was 87 dB. These are certainly respectable.

If there is a headroom problem with the preamp, it is not obvious. It tests ok, and sounds fine using some pretty high-output cartridges in the face of any likely output from any cartridge.

I personally use a Shure V15xMR, whose data sheet is where I got the inductance and

resistance figures that I used. But I have tried the preamp with a Stanton 681EEE, which audibly has much higher sensitivity.

Again, to address this issue by reference to the application note: "It should be noted that most real cartridges are very limited in their ability to track such large ("superdisc" record-my words) velocities, and will not generate preamplifier output levels above 1V rms even under high groove velocity conditions."

Again, I see little justification to design to a non problem. In fact, this is one of the most oft-repeated concerns about phono preamp design and yet seems to have almost no practical significance.

Folks, the cartridge will very likely distort due to inability to track before its output will exceed the preamp's output limitation! The very same loud passages that were distorted when played through my Dynaco and Krell preamps still distort through my circuit. The ones that don't distort through the Dynaco and Krell don't distort through mine, either.

I recently read an article involving a former designer of phono preamps. He stated that, in testing various design variations for listener impression, accuracy of RIAA tracking correlated most closely with a favourable rating. If that is true, then using a design such as mine with accuracy of ±0.1dB would seem to be one of the best approaches, notwithstanding the concerns cited by Mr Self.

I don't try to reinvent the wheel. Mr Self needs to take up his quarrel with the authors whose articles I used in reference and as my design basis. If my article or circuit is in error, it is because I merely followed the wrongful ways of some pretty astute designers.

I had a friend with a pretty good set of ears give the preamp a "thumbs up," too and I have a lot more confidence in him than any theoretical considerations that would seem to have little practical applicability in the present case. ■

Obituary – Karl-Heinz Lipschutz

We have learned of the death of Heinz Lipschutz at the age of 80, after many months of poor health. He left no family.

Heinz was known in several fields of interest: aviation, electronics (radio and audio), combustion engine design and building and, perhaps most of all, he was well known for the 44 years he spent in trying to persuade the MoD to show some interest in his design for a submersible craft, the U-plane. Other navies have now taken it up.

In electronics, he first came up against officialdom in 1939, when he presented to the Air Ministry the design of a navigation aid for bombers (*EWV*, May, 1992). It used radio direction finding in a novel arrangement and was capable of extension to provide an inertial navigation system. Again, the development was turned down, even though it had been built and successfully tested.

He was born in 1920 in Germany to a Jewish family and fortunately went with his family to Palestine, having matriculated in 1936. He worked at several stop-gap jobs until 1939, when he was taken on by the British-controlled Dept of Civil Aviation at Lydda (Lod) Airport, in meteorological work and air traffic control, later working with the RAF.

He became involved with designing and constructing broadcasting equipment for the British Mediterranean Broadcasting Station and, in 1948, was co-founder of Kol Israel, the Voice of Israel broadcasting station.

Aviation interests took him to El Al, where he was a Flight Radio Officer, and later to Cambrian Airways in Cardiff as a Captain (he had taken out a private pilot's licence in 1939 and had built several light aircraft).

He will be missed by many friends at Cambrian and in other fields, not least this one. Philip Darrington

NEW THOUGHTS ON EMC

Ian Darney
presents a new
approach to EMC
with a view to
demystifying the
subject.

During the last half-century, the subject of electromagnetic compatibility, or EMC for short, has become increasingly complex and confusing. It now presents an onerous burden to the system designer.

EMC is just another functional requirement on a system, and can be treated as such. All that is needed is an understanding of the coupling mechanisms. Given such an understanding, a few simple guidelines can be formulated.

Many books and learned articles have been published. None of them adopts the approach outlined here.

Circuit modelling

It is not unreasonable to suggest that any EMC problem can be analysed in terms of circuit modelling.

A wealth of analytical tools is available to anybody who has completed a course in basic circuit design. Just as circuit diagrams can be used to describe how the signals in a system are processed, so they can be used to define the interference coupling mechanisms. A circuit diagram gives the whole picture.


There is no point in trying to understand how a multivibrator works by focussing attention on the properties of resistors, or capacitors, or transistors. Analysing the electric and magnetic fields at different locations is just as futile, when assessing the EMC of a system.

The ground plane

A widespread belief exists in the engineering profession that the construction of an equipotential ground plane is an essential feature of any good EMC design. This is less likely to be successful than the search for the Holy Grail, because there is no such thing as the equipotential ground plane.

Figure 1 illustrates the concept of the conducting plane and the image conductor. The plane lies on the x-z axis and the conductor is routed above it, parallel to the z-axis. When an alternating voltage source is connected at one end, and a short circuit placed at the other, a current flows.

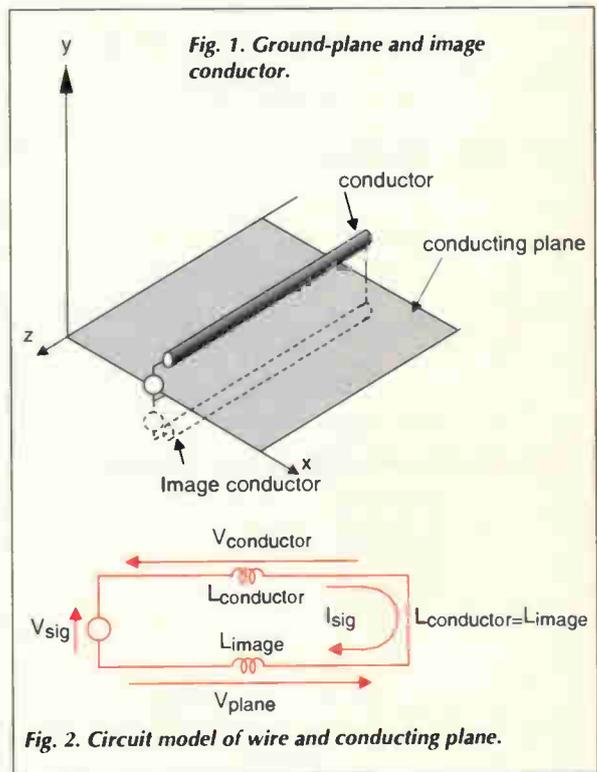It is true that, along any line on the surface parallel to the x-axis, the voltages are all the same. But it is not true that the entire plane is an equipotential surface. Along any line



parallel to the z-axis, the voltage varies continuously.

As far as the electromagnetic field is concerned, replacing the conducting plane with the image conductor makes absolutely no difference. Figure 2 is a circuit model of the upper conductor and its image. Since the image has identical physical properties, it must also have identical electrical properties. The

ground plane can be represented by an inductance, and the value of that inductance is the same as the signal conductor.

Since the return current is the same magnitude as the signal current, it

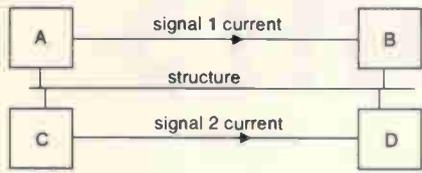


Fig. 3. Two separate wires along the structure.

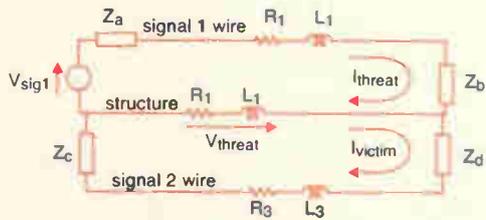


Fig. 4. Circuit model of coupling between two loops.

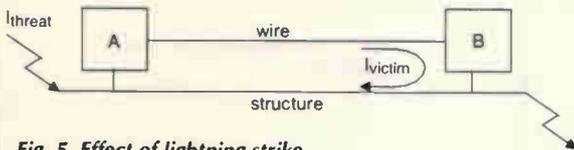


Fig. 5. Effect of lightning strike.

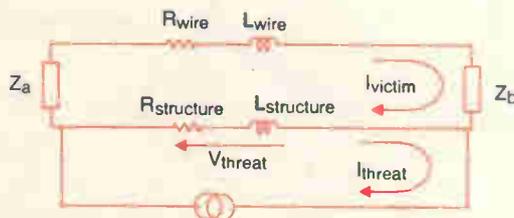


Fig. 6. Circuit model of lightning strike conditions.

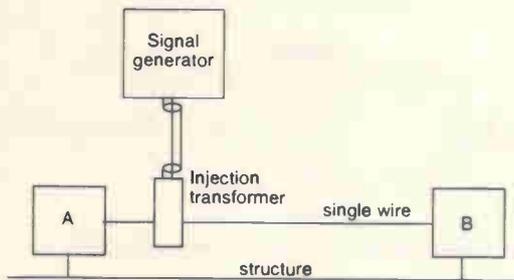


Fig. 7. Set-up for conducted susceptibility test.

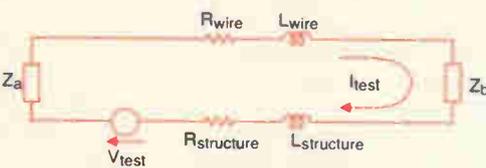


Fig. 8. Circuit model of conducted susceptibility test.

follows that the voltage drop along the ground plane is also equal to that in the signal conductor. Most definitely, the voltage is not zero.

However, this does not mean that the ground plane has no practical value. When implemented as one layer of a multi-layer printed circuit board, it acts as a dedicated return conductor for every signal track on the adjacent surface.

The return current is concentrated in that region of the plane immediately adjacent to the relevant signal track. Crosstalk between signals is minimised.

Intra-system design

Figure 3 illustrates an intra-system problem. During normal operation, signal 1 is carried from A to B, and signal 2 is carried from C to D. Both use the structure as the return conductor.

Coupling between the two signals can be analysed using the model of Fig. 4, where it is assumed that signal 1 is the threat, and signal 2 is the victim. If it is initially assumed that signal 2 is zero, then any voltages in the victim loop must be due to interference.

Component values for the circuit model can be derived from the physical construction of the assembly, or from electrical measurements made with general-purpose test equipment.¹

When values have been assigned to all components of the model, then circuit analysis can be used to determine the level of interference in the victim loop. Spicycle² makes this task easy.

The results can be compared with the characteristics of signal 2, an assessment made of system performance, and an informed decision made on the design of the interface circuitry for C and D.

There are other options. Interface A or interface B could be redesigned to minimise the interference created by the threat current, or the layout of the cables could be altered.

Circuit loops

Circuit diagrams normally show a section of a system, with the various inputs and outputs displayed as open-circuit terminals. The interconnections between circuit sections are seldom depicted either. Few people are interested in drawings of parallel lines.

When electromagnetic coupling is being analysed, the focus of attention is reversed. The function of circuit sections is largely irrelevant.

The purpose of Fig. 4 is to analyse the effects of the magnetic field surrounding the three conductors. Values must be calculated for the loop currents I_{threat} and I_{victim} before spurious voltages at the interfaces can be determined. Such a calculation is only possible if all components of Fig. 4 are defined. If any detail is omitted, analysis is impossible.

So, every loop of the circuit under review must be completely defined.

Inter-system problems

Where the source of interference is outside the control of the designer, it is still possible to predict the response of the circuit-under-review.

Figure 5 illustrates a problem. Equipment units A and B are mounted on a framework which is subject to lightning strikes. A single wire is used to carry a signal from A to B, with the structure used as the return path. What level of protection is needed at the interface circuitry to ensure that the system survives a strike?

Figure 6 shows the circuit model. Component values are determined as before.¹

A waveform is assumed for the lightning pulse, and a current generator is created to simulate that current. Carrying out a circuit analysis of the model enables currents and voltages at Z_a and Z_b to be predicted.

Predicting EMC test results

Figure 7 illustrates the set-up for a typical conducted susceptibility test. A toroidal injection transformer is used to induce a predefined voltage into the loop formed by cable and structure. The circuit model is shown in Fig. 8. Here, V_{test} simulates the voltage applied by the test equipment.

Again, frequency response analysis, or transient analysis, can be used to predict how the system will respond to an externally induced signal.

If the prediction is favourable, the system can confidently be submitted for formal EMC testing. If unfavourable, modifications can be carried out, and the cost of failure will be avoided.

Correlating results

A linear network that contains one or more voltage or current sources can be replaced by a single voltage source and a series impedance. (Thevenin's theorem). Hence, the set-up of Fig. 7 can be correlated with conditions during a lightning strike (Fig. 5) or with interference from another circuit in the equipment under review (Fig. 3).

In fact, any number of interference sources can be treated as a single voltage source in series with the structure.

The structure as a shield

The first line of defence of any system from external electromagnetic fields is the outer conducting shield. This could be the metal of an equipment box, an aircraft fuselage, or the framework of a building.

External electromagnetic energy is converted into transient currents in the shield, rather than in the functional circuitry. Transient voltages will be developed along the paths that the current takes, due to the shield inductance.

From the point of view of circuitry inside the shield, the source of interference is a voltage generator in series with the inductance and resistance of the shield.

In this context, the terms 'shield', 'ground', 'earth', 'structure', and 'framework' are synonymous

Return conductors

Up to this point, it has been assumed that all signals use the structure as the return path. It has been shown that any such configuration is subjected to the full threat voltage. (V_{threat})

If this 'single-wire' configuration is adopted, then every interface must be designed to withstand that level of threat.

A significant degree of protection can be provided, by routing a return conductor alongside every signal conductor, as illustrated in Fig. 9.

The circuit model for this

configuration is shown in Fig. 10, where it is assumed that the return conductor is grounded at both ends.

The inductors L_{gnd} and L_{ret} act as a potential divider to reduce the voltage induced in the inner loop. As a result, the differential current, I_{diff} , is significantly less than the common-mode current I_{cm} . The effect of interference on the system is reduced.

If the wires are close together, L_{sig} and L_{ret} are less than L_{gnd} , improving common-mode rejection.

If in Fig. 10, the voltage source were in series with Z_a , and V_{threat} was zero, then I_{cm} would be less than I_{diff} . Emissions from power supply wiring would be reduced.

Ground loops

It does not take long to deduce that the inclusion of return conductors will create innumerable ground loops in a normal system. This is no bad thing. Fear of ground loops is akin to being scared by bogeymen.

Every ground loop provides a measure of common-mode rejection.

Current balance

If the two conductors of Fig. 10 were identical, then the resistance and inductance values would also be equal. If the common-mode current were to be shared equally, then V_{sig} would be equal to $V_{transfer}$. There would be no interference. Figure 11 illustrates this concept.

In Fig. 12, this circuit is viewed from the point of view of its normal function. Current in the signal conductor is balanced precisely by current in the return conductor, and

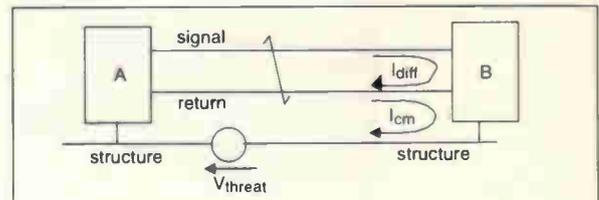


Fig. 9. Adding a return conductor.

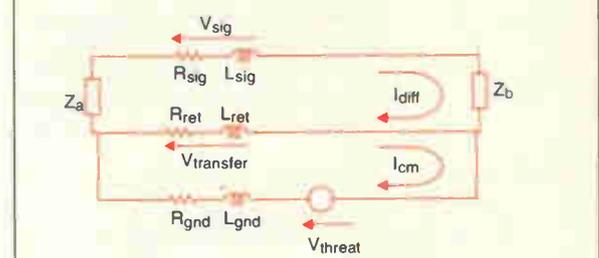


Fig. 10. Circuit model of three-conductor configuration.

the common-mode current becomes zero. There is minimal emission.

So, if the circuit design ensures that there is current balance in the signal and return conductors, then maximum common-mode rejection and minimum emission can be achieved.

Screened cable

Another way to improve common-mode rejection is to use a screened cable, as illustrated in Fig. 13.

The circuit model for this configuration is shown in Fig. 14. Here, the transfer impedance between the common-mode loop and the differential loop is just the resistance of the screen. At low frequencies, common-mode rejection is minimal.

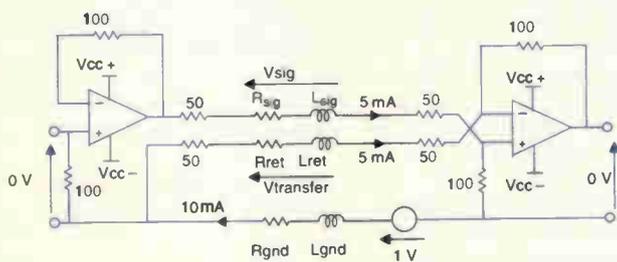


Fig. 11. Balancing the common-mode current.

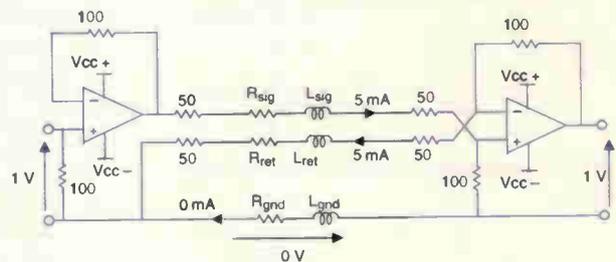


Fig. 12. Balancing the differential current.

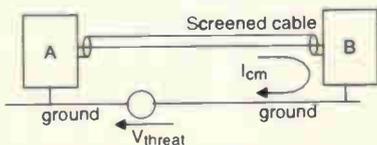


Fig. 13. Circuit configuration - screened cable.



Fig. 14. Circuit model, screened cable, grounded at both ends.

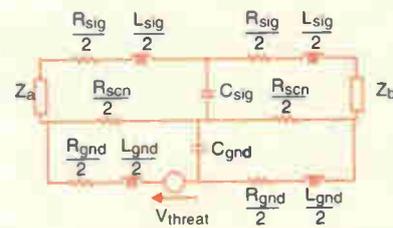


Fig. 15. Circuit model of screened cable - including capacitors.

but as the frequency increases, the impedance of L_{gnd} increases. I_{cm} decreases, the voltage across R_{scn} decreases, I_{diff} decreases, and so does the level of interference at the interface circuitry.

Capacitive effect

Taking capacitance into account, the circuit model changes to that shown on Fig. 15. Carrying out an analysis of the frequency response reveals that the common-mode current will drop to a minimum, then rise again to a peak. At this peak, common mode

rejection is minimal.

Even so, performance of a screened cable is better than the single wire or wire-pair configurations.

Floating configuration.

By removing the link between unit B and structure, that interface can be made to float, giving rise to the configuration of Fig. 16. The circuit model now becomes as shown in Fig. 17. It is obvious that for the floating configuration, common-mode rejection is excellent at low frequencies. There is virtually no common-mode current.

However, as the frequency increases, the impedance of C_{gnd} decreases, I_{cm} rises and so does $V_{transfer}$. Interference level rises at 20dB per decade. Then the situation worsens. Inductance L_{gnd} comes into play, and the slope of the curve increases, and continues to increase until the response reaches a resonant peak. It would be unwise to expect much more than 10dB of common mode rejection at that frequency.³

Transmission-line considerations

When the loop formed by cable screen and structure is treated as a transmission line, a better explanation for the performance of the floating and grounded configurations emerges

When the floating configuration is used, and the frequency of the interference reaches that corresponding to the quarter-wavelength of the line, voltage reflection occurs at the open-circuit termination, with current reflection at the short-circuited termination. The amplitude of the current at the grounded termination builds up to a peak and a high level of interference is observed in the differential loop.³

When both ends are grounded, and the frequency of the interference corresponds to the half wavelength of the line, current reflections occur at both ends of the line. Again, the level of interference in the inner loop reaches a peak value.³

The inevitable conclusion is that neither the grounded configuration nor the floating configuration can give a consistently good performance across the entire spectrum. Even so, they offer a vastly improved performance on the 'single-wire' configuration.

If the length of the line is defined, the frequency of resonance can be predicted.

Damping resistors

As well as providing an explanation to the problem of resonance, transmission line theory offers a solution. Terminate each line with a damping resistor, ideally, with the characteristic impedance.

Fig. 18 shows how voltage reflections can be avoided at a floating termination, by adding damping resistors. Since there are two loops involved, there are two transmission lines to be terminated. Values for R_{cm} and R_{diff} can range from less than 50Ω to 377Ω, depending on the configuration.

Fig. 19 shows one way of terminating a wire-pair when the return conductor is grounded at both ends. A common-mode transformer is used to insert a resistance in series with the cable. As far as differential signals are concerned, the transformer is transparent; any voltage across the signal winding is matched precisely by a voltage across the return winding.

The performance of this configuration is better than that of the common-mode choke, which looks like an open-circuit at high frequencies. As with the floating configuration, an open-circuit causes resonant peaks.

A common-mode resistance can be inserted into a screened cable without compromising the integrity of the screen. Just wind a few turns of cable onto a ferrite core and add a resistive loop.

Conclusion

A method of analysing various types of interference problems has been introduced. I have demonstrated that circuit modelling can be used to provide a clear understanding of the coupling mechanisms. A number of simple guidelines have been formulated.

Designing circuits to minimise interference is not particularly difficult.

References

1. Ian Darney, 'Bench testing for EMC', *Electronics World*, February 2000.
2. Spicyle. Those Engineers Ltd, 31 Birkbeck Road, London. NW7 4BP
3. Ian Darney, 'The common-mode resistor', *Electronics World*, August 2000.

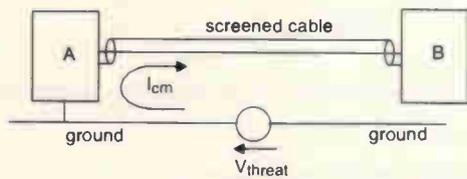


Fig. 16. Screened cable - floating.

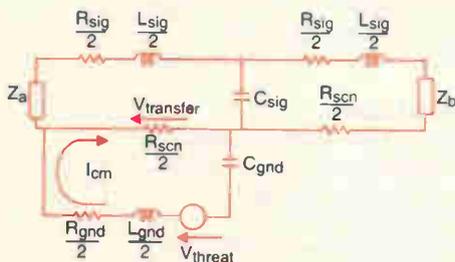


Fig. 17. Circuit model of screened cable - floating.

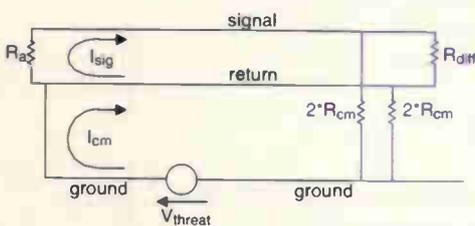


Fig. 18. Damping voltage reflections at a floating interface.

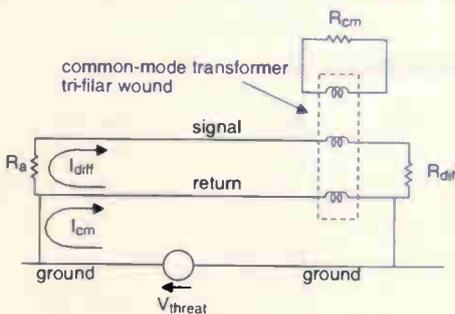


Fig. 19. Damping current reflections at a grounded interface.

The biosensor: electronics meets biology

Advances in materials and techniques have made sensors smaller and more sensitive than ever. Despite that, sensors still rely on the same principles of physics and chemistry that were used to make the measurements of physical parameters in the early days.

Now though, there is a new class of device coming into wide-scale use. It is based on biology and biochemistry – fields of science until now largely unexploited in instrumentation and control.

These sensors will determine the concentration of many of the substances found in industry, the environment and living organisms – including humans – that previously were not measurable electronically. Furthermore they will do this with a selectivity and sensitivity normally unachievable with standard sensors. The device is the biosensor, which the dictionary describes as “a device that uses a living organism or biological molecules, especially enzymes or antibodies, to detect the presence of chemicals”.

Early days

Perhaps the first sensor ever manufactured was Galileo's thermometer Fig. 1, made around 1592 AD. This was followed half a century later by Torricelli's barometer: both were instruments for measuring physical parameters of course.

It took until the nineteenth century however before the rise of the science of electrochemistry. The increase in knowledge in this field was primarily due to the work of Michael Faraday. It eventually led to the development of sensors capable of measuring the presence and concentrations of atoms and ions in solution.

Perhaps the best known of these is the pH electrode, used for measuring the concentrations of hydrogen ions in solution, a measure of the

solution's acidity. An important class of this type of electrode is the ion-selective electrode, which can be made sensitive to a particular ion through the use of a membrane that is only permeable to ions of a certain size. These membranes are often made of glass, Fig. 2.

The new generation of sensors now coming into widespread use takes this development a stage further. These sensors combine “traditional” physical or chemical principles with those of biochemistry and biology.

Interestingly this has come about because of a better understanding of how biological materials work on a chemical and physical level. This has enabled biological molecules to be linked directly to electrochemical and physical sensing devices.

To date, the main use of these devices has been in the health-care area, where measurements of the levels of gases, ions and metabolic products in the blood are often the best indicators of a patient's state of health. Using these devices in conjunction with some electronic indication can give a much quicker and more cost-effective result than a laboratory analysis.

These instruments are also making their way into high-street stores. Perhaps the best examples are the blood glucose level indicators available from chemists' outlets to aid sufferers of diabetes in the control of their blood glucose levels.

However, these devices are now of growing significance in the relatively new biotechnology industries. There, they are used as monitoring and control sensors in the large-scale production of materials in fields as diverse as brewing and drug manufacturing.

They are also finding applications in industrial-process effluent control, in monitoring for gases in the mining industry and in pollution monitoring in the general environment. This

Biological materials combined with traditional transducers allow substances to be analysed much more rapidly than is possible using conventional laboratory techniques. David Clark looks at a device set to flourish in the twenty-first century – the biosensor.

article takes a look at how biological materials can be connected into the electronic world, the interface that makes all these applications possible.

The biosensor

A biosensor consists of three main components: a biologically active agent, a transducer for generating a non-biological output that can be connected to some form of instrumentation and a fixing agent. This fixer keeps the agent

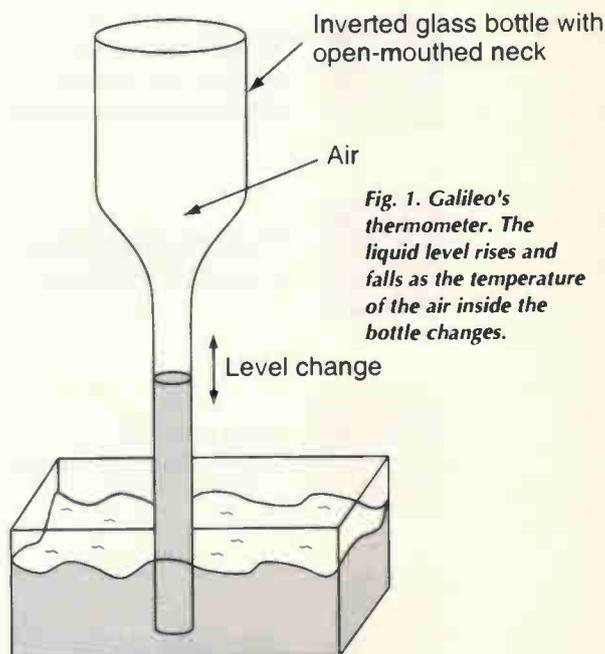


Fig. 1. Galileo's thermometer. The liquid level rises and falls as the temperature of the air inside the bottle changes.

in position, provides a medium for keeping the agent stable, allows the reactant access to the agent, and links the agent's output to the transducer, Fig. 3.

The next sections look in more detail at each of these three components.

The transducer. With perhaps one notable and fascinating exception – surface plasmon resonance, described later – the transducer part of a biosensor operates on the same principles as the traditional physical and electrochemical sensors. The transducer must of course respond to

Fig. 2. Ion-selective electrode. A potential difference, related in value to the concentration in solution of the ion being analysed, develops between A and B.


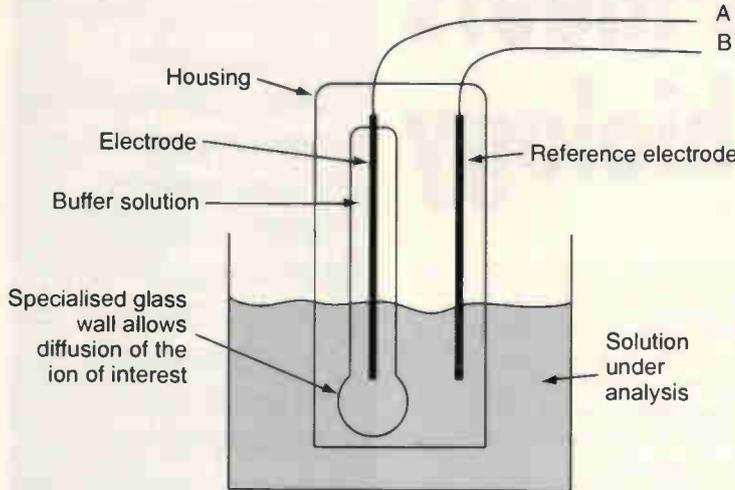


Fig. 3. Basic biosensor comprises three main parts – a biologically active agent, a transducer and a fixing material to hold the two together.

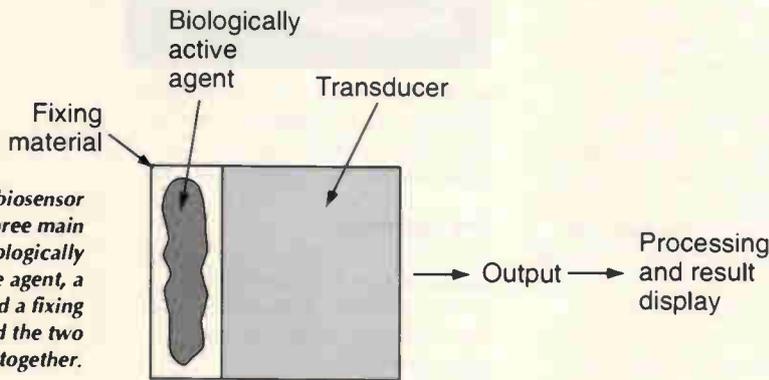

the output of the biological agent. Depending on the agent, this output can be electrical, physical or optical.

Electrical transducers can be amperometric, i.e. current measuring, potentiometric, i.e. voltage measuring, or even field-effect transistor (FET) linked. Here the gate of an FET is in intimate contact with the biological material. Changes in charge distribution within a biological material occur as a result of chemical reactions. These changes in charge directly control the FET. It is relatively easy to make the FET part of the signal-processing electronics associated with the sensor.

Outputs that can be categorised as physical include the microscopic changes of mass, conductivity, dielectric strength and temperature that can occur when reactions take place. These effects can be monitored directly or converted to electrical measurements using fairly straightforward techniques.

Optical outputs might involve monitoring via fibre optics. Changes in transparency, i.e. change in light transmission properties, can be monitored optically. Many organic compounds absorb very specific wavelengths of visible and ultra-violet light. Bioluminescence – the direct conversion of chemical energy to light energy by biochemical means – can also be monitored optically.

Output detection using surface plasmon resonance can also be considered an optical technique.

The fixer. One of the main problems in using biological material as part of a sensor is in fixing it in position as part of the sensor. As well as holding the material in position, the method chosen must also maintain it in an environment in which it remains active. Of course the fixing method must also ensure that the material is accessible to the substance which it is measuring.

There are four ways of achieving this. The material can be fixed by being: adsorbed onto a surface, held behind a membrane, held within a matrix or chemically bonded. Fig. 4.

The most dramatic advances that have come about in this sensor technology however have occurred due to the recent developments in knowledge of how biomaterials work at molecular level.

The biological agent. Currently there are four main classes of biomaterial used in biosensors. These are: enzymes, antibodies, receptor proteins, and whole cells and tissues. In the future, it is possible that even

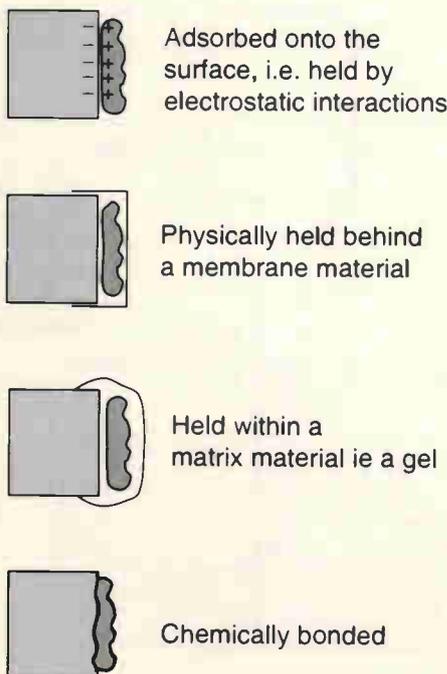


Fig. 4. Methods of fixing biological material.

whole organisms could be used as biological detectors.

The most useful aspect of biological materials is that many only react with specific materials. Enzymes are perhaps the best-known example. They are the catalysts of the biological world; without them life as we know it would not exist.

Enzymes function by reducing the energy necessary for a reaction to begin, the activation energy, and achieve this at biological molecule level by having a structural shape that 'fits' - like a lock and key - with the molecules taking part in the reaction, **Fig. 5**.

As a consequence, enzyme action is very specific, each type catalysing only one reaction. As a result, it can be used to detect single substances in an environment where many may be present.

A good example of this class is the glucose oxidase enzyme, which can be used in biosensors for measuring glucose levels in blood. Here the shape of the glucose molecule is such that it fits into binding sites on the enzyme molecule.

The interaction affects the energy levels associated with the bonds between the atoms, and gluconic acid and hydrogen peroxide are produced as the glucose reacts with oxygen. This means that the concentration of glucose can be determined by measuring one of three changes - the reduction in oxygen concentration, the increase in acid concentration or the increase in hydrogen peroxide concentration.

There is a simple electrochemical transducer for detecting each of these three substances - the pH electrode for example will measure the acid concentration very simply.

Antibodies. The second class of biomaterial is the antibody, or immunoglobulin protein: this is also the second most frequently encountered biomaterial used in biosensors.

The antibody is a fundamental part of the body's immune system. There is a different type of antibody for every type of particle the body recognises as 'foreign', an example of which is an infective agent like a bacterium. These foreign particles are known as antigens. The antibody binds tightly to the antigen for which it is specific, just as an enzyme binds to a reacting molecule. **Figure 6** gives an indication of the action of antibodies.

In the immune system, this triggers a further process that attacks the foreign particle; in the biosensor

however the property change that occurs as the antigen binds to the antibody is measured with an associated transducer.

The activity of antibody-based sensors means they are primarily useful in a medical context.

Receptor proteins. The receptor protein is a very flexible class of biomaterial for biosensor use. There are receptor proteins for many different types of biologically active materials including hormones and neurotransmitters, the chemicals that mediate the activity of the nervous system.

Drugs also usually act via receptor proteins. In biological cells the binding of the appropriate molecule to the receptor protein triggers the selective, active transport of another substance across the cell membrane, a normal, vital part of cell function. **Figure 7** shows how the receptor protein works.

For a biosensor this action means that a receptor protein can be chosen to give a detector that only responds to the hormone, drug, etc., of interest.

The use of whole cells and tissue in biosensors is more complex, primarily since living tissue needs a supply of nutrient and oxygen. Nevertheless the principle is the same; in the nose for example, particular tissues respond to the particular molecules that 'have' a particular smell. So a biosensor with some of this tissue as the detector

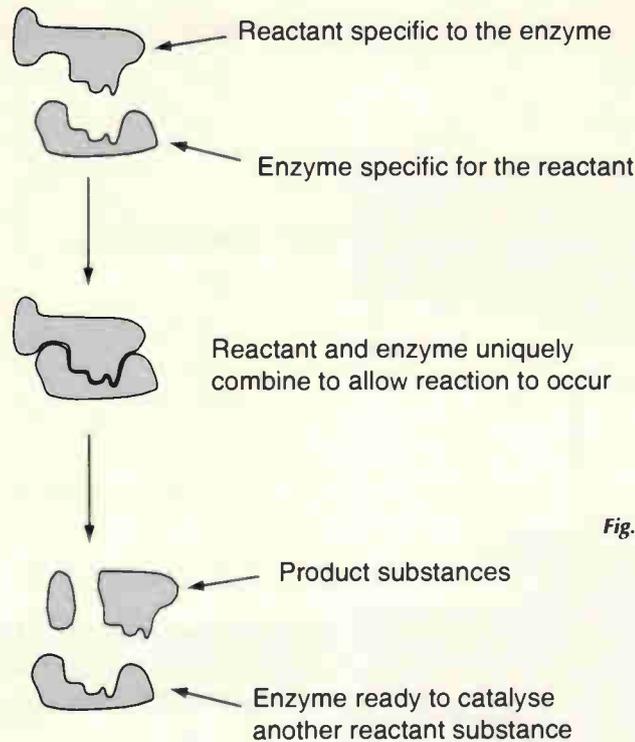


Fig. 5. Enzyme action.

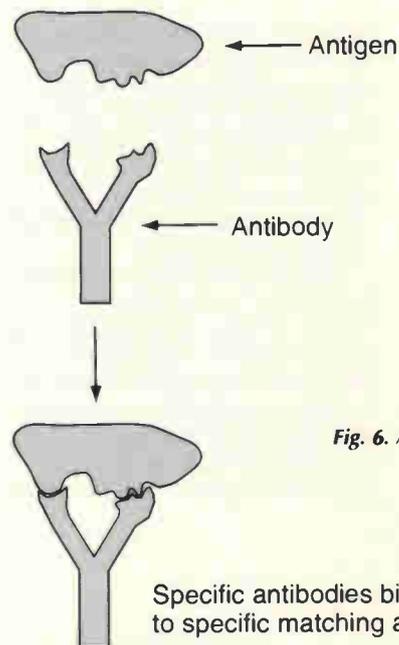


Fig. 6. Antibody action.

could respond to the presence of those molecules.

Another, non-technical, complexity in this area is of course an ethical one concerning the source of this living material, whether animal or perhaps 'cloned'.

Surface-plasmon resonance

Changes that occur in biological molecules are subtle and often the reactions only involve one or two

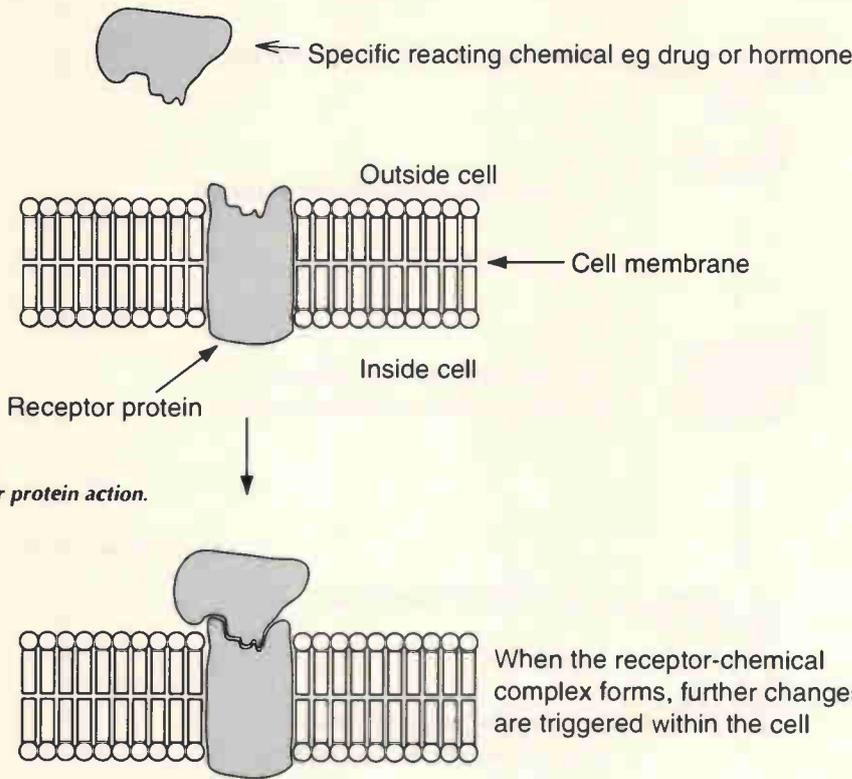


Fig. 7. Receptor protein action.

molecules. This gives biosensors their sensitivity advantage over conventional sensors as well as the advantage of their selectivity. It does however mean that the associated transducer also needs to be sensitive enough to convert the biological effect to one that can drive processing and display instruments.

Specialised techniques can be used to detect the small changes in voltage, current, temperature etc. that are used in conventional transducers. However an exciting new technique has been developed that enables the monitoring of the activity of biological molecules directly, one that operates at sub-atomic level. This

technique is called surface plasmon resonance, Fig. 8.

The atomic and molecular structures, and hence properties of materials, are determined primarily by the electrostatic forces between the charges on the atoms and electrons that compose that material. Quantum theory explains that the distribution of these charges is not fixed, as in the classical description of electron orbitals. Rather, it is subject to random fluctuations, the electron orbitals for example being the 'places' where the electrons are most likely to be found at any instant.

A 'packet', or quantum, of energy associated with this charge

fluctuation can be considered to act like an electron particle, and this type of 'quasi'-particle is known as a plasmon. Just as atomic particles fixed in a lattice can vibrate and have a resonant frequency associated with them due to the energy of the bonds holding them, plasmons too can vibrate and have a resonant frequency associated with them.

At the surface of a material, for example a thin film of gold, these plasmons can be excited by a source of energy, for example photons of light. These energy interactions affect the reflection of that light.

If a thin layer of biological material is attached to the gold surface, the energy interactions between the biological and gold materials will give a particular resonant frequency and angle of reflection for light directed at the surface. If the energy interactions are then modified, for example by the biological material binding to something else on its 'outer' surface, the resonant frequency and the angle of reflection will change.


So, by simply directing a beam of polarised light at the gold film-biological material interface and measuring the change in the angle of reflection, a highly sensitive method of detecting a substance that specifically binds to the biological material is obtained.

Prevention better than cure


Medical treatments are tending to become increasingly based on prevention through routine clinical testing, followed by early intervention when potential problems are recognised.

Similarly, better environmental protection is based on preventing contaminants reaching the environment in preference to cleaning pollution up after it has occurred. The need for increasingly specific and sensitive detectors for the relevant substances is therefore becoming greater.

Scientists are rapidly developing the ability to 'engineer' biological materials to specific requirements. Technological advances are enabling in many cases the agent and fixing medium to be screen-printed onto an electrode. This will allow the mass production of inexpensive biosensors, and it means that these devices are likely to be making greater and greater inroads into everyday life in the coming years, making a significant contribution to an increasingly healthy society and 'green' environment.

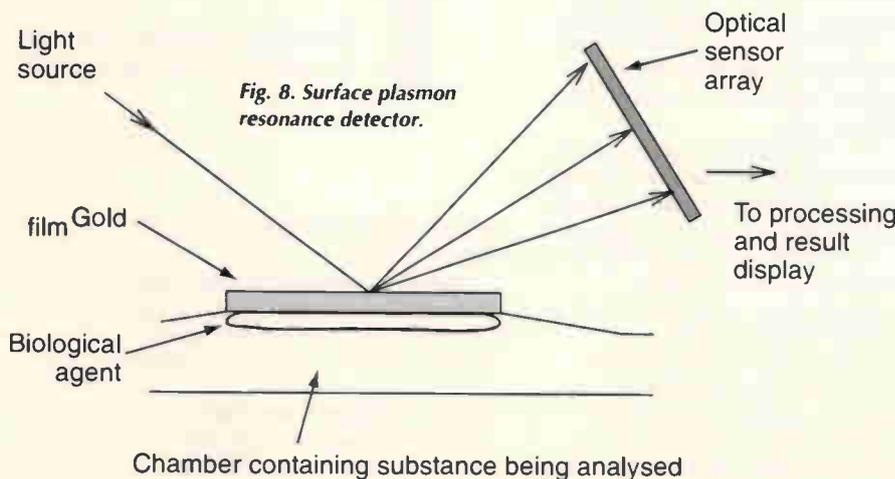

TiePieScope HS801 PORTABLE MOST

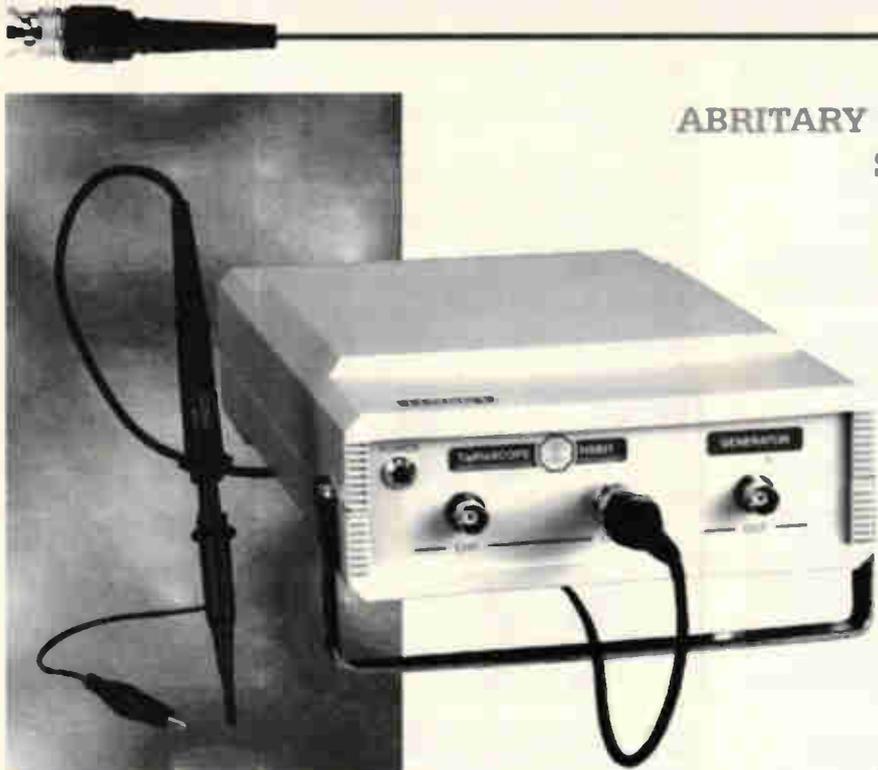

ARBITRARY WAVEFORM GENERATOR-
STORAGE OSCILLOSCOPE-
SPECTRUM ANALYZER-
MULTIMETER-
TRANSIENT RECORDER-

Reliability

- The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (arbitrary waveform generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.
- The versatile software has a user-defined toolbar with which over 50 instrument settings quick and easy can be accessed. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.
- When a quick indication of the input signal is required, a simple click on the auto setup button will immediately give a good overview of the signal. The auto setup function ensures a proper setup of the time base, the trigger levels and the input sensitivities.
- The sophisticated cursor read outs have 21 possible read outs. Besides the usual read outs, like voltage and time, also quantities like rise time and frequency are displayed.
- Measured signals and instrument settings can be saved on disk. This enables the creation of a library of measured signals. Text balloons can be added to a signal, for special comments. The (colour) print outs can be supplied with three common text lines (e.g. company info) on three lines with measurement specific information.
- The HS801 has an 8 bit resolution and a maximum sampling speed of 100 MHz. The input range is 0.1 volt full scale to 80 volt full scale. The record length is 32K/64K samples. The AWG has a 10 bit resolution and a sample speed of 25 MHz. The HS801 is connected to the parallel printer port of a computer.
- The minimum system requirement is a PC with a 486 processor and 8 Mbyte RAM available. The software runs in Windows 3.xx / 95 / 98 or Windows NT and DOS 3.3 or higher.
- TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 4WJ, UK
Tel: 01480-460028; Fax: 01480-460340

TiePie engineering (NL),
Koperslagersstraat 37, 8601 WL SNEEK
The Netherlands
Tel: +31 515 415 416; Fax +31 515 418 819

Web: <http://www.tiepie.nl>

WEB DIRECTIONS

ACQUIVISION

<http://www.acquivision.com>

AcquiVision solutions, including XY-Plotting, Oscilloscopes (with FFT), Data Logging and Custom Software, have been getting the most from computers since 1994. Download software. Telephone (01903)830502.

AQUILA VISION

<http://www.aquila-vision.co.uk>



Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general interest CD-ROM's.

ALCATEL COMPONENTS

<http://www.components@alcatel.de>


ASHWELL ELECTRONICS

<http://www.ashwell-hq.com>

Ashwell provide technical support for Apex Microtechnology op-amps and DC/DC'S; Aeroflex; EMP filtered connectors; M S Kennedy; Mitech obsolescence; NSC Mil/Aero; Teledyne Relays and isocom mil/optocouplers.

ARCOM

<http://www.arcomcontrols.com/ew/>

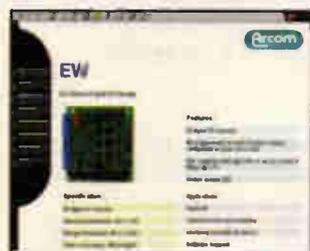

A leading international supplier of communication and control technology to industry, Arcom provides leading edge solutions through a comprehensive range of market leading products.

BROADCASTING COMMUNICATIONS SYSTEMS

www.broadercasting.co.uk

WINRADIO now brings you a complete choice in personnel computer controlled

radio scanning and reception solutions ● Broadcast ● Media ● Monitoring ● Professional Amateur Radio communications

BEDFORD OPTO TECHNOLOGY LTD

<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and custom, LED bargraphs, circuit board indicators, stand offs, transmissive/reflective switches, baseefa optocouplers tubular and surface mount, panel mount LED assemblies.

CONCEPT ELECTRONICS

<http://www.conceptkey.co.uk>

Concept Keyboards are specialists in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

CONTROL SOLUTIONS

www.controlsolutions.co.uk

Data acquisition and control for beginners, hobbyists, and professionals. Perform mathematical and logical operations on data in real time. Email: info@controlsolutions.co.uk.

COOKE INTERNATIONAL

<http://www.cooke-int.com>
e-mail: info@cooke-int.com




Stockists of Quality Used Electronic Test Instruments and Operating & Service Manuals.

CROWNHILL ASSOCIATES LTD

<http://www.crownhill.co.uk>

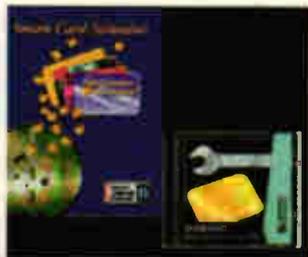Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.



DANIEL MCBREARTY

<http://www.danmcb.demon.co.uk/eng.html>

Experienced engineer based in London, specialist in audio and control systems. Available for design, project engineering or general consultancy. Background of high-quality work.

DESIGNER SYSTEMS CO.


<http://www.designersystems.co.uk>



Electronic product design company with over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.

ECM SELECTION

<http://www.ecmsel.co.uk>

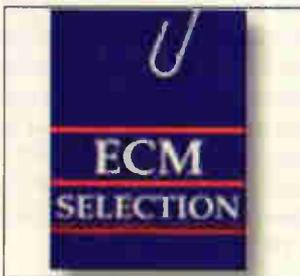

For the pick of the UK's Top High-Tech Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager - £22,000 - £70,000

EDWIN PCB DESIGN SOFTWARE

<http://www.swifteurotech.co.uk>

Swift Eurotech supply the best-selling EDWin CAD/CAE system for PCB design, including schematics, simulation and PCB design. Discounts up to 60% for non-commercial users.


ELECTRONICS AND COMPUTING PRINCIPLES

<http://www.eptsoft.com>

Studying electronics or computing or just want to keep up-to-date in an easy and enjoyable way, then this fully interactive software is for you.

EQUINOX TECHNOLOGIES UK LTD

<http://www.equinox-tech.com>

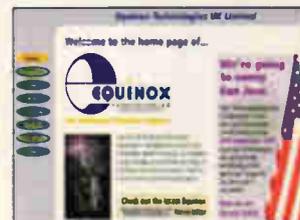

Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards


FLASH DESIGNS LTD

<http://www.flash.co.uk>

Flash supply low cost AVR ISP programmers (£39), MINI-ICE starter kits (from £69), Portable Easy-ICE emulators (from £199), ICE Adapters & 'C' compilers for any ATMELE AVR, MCS51, Dallas, Hitachi H8 microcontroller. Download FLASH NEWS now, Watch out for Special Offers'. ARE YOU developing code in a Flash?

GOOT PRODUCTS

<http://www.kieagoot.co.uk>

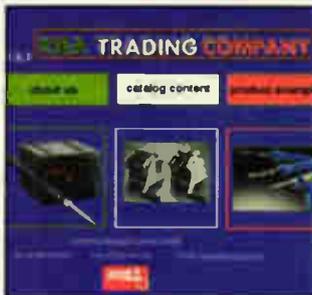

Kiea Trading Company is the sole agent of Goot products. We specialise in supplying the soldering and desoldering product range manufactured by Goot Japan for the UK market. Goot uses advanced production technology to manufacture high quality soldering iron products for industrial, professional and general purpose use.

HSPS LTD

<http://dspace.dial.pipex.com/hsp5/>

FILTER DESIGNER - Advanced analog and digital filter design software for the PC. - Standard and Professional versions. - Free download of Evaluation version.

To reserve your web site space contact Pat Bunce

Tel: 020 8652 8339 Fax: 020 8652 3981

HTB ELEKTRONIK

<http://www.htb-elektronik.com>

We are selling second-hand test & measurement equipment and accessories for over 10 years, from all leading manufacturers.

LEVY/LATHAM GLOBAL

<http://www.levylatham.com>

U.S. Military Surplus meters, plug-ins, test sets, oscilloscopes, power supplies, signal generators, spectrum analyzers and radio components from Tektronix, Hewlett Packard, Sony, Phillips and more!


LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

MATTHEY MICROFILTERS

<http://www.microfilters.net>

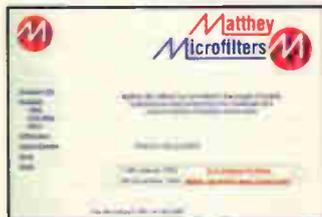

30 years experience in the design and manufacture of high quality passive filters and delay lines. Used in Broadcast, Telecommunications, Medical, Multimedia, and Computer industries.

MATRIX MULTIMEDIA LTD

www.matrixmultimedia.co.uk



Matrix Multimedia publishes a number of highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

NEWNES - BOOKS FOR THE ELECTRONICS WORLD

<http://www.newnespress.com>
Over 300 books and information packages



for those working with electronics and engineering technology. Visit our site for a free catalogue and downloads.

NORCALL

<http://www.norcall.co.uk>

Suppliers and repairers of MOBILE RADIO equipment

SALES

HIRE

REPAIR

Huge stocks of used radios and spares
Pye Philips Simoco Icom Kenwood
Standard Clearstone Maxon Yaesu Key
Midland.

WE CAN PROGRAM ANYTHING

24hr Service

OMEGA RESEARCH LTD

<http://www.omega-research.co.uk>

"SMD prototyping adapters. Unique, flexible, low cost adapters to allow bench working with SM devices. Range suits most devices down to 0.5mm pitch."

PCA: PHILIP COLLINS & ASSOCIATES PTY. LTD

<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transceivers from any tone phone.

POLY-FLEX CIRCUITS LTD

<http://www.polyflex.com>

Design, manufacture and population of printed polyester flexible circuits, including Flip Chip on Flex providing practical, low cost, reliable solutions for today's small lightweight products.

QUASAR ELECTRONICS

www.quasarelectronics.com



Over 250 electronic kits, projects and ready built units for hobby, educational & industrial applications.
TEL: 01279 306504, FAX: 07092 203496
or EMAIL: ewsales@quasarelectronics.com

QUILLER ELECTRONICS

<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

RADIOMETRIX

<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use.

RADIO-TECH LIMITED

<http://www.radio-tech.co.uk>

Radio modules, modems, telemetry, audio transmitters, pagers, antenna, remote controls and much more. All UK designed and manufactured.


RALFE ELECTRONICS



professional test & measurement
www.ralfe-electronics.co.uk

RD RESEARCH

<http://www.looking.co.uk/spice>

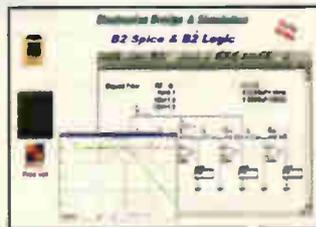

Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.

RS COMPONENTS LTD

<http://rswww.com>




The award winning on-line service from RS
- 110,000+ products available
- Technical data library
- Stock availability check
- Integrated on-line purchasing
- Order by 8pm - with you tomorrow.

SOFTCOPY

<http://www.softcopy.co.uk>

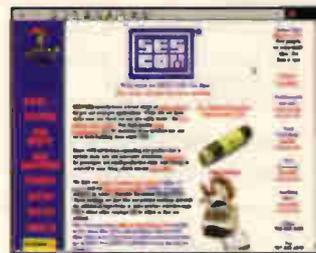As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.



SESCOM, INC.

<http://www.sescom.com>

SESCOM, INC. is a 30-year manufacturer of audio "problem solvers" and transformers. We also offer easily-fabricated aluminum enclosures for small production runs and prototypes.

STAFFORDSHIRE WIRELESS COMPANY

<http://www.staffs-wireless.com>

Wireless, communication, test equipment, bought and sold for very competitive prices visit our web site or telephone John on 01889 569928 or 0973 296461.

SUPRA AUDIO CABLES

<http://www.jenving.se>

Jenving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.



TEMWELL CORPORATION

<http://www.temwell.com.tw>

Manufacturer & Exporter of Heical BPF Filter, 30 Watts BPF Power Filter and Handset/Base Station Duplexers

TEST EQUIPMENT SOLUTIONS

<http://www.TestEquipmentHQ.com>

Quality second user test equipment with full warranty and support. All types of equipment from all leading manufacturers including general purpose, communications and industrial test.



WEB DIRECTIONS

TELNET

<http://www.telnet.uk.com>

Top quality second-user Test and Measurement Equipment
eMail telnetkm@msn.com

THOSE ENGINEERS LTD

<http://www.spiceage.com>



Working evaluations of SpiceAge mixed-mode simulator, Spicycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

THERMOSPEED

<http://www.thermospeed.co.uk>



Temperature and pressure, control and instrumentation. Full on-line purchasing.
* Overnight ex-stock delivery
* Create your own hotlist
* Download datasheets
* Full technical support

TOTAL ROBOTS

<http://www.totalrobots.co.uk>

Robot Kits and Control Technology products, including OOPic the first Object-Directed Programmable Integrated Circuit. Secure on-line ordering and fast delivery.

TRIDENT MICROSYSTEMS LTD

<http://www.trident-uk.co.uk>

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

TOWER HILL TECHNICAL SERVICES

<http://www.towerhillaerials.com>



Everything you need for DIY Satellite & TV aerial installation. The one stop shop for TV, FM, Satellite, Amateur Radio PMR Aerials, Distribution Equipment, Cable & Accessories.

TECHNICAL AND SCIENTIFIC SUPPLIES

<http://www.technicalscientific.com>

Suppliers of pre-1985 equipment and components.
- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

VANN DRAPER ELECTRONICS LTD

<http://www.vanndraper.co.uk>

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>



VUTRAX electronic schematic and pcb design system for Windows 95, 98 and NT. Limited Capacity FREE version downloads available, all upgradeable to various customised levels.

WOOD & DOUGLAS

<http://www.woodanddouglas.co.uk>

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for International telemetry, data, voice & video wireless communications.

UK ELECTRICAL DIRECT

<http://www.uked.com>

For a comprehensive on-line directory, buyers guide and resource locator for the UK Electrical Industry look at this site. Many of the companies listed have links to their own web sites, making

this a one-stop shop for a huge amount of information.

UK MAILING LIST GROUP

http://www.egroups.com/list/uk_tvrepair

Following on from the newsgroup discussion last month there is a UK Email group for TV technicians where you can send an Email to everyone in the group. There's just over 30 people in the group at present. For more details and how to register look at the egroup home page. Just a general comment though - you do have to be careful who you give your Email address to so that you can avoid "spamming" - that is getting lots of unwanted Email about dubious Russian site (amongst others).

REED CONNECT

<http://www.reedconnect.net/>

Another free internet access site, this time from Reed Business Information. However the site possesses a useful UK People and Business Finder, with an e-mail search. There's also business news and local information, and some good links to directory sites.

REPAIRWORLD

<http://www.repairworld.com>

Repairworld is a sophisticated US based fault report database which is updated bi-weekly. It operates on a subscription basis and describes itself as an "affordable solution for all technicians". You can see some samples of the material for free, monitors, VCR, DVD and Camcorders being of particular relevance to UK users. The site also provides a "chat room".

**Pat Bunce on
020 8652 8339
or fax on 020 8652 3981.
or e-mail:
pat.bunce@rbi.co.uk**

Put your web address in front of 21 000 electronics enthusiasts and experts. *Electronics World* acknowledges your company's need to promote its web site, which is why we are now dedicating pages in every issue to announce your **WEB ADDRESS.**

This gives other readers the opportunity to look up your company's name, to find your web address and to browse the magazine page to find new sites.

We understand that cost is an important factor, as web sites are an added drain on budgets. But we are sure you will agree that the following rates make all the difference:

FOR 12 ISSUES:

Lineage only will cost £150 for a full year just £12.50 per month.

This includes your company's name, web address and a 25-word description.

Lineage with colour screen shot costs £350 for

a full year, which equates to just £29.17 per month.

This price includes the above mentioned information, plus a 3cm screen shot of your site, which we can produce if required.

To take up this offer or for more information ring:

**Pat Bunce on 020 8652 8339
or fax on 020 8652 3981.
or e-mail: pat.bunce@rbi.co.uk**

Company name	Web address

Fully Warranted Bargain Test Equipment.....call 020 8943 4477 NOW!

AMPLIFIERS & ATTENUATORS

BIRD		
8323	100 Watt 500 MHz Attenuator	£275
8343-200	100 Watt 1GHz RF Attenuator	£300
KALMUS		
225LC	0.01 to 200MHz 25 Watt Power Amplifier	£1750

DATA COMS & TELECOMS

ACACIA		
Clarinet-Book	ISDN SO/EI Protocol Analyser	£16500
ADTECH		
SX12-1	100bps to 2 Mbps Data Channel Simulator	£11000
AGILENT TECHNOLOGIES (HP)		
37717C	PDH/SDH Transmission Test Set	£3000
CONSULTRONICS		
Auto Tims III	Automatic Data Line Analyser	£3500
FIREBERD		
6000FE	Communications Analyser 2522 with option 4	£4950
ICT		
Victoria	SDH/PDH STM-1 1310 Analyser	£9500
SUNRISE		
SUNSET E10	2Mbit/s PCM/DATA Channel Analyser	£4500
WAVE TEK WANDER GOLTERMANN		
ANT-20	STM-1/4 1310/1550nm Jitter TX & RX	£22000
DLA-9D	Data Line Analyser	£4500
PA-41	2Mbps Frame and Signalling Analyser	£5500
PFA-35	Communications Analyser	£4000

OPTICAL

AGILENT TECHNOLOGIES (HP)		
E6000A/05A	850/1300nm Mini OTDR	£5750
FUJIKURA		
FSM-16S	Fusion Splicer Single Mode	£5750

POWER METERS

BIRD		
43	2.7GHz 10 KW ThruLine Wattmeter	£350
4304A	1GHz 500W ThruLine Wattmeter	£325
4410A	2.3GHz 10KW ThruLine Wattmeter	£150

SIGNAL SOURCES

AGILENT TECHNOLOGIES (HP)		
8656B	Signal Generator	£950
8657A	Signal Generator	£950
IFR (MARCONI)		
2019	Synthesised Signal Generator	£750
2019A	Synthesised Signal Generator	£850
2022	Synthesised Signal Generator	£950
2305	Modulation Meter	£700

TV BROADCAST

AGILENT TECHNOLOGIES (HP)		
3010R	Calan Sweep/ Ingress Analyser	£3500
PHILIPS		
PM5639/00	Handheld TV Colour Analyser	£2500
TEKTRONIX		
DMA 120	Demodulator Analyser	POA

MISCELLANEOUS

AGILENT TECHNOLOGIES (HP)		
3586C	Selective Level Meter	£500

CALIBRATORS & STANDARDS

DRUCK		
DPI 601	0 to 2 bar Digital Pressure Calibrator	£400
DPI 601 I /S	Pressure Calibrator (0-20 bar)	£650
DPI 601 I /S	Pressure Calibrator (160 Bar)	£700
DPI 601 I /S	Pressure Calibrator (400 Bar)	£750
HAWEN AUTOMATI N		
SPEC-CAL	Process Calibrator	£950
QUARTZLOCK		
2.A	Off Air Frequency Standard	£475

DIGITAL DESIGN & TEST

AGILENT TECHNOLOGIES (HP)		
5006A	Signature Analyser	£550
GOULD		
K50	Logic Analyser	£550

FREQUENCY COUNTERS

PHILIPS		
PM6652	Counter	£500

OSCILLOSCOPES

FLUKE		
PM199	200 MHz 2.5 G/S Digital Scope	£1500
PM3394B/084	4 Channel 200 MHz Combiscope	£3250
MATSU		
6612	60 MHz Oscilloscope	£350
8606C	60 MHz Oscilloscope	£250
8608	100 MHz Oscilloscope	£300
LECROY		
9314AM	4 Channel 300MHz Oscilloscope	£3000
TEKTRONIX		
TDS 3014	100MHz GSM 4 Channel DPO with battery	£2450
TDS3014	100 MHz GSM 4 Channel DPO (no battery)	£2250

POWER SUPPLIES

AGILENT TECHNOLOGIES (HP)		
E3632A	15V/7A, 30V/4A Single Output	£450
APC		
Smart UPS600	600W backup PSU	£450
EMERSON		
1000 GX5	UPS	£250
2500 GX5	UPS	£450
GXT 2000	2 KVA on line UPS	£600
FARNELL		
PDD3010A	Power Supply	£300
FLUKE		
PM2832/014	60V / 2A Dual DC PSU	£975
MERIN GERIN		
Prowatt 1500I	12V DC to AC Power Inverter	£300
PULSAR		
ESV20 2KVA	UPS	£550
THURLBY THANDAR		
CPX200	Powerflex Dual O/P PSU	£400
PL3300DP	Dual PSU 0-32V 0-3A	£350

VOLTMETERS & MULTIMETERS

FLUKE		
87	Digital Handheld Multimeter	£220

RECORDERS & DATA ACQUISITION

ASTROMED		
Dash TV	4 Channel Thermal Array Recorder	£3000
GRAPHTEC		
WR8000-16	16 Channel Thermal Array Recorder	£3750
WR8000-8	8 Channel Thermal Array Recorder	£2750
WR8500	8 Channel Thermal Recorder	£4000
WR9000	8 Channel Thermal Recorder	£5950
YOKOGAWA		
DL-708	8 Channel Recorder	£3750
LR4100/25	2 Channel Recorder with Disk Drive	£1750
LR4100 /35	3 Channel Recorder with Disk Drive	£2250
LR4100/45	4 Channel Chart Recorder	£2500
OR-341	4 Channel Handy Recorder	£2000

ELECTRICAL & POWER

GRANITEZ		
PP1	Power Platform PQ plus Mains Analyser	£6500
HARVEY		
5000	3 Phase Power Demand Analyser	£1950
KITHLEY		
2000	Multimeter	£550
MEGGER		
D7001	'Ducter Digital Ohm Meter	£1250

ANALYTICAL & ENVIRONMENTAL TEST

AIRFLOW DEVELOPMENTS		
AV2	Vane Anemometer	£400
BRUEL & KJAER		
2231M	Precision Sound Level Meter	£1900

 **Livingston**

www.livingston-europe.com

Accurate recruitment information when you need it.

Simple Really.

now to go .

ut our comprehens
g a vast archive of
regularly, the r

peractive .

Jobs

Our appointments service is
online electronics engineer
market



Free Career H
Electronics Wee
HyperActive ha
with the online
service totaljob
its users a F



http://
ELECTRONICS
WEEKLYonline

Upd.
• In
• M



Contract



Every week HyperActive ha
contract vacancies that are
anywhere else! Click the lo
search screen and choos
"Job Type." field.



ElectronicsWEEKLY

HyperACTIVE

www.electronicweeklly.co.uk

Executive Recruitment Services plc



Manufacture and Test

Email: nathan@soljobs.com Website: www.soljobs.com
Solution Technical Recruitment, The Tower House,
High Street, Aylesbury, Bucks. HP20 1SQ
Tel: 01296 336036 Fax: 01296 336037

MANUFACTURING ENGINEER

North West circa £28k + Bonus

One of the UK's foremost communications companies is looking to recruit Manufacturing Engineers working with the most advanced telecommunications products. You will be responsible for the introduction or new product and the development of the PCBA processes by investigating and introducing new equipment, materials and the latest processes. The ideal candidate will have a good working knowledge of SMT processes and machines as well as being able to problem solve and implement process improvements in a high volume manufacturing environment incorporating small and major step improvements. Ideally you will have at least an HNC in a manufacturing discipline or electronics, but experience and a proven track record within the industry is essential.

AVIONICS TECHNICIAN

Northern Home Counties circa £24k + O/t + Bonus

This Avionics service centre based near Heathrow has repair, overhaul, modification and transcription capability, backed with engineering support and training facilities. They currently are looking to recruit three experienced avionic technicians ideally with a minimum five years in the repair to component level of airborne navigation, communication and radar products. The right candidates can expect to earn an excellent salary as well as O/t, AOG Bonus and Life Assurance.

MAINTENANCE TECHNICIAN

Middlesex up to £24k

Our client develops and licenses novel LCD technologies and creates advanced optoelectronic products and solutions. A vacancy has now arisen for a Cleanroom Maintenance Engineer to support the continued growth of their product and service sales. The key responsibility will be to maximise the uptime of fabrication facilities and equipment, which is likely to involve management of service contractors, first-line trouble shooting and repair as well as routine testing and maintenance. The role will involve working with vacuum deposition, air-conditioning and other electro-mechanical systems. The successful applicant will ideally have experience of preventative maintenance and repair in a production environment, although field service experience would also be considered. This experience should have been gained over a minimum of five years. Experience of working in a cleanroom environments is highly desirable.

These are just a few of our current permanent opportunities, for more details on these and other positions call Nathan Davis for an informal discussion



Hardware

Email: jamesc@soljobs.com Website: www.soljobs.com
Solution Technical Recruitment, The Tower House,
High Street, Aylesbury, Bucks. HP20 1SQ
Tel: 01296 336036 Fax: 01296 336037

ANALOGUE ELECTRONICS ENGINEER

Cambridgeshire £ Excellent + Benefits + Stock

This consultancy spin-out is looking for an analogue electronics engineer with a broad experience of designing in analogue electronics to work in an exciting new field. Previous experience could include power supply design, DC-DC converter design, control and servo system design. The interfacing of electronic and/or electro-mechanical systems to microprocessor based control systems is a must. Being used to designing high performance electronics for aggressive cost control will be vital as will being used to working unsupervised on your own as well as being part of a very committed team. The rewards are superb (relocation available) as is the technology involved.

Ref: 4909

SENIOR HARDWARE ENGINEER

Yorkshire up to £40k + Benefits + Stock

This market leading client requires senior engineers to work on design, test and approvals of hardware for Advanced Set Top Boxes. Experience of Embedded Microprocessors and design issues such as Design for Manufacture and EMC constraints, as well as Board-Level Layout, Schematics and Analogue Design. Educational requirements B.Sc/HND in Electronics or similar with postgraduate experience required. Essential technical requirements: Microprocessor hardware - memory etc, High Speed Digital board level design (interfacing, loading, tracking, decoupling), board debug/commissioning/trouble shooting, some analogue design. Additional skills: RISC, CPUs eg Hitachi, MIPS ARM, Modem, xDSL, cable hardware, Ethernet hardware, Power supplies, Verilog schematic capture tools, Design for Manufacture, EMC, High Volume, Wireless technology eg DECT. Get involved with the best and get well rewarded in salary and benefits (relocation available)

Ref: 2108

SENIOR AND JUNIOR FPGA DESIGN

Hampshire £ Superb + Benefits

This well established company currently has a vacancy for electronics design engineers to design high function Field Programmable Gate Arrays (FPGAs) including functions such as data processing, pattern recognition, memory management and PCI implementation. Experience required junior 18 months+ (superb training available), senior 4 years+ of electronics and ASIC or FPGA development experience. Also high speed logic design skills using VHDL, ability to communicate well within a small, highly skilled team, ability to estimate accurately time required to develop and debug FPGA designs and to work to aggressive time scales. Experience useful of network technologies, including one or more of the following: Gigabit Ethernet, Fast Ethernet, ATM, SONET. Excellent rewards and benefits.

Ref: 2562

OPPORTUNITIES, OPPORTUNITIES, OPPORTUNITIES, OPPORTUNITIES

None of the above appeal? If you are a Hardware Engineer then I have a wide range of opportunities in the UK and Republic of Ireland, one of which could be the one for you and your career. Telephone or email me with details of what you want and leave the rest to me. This is a free service to you.



Software

Email: mayurr@soljobs.com Website: www.soljobs.com
Solution Technical Recruitment, The Tower House,
High Street, Aylesbury, Bucks. HP20 1SQ
Tel: 01296 336036 Fax: 01296 336037



Test and Development

Email: jimmy@soljobs.com Website: www.soljobs.com
Solution Technical Recruitment, The Tower House,
High Street, Aylesbury, Bucks. HP20 1SQ
Tel: 01296 336036 Fax: 01296 336037

SENIOR APPOINTMENT - HEAD OF UMTS DEVELOPMENT

Central London £ Outstanding + Benefits

A dynamic and fast moving organisation, with an impeccable reputation with the digital audio broadcast market, is seeking a high calibre candidate to become Head of UMTS Development. You will lead a team of development staff, and take responsibility for the quality and functionality of assigned software products from initial concept to customer delivery. A strong management background is crucial, along with a minimum exposure period of six years to project life cycles and project scheduling. A degree in computer science, engineering or mathematics is required with a minimum 2:1 pass. You will have related software development experience in C++, real-time, COM, UML, OOAD and have experience of digital communications. Salary and package will reflect this senior position.

Ref: 4328

DSP SOFTWARE ENGINEERS

Hertfordshire £ Market Leading + Benefits Package

This outstanding organisation designs and manufactures a range of products that exploit wireless GSM technology. Due to their rapidly growing client base and respectability, they currently require DSP Software Engineers with ambition, self motivation and the hunger to rise to new challenges. Experience in developing and debugging real-time systems is essential, along with at least one year's practical use of DSP assembler language (not just using C compiler), two plus years practical use of C++ is also essential, along with familiarity with DOS/Windows/scripting languages (eg PERL). Basic knowledge of digital hardware, good knowledge of Digital Signal Processing Theory (Nyquist sampling, GSMK Modulation, Channel Coding, etc.) and DSP algorithm design (preferably in communications systems) will be required to succeed. Market leading salaries and packages will be offered to the successful applicants.

Ref: 4424

PROTOCOL CONSULTANT

Cambridgeshire £50-100k + Benefits

An excellent opportunity within a dynamic and fast moving company with a distinct vision of the future of mobile communications. An exceptional engineer is required, who has been exposed to the latest technologies such as GSM, GPRS, WAP, UMTS and Bluetooth. You will have at least 10 years strong C coding experience in a product development environment, along with design/implementation using RTOS for multi-tasking applications, experience of GSM/GPRS/UMTS protocol type approval process, use of SDL and message sequence charts, direct experience of L2 and L3 mobile comms protocols. This senior position will be challenging as you will have complete technical authority on the requirements, architecture, design and implementation of L2/L3 GSM/GPRS/UMTS terminal protocols.

Ref: SMRU

These are just a handful of our current opportunities for Sales, Marketing and Applications professionals. For more information and an informal discussion please contact Andrew Raymond on 01296 336036 or e-mail him at andy@soltech.co.uk

TECHNICAL AUTHOR

Yorkshire £ Excellent

This leading Telecommunications Company are looking for a Technical Author. The ideal candidate will prepare technical customer documentation for new products for both conventional publishing (user manuals) and web distribution. To maintain and update existing documentation, prepare technical documentation for internal use in sales, marketing and service. To prepare and maintain graphic and text source database. The candidate should have a degree in a technical field (electrical engineering, electronics, telecommunications, physics, computer science) or two years equivalent experience. He/she should have excellent communication skills, a working knowledge of office and drawing applications in the Windows environment, using tools such as Adobe FrameMaker and Corel Draw. The candidate must be prepared to travel occasionally in Europe. An excellent salary and career prospects are on offer.

TEST DEVELOPMENT ENGINEER

South Wales £ Excellent

Our client develops and manufactures leading edge technology Power Amplification products for the wireless telecommunications arena. They are looking for a Test Development Engineer with a minimum of five years experience in the Test Development field, which should have included creating test specifications and general test documentation, producing test systems and integrating them into production. Designing for test Labview/LabWindows programming with supporting documentation. The candidate should have working knowledge of RF (instrumentation field would be best) and should be strong willed, self motivated with an ability to work unsupervised. An excellent package and salary is on offer.

VALIDATION ENGINEER

Berkshire £ Excellent

Our client specialises in the Semiconductor Industry and is currently looking for a Validation Engineer. The ideal candidate will need at least five years experience in a role with exposure to complex digital hardware products, such as microprocessors or DSP devices, and their associated software tools. Knowledge of complex simulation techniques and tools is essential. He/she should have knowledge of configuration management techniques, emulation technology, programming in high and low level languages although this is not essential. The candidate should have a degree in either Electronics or a Computing subject, but if a degree is attained in a different subject, then the degree must be of a higher pass. The candidate must also be prepared to travel. This will suit a person seeking a role that requires a mix of hardware and software skills, applied in a company that is developing the latest microprocessor and compiler technologies. The candidate should be flexible and pragmatic, with good attention to detail. An excellent salary and package is on offer for this challenging and prosperous role.

These are just a few of our current permanent opportunities, for more details on these and other positions call Jimmy Fletcher for an informal discussion.

Submerge yourself in a role with a difference

Analogue Electronics Design Engineer · Competitive package · Hainault

Kelvin Hughes, the marine and naval arm of the Smiths Group plc, is internationally renowned for pioneering developments in navigational technology. With naval and commercial marine customers worldwide, we provide a range of products from integrated bridge systems, nautical charts and books to navigational radar and radio communications systems. We are now looking for a talented and experienced professional to take on the rare role of Analogue Electronics Design Engineer.

A proven RF all-rounder, with 5 years' experience in analogue design, you will bring with you an in depth grounding in one of the following:

- 60MHz IF log receivers.
- Magnetron modulators.
- CRT-based display monitors.
- Solid-state motor control.

Your reward will be a role with considerable latitude in this field and genuine opportunity to broaden your horizons. We are talking about a remit that includes Production and Marine Services support,

financial and technical project management, analogue advice on future developments, general technical support to other RF services and key costing proposals.

On a personal level, you will bring high levels of initiative, time management and teamwork. The last of these is particularly important in light of our new value-streaming work patterns where fluid multi-divisional groups are set up to learn from each other.

In addition to the opportunity to drive what is a truly unique and dynamic position, we are offering excellent prospects for progression, together with a competitive rewards package.

To apply, please write with your CV, to: Margaret Bundy, HR Department, Kelvin Hughes, New North Road, Hainault, Ilford, Essex IG6 2UR.

Closing date: 19th April 2001.

For more information please visit our website at www.kelvinhughes.co.uk

We positively welcome applications from suitably qualified individuals irrespective of racial origin, sex or disability.

KELVIN HUGHES

Kelvin Hughes Limited is the Naval and Marine Division of Smiths Aerospace

The Success is Yours

Hardware & Optical

ASIC Consultants

Berks/Bristol to £60K
UK base and multi national links. Design of digital and mixed signal ASIC plus application engineering. Travel to USA. Knowledge of Mentor useful. Bonus, relocation and several company perks.
email: gordon_short@ers.co.uk
Ref: GS1400

Project/Principal RF Engineers

Glos/Avon/Cambs £30-50K
Real engineering - not packaging! Let your design skills roam over several projects from miniature transmitters to satellite systems. Excellent conditions and housing in an attractive and low cost area.
email: gordon_short@ers.co.uk
Ref: GS1402

High Speed Optical Design Engineers

Northampton/London/Oxford/Southampton to £45K+
You will be responsible for the organisation, planning and control of the technical development of applications and test methods for Optoelectronic Components and Sub Systems. Experience of Opto components in systems, electronics and circuit design plus a good understanding of modern wideband Optical layout and simulation tools and advantage. Superb opportunity at this multi national.
email: paul_gurney@ers.co.uk
Ref: PG1401

III-V Device Technology Specialist

Northampton/E Anglia/Oxford to £40K+
With experience of III-V process technology you will take the lead role in developing new processes and will support new and exiting R&D projects. Great benefits, internal opportunities, relocation and stock options.
email: paul_gurney@ers.co.uk
Ref: PG1403

Telephone/fax/email CV's to:

Gordon direct tel: 01442 847426 Paul direct tel: 01442 847468



ERS Communications

at..... ERS Communications

575-599 Martlet Road, Hemel Hempstead, Herts HP2 7DX
Fax: 01442 215486

website: www.ers.co.uk/communications

ERS Communications is a member of the Executive Recruitment Services plc group of companies



Cheltenham Induction Heating Limited

We require a

POWER ELECTRONICS DEVELOPMENT ENGINEER

who has experience of medium to high power switching applications (like SMPS, motor drives and induction heating).

Duties will include:-

- New product conception
- Turn the concept into reality
- Design and test of prototype circuits
- Evaluate and debug pre-production design
- Development of existing technology

Reporting:- As a key member of the Development Team, the Development Engineer will be directly responsible to the Group Technical Director.

Salary:- >£25k depending on experience and ability.

Location:- Cheltenham (relocation assistance if appropriate).

C.I.H. Ltd manufacture high power, load resonant inverters (induction heaters). We have a worldwide reputation for supplying quality products for use in industrial, scientific and medical applications.

We have licensing agreements in several countries, including the USA, whereby products of our design are manufactured under our license.

We use FET and IGBT power technology typically working in the 3kHz to 1MHz range and we produce equipments with continuous output powers of one kW to hundreds of kW's.

In the first instance, please send a current CV and covering letter to Andy Davies, Managing Director of:

Cheltenham Induction Heating Ltd
Saxon Way, Battledown Industrial Estate, Cheltenham,
Gloucestershire GL52 6RU
www.cih-group.co.uk

As an advertiser you can be certain that your sales message is going to be read by decision-making electronics professionals with the power to purchase your products.

Service

Link

The pre-paid rate for semi-display setting is £17 per single column centimetre (maximum 4cm). Box number £22 extra. All prices plus 17½% VAT. All cheques, postal orders etc to be made payable to Reed Business Information. Advertisements together with remittance should be sent to Electronics World Classified, 12th Floor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.
Fax: 0208 652 3981. Tel: 0208 652 8339

ARTICLES WANTED

TOP PRICES PAID

For all your valves, tubes, semi conductors and ICs.

Langrex Supplies Limited

1 Mayo Road, Croydon, Surrey CR0 2QP
TEL: 020 8684 1166 FAX: 020 8684 3056

Rack Enclosures
 New and Used most sizes
 16U to 50U side and rear panels
 mains distribution 19" Panel mounts
 optima eurocraft. Prices from £45 +vat

M&B Radio
 86 Bishopsgate Street Leeds LS1 4BB
 Tel. 0113 2702114 Fax. 0113 2426881

PRINTED CIRCUIT BOARDS DESIGNED & MANUFACTURED

- Prototype or production quantities
- Fast turnround available
- PCBs designed from circuit diagrams
- Almost all computer files accepted
- PCB assembly - mechanical assembly
- Full product design-manufacture-test-repair

agar TEL 028 9073 8897
 Circuits FAX 028 9073 1802
 agar@argonet.co.uk
 Unit 5, East Belfast Enterprise Park
 308 Alberbridge Rd, Belfast BT5 4GX

POWER SUPPLY DESIGN

Switched Mode PSU
 Power Factor Correction
designed to your specification

Tel/Fax: 01243 842520
 e-mail: eugen_kus@cix.co.uk
Lomond Electronic Services

BEST CASH PRICES PAID

For all valves KT88
 PX4 and other audio types
 Wide range of valves and CRT
 stocked

Tel: 01403 784961

Minimum Order UK -
 £50+VAT+Freight

Billington Export Ltd. Fax: 01403 783519
 Email: sales@bel-tubes.co.uk
 Sussex RH14 9EZ Visitors by appointment

SERVICES

From **Concept** 48 HOUR SERVICE
 To **Production**

Electronic design and engineering services for the new millennium:

- Embedded control
- Telecommunication products
- Datacommunication products
- SM PSU and battery management
- Wireless transmission systems
- Audio and Video processing
- DVD control systems
- Internet site and graphics authoring
- PCB design
- Schematic layout and re-drawing
- Technical documentation & translation

Tel/Fax: +44 (0) 1872 223306
 Email: sales@designersystems.co.uk

Microchip Consultant Program Member

Designer Systems

see our web site @ <http://www.designersystems.co.uk>

As an advertiser you can be certain that your advertisement is going to be read by **DECISION-MAKING ELECTRONIC PROFESSIONALS**

with the **POWER TO PURCHASE** your products

Why not let **Electronics World** help you?

Call Pat Bunce

Tel: 020 8652 8339

Fax: 020 8652 3981

E-mail: patbunce@rbi.co.uk

LINEAGE

ROTEK 6000 AC/DC Multi meter calibrator together with 50 amp adaptor and manual. Also time DC voltage calibrator 20035. Tel: 0116 244 2211 days. 0116 288 4184 evenings.

P&P ELECTRONICS, Prototype Electronic System Designs by degree qualified staff. Tel: 01924 402931.

ELECTRONIC UPDATE

HIOKI
 8807-01, 8808-01 MEMORY RECORDER



CE

New Coverage with Data/Hubb Printer
 B5-Sized Handy-Recorder with Color Display

Hioki's New 8807/8808 Memory Recorder

These compact, light recorders have 2 or 4 analogue channels with isolated inputs, PC card slot, fax/modem communication function, versatile trigger functions and 3-way power. They are ideal for a variety of applications requiring long memory lengths and high transient speed capability.

Telonic Instruments Ltd
 Tel: 0118 978 6911
 Fax: 0118 979 2388

CIRCLE NO.126 ON REPLY CARD

**DAQ Designer™
 2001**




National Instruments new **DAQ Designer™ 2001** is a FREE CD that helps engineers and scientists interactively configure custom measurement systems. **DAQ Designer™ 2001** includes the capability to recommend real-time data acquisition and motion control hardware and software.
 Phone: 01635 523545
 Fax: 01635 524395
 E-mail: info.uk@ni.com
 Web: www.ni.com/uk

CIRCLE NO.127 ON REPLY CARD



SUPPLIER OF QUALITY USED TEST INSTRUMENTS

OPERATING & SERVICE MANUALS

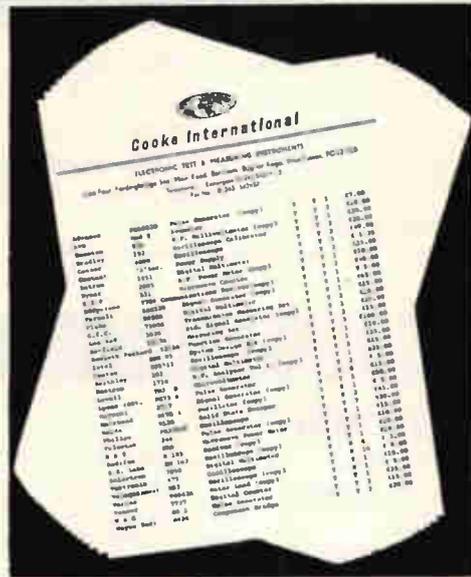

NEW
Address and
Contact Numbers
1st March 2001


**Cooke
International
Second User
ELECTRONIC
TEST AND
MEASURING
INSTRUMENTS**

Unit 9,
Ford Lane
Business Park,
Ford, Arundel,
West Sussex
BN18 0UZ, UK
Tel:
(+44) 0 1243 555590

Fax:
(+44) 0 1243 551455

E-Mail:
info@cooke-int.com

Web:
http://www.cooke-int.com

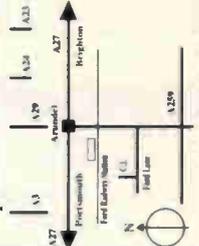

CIRCLE NO. 128 ON REPLY CARD

ADVERTISERS' INDEX

ADEPT SCIENTIFIC.....	343	LIVINGSTON.....	403
BETA.....	329	MILFORD INST.....	361
CONFORD ELEC.....	325	PICO.....	329
COOKE INTERNATIONAL.....	408	QUICKROUTE.....	322
CRICKLEWOOD.....	371	RAMCO.....	325
CROWNHILL.....	349	RD RESEARCH.....	322
DATAMAN.....	OBC	SEETRAX.....	371
DISPLAY ELECTRONICS.....	373	SIGHTMAGIC.....	325
EPTSOFT.....		STEWART OF READING.....	343
INTEC ASSOCIATES.....	329	SURREY ELECTRONICS.....	371
JOHNS RADIO.....	365	TELNET.....	IFC
JPG ELECTRONICS.....	361	TEST EQUIP SOLUTIONS.....	339
LABCENTER ELECTRONICS.....	375	TIE PIE.....	399
LANGREX.....	361	WEB PAGES.....	400, 401, 402

For more information about any of the products or services in this issue of **ELECTRONICS WORLD**, simply ring the relevant enquiry number. Enquiry numbers may be found at the bottom of each individual advertisement.

101 102 103 104 105 106 107 108 109 110 111
112 113 114 115 116 117 118 119 120 121 122
123 124 125 126 127 128 129 130 131 132 133
134 135 136 137 138 139 140 141 142 143 144
145 146 147 148 149 150

500 501 502 503 504
505 506 507 508 509 510 511 512 513 514 515
516 517 518 519 520 521 522 523 524 525 526
527 528 529 530 531 532 533 534 535 536 537
538 539 540 541 542 543 544 545 546 547 548
549 550 551 552 553 554 555 556 557 558 559
560 561 562 563 564 565 566 567 568 569 570
571 572 573 574 575 576 577 578 579 580 581
582 583 584 585 586 587 588 589 590 591 592
593 594 595 596 597 598 599 600

Name	_____
Job title	_____
Company Address	_____ _____ _____
Telephone	_____
Only tick here if you do not wish to receive direct marketing promotions from other companies. <input type="checkbox"/>	

MAY 2001

Newsagent order form

Pass this order form to your newsagent to ensure you don't miss the next issue of *EW*.

To.....
(name of Newsagent)

Please reserve me the June issue of *Electronics World* and continue to order every month's issue until further notice

Name.....

Address.....
.....
.....

Thank you

Subscribe today!

Guarantee your own personal copy each month

Save on a 2 year subscription

Subscribe today!

Guarantee your own personal copy each month

Save on a 2 year subscription

Postage will be paid by licensee

Do not affix postage stamps if posted in Gt. Britain, Channel Islands, N. Ireland or the Isle of Man.

Business Reply Service
Licence No. CY711

ELECTRONICS WORLD
Reader Information Service
Reed Business Information
Oakfield House
Perrymount Road
Haywards Heath
Sussex RH16 3BR

SEE OVER!



ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD

SUBSCRIPTION CARD

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ _____ made payable to Reed Business Information
Please charge my Mastercard/Visa/Amex account

With £ _____ Expiry Date _____

Signature _____

Name _____

Job Title _____

Address _____

Postcode _____

Tel: _____ Country _____

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
Airmail	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:
ELECTRONICS WORLD
P.O. Box 302
Haywards Heath,
West Sussex RH16 3DH UK.

CREDIT CARD HOTLINE
Tel: +44 01444 445566
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing/promotion from other companies

ELECTRONICS WORLD

INCORPORATING WIRELESS WORLD

SUBSCRIPTION CARD

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ _____ made payable to Reed Business Information
Please charge my Mastercard/Visa/Amex account

With £ _____ Expiry Date _____

Signature _____

Name _____

Job Title _____

Address _____

Postcode _____

Tel: _____ Country _____

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
Airmail	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:
ELECTRONICS WORLD
P.O. Box 302
Haywards Heath,
West Sussex RH16 3DH UK.

CREDIT CARD HOTLINE
Tel: +44 01444 445566
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing/promotion from other companies

'Electronics and Computing Principles V7'

'95, '98, NT or 2000 Principles V7'

Studying electronics or computing or just want to keep up-to-date in a easy and enjoyable way, then this fully interactive software is for you.

Visit eptsoft.com or telephone for full details of more than a thousand menu items.

Electronics:-

Atomic Structures, DC Current flow, Basic Electronics, Simple DC Circuits, Types of Switching, Variable Voltages, Ohm's Law, DC Voltage, AC Current, Series/Parallel Resistors, AC Measurements, AC Voltage and Current, AC Theory, RCL Series/Parallel Circuits, Capacitance, Inductance, Inductors, Impedance, Communication System, Signals, Attenuators, Passive/Active Filters, Tuned Circuits, Coupling and Selectivity, Oscillators, Circuit Theorems. Diode Theory, Diode Applications, Transistor Theory, Bipolar Transistor, Transistor Configurations, Transistor Circuits, Field Effect Transistors, Operational Amplifier Theory and Applications, Sum and Difference Amplifiers.

Electrical:-

DC and AC Power, SCR, Power Supplies, Voltage Regulators, Magnetism, Motors/Generators, Transformers, Three Phase Systems.

Digital Techniques:-

Logic Gates, Flip Flops, Combinational Logic, Counters, Counting, Shift Registers, Logic Interfacing, Timers, Boolean Algebra and DeMorgan's Theorems.

Microprocessors and PIC Microcontrollers:-

Basic Micro Computer, Busses, A.L.U, Clock and Reset, Instructions and Memory Cells, ROM and RAM, Memory Addressing, Applications, PIC Introduction, PIC16F84 Architecture, PIC16C71 A/D, I/Os, Bit, Literal and Control Instructions.

eptsoft limited. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.
Tel: +44 (0)1376 514008. Fax: +44 (0)870 0509660. Email: info@eptsoft.com.

Switch, Delta, Visa and MasterCard accepted.

No additional postage or airmail charges.

Personal user £99.95 +VAT
Education £299.95 +VAT
(Includes unlimited multi-user site licence.)

Measurement and Component Testing:-

Analogue multi-meter, Measurement, Component Testing.

Mathematics:-

Simple Numbers, Number Types, Roots, Triangle Ratio's, Triangle Angles, Area, Surface Area and Symmetry, Volume, Percentages, Ratio's, Fractions, Vectors, Circle Angles, Laws, Algebra Rules, Powers, Simplifying, Equations, Graphing, Slope and Transitions, Angles, Complex Numbers, Statistics, Lottery Number Prediction, Physical Science.

Computer Science:-

Hardware Devices, Data Structures, Data Files, Binary Numbers, Binary Arithmetic.

Toolbox:-

DC Calculations, AC Calculations, Numbers, Applications.

Self-Assessment Questions:-

DC, AC, Power, Semi-Conductors, Op-Amps, Digital, Mathematics.


Components and Equipment Picture Dictionary:-

High quality digital camera images and explanatory text.

ELECTRONICS LAB (Optional add-on hardware).

STILL THE WORLD'S MOST POWERFUL PORTABLE PROGRAMMERS?

£495+VAT

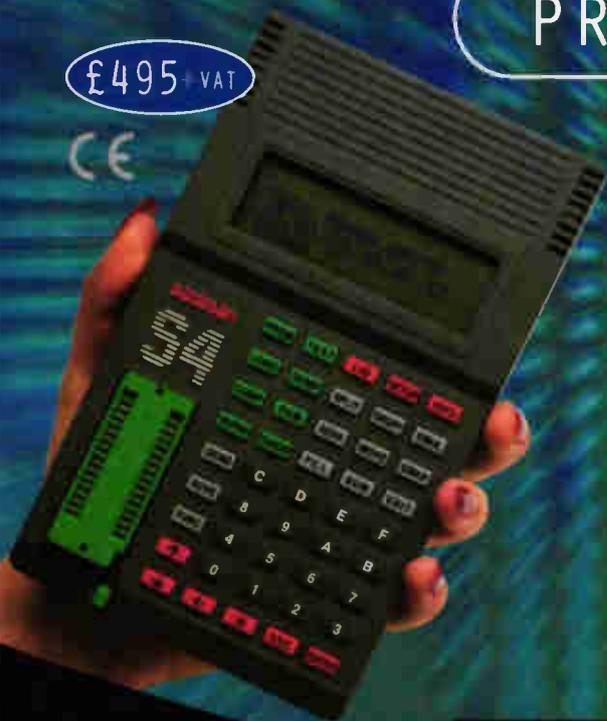

NEW MODEL



£795+VAT

SURELY NOT.
SURELY SOMEONE SOMEWHERE HAS
DEVELOPED A PORTABLE PROGRAMMER
THAT HAS EVEN MORE FEATURES, EVEN
GREATER FLEXIBILITY AND IS EVEN
BETTER VALUE FOR MONEY.

ACTUALLY, NO. BUT DON'T TAKE OUR
WORD FOR IT. USE THE FEATURE
SUMMARY BELOW TO SEE HOW OTHER
MANUFACTURERS' PRODUCTS COMPARE.

DATAMAN - 48LV

- Plugs straight into parallel port of PC or laptop
- Programs and verifies at 2, 2.7, 3.3 & 5V
- True no-adaptor programming up to 48 pin DIL devices
- Free universal 44 pin PLCC adaptor
- Built-in world standard PSU - for go-anywhere programming
- Package adaptors available for TSOP, PSOP, QFP, SOIC and PLCC
- Optional EPROM emulator

DATAMAN S4

- Programs 8 and 16 bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 microcontrollers and more
- EPROM emulation as standard
- Rechargeable battery power for total portability
- All-in-one price includes emulation leads, AC charger, PC software, spare library ROM, user-friendly manual
- Supplied fully charged and ready to use

S4 GAL MODULE

- Programs wide range of 20 and 24 pin logic devices from the major GAL vendors
- Supports JEDEC files from all popular compilers

SUPPORT

- 3 year parts and labour guarantee
- Windows/DOS software included
- Free technical support for life
- Next day delivery - always in stock
- Dedicated UK supplier, established 1978

Still as unbeatable as ever. Beware of cheap imitations. Beware of false promises. Beware of hidden extras. If you want the best, there's still only one choice - Dataman.

Order via credit card hotline - phone today, use tomorrow.

Alternatively, request more detailed information on these and other market-leading programming solutions.

MONEY-BACK 30 DAY TRIAL

If you do not agree that these truly are the most powerful portable programmers you can buy, simply return your Dataman product within 30 days for a full refund

hotline
01300 320719



Orders received by 4pm will normally be despatched same day.
Order today, get it tomorrow!

DATAMAN

Dataman Programmers Ltd, Station Rd,
Maiden Newton, Dorchester,
Dorset, DT2 0AE, UK
Telephone +44/0 1300 320719
Fax +44/0 1300 321012
BBS +44/0 1300 321095 (24hr)
Modem V.34/V.FC/V.32bis
Home page: <http://www.dataman.com>
FTP: [ftp.dataman.com](ftp://ftp.dataman.com)
Email: sales@dataman.com