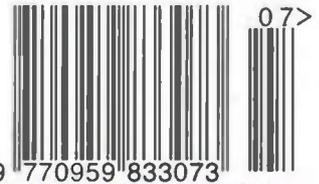


Special offer - 600W audio amp module!

ELECTRONICS WORLD

ISSN 0959-8332



9 770959 833073

JULY 2001 £2.80

Phase-shifting digital sig gen

**EMI tips
and fixes**


**Pseudo
random bits**

**Colliding
capacitors**

**Writing code
for DSP**

Circuit ideas:

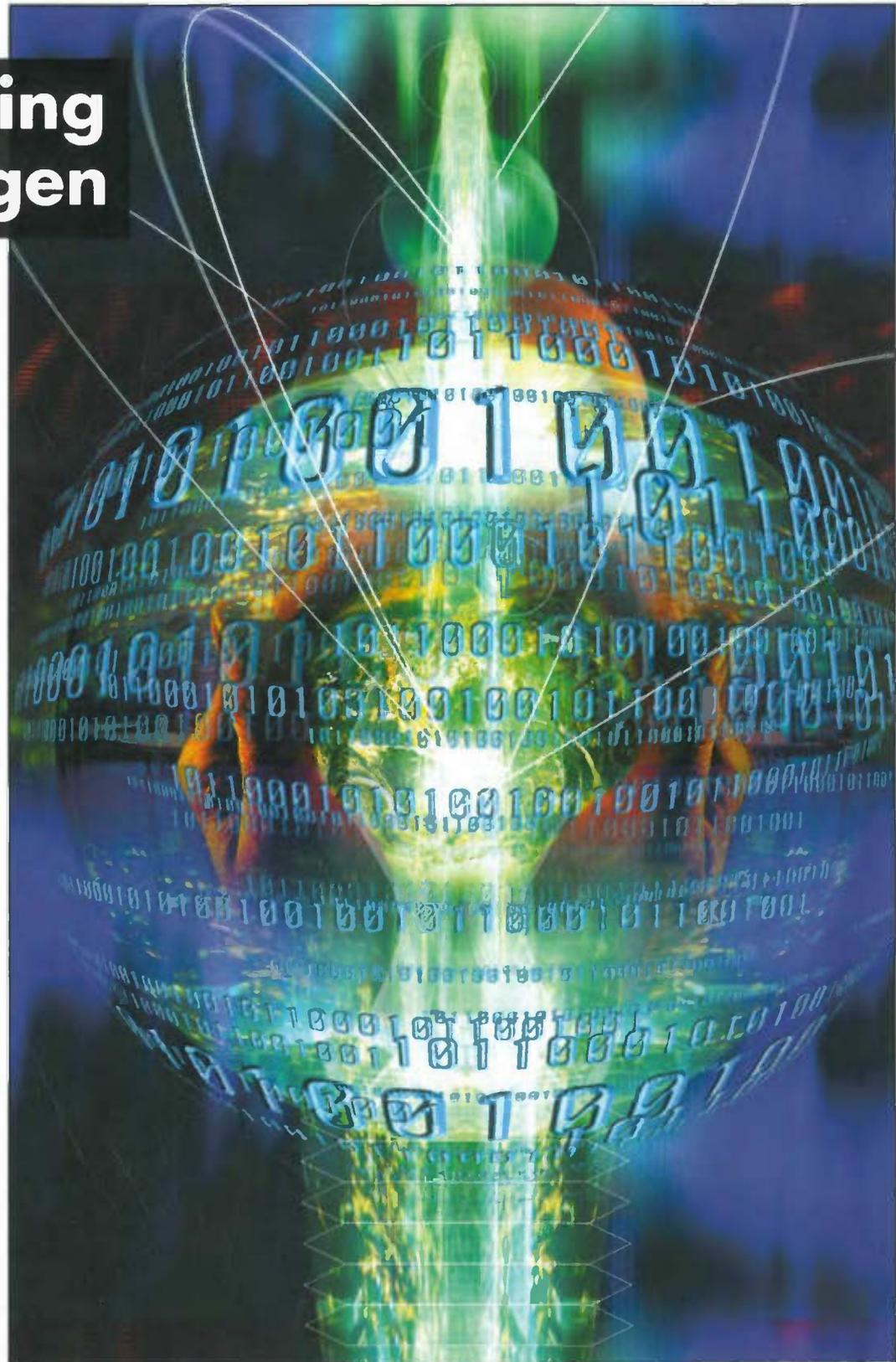Mains glitch detector
Phase shifter
Step motor PC
interface
Sweep enhancer
Microcurrent
amplifier
3-phase indicator
Serial keypad
interface



Telnet


Tel: 02476 650702

Quality second-user test & measurement equipment

NEW PHONE CODE FOR COVENTRY 02476

Radio Communications Test Sets

Marconi 2955	£1500
Marconi 2955B/60B	£3995
Marconi 2955A	£2000
Marconi 2955R	£2200
Marconi 2945 Comms service monitor	£4500
Anritsu MS55A2	£1200
Hewlett Packard 8922B (GSM)	£4000
Hewlett Packard 8920A (opts 1,2,3,4,5,11)	£5250
Hewlett Packard 8920B (opts 1,4,7,11,12)	£7250
Hewlett Packard 8922M	£6000
Schlumberger Stablock 4031	£3500
Schlumberger Stablock 4040	£1500
Racal 6111 (GSM)	£1750
Racal 6115 (GSM)	£3995
Rhode & Schwarz CMTA 94 (GSM)	£4995
Rhode & Schwarz CMT 55 (2GHz)	£8000
Rhode & Schwarz CMT 90 (2GHz) DECT	£4995
Wavetek 4103 (GSM 900) Mobile phone tester	£1500
Wavetek 4106 (GSM 900, 1800, 1900) Mob. Phone tester	£2200

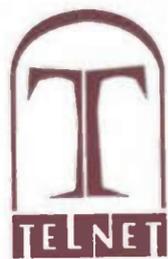

Fax 02476 650 773

MISCELLANEOUS

Eaton 2075-2A - Noise Gain Analyser	at £2750
EIP 548A 26.5GHz Frequency Counter	£1995
ENI 440LA (150KHz-300MHz) 35 Watt Power Amp	£2500
ENI 1040 (10KHz-500KHz) 400 Watt Power Amp	£2750
Fluke 5100A/5100B/5200A - Calibration Units (various available)	from £1000
Fluke 2620 Data Buckets	£500
Fluke 45 Dual Display W/meter (IEEE)	£550
Hewlett Packard 339A Distortion measuring set	£1200
Hewlett Packard 778D Dual-Directional Couplers	£650
Hewlett Packard 3488A - Switch/Control unit	£250
Hewlett Packard 3457A multi meter 6 1/2 digit	£950
Hewlett Packard 3784A - Digital Transmission Analyser	£4500
Hewlett Packard 3785A - Jitter Generator & Receiver	£1250
Hewlett Packard 5385A - 1 GHz Frequency counter	£650
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6622A - Dual O/P system p.s.u.	£1250
Hewlett Packard 6624A - Quad Output Power Supply	£2000
Hewlett Packard 6632A - System Power Supply (20v-5A)	£800
Hewlett Packard 8350B - Sweep Generator Mainframe	£1500
Hewlett Packard 8656A Synthesised signal generator	£850
Hewlett Packard 8656B Synthesised signal generator	£1250
Hewlett Packard 8657A Synth. sig. gen. (0.1-1040MHz)	£1750
Hewlett Packard 8901B - Modulation Analyser	£2750
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1250
Hewlett Packard 16500A + B - Logic Analyser Mainframes	from £1000
Hewlett Packard 16501A/B & C - Logic Analyser System Expander Frame	from £2000
Hewlett Packard 37900D - Signalling test set	£3750
Hewlett Packard 83220A DCS/PCS test sets	£3000
Hewlett Packard 8657B - 100KHz-2060 MHz Sig Gen	£3995
Hewlett Packard 8657D - XX DQPSK Sig Gen	£3995
Hewlett Packard 8130A - 300 MHz High speed pulse generator	£4500
Hewlett Packard 4275A LCR Meter (10KHz-10MHz)	£2520
Hewlett Packard 4276A LCR Meter (100Hz-20KHz)	£3250
Marconi 1066B - Demultiplexer & Frame Alignment Monitor (140MBIT to 64KBIT)	£1500
NEW	
Marconi 2305 - modulation meter	£1750
Marconi 2610 True RMS Voltmeter	£999
Marconi 6950/6960/6980B Power Meters & Sensors	£550
Marconi 2840A 2MB/s Transmission Analyser	from £400
Philips 5515 - TN - Colour TV pattern generator	P.O.A.
Philips PM 5193 - 50MHz Function generator	£1400
Leader 3216 Signal generator 100KHz - 140MHz - AM/FM/CW with built in FM stereo modulator (as new) a snip at	£1500
Racal 1992 - 1.3GHz Frequency Counter	£795
Rhode & Schwarz NRV dual channel power meter & NAV Z2 Sensor	£500
Syston Donner 6030 - 26.5GHz Microwave Freq Counter	£1250
Tektronix ASG100 - Audio Signal Generator	£1995
Wavetek 178 Function generator (50 MHz)	£750
Wayne Kerr 3245 - Precision Inductance Analyser	£950
Wayne Kerr 6245 - Precision Component Analyser	£1995
	£2500

Hewlett Packard 8642A - high performance R/F synthesiser (0.1-1050MHz)	£4750
3335A - synthesiser (200Hz-81MHz)	£2200
Hewlett Packard 436A power meter and sensor (various)	from £750
437B power meter and sensor (various)	from £1100
Hewlett Packard Marconi 6310 - programmable sweep generator (2 to 20GHz) - new	£2750
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£3500
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£5750
Hewlett Packard 5370B - universal time interval counter	£1500
Hewlett Packard 8662A synth. sig. gen. (10kHz to 1280MHz)	£8250
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	£2500
Hewlett Packard 3314A Function Generator 20MHz	£1250
Hewlett Packard 8904A Multifunction Synthesiser (opt 2+4)	£1950
R&S SMG (0.1-1GHz) Sig. Generator (opts B1+2)	£2950

OSCILLOSCOPES

Gould 400 20MHz - DSO - 2 channel	£800
Gould 1421 20MHz - DSO - 2 channel	£600
Gould 4068 150MHz 4 channel DSO	£1500
Gould 4074 100MHz - 400 Ms/s - 4 channel	£1350
Hewlett Packard 54201A - 300MHz Digitizing	£995
Hewlett Packard 54800A - 100MHz - 2 channel	£750
Hewlett Packard 54502A - 400MHz - 400 MS/s 2 channel	£1800
Hewlett Packard 54810A 'Infinium' 500MHz 2ch	£4000
Hewlett Packard 54520A 500MHz 2ch	£3000
Hameg 205-2 20MHz DSO	£550
Hitachi V152/V212/V222/V302B/V302F/V353F/V550B/V650F	from £125
Hitachi V1 100A - 100MHz - 4 channel	£900
Intron 2020 - 20MHz - Dual channel D.S.O. (new)	£450
Iwatsu SS 5710/SS 5702	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lectro 9314L 300MHz - 4 channels	£3000
Meguro MSO 1270A - 20MHz - D.S.O. (new)	£450
Philips PM3094 - 200MHz - 4 channel	£1750
Philips 3295A - 400MHz - Dual channel	£1995
Philips PM3392 - 200MHz - 200Ms/s - 4 channel	£750
Philips PM3070 - 100MHz - 2 channel - cursor readout	£350
Tektronix 465 - 100MHz - Dual channel	from £450
Tektronix 464/466 - 100MHz - (with ANL storage)	£650
Tektronix 475/475A - 200MHz/250MHz - 2 channel	£350
Tektronix 468 - 100MHz - D.S.O.	£650
Tektronix 2213/2215 - 60MHz - Dual channel	£350
Tektronix 2220 - 60MHz - Dual channel D.S.O	£995
Tektronix 2235 - 100MHz - Dual channel	£995
Tektronix 2221 - 60MHz - Dual channel D.S.O	£900
Tektronix 2245A - 100MHz - 4 channel	£2450
Tektronix 2440 - 300MHz/500 MS/s D.S.O.	£1000
Tektronix 2445A/2445B - 150MHz - 4 channel	£1200
Tektronix 2445 - 150MHz - 4 channel + DMM	£995
Tektronix TAS 475 - 100MHz - 4 channel	from £200
Tektronix 7000 Series (100MHz to 500MHz)	from £2500
Tektronix 7104 - 1GHz Real Time - with 7A29 x2, 7B10 and 7B15	from £1250
Tektronix 2465/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 2430/2430A - Digital storage - 150MHz	£750
Tektronix TDS 310 50MHz DSO - 2 channel	£850
Tektronix TDS 320 100MHz 2 channel	£1250
Tektronix TDS 340A 100MHz DSO - 2 channel	

SPECTRUM ANALYSERS

Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£850
Anritsu MS 610B 10KHz - 2GHz - as new	£3500
Anritsu MS3606B (10KHz-1GHz) network Analyser	£3500
Advantest/TAKEDA RIKEN - 4132 - 100KHz - 100MHz	£1500
Hewlett Packard 8756A/8757A - Scalar Network Analyser	from £1000
Hewlett Packard 853A Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£2750
Hewlett Packard 182T Mainframe + 8559A Spec. An. (0.01 to 21GHz)	£3500
Hewlett Packard 8568A (100Hz - 1500MHz) Spectrum Analyser	£3995
Hewlett Packard 8567A - 100Hz - 1500MHz	£3995
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£1500
Hewlett Packard 8754A - Network Analyser 4MHz-1300MHz	£3995
Hewlett Packard 3561A Dynamic signal analyser	£3250
Hewlett Packard 3560A Dynamic signal analyser	£3500
Hewlett Packard 3753A (3000KHz-3GHz) Network An.	£1950
IFR A7550 - 10KHz-1GHz - Portable	£700
Meguro - MSA 4901 - 30MHz - Spec. Analyser	£995
Meguro - MSA 4912 - 1 MHz - 1GHz Spec. Analyser	£3750
Tektronix 2712 Spec. Analyser (9kHz - 1.8GHz)	£2750
Wandel & Goltermann TSA-1 system analyser (100Hz-180MHz)	£1750
Wiltron 6409 - 10-2000MHz R/F Analyser	

All equipment is used - with 30 days guarantee and 90 days in some cases. Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate, Coventry CV3 2SF. CIRCLE NO. 101 ON REPLY CARD

Tel: 02476 650 702
Fax: 02476 650 773

CONTENTS

491 COMMENT

A lesson in new technology

492 NEWS

- Airship detects battlefield mines
- Nanometre tubes for FETs
- Class-D with 0.03% distortion
- New material focuses microwaves
- LEDs for domestic lighting?
- LCD read-out with no power
- Solar cell promises 50% efficiency
- Steerable solid-state antenna

498 ELASTIC CAPACITORS

Electronic engineers understand capacitors but they tend to view colliding bodies as mysterious - but both are expressions of the same formulae, explains **Andrew Robertson**

500 PSEUDO-RANDOM BITS

Pseudo-random bit sequences are used in communications, testing, audio and many other areas. **Ian Hickman** explains their benefits.

504 EMI TIPS AND FIXES

Leading off with an EMI background, **Joe Carr** presents tips and fixes for minimising interference.

510 ANALOGUE I/O FOR THE PC

Tariq Iqbal's analogue i/o card for the PC provides eight 12-bit resolution inputs and one 8-bit output. QuickBasic routines demonstrate how easy it is to read and write analogue voltages.

514 PHASE-SHIFTABLE SIGNAL GENERATOR

Having two identical but phase-shifted sine waves is useful for testing, but generators capable of producing them are rare. **W Q Yang** and **T Y Ng** have designed a digital synthesiser producing dual 16MHz signals under RS232 control.

522 DESIGNING WITH DSP

Patrick Gaydecki explains how to produce software for digital signal processing. "The idea that DSP chips are more difficult to program than the average microprocessor is a myth," he argues.

527 NEW PRODUCTS

New product outlines, edited by **Richard Wilson**

538 PRO AUDIO-VISUAL ROUTER

Emil Vladkov's audio and video router system allows you to select one of eight video inputs and one of eight stereo audio channels using either a keypad or a PC. This second article looks at the software needed.

544 CIRCUIT IDEAS


- Mains glitch detector
- 3-phase sequence indicator
- Interface for sweep display.
- Simple stepper-motor drive.
- A microcurrent amplifier
- Keyboard has serial interface
- Unity-gain phase shifter

551 LETTERS


Input-filter distortion, Tracking RCCB nuisance trips, Drag factor, Sub-bass challenged, EMC and the DIY PC, Linux, Valve substitutes, E-series anomalies

560 WEB DIRECTIONS

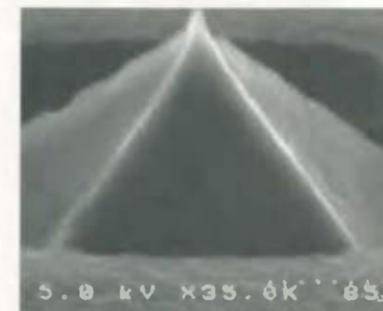
Useful web addresses for the electronics designer.



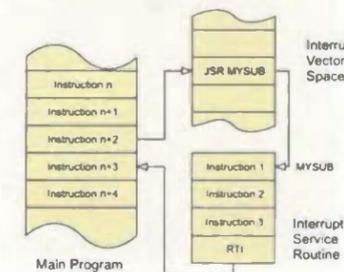Solar cells using diamond films promise 50% efficiency and at a cost of just a dollar per square centimetre - this and much more news starting on page 492.



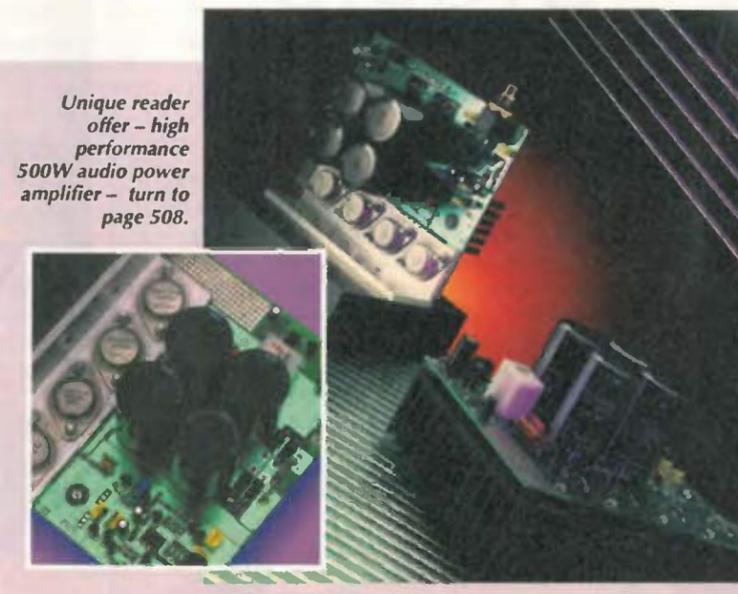"Programming a DSP chip is no more difficult than programming a microcontroller," argues **Patrick Gaydecki**. Find out for yourself on page 522.



Unique reader offer - high performance 500W audio power amplifier - turn to page 508.

August issue on sale 5 July

Sinking fast with poor tech support?
Expensive maintenance fees?
costly upgrades?
old fashioned software?

Realise your potential & break free with EDS!

electronic design STUDIO

Introducing EDS Advance the new modular electronics design system that includes simulation, schematic, PCB, autorouting and CAD/CAM modules as standard.

Our powerful Integrated development environment brings powerful management to your projects and now features 3D style PCB footprints, Viper rip up and retry autorouter, shape based design rule checking, full copper pour support with unlimited automatic zones and split power planes, cross probing between schematic/pcb/netlist, netlist navigator, wizards to automate key features, DTP quality feature rich schematics, 2000 look and feel, and a wide range of import/export options.

If you are struggling with your existing system and feel its time for a change, why not give us a call and we will send you our free information pack. Or visit our web site and download a free trial copy of EDS.

Try before you Buy at www.quickroute.co.uk



Quickroute Systems Ltd,
Regent House, Heaton Lane,
Stockport SK4 1BS UK
Tel 0161 476 0202 Fax 0161 476 0505
Email: info@quicksys.demon.co.uk



CIRCLE NO.105 ON REPLY CARD

Customised design services from Intec Associates Limited

INTEC look for interdisciplinary collaborations with experts who work in other fields. We supply creative and cost-effective solutions.

Key expertise

- PC interfacing applications
- Implementation of PIC micro-controllers and PC-104
- Implementation of radio linkers
- Implementation of sensors
- Analogue and digital circuit design
- PC software development using VB, VC, Java, Turbo Pascal and Delphi

Applied areas

- Standalone data logger using PIC micro-controller
- Standalone devices using PIC micro-controller
- Data logging/control system using PCs or PC-104
- Remote data logging/control via radio link
- Remote data logging/control via telephone line

Intec instant solutions

- PC-based data loggers controllers
- Standalone data loggers
- Sound loggers
- Remote control and telemetry applications

www.intec-group.co.uk

11 Sandpiper Drive, Stockport, Cheshire, SK3 8UL, UK
Tel: +44 (0)161 477 5855 Fax: +44 (0)161 477 5755
E-mail: mail@intec-group.co.uk

CIRCLE NO.106 ON REPLY CARD

PCB-POOL

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

- Prototypes at a fraction of the cost
- Tooling and setup included
- Any contour
- Fr4 1.6mm, 35µm Cu
- Industry standard quality
- Follow up series runs
- CAM / CAD consulting

PRICE EXAMPLE
1 EUROCARD 05/PTN
+ Tooling
+ Photoplots
+ VAT
= £ 29.89*

*Sterling rates may vary Price = € 49

€49



Tel: +353 (0)61 701170
Fax: +353 (0)61 701164
E-Mail: sales@pcbpool.com

Freephone
0800-389 8560

Simply send your files and order ONLINE

WWW.PCB-POOL.COM

Protel orcad EDWIN GraphiCode

CIRCLE NO.107 ON REPLY CARD

EDITOR
Martin Eccles
020 8643 3614

CONSULTANT
Ian Hickman

EDITORIAL
ADMINISTRATION
Jackie Lowe
020 8643 3614

EDITORIAL E-MAILS
J.lowe@cumulusmedia.co.uk

GROUP SALES
EXECUTIVE
Pat Bunce
020 8643 8339

ADVERTISEMENT
E-MAILS
p.bunce@cumulusmedia.co.uk

EDITORIAL FAX
020 8643 8952

CLASSIFIED FAX
020 8652 2016

NEWSTRADE ENQUIRIES
020 7907 7777

ISSN 0959-8332

SUBSCRIPTION HOTLINE
Tel (0) 1444 475662
Fax (0) 1444 445447

SUBSCRIPTION QUERIES
Tel (0) 1444 445566
Fax (0) 1444 445447

A lesson in new technology

Many of you will be aware that the numbers of young people leaving school and considering a career in electronics and similar disciplines has been falling for years. Depending on who you listen to, this fall is either worrying or disastrous.

As someone who works with both schools and industry I am aware that many of my industrial colleagues are extremely concerned about future recruitment.

Here in Staffordshire, electronics companies are experiencing great difficulty in expanding due to the lack of quality electronics and other manufacturing engineers. As a result, electronics specialists are being appointed from all corners of the globe – but this source is not infinite.

Following the government hype regarding 'education, education, education', you could be led to believe that a new generation of high calibre students is in the pipeline about to burst out of our schools to revive the nation's manufacturing base. Don't hold your breath.

Unfortunately, governments have difficulty distinguishing between 'technology in schools' and 'design and technology' as defined in the National Curriculum.

Several months ago, the government announced that a further £400m would be provided for 'Technology' in schools. Some took this as being the key to turning a new generation towards electronic design and manufacture.

In those schools where targeted investment has taken place, the experience known to many older readers as 'Craft' or CDT is now a cutting-edge subject, well matched to the 21st century. In the majority of schools 'hands-on' electronic design and manufacture teaching – if undertaken at all – takes place in design and technology lessons.

Unfortunately, I believe that little of this new funding will find its way into design and technology. If it doesn't, it will have little effect on the nurturing of the future engineers that industry and the country needs.

Although there has been considerable expenditure in general career development for teachers, we have only scratched the surface in updating the skills of specialist teachers in the new technologies – especially electronics. Unlike the wood and metal ages, these new technologies change rapidly, requiring regular career development for staff. Much of this practical career development was provided by local Education Authorities but sadly this has all but disappeared.

I doubt if the new funding will have any effect unless we see directives to equip the country's design, technology and science facilities with

adequate levels of dedicated 'information and communications technology' hardware, ICT for short, suitable applications software and manufacturing facilities appropriate to 2001 rather than 1951.

Unfortunately, in many schools this new technology hardware will not be used for designing electronics systems, controlling electrical components via control interfaces, data logging, scientific analysis or allowing young people to design using some of the excellent CAD/CAM software now available.

Only a tiny percentage of schools will allow some of the funds to be spent on the purchase of dedicated design, technology and science computers, CAD/CAM equipment, PIC systems or ICT controlled manufacturing equipment. Instead the vast majority of this new funding will probably go on supporting ICT in English, business studies, leisure and tourism, geography – and every other subject area.

This of course is no bad thing. Our future engineers need a high quality general education in all subjects. But these areas of the curriculum have little to do with electronic design & manufacture.

The solution – or at least a move in the right direction – would be to set a standard benchmark of minimum ICT requirements for all schools, in design, technology and science departments. If £400m were ring fenced and only given to the country's high schools, design, technology and science departments, each would receive approximately £50000 each.

You will appreciate that to purchase some small CAD/CAM manufacturing equipment, software and 20 computers will quickly swallow up this sum. This assumes that the environment is suitable for these modern technology activities – which is unlikely in many schools.

We also have the career development aspect, to teach electronics and integrate all the ICT requires considerable knowledge. This requires intensive long-term investment in training. All of this could cost in excess of £200 000 per school, minimum!

If science and technology is to be the base of this country's future economy, as stated by Lord Sainsbury and other government ministers over the past six months, we need some major dedicated funding for these subjects in the nations schools, primary and secondary. This is especially important in the secondary sector where the specialist ICT equipment, software and manufacturing equipment for design, technology and science is vital.

John Hindhaugh, Director Staffordshire SATRO

Electronics World is published monthly. By post, current issue £2.80, back issues (if available). Orders, payments and general correspondence to Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ.

Newstrade: Distributed by COMAG Tavistock Road, West Drayton, Middlesex, UB7 7QE Tel 01895 444055

Subscriptions: Quadrant Subscription Services, Oakfield House Perryman Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year UK £36.00 2 years £58.00 3 years £72.00. Europe/EU 1 year £36.00 2 years £82.00 3 years £103.00 ROW 1 year £61.00 2 years £98.00 3 years £123

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of

America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Colchester) Ltd, Filmsetting by JJ Typographics Ltd, Unit 4 Baron Court, Chandlers Way, Southend-on-Sea, Essex SS2 5SE.

Cumulus
BUSINESS MEDIA

Class-D amplifier chip boasts 300W and 0.03% distortion

Digital reproduction is creeping up the audio chain and has reached the power stage of many low-cost amplifiers – particularly in those, like answer-phones and TVs, where quality is not top of the list.

Now Texas Instruments claims to have bought the well-known Class-D attribute of high-power efficiency to a real high-power hi-fi design.

It is to sell an all-digital amplifier subsystem chip that should deliver over 300W with THD+N below 0.03% (20Hz to 20kHz) and a 110dB dynamic range measured at the

speaker – when the complete reference design becomes available later this year – claims the company.

It also says that a variable power rail design, which it is keeping up its sleeve, will allow a dynamic range of 130-140dB.

The TAS5015 digital modulator is the heart of the amplifier. It is a 24-bit multi-standard, multi-sample rate (32 to 192kHz) device that processes a digital pulse-code modulated input into a pulse-width modulated output ready for a power output stage.

TI has designed a suitable discrete

power stage, which will only be available under licence, that converts the PWM signal up to the power level required at the speaker.

The company claims that the reference design will dissipate less than one-tenth the power of class-A and class-AB amplifiers.

The technology, called equibit, comes through TI's acquisition of Toccata Technology last year.

Samples of the chip have been distributed to licensees already. Price, to those who can afford a licence, will be around \$25 in quantity.

Satellite's momentum wheel develops 5.2Nms from just 6W

Surrey Satellite Technology (SSTL) has made the momentum wheel which will fly on the Rosetta spacecraft, due to land on comet '46 P/Wirtanen' on 29th November 2011.

The wheel will be mounted inside the satellite so that the spin direction

is inertially fixed, giving the satellite an inherent gyroscopic rigidity.

By changing the momentum wheel's speed over a limited range – less than 10% of the nominal speed of a few thousand revolutions a minute – the satellite can be rotated around

the spin direction. In this way, rotational momentum can be exchanged between the wheel disc and the satellite's body.


This momentum wheel is unique, says SSTL, in that it provides 5.2Nms of momentum with a power dissipation of only 6W.

In flight, it will have to survive a nine year cruise in space before it is fired-up and used to manoeuvre the craft during the final 20 hours of approach and landing on the comet.

Dry lubricated bearings and low-friction operation are the keys to long life in a vacuum says SSTL. Details of the Rosetta Mission are available at,

http://spdex.t.estec.esa.nl/content/doc/e7/2279_.htm and www.sstl.co.uk

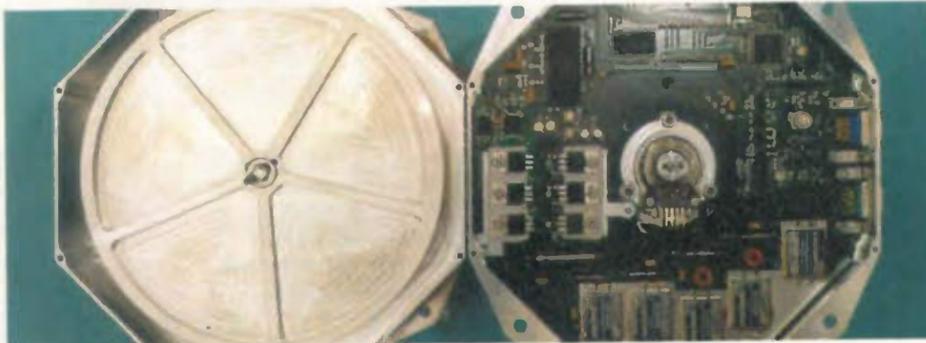Momentum wheel's end casing showing its interface circuitry.



New unique material focuses microwaves

A material with a negative refractive index at certain microwave frequencies has been created by physicists from the University of California in San Diego.

Future generations of the material could, the developers say, lead to highly directional aerials and perfect lenses that focus microwaves or light to a point.

"The experiments we report confirm earlier theoretical predictions that a new, unique, class of materials can cause electromagnetic waves, such as radar and microwaves, to bend in a direction opposite to the way they travel through all other known materials," said Sheldon Schultz, professor of physics at UCSD.

The work by Schultz' team proves an idea put forward by Professor John Pendry, head of physics at Imperial College, London.


He suggested that some composite materials with negative permeability and negative permittivity would have bizarre properties such as to make convex lenses behave as concave while flat sheets would focus light to a spot.

So-called metamaterials with negative permeability and negative permittivity lead to a negative refractive index, which means the material breaks Snell's Law.

Any EM radiation incident at a boundary will be refracted in an unexpected direction.

A microwave beam incident on Schultz' material refracts to the same side of the normal as the incident ray.

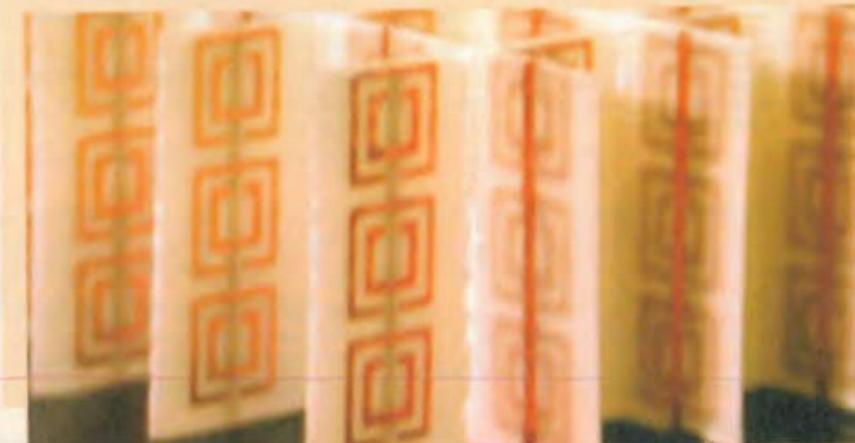"If these effects turn out to be possible at optical frequencies, this material would have the crazy property that a small flashlight shining on a flat slab would produce a focus at a point on the other side," said Schultz.



LEDs for domestic lighting?

The domestic light bulb may be a step closer to the history books when Philips Research in the US has finished its latest development.

It is setting out to discover how LEDs can realistically be used for home lighting. LEDs – even the latest which rival light bulbs in power efficiency – have to be used in bunches to get sufficient light for illumination.

Unfortunately chip-to-chip variation means that the output can be blotchy and vary from assembly to assembly.

The company is developing ways to optically mix the light coming out of the LEDs, as well as control

algorithms to allow the effective colour of the assemblies to be varied to suit mood and tastes within the home.

One aim is to generate control algorithms that carefully balance the many variations which occur in LEDs, said the company.

Algorithms so far developed also include compensation for device to device light output variations, output drop with age, change with temperature and wavelength variation with current.

At the moment, some form of initial calibration is required. Eventually an in-room sensor may feed back enough information to

allow 'plug-and-play' swapping of LED-based lamps.

Backlighting of LCDs may be the first application for the new algorithms, which have been written for Philips' microcontrollers.

Optical fibre survives oil-well drill tip

New Mexican research centre Sandia Labs has shown that optical fibre is tough enough to survive in an operating oil-well drill without additional armour.

Previously it was thought that the fibre would be too fragile to last long enough to do any useful work within the hollow drill, which also carries abrasive liquid 'lubricant'.

The findings come out of a research project to increase the data rate of live in-well sensing during drilling operations.

Fibre, protected only by a thin protective plastic coating, survived the few hours needed to make measurements in a 1000m test drill, transmitting information about temperatures, pressure, chemistry, and rock formation at 1Mbit/s. Researchers predict the scheme should be good for wells 6000m deep.

After use the fibre is ground up by the drill bit. Why it survives is not yet proven, but it is suspected that it 'gives' when brushed by particles in the lubricant and also tends to cling to the inside wall of the drill.

MPEG4 edges closer

Audio and video compression system MPEG4 has taken another step closer to full industry acceptance as three key organisations agree on a standard.

The International Telecommunications Union (ITU), 3G Partnership Project (3GPP) and Internet Engineering Task Force have pledged their support for a format proposed by five Japanese companies.

Their support for any MPEG4 format is said to be critical for delivery of MPEG4 over the Internet.

The five developers of the format are Matsushita Electric, NEC, NTT, Oki Electric and Toshiba.

Rather than using TCP/IP, the conventional Internet protocol, they have based their standard upon the real-time transport protocol (RTP).

Audio and video are a problem for TCP/IP because of their inherent real-time character. When data is

lost, TCP/IP retransmits, which can cause annoying delays to the service or even out of order sequencing.

On the other hand RTP does not retransmit and adds time stamps to the packet headers in order to keep audio and video synchronised. Sequence numbers make sure that packet losses don't cause major timing problems.

Designed for lossy media such as mobile phones, MPEG4 is expected to become the main compression standard for telecoms, local-area networks and the Internet.

Video over wired or wireless links can have data rates of between 5 and 64kbit/s, while standard TV is between 2 and 8Mbit/s.

The data, whether audio or video, is split into a series of objects, for example a background, table and a human body. If only the human face moves from one scene to another, only the relevant data is transmitted, reducing bandwidth requirements.

High-performance Bluetooth

A Bluetooth radio chip has been developed by STMicroelectronics using intellectual property from Parthus Technologies, the Irish design house.

Aimed at battery operated products such as mobile phones and PDAs, the radio uses a low intermediate frequency design.

ST will use its BiCMOS silicon germanium process to manufacture the chip. Current consumption is claimed to be 30mA in receive mode and 30mA when transmitting at maximum power.

"Exploiting ST's silicon germanium technology has enabled

us to create the highest performing Bluetooth radio on the market," said Kevin Fielding, president of Parthus.

On its own the chip can transmit at Bluetooth's Class 2 and 3 levels, good for up to 10m. With the addition of an extra power amplifier, it can manage Class 1 operation, which takes its range up to 100m.

In order to bring Bluetooth products to market quickly, the specification has very relaxed requirements. Bit error rate, for example, is only required to be 10^{-3} at -70dBm. The ST/Parthus chip has a claimed BER of 10^{-6} at -75dBm.


LCD read-out with no power

E Ink has demonstrated a 12-inch active matrix 'electronic ink' display that retains its image on power-down.

The company started off with an active matrix donated by IBM and added the ink, which works through the electrostatic attraction of coloured particles.

The black ink on white background avoids the need for backlighting, claims the company, while brightness is up to six times better than LCD, it said.

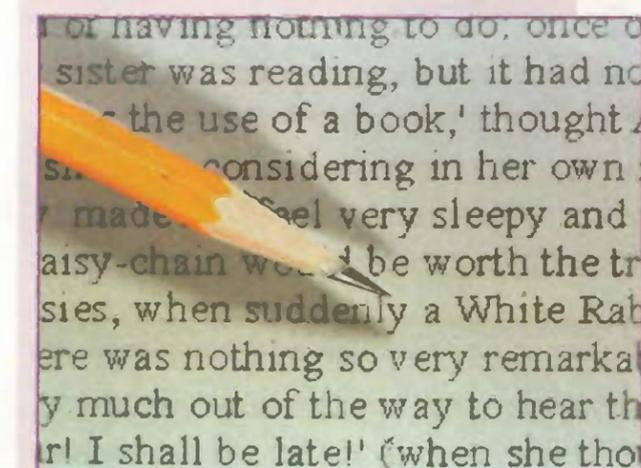
E Ink and IBM will deliver a joint paper describing the display at the Society for Information Display conference in San Jose in June.



Solar cell promises 50% efficiency

Scientists at Vanderbilt University in Tennessee are promising a solar cell that converts sunlight at 50 per cent efficiency. Moreover the design will cost just \$1 per square

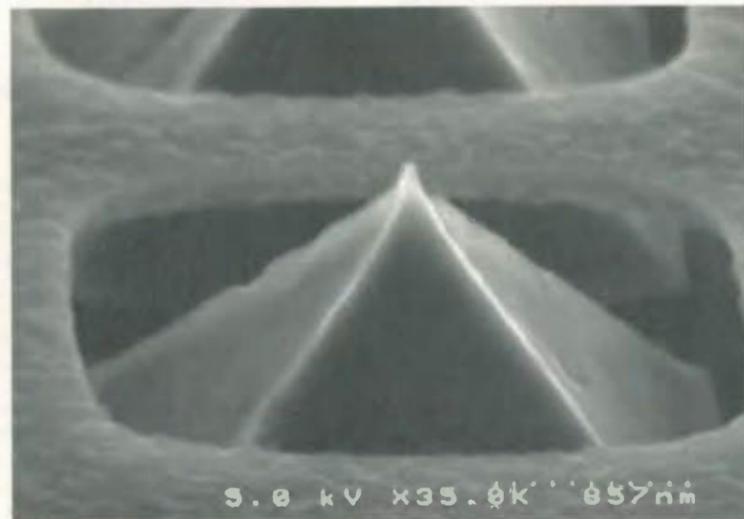centimetre, the researchers claim. Professor Timothy Fisher says his polycrystalline diamond films would be well suited to space applications as they can withstand



the high level of cosmic radiation. Efficiency of conventional solar cells can be reduced by a half after ten years in space.

Fisher's diamond-film structure includes pyramids, about ten million per square centimetre, separated from the cell's anode by a small gap. The cathode is attached to the back of the film.

Sunlight hits the cathode and heats it to around 1000°C, causing streams of electrons to flow from the pyramid tips to the anode.

The resulting large current and small voltage are passed through a DC-to-DC converter at around 90 per cent efficiency, says Fisher.

Costs are kept down as the diamond film can be deposited from methane using chemical vapour deposition.

The goal of current research at the University is to produce a prototype 1cm square cell turning out 10W of power at 1000°C.

Steerable solid-state antenna for mobile phones

Cambridge start-up Antenova has garnered £3.4m in venture capital funding to develop a steerable solid state antenna.

Launched late last year, Antenova is developing directional and steerable antennas aimed at mobile phones.

By directing the RF, mobile phone systems can physically split cells and radiation to the user can be reduced.

The steerable side of the design ensures a phone stays in contact with the base station as the user changes position.

By avoiding 360° transmission, power consumption is also reduced, the firm says. And because the antenna is directional, signal processing needs are reduced.

The antenna is formed from three strip-lines on the mobile phone's

PCB. This gives it directional control with a 60° resolution.

First working prototypes are due by the end of this year.


A spin-off from radio frequency location company ActiveRF, Antenova holds licences for technology developed at Sheffield University and Griffith University in Australia. Funding has come from the Cambridge Gateway fund.

Steerable mirrors at heart of Texas Instruments' optical comms systems

Texas Instruments has announced an optical communication system based on steerable mirrors.

It is a point-to-point system which will send 100Mbit/s Ethernet hundreds of metres or up to 50 metres with a class 1 laser,

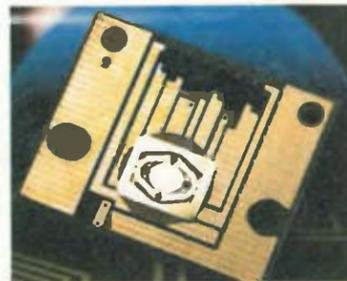Optical terminals made from TI parts could be tennis-ball size and will be handled much like a Webcam. Users will plug into a computer and point them at a similar terminal to establish a link. No precision alignment is needed.



Central to operation is a two-axis analogue steerable mirror.

Far bigger than its micromirrors, but small at only 3.2 by 3.6mm, it is controlled by a DSP to establish alignment and compensate for vibration.

TI is making an evaluation kit, including a DSP, analogue chip, packaged mirror and software, in prototype quantities, production is probably a year away.



WAP addresses reduced to a number... Typing in WAP addresses using only the 12 keys of a phone keypad is an irritation that may go away with a development from AirClic. In a trial in Sweden the company has replaced WAP addresses with a key-pad-friendly number. The user either types in the number, or scans a special mini bar code into the phone. Apparently, it only takes minutes to register any phone, PC or PDA with the company to use the system.

Now supports the MC68HC11 and PIC16F877

PROTEUS VSM

Virtual System Modelling


Build It In Cyberspace

www.labcenter.co.uk

CIRCLE NO. 109 ON REPLY CARD

Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time.*

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.

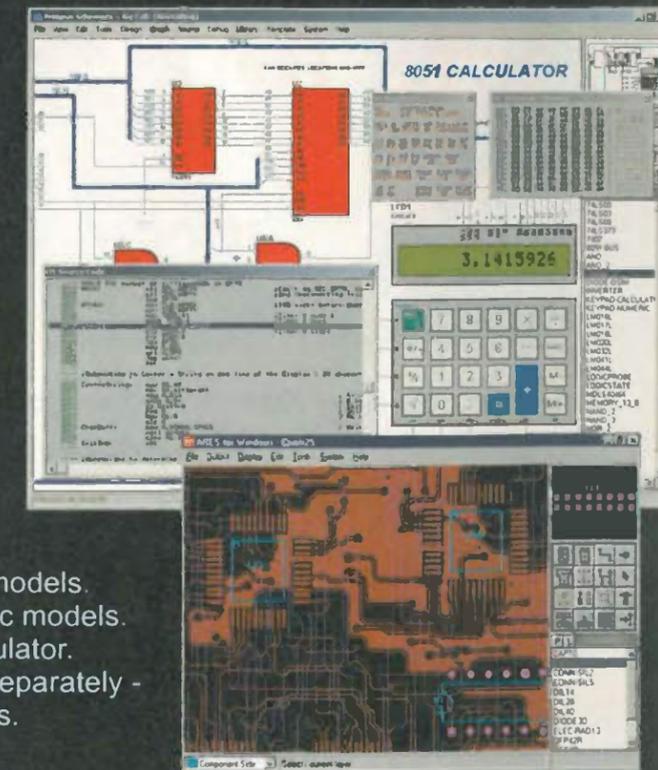

*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II.

labcenter
Electronics

Write, phone or fax for your free demo CD - or email Info@labcenter.co.uk.
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

Elastic

capacitors



Electronic engineers understand capacitors but they tend to view colliding bodies as mysterious – a strange mindset since they are both expressions of the same formulae, as Andrew Robertson explains.

What do colliding bodies and capacitors have in common? Not a lot one might think, apart of course from both being described by the ubiquitous $a=bc$ and its integral $a=1/2bc^2$, i.e.,

$$\begin{aligned} \text{momentum} &= mv \\ \text{kinetic energy} &= 1/2mv^2 \end{aligned}$$

and,

$$\begin{aligned} \text{charge} &= CV \\ \text{charge energy} &= 1/2CV^2 \end{aligned}$$

Beyond this, few textbooks make more than passing comment of correspondence, but one must bear in mind that formulae only describe – they don't define.

Non-elastic interactions

If a body travelling with a velocity of v collides *non-elastically* full face with a stationary body of identical mass, the two bodies unite and move in the same direction as the original moving body but with a velocity of $1/2v$. Momentum, being inviolate, prevails.

The energy embarrassment to satisfy $1/2mv^2$ is liberated ultimately as heat. Likewise, but with a change of terms, this dissipation of energy occurs in the classical example of Fig. 1.

With identical capacitors and initially only C_1 charged to V , closing the switch results in a voltage of $1/2V$ in each capacitor. Charge conservation, also inviolate, substitutes for momentum, capacitance for mass and voltage for velocity.

Regardless of the impedances of the physical components, be they large or diminishingly small, energy is conveniently disposed of in heating, electromagnetic radiation and even sound. In purely theoretical conditions – which would evoke Maxwell's equations – the 'spare' energy will be still be liberated from the system. We have therefore in a sense 'inelastic' capacitors.

Momentum and charge of the whole universe is by all accounts absolute, and probably zero. In all known interactions, momentum and charge will always be preserved at the expense of system energy. So, regardless of relative masses or capacitances where the second body is initially stationary (or uncharged), it follows that, for inelastic collisions, combined velocity is,

$$\frac{\text{mass}_1 \times \text{velocity}_1}{\text{mass}_1 + \text{mass}_2}$$

or, for (inelastic) capacitors, combined voltage is,

$$\frac{C_1 \times V}{C_1 + C_2}$$

Elastic interactions

Consider now the *elastic* collision of two identical masses, initially one moving and the other stationary. For simplicity, this is restricted to a full face collision.

The first body will transfer all its momentum *and* energy to the second body. This absolute condition is only realised at atomic level but can be approached in the 'real world'.

So what of a capacitor equivalence? Conventional wisdom conjures up the 'inelastic' situation, but there is a way. In Fig. 2, where only C_1 is initially charged and $C_2=C_1$, with idealised components the entire charge *and* energy are transferred when the switch is closed. As with collisions, losses cannot be avoided but can be minimised with a high-Q inductor and synchronous switch replacing the diode and switch.

At first glance, the inductor's action may appear strangely oblig-

ing but the arrangement is simply a tank circuit, with the condition at the instant of switch closure being the voltage crest of an oscillatory cycle. After 180° , the voltage across the inductor will be reversed, current will have fallen to zero and further oscillation and charge exchange is blocked by the diode.

The system energy will be again solely capacitive, having been transferred by way of the inductor intermediary from C_1 to C_2 . Of course for the oscillatory cycle, the two capacitors are in effect only one in series combination, charged to V_3 . This is true for both the initial and final conditions since our voltage reference is their junction. In this simplest case it is zero, as initially is the voltage of the second capacitor. Ergo that capacitor equates to an initially stationary body in our voltage reference frame.

Notably, the voltage V_3 reversing between the top ends of the capacitors is analogous to a primary law of elastic collision, namely, *the relative velocity of two particles in a full face elastic collision is unchanged in magnitude but reversed in direction*. We have now 'elastic' capacitors.

Dissimilar capacitances

The special case of equal masses is familiar and almost intuitive, but what of the resultant velocities of dissimilar masses in an elastic collision? Although second nature to the atomic physicist, this may not be so for the electronics engineer. The formulae are not difficult to derive by manipulation of momentum and energy equations, but can also be derived from basic electronic principles. Consider Fig. 2 with dissimilar (or identical) capacitors. Series capacitance is,

$$\frac{C_1 \times C_2}{C_1 + C_2}$$

In the elastic interaction – i.e. 180° of an undamped oscillation – the voltage across the capacitors is reversed, which is to say that voltage *change* across the capacitors is twice V_{3i} . Note that the subscripts i and f denote the initial and final states before and after switch closure. This means that charge flow is,

$$C_{\text{series}} \times 2 \times V_{3i}$$

Charge in C_2 was initially zero so charge flow is equal to charge transferred from C_1 to C_2 . But since V_{2i} is zero, $V_{3i}=V_{1i}$, and since,

$$V = \frac{Q}{C}$$

resultant voltage V_{2f} across C_2 is,

$$\begin{aligned} \frac{Q_{\text{transferred}}}{C_2} &= \frac{C_1 \times C_2 \times 2 \times V_{1i}}{C_1 + C_2 \times C_2} \\ &= \frac{C_1 \times 2 \times V_{1i}}{C_1 + C_2} \end{aligned} \quad (1)$$

resultant voltage V_{1f} across C_1 is,

$$\begin{aligned} \frac{Q_{\text{initial}} - Q_{\text{transferred}}}{C_1} &= \frac{(C_1 \times V_{1i}) - \left(\frac{C_1 \times C_2 \times 2 \times V_{1i}}{C_1 + C_2} \right)}{C_1} \\ &= V_{1i} \left(1 - \frac{2 \times C_2}{C_1 + C_2} \right) \\ &= V_{1i} \frac{C_1 - C_2}{C_1 + C_2} \end{aligned} \quad (2)$$

It should come as no surprise that with a change of terms, equations 1 and 2 are the same as the equations for elastic mass interactions.

The quantitative world

Simple though the formulae are, it is quite pleasing to have arrived at them from knowledge of a different discipline. It could be inferred from this method of calculation that two masses in an elastic collision act arithmetically like two capacitors in series. In other words, the product divided by the sum. Intuitively it is difficult to appreciate why this should be so, although an atomic physicist might feel otherwise.

A point of caution, apparent from equation 2 – beware of inductors feeding capacitance in power feeds or signal paths. Under favourable conditions, as exploited in applications such as thyristor commutation, the transient voltage across capacitance can reverse or aspire to reach twice the applied voltage.

With extreme values of C_1 and C_2 , if C_1 is much less than C_2 , C_2 will remain at almost zero volts, while the voltage on C_1 will be almost unaltered in magnitude but reversed in polarity. Where C_1 is much greater than C_2 , C_2 will charge to nearly $2V_{1i}$, while the voltage on C_1 will remain almost unaltered.

The voltage reversing and doubling ties up nicely with the mass analogy. If a super bouncy ball is thrown at a wall it comes back at the same speed – almost. Change the reference and it is the same as throwing a wall at a bouncy ball, whereby the resulting velocity of the ball will be nearly twice that of the wall.

The derived formulae relating to inelastic and elastic collisions between one moving and one stationary object can be augmented

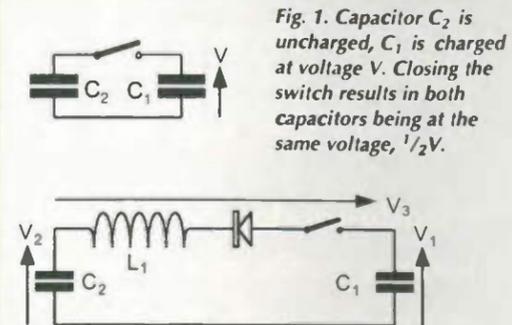


Fig. 1. Capacitor C_2 is uncharged, C_1 is charged at voltage V . Closing the switch results in both capacitors being at the same voltage, $1/2V$.

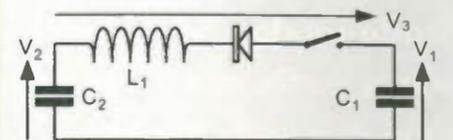


Fig. 2. In this circuit, with idealised components, the entire charge and energy are transferred from the charged capacitor when the switch is closed.

to describe interactions between bodies or capacitors with any initial starting condition. Interaction between two moving bodies equates to both capacitors having an initial charge but the analysis still holds true. One can even incorporate coefficients of restitution and resistance as imperfect components in the mechanical and electrical systems.

There are limits though. In more complex states, such as where the collision is not full face or asymmetry of the bodies impart spin, the elegance of the equivalence becomes strained. Also, the assertion of charge conservation is appropriate but not altogether accurate – capacitor charge is perhaps better viewed as charge differential.

When a body – a capacitor would do – is thrown into the air, the world moves in the opposite direction. The charge of that capacitor – the complementary effect of momentum – is not quite so absolute.

If, for instance, two identical capacitors are charged in series, then in their charged state reconnected in parallel, the voltage halves but the capacitance quadruples. By manipulation of each capacitor's zero reference, there is a doubling of charge. In the world of momentum, contrary to what, say, advocates of gyroscopic levitation would appear to expound, there is no likely analogue.

So is there benefit from viewing capacitor charging as elastic and inelastic collisions, or *vice versa*? Certainly, if one's inclination is to subjectively 'feel' the physical world. The two environments are merely different expressions of underlying fundamentals, not formulae coincidence. It is akin to describing electricity in terms of water flow.

The appreciation is not Grand Unification Theory, but such comparison can aid insight and hence possibly improve circuit design.

Finally, thanks to Glenn O'Dell for his help in preparing this article. ■

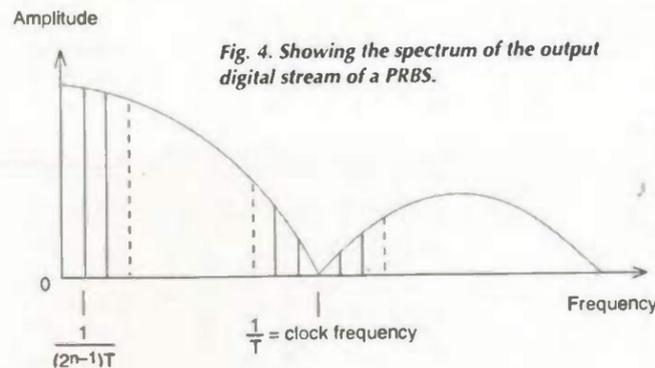


Fig. 4. Showing the spectrum of the output digital stream of a PRBS.

Time-reversed sequences

The arrangement to produce the time reverse of a given sequence can be derived from the polynomial of that sequence, by deriving the 'reciprocal polynomial'. Given an irreducible polynomial $f(x)$ - one that gives a maximal length sequence - the reciprocal polynomial is $x^n[F(1/x)]$

Taking the ninth degree example of Fig. 1, where the generating polynomial is $x^9+x^6+x^4+x^3+1$, the reciprocal polynomial is,

$$x^9 \left[\left(\frac{1}{x}\right)^9 + \left(\frac{1}{x}\right)^6 + \left(\frac{1}{x}\right)^4 + \left(\frac{1}{x}\right)^3 + 1 \right]$$

Multiplied out, this gives,

$$1 + x^3 + x^5 + x^6 + x^9 \text{ or } + x^9 + x^6 + x^5 + x^3 + 1$$

So an LFSR with exclusive-or feedback from the ninth, sixth, fifth and third stages will provide the reverse time sequence of one with EXOR feedback from the ninth, sixth, fourth and third stages. Stated more simply, every term x_r is replaced by a term x_{n-r} . Here, r is less than n .

Convolvers for spread-spectrum systems

With a chipping rate of 6.3Mb/s, the spread-spectrum signal needs to be 'collapsed' at the receiver, back to the original unspread 100kb/s data. This is usually done at a convenient intermediate frequency, the receiver being up to this point a conventional superheterodyne type.

In one arrangement, the IF signal is fed into one transducer port of a convolver consisting of a SAW (surface acoustic wave) device using, typically, lithium-niobate material. The signal proceeds across the device as a surface acoustic wave, passing underneath a 'collector' electrode, forming the device's output. Another input, physically at the opposite end, is fed with a signal at the IF centre frequency, consisting of a CW (continuous wave) signal that has been chipped with the time reverse sequence.

Under the collector, the two surface waves, travelling in opposite directions, interact due to the piezo-electric non-linearity of the material, to provide an output at the original 100kb/s data rate. Thus the spread data is collapsed back to the original data rate. On the other hand, any interference, such as an attempt at jamming with a CW signal, is spread out by the local reverse sequence signal, to a low level. With the chipping rate at 63 times the data rate, the device provides - ideally - 18dB of 'processing gain' to the wanted signal, hopefully raising it above the level of the now spread interference.

Creating a noise source

Since the maximal length sequence for an LFSR with n stages is 2^n-1 , there is a component in the output at a frequency of $f_{min}=f_c/(2^n-1)$, where f_c is the clock frequency. There are components also at all harmonics of the minimum frequency f_{min} , up to the clock rate.

The envelope of this spectrum is the well known $\text{sinc}x$ function, and the first zero of this occurs at the clock rate, as in Fig. 4. Only the first of the higher order loops of the spectrum is shown. This spectrum is caused by the distribution of different length sequences of 0s and 1s in the overall sequence, which is as shown in Table 2. This table is taken from reference 2, which contains much further useful information.

As the longest runs in the overall sequence are n ones and $(n-1)$ noughts, if the sequence is low-pass filtered with a cut-off frequency lower than f_c/n , different length sequences of ones and noughts will result in different length positive- or negative-going ramps, all of the same slope.

Fig. 5. Showing how low-pass filtering the sequence provides a random noise-like waveform. This illustration is reproduced from reference 3.

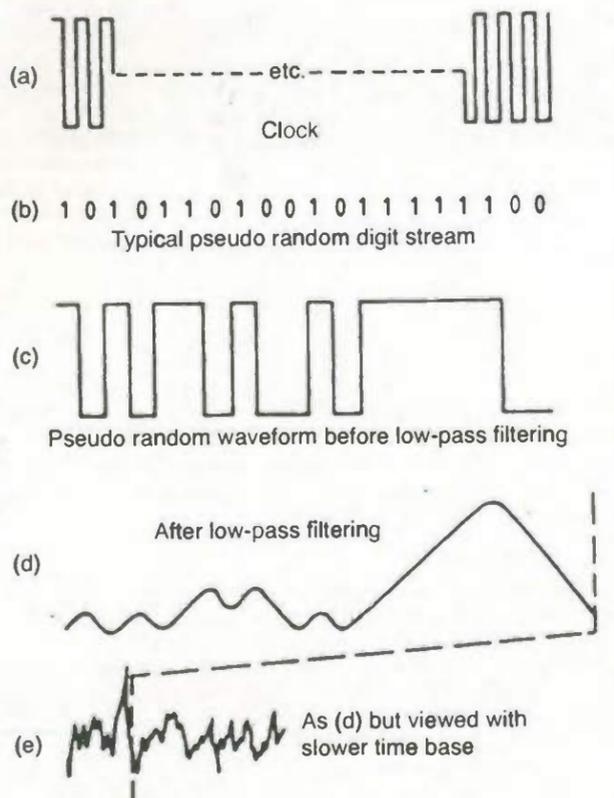


Table 2

Number of runs of consecutive 0s and consecutive 1s, up to n ones and $n-1$ noughts in the maximal-length output sequence of an n stage LFSR using exclusive-or gating. In this case, n noughts is the forbidden degenerate state.

Run length	Consecutive 1s	Consecutive 0s
n	1	0
$n-1$	0	1
$n-2$	1	1
$n-3$	2	2
$n-4$	4	4
...		
2	$2n-4$	$2n-4$
1	$2n-3$	$2n-3$

The result is a random noise-like waveform, as illustrated in Fig. 5. This is taken from reference 3, which describes an instrument that did not work exactly as planned. It was supposed to produce audio-frequency noise from a maximal-length sequence, but the article stated that start-up was like Fig. 3, whereas a maximal length sequence must start up immediately, as in Fig. 2.

The error was promptly pointed out by a reader, it being always open season for shooting down authors - a healthy tradition of this journal. The noise source was however used in a more recent article⁴ and the operation of the instrument was investigated.

This investigation cleared the original fault, and uncovered an interesting and unexpected fact: a low-pass filtered PRBS does not necessarily provide a Gaussian amplitude distribution. A redesign was therefore incorporated to provide the desired distribution, but that must be a subject of a later article.

Meanwhile, if you want to experiment with LFSR PRBS generators of different lengths, the necessary taps for shift registers with up to 32 stages long are given in reference 5. For most register lengths, there is a 'trinomial', - a polynomial with just the three terms x^n , x to some lower power, and unity. These can be implemented with a single EXOR gate.

Reference 6 gives taps for lengths up to 45 stages for those degrees that have a trinomial. This list of trinomials is extended, for degrees up to 1000 (!), in reference 7.

Reference 8 points out that a pseudo-random binary sequence generator can be made from just a CD4006 18-

stage shift register and a CD4070 quad exclusive-or gate - and of course a clock source. The length of the sequence is $2^{18}-1$ or 262 143 bits long.

References

1. Error correcting codes, Peterson and Weldon, M.I.T. Press, 1st Ed. 1961 (later editions available).
2. Pseudo noise sequences for engineers, R N Mutagi, *Electronics & Communication Engineering Journal* (IEE), April 1996, pp. 79-87.
3. Wide-range noise generator, Ian Hickman, *Wireless World* July 1982, pp. 38-40.
4. Waveform Distributions (Beginners' Corner), Ian Hickman, *Electronics World* January 2001, pp. 54-57.
5. The Ouroboros, Clive Maxfield, *EDN* 4 Jan 1996, pp. 135-142 (Note: the left hand column of Fig. 2 is wrong).
6. On the factorization of trinomials over GF(2), S W Golomb, L R Welch and A Hales, Memorandum No 20-189, Jet Propulsion Laboratory, California Institute of Technology, Pasadena, California, 1959. This article is quoted in Pseudorandom-sequence generation with trinomials, W Freeman, *Electronic Product Design* 1988, pp. 18 and 19.
7. On primitive polynomials (mod 2), N Zierler and J Brillhart, *Information and Control*, December 1968, 13, pp. 54-544.
8. 250k bit sequence generator, A S Poulton, *Electronic Product Design*, Oct. 1982, p. 27.

THE OSCILLOSCOPE IS MOVING ON...

Features:

- ▲ A fraction of the cost of benchtop scopes
- ▲ Save multiple setups, for ease of use
- ▲ Save, print and e-mail your traces
- ▲ FREE software and upgrades
- ▲ Automated measurements
- ▲ Large colour displays
- ▲ Scope, spectrum analyser & meter functions

Ask for a **FREE** catalogue and demo software, or visit:

www.picotech.com



...DON'T GET LEFT BEHIND

Tel: +44 (0) 1480 396395, Fax: +44 (0) 1480 396296, E-mail: post@picotech.com

CIRCLE NO. 110 ON REPLY CARD

EMI tips and fixes

Leading off with an EMI backgrounder, Joe Carr presents tips and fixes for minimising interference.

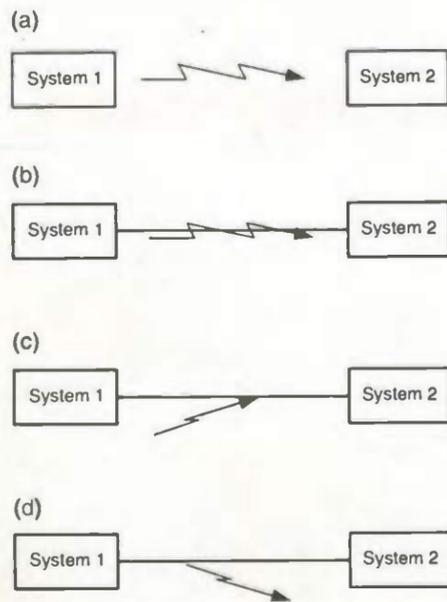


Fig. 1. There are two basic ways in which EMI is transmitted; radiation, a) and conduction, b). Conduction from radiation entering the system is represented in c), while d) shows radiation resulting from conduction.

Electronic pollution is all around us. Radio and noise waves impinge on us all of the time. Never has electromagnetic interference (EMI) been so great as it is today.

One source defines EMI thus: "...electromagnetic interference is a degradation in performance of an electronic system caused by an electromagnetic disturbance." At worst, EMI can cause a loss of human life, as when it interferes with an aircraft or automobile electronic system. At best, it will pass unnoticed or will interfere with the electronic system on a sub-audible basis.

The European Community has issued regulations pertaining to EMI in all manner of electrical and electronic equipment. Any electrical and electronic product sold in Europe must exhibit that it neither emits nor is affected by radiation and conduction of EMI. In other words, it must be electromagnetically compatible (EMC).

Means of EMI transmission

EMI is transmitted from the source to the victim system in two basic ways: conduction and radiation. The difference is that the EMI travels along a wire in conduction, and travels by air in radiation. In general (but not always), radiation Fig. 1a), occurs at high frequencies above 30MHz, and conduction Fig. 1b), occurs at frequencies less than 30MHz.

In some cases, both radiation and conduction can occur. In those cases, either radiation occurs first, and then the wave is conducted into the equipment on a line, Fig. 1c), or the radiation occurs after conduction Fig. 1d).

In general, the existence of EMI can occur only if:

- there is a source of energy,
- there is a receiver of that energy, and
- there is a transmission path between the two.

If any of the three does not exist, EMI cannot occur.

What we do about EMI depends on the situation. For example, in the case of some noise sources we can turn it off or otherwise suppress it. In other cases, we might have to live with the effects of EMI as best we can.

Electronic noise

Noise comes in two different types: continuous and transient. By definition, noise has been standardised as 'transient' if it lasts less than a sixtieth of a second, i.e. 16.67ms, and continuous if it lasts longer.

Continuous noise. Low-frequency noise sources include fluorescent lights, electric motors, and switching-mode DC power supplies. High-frequency noise is mostly radio-frequency interference, or RFI. It can originate in either radio transmitters, computer clocks or other sources.

In the typical RFI environment, signals levels can be between a few microvolts/metre and 300V/metre. While the latter field strengths are only found close to transmitting antennas for high-power radio and radar stations, anything in excess of 1V/m can cause damage to unprotected circuits.

Test specifications for commercial systems may call for protection to 10V/m, while automotive and medical environments can call for up to 200V/m and military environments up to 300-400V/m.

Analogue circuitry tends to be more influenced by RFI than digital circuitry because it can be interfered with by lower voltage fields.

Transient noise. A 'transient' is any temporary over voltage or over power condition that lasts for less than 16.6ms. Transients are either repeatable or random in nature. An example of the repeatable type of transient is the discharge of an inductor or capacitor. Examples of random type transients include electrostatic discharge (ESD), lightning, and the nuclear electromagnetic pulse.

In the case of lightning, Fig. 2 shows the exposure of the US electrical power system to lightning strikes. Clearly, high-voltage lines are struck more frequently than low voltage lines. Unfortunately, that exposure transmits along the lines to your home or business to disrupt electronic circuits.

In fact, the lightning doesn't have to actually strike the line. Coupling via inductance, it can cause disruptive currents to flow in the power system by striking something close!

Counters to EMI

There are two effective ways to counter EMI: shielding and filtering, Fig. 3. Shielding is used to guard against radiation interference, whilst the filter is used to guard against conduction interference. The filters have the advantage of being bi-directional, so they also prevent interference from flowing out of the system as well as prevent it from flowing in.

Shielding. Shielding is used to attenuate the interfering RF signal before it reaches the protected circuitry. Very frequently, the hidden difference between a higher-priced appliance and a lower-priced one is in the internal shielding that one gets. Consider computer monitors for example. The principal difference between a high-priced model and a cheap one is in the shielding that is provided.

Unfortunately, all shielded enclosures for electronic projects are not created equal. Some enclosures are butt fitted, and have dimples or notches to hold the half shells together. As far as I am concerned,

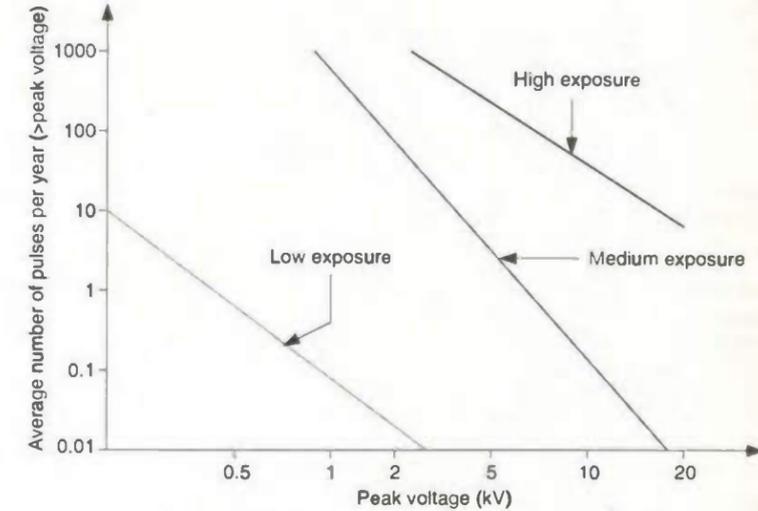


Fig. 2. Average lightning strikes against USA power systems.

the minimum requirement for low-frequency radiation noise is shown in Fig. 4a). Note that the flange of the lower half shell overlaps the upper half shell by at least 4 to 6mm.

Four screws, of which only two are shown, hold the assembly together. For high frequencies, even this box is insufficient, but it can be made suitable by adding of more screws, Fig. 4b). The rules are that the screws should be not more than one half wavelength apart, and one-eighth wavelength is better.

Filtering. Filtering can take on different meanings for different situations. In general, most EMI filters are low-pass filters, although high-pass and bandpass filters exist. In some cases of a particular interference being the cause of interference, a notch filter may be used.

In general, a perfect, ideal single component filter – either a capacitor or inductor – has a theoretical roll-off or gain of -20dB/decade, with a practical maximum of something between -60 and -120dB. In fact, real components do not achieve that theoretical goal. Capacitors are more useful in high-impedance circuits, whereas inductors are more useful in lower impedance circuits.

Perhaps the simplest form of single component filter is the feedthrough capacitor, also known as an 'EMI filter'. When combined with good shielding, such a capacitor can be quite sufficient.

Figure 5 shows two methods of passing a feedthrough capacitor through a shielded panel. Figure 5a) shows the screw-in variety. The threaded nut is cinched tight against the chassis or panel. Figure 5b) shows the installation of a solder-in type of feedthrough capacitor. A

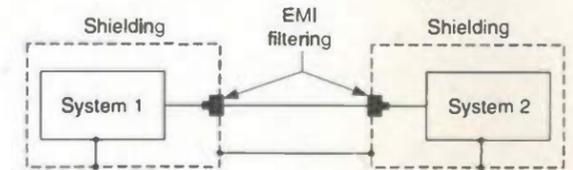


Fig. 3. Shielding and EMI filtering are suitable defenses.

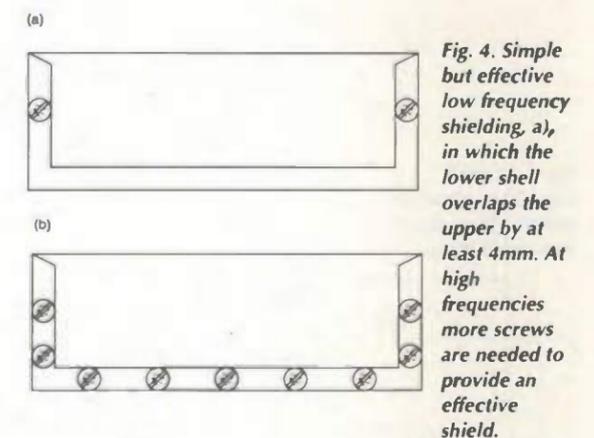


Fig. 4. Simple but effective low frequency shielding, a), in which the lower shell overlaps the upper by at least 4mm. At high frequencies more screws are needed to provide an effective shield.

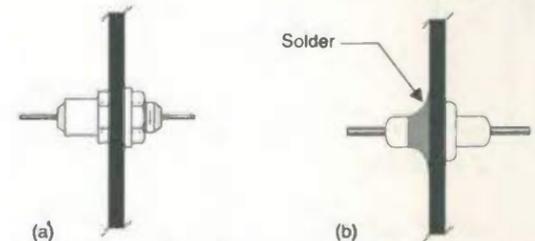


Fig. 5. Two types of feedthrough capacitor.

small fillet of solder is used to hold the capacitor against the chassis or panel. This type of capacitor assumes a solderable chassis or panel, thus it eliminates the use of aluminium.

Where greater suppression is needed, a combination of L and C elements is needed. A two-component L-section filter is shown in Fig.

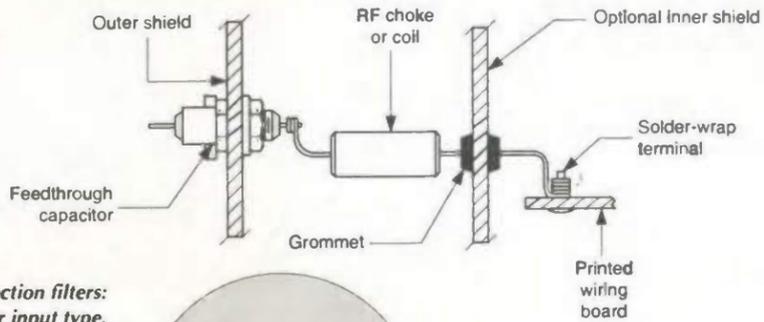


Fig. 6. Simple L-section filters: a) internal capacitor input type. b) external inductor input type.


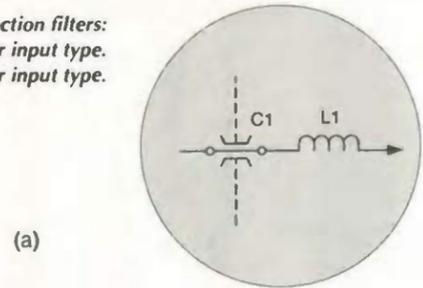



Fig. 7. Several impedance situations and the filters to implement them.

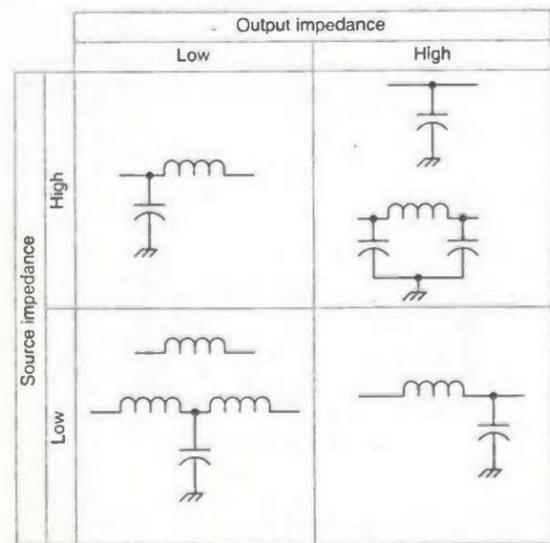

6a). This filter produces a theoretical gain of -40dB/decade , which means 100:1 per decade between input and output signals. Such a filter can be used at any frequency, although the values will tend to differ between, say, LF and VHF. The ideal is to keep the lead lengths as short as possible to prevent radiation of the signal. As an alternative, a higher-order filter can be realised by replacing the grommet in Fig. 6a) with a second feedthrough capacitor. In that case, a theoretical gain of -60dB/decade is realised.

In Figure 6b) you can see a case where the opposite situation occurs, i.e. the inductor input L-section

Fig. 8. Differential signals, a), versus common-mode signals, b).

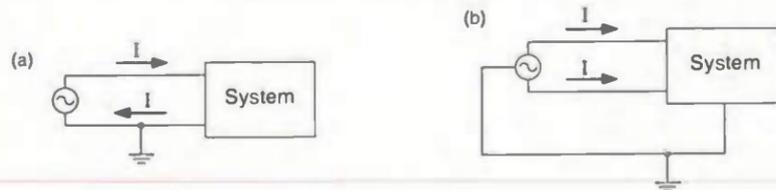

filter. In this case, the inductor or RF choke is mounted external to the chassis, and directly drives the feedthrough capacitor.

Figure 7 shows a graphic of what filters to use when the source impedances are known. For example, in the case where the input impedance and the output impedance are both low, then use either a single inductor or RF choke, or a T-filter consisting of two inductors and a capacitor.

When the source impedance is high, and the output impedance is low, then use a single capacitor input L-section filter. Similarly, when the input impedance is low, and the output impedance is high, use an inductor input L-section filter.

Finally, when the input and output impedances are both high, use either a single capacitor, or a pi-section filter as shown.

Common-mode and differential currents

Noise currents can flow in two modes: differential and common mode. These are defined as follows:

Differential mode. As shown in Fig. 8a) there is a conducted signal on a signal line that is returned along the return line, or via a grounded connection. The noise current is characterised by the arrows flowing in different directions.

Common mode. In common mode, conduction noise appears in multiple conductors flowing in the same direction.

The filtering necessary for differential and common mode filtering is different. In differential-mode filtering, it is necessary to place a filter in series with the 'hot' lead, with suitable bypassing to ground. In the common mode case the same filtering must be applied to all affected leads.

Figure 9 shows a filter that is suitable for both differential and common-mode forms of EMI.

AC power-line filtering

The AC power lines are a source of

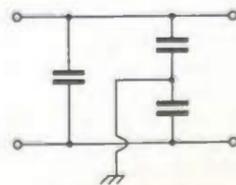


Fig. 9. Filter for both differential and common mode signals.

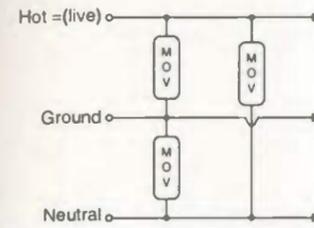


Fig. 10. Metal oxide varistors (MOV) use on AC power mains for clamping spikes.

conducted EMI and must be filtered extensively to make them really clean.

Not only should the AC lines be filtered against RFI, but also against lightning strikes at a distance. The lightning and other high-voltage transients can be handled as per Fig. 10 with metal oxide varistors, or MOVs. These devices are made by various suppliers, and can act like a pair of zener diodes back-to-back. In other words, they snip the high voltage transient to a lower level, regardless of polarity.

Basically, MOVs act like an insulator at lower voltages. But when a certain critical threshold voltage is exceeded, the varistor develops a low resistance, shunting the offending voltage transient to a low value. Varistors are used primarily for transient voltage spikes on the AC power line.

For RFI, a filter must be provided to the AC power line. Figure 11 shows a suitable filter that affects both common-mode and differential RFI on the line. When the values are high enough, it will also protect somewhat against lightning and other transients. This is because those transients have a high frequency component as well as the fundamental frequency.

Suitable filters have been moulded into AC power line sockets.

Special medical EMI problems EMI problems exist in medical electronic devices such as electrocardiograph (ECG) or electroencephalograph (EEG) machines. These machines have to process signals in the order of a few microvolts to about a millivolt in the presence of strong interfering signals.

In addition to regular RFI problems, there are two additional problems. First, there is the problem of the defibrillator. This is a high voltage - several kilovolts in fact - capacitive discharge device used to 'jump start' the heart of a patient undergoing resuscitation.

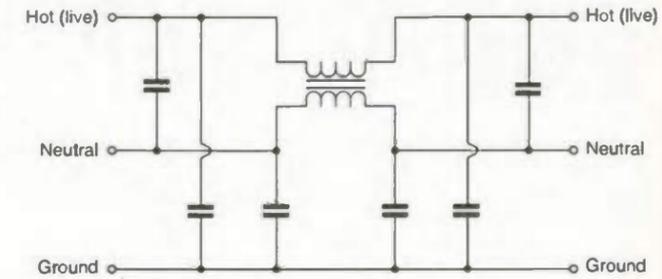


Fig. 11. AC power mains filter.

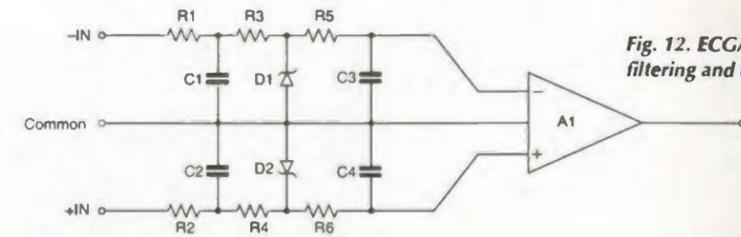


Fig. 12. ECG/EEG preamplifier filtering and defibrillator protection.

The second problem is in the application of 500kHz to 2500kHz high powered RF electrosurgery units just a few centimetres from the site of the EEG or ECG electrodes. As much as 400 or 500 watts of RF could be applied to the 'circuit' only a few centimetres from the pick-up electrodes!

Figure 12 shows the input to a bioelectric amplifier suitable for EEG or ECG use in the presence of high electrical or electromagnetic fields. Both defibrillator and electro-surgery units can be accommodated by the filtering shown.

Signals involved in ECG and EEG are below 100Hz, so an RC filter will suffice in this case. The RC filter consists of resistors R1 through R6, and capacitors C1 through C4. This is a low-pass filter.

The defibrillator protection is the zener diodes and series resistors R1-R3 and R2-R4 between the source and amplifier A1. Sometimes, in older machines neon glow lamps like the NE-2 are used instead of the zener diodes. The disadvantage of the neon lamps is their relatively high protection voltage.

Computer EMI

The case of computer EMI is very serious. Just place an AM radio anywhere close to a modern computer, and you will hear lots of hash. In fact, with computer clock speeds reaching several hundred megahertz, the interference to FM radios can be tremendous.

Figure 13 shows a method for connecting a digital connector pin that can carry EMI to a printed wiring board. The ferrite beads act like little RF chokes, so will elimi-

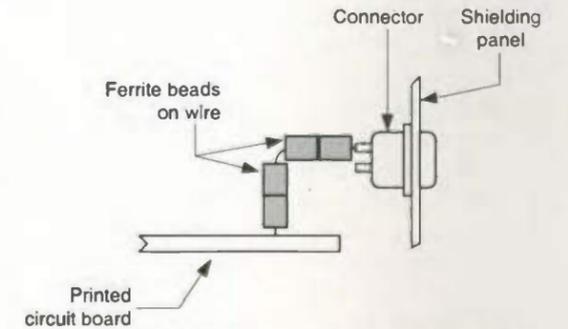


Fig. 13. Computer connector fitted with ferrite beads.

nate RFI in the VHF/UHF region. Because the filtering is bi-directional, it will attenuate noise going out as well as coming into the computer.

The principal offender with respect to noise from computer systems is the monitor. This is because of two factors. First, the deflection circuits tend to operate in frequency ranges - under 40kHz - that are below many other systems, and they have lots of harmonics. Second, those deflection circuits tend to be high power.

The answer to the problem is to place shielding around the circuits, and placing a common-mode choke in the signal line.

In summary

EMI protection is often an afterthought in the design of electronic equipment. It should be a first requirement, but unfortunately this isn't often the case. The methods that I have just discussed will go a long way towards suppressing the RFI or transient conditions on the signal or power lines.

Reader offer

600W MOSFET power amplifier

£100

fully inclusive of vat and UK postage

Profusion's extremely high reliability Exicon MOSFET amplifier comes complete with comprehensive technical application and engineering documentation. This is an evaluation amplifier, hence there's flexibility in how you configure it.

These monophonic modules provide class-leading performance in power amplification, delivering from 100W to over 500W with additional heat sinking into 4Ω.

Features include; total harmonic distortion less than 0.01% at 1kHz, a slew rate of over 100V/μs and a power bandwidth of more than 100kHz.

Normally, this ready-built evaluation amplifier costs £95 plus postage and packing and VAT. Using the coupon accompanying this advertisement, *Electronics World* readers can obtain it for £85 plus VAT – with free delivery anywhere in the UK.

A PDF file containing a description of the amplifier together with circuit diagram can be obtained by e-mailing gs@profusionplc.com. Please use the subject heading 'Electronics World'.


Details on power supply and implementation requirements are given in comprehensive documentation accompanying the amplifier module.

For overseas mailing details, contact Profusion plc, Aviation Way Southend-on-Sea Essex SS2 6UN, UK. Tel: +44 (0) 1702 543500, fax: +44 (0) 1702 543700, e-mail: gs@profusionplc.com

Why Exicon MOSFETs?

Exicon MOSFETs are of a rugged design and free from thermal runaway, making them extremely reliable.

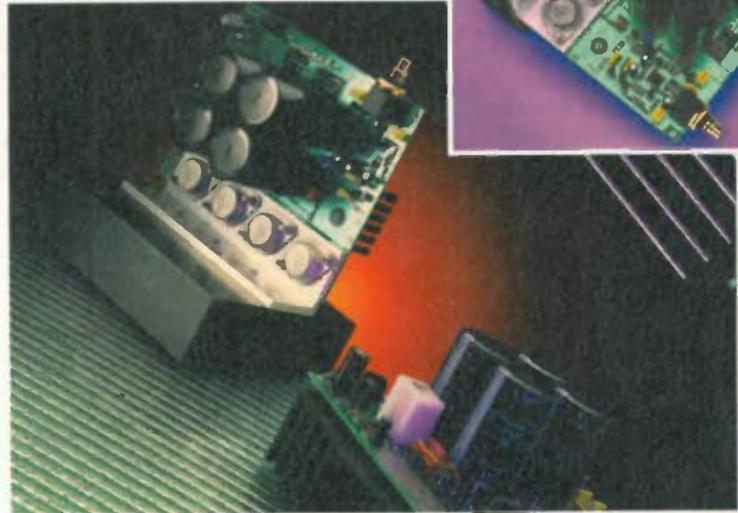Typical output power of these products ranges from 100W to more than 3kW. Their applications are audio power amplifiers for use with high power PA systems, musical instruments and hi-fi equipment. Industrial applications will be linear motor drives, linear inverters and vibration tables.



Use this coupon to order your Exicon MOSFET Evaluation Amplifier

Please send me Exicon MOSFET evaluation amplifiers at the special offer price of £100 fully inclusive*.

Name

Company (if any)

Address

Phone number/fax

Total amount £.....

Make cheques payable to Profusion plc
Or, please debit my Master/Visa card.

Card type (Master/Visa)
Card No
Expiry date

Please mail this coupon to
Profusion plc, Aviation Way, Southend-on-Sea, Essex SS2 6UN, UK.
Tel: +44 (0) 1702 543500 Fax: +44 (0) 1702 543700
e-mail: gs@profusionplc.com
*Readers outside the UK please contact Profusion for a quote for shipping.


Unique Audio Components for Innovative Electronic Engineering

That Corporation
Wolfson
Exicon
Neutrik
Semelab

Sanyo
JRC
Sanken
Trobo
Fagor



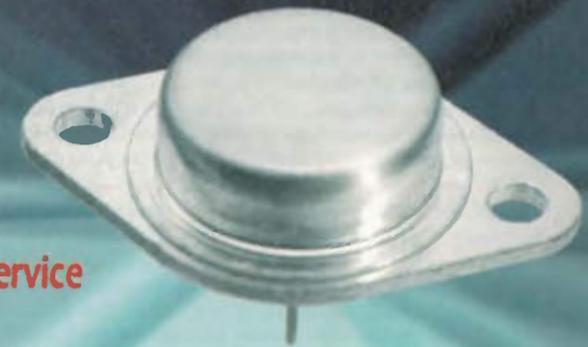- Easy on-line Ordering
- Fast Delivery by UPS
- Worldwide Distribution
- Download Free Data Sheets
- Guaranteed Quality Products & Service



Profusionplc.com

Profusion plc Aviation Way Southend Essex SS2 6UN UK
Tel: +44 (0) 1702 543500 Fax: +44 (0) 1702 543700



Cert No. RS34065

Analogue I/O for the PC

Plugging into a PC's ISA slot, Tariq Iqbal's analogue i/o card provides eight 12-bit resolution inputs and one 8-bit output. A few QuickBasic routines - including one for displaying thermocouple temperature - demonstrate how easy it is to read and write analogue voltages.



of the PPI. Port B and the upper half of port C are used to interface a a-to-d converter.

Three least-significant bits of port C are used to switch analogue multiplexer. Bit 3 of port C is used for starting a conversion, Fig. 1. A detailed circuit diagram is presented in Fig. 2.

Address decoding corresponding to address 792 is achieved by two 74LS85 comparators and a 74LS00 NAND gate. The 74LS245 bus transceiver is meant to provide protection against any bus clash.

A DAC0800 d-to-a converter is interfaced to port A of the 8255 PPI. The a-to-d converter is a 12-bit resolution AD574 from Analog Devices. Lower byte data output of this device is supplied directly to port B of 8255, while a nibble of high byte is supplied to the upper nibble of port C.

A start-of-conversion pulse following the sequence high→low→high is generated and supplied to the a-to-d converter by port C, bit 03 of the 8255. In this card the a-to-d converter is configured to measure input voltages in the range ±5V DC.

To increase the number of channels to 8 inputs a 4051B analogue multiplexer is used at the input of a-to-d converter. Channel selection is made by the lower 3 bits of port C.

Inputs marked CH0-CH4 are directly available on the 25pin connector and they have a signal range of ±5V DC.

Two AD595 thermocouple amplifiers and one AD521 instrumentation amplifier are also present on the card. Channels 5 and 6 are reserved for the thermocouple amplifiers. Two K type thermocouples may be directly interface with this card.

Hardware details

Interfacing of the a-to-d and d-to-a converters to the ISA bus is done using an 8255A parallel peripheral interface. The d-to-a converter connects to port A

Channel 7 is reserved for the instrumentation amplifier, whose gain can be selected as 100 or 1000 by a slide switch. The AD521 instrumentation amplifier can be used for interfacing with resistance bridges - e.g. strain gauge - and various other sensors like thermistors and RTDs.

On my prototype, +12V, -12V, +5V and -5V supplies from the PC are also available on the 25 pin D-type connector.

Table 1 provides necessary addresses of I/O card and control word. Table 2 gives the details of I/O available on 25 pin D-type connector.

Table 1. Addresses of the I/O card.

Address	Function
795	Control word
792	Port A
793	Port B
794	Port C

Table 2 Signals at I/O card connector

Pin	Signal
1	GND
2	Analogue input CH 0
3	Analogue input CH 1
4	Analogue input CH 2
5	Analogue input CH 3
6	Analogue input CH 4
7	GND
8	-TC _{in} CH#5
9	+TC _{in} CH#5
10	GND
11	-TC _{in} CH#6
12	+TC _{in} CH#6
13	GND
14	-IN CH#7
15	+IN CH#7
16	GND
17	Analogue output
18	NC
19	NC
20	NC
21	NC
22	-12V From PC bus
23	+12V From PC bus
24	-5V From PC bus
25	+5V From PC bus

Fig. 1. Block diagram of the analogue I/O card for the PC.

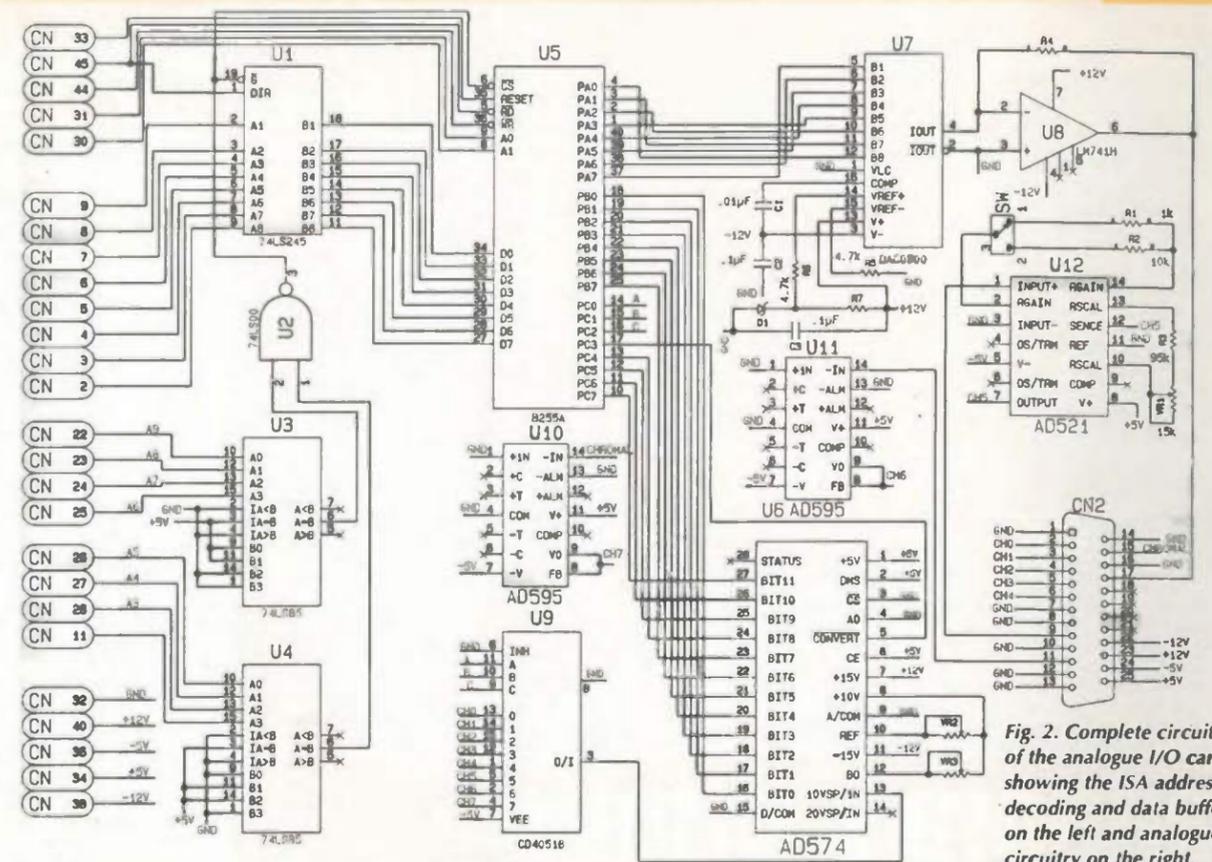
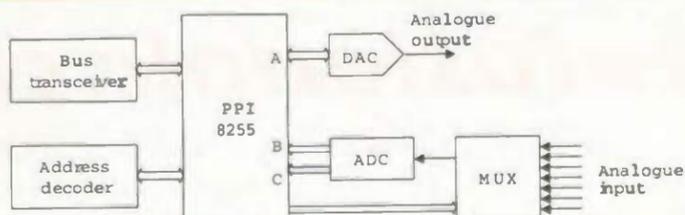


Fig. 2. Complete circuit of the analogue I/O card, showing the ISA address decoding and data buffering on the left and analogue circuitry on the right.

Programming

Programming of the I/O card is relatively simple using Microsoft's QuickBasic. A routine for reading data from channel 0 is provided in List 1. After a start of conversion first a low byte is read and then low nibble of high byte is read.

Output from the a-to-d converter is constructed by com-

paring low and high bytes. Since the input range of converter is ±5V, a simple calibration equation at the end of program is used to transform the converter's output into equivalent voltage.

A program for providing an analogue voltage output is given in List 2. Analogue output is in the range is 0 to 10V. Sending 00 to address 792 results a 0V at the output, while sending 255 to the same address results a 10V at the output. This routine generates a saw tooth waveform at the output. Any desired voltage can be generated at the d-to-a converter's output by using List 3.

A simple program to read K type thermocouple attached to pin 8 and 9 of the D-type connector is in List 4. Output of the thermocouple amplifier AD595 is calibrated at 10mV/°C.

It is useful to allow a prototyping area on the card for building additional interfacing circuits. I have used this card to measure parameters such as blood pressure, motor angular velocity, motor position, flow rate, respiration rate, body temperature, force on a load cell, and water level. This is a multipurpose card and has many applications.

List 1. A routine for reading an analogue voltage applied to channel 0 of the I/O card could be written as follows.

```

OUT 795, 138 'CONTROL WORD
CH% = 0
SC% = CH% + 8
OUT 794, SC% : OUT 794, CH% : OUT 794, SC%
LB% = INP(793) : HB% = INP(794)
HB% = HB% \ 16
d% = LB% + HB% * 256
VOLTS = d% / 4096 * 10.14 - 5.07
    
```

List 2. Routine for writing values to the analogue output port to produce a sawtooth waveform.

```

OUT 795, 138
10 FOR N% = 0 TO 255
OUT 792, N%
NEXT N%
GOTO 10
    
```

List 3. Routine for producing a specific voltage at the d-to-a converter's output.

```

OUT 795, 138
10 INPUT "VOLTS TO BE OUTPUTTED" = ";V
OUT 792, CINT(V*25.5)
GOTO 10
    
```

List 4. Simple routine for reading and displaying the temperature of a thermocouple.

```

OUT 795, 138 'CONTROL WORD
CH% = 5
SC% = CH% + 8
OUT 794, SC% : OUT 794, CH% : OUT 794, SC%
LB% = INP(793) : HB% = INP(794)
HB% = HB% \ 16
d% = LB% + HB% * 256
VOLTS = d% / 4096 * 10.14 - 5.07
Temp = 100 * VOLTS
Print "Temperature C° = "; Temp
    
```



Pandora's drums

Unique and atmospheric music recorded in the early 1900s – the days before 78s.

£11.99

Available exclusively from
Electronics World

21 tracks – 72 minutes of recordings made between 1900 and 1929. These electronically derived reproductions are no worse than – and in many cases better than – reproductions of early 78rev/min recordings – some are stunning...

All tracks on this CD were recorded on DAT from cylinders produced in the early 1900s. Considering the age of the cylinders, and the recording techniques available at the time, these tracks are of remarkable quality, having been carefully replayed using modern electronic technology by historian Joe Pengelly.

Use this coupon to order your copy of Pandora's drums

Please send me CD(s) at £11.99 each including VAT plus £1.50 carriage per order, for which I enclose:

Cheque

Credit card details tick as appropriate

Name

Address

Phone number

Total amount £.....

Make cheques payable to Cumulus Business Media
Or, please debit my credit card.

Card type (Master/Visa)

Card No

Expiry date

Please mail this coupon to *Electronics World*, together with payment. Alternatively fax credit card details with order on 020 8643 8952.

Address orders and all correspondence relating to this order to Pandora's drums, Electronics World, Cumulus Business Media, Anne Boleyn House, 9-13, Ewell Road, Cheam, Surrey, SM3 8BZ

Track

- 1 *Washington Post March*, Band, 1909
- 2 *Good Old Summertime*, The American Quartet 1904
- 3 *Marriage Bells*, Bells & xylophone duet, Burckhardt & Daab with orchestra, 1913
4. *The Volunteer Organist*, Peter Dawson, 1913
5. *Dialogue For Three*, Flute, Oboe and Clarinet, 1913
6. *The Toymaker's Dream*, Foxtrot, vocal, B.A. Rolfe and his orchestra, 1929
- 7 *As I Sat Upon My Dear Old Mother's Knee*, Will Oakland, 1913
- 8 *Light As A Feather*, Bells solo, Charles Daab with orchestra, 1912
- 9 *On Her Pic-Pic-Piccolo*, Billy Williams, 1913
- 10 *Polka Des English's*, Artist unknown, 1900
- 11 *Somebody's Coming To My House*, Walter Van Brunt, 1913
- 12 *Bonny Scotland Medley*, Xylophone solo, Charles Daab with orchestra, 1914
- 13 *Doin' the Raccoon*, Billy Murray, 1929
- 14 *Luce Mia!* Francesco Daddi, 1913
- 15 *The Olio Minstrel*, 2nd part, 1913
- 16 *Peg O' My Heart*, Walter Van Brunt, 1913
- 17 *Auf Dem Mississippi*, Johann Strauss orchestra, 1913
- 18 *I'm Looking For A Sweetheart And I Think You'll Do*, Ada Jones & Billy Murray, 1913
- 19 *Intermezzo*, Violin solo, Stroud Haxton, 1910
- 20 *A Juanita*, Abrego and Picazo, 1913
- 21 *All Alone*, Ada Jones, 1911

Total playing time 72.09

21 tracks – 72 minutes of music
Published by *Electronics World*. All recordings reproduced by Joe Pengelly.

OLSON

Connecting to the 21st century
with 40 years of experience

OFFER NO. 113 ON REPLY CARD

OLSON networking products



OLSON distribution panels



OLSON IEC 320 connection



2000 Product Guide

Call for
our NEW
products
catalogue
today!

020 8905 7273

OLSON ELECTRONICS LIMITED



1961-2001

OLSON HOUSE, 490 HONEYPOT LANE, STANMORE, MIDDX HA7 1JX
TEL: 020 8905 7273 FAX: 020 8952 1232
e-mail: sales@olson.co.uk web site: http://www.olson.co.uk

Being able to create two identical but phase-shifted sine waves is useful for testing, but generators capable of producing them are rare. To rectify this, **W Q Yang** and **T Y Ng*** have produced a design using two high-performance direct digital synthesis chips to produce two 1V signals at frequencies up to 16MHz. Under the control of an RS232 port, these signals can be used together, with fully adjustable phase shift, or independently.

Phase-shiftable signal generator

Many applications in industry and laboratories require the use of signals with certain phase difference or of adjustable phase shift between two signals. Phase-sensitive demodulation is one example, whose output depends on the phase difference between input signals.

Other examples include signal mixers, vector generators, selective voltmeters, rotational torque induction, etc. All of these applications lead to the demand for highly versatile signal generators that can provide the user with full control over the signal's amplitude, frequency and phase.

The phase of a signal can only be measured and shifted with respect to a reference signal. There are no simple and direct methods to generate phase shifts.

At present, phase differences between signals are produced using dedicated phase-shifting networks and circuits that provide limited and inflexible phase shifts. Although function generators are well established as the most versatile of signal sources, they do not have the capability to change the phase of the signals. This is a major drawback – especially when phase shifting or phase difference between signals is required.

Direct digital synthesis, or DDS for short, has long been recognised as a superior technique for generating highly accurate signals of low distortion over a wide frequency range. With DDS, the amplitude, frequency and phase of the generated signals can be easily and instantaneously controlled.

Using two DDS chips, we have developed a dual synchronous DDS signal generator. It is small, lightweight and has all the advantages of DDS technology in term of performance and cost.

The generator derives its power through an external 9V power adapter. It can be operated through a PC's RS232 serial port with the developed Visual Basic software and the generated signals are fully user programmable.

Both DDS chips can be operated individually to produce two independent signals, or as a synchronous pair to produce two signals with the same frequency up to 16MHz. But the phase between them can be adjusted. Figure 1 shows the prototype.

In the first part of this article, details of the hardware and the operational principle of the system are given. The second part shows the user interface created using Visual Basic for controlling the signal generator, and lastly test results are given and future developments are suggested.

A block diagram of the generator is shown in Fig. 2 and Fig. 3 shows its detailed circuit. The system is made up of four parts: power supply, serial-to-parallel interface, data latching circuit and DDS chips and clock.

A 9V power adapter forms an external power source and a 78L05-voltage regulator provides the on-board power supply. The generator employs two AD7008 chips as a pair of signal generating sources controlled serially via the PC's RS232 port.

*Dr Yang is with UMIST, as was his co-author Mr Ng at the time of writing.

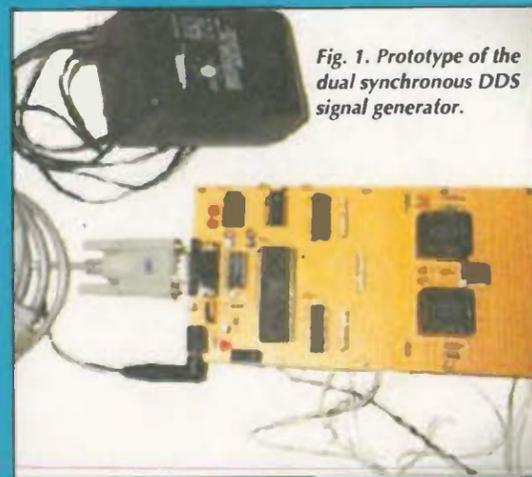


Fig. 1. Prototype of the dual synchronous DDS signal generator.

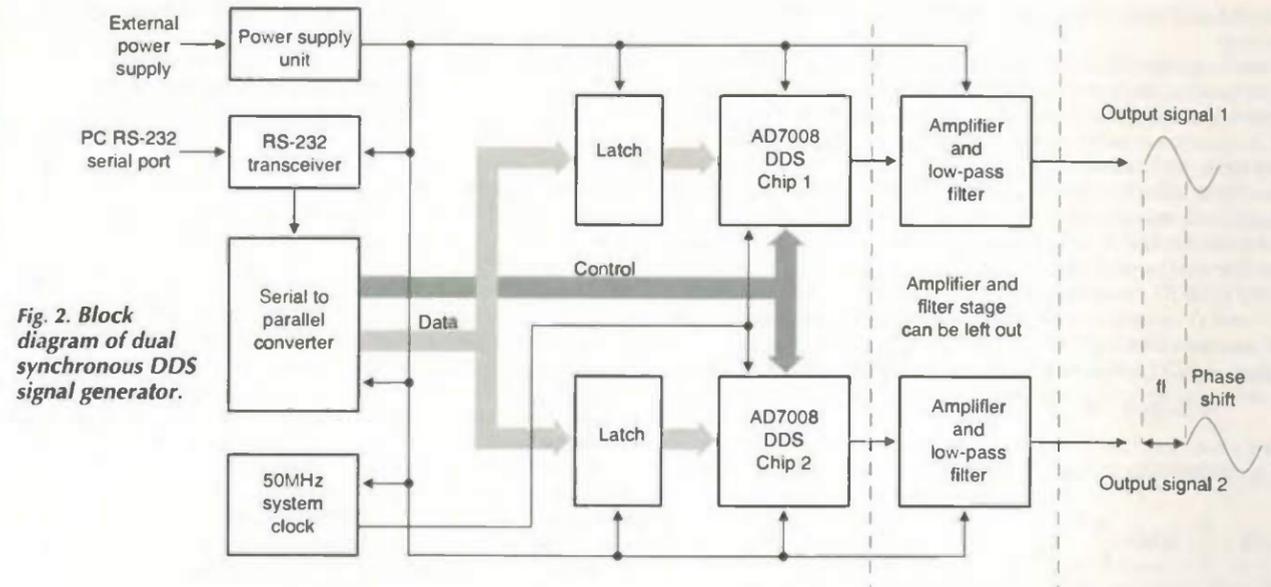


Fig. 2. Block diagram of dual synchronous DDS signal generator.

Digital synthesiser chip details

Analog Devices' AD7008 is a DDS device integrated on a single CMOS chip. A detailed introduction to DDS theory and the operation and control of the AD7008 DDS chip can be found in its data sheet.

Figure 4 is the functional block diagram of the chip. It consists of a numerically-controlled oscillator, or NCO, employing a 32-bit phase accumulator, sine and cosine look-up tables in ROM, in-phase and quadrature modulators and a 10-bit d-to-a converter.

Clock rates up to 50MHz are supported and the chip is capable of phase modulation, frequency modulation and both in-phase and quadrature amplitude modulation. The generated signal is controlled by loading values into the chip's registers either through its parallel interface or the serial interface. Registers 'Freq0 reg' and 'Freq1 reg' determine the frequency, 'Phase reg' determines the phase and 'IQMOD' determines the amplitude.

Read-only memory stores the quantised amplitude values of a sine/cosine wave. Given a phase step value – ΔPhase – stored in FREQ0 or FREQ1, the phase accumulator steps through the ROM repeatedly to produce the sine/cosine values. The sum of the two values is input to the d-to-a converter and a sinusoidal waveform of the desired frequency, f_{signal} , is reconstructed at the converter's output. Tuning for the chip is determined as follows.

$$f_{signal} = \frac{\Delta Phase \times f_{clock}}{2^{32}} \quad (1)$$

Here, $0 \leq \Delta Phase < 2^{32}$. Solving for ΔPhase,

$$\Delta Phase = \frac{f_{signal} \times 2^{32}}{f_{clock}} \quad (2)$$

From the second equation, the ΔPhase required to produce a specific f_{signal} is determined and loaded into either of the FREQ registers.

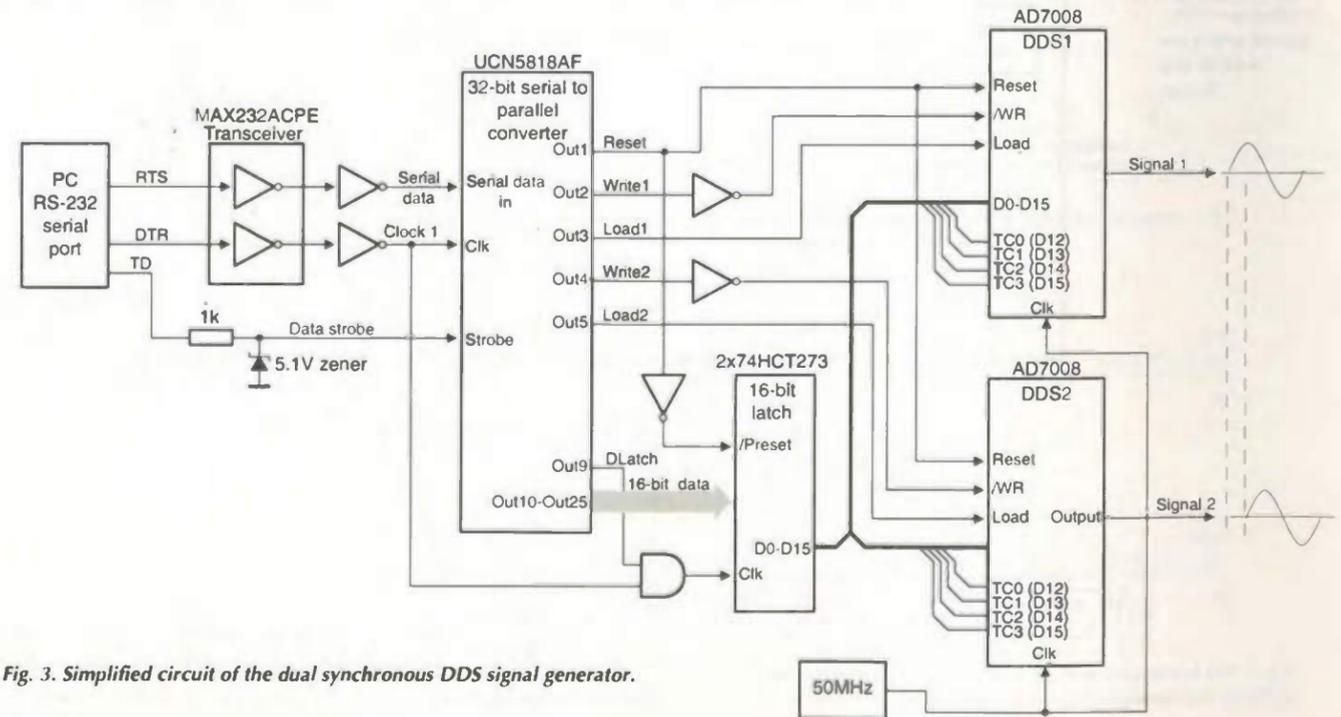


Fig. 3. Simplified circuit of the dual synchronous DDS signal generator.

The FSELECT pin is then used to select the register for generating the signal.

Even though the phase of the output signal can be offset using the 12-bit phase register, accurate phase shift cannot be produced due to the limited phase resolution provided by the register. Quadrature amplitude modulation is performed using IQMOD to generate the desired signal phase shift instead.

The 20-bit IQMOD register is used to control the amplitude of the cosine (I) and sine (Q) signal components generated from the ROM. Its first 10 bits, bits 0 to 9, define the I amplitude. The next 10, bits 10 to 19, define the Q amplitude.

Using IQMOD, quadrature amplitude modulation can be performed. The I and Q components are summed together before entering the DAC and their sum is given by,

$$I\text{component} + Q\text{component} = A \cos \omega t + B \sin \omega t = R \sin(\omega t + \theta) \quad (3)$$

where,

$$R = \sqrt{A^2 + B^2}$$

$$\cos \theta = \frac{B}{R}, \sin \theta = \frac{A}{R}$$

Equation 3 shows that by summing the I and Q components together, a signal of amplitude R and phase angle θ is produced. The values of R and θ depend on two amplitudes, A and B. Conversely, given the desired signal amplitude R and phase angle θ, the required amplitudes of the I and Q components can be determined by equations 4 and 5.

$$A = R \sin \theta \quad (4)$$

$$B = R \cos \theta \quad (5)$$

Here, $0 \leq R \leq 1V_{pk-pk}$ and $0^\circ \leq \theta \leq 360^\circ$. By loading the determined A and B values into IQMOD, the generated signal will have the desired amplitude and phase shift.

Capable of producing low distortion signals on its own, the AD7008 chip does not require additional output signal conditioning. It has an output compliance of 1V pk-pk.

Serial-to-parallel interface

In this design, a PC's RS232 is used to control the generator. Figure 5 shows that RS-232 port has only three output pins for sending signals, namely RTS, DTR and TD. These are not enough for sending data to and controlling the AD7008 chips.

Therefore, a serial-to-parallel interface is used to produce a 16-bit data bus and a 5-line control bus to both AD7008s. The AD7008 chips are configured to operate in 16-bit parallel-loading mode. Serial signals sent from the RS232 port to the generator are converted into parallel form for use as either control signals or as data to be loaded into the chip's registers.

Data control signals RTS and DTR are first converted from RS-232 voltage level into TTL using a MAX232ACPE low power RS-232 transceiver. The transmit-data pin TD is converted into -0.6V to +5.1V using a voltage clamping circuit consisting of a resistor and a zener diode, Fig. 3.

The UCN5818AF chip is a 32-bit serial-to-parallel converter chip that forms the heart of the serial-to-parallel interface. It is basically a 32-bit shift register with parallel latched outputs as shown in Fig. 6. RTS is used for sending serial data to the converter. DTR is used as clock signal (Clock 1) to shift in the data and TD is used as a data strobe to internally latch the data stored in the shift register to the chip's output.

Referring to Fig. 7, serial data presented by RTS at the

Fig. 4. Block diagram of Analog Devices' AD7008 synthesiser chip - two of which are used in this design.

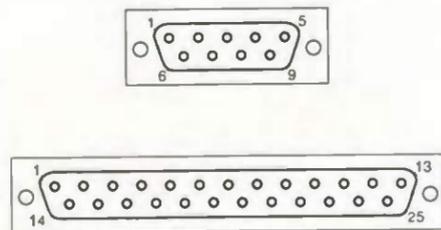
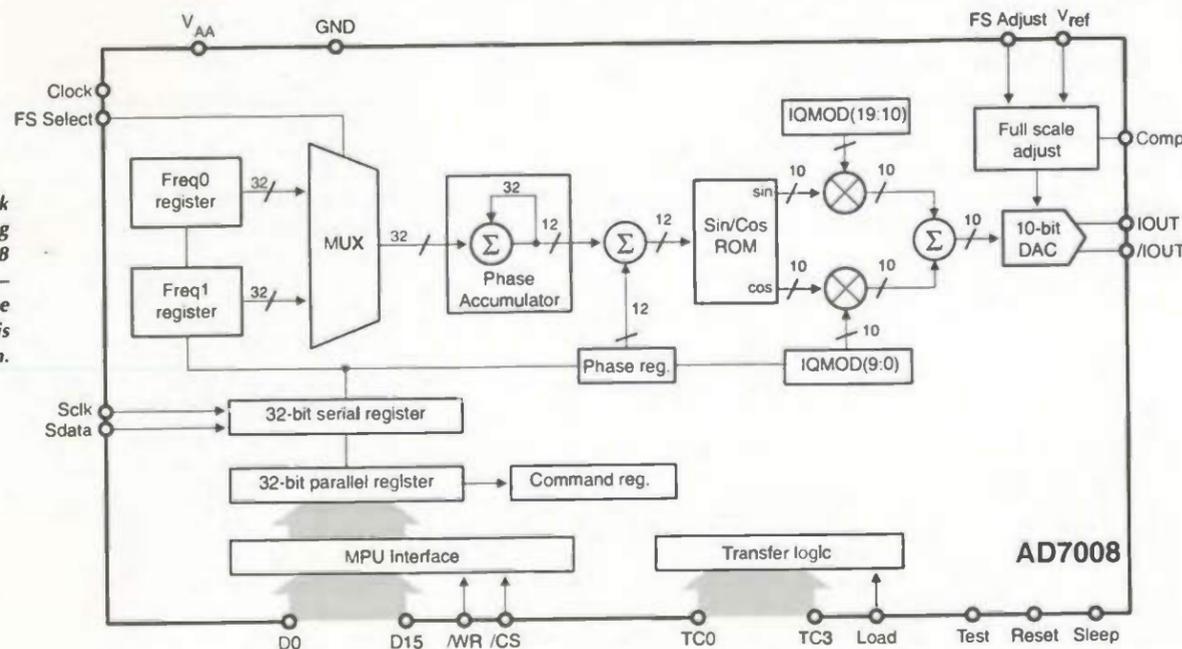


Fig. 5. Pin layout and functions of the RS232 connectors on PCs, a) 9-pin male socket. b) 25-pin male socket.

No. of pins	Name	Direction (for PCs)	Description
25	9		
1	Pro		Protective ground
2	TD	Output	Transmit data
3	RD	Input	Receive data
4	TRS	output	Request to send
5	CTS	input	Clear to send
6	DSR	Input	Data set ready
7	GND		Signal ground (common)
8	DCD	Input	Data carrier detected
20	DTR	Output	Data terminal ready
22	RI	Input	Ring indicator
23	DSRD	I/O	Data signal rate detector

UCN5818AF's input is shifted into the shift registers bit by bit towards the serial data output at the positive transition of each Clock 1 (DTR) pulse. Data stored in the shift registers are then internally latched to their respective outputs in parallel when the STROBE signal (TD) is high. The internal latches continue to accept new data as long as STROBE (TD) is high.

Data in 32-bit serial form sent from the PC to the signal generator are converted into parallel form for use as 16-bit direct digital synthesis data or five control signals to both AD7008 chips by the UCN5818AF chip.

Serial data is in one of two forms. These are control and DDS data, as shown in Fig. 8. This data is shifted into UCN5818AF starting from the most significant bit (MSB).

Bit 8, also called the DLATCH bit, distinguishes the two formats. Serial format DDS data is represented by a high DLATCH bit and control data is indicated by a low DLATCH bit.

Corresponding to the serial data format, UCN5818AF's parallel outputs are classified into respective control and DDS data lines, Tables 1 and 2. Output OUT 10 to OUT 25 of the serial-to-parallel chip are

used for 16-bit DDS data while OUT 1 to OUT5 are used for control signals.

The DDS data has to be present when control signals are sent to the AD7008 chips. Therefore, the UCN5818AF's outputs can only be used for sending DDS data or control signals at any one time. This is accomplished by using an external data latching circuit.

Output OUT 9 corresponds to the DLATCH bit of the serial data. It is used for enabling the data latching circuit each time DDS data are sent and disabling it whenever control signals are sent. Once the DDS data is latched by the data latching circuit, the UCN5818AF outputs are then used for sending control signals to either one or both AD7008s.

Data latching details

Two 74HCT273 8-bit latches combine to form the 16-bit data latch. The latches are enabled only when OUT 9 (DLATCH) is high and DDS data will be latched for every subsequent clock pulse produced by DTR.

Serial interface line DTR is also used as Clock 1 for shifting serial data into UCN5818AF. For every clock pulse, a new serial data bit is

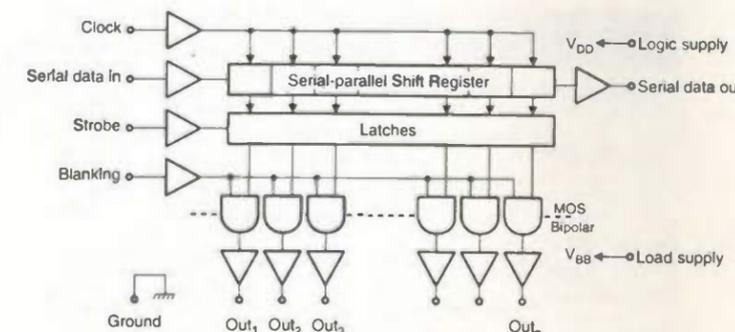
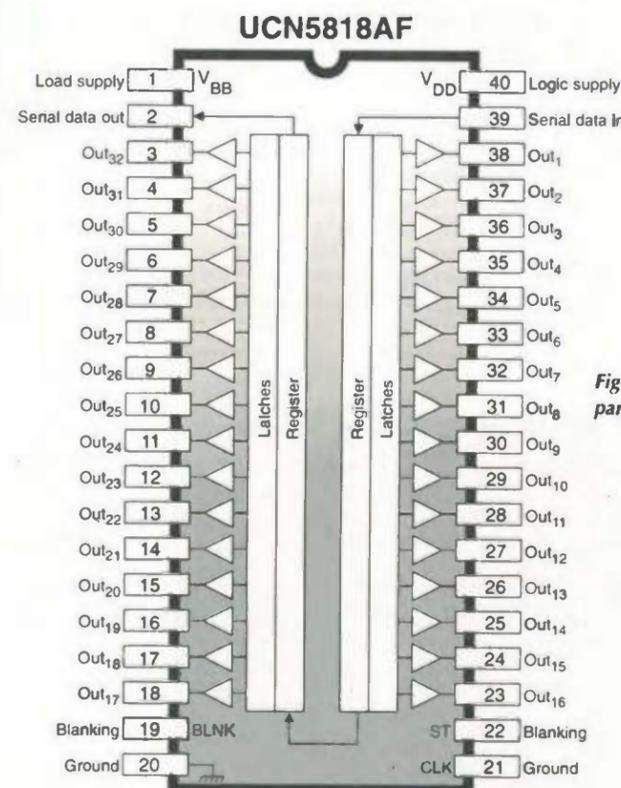


Fig. 6. Pin-out and internal block diagram of the UCN5818AF serial-to-parallel converter.

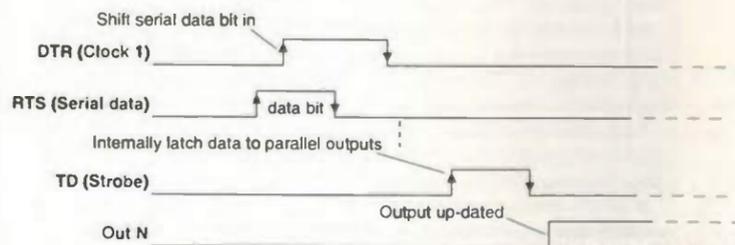


Fig. 7. Timing sequence of the serial-to-parallel converter chip.

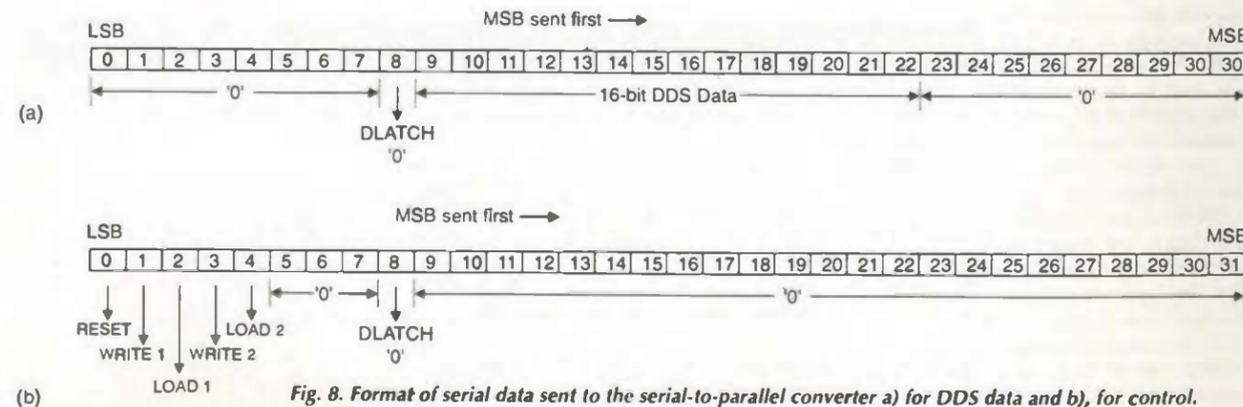


Fig. 8. Format of serial data sent to the serial-to-parallel converter a) for DDS data and b), for control.

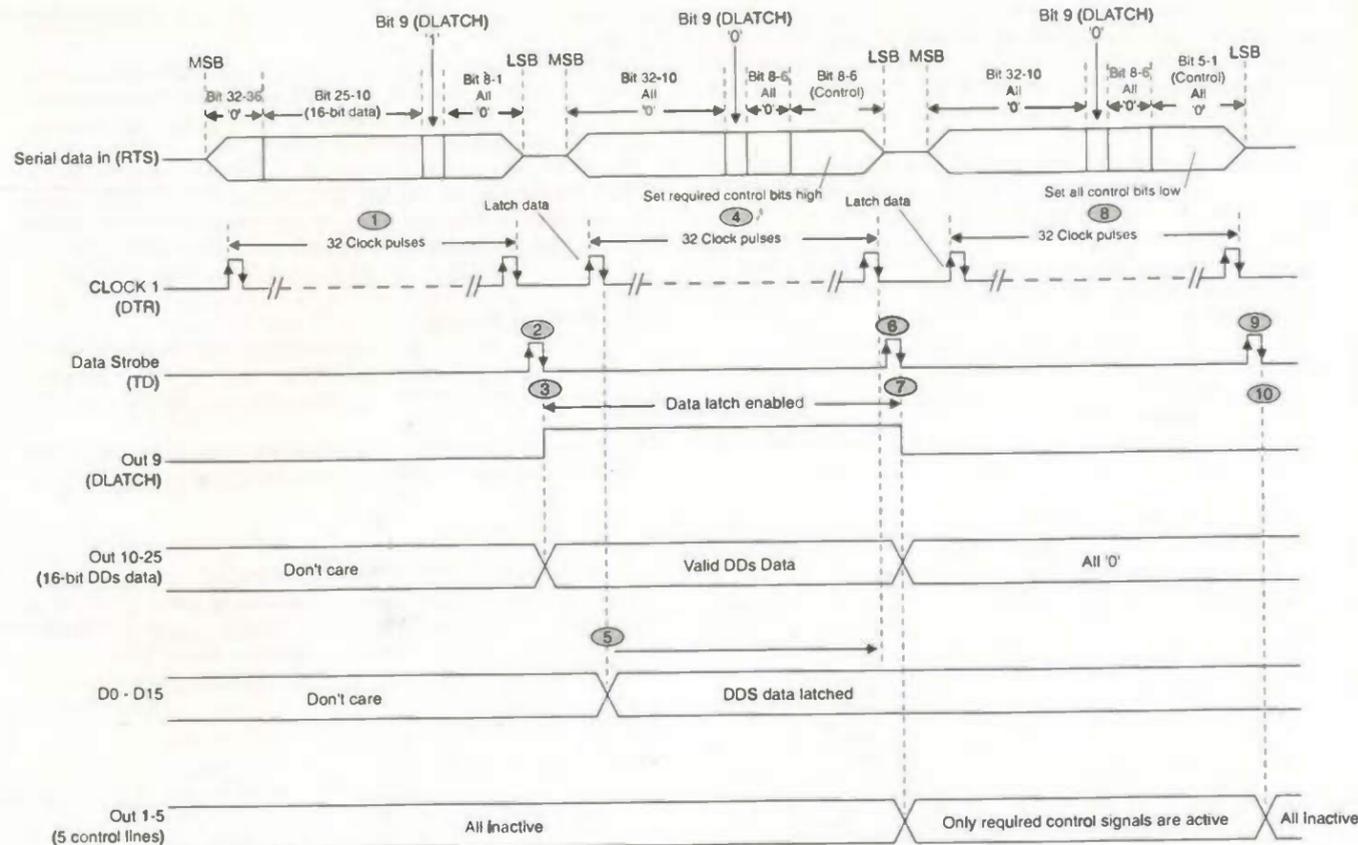


Fig. 9. Sequence of a WRITE or LOAD operation to the generator.

shifted into UCN5818AF but will not be sent to its parallel output until STROBE (TD) is high. At the same time, if OUT 9 is high, data will be latched into the 16-bit data latch.

All DDS data are sent serially to UCN5818AF with a high DLATCH bit. Once converted to parallel, the DDS data is presented to the 16-bit latch through OUT10 to OUT25 with OUT9 high. The data is then latched when control serial data is next shifted into UCN5818AF.

As control serial data is associated with a low DLATCH bit, the parallel form disables the latch and control signals are sent to AD7008 chips without affecting the data.

With this arrangement, the UCN5818A's parallel outputs are used for sending data to and controlling the AD7008 chips independently at any time.

Implementing the DDS chips

Control signals from OUT1 to OUT5 require that control serial data be sent twice. The required control signals are activated by first sending serial data with the corresponding control bits set high. A second set of serial data is then sent with all bits set to low to deactivate the signals. Each AD7008 has its own WRITE and LOAD lines, but they share the same RESET signal.

Loading DDS data to the registers of AD7008 requires two operations. The data is first written into the chip's parallel register and then loaded to the selected register. Since the DDS data is latched to both AD7008s, it can be loaded to an individual chip or both chips simultaneously, depending on the

Table 1

Parallel outputs from the serial-to-parallel converter perform the following functions, needed to control the DDS chips.

Serial data bit	Parallel output	Control lines	Functions
0 (LSB)	OUT 1	RESET	RESET data latching circuit & both DDSs
1	OUT 2	WRITE 1	Write to DDS 1
2	OUT 3	LOAD 1	Load to DDS 1
3	OUT 4	WRITE 2	Write to DDS 2
4	OUT 5	LOAD 2	Load to DDS 2
5	OUT 6	Spare	Not used
6	OUT 7	Spare	Not used
7	OUT 8	Spare	Not used
8	OUT 9	DLATCH	Enable data latching circuit

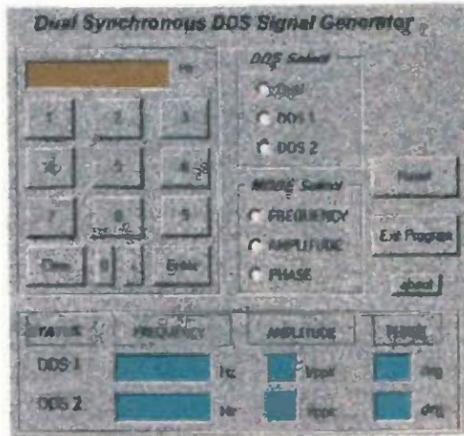


Fig. 10. This user interface has been developed by the authors to help get the design up and running.

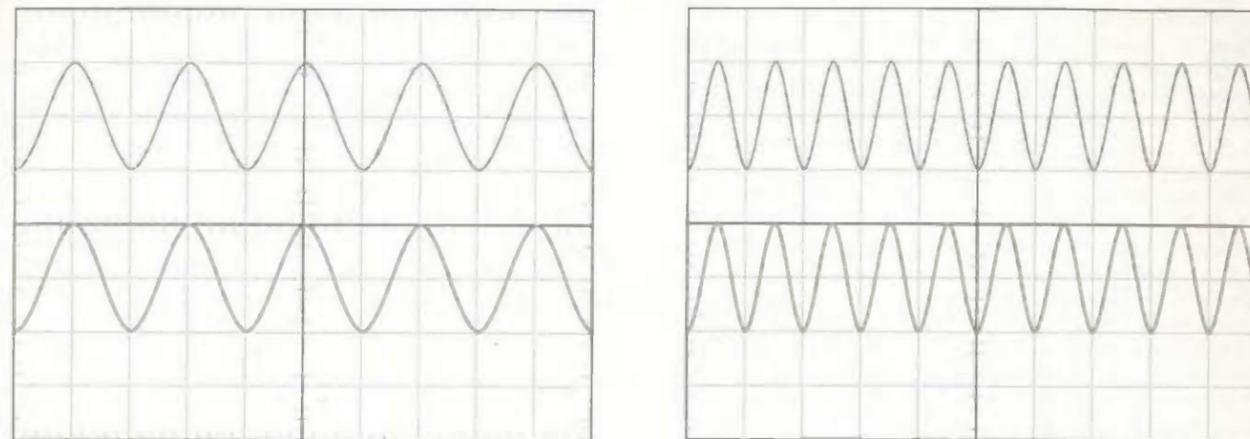


Fig. 11. Signals generated in 'Dual' mode with fixed amplitude and phase of 1V pk-pk and 0° respectively, and varying frequency of 50kHz, left, and 1MHz, right.

settings of control bits in the control serial data sent. To load the data into a particular chip, only that chip's control signals are activated. If both chips are to be loaded at once, their control signals are activated simultaneously.

On the synthesiser chips, TC₀ to TC₃ represent the transfer control address bus connected to D₁₂ to D₁₅ of the 16-bit latch respectively. The transfer control address is sent in the same way as DDS data.

Only the four most-significant bits contain the address of the destination register into which the written data is to be loaded. This address has to be present before a load can be executed.

Both WRITE and LOAD operations are similar. The exception is that the DDS data sent in a LOAD operation is used as a transfer control

Table 2

Data outputs from the serial-to-parallel converter to the synthesiser chips.

Serial data bit Functions*	parallel output	Data lines	Data lines
9	OUT 10	D0	D0
10	OUT 11	D1	D1
11	OUT 12	D2	D2
12	OUT 13	D3	D3
13	OUT 14	D4	D4
14	OUT 15	D5	D5
15	OUT 16	D6	D6
16	OUT 17	D7	D7
17	OUT 18	D8	D8
18	OUT 19	D9	D9
19	OUT 20	D10	D10
20	OUT 21	D11	D11
21	OUT 22	D12	D12
22	OUT 23	D13	D13
23	OUT 24	D14	D14
24	OUT 25	D15	D15
25-31 (MSB)	OUT 26-32	unused	-

*DDS data bits to both synthesiser chips

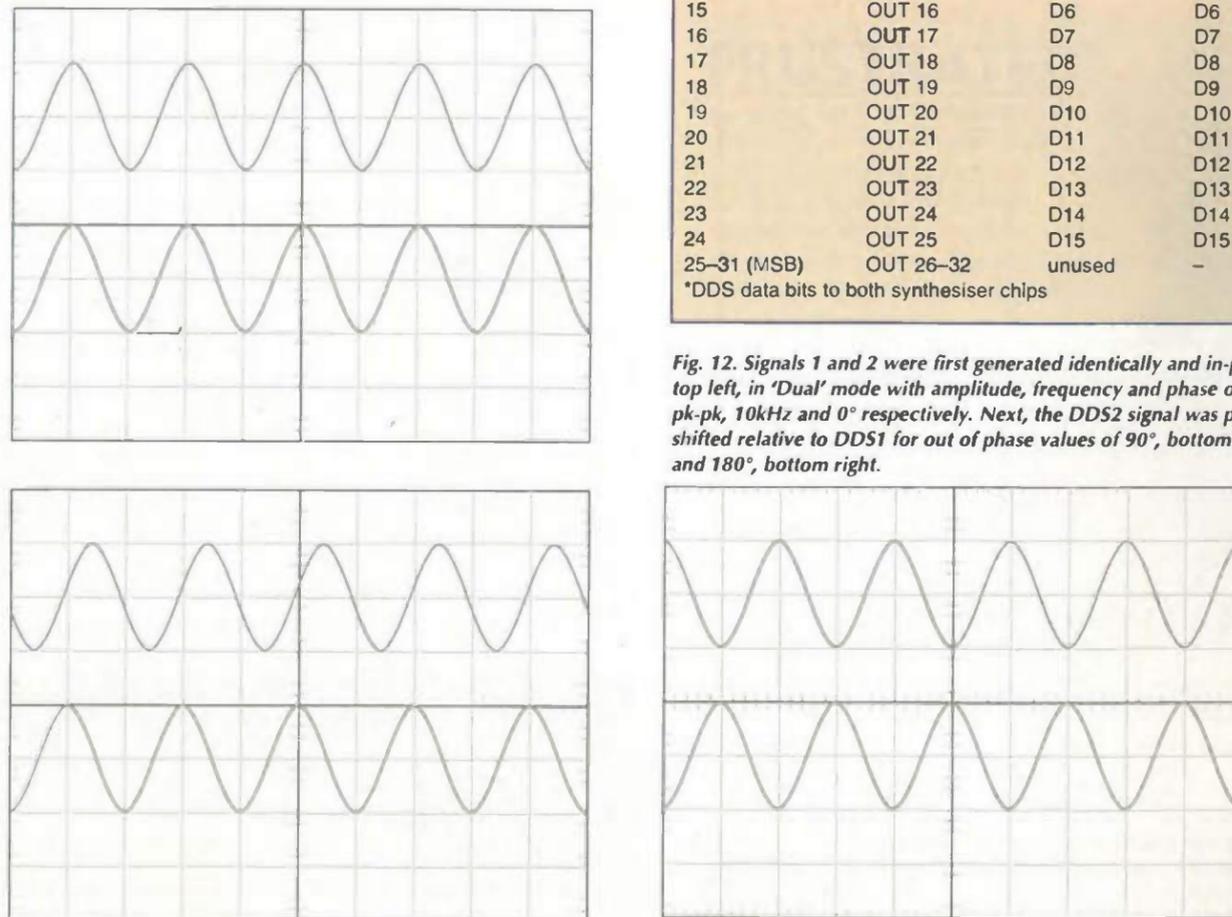


Fig. 12. Signals 1 and 2 were first generated identically and in-phase, top left, in 'Dual' mode with amplitude, frequency and phase of 1V pk-pk, 10kHz and 0° respectively. Next, the DDS2 signal was phase shifted relative to DDS1 for out of phase values of 90°, bottom left, and 180°, bottom right.

address to both chips. It is not used for writing into the parallel registers. Figure 9 is a sequence diagram of a WRITE or LOAD operation.

With this design, each WRITE or LOAD operation to the DDS chips requires three 32-bit serial data transfer cycles. One sends 16-bit DDS data and two activate and deactivate the control signals.

After powering up or resetting the generator, both AD7008 chips are synchronously configured by setting their command register bits as in Table 3. Unlike other registers, the command register only requires a WRITE and a LOAD operation.

The 16-bit DDS data are written into the parallel register, but only the least-significant 4 bits (D_0 to D_3) are loaded into their command registers for chip configuration.

System overview

This generator is capable of producing two signals of up to 16MHz with maximum amplitude of 1V pk-pk. However, the signals can be externally amplified and filtered if required. It has two modes of operation determined by the control serial data received from the PC.

Table 3

DDS configurations used in the system.			
Command register bits	Configuration data bit	Setting	Mode
CR0	D0	1	16-bit parallel loading enabled
CR1	D1	0	Normal operation
CR2	D2	1	Amplitude modulation enabled
CR3	D3	0	Synchroniser logic enabled

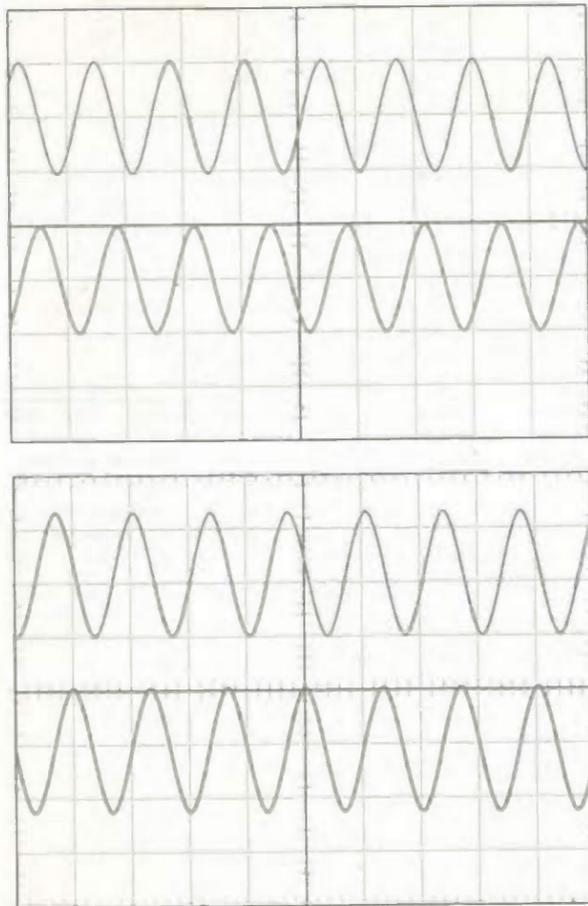


Fig. 13. Top: dual 30kHz, 1V pk-pk signals with DDS2 signal shifted 130°. Bottom: dual 150kHz signals, 0.5V pk-pk signals with DDS1 shifted by 80°.

In 'individual mode', DDS data are loaded into the selected AD7008 and only the respective output signal is affected. In 'dual synchronous DDS mode', the data is loaded into both AD7008 synchronously and both output signals are affected in similar ways at the same time.

Signal frequency is determined by the value loaded into FREQ register. Both amplitude and phase are determined by that loaded into the IQMOD register.

The key feature of this signal generator is its capability to shift the generated signals over the range of 0° to 360°. Two identical signals of zero phase difference are generated in dual mode, and the desired phase difference is then set by phase shifting either signal in individual DDS mode. This allows the phase of either signal to be shifted accurately with reference to the other as desired.

User interfacing

We have developed a user interface and control program using Visual Basic 6. It allows the user to operate the generator from a PC. The developed user interface is shown in Fig. 10.

There's a numerical keypad in the graphical display. The user can enter the values for the signal's frequency, amplitude and phase and the unit automatically changes to 'Hz', 'Vppk' or 'Deg' respectively, depending on which component is selected.

The 'DDS Select' allows the user to select which AD7008 chips the values are entered to: DDS1, DDS2 or both. By selecting 'Dual', the entered values are loaded to both AD7008s synchronously to generate two identical and in-phase signals. One signal's phase then be shifted with respect to the other by entering the phase value for either DDS1 or DDS2. Each time a frequency, amplitude or

phase value is entered, the affected AD7008 chip status is updated respectively.

From frequency, amplitude and phase information entered by the user, the control program uses equation 2 to calculate the Δ Phase value to be loaded into AD7008's FREQ register. It also uses equations 4 and 5 to determine the A and B values to be loaded into IQMOD register. The values are then converted into DDS data and loaded into the respective registers of the select AD7008 to generate the desired signals.

Test results

We have tested the generator using the software just mentioned for different values of frequency, amplitude and phase in various 'DDS Select' modes. The generated signals were examined using an oscilloscope, Figs. 11, 12, 13 and 14. Signal 1 was generated by DDS1 and signal 2 by DDS2.

The results show that the signals are generated accurately in amplitude, frequency and phase in relation to the values entered. With this generator, it is now possible to produce fully-adjustable signals in terms of frequency, amplitude and phase.

Future developments

The signal-generator prototype was developed for use with a PC. By replacing the PC with a microcontroller, the generator could be turned into a stand-alone instrument.

In addition, amplifiers and filters could be incorporated to increase the amplitude range of the signals and to remove high frequency harmonics.

Software availability

While developing this signal generator, the authors produced rudimentary Visual Basic software that provides an interface between the PC and generator. To obtain a copy of the software free of charge, e-mail j.lowe@cumulusmedia.co.uk.



Innovative ideas



New product news



Updates on research



Circuit diagrams

For your eyes only

Subscribe **NOW** and get your own copy of **Electronics World**

See reverse for details...



You can

save

up to £1000

per employee each year through waste minimisation



Environment & Energy Helpline 0800 585794

Free Independent Confidential Advice
HELPLINE | SITE VISITS | BEST PRACTICE GUIDES
WORKSHOPS | CLUBS | CASE STUDIES
Internet: www.envirowise.gov.uk

CIRCLE NO.115 ON REPLY CARD

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



- 2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
- ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
- BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS
- BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY
- BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS
- DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
- KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
- MC MDA J MJE MJF MM MN MPS MP5A MP5H MP5U
- MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
- SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
- STRM STRS SVI T TA TAA TAG TBA TC TCA TDA TDB
- TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
- UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
- ZTX + many others

We can also offer equivalents (at customers' risk). We also stock a full range of other electronic components. Mail, phone, Fax, Credit Card orders & callers welcome.



Cricklewood Electronics Ltd
40-42 Cricklewood Broadway, London NW2 3ET
Tel:020 8452 0161 Fax: 020 8208 1441

CIRCLE NO.116 ON REPLY CARD

Yes I'd like to subscribe to **Electronics World Today!**

Please enter my subscription for one of the following terms. When I subscribe for three years, I pay the price or just two years.

- | | | | |
|--|------------------------------|-------------------------------|-------------------------------|
| | UK | Europe | Rest of World |
| <input type="checkbox"/> 3 years (36 issues) | <input type="checkbox"/> £72 | <input type="checkbox"/> £103 | <input type="checkbox"/> £123 |
| <input type="checkbox"/> 1 year (12 issues) | <input type="checkbox"/> £36 | <input type="checkbox"/> £51 | <input type="checkbox"/> £61 |

On every issue:

- Detailed circuit diagrams
- New product news
- Informative design-orientated explanations
- CAE software

...all this delivered direct to your door each month!

Full money back guarantee

If you're not completely satisfied with **Electronics World** within the first 60 days we'll refund your money in full - no questions asked.

Please allow 28 days for delivery of your first issue.

Reed Business Information Limited may use this information for direct marketing purposes, from ourselves or other companies. If you do not wish to receive direct marketing visit our data protection web page at www.reedbusiness.com/dataprotection or write to us at RBI, Freeport CC2619, Haywards Heath RH16 3BR, UK

REED BUSINESS INFORMATION Reed Business Information Limited, Quadrant House, The Quadrant, Sutton, Surrey, SM2 SAS, UK. (Registered number 151537)

Three ways to pay

- I enclose a cheque for £_____ made payable to Electronics World.
- Please charge my Visa/Mastercard/American Express/Diners Club/Switch/Delta (Please delete as appropriate)

Card number _____
(Switch/Delta only)

Expiry date / / Valid from / / Issue no.

Signed _____ Date _____

- Please invoice me/my company. Purchase Order No. _____

Name _____

Job title _____

Company _____

Address _____

Tel No. _____ Fax No. _____

E-mail address _____

Company VAT registration number _____

Return your completed form to:
 Electronics World Subscriptions, FREEPOST RCC 2619,
 PO BOX 302, HAYWARDS HEATH, UK, RH16 3BR

Fax: +44 (0)1444 445447 E-mail: rbi.subscriptions@rbi.co.uk

Credit Card Orders - (quoting code 158)

Tel: +44(0)1444 475662

to be loaded into AD7008's FREQ register. It also uses equations 4 and 5 to determine the A and B values to be loaded into IQMOD register. The values are then converted into DDS data and loaded into the respective registers of the select AD7008 to generate the desired signals.

Test results

We have tested the generator using the software just mentioned for different values of frequency, amplitude and phase in various 'DDS Select' modes. The generated signals were examined using an oscilloscope, Figs. 11, 12, 13 and 14. Signal 1 was generated by DDS1 and signal 2 by DDS2.

The results show that the signals are generated accurately in amplitude, frequency and phase in relation to the values entered. With this generator, it is now possible to produce fully-adjustable signals in terms of frequency, amplitude and phase.

Future developments

The signal-generator prototype was developed for use with a PC. By replacing the PC with a microcontroller, the generator could be turned into a stand-alone instrument.

In addition, amplifiers and filters could be incorporated to increase the amplitude range of the signals and to remove high frequency harmonics.

Software availability

While developing this signal generator, the authors produced rudimentary Visual Basic software that provides an interface between the PC and generator. To obtain a copy of the software free of charge, e-mail j.lowe@cumulusmedia.co.uk.

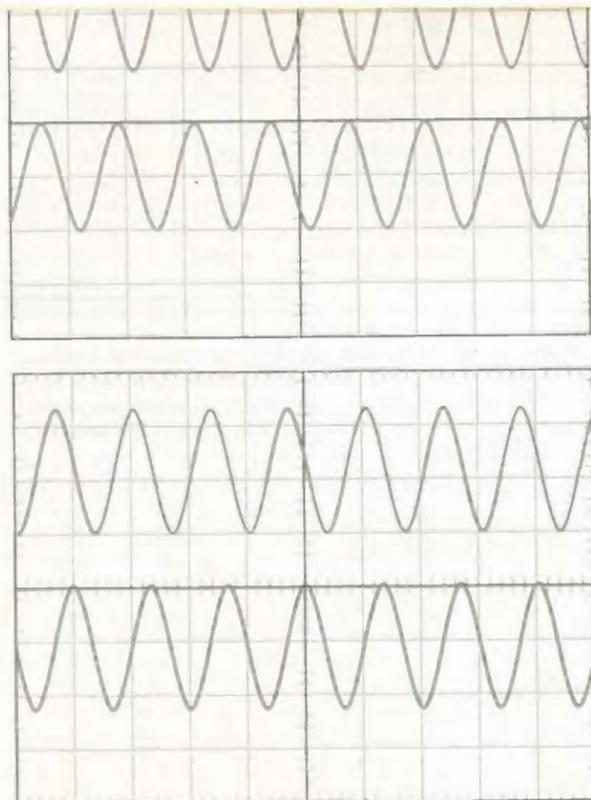



Fig. 13. Top: dual 30kHz, 1V pk-pk signals with DDS2 signal shifted 130°. Bottom: dual 150kHz signals, 0.5V pk-pk signals with DDS1 shifted by 80°.




Quality Alphanumeric backlit LCDs in 4x40, 2x40, 4x20, 2x20 and 2x16 formats

Supplied either bare or pre-fitted with one of our Eze-Use, Serial interface boards with options such as software buzzer control, backlight control, operator interface, start-up message, big character generation, and PC-AT Keypad /mouse interface - all at very competitive pricing. We also stock Serial Interface Graphic modules and front panel bezels for all our LCDs. Please call (01977 683665) or check our web site (www.milinst.com) for full details and pricing.

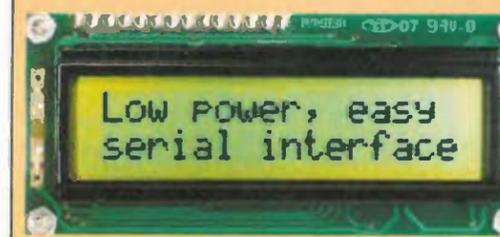Milford Instruments - your total LCD solution



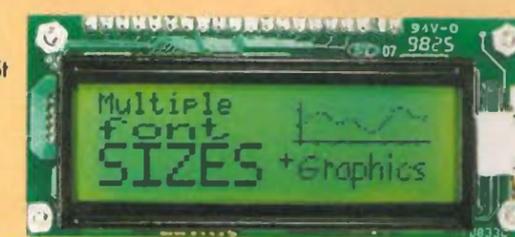Milford Instruments
 Milford House, 120 High St
 South Milford
 LEEDS LS25 5AQ
 Tel 01977 683665
 Fax 01977 681465
www.milinst.com



CIRCLE NO.114 ON REPLY CARD



You can

save

up to £1000

per employee each year
 through waste
 minimisation



Environment & Energy Helpline
 0800 585794

Free Independent Confidential Advice
 HELPLINE | SITE VISITS | BEST PRACTICE GUIDES
 WORKSHOPS | CLUBS | CASE STUDIES
 Internet: www.envirowise.gov.uk

CIRCLE NO.115 ON REPLY CARD

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
 ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
 BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS
 BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY
 BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS
 DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
 KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
 MC MDA J MJE MJF MM MN MPS MP5A MP5H MP5U
 MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
 SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
 STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
 TEA TIC TIPL TEA TL TLC TMP TMS TPU U UA
 UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
 ZTX + many others

We can also offer equivalents (at customers' risk). We also stock a full range of other electronic components. Mail, phone, Fax, Credit Card orders & callers welcome.



Cricklewood Electronics Ltd
 40-42 Cricklewood Broadway, London NW2 3ET
 Tel: 020 8452 0161 Fax: 020 8208 1441

CIRCLE NO.116 ON REPLY CARD

Designing with DSP

Having covered the hardware needed to implement a simple DSP system in last month's article, **Patrick Gaydecki** now explains how to produce the software. "The idea that DSP chips are more difficult to program than the average microprocessor is a myth," he argues.

In this third article explaining how to implement digital signal processors, or DSPs, I will be discussing the DSP56000's language. This language is used by all members of the family including the DSP56002. I will also explain the steps involved in coding, simulating and executing programs for this DSP device.

To give the subject a hands-on flavour, I will be presenting a very simple program to emphasise the link between the language and the hardware sub-systems of the DSP56002. Finally, I will be exploring the way in which system interrupts are implemented, as interrupts are crucial to the way the device operates in many environments.

Knowing the language set enables the system described in last month's article to perform some truly impressive real-time processing of live audio signals. Before you begin though, it is worth bearing in mind three points.

Firstly, the results obtained from cer-

tain operations in this language might initially appear surprising and counter-intuitive in comparison to those from general-purpose microprocessors. This is because the language involves fixed-point, fractional arithmetic.

Secondly, in common with other modern DSP devices of its kind, this processor has an extraordinarily wide-ranging syntax. There is only enough space to cover part of its functionality here.

Thirdly, it is a myth that the DSP device is difficult to program; it is quite straightforward, and the basics given below provide a good springboard to explore the full breadth of this device's capability.

The arithmetic and logic unit

The ALU has ten data registers. Data input register X is subdivided into X0 and X1 while data input register Y is subdivided into Y0 and Y1. In addition, the data accumulator register A is

subdivided into A0, A1 and A2 while the data accumulator register B is subdivided into B0, B1 and B2, making ten registers in all.

The X and Y registers are each 48 bits wide. Hence X0, X1, Y0 and Y1 are each 24 bits wide. Both X and Y can be addressed as 48 bit or 24 bit registers.

Both A and B registers are each 56 bits wide. Registers A0, A1, B0 and B1 are each 24 bits wide while registers A2 and B2 are each 8 bits wide. Both A and B can be addressed as a whole or according to their subdivisions, as in the case for X and Y.

The DSP56000 family represents its data using two's complement fractional format, in which only numbers (operands) within the range ± 1 may be represented. The resolution depends on the word length.

If the operand is represented as a word, it has 24-bit resolution – or one part in 16777216. If it is represented as a long word, it has 48-bit resolution. Table 1 shows how the DSP56002 uses 2's complement arithmetic to represent words. The same scheme may be applied to long words.

From the Table 1, you can see that positive numbers from 0 to $1-2^{-23}$ are

represented in hexadecimal from 0 to 7FFFFFFF₁₆, and negative numbers from -1 to -2^{-23} are represented from 800000₁₆ down to FFFFFFFF₁₆ respectively. Note that in word format, six hexadecimal symbols are required, since each symbol requires 4 bits and a word is 24 bits wide.

Single-statement syntax

In common with other DSP languages, the DSP56000 assembly code allows certain multiple statements to be included within a single instruction. Due to the nature of its architecture, it can execute these in parallel.

In this section, I will deal only with single-statement instructions. These follow the general syntax,

```
<OPCODE> <SOURCE
  OPERAND>, <DESTINATION
  OPERAND> ; comment
```

A space is required between the opcode – i.e. the instruction – and the source operand, but no spaces are allowed between operands. Comments are preceded by a semicolon.

Within the instruction, a '#' symbol preceding a number (operand) implies that it is a literal value. If this is omitted, the number is a memory reference. A '\$' symbol preceding a number means that it is expressed in hexadecimal form. If it is omitted, the format is decimal.

It is very important to remember that since the processor uses fractional arithmetic, it loads literal values into its arithmetic and logic unit registers with left justification. Hence the command,

```
MOVE # $20, X0
```

places the value 200000₁₆ into X0, not 000020₁₆. The best way of thinking about this is to assume a decimal point to the left of the register. If you want to force a number to be right justified, you use the right-caret thus:

```
MOVE #>$2, X0.
```

This would load X0 with 000002₁₆. One of the nice things about DSP56000 assembly language is that you can use decimal numbers directly. Thus the instruction,

```
MOVE #0.25, X0
```

achieves exactly the same result as,

```
MOVE #>$200000, X0
```

Those of you who are new to this language may well consider a processor that can only handle numbers less than or equal to ± 1 to be extraordinarily limited. In fact, nothing could be fur-

Table 2. Summary of key DSP56000 'register-direct' addressing modes.

Sub-type	Instruction	Operand before	Operand after
Ordinary	MOVE X1,A0	X1=\$000123	A0=\$000123
Immediate	MOVE # \$818181,A0		A0=\$818181
Immediate to 56 bit	MOVE # \$818181,A		A1, A2 unchanged
Immediate short	MOVE # \$81,A1		A=\$FF818181000000
Immediate short to A	MOVE # \$81,A		A=\$00000810000000
Absolute	MOVE X:\$200,A0	X:\$200=\$123456	A0=\$123456
Absolute short	MOVE A1,X:\$2	A1=\$123456	X:\$2=\$123456
I/O short	MOVEP A1,X:\$FFE	A1=\$123456	X:\$FFE=\$3456

Table 3. Summary of key 'register indirect' addressing modes for the DSP56000.

Subtype	Instruction	Operand before	Operand after
No offset	MOVE B1,Y:(R0)	B1=\$123456 R0=\$1200	Y:\$1200=\$123456
Post increment by 1	MOVE B0,Y:(R0)+	B0=\$123456 R0=\$1200	Y:\$1200=\$123456 R0=\$1201
Post decrement by 1	MOVE B0,Y:(R0)-	B0=\$123456 R0=\$1200	Y:\$1200=\$123456 R0=\$11FF
Post increment by offset register	MOVE B0,Y:(R3)+N3	B0=\$123456 R3=\$1200 N3=3	Y:\$1200=\$123456 R3=\$1203
Post decrement by offset register	MOVE B0,Y:(R3)-N3	B0=\$123456 R3=\$1200 N3=3	Y:\$1200=\$123456 R3=\$11FD
Index + offset register, indirect	MOVE B0,Y:(R3+N3)	B0=\$123456 R3=\$1200 N3=3	Y:\$1203=\$123456 R3=\$1200

ther from the truth; it is simply a question of scaling. Its all-important properties are the resolution and speed at which it can conduct multiplications, additions and shifts.

The above rule for left justification does not apply when performing register-to-register moves, where data position is preserved. Neither is it the case for moving literals to peripheral (control) registers as opposed to ALU registers. This is because these registers perform control rather than arithmetic functions.

In addition to the data registers, the address-generation unit (AGU) has 24 16-bit address registers that are used to hold the addresses of data referenced by the instructions. These are:

```
Rn, n=0...7 (address)
Nn, n=0...7 (offset)
Mn, n=0...7 (modifier)
```

Each R register is associated with an N and M register according to its subscript *n*. Register R is used to locate operands in memory, while N provides

an offset to an R address and M specifies the kind of addressing that is being performed.

Three types of addressing are possible: linear (default), reverse carry (for FFTs) and modulo, for accessing circular buffers. Modulo addressing is used extensively for real-time filtering operations.

Addressing modes

A DSP56000 instruction, or op-code, consists of one or two 24-bit words. There are fourteen addressing modes possible, and some of the more important ones are summarised in Tables 2 and 3.

A number of points concerning Table 2 is worth noting. First, with simple immediate addressing (2nd listed), only the sub-register specified, in this example A0, will have its contents changed. Secondly, with immediate to 56-bit (3rd listed), the data are left justified as discussed above. Furthermore, in this case a negative number has been loaded. This is because it is greater than

Table 1. Fractional format data representation in DSP56000 language.

Number range	-1	-2^{-23}	+0	$+1-2^{-23}$
As power	2^{23}	$2^{24}-1$	0	$2^{23}-1$
Hex number	800000 ₁₆	FFFFFF ₁₆	000000 ₁₆	7FFFFFF ₁₆

7FFFFFFF₁₆, and so register A2 sets all bits to 1, i.e. A2=FF₁₆ to indicate this.

Finally, with I/O short addressing (bottom row), a peripheral register is being addressed. Several DSP56002 peripheral registers are 16-bit or smaller, and are not arithmetic. Hence the data are right justified.

There's a number of other variants of these addressing modes, but the ones listed above are certainly the most commonly used.

Instructions and parallel operations

There are 62 instructions in the DSP56000's language. These are divided into the following groups: move, arithmetic, logical, bit manipulation and program control.

I have already mentioned single statement instructions. However, there are thirty instructions that can specify one or two parallel data moves in one instruction cycle in parallel with the opcode.

An instruction with the same source transferring to several destinations is permitted. However, an instruction with several sources transferring to the same destination is not. Table 4 below is by no means an exhaustive list, but it does provide details on some of the more frequently used instructions.

For further information, take a look at the DSP56000's user manuals,

details of which are given later.

The really impressive thing about these instructions is that they are carried out in a single instruction cycle. Look, for instance, at the final instruction, i.e.

```
MAC X0,Y0,A X:(R0)+,X0 Y:(R4)+,Y0
```

This is performing a multiplication, a summation, two data moves and two register updates. For a DSP56002 clocked at 60MHz, this entire list of actions takes a mere 33ns.

Developing a program

Once you have written a DSP56000 routine using any standard text editor, it may be assembled using an assembler program supplied by Motorola. Typically, the instruction might be,

```
asm56000 -a -b -l myprog
```

where the '-a' option specifies the code is to be generated using absolute addresses, the '-b' option specifies the generation of a .CLD Motorola object file, and the '-l' option specifies that the assembler is to generate an assembled program listing.

If the assembled program contains no syntax errors, it may then be downloaded to the target processor and run. However, just because a program assembles correctly, it does not mean that it will do what it is supposed to. Hence it is often a good idea to load the program into a DSP56002 simulator.

This allows you to step through the code, instruction by instruction.

The simulator shows how the memory and register contents change as each instruction is executed. Figure 1 below shows a display from the simulator provided by Motorola. If the program performs correctly on the simulator, you can be fairly sure that it will also perform correctly in the target system.

Simple square-wave oscillator

Take a look at the following code fragment:

```
MOVEP #1FF,X:$FFE3
; enable port C all
output
LOOP MOVEP #1FF,X:FFF5
; pulse all pins
high
MOVEP #0,X:FFF5
; pulse all pins low
JMP LOOP
```

The first line places 1FFF₁₆ (11111111₂) in the peripheral register located at X:\$FFE3. This is the port C data direction register, and this configures all the pins for output.

In the next line, all the output pins are taken high because X:\$FFE5 is the location of the port C data register. In the following line, they are returned to zero and then a return is made to pulsing the pin high, with the JMP instruction.

You can calculate very precisely the frequency of this oscillator, since each instruction takes a fixed number of clock cycles. There are three instructions in the loop, i.e. two MOVEP instructions and one JMP instruction. Each takes 4 clock cycles to execute. Hence if the DSP56002 is clocked at 32MHz, the above code will generate a pulse train at 2.66667MHz. The frequency can be altered by including NOP instructions (no operation), which require two clock cycles.

Using interrupts


DSP56002 interrupts may be generated from many sources, for example, the SCI, the SSI, the timer, from a hardware input signal, and so on. When the processor receives an interrupt, it completes its current instruction and places the contents of the program counter (PC) and status register (SR) in an area called the stack (i.e. this represents work in progress). The stack is a reserved block of internal memory, 15 x 32-bits wide.

Now, a jump to a specific address in memory called an *interrupt vector* occurs. In turn, this vector holds an

Table 4. Some key multiple-statement instructions in the DSP56000 language set.

Description	Instruction	Operands before	Operands after
Add B to A and move S81 to B0 in parallel, unsigned	ADD B,A #S81,B0	A=\$00111111000000 B=\$00222222FF0000	A=\$00333333FF0000 B=\$00222222000081
Add B to A and move S81 to B in parallel, signed	ADD B,A #S81,B	A=\$00111111000000 B=\$00222222FF0000	A=\$00333333FF0000 B=\$FF810000000000
Add B to A and move X1 to B in parallel	ADD B,A X1,B	A=\$00111111000000 B=\$00123456111111 X1=\$900000	A=\$00234567111111 B=\$FF900000000000
Add B to A and update R1 in parallel	ADD B,A (R1)+N1	R1=\$1000 N1=\$4	R1=\$1004
Add A to B and move A to memory in parallel	ADD A,B A,X:\$1000	A=\$00123456000000 B=\$00111111000000	B=\$00234567000000 X:\$1000=123456
Multiply Y1 and X1, place result in A and move X0 to Y0 in parallel	MPY Y1,X1,A X0,Y0	Y1=\$400000 X1=\$400000 X0=\$123456	A=\$00200000000000 Y0=\$123456
Multiply-accumulate X0 & Y0 to A, place content of X:(R0) into X0, update R0, place content of Y:(R4) into Y0 & update R4, all in parallel	MAC X0,Y0,A X:(R0)+,X0 Y:(R4)+,Y0	X0=\$400000 Y0=\$400000 A=\$00123456000000 R0=\$4 R4=\$3 Y:(R4)=\$565656 X:(R0)=\$232323	X0=\$232323 Y0=\$565656 A=\$00323456000000 R0=\$5 R4=\$4

Fig. 1. Screen shot of the Motorola DSP56000 family simulator.

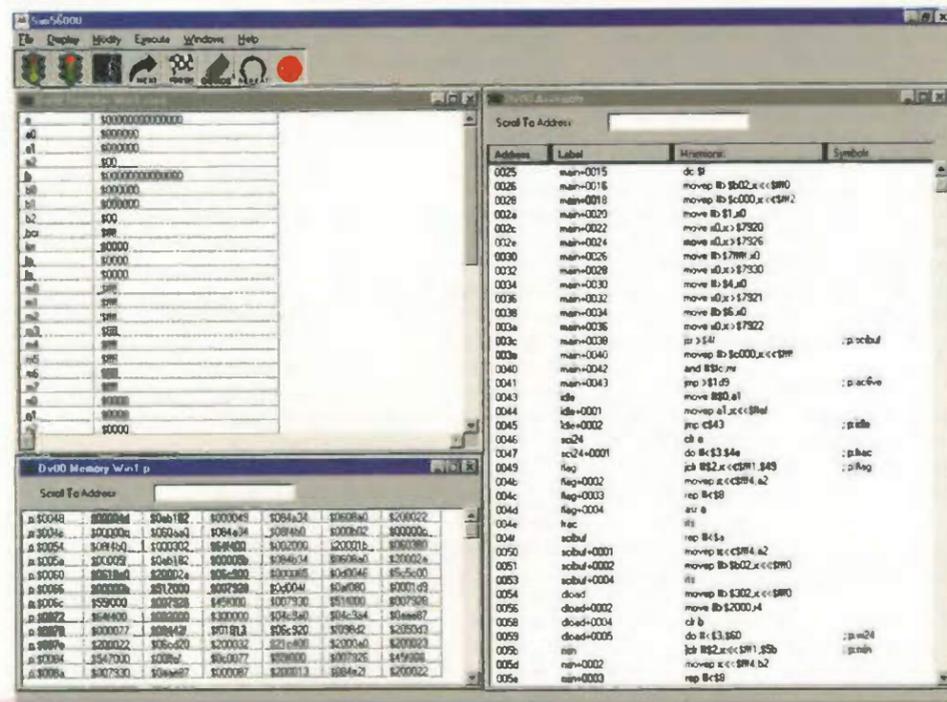

instruction to jump to the address at which the interrupt service routine (ISR) starts. It jumps to the ISR, executes it and after completion, restores the PC and SR, continuing from where it left off within the main program. This sequence of events is shown in Fig. 2.

All the DSP56002 interrupt vectors are located in program memory space between P:\$0 - P:\$3F, and each vector is associated with a specific type of interrupt. Each vector is always only two words in length. For example, the interrupt associated with the SCI resides at P:\$14 - P:\$15. This is fixed by the design.

It is up to the programmer to ensure something sensible is programmed here if an SCI interrupt occurs. This is usually a jump to subroutine instruction (JSR), followed by its address, for example,

```
JSR mysub
```

Here, *mysub* is the label at the start of the ISR. The ISR must end with the RTI instruction (return from interrupt) if JSR is specified in the interrupt vector. The DSP56002 will only jump to an interrupt vector if that particular interrupt has been enabled. Otherwise, it ignores it and carries on with the main program.

It is not mandatory that a JSR instruction be specified in the interrupt

vector. However, in this case the programmer will be required to know the address to which program control should be returned once the ISR is complete.

In summary

In the next and final article in this series, I will be looking at how to program the system to do so real-time processing, and how to use interrupts to communicate with a PC through the serial interface.

Further reading

- DSP56002 Digital Signal Processor User's Manual Motorola Inc. Document DSP56002UM/AD (1993)
- DSP56000 Digital Signal Processor Family Manual Motorola Inc. Document DSP56KFAMUM/AD (1995)


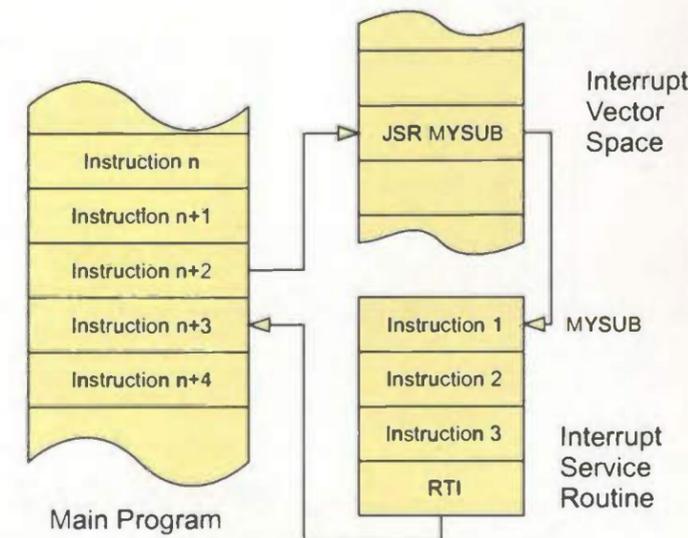


Fig. 2. Sequence of events involved in an interrupt.

**New Version
2001 out now!**

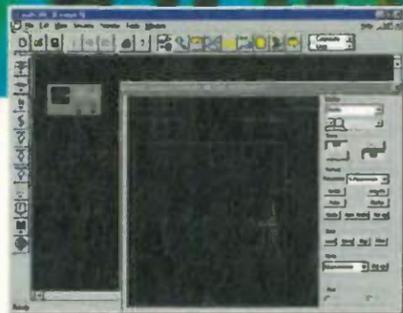

"multiSIM could very well herald the next step forward in PCB design methodology, because it can co-simulate both HDL and SPICE components... at a very affordable price"

Rint Glover, I.D. Industry Analyst - President of I.D. Today

SIMPLY THE BEST

Schematic Capture, Simulation & Programmable Logic

multiSIM - the professional design solution from Electronics Workbench.

Schematic capture, SPICE/VHDL/Verilog co-simulation of analogue and digital parts, built-in analyses and virtual instruments, and a huge library of parts in a single, affordable package.

Call **01462 480055** today for your FREE product guide or visit www.adeptscience.co.uk



Adept Scientific plc, Amor Way, Letchworth, Herts SG6 1ZA
Tel: 01462 480055 • Fax: 01462 480213
Email: ewb@adeptscience.co.uk
WebStore: www.adeptstore.co.uk

**Electronics
WORKBENCH**
multiSIM

Copyright © 2001 Adept Scientific plc. All rights reserved. All trademarks recognised.

CIRCLE NO.111 ON REPLY CARD

Professional PCB Layout for Windows at Computer Store Prices!

Easy-PC For Windows 4.0

now reads Ultiboard designs/libraries*

Suddenly, a professional level PCB layout product is available at a realistic price. Just check the specification and see what excellent value you get with Easy-PC For Windows. Then test before you buy with a demo version - you will be simply amazed with Easy-PC For Windows.

True Windows 32 bit product
Integrated Schematics and Layout as standard
Windows drag & drop throughout
Multiple documents open within display
Technology files for fast start-up
Tiled display - Cascade, Vertical, Horizontal
Multi-level Undo/Redo
Integrated standard AutoPlace
Optional shape based AutoRouter
Full Copper Pour
Split powerplanes
Unlimited signal/powerplane layers
Unlimited non-electrical/doc layers
Keep out/keep in areas for routing
R/H mouse menu support
Pan across design to cursor position
Cross probing between Schematics and PCB
Full forward & backward annotation Schematics /PCB
Modeless driven operation, no menu selection required

Over 7,000 users must be right!

Consistently, one of Europe's most popular PCB Layout products for Windows 95/98/NT/2000, Easy-PC has won praise from users for the wealth of features within each new release. Many of these new features are normally only found in the world's most expensive PCB Layout software packages.

Now try Easy-PC For Windows for yourself !

*Ultiboard is a trademark of Ultimate Technology

Number One Systems

Call +44 1684 773662 or Fax +44 1684 773664

E-mail info@numberone.com

call us for a demonstration copy or download from www.numberone.com

Number One Systems, Oak Lane, Bredon, Tewkesbury, Glos, GL20 7LR, UK

CIRCLE NO.112 ON REPLY CARD

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Intelligent UPS with regulated output

New from Amplicon Liveline are King uninterruptible power supplies with regulated output voltage within ± 25 per cent of the input voltage. If this is exceeded, the battery supplies the output voltage. A battery capacity of up to 7Ah is available and can filter spikes from the supply. Batteries provided are hot swappable and user replaceable. Parallel



operation is available for larger loads. The units have automatic and manual control facilities, and internal clock for scheduled power up and power down.
Amplicon Liveline
Tel: 01273 570220
www.amplicon.com

Efficient battery-voltage step-up converter

A single-cell IC and discrete combination from Zetex is for DC/DC applications where step-up conversion from a low input voltage is required. The ZXSC100 operates from a NiCd or NiMH cell. Efficiency is above 82 per cent, maintained even as the battery voltage falls below 1V. The circuit will start under full load conditions and maintains regulation down to an input voltage of 0.926V. It generates the control signals for the ZXT14 Super-SOT4 pass transistor, which has a saturation resistance down to 13m Ω . Quiescent current is typically 150 μ A. The chip has a

programmable output voltage, which can be set to anywhere between the input battery voltage and the maximum V_{ce} rating of the pass transistor.
Zetex
Tel: 0161 622 4460
www.zetex.com

Digital multimeter for cat IV safety ratings

Fluke has introduced the 170 series of digital multimeters for category IV safety ratings. They are for front-line industrial, electrical and electronic technicians and engineers for use up to 1kV and 10A AC or DC. Models 175, 177 and 179 are for use from relatively clean bench areas to harsh work environments. The true-rms engine has 0.09 per cent accuracy (177 and 179) with 6000 counts of resolution on a backlit display. The meters provide minimum, maximum and average recording, auto-hold and display hold for troubleshooting. The meters



emit an audible tone to signal that a new minimum or maximum reading has been sensed and stored. Frequency, capacitance and resistance ranges are up to 100kHz, 10000 μ F and 50M Ω .
Fluke
Tel: 01207 9420700
www.fluke.com


SM inductors benefit from protection case

Cooper Electronic Technologies has expanded its Coiltronics

IP software is compatible with third party EDA and debug tools

An IP module library and compatibility with third party EDA and debug tools are provided by Triscend's Fastchip software. Windows based, it manages the configurable system-on-chip (CSoC) design process for the firm's 8-bit E5 and 32-bit A7 products. The library of pre-licensed, pre-verified drag-and-drop IP software modules includes a two-wire serial I²C-compliant interface, a quarter VGA LCD controller and a triple DES controller. The modules can be parameterised to meet application needs. The basis to the IPMI protocol, the I²C module is for enclosure management applications, operating in multi-master, slave only or master-only modes. By adjusting settings, the QVCA LCD controller module supports various single drive STN panels and colour and monochrome displays. The triple DES controller module is for POS terminal work. It also supports the Synplify logic synthesis tool from Synplicity. Operability with Wind River's Visionprobe II design tool and Visionclick source level debugger has been changed so logic designers can access and control the entire CSoC.

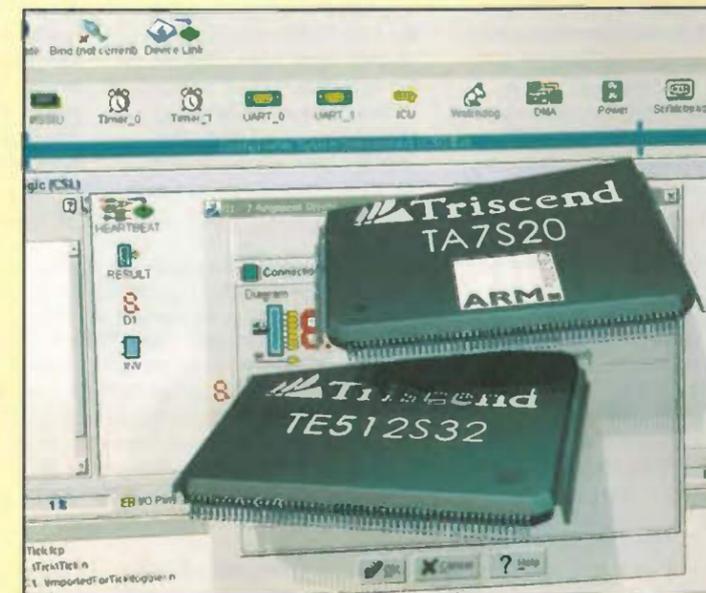Amplicon Liveline
Tel: 01273 570220
www.amplicon.com



Please quote *Electronics World* when seeking further information

range of Uni-Pac surface mount inductors with the UP1B, UP2B, UP3B and UP4B with protective cases to reduce the risk of core breakage. They are for use within energy storage applications and DC/DC converters. Operating temperature is -40 to +85°C ambient with an rms current rating of 19.2 to 0.47A. Standard inductance is set at 0.47 to 100µH; modified values for higher applications are available on request.

Cooper
Tel: 01373 472148
www.cooperindustries.com

Solid-state relays

Crydom has introduced six and eight-pin DIP solid-state relays. The G2 devices are available in contact configurations, including form A, dual form A, form B, dual form B and one form A one form B. All can be wired for AC operation or one of three DC configurations. They can switch AC or DC voltages from the microvolt and nanoamp range up to 400V and 400mA, and can be wired in

series to achieve switching in the kilovolt range. Typical input voltage and current are 1.25V DC at 5mA. Dielectric strength input to output is 3750V and capacitance is 0.8pF for single-relay and 1.2pF for dual-relay devices. Power dissipation is 500 or 600mW respectively.

Crydom
Tel: 01444 473555
www.crydom.com

Programmable ASSP with a PLD core

Altera has announced the availability of its Mercury programmable ASSP. It integrates the functions of a transceiver ASSP with a PLD core. The clock data recovery (CDR) transceivers within the device eliminate frequency barriers by providing data rates up to 1.25Gbit/s and a CDR bandwidth of up to 45Gbit/s. It has a distributed multiplier capability. Uses include serial backplane, chip-to-chip and line side applications. Versions provide 8 or 18 channels of CDR capability on one device. The device is made on a CMOS process.

Altera
Tel: 01494 602000
www.altera.com

16-bit micro with 32kbyte on-chip SRAM

Hitachi has introduced a 16-bit microcontroller with 32kbyte on-chip SRAM. Versions include the H8S/2329F with 384kbyte on-chip flash (3.3V, 25MHz), the ROMless H8S/2324 (3.3V, 25MHz) and the ROMless H8S/2394 (5V, 20MHz). At 25MHz, these devices provide



about 12Mips Dhrystone if executing from on-chip memory. They are almost pin-compatible with the H8S/2357F, 2350 and 2532. Each device has the same peripheral set including a DMA controller with four channels and a data transfer controller. A bus state controller divides the 16Mbyte memory into eight areas. Parameters can be programmed into each to allow glueless access to external memories and peripherals. A six channel 16-bit timer provides 16 input capture and output compare registers. The chips also have two 8-bit timers, which provide a reduced timer functionality during low activity. A programmable pulse generator has 16 real-time outputs that drive data patterns onto the pins under timer control. This eliminates the jitter that would normally be associated with interrupt-driven operation. Three serial ports provide asynchronous, synchronous and multi-master operation, as well as support for a subset of ISO7816-3, while an eight channel 10-bit ADC provides results within 7µs at 20MHz. The ADC is complemented by a two-channel 8-bit DAC.
Hitachi Europe
Tel: 01628 585163
www.hitachi-eu.com

Wireless platform ups 36 channel density

Blue Wave Systems has launched the Comstruct CPC1/C6800 wireless platform, which will let 3G developers increase base-station transceiver channel density. It is based on the TMS320C6415 and C6416 DSPs from Texas Instruments. The open architecture lets it be closely coupled with a user's Asic technology, letting wireless equipment suppliers develop combined DSP and Asic base-station transceivers. The C6416 includes coprocessors and I/O interfaces targeted at 3G wireless base-stations. On-chip coprocessors for Viterbi and turbo coding eliminate the need for external error correction coprocessors. Data paths on the platform provide up to 6Gbit/s rates to support multiple receivers. Interprocessor communications let developers specify a DSP for chip rate or symbol rate processing to ensure the system is balanced, depending on the ratio of voice and data services offered.
Blue Wave Systems
Tel: 01509 63444
www.bluew.com

16-bit microcontroller operates at 40MHz

STMicroelectronics has presented a 16-bit automotive-grade microcontroller chip with embedded flash memory based on the ST10 core. For applications such as engine control, the chip operates at up to 40MHz. Memory embedded in the ST10F269 is based on single-voltage flash technology operating at 5V.



Transceiver uses direct conversion

Hitachi has introduced the HD155141F, or B4, integrated transceiver using direct conversion technology. The receiver incorporates a flexible, configurable analogue IQ interface and an integrated and automated DC offset cancellation circuit. These enable baseband compatibility without the need for special hardware or complex DSP algorithms. The device supports dual-band applications in the GSM900 and either DCS1800 or PCS1900 bands. It is GPRS compliant up to class 12. Support tools, including evaluation boards and


application notes, are available. The transceiver incorporates on-chip LNAs. All filtering required after the LNA in the receive path is integrated inside the device. An offset PLL transmitter reduces TX filtering and insertion loss. State machine control is through a standard three-wire bus. It uses a 0.35µm BiCMOS process and is housed in a 56-pin TQFP with a 9 by 9mm footprint and 0.5mm pin pitch.
Hitachi Europe
Tel: 01628 585163
www.hitachi-eu.com

Please quote *Electronics World* when seeking further information

LVDS transmits at high speed

National Semiconductor unveiled several low voltage differential signalling (LVDS) data transmission products at DesignCon 2001. They include devices with on-chip test capability for telecoms and datacomms systems, mobile phone base-stations and Internet infrastructure equipment. LVDS technology is suitable for point-to-point and multipoint data transfer. Also on show were IEEE1149.1 JTAG compliant LVDS devices with boundary scan test access to improve fault coverage by providing test access to the boundaries of a chip, enabling structural and connector test capability. IEEE1149.1 defines a four-wire digital interface to a standard test access port

on each compliant device. The DS92LV16 is a single-chip 16:1 LVDS serializer and 1:16 deserializer. The 1.28Gbit/s design can be used to construct 16 bidirectional point-to-point links across two pairs between two of the parts. The clocking scheme allows variable input rates from 30 to 80MHz with a ±5 per cent clocking disparity between chips. Built-in local and line loop-back modes facilitate segregation of pre-specified parts of the system by the repetition of signals back to the board (local) or back to the cable or backplane (line).
National Semiconductor
Tel: 00 49 8141 351443
www.crydom.com

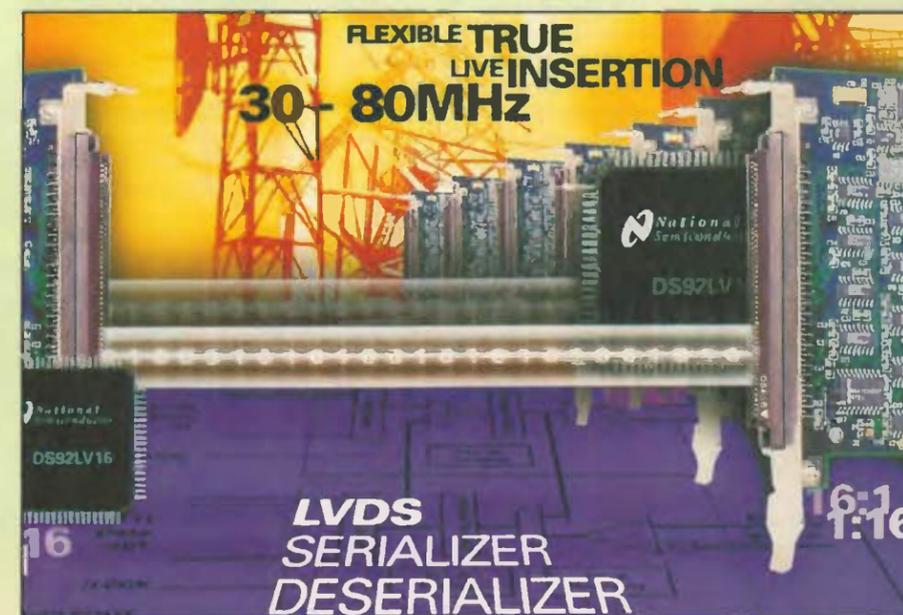

Microwave analyser from 10MHz to 46GHz

IFR has announced a 46GHz microwave system analyser. The 6845 MSA is a 10MHz to 46GHz spectrum analyser with a full bandwidth, independently controlled tracking generator. It includes a synthesised source and three-channel scalar analyser, and is an aid for the manufacture, installation and maintenance of radio links, satellite links and microwave systems. It includes a 46GHz tracking generator, which acts as transmitter and receiver when testing up and down links. The instrument is aimed at manufacturing, installation and maintenance of point-to-point and point-to-multi-point radios and satellite communications

equipment. It is suitable for testing components and assemblies used in radio and military systems, and can measure return loss and fault location on antennas and feeders at mobile communications base-stations as well as verifying radio performance through the modulation spectrum. For insertion and reflection measurements, the tuned input gives a dynamic range of 70dB at 40GHz. The ability to set the spectrum analyser and source frequencies independently in CW and swept modes simplifies the testing of mixers, up and down converters and frequency multipliers and dividers.
IFR Systems
Tel: 01438 772087
www.ifs.com

Voice coil actuators come in flat format

Denitron has developed voice coil actuators with a flat format for packing in confined places. Applications include printing heads where an array of flat coils is stacked close to emboss coded information in tickets for security. Other applications are



NEW PRODUCTS

Please quote *Electronics World* when seeking further information

in locks, security equipment and textiles machinery. They can be driven electrically in either direction, so a spring is not required to act in the return direction. Devices can have a profile of less than 1mm and their action is the same as that used in cylindrical actuators. *Densitron Control Systems*
Tel: 01959 642000
www.densitron.com

Embedded PGA cores for Asics and ASSPs

Actel has introduced its Varicore embedded PGA IP cores for Asic and application specific standard product systems on a chip. The unit is based on technology from Prosys Technology and Gatefield, which Actel bought last year. These blocks have been designed using 0.18µm CMOS SRAM technology. Additional cores are being developed for smaller process geometries.

Actel
Tel: 020 7823 3226
www.actel.com

JTAG emulators for config processors

Arc Cores has announced two JTAG emulators that provide development and test capabilities for configurable processors. The emulators from Corelis use Arc's on-chip debug capabilities to support any processor clock speed at which the target system runs. The Scanice and Netice emulators use the JTAG port on Arc's Tangent processor to provide access to its on-chip debug facilities. Both include the Metaware Windows 95, 98, NT and 2000 compatible Seecode source-level debugger. For JTAG emulation access, the Scanice uses a PCI bus JTag controller that is installed in a PC and the Netice a LAN-based Ethernet JTAG controller. On-chip debug capabilities provide non-intrusive memory access and multi-core debug, and do not need debug firmware. To support real-time debugging, the on-chip logic lets the user examine memory locations without stopping the processor. Debug operations can be achieved with no resident code

running on the CPU. Programs and data can be downloaded to any part of the system RAM through the JTAG port without a resident loader program or a ROM emulator.
ARC Cores
Tel: 0208 236 2800
www.arccores.com

Digital pressure sensor weighs 30g

The UZU3 digital pressure sensor from Matsushita weighs 30g and is for robotics or automated manufacturing systems. A panel-mounting bracket lets multiple sensors be mounted directly on top of each other without a space between adjacent sensors. The device has a two-colour (red and green) display that changes colour if the detected pressure exceeds the user-defined set point. This lets the operator confirm output status at a glance. The display can also be changed from digital to analogue, indicated as a bar display. Response time is 2ms. A chatter prevention function lets the response time be adjusted so insignificant pressure fluctuations can be ignored. There are four output modes - hysteresis, window comparator, automatic sensitivity setting and forced output. Vacuum, positive and compound pressure types are available. The compound type serves pressure requirements between ±100kPa.

Matsushita
Tel: 01908 350700
www.matsushita.co.uk

Rad hardened mosfet at 1000V

International Rectifier has introduced a 1000V radiation-hardened (rad-hard) power Mosfet. The IRHY7G30SE 1000V device is a significant rating improvement on previously available 600V rad-hard Mosfets, said the company. As a result, said the company, it can be used to replace less efficient bipolar transistors in high-voltage applications, and also enables designers to accommodate safe DC-rating conditions without losing functionality. Typical applications include travelling



wave tube amplifiers, which are used to amplify microwave signals in satellite communications systems. The 1000V Mosfet is an enhancement-mode n-channel device, made with IR's proprietary radiation-hardened gate- and field-oxidation process to achieve single-event upset and total ionising dose

hardness requirements. The device is single event effect hardened with linear energy transfer of 37MeV/(mg/cm²) and retains virtually identical electrical performance up to 100Krad (Si) total dose, said the firm.
International Rectifier
Tel: 020 8645 8003
www.irf.com



Connector for secure digital memory cards

Honda has launched a range of low-profile slot connectors for use with the latest secure digital (SD) solid-state, removable memory cards. Designed for use in telecoms and datacoms applications as well as hand-held devices, the connectors incorporate a card retention mechanism for additional security. The connectors accept standard SD memory card sizes and feature a patented 'push-push' eject mechanism, which provides a reliable alternative to snap-in alternatives, said the supplier. The SD card is inserted into and ejected out of the connector body by a simple tactile push action. SD memory cards provide removable storage for up to 64Mbyte of encrypted data and feature mechanical card detection and write protect. Incorporating a three-stop sequential contact design, the series accepts standard 7-position multi-media cards as well as the thicker, 9-position SD cards. An optional card detect feature is also available and SM terminations are housed beneath the connector body to reduce overall size. Furthermore, the low profile design meets published MMC and SD specifications.
Honda Connectors
Tel: 01793 523388
www.hondaconnectors.com

TiePieScope HS801 PORTABLE MOST



ARBITRARY WAVEFORM GENERATOR-
STORAGE OSCILLOSCOPE-
SPECTRUM ANALYZER-
MULTIMETER-
TRANSIENT RECORDER-

Reliability

- The sophisticated cursor read outs have 21 possible read outs. Besides the usual read outs, like voltage and time, also quantities like rise time and frequency are displayed.
- Measured signals and instrument settings can be saved on disk. This enables the creation of a library of measured signals. Text balloons can be added to a signal, for special comments. The (colour) print outs can be supplied with three common text lines (e.g. company info) on three lines with measurement specific information.
- The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (arbitrary waveform generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.
- The versatile software has a user-defined toolbar with which over 50 instrument settings quick and easy can be accessed. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.
- When a quick indication of the input signal is required, a simple click on the auto setup button will immediately give a good overview of the signal. The auto setup function ensures a proper setup of the time base, the trigger levels and the input sensitivities.
- The HS801 has an 8 bit resolution and a maximum sampling speed of 100 MHz. The input range is 0.1 volt full scale to 80 volt full scale. The record length is 32K/64K samples. The AWG has a 10 bit resolution and a sample speed of 25 MHz. The HS801 is connected to the parallel printer port of a computer.
- The minimum system requirement is a PC with a 486 processor and 8 Mbyte RAM available. The software runs in Windows 3.xx / 95 / 98 or Windows NT and DOS 3.3 or higher.
- TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 4WJ, UK
Tel: 01480-460028; Fax: 01480-460340
- TiePie engineering (NL), Koperslagersstraat 37, 8601 WL SNEEK The Netherlands
Tel: +31 515 415 416; Fax +31 515 418 819

Web: <http://www.tiepie.nl>

CIRCLE NO. 117 ON REPLY CARD

NEW PRODUCTS

Please quote **Electronics World** when seeking further information

FR-V chip based on VLIW architecture

Fujitsu is releasing its Leo FR-V VLIW chip designed around the company's FR500 core for the European navigation market. The 32-bit, four-way VLIW has media and graphics enhancements, and is software compatible with the firm's MB93501. It is modular and expandable, with the memory management unit being ARM compatible with Windows CE support. Internal frequency is 266MHz, and the chip has an external flexible 32-bit system bus operating at 66MHz, 1.8V, and a set of generic and automotive specific peripherals. The architecture can execute parallel instructions. The compiler rather than the processor is responsible for guaranteeing simultaneous issuing of each packet. There are six execution units on the processor - two integer units, two floating point units and two media execution units, all running in parallel. Its compiler decides which unit is going to carry out a command using VLIW. The CPU core provides a peak performance of 1064Mips, 1.064GFlops and 4256Mops at 266MHz, integer operation, floating-point and media.

Fujitsu Microelectronics
Tel: 01628 504600
www.fujitsu-fme.com

Miniature coaxial connectors on the edge


Developed for those PCB applications where space is at a premium, Radiall said its MC-Card can be used in either edge card or on board applications (i.e. PCMCIA or ISA cards). The connector



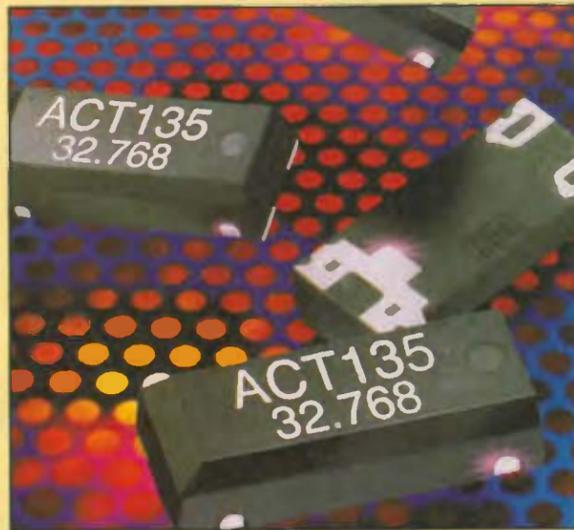32.768kHz SM crystal is stable to ±20ppm

The ACT135 is a surface mount 32.768kHz crystal, from Advanced Crystal Technologies. It has stability to ±20ppm and operates from -40 to +85°C. Applications include portable equipment for industrial, consumer and white goods markets. Measuring 6.8 by 3.0 by 1.7mm, it can also be used in personal equipment such as watches and other timing or data logging instruments. Ageing stability is 13ppm at 25°C (±3°C), and shock resistance is ±5ppm maximum. It is suitable for automatic placement from tape and reel.

ACT
Tel: 0118 979 1238
www.actcrystals.com



operates from DC to 8GHz with an impedance of 50Ω. Specified for over 5000 matings, it features snap-on mating for security of the connection. A switch version is available and various interface lengths can be produced to allow products not to mate with the standard connector, in conformance to Section 15.203 of FCC standard requirements.

Radiall
Tel: 020 8997 8880
www.radiall.co.uk

SM electronics are hot hat devices

Available from Nichicon (Europe) is the UN series of bipolar, "Top Hat" surface mount electrolytic capacitors. Available in diameters: 12.5, 16, 18 and 20mm, the capacitors operate across a temperature of -55 to 105°C. Suitable for automatic insertion using carrier tape and tray the series has a working voltage of 6.3 to 100V and capacitance 22 to 3300µF 20 per cent tolerance. Load life of the SM electrolytic capacitors is 64 000 hours at 55°C. Allowable ripple is 830mA max (at 105°C) depending on capacitance and working voltage. Size range is 12.5(D) by 13.5(L) mm by 20 by 21.5mm.

Nichicon
Tel: 01276 685393
www.nichicon.co.uk



32-bit Risc MCU with on-chip mask ROM

Epson has developed a 32-bit Risc MCU integrating peripheral circuits with built-in ROM based on its own EOC33209. Two models, the EOC33264 and the EOC332129, include a built-in high-speed MAC (multiplication & accumulation) instruction, a multiplexed A/D converter, DMA, HDMA, 4 channels, SIO and various timers. These functions make them suitable for classic DSP applications especially for software codec and signal processing (voice recognition and text-to-speech), said the company.

Epson Electronics
Tel: 00 49 89 14005 227
www.epson-electronics.de

Programmable caps to replace inductors

Maxim Integrated Products has introduced its first electronically programmable capacitor with high self-

resonant frequency and 32 discrete capacitance steps. Housed in an SC70 package (2.2mm x 2.4mm), the MAX1474 is designed to replace mechanical inductors in common tuning circuits. It can be set to any one of 32 discrete capacitance steps ranging from 6.26pF to 12.74pF in 0.2pF increments.

Application circuits can be used to increase the capacitance range, increase capacitance steps, or to multiply the Q-value to fit a particular application. Because the capacitors are actually implemented in silicon, there is virtually no drift over time, said the firm and the temperature drift coefficient is less than 33ppm/°C. A Q of 50 is possible. Two pins are used to program the MAX1474. Capacitance values are selected by raising the enable pin and sending the device a discrete number of pulses corresponding to the desired capacitance value. It does not require a clock and will retain the programmed capacitance value for as long as power is supplied. If the system is dynamic and has the ability to retune itself, the capacitance value can easily be changed at any time by simply raising the enable pin and sending the desired number of pulses. Applications include post-trim of low-cost regenerative stages,

MARCONI 2019A
AM/FM synthesised signal generator 80kHz-1040kHz
NOW ONLY £400

- H.P. 3312A Fun Gen 0.1Hz-13MHz...£300
- AM/FM Sweep/Tr/Gate/Burst etc. H.P. 3310A Fun Gen 0.005Hz-5MHz...£125
- Sine/Sq/Tri/Ramp/Pulse FARNELL LFM4 Sine/Sq Oscillator 10Hz-1MHz...£125
- Low distortion TTL Output, Amplitude Meter H.P. 545A Logic Probe with 546A Logic Pulser...£90
- and 547A Current Tracer
- FLUKE 77 Multimeter 3 1/2 digit Handheld...£60
- FLUKE 77 Series 11...£70
- HEME 1000 LCD Clamp Meter 0-1000A In Carrying Case...£60

RACAL 900B AUTOMATIC MODULATION METER AM/FM 1.5MHz-2GHz ONLY £95

- H.P. 8494A Attenuator DC-4GHz 0-11dB N/SMA...£250
- H.P. 8492A Attenuator DC-18GHz 0-6dB APC7...£95

MANY OTHER ATTENUATORS, LOADS, COUPLERS etc AVAILABLE

DATRON 1061 HIGH QUALITY 5% DIGIT BENCH MULTIMETER True RMS/4 wire Res/Current Converter/IEEE £150

- MARCONI TF2015 AM/FM sig gen, 10-520MHz...£175
- RACAL 900B Auto Mod Meter, 1.5MHz-2GHz...£200
- LEVELL TG2000MP RC Oscillator, 1Hz-1MHz...£50
- Sine/Sq Meter, battery operated (batts not supplied)
- FARNELL LF1 Sine Sq Oscillator, 10Hz-1MHz...£75
- RACAL/AIM 9343M LCR Databridge, Digital Auto...£200

STILL AVAILABLE - PREVIOUSLY ADVERTISED WITH PHOTOS

- MARCONI 893C AF Power Meter, Sine Measurement Unused...£100
- Used...£50
- MARCONI 893B - No Sine...£30
- MARCONI 2610 True RMS Voltmeter Autorange 5Hz-25MHz...£195
- GOULD J3B Sine/Sq Osc. 10Hz-100kHz Low distortion...£75-£125
- AVO 8MHz in Ever Ready Case, with leads etc...£80
- Others Avos from £50
- GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused...£75
- GOODWILL GVT427 Dual Ch AC Millivoltmeter...£100-£125
- 10mV-300V in 12 Ranges Freq 10Hz-1MHz...£125
- SOLARTRON 7150 DMM 6 1/2 digit True RMS - IEEE SOLARTRON 7150 Plus...£196-£150
- £200
- SOLARTRON 7150 Plus...£200
- RACAL TRUE RMS VOLTMETERS 9300 5Hz-20MHz usable to 60MHz, 10V-316V...£95
- 9300B Version...£150
- 9301/8302 RF Version to 1.5GHz from...£200-£300

CLASSIC AVOMETER DA 116 DIGITAL 3.5 DIGIT COMPLETE WITH BATTERIES AND LEADS ONLY £30

SOLARTRON 7045 BENCH MULTIMETER 4 1/2 digit BRIGHT LED WITH LEADS ONLY £30

IT'S SO CHEAP YOU SHOULD HAVE IT AS A SPARE

- HUNTRON TRACKER Model 1000...£125
- H.P. 5315A Universal Counter, 1GHz, 2-ch...£80
- FLUKE 8050A DMM 4 1/2 digit 2A True RMS...£75
- FLUKE 8010A DMM 3 1/2 digit 10A...£50

TIME 1051 Low Ohm Res Box 0.01ohm to 1M Ohm in 0.01ohm steps. Unused £100

STEWART of READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: (0118) 9268041 Fax: (0118) 9351696
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

LANGREX SUPPLIES LTD
DISTRIBUTORS OF ELECTRONIC VALVES TUBES AND SEMICONDUCTORS AND I.C.S.
1 MAYO ROAD • CROYDON • SURREY CR0 2QP
24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS
email: langrex@aol.com

AZ31	8.00	KT66 Special	20.00	5Z4GT	3.00	6UBA	1.50
CL33	15.00	KT88 Special	20.00	6AU6	2.00	6V6G	10.00
E88CC	8.50	OA2	3.00	6AR5	6.00	6V6GT	6.00
E180F	3.50	OB2	3.00	6AS7G	7.50	6X4	3.00
E810F	20.00	OC3	3.00	6AU5GT	4.00	6X5GT	3.00
EABC80	4.00	OD3	3.00	6AU6	2.00	12AT7	3.00
EB91	1.50	PCF80	2.00	6B4G	4.00	12AU7	3.50
EBF90	1.50	PCL82	2.50	6BA6	1.50	12AX7	5.00
EBF89	1.50	PCL85/805	2.50	6BE6	1.50	12AX7A	7.50
EBL31	25.00	PCL86	2.50	6BH6	2.00	12AX7WA	6.00
ECC33	12.00	PD500	8.00	6BO7A	2.00	12BE6	2.00
ECC35	12.00	PL36	3.00	6BR7	4.00	12BH7	10.00
ECC81	3.00	PL81	2.00	6BR8	4.00	12BY7A	7.00
ECC82	5.00	PL504	3.00	6BW6	4.00	12DW7	15.00
ECC83	3.00	PL508	3.00	6BW7	3.00	12E1	10.00
ECC85	5.00	PL509/519	10.00	6BX7GT	7.50	13E1	85.000
ECC88	6.00	PL802	4.00	6BZ6	3.00	572B	27.50
ECC808	15.00	PY500A	3.00	6C4	2.00	805	45.00
EFC80	1.50	PY800/801	1.50	6CB8A	3.00	807	7.50
ECH35	3.50	QOV02-6	12.00	6DC6G	5.00	811A	10.00
ECH42	3.50	QOV03-10	5.00	6CL6	3.00	812A	55.00
ECH81	3.00	QOV03-20A	10.00	6CG7	7.50	813	27.50
ECL82	5.00	QOV06-40A	12.00	6CH6	3.00	833A	85.00
ECL86	5.00	QOV06-40A	12.00	6CH4	8.00	866A	20.00
ECLL800	25.00	UABC80	1.60	6D05	17.50	872A	30.00
EF37A	3.50	UCH42	5.50	6DO6B	10.00	931A	25.00
EF39	2.75	UCL82	2.00	6F6G	8.00	2050A	12.50
EF40	4.00	UCL83	2.00	6FQ7	7.50	5687WB	6.00
EF86	5.00	UF89	4.00	6GK6	4.00	5763	8.00
EF91	2.00	UL41	12.00	6J5G	6.00	5814A	5.00
EF183/4	2.00	UL84	3.00	6J5M	4.00	5842	12.00
EL33	15.00	UY41	4.00	6J7	3.00	6072A	6.00
EL34	5.00	UY85	2.00	6J8A	27.50	6080	6.00
EL34G	5.00	VR105/30	3.00	6JEC	27.50	6146B	15.00
EL36	5.00	VR150/30	3.00	6JS8C	27.50	6201	8.50
EL41	3.50	Z759	10.00	6K6GT	4.00	6366A	35.00
EL84	3.00	Z803U	15.00	6L6G	15.00	6550A	25.00
EL95	2.00	ZD21	3.50	6L6GC	17.50	6883B	15.00
EL360	15.00	3B2B	12.00	6L6WGB	10.00	607	7.50
EL509/519	7.50	4CX250B	45.00	607	8.00	7025	26.00
EM34	25.00	5R4GY	7.50	6SA7	3.00	7027A	26.00
EM81A/7	5.00	5U4G	10.00	6SC7	3.00	7360	26.00
EN91	7.50	5U4GB	10.00	6SG7	3.00	7581A	15.00
EZ80/EZ81	5.00	5V4G	5.00	6SJ7	3.00	7586	15.00
GZ32	8.50	5Y3GT	2.50	6SK7	3.00	7587	20.00
GZ33/37	15.00	5Z4	5.00	6SN7GT	7.50		
KT61	15.00	5Z4G	6.00	6SN7GT	7.50		

OPEN TO CALLERS MON-FRI 9AM-4PM. CLOSED SATURDAY
This is a selection from our stock of over 6,000 types. Please enquire for types not listed. Obsolete items are our speciality. Valves are new mainly original British or American brands.
Terms CWO/min order £10 for credit cards.
P&P 1-3 valves £2.00, 4-5 valves £3.00
Add 17.5% VAT to total including P&P

SCOPE FOR IMPROVEMENT GOULD OS 300 OSCILLOSCOPE DUAL TRACE 20MHz TESTED WITH MANUAL FOR THE FIRST TIME EVER ONLY IT'S SO CHEAP YOU SHOULD REPLACE THAT OLD SCOPE £95

- MARCONI 2022E Synthesised AM/FM Sig Gen 100Hz-1.01GHz LCD Display etc...£525-£750
- H.P. 8557A Synthesised 2.18GHz Sig Gen...£4000
- H.P. 8557A Synthesised 100Hz-1040MHz Sig Gen...£2800
- H.P. 8558B Synthesised 100Hz-990MHz Sig Gen...£1350
- H.P. 8558A Synthesised 100Hz-990MHz Sig Gen...£395
- H.P. 8640A AM/FM 500Hz-1024MHz Sig Gen...£400
- H.P. 8640A AM/FM 500Hz-512MHz Sig Gen...£250
- PHILIPS PMS328 100Hz-180MHz with 200MHz Sig Gen Freq Counter IEEE...£550
- RACAL 9081 Synth AM/FM Sig Gen 5-520MHz...£250
- H.P. 3325A Synth Function Gen 21MHz...£600
- MARCONI 650C Amplitude Analyser...£1500
- H.P. 4275A LCR Meter 10Hz-10kHz...£2750
- H.P. 8930A Distortion Analyser...£1000
- WAYNE KERR 3245 Inductance Analyser...£2000
- H.P. 8112A Pulse Generator 50MHz...£1250
- DATRON AutoCal Multimeter 5 1/2-7 1/2 digit 1065/1061A/1071...from £300-£900

ROHOE & SCHWARZ APH 62 SYNTHESISED 1Hz-260kHz SIGNAL GENERATOR, BALANCED/UN-BALANCED OUTPUT, LCD DISPLAY £425

- H.P. 6012B DC PSU 0-60V, 0-50A 1000W...£1000
- FARNELL AP60/50 1kW Autotranging...£1000
- FARNELL H60/50 0-50V, 0-50A...£750
- FARNELL H60/25 0-50V, 0-25A...£400
- Power Supply HPS3010 0-30V, 0-10A...£140
- FARNELL L30-2 0-30V, 0-2A...£80
- FARNELL L30-1 0-30V, 0-1A...£60

PORTABLE APPLIANCE TESTER MEGGER PAT2 Only £180

SPECTRUM ANALYSERS

- ADVANTEST R3261A 9kHz-2.6GHz Synth...£4000
- EATON/ALTECH 757 0.001-22GHz...£2500
- TEKTRONIX 492 50kHz-18GHz...£3500
- H.P. 8558B with Main Frame 100kHz-1500MHz...£1250
- H.P. 853A (Dig Frame) with 8559A 100kHz-21GHz...£2750
- H.P. 3580A Audio Analyser 5Hz-50kHz As new...£1000

UNUSED OSCILLOSCOPES

- TEKTRONIX TAS485 4 Ch 200MHz etc...£900
- H.P. 54605 Dual Trace 100MHz 20MS/S...£900
- TEKTRONIX THS720A Dual Trace L.C.D. 100MHz 500MS/S...£900
- TEKTRONIX THS 720P as THS 720A, power measurement...£1300
- TEKTRONIX THS 710 Dual Trace, 60MHz 250MS/S...£750
- HITACHI VC6523 Dual Trace, 20MHz 20MS/S Delay Cursor etc...£800

OSCILLOSCOPES

- PHILIPS PM3092 2+2 Ch 200MHz, Delay etc...£800
- As new...£950
- PHILIPS PM3082 2+2 Ch 100MHz, Delay etc...£700
- As new...£800
- TEK TAS465 Dual Trace 100MHz, Delay...£800
- TEK 2465B 4 Ch 400MHz Delay Curs...£1250
- TEK 2465 4 Ch 300MHz Delay Curs...£900
- TEK 2445/A/B 4Ch 150MHz, Delay etc £500-£900
- TEK 468 Dig Storage, Dual 100MHz Delay...£450
- TEK 466 Analogue Storage, Dual 100MHz...£250
- TEK 485 Dual Trace 350MHz, Delay...£600
- TEK 475 Dual Trace 200 MHz, Delay...£400
- TEK 465B Dual Trace 100MHz, Delay...£325
- PHILIPS PM3217 Dual Trace 50MHz Delay...£250-£300

RACAL RECEIVER RA1772 50kHz-30MHz, LED display, Basically working £250

USED EQUIPMENT - GUARANTEED. Manuals checked. This is VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

PPM5
20 pin DIL Peak Programme Meter
PROFESSIONAL MEASUREMENT OF AUDIO LEVEL

Consumption 3mA. Fully meets BS5428-9

★ PPM10 In-Vision PPM and Chart Recorder ★ Advanced Active Aerial 4kHz-30MHz ★ Stabilizer frequency shift units for howl reduction ★ Stereo Variable Emphasis Limiter ★ PPM9, PPM5 hybrid and PPM8 IEC/DIN -50/+6dB drives and movements ★ Broadcast Monitor Receiver 150kHz-30MHz ★

SURREY ELECTRONICS LTD
The Forge, Lucks Green, Cranleigh GU6 7BG
Telephone: 01483 275997 Fax: 01483 276477

NEW PRODUCTS

Please quote **Electronics World** when seeking further information

tunable RF stages, garage door openers, keyless entry, industrial wireless control, and precision trimming of capacitive-based sensors.


Maxim

Tel: 0118 930 3388

www.maxim.com

Frequency converters have variable outputs

Magnus Power has launched the redesigned LP series of frequency converters, which is offered with either single or three phase output. The single phase range consists of the LP300, 600 and 1000 and is rated at 300, 600 and 1kVA respectively. Each model has an output frequency that is variable from 45Hz to 440Hz. Output voltage varies from zero to maximum in two ranges, usually 0-135V, and 0-270V. Output current

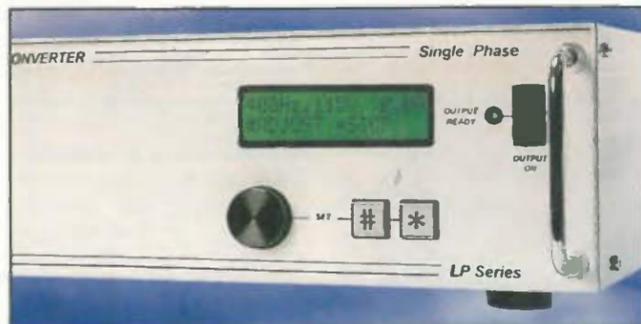

capability is doubled on the lower range.

Magnus Power

Tel: 0116 2672856


www.magnus-

sales@kvaerner.com

TFT-LCD module with A/D conversion board

Customised versions are available on request. Semicon is offering a 15in TFT-LCD module that

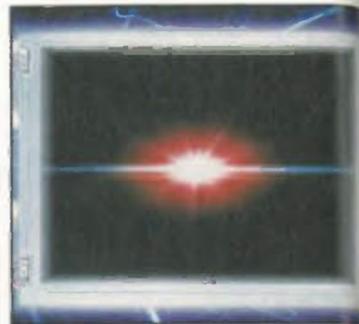incorporates the A/D conversion board. Eliminating the need for a discrete A/D circuit and the associated interfaces to the LCD module, Hyundai's HM15X11 and HM15X12 LCD modules support XGA resolution, 16.7 million colours and a refresh rate of up to 75Hz, without external frame memory. Features also include automatic detection of changes in input



display mode and frame rate and power management capabilities that meet DPMS and VESA requirements. The CCFL backlight delivers a typical brightness of 200cd/m² (at 6.0mA), whilst an option allows luminance to vary according to the ambient brightness.

Semicon

Tel: 01279 422224

www.semicon.co.uk

BOOK TO BUY

Servicing Audio and Hi-Fi Equipment

Return to Jackie Lowe, Cumulus Business Media
Anne Boleyn House, 9-13 Ewell Road, Cheam,
Surrey, SM3 8BZ

Please supply the following title:

Servicing Audio and Hi-fi Equipment

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Mastercard/Visa/Cheque/PO

Cheques should be made payable to Cumulus Business Media

Credit card no _____

Card expiry date _____

Signed _____

'Its readers will benefit from its wealth of easily assimilated information, and repairs hitherto thought impossible will speedily become routine. And the first may well cover its purchase price. Congratulations on a comprehensive, well-written and lucid work' *Electronics Informer*.

'Interesting, entertaining and useful for both practitioners and teachers. All round a satisfying book which deserves to be considered as a tool rather than an ornament collecting dust on the shelf.' *Skillset Newsletter*


Service engineers and technicians have come to regard this book as essential to their work. As a bench-side companion and guide it has no equal. Its purpose is to ease and speed up the processes of fault diagnosis, repair and testing of all classes of home audio equipment: receivers, amplifiers, recorders and playback machines. The mechanics and electronics of domestic audio are examined by Nick Beer in a down-to-earth and practical way, concentrating on what goes wrong, how to track down problems, and how to solve them.

A symptom index and comprehensive manufacturer and supplier guide allow quick access to specific advice and suggestions.

The third edition is bang up to date with the latest technology - DVD, CD Recordable, PC audio systems. There is also new material on PA equipment.

UK Price: £32.00 Europe £34.00 ROW £36.50

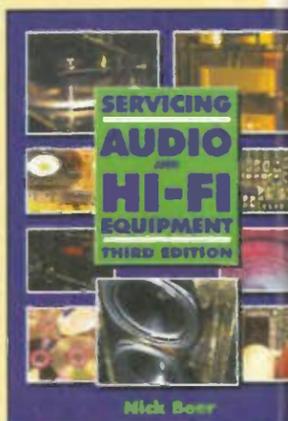****Price includes delivery and packing****



* Essential bench companion for all service engineers.

* New technology such as DVD and expanded material on MiniDisk will ensure another successful launch to this new edition

BOOK TO BUY

The definitive biography of the century's godfather of invention—from the pre-eminent Edison scholar "Israel's meticulous research and refusal to shy away from the dodgier aspects of Edison's personality offers a fresh glimpse into the life of the inventor."—*New Scientist*

"Remarkable."—*Nature*


"An authoritative look into Edison's working methods, here leavened by enough personal detail to give the achievements shape."—*Publishers Weekly*

"Israel's book should go a long way toward taking Edison out of the shadows and placing him in the proper light."—*Atlanta Journal-Constitution*

"Exhaustively researched, with strong emphasis on Edison's methods and achievements."—*Kirkus Reviews*

The conventional story of Thomas Edison reads more like myth than history: With only three months of formal education, a hardworking young man overcomes the odds and becomes one of the greatest inventors in history.

But the portrait that emerges from Edison: A Life of Invention reveals a man of genius and astonishing foresight whose career was actually a product of his fast-changing era. In this peerless biography, Paul Israel exposes for the first time the man behind the inventions, expertly situating his subject within a thoroughly realized portrait of a burgeoning country on the brink of massive change. Informed by Israel's unprecedented access to workshop diaries, notebooks, letters, and more than five million pages of archives, this definitive biography brings fresh insights to a singularly influential and triumphant career in science.

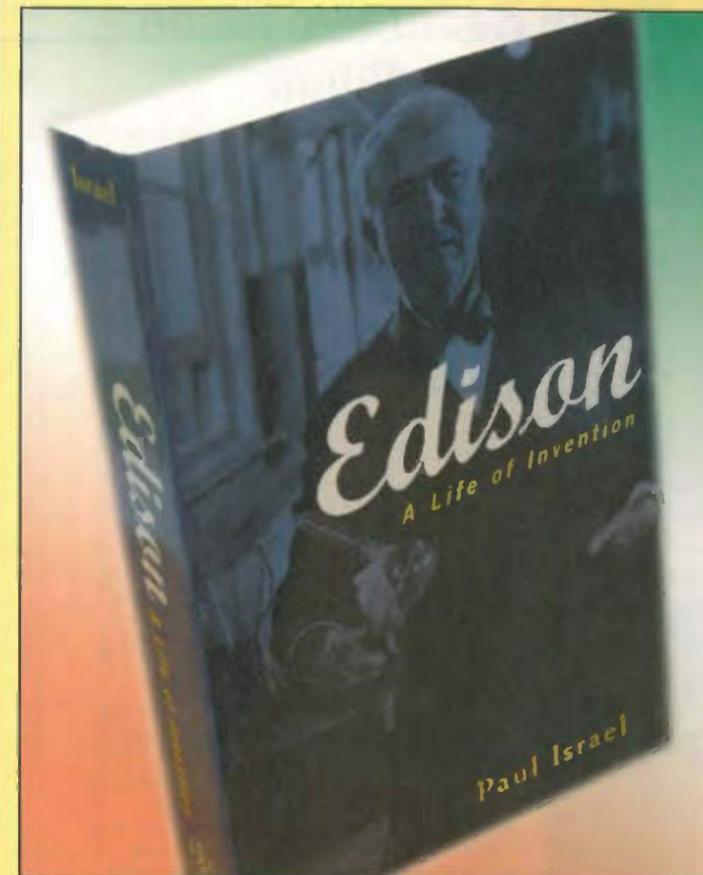

Post your completed order form to:-
Jackie Lowe, Cumulus Business Media,
Anne Boleyn House, 9-13 Ewell Road, Cheam,
Surrey, SM3 8BZ

Fax your completed order form to 020 8643 8952
UK Price: £16.50 Europe £18.50 ROW £21.00

How to pay (Edison) paperback

I enclose a cheque/bank draft for £ _____
(payable to Cumulus Business Media)

Please charge my credit/charge card

Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

BOOK TO BUY

Valve Radio and Audio Repair Handbook

* A practical manual for collectors, owners, dealers and service engineers * Essential information for all radio and audio enthusiasts * Valve technology is a hot topic

This book is not only an essential read for every professional working with antique radio and gramophone equipment, but also dealers, collectors and valve technology enthusiasts the world over. The emphasis is firmly on the practicalities of repairing and restoring, so technical content is kept to a minimum, and always explained in a way that can be followed by readers with no background in electronics. Those who have a good grounding in electronics, but wish to learn more about the practical aspects, will benefit from the emphasis given to hands-on repair work, covering mechanical as well as electrical aspects of servicing. Repair techniques are also illustrated throughout.

This book is an expanded and updated version of Chas Miller's classic Practical Handbook of Valve Radio Repair. Full coverage of valve amplifiers will add to its appeal to all audio enthusiasts who appreciate the sound quality of valve equipment.

Contents: INCLUDES: Electricity and magnetism; Voltage, current, resistance and Ohm's Law; Real life resistors; Condensers; Tuning; Valves; Principles of transmission and reception; Practical receiver design; Mains valves and power supplies; Special features of superhets; Battery and mains battery portable receivers; Automobile receivers; Frequency modulation; Tools for servicing radio receivers; Safety precautions; Fault finding; Repairing power supply stages; Finding faults on output stages; Faults on detector/AVC/AF amplifier stages; Finding faults on IF amplifiers; Faults on frequency-changer circuits; Repairing American 'midget' receivers; Repairing faults on automobile radios; Repairing battery operated receivers; Repairing FM and AM/FM receivers; Public address and high fidelity amplifiers.



UK Price: £22.50 Europe £25.00 ROW £27.00

** Price includes delivery and packing **

Return to Jackie Lowe, Cumulus Business Media
Anne Boleyn House, 9-13 Ewell Road, Cheam,
Surrey, SM3 8BZ

Please supply the following title:

Valve Radio and Audio Repair Handbook

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Mastercard/Visa/Cheque/PO

**Cheques should be made payable to
Cumulus Business Media**

Credit card no _____

Card expiry date _____

Signed _____

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

USB 2.0 controller with serial interface engine

Cypress Semiconductor has added to its recent USB 2.0 controller announcement with a serial interface that provides a 480Mbit/s USB 2.0 connection to a peripheral containing a microcontroller. It does this without draining the controller's resources, said the firm. The EZ-USB SX2 integrates a USB 2.0 transceiver, a PLL, an SIE, a 4kbyte FIFO, and a local bus interface. The integrated SIE takes care of USB housekeeping chores, so the microcontroller can spend its resources on the peripheral application.

Cypress Semiconductor
Tel: 01707 378700
www.cypress.com

10-bit Gunning logic transceiver

Fairchild Semiconductor has added the GTLP10B320 to its range of Gunning logic transistor (GTLP) products. It is a 10-bit

universal bus transceiver, with separate LVTTTL inputs and outputs, as well as a feedback path for diagnostics, that provides LVTTTL to GTLP signal level translation. High-speed backplane operation is a direct result of GTLP's reduced output swing, high drive, reduced input threshold levels, and output edge rate control, said the firm. GTLP is the firm's derivative of the Gunning Transistor Logic (GTL) JEDEC standard JESD8-3. All devices are process, voltage and temperature compensated. While many transceiver technologies are designed and specified for lumped-load environments, this device is optimised for distributed-load environments that characterise backplane applications. Designed using BiCMOS process technology, the GTLP devices operate at 3.3V and provide 50mA drive for backplane environments. ■

Fairchild Semiconductor
Tel: 001 888 522 5372



Development environment for Motorola MSC8101 DSP

Green Hills Software has introduced the Multi 2000 integrated development environment (IDE) for Motorola's MSC8101 DSP based on the Starcore SC140 core. The IDE has a C and C++ optimising compiler for the Starcore SC140 EFR benchmarks and provides editing, debugging, profiling and project management capabilities. It automates software development. The source-level debugger, with incremental debug capability that supports process- and system-level debug, is RTOS aware, which lets designers debug and tune applications at a task level. An instruction set simulator lets programmers develop and test code on a PC or workstation without the target hardware. The compiler automatically partitions C programs for execution on the DSP's Mac, ALU and BFU processors. It also provides more than 100 optimisations to boost performance and code efficiency. The compiler increases parallelism by reordering operations within loops, and reduces looping overhead by supporting zero-overhead hardware looping for loops that are nested up to four deep. It collects frequently used data and places it in the lower 16 bits of the address space. This lets the data be accessed using 32-bit instructions, thereby improving VLES packing efficiency.

Green Hills Software
Tel: 01494 429336
www.ghs.com

WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES (using a video capture card)



"Liesgang diav" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + vat = £43.48

30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole £35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses. £32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle £15.97 + vat = £18.76

VSL4022F 4mm F1.22 63x47 degrees viewing angle £17.65 + vat = £20.74

VSL6022F 6mm F1.22 42x32 degrees viewing angle £19.05 + vat = £22.38

VSL8020F 8mm F1.22 32x24 degrees viewing angle £19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle £26.43 + vat = £31.06

VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle £77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat

1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.)

the pack is new and unused and can be broken open quite easily £7.46 + vat = £8.77

Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS

276-278 Chatsworth Road, Chesterfield, S40 2BH.
Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch
Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

CIRCLE NO. 120 ON REPLY CARD

The Stereo Headphone Amplifier Box

Balanced or unbalanced line inputs to stereo headphone output
Professional portable units operating from an internal PP3 battery or external mains adaptor



*Precision transformerless differential left and right inputs
*Wide range of headphone drive impedances *High common mode rejection *Low noise and distortion *Low quiescent power consumption for extended battery life *Extensive RFI protection

The Balance Box (mic/line amplifier) - The Phantom Power Box - The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW
Information line 01428 751469 Fax 751223

E-mail contact@confordelec.co.uk
Web http://www.confordelec.co.uk/

CIRCLE NO. 121 ON REPLY CARD

Need directing to filters...

cables, connectors or sockets?

Whatever your business needs find it on kompass.com.

WWW.KOMPASS.COM

1.5 million companies worldwide at your fingertips.

Telephone: +44(0)1342 335876.

CIRCLE NO. 122 ON REPLY CARD

Pro audio-visual router

Available commercially as the AVRS8x4, Emil Vladkov's audio and video router system allows you to select one of eight video inputs and one of eight stereo audio channels using either a keypad or a PC. This second article looks at the multiplexer's software.

Audio specifications

Input	
Impedance	>20kΩ balanced (600Ω option)
Level	+27dBμ maximum
Number of inputs	8-balanced stereo
Common mode rejection	>40dB, 20Hz to 20kHz
Output	
Impedance	600Ω balanced
Level	+27dBμ maximum
Number of outputs	2 balanced stereo
Gain	1
Frequency response	≤±0.25dB, 20Hz±20kHz
Total harmonic distortion	0.03%, 20Hz to 20kHz
Intermodulation distortion	<0.05 % (SMPTE)
Crosstalk	> 60dB to 20kHz
Noise Floor	-75dBμ, 30kHz BW
Coupling	DC
DC on output	±50mV maximum

In the first article describing this professional audio-visual router, I looked at the hardware side of the design. Many of the router's functions are carried out in software by code in the router microcontroller's on-chip PROM. The program that forms the user interface to the PC can be used to add further features.

Software, and router configurations used in a typical studio environment, are the subjects of this second article.

Software for the router's microcontroller

It is not possible to publish the whole firmware assembler code for the VRS-8x4 video switcher, the ARS-8x2 audio switcher and the PVR5-1 keyboard, due to the limited amount of space available. However, the source code can be obtained via e-mail, as can the object code, which is available free of charge.

Object code for those of you who want to use it without any modifications is given in Listings 1-3, presented later in the article.

Code for the video and audio switchers has to be burned into a standard 27256-type 32K PROM.

The code for Atmel's 89C2051 micro can be programmed into the controller's onboard flash with a parallel port programmer. You can buy such a programmer or build one yourself using the documentation, provided on Atmel's web-site (<http://www.atmel.com>).

Configuration commands

Usually, the user will control the complete routing system through its own keyboard or via a PC serial link. If you want to build your own interface or control the system through a terminal emulation program (set to 9600/8/1/N) you need to know the serial commands that the firmware can understand. These are listed in Table 1.

All commands are ASCII-strings. Each command ends with a carriage return – not with a carriage return plus line feed.

It is worth mentioning how the keyboard retrieves the active configuration after power is applied. Imagine you have a valid start-up

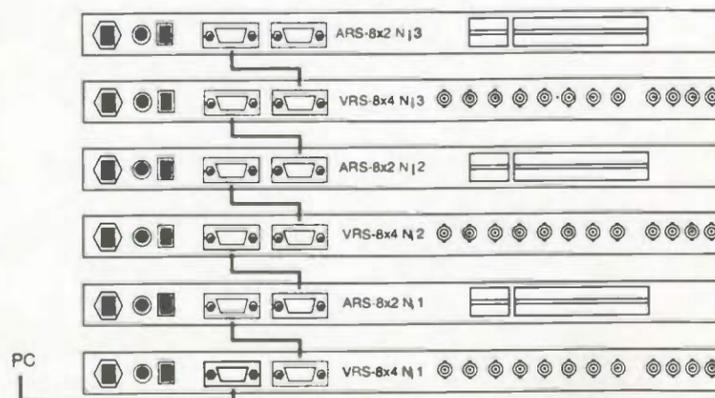


Fig. 1. Three video and audio router pairs daisy chained and controlled via a PC.

Table 1. These are the serial commands to which the audio-visual router system responds.

Audio and video router commands:

Command	Description
Out1InX	Connects Output 1 to Input X (number 1 to 8)
Out2InX	Connects Output 2 to Input X (number 1 to 8)
Out3InX	Connects Output 3 to Input X (number 1 to 8) - ignored by ARS-8x2
Out4InX	Connects Output 4 to Input X (number 1 to 8) - ignored by ARS-8x2
Out1InD	Disable Output 1
Out2InD	Disable Output 2
Out3InD	Disable Output 3 - ignored by ARS-8x2
Out4InD	Disable Output 4 - ignored by ARS-8x2
Out1234InXXXX	All outputs configure command, X is a number between 1 and 8 or D for disable
SOut1234InXXXX	Save StartUp configuration command, X is a number between 1 and 8 or D for disable
DIXXXDXIXXXDIXXX...	Configure command for stacked devices. Up to 4 devices can be connected, so the command can contain up to 4 sections. The first section is for the first device in stack, the second for the second device and so on. X is a number between 1 and 8 or D for disable.
SOut1234InXXXXInXXXX...	Save StartUp configuration command for stacked devices. X is a number between 1 and 8 or D for disable.
GetConf	Gets the current configuration command. The switcher returns the configuration for Output 1 and Output 2 in the format Out1InXOut2InX. This command is issued by the PVR5-1 keyboard.
GetConfF	Gets the full current configuration command. The switcher returns the configuration for Output 1, Output 2, Output 3 and Output 4 in the format Out1InXOut2InXOut3InXOut4InX. This command is issued by the PC interface software.

Keyboard commands:

Command	Description
Out1InXOut2InX	Configure the keyboard command - internal registers are set up and the corresponding LEDs are enabled according to the current configuration.

configuration, or you have set up the connection paths through a PC interface and you change the control method from PC to keyboard on the fly. This is possible by the way.

The corresponding LEDs on the video router have to be lit and that the internal configuration registers of the keyboard software need to know the current configuration. This is done in as follows.

After power is applied the keyboard, the microcontroller waits 100ms and then issues the 'GetConf' command. The router

acknowledges this command by returning the active configuration in an 'Out1InXOut2InX' format. This format is a command for the video router and is used by the 89C2051 code to set up the internal registers and to light the appropriate LEDs.

An interesting situation arises if you control the 8-by-4 video matrix using an 8-by-2 keyboard. You will not be making full use of the crosspoint switch in this case, but if you do not need the capacity, there is little point in implementing the full keyboard.

From the keyboard, you can specify connections only for two outputs – outputs 1 and 2 in this case. However, the keyboard subsystem is designed so that it also configures output 3 to mirror output 1 and output 4 to mirror output 2. These additional outputs can be used for monitoring purposes.

Typical configurations

This section outlines some typical configurations of the routing system that you might find useful in studio applications.

Audio follows video router, PC control. In the configuration shown in Fig. 1, the whole system is controlled via a host PC using appropriate software.

My PC graphical user interface software supports up to four stacked pairs of audio and video routers. Using this software, Fig. 2, the 'Audio' check box in the control window of the PC interface (details later) has to be checked for correct operation.

In this configuration the user can control up to four audio and video switcher pairs completely independently. Each device pair responds only to serial commands from the PC that are designated for it. You don't need four serial ports or four PCs to control the four switchers in your studio – you have only one single interface.

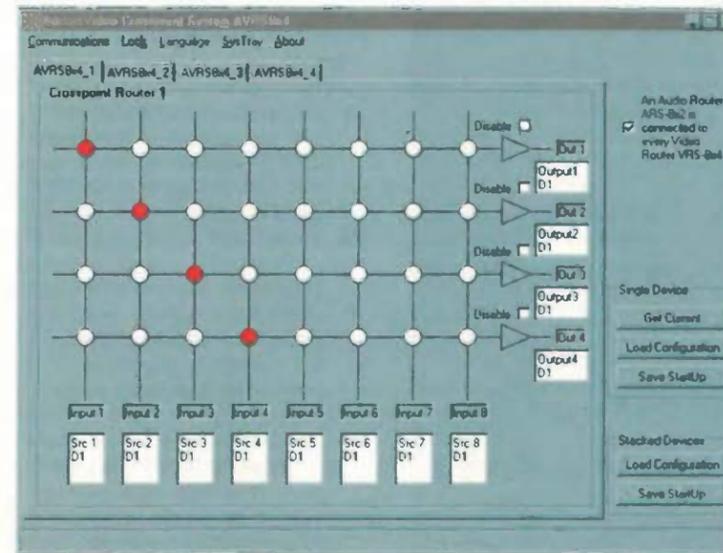


Fig. 2. Screen shot of the author's Windows software for controlling single or multiple audio and video routers.

Fig. 3. In this configuration, an ARS-8x2 audio and a VRS-8x4 video router are controlled via a PVRS-1 keyboard.


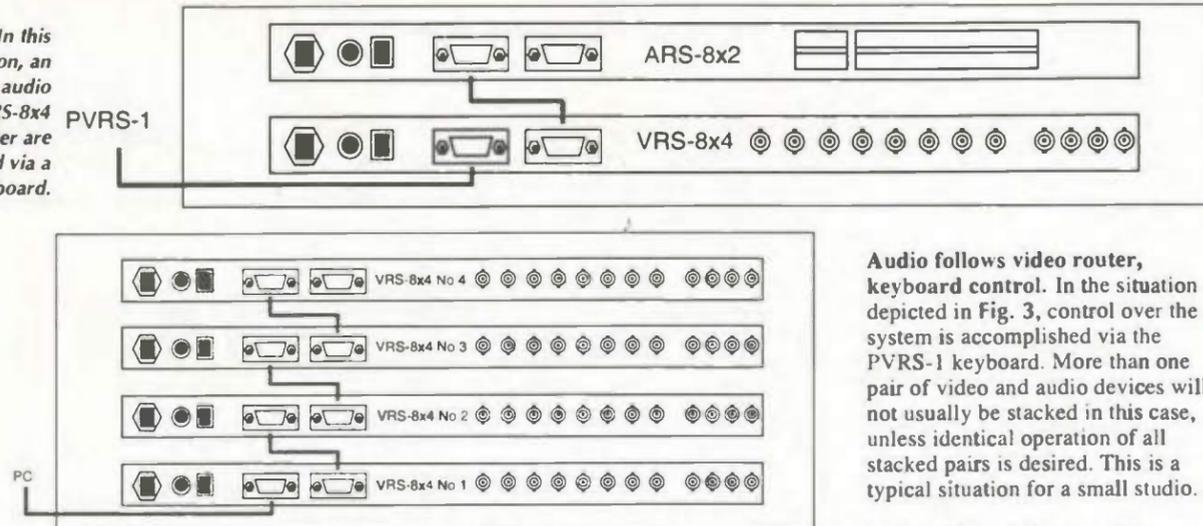


Fig. 4. It is possible to stack just video routers or audio routers and control them via a PC.

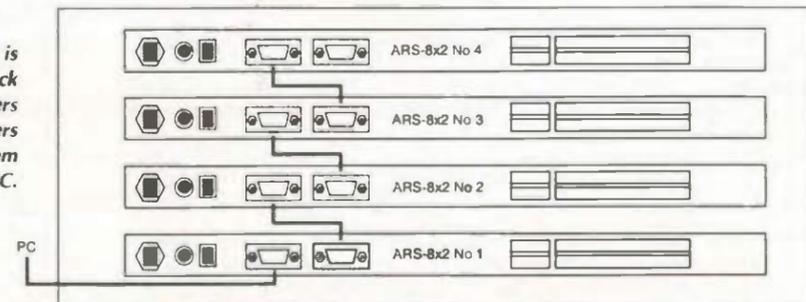

Video specifications of the 8x4 audio-visual multiplexer

Input	
Video type	Composite DC or AC coupled, backporch at ground
Impedance	75Ω, internally terminated
Number of inputs	8
Return loss	>40dB to 10MHz
Level	1V p-p nominal +1.5V to 0.5V
Sync input	1V p-p composite video or 0.4V p-p composite sync
Synchronisation	From input 1 or sync input jumper selectable
Output	
Number of outputs	4
Impedance	75ΩDC (or AC) coupled
Return loss	>40dB to 10MHz
Frequency response	<±0.5dB to 5MHz 3dB bandwidth 90MHz
Gain	1 ±0.05dB
Differential phase	<0.140
Differential gain	<0.13%
Tilt	<0.1% (DC coupled mode)
Sync output	2.5Vp-p (loaded 75Ω) from sync Input or input 1 depending on jumper position
Crosstalk	>55dB worst case @ 4.43MHz >65dB typ. @ 4.43MHz
S-to-n, inc. hum	>70dB unweighted wideband >76dB unweighted to 10MHz
Switch	Vertical interval (external sync or from master input signal)
Electrical	
Power consumption	Approximately 8W

Note: some specifications will depend on PCB layout. Figures given are for author's design.

Audio follows video router, keyboard control. In the situation depicted in Fig. 3, control over the system is accomplished via the PVRS-1 keyboard. More than one pair of video and audio devices will not usually be stacked in this case, unless identical operation of all stacked pairs is desired. This is a typical situation for a small studio.

Independent video or audio stacks, mostly PC control. In this case, Fig. 4, all devices in the stack are of the same type. They are either VRS-8x4 video routing systems or ARS-8x2 audio routing systems. Control is usually performed via a host PC.

As in the case of the keyboard control, all devices will be loaded with the same configuration. Up to four devices can be controlled through the GUI application software that I developed.

The 'Audio' check box in the Windows interface is not checked in the depicted configuration – even if you are using only audio routers. This check box is only meaningful when you are using the audio-follows-video configuration.

Creating a graphical user interface

My user interface, Fig. 2, is compiled to run in Windows 95/98 environment. It has the following menus:

- Menu 'Communications' – the user can select the COM port of the PC, connected to the system. The software supports COM1 to COM4.
- Menu 'Lock' – the application software is locked and unlocked with this menu. When locked, the user can change the connection patterns of all stacked devices, but can not download the selected configuration to the target device. In this way, accidental switching and possible errors and program drops are prevented. This function is the same as the hardware lock switch on the PVRS-1 keyboard.
- Menu 'Language' – the application software supports two languages – English and my

Listing 1. Video switcher firmware.

```

:030000000200807B
:0800030012066B3232323278
:08000B0012066E323232326D
:08001300323232323232255
:08001B00323232323232324D
:0800230012028323232329F
:1000800075A800D2B5D2B4C2D1E5877C2E7F58775AD
:100090008DFD758BFD758921D28E759850D2B9D2A0
:1000A000B8D2ACD2AF4C0E07980E4C312074640D6
:1000B000F9B45A06D0E02401C0E07990E4C31207F5
:1000C0004640F9B45A06D0E02402C0E079A0E4C367
:1000D00012074640F9B45A06D0E02404C0E0D0E04C
:1000E000B4000302010DBA070280030201F21208FA
:1000F0002378307900E4C312074640F9B60809B4C2
:10010000DF31202AF08F08F08F08F08F79007A4D
:100110004F120914E4C3D2D112070740F4097A75CB
:10012000120914E4C3D2D112070740F4097A7412F9
:100130000914E4C3D2D112070740F4097A31120935
:1001400014E4C3D2D112070740F4097A3212091419
:10015000E4C3D2D112070740F4097A33120914E438
:10016000C3D2D112070740F4097A34120914E4C348
:10017000D2D112070740F4097A49120914E4C3D214
:10018000D112070740F4097A6E120914E4C3D21E0
:1001900012070740F4097A44120914E4C3D2D112B9
:1001A000070740F4097A44120914E4C3D2D11207B4
:1001B0000740F4097A44120914E4C3D2D11207074
:1001C00040F4097A44120914E4C3D2D1120707405B
:1001D000F4097A53120914E4C3D2D112070740F488
:1001E000097A0D120914E4C3D2D112070740F412A0
:1001F00007EC79807A5A120914E4C3D2D11207074
:1002000040F479907A5A120914E4C3D2D112070744
:1002100040F479A07A5A120914E4C3D2D112070724
:1002200040F41209140200ECC2AC7830C298E5998D
:10023000F608B40D0FC2981202AFD2AC2278307615
:100240001BD2AC223098FDC298E599F608B66F022F
:100250007830B40DEF80DE22782F794F0809E6F769
:10026000B60DF92C2AC782F08C29986993099FD53
:10027000B60DF5C299D2AC22C2AC783508C29986C7
:10028000993099FDB60DF5C299D2AC22C2AC782F47
:1002900008C29986993099FDB634F5C299783D081F
:1002A000C29986993099FDB60DF5C299D2AC2278E3
:1002B00030B64F3F08B6753B08B674370808B649E4
:1002C0003208B66E2E0808B60D29783386F07836D7
:1002D000E67833B63103FC8010B63203FD800AB6EF
:1002E0003303FE8004B63401FF12055E120642128B
:1002F0000264227830B6474708B6654308B6743FB3
:1003000008B6433B08B66F3708B66E3308B6666F9B
:1003100008B60D2E2AC900922120901C2998C991F
:100320003099FDC299900929120901C2998D99301D
:1003300099FDC29975990D3099FDC299D2AC2202EE
:100340000392B6464D08B60D49C2AC900922120977
:1003500001C2998C993099FDC2999009291209011D
:10036000C2998D993099FDC299900930120901C244
:10037000998E993099FDC299900937120901C29955
:100380008F993099FDC29975990D3099FDC299D216
:10039000AC227830B64F5108B6754D08B67449088E
:1003A000B6314508B6324108B6333D08B63439088F
:1003B000B6493508B66E31783DB60D2C7839E6FC75
:1003C00075F03112055E08E6FD75F03212055E0823
:1003D000E6F75F03312055E08E6FF75F03412058F
:1003E0005E120642120264227830B6536208B64F9B
:1003F0005E08B675A08B6745608B6315208B63259
:100400004E08B6334A08B6344608B6494208B66E6B6
:100410003E783EB60D3C7900783008E6FA120914B1
:10042000E4C3D2D112070740F409B60DED197A538F
:10043000120914E4C3D2D112070740F4097A0D124D
:100440000914E4C3D2D112070740F41207EC2202C8
:100450000491B6493C7900783008E6FA120914E4B0
:100460000C3B2D112070740F409B83EED197A5312EE
:100470000914E4C3D2D112070740F4097A0D120916
:1004800014E4C3D2D112070740F41207EC12028C15
:10049000227830B64F5208B6754E08B6744A08B680
:1004A000314608B6324208B6333E08B6343A08B68A
:1004B000493608B66E32783DB6643208B66D297808
:1004C00039E6FC75F03112055E08E6FD75F0321272
:1004D0005E08E6FE75F03312055E08E6FF75F06E
:1004E0003412055E120642227830B6443908B64905
:1004F000357836B6443008B66492C7832E6FC75F0CB
:100500003112055E08E6FD75F03212055E08E6FE62
:1005100075F03312055E08E6FE75F03412055E12C1
:100520000642120278227830B6443208B6492E7854
:1005300036B60D297832E6FC75F03112055E08E614
:10054000FD75F03212055E08E6FE75F03312055EA9
:1005500008E6FE75F03412055E120642222B4311D
:1005600004740080368432047401802FB8330474F0
:1005700028028B4340474038021B43504740480E8
:100580001AB4360474058013B437047406800CB4AE
:10059000380474078005B4442E7408C0E0E5F0B454
:1005A000310775F000D0E08021B4320775F010D02B
:1005B000E08017B4330775F020D0E0800D84340725
:1005C00075F030D0E08003D0E02245F0F590C2967F
:1005D000D29790000F0D296540FB4000474FE80BD
:1005E00036B4010474FD802FB4020474FB8028B477
:1005F00030474F78021B4040474EF801AB4050472
:1006000074DF0813B4060474BF800CB40704747FD5
:100610008005B4080074FFC0E0E5F0B400059080E8
:100620000801BB410059088008013B420059090C2
:100630000800BB43005909080003908800D0E0A3
:10064000F022758A00758C4C2D5C289C28DD2A8A1
:10065000D2A9D28C30D5FDC2A9C28CC2A8C2D5D233
:1006600097D296C29700000D2972D2D522D2D537
:1006700022120681C4C0E0E5F0120681D0F045F0F8
:1006800022B43003740022B43103740122B4320363
:10069000740222B43303740322B43403740422B406
:1006A0003503740522B43603740622B43703740785
:1006B0002B43803740822B43903740922B4410304
:1006C000740A22B44203740B22B44303740C22B4A0
:1006D0004403740D22B44503740E22B44603740F10
:1006E00022B46103740A22B46203740B22B463035C
:1006F000740C22B46403740D22B46503740E22B426
:100700006603740F22E42230D12112076C401A23B1
:1007100044A0C2E0120794400DE91207944007EA92
:100720001207944001C3120786C2D121212076C40FF
:10073000142344A0D2E012079440071207B91207D0
:10074000DFC31207862C0F0F5F12076C401A23AF
:1007500044A0C2E0120794400DE91207944007E557
:10076000F12C020769120786D0F02D2D2B5D2B47C
:1007700030B51130B40E00C2B500000000C2B4A4
:10078000C30207850322C2B50000D2B4000000026
:1007900000C3B2D112070740F409B83EED197A5312EE
:1007A00000000C2B4D5F0F1D2B5000D2B4000010
:1007B000000A2B5C2B4D0F02D2D2B5C0F075F008E
:1007C0000000D2B4000A2B533C2B4D5F0F1D01D
:1007D000F022C2B5000D2B40000000C2B422D2A0
:1007E000500028B608B600000000C2B42120914798E
:1007F0000E4C312074640F9A742029F9120914DB
:10080000E4C3D2D112070740F4742029F912091465
:10081000E4C3D2D112070740F4E9C39440F909BAFE
:10082000DC22E4C0E07900E4C312074640F9F599
:10083000F0742029F9E4C312074640F9B5F009091C
:10084000B40DE5D0E004C0E07900E4C312074640EF
:100850009F9F0744029F9E4C312074640F9B5F000
:100860000A9B40DE5D0E0040C0E07920E4C31225
:10087000074640F9F5F0742029F9E4C31207464011
:100880009F9B5F00B09B40DE5D0E004040C0E00E4
:100890000E084000122B40107790075F0408018B47
:1008A0000207790075F020800E40307792075F0F7
:1008B000208029B4060022E4C312074640F9FAE575
:1008C000F029F9120914E4C3D2D112070740F4E960
:1008D000C395F09BA0DDF12091422E4C3120717
:1008E0004640F9FAE9C395F0F9120914E4C3D2D1EC
:1008F00012070740F40F5F029F909BA0DDF120914CF
:1009000022E493B48002E42C299F593099FDC2A1
:1009100099A380ED75F025E4D5F0012D5E0FD80A6
:10092000F7224F757431496E804F757432496E806D
:100930004F757433496E804F757434496E805652CA
:10094000532D3878342C20436F707972696768743E
:1009500020432032303020456D696C20566C6168
:04096000646B6F76DF
:00000001FF
    
```

native language Bulgarian. The source code for the GUI interface can be obtained, details later, so if another language is desired, the modifications can be easily done.

- Menu 'SysTray' – the application is minimised as icon in the system tray and can be activated every time the need arises. This feature is especially useful if the host PC is used for controlling other equipment at the same time. In this case, the operator does not want to be distracted by too many virtual control panels. The software for this menu is written by E. Spencer (elliott@spnc.demon.co.uk) and is public domain.
- Menu 'About' – gives information about the current version of the software.

The software also has the following ancillary control functions:

- 'AVRS8x4_1, AVRS8x4_2,

AVRS8x4_3, AVRS8x4_4' tab strip – this strip gives the configuration area the same look as the dividers in a notebook. So multiple configuration planes, one for each stacked AV system pair, are defined in the same area of the window. The maximum number of stacked systems is four, so there are four tab strips.

- 'Crosspoint Router 1, 2, 3, 4' frames – the frames for the stacked devices in sequential numerical order are switched by the tab-strip controls. In every frame, a visual representation of the 8x4 connection matrix is given. For the audio router, only rows 1 and 2 have meaning. Rows 3 and 4 can be specified as connections, but this will not have any effect on the audio router, since it has only two outputs. A valid connection can be performed by clicking on the connection circle. The active circle is highlighted in red. Clicking on the red circle again

will disable the activated connection. The selected configuration pattern(s) becomes active after the corresponding 'Load Configuration' buttons are pressed. So the operator has first to specify the configuration pattern and then to load it into the system.

- 'Disable' check box – this box is used to disable the corresponding output of the matrix.
- 'Output-, Input-' text box labels – using these controls, the user

Software availability

Object code contained in Listings 1-3 is available free of charge. The same code together with the author's Protel PCB layout and Windows 95/98 GUI is available for £15. Source code for the design is also available direct from the author. Its price will depend on whether your application is for commercial or domestic use. E-mail Ms Jackie Lowe at j.lowe@cumulustmedia.co.uk with your requirements.

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.

Send your ideas to: Jackie Lowe, Room L514, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

Glitch detector and delay

Restoration of supply after a power cut or switching of heavy duty equipment can cause power glitches that may be detrimental to some types of equipment.

One example is the ubiquitous PIR/security light. In some cases a multiple glitch can replicate the manual switching mode initiating a permanently on condition. If left, this is wasteful of power, causes unwanted light pollution and in a lengthy absence of the occupant can indicate empty premises to a potential burglar.

This circuit produces a delay on initially switching on and then monitors the supply to detect such glitches, introducing a delay and isolating the power supply. In my case this is to several security lights but the circuit may be of use to protect other types of equipment where sudden surges may cause a fault, damage or mis-operation.

A two-diode full wave rectifier

circuit produces a waveform which is shaped to produce narrow negative pulses at 10ms intervals. These are applied to a MC 14528B re-triggerable monostable with a time constant slightly longer than 10ms.

A missing pulse such as that caused by a mains glitch or drop-out will fail to extend the monostable period just before the end of its natural period. It therefore times out and the edge triggers a second monostable with a time constant of around 15s.

Diode LED2 is illuminated indicating that the power supply to external equipment is switched off. A positive level is available from pin 10 or a negative level from pin 9 of the MC 14528B to suit any switching requirement. Mechanical relays, solid-state relays and triacs can be accommodated.


In my case, a small 12V relay switches others with higher contact ratings, and manual switching is added

to control the security lights. The delay remains until such time as normal 10ms pulses return and both monostables return to their initial state.

Apart from any desired changes to the final delay period, the only adjustment is that of the 100kΩ 10-turn preset VR1. This should be adjusted until LED1 just turns off, or pin 7 may be observed on a scope until the 10ms pulses disappear. If other than an 18V transformer is used, it may be necessary to adjust the value of the bottom left 4.7kΩ resistor, just under point a, to produce suitable 10ms pulses.

A normally-closed push-button switch in one leg of the rectifier circuit is used to test the system, changing the rectified output waveform from 10ms to 20ms.

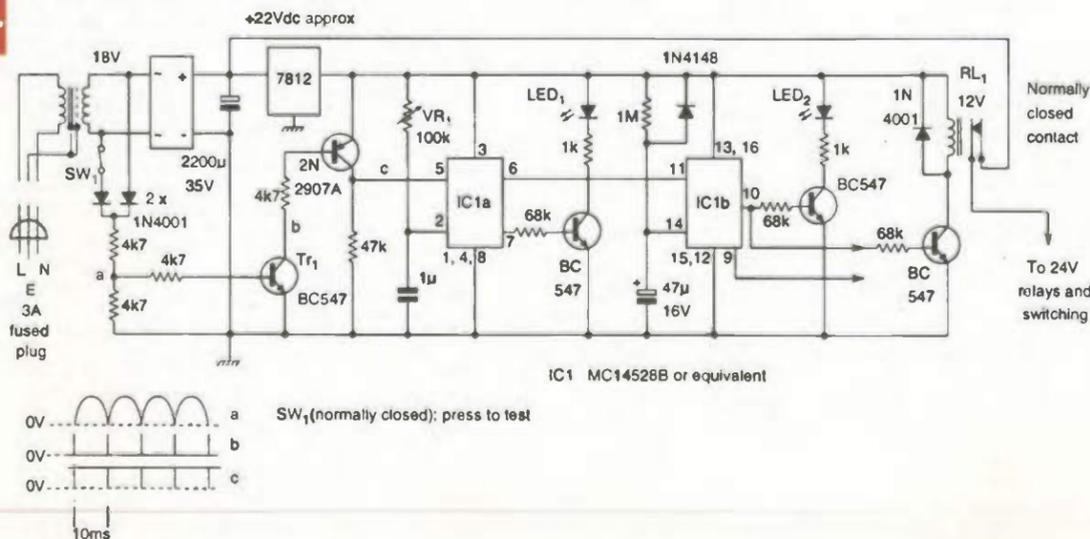N L Smith
Stoke-on-Trent
Staffordshire
F3



£50 winner

Unity-gain phase-shifter

An operational-transconductance amplifier – OTA for short – is at the heart of this phase shifter.

The relationship between e_o and e_i can be derived by using the formulae below. If e_- and e_+ are the voltages at the negative and positive inputs of the OTA respectively, and assuming $\gg R_2$ and that the gain of the output buffer is unity, then:

$$e_- = (e_i + e_o) \frac{R_2}{R_1} \quad e_+ = 0 \quad (1)$$

$$i = (e_+ - e_-) = -(e_i + e_o) g_m \frac{R_2}{R_1}$$

$$e_o - e_i = i \frac{1}{j\omega C} \quad (2)$$

$$i = (e_o - e_i) j\omega C$$

Since (1)=(2) then,

$$-(e_i + e_o) g_m \frac{R_2}{R_1} = (e_o - e_i) j\omega C$$


$$\frac{e_o}{e_i} = \frac{R_2 g_m - R_1 j\omega C}{R_2 g_m + R_1 j\omega C} = A$$

The absolute value of A is 1; the phase-shift is found to be:


$$\sin \phi = \frac{-2R_1 R_2 g_m \omega C}{R_2^2 g_m^2 + R_1^2 \omega^2 C^2}$$

In practice, with the components shown in the diagram and a source frequency of 1000Hz, the phase can be shifted between 210° and 330°. The 1nF capacitor can be scaled as required for other frequency ranges.

W. Dijkstra
Waalre
Netherlands
E98

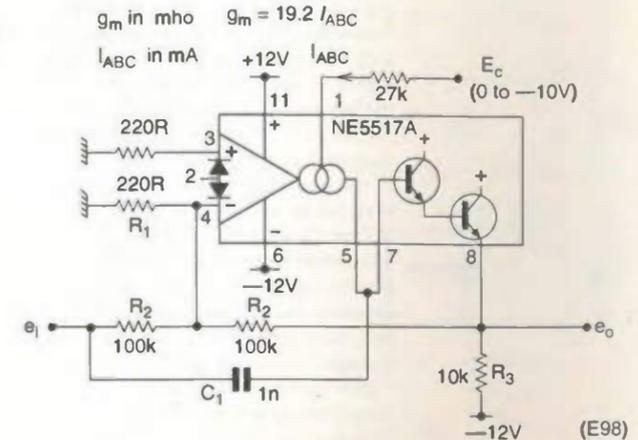

Ten year index: new update

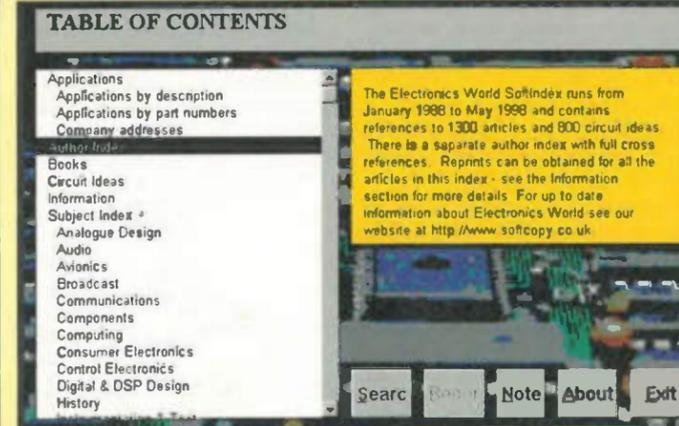

www.softcopy.co.uk

Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* indexes on paper for volumes 100, 101, and 102 are available at £2 each, excluding postage.

Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications – including a synopsis for each.

The EW index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format.

Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Ordering details

The EW index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders

Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquires about photocopies etc please send an sse to SoftCopy Ltd. Send your orders to **SoftCopy Ltd, 1 Vineries Close, Cheltenham GL53 0NU.**

Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

A versatile interface for a narrow frequency sweep display

Frequency-sweeping signal generators – or sweepers – can be used with an oscilloscope to display frequency response characteristics of a device under test. Often they have a provision for an external drive to the frequency sweep circuitry.

If a ramp output from the sweeper is available to feed the X-amplifier of the oscilloscope, the scan rate may not be low enough to display accurately a steep-sided narrow bandwidth response, such as that of a crystal filter. In such cases, a separate variable frequency ramp generator has to be used for the sweeper's external input.

If an oscilloscope having an X-sweep output (ramp output) is used with the sweeper, then this ramp can drive the external input of the sweeper, thus controlling the scan rate from the scope. However, it is likely that a direct connection of the ramp output to the sweeper's external input would be unsatisfactory – possibly even catastrophic.

Some form of signal conditioning/buffering between sweeper and scope is essential. This could provide a suitable polarity and amplitude of ramp voltage from a low source impedance to drive the sweeper for a linear frequency/X-sweep display on the oscilloscope.

An inverting/non-inverting amplifier, having a gain continuously variable between +1 and -1 has been described previously in Circuit Ideas¹. An adaptation of this circuit could form an interface unit between the sweeper and scope, to provide

flexibility of ramp output amplitude and polarity.

In a conventional swept display, frequency increases left-to-right along the X-scan. A ramp having either a positive or negative slope will be required, according to the sweeper's external input characteristics of frequency *versus* voltage. This polarity selection, together with control of ramp output from the interface, is provided by the continuously variable +1 to -1 feature.

Ramp output voltage can be made to have nominally equal excursions either side of zero. An additional control offsetting the zero allows you to centre the display on the scope screen.

A similar shift of the display by a pre-determined fixed amount, as and when required, can be derived from a stabilised voltage source in the interface. This gives a frequency calibration in terms of displayed frequency sweep, i.e. kilohertz per division on the scope screen graticule, at any particular sweep width. This facility is useful if no frequency markers are available or they are too widely spaced to cater for narrow frequency sweeps.

The circuit shown is of a battery powered interface for a specific application, using a Marconi TF2008 swept signal generator and a Gould OS250 oscilloscope. The oscilloscope ramp output is 0 to +10V from a nominal 18kΩ source. The sweeper external input characteristic is 35kHz per volt on the particular RF frequency range in use.

Calibration voltage, derived from a 1.23V band-gap reference IC₂, is set by choice of R₂ to produce a 10kHz shift of the display when the push-button switch is operated. A ramp output of +2.5V is obtained with the value of R₁ shown, but this can be adjusted to suit other source resistances and voltages of a scope ramp output.


The time-constant of C₁ × R₁ must be large enough to pass without distortion the lowest sweep frequencies used. In the application described, this was 5Hz.

The polarity of C₁ must suit the oscilloscope's ramp polarity. If a greater output than +2.5V is required, then a higher rail voltage and/or an IC₁ capable of a peak-to-peak output swing closer to the rail voltages than that provided by the MC1458 will be needed to avoid limiting.

The interface provides smooth control of sweep width between maximum and zero, so very narrow sweeps are easily set up. These, in conjunction with an 80dB dynamic range log-amp detector feeding the scope Y-amp, enable crystal filter response characteristics to be displayed over a large portion of the scope screen, making it easy to measure bandwidths and shape factors.

Ross Muddell
Malvern
Worcestershire
E78

Reference
1. EW/WW Aug. 1994 p. 688.

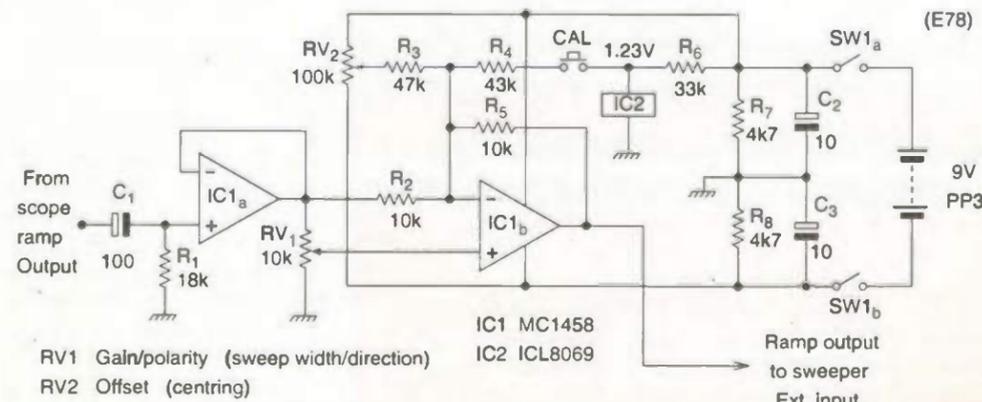

Simple stepper-motor drive

This stepper motor control circuit – or 'translator' – comprises a shift register and clock source, Fig. 1. Outputs Q_A-Q_C are gated so that if any one is high, a zero is clocked into the first stage output Q_A. When the first three stages all hold zeros, a one appears at the right-shift input. On subsequent clock pulses this is gated into Q_A, and subsequently propagates through the other stages. Thus a continuous circulating wave drive sequence is obtained.

The outputs Q_A to Q_D drive four power amplifiers, each as in Fig. 2. The wave drive sequence can be gated with NOR gates as in Fig. 3, to provide a two-phase drive sequence. In order to change the direction of the stepper motor, inputs at S₀ and S₁ are set high or low with switch SW₁. R₁ resets the translator.

The advantage of this circuit is its immunity to noise. If a noise pulse disrupts any of the Q_n outputs, the sequence is automatically re-established by succeeding clock cycles. R₂ is a reset for the clock circuit.

V Gopalakrishnan
Bangalore
India
E79

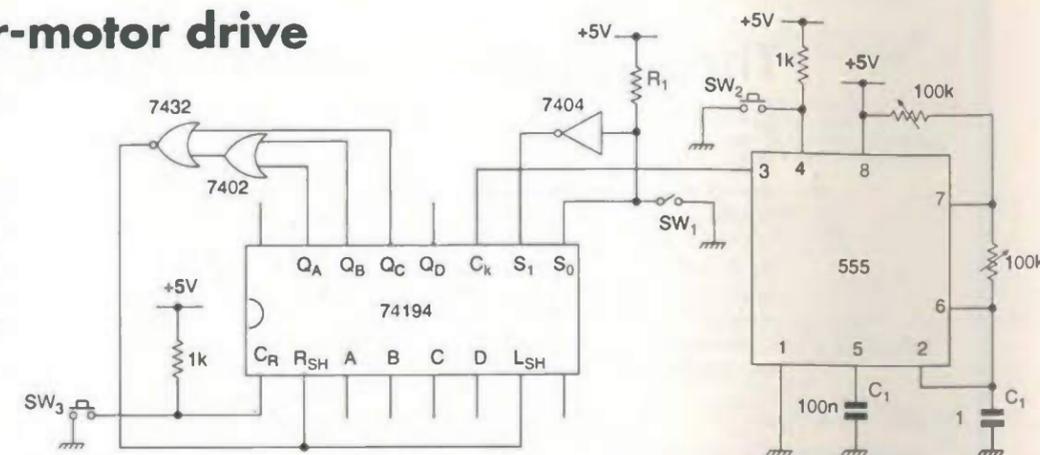


Fig. 1. Stepper motor controller using a shift register.

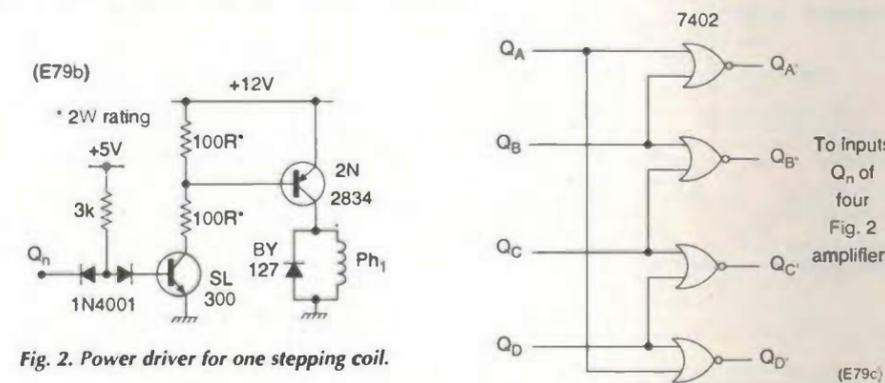


Fig. 2. Power driver for one stepping coil.

Table. Wave drive sequences without the modification in Fig. 3, and two-phase drive, as obtained with the modification.

Wave drive sequence				Two-phase drive sequence			
Q _A	Q _B	Q _C	Q _D	Q _{A'}	Q _{B'}	Q _{C'}	Q _{D'}
1	0	0	0	1	1	0	0
0	1	0	0	0	1	1	0
0	0	1	0	0	0	1	1
0	0	0	1	1	0	0	1

A microcurrent amplifying stage


A common-source amplifying stage using a single field-effect transistor can ensure enormously large voltage gain, if the field-effect transistor's drain current is very small. An example circuit is shown here.

PSPICE simulation of the circuit has shown that the voltage gain factor of the amplifying stage is equal to 5500. But that is not the limit. Replacing resistors R₄ and R₃ by 10MΩ types makes the voltage gain factor equal to 17000. The maximum

possible value of the voltage gain factor depends on the drain-source and drain-gate leakage currents of the field effect transistor and can be very large.

A similar arrangement was used in the days of valves, with a pentode used in the 'starvation' mode. In both cases, the large gain is bought at the expense of limited bandwidth.

S Chekcheyev
Tiraspol
Moldova F6

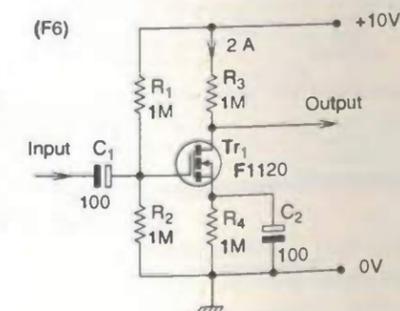

Three-phase sequence indicator

Phase rotation or phase sequence is an important parameter of a three-phase supply, as the direction of rotation of induction motors will depend on it. In some cases, serious damage to machinery may result if the driving motor is reversed. In such cases, local protection against phase reversal is essential.

The circuit given here is probably the simplest and the lowest cost

solution possible for providing an indication of the direction of phase rotation. It is readily adapted to provide an interlock, to prevent operation with the wrong phase sequence.

The circuit makes use of the fact that in a three-phase system, the voltage vectors of two phase terminals with respect to the third phase have a phase difference of 60°. Whichever voltage leads the other is an indication of phase sequence.

If the phase A leads phase B, the transistor Tr_1 receives base current first and LED_2 will light when phase B becomes positive. At that time Tr_1 will not receive base current since Tr_2 is conducting, and therefore LED_1


will remain switched off even when the phase B becomes positive later.

Should the phase sequence be reversed, Tr_1 receives base current first and only LED_1 will light in the same manner. Therefore LED_1 and LED_2 will indicate clockwise and anti-clockwise phase rotations of the supply respectively.

If one of the LEDs is replaced with an opto-coupler, a signal can be obtained at a potential close to the ground level. This may be used to interlock the motor starting switch gear so that motor will not operate in the reverse direction.

C Palihawadana
Dehiwala
Sri Lanka

F9

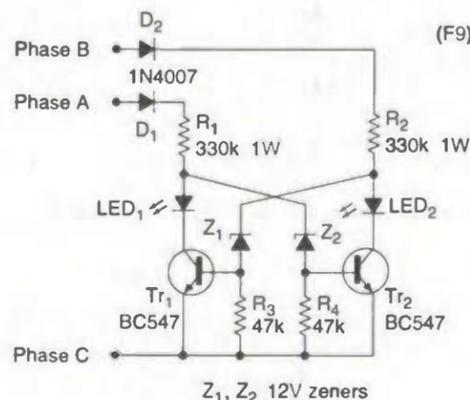

Important note

- All the components of the circuit will be live at near phase voltage, so the circuit is potentially lethal.
- The circuit can be used on supplies up to 400V phase-to-phase voltage.

Keyboard has serial interface

This circuit is based on the UCN5833 IC, which is a 32-bit serial-input latched driver with 32 open-collector outputs. Control pins are clock, serial data in, serial data out and strobe, i.e. output enable.

The keyboard is controlled by a microprocessor or microcontroller using three output pins and two input

pins. The software should implement the following steps.

At power on, the software should disable the output enable line and zero all 32 shift registers stages by clocking in zeros until the serial data out line reads zero continuously.

Now the serial data in line is taken high for one clock, and this is then


circulated through the shift registers on subsequent clock pulses. When the circulating high bit reaches any pressed key latch, the open-collector transistor of the latch conducts and the controller is informed of the key closure by the opto-coupler output 'key sense' signal.

This information is stored along with the clock pulse count - which is reset every 32 counts. The same key is then repeatedly sensed for key release when corresponding clock period is reached. Once the key release is detected, the program can jump to the appropriate action routine.

Note that the clock frequency should be chosen to ensure that there are several samples of any key pressed. Precautions should be included to deal with two key roll-over; a detected second key-press being ignored until the first key release is sensed.

Jayant Kathe
Mumbai
India

F2

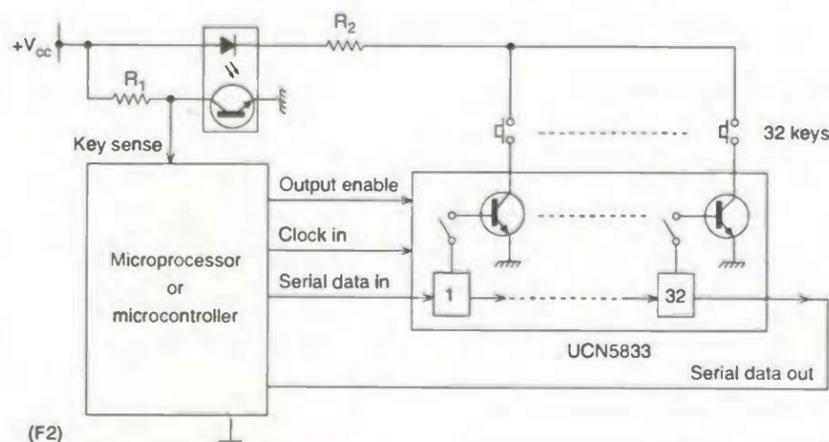

SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK

Ring for Latest Reduced Prices on this advert

HP8444A Tracking Generator • 5-1300Mc/s - £450.
HP8444A OPT 059 Tracking Gen • 5-1500Mc/s - £650.
HP35601A Spectrum Anz Interface - £300.
HP4953A Protocol Anz - 3400.
HP8970A Noise Figure Meter + 346B Noise Head - £3k.
HP8755A+B+C Scalar Network Anz PI - £250 + MF 180C - Heads 11664 Extra - £150 each.
HP3709B Constellation ANZ £1,000.
FARNELL TVS70MKII PU 0.70V 10 amps - £150.
MARCONI 6500 Network Scalar Anz - £500. Heads available to 40GHz many types in stock.
Mixers are available for ANZs to 60GHz.
Racal/TF2374 Zero Loss Probe - £200.
Racal/Dana 1250-1261 Universal Switch Controller + 200Mc/s Pi Cards and other types.
Racal/Dana 9303 True RMS Levelmeter + Head - £450.
TEKA6902A also A6902B Isolator - £300-£400.
TEK CT-5 High Current Transformer Probe - £250.
HP Frequency comb generator type 8406 - £400.
HP Sweep Oscillators type 8650 A+B + plug-ins from 20Mc/s to 18GHz also 18-40GHz.
HP Network Analyser type 8407A + 8412A + 8601A - 100Kc/s - 110Mc/s - £500 - £1000.
HP 8410 A-B-C Network Analyser 110Mc/s to 12 GHz or 18 GHz - plus most other units and displays used in this list up to - 8411A-8412-8413-8414 8418-8740-8741-8742-8743-8744-8650. From £1k.
Racal/Dana 9301A-9302 RF millivoltmeter - 10-20GHz - only in stock £250-£400.
Racal/Dana Modulation Meter Type 6009-6008-6007-6006 - 1.5GHz - £150/£250 - 9000A-9000B - £250.
Marconi Microwave 6600 100W test set, mainframe with 6650F - 18-26.5 GHz or 6650PI - 26.5-10GHz-£750 or only £600 MF only £250.
Gould J38 test oscillator manual - £150.
Baird Strobil Variable Inter EF3 0.1Hz-100Kc/s - £100.
• Many other makes in stock.

Anritsu MN958 Variable Att. 1300 £100.
Photo Dyne 1950 XR Continuous Att. 1300 - 1500 £100.
Photo Dyne 1800 FA Att £100.
Cossor-Raytheon 108L Optical Cable Fault Locator 0-1000M 0-10kM £200.
TEK P6701 Optical Converter 700 MC/S 850 £250.
TEK OF150 Fibre Optic TDR - £750.
HP81512A Head 150MC/S 950-1700 £250.
HP84801A Fibre Power Sensor 600-1200 £250.
HP81588 ATT OPT 002+011 1300-1550 £300.
HP81519A RX DC 400MC/S 550-950 £250.
STC OFR10 Reflectometer - £250.
STC OFSK15 Machine jointing + eye magnifier - £250.

MARCONI 2370 SPECTRUM ANALYZERS - HIGH QUALITY - DIGITAL STORAGE - 30Hz-110MHz - large qty to clear as received from Gov - all sockets in this complete or add £100 for basic testing and adjustment - callers preferred - pick your own from the next page - discount on qty's of five.
A EARLY MODEL GREY - horizontal alloy cooling fins - £200.
B LATE MODEL GREY - vertical alloy cooling fins - £300.
C LATE MODEL BROWN - as above (few only) - £500.

MISCELLANEOUS ITEMS
HP 4261 LCR meter - £650.
HP 4274 FX LCR meter - £700.
HP 3488 Switch Control Unit - £500.
HP 75000 VXI Bus Computers - £1300 DVM quantity.
HP 83220A GSM S/W PC 1990/1990MC/S - £100 for use with 832A - £200.
HP 1630 1001 1050 Logic ANZ's in stock - £100.
HP 8754A Network ANZ Hz 4-2000MC/S - 8502A + Cables - £200.
HP 8754A Network ANZ Hz 4-2000MC/S - 8502A + Cables - £200.
HP 8754A Network ANZ Hz 4-2000MC/S - 8502A + Cables - £200.
HP 8754A Network ANZ Hz 4-2000MC/S - 8502A + Cables - £200.
HP 8754A Network ANZ Hz 4-2000MC/S - 8502A + Cables - £200.

OSCILLOSCOPES
TEK 465-465B 100MC/S + 2 probes - £250-£300.
TEK 466 100MC/S storage + 2 probes - £200.
TEK 475-475A 200MC/S 250MC/S + 2 probes - £300-£350.
TEK 2213-2213A-2215-2216-2217-2218-2219-2220-2221-2222-2223-2226-2245-60-61-62-63-64-65-66-67-68-69-70-71-72-73-74-75-76-77-78-79-80-81-82-83-84-85-86-87-88-89-90-91-92-93-94-95-96-97-98-99-100-101-102-103-104-105-106-107-108-109-110-111-112-113-114-115-116-117-118-119-120-121-122-123-124-125-126-127-128-129-130-131-132-133-134-135-136-137-138-139-140-141-142-143-144-145-146-147-148-149-150-151-152-153-154-155-156-157-158-159-160-161-162-163-164-165-166-167-168-169-170-171-172-173-174-175-176-177-178-179-180-181-182-183-184-185-186-187-188-189-190-191-192-193-194-195-196-197-198-199-200-201-202-203-204-205-206-207-208-209-210-211-212-213-214-215-216-217-218-219-220-221-222-223-224-225-226-227-228-229-230-231-232-233-234-235-236-237-238-239-240-241-242-243-244-245-246-247-248-249-250-251-252-253-254-255-256-257-258-259-260-261-262-263-264-265-266-267-268-269-270-271-272-273-274-275-276-277-278-279-280-281-282-283-284-285-286-287-288-289-290-291-292-293-294-295-296-297-298-299-300-301-302-303-304-305-306-307-308-309-310-311-312-313-314-315-316-317-318-319-320-321-322-323-324-325-326-327-328-329-330-331-332-333-334-335-336-337-338-339-340-341-342-343-344-345-346-347-348-349-350-351-352-353-354-355-356-357-358-359-360-361-362-363-364-365-366-367-368-369-370-371-372-373-374-375-376-377-378-379-380-381-382-383-384-385-386-387-388-389-390-391-392-393-394-395-396-397-398-399-400-401-402-403-404-405-406-407-408-409-410-411-412-413-414-415-416-417-418-419-420-421-422-423-424-425-426-427-428-429-430-431-432-433-434-435-436-437-438-439-440-441-442-443-444-445-446-447-448-449-450-451-452-453-454-455-456-457-458-459-460-461-462-463-464-465-466-467-468-469-470-471-472-473-474-475-476-477-478-479-480-481-482-483-484-485-486-487-488-489-490-491-492-493-494-495-496-497-498-499-500-501-502-503-504-505-506-507-508-509-510-511-512-513-514-515-516-517-518-519-520-521-522-523-524-525-526-527-528-529-530-531-532-533-534-535-536-537-538-539-540-541-542-543-544-545-546-547-548-549-550-551-552-553-554-555-556-557-558-559-560-561-562-563-564-565-566-567-568-569-570-571-572-573-574-575-576-577-578-579-580-581-582-583-584-585-586-587-588-589-590-591-592-593-594-595-596-597-598-599-600-601-602-603-604-605-606-607-608-609-610-611-612-613-614-615-616-617-618-619-620-621-622-623-624-625-626-627-628-629-630-631-632-633-634-635-636-637-638-639-640-641-642-643-644-645-646-647-648-649-650-651-652-653-654-655-656-657-658-659-660-661-662-663-664-665-666-667-668-669-670-671-672-673-674-675-676-677-678-679-680-681-682-683-684-685-686-687-688-689-690-691-692-693-694-695-696-697-698-699-700-701-702-703-704-705-706-707-708-709-710-711-712-713-714-715-716-717-718-719-720-721-722-723-724-725-726-727-728-729-730-731-732-733-734-735-736-737-738-739-740-741-742-743-744-745-746-747-748-749-750-751-752-753-754-755-756-757-758-759-760-761-762-763-764-765-766-767-768-769-770-771-772-773-774-775-776-777-778-779-780-781-782-783-784-785-786-787-788-789-790-791-792-793-794-795-796-797-798-799-800-801-802-803-804-805-806-807-808-809-810-811-812-813-814-815-816-817-818-819-820-821-822-823-824-825-826-827-828-829-830-831-832-833-834-835-836-837-838-839-840-841-842-843-844-845-846-847-848-849-850-851-852-853-854-855-856-857-858-859-860-861-862-863-864-865-866-867-868-869-870-871-872-873-874-875-876-877-878-879-880-881-882-883-884-885-886-887-888-889-890-891-892-893-894-895-896-897-898-899-900-901-902-903-904-905-906-907-908-909-910-911-912-913-914-915-916-917-918-919-920-921-922-923-924-925-926-927-928-929-930-931-932-933-934-935-936-937-938-939-940-941-942-943-944-945-946-947-948-949-950-951-952-953-954-955-956-957-958-959-960-961-962-963-964-965-966-967-968-969-970-971-972-973-974-975-976-977-978-979-980-981-982-983-984-985-986-987-988-989-990-991-992-993-994-995-996-997-998-999-1000-1001-1002-1003-1004-1005-1006-1007-1008-1009-1010-1011-1012-1013-1014-1015-1016-1017-1018-1019-1020-1021-1022-1023-1024-1025-1026-1027-1028-1029-1030-1031-1032-1033-1034-1035-1036-1037-1038-1039-1040-1041-1042-1043-1044-1045-1046-1047-1048-1049-1050-1051-1052-1053-1054-1055-1056-1057-1058-1059-1060-1061-1062-1063-1064-1065-1066-1067-1068-1069-1070-1071-1072-1073-1074-1075-1076-1077-1078-1079-1080-1081-1082-1083-1084-1085-1086-1087-1088-1089-1090-1091-1092-1093-1094-1095-1096-1097-1098-1099-1100-1101-1102-1103-1104-1105-1106-1107-1108-1109-1110-1111-1112-1113-1114-1115-1116-1117-1118-1119-1120-1121-1122-1123-1124-1125-1126-1127-1128-1129-1130-1131-1132-1133-1134-1135-1136-1137-1138-1139-1140-1141-1142-1143-1144-1145-1146-1147-1148-1149-1150-1151-1152-1153-1154-1155-1156-1157-1158-1159-1160-1161-1162-1163-1164-1165-1166-1167-1168-1169-1170-1171-1172-1173-1174-1175-1176-1177-1178-1179-1180-1181-1182-1183-1184-1185-1186-1187-1188-1189-1190-1191-1192-1193-1194-1195-1196-1197-1198-1199-1200-1201-1202-1203-1204-1205-1206-1207-1208-1209-1210-1211-1212-1213-1214-1215-1216-1217-1218-1219-1220-1221-1222-1223-1224-1225-1226-1227-1228-1229-1230-1231-1232-1233-1234-1235-1236-1237-1238-1239-1240-1241-1242-1243-1244-1245-1246-1247-1248-1249-1250-1251-1252-1253-1254-1255-1256-1257-1258-1259-1260-1261-1262-1263-1264-1265-1266-1267-1268-1269-1270-1271-1272-1273-1274-1275-1276-1277-1278-1279-1280-1281-1282-1283-1284-1285-1286-1287-1288-1289-1290-1291-1292-1293-1294-1295-1296-1297-1298-1299-1300-1301-1302-1303-1304-1305-1306-1307-1308-1309-1310-1311-1312-1313-1314-1315-1316-1317-1318-1319-1320-1321-1322-1323-1324-1325-1326-1327-1328-1329-1330-1331-1332-1333-1334-1335-1336-1337-1338-1339-1340-1341-1342-1343-1344-1345-1346-1347-1348-1349-1350-1351-1352-1353-1354-1355-1356-1357-1358-1359-1360-1361-1362-1363-1364-1365-1366-1367-1368-1369-1370-1371-1372-1373-1374-1375-1376-1377-1378-1379-1380-1381-1382-1383-1384-1385-1386-1387-1388-1389-1390-1391-1392-1393-1394-1395-1396-1397-1398-1399-1400-1401-1402-1403-1404-1405-1406-1407-1408-1409-1410-1411-1412-1413-1414-1415-1416-1417-1418-1419-1420-1421-1422-1423-1424-1425-1426-1427-1428-1429-1430-1431-1432-1433-1434-1435-1436-1437-1438-1439-1440-1441-1442-1443-1444-1445-1446-1447-1448-1449-1450-1451-1452-1453-1454-1455-1456-1457-1458-1459-1460-1461-1462-1463-1464-1465-1466-1467-1468-1469-1470-1471-1472-1473-1474-1475-1476-1477-1478-1479-1480-1481-1482-1483-1484-1485-1486-1487-1488-1489-1490-1491-1492-1493-1494-1495-1496-1497-1498-1499-1500-1501-1502-1503-1504-1505-1506-1507-1508-1509-1510-1511-1512-1513-1514-1515-1516-1517-1518-1519-1520-1521-1522-1523-1524-1525-1526-1527-1528-1529-1530-1531-1532-1533-1534-1535-1536-1537-1538-1539-1540-1541-1542-1543-1544-1545-1546-1547-1548-1549-1550-1551-1552-1553-1554-1555-1556-1557-1558-1559-1560-1561-1562-1563-1564-1565-1566-1567-1568-1569-1570-1571-1572-1573-1574-1575-1576-1577-1578-1579-1580-1581-1582-1583-1584-1585-1586-1587-1588-1589-1590-1591-1592-1593-1594-1595-1596-1597-1598-1599-1600-1601-1602-1603-1604-1605-1606-1607-1608-1609-1610-1611-1612-1613-1614-1615-1616-1617-1618-1619-1620-1621-1622-1623-1624-1625-1626-1627-1628-1629-1630-1631-1632-1633-1634-1635-1636-1637-1638-1639-1640-1641-1642-1643-1644-1645-1646-1647-1648-1649-1650-1651-1652-1653-1654-1655-1656-1657-1658-1659-1660-1661-1662-1663-1664-1665-1666-1667-1668-1669-1670-1671-1672-1673-1674-1675-1676-1677-1678-1679-1680-1681-1682-1683-1684-1685-1686-1687-1688-1689-1690-1691-1692-1693-1694-1695-1696-1697-1698-1699-1700-1701-1702-1703-1704-1705-1706-1707-1708-1709-1710-1711-1712-1713-1714-1715-1716-1717-1718-1719-1720-1721-1722-1723-1724-1725-1726-1727-1728-1729-1730-1731-1732-1733-1734-1735-1736-1737-1738-1739-1740-1741-1742-1743-1744-1745-1746-1747-1748-1749-1750-1751-1752-1753-1754-1755-1756-1757-1758-1759-1760-1761-1762-1763-1764-1765-1766-1767-1768-1769-1770-1771-1772-1773-1774-1775-1776-1777-1778-1779-1780-1781-1782-1783-1784-1785-1786-1787-1788-1789-1790-1791-1792-1793-1794-1795-1796-1797-1798-1799-1800-1801-1802-1803-1804-1805-1806-1807-1808-1809-1810-1811-1812-1813-1814-1815-1816-1817-1818-1819-1820-1821-1822-1823-1824-1825-1826-1827-1828-1829-1830-1831-1832-1833-1834-1835-1836-1837-1838-1839-1840-1841-1842-1843-1844-1845-1846-1847-1848-1849-1850-1851-1852-1853-1854-1855-1856-1857-1858-1859-1860-1861-1862-1863-1864-1865-1866-1867-1868-1869-1870-1871-1872-1873-1874-1875-1876-1877-1878-1879-1880-1881-1882-1883-1884-1885-1886-1887-1888-1889-1890-1891-1892-1893-1894-1895-1896-1897-1898-1899-1900-1901-1

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture & full details

FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are **BRAND NEW** or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95 (B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95 (B)
- 5 1/4" Teac FD-55FR 1.2 Meg (for IBM pcs) RFE £18.95 (B)
- 5 1/4" Teac FD-55F 0.3 U 720K 40B0 (for BBC's etc) RFE £29.95 (B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95 (B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £29.95 (B)
- Table top case with integral PSU for IBM 5 1/4" Floppy / HD £210.00 (E)
- 8" Shugart 800/801 8" SS refurbished & tested £210.00 (E)
- 8" Shugart 810 8" SS HH Brand New £195.00 (E)
- 8" Shugart 851 8" double sided refurbished & tested £260.00 (E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00 (E)
- 8" Mitsubishi M2896-63 02U DS slimline NEW £295.00 (E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00 (E)

HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) New £79.95
 - 2 1/2" TOSHIBA MK2101MAN 2.18 Gb laptop (19 mm H) New £89.50
 - 2 1/2" TOSHIBA MK4303MAT 4.3Gb laptop (8.2 mm H) New £105.00
 - 2 1/2" TOSHIBA MK6409MAV 3.1Gb laptop (12.7 mm H) New £190.00
 - 2 1/2" to 3 1/2" conversion kit for PCs, complete with connectors £14.95
 - 3 1/2" FUJI FK-309 26 20mb MFM I/F RFE £59.95
 - 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE £59.95
 - 3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE £69.00
 - 3 1/2" QUANTUM 40S Prodril ve 42mb SCSI I/F, New RFE £49.00
 - 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb £69.95
 - 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested £69.95
 - 5 1/4" HP 97548 85 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 8" NEC D2246 85 Mb SMD interface. New £199.00
 - 8" FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00
 - 8" FUJITSU M2392K 2 Gb SMD I/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (C1)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3445ETKL 14" Industrial spec SVGA monitors £245
- FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
- FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
- 1kW to 400 kW - 400 Hz 3 phase power sources - ex stock EPOA
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM 53F5501 Token Ring IC5 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360.11805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(2M) 64 i/o EPOA
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £6500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 03 10KHz-1 GHz RF signal generator, New £4995
- HP1650B Logic Analyser £3750
- HP3781A Pattern generator & HP3782A Error Detector EPOA
- HP621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP626A Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz four channel test set EPOA
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £7900
- HP A1, A0 8 pen HPGL high speed drum plotters - from £550
- HP DRAFTMASTER 1 B pen high speed plotter £750
- EG+G Brookdeal 95035C Precision lock in amp £1800
- View Eng. Mod 1200 computerised inspection system EPOA
- Sony DXC-3000A High quality CCD colour TV camera £995
- Kelthley 590 CV capacitor / voltage analyser EPOA
- ICR40 dual 40 channel video recorder system £3750
- Fisker 45KVA 3 ph On Line UPS - New batteries £9500
- Emerson AP130 2.5KVA industrial spec UPS £2100
- Manly Tally MT645 High speed line printer £2200
- Intel SBC 486/33SE Multibus 485 system, 8Mb Ram £345
- Siemens K4400 64Kb to 140Mb demux analyser £2950

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
10,000,000 Items EX STOCK
For MAJOR SAVINGS
CALL OR SEE OUR WEB SITE www.distel.co.uk

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with the 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PCs in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed. In EXCELLENT like used condition. Order as Tilt & Swivel Base £4.75 Only £119 (E) MITS-SVGA VGA cable for IBM PC included.

External cables for other types of computers available - CALL.
Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multi sync etc. Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed. Dimensions: W14" x H12 3/4" x 15 1/2" D. Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered. Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 kHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/4" x 12" x 11". Good used condition. Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive leak style case. Perfect for Schools, Shops, Discos, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)
We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock. Call or see our web site.

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

- OPT Rack 1 Complete with removable side panels. £345.00 (G)
- OPT Rack 2 Rack, Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 1/4" W)

Sold at LESS than a third of makers price !!
A superb buy at only £245.00 (G)
42U version of the above only £345 - CALL
12V BATTERY SCOOP - 60% off !!
A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12V DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each. Our Price £35 each (C) or 4 for £99 (E)

RELAYS - 200,000 FROM STOCK

Save ££££ by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££s

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power 1 A quality product featuring a fully cased COLOUR CCD camera at a give away price 1 Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web Cam's etc., etc. Web ref = LK33 ONLY £99.00 or 2 for £180.00 (E)

SOFTWARE SPECIALS

- NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
 - ENCARTA 95 - CDROM, Not the latest - but at this price 1 £7.95
 - DOS 5.0 on 3 1/2" disks with concise books c/w QBasic £14.95
 - Windows for Workgroups 3.11 + Dos 6.22 on 3.5" disks £55.00
 - Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
- shipping charges for software is code B

Letters to the editor

Letters to "Electronics World" Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS
e-mail jackie.lowe@rbi.co.uk using subject heading 'Letters'.

Input-filter distortion

I thank Graham Maynard (EW Jan. 2001) for taking the time to reply to my letter. Unfortunately, he has failed to explain the quantum of distortion claimed and his analysis of the cause is specious.

As all aspects must be addressed technically, competently, and rationally, please allow me to explain, and hopefully promote a more accurate understanding of the relevant issues.

To the best of my knowledge and understanding, linear distortion is measured in terms of amplitude, phase, and time, with the units used being decibels (or ratios of power, voltage, pressure, etc), degrees (or radians) and seconds.

I have yet to see explained how it might be expressed as a percentage like non-linear distortion, as Graham does. He gives me no formula or other clue as to how this might be done.

My understanding of linear fundamentals

appears not to be the same as Graham's. For audio it is pointless to consider the effects of a circuit at one frequency for the purpose of determining the extent of any linear distortion.

Graham is correct in that the filter "introduces a tiny delay", but he is incorrect in suggesting that it "increases sharply with frequency", certainly within the range of human hearing.

What in fact happens is that the filter introduces a pretty uniform 2.2µs delay over the entire audio band, with a maximum variation of less than 160ns. This is nearly identical to the effect that would be produced by sending the signal down a perfect transmission line with a transit time of 2.2µs. This would be inaudible since the same time delay is forced on all signal components.

I know of no reliable evidence that the effects above 20kHz are audible. I reject any and all claims not backed by properly conducted research.

This can be easily demonstrated with a

very simple PSPICE simulation.

- * LP RC circuit for Group Delay Measurement
- * rc_gd01.CIR
- *
Vin 1 0 AC 1 0
R1 1 2 10k
C1 0 2 220pF
.AC DEC 500 100Hz 1000kHz
.PROBE
.END

By running PROBE and plotting vg(2), you will get a plot of the group delay through the circuit. The delay at 100Hz is 2.2µs and the delay at 20kHz is just over 2.04µs.

Over the range of human hearing the variation is smaller. To put this in some perspective, if you moved your head back about two thirds of a millimetre you would get pretty much the same audible effect - virtually none. I don't think anyone is likely to think that was important.

When one considers common listening

Tracking down mains earth leakage

A while ago, I suffered from my regular tripping of my domestic mains earth-leakage detector.

The trips occurred about every month or two - but sometimes two or three times in a 24 hour period, and the problem could have been on any of eight lighting circuits or six ring mains. Almost invariably the breaker would hold in immediately after a trip, and frequently, nobody had been turning anything on or off in the house.

I concluded, therefore, that there was earth leakage current running all the time, but that random fluctuations were causing it to just reach the trip threshold. In order to measure this, initially I tried winding a few turns of wire round both line and neutral feeds to the fuse box, and connecting a multimeter on AC volts. Not sensitive enough.

After further head scratching, I remembered that I had an old line output transformer in my junk box. By demounting the clamp and re-assembling the core round the incoming mains, the EHT winding produced an output of about 45mV with the house fully powered up - which is enough to measure.

By turning off all the trips, the voltage

reduced to virtually zero, suggesting that I was now indeed measuring the residual current. Bringing the circuits back on one at a time, I found that each one added a few millivolts to the reading, but that one ring main added about 15mV.

First I unplugged all the earthed appliances, judging that a device with a two-core mains lead could not possibly leak to earth. Wrong. It turned out that a television was leaking out to its aerial lead - not much, measured at about 5mA - but we'd be better off without it..

Interestingly, I had noticed that trips seemed more common in wet weather, and I suspect this has something to do with the conductivity of the chimney on which the aerial is mounted...

But there remained the puzzle of why the earth current rose a little with each circuit.

Surely they couldn't all have faults on them? To find this out, I replaced the multimeter with an oscilloscope. To my horror, I found that the waveform coming out of the EHT winding looked like a field of long grass - not the sinewave I was expecting. A moment's thought then told me that any capacitance to earth would provide a low impedance path to any noise

on the incoming mains.

My first question, then, is whether or not this would contribute to RCCB trips?

Deciding that I was more interested in resistive - rather than reactive - leaks to earth, I now added a simple RC filter of 10k/330nF to allow me to see the 50Hz component. I was rewarded with a slightly rough sinewave.

Using the second channel on the 'scope to monitor the line, I could see that there was a phase lead. This confirmed my suspicion that it is capacitance between the line and earth that accounts for most of the current measured.

I should mention that my household is littered with kit with switch-mode PSUs - e.g computers, TVs - all of which no doubt have filter capacitors down to ground in an attempt to clean up the resulting mess.

So here is my next question. Is it true that mains cabling capacitance and filter capacitors at SMPS inputs will permit a certain amount of standing 'leakage'. By this I mean is the actual earth fault current required to trip the breaker is considerably less than the 30mA rating on the breaker?

Chris Miller
Via e-mail

DISTEL on the web !! - Over 16,000,000 Items from stock - www.distel.co.uk

DISPLAY
-ELECTRONICS-

ALL MAIL TO
Dept ww, 29/35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5.30

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On E8A Bus Route
N. Thornton Heath &
Selhurst Park SR Rail Stations

NEW DISTEL
Visit our web site
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (C1)=£12.50, (D)=£15.00, (E)=£18.00, (F)=£20.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged © Display Electronics 1999. E & O.E. 07/99.

CIRCLE NO. 124 ON REPLY CARD

environments, one sees how insignificant this is. Hardly anyone hears anything in a free acoustic field. Most of us spend our lives in an acoustic near field of some description. Those that spend all their listening time in anechoic chambers might be excepted.

This means that there are peaks and troughs across the audio band, and these will change with position. For example, my favourite chair has a moderately high back, which ends a few centimetres below my ears – even if I slump down. I notice that there are distinct – but not serious – changes in the spectral quality if I move my head forward or back by 3 to 5cm.

Clearly, to avoid any linear distortion in that chair – well, I'm assuming it is the chair's fault – I obviously need to have a frame fitted that rigidly fixes my head on one position relative to the speakers.

But this would do nothing to address other problems caused by opening or closing doors and windows, rearranging the furniture, or the presence of any friends I might have over to enjoy the music with me.

These effects are not caused by signal delays but by reflection and diffraction of the

sound by objects in the listening room. These all affect the sound field in one way or another. They would even do so in an anechoic chamber, unless their shapes and surfaces were treated.

I think if anyone does try switching Graham's filter in and out, and they do detect some audible difference, then it is likely to be a product of their imagination and not any physical or auditory effect. Double blind testing is about the only way I know of to avoid the bogeys of human bias and misconception whatever their sources.

Cyril Bateman's contribution on the matter (EW Jan. 2001), while informative, is irrelevant. Having spent some years working with banks of aging Plessey Ducon electrolytic capacitors, I am quite aware that real components are not ideal.

It was pretty clear from the context of Graham's letter that he was talking about linear distortion, to which Cyril's comments are not germane. But thanks for sharing it Cyril.

Phil Denniss
Sydney, NSW
Australia

Graham replies...

What a real shame it is that Mr Denniss did not follow my suggestion and try these values for himself, for they are audible on a system that is not already filtered. No amount of theorising or self opinionation can alter reality.

Mr Denniss' forthright 2.2µs group delay explanation shows that he firmly believes the filter cannot affect audio dynamics. Unfortunately, he has incorrectly assumed that an electrical RC filter behaves as if it is a propagational transmission line.

As I wrote, these filters do not distort LF, but they do reduce clarity by having a HF effect. This effect is initially asymmetrical and lasts for longer than the spot frequency 'group delay' period. This is especially so at frequencies where the phase-lag 'delay' is no longer insignificant.

The greater the RC phase lag, the greater the initial asymmetry and waveform distortion, which becomes severe on sharp leading edges. See the 20kHz simulation, Fig. 1, for clarification; at LF there is similar delay but minute and quite insignificant error.

Stranger than fiction...

In his article 'Dome myths exploded' in the February 2001 issue, John Watkinson said that the old air-cooled Volkswagen bus had a better drag coefficient than the Jaguar E type. Where did he get this information? I am not doubting him; I just would like to see published data.

Jose Senna
Via e-mail

John replies...

My figure for the drag coefficients of the E-type Jaguar and the VW bus came from tests done at MIRA. These were quoted in a set of books called 'Our Four Wheels'

published by Orbis in 1973.

The VW bus (Cd=0.42) was described for low drag and includes a number of features, based on Kamm's work, which was well ahead of its time.

The nose is curved and the front bumper acts as a spoiler. The underbody is flat and smooth. The air intakes for engine cooling are at the rear of each side, behind the windows. These scoop in the boundary



layer, leaving more energetic air to negotiate the change of cross section at the tailgate. This reduces turbulence.

The E-type (Cd=0.44) was designed to be pretty, which it is. But aerodynamically it was poor. The long pointed nose forced air under the car and there was no spoiler. The long tapered tail meant that flow separation occurred well forward at a variable point and the large surface area of the tail was

just producing profile drag. The contemporary Citroen DS19 had a Cd of 0.31.

Incidentally, the XJS which followed the E-type was wind tunnel tested and put all this right. There is a spoiler and a large smooth undertray at the front, and the famous 'flying buttresses' at the rear follow the path of the vortex structure leaving the roof and sides.

The sharp inner lip of the buttresses and the end of the rear roof produce a defined separation point and I wouldn't part with mine.

A VW concept van based on the old 1950s Ti split-screen van – dubbed the Microbus and hailed as the bus of the future.

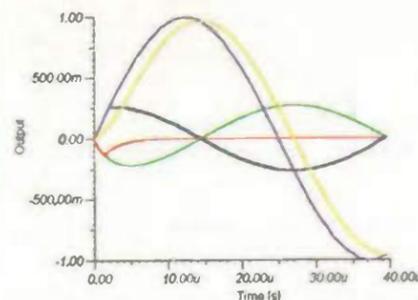


Fig. 1. 20kHz simulation highlighting RC phase lag.

The non-linear phase lagging AF error wave components that I wrote about can be much greater than people realise.

At the end of a delay line my input-output difference curve would be an error free negative maximum at 2.04µs. See the 43.5mV difference between too small a negative peak, when compared to the normal positive (group delay) peak, and this within a 40µs time frame – most significant when compared with the 1V, 50µs original – but then I never did want to 'fuss' this much as Mr Denniss has already accused me.

No filter. No real-life error. Thus I'll leave Mr Denniss to ponder what happens to leading edges of waveform transients when they pass through his delay line. We cannot have one examination for LF and another for more dynamic signals.

Incidentally, the filter proposed by Mr Ellis (it is not mine as Mr Denniss writes) limits slew in a 50W, 8Ω amplifier to 17V in 2.2µs. This is slow by today's standards, and I'm sure that Mr Denniss is as able as I am to understand the error that extends to 10µs, and the perceived lack of transmission line delay. He probably has already PSPICed this aspect in the normal course of his work, but not yet thought this far forward.

Also, I have checked both my letters and thus Mr Denniss must have misread me to misquote. It is he who has written 'delay' where I wrote of a "...phase shift' that increases sharply with frequency...".

He infers human bias and imagination where I have actually taken the trouble to check these filters in isolation for their additional input-n.f.b. impact on amplifier input circuitry. I have no reason to make false report about my real-life findings of the 1970s and 1990s, which computers are now able to examine.

He also intimates that I was talking about linear distortion. That was not clever.

Sprint timer

The 'Infra-red sprint timer' in the April issue is not new. In January 1985 I designed the STAR System – and acronym for 'Sprint Timer Analyser & Recorder' – for the Sports Institute of South Australia. It used a Tandy TRS80 Model 100, modified intruder-alarm beam break detector, a TRP-100 printer

plotter and a CCR-82 cassette recorder.

The system was used to plot a sprinter's startup, and 'finish' velocity and acceleration/deceleration. The implication is that sprinters – runners, skaters and cyclists – all slow down before they reach the finish line.

Manager of the Sports Institute Mike Nunan suspected this, but couldn't prove it until the timer became available. So the philosophy is now to train athletes to treat the finish line 100m ahead, so they don't slow down at a critical phase.

Accuracy of the system was about 100mm or 1/100 second. Printouts were: distance versus time, acceleration versus time, velocity versus time.

John Ingram
Australia
Via e-mail

Sub-bass challenged

I am afraid that Mr Maynard, with his Bass Boost circuit in *Electronics World's* February 2001 issue, has been labouring under a misapprehension.

To compensate for the natural fall-off in response of loudspeaker systems at low frequencies, we do not need phase advance as the frequency is reduced – the loudspeaker is already doing that! We need to compensate for what is actually happening.


The voltage to acoustic-pressure low-frequency equivalent circuit of a typical loudspeaker system will be similar to that shown in Fig. 1a). This is a two-pole filter whose resonant peak will be determined by the damping resistor R. Unfortunately, the vast majority of loudspeaker systems are far too under-damped – hence the familiar 'boom boom' sound.

What does 'engineer' mean?

The shortage of engineers in Britain is primarily due to the fact that the title, 'engineer' has no meaning in Britain, and also to the low salary levels offered to well qualified engineers. If you look at the number of engineering graduates who actually take up engineering careers, you will probably discover that it is less than 50%.

The shortage of engineers with a hands-on approach is primarily due to the decline in manufacturing, research and design, that has occurred in recent years in Britain. This decline has meant that these people have also taken jobs in more secure occupations.

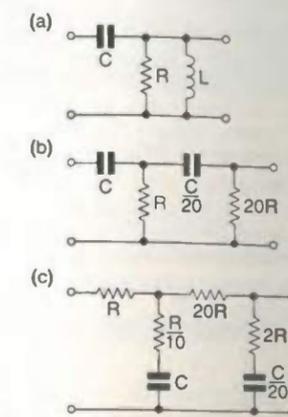The various training schemes, that have been introduced have done little to resolve this problem. For the most part they do not meet the needs of the electronics industry, as the course content is theoretical and



The equivalent circuit of a well-damped system, where the resonance effect can be discounted, will approximate to Fig. 1b). Resistor values are shown increasing in value to prevent the later stages appreciably loading up the earlier ones.

The transfer-function of the individual stages is of the form $ks/(1+ks)$, where $k=C/R$ and s can be replaced by $j\omega$ when you are looking at the sine wave response.

To give good transient response, a bass-boost system, must correctly compensate for this effect down to as low a frequency as is practicable.

Mathematically, you need to solve the equation $T.(ks/(1+ks))=1$, where T is the transfer function of the compensating network. Multiplying both sides of the equation by $1+ks$ gives $T.ks=1/(1+ks)$. Hence $T=(1+ks)/ks$. This simplifies to $T=1+1/ks$. This is unity gain added to the output of a perfect integrator.

An approximate integrator can be made from a RC network as shown in Fig. 1c). This will need amplification to restore unity high-frequency gain. This is the same circuit

often several years out of date.

The Society of Engineers, which is Britain's third oldest professional engineering body, realised this problem. It has restructured its examinations to meet the requirements of modern electrical and electronic engineering.

The design and project papers are completed by the candidate at home over a specified period of time. These provide the candidate with the opportunity to demonstrate that he or she has a practical approach to engineering as well as a theoretical knowledge. This means the candidate has often to research topics or regulations to ensure that the paper is completed successfully.

If any of you want to find out more about The Society of Engineers and its examinations, telephone 01206 263332 or e-mail secretary@society-of-engineers.org.uk.

David Purnell
via email

that Mr Maynard dismissed in referring to his Fig. 1.

In fact Mr Maynard's circuit will make the bass transient response worse, not improve it. The simple circuits, with a well-damped loudspeaker system, can do all the necessary compensation.

Readers would be far better advised to use simple bass-boost circuits and, if necessary, put some good acoustic damping material into their loudspeaker cabinets. Dare I suggest long-fibre wool?

Arthur R Bailey PhD MSc FIEE
Ilkley
West Yorkshire

Graham replies...

I thank Arthur Bailey for his letter in response to my sub-bass equaliser article. Mr Bailey has many decades of hands-on audio experience and I much respect his work, but my article approaches sub-bass reproduction from an historically unconventional starting point.

I too have done my work carefully, and thus I trust that he will understand differences which at first sight are not clear, for my equaliser does do exactly as he suggests. It compensates for what is actually happening; theoretically as well as practically.

'E-bass' is not a phase-altering bass boost system. It is a phase-linear and adjustable sub-bass equaliser that has been specifically designed for use with strongly constructed bass drivers. Because these drivers are driven

only at frequencies below their deliberately raised cabinet resonance, they transduce with much less phase error than when mounted in our conventional cabinets.

I agree with Mr Bailey that we do not want any phase advance with reducing frequency. Nor do we want even the changes that occur due to loudspeaker resonance. But cabinet damping alone cannot prevent these.

Long-fibre wool might reduce system 'Q' and the sharpness of the resonant phase change, but the phase change still occurs. In conventional cabinets the effects are always audible at sub-bass frequencies.

Dare I say that we have allowed ourselves to become used to it, because of the difficulties presented in overcoming the problem! Bass boost cannot help either, for it only adds to the overall phase distortion; it might improve some sounds at some frequencies, but it is deleterious to others.

Unfortunately, Mr Bailey has introduced theoretical representations that are not always properly understood. These place me in a position where I must respond.

I agree that his Fig. 1c) circuit will equalise his Fig. 1b) characteristics. I also agree that his Fig. 1a) is a fair representation; but where has the driver-cabinet combination gone in Fig. 1b)?

Applying $C=22\mu\text{F}$ and $R=150\Omega$ to Fig. 1b) leads to a -12dB roll-off below a -3dB turnover at 80Hz . But the real-life cabinet resonance that produces a peak and tightens the phase change about its frequency of occurrence is missing!

Yes, his Fig. 1b) does create a leading characteristic. In real life though, the compact sub-bass loudspeaker is electrically connected such that it runs properly in phase at sub-bass frequencies. It actually develops a lag only at frequencies close to the deliberately raised resonance, which is not driven.

Also, with a steep-cut electronic crossover – having phase changes of its own that can never be properly avoided, as with all crossovers – the amplifier is then able to directly exert a high degree of linear cone control all frequencies. This means that it will electrically dampen loudspeaker system induced, resonant frequency resultants where they have not been fundamentally energised. Such resultants are unavoidable within all loudspeakers.

Thus I have not been labouring under a misapprehension. I have actually tried my Fig. 1, which is Mr Bailey's Fig. 1c). In real-life it sounds atrocious when applied to a phase linear sub-bass reproducer.

I sought other 'ears' to confirm whether my own observations were correct. It took me ages to get my head around what was actually happening; also to get beyond conventional circuits.

My real-life findings appeared to conflict with what I had read through the decades. But I could not be so brash as to say 'if the theory does not fit, then change the theory'. My findings could not be disputed either. It was my own interpretation and application that had to be re-evaluated.

In common with other integrator circuits, Mr Bailey's Fig. 1c) network shifts the entire sub-bass spectrum into what is virtually a lagging quadrature. This would then re-mix with bass harmonics plus other mid and treble signals that have been simultaneously amplified.

There is a distracting 25ms delay at 20Hz. Overall reproduction literally falls apart because a resistively-operating sub-bass loudspeaker cannot be made to compensate by transducing electrical waveforms before they arrive.

I wrote that I used a dual-beam oscilloscope to observe and measure these time differences, and I worked away until they were minimised by a circuit that would not overdrive at infra-sound frequencies. My own hands-on work was completed without the aid of computers, but these were later used to confirm measurements and then to draw up the article.

My equaliser circuit offers an alternative possibility for level and flat-phased sub-bass reproduction. I implore that anyone who might feel a need to comment to please audition what is possible before putting pen to paper.

Just because I prefer compact sub-bass does not mean that I advise readers not to construct heavy and large conventional cabinets that leave drivers at risk of over excursion and introduce a ludicrous phase change at sub-bass frequencies. When it

Antennas and propagation for wireless communication systems

This will be a vital source of information on the basic concepts and specific applications of antennas and propagation to wireless systems, covering terrestrial and satellite radio systems in both mobile and fixed contexts. Antennas and propagation are the key factors influencing the robustness and quality of the wireless communication channel and this book includes:

- Illustrations of the significance and effect of the wireless propagation channel
- Overview of the fundamental electromagnetic principles underlying propagation and antennas
- Basic concepts of antennas and their application to specific wireless systems
- Propagation measurement, modelling and prediction for fixed links, macrocells, microcells, picocells and megacells

- Narrowband and wideband channel modelling and the effect of the channel on communication system performance
- Methods that overcome and transform channel impairments to enhance performance using diversity, adaptive antennas and equalisers

It will be essential reading for wireless communication engineers as well as for students at postgraduate or senior undergraduate levels.

Distinctive features of this book are:

- Examples of real world practical system problems of communication system design and operation
- Extensive worked examples
- End of chapter questions
- Topical and relevant information for and about the wireless communication industry

Post your completed order form to:
Jackie Lowe, Cumulus Business Media,
Anne Boleyn House, 9-13 Ewell Road,
Cheam, Surrey, SM3 8BZ

Fax your completed order form to
020 8643 8952
UK Price: £42.50 Europe £45.00 ROW £47.50
Price includes delivery

Sampling 'scope memories

Firstly, one issue without an article by Ian Hickman is bad enough, but two issues without is a disaster!

Secondly, in the the March 2000 issue, we were presented with a most interesting insight into sampling techniques – sufficient to divert my attention from trying to improve the performance of a TDA8703 a-to-d chip.

Not having such a well filled spares box I used a BFR93A with BAT83 diodes. Coupled with a PIC16F877 and a bit of programming this reproduced a 50MHz square wave quite well on the computer. Unfortunately it had to be driven from a low impedance as the suggested active probe (May 1996) using a MAX4005 converted square waves above some 20MHz to fairly good sine waves!

However, with the original article we were admonished to 'Watch this space...' Well I have but to no avail. Is it not about time that the recent gaps were filled with the promised follow up article?

John Kanaar
Via e-mail

Ian replies...

John, I am afraid that readers have been "watching this space" for far longer than I intended. The missing part of the design is the trigger and incremental delay processing, to reconstruct the sampled waveform.

I had in fact done quite a lot of work on this part of the design before developing and publishing the sampling circuitry. But for various reasons, it has languished on the back burner.

At the moment, apart from my many non-electronic activities, I have a new edition of one of my books to complete by late summer, but after that, I intend to return to and finish the sampling 'scope design.

ANTENNAS AND PROPAGATION FOR WIRELESS COMMUNICATION SYSTEMS

SIMON R. SAUNDERS

How to pay

Antennas and propagation for wireless communication systems

I enclose a cheque/bank draft for £ _____
(payable to Cumulus Business Media)

Please charge my credit/charge card
 Mastercard American Express Visa Diners Club

Credit Card No: _____ Expiry Date: _____

Signature of Cardholder _____

Cardholder's statement address: (please use capitals)

Name _____

Address _____

Post Code _____ Tel: _____

comes down to it, neither system is anywhere near perfect.

What I would suggest though is that you might try both, and then see which you would rather live with. It is possible that anyone then building up a new system might actually choose to use much smaller conventional stereo loudspeakers as head height satellites, and then take the overall system response down to the lower limit of human hearing by using compact 'e-bass' technology.

Graham Maynard
Newtownabbey
Northern Ireland

EMC and the DIY PC

Regarding John Woodgate's letter in the May 2001 edition of *Electronics World*, unless the requirements have changed in the past few years, he is incorrect to say that CE certification is required for an individually built PC.

While it is true that the European EMC Directive applies to all electronic equipment, whether 'placed on the market' or 'brought into service' (without being first placed on the market), the requirement for CE marking, and hence declaration and hence probable need for testing, only applies to products placed on the market. In other words your home built PC is required to meet the regulations but you are not required to demonstrate that it does.

In effect the Directive empowers the 'Powers that be' to do something if you are causing a problem – to require you to fix it at your own cost. Otherwise, it only requires you to not knowingly cause a problem.

John comments that he has had PC suppliers respond to his querying PC EMC performance by saying that 'all the parts were CE

marked'. It is important to understand that this is not a defensible position on behalf of the manufacturers. At the very least they must obtain the 'Declaration of Conformity' from the manufacturers of the component parts to ensure that the declaration which the CE marking represents actually covers the requirements that the PC manufacturers need to meet.

The classic example for this is the power supply module. Within the context of the European Directives this is treated as a component, not a product. As a component, it is exempt from the EMC Directive, but is covered by the Low Voltage Directive (think of this as the safety directive).

The power supply has to have CE marking affixed to show compliance with the safety requirements, but this says *nothing* about its EMC performance. The onus is on the PC manufacturer to place a commercial requirement on the power supply manufacturer that the power supply should be designed so that when the PC manufacturer affixes CE marking to the PC that the EMC requirements will be met.

Philip Williams BSc CEng
Harlow
Essex

In the May issue, Robert Atkinson rightly picked me up on a statement I had made concerning the EMC requirements for home-built pcs. I had said "...but there are no requirements for home built machines. (If a company builds a non-compliant computer it can be prosecuted, but an individual can buy the same parts, make the same machine, and not have a problem.)" Mr Atkinson was right in the sense that the passage was poorly worded and could easily be misinterpreted.

This is a very difficult area for all concerned. In the UK we first have the 51 page Statutory Instrument 1992: no 2372 "The Electromagnetic Compatibility Regulations". Then we have S.I. 1994: no 3080, the 8 page amendment to the regulations. These are the key legal enactments of the 89/336/EEC, the EMC directive. And then we have the official guidelines on the application of the directive. These run to 59 pages in Word format.

For those interested in the guidelines, they are available from several sites on the web. The DGIII site has a very long URL so you might prefer either www.eucs.com/news.htm or www.emc-journal.co.uk.

Now these guidelines are official, but not legally binding. This in itself is tricky. The bottom line is that regardless of the expertise of the person you consult on this matter, the only final arbiter is a court of law.

Bearing this *caveat* in mind, clause 6.4.1 of the guidelines allows an end user to construct a computer system from CE marked parts with no further testing, marking or declaration. This is intended to be for separately buying and plugging together a main box, a monitor, a printer, a scanner, etc. This is analogous to making up a hi-fi system from parts. However, a retailer selling this system as a complete unit is in a different position.

Now making the main computer unit from a mother board and plug-in cards is arguably stretching this clause somewhat.

Nevertheless it is done extensively. Another clause is also of interest to the home pc builder; clause 7.3. "Modifications carried out by the end-user (under his responsibility)" covers a multitude of sins. They are not covered by the EMC directive, but by "product liability and other pertinent legislation". My current pc, for example, was a store-bought 486DX-33 until 'upgraded' by

utterly dire – either failing to work properly, or restricting the programmer to a poor subset of features available on the various platforms. We ended up establishing our own abstraction of the Windows APL.

It is the experience of the time/effort devoted to this that makes me dread a return to a multi-platform marketplace.

On the other hand, were Linux to end up providing a Win 32 compatible API, this would give it a realistic chance to become main-stream because users and developers alike could then migrate without major disruption.

Perhaps the first step would be for the US authorities to force Microsoft to make Win32 an open standard? Such a development would also force a degree of stability which would do wonders for the reliability of application software.

John Jameson
Managing Director
Labcenter Electronics

John replies:

Daniel is quite correct in saying that multi-platform GUI/API solutions have been tried in the past. In the days when there was need to support MS-DOS, Windows and Mac OS we looked at various commercial solutions. Unfortunately, everything on offer was

holding down the shift key doesn't work. But otherwise it functions. Not bad for an eComStation beta and an Odin pre-alpha. Can't wait for the GA's.

A second purpose is to provide a common API that programmers can use to produce programs that run on Win32, OS/2 and Linux. Attempts at this sort of thing have been tried in the past, but there are a lot of volunteers working on this and several large companies cheering and throwing services their way.

Daniel Carroll
Principal Cyclotron Engineer
King Faisal Specialist Hospital &
Research Centre
Riyadh

About valve substitutes

In the May issue's letters column, Ranulph Poole asked if anyone knows about commercial solid-state valve substitutes.

In the Italian magazine *Sperimentare*, November 1977, page 1141, I found the following replacement suggestions for the BC-221 apparatus and others, to be made placing the semiconductors inside the empty base of an old tube.

"For the tube 77 use a 2N3085 JFET, source to pin 5 of the tube base, drain to the pin 2, gate to a lug (that I think that it is applied to the tube base, and is intended to replace the tube cap); other pins not connected.

Again for the tube 77, using a 3N128 MOSFET, source to pin 5 of the tube base, drain to the pin 2, gate to a lug, and screen/substrate to the pin 1; other pins not connected.

For the tube 76, use a JFET C610, source to the pin 4, gate to the pin 3, drain to the pin 2; others pin not connected.

For the tube 6A7 place a 2.2kΩ resistor to the pin 6, a 270pF capacitor to the lug, join together the free ends of the resistor and of the capacitor.

Place a first MPF107 JFET, source to the joint just made, gate to the pin 5, drain to the pin 4. Place a second JFET MPF107, source to the pin 6, gate to the lug, drain to the pin 2; others pin not connected."

However, I think that these are neither commercial replacements nor truly direct replacements, as the power supply will have to be reduced.

I think that 'direct' replacements for rectifier tubes have been made by International Rectifier, but I could not find any reference to them.

● **Battery pack short-circuit protector:** the circuit published on page 382 of the May 2001 issue does not seem to work correctly as it is drawn.

new motherboards, hard drives, ram, processors, etc., to a Pentium III. Only the monitor and the sound card are now original in fact! At least I had enough inside knowledge to buy a new case with decent EMI protection.

However, what about poor Joe Public? (S)he is not required to produce a certificate of competence to build a pc, and yet can buy all the bits to do so. The only unambiguous point is that if you make a pc for someone else, regardless of whether you get paid for it or not, you are definitely technically committing an offence if it is not CE marked as a system. If you make one for yourself, that seems relatively ok, provided you never sell it or give it away – without first CE marking it.

The idea of making Joe Public guilty of the crime of not CE marking his own equipment seems untenable. He can of course be

The current of the main cell pack is flowing through the 3.6V Li-ion battery. The "Cellpack V_{cc}" connection should go to the left terminal of R_{sense}, that is, to the negative pole of the Li-ion battery.

Ezio Rizzo
Italy

High-voltage amplifier

With reference to Arni Ingvarsson's letter in the May issue describing his high-voltage transistor power amplifier to drive electrostatic speakers, why use transistors?

If you want to run a 5kV HT line then surely a valve output stage would be a more appropriate choice? After all, the Quad 22 valve amplifier was designed to drive the complex load presented by electrostatic speakers without the threat of instant failure posed by those expensive three-legged fuses.

With a 5kV HT supply and a push-pull output stage you could dispense with the output transformer and use AF chokes for anode loads, the speaker feed being taken directly from the anodes. However, I must admit I don't like the idea of external speaker wiring carrying five thousand volts!

Quad amplifiers had the usual low impedance output intended to drive either conventional speakers or the Quad ES units. With the electrostatic speakers, the low signal voltage from the amplifier was stepped up to the required level by a transformer in the ES speaker unit.

Regarding Ranulph Poole's letter in the same issue, I remember plug-in solid-state replacements being available for the valved video output stages in early seventies Pye colour TVs. The video output PCB was densely populated with components including hot running power resistors.

The heat from those together with the four closely spaced valves fitted on the panel gently toasted the Paxolin until it

was sufficiently charred to allow heavy leakage currents to flow.

It was not unknown for the solder securing the valve holders to the print to melt. The only option was to replace the complete panel.

The solid-state replacement modules were supposed to be cooler running, and used a high-voltage FET. The module was built on a B9A plug and intended to be quite literally a plug-in replacement.

Unfortunately they weren't very reliable; although it must be borne in mind that high-voltage semiconductor technology was in its infancy – well, OK, its adolescence – at the time. Not only that, the dissipation of the power transistor was the same as the anode dissipation of the valve it replaced. The only saving was in heater power, which in the application under discussion made only a minor contribution to the problem.

When I was in my teens back in the sixties, I used to play around with what were even then old valve radios. When the 6V6 failed in my bedroom set I simply plugged in one of its cousins – a 6L6. The 6V6 shares an identical pin-out with the 6L6 and 6F6.

While the 6V6 and 6F6 are pentodes the 6L6 is a beam tetrode, indeed the famous 807 transmitter PA bottle is basically a 6L6 with a top-cap.

Substituting one of the alternatives for a dead 6V6 should be done with care, as the heater currents are somewhat higher. The cathode bias resistor's value also needs to be changed. Heater current and grid bias voltages, for 250V on the anode, are as follows: 6V6, 0.45A, -12.5V; 6L6, 0.9A, -4V; 6F6, 0.7A, -16.5V.

It's even possible to fit an EL34, but the heater current is a hefty 1.6A and as well as changing the cathode resistor value, pin 1 (g3) must be connected to the cathode.

Pete Roberts
Via e-mail

viewed as a black art. Ian is quite right when he identifies that we need to focus attention on the too often neglected electrical properties of the circuit interconnections. I would commend readers to develop the type of thinking that Ian recommends and I, for one, will seek to learn from his evident experience in the field.

However I want to take issue with him over his view of the equipotential plane and particularly his assertion that there is a voltage drop along the ground plane equal to that in the signal conductor. It is the correct approach to consider the action of the ground plane by imagining an image of the conductor, but this actually leads to the opposite conclusion.

The image conductor is to be imagined to exist the same distance from the ground-plane surface, but on the opposite side of it.

Get in Linux

Regarding John Jameson's letter in the April issue, I certainly can commiserate, being in the midst of a programming project myself. But there is an alternative that may please his programmers – though his customer service department may wince.

There are two related projects, Wine on Linux and Odin on OS/2, that are API redirectors/replacements. These allow Win32 programs to run on their respective host systems.

While they are definitely works in progress, they already allow many Windows 95/98/2000/ME/NT programs to run.

I have Mr Jameson's Proteus electronics design system running on a preview version of eComStation – the upcoming version of OS/2 – with a daily build of Odin. Is it perfect? No. I have to manually refresh sometimes as repainting still has bugs, and panning by moving the mouse while

At every point on the image conductor a potential exactly opposite to that on its real counterpart and a current equal in magnitude and flowing on the opposite direction is visualised. If you now consider the electric field that exists between this image conductor and the real conductor, it will be at a potential of zero midway between the conductors throughout their length. This confirms that there is not potential difference across the ground plane.

Indeed it is actually the need to fulfil the requirement that there be no potential across the ground plane that leads to the develop-

ment of the image representation. It is also incorrect to assign the image inductance and resistance values to the current flowing in the ground plane. They do have to be assigned to the image conductor, but only along with assigning an image voltage source and load resistance hence maintaining the resultant current flow in the real conductor to the same as it would be if there were a true short circuit between the ground plane end of the load impedance and the ground plane end of the source.

Ian is correct in saying that the return current flowing in the ground plane is

restricted to an area immediately beneath the conductor – at high frequency only. This would suggest some inductance associated with this flow, but not equal to that of the forward conductor. It may well be that Ian has experienced voltage drops between points designated as ground. If so this represents an inadequacy of the ground plane and in these circumstances the image representation would break down.

A particularly important property of the ground plane is that it should be continuous under the forward conductor's path. Any break in the ground plane continuity will force the return current to take a path other than directly under the forward conductor this can greatly increase the area enclosed by the forward and reverse currents and hence compromise the EMC performance.

At first I was surprised to read Ian's recommendation that the situation with a conductor over a ground-plane be improved by connecting a ground return wire in parallel with the ground plane. In my mind's eye I visualised a conductor running, say, 4in (200mm) over a ground plane with source and load connected. I then envisage laying a conductor from ground plane end of the load across the surface of the ground plane to the ground plane end of the source. I am pretty sure that a negligible current would flow in this wire. It would be easy enough to check this with a suitable set up including an rf current probe if someone wanted to try it.

It then occurred to me that Ian probably intended that the return conductor be run immediately adjacent to the original conductor and not along the ground plane. The effect of this is indeed interesting. This second conductor now forms a short circuited secondary of a transformer of which the original conductor is the primary. As a result a current will be induced in this conductor opposite to that in the original conductor hence generating an opposing radiated field and reducing emissions (and by reciprocity improving immunity).

The effect will be limited by the effectiveness of the coupling between the two conductors. If perfect there would now be no current flowing in the ground plane at all. Indeed the effectiveness would be improved by disconnecting the ground plane at the load (or source) end and so forcing all the return current through the second conductor. A further improvement can then be achieved by twisting the conductors together.

Could I appeal to Ian to consider writing a further article – or the editor to reference an existing article if such exists – dealing with the importance of the areas being enclosed by the loops formed by forward and reverse connections from source to load? Visualising these can be of great help in understanding what reduces emissions and improves immunity.

Philip Williams BSc CEng.
Harlow
Essex
Via e-mail

E-series anomalies

Referring to the letter on E series resistors in the March issue, I do not understand how Mr Gundry calculated the errors in the E12 series. I think that the best method to clarify things is to reproduce the calculations here.

The first column shows the theoretical values using the 12th root of 10, rounded to 2 decimal places. In the second column is results from the 1st column rounded to 2 digits. The third column contains the E12 series. Numbers in bold type are the ones that differ.

10	10	10	
		-0.95%	
12.12	12	12	3.17%
14.68	15	15	
		-0.95%	
17.78	18	18	0.88%
21.54	22	22	-2.45%
		1.3%	
26.10	26	27	1.588%
		-0.88%	
31.62	32	33	-1.98%
		-2.45%	
38.31	38	39	-0.083%
		-0.528%	
46.42	46	47	0.48%
		-1.65%	
56.23	56	56	0.228%
68.13	68	68	0.748%
		-0.47%	
82.54	83	82	-0.55%
		0.66%	

The percentages in between are the ratio errors between neighbours compared with the 12th root of 10. As you can see, there is no advantage in the E12 series compared with the mathematically built series. On the contrary, the choice was unfortunate because it avoids easy computing of

Fig. 1. Program for determining the E48 value nearest to a given number using an HP48 or similar.

$$/ '10^{(1/48)} @ x y 'y^{IP(LN(x*\sqrt{y})/LN(y))' EVAL -3 RND TM$$

resistor values in some programs.

The E24 series has the same problem, as it was made compatible with E12. Series E48 and E96 were built from scratch and are mathematically correct.

As an example, a very useful program that runs on an HP48 or similar is shown as Fig. 1. It transforms any number to the nearest value of the E48 series. For E96 change "48" to "96".

Francisc Casanellas Chartered Engineer, MIEE, Senior MIEEE
Barcelona
Spain

With reference to the discussion in your journal about E-series resistors, I first made the acquaintance of this series of values about 54 years ago. They were manufactured by Erie and supplied in long flat green boxes in 1/2 and 1 watt ratings and were made of carbon.

I have always understood that the E designation originated because the resistors were made and supplied by (E)rie and that those particular ohmic values were arrived at by the constraints imposed by the post-war period.

I believe that although a full range was desirable, it was not practicable. An excellent compromise was derived by some genius at Erie and marketed accordingly.

As an aside, I have in my possession a tattered and fragile copy of P. H. Brans' Radio Valve *Vade Mecum* dated 1946. Amongst many other things, it gives details of some German valves that contained, within the one glass envelope, three valves coupled internally by capacitors (anode to grid) and decoupled by built in resistors (grid to cathode).

Can these be considered to be the first attempt at integrated circuits? As well as having a manufacturers designation they were called Wunderlich valves.

Jim McDermott

Via e-mail

Self on Audio

Douglas Self

The cream of 20 years of Electronics World articles (focusing on recent material)

A unique collection of design insights and projects - essential for all audio designers, amateur and professional alike.

Scientific electronics based on empirical data

Douglas Self has been writing for Electronics World and Wireless World over the past 20 years, offering cutting-edge insights into scientific methods of electronics design.

This book is a collection of the essential Electronics World articles, covering twenty years of amplifier technology but with a very strong bias towards more recent material. The articles include self-build projects as well as design ideas and guidance for the professional audio designer. The result is a unique collection of design insights and projects - essential for all audio designers, whether amateur or professional.

Contents: Introduction; PRE-AMPLIFIERS: An advanced preamplifier MRPI; High-performance preamp MRP4; Precision preamp MRP10; Moving-coil head amp; Preamp '96 I; Preamp '96 II; "Overload Matters" (RIAA overload); Balanced line inputs and outputs, part 1; Balanced line inputs and outputs, part 2; POWER AMPLIFIERS: FETs less linear than BJTs; Distortion in power amplifiers 1-8; Distortion residuals; Trimodal part 1, 2; Load-invariant power amp INVAR.DOC; Common-emitter amps; Two-stage amplifiers; SPEAKERS: Excess speaker currents; Class distinction (amp classification); Relay control; Power partition diagrams; Audio power analysis.



Self
on
Audio
DOUGLAS SELF

Douglas Self has dedicated himself to demystifying amplifier design and establishing empirical design techniques based on electronic design principles and experimental data. His rigorous and thoroughly practical approach has established him as a leading authority on amplifier design.

Readership: Audio electronics enthusiasts;
Professional amplifier designers;
Power amp users
Paperback
Pages: 416pp

UK Price: £26.50 Europe £27.50 ROW £28.50

Return to Jackie Lowe, Cumulus Business Media
Anne Boleyn House, 9-13 Ewell Road, Cheam,
Surrey, SM3 8BZ

Please supply the following title:

SELF ON AUDIO

Name	Total _____
Address	
Telephone	Postcode _____
Method of payment (please circle)	
Mastercard/Visa/Cheque/PO	
Cheques should be made payable to Cumulus Business Media	
Credit card no _____	
Card expiry date	
Signed	

WEB DIRECTIONS


ACQUIVISION

<http://www.acquision.com>

AcquiVision solutions, including XY-Plotting, Oscilloscopes (with FFT), Data Logging and Custom Software, have been getting the most from computers since 1994. Download software, Telephone (01903)830502.

AQUILA VISION

<http://www.aquila-vision.co.uk>

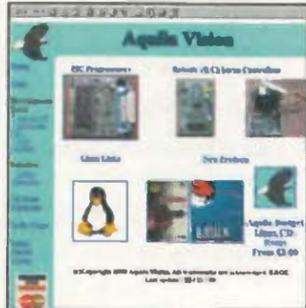

Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general interest CD-ROM's.

ALCATEL COMPONENTS

<http://www.components@alcatel.de>

ASHWELL ELECTRONICS

<http://www.ashwell-hq.com>

Ashwell provide technical support for Apex Microtechnology op-amps and DC/DC'S; Aeroflex; EMP filtered connectors; M S Kennedy; Mintech obsolescence; NSC Mil/Aero; Teledyne Relays and isocom mil/optocouplers.

ARCOM

<http://www.arcomcontrols.com/ew/>



A leading international supplier of communication and control technology to industry, Arcom provides leading edge solutions through a comprehensive range of market leading products.

A.R.S.

<http://www.ars-surplus-stock.com>

We buy electronic, electrical, computer and test equipment. Visit our website or e-mail us at info@ars-surplus-stock.com Telephone us on 01271 867285

BROADERCASTING COMMUNICATIONS SYSTEMS

www.broadercasting.co.uk

WINRADIO now brings you a complete choice in personnel computer controlled radio scanning and reception solutions ● Broadcast ● Media ● Monitoring ● Professional Amateur Radio communications

BEDFORD OPTO TECHNOLOGY LTD

<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and custom, LED bargraphs, circuit board indicators, stand offs, transmissive/reflective switches, baseafe optocouplers tubular and surface mount, panel mount LED assemblies.

CONCEPT ELECTRONICS

<http://www.conceptkey.co.uk>

Concept Keyboards are specialists in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

CONTROL SOLUTIONS

www.controlsolutions.co.uk

Data acquisition and control for beginners, hobbyists, and professionals. Perform mathematical and logical operations on data in real time. Email: info@controlsolutions.co.uk.

COOKE INTERNATIONAL

<http://www.cooke-int.com>
e-mail: info@cooke-int.com



Stockists of Quality Used Electronic Test Instruments and Operating & Service Manuals.

CROWNHILL ASSOCIATES LTD

<http://www.crownhill.co.uk>

Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart



Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.

DANIEL MCBREARTY

<http://www.danmcb.demon.co.uk/k/eng.html>

Experienced engineer based in London, specialist in audio and control systems. Available for design, project engineering or general consultancy. Background of high-quality work.

DESIGNER SYSTEMS CO.

<http://www.designersystems.co.uk>

Electronic product design company with over a decade of experience promoting



it's own product range and designing and manufacturing innovative products for client companies/individuals.

ECM SELECTION

<http://www.ecmsel.co.uk>

For the pick of the UK's Top High-Tech



Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager - £22,000 - £70,000

EDWIN PCB DESIGN SOFTWARE

<http://www.swifteurotech.co.uk>

Swift Eurotech supply the best-selling EDWIN CAD/CAE system for PCB design, including schematics, simulation and PCB design. Discounts up to 60% for non-commercial users.

ELECTRONICS AND COMPUTING PRINCIPLES

<http://www.eptsoft.com>

Studying electronics or computing or just want to keep up-to-date in an easy and enjoyable way, then this fully interactive software is for you.

EQUINOX TECHNOLOGIES UK LTD

<http://www.equinox-tech.com>



Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

FARADAY TECHNOLOGY LTD

<http://www.faradaytech.co.uk>



Over 17 years experience in the design and manufacture of high quality passive filters and delay lines. Used in Broadcast, Telecommunications, Medical, Multimedia, and computer industries. Currently exporting worldwide

FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

FLASH DESIGNS LTD


<http://www.flash.co.uk>

Flash supply low cost AVR ISP programmers (£39), MINI-ICE starter kits (from £69), Portable Easy-ICE emulators (from £199), ICE Adapters & 'C' compilers for any ATME AVR, MCS51, Dallas, Hitachi H8 microcontroller. Download FLASH NEWS now. Watch out for Special Offers! ARE YOU developing code in a Flash?

GOOT PRODUCTS

<http://www.kieagoot.co.uk>

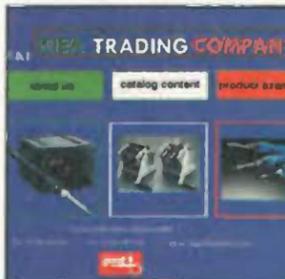Kiea Trading Company is the sole agent of



To reserve your web site space contact Pat Bunce

Tel: 020 8652 8339 Fax: 020 8652 3981

Goot products, We specialise in supplying the soldering and desoldering product range manufactured by Goot Japan for the UK market. Goot uses advanced production technology to manufacture high quality soldering iron products for industrial, professional and general purpose use.

HSPS LTD

<http://dSPACE.dial.pipex.com/hsp/>

FILTER DESIGNER - Advanced analog and digital filter design software for the PC. - Standard and Professional versions. - Free download of Evaluation version.

HTB ELEKTRONIK

<http://www.htb-elektronik.com>

We are selling second-hand test & measurement equipment and accessories for over 10 years, from all leading manufacturers.

LEVY/LATHAM GLOBAL

<http://www.levylatham.com>

U.S. Military Surplus meters, plug-ins, test sets, oscilloscopes, power supplies, signal generators, spectrum analyzers and radio components from Tektronix, Hewlett Packard, Sony, Phillips and more!

LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

MATRIX MULTIMEDIA LTD

www.matrixmultimedia.co.uk
Matrix Multimedia publishes a number of highly interactive CD ROMs for learning



electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

NEWNES - BOOKS FOR THE ELECTRONICS WORLD

<http://www.newnespress.com>
Over 300 books and information packages



for those working with electronics and engineering technology. Visit our site for a free catalogue and downloads.

NORCALL

<http://www.norcall.co.uk>

Suppliers and repairers of MOBILE RADIO equipment SALES HIRE REPAIR Huge stocks of used radios and spares Pye Philips Simoco Icom Kenwood Standard Clearstone Maxon Yaesu Key Midland. WE CAN PROGRAM ANYTHING 24hr Service

OMEGA RESEARCH LTD

<http://www.omega-research.co.uk>

"SMD prototyping adapters. Unique, flexible, low cost adapters to allow bench working with SM devices. Range suits most devices down to 0.5mm pitch."

PCA:PHILIP COLLINS & ASSOCIATES PTY. LTD

<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transmitters from any tone phone.

POLY-FLEX CIRCUITS LTD

<http://www.polyflex.com>

Design, manufacture and population of printed polyester flexible circuits, including Flip Chip on Flex providing practical, low cost, reliable solutions for today's small lightweight products.

QUASAR ELECTRONICS

www.quasarelectronics.com



Over 250 electronic kits, projects and ready built units for hobby, educational & industrial applications. TEL: 01279 306504, FAX: 07092 203496 or EMAIL: ewsales@quasarelectronics.com

QUILLER ELECTRONICS

<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

RADIOMETRIX

<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use.

RADIO-TECH LIMITED

<http://www.radio-tech.co.uk>

Radio modules, modems, telemetry, audio transmitters, pagers, antenna, remote controls and much more. All UK designed and manufactured.


RALFE ELECTRONICS



professional test & measurement www.ralfe-electronics.co.uk

RD RESEARCH

<http://www.looking.co.uk/spice>

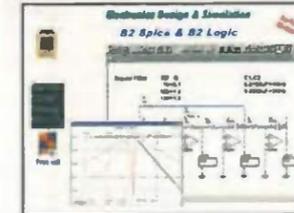

Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.

RS COMPONENTS LTD

<http://rswww.com>



The award winning on-line service from RS - 110,000+ products available - Technical data library - Stock availability check - Integrated on-line purchasing - Order by 8pm - with you tomorrow.

SOFTCOPY

<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.



SESCOM, INC.

<http://www.sescom.com>

SESCOM, INC. is a 30-year manufacturer of audio "problem solvers" and transformers. We also offer easily-fabricated aluminum enclosures for small production runs and prototypes.

STAFFORDSHIRE WIRELESS COMPANY

<http://www.staffs-wireless.com>

Wireless communication, test equipment, bought and sold for very competitive prices visit our web site or telephone John on 01889 569928 or 0973 296461.

SUPRA AUDIO CABLES

<http://www.jenving.se>

Jenving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.



TEMWELL CORPORATION

<http://www.temwell.com.tw>

Manufacturer & Exporter of Heical BPF Filter, 30 Watts BPF Power Filter and Handset/Base Station Duplexers

TEST EQUIPMENT SOLUTIONS

<http://www.TestEquipmentHQ.com>

Quality second user test equipment with full warranty and support. All types of equipment from all leading manufacturers including general purpose, communications and industrial test.



WEB DIRECTIONS

TELNET

<http://www.telnet.uk.com>

Top quality second-user Test and Measurement Equipment
eMail telnetkm@msn.com

THOSE ENGINEERS LTD

<http://www.spiceage.com>



Working evaluations of SpiceAge mixed-mode simulator, Spicycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

THERMOSPEED

<http://www.thermospeed.co.uk>



ThermoSpeed

Over 20 years of experience in the microwave design



Temperature and pressure, control and instrumentation. Full on-line purchasing.
* Overnight ex-stock delivery
* Create your own hotlist
* Download datasheets
* Full technical support

TOTAL ROBOTS

<http://www.totalrobots.co.uk>

Robot Kits and Control Technology products, including OOPic the first Object-Oriented Programmable Integrated Circuit. Secure on-line ordering and fast delivery.


TRIDENT MICROSYSTEMS LTD

<http://www.trident-uk.co.uk>

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

TOWER HILL TECHNICAL SERVICES

<http://www.towerhillaerials.com>

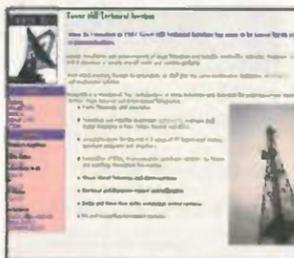

Everything you need for DIY Satellite & TV aerial installation. The one stop shop for TV, FM, Satellite, Amateur Radio PMR Aerials, Distribution Equipment, Cable & Accessories.

TECHNICAL AND SCIENTIFIC SUPPLIES

<http://www.technicalscientific.com>

Suppliers of pre-1985 equipment and components.
- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

VANN DRAPER ELECTRONICS LTD

<http://www.vanndraper.co.uk>

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>



VUTRAX electronic schematic and pcb design system for Windows 95, 98 and NT. Limited Capacity FREE version downloads available, all upgradeable to various customised levels.

WOOD & DOUGLAS

<http://www.woodanddouglas.co.uk>

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for International telemetry, data, voice & video wireless communications.

UK ELECTRICAL DIRECT

<http://www.uked.com>

For a comprehensive on-line directory, buyers guide and resource locator for the UK Electrical Industry look at this site. Many of the companies listed have links to their own web sites, making

this a one-stop shop for a huge amount of information.

UK MAILING LIST GROUP

http://www.egroups.com/list/uk_tvrepair

Following on from the newsgroup discussion last month there is a UK Email group for TV technicians where you can send an Email to everyone in the group. There's just over 30 people in the group at present. For more details and how to register look at the group home page. Just a general comment though - you do have to be careful who you give your Email address to so that you can avoid "spamming" - that is getting lots of unwanted Email about dubious Russian site (amongst others).

REED CONNECT

<http://www.reedconnect.net/>

Another free internet access site, this time from Reed Business Information. However the site possesses a useful UK People and Business Finder, with an e-mail search. There's also business news and local information, and some good links to directory sites.

REPAIRWORLD

<http://www.repairworld.com>

Repairworld is a sophisticated US based fault report database which is updated bi-weekly. It operates on a subscription basis and describes itself as an "affordable solution for all technicians". You can see some samples of the material for free, monitors, VCR, DVD and Camcorders being of particular relevance to UK users. The site also provides a "chat room".

Pat Bunce on
020 8652 8339
or fax on 020 8652 3981.
or e-mail:
pat.bunce@rbi.co.uk



Electronics World reader offer: x1, x10 switchable oscilloscope probes, only £21.74 a pair, fully inclusive*

*Additional pairs as part of the same order, only £19.24 each pair.

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____

Telephone _____

Method of payment (please circle)

Cheques should be made payable to

Cumulus Business Media

Access/Mastercard/Visa/Cheque/PO

Credit card no _____

Card expiry date _____

Signed _____

Please allow up to 28 days for delivery

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74
UK/Europe to Probe Offer, Jackie Lowe,
Cumulus Business Media, Anna Boleyn
House, 9-13 Ewell Road, Cheam,
Surrey, SM3 8BZ

Readers outside Europe, please add
£2.50 to your order.

Specifications

Switch position 1	
Bandwidth	DC to 10MHz
Input resistance	1MΩ - i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC
Switch position 2	
Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10MΩ ±1% if oscilloscope i/p is 1MΩ
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC

Switch position 'Ref'
Probe tip grounded via 9MΩ, scope i/p grounded

Put your web address in front of 21000 electronics enthusiasts and experts.

Electronics World acknowledges your company's need to promote its web site, which is why we are now dedicating pages in every issue to announce your WEB ADDRESS.

This gives other readers the opportunity to look up your company's name, to find your web address and to browse the magazine page to find new sites.

We understand that cost is an important factor, as web sites are an added drain on budgets. But we are sure you will agree that the following rates make all the difference:

FOR 12 ISSUES:

Lineage only will cost £150 for a full year just £12.50 per month.

This includes your company's name, web address and a 25-word description.

Lineage with colour screen shot costs £350 for

a full year, which equates to just £29.17 per month.

This price includes the above mentioned information, plus a 3cm screen shot of your site, which we can produce if required.

To take up this offer or for more information ring:

Pat Bunce on 020 8652 8339
or fax on 020 8652 3981.
or e-mail: pat.bunce@rbi.co.uk

Company name	Web address

Reader offer

10MHz single-trace oscilloscope for under £200

The Tecstar CS1010 oscilloscope is easy to operate and highly reliable. It is an ideal instrument for research, production, education and development work. This is a compact and portable oscilloscope with a frequency bandwidth of 10MHz and sensitivity of 5mV/div to 5V/div. It is equipped as standard with a switchable x10:1 probe, extending the sensitivity up to 50V/div. The horizontal timebase is 0.1s/div to 0.1µs/div.

- Simple operation
- Portable, small and lightweight
- Excellent Triggering



Features

- 10MHz bandwidth
- High brightness
- Calibration output
- Variable-Y attenuation
- AC DC and Ground
- Auto, Normal and TV triggering
- Variable trigger level
- +ve or -ve Ext trigger modes
- Internal, External or Line trigger
- Complete with x1/x10 probes
- Low cost

Vertical system

Sensitivity	5mV/div-5V/div±3%
Trimming ratio	2.5:1
Rise time	35ns
Bandwidth (-3B)	DC:0-10MHz AC:10Hz

Trigger system

Int trigger sensitivity	1 div
Ext trigger sensitivity	0.3V
Ext. trig. input impedance	1MΩ, 30pF
Ext. trig. max. input	400V pk
Trigger sources	Int, Line, Ext
Trigger mode	Norm, AUTO, TV

Horizontal system

Sweep time	0.1s/div-0.1ms/div, ±3%
Trimming ratio	≥2.5:1

X-Y mode

Sensitivity	0.2V/div-0.5V/div
Bandwidth (-3dB)	DC: 0-1MHz AC:10Hz-1MHz

Calibration signal

Waveform	Symmetric square wave
Amplitude	0.5V±2%
Frequency	1kHz±2%

CRT

Display area	8 x 10div (1div=6mm)
Accelerating voltage	1200V
Display colour	Green

Power source

Voltage range	220V ±10%
Frequency	50Hz ±2Hz
Power consumption	25W

Physical features

Weight	3kg
Dimensions (H x W x D)	190 x 130 x 270mm

Working environment

Working temperature	5°C to 40°C
Storage environment	-30°C to 60°C, 10-80%RH
Working altitude	2000m

Use this coupon to order your 10MHz CS1010 oscilloscope

Please send me 10MHz oscilloscopes at the special offer price of £193.88 each - including VAT and UK carriage*.

Name _____

Company (if any) _____

Address _____

Phone number/fax _____

Total amount £ _____ - _____

Make cheques payable to Tecstar Electronics Ltd

Or, please debit my Master/Visa card.

Card type (Master/Visa) _____

Card No _____

Expiry date _____

*£159.00 ex. VAT, £6 UK carriage, £14 overseas.

Please mail this coupon to EW offer, TECSTAR Electronics Ltd, Unit 1 Nuffield Road, St Ives, Huntingdon, Cambs. PE27 3LX, Tel 01480 399 499, Fax 01480 399 503. email: soles@tecstar.co.uk

As an advertiser you can be certain that your sales message is going to be read by decision-making electronics professionals with the power to purchase your products.

Service

Link

The pre-paid rate for semi-display setting is £17 per single column centimetre (maximum 4cm). Box number £22 extra. All prices plus 17½% VAT. All cheques, postal orders etc to be made payable to Reed Business Information. Advertisements together with remittance should be sent to Electronics World Classified, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8DZ. Tel: 020 8643 6207. Fax: 020 8770 2016

SERVICES

From **Concept** To **Production** **48 HOUR**

Electronic design and engineering services for the new millennium

- Embedded control
- Telecommunication products
- Data communication products
- SM PSU and battery management
- Wireless transmission systems
- Audio and Video processing
- DVD control systems
- Internet site and graphics authoring
- PCB design
- Schematic layout and re-drawing
- Technical documentation & translation

Tel/Fax: +44 (0) 1872 223306
Email: sales@designersystems.co.uk

see our web site @ <http://www.designersystems.co.uk>

Designer Systems

PRINTED CIRCUIT BOARDS
DESIGNED & MANUFACTURED

- Prototype or production quantities
- Fast turnaround available
- PCBs designed from circuit diagrams
- Almost all computer files accepted
- PCB assembly - mechanical assembly
- Full product design-manufacture-test-repair

agar TEL 028 9073 8897
Circuits FAX 028 9073 1802
agar@argonet.co.uk
Unit 5, East Belfast Enterprise Park
308 Albertbridge Rd, Belfast BT5 4GX

POWER SUPPLY DESIGN

Switched Mode PSU
Power Factor Correction
designed to your specification

Tel/Fax: 01243 842520
e-mail: eugen_kus@cix.co.uk
Lomond Electronic Services

FOR SALE

RF DESIGN SERVICES

All aspects of RF hardware development considered from concept to production.

WATERBEACH ELECTRONICS

www.rlaver.dial.pipex.com
TEL: 01223 862550
FAX: 01223 440853

WANTED

BEST CASH PRICES PAID

For all valves KT88
PX4 and other audio types
Wide range of valves and CRT stocked

Tel: 01403 784961
Minimum Order UK - £50+VAT+Freight

Billington Export Ltd. Fax: 01403 783519
Email: sales@bel-tubes.co.uk
Sussex RH14 9EZ
Visitors by appointment

Please mention Electronics World when replying to advertisements

ARTICLES WANTED

TOP PRICES PAID

For all your valves, tubes, semi conductors and ICs.

Langrex Supplies Limited
1 Mayo Road
Croydon, Surrey CR0 2QP
TEL: 020 8684 1166
FAX: 020 8684 3056

19" Rack Enclosures
New and Used most sizes
16U to 50U side and rear panels
mains distribution
19" Panel mounts
optima eurocraft
Prices from £45 + vat
M&B Radio
86 Bishopgate Street
Leeds LS1 4BB
Tel. 0113 2702114
Fax. 0113 2426881

Please note our new address:

Cumulus Business Media
Anne Boleyn House
9 - 13 Ewell Road
Cheam
Surrey
SM3 8DZ

Tel: 020 8643 6207

Fax: 020 8770 2016

Email:
P.bunce@cumulusmedia.co.uk

Research and Development Engineers

Audio Partnership PLC is one of the UK's largest Hi-Fi manufacturers with a portfolio of brands including Cambridge Audio, Synergy, Mordaunt-Short, Gale, Opus, TDL, Audio Innovations and Ariston Acoustics.

Due to continued expansion and an ambitious product development programme Audio Partnership is now expanding and re-fitting the R & D department which now occupies its own floor of our HQ building at London Bridge.

The successful candidates will join our current highly motivated team of 9 engineers and will gain a uniquely wide design experience working on products in the many areas of Audio Electronics that we are active in

We seek self-motivated individuals, preferably with previous design experience in audio or a similar discipline.

Hardware Engineer

Previous experience in audio electronics required. Knowledge of some or all of the following areas advantageous: filters, digital audio, video routing, amplifier design, digital amplifiers, PCB layout, awareness of EMC/LVD and approval procedures. Salary to £35,000.

Software Engineer

PIC programmer required with 2+ years experience of embedded control applications. Salary to £25,000

For further details please send a CV or contact us in confidence as below:

Matthew Bramble, Technical Director, Audio Partnership PLC, Gallery Court, Hankey Place, London SE1 4BB.

t: 0207 940 2200 f: 0207 940 2233 e: matthew@audiopartnership.com w: www.audiopartnership.com



Do you have a vacancy that you want to fill fast?

Then why not let Electronics World help you find that right candidate.

For further information on recruitment contact

Pat Bunce
Tel: 020 8643 6207

Email:
P.bunce@cumulusmedia.co.uk

Product Support Manager

Growing Midlands-based company in HEVAC industry is looking for a qualified and experienced Product Support Manager to take prototypes and develop them into live products.

Position will include considerable self-management, working to deadline and budget. This will involve visiting live site situations, as well as team working at head office.

Experience in Building Control Network systems advantageous, computer literacy essential.

All replies to:

Box 24
c/o Electronics World
Cumulus Business Media
Ann Boleyn House
9 - 13 Ewell Road
Cheam
Surrey SM3 8DZ

T & M EQUIPMENT




- AORET 740A signal generator 0.1-1120MHz £1000
- ANRITSU ME520B digital transmission analyser with MH370A jitter mod oscillator £4000
- ANRITSU ML93A optical power meter with MA96A power sensor £500
- IFR (MARCONI) 2610 true rms voltmeter £500
- IFR (MARCONI) 2955 mobile radio test set £1500
- IFR (MARCONI) 2022C 10kHz to 1GHz synthesized signal generator £1000
- NARDA 8305 broadband isotropic radiation monitor 0.3-18GHz £500
- RACAL DANA 1992 frequency counter 1.3GHz £500
- RACAL 6102 gsm test set £1000
- ROHDE AND SCHWARZ UAF video analyser £4000
- SCHAFFNER 200E/203A/222A line voltage simulator/interference simulator £1000
- SCHAFFNER 200E mainframe £500
- WANDEL AND GOLTJERMANN PF4 bit error rate tester (BN911.01) £1500
- Option 00.01 £500
- WAVETEK 1080 sweep generator 1-1000MHz £500
- WAVETEK 4106GPP handheld GSM mobile phone test set £500
- WILTRON 6640B sweep generator 26.5-40GHz £2500

ralfe electronics *exclusively* Professional T&M

- Unit 1 Olds Close
- Olds Approach
- Watford - Herts WD1 8RU - England
- TEL (+44) 01923-721396
- FAX (+44) 01923-721402
- EST 45 YRS

AGILENT TECHNOLOGIES

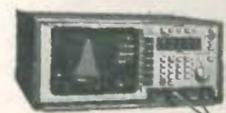

- 1145A active probe 2-channel (list 3725) £350
- 3336A level generator £1000
- 214E pulse generator £1500
- 10715A digital generator £1000
- 346A noise source £850
- 8904A synthesizer function generator £1000
- 8018A serial data generator £1000
- 8115A digital signal generator (order pods separately) £2500
- 83440C lightwave detector 20GHz 1300/1550nm £2000
- 85033D 3.5mm calibration kit 30kHz to 6GHz (list 2381) £1500
- 85032B N-type calibration kit (list 1578) £850
- 85033B 3.5mm verification kit £2000
- 85056D 2.4mm economy calibration kit (list E4904) £2500
- 85056K calibration kit (list 6381) £3500
- 85132F 7mm to 3.5mm flexible test port cable set (list E2682) £1750
- 85132F 2.4mm flexible test port cable set (list 4249) £2500
- 8594E 2.9GHz spectrum analyser options/D41/101/105 (list-E11k) £7500
- 8657A synthesized signal generator 0.1 - 1040MHz £2000
- 8657B synthesized signal generator 0.1 - 2080MHz £4000
- 8903B/10/51 audio analyser £2000
- 8903E audio analyser £1250
- 8922 E, F, G and H gsm test sets, each £1500
- E1413C a/d converter (VXI based) (list 4832) £1000
- E1415A algorithmic closed loop controller (VXI based) (list E5221) £2000
- E1610A VXI card 34Mbit/s line interface for BSTS £2500
- E1697A VXI card 155Mbit/s optical line interface £5000
- E5200A broadband service analyser, options £5000
- 02705/1/22/122/138/138/138/139 £5000
- J2171A ethernet interface module £1500
- J2215A FDDI multimode test set £1000
- J3911A multiprotocol token ring LAN probe £2000
- J3914A E1 WAN probe £2000
- J3921A E3 ATM probe £6500
- J3935A Telegra D analyser /201/202 options (list E13250) £6500
- J3972A 3c/STM-1 performance enhanced ATM probe £6500
- R85026A 26.5 - 40GHz waveguide detector £650

NEW INTO STOCK THIS MONTH, AGILENT UNITS

- 8714ES/100 3GHz network analyser. option 100 (fault location) (List over £18000) £13500
 - 8722ET network analyser 50MHz - 40GHz, with options 010 (time domain) and 1D5 (Hi-stab) (List-£57k). £45000.
 - 8653ES network analyser with 006 nad 010 (6GHz + time-domain options) (List £32k) £25000.
- All above supplied with new Agilent calibration and 1 year warranty.

All equipment sold calibration-checked by independent laboratories and carries un-conditional refund and 90-day guarantees.

TEST EQUIPMENT WANTED.
TOP PRICES PAID FOR PROFESSIONAL HIGH-END UNITS
AGILENT TECHNOLOGY SPECIALISTS.
FOR COMPLETE STOCK LISTING PLEASE CHECK OUR WEBSITE
www.ralfe-electronics.co.uk



ELECTRONIC UPDATE

Hioki's New 8807/8808 Memory Recorder

These compact, light recorders have 2 or 4 analogue channels with isolated inputs, PC card slot, fax/modem communication function, versatile trigger functions and 3-way power. They are ideal for a variety of applications requiring long memory lengths and high transient speed capability.

Telonic Instruments Ltd
Tel: 0118 978 6911
Fax: 0118 979 2388

CIRCLE NO. 125 ON REPLY CARD

DAQ Designer™ 2001

National Instruments new DAQ Designer™ 2001 is a FREE CD that helps engineers and scientists interactively configure custom measurement systems. DAQ Designer™ 2001 includes the capability to recommend real-time data acquisition and motion control hardware and software.

Phone: 01635 523545
Fax: 01635 524395
E-mail: info.uk@ni.com
Web: www.ni.com/uk

CIRCLE NO. 126 ON REPLY CARD

ELECTRONICS WORLD

UNBEATABLE OFFER - 50% off cover price for 12 issues!

Audio visual router
Impedance meter
Understanding transformers
EC residential banks
Hands-on DSP design
Fiber-optic I/O interface

Circuit ideas:
Low power class A audio amplifier
High speed PIC microcontroller
Spectrum analyser
Microcontroller
Supply regulator
Frequency divider

CIRCLE NO. 127 ON REPLY CARD

ELECTRONICS WORLD covers topics of most interest to the readers. Every section of the magazine is of interest and value to the Electronics Professionals who buy Electronics World every month. Your advertisement will appear in an environment which captures and holds the readers interest.

For further information call Pat Bunce
Tel 020 8643 6207
Fax 020 8770 2016
E-mail: P.bunce@cumulusmedia.co.uk

Low V _f Schottky Rectifiers		
CMSH1-20ML	1.0 Amp series	SMA
CMSH2-70L	2.0 Amp series	SMB
CMSH3-20L	3.0 Amp series	SMC
CSHD5-2M	5.0 Amp series	DPAK
CSHD10-45L	10 Amp series	
Low Leakage High Voltage Devices		
CMP03003	Single	
CMP03003A	Dual Common Anode	
CMP03003C	Dual Common Cathode	SOT-23
CMP03003S	Dual In Series	
Ultra Low Leakage Devices		
CMP08001	Single	
CMP08001A	Dual Common Anode	
CMP08001C	Dual Common Cathode	SOT-23
CMP08001S	Dual In Series	
CMD08001	Single	SOD-323
CMD08001	Single	SOD-323

EED ENERGY EFFICIENT DEVICE

Energy Efficient Devices (EEDS):
Central Semiconductor's new family of Energy Efficient Devices (EEDs) are designed to reduce the power requirements necessary for today's portable electronic products. With V_f as low as 0.35V, Central's Schottky Rectifiers are the perfect solution for battery powered hand-held applications such as PDAs, pagers, laptops and cell phones. In addition, the Low Leakage 200 Volt diodes and Ultra Low Leakage diodes provide design engineers with yet another tool for controlling size, power management, and battery conservation. Central Semiconductor is dedicated to complete customer satisfaction, perfect quality, on-time delivery, and reasonable prices. Visit our website at www.centraisem.com for current information on all devices manufactured by Central.

MB COMPONENTS
Tel: 01420 542500 Email: sales@mbcomponents.co.uk

Central Semiconductor Corp. THE FUTURE OF SMD

CIRCLE NO. 128 ON REPLY CARD




Cooke International

Second User ELECTRONIC TEST & MEASURING INSTRUMENTS
Operating & Service Technical Manuals



Tel: (+44) 0 1243 555590 Fax: (+44) 0 1243 551455
Unit 9, Ford Lane Business Park,
Ford, Arundel, West Sussex.
BN18 0UZ. (U.K)

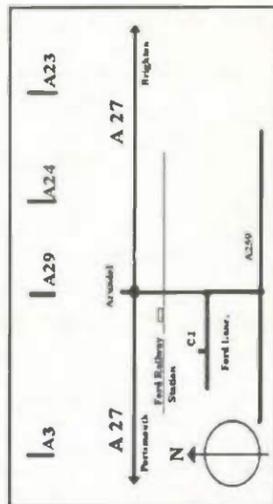E-Mail: info@cooke-int.com Web: http://www.cooke-int.com
All Our Equipment is Ex-Stock Ready for Next Day Worldwide Shipping.
Customers Welcome (Please call to make Arrangements)



CIRCLE NO. 129 ON REPLY CARD

ADVERTISERS' INDEX

ADEPT SCIENTIFIC.....526	LABCENTER ELECTRONICS.....497
BETA.....490	LANGREX.....533
CONFORD ELEC.....537	MILFORD INST.....521
COOKE INTERNATIONAL.....568	OLSON ELECTRONICS.....513
CRICKLEWOOD.....521	PICO.....503
CROWNHILL.....IBC	QUICKROUTE.....490
DISPLAY ELECTRONICS.....550	SIGHTMAGIC.....526
ENVIROWISE.....521	STEWART OF READING.....533
EPTSOFT.....OBC	SURREY ELECTRONICS.....533
INTEC ASSOCIATES.....490	TELNET.....IFC
JOHNS RADIO.....549	TEST EQUIP SOLUTIONS.....493
JPG ELECTRONICS.....537	TIE PIE.....531
KOMPASS.....537	WEB PAGES.....560, 561, 562

ELECTRONICS WORLD READER INFORMATION SERVICE

For more information about any of the products or services in this issue of **ELECTRONICS WORLD**, simply ring the relevant enquiry number. Enquiry numbers may be found at the bottom of each individual advertisement.

101	102	103	104	105	106	107	108	109	110	111
112	113	114	115	116	117	118	119	120	121	122
123	124	125	126	127	128	129	130	131	132	133
134	135	136	137	138	139	140	141	142	143	144
145	146	147	148	149	150					
						500	501	502	503	504
505	506	507	508	509	510	511	512	513	514	515
516	517	518	519	520	521	522	523	524	525	526
527	528	529	530	531	532	533	534	535	536	537
538	539	540	541	542	543	544	545	546	547	548
549	550	551	552	553	554	555	556	557	558	559
560	561	562	563	564	565	566	567	568	569	570
571	572	573	574	575	576	577	578	579	580	581
582	583	584	585	586	587	588	589	590	591	592
593	594	595	596	597	598	599	600			

Name _____
 Job title _____

 Company Address _____

 Telephone _____ JULY 2001

Only tick here if you do not wish to receive direct marketing promotions from other companies.

Newsagent order form

Pass this order form to your newsagent to ensure you don't miss the next issue of *EW*.

To
(name of Newsagent)

Please reserve me the August issue of *Electronics World* and continue to order every month's issue until further notice

Name.....
Address.....
.....
.....

Thank you

Subscribe today!

Guarantee your own personal copy each month

Save on a 2 year subscription

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD

Subscribe today!

Guarantee your own personal copy each month

Save on a 2 year subscription

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD

Postage will be paid by licensee

Do not affix postage stamps if posted in Gt. Britain, Channel Islands, N. Ireland or the Isle of Man

Business Reply Service
Licence No. CV711

ELECTRONICS WORLD
Reader Information Service
Reed Business Information
Oakfield House
Perrymount Road
Haywards Heath
Sussex RH16 3BR

211

SEE OVER!

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD

SUBSCRIPTION CARD

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ _____ made payable to Reed Business Information
Please charge my Mastercard/Visa/Amex account

With £ _____ Expiry Date _____

Signature _____

Name _____

Job Title _____

Address _____

Postcode _____

Tel: _____ Country _____

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
Airmail	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:
ELECTRONICS WORLD
P.O. Box 302
Haywards Heath,
West Sussex RH16 3DH UK.

CREDIT CARD HOTLINE
Tel: +44 01444 445566
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

ELECTRONICS WORLD
INCORPORATING WIRELESS WORLD

SUBSCRIPTION CARD

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ _____ made payable to Reed Business Information
Please charge my Mastercard/Visa/Amex account

With £ _____ Expiry Date _____

Signature _____

Name _____

Job Title _____

Address _____

Postcode _____

Tel: _____ Country _____

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
Airmail	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:
ELECTRONICS WORLD
P.O. Box 302
Haywards Heath,
West Sussex RH16 3DH UK.

CREDIT CARD HOTLINE
Tel: +44 01444 445566
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

SMART CARD SOLUTIONS

Crownhill Associates
smart electronic solutions

Visit our web site: www.crownhill.co.uk

ChipDrive Starter pack

ChipDrive Microh - serial port card terminal
Samples of Smart cards (6 cards)
Source code examples on CD ROM (VB3,4,5,6, Delphi & C)
Windows API Description, Windows DLL Documentation on CD ROM (PDF format)
Smart card data sheets (PDF format)

£69.95 +vat

SmartCard Programmers from £9.99 1off

29.95 +Vat

SIM Card Editor for Mobile Phones

This advanced editor allows the user to modify, copy and print data held on any GSM SIM card. No longer do you have to battle with complicated programming sequences on the numeric keypad of your mobile phone. Simply connect the SIM card READER

WRITER to your PC, install the easy to use software to:

- View and Print a detailed card profile
- Edit, Delete or Add phone book entries
- Edit, Delete or Add SMS messages
- PIN administration. Enable and Up-Date PIN1/2, unlock PIN's, Display the error counter for each PIN
- Archive SIM Card data to hard drive, copy Save and restore complete card data sets.
- Copy SIM card data from card to card
- Charge Control. set up charge counter limit, display current charge value, setup displayed price per unit.
- View and change preferred service providers

Includes:
SIM Card Reader Writer
Mini SIM Adapter
Software on CD-ROM
OnLine user Guide and Help
Requires Windows 95/98, NT, 2000 & Pentium Class PC


CIRCLE NO. 102 ON REPLY CARD

32, Broad Street, Ely
Cambridge, CB7 4AH

Tel: +44 (0) 1353 666709
Fax: +44 (0) 1353 666710

All prices exclude VAT postage and packing

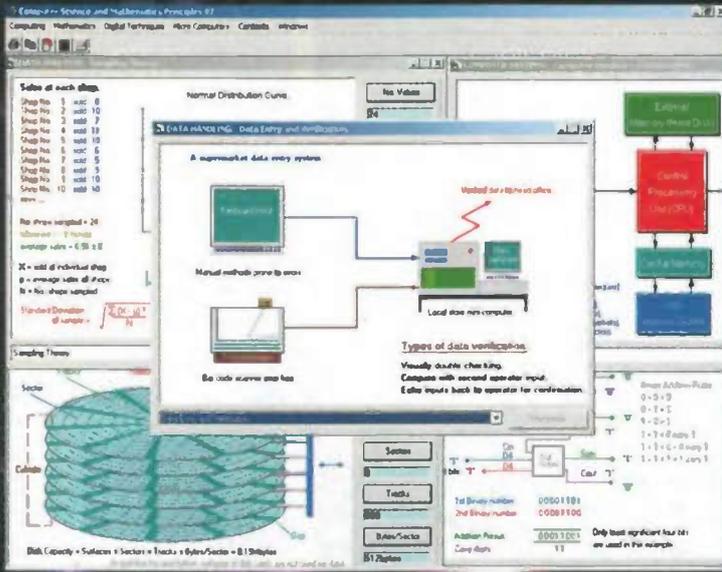'Computer Science & Mathematics Principles V7'



Computer Science:-

Hardware Devices, Data Structures, Data Files, Computer Systems, Data Handling, System Development, Computer Programming, Data Analysis, Binary Numbers, Binary Arithmetic.

Digital Techniques:-

Logic Gates, Flip Flops, Combinational Logic, Counters, Counting, Shift Registers, Boolean and DeMorgan's Theorems.

Microcomputers:-

Microprocessors, Basic Micro Computer, Busses, Memory Addressing, A.L.U. Clock and Reset, Instructions and Control, Memory R/W, Addressing, Instructions #1, Instructions #2, Instructions #3

Mathematics:-

Simple Numbers, Number Conversion, Number Types, Roots, Triangle Ratio's, Triangle Angles, Area, Surface Area & Symmetry, Volume, Percentages, Ratio's, Fractions, Vectors, Circles Angles, Laws, Algebra, Rules, Algebra. Rules, Powers, Simplifying, Equations, Graphing, Slope & Translation, Curves & Angle Conversion, Physical Science.

Personal user £59.95 +VAT

Education* £299.95 +VAT

(*Includes unlimited multi-user site licence.)

'Electronics and Computing Principles V7'

Electronics:-

Atomic Structures, DC Current flow, Basic Electronics, Simple DC Circuits, Types of Switching, Variable Voltages, Ohm's Law, DC Voltage, DC Current, Series/Parallel Resistors, AC Measurements, AC Voltage and Current, AC Theory, RCL Series/Parallel Circuits, Capacitance, Capacitors, Inductance, Inductors, Impedance, Communication System, Signals, Attenuators, Passive/Active Filters, Tuned Circuits, Coupling and Selectivity, Oscillators, Circuit Theorems. Diode Theory, Diode Applications, Transistor Theory, Bipolar Transistor, Transistor Configurations, Transistor Circuits, Field Effect Transistors, Operational Amplifier Theory and Applications, Sum and Difference Amplifiers.

Electrical:-

DC and AC Power, SCR, Power Supplies, Voltage Regulators, Magnetism, Motors/Generators, Transformers, Three Phase Systems.

Digital Techniques:-

Logic Gates, Flip Flops, Combinational Logic, Counters, Counting, Shift Registers, Logic Interfacing, Timers, Boolean Algebra and DeMorgan's Theorems.

Microprocessors and PIC Microcontrollers:-


Basic Micro-Computer, Busses, A.L.U. Clock and Reset, Instructions and Control, Memory Cells, ROM and RAM, Memory Addressing, Instructions, PIC Introduction, PIC16F84 Architecture, PIC16C71 A/D, Byte, Bit, Literal and Control Instructions.

Measurement and Component Testing:-

Analogue multi-meter, Measurement, Component Testing

Mathematics:-

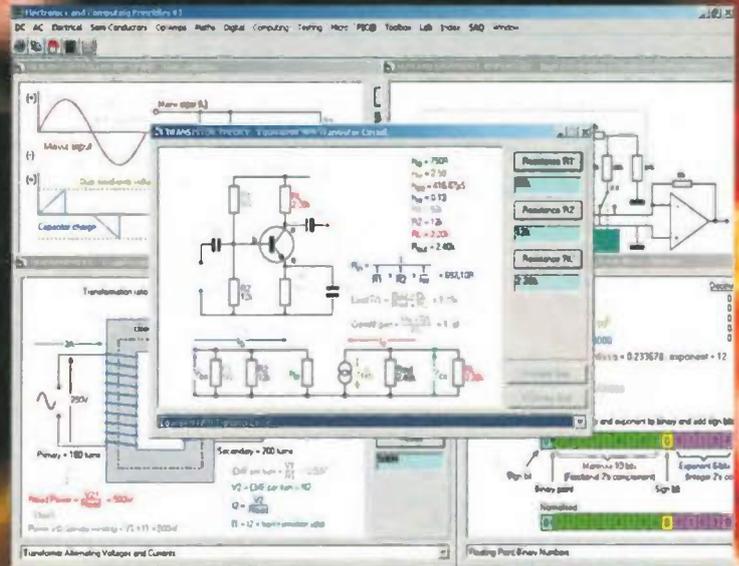Simple Numbers, Number Types, Roots, Triangle Ratio's, Triangle Angles, Area, Surface Area and Symmetry, Volume, Percentages, Ratio's, Fractions, Vectors, Circle Angles, Laws, Algebra Rules, Algebra, Powers, Simplifying, Equations, Graphing, Slope and Translation, Phase Angles, Complex Numbers, Statistics, Lottery Number Predictor, Physical Science.



Computing:-

Hardware Devices, Data Structures, Data Files, Binary Arithmetic, Binary Arithmetic.

Toolbox:-

DC Calculations, AC Calculations, Numbers, Applications

Self-Assessment Questions:-

DC, AC, Power, Semi-Conductors, Op-Amps, Digital, Mathematics.

Components and Equipment Picture Dictionary:-

High quality digital camera images and explanatory text.

Personal user £99.95 +VAT

Education* £299.95 +VAT (*Includes unlimited multi-user site licence.)

Truly interactive PC based courses on CD-ROM for Windows '95, '98, NT and 2000

Visit www.eptsoft.com or telephone for full details.

eptsoft limited, Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.

Tel: +44 (0)1376 514008. Fax: +44 (0)870 0509660. Email: Info@eptsoft.com. Switch, Delta, Visa and MasterCard accepted. No additional postage or airmail charges.