

**Competition winner:** receiving pulsed ultrasonics

# ELECTRONICS WORLD



SEPTEMBER 2001 £2.80

**Bar codes  
demystified**

**Code-hopping  
remote control**

**Opto audio link**

**Superhet  
techniques**

**Audio filter  
using DSP**

**Is Linux for  
you?**

**Circuit ideas:**

**Analogue interface for LPT**

**Stable go/no-go indicator**

**Audio opto isolator**

**Emergency light**

**PWM motor controller**





Now  
Supports the  
**MC68HC11**  
and  
**PIC16F877**

# PROTEUS VSM

Virtual System Modelling


Build It In Cyberspace

[www.labcenter.co.uk](http://www.labcenter.co.uk)

CIRCLE NO. 104 ON REPLY CARD

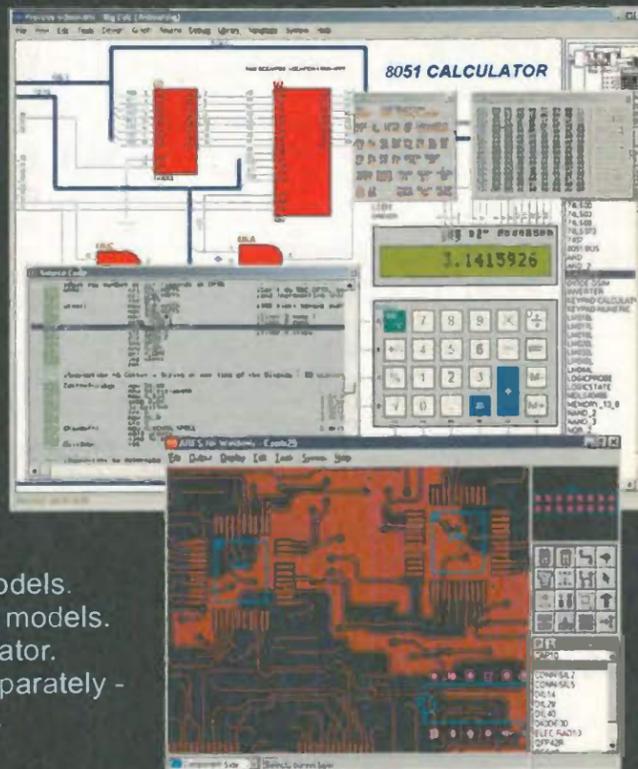**Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time.\***

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.



\*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium II.

Write, phone or fax for your free demo CD - or email [info@labcenter.co.uk](mailto:info@labcenter.co.uk).  
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

labcenter  
Electronics

EDITOR  
Martin Eccles

CONSULTANT  
Ian Hickman

EDITORIAL  
ADMINISTRATION  
Jackie Lowe  
020 8722 6054

EDITORIAL E-MAILS  
[J.lowe@cumulusmedia.co.uk](mailto:J.lowe@cumulusmedia.co.uk)

GROUP SALES  
EXECUTIVE  
Pat Bunce  
020 8722 6028

ADVERTISEMENT  
E-MAILS  
[p.bunce@cumulusmedia.co.uk](mailto:p.bunce@cumulusmedia.co.uk)

EDITORIAL FAX  
020 8643 8952

CLASSIFIED FAX  
020 8770 2016

NEWSTRADE ENQUIRIES  
020 7907 7777

ISSN 0959-8332

SUBSCRIPTION HOTLINE  
Tel (0) 1444 475662  
Fax (0) 1444 445447

SUBSCRIPTION QUERIES  
[rbp.subscriptions@rbi.co.uk](mailto:rbp.subscriptions@rbi.co.uk)  
Tel (0) 1444 445566  
Fax (0) 1444 445447

## It's official - work isn't fun any more

Staff are spending ever more 'working' time surfing Web pages that have nothing to do with work—and nearly half waste over three hours a week of their employers' time in this way.

But if you thought sex was the most popular subject that they 'research' in company time, you'd be utterly wrong. So what's the key attraction? Why, finding a better job!

That's the verdict of a recent survey by Vault.com, which found that nearly 40 per cent of personal Internet use at work was related to looking for a better position. It speaks volumes of course and points to the dissatisfaction that many employees feel today.

According to one survey, some 85 per cent of the American workforce is disenchanted with their job or career and figures are most likely similar in other industrialised countries.

In a recent *US News & World Report* survey, people were asked how happy they were with their lives. The three areas where people were overwhelmingly dissatisfied were jobs, finances, and leisure time. For most people finances are inextricably linked with a job, while discontentment with the job influences one's leisure time.

Many people feel underpaid and overworked, often finding themselves dwelling over work issues when they're supposed to be relaxing. So the source of most dissatisfaction is the job.

That's bad news because unhappy, stressed-out employees do not make productive workers. According to Linda Rosenstock, director of the National Institute of Occupational Safety and Health, people who are stressed at work cost companies more money, suffering more heart disease, increased injury risk and other kinds of medical problems.

The causes are all too familiar - heavy workload; long hours; no decision-making power; poor social environment; conflicting or uncertain job expectations; job insecurity; or lack of growth opportunities.

Specific reasons are not hard to find; a MORI poll conducted for telecoms vendor Mitel cites aggravation on the way to and from work as the most annoying aspect of the job (41 per cent of employees), closely followed by workplace politics (37 per cent) and constant interruptions (33 per cent).

No fewer than 42 per cent would seriously consider changing jobs to avoid these distractions. Over a quarter would accept a salary cut just to have the freedom of working in peace.

With so much evidence of dissatisfaction with workplace conditions, one might imagine that employers in the electronics, communications and

IT industries would take the problem seriously now.

Of course, this disharmony may be entirely intentional - part of the grand plan. That's because people reportedly work harder when they're feeling rotten.

Studies by psychologists from the University of Alberta reveal that cheerful folk waste time maintaining their happy moods, while their fed-up workmates just get on with the job.

Four groups of people were observed building circuit boards on a production line. While the cheerless characters worked no faster, they made half as many mistakes as their more jovial colleagues. Drawing on long-established distraction theories, the explanation is that disenchanted people lose themselves in work to take their minds off their miseries.

Working yourself to distraction is hardly the solution, though. Tom Welsh, the self-styled premier authority on new solutions for career satisfaction and owner of the delightfully named website [www.workhappy.com](http://www.workhappy.com), declares that unfulfilled workers are probably in the wrong profession, pursuing unsuitable careers that make their lives miserable.

Working longer hours is not the answer either. Already 44 per cent of Americans call themselves workaholics, well over 100 million, working an average of 47 hours a week. Within Europe it's British workers who work the longest hours.

In the electronics industry the problem is particularly subtle and deep. One report tells of a software engineer who was "too busy" to drive some distance to Workaholics Anonymous meetings for help with his addiction. In desperation he set up an Internet chapter of the organisation and now airs his grievances on line with the other workaholics who attend these digital meetings.

According to Tom 'Work Happy' Welch, the solution lies in discovering who you really are, identifying what you want out of your job and your life, and learning how to achieve it. You can love your work, gain control over your future, earn more money, and live a happier, healthier life. All it takes is a little planning and some focused action.

That may be, but employers could do their bit as well, instilling pride in work well done, also keeping employees informed and acknowledging the value of their individual contribution.

Since time immemorial managers who express personal interest in their employees have always managed to get more output. But even this lesson seems to have been forgotten. Perhaps they are "too busy" as well.

Andrew Emmerson

*Electronics World* is published monthly. By post, current issue £2.80, back issues (if available). Orders, payments and general correspondence to Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ.

Newstrade: Distributed by COMAG, Tavistock Road, West Drayton, Middlesex. UB7 7QE Tel 01895 44055.

Subscriptions: Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 01444 445566. Please notify change of address. Subscription rates 1 year UK £36.00 2 years £58.00 3 years £72.00. Europe/Eu 1 year £36.00 2 years £82.00 3 years £103.00. ROW 1 year £61.00 2 years £98.00 3 years £123.

Overseas advertising agents: France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of

America: Ray Barnes, Reed Business Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Colchester) Ltd, Filmsetting by JJ Typographics Ltd, Unit 4 Baron Court, Chandlers Way, Southend-on-Sea, Essex SS2 5SE.

**Cumulus**  
BUSINESS MEDIA

# UPDATE

## Microchip combines PIC microcontroller with DSP

At last Microchip, makers of the popular PICmicro range of microcontrollers, has revealed details of its forthcoming dsPIC DSP-microcontroller combination.

It will be a single-instruction stream non-pipelined modified Harvard machine with a 16-bit data RISC core and 16-bit DSP engine.

The instruction set architecture has been designed, 'to be highly efficient for C compilers and RTOSs,' said Microchip. Towards this vectored exception processing supporting eight user-prioritised, fixed latency, interrupts and seven traps, is included.

Applications foreseen include motor control, Internet-connected appliances, automotive products,

power supply management and speech recognition.

Microchip claims dsPIC will be supported by its own tools, application specific libraries and third-party tools. Devices are planned in packages with from 28 to 100 pins and will operate from 2.5 to 5.5V with a variety of power saving modes.

The company's 0.5µm flash process will be used. Beta sampling is planned for the fourth quarter of 2001 with volume production in 2002.

### PIC with DSP – performance

#### The chip

30Mip/s  
94 instructions  
11 addressing modes  
up to 4 Mbytes x 24 flash  
up to 32K x 16 ram

#### DSP engine

16-bit by 16-bit multiplier  
40-bit adder  
two 40-bit saturating accumulators  
40-bit bi-directional barrel shifter

#### Peripherals


fault-tolerant oscillator  
up to 8 capture and 8 compare functions  
dedicated motor control/power conversion PWM  
Quadrature Encoder Interface  
Interfaces for RS-485, UART, I<sup>2</sup>C, SPI, AC97, CAN, I<sup>2</sup>S  
up to five 16-bit timers  
watchdog timer  
up to 80 I/O bi-directional ports  
10-bit high-speed simultaneous sampling a-to-d converters  
12-bit A/D converters.

## Electronic ink display inventor teams with Philips

E Ink, inventor of a display technology that relies on the electrostatic attraction of tiny coloured particles in a liquid, has revealed yet another prototype. This time it is with Philips Components.

The announcement comes only four months after E Ink agreed to develop and commercialise active-matrix electronic ink displays. The prototypes use a 13cm sheet of E Ink's electronic ink with Philips' active matrix backplanes and drivers.

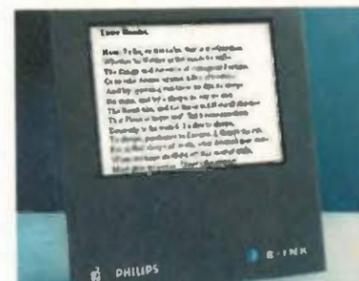The modules can display monochrome and grey-scale images with a resolution of 80dpi. The partners intend to be selling high-resolution electronic ink displays for



smart hand-held devices in 2003.

Unlike LCDs, E Ink's displays do not need polarisers and have a high contrast ratio and a wide viewing angle. The company already has ties with IBM (*Electronics World*, July 2001), and has shown a simple coloured prototype.

## Snake sensors detect changes down to 0.001°C

Poisonous snakes could be the inspiration behind a new generation of infra-red imagers if the University of Texas has anything to do with it.

Crotalines, better known as pit vipers, have unusual 'pit organs' that the snakes use to locate warm-blooded prey. The nerve-rich depression is located in front of the snake's eye and harbours heat-sensors so sensitive the snake can detect a mouse several metres away.

Researchers say the viper's sensing system responds to temperature changes "much less than one-thousandth of a degree centigrade".

Man-made sensors with a similar sensitivity apparently need cooling to -200°C.

The picture shows researcher Dmitriy Protsenko (left), and Professor John Pearce collecting images using a thermographic camera as part of the research programme.

## B<sup>2</sup> Spice 2000

Professional analogue and digital circuit design for the PC and Mac

Accurate results that can be relied on

B<sup>2</sup> Spice 2000 is used by thousands of universities and businesses in the UK and abroad and conforms to the Berkeley SPICE standard. Details of education discounts and site licences are available on request.

Just a few of the features:

Uses the latest Xspice engine for accurate mixed mode simulation. Parameterised AC and transient sweep, Monte Carlo analyses, new Xspice simulations and new noise and distortion analyses. Plus all the model libraries are included in the price, over 7000 parts included.

B<sup>2</sup> Spice 2000 also comes with a powerful model editing package that allows you to create and modify parts and make changes to the libraries.

The best way to see if this software is what you need is to try it - risk free for 30 days.



Telephone 01603 872331 or visit [www.spice-software.com](http://www.spice-software.com)

RD Research, Research House, Norwich Road, Eastgate, Norwich NR10 4HA  
Tel: 01603 872331 Email: [rd.research@paston.co.uk](mailto:rd.research@paston.co.uk) [www.looking.co.uk/spice](http://www.looking.co.uk/spice)  
\*Please add £5.00 postage and packing. All trademarks acknowledged



CIRCLE NO.105 ON REPLY CARD



## Quality Alphanumeric backlit LCDs in 4x40, 2x40, 4x20, 2x20 and 2x16 formats


Supplied either bare or pre-fitted with one of our Eze-Use, Serial interface boards with options such as software buzzer control, backlight control, operator interface, start-up message, big character generation, and PC-AT Keypad /mouse interface - all at very competitive pricing.

We also stock Serial Interface Graphic modules and front panel bezels for all our LCDs. Please call (01977 683665) or check our web site ([www.milinst.com](http://www.milinst.com)) for full details and pricing.


Milford Instruments - your total LCD solution



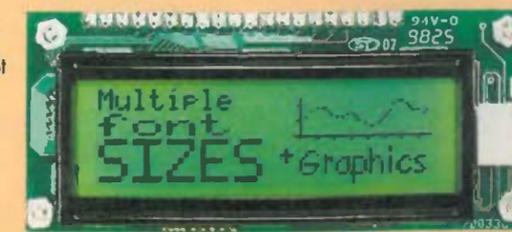Milford Instruments  
Milford House, 120 High St  
South Milford  
LEEDS LS25 5AQ  
Tel 01977 683665  
Fax 01977 681465  
[www.milinst.com](http://www.milinst.com)



CIRCLE NO.106 ON REPLY CARD

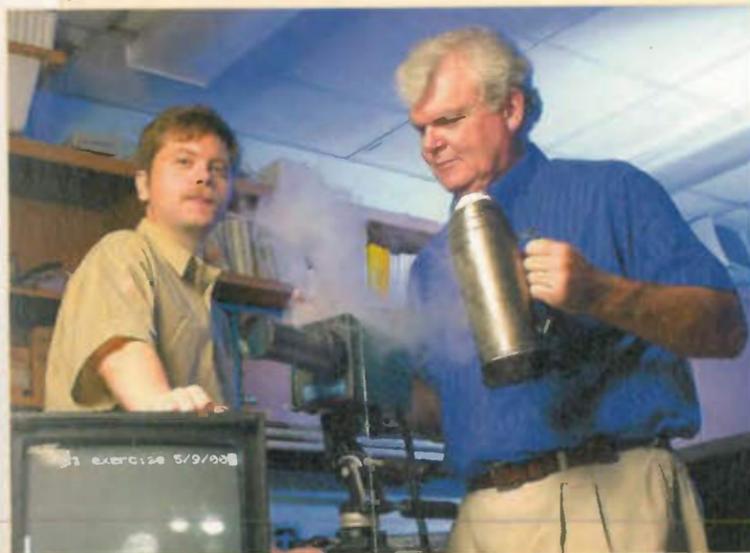


## Fuel cells deliver up to 3kW and run on any hydrocarbon fuel

Fuel cells developed by German firm NovArs look set to go into pilot production.

NovArs' US technology backer Manhattan Scientifics aims to start pilot production of fuel cells aimed at portable electronics such as power tools, home generators and lap-top computers.

The cells are based on a proton exchange membrane (PEM), which can extract hydrogen from almost any hydrocarbon fuel.

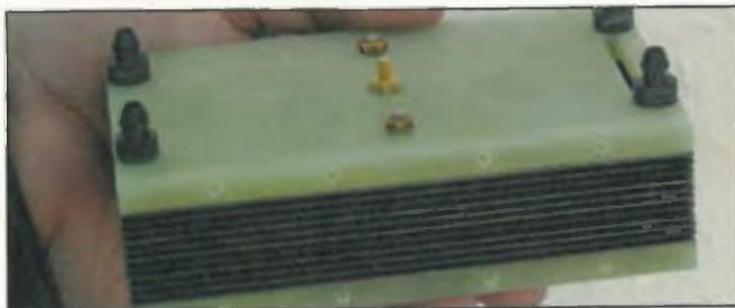Power outputs range from 2W to 3kW, the firm said. Energy density is around 115Wh/l, several times higher than lead acid batteries.



Manhattan has contracts to produce fuel cells for motorbike manufacturer Aprilia, vacuum cleaner maker Electrolux and the US Army.

The firm is discussing building a small production line with several companies, it said, which could be based in the US, Europe or Japan.

## Light-emitting plastics a step closer to production

Cambridge Display Technology (CDT) has signed a deal with Tokki to co-develop production equipment for light-emitting polymer (LEP) displays.

CDT LEPs are one of the two technologies vying for space in the plastic semiconductor displays market, which has yet to develop. Many predict that plastic displays

will dominate the front of mobile phones and personal organisers in the next few years. Organic light-emitting diodes, or OLEDs, from Kodak and its licensees are the other technology – which seems to be slightly ahead in the race to market at the moment.

The CDT-Tokki agreement covers the next generation of Tokki's volume manufacturing physical vapour-deposition (PVD) and encapsulation technology.

Development work will include looking for encapsulation techniques to reduce cost and improve display life.

CDT has purchased a 355mm Tokki PVD machine to be installed at its pilot development line, currently under construction in Godmanchester near Cambridge. This facility is expected to come on line in early 2002.

Nissei Sangyo will be Tokki's exclusive distributor for equipment developed in the deal.

LEP displays took another step towards production recently when Osram Opto Semiconductors (Osram OS) brought forward production plans for LEP displays.

It was due to start manufacture in 2002, but in a statement said it, "expects to bring a commercial LEP display manufacturing plant in Penang, Malaysia on stream during 2001."

According to Osram OS, which is a joint venture between Osram (51 per cent) and Infineon, it already has an LEP pilot line in San Jose.

Its licence allows Osram to

manufacture and sell LEP displays up to 1/4 VGA pixel format with rights to license higher information content in the future.

The right to manufacture lighting devices is also permitted by the licence.

Osram said it will initially develop OEM LEP products for mobile, cellular and automotive applications.

## SM power inductors for small PSUs

Surface-mount power inductors aimed at shielding in lap-top computers and other handheld equipment and mobile products have been introduced by US firm Coilcraft. The inductors have a footprint of 3.7 by 3.7mm, and a height of just 2.6mm. Components in the 1008PS series have inductances ranging from 1 to 1000µH and saturation currents up to 3A. A designer's kit is available from order.coilcraft.com.



## Bipolar transistor achieves 210GHz

IBM Microelectronics has developed a silicon germanium heterojunction bipolar transistor (HBT) running at 210GHz.

The move marks a big step forward, which could extend silicon's reach to the 40Gbit/s communications market and beyond.

IBM exceeded 200GHz by taking its 0.18µm SiGe process, which runs at up to 130GHz, and reducing the vertical thickness of the transistor's base.


With a cut-off frequency ( $f_T$ ) of 210GHz, IBM's transistor is not only 75 per cent faster than its own previous devices, it is significantly faster than any other published SiGe transistor. Hitachi, for example, last year detailed a 0.2µm SiGe HBT with an  $f_T$  of 76GHz.

Other materials, such as indium phosphide, are being touted for high speed comms applications due to higher performance, but they are more expensive to manufacture. IBM claims its HBT, compared to a similar speed InP device, uses 20 per cent less current – around 1mA.

What's interesting is that IBM's process differs little from other companies' devices. HBTs are built on a 0.18µm BiCMOS process with an emitter area of 0.2x1µm.

The major difference comes with the thickness of the base region. Although grown epitaxially like most HBTs, the base has an undisclosed thickness. This reduces the transit time of electrons across the base, which directly affects the cut-off frequency.

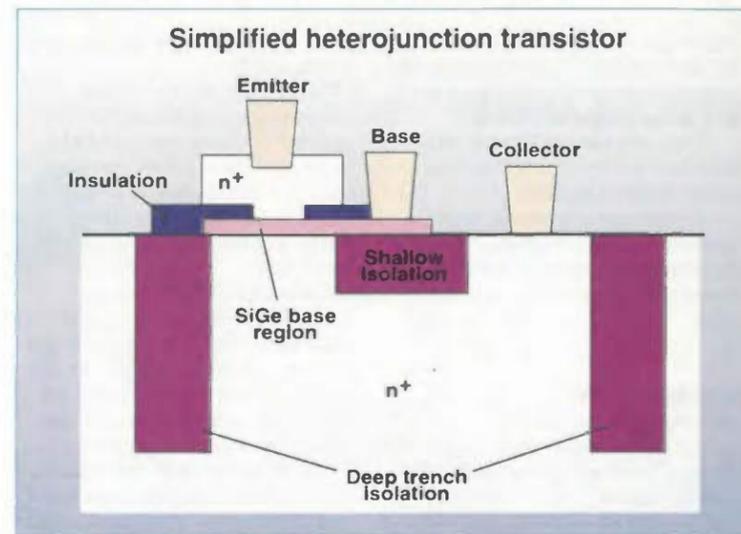Furthermore the amount of germanium in the base is graded, from almost none at the base-emitter junction to between 20 to 30 per cent at the base-collector junction. This brings



This simplified HBT shows its vertical structure. Deep trench isolation protects individual transistors, while a shallow trench separates the base-emitter junction from the collector connection.

into question the device's claim to be an HBT at all.

"There is a small percentage of germanium at the base-emitter junction, so there is a heterojunction effect, seen in an increase of the current gain," said Seshandri Subbanna, senior engineering manager for analogue and mixed signal at IBM. "The main heterojunction is at the collector-base junction."

Subbanna's engineers expect to have manufactured simple circuits based on the HBTs by the end of the year.

● In a separate announcement, IBM said it will add 'strained silicon' to its CMOS manufacturing within two years, a process it claims will increase switching speeds by 35 per cent.

"The limiting factor for switching speeds is the mobility of electrons and holes," said Helmut Schettler from

IBM. Strained silicon increases electron mobility by 70 per cent, he said.

Strained silicon is made by growing a silicon layer on top of a lattice with a slightly larger inter-atom spacing. This is often a 75/25 silicon/germanium layer giving a one per cent expansion.

If the top layer of silicon is fairly thin, as it is in a fet's channel, then the silicon retains the spacing of the substrate and is said to be strained.

Even a one per cent larger lattice increases degeneracy of the silicon's conduction band, trapping electrons and reducing the scattering of free electrons in the lattice. This increases mobility.

IBM has completed some test structures using strained silicon and expects to have it in production by 2003. "It's a question of getting a reliable process," Schettler said.


## New package options for smaller circuit boards

Texas Instruments has developed a family of packages for simple logic chips which can cut circuit board footprints by 70 per cent, compared with its previous packaging.

Called NanoStar, the 5- and 8-pin packages are aimed at single and dual logic gates, often used in products such as mobile phones, laptops, MP3 players and other hand-held equipment.

Until now TI has used the 5-pin SC-70 package for single gate logic. NanoStar has a footprint of 1.4 by 0.9mm, or 1.26mm<sup>2</sup>, which means it uses 70 per cent less board space than SC-70. Its height is 0.5mm.

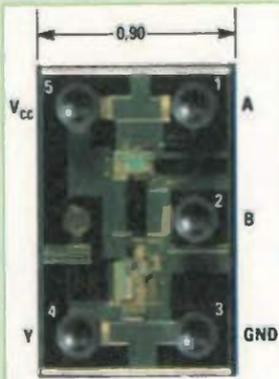Connection to the PCB is via eutectic solder balls – the mixture of metals in the balls melt and solidify at the same temperature. Thermal properties are improved compared with the SC-70 packages, TI said.



## Java makes robot clap

The JavaOne Developers Conference in San Francisco saw the emergence of the "Ultimate Wireless Lego Robot", or so Motorola claimed.

Together with Flashline, Motorola assembled the robot to demonstrate their wireless data technology.

Users remotely sent commands from a Motorola i50sx phone through the Internet to the robot, which will dance, clap its hands, wag its tail, and move around in response.

Both the handset and the application use Java J2ME, one of the smaller versions of Java aimed at portable applications. The Internet connection is 'always-on' and the software is bolted together from re-usable modules.



## First products using Indium phosphide semis available next year

Indium phosphide, one of the new breed of high-performance compound semiconductors, is set to appear next year in a commercial product.

TRW, with partner Hitachi, will introduce InP devices into mobile phone handsets in 2002.

InP is an exotic material, until recently confined to laboratories, but its phenomenal speed is tempting manufacturers to bring it into the open.

faster but TRW's test gear ran out of steam.

Direct integration of optical components is another possibility with InP. Devices such as LEDs, lasers, and photodiodes operating in the 1.3-1.55  $\mu\text{m}$  (optical fibre) region may be made alongside HEMTs and HBTs (heterojunction bipolar transistors).

These speed, efficiency and versatility advantages have been more than offset by cost, yield, and reliability problems, as well as lack of high quality large-diameter InP substrates – which are fragile and brittle when you can get them.

According to TRW, InP shares many of these problems with GaAs and the company introduced a high-

volume commercial GaAs HBT process in 1993 when others thought it was years away.

Its InP process is modelled on a 1  $\mu\text{m}$  descendant of its original GaAs process. Steps transferred include substrate supply (75mm now, 100mm in development), epitaxy (molecular beam), yield and backside processes.

It claims process yields equivalent to those of GaAs HBT processes on its space-qualified 75mm InP process. The 100mm process will be for commercial and space applications.

Reliability is high, says the company, with MTTF (mean-time-to-failure) values of  $10^7$  to  $10^9$  hours for devices at 125°C ambient.

### InP applications – according to TRW

- mobile phone handset power amplifiers
- digital and microwave ICs for satellite payloads
- 40 and 80Gbit/s optical network components
- integrated fibre-optic receivers
- Ku-band to above-V-band LNAs, VCOs and PAs
- components for 'last mile' broadband access
- 60GHz wireless picocells
- 94GHz wireless links.

"TRW's baseline InP HEMT [high electron mobility transistor] process with 65 per cent indium in the channel yields devices with an  $f_t$  of 300GHz and an  $f_{max}$  of 450GHz. InP HEMTs exhibit higher gain than GaAs HEMTs, as well as a lower noise figure and better PAE [power-added efficiency]," claimed the company in a paper last year.

And TRW has made an InP static frequency divider that operates at least 80.1GHz – way over the head of silicon. In fact, it could have been

### Mini mouse is world's smallest

This is the smallest manual input device in the world, claims its maker InControl Systems.

Called Piccolo Point, this is a force sensitive mini-joystick – shown in the picture combined with push-buttons to make a mouse.

It is aimed at wireless and hand-held products and is under 4mm thick with a 14 by 18.5mm footprint – including connector – and with a predicted life of ten million operations.

The company also offers a custom microcontroller that emulates a serial or PS/2 mouse and works with standard mouse drivers, or the user can exploit unused resources in an existing microcontroller to support pointing.

Piccolo Point is available from Diamond Electronics.



### Diagonal routing promises faster chips with lower power consumption

A consortium of companies has set up an initiative to promote diagonal routing inside ICs, a technique that could increase speeds, cut power drain and improve yield.

Called the X Architecture, the technique rotates the fourth and fifth metal layers through 45°. Standard chips are arranged

with metal layers in the so-called Manhattan layout, alternately running horizontally and vertically.

While using diagonal lines is hardly new, the idea of devoting two whole layers to 45° lines is a bold move.

This simple change to the orientation of two metal layers could reduce the length of any single interconnect by up to 30 per cent.

An entire cross-section of the industry from EDA firm Simplex, through a number of mask and equipment makers, to semiconductor manufacturers STMicroelectronics and Toshiba are promoting the move.

In fact Toshiba and Simplex claim to have been working on a production system for over two years.

"As we developed the technology that enables the X Architecture, we worked closely with our partner Toshiba over

several years to prove the manufacturability of this new architecture," said Aki Fujimura, president and CEO of Simplex.

On typical chip designs, the firms reckon the total interconnect length is cut by 20 per cent. Consequently performance increases by 10 per cent and power dissipation drops by a fifth.

Perhaps even more significant is the claim that the process could increase the number of dies per wafer by 30 per cent.

"In today's era of five-plus metal-layer designs, the advantages of using diagonal lines are tremendous in terms of chip performance, as well as area," said Dr Kenji Yoshida, v-p of engineering at Japan's Semiconductor Technology Academic Research Center.

Using metal layers four and five means that existing library cells and intellectual property blocks are unaffected as they use lower metal layers.


## THE OSCILLOSCOPE IS MOVING ON...

### Features:

- ▲ A fraction of the cost of benchtop scopes
- ▲ Save multiple setups, for ease of use
- ▲ Save, print and e-mail your traces
- ▲ FREE software and upgrades
- ▲ Automated measurements
- ▲ Large colour displays
- ▲ Scope, spectrum analyser & meter functions

Ask for a FREE catalogue and demo software, or visit:

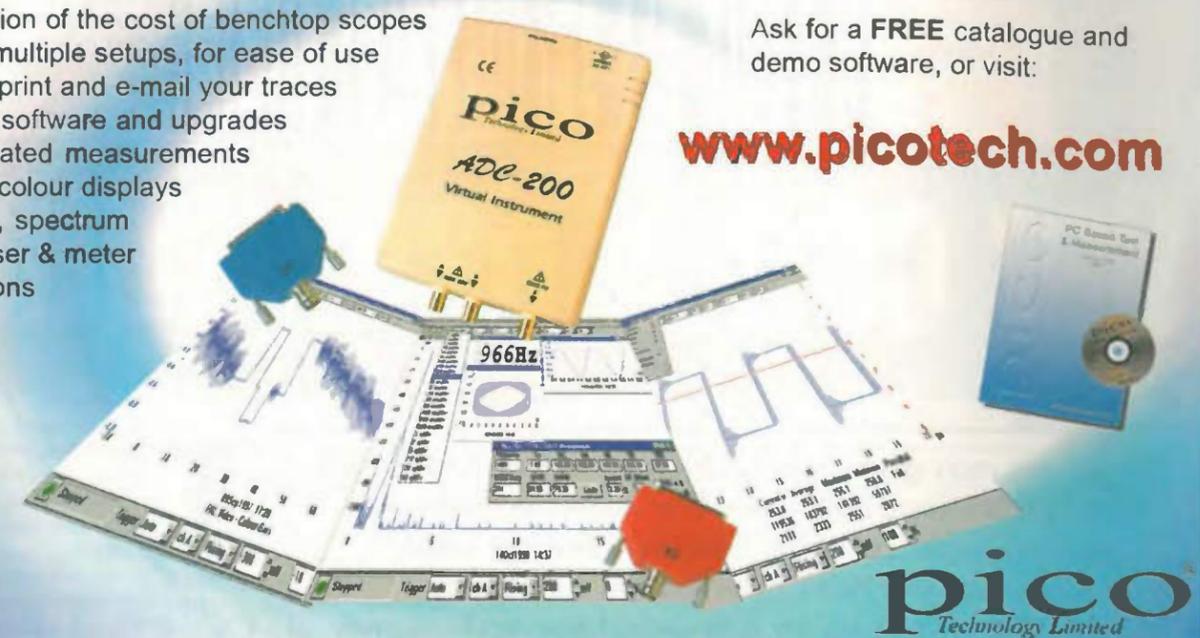[www.picotech.com](http://www.picotech.com)



...DON'T GET LEFT BEHIND

Tel: +44 (0) 1480 396395, Fax: +44 (0) 1480 396296, E-mail: [post@picotech.com](mailto:post@picotech.com)

CIRCLE NO. 107 ON REPLY CARD

# RANGER XL

The Complete Integrated Schematic PCB Layout Package

# Too good for words



### The New Ranger XL Series

Ranger 2 for Windows	£60
<b>NEW</b> Ranger 2XL	£500
<b>NEW</b> Ranger XL from	£950
<b>FREE</b> Website Download Demo	

**SEETRAK**  
Advanced Systems & Technology for PCB Manufacturers

Old Buriton Lime Works, Buriton, Petersfield, Hants. UK GU31 5SJ  
Tel: (44) 01730 260062 Fax: (44) 01730 267273

CIRCLE NO. 108 ON REPLY CARD



# Bar codes demystified

**Roger Thomas** gives a brief history of bar codes and the organisations that issue bar-code numbers. He details the most common bar-code format used in retailing, and provides information on how to decode the stripes using a low-cost bar-code wand, PIC microcontroller and software.



**T**here are many different bar-coding schemes in operation, but for retail products the EAN-13 system is used.

Products that are only sold in one store – i.e. own label goods – or require weighing and labelling in-store are not part of this scheme.

An EAN-13 bar code allows for unique product identification using thirteen numbers. Bar codes found on food and household products do not include the price or product description. This information is obtained from the computer system that the scanning equipment is connected to.

## Bar-code numbering

In the UK, the organisation that allocates company prefix numbers is called e-centre. This is the trading name of the Association for Standards and Practices in Electronic Trade – EAN UK Ltd. It was launched on 7 October 1998 with the merger of the Article Number Association and the Electronic Commerce Association.

Article Number Association, or ANA, was the UK authority for company prefix numbers and established in 1976. The Electronic Commerce Association was formed in 1987, originally as the EDI Association, but in 1996 it broadened its activities to incorporate electronic commerce.

ANA was a founder member of the European Article Numbering, or EAN, Association formed in February 1977 with its headquarters based in Brussels. The name was changed in 1992 to EAN International to indicate that its activities are no longer confined to Europe.

EAN International is represented in 99 countries by local offices. It was founded to create a compatible bar-

coding system based on the North American bar-coding system known as Universal Product Code, or UPC.

## UPC format

The UPC coded bar code was adopted by the North American retail industry in 1973. American Uniform Code Council (UCC) administers the allocation of UPC numbers.

A UPC number is a twelve digit number with the first digit being a number-system character. The following table shows what each system number represents.

0	UPC retail number
1	reserved
2	items that need to weighed
3	drugs and health related products
4	used for in-store labelling
5	coupons
6	UPC retail number
7	UPC retail number
8	reserved
9	reserved

After this number, there follows a five-digit company number – allocated by UCC – and a five-digit product number, assigned by the company. This provides 100 000 companies the ability to number 100 000 products for each system number.

The last digit is a check digit. At present, UPC numbers 1, 8, 9 have not been allocated giving scope for additional 300 000 company-prefix numbers.

## EAN format

EAN-13 is a thirteen number group structured in a similar way to UPC number. However there is no system number. This is replaced by a country prefix. Following the country prefix, there is a unique company prefix, product number and a check digit. This check digit ensures that the bar code has been correctly scanned.

The country prefix is the first two or three digits of the bar-code number.

For the UK, the country prefix is 50, Fig. 1. If a bar code starts with 50, this does not necessarily mean that the UK is the country of origin for the product though.

Unlike UPC, the EAN scheme has the company prefix and product numbers of variable length. Varying the length of the company prefix makes for a more efficient use of the numbers. If a company only needs to number 100 products then they are

provided with a longer company prefix than a company needing to number 10 000 products.

Each nine-digit company-prefix number can be used to create up to 1000 different product numbers. Eight digit prefix numbers can be used to create up to 10 000 numbers and seven digit prefix numbers can be used to create up to 100 000 numbers. The company allocates the individual product numbers – not the organisation that allocated the company prefix.

## Coupon code

Two prefixes have been reserved for use on EAN coded redemption coupons. Prefix 98 is used for a coupon that might cross national boundaries and prefix 99 is reserved for national coupons.

For example 99 YYYY NNN VVV C comprises YYYY, which is the coupon issuer number, NNN the coupon reference number, VVV the redemption value and C is the check digit.

The redemption value range of the coupon is from 1p (VVV = 001) to £9.98 (VVV = 998); the decimal point is fixed. For values greater than £9.98 the code 999 is used and the redemption value entered at the checkout. Coupons that offer free goods are encoded by VVV=000. Coupon numbers may be re-issued after 36 months has lapsed.

## ISBN book codes

The International Standard Book Number (ISBN) is a unique ten-digit number allocated to every book by its publisher. The ISBN system was in use before the EAN-13 numbering system was adopted.

An ISBN code consists of four parts. The first part indicates the language or country of origin and can be a one, two or three digit number. For example, a 0 or 1 number indicates the book is written in the English language. The number 2 is for books in the French language, 3 for books in the German language, 4 for books published in Japanese. The second part indicates the publisher and the third part the book number allocated by the publisher. The size of each field is not fixed and the last digit is the check digit.

ISBN codes are represented in the EAN/UCC-13 coding scheme by adding a 978 prefix. The final digit is the EAN/UCC calculated check digit and not the original ISBN check digit.

Check digits in the ISBN system use a different algorithm. It is

Fig. 1. List of European country-prefix codes.

Austria	90 and 91
Belgium and Luxembourg	54
Denmark	57
Finland	64
France	30 to 37
Germany	400 to 440
Greece	520
Ireland	539
Italy	80 to 83
Netherlands	87
Norway	70
Portugal	560
Spain	84
Sweden	73
Switzerland	76
United Kingdom	50

possible that the original ISBN book number – and possibly the associated ISBN bar code – will also be printed near the EAN/UCC-13 bar code. If the original ISBN number is printed, the different fields can be separated by hyphens.

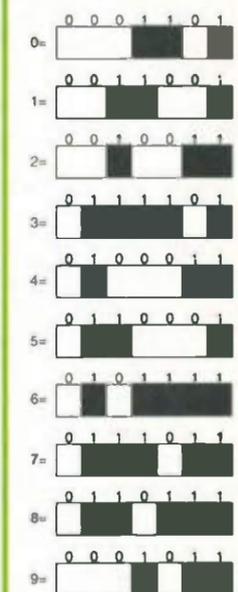


Fig. 2. Bar code 'Table A', top, and the same table converted to a number, below.

[0]	0001101 = 13
[1]	0011001 = 25
[2]	0010011 = 19
[3]	0111101 = 61
[4]	0100011 = 35
[5]	0110001 = 49
[6]	0101111 = 47
[7]	0111011 = 59
[8]	0110111 = 55
[9]	0001011 = 11

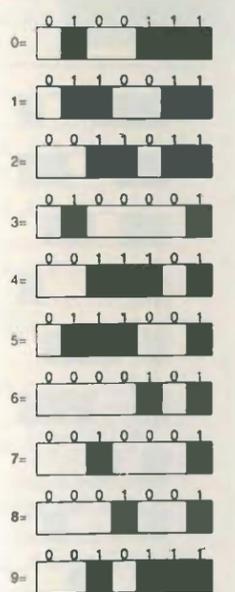


Fig. 3. Bar code 'Table B', top, and its related numbers, below.

[0]	0100111 = 39
[1]	0110011 = 51
[2]	0011011 = 27
[3]	0100001 = 33
[4]	0011101 = 29
[5]	0111001 = 57
[6]	0000101 = 5
[7]	0010001 = 17
[8]	0001001 = 9
[9]	0010111 = 23

Fig. 4. Encoding of the first number of the bar code.

0	AAAAAA
1	AABABB
2	AABBAB
3	AABBBA
4	ABAABB
5	ABBAAB
6	ABBBAA
7	ABABAB
8	ABABBA
9	ABBABA

Next to the bar code there may also be an additional five-number bar code. If this bar code is the book's price, then it will begin with a 0 for the price in pounds and 5 for the price in US dollars. A code of 90000 indicates that the book has no suggested retail price. Any other number beginning with 9 is used internally by the publishers.

The 978 number scheme is also used to identify computer CD-ROM software used for education or reference – including catalogues on

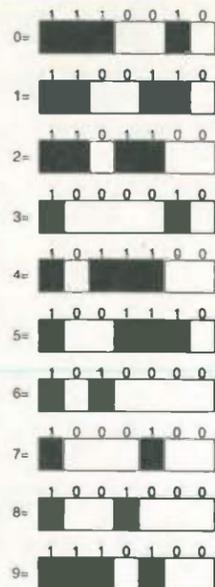


Fig. 5. Bar code 'Table C', top, and decoded numbers, below.

[0]	1110010 = 114
[1]	1100110 = 102
[2]	1101100 = 108
[3]	1000010 = 66
[4]	1011100 = 92
[5]	1001110 = 78
[6]	1010000 = 80
[7]	1000100 = 68
[8]	1001000 = 72
[9]	1110100 = 116

CD. Music CDs or games CDs are not included in the 978 numbering scheme and use a normal EAN/UCC-13 number.

#### ISSN periodical codes

A system used to identify serial publications, such as newspapers and magazines, is called the International Standard Serial Numbering, or ISSN, scheme. An ISSN number is coded in the EAN/UCC-13 scheme with a 977 prefix. These EAN/UCC-13 bar codes can also have a separate two digit extension code.

For daily publications the number is 977 SSSSSS PD C WW. Here, 977 is the ISSN prefix number and SSSSSS the ISSN number. Letter P indicates change of price. It is increased in value by one each time the price rises. The 'D' indicates the day of the week – week starts Monday – while C is the EAN/UCC check digit. Finally, WW is the week number represented by a separate two digit symbol.

For weekly publications the number is 977 SSSSSS PP C WW. In this case, 977 is the ISSN prefix number and SSSSSS the ISSN number. The 'PP' indicates change of price, rising by one for each price increase. Letter C represents the EAN/UCC check digit while WW represents the week number as a separate two digit symbol.

For monthly publications this additional two-digit bar code indicates the month.

#### UPC in Europe

Products identified with UPC bar codes have been scanned without any problem in Europe. The twelve-digit UPC number can be processed by preceding the number with 0 to make it EAN-13 compatible.

However, the reverse has not always been true in that some European suppliers have had to obtain UPC numbers if their product was to be sold in North America. The problem is not with the scanner equipment but incompatibility due to many American retail computer database systems not being able to handle the extra digit, or the variable length product and company number.

#### UPC future

The Uniform Code Council organisation is expected to use all of its company prefix numbers by the year 2005. Consequently the UCC has established the 1 January 2005 for all retailers to accept the EAN-13 code, as well as the UPC code, at the point

of sale terminals.

This date was agreed in May 1997 at a joint meeting between the UCC and EAN International. UCC acquired country prefixes 10, 11, 12 and 13 from EAN International. After the 1 January 2005, thirteen digit EAN-13 numbers will, for the first time, be allocated by the UCC.

There is no ambiguity between the EAN and UCC numbers. The existing twelve-digit UPC number is not being replaced by EAN-13, but adopting the EAN-13 format allows for expansion and a global numbering system.

#### UK bar codes

If you look at a typical EAN-13 bar code number, the 5 (first number of the UK 50 country prefix) is shown on the left before the guide bars. The first country prefix number is not directly incorporated as bar stripes but is encoded by the choice of which characters are taken from Fig. 2 or Fig. 3 for a given position. These are often referred to as Table A and Table B.

For example, UK bar code use the sequence 'ABBAAB' to signify the number 5, Fig. 4. The first number to be coded (0) is taken from Fig. 2. The second and third numbers use Fig. 3, and so on. Similarly the table sequence 'ABBABA' is used to denote the number 9 – used for magazines and books.

Only twelve numbers are actually encoded in the bar-code stripes. The last six numbers are taken from Fig. 5 (i.e. Table C). Definitions in this table are the reverse of those in Fig. 3.

Each number definition is unique so there are no duplicate patterns.

#### Bar-code forms

EAN/UCC-13 uses proportional coding with four different widths. When printed, this is more space efficient than coding the number in binary. There are no inter-character gaps – spaces are part of each number definition.

In addition to the bar-coded twelve numbers, there are two guide characters and a centre character. These guide bars may be extended below the rest of the bar code.

To increase scanning reliability, not all the possible character permutations are used. The maximum black or space width is four and there are always two sets of bars and two sets of spaces per number. Overall, there is virtually an equal number of bars to spaces per bar-code number.

Bar-code definitions on the left side of the centre guide bar all start with a

space and end with a bar. With bar codes on the right the converse is true starting with a bar and ending with a space. A blank area – referred to as the 'quiet zone' – must appear before and after the bar code. Bar-code scanners use this zone to determine the exact beginning and end of the bar code.

#### Bar-code wand

Quality bar-code wands are often manufactured with a metal barrel; cheaper wands tend to be made of plastic. These wands look like a large pen. At one end there will be a small lens and at the other end a lead.

The wand must be able to distinguish between the bar-code bars and the gap between the bars. To do this, most hand-held wands use several red light emitting diodes that are used to illuminate the bar code with visible red light and a photocell light detector in the centre of these leds. The light detector converts the reflected optical signal into a digital signal that is then fed to the microcontroller.

The printed bar should absorb the light, while the background reflects the light back to the wand detector, the detector responds to this intensity change. A return signal above a certain threshold will produce a logic 0 and below this threshold will produce a logic 1. Consequently as the wand is moved across the bar code the background produces a logic '0' and a bar is logic '1'.

Place the wand to the left of the bar code in the blank area just before the bar code. The wand is held like a pen and a straight line is lightly drawn across the entire bar code. If it does not scan the first time then do not press down harder the second time as this makes no difference.


Initially it may take a few attempts to scan a bar code before the correct position and speed are found.

#### Wedge

Having scanned a bar code for data capture, the information needs to be input into application program. This data transfer is often achieved using a keyboard 'wedge'.



There are two versions of the wedge – hardware and software. With the hardware wedge, the keyboard from the PC is plugged into the wedge, as is the bar-code scanner. The wedge is then plugged into the PC keyboard port. Whenever a bar code is scanned the wedge sends this data to the PC as if the bar-code number was entered using the keyboard.

Fig. 6. Block diagram of bar-code reader, together with the complete circuit, apart from the power supply and wand.

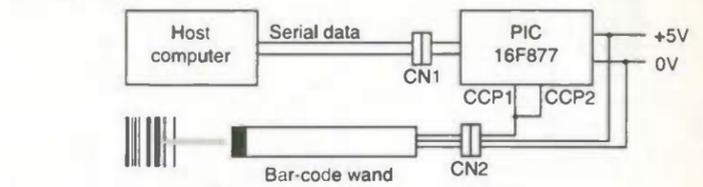

Component list for bar-code decoder	
IC <sub>1</sub>	PIC 16F877
IC <sub>2</sub>	74LS14
C <sub>1</sub>	10µF
C <sub>2</sub>	1nF
C <sub>3,4</sub>	15pF
R <sub>1,3</sub>	470Ω
R <sub>2</sub>	1kΩ
X <sub>1</sub>	20MHz crystal
CN <sub>1</sub>	serial connection
CN <sub>2</sub>	wand connection

Power wiring list.	
+5V	PIC pin 1
+5V	PIC pin 11
+5V	PIC pin 32
+5V	wand pin 9
+5V	74LS14 pin 14
0V	PIC pin 12
0V	PIC pin 31
0V	wand pin 7
0V	74LS14 pin 7

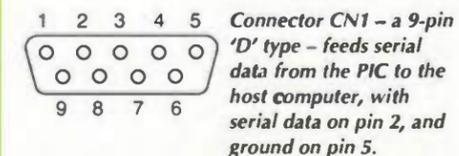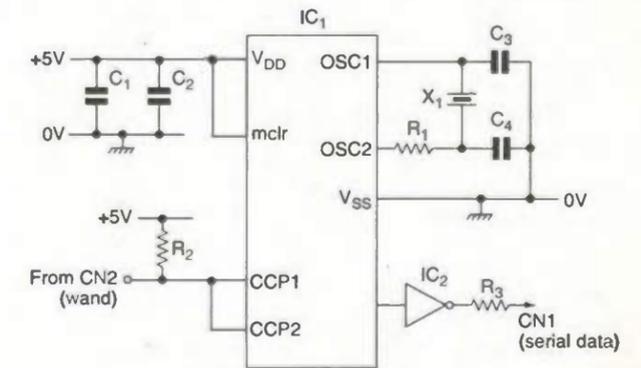

Feeding serial data from the wand to the pic, 9-pin 'D' socket CN2 has ground on pin 7, the wand signal on pin 2 and +5V on pin 9.

A software wedge is used with a lap-top computer or portable terminal where there is no external keyboard port. The bar-code scanner is connected to the serial or usb port. Software reads the data from the bar-code scanner; converts and sends this information to the keyboard buffer. The bar-code data then appears in the application program as if it was entered using the keyboard.

Any program that expects bar-code numbers to be entered manually via the keyboard can be used with a suitable wedge without any need for the program to be modified.

#### Wand connections

An external five-volt power supply will be required to power the wand and PIC circuit. A wand requires about 40mA continuous current.

#### Bar-code colours

Bar codes do not have to be printed in black on white but this is usually the easiest – and safest – print option. Red, yellow, and white are suitable background colours as they will reflect the scanner light. Blue, green, dark brown and violet can be used for the printed bar as they appear black under the red scanner light.

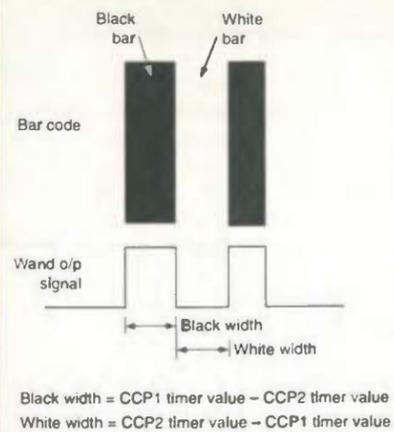


Fig. 7. Using capture register and timer values to calculate bar widths.

Usually, only three wand connections are required. The connections are power, i.e. +5V, and ground, and signal output. These connectors are usually a 9-pin 'D', but other connectors are possible. Most bar-code wands have an open-collector data output, in which case a pull-up resistor,  $R_2$ , is required.

Wand output connects directly to the 16F877 PIC, which converts the TTL signal from the wand into bar-code widths. These different bar-code widths are converted by the PIC software into a series of numbers and transmitted via a ttl buffer to the serial port of the computer, Fig. 6.

#### Timing-bar widths

Using the microcontroller's 16-bit timer, namely timer 1, the bar-code width can be calculated. Timer 1 is in counter mode and is free running. The 20MHz clock is internally divided by four and the prescaler is also set to divide by four, therefore the clock to the timer is running at 1.25MHz.

The bar-code wand output, Fig. 6,

#### Bar-code trivia

In 1967 the Association of American Railroad selected a bar-code identification system to keep track of the rolling stock. The first test of the system was in 1961.

Each carriage was given a four-digit number to identify which railroad owned it and a six-digit identity number. These bar-code stripes were placed on the side of the rolling stock using reflective material.

This was the first attempt at an industrial application of bar-code technology, previous systems have all been associated with retailing. It took until the mid 1970's before the majority of the rolling stock had these bar codes. However for cost and other reasons the system was abandoned in the late 1970s.

Also in 1967, RCA installed one of the first retail scanning systems at a store in Cincinnati. A set of concentric circular bars and spaces of varying widths represented the product number. These bar codes were not pre-printed on the product but these labels were put on each item by the store. Retail industry recognised the advantages of this technology to speed up the check-out process and for inventory control but this could only be achieved with industry wide standards.

In 1970 the US Supermarket Ad Hoc Committee was formed and the result was the Universal Grocery Products Identification Code. Three years later the UPC (Uniform Product Code) numbering system using linear bar-code symbols was adopted.

On 26th June 1974 at a super-market in Troy, Ohio the first retail product with a UPC bar code was scanned using one of the first bar-code scanners installed. The scanner was manufactured by National Cash Register Company - now known as NCR - and the product was a packet of Wrigley's chewing gum.

For those that do not have a 16F877 programmer I can supply a programmed PIC for £20, this includes the Windows 95/98 software. PIC and MPLAB are registered trademarks of Microchip Technology Incorporated, USA.

Windows 95/98 is a registered trademark of the Microsoft Corporation.

connects to both capture pins on the PIC16F877. Register CCP1 is triggered on the black to white transitions (logic 1→0) and CCP2 is triggered on a white to black transition (logic 0→1).

Whenever there is a rising or falling edge generated by the bar-code wand output then timer 1 value is read.

Timer 1 is not reset when its value is read, when it reaches its maximum value of  $FFFF_{16}$  it starts counting up

from zero. This does not pose any problems if the two timer readings are either side of this timer event as the width calculation is done using unsigned 16-bit integer arithmetic.

#### Calculating bar widths

The program waits until the bar-code wand detector output goes low and the start of the quiet zone is assumed. PIC programming times the width of the first black bar (guide bar). This value is used as the initial reference value for black bars (width=1).

Next the width of the first white bar - i.e. the gap between guide bars - is measured. This will be used as the initial reference value for white bars (width=1). The second black guide bar is timed and the average taken of both black guide bar values by adding both results and dividing by 2.

Software will 'time out' after approximately 20ms of inactivity after the start of scan. If this happens, a suitable error message is appended to the numbers already scanned in.

Black and white width values are calculated independently of each other. The width value is used as the basis of comparisons for all following width timing calculations. In theory, the black and white width values

should be the same but having them separate reduces any problems caused by variation in the quality of bar-code printing.

If the timer width of a subsequent single width is less than the reference value then the reference width becomes this new value. Whatever number is encoded in the stripes there will always be the two middle single width guide bars for reference. If the width=2 reference value is different from a scanned bar, then this new value is divided by 2 and made the new single-width reference value. This ensures that if the speed at which the wand is moving across the bar code changes, then the subsequent measurements will still be accurate. There will be some variation in scanning speed as a constant speed across the whole bar code is very unlikely.

If the bar width time value is less than 150% of the appropriate reference value then bar width is one. If the timed bar is between 150% and 250% of the reference value then bar width is two. If the bar width is between 250% and 350% of the reference value then bar width is set to three. If the bar width is greater than 350% of the reference value then bar width is four.

#### Bar width into binary

The various bar-code widths are measured and converted into a binary sequence according to the bar width. This sequence should begin with

#### Calculating the check digit

Here is an illustration of how the simple formulas needed for calculating the EAN/UPC check digit are used.

Example: calculate the check digit (C) for the EAN/UCC-13 number:

501234576421C

Starting on the left side of the number add together all alternate even numbers:

$0+2+4+7+4+1=18$

Multiply the result by three:

$18 \times 3 = 54$

Add together the remaining odd numbers:

$5+1+3+5+6+2=22$

Add both results together:

$54+22=76$

The check digit is the smallest decimal number which, when added to the previous result, produces a number divisible by 10

$76+C=80$

$C=80-76$

$C=4$

The full number is 5012345764214

'101', which represents black, white, black single width guide bar and is checked by the software. If it is missing then an error message is sent to the PC and the rest of the scan is ignored as the software does not have a valid reference value.


Likewise, the software checks that the middle guide bars are also present. If they are not, then the error message is sent. These guide bars are not part of the bar-code number and are subsequently ignored by the software.

#### Converting bar binary into numbers

As already established, each bar-code number is uniquely defined using, in effect, a seven-bit binary definition. Each bar-code number binary definition is converted into a number.

The scanned bar code starts off as a binary number and is also converted to its equivalent number. The appropriate table is searched, looking for a numeric match for each number. For example, if the first bar-code

Fig. 8. HyperTerminal, which is part of Windows 95/98, can be used to display numbers received through the RS232 port. Among the bar codes displayed here is a German code (40) found on a soft drinks plastic bottle

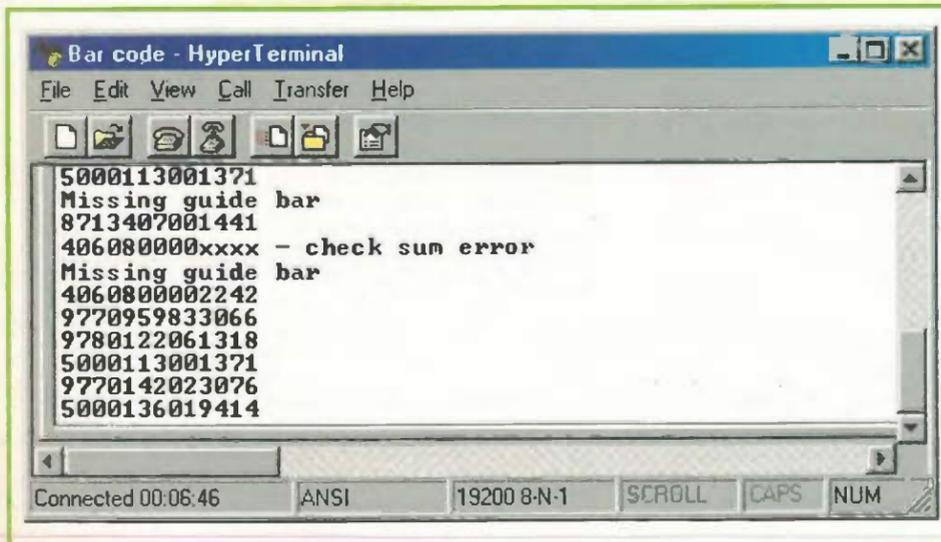


#### PC software

I have produced Windows 95/98/ME software that has the ability to check that a EAN/UCC-13 bar-code number is valid. It also determines which country allocated the bar code from the country prefix number. Bar-code numbers can be typed in from the keyboard, as well as being scanned.

The software can also generate EAN/UCC-13 bar codes. The resulting bit maps can be copied to the clipboard and pasted into another application.

The software includes a simple text-based user defined database. If the bar-code number matches a bar code within the database then text information contained in the database is displayed. This helps demonstrate how bar codes can be used for inventory or asset tracking systems.

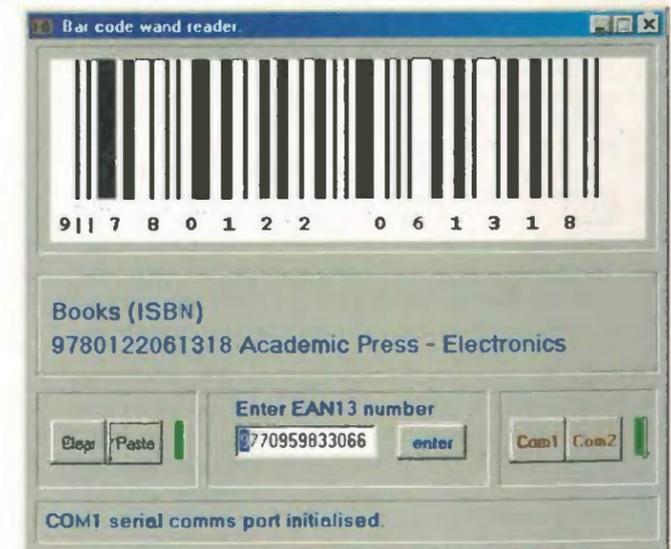If you are interested in this software, please write to me, Roger Thomas, at 24 Slave Hill, Haddenham, Aylesbury, Buckinghamshire HP17 8AZ. I can also supply a pre-programmed PIC 16F877 for £20. This price includes the Windows software.



Windows software, available from the author, shown here checking a scanned magazine bar code in the database.

sequence number is 13 – which it will be for a UK bar code – then a match is found in table A, Fig. 2, and '0' is returned. If there is no match then an 'x' is sent indicating a scanning error.

Depending on whether table A or B provided the first six numbers this also determines the first number, which is the country prefix. Consequently all numbers have to be stored so that the first number can be decoded from Fig. 4 and transmitted first.

If one of the first six numbers has not scanned properly then the first number cannot be derived and an 'X' is sent as the first number.

Once the bar code is converted into a thirteen-digit number, it needs to be verified to see if it has been

scanned correctly. This is done by removing the last digit – the check digit – and using all the remaining numbers to generate a check number. If the scanned number includes an 'x' then the scanned bar-code number will automatically fail.

The algorithm to create this check digit is the same one that was originally used. Both UPC and EAN-13 use the same formula. This calculated number is compared with the scanned check digit. If they are the same then this verifies the bar code has been scanned correctly; if not the bar code is rejected and a 'check-sum error' message sent to the computer.

Using List 1, programmed into a PIC, data is transmitted from the microcontroller at 19200 baud, 8-bit

data and no parity. Although the microcontroller has a built-in serial port, it is necessary to invert the data using a 74LS14 buffer. This inversion would normally happen when using a serial interface driver but as data is flowing one way a serial interface driver is not needed.

#### Terminal software

As the output from the PIC microcontroller is the bar-code number or error messages in plain text (ASCII) then the Hilgraeve HyperTerminal software – supplied with Windows – can be used to view this information, Fig. 8. Set the HyperTerminal properties as 'direct to com'. Set the Port Setting as follows 19200 bits per second, 8 data bits, no parity, 1 stop bit, and no flow control. ■

**List 1. PIC object code for reading bar codes and conveying the number via RS232 to a PC. When programmed into a flash PIC16F877, this hexadecimal code allows the decoding of a EAN/UCC-13 bar code and sends the bar-code number to the PC. This PIC code is intended for personal use only, any commercial use requires written agreement from the author.**

Microchip MPLAB assembler software saves the PIC object code in INHX8M format. All numbers are in hexadecimal and each line starts with a colon. After the colon each line starts with the number of data bytes followed by the address and the PIC object code, the last byte is the line checksum.

Using a text editor, such as Windows Notepad, enter the hex data and save the data in a file with a hex extension (for example barcode.hex).

If the PIC programmer is being used in conjunction with the Microchip MPLAB software then select the import (import to memory) option from the file menu. Find the appropriate directory and select the barcode.hex file. To view the hex code that will be programmed into the PIC16F877, select from the Windows menu the 'Program Memory' option.

When programming the flash PIC, ensure that the PIC configuration options are set to the following - oscillator mode is set to HS (high speed), watchdog timer is off and power up timer is enabled.

If you don't relish the thought of typing this in, e-mail j.lowe@cumulusmedia.co.uk using the subject heading 'bar codes'.

```
:100000006628423461347234203463346F3464348B
:100010006534203472346534613464346534723448
:100020002034703472346F346734723461346D3418
:1000300020347734723469347434743465346E34F3
:10004000203462347934203452346F346734653468
:1000500027342034543468346F346D346134733402
:10006000A340D3420342D3420346334683465343C
:1000700063346B342034733475346D342034653418
:10008000723472346F3472340A340D344D3469343E
:100090007334733469346E346734203467347534A0
:1000A00069346434653420346234613472340A341F
:1000B000D3420342D342034743469346D34653477
:1000C00020346F34753474340A340D3425254825B2
:1000D0006B20682866280C1DC0280C111608A0008B
:1000E000A1011C08A002031CA1032008AB002108E9
:1000F000AC002B08A0002C08A1000030A2000130A9
```

```
:10010000A30068252008AB002108AC002B08A00044
:100110002C08A1001508A0070318A10A1B08A002BB
:10012000031CA1032008AB002108AC00B00131087A
:100130000319C0283208A0003308A100FF30A20034
:10014000030A002031DA2010030A102031DA20184
:100150002208A000A1000319BD282B08A0002C082C
:10016000A1002008B2002108B3002B08A0002C0831
:10017000A1002008B4002108B5000130BB000B210C
:10018000D1CF2280D101C08A000A1011608A002E9
:10019000031CA1032008AB002108AC002B08A00021
:1001A0002C08A1000030A2000130A300682520081F
:1001B000AB002108AC002B08A0002C08A1001B08F8
:1001C000A0070318A10A1508A002031CA103200818
:1001D000AB002108AC00B0013108013C0318F22843
:1001E000BB0175210C1C0A290C10B00A3008023C16
:1001F000031D0A293108143C03180029BE14682283
:100200003E11BE100130B100B201B301BC01BD010D
:100210000C25B00108003208A0003308A10003300B
:10022000A200030A30081252008B6002108B700F5
:100230002B08A0002C08A1003608A2003708A30054
:10024000C62503192529B10174292B08A0002C0803
:10025000A1003608A002031CA1033708A102200850
:10026000B8002108B9000130BA00DF213808A00029
:100270003908A1003208A2003308A300B7250319EA
:1002800052293808A0003908A1003208A002031C36
:10029000A1033308A1022008B8002108B900BA0A56
:1002A000DF2136293A08013C031D5E292B08A000F6
:1002B0002C08A1002008B2002108B3003A08023C33
:1002C000031D6F292B08A0002C08A1000230A200FA
:1002D0000030A30081252008B2002108B3003108B6
:1002E000643C03187429B10108003408A0003508E3
:1002F000A1000330A200030A30081252008B60031
:100300002108B7002B08A0002C08A1003608A20085
:100310003708A300C62503198F29B101DE292B0850
:10032000A0002C08A1003608A002031CA103370876
:10033000A1022008B8002108B9000130BA00DF216D
:100340003808A0003908A1003408A2003508A3002D
:10035000B7250319BC293808A0003908A1003408C2
:10036000A002031CA1033508A1022008B80021083F
:10037000B900BA0ADF21A0293A08013C031DC829A7
:100380002B08A0002C08A1002008B4002108B5000B
:100390003A08023C031DD9292B08A0002C08A10013
:1003A0000230A2000030A30081252008B4002108FB
```

```
:1003B000B5003108643C0318DE29B10108003C088F
:1003C000A0000230A1005A25BC003C083B07BC003D
:1003D000B10A3108043C031DF6293C08053C031D05
:1003E000F3293E14F4293E10BC01672A31080B3C66
:1003F000031DFE29E2222E08C100672A3108123CA3
:10040000031D062AE2222E08C200672A3108193C81
:10041000031D0E2AE2222E08C300672A3108203C61
:10042000031D162AE2222E08C400672A3108273C41
:10043000031D1E2AE2222E08C500672A31082E3C21
:10044000031D262AE2222E08C600672A3108323C04
:10045000031D342A3C08053C0030031DFF3E0319F0
:10046000322A3E10BC01672A31083A3C031D3C2A5F
:10047000F8232E08C700672A3108413C031D442A8F
:10048000F8232E08C800672A3108483C031D4C2A6F
:10049000F8232E08C900672A31084F3C031D542A4F
:1004A000F8232E08CA00672A3108563C031D5C2A2F
:1004B000F8232E08CB00672A31085D3C031D672A0C
:1004C000F8232E08CC0041242E08C0006822080022
:1004D000B101B0013E187E2AAD012D08123C031C6B
:1004E0007D2A4630A000030A1002D08A200A30103
:1004F000D525AE000625AD0A6D2AE02A3E1D832AC9
:100500005830AE000852A4008AE0006254108AE00EE
:1005100006254208AE0006254308AE00062544081D
:10052000AE0006254508AE0006254608AE000625A5
:100530004708AE0006254808AE0006254908AE006B
:1005400006254A08AE0006254B08AE0006254C08D5
:10055000AE000625BE1CBE2AAD012D080C3C031CB6
:10056000BD2A5930A000030A1002D08A200A3012F
:10057000D525AE000625AD0A6D2AE02A3E1D832AC8
:100580007A30AE00C42A89242E084C02031DCF2ADB
:10059000A30AE0006250D30AE000625E02AAD017A
:1005A0002D08133C031CE02A3230A000030A100CB
:1005B0002D08A200A301D525AE000625AD0AD02A3C
:1005C0000C2508007830AE003C080D3C031DF12AD4
:1005D0003208A0002C08A1000230A1005A25BD0019
:1005E000F12B3C08193C031DFE2A3130AE003D08BA
:1005F000A0000230A1005A25BD00F12B3C08133C9D
:1006000031D0B2B3230AE003D08A000230A100CC
:100610005A25BD00F12B3C083D3C031D182B3330FF
:10062000AE003D08A0000230A1005A25BD00F12B0C
:100630003C08233C031D252B3430AE003D08A000B0
:100640000230A1005A25BD00F12B3C08313C031DAE
:10065000322B3530AE003D08A0000230A1005A25F3
:10066000BD00F12B3C082F3C031D3F2B3630AE0064
:100670003D08A0000230A1005A25BD00F12B3C0826
:100680003B3C031D4C2B3730AE003D08A000023030
:10069000A1005A25BD00F12B3C08373C031D592B06
:1006A0003830AE003D08A0000230A1005A25BD0040
:1006B000F12B3C080B3C031D662B3930AE003D0886
:1006C000A0000230A1005A25BD00F12B3C08273CB8
:1006D000031D742B3030AE003D08A0000230A10095
:1006E0005A25BD00BD0AF12B3C08333C031D822B6B
:1006F0003130AE003D08A0000230A1005A25BD00F7
:10070000BD0AF12B3C081B3C031D902B3230AE0080
:100710003D08A0000230A1005A25BD00BD0AF12B02
:100720003C08213C031D9E2B330AE003D08A00049
:100730000230A1005A25BD00BD0AF12B3C081D3C2A
:10074000031DAC2B3430AE003D08A0000230A100E8
:100750005A25BD00BD0AF12B3C08393C031DBA2BBC
:100760003530AE003D08A0000230A1005A25BD0082
:10077000BD0AF12B3C08053C031DC82B3630AE00EA
:100780003D08A0000230A1005A25BD00BD0AF12B92
:100790003C08113C031DD62B3730AE003D08A000AD
:1007A0000230A1005A25BD00BD0AF12B3C08093CCE
:1007B000031DE42B3830AE003D08A0000230A1003C
:1007C0005A25BD00BD0AF12B3C08173C031DF12B37
```

```
:1007D0003930AE003D08A0000230A1005A25BD000E
:1007E000BD0ABC012E08783C031DF72B3E150800FE
:1007F0007830AE003C08723C031D012C3030AE0056
:100800003F2C3C08663C031D082C3130AE003F2CC9
:100810003C08663C031D0F2C3230AE003F2C3C08D2
:10082000423C031D162C3330AE003F2C3C085C3C90
:10083000031D1D2C3430AE003F2C3C084E3C031DE4
:10084000242C3530AE003F2C3C08503C031D2B2C93
:100850003630AE003F2C3C08443C031D322C373070
:10086000AE003F2C3C08483C031D392C3830AE000C
:100870003F2C3C08743C031D3F2C3930AE00BC01BA
:1008800008007830AE003D08003C031D4A2C303093
:10089000AE00882C3D080B3C031D512C3130AE00BE
:1008A000882C3D080D3C031D582C3230AE00882C9E
:1008B0003D080E3C031D5F2C3330AE00882C3D08F4
:1008C000133C031D662C3430AE00882C3D08193CC7
:1008D000031D6D2C3530AE00882C3D081C3C031DDB
:1008E000742C3630AE00882C3D08153C031D7B2C43
:1008F0003730AE00882C3D08163C031D822C383062
:10090000AE00882C3D081A3C031D882C3930AE00FF
:100910008004108A000A1014308A0070318A10A8C
:100920004508A0070318A10A4408A0070318A10A51
:100930004908A0070318A10A4B08A0070318A10A39
:100940002008B8002108B9003808A0003908A10023
:100950002030A002031CA1030130A1022008B8002E
:100960002108B9003808A0003908A1000330A2000E
:10097000030A30068252008B8002108B900380815
:10098000A0003908A1004008A0070318A10A4208E6
:10099000A0070318A10A4408A0070318A10A4608E3
:1009A000A0070318A10A4808A0070318A10A4A08CB
:1009B000A0070318A10A2008B8002108B9003808C8
:1009C000A0003908A1002030A002031CA1030130BF
:1009D000A1022008B8002108B9003808A000390891
:1009E000A1000A30A2000030A30087252008B8002B
:1009F0002108B9003A30A00038082002AE002E08C5
:100A00003A3C031D052D3030AE0008000C1A092DAC
:100A1000062D2E08990008007830C0007830C100FB
:100A20007830C2007830C3007830C4007830C50018
:100A30007830C6007830C7007830C8007830C900F8
:100A40007830CA007830CB0008008316181583125E
:100A50004308316990018131812831298178316C2
:100A600098168312901610129010901110140430E2
:100A7000970005309D000130A000030A100200843
:100A8000B2002108B300B001B101BE010C2508007D
:100A9000AD012D08303C031C592D0130A00003061
:100AA000A1002D08A200A301D525AE000625AD0AA0
:100AB000492D0800A2010310A00C031C622D21087F
:100AC000A2070310A10D2008031D5B2D2208080BA
:100AD000A401A5010310A10CA00C031C762D220873
:100AE000A4070318A50A2308A5070310A20DA30D48
:100AF00020082104031D6A2D2408A0002508A10058
:100B0000080087252408A0002508A1000800A401EA
:100B1000A501220823040319B62D0130A600A70160
:100B2000A31B982D0310A60DA70DA20DA30D902DAC
:100B30002308210203199F2D031CAF2DA32D22088A
:100B40002002031CAF2D2208A002031CA1032308CE
:100B5000A1022608A4070318A50A2708A507031061
:100B6000A30CA20CA70CA60C031C982D08002108AE
:100B70002302031DBD2D20082202031CC22DA0014B
:100B8000A1010800FF38A000A100080023082102ED
:100B9000031DCC2D22082002031CD12A001A10190
:100BA0000800FF38A000A10008002008A2070319D0
:0C0BB000A10A210823078A002208820005
:02400E00020F9F
:00000001FF
```

# Is Linux for you?

If you design via CAD running under Windows, the chances are you've been frustrated by operating system crashes. Relatively speaking, Linux is very low cost, and according to Rod Cooper's experiences, it's well worth finding out how your favourite applications will run under it.



The fact that well-respected companies like IBM, Compaq and Dell now offer Linux as standard on their computers, and that large software companies like Oracle and Corel are producing applications for Linux means that this OS has to be taken seriously.

Linux is certainly worthy of attention by anyone using the PC professionally as a tool to do his/her job. One purpose of this review is to demonstrate to engineers not only that you can perform CAD, but also all the other tasks that might be incidental to an engineer's job, such as report writing, spreadsheets, databases etc.

The review does not attempt to describe how to run Linux – neither does it explain how Linux came about. You get all this information on the internet or from a Linux hand-book.

Linux is a product of the Internet, and indeed it would have been impossible for it to reach such a stage of prominence without it. If you have no Internet access you will be at a disadvantage. Alternatively though, there is general Linux literature on the market, and a few Linux magazines are now available.

## Background to Linux

When I briefly looked at Linux a few years ago it was a tough, command-line operating system with a well-deserved reputation for being difficult to install. It offered all the disadvantages of DOS with very few redeeming features. The thing that has changed Linux out of all recognition and boosted its popularity is the relatively recent addition of Windows-like GUIs.

Whereas Microsoft is busy trying to camouflage the DOS origins of Windows 9x, users of Linux are actually encouraged to step outside the GUI and use the command line and generally get involved in the nuts-and-bolts of the Linux system. However, if you want to, you can remain to a large

extent inside the cocoon of the Windows-like GUI and ignore this side of things.

## Reasons behind a swing to Linux

Although Linux is inexpensive compared to Windows, this alone is not sufficient reason to change over to it. The effort needed in the learning curve, and the time taken to convert machines over to Linux, and the cross-platform compatibility question, should make you examine your reasons for swapping to Linux most carefully. There are possibly many more reasons than those I have listed here, but I can see six main reasons why anyone should want to ditch Windows either partly or wholly, and contemplate taking up Linux. These six are as follows;

**1. Reliability.** One of the problems with Windows is that every release has been 'hyped'. The promise has been constantly held out to solve the existing problems in the newest, latest version, but purchasers have been left with a vague feeling of disappointment with every successive issue.

What purchasers actually got was lots of extra features, which tended to obscure the reality – that the basics, in particular the lack of reliability and security had not been attended to sufficiently.

A respected writer in a well-known IT publication commented recently that most of the crashes in Windows were caused by the operators themselves. This is probably quite correct. He then on to say that he only crashed Windows once a month. This speaks volumes. If an expert crashes once a month, what chance have the rest of us got?

Some of these inherent faults have been addressed in Windows 2000 – but not all. Potential users may be put off by the cost of Windows 2000 and the incompatibility with current Windows 9x software. It also demands more PC

## Running Windows applications under Linux

Using a virtual machine to run Windows is an old idea but it works well. It was used in IBM's OS2 Warp operating system. A copy of Windows 3.1 – called naturally enough Win-OS2 – was included with OS2 to cater for those who wanted to continue to use their existing Windows 3x applications, but who also wanted to use the superior OS2.

With OS2, a virtual DOS machine was created by OS2 on which Windows 3.1 ran. This version of Windows included the W32s extension for running 32bit applications.

There were considerable benefits to doing things this way. IBM claimed that OS2 could run Windows applications better than Windows itself – and it did. Stability was improved, and there was some crash protection.

There are commercial products that do the same trick for Linux and offer the same benefits. The two most well-known are VMWare and Win4Lin.

To use a virtual machine – or VM – you need a copy of Windows to install after you have installed the VM. The installation of a Linux VM and then Windows is very time-consuming and needs to be done carefully.

I found that installing VMWare in particular is not user-friendly. If you plan on using it I recommend a few months' practice with Linux first. VMWare can handle Windows 9x, NT and 2000 and costs \$299.

Win4Lin is tailored for Windows 95 and 98 and costs \$49.

### Using an emulator

The doppelganger approach has the potential to be the best system of all. But unfortunately it is not fully developed yet.

The idea behind Wine is that if an alternative Linux-based set of APIs – or Application Protocol Interfaces – was presented to a Windows application instead of the regular Microsoft APIs, then it could be fooled into accepting Linux as Windows.

As far as an application is concerned, an API making a call on Linux is just as good as an API making a similar call on Windows. This is a variation on the old saying that a nod is as good as a wink to a blind horse.

For this technique to work, a full set of Linux APIs is required. Here is the snag; the developers have only done around 90% of the equivalent Windows APIs. If an application needs one of the missing APIs, it is not possible to run it successfully. Although I would not recommend the current Wine for complete beginners, it only needs a basic grasp of Linux to have a go at it.

Wine is truly the key to the future popularity of Linux. It solves the dilemma under discussion completely. And because it's a non-commercial program, it's free.

resources, and it takes a lot of disk space. Not surprisingly, this has resulted in a less than complete take-up.

Microsoft's advertising suggests that Windows 2000 is now 50 times more reliable than Windows 9x, but how does this compare to Linux?

Bloor Research set up two servers, one running NT and the other Linux, and ran them under the same conditions for a year. Linux was stopped once, due to hard disk failure. NT crashed 26 times due to memory problems, a further 8 times due to file management and yet a further 33 times due to other problems. Most Windows users will be familiar with what these "other problems" were.

Windows 2000 of course uses the NT kernel. This begs an obvious question...

**2. Politics.** The political-legal rumpus between the USA's Dept of Justice and Microsoft has left a bad odour in its wake, and the wrangling is still not over. Linux is to all intents and purposes free.

**3. Immunity from viruses.** If you have been the victim of a virus attack via Windows, things are never quite the same again, especially if it was you who exposed your company and colleagues to such things as the Love Bug disaster.

It is easy to become a little paranoid about the virus menace. Linux has escaped lightly, but this is not, as some

detractors have stated, due to the lack of Linux users. Indeed, Linux is used by very many internet servers so it cannot be that! These detractors speak in ignorance. The fact is that Linux is inherently virus-resistant.

**4. Low cost.** Linux itself – or GNU Linux to give it its correct title – is essentially free. It is released under the 'General Public License' by the GNU foundation. A copy is also included in the handbooks provided with the various distributions. Among other things, the license attempts to guarantee that Linux cannot be easily hijacked by proprietary companies, so it is likely to endure.

The word "free" in this context is more a right to freely receive, modify and distribute the software than freedom from price. You can charge for this service if you want. A more accurate description for Linux would be "nearly free". Although you can download a version of Linux from the internet for nothing more than the cost of the call, assembling a version as good as the commercial versions is a mammoth task and definitely not for a beginner.

**5. Ability to modify.** Linux is not only nominally free, but includes the source code. This applies to many applications also, and means that, if you want to make modifications for a special usage,

you can. The scope this offers developers is immense and is in sharp contrast to the world of Windows, where Microsoft and the third party application companies keep their source code a closely guarded secret and charge for any development assistance.

**6. Fewer chores.** I personally don't like backing up frequently, or defragmenting the hard drive. Defragmenting a HDD may seem to some to be a relatively unimportant chore which only needs to be done once in a while, but as drives have got larger and software bloated out to match, it has become an ever more time-consuming process.

However, there are some PC activities in Windows that demand frequent defragmenting so you just can't get away from it. Writing CDs with a CD-burner is one example. Here, it is advisable to defragment before writing to an audio CD in order to get a clean recording, especially if you want to avoid the dreaded buffer under-run. The important thing to note here that Linux fragments very slowly, being essentially self-defragmenting, so needs very little attention in this respect.

## Potential snags to Linux

I should emphasise before you read this section that pointing out some of the snags of Linux is not an attempt at deni-

## Mandrake Linux 7

Produced by the French company MandrakeSoft,


Mandrake is a well-regarded distribution.

Despite being on just one CD, this version was a complete fully-functional Linux system with a large number of applications and utilities. Mandrake Linux is one of the versions you can get for £2.50 from The Linux Emporium, and as such is ideal for trying out a Linux system without committing yourself to buying the full distribution.

Version 7.0 is well worth consideration if you have a machine with 32 MB and RAM and do not want to upgrade with more RAM. It is a compact and useful Linux package.

Version 7.2 – the current version – is much enlarged, occupying seven CDs. It exhibits many small but regular incremental advances typical of Linux development – in contrast to Windows.

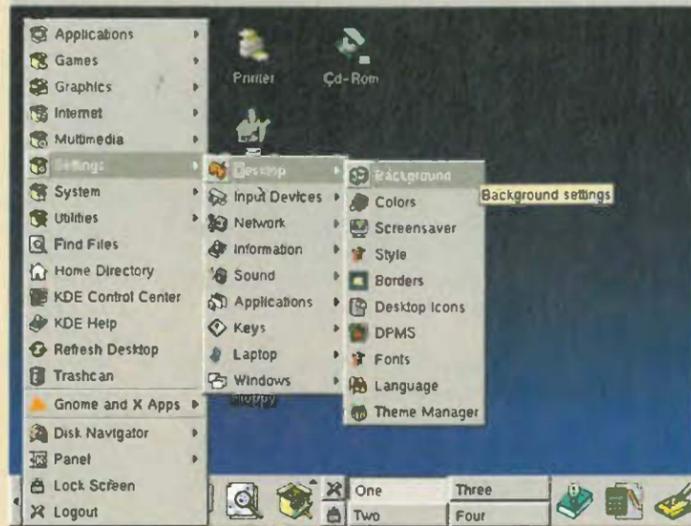For the beginner the main advantage of version 7.2 is provision of the large pool of applications. You will not have to supplement your installation by chasing all over the Internet for what you want – it's right there for you to pick. And if you want to try out voice operation then the availability of ViaVoice and StarOffice will certainly be of interest.



The cascading menu system works in just the same way as Windows although the contents may have unfamiliar names.

grating Linux, merely to present it in a 'warts and all' style so that a newcomer can come to an informed decision.

**Linux nomenclature.** Part of the problem of converting over to Linux is the jargon. Initially you will feel as though you are in a foreign land and cannot speak or understand the language. The impact of this should not be underestimated, but it is not an insuperable problem by any means.

No-one should consider themselves locked in to the Windows system just because the jargon in Linux is different.

The Linux community seems to revel in its own particular brand of jargon. Why, for example, does a program for zipping files have to be called 'tar'. Why not 'LinuxZip'\* which most people could understand? Does an installing program have to be called DrakX instead of LinuxInstall or Linstall?

The recursive acronym is popular. GNU stands for Gnu's Not Unix for example. The play on words and hidden reference is also often used. 'Bash' is not some useful program for terminating wayward applications, but a popular command shell – the equivalent of command.com in DOS – standing for Bourne Again Shell, after the Bourne shell in UNIX.

Similarly, you will be initially perplexed to be involved in such things as 'globbing', 'mounting' and of course 'unmounting'.

The jargon is so obtuse and there is so

much of it, that it is not a bad idea to get hold of a Linux glossary and keep it at hand during the initial learning process.

Understandably, Linux aficionados tend to be fiercely defensive of the system they helped create so nothing is likely to change in this area – you just have to go along with it.

**Hardware incompatibility.** Linux will run on PCs with the 386-type architecture, so almost any PC based on Intel or its clones can accommodate it. I tested it on an AMD-based PC and it ran well. I say almost any because some recent distributions of Linux, such as Mandrake and SuSe, are optimised for the Pentium processor.

It is still possible to run a version of these on an 'old' 486 but you need to be aware of the likely snags.

Although there is no significant problem with CPUs, there is a problem with certain peripherals because not many manufacturers write drivers for Linux. Windows has by far the largest number of drivers attributed to it.

Some manufacturers even appear to be stubbornly ignoring Linux, but this situation is changing. For example, Lexmark has just issued a colour printer driver for Linux – the first manufacturer to do so.

Nevertheless, there are long lists of drivers in Linux for printers, monitors, video cards etc and a good distribution of Linux will install without undue difficulty on a modern machine with plug-and-play peripherals, but there are areas

where care is still needed.

There is likely to be little or no difficulty with keyboards, mice, CD-ROMS, hard drives and the like. A Linux distribution such as SuSe will detect most plug-and-play devices, and the latest versions offer USB support. But ISA cards have to be manually configured.

You are unlikely to be completely blocked unless you have elderly devices or a new peripheral. For example, I came unstuck with my relatively new Samsung SF 4300, which is a scanner, colour printer and fax all in one. No driver here – not even on the remote horizon. Interestingly, there is no driver from Samsung for Windows 2000 either!

The big exception to the general rule is the area of modems, which is a veritable mine field. The reason for this is that unfortunately many modem manufacturers have succumbed to the Wintel monopoly and produced so-called Winmodems – sometimes called soft modems. These have very few components on the pcb, and rely on Windows software and to some extent use the PC's hardware instead of their own in order to function.

If you have a motherboard with a built-in modem, it is almost certain to be of this type. The advantage is one of cost – a Winmodem is comparatively cheap to manufacture because it is, in effect, only half a modem. The big snag is that the Winmodem takes a slice of the PC's resources when operating.

## SuSE Linux

SuSE Linux has won several awards for the high quality of its distribution. It also has much more printed documentation than its rivals, in the form of manuals, installation guide etc.


There are two versions, Personal at £25.99 and Professional at £44.99. The Pro version comes on six CDs and includes a huge amount of software covering almost everything you would want to do with a PC.

It will consume around 8 GB of hard disk space if you install it all. This is more software than most people will ever need, but some programs overlap, and some are mutually exclusive, so installing it all is unwise even if you have a big enough hard disk.

A DVD is included in the pack as an alternative installation medium, SuSE being the first Linux distribution to use this format. A floppy boot disk is also included, which is most useful if you find you can't boot from the CD-rom.

The Pro version includes software tools for developers and servers, video-conferencing, Java 2. Of course, by providing such a vast array, there will be many programs that you won't be interested in, but on the other hand there is bound to be something for everyone.

The Personal edition comes on just two CDs. Both Personal and Pro include the excellent StarOffice suite. SuSE Linux has an easy installation system, extensive documentation and a very large collection of Linux applications in its CDs. However, having a huge number of applications would be no good for the newcomer if he could not sort them all out, and it is here that SuSE excels with its install/uninstall and indexing system. The RAM requirements for running the graphical installer YAST2 may seem high, but even entry-level PCs now come with more than is

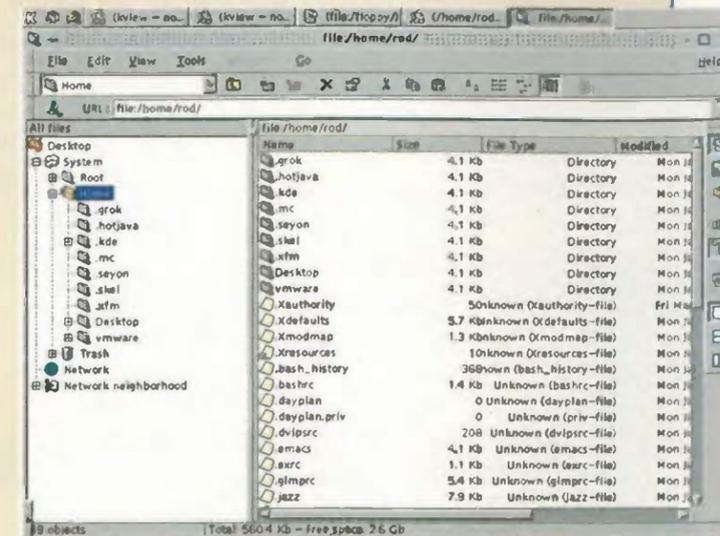

SuSE's equivalent to Windows Explorer. The directory tree should be familiar in style if not in content. Some of the files in the Home directory are displayed on the right hand side. Note that the panel bar has been rolled up to one side to increase usable screen area.

needed, so this is no longer such an issue.

The overall impression is that SuSE Linux is a well-presented, thoroughly designed and workable OS, and has the best selection of Linux applications.

At present, Linux cannot work with them. All this may change, since steps are being taken to remedy this situation. It is a good idea to firstly visit the web site [www.linmodems.org](http://www.linmodems.org) to get the latest information and then proceed with the link to <http://www.o2.net/~gromitk/html>, where, fortunately for beginners, there is a list of modems that do and do not work with Linux. Be warned this is a very long list.

I would not delay adopting Linux as an OS just because you have a software modem and need to replace it. In the overall context, replacing the modem is a small price to pay for adopting Linux. Just remind yourself about Linux's freedom from virus attack, for example, and the low cost, and the reliability.

If you decide to replace your modem, it is best to check with the sellers that it will indeed work with Linux, and that you can get a refund if it does not.

**Difficult to use.** There is no doubt that Linux used to be a computer buff's operating system. It was created by – and for the use of – those with a special interest in this field. I doubt if the rest of us mortals who use the computer for the mundane tasks like CAD, CAM and so

on were originally taken into consideration. The legacy of all this is that Linux is not a system that is as easy to use or as intuitive as Windows. But in the long term, I do not think this should not bother most PC-users who have already mastered Windows.

As an instance of this, when installing new software, there is no friendly 'Installshield' system. Each application in Linux seems to have its own method, and this can range from difficult to ghastly.

To take an example, Acrobat Reader is available for both Windows and Linux. In Windows, you insert the CD, start Explorer, access the file, start it with a double click, you read the agreement, and it needs just a couple of mouse clicks to install it into the chosen directory, clean and simple.

In Linux, you need to log in as root, mount the CD-ROM, start File Manager, access the file `linux-ar-405.tar.gz` and transfer it by drag-and-drop to a temporary folder on the hard disk, access the command line and hence the temporary folder, then type the gobbledegook `"tar xzf linux-ar-405.tar.gz"` at the command line. You then type `"cd /LINUXR.install"` and press enter. Then type `"/INSTALL"` and press enter to

start installation. Read the agreement, choose the directory, and you are finished.

**Incompatibilities within Linux.** There is broad compatibility between the various Linux kernels, and between the different distributions, but there are occasions when this is not true. Linux is under continual development so there are various kernels in circulation at any one time.

It is possible to up-date them, and this can be compared to up-dating Windows with a service pack. Kernels with an odd number tend to be versions under development and the even numbered ones like 2.2.14 are the ones to aim for.

In the short time I spent doing this review, I came across two incompatibilities. In one, a device driver, would not work because it demanded a kernel version earlier than the one I had. The second was with a program that would not work with the distribution I was using with at the time, which happened to be Mandrake Linux 7.0. It would, however, work with the others.

Occasionally, one program will not work without the presence of another one. These situations are called interdependencies and are frequently encountered.

## Corel Linux version 1.2

Corel Linux is easier to install and slightly more Windows-like than its rivals, and for these reasons is popular with newcomers to Linux.

Early releases of Corel-Linux came in for some criticism from reviewers because there were a few bugs and some errors of judgement about the interface. I am happy to say that these appear to have been put right in the second edition of Corel-Linux.

The OS installed smoothly and ran well on both test machines.

It must be pointed out that Corel-Linux is a lean distribution compared to SuSE and Mandrake. A typical Corel installation takes up about 600MByte, mainly because there are nowhere near as many applications provided with this distribution which consists of just one CD. Compare this with the six or seven CDs of SuSE and Mandrake. On the other hand, Corel Linux does not cost as much as these two.


This does not mean to say Corel have skimmed on the basic implications needed for smooth running of your system. There are still plenty of utilities and even a few games.

Although the two other Linux distributions mentioned in this article have GUIs that look uncannily like the Windows desktop layout at first glance, Corel has gone step further to make Linux just a little more Windows-like.

One thing acting in Corel's favour is the porting of its well-known and acclaimed Windows programs like Corel PhotoPaint, WordPerfect and CorelDraw over to Linux. This is a big advantage to those who already use these programs, because they can slip from Windows to Linux almost effortlessly.

Incidentally, Corel's PhotoPaint is offered free.

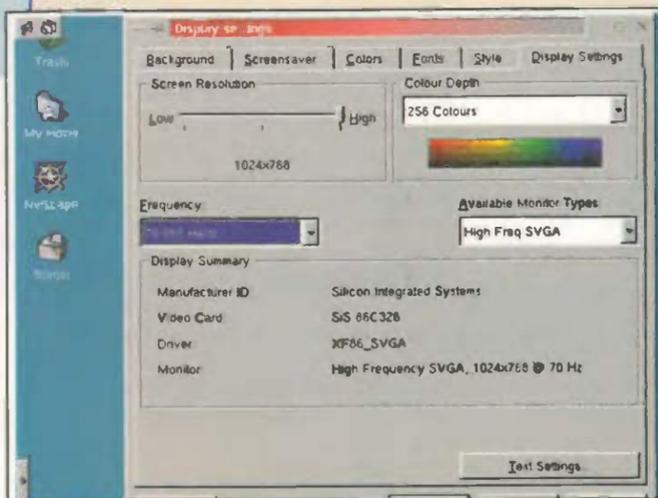*Setting up the resolution and refresh rate for large monitors for CAD can sometimes be tricky, but this window from Corel Linux shows how clear and simple it is with Corel Linux.*



Usually, a distribution will have sorted these out for you on installation and there is no problem. But sooner or later you will come across this snag. Finding and then installing the required program or file is not easy for the beginner.

Added to this little difficulty is the program that will not work until you delete another program already in the system. I had this trouble with Wine – the Windows emulator. The version from Codeweavers that I wanted to use would not co-exist with the version that came with the distribution and required it to be deleted manually before it would even attempt installation. A Windows application would most likely have up-graded automatically in this situation.

Another trend is that some programs are being described as 'Gnome compliant' for use with the Gnome desktop or 'KDE compliant' for use with KDE, implying a split within Linux into two camps. How far this trend will go is uncertain, and only time will tell.

### Too much choice?

One would not normally think of a surfeit of choice as a snag but as an advantage. In fact, the breadth of choice in Linux is often cited as something beneficial by those who promote Linux – shades of 'it's not a bug; it's a feature'!

To give just one example, having two

very similar desktop GUIs like KDE and Gnome for Linux, instead of one highly-developed one, seems such a waste of effort to the outside observer. They do, it is true, have a few different features and operate in slightly different ways, but this is re-inventing the wheel with a vengeance. There were good reasons for this split effort, and you can discover them if you dig about on the Web.

The excess of choice puts the beginner in a quandary. Which one should he or she go for? Learning how one desktop operates is fair enough – learning how two or three work seems like excessive effort to a Windows refugee. To include two or more desktops when you install Linux and invite users to alternate between them in order to use different features seems slightly crazy to anyone but a Linux fanatic – but this is exactly what some distributions do.

### Other snags

There are only a few other snags in Linux. For example, you may find no undelete feature. If you use the delete command it's gone for good.

If you are in 'root' and this file this happens to a system file, then you really are in a fix. It would probably mean re-installing your OS.

However, this is only true at the time of writing. Things are developing so

quickly in Linux that you may find it has been added by the time you read this. Other new features are also appearing rapidly, so if you require a particular feature, then you had better check the distribution you are interested in first.

Although the KDE and Gnome desktops are well designed, they do not yet have the spread of features that Windows has. For example, I missed the Windows Troubleshooters.

In Linux, there is plenty of advice on trouble-shooting, but I found few graphical tools to help to implement it. Linuxers tend to revert to the command-line.

### Books on Linux

As for books on Linux, there are hundreds, but locating them is not at all easy. I checked the computer book section at my local WH Smiths for example and although they had dozens of Windows books, there was not a single one on Linux.

PC World fared a little better with just one small shelf devoted to Linux. My local book store (Ottakars) did surprisingly well with a couple of dozen Linux books.

If you want real choice combined with short reviews from people who have read the books already though, Amazon.com is hard to beat.

If you are already a Windows user, you might look at Penfold's "Linux for Windows Users" but this is only a slim volume. If you like a graphical approach, and want a more substantial book then look at Bellomo's "Linux" from IDG. Although this is Red-Hat based and therefore Gnome-oriented, much of it is applicable to other systems.

### Summing up

Linux at present is not quite as intuitive, user-friendly or as GUI-oriented as Windows, but is not far behind and is making rapid progress.

I would hesitate to recommend it to all members of the PC-owning public as a complete replacement for Windows just yet. Those of you who use your PC

mainly as a games machine will be wasting your time; but those who use it to surf the Net will benefit from its security, engineers will benefit from its stability, scalability, flexibility – and everyone will benefit from Linux being nearly-free.

If you are fully conversant with the PC and Windows and appreciate what Linux has to offer, and are prepared to re-learn a certain amount, I think the advantages far outweigh the disadvantages.

If you are serious about finding an alternative to Windows, there is no significant reason to procrastinate on adopting Linux. Whether you can swap over partially or in full is to some extent dependent on what you do with your PC.

Windows may not disappear, but it would be most unlikely not to wane in the face of the Linux onslaught. This is not just because Linux is free and Windows expensive, but because you can in fact run Windows applications on Linux, effectively making Windows redundant.

There are various ways you can recycle your present collection of Windows applications in a Linux system using a virtual machine or a Windows emulator like Wine.

The best way to find out is through experimentation. Try using a caddy system for your hard drives and have a separate drive with Linux installed on it. An alternative is dual booting, but this can be confusing.

## Useful web addresses

- <http://www.linux.com>
  - <http://www.linux.org>
  - <http://www.linuxemporium.co.uk>
  - <http://www.winehq.com>
  - <http://www.codeweavers.com>
  - <http://www.freshmeat.net>
- Two websites giving general and comprehensive information about Linux. A good UK source of cheap and sometimes free Linux programs.
- Two sources of information about the Wine project. A source of Linux applications with a searchable database.

# Professional PCB Layout and Simulation for Windows at Computer Store Prices!!

From Only

**£97**

**Easy-PC for Windows 5**

*Easy-PC for Windows delivers world-beating PCB design performance, with levels of quality and pricing that is changing PCB Layout forever. Call us for a CD or download a demo version of this amazing product to be convinced.*

**A selection from the high value feature set..**

- ◆ True Windows 32 bit product with Windows Interface
- ◆ Integrated Schematics and Layout as standard
- ◆ Windows drag & drop throughout
- ◆ Multiple documents within display
- ◆ True Type fonts - new in release 5
- ◆ Mouse wheel controlled Zoom In/ Out - new in release 5
- ◆ Multi-level Undo/Redo
- ◆ Integrated standard AutoPlace
- ◆ Optional shape based AutoRouter
- ◆ Full Copper pour with Split Powerplanes
- ◆ Visualisation of inner power-planes - new in release 5
- ◆ Formattable Parts Lists / Pick & Place
- ◆ Unlimited signal/powerplane/non-electrical/doc layers
- ◆ Keep In/Out areas for routing
- ◆ Right-hand mouse menu support
- ◆ Full forward and backwards annotation SCM/PCB

.....and so much more!

For more information on Easy-PC/Easy-SPICE or for a demo copy call

Number One Systems on ++44 (0)1684 773662 fax ++44 (0)1684 773664 or

E-mail [info@numberone.com](mailto:info@numberone.com)

or you can download demo copies from [www.numberone.com](http://www.numberone.com)

Number One Systems, Oak Lane, Bredon, Tewkesbury, Glos, GL20 7LR

# Code-hopping remote control

Pei An has developed a highly secure wireless remote-control system based on Microchip's Keeloq code-hopping chips. One control receiver can recognise up to four transmitters, each with four push-buttons.

Remote control via RF is widely used in applications such as remote key entry system, alarm systems, gate and garage door openers and burglar detection systems. Conventional remote control systems offer limited security due to two shortcomings: a) the combination of

possible code combinations is relatively small. Using code grabbing and scanning techniques, an unauthorised person can easily override the security measures.

Microchip's Keeloq hopping code system has two outstanding features. The first one is that a 66-bit transmission code is used. There are  $7.3 \times 10^{19}$  combinations. This makes code scanning impossible to apply. Scanning at a rate of 8 times per second, it would take  $2.3 \times 10^{11}$  years to break the code.

The second feature is that during its working life, the receiver will probably never respond to the same code twice. If the remote control is used eight times a day, 22 years will pass before the receiver responds to the same code again. This renders a code grabber useless.

The present design uses a hopping-code encoder and decoder pair, namely the HCS301 and HCS512. In a system, up to four transmitters can be acknowledged by one receiver. For transmitting and receiving data, a UHF FM radio link from Radiometrix is used.

The system has a communication distance of 150 metres over open ground and 50 metres in building. Figure 1 illustrates the Keeloq remote control system.

## Hopping encoder

The HCS301, Fig. 2, has four inputs, labelled S0 to S3. Output PWM provides pulse width modulation and the -LED line connects to the cathode of a LED. When the HCS301 is activated, the LED illuminates. Pin functions are given in Table 1.

Once there is a change in status in S0 to S3 from logic 0 to 1, the HCS301 produces a 32-bit hopping code – i.e. encrypted data – generated by an encryption algorithm. It combines this with a 28-bit serial number, a 4-button press code and 2 status bits to create a 66-bit data stream. The last 34 bits can be either unencrypted or encrypted depending on user's setup. The serial data stream appears at the PWM pin, Fig. 3.

An 12-by-16-bit EEPROM inside the HCS301 holds an encryption key, device serial number, synchronisation counter and a configuration word. They are used by the encoder to create the 66-bit serial data. Contents of the EEPROM are programmed by a Keeloq programmer. The contents are read-protected.

Programmer software, which runs on a PC, asks users to input a 64-bit manufacturer's code and a 28-bit serial number. The two codes are then processed by a key-generation algorithm to create the 64-bit encoder key.

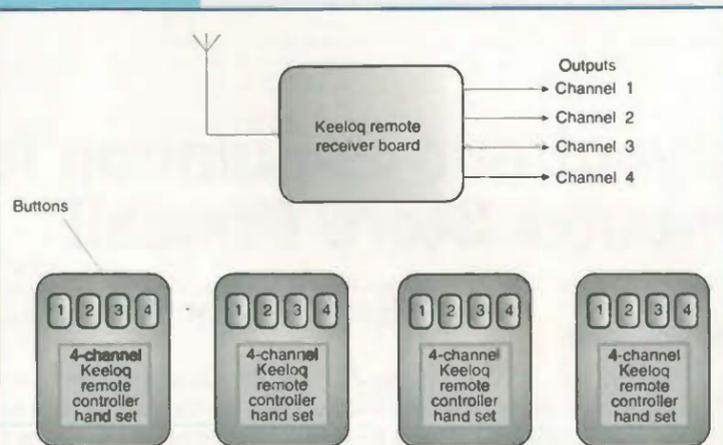


Fig. 1. The Keeloq radio-link remote controller contains up to four remote-control hand sets and one receiver.

the code they transmit is fixed and. b) the number of

Table 1

### Pin functions of HCS301 encoder.

Pin	Pin name	Description
1	S0	Switch input 0
2	S1	Switch input 1
3	S2	Switch input 2
4	S3	Switch input 3
5	VSS	Ground
6	PWM	Pulse-width modulation (PWM) output pin or data pin for programming mode
7	-LED	Cathode connection for directly driving -LED during transmission
8	VDD	Positive supply voltage (3.5V to 13V)

The encoder key and the serial number are programmed into the EEPROM, in Fig. 4.

Changes in the transmitted code for each transmission are based on a 16-bit synchronisation counter. The value in the counter is updated each time a button is pressed.

When the logic status of S0 to S3 lines change from 0 to 1, the encoder carries out an operation as shown in Fig. 5. The encoder key and synchronisation counter are processed by a Keeloq encryption algorithm to generate the 32-bit hopping code (encrypted data). Because of the complexity of the code-encryption algorithm, a change in one bit of the synchronisation value will result in a large change in the hopping code.

The data stream can be transmitted out in four speeds. Using a basic pulse width of  $400\mu\text{s}$ , representing the slow speed, a code transmission period is 108ms and the data transmission rate is 833bit/s. If the basic pulse width is  $100\mu\text{s}$  – the fastest speed – a complete code transmission takes 27ms.

Flow of the encoder's operation is shown in Fig. 6.

## Decoder details

The Microchip HCS512, Fig. 7, is a code-hopping decoder that is compatible with the HCS301 encoder. Table 2 shows its pin functions.

Before a transmitter can be used with a receiver, it must 'learn' the receiver. During learning, the serial

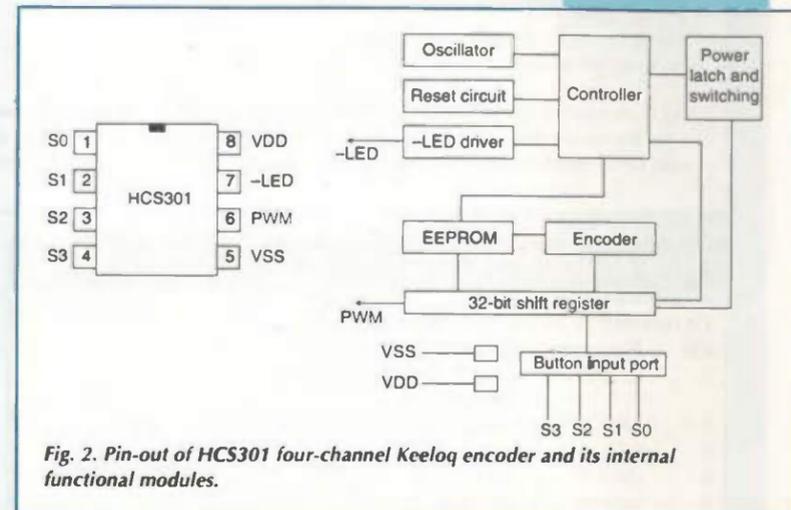


Fig. 2. Pin-out of HCS301 four-channel Keeloq encoder and its internal functional modules.

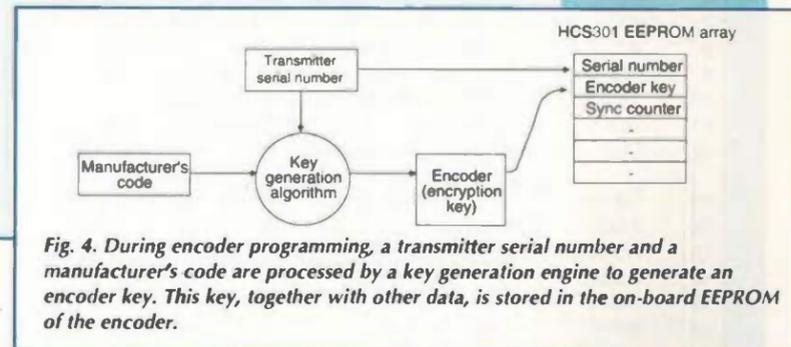


Fig. 4. During encoder programming, a transmitter serial number and a manufacturer's code are processed by a key generation engine to generate an encoder key. This key, together with other data, is stored in the on-board EEPROM of the encoder.


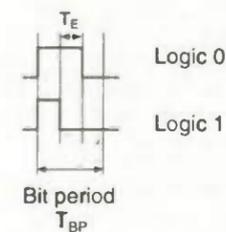
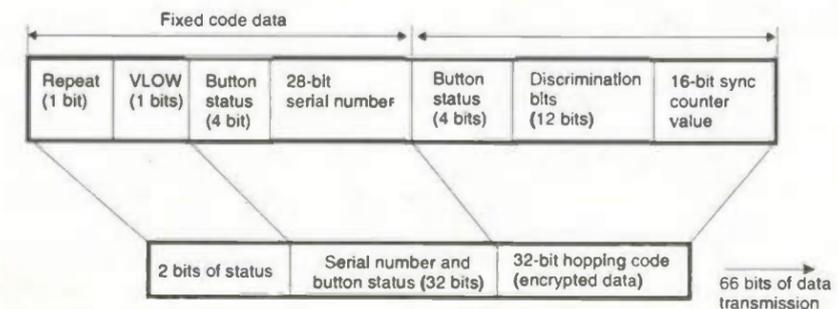


Fig. 3. The Keeloq encoder produces a serial data stream at its output after one of its inputs – S0 to S3 – changes status. The serial data contains a preamble, a header, a 32-bit encrypted portion and a 34-bit fixed portion.

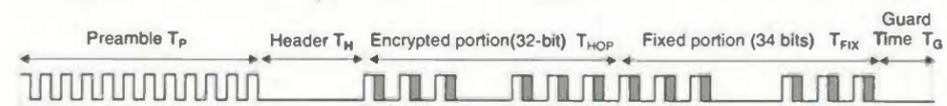

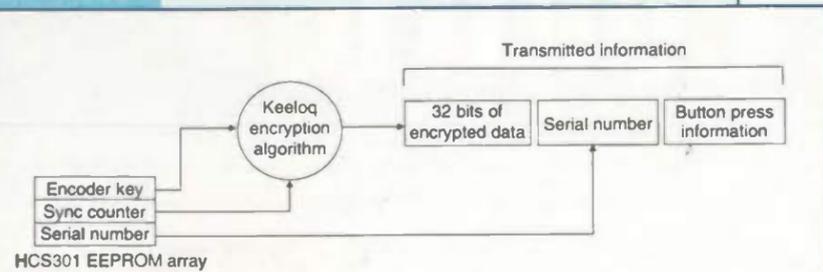


Fig. 5. In normal operation mode, the encoder key and the counter are processed by a Keeloq encryption engine to produce 32-bit encrypted data. These 32 bits, together with serial number and other information, form the 66 bits waiting for transmission.

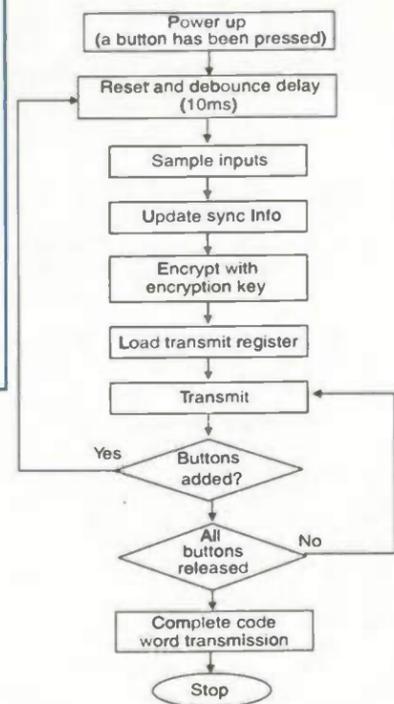


Fig. 6. Flowchart of the operation of the encoder.

If a decoder receives a message whose format is valid, the serial number is checked. If it is from a transmitter that has already been 'taught', the message is decrypted and the decrypted synchronisation counter is checked against what is stored for that transmitter. If the counter value is verified, the button status is loaded and status appears at S0 to S3, Fig. 8.

The decoder features a complex synchronisation technique to add security. If the stored counter value for a transmitter and the counter value that was just decrypted are within 16 of each other, the counter is stored and the command is executed.

If the counter value was not within 16, but is within 16 000, the synchronisation value is stored in a temporary location, and the system waits for another

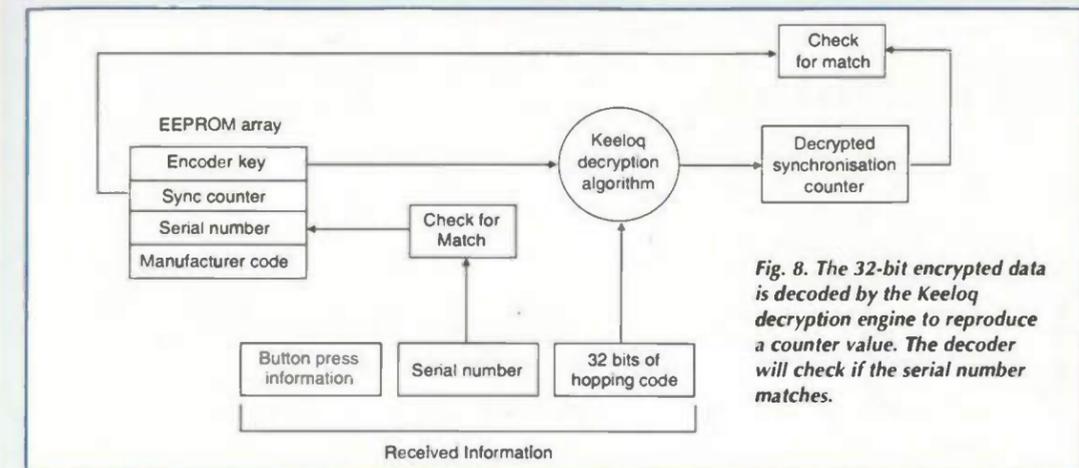


Fig. 8. The 32-bit encrypted data is decoded by the Keeloq decryption engine to reproduce a counter value. The decoder will check if the serial number matches.

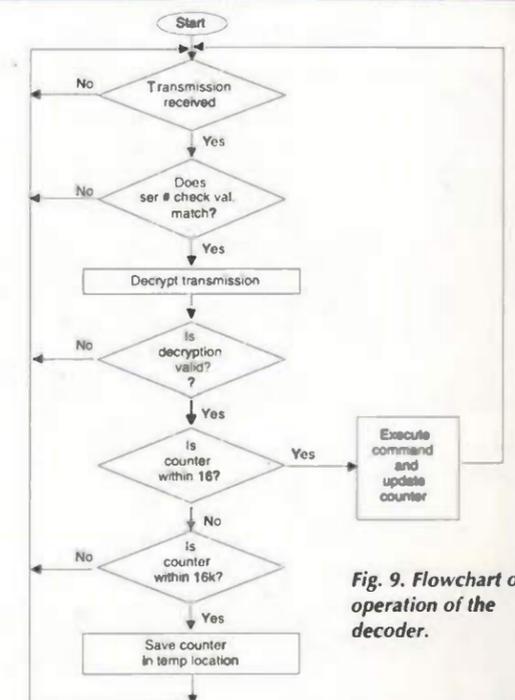


Fig. 9. Flowchart of the operation of the decoder.

transmission. When the next valid transmission is received, it checks the new value with the one in the temporary storage. If the two values are sequential, a new synchronisation starts up.

If the counter value was outside 16 000, the transmitter will not work and must be re-taught.

Flowchart of the decoder's operation is shown in Fig. 9.

#### Wireless Tx/Rx pair

Radiometrix' TX2 and RX2 UHF transmitter<sup>2</sup> and receiver are used for the wireless link, Fig. 10. The TX2 is a two-stage SAW-controlled FM UHF transmitter and RX2 is a double-conversion FM superhet UHF receiver. Both the TX2 and RX2 have two frequency versions: 418MHz for UK use and 433.92MHz for European use. They are type-approved to ETS300-200 and EMC conformant to ETS300-683.

Because the modules are type-approved, provided that they are used in the manufacturer's specified conditions with an appropriate antenna, the final products do not need further approval by radio authorities.

The transmitter/receiver combination is designed to transmit digital data up to 14kbit/s (A version) over a distance of 300 metres over open ground. The digital signal emanating from transmitter to receiver should have a mark-to-space ratio ranging from 20% to 80% averaged over 30ms (A version).

Table 2

#### Pin functions of the HCS512 decoder.

Pin	Pin name	Description
1	-LRNIN	Learn input, to initialise learning. 10kΩ pull-up required
2	LRNOUT	Learn output to indicate learning in progress
3	NC	
4	-MCLR	Master clear
5	Ground	Ground
6	S0	Switch input 0. Source 20mA and drain 25mA
7	S1	Switch input 1, Source 20mA and drain 25mA
8	S2	Switch input 2, Source 20mA and drain 25mA
9	S3	Switch input 3, Source 20mA and drain 25mA
10	Vlow	Transmitter battery low indication output
11	SLEEP	Connected to RFIN to allow wake-up from sleep
12	CLK	Clock in programming mode and in synchronous mode
13	DATA	Data in programming mode and in synchronous mode
14	VDD	Positive supply voltage (3.5V to 13V)
15	OSCout	Oscillator out
16	OSCin	Oscillator in (4MHz). R=10kΩ and C=10pF
17	NC	
18	RFIN	Serial data input from receiver

number, synchronisation counter and encoder key of the transmitter are stored in the EEPROM of the decoder. Up to four transmitters can be 'taught' by one receiver decoder.

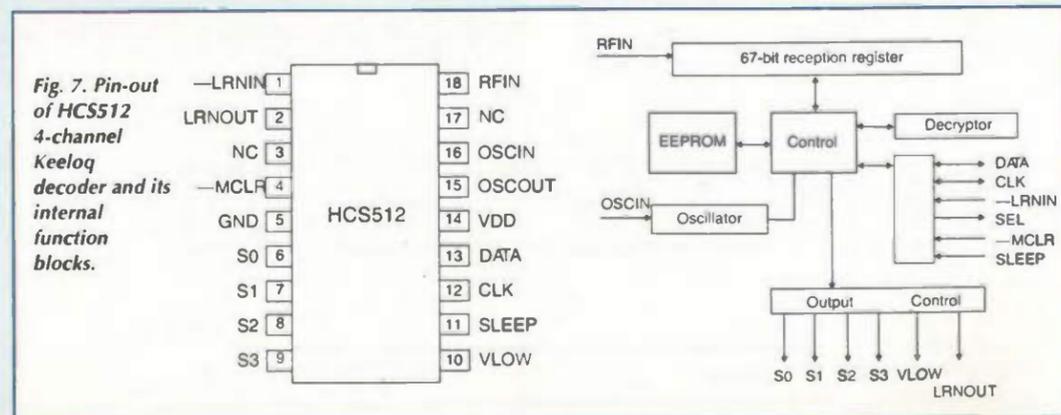


Fig. 7. Pin-out of HCS512 4-channel Keeloq decoder and its internal function blocks.



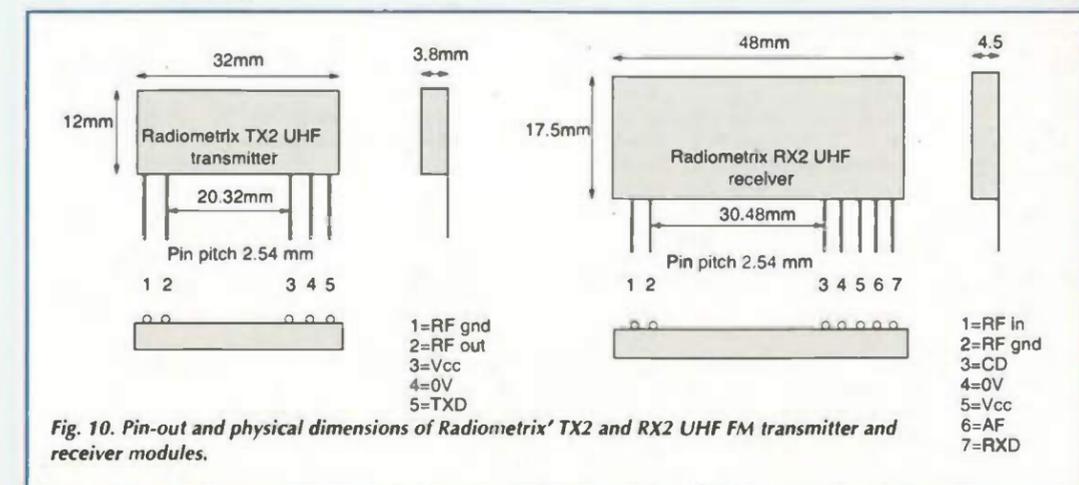


Fig. 10. Pin-out and physical dimensions of Radiometrix' TX2 and RX2 UHF FM transmitter and receiver modules.

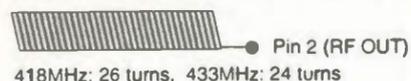
0.5 mm diameter enamelled copper wire close wound on 3.2mm dia former



a. Helical type

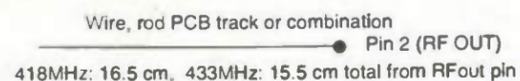

c. Whip type

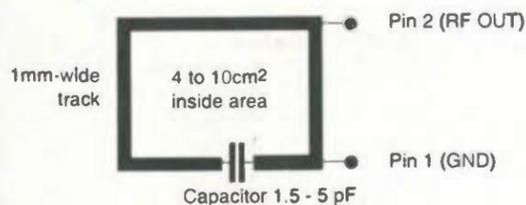

b. Loop type

Antenna performance chart	Helical	Loop	Whip
Ultimate performance	✓✓	✓	✓✓✓
Ease of set-up	✓✓	✓	✓✓✓
Size	✓✓✓	✓✓	✓
Immunity to proximity de-tuning	✓✓	✓✓✓	✓

Fig. 11. Three variants of antenna for the TX2 and RX2 modules.

The time between a data transition is from 0.07ms to 15ms (A version). If an equal mark and space square wave is transmitted from the transmitter to the receiver, the frequency of the signal should be within 6Hz to 7kHz (A version).

The antenna of the transmitter can have three versions: the helical type, the loop type and the whip type, Fig. 11. The helical option is the smallest. It needs to be optimised for the exact wavelength in use.

The loop antenna consists of a loop of PCB track,

which is tuned by a variable capacitor. The whip-type antenna is a wire, rod, PCB track or combinations. How the three types of antenna are constructed and a comparison of their performances are given in the diagram.

#### Circuit of transmitter

Figure 12 is the circuit diagram of the transmitter. Four press-to-make switches are connected to S0 to S3 of the HCS301.

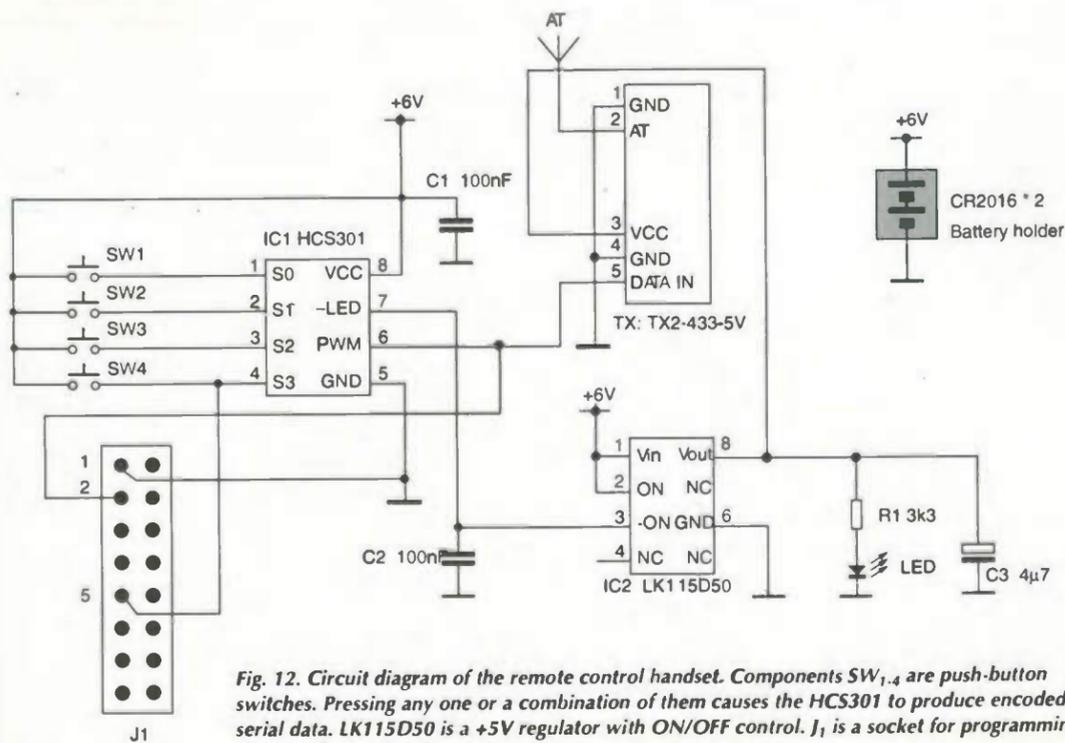


Fig. 12. Circuit diagram of the remote control handset. Components SW<sub>1-4</sub> are push-button switches. Pressing any one or a combination of them causes the HCS301 to produce encoded serial data. LK115D50 is a +5V regulator with ON/OFF control. J<sub>1</sub> is a socket for programming the encoder in-circuit.

Output -LED connects to the ON/OFF pin of a +5V LK115D50 regulator. During a code transmission, the -LED pin goes low, enabling the regulator to output +5V DC to the TX2 transmitter module.

Two CR2016 3V button cells are used to power up the system. The LK115D50 has a dropout voltage of 0.17V with a sleep mode current of 0.01µA and an operating current of 280µA.

A 16-way DIL pin header is used to connect to a Keeloq programmer via a ribbon cable. The antenna in the design is a whip-type.

The complete circuit can be constructed on a single-sided pcb and housed in a slim box with four buttons, Fig. 13.

#### Receiver circuitry

The circuit of the receiver is shown in Fig. 14. Six LEDs indicate the logic statuses of S0 to S3, learning mode and low voltage on the transmitter. Switch SW<sub>1</sub> is used to set the encoder to enter learning mode. The MCP809 supervisory IC generates a reset signal for the HCS512.

A low-power, low-dropout +5V voltage regulator, namely a TC55RP5002, is used to produce the +5V supply. Connector TP<sub>1</sub> is a 16-way DIL header for connecting the receiver to a Keeloq programmer via a ribbon cable.

In the prototype, the antenna for the receiver is a whip-type. The complete circuit can be constructed on a single-sided pcb, Fig. 13.

#### Programming the encoder/decoder

For my design, I used the programmer supplied with the Keeloq evaluation kit. This kit is designed to give the user the opportunity to evaluate the Keeloq code-hopping technique quickly and easily without having to make a large capital investment.

All the hardware and software necessary to implement a fully functional remote control system is contained in the evaluation kit. This kit also demonstrates all of the operating modes of the HCS301 and HCS501 and other chips.

Windows-based software included can be used to program encoders and decoders. The software requires you to input some information. Encoder key, configuration information and other user selectable information are automatically programmed into the encoder's and decoder's EEPROM.

The programmer can be used for programming the HCS chips in-circuit. During programming, the current encoder boards and decoder boards should be connected to the programmer via a ribbon cable, Fig. 15. Note that the power supply to the decoder board should be disconnected before programming. For the transmitter, there is no need to remove batteries before programming.

#### Using the system

A full system consists of a receiver and four remote-control key fobs. The HCS301 encoder and HCS512 decoder must be programmed first by the Keeloq programmer. Note that during encoder programming, a slow data rate is selected. Before a remote control system can fully operate, all key fobs must be 'taught' by the receiver one by one.

If a remote control is recognised by the receiver, the 'Learn' LED flashes. The output status of S0 to S3 does not change.

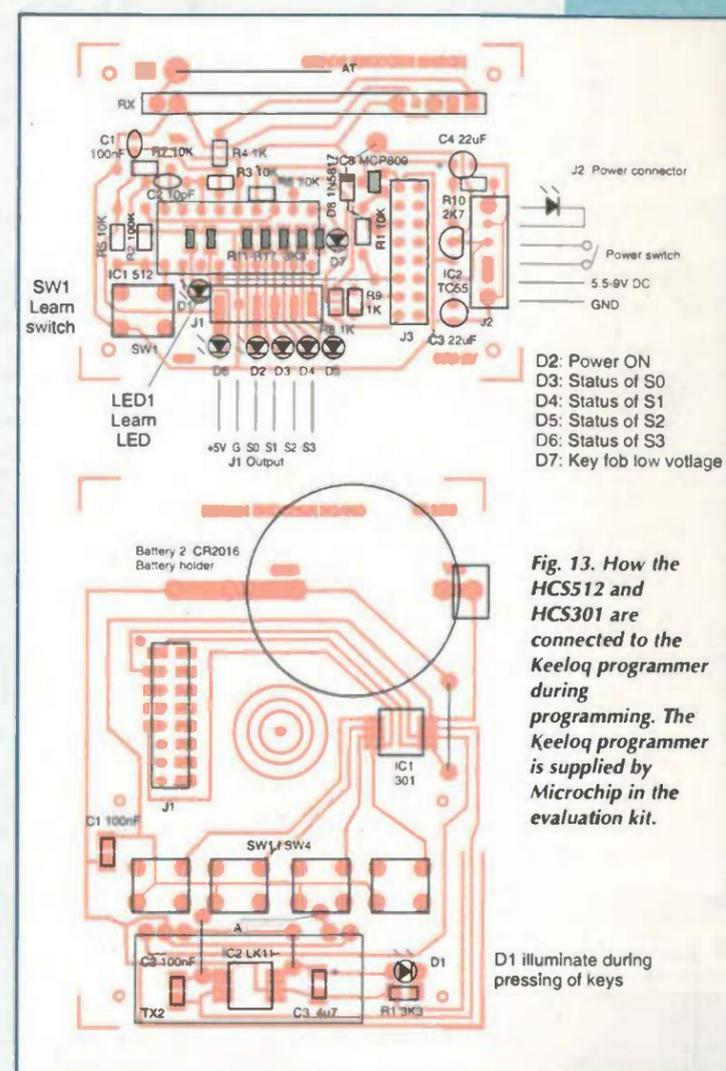


Fig. 13. How the HCS512 and HCS301 are connected to the Keeloq programmer during programming. The Keeloq programmer is supplied by Microchip in the evaluation kit.

#### Technical support

A designer's kit is available from the author. The kit includes PCBs and components. Please direct your enquiry to Dr Pei An by e-mail: pan@intec-group.co.uk or send a stamped s.a.e. to 'Keeloq', Electronics World, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ.

During learning, the 'Learn' process, the switch on the receiver is pressed first. The 'Learn' LED should illuminate. Next press any button on the remote-control key fob. The 'Learn' LED turns off.

Now press any button on the key fob again. The 'Learn' LED flashes for four seconds or so then turns off. This indicates that this particular key fob is properly 'taught'. If a button is pressed again, the status of S0 to S3 will change.

If the 'Learn' switch is pressed and held for more than eight seconds the receiver clears all the records in its memory. In this case, the 'Learn' LED illuminates and after eight seconds, it turns off. All remote control key fobs must be 'taught' again.

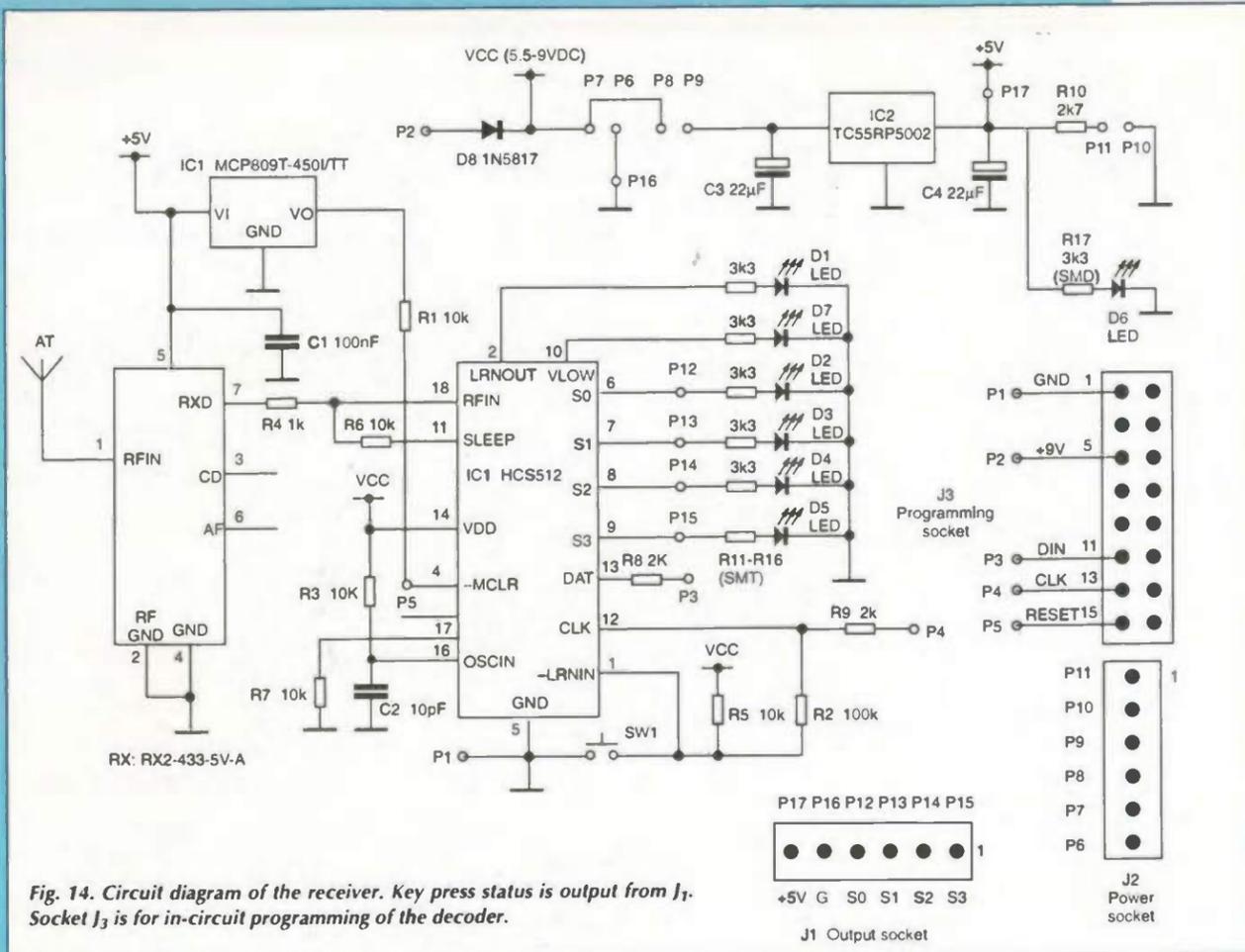


Fig. 14. Circuit diagram of the receiver. Key press status is output from J<sub>1</sub>. Socket J<sub>3</sub> is for in-circuit programming of the decoder.

NOTE: power disconnected from the board!!

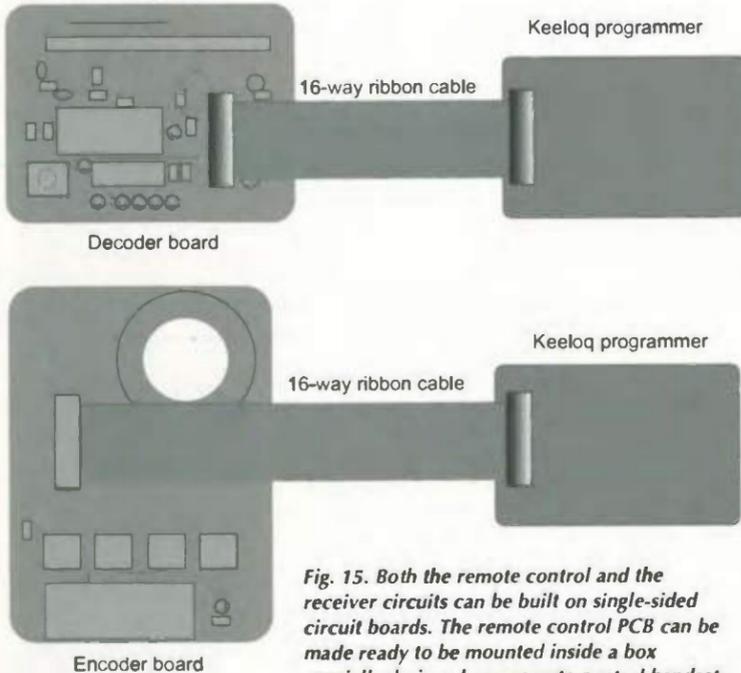


Fig. 15. Both the remote control and the receiver circuits can be built on single-sided circuit boards. The remote control PCB can be made ready to be mounted inside a box specially designed as a remote control handset, as are the PCBs supplied by the author.

### Expanding the system

Outputs from the HCS512 can drain 25mA and source 20mA and the voltage level is 0 to 5V. They can drive light loads such as relays or LEDs.

Using relays, power transistors, CMOS, smart PROFET, OptoCMOS or optically isolated solid-state relays, heavier loads or high voltage loads can be controlled.

### Acknowledgement

I would like to thank Mr Kangeyan from Radiometrix Ltd for his help on this design.

### References

- Secure data products handbook, Microchip, 1998, www.microchip.com
- Data sheets for TX2 and RX2 which are available from Radiometrix Ltd, 44(0)208 428 1220. Web site: www.radiometrix.co.uk

# Letters to the editor

Letters to "Electronics World" Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam Road, Surrey SM3 8BZ  
e-mail j.lowe@cumulusmedia.co.uk using subject heading 'Letters'.

## Phono preamp for the CD era

I am happy that there has been such interest in my circuit. I am somewhat surprised though given that it is 2001 and digital audio technology has overshadowed analogue audio.

Referring to the August issue, the letters from Mr Hall and Mr Tutt were greatly appreciated. There seems to be an unfortunate decline in civility in public discourse. It should be possible to be critical without being offensive. While it is disappointing to receive criticisms of one's work such as Mr Self offered, it would discourage me only if the criticisms reflected real design problems.

The phono preamplifier had already been in constant use in my system for almost one year when the article was published so I felt pretty confident that it was reliable as well as subjectively pleasing.

Mr Walt Jung gives a good example of how to craft a critical response without engendering offence. He also is absolutely correct. I erred when I stated that the design is entirely JFET.

I am astounded that I made this error since I taught this very topic before the article was written and had specifically presented the course textbook material from page 690 and figure 13.30 of 'Microelectronic Circuits' by Muhammad H. Rashid. There, it clearly indicates that one-half of the diff-amp gain comes from the left-hand side of the differential amplifier through the current mirror. A similar explanation can be found in many treatises on op amp design, some of which I had also read prior to the design of this preamp.

However, my error in explaining how the circuit operates in no way affects actual circuit operation. I, like Walt, have no problem with signals passing through BJTs in properly designed circuits. There is, however, almost a cult following for all-JFET or all-MOSFET circuitry and it had been my intent to have no signal pass through a BJT. This can be accomplished, by the way, in several different ways while retaining the folded-cascode single-stage op-amp topology. I have played around successfully with such modifications on breadboard. I did not pursue them because they did not significantly improve the objective performance of the circuit.

In the same issue, I do not know how

Mr Schick could conclude from my reply to Mr Self that I did not understand AN-346. My reply was based not only on my understanding of AN-346, but also of AN-104, aptly entitled "Noise Specs Confusing," which specifically addresses noise in a phono preamp. It uses the model for the Shure V15, Type III cartridge that is similar, although not identical, to my V15xMR.

Furthermore, William Chater in his article "A Mostly MOS Preamp," (*The Audio Amateur*, 1/90) lists the important noise sources that would have either the Type III or xMR cartridge resistance, itself, as the greatest single contributor to broadband noise. It was that article that prompted my statement that the cartridge was the biggest contributor to noise, a statement that apparently prompted this whole, largely unimportant flurry of comments and counter-comments.

However, it should be allowed by anyone discussing this subject that the input transistors, the cartridge resistance, or the 47kΩ resistor can be the biggest contributor. This depends upon whether or not one wants to factor in weighting curves based on hearing characteristics, cartridges with greater or lesser inductance and or resistance, particular BJT or FET input devices, etc. It also depends on whether one is talking about spot noise or broadband noise, and if broadband noise the specific band.

In any event, the title of my master's thesis was "A Method for the Determination of the High-Frequency Noise Spectrum of a Radio-Frequency Plasma." I probably do not need a tutorial on the subject of noise from either Mr Self or Mr Schick.

Perhaps my statement about PSpice inspired Mr Schick's comments. I was trying to be modest. I own five books on PSpice and have used it extensively for the last five years. There is nothing magical about PSpice; it does the same sort of circuit and network analysis that the human would do if the human could readily solve the often-unwieldy equations. While PSpice does occasionally fail to converge on a solution, I have found this to be unusual.

Also, I have never seen PSpice do anything "strange or unusual." In the case of the noise analysis that I did using PSpice, it showed the same increasing contribution of the 47kΩ resistor with frequency due to increasing reactance of the cartridge inductance that the analysis

## EAS - customer friendly?

Electronic Articles Surveillance (EAS) systems are being used in an increasing number of shops, department stores and libraries.

However, there has been very little discussion about the question of whether exposure to electromagnetic fields from this equipment might pose a health risk - particularly for vulnerable groups such as children and expectant mothers.

According to shops that use EAS, the manufacturers carry out measurements of the electromagnetic fields generated by their equipment - under laboratory conditions in which background sources of electromagnetic fields are eliminated - but the data is not shared with the companies that buy and install the equipment. Under these circumstances, one wonders whether the right balance is always reached between the security benefits of EAS technology and the need to limit people's exposure to electromagnetic fields in public areas.

Are some EAS systems more customer-friendly than others? What different technologies are involved and what is the strength of the electromagnetic fields emitted by these devices once they are actually installed?

Can any readers shed light on the subject or perhaps suggest which organisations or university research departments might have the answers?

**Name and address supplied**

in AN-104 showed and to which Mr. Self alluded.

While the program failed to predict the low-amplitude, high-frequency oscillation in the real second stage, a second look at PSpice simulation results showed a "peaking" in the response at that frequency. The very same value of capacitance that tamed the actual oscillation is the one that PSpice simulation showed to be required to eliminate the peaking.

Although I designed three successful power amplifiers bereft of access to PSpice, I would no longer go directly

## Global warming?

Regarding the solar cell story on page 496 of the July 2001 issue, on Earth, the solar power incidence per square metre is seldom much more than 1kW. Per square centimetre, this amounts to 100mW.

I'm amazed that one square centimetre of this new solar cell will deliver 10 watts at a temperature of 1000°C from this. Presumably, this cell needs to be placed closer to the sun, or under a focussing device, to achieve such figures.

**Michael Edinger**  
Via e-mail





# Designing with

# DSP

## Design your own DSP audio filter

In this fourth and final article on implementing and programming real-time digital-signal-processing systems Patrick Gaydecki describes how to produce a real-time audio filter based on the simple hardware discussed in the June issue.

**F**or those of you who haven't seen my previous articles, I have been using the DSP56002 to help explain how to design using DSP chips in general.

In this final article dealing with designing and programming DSP systems, I will be discussing how to configure the DSP56002. In particular, I will show how to initialise the phase-locked loop, the bus-control register – which controls memory access timing – the synchronous serial interface (SSI) for a-to-d and d-to-a converter communications and the serial communications interface (SCI) for communicating with a PC.

I will also look at how the simple system designed in the second article can be programmed to respond to interrupts, and how you can write software for real-time filtering of audio signals.

As discussed earlier, the DSP56002 has a register-based architecture, in common with most other processors of this type. Thus, to enable certain

### Design your own digital filter with no knowledge of maths?

Dr Gaydecki has developed a Windows-based application that allows you to design an audio-band filter on your PC and download it to the evaluation DSP system described in the second article in the series. If we get enough interest, we will look into the viability of producing PCBs and making the software available. E-mail [j.lowe@cumulusmedia.co.uk](mailto:j.lowe@cumulusmedia.co.uk) with the subject heading 'Interested in DSP'.

functions or configure the various sub-systems to operate in a particular way, appropriate words (bit patterns) must be loaded into the associated control registers.

All of the control registers are mapped into 'x-data' memory space, residing between locations X:\$FFDE and X:\$FFFF.

### Configuring the phase-locked loop


In the design covered in the second article, a control pin termed PINIT was tied low. This means that after reset, the PLL is disabled and the

DSP56002 operates at the externally applied clock frequency. Hence if the clock frequency is 10MHz, the device operates at 5 MIPS, since each instruction requires two clock cycles.

In order to take advantage of a higher MIPS rate, it is necessary to multiply the applied clock frequency; this is done by activating the internal PLL.

The PLL control register (PCTL) is a 24-bit register located at address X:\$FFFD. The bits are arranged as in Table 1.

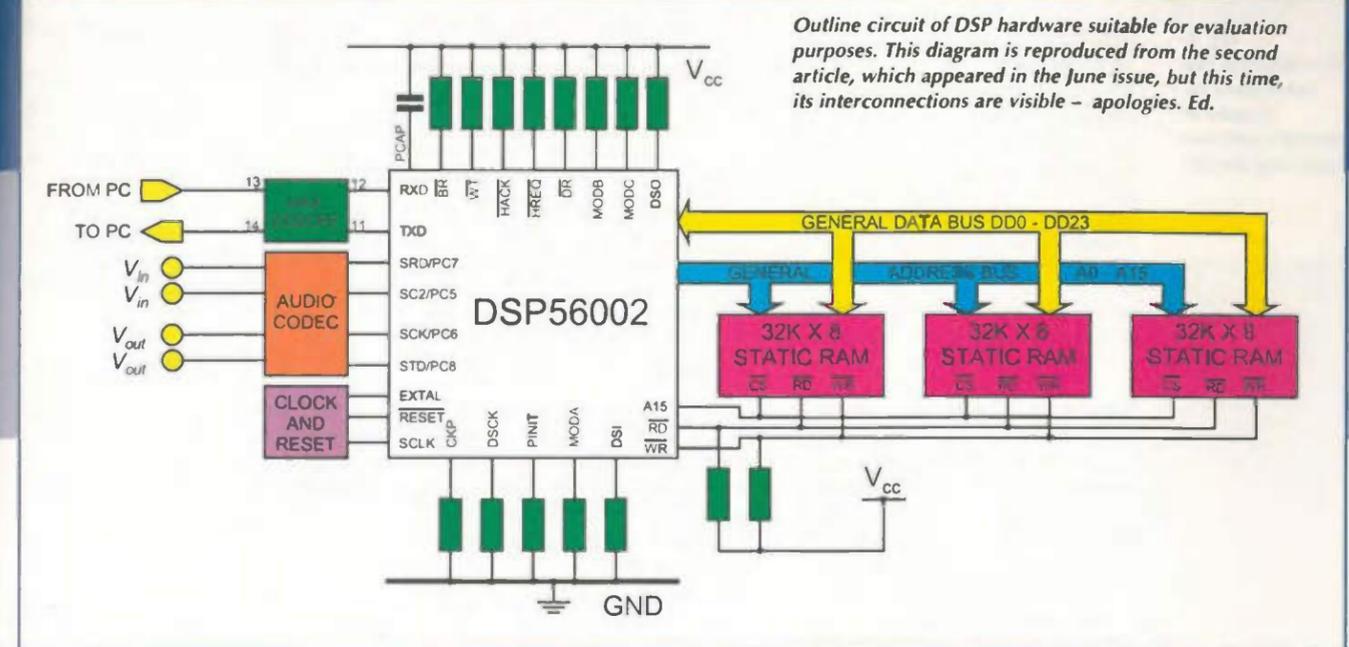Bits MF0-MF11 are loaded with a bit pattern that determines the multiplication factor (MF) applied to the clock frequency. A value of 0 specifies an MF of 1, a value of 1 gives an MF of 2, a value of 2 gives an MF of 3 and so on up to FFF<sub>16</sub>, which gives an MF of 4096. In Motorola parlance, the hexadecimal



Outline circuit of DSP hardware suitable for evaluation purposes. This diagram is reproduced from the second article, which appeared in the June issue, but this time, its interconnections are visible – apologies. Ed.

number FFF<sub>16</sub> would be written as \$FFF.

Similarly, bits DF0-DF3 determine the division factor (DF). A value of 0 specifies a DF of 2<sup>0</sup>, a value of 1 gives a DF of 2<sup>1</sup> and so on up to F<sub>16</sub>, which yields a DF of 2<sup>15</sup>.

The XTLD bit controls the on-chip oscillator output, XTAL. If the internal oscillator is not used, as in the design in question, the bit should be set, disabling the XTAL output. This minimises RF noise.

The PSTP bit determines whether or not the PLL and the on-chip oscillator operate when the DSP56002 is in a STOP processing state – i.e. suspended. This is normally cleared.

The PEN bit enables or disables the PLL. During reset, the logic level present on the PINIT pin is loaded into the PEN bit. After reset, the PINIT pin is ignored. Hence in this system, which is typical, the PLL is initially deactivated, and must be activated by setting PEN to 1.

Bits COD0-COD1 enable or disable the CKOUT pin, which is synchronised to the internal clock when the PLL is enabled. It is recommended that if this pin is not used, as in this case, it should be disabled by setting both bits to 1.

The value held in the CSRC bit

determines whether the clock signal for the core is taken from the output of the voltage-controlled oscillator, in which case it is logic 1, or the divider within the PLL, which is represented by logic 0. Here it is set to 0.

The value held in the CKOS bit determines the source of the clock signal for the CKOUT pin. When CKOS is logic 1, the clock source is the output of the voltage-controlled oscillator. If CKOS is logic 0, the clock source is the divider within the PLL. In this case, it is again set to 0.

As an example, if the externally applied clock frequency is 10MHz and you want an internal clock of 60MHz, i.e. an MF of 6 and a DF of 1, the bit pattern in Table 2 needs to be set.

In hexadecimal, the value in the table is 1D0005. The instruction:

```
MOVEP #1D0005,X:$FFFD
```

achieves the desired result of multiplying the internal clock frequency six times, yielding a processing speed of 30MIPS. For more details on the PLL, see reference 1.

### Access speed of the external memory bus

The DSP56002 can be configured to

Table 1. Bit functions of the DSP chip's PLL control register.

Bits	Mnemonic	Description
0-11	MF0-MF11	Multiplication factor bits
12-15	DF0-DF3	Division factor bits
16	XTLD	XTLD disable bit
17	PSTP	Processing state bit
18	PEN	PLL enable bit
19-20	COD0-COD1	Clock output disable bits
21	CSRC	Chip clock source bit
22	CKOS	CKOU clock source bit
23		Reserved; write as zero.

operate with memory chips of various speeds by inserting wait states during the access cycle of the external memory bus. If the WT pin is deasserted – i.e. tied to logic high, as in this case – then the number of wait states inserted is equal to the value held in the bus control register (BCR), located at X:\$FFFE.

Since the system in question has been designed with high-speed RAM with an access time of 10ns in accordance with the full-speed access cycle, no wait states are necessary. Thus the command:

```
MOVEP #0,X:$FFFE
```

ensures the external memory bus is

Table 2. Bit pattern in the PCTL register to obtain a 60MHz internal clock from a 10MHz external clock.


23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
0	0	0	1	1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1

Dr Patrick Gaydecki is a Senior Lecturer with the Department of Instrumentation and Analytical Science at UMIST in Manchester.

### Previous articles in this set...

- April 2001 issue – overview of DSP technology.
- June 2001 issue – interfacing a DSP with peripheral chips, features details of a simple, working DSP hardware system.
- July 2001 issue – programming and software issues.

Fig. 1. Synchronisation and data signals for transfer of information between a codec and the SSI.

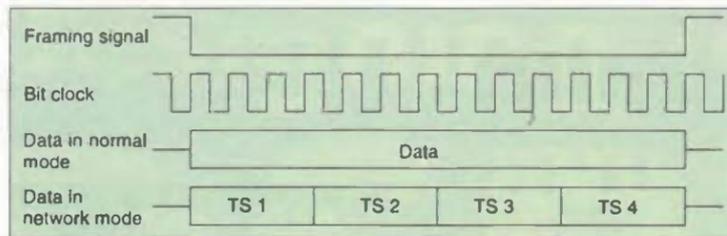

operating at full speed. For more details on bus wait states, see reference 2.

### Synchronous serial interface

As discussed in the second article, the a-to-d and d-to-a converters normally connect to the SSI of the DSP56002.

Two modes of communication are possible, namely 'normal' and 'network'. In normal mode, one datum word is sent by the a-to-d

converter to the DSP per frame, or to the d-to-a converter from the DSP.

This is the case for a single-channel system.

For a stereo or surround-sound system, multiple words are sent within a frame. Each word within a frame occupies what is termed a time slot. Figure 1 shows the signals required for normal and network mode operation.

Assume for the time being that the

a-to-d converter generates the framing and bit clock signals. These are fed both to the DSP56002 and the d-to-a converter. Again, this is typically the case. The DSP56002 is therefore said to be operating as a slave device.

It is important to bear in mind that, apart from the mode, data may be clocked into and out of the SSI using polled or interrupt-driven communication. For simplicity, I will consider a single-channel normal-mode system.

The SSI starts to read in the datum bits when it detects the leading edge of the framing signal. Each bit is read in synchrony with the bit clock.

Once a complete word has been read, bit 7 in the SSI status register (SSISR) is automatically set to 1. This is located at X:\$FFEE. This bit can either be continually tested – i.e. polled – or it can be used to trigger an interrupt. Either way, once it is set the DSP core can read the datum word into a core register or memory and start processing it.

To use the SSI for a-to-d and d-to-a communication, it must first be enabled as a synchronous interface, since it has a dual function. It may also operate as a general-purpose I/O port. Thus, the appropriate bits must be set in the port C control register (PCC), located at X:\$FFE1. In this case, the upper five bits must be set.

Next, it must be configured for a particular mode by loading the appropriate words into the SSI control registers A and B (CRA and CRB), located at X:\$FFEC and X:\$FFED respectively. The DSP56002 can be configured to accept data-converter word lengths of 8, 12, 16 or 24 bits. For normal-mode polled communication with 16-bit resolution in which the DSP56002 operates as a slave, bits are set as in Table 3. Hence,

$CRA=0100000000000000_2=4000_{16}$

and,

$CRB=0011001000000000_2=3200_{16}$

Listing 1 contains a code fragment that reads data in from the a-to-d converter and sends it straight out again to the d-to-a converter. Note how compact it is.

### Using the SCI receive interrupt

The listing shows how the system can take data from the a-to-d converter and then send it to the d-to-a converter. But since no interrupts are enabled, it is locked in an endless loop until the processor is reset or the

power removed.

By enabling the SCI receive interrupt, it is possible to communicate with the device through the serial port while it is running the program. You might want to do this if, for example, the program was performing some additional processing and you wanted to change the gain of the output data on the fly by sending commands through the SCI.

Principles of SCI interrupts were outlined at the end of my third article.

In order to enable the SCI interrupt, you need to do three things. First, set up the SCI control register (SCR) to generate an interrupt if a character is received. Also make sure it is set up for a standard protocol (e.g. 8 data bits, 1 start and stop bits). The SCR is located at X:\$FFF0.

Next, set the interrupt priority level in the interrupt priority register (IPR) located at X:\$FFFF. And finally, unmask the interrupt using the mode register (MR).

Without getting bogged down in too much detail, the first three instructions in the code fragment in Listing 2 accomplish these three tasks respectively. After this, you have the code to read and write a-to-d and d-to-a converter data as above.

If an SCI interrupt occurs, the program counter needs to know where to look for the interrupt service routine, so remember that you also need a

JSR mysub

instruction located at P:\$14. Look back at the third article for more details on this. After the main code, we have a label that indicates the start of the interrupt service routine. This must end with an RTI instruction. Code for this is in listing 2.

### Putting it all together – simple filtering

One of the most common applications of DSP devices is signal filtering. They are ideal for this, since digital filters really just involve a large number of multiplications, additions and shifts – operations they are very good at doing quickly.

Although the mathematics behind digital filters is beyond the scope of these articles, I can at least discuss the method by which these algorithms are implemented.

Real-time digital filters generally come in two flavours: finite-impulse response (FIR) and infinite-impulse response (IIR). Let's consider the first type. With FIR filters, the

incoming signal points are multiplied by a set of numbers – called taps or coefficients – and added together to produce one new, filtered, value. This process is repeated each time a new signal point is acquired.

The number of coefficients in the filter kernel varies widely – anywhere between 3 and 1023 is common,

depending on the filter required. For example, a simple five-point running mean filter would comprise five taps, each of value 0.2. This process is formally termed 'convolution'. Many textbooks have been dedicated to this subject – in particular, how to choose the values of the taps to generate a particular frequency response.

Listing 1. Simple a-to-d converter read and d-to-a converter write routine.

```
ORG P:$0
    MOVEP #1F0,X:$FFE1 ; SSI mode
    MOVEP #4000,X:$FFEC ; Configure CRA and CRB for 16-bit
    MOVEP #3200,X:$FFED ; data, normal mode
LOOP1 JCLR #7,X:$FFEE,LOOP1 ; Wait for 16-bit word from ADC
    CLR A
    MOVE X:$FFEF,A1 ; Read data into A
    MOVE A1,X:$FFEF ; Send to DAC
    JMP LOOP1
END
```

Listing 2. Code fragment showing enabled SCI receive interrupt.

```
MOVEP #0B02,X:$FFF0 ; Set up SCI and enable receive interrupt
MOVEP #0C000,X:$FFFF ; Set interrupt priority level in IPR
ANDI #SFC,MR ; Unmask interrupts in the Mode Register (MR)
MOVEP #1F0,X:$FFE1 ; SSI mode
MOVEP #4000,X:$FFEC ; Configure CRA and CRB for 16-bit
MOVEP #3200,X:$FFED ; data, normal mode
LOOP1 JCLR #7,X:$FFEE,LOOP1 ; Wait for 16-bit word from ADC
    CLR A
    MOVE X:$FFEF,A1 ; Read data into A
    MOVE A1,X:$FFEF ; Send to DAC
    JMP LOOP1
MYSUB MOVEP X:$FFF4,A2 ; Start of interrupt service routine. This reads
; one character from the SCI
RTI ; Return from subroutine
END
```

Listing 3. Complete algorithm for nine-point running mean filter in real time, incorporating full speed memory access and SCI interrupts. Code length does not change with increased filter length.

```
MOVEP #1D005,X:$FFFD ; Set up PLL
MOVEP #0,X:$FFFE ; Set up address bus: no wait states
MOVEP #0B02,X:$FFF0 ; Set up SCI and enable receive interrupt
MOVEP #0C000,X:$FFFF ; Set interrupt priority level in IPR
ANDI #SFC,MR ; Unmask interrupts in the Mode Register (MR)
MOVEP #1F0,X:$FFE1 ; SSI mode
MOVEP #4000,X:$FFEC ; Configure CRA and CRB for 16-bit
MOVEP #3200,X:$FFED ; data, normal mode
MOVE #0,1111,A0 ; Next 4 instructions load taps into memory
MOVE #0,R0
DO #9,FILL
    MOVE A0,Y:(R0)+
FILL
    MOVE #0,R0 ; Next 4 instructions set up modulo addressing
    MOVE #0,R4
    MOVE #8,M0
    MOVE #8,M4
LOOP JCLR #7,X:$FFEE,LOOP ; Get ADC data
    MOVEP X:$FFEF,X0
    CLR A X0,X:(R0)+ Y:(R4)+,Y0 ; Next 4 instructions perform the
filtering
    REP #8
    MAC X0,Y0,A X:(R0)+,X0 Y:(R4)+,Y0
    MACR X0,Y0,A (R0)-
    MOVE A,X:$FFEF ; Output the filtered data to the DAC
    JMP LOOP
END
```

Fig. 2. Software design interface for the Kemo KDF real-time digital filter system.

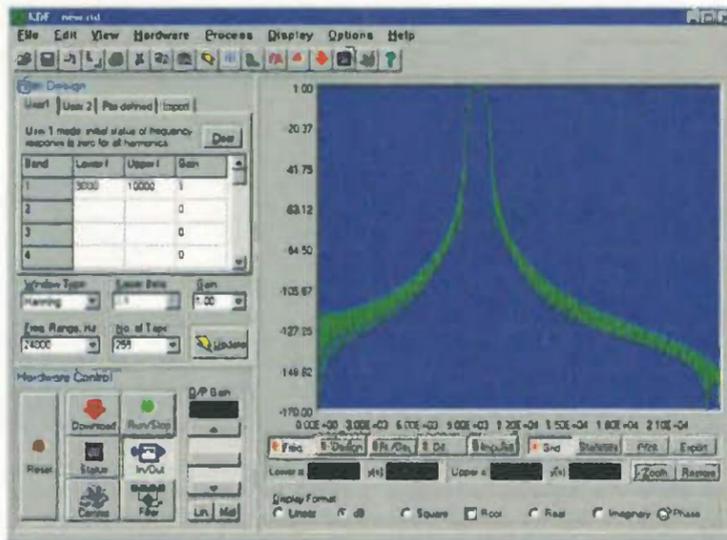


Table 3. With bits set as follows, the DSP56002 operates as a slave with normal-mode polled communication and 16-bit resolution.

CRA bits 0-7 (Pre-scale modulus): set to 0 (only used if DSP is master).  
 CRA bits 8-12 (DC): set to 0, since this is equal to the number of words per frame minus 1.  
 CRA bits 13-14 (WL0-WL1): set to 1 and 0, giving a word length of 16-bits.  
 CRA bit 15 (PSR): set to 0, as this is not needed in slave mode.

CRB bits 0-3: set to 0, as they are not used.  
 CRB bits 4-5: set to 0, as external frame and bit clocks are supplied by the ADC.  
 CRB bit 6: set to 0, as the MSB in/out is first and the LSB is last.  
 CRB bits 7-8: set to 0, as the WL bit clock is used for both TX/RX.  
 CRB bit 9: set to 1 for synchronous clock control.  
 CRB bit 10: set to 0 for continuous clock.  
 CRB bit 11: set to 0 for normal mode.  
 CRB bits 12-13: both set to 1 to enable RX and TX.  
 CRB bits 14-15: Not set here since interrupts are not required, i.e. polled-mode is used.

The convolution expression is given in mathematical terms as,

$$y[n] = \sum_{k=0}^{M-1} h[k]x[n-k]$$

where  $x[n]$  represents the input signal,  $y[n]$  represents the output signal,  $h[k]$  represents the filter kernel and  $M$  is the number of taps.

Digital signal processors perform one multiplication, addition and shift in one instruction. Hence simple arithmetic shows that at 30 MIPS, an audio signal sampled at 44.1kHz could be filtered using a kernel comprising up to 680 taps. A filter with this many taps can be designed with a sharpness far beyond what is normally possible with analogue types.

To implement filters using the DSP56002, a special kind of addressing termed *modulo addressing* is used. There's more on this in my third article. Code shown in Listing 3 implements a simple nine-point running mean filter. It also sets up the PLL, the external memory bus and

the SCI interrupt, in the manner discussed above.

For more information on filtering using the DSP56002, see reference 3.

#### Commercial DSP Filters

There is a huge range of DSP products on the market, intended both for the professional engineer and the amateur enthusiast. One such system is supplied by Kemo Ltd, called the KDF, specifically aimed at audio bandwidths.

This product incorporates a Windows-based software system for designing the filter, and a DSP hardware module that executes the filter in real-time. No knowledge of mathematics is required. Once the user is happy with the design, it can be sent to the hardware from the same package with the click of a button.

Figure 2 shows the design interface. The nice thing about the system is that completely arbitrary filter shapes can be specified, either using its design facility or by importing ASCII text files representing the frequency response.

#### In summary

We hope that this series of articles on DSP systems design and programming has been a useful introduction to the subject. DSP is a truly enormous branch of learning, and one of the fastest growing and most important technologies of our time.

Although the learning curve is a little steep to start with, the rewards, in terms of intellectual satisfaction, are well worth the effort. Happy experimenting!

#### References

1. 'DSP56002 Digital Signal Processor User's Manual', Motorola Inc., document DSP56002UM/AD, 1993.
2. 'DSP56000 Digital Signal Processor Family Manual', Motorola Inc., document DSP56KFAMUM/AD, 1995.
3. El-Sharkawy, 'Digital Signal Processing Applications with Motorola's DSP56002 Processor', pub. Prentice-Hall Inc., NJ, USA, 1996.

# NEW PRODUCTS

Please quote *Electronics World* when seeking further information

#### Ethernet and Internet connectivity demo kit

An Ethernet and Internet demonstration kit from Unique Memec includes a TCP/IP stack to enable embedded connectivity over industrial and appliance networks. The kit provides tools to explore and evaluate Microchip's various TCP/IP products. The heart of the Microchip Picdem Net kit is a demonstration board based on the 40-pin PIC16F877 flash microcontroller. TCP/ICP firmware is used for the network interface. After the initial setup of the IP and Ethernet address, performed via the RS232 port using a standard terminal program, engineers can choose to access the various functions of the board through a network or via the Internet. The board has Ethernet and RS232 interfaces. Engineers use a standard web browser, such as Netscape Navigator, to display inputs from the board (potentiometers and switches) and drive the LCD and control LEDs. Status indicators and user interface devices, including

a 16 by 2 LCD indicator and LEDs, are provided. The PIC16F877 device acts as a web server with the ability to serve HTML web pages. The kit also includes Microchip's MPLab integrated development environment, user's guides, category five Ethernet cable, DB9 serial cable and universal power supply.

Unique Memec  
Tel: 01296 397396  
www.unique.memec.com

#### Band-three TX for digital/analog TV

The NM and NW700 from Rohde & Schwarz are Band three transmitters for analogue and digital television. They use liquid cooling. The amplifiers have an integrated power supply, can be serviced during operation and are of modular design. The firm's real-time TV test receiver EFA comes in a 3HU chassis and can handle all terrestrial modulation for the US market. Operating in the VHF and UHF range, it demodulates digital (8VSB), analogue (M/NTSC) and US

cable (ITU-R J83/B) signals. Digital formats are analysed in real time and demodulated to MPEG2 transport streams via SMPTE310 or ASI serial interfaces. The M/NTSC standard is demodulated to video and audio baseband.

Rohde & Schwarz  
Tel: 0049 894129 11765  
www.unique.memec.com

#### Processors for VoDSL gateways

Texas Instruments has announced DSL communications processors for home and office routers and voice over DSL gateways. The integrated silicon and software chip sets use the firm's programmable DSP-based DSL physical layer, Telogy Software VoDSL products and the same broadband access communications processor architecture as TI's recently announced VoIP gateway and Docsis-ready, voice-over cable modems. Providing integrated support for wireless and wired networking standards, the AR5D00, AR5V10 and

AR5V20 help consumers network multiple PCs and Internet appliances, manage multiple Internet accounts and have access to entertainment and business services such as streaming video and audio, real-time video conferencing and virtual private network security. The AR5D00 is a chip set for home, Soho and SME routers. The AR5V10 chip set is for integrated access devices, residential gateways and Soho gateways to deliver up to four packetised voice lines and high-throughput data. The AR5V20 lets IADs and SME gateways support up to eight packetised voice channels. They support IEEE802.11, Wi-Fi, Bluetooth, Ethernet, IEEE1394, USB, Powerline and Home Phone Networking Alliance standards. All three support Linux turnkey communications processor software including a TCP/IP network stack with network management features or the VxWorks board support package.  
Texas Instruments  
Tel: 01604 663000  
www.ti.com

### The Phantom Power Box

48 volt microphone phantom powering unit  
Professional portable units operating from an internal  
PP3 battery or external mains adaptor



- ★ Suitable for converting any microphone amplifier to P48 standard phantom power
- ★ High efficiency DC to DC converter for extended battery life
- ★ Accurate line balance for high common mode rejection
- ★ Low noise and distortion
- ★ Extensive RFI protection

The Balance Box (mic/line amplifier) – The Headphone Amplifier Box – The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphook Hants GU30 7QW  
Information line: 01428 751469 Fax: 751223  
E-mail contact@confordelec.co.uk  
Web http://www.confordelec.co.uk/

CIRCLE NO. 113 ON REPLY CARD

## PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

- ▶ Prototypes at a fraction of the cost
- ▶ Tooling and setup included
- ▶ Any contour
- ▶ Fr4 1.6mm, 35µm Cu

- ▶ Industry standard quality
- ▶ Follow up series runs
- ▶ CAM / CAD consulting

PRICE EXAMPLE

**1 EUROCARD DSP1H**

+ Tooling

+ Photoplots

+ VAT

**= £ 29.89\***

\*Sterling rates may vary Price = € 49

**€49**

**FREE**

with first order

Freephone

**0800-389 8560**

Tel: +353 (0)47 701170  
Fax: +353 (0)47 701164  
E-Mail: sales@pcb-pool.com

Simply send your files and order ONLINE:


## WWW.PCB-POOL.COM

CIRCLE NO. 111 ON REPLY CARD
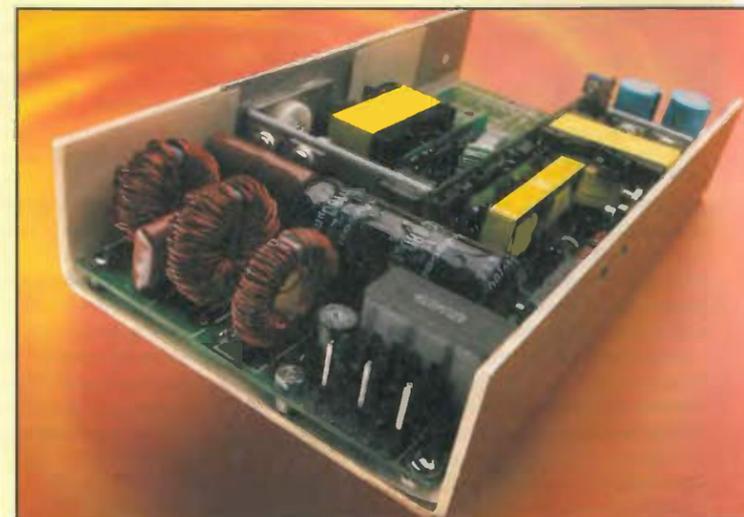
#### Single-output 48V supply delivers 300W

Digital Power has announced the EPower 300T single output, 48V supply that gives 300W from a 17.3 by 9.7 by 3.0cm package. Power density is 0.61 W/cm<sup>3</sup> and it is for use in telecoms systems. Efficiency is up to 85 per cent, achieved by using synchronous rectifiers. In this topography, conventional diode rectifiers have been replaced by MOSFETs, which are turned on and off synchronously with the power converter. Each MOSFET behaves like a diode, letting it conduct in only one direction, but with lower forward voltage drop and rectification losses. The components for the two main outputs are along each side of the chassis to provide cooling without additional, separate heat sinks. This also improves lengthwise airflow. It incorporates conventional input power factor correction and EMI line filtering circuitry. The PFC circuit provides a 90 to 250V AC universal input, and the design uses surface mount components and tantalum capacitors.

Digital Power  
Tel: 01722 413060  
www.greshampower.com



Please quote *Electronics World* when seeking further information

### Connector enables 5.0Gbit/s connection

Teradyne has announced a six-row version of its VHDM high-speed differential connector. It will support point-to-point backplane connections up to 5.0Gbit/s. Applications include Sonet OC-48, OC-192 and OC-768 systems, 10Gbit/s Ethernet, terabit routers, optical networking equipment, servers and data storage systems. The connector uses an orthogonal in-line grid rather than a staggered grid, allowing for traces up to 10mm wide and letting traces run through the connector without jogs.

*Teradyne*  
Tel: 01344 426899  
www.teradyne.com

### Analogue output photocoupler

NEC Electronics' PS8601 eight-pin photocoupler provides a maximum supply voltage of 35V, response of 0.8µs and isolation voltage of 5kV rms. The single chip photocoupler contains a GaAlAs LED on the input side and a p-n photodiode and amplifier transistor on the output side. Applications



include interface circuits for instrumentation, control equipment, computer and peripheral manufacturing and electrical isolation of TV video terminals. Allowing voltage peaks up to 8kV, it has an operating temperature between -55 and +100°C. It is available in two packages – plastic DIP or as the PS8601L in a lead bending Gull-wing type for surface mount.

*NEC*  
Tel: 01908 691133  
www.euk.nec.co.uk

### Gigabit Ethernet core for copper and fibre

LSI Logic has introduced a Gigabit Ethernet core for use in copper and fibre networks. The E1110 core is a 10/100/1000baseT Ethernet media access controller. It can support applications from 10 to 1000Mbit/s on one platform and suits embedded applications including switches, routers, servers and desktop computers. A programmable 10, 100 and 1000Mbit/s data rate option supports data transfer of Jumbo frames up to 10000bytes.

*LSI Logic*  
Tel: 00 1 408 433 8000  
www.lsillogic.com

### IR receiver resists the light


An infra-red receiver module with an internal automatic gain control to increase immunity against light disturbances caused by energy-saving lamps has been announced by Vishay Intertechnology. The Telefunken TSOP700 combines

a photodetector and preamplifier in one package. It has a 455kHz carrier frequency and is for use in multimedia products and applications, including interactive TV, video conferencing systems, game controllers, interactive toys, wireless keyboards, wireless mice and remote controls. The receiver can handle up to 20kbit/s at a transmission distance of up to 20m. With an internal band filter, it is for PCM frequencies and provides TTL and CMOS compatibility. Power consumption is 10mW and it can operate from supply voltages from 2.7 to 5.5V. Rated for temperatures between -25 and +85°C, the device provides an output current of 5mA, with a demodulated output signal that can be directly decoded by a microprocessor. It measures 6 by 8.25 by 5.6mm. Receiver start-up time is 50µs and receiver data delay time 18µs.

*Vishay*  
Tel: 00 1 610 644 1300  
www.vishay.com
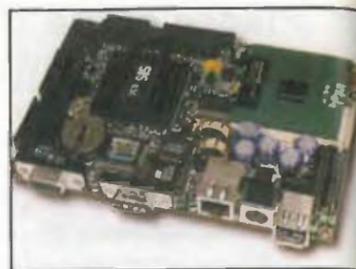
### SBC for embedded multimedia

Diamond Point has launched the Inside Technology 786LCD/3.5 single board computer in 8.9cm format. Incorporating an integrated SiS 630 chip set with hardware accelerated MPEG-2 and DVD decoding to support high-end embedded multimedia applications, the board integrates Intel socket 370 Pentium III and Celeron processors and a 128-bit 2D and 3D hardware accelerated



graphics controller with up to 64Mbyte of shared video memory. The controller can drive flat panel plasma, TFT LCD and CRT displays at a resolution of 1920 by 1200 in 16 million colours. Optional graphics modules, including Panellink, LVDS, 50-pin LCDconnect and DVI TV-out including CRT2 and S-Video composite (Pal and NTSC) are available, with a Soundblaster Pro 16 compatible virtual AC-3 surround sound SPDIF 4Mbit/s IrDA infra-red communications module. For PC/104+ and ISA bus access, the board is powered by an onboard lithium battery. Connection for an external battery is also provided. A 10/100baseT Fast Ethernet port, two NS16C550 RS232 serial ports with 16byte Fifo buffer, bidirectional Centronics port offering ECP or EPP mode and five-channel USB port are provided.

*Diamond Point*  
Tel: 01634 722390  
www.dpie.com

### Dual clock oscillator has six operational modes

National Semiconductor has announced an 8-bit Cop8flash microcontroller with multiple power save operating modes.

With two on-chip oscillators and six operating modes, the device can monitor a system's environment, including temperature, humidity, voltage, current, pressure and power. This makes it suitable for analogue sensor applications in white goods, security systems, information appliances and mobile phones. It can also be used in personal access device touch screens and applications requiring power management, user interface, LCD brightness and contrast control, and battery charging. It consumes dynamic currents at 3.0V from 24µA to 3.3mA. The product has 32kbyte of on-chip flash and a six-channel, 10-bit a-to-d with an input filter path and multiplexer output. With its filter path, the device's integrated 10-bit successive approximation analogue-to-digital converter lets designers insert external circuitry, such as a low-pass filter, between the 16 input-channel analogue multiplexer's output and the direct a-to-d input.

*National Semiconductor*  
Tel: 01870 2402171  
www.national.com

### 8-bit embedded applications get Ethernet reference

For embedded applications using 8-bit microcontrollers, a reference design from Triscend allows Ethernet connectivity. Based on the company's E5 configurable system-on-chip device, the design uses two chips. It combines an accelerated 80C51 microcontroller core, capable of delivering 10Mips, with embedded programmable logic, and uses the CS8900A Ethernet Mac phy from Cirrus Logic and the CMX-Micronet TCP/IP stack from CMX Systems.

*Triscend*  
Tel: 01628 681565  
www.triscend.com

### Linear address range to 16Mbyte

Philips Semiconductors has announced the 87C51Mx2 microcontroller family including an 8-bit 80C51 supporting up to


Please quote *Electronics World* when seeking further information

### Multiport RJ-45 connectors

Pulse has announced the Pulsejack Harmonica family of multiport RJ-45 connectors with integrated magnetics. Developed with Tyco Electronics, the two-tier-stacked eight, 12 and 16-port connectors provide isolation and EMI suppression for 10/100baseT computer and telecoms networks. The two-by-four eight-port J2042H3A, two-by-six 12-port J2045H3B and

two-by-eight 16-port J2039H3C connectors use the firm's Interlock base construction that reduces the stresses of human handling of subcomponents such as coils, leads and connecting wires.

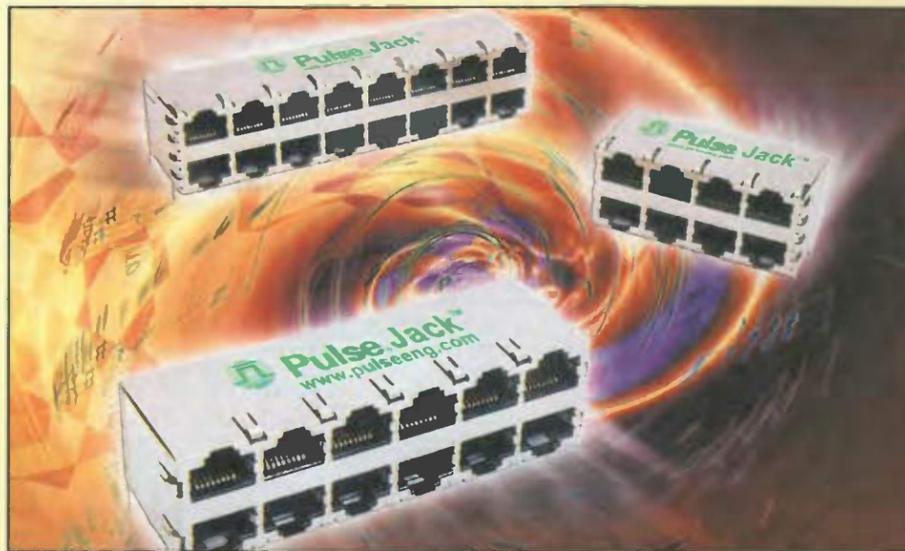*Pulse*  
Tel: 01483 401700  
www.pulseeng.com



16Mbyte of on-chip linear addressable memory for communications and consumer markets. The microcontrollers are based on the firm's 51Mx core, claimed to combine an increase in on-chip program and data memory with high-level C language performance. Binary object code compatibility is maintained, so engineers can reuse existing 80C51 codes. The architecture also retains 80C51 bus compatibility to allow reuse of peripherals and Asics. The 51Mx's 23-bit linear address supports up to 16Mbyte of on or off-chip program and data memory. The program counter is extended to 23-bit and the stack pointer to 16-bit. A 23-bit extended data pointer, with two 24-bit universal pointers using existing general purpose registers, creates a 16Mbyte linear address range for C compilers. The 87C51MC2 comes with 96kbyte of OTP memory and 3kbyte of RAM and the 87C51MB2 with 64kbyte of OTP and 2kbyte of RAM. Both operate with supply

voltages from 2.7 to 5.5V and run at up to 24MHz (5V) with a typical instruction cycle time of 250ns.

*Philips Semiconductor*  
Tel: 00 31 40 272 2091  
www.semiconductor.philips.com

### Audio d-to-a converter for CD players

Wolfson's stereo digital-analogue conversion technology is at the heart of two CD players from Rega Research. Sounds from the Rega Planet 2000 and Jupiter models depend on ICs based on the WM8716 multi-bit, 192kHz stereo d-to-a converter using a sigma-delta conversion technique to improve signal-noise performance and reduce clock jitter effects.

*Wolfson*  
Tel: 0131 6679386  
www.wolfson.com

### Modular DSPs use FPGAs

Hunt Engineering has extended its Heron range of modular

products for DSP with versions that use Xilinx FPGAs for DSP processing and flexible I/O. They let digital radio users remove an IF stage from their system by digitising directly at 100MHz and performing digital down conversion in the FPGA. When fitted to a Heron module carrier such as the HEPC8 PCI card, they can have their program downloaded from the PC over the serial bus. This lets users program and reprogram them as they would with the DSP elements of the system. There are three modules with FPGAs, each 10.16 by 6.35cm. The FPGA1 covers Virtex gate counts between 50k and 200k gates and the FPGA2 Virtex devices between 400k and one million gates. The IO1 combines a Spartan II FPGA with 200k gates with two channels of 105MS/s 12-bit A/D. Each input has a separately controllable programmable gain stage. The Spartan II FPGAs module allows the use of Xilinx Webpack development tools. The modules that use the Virtex



### Smartcard connector avoids PCB redesign

By encapsulating its L26 smartcard connector in a metal casing and adding a flexible printed circuit cable, FCI has introduced a panel mounted smartcard connector that lets OEMs upgrade equipment fascias without modifying PCB layouts. With its one piece construction, the Z00 connector comes with a choice of flexible printed circuit cables between 58 and 155mm long. Two connector bodies are available, handling card penetration depths of 25 and 35mm from card edge to panel surface. Card

detection is via an integral normally closed, self-cleaning, wiping blade switch. Providing a choice of eight or 16 sliding contacts, the connector meets ISO7816 and Afnor LTE93421 standards. With the option of in-line capacitors, the flexible printed circuit cable complies with Europe Master Visa recommendations on signal integrity. The cable termination pitch can be either 1 or 1.25mm.

*Digital Power*  
Tel: 01722 413060  
www.greshampower.com

**NEWPRODUCTS**

Please quote **Electronics World** when seeking further information


and Virtex II FPGAs have more gate densities and features, but require the Foundation, Foundation ISE or Xilinx Simulink System Generator, which must be licensed from Xilinx. In the licensed software, Xilinx includes IP cores for DSP for configuring FFTs, correlators and filters. **Hunt Engineering**  
Tel: 01278 760188  
www.hunteng.com

**TFT LCD industrial panel PC**

Advanced Modular Computers has launched the AMC-5030, a 38cm TFT LCD panel mount PC with a maximum resolution of 1024 by 768. Its aluminium front panel meets Nema 4 or IP65 standards. It can handle temperatures up to 50°C and non-condensing humidity levels up to 85 per cent. The model comes with a 90W power supply, three drive bays and the POS-566 socket seven card with processing speeds up to 100MHz. Onboard features include VGA with 2Mbyte EDO RAM, audio, 10/100Mbit/s Ethernet controller, digital I/O and one disk-on-chip socket. Dimensions are 395 by 277 by 141.2mm. A Dynapro resistive touch type screen is an option, bypassing requirements for a separate keyboard. **AM Computers**  
Tel: 01753 580660  
www.amculc.com

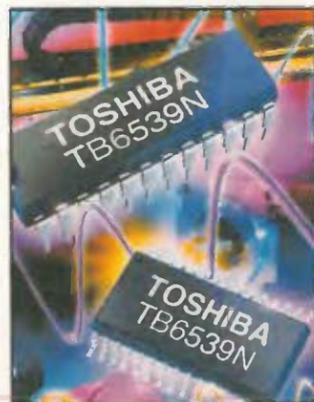**PWM motor controller**

Toshiba Electronics has introduced a PWM three-phase



brushless motor controller IC with an external power FET module to produce a sinusoidal motor coil current waveform, so reducing electrical and acoustic noise. Using a dual modulation technique, the TB6539F/N can generate the sinewave output without the need for an additional external microcontroller. The device also has a built-in dead time function, which allows safe operation of the power FETs in push-pull configuration. **Toshiba Electronics**  
Tel: 00 49 211 5296254  
www.toshiba-europe.com

**Multilayer ceramic chip capacitors**

Multilayer ceramic chip capacitors have been announced by Vishay Intertechnology. The Vitramon VJ0612 capacitor will be used for high-frequency

decoupling and bypass in laptop and desktop computers. Its VTOP housing lets designers place the capacitors underneath ICs. The VJ9743, VJ9742, VJ9741 and VJ9740 each measure 0.16 by 0.32cm, with maximum thickness options of 0.051, 0.066, 0.071 and 0.076cm, respectively. The chips can reduce AC noise in multi-chip modules. The VJ0612 has an inductance of 0.5nH. **Vishay**  
Tel: 00 1 610 644 1300  
www.vishay.com


**Serial EEPROM supporting ACR**

A serial EEPROM from Unique Memec supports the advanced communications riser (ACR) special interest group specification. Microchip's 24LC09 EEPROM provides the

enumeration memory for next-generation PC audio modem riser cards using a nonstandard address that lets the computer automatically detect and configure riser cards with standard plug-and-play capability. Each card provides intelligent modem, audio and network capabilities. The system bios of an ACR-compatible PC can communicate with the riser card, making it transparent to the computer's operating system. **Unique Memec**  
Tel: 01296 397396  
www.unique.memec.com

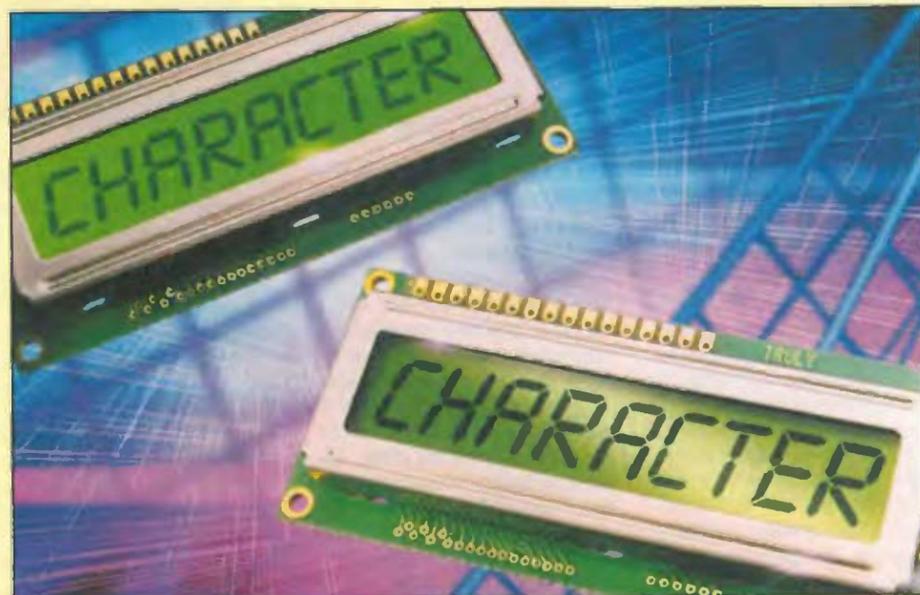**VCO has differential buffered output**

Maxim Integrated Products has introduced the Max2753 2.4GHz monolithic VCO with differential output. It integrates



**Single and dual-row LCD modules**

Single and dual-row LCDs from Gothic Components display up to 32 characters and are available in various sizes, formats and colour options. The Truly 161 and 162 series includes TN and STN character display modules for designers creating equipment such as test and measurement instruments, pagers, personal audio, communication equipment and calculators. This range comprises four 16 character by one line displays, and nine of 16 character by two lines, with viewing areas from 64 to 99mm, and character sizes from

2.95 to 4.84mm. Displays are available in TN black character or STN blue character with options of colour polariser, colour backlighting, EL or LED. Polarisers come in grey, yellow-green or blue, or positive or negative, and backlights in blue, amber, yellow-green and white. Basic modules are available in transmissive, transreflective or reflective. **Gothic Computers**  
Tel: 0118 978 7848  
www.gothiccomputers.com

Visit our website  
www.distel.co.uk

**THE ORIGINAL SURPLUS WONDERLAND!**  
THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always  
wanted for cash!

**THE AMAZING TELEBOX**

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &  
VIDEO TUNER  
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95  
TELEBOX STL as ST but fitted with integral speaker £39.50  
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £69.95  
For overseas PAL versions state 5.5 or 6 mHz sound specification.  
\*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

**NEW** State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**  
See www.distel.co.uk/data\_my00.htm for picture & full details

**FLOPPY DISK DRIVES 2 1/2" - 8"**

All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 unlisted drives for spares or repair.

3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only	£25.95(B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£18.95(B)
5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pcs) RFE	£18.95(B)
5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE	£29.95(B)
5 1/4" BRAND NEW Mitsubishi MF355B 1.4 Meg	£25.95(B)
Table top case with integral PSU for Hi 5 1/4" Floppy / HD	£29.95(B)
8" Shugart 80/801 8" SS refurbished & tested	£210.00(E)
8" Shugart 810 8" SS Hi Brand New	£195.00(E)
8" Shugart 851 8" double sided refurbished & tested	£260.00(E)
8" Mitsubishi M2894-63 double sided NEW	£295.00(E)
8" Mitsubishi M2896-63-02U DS simline NEW	£295.00(E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00(E)

**HARD DISK DRIVES 2 1/2" - 14"**

2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H)	New £79.95
2 1/2" TOSHIBA MK2101MAN 2.1Gb laptop (19 mm H)	New £89.50
2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H)	New £105.00
2 1/2" TOSHIBA MK6409MAV 3.1Gb laptop (12.7 mm H)	New £190.00
2 1/2" to 3 1/2" conversion kit for PCs, complete with connectors	£14.95
3 1/2" FUJITSU FK-309-26 20mb MFM I/F RFE	£59.95
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE	£59.95
3 1/2" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE	£69.00
3 1/2" QUANTUM 40S Prodril ve 42mb SCSI I/F. New RFE	£49.00
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE	£49.95
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95
5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested	£69.95
5 1/4" HP 97548 850 Mb SCSI RFE tested	£99.00
5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested	£195.00
8" NEC D2246 85 Mb SMD interface. New	£199.00
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00
8" FUJITSU M2392K 2 Gb SMD I/F RFE tested	£345.00

Many other drives in stock - Shipping on all drives is code (C1)

**TEST EQUIPMENT & SPECIAL INTEREST ITEMS**

MITEL FA3445ETKL 14" Industrial spec SVGA monitors	£245
FARNELL 0-60V DC @ 50 Amps, bench Power Supplies	£995
FARNELL AP3080 0-30V DC @ 80 Amps, bench Suppy	£1850
1kW to 400 kW - 400 Hz 3 phase power sources - ex stock	£POA
IBM 8230 Type 1, Token ring base unit driver	£760
Wayne Kerr RA200 Audio frequency response analyser	£2500
IBM 53F5501 Token Ring ICS 20 port lobe modules	£750
IBM MAU Token ring distribution panel 8228-23-5050N	£95
AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE	£550
ALLGON 8360.1 1805-1880 MHz hybrid power combiners	£250
Trend DSA 274 Data Analyser with G703(2M) 64 io	£POA
Marconi 6310 Programmable 1 to 22 GHz sweep generator	£6500
Marconi 2022C 10KHz-1GHz RF signal generator	£1550
Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New	£4895
HP1660B Logic Analyser	£3750
HP3781A Pattern generator & HP3782A Error Detector	£POA
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts	£1800
HP6264 Rack mount variable 0-20V @ 20A metered PSU	£875
HP54121A DC to 22 GHz four channel test set	£POA
HP8130A opt 020 300 MHz pulse generator, GPIB etc	£7900
HP A1, A0 8 pen HPGL high speed drum plotters - from HP DRAFTERMASTER 1 8 pen high speed plotter	£550
EG+G Brookdeal 95035C Precision lock in amp	£750
View Eng. Mod 1200 computerised inspection system	£1800
Sony DXC-3000A High quality CCD colour TV camera	£995
Keithley 590 CV capacitor / voltage analyser	£POA
Racal ICR40 dual 40 channel video recorder system	£3750
Fiskers 45KVA 3 ph On Line UPS - New batteries	£9500
Emerson AP130 2.5KVA industrial spec UPS	£2100
Magn Tally MT645 High speed line printer	£2200
Intel SBC 486/133SE Multibus 486 system, 8Mb Ram	£945
Siemens K4400 64Kb to 140Mb demux analyser	£2950

**IC's - TRANSISTORS - DIODES**

OBSELETE - SHORT SUPPLY - BULK  
10,000,000 Items EX STOCK  
For MAJOR SAVINGS  
CALL OR SEE OUR WEB SITE www.distel.co.uk

**VIDEO MONITOR SPECIALS**

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PCs in CGA, EGA, VGA & SVGA modes. BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched lacaplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT title used condition.

T/R & Swivel Base £4.75  
VGA cable for IBM PC included.  
External cables for other types of computers available - CALL

Only £119 (E) Order as MITS-SVGA  
Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc. Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed £199.00 (E) Dimensions: W14" x H12 3/4" x 15 1/2" D.

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/4" D. 240 V AC mains powered. Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition. Only £125 (E)

**20" 22" and 26" AV SPECIALS**

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. in EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

We probably have the largest range of video monitors in Europe, All sizes and types from 4" to 42" call for info.

**DC POWER SUPPLIES**

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call or see our web site.

**19" RACK CABINETS**

Superb quality 6 foot 40U Virtually New, Ultra Smart Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/4" D x 22" W. Order as: OPT Rack 1 Complete with removable side panels £345.00 (G) OPT Rack 2 Rack Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories 19" 22" & 24" wide 3 to 46 U high. Available from stock !!

**32U - High Quality - All steel RakCab**

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five security 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)

Sold at LESS than a third of makers price !!

A superb buy at only £245.00 (G) 42U version of the above only £345 - CALL

**12V BATTERY SCOOP - 60% off !!**

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SB515 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each. **Our Price £35 each (C) or 4 for £99 (E)**

**RELAYS - 200,000 FROM STOCK**

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

**COLOUR CCD CAMERAS**

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full autolight sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc. etc. Web ref = LK33 **ONLY £99.00 or 2 for £180.00 (B)**

**SOFTWARE SPECIALS**

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. **ONLY £89.00 (A)**  
ENCARTA 95 - CDROM, Not the latest - but at this price! £7.95  
DOS 5.0 on 3 1/2" disks with concise books c/w QBasic £14.95  
Windows for Workgroups 3.11+ Dos 6.22 on 3.5" disks £55.00  
Wordperfect 6 for DOS supported on 3 1/2" disks with manual £24.95 shipping charges for software is code B

**DISTEL on the web !! - Over 16,000,000 Items from stock - www.distel.co.uk**

**DISP** **ELECTRONICS**

**ALL MAIL TO**  
Dept ww, 29/35 Osborne Rd  
Thornton Heath  
Surrey CR7 8PD  
Open Mon - Fri 9.00 - 5.30

**LONDON SHOP**  
Open Mon - Sat 9.00 - 5.30  
215 Whitehorse Lane  
South Norwood  
On 58A Bus Route  
N. Thornton Heath &  
Saihurst Park SR Rail Stations

**DISTEL ©**  
Visit our web site  
www.distel.co.uk  
email = admin@distel.co.uk

**ALL ENQUIRIES**  
**0208 653 3333**  
FAX 0208 653 8888

All prices for UK Mainland UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.50, (E)=£15.00, (F)=£20.00, (G)=CALL. Allow approx 8 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1999, E & O.E. 07/99.

## NEWPRODUCTS

Please quote *Electronics World* when seeking further information

the oscillator, tank circuit and a matched output buffer in an eight-pin µMax package. The VCO is compatible with integrated transceiver ICs with a low IF architecture, which typically require an off-chip VCO and a differential interface to reduce spurious noise. Applications include cordless phones, HomeRF, Bluetooth and other proprietary radios operating in the 2.4GHz ISM band. Oscillator frequency tuning is factory adjusted to guaranteed limits from 2400 to 2500MHz with a +0.4 to +2.4V tuning voltage input range. The oscillator signal is buffered by a differential amplifier stage to provide -8dBm output power. This buffer stage also isolates the oscillator from load impedance variations. Oscillator phase noise is typically -130dBc/Hz at 4MHz offset. The VCO operates from a +2.7 to +5.5V supply. Internal regulation of the oscillator supply voltage eliminates the need for a dedicated external low dropout regulator. The VCO consumes 8.6mA of current. In shutdown mode, the current is reduced to 0.2µA. An evaluation kit is available.

**Maxim**  
Tel: 0118 930 3388  
www.maxim-ic.com

### Signal integrity tool suits optical PCBs

Ansoft has released version 3.7 of its PCB/MCM signal integrity tool for PCB needs in optical networks, memory interfaces and multi-gigabit transmission systems. The 3D extraction engine lets designers address problems such as power and ground bounce, simultaneous switching output noise and parasitic extraction (R, L, C, G) for any 3D structure on the PCB. It has interfaces that let it automatically read-in and characterise an entire PCB or MCM designed in Cadence's Allegro or Mentor Graphics' Boardstation. During the analysis, the designer can choose whether to analyse particular structures and nets in full 3D or a mixture of 2D and 3D. Any type of non-ideal power or ground plane (partial

### LCD driver-IC tester

Advantest's LCD driver test system is designed for the testing devices such as thin film transistor (TFT) drivers, and chips that integrate both a controller and a LCD driver. The T6371 can simultaneously test a maximum of either two TFT drivers or four chips that contain a controller and a LCD driver. It can also be used to perform voltage measurements of drivers with a maximum of 128 pins and capable of digital testing at up to 125MHz. For testing multiple-pin ICs, the unit can measure LCDs that have a maximum of 1,280 pins. The system also employs a per-pin comparator architecture, which enables the user to perform high-speed function testing. The system's testing station can simultaneously measure up to four such devices.

**Advantest**  
Tel: 0049 8999 312129  
www.advantest.de



plane, split plane, random holed or meshed plane) can be analysed. It can also analyse single-chip, few chip or multi-chip (system-on-package) designs from Cadence's Advanced Package Designer. The software uses the partial element equivalent circuit method to produce a distributed 3D model. This method lets the tool create accurate models of high-speed traces such as differential pairs and source-synchronous data lines. The distributed nature of the model allows the effect of each individual interconnect structure - including the effect of the non-ideal ground planes - on the signal to be seen in Spice.

**Ansoft**  
Tel: 020 8891 6106  
www.ansoft.com

### PCI-X & PCI analyser and exerciser

Acal Electronics has introduced the PBT-615 state analyser for PCI-X and PCI bus. Made by VMetro, it is a single-slot PCI card that contains a logic analyser and optional exerciser. The unit can capture and trigger on all bus activity in 32 and 64-bit PCI-X and PCI bus

motherboards through a PCI expansion slot at speeds up to 100MHz. By equipping it with an optional piggyback module with a 500MHz timing analyser and a PCI-X anomaly trigger unit, it can automatically detect PCI-X protocol or timing violations. The analyser part provides non-intrusive and stand-alone operation as seen from the host computer to be analysed. This is possible because it is equipped with its own processor communications ports (RS232 and USB) and firmware in flash PROMs. The analyser can be operated from a PC running VMetro's graphical user interface, Busview for Windows, from a standard Ascii terminal, or using a terminal emulator on a PC or Unix workstation. The protocol-sensitive sampling of bus cycles for state analysis means the bus analysers know the bus protocol of the target bus to ensure that sampling takes place at the right moments. This gives a trace that includes many types of bus activity, such as arbitration, interrupts and cache cycles, and ensures that the bus is not sampled at unimportant times.

**Acal Electronics**  
Tel: 01252 858585  
www.acalelec.co.uk

### Oscillator requires one resistor

The Linear Technology LTC1799 is a SOT23 packaged oscillator IC that generates any frequency from 1kHz to 30MHz. The frequency can be set within ±2.5 per cent by adding a 1 per cent resistor or ±1.6 per cent with a 0.1 per cent resistor. There is no need for a crystal, ceramic resonator, capacitor or external reference clock. Accuracy is maintained over all supply and temperature variations, drifting typically less than 0.004 per cent per °C and 0.05 per cent per volt. Maximum supply current at 5V for a 10MHz output is 2.4mA from -50 to +85°C. Applications include localised clocks, synchronisation of switching power supplies and driving switched capacitor filters.

**Linear Technology**  
Tel: 01276 677676  
www.linear-tech.com

### Materials absorb microwaves

Two flexible, absorbent EMI materials have been introduced by Murata. The EA10 prevents abnormal oscillation in high frequency modules and

### MARCONI 2019A

AM/FM synthesised signal generator 80KHz-1040KHz  
**NOW ONLY £400**

H.P. 3312A Fun Gen 0.1Hz-13MHz £300  
AM/FM Sweep/TruGate/Burst etc. H.P. 3310A Fun Gen 0.005Hz-5MHz £125  
Sine/Sa/Tru/Ramp/Pulse FARNELL LFM4 Sine/Sq Oscillator 10Hz-1MHz £125  
Low distortion TTL Output Amplitude Meter H.P. 545A Logic Probe with 546A Logic Pulser £90  
and 547A Current Tracer £90  
FLUKE 77 Series 11 £70  
HEME 1000 LCD Clamp Meter 0-1000A In Carrying Case £60

**RACAL 9008 AUTOMATIC MODULATION METER AM/FM 1.5MHz-2GHz ONLY £95**

H.P. 8494A Attenuator DC-4GHz 0-11dB N/SMA £250  
H.P. 8492A Attenuator DC-18GHz 0-6dB APC7 £95  
MANY OTHER ATTENUATORS, LOADS, COUPLERS etc AVAILABLE

**DATRON 1061 HIGH QUALITY 5% DIGIT BENCH MULTIMETER True RMS/A wire Res/Current Converter/IEEE £150**

MARCONI TF2015 AM/FM sig gen, 10-520MHz £175  
RACAL 9008 Auto Mod Meter, 1.5MHz-2GHz £200  
LEVELL TG2000MP RC Oscillator, 1Hz-1MHz £50  
Sine/Sq. Meter, battery operated (batts. not supplied)  
FARNELL LFI Sine Sq. Oscillator, 10Hz-1MHz £75  
RACAL/AM 9343M LCR Databridge, Digital Auto £200

### STILL AVAILABLE - PREVIOUSLY ADVERTISED WITH PHOTOS

MARCONI 893C AF Power Meter Sine Measurement Unused £100  
Used £60  
MARCONI 893B - No Sine £30  
MARCONI 2610 True RMS Voltmeter Autoranging 5Hz-25MHz £195  
GOULD J38 Sine/Sq Osc. 10Hz-100KHz Low distortion £75-£125

AVD 84K6 in Ever Ready Case, with leads etc. £80  
Others Avos from £50

GOODWILL GFC8010G Freq. Counter 1Hz-120MHz Unused £75  
GOODWILL GVT427 Dual Ch AC Millivoltmeter £100-£125  
10mV-300V in 12 Ranges Freq 10Hz-1MHz  
SOLARTRON 7150 DMM 6 1/2 digit True RMS - IEEE £95-£150

SOLARTRON 7150 Plus £200

**RACAL TRUE RMS VOLTMETERS**  
9300 5Hz-20MHz usable to 60MHz, 10V-316V £95  
9300B Version £150  
9301/9302 RF Version to 1.5GHz from £200-£300

**HIGH QUALITY RACAL COUNTERS**  
9904 Universal Timer Counter, 50MHz £50  
9915 Counter, 10Hz-620MHz £75  
9918 Counter, 10Hz-560MHz, 9-digit £50  
FARNELL AMM255 Automatic Mod Meter 1.5MHz-2GHz Unused £400

**CLASSIC AVDMETER DA 116 DIGITAL 3.5 DIGIT COMPLETE WITH BATTERIES AND LEADS ONLY £30**

**SOLARTRON 7045 BENCH MULTIMETER**

4 1/2 digit BRIGHT LED WITH LEADS ONLY £30

IT'S SO CHEAP YOU SHOULD HAVE IT AS A SPARE

HUNTRON TRACKER Mode 1000 £125  
H.P. 5315A Universal Counter, 1GHz, 2-ch £30  
FLUKE 8050A DMM 4 1/2 digit 2A True RMS £75  
FLUKE 8010A DMM 3 1/2 digit 10A £50

**TIME 1051 Low Ohm Res Box 0.01ohm to 1M Ohm in 0.01ohm steps. Unused £100**

### STEWART of READING

110 WYKHAM ROAD, READING, BERKS RG6 1PL  
Telephone: (0118) 9268041 Fax: (0118) 9351696  
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

### SCOPE FOR IMPROVEMENT

**GOULD OS 300 OSCILLOSCOPE DUAL TRACE 20MHz TESTED WITH MANUAL FOR THE FIRST TIME EVER ONLY IT'S SO CHEAP YOU SHOULD REPLACE THAT OLD SCOPE £95**

MARCONI 2022E Synthesised AM/FM Sig Gen £325-£750  
100Hz-101MHz LCD Display etc

H.P. 8575A Synthesised 2-18GHz Sig Gen £4000  
H.P. 8574 Synthesised 100kHz-1040MHz Sig Gen £2000  
H.P. 8556B Synthesised 100kHz-990MHz Sig Gen £1350  
H.P. 8556A Synthesised 100kHz-990MHz Sig Gen £995  
H.P. 8540A AM/FM 500kHz-1024MHz Sig Gen £400  
H.P. 8540A AM/FM 500kHz-512MHz Sig Gen £250

PHILIPS PM5328 100MHz-180MHz with 200MHz Sig Gen Freq Counter IEEE £350

RACAL 9081 Synth AM/FM Sig Gen 5-820MHz £250  
H.P. 3252A Synth Function Gen 21MHz £600  
MARCONI 6500 Amplitude Analyser £1500  
H.P. 4275A LCR Meter 10kHz-10MHz £2750  
H.P. 4275A LCR Meter 10kHz-10MHz £1000  
WAYNE KERR 3245 Inductance Analyser £2000  
H.P. 8112A Pulse Generator 50MHz £1250  
DATRON AutoCal Multimeter 5 1/2-7 1/2 digit 106S1061A/1071 from £300-£600

MARCONI 2400 Frequency Counter 20GHz £1000  
H.P. 5308B Frequency Counter 30GHz £2000  
H.P. 5342A 10Hz-18GHz Frequency Counter £800  
BAK Accelerometer type 4366 £300

H.P. 11692D Dual Directional Coupler 2MHz-180MHz £1800  
H.P. 11691D Dual Directional Coupler 2MHz-180MHz £1250

TEKTRONIX P6109B Probe 100MHz Readout Unused £50  
TEKTRONIX P6106A Probe 250MHz Readout Unused £85  
FARNELL AMM2000 Auto Mod Meter, 10Hz-2.4GHz Unused £350  
MARCONI 2365 Mod meter, 500kHz-800Hz from £750

**ROHDE & SCHWARZ APM 62 SYNTHESISED 1Hz-250kHz SIGNAL GENERATOR. BALANCED/UN-BALANCED OUTPUT. LCD DISPLAY £425**

H.P. 6012B DC PSU 0-60V, 0-50A 1000W £1000  
FARNELL AP60/50 1kW Autoranging £1000  
FARNELL H60/50 0-60V, 0-50A £750  
FARNELL H60/25 0-60V, 0-25A £400  
Power Supply HPS3010 0-30V, 0-10A £140  
FARNELL L30-2 0-30V, 0-2A £80  
FARNELL L30-1 0-30V, 0-1A £50

Many other Power Supplies available  
Isolating Transformer 240V In/Out 500VA £40

**PORTABLE APPLIANCE TESTER MEGGER PAT2 Only £180**

USED EQUIPMENT - GUARANTEED. Manuals supplied  
This is VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

### SPECTRUM ANALYSERS

ADVANTEST R3261A 9kHz-2.5GHz Synth £4000  
EATON/AILTECH 757 0.001-22GHz £2500  
TEKTRONIX 492 50KHz-18GHz £3500  
H.P. 8558B with Main frame 100kHz-1500MHz £1250  
H.P. 853A (Dig Frame) with 8558A 100kHz-21GHz £2750  
H.P. 3580A Audio Analyser 5Hz-50kHz As new £1000  
B & K 2033R Signal Analyser £1500  
MARCONI 2382 100Hz-400MHz High Resolution £2000  
H.P. 182 with 8557 10kHz-350MHz £500  
MARCONI 2370 30Hz-110MHz from £500  
HF11 Systems 8553 1kHz-110MHz from £500  
8554 500kHz-1250MHz from £750, 8555 10MHz-18GHz from £1000

### UNUSED OSCILLOSCOPES

TEKTRONIX TAS485 4 Ch 200MHz etc £900  
H.P. 54600E Dual Trace 100MHz 20MS £900  
TEKTRONIX THS720A Dual Trace L.C.D. 100MHz 500MS £900  
TEKTRONIX THS 720P as THS 720A, power measurement £1300  
TEKTRONIX THS 710 Dual Trace, 60MHz 250MS/5 £750  
HITACHI VC6523 Dual Trace, 20MS/5/S Delay Cursor, etc £600

### OSCILLOSCOPES

PHILIPS PM3092 2+2 Ch 200MHz. Delay etc £950  
800L As new £950  
PHILIPS PM3082 2+2 Ch 100MHz. Delay etc £700. As new £800  
TEK TAS485 Dual Trace 100MHz. Delay £800  
TEK 2465B 4 Ch 400MHz. Delay Curs £1250  
TEK 2465 4 Ch 300MHz. Delay Curs £900  
TEK 2445A/B 4Ch 150MHz. Delay etc £500-£900  
TEK 468 Dig Storage. Dual 100MHz Delay. £450  
TEK 466 Analogue Storage. Dual 100MHz. £250  
TEK 465 Dual Trace 350MHz Delay £600  
TEK 475 Dual Trace 200 MHz. Delay £400  
TEK 465B Dual Trace 100MHz. Delay £325  
PHILIPS PM3217 Dual Trace 50MHz Delay £250-£300

GOULD OS1100 Dual Trace 30MHz Delay £200  
HAMEG HM303 4 Dual Trace 30MHz £325  
HAMEG HM303 Dual Trace 30MHz £300  
HAMEG HM203 7 Dual Trace 20MHz £250  
FARNELL DTV20 Dual Trace 20MHz £180  
MANY OTHER OSCILLOSCOPES AVAILABLE

**RACAL RECEIVER RA1772 50KHz-30MHz LED display. Basically working £250**

CIRCLE NO. 114 ON REPLY CARD

### WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES (using a video capture card)



"Liesegang diav" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk £91.91 + vat = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12V DC 150mA

47MR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye) £37.00 + vat = £43.48

30MP size 32x32x14mm spy camera with a fixed focus pln hole lens for hiding behind a very small hole £35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses £32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris  
VSL1220F 12mm F1.6 12x15 degrees viewing angle £15.97 + vat = £18.76  
VSL4022F 4mm F1.22 63x47 degrees viewing angle £17.65 + vat = £20.74  
VSL6022F 6mm F1.22 42x32 degrees viewing angle £19.05 + vat = £22.38  
VSL8020F 8mm F1.22 32x24 degrees viewing angle £19.90 + vat = £23.38

Better quality C Mount lenses  
VSL1614F 16mm F1.6 30x24 degrees viewing angle £26.43 + vat = £31.06  
VWL813M 8mm F1.3 with Iris 56x42 degrees viewing angle £77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat 1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbitec mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily £7.46 + vat = £8.77

Please add 1.66 + vat = £1.95 postage & packing per order

### JPG ELECTRONICS

276-278 Chatsworth Road, Chesterfield, S40 2BH.  
Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch  
Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

CIRCLE NO. 115 ON REPLY CARD

### FRUSTRATED!

Looking for ICs TRANSISTORS? A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD  
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF  
BFR BFS BFT BFW BFX BFLY BLX BS BR BRX BRY BS  
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY  
BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS  
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA  
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB  
MC MDA J MJE MJF MM MN MPS MPA MSH MPSU  
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB  
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD  
STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB  
TEA TIC TIP TIPL TE TL TLT TMP TMS TPU U UA  
UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN  
ZTX + many others

We can also offer equivalents (at customers' risk). We also stock a full range of other electronic components. Mail, phone, Fax, Credit Card orders & callers welcome.



**Cricklewood Electronics Ltd**  
40-42 Cricklewood Broadway, London NW2 3ET  
Tel: 020 8452 0161 Fax: 020 8208 1441  
www.cricklewoodelectronics.co.uk  
E-mail: sales@cricklewoodelectronics.com

CIRCLE NO. 116 ON REPLY CARD

## NEWPRODUCTS

Please quote *Electronics World* when seeking further information

suppresses interference between circuits. The EA20 has high- $\mu$ , high-loss characteristics for suppression over a wide band in digital products. Both microwave absorbers cover 0.1 to 20GHz and can be introduced at any stage in the sequence from design to delivery. The silicon-based materials are flexible and can be held in place with adhesive tape. Thicknesses available are from 0.2 to 2.7mm. The thickness depends on the frequency to be suppressed. Custom sizes can be supplied.

Murata

Tel: 01252 811666  
www.murata.co.uk

### Connector with 0.6mm pitch

Harwin's latest range of surface mount ultra-fine pitch connectors, called the MP6 connector series is a 0.6mm pitch board mounting connector provide stacking heights of 3mm, 4mm and 5mm between boards. They are available with up to 100 contact positions, polarised to prevent mis-mating and equipped with locating pegs for accurate PCB placement. Metal latching clips are available upon request if additional strain relief is required. The housings are manufactured from glass filled LCP and have a UL94V-0 flammability rating. The housing has a minimum insulation resistance of 100m $\Omega$  and dielectric withstanding voltage of 200V AC. Standard packaging is tape and reel



format on 330mm reels using embossed carrier tape with removable pick and place pads for automatic placement.

Harwin

Tel: 023 9237 0451  
www.harwin.com

### Full duplex OC-48 ATM OAM processor

Vitesse Semiconductor has announced the Monitor 4.8 manager for operations, administration and maintenance (OAM) network traffic at OC-48 data rates. This IC provides ATM layer functions for OAM and protection switching cell processing. Throughput is 4.8Gbit/s with 512k individual connection flows (256k full duplex flows) in VC, VP, VP/VC or VP/VC switch configurations. For use with the firm's Pacemaker 2.4, a traffic management and SAR device, the IC is for line card ATM cell and packet processing. When used with the firm's IQ2000

network processor, switch fabric components and framer-mapper devices, the family provides system designers with an end-to-end chip level product for next generation Internet infrastructure equipment. It is a silicon implementation of the ITU I.630 protection switching standard, and provides per connection activation and deactivation of OAM flows with performance and fault monitoring on all 256k connections independently. It interfaces with the outside world via four independent standard Utopia ports and a 32-bit 66MHz PCI interface for connection to a host CPU.

Vitesse Semiconductor  
Tel: 001 310 937 1594  
www.vitesse.com

### Supervisors monitor down to 300mV


Two dual voltage supervisor ICs for monitoring power supplies down to 300mV have been developed by Micrel Semiconductor. Available in the firm's Ittybitty SOT23-5 packaging, the MIC2774 and MIC2777 have a choice of preprogrammed voltage options and quiescent currents. One of the monitoring inputs is user-adjustable and the other is preprogrammed at the factory. Options accommodate standard logic supply voltages. Power supply current is 3.5A. The MIC2777 has active-high and active-low reset outputs; manual reset capability can be achieved by adding an external

reset switch. The MIC2774 has a standard pin out with a dedicated manual reset input and a choice of active-high, active-low or open-drain active-low reset outputs. They are made on a BiCMOS process. Micrel Semiconductor  
Tel: 01635 524455  
www.micrel.com
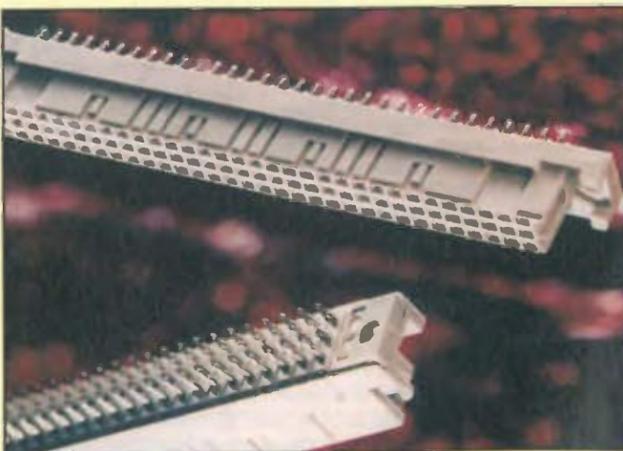
### 512kbit flash with random read

STMicroelectronics has announced a 512kbit flash memory device with sequential and random read operation, page mode programming, sector and bulk erase modes, and a 20MHz SPI-compatible serial bus.

Like its 1Mbit predecessor, the non-volatile field-programmable 512kbit (64k by 8 bit) M25P05 is targeted at applications for the storing of code and blocks of data in industrial, consumer and telecoms products, says the supplier. The flash chip contains two sectors of 256 pages each. Because one page is 128 bytes wide, the entire memory can be viewed as 512 pages or 65 536 bytes. The memory's page program instruction writes one to 128 bytes at a time. The memory can be erased at once using a bulk erase instruction. Alternatively, one sector at a time can be erased using a sector erase instruction. There is a 26ms full memory read operation at 2.7V; 3ms (typical) for 128-byte page programming; and 256kbyte



### Press-fit connectors for D-sub and 2mm

Northern Connectors offers press-fit connectors including the Harting DIN41612 and the Harbus 64 range. In addition, the distributor will provide press-fit products for both: D-Sub straight and right angle IDC boxed headers, hard metric 2mm connectors, and SCSI as well as BNC connectors.

To achieve the packing densities required, back-panel PC boards are in the form of multilayer boards which use press-fit termination. The press-fit pins are inserted and adapt to the hole within the PC board. Electrical contact is made solely by pressure and cold welding of contact surfaces within the insertion zones.

Northern Connectors

Tel: 01744 815001

www.northern.connectors.com

# BOOKS TO BUY




### PASSIVE COMPONENTS FOR CIRCUIT DESIGN

Passive Components for Circuit Design is a unique introduction to this key area of analog electronics designed for technician engineers and anyone involved in circuit design. The coverage encompasses all component types capable of power amplification: resistors, capacitors, transformers, solenoids, motors and transducers. The behaviour of the components is explored along with the different types available and the principles of circuit design. Tolerances, stability, variation with temperature, reliability and manufacturing standards are all covered. Reading this book will improve your skills in component selection and analog circuit design. These are essential skills not only for the analog designer, but for all circuit designers, professional or amateur.

**Contents:** Preface; Fundamentals; Fixed resistors; Variable resistors, potentiometers and diodes; Capacitors; Inductors and inductive components; Inductive devices; Transducing components; SMT; Hardware; Index

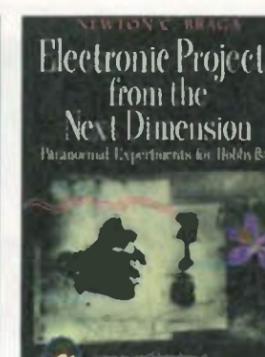**Readership:** Technician engineers, circuit designers, advanced hobbyists  
Pages: 304pp  
**Price: UK £22.00**  
**Europe £24.00**  
**ROW £26.00**




### ELECTRONIC PROJECTS FROM THE NEXT DIMENSION

For years paranormal scientists have explored the detection and documentation of spirits, auras, ESP, hypnosis, and many more phenomena through electronics. Electronic Projects from the Next Dimension provides useful information on building practical circuits and projects, and applying the knowledge to unique experiments in the paranormal field. The author writes about dozens of inexpensive projects to help electronics hobbyists search for and document their own answers about instrumental transcommunication (ITC), the electronic voice phenomenon (EVP), and paranormal experiments involving ESP, auras, and Kirlian photography.

Although paranormal studies are considered esoteric, Electronic Projects from the Next Dimension teaches the technical skills needed to make devices that can be used in many different kinds of experiments. Each section indicates how the circuit can be used in paranormal experiments with suggestions about procedures and how to analyze the results.

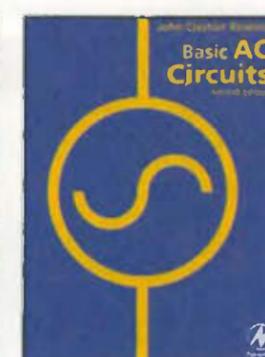**Contents:** White noise generators for use in instrumental transcommunication (ITC) and electronic voice phenomenon (EVP) experiments; Practical circuits for image experimentation, such as a



### BASIC AC CIRCUITS

This is the step-by-step approach for beginners. This self-paced individualized learning tool covers concepts, terms, and the mathematics required to understand AC circuit problems. It has been designed to improve analysis techniques for prediction and control development.

**Readership:** Beginners meeting AC circuits for the first time; students; technicians  
Pages: 921 pp  
**Price: UK £27.00**  
**Europe £29.00**  
**ROW £31.00**

wireless sparkling image generator, horizontal bar generator, brontophic sound, magnetic field generator, high-voltage generators (Kirlian Machine's I & II); Paranormal skills experiments with temperature change, polygraph, electro-shock, random number generation, UFO detection, and ghost-finding.

**Readership:** Hobbyists, Electronics Enthusiasts  
Pages: 256pp  
**Price: UK £22.00**  
**Europe £24.00**  
**ROW £26.00**

**Post your completed order form to:-**  
**Jackie Lowe, Cumulus Business Media,**  
**Anne Boleyn House, 9-13 Ewell Road,**  
**Cheam, Surrey, SM3 8BZ**

**Fax your order form to 020 8643 8952**

### How to order

#### Book Title \_\_\_\_\_

I enclose a cheque/bank draft for £ \_\_\_\_\_  
(payable to Cumulus Business Media)

Please charge my credit/charge card

Mastercard  American Express  Visa  Diners Club

Credit Card No: \_\_\_\_\_

Expiry Date: \_\_\_\_\_

Signature of Cardholder \_\_\_\_\_

Cardholder's statement address: (please use capitals)

Name \_\_\_\_\_

Address \_\_\_\_\_

Post Code \_\_\_\_\_

Tel: \_\_\_\_\_



### INTERFACING WITH C

A practical and painless way of becoming an expert C programme New edition also covers C++ and the Windows environment Get up to speed with the essential maths needed for C without having to buy a university maths text!

**Price: UK £18.00**  
**Europe £20.00**  
**ROW £22.00**

## NEWPRODUCTS

Please quote *Electronics World* when seeking further information

sector and 512kbyte erase operations of 1s and 2s (typical), respectively. Allowing either random or sequential read operations, the serial memory reduces the number of instructions needed compared to a parallel architecture, simplifying development. The four-wire SPI-compatible serial interface clocks at a top rate of 20MHz. *STMicroelectronics*  
Tel: 01628 890800  
www.st.com

### Surface-mount DC-to-DC converters for 100A

Vicor has introduced a surface mount interface accessory, called SurfMate, which is designed for use with pin-compatible 2nd generation DC-to-DC converters and accessory modules. According to the supplier this will allow designers and assemblers to surface mount high-density DC-to-DC converters with current ratings up to 100A. It uses a pair of surface mounted headers that contain sockets to accept the input and output pins of the converter module. The header assembly is compatible with any thickness PCB, does not increase the module mounting height above the board, and is available for all three standard module sizes – Maxi, Mini, and Micro (full, half and quarter brick DC-to-DC converters). The interfaces are packaged in standard recyclable JEDEC trays for use with automated pick and place equipment and are compatible with standard reflow solder operations. After

### One-phase 'green' fan

The Green Motor fan range from Sunon has been awarded ISO14001. The range includes axial fans from 17 by 17 by 8mm frame size to 120 by 120 by 38mm, and microblowers from 35 by 35 by 4.8mm to 45 by 45 by 9mm. They use a one phase full-wave winding mechanism to reduce material waste, increase torque and reduce failure rate during production. The motor bobbin, which protects the coil, is produced from a high-temperature resistant, non-flammable and insulating engineering thermoplastic. This lets the fan motor be operated at an ambient temperature up to 90°C. *Sunon*  
Tel: 0031 1461 54515  
www.sunon.fr



reflow, the modules are inserted into the sockets. *Vicor*  
Tel: 01276 678222  
www.vicr-europe.com

### Power switch IC supports USB wake-up


USB power switch ICs offering advanced configuration and power interface (ACPI) wake-up capabilities are available from Micrel Semiconductor. MIC2010 series devices include four dual-channel protected Mosfet switches optimised for universal serial bus (USB) wake-up capabilities supported by ACPI for desktop PCs. When the PC is active, these devices will guarantee 500mA continuous output current per channel as required by USB. When the PC is placed in the ACPI S3 sleep state, the outputs are switched to the 5V standby supply available in ATX style power supplies. In this state, the continuous output current is reduced to 100mA, or to a user-adjustable value. This reduction protects the smaller current capacity of the standby supply in case of short-circuit faults. When the PC is returned to the active SO state, the outputs are switched to the 5V main supply. The four devices include the MIC2010, MIC2012, MIC2070 and MIC2072. The MIC2010 offers adjustable auxiliary

current limiting for more precise control, whereas the MIC2012 has preset current limits for the auxiliary mode. The MIC2070 and MIC2072 provide a circuit breaker function that latches the

output(s) off when an over current condition is detected, reducing power consumption during a fault. *Micrel Semiconductor*  
Tel: 020 7823 3224  
www.micrel.com
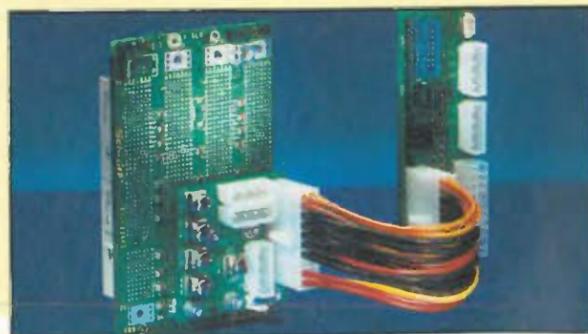
### Modular compact PCI backplane

Schroff has introduced a modular CompactPCI backplane with a power supply interface for industrial and telecoms users. The various modules can be combined into a system whose flexibility allows the construction of prototypes and short-production-run models. The backplane consists of modular backplanes, power piggybacks and one or more power backplanes. The modular backplanes comply with revision 3.0 of the CompactPCI core specification. Models with three to eight slots are available in 3 or 6U formats. The five and seven-slot versions are bridgeable. All can be abutted without losing a slot width. The piggyback board, which is plugged directly into the rear of the backplane, is used for connecting each power supply. This board contains an ATX connector, various universal supply terminals for M4 eyelets (power bugs) and three drive connectors. The board both enables power to be fed to the backplane from various sources, and serves as a central node for power distribution in the system. *Micrel Semiconductor*  
Tel: 020 7823 3224  
www.micrel.com



## TiePieScope HS801 PORTABLE MOST




ARBITRARY WAVEFORM GENERATOR-  
STORAGE OSCILLOSCOPE-  
SPECTRUM ANALYZER-  
MULTIMETER-  
TRANSIENT RECORDER-

# Reliability

- The sophisticated cursor read outs have 21 possible read outs. Besides the usual read outs, like voltage and time, also quantities like rise time and frequency are displayed.
- Measured signals and instrument settings can be saved on disk. This enables the creation of a library of measured signals. Text balloons can be added to a signal, for special comments. The (colour) print outs can be supplied with three common text lines (e.g. company info) on three lines with measurement specific information.
- The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (arbitrary waveform generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.
- The versatile software has a user-defined toolbar with which over 50 instrument settings quick and easy can be accessed. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.
- The HS801 has an 8 bit resolution and a maximum sampling speed of 100 MHz. The input range is 0.1 volt full scale to 80 volt full scale. The record length is 32K/64K samples. The AWG has a 10 bit resolution and a sample speed of 25 MHz. The HS801 is connected to the parallel printer port of a computer.
- The minimum system requirement is a PC with a 486 processor and 8 Mbyte RAM available. The software runs in Windows 3.xx / 95 / 98 or Windows NT and DOS 3.3 or higher.
- TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 4WJ, UK  
Tel: 01480-460028; Fax: 01480-460340
- TiePie engineering (NL), Koperslagersstraat 37, 8601 WL SNEEK The Netherlands  
Tel: +31 515 415 416; Fax +31 515 418 819



CIRCLE NO. 119 ON REPLY CARD

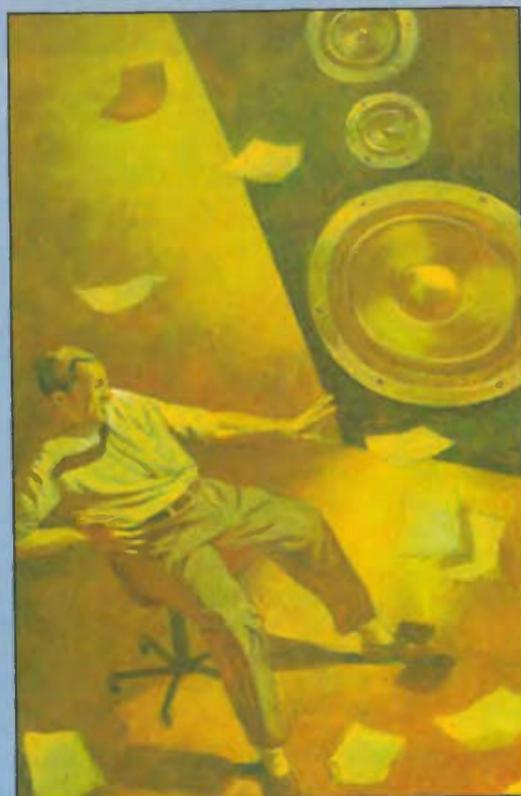

**A reader came up with the idea of reducing woofer distortion by using motional feedback derived from pressure changes inside the cabinet, as opposed to voice-coil position. "So why is no one using it?" he asks John Watkinson...**

# BASS PERFECTION?

**R**egular Speakers' Corner reader John Cole, from Devon, recently wrote in with a suggestion for improving bass response. John wondered why the idea wasn't used in practice. He wrote as follows:

"At 100Hz the wavelength is three metres, at 50Hz six, so to a reasonable approximation, a normal sized speaker is a point source that simply sucks and blows air. The material of the speaker has a constant volume, so where is the change of volume to accommodate that air? Clearly it's the change in volume of the air being compressed and rarefied in the box. That must be true even for a vented enclosure, as long as the vent and the driver are close together in wavelength terms. Inside the box there's essentially a single pressure, since again the space is small compared to a wavelength, and to a good approximation its change is proportional to the change in volume, being a fraction of atmospheric pressure.

The next step is obvious. Mount a pressure-sensitive microphone or – in these days when piezo-resistive devices are commonplace – a fast acting pressure sensor within the box and use feedback to constrain its output to follow the signal input at bass frequencies. Unlike motional feedback, that

measures the coil position, this scheme uses a readily available linear transducer and doesn't require the cone to remain rigid as it strains against the internal pressure. Tell me please, why will it not work?"


I like questions like this because to answer properly requires a wide range of technologies to be considered. Let's start with the acoustics.

It is absolutely true that the average-sized speaker can be considered a point source that sucks and blows at low frequencies. The radiation is proportional to the volume velocity of the diaphragm.

However, the pressure in the box isn't, unless the box has infinite volume. Figure 1 shows a finite box with a moving diaphragm. It assumed that the diaphragm is ideal, such that it moves an equal amount inwards and outwards due to a sinusoidal drive signal. However, this does not result in a sinusoidal pressure waveform in the box. Figure 1 shows why.

If it is assumed that the diaphragm displacement is 10 percent of the static volume of the box, then when the diaphragm moves in, the volume falls to 0.9 of the static volume, so that the pressure goes up to  $1/0.9=1.1111$  times static. However, when the diaphragm moves out, the volume increases to 1.1 times static, so the pressure falls to  $1/1.1=0.909$  times static.

Figure 1b) shows that in the resultant pres-

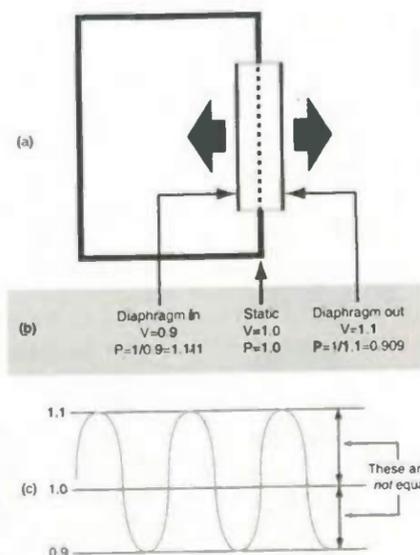

**Fig. 1. Illustration a) represents diaphragms in a sealed box while b) indicates pressure resulting from 10% volume change. Drawing c) shows how the pressure waveform is distorted.**

sure waveform, the positive peak would be 11 percent bigger than static whereas the negative peak would be 9 percent smaller than static. Figure 1c) shows the pressure/volume relationship, which is not linear. If the loudspeaker were to be servoed such that the box

pressure was sinusoidal, the radiation would not be sinusoidal and the result would be harmonic distortion.

The assumptions made about this technique applying to reflex speakers are only true in the steady state condition, when the speaker has been emitting a sine wave for some time. In that case there will be a single pressure in the box which would be a sine wave distorted by the mechanism above.

However, there is more to sound reproduction than steady state. The time domain is more important. To take an analogy, a car that could do 150mile/h wouldn't be useful if it took two hours to reach that speed.

In the case of audio, sine waves don't carry any information because they have no bandwidth. Information in audio is carried in transients and it is important to reproduce them accurately. This requires linear-phase loudspeakers.

Reflex speakers simply cannot reproduce transients because the delays involved in establishing port resonances – and their subsequent decay – destroy phase linearity. In the light of modern active speaker technology, reflex speakers are inaccurate and obsolete.

### Feedback won't fix it

The other point worth making in regard to this query is that it is all too easy to suggest 'fixing' a problem by putting feedback

around something. In the same way that most speaker designers have a fixation with frequency response, it seems that most electronics engineers have a fixation with negative feedback as a universal solution. Unfortunately it's not that simple.


When considering a loudspeaker drive unit in a box, Fig. 2 shows that it is a resonant system having a fundamental frequency within the audio band. The phase response below this resonance is 180° out from the phase response above.

The question then is do we want negative feedback above the resonant frequency which becomes positive feedback below, or vice versa? Of course neither of these approaches would work; they would be unstable. In order to use negative feedback around a loudspeaker, it is necessary to construct a compensating circuit that has the inverse phase characteristic to the drive unit and incorporate it in the feedback loop. Doing this is not a trivial matter.

The other problem with negative feedback is that it only works when there is some loop gain left. This means that the operating bandwidth and power output of negative feedback systems must be significantly less than the open loop characteristics.

### A very precise donkey

Feedback may linearise and extend bandwidth at small amplitudes, but as amplitude

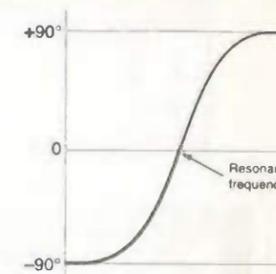

**Fig. 2. Phase characteristic of woofer around resonance makes feedback difficult to stabilise.**

increases, the system may just go open loop. You can't make a racehorse by putting feedback round a donkey. Instead you get a slower but very precise donkey.

These restrictions do not apply so much to feedforward because there is no requirement for loop gain – because there is no loop. In such a way we have arrived at another reason why Mr Cole's idea and other active technologies are seen so infrequently: the number of loudspeaker designers who can coherently explain the difference between feedback and feedforward is very small indeed.

You don't generally need those skills to take commoditised drive units from Taiwan and fit an MDF box around them. Worrying about phase linearity would cut into the time taken polishing the veneer.

## Valve Radio and Audio Repair

\* A practical manual for collectors, owners, dealers and service engineers \* Essential information for all radio and audio enthusiasts \*



UK Price: £22.50 Europe £25.00 ROW £27.00  
\*\* Price includes delivery and packing \*\*

This book is not only an essential read for every professional working with antique radio and gramophone equipment, but also dealers, collectors and valve technology enthusiasts the world over. The emphasis is firmly on the practicalities of repairing and restoring, so technical content is kept to a minimum, and always explained in a way that can be followed by readers with no background in electronics. Those who have a good grounding in electronics, but wish to learn more about the practical aspects, will benefit from the emphasis given to hands-on repair work, covering mechanical as well as electrical aspects of servicing. Repair techniques are also illustrated throughout. This book is an expanded and updated version of Chas Miller's classic Practical Handbook of Valve Radio Repair. Full coverage of valve amplifiers will add to its appeal to all audio enthusiasts who appreciate the sound quality of valve equipment.

Post to Jackie Lowe, Cumulus Business Media,  
Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ

### How to pay

(Valve Radio and Audio Repair Handbook) paperback

I enclose a cheque/bank draft for £ \_\_\_\_\_ (payable to Cumulus Business Media)

Please charge my credit/charge card  
 Mastercard  American Express  Visa  Diners Club

Credit Card No: \_\_\_\_\_ Expiry Date: \_\_\_\_\_

Signature of Cardholder \_\_\_\_\_

Cardholder's statement address: (please use capitals) \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Post Code \_\_\_\_\_ Tel: \_\_\_\_\_

# Designing radio receivers II

Joe Carr discusses receiver design from the ground up. This second article looks at elements of the superheterodyne

In the first article of this set I looked at the various receiver architectures on the market, ending with the superheterodyne. This month I will be covering the various circuits within the superheterodyne receiver, starting a discussion of receiver performance parameters.

## Front-end circuits

The principal task of the front-end and frequency-translator sections of the receiver in Fig. 1 is to select the signal and convert it to the intermediate frequency. In many radio receivers though, there may be additional functions.

In some cases – but not all – an RF amplifier will be used ahead of the mixer. Typically, these amplifiers have a gain of 3 to 10dB, with 5 to 6dB being very common. The

tuning for the RF amplifier is sometimes a broad band-pass fixed frequency filter that admits an entire band. In other cases, it is a narrow band, but variable frequency, tuned circuit.

## Intermediate-frequency amplifier

The IF amplifier is responsible for providing most of the gain in the receiver, as well as the narrowest band-pass filtering. It is a high gain, often multi-staged, tuned-radio-frequency amplifier with a single frequency.

For example, one HF shortwave receiver block diagram lists 120dB of gain from antenna terminals to audio output. Of these, 85dB come from the 8.83MHz IF amplifier chain.

In the example of Fig. 1, the receiver is a single conversion design, so there is only one IF amplifier section.

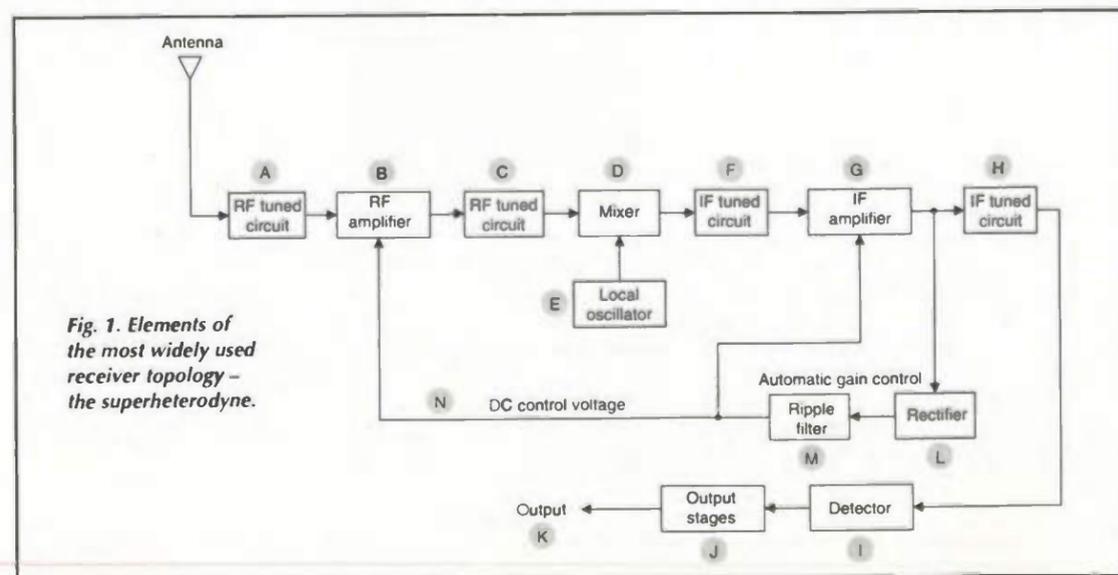


Fig. 1. Elements of the most widely used receiver topology – the superheterodyne.

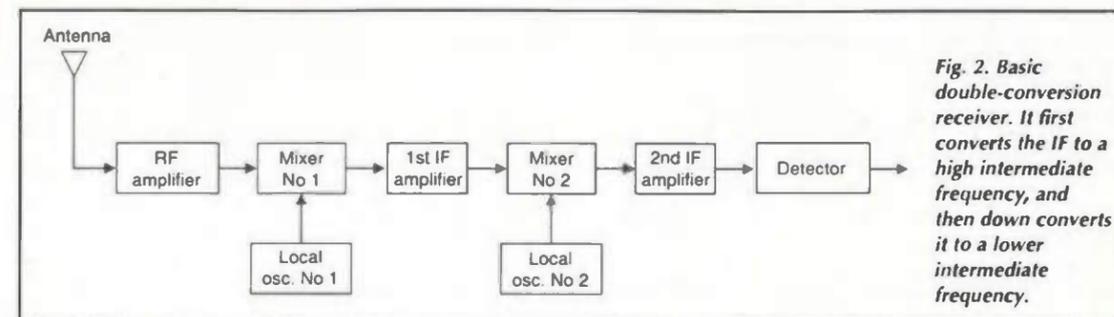


Fig. 2. Basic double-conversion receiver. It first converts the IF to a high intermediate frequency, and then down converts it to a lower intermediate frequency.

## Detector stage

The detector demodulates the RF signal, and recovers whatever audio – or other information – is to be heard by the listener.

In a straight AM receiver, the detector will be an ordinary half-wave rectifier and ripple filter. In this case it is called an envelope detector.

In other detectors – notably double sideband suppressed carrier (DSBSC), single-sideband suppressed carrier (SSBSC or SSB), or continuous wave (CW or Morse telegraphy), a second local oscillator is heterodyned with the IF signal. This is usually called a beat frequency oscillator (BFO) and it operates near the intermediate frequency.

The resultant difference signal is the recovered audio. That type of detector is called a product detector. Many AM receivers today have a sophisticated synchronous detector, rather than the simple envelope detector.

## Amplifying the audio signal

Audio amplifiers are used to finish the signal processing. They boost the output of the detector to a usable level to drive a loudspeaker or set of earphones.

Audio amplifiers are sometimes used to provide additional filtering. It is quite common to find narrow band filters to restrict audio bandwidth, or notch filters to eliminate interfering signals that make it through the IF amplifiers intact.

## Double and triple-conversion receivers

Double and triple-conversion receivers are designed to take advantage of two aspects of radio design. The first is the fact that a high intermediate frequency will yield superior image performance, and the second is that it is easier to get high gain and bandwidth limiting filter characteristics at low frequencies.

Figure 2 shows a basic double-conversion receiver. It first converts the IF to a high intermediate-frequency, and then down converts it to a lower IF.

The particular frequencies selected for the first and second IF depend on the application. In high-frequency shortwave receivers, the first IF will be in the order of 50MHz to gain the advantages of a high intermediate frequency – namely better image response. The second IF will be 10.7 MHz, 9MHz, 8.83MHz or 455kHz depending on the design.

In the VHF/UHF bands the high IF may be 10.7MHz, 50MHz or 70MHz, whereas the second IF will be 10.7MHz or 455kHz, depending on the design.

## Direct-conversion receivers

The direct conversion receiver (DCR) is a sub-set of the superheterodyne in which the intermediate frequency is equal to the base-band frequencies. It converts radio signals directly to audio, rather than to an IF.

The local oscillator on the direct-conversion receiver is tuned to either the RF signal, or to a certain offset that

depends on the tone that you wish to listen to in CW reception. The result is direct audio conversion in the DCR receiver.

## Receiver performance factors

There are three basic areas of receiver performance that must be considered. Although interrelated, they are sufficiently different to merit individual consideration: noise, static attributes and dynamic attributes. I will look at all of these areas. But first let's look at the units of measure that we will use.

**Input signal voltage.** Input signal level, when specified as a voltage, is typically stated in either microvolts ( $\mu\text{V}$ ) or nanovolts ( $\text{nV}$ ). The volt is simply too large a unit for practical use on radio receivers. Signal input voltage – or sometimes power level – is often used as part of the sensitivity specification, or as a test condition for measuring certain other performance parameters.

There are two forms of signal voltage that are used for input voltage specification: source voltage  $V_{EMF}$  and potential difference  $V_{PD}$ , as illustrated in Fig. 3. The source voltage  $V_{EMF}$  is the open-terminal, i.e. no load, voltage of the signal generator or source. Potential difference,  $V_{PD}$ , is the voltage that appears across the receiver antenna terminals with the load connected. The load is the receiver antenna input impedance,  $R_{in}$ .

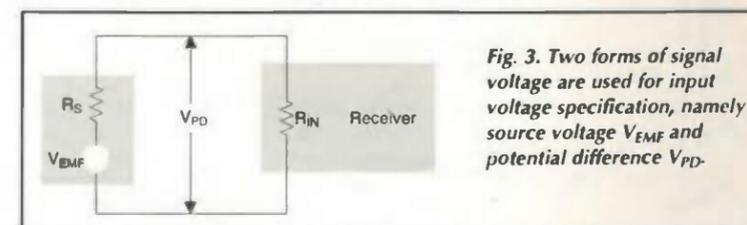


Fig. 3. Two forms of signal voltage are used for input voltage specification, namely source voltage  $V_{EMF}$  and potential difference  $V_{PD}$ .

When  $R_S = R_{in}$ , the preferred 'matched impedances' case in radio receiver systems, the value of  $V_{PD}$  is one-half  $V_{EMF}$ . This can be seen in Fig. 3 by noting that  $R_S$  and  $R_{in}$  form a voltage divider network driven by  $V_{EMF}$ , and with  $V_{PD}$  as the output. This is,

$$V_{PD} = \frac{V_{EMF} R_{IN}}{R_S} \quad (1)$$

It requires only a little algebra to convert signal levels from one unit of measure to another. See the end of the panel entitled 'Special units'. This job is sometimes necessary when a receiver manufacturer mixes methods in the same specifications sheet. In the case of dBm and dB $\mu\text{V}$ , 0dB $\mu\text{V}$  is  $1\mu\text{V}$   $V_{EMF}$ , or a  $V_{PD}$  of 0.5V, applied across 50 $\Omega$ , so the power dissipated is  $5 \times 10^{-15}$  watts, or -113dBm.

## Noise considerations

A radio receiver must detect signals in the presence of noise. The signal-to-noise ratio, or SNR, is the key here

because a signal must be above the noise level before it can be successfully detected and used.

Noise comes in a number of different guises, but for sake of this discussion we can divide them into two classes: sources external to the receiver and sources internal to the receiver.

There is little one can do about the external noise sources, for they consist of natural and man-made electromagnetic signals that fall within the pass-band of the receiver. Figure 4a) shows an approximation of the external noise situation from the middle of the AM broadcast band to the low end of the VHF region. A somewhat different view, which captures the severe noise situation seen by receivers, is shown in Fig. 4b).

One must select a receiver that can cope with external

noise sources – especially if the noise sources are strong.

Some natural external noise sources are extraterrestrial. For example, if you aim a Yagi beam antenna at the eastern horizon prior to sunrise, a distinct rise of noise level occurs as the Sun slips above the horizon. This is especially so in the VHF region – the 150-152MHz band is used to measure solar flux.

The reverse occurs in the west at sunset, but it is less dramatic because atmospheric ionisation decays much slower than it is generated.

The receiver's internal noise sources are determined by the design of the receiver. Ideal receivers produce no noise of their own. Output from the ideal receiver would contain only the noise that was present at the input along with the radio signal. But real receiver circuits produce a certain level of internal noise of their own.

Even a simple fixed-value resistor is noisy. Figure 5a) shows the equivalent circuit for an ideal, noise free resistor, while Fig. 5b) shows a practical real-world resistor.

The noise in the real-world resistor is represented in Fig. 5b) by a noise voltage source,  $V_n$ , in series with the ideal, noise free resistance,  $R_i$ . At any temperature above absolute zero – i.e. 0K or about -273°C – electrons in any material are in constant random motion.

Because of the inherent randomness of that motion, however, there is no detectable current in any one direction. In other words, electron drift in any single direction is cancelled over even short time periods by equal drift in the opposite direction.

Electron motions are therefore statistically de-correlated. There is, however, a continuous series of random current pulses generated in the material, and those pulses are seen by the outside world as noise signals.

If a perfectly shielded 50Ω resistor is connected across the antenna input terminals of a radio receiver, the noise level at the receiver output will increase by a predictable amount over the short-circuit noise level. Noise signals of this type are called by several names: thermal agitation noise, thermal noise, or Johnson noise. This type of noise is also called 'white noise' because it has a very broadband – nearly Gaussian – spectral density.

The thermal noise spectrum is dominated by mid-frequencies – of  $10^4$  to  $10^5$ Hz – and is essentially flat. The term 'white noise' is a metaphor developed from white light, which is composed of all visible colour frequencies. The expression for such noise is:

$$V_n = \sqrt{4KTRB} \quad (4)$$

Here,  $V_n$  is the noise potential in volts,  $K$  is Boltzmann's constant ( $1.38 \times 10^{-23}$  J/K) and  $T$  is the temperature in kelvins, normally set to 290 or 300K by convention. Also,  $R$  is the resistance in ohms and  $B$  is the bandwidth in hertz.

Table 1 and Fig. 6 show noise values for a 50Ω resistor at various bandwidths out to 5kHz and 10kHz, respectively. Because different bandwidths are used for different reception modes, it is common practice to delete the bandwidth factor in equation 4 and write it in the form:

$$V_n = \sqrt{4KTR} \quad V / \sqrt{\text{Hz}} \quad (5)$$

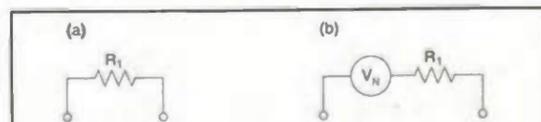


Fig. 5. Even a simple fixed-value resistor is noisy. The equivalent circuit for an ideal, noise free resistor is shown in (a), while (b) shows a practical real-world resistor.

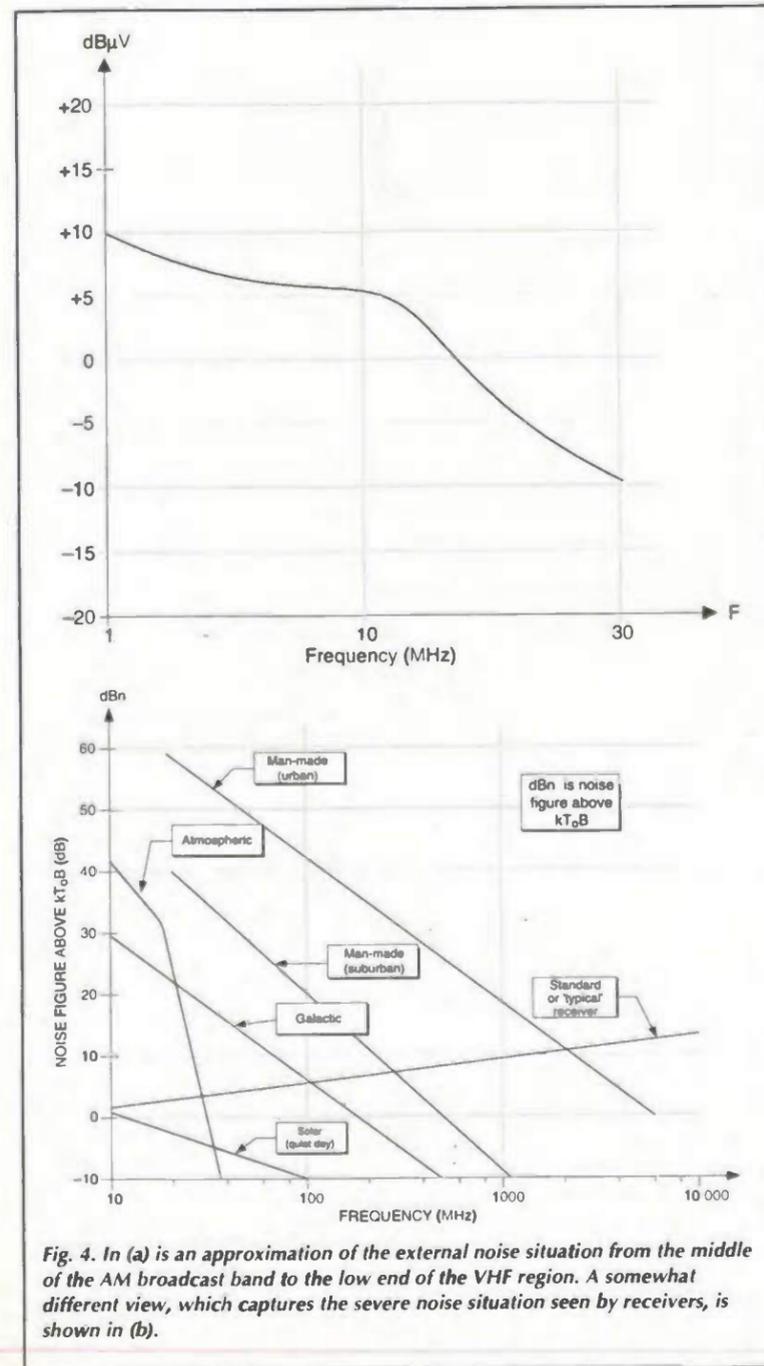


Fig. 4. In (a) is an approximation of the external noise situation from the middle of the AM broadcast band to the low end of the VHF region. A somewhat different view, which captures the severe noise situation seen by receivers, is shown in (b).

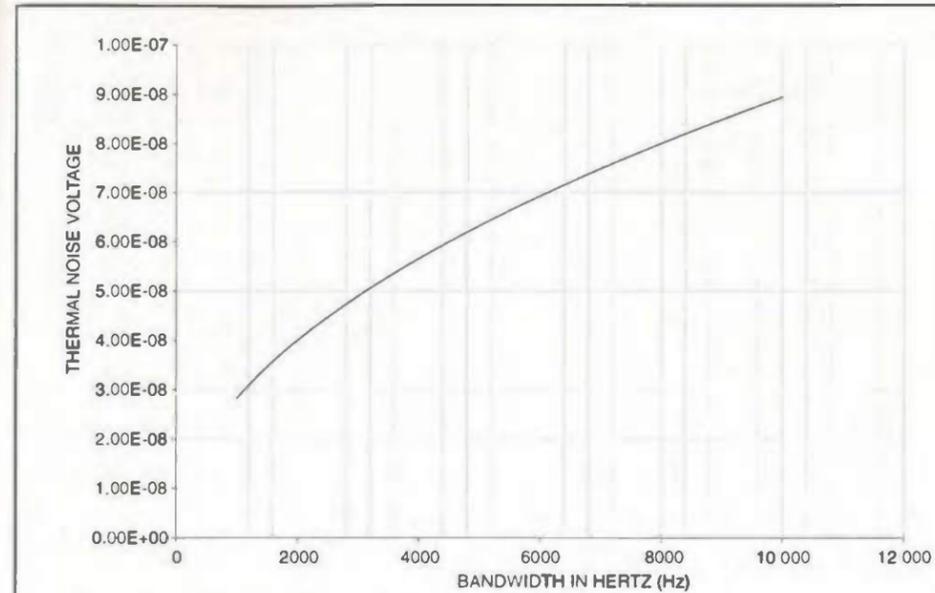


Fig. 6. Noise values for a 50Ω resistor at various frequencies.

Table 1. Noise values for a 50Ω resistor at various frequencies.

BW (Hz)	Noise voltage x E-08
500	1
1000	1.41
1500	1.73
2000	2
2500	2.24
3000	2.45
3500	2.65
4000	2.83
4500	3
5000	3.16
5500	3.32
6000	3.46
6500	3.61
7000	3.74
7500	3.87
8000	4
8500	4.12
9000	4.24
9500	4.36
10000	4.47

With equation 5, you can find the noise voltage for any particular bandwidth by taking its square root and multiplying it by the equation. This equation is essentially the solution of the previous equation normalised for a 1Hz bandwidth.

**Signal-to-noise ratio**

Receivers are evaluated for quality on the basis of signal-to-noise ratio, also known as S/N or 'SNR', and sometimes denoted  $S_n$ .

The goal of the designer is to enhance the SNR as much as possible. Ultimately, the minimum signal level detectable at the output of an amplifier or radio receiver is that level which appears just above the noise floor level. Therefore, the lower the system noise floor, the smaller the minimum allowable signal.

**Noise factor, noise figure and noise temperature.** The noise performance of a receiver or amplifier can be defined in three different, but related, ways: noise factor ( $F_n$ ), noise figure (NF) and equivalent noise temperature ( $T_e$ ); these properties are definable as a simple ratio, decibel ratio or Kelvin temperature, respectively.

**Noise factor ( $F_n$ ).** For components such as resistors, the noise factor is the ratio of the noise produced by a real resistor to the simple thermal noise of an ideal resistor. The noise factor of a radio receiver – or any system – is the ratio of output noise power,  $P_{no}$ , to input noise power,  $P_{ni}$ .

$$F_n = \left[ \frac{P_{no}}{P_{ni}} \right]_{T=290K} \quad (6)$$

In order to make comparisons easier the noise factor is usually measured at the standard temperature  $T_o$  of 290K – standardised room temperature – although in some countries 299K or 300K are commonly used. The differences are negligible.

It is also possible to define noise factor  $F_n$  in terms of the output and input signal-to-noise ratios:

$$F_n = \frac{S_{NI}}{S_{NO}} \quad (7)$$

Here,  $S_{NI}$  is the input signal-to-noise ratio and  $S_{NO}$  is the output signal-to-noise ratio.

**Noise figure (NF).** The noise figure is frequently used to measure the receiver's 'goodness,' i.e. its departure from 'idealness.' Thus, it is a figure of merit. The noise figure is the noise factor converted to decibel notation:

$$NF = 10 \log(F_n) \quad (8)$$

Here, NF is the noise figure in decibels,  $F_n$  is the noise factor and log refers to base-10 logarithm.

**Noise temperature ( $T_e$ ).** The noise 'temperature' is a means for specifying noise in terms of an equivalent noise temperature. That is, the noise level that would be produced by a matching resistor – 50Ω for example – at that temperature, expressed in kelvins.

Evaluating the noise equations shows that the noise power is directly proportional to temperature in kelvins. It also shows that noise power collapses to zero at the temperature of absolute zero (0K).

Note that the equivalent noise temperature  $T_e$  is not the physical temperature of the amplifier, but rather a theoretical construct that is an equivalent temperature that produces that amount of noise power in a resistor. The noise temperature is related to the noise factor by:

$$T_e = (F_n - 1) T_o \quad (9)$$

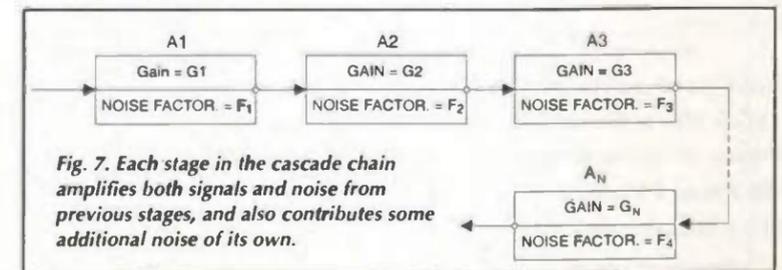


Fig. 7. Each stage in the cascade chain amplifies both signals and noise from previous stages, and also contributes some additional noise of its own.

and to noise figure by,

$$T_e = KT_o \log^{-1} \left[ \frac{NF}{10} \right] - 1 \quad (10)$$

Noise temperature is often specified for receivers and amplifiers in combination with, or in lieu of the noise figure.

**Noise in cascade amplifiers**

A noise signal is seen by any amplifier following the noise source as a valid input signal.

Each stage in the cascade chain, Fig. 7, amplifies both signals and noise from previous stages, and also contributes some additional noise of its own. Thus, in a cascade amplifier the final stage sees an input signal that consists of the original signal and noise amplified by each successive stage plus the noise contributed by earlier stages.

The overall noise factor for a cascade amplifier can be calculated from Friis' noise equation,

$$F_N = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots + \frac{F_N - 1}{G_1 G_2 \dots G_{N-1}} \quad (11)$$

Here,  $F_N$  is the overall noise factor of  $N$  stages in cascade,  $F_1$  is the noise factor of stage 1,  $F_2$  is the noise factor of stage 2,  $F_N$  is the

noise factor of the  $n$ th stage,  $G_1$  is the gain of stage 1,  $G_2$  is the gain of stage 2 and  $G_{N-1}$  is the gain of stage  $(N-1)$ .

As you can see from Friis' equation, the noise factor of the entire cascade chain is dominated by the noise contribution of the first stage or two. High-gain, multi-stage RF amplifiers typically use a low-noise amplifier, or LNA, circuit for the first stage or two in the cascade chain. Thus, you will find an LNA at the feed point of a satellite receiver's dish antenna, and possibly another one at the input of the receiver module itself. Other amplifiers in the chain might be more modest without harming system performance.

The matter of signal-to-noise ratio (S/N) is sometimes treated in different ways that each attempt to crank some reality into the process. The signal-plus-noise-to-noise ratio (S+N/N) is found quite often. As the ratios get higher, the S/N and S+N/N converge (only about 0.5dB difference at ratios as little as 10dB). Still another variant is the SINAD (signal-plus-noise-plus-distortion-to-noise) ratio.

The SINAD measurement takes into account most of the factors that can deteriorate reception. ■

The next article in this set will look at the receiver noise floor and the static measures of receiver importance, such as sensitivity and selectivity.

## Antennas and propagation for wireless communication systems

**How to pay**

Antennas and propagation for wireless communication systems

I enclose a cheque/bank draft for £ \_\_\_\_\_  
(payable to Cumulus Business Media)

Please charge my credit/charge card

Mastercard  American Express  Visa  Diners Club

Credit Card No: \_\_\_\_\_ Expiry Date: \_\_\_\_\_

Signature of Cardholder \_\_\_\_\_

Cardholder's statement address: (please use capitals)


Name \_\_\_\_\_

Address \_\_\_\_\_

Post Code \_\_\_\_\_ Tel: \_\_\_\_\_

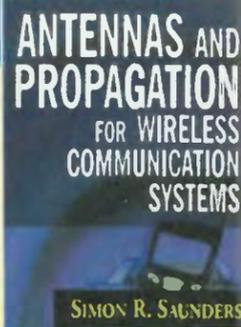**Post your completed order form to:-**

Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road Cheam, Surrey, SM3 8BZ  
UK Price: £42.50 Europe £45.00 ROW £47.50  
Price includes delivery



This will be a vital source of information on the basic concepts and specific applications of antennas and propagation to wireless systems, covering terrestrial and satellite radio systems in both mobile and fixed contexts. Antennas and propagation are the key factors influencing the robustness and quality of the wireless communication channel and this book includes:

- Illustrations of the significance and effect of the wireless propagation channel
  - Overview of the fundamental electromagnetic principles underlying propagation and antennas
  - Basic concepts of antennas and their application to specific wireless systems
  - Propagation measurement, modelling and prediction for fixed links, macrocells, microcells, picocells and megacells
  - Narrowband and wideband channel modelling and the effect of the channel on communication system performance
  - Methods that overcome and transform channel impairments to enhance performance using diversity, adaptive antennas and equalisers
- It will be essential reading for wireless communication engineers as well as for students at postgraduate or senior undergraduate levels.**
- Distinctive features of this book are:**
- Examples of real world practical system problems of communication system design and operation
  - Extensive worked examples
  - End of chapter questions
  - Topical and relevant information for and about the wireless communication industry



## Electronics World reader offer: x1, x10 switchable oscilloscope probes, only £21.74 a pair, fully inclusive\*

\* Additional pairs as part of the same order, only £19.24 each pair.

Please supply the following:

**Probes**

Name \_\_\_\_\_ Total \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Postcode \_\_\_\_\_ Telephone \_\_\_\_\_

Method of payment (please circle)

**Cheques should be made payable to**

**Cumulus Business Media**

Access/Mastercard/Visa/Cheque/PO

Credit card no \_\_\_\_\_

Card expiry date \_\_\_\_\_ Signed \_\_\_\_\_

Please allow up to 28 days for delivery

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74

UK/Europe to Probe Offer, Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ

Readers outside Europe, please add £2.50 to your order.

**Specifications**

<b>Switch position 1</b>	
Bandwidth	DC to 10MHz
Input resistance	1MΩ - i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC
<b>Switch position 2</b>	
Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10MΩ ±1% if oscilloscope i/p is 1MΩ
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC

**Switch position 'Ref'**  
Probe tip grounded via 9MΩ, scope i/p grounded

## Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly.

Send your ideas to: Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ

## Stable go/no-go voltage indicator

The following circuit gives instant indication if a voltage is between two pre-set limit values or if it falls outside the limits. It has a temperature-stable internal voltage reference and so its accuracy is essentially determined by the stability of the external resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .

At the core of the circuit is the TL4301, which behaves like a switch with an elevated trigger threshold. A simplified circuit below depicts the behaviour. When the trigger voltage is above 2.5V, the device is on. When the trigger voltage is below 2.5V, it is off.

In the basic circuit, the trigger voltage presented to pin 3, is determined by the ratio of  $R_1/R_3$  and  $R_2/R_4$ .

When the measured voltage  $V$  is below the lower limit determined by the values of  $R_1$ ,  $R_2$ ,  $T_1$  and the LED will be off. When voltage  $V$  is above the lower limit but smaller than the upper limit,  $T_1$  will be on and the LED will light.

The voltage is within the limit conditions. When  $V$  is above both limits,  $T_2$  is also on and the LED is extinguished. Accuracy of the circuit is independent of supply voltage.

For go/no-go measurements on low impedance voltages – for example a check on power supply rail voltages, etc. – the LED can be powered from the voltage being measured. The only inaccuracy this will introduce is any drop in the voltage under test due to supplying the current for the LED. If the impedance is low and there is sufficient current available, this should be negligible.

The value of  $R_1/R_2$  etc., can be calculated to set a particular threshold voltage by,


$$V_{lower\ limit} = \frac{2.5(R_1 + R_3)}{R_3}$$

$$V_{upper\ limit} = \frac{2.5(R_2 + R_4)}{R_4}$$

The table gives some useful values for common voltages.

John Rowe  
Tai Po  
Hong Kong  
F35

£75 winner

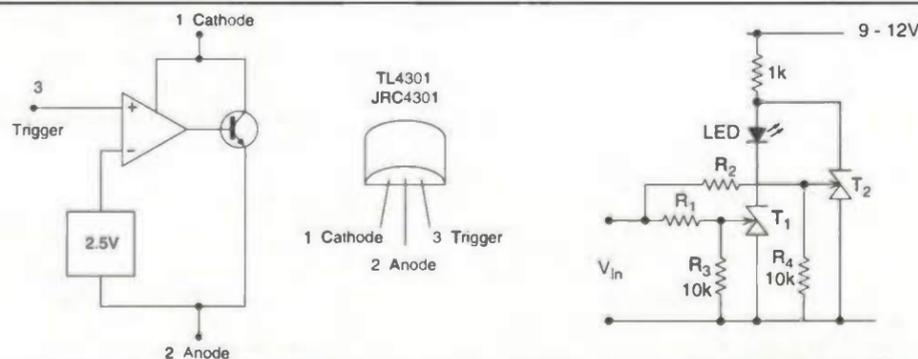

$V_{lower\ limit}$	$V_{upper\ limit}$	$R_1$	$R_2$	$R_3, R_4$ (all 10kΩ)	Application
17V	19V	58k	66k		LNB H voltage
14.25	15.75	47k	53k		15V regulator
12.5	14	40k	46k		LNB V voltage
11.4	12.6	35k	40.6k		12V regulator
9.5	12	28k	38k		Scart pin 8 (4x3)
4.75	5.25	9k	11k		5V regulator
4.5	7.0	8k	18k		Scart pin 8 (16x9)

## An optical audio isolator

A challenge recently arose to transfer audio across a high-voltage boundary without using transformers or capacitors, or RF of any kind. Initial tests with photovoltaic isolators, such as the PV15100 indicated that audio transfer was just about possible, but signals heard on common low-impedance headphones were very weak and distorted. So I developed the active circuit shown in Fig. 1.

It makes use of a matched pair of MCT2E single-transistor opto-couplers, which have a current-transfer-ratio of approximately 100%. The output side is powered from a pair of 1.5V cells. On the input side, it is essential to bias the LEDs in the couplers with about 1V, provided by  $R_2$ ,  $D_1$ ,  $D_2$  and  $R_3$ ,  $D_3$ ,  $D_4$ . These are fed from another pair of 1.5V cells.

Resistors  $R_2$  and  $R_3$  are chosen so that a standing current of about 600pA flows through the output transistors, thus eliminating crossover distortion.


When a signal is applied via  $R_1$ , a linear transfer is obtained, and the frequency response extends from below 100Hz to above 10kHz. Note that the circuit is essentially current-driven, and  $R_1$  may need to be altered to suit your hi-fi amplifier.

To power-down, it is necessary to disconnect the cells on the input side only, since the output ones then suffer less than 100nA transistor leakage current only.

For stereo, the batteries are shared between the two

channels. In certain airliners, the audio to headphones is literally 'piped', but transfer through air was outside the scope of this wager!

C J D Catt  
Cambridge  
F46

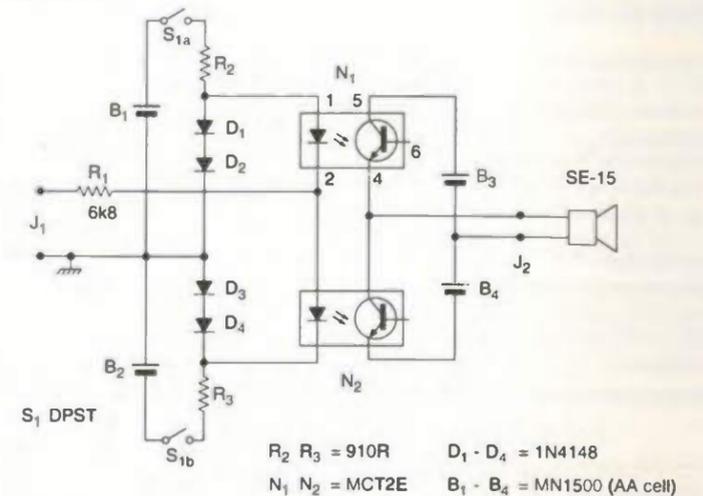

## Ten year index: new update

**TABLE OF CONTENTS**

- Applications
  - Applications by description
  - Applications by part numbers
  - Company addresses
- Books
  - Circuit Ideas
  - Information
  - Subject Index
  - Analogue Design
  - Audio
  - Antonics
  - Broadcast
  - Communications
  - Components
  - Computing
  - Consumer Electronics
  - Control Electronics
  - Digital & DSP Design
  - History

The Electronics World SoftIndex runs from January 1988 to May 1996 and contains references to 1300 articles and 800 circuit ideas. There is a separate author index with full cross references. Reprints can be obtained for all the articles in this index – see the information section for more details. For up to date information about Electronics World see our website at <http://www.softcopy.co.uk>

Search Copy Note About Exit

[www.softcopy.co.uk](http://www.softcopy.co.uk)

Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* index indexes on paper for volumes 100, 101, and 102 are available at £2 each, excluding postage.

## Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications – including a synopsis for each.

The EW index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format. Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

### Ordering details

The EW index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders. Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide. For enquires about photocopies etc please send an sae to SoftCopy Ltd. Send your orders to **SoftCopy Ltd, 1 Vineries Close, Cheltenham GL53 0NU.** Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

## Emergency light and alarm

This emergency light and alarm is powered by two AA Ni-Cd batteries and features four switchable options.

The circuit is permanently plugged into a mains socket and Ni-Cd batteries are trickle-charged. When a power outage occurs, the lamp automatically illuminates. Instead of illuminating a lamp, an alarm sounder can be chosen.

When power is restored, the lamp or the alarm is switched off. A switch provides a 'latch-up' function, in order to extend lamp or alarm operation even when power is restored.

Circuit operation is as follows. Mains voltage is reduced to about 12V DC at the 10µF capacitor's terminals, by means of the reactance of the 330nF 400V capacitor and the diode bridge. Thus avoids the use of a mains transformer.

Trickle-charging current for the battery is provided by the series 390Ω resistor, diode and the green LED that also monitors the presence of mains supply and correct battery charging.


BC327 and BC337 transistors form a self-latching pair that start operating when a power outage occurs. In this case, BC547 biasing becomes positive, so this transistor turns on the self-latching pair.

If SW<sub>3</sub> is set as shown in the circuit diagram, the lamp illuminates via SW<sub>2</sub>, which is normally closed; if set the other way, a square wave audio frequency generator formed by the rightmost couple of transistors and related components is activated, driving the loudspeaker.

If SW<sub>1</sub> is left open, when mains supply is restored the lamp or the alarm continue to operate. They can be disabled by opening the main on-off switch SW<sub>2</sub>.

If SW<sub>1</sub> is closed, restoration of the mains supply terminates lamp or alarm operation, by applying a positive bias to the base of the p-n-p transistor.

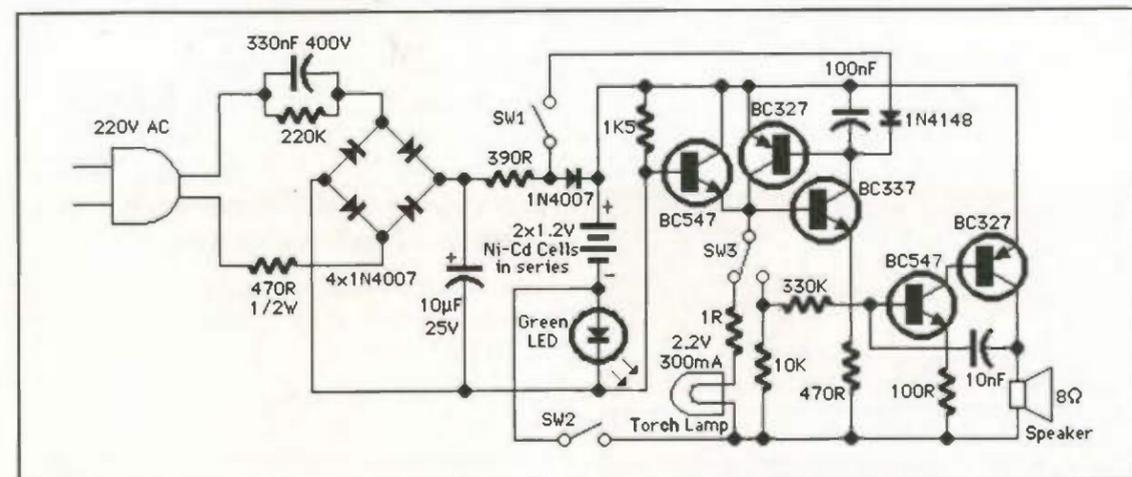**Flavio Dellepiane**  
Genoa  
Italy  
F48



## Slow diode as fast spike suppressor

One of the most accommodating features of 'flyback' – also known as 'boost' – switch mode is that the primary-to-secondary flyback voltage is proportional to the turns ratio under any load condition. Voltage is therefore easily regulated by sensing the primary voltage.


One upset though is that spikes rise to the clamp or snubber voltage due in the main to stray inductance. The solution is

generally to sample after a slight delay to let things settle down. This works well, especially with dedicated management hardware, but is not ideal for minimalist design.

Disregarding the tenet, 'don't let slow diodes anywhere near switchers,' if the feedback is via a 1N4000 series or similar slow diode, spikes are blocked, in effect delaying sampling. A nominal resistance load is of course required but this is high and may by default be that of the input resistance of the control elements.

Maximum switching speed is not specified for such devices, but a slow diode can be relied on to be slow. Inhibiting of spikes and fast transients is pretty efficient. This 'wheeze' has been found to be reliable, accurate, repeatable and economical. Sometimes it pays to think laterally, and application is of course not limited to this example. One could envisage a cheaper – and perhaps more effective – alternative to, say, data line filters.

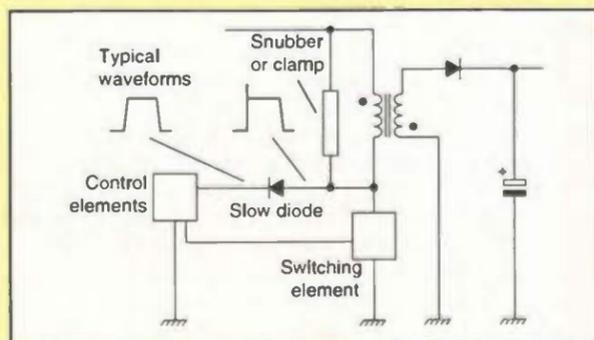**Andy Robertson**  
Girvan  
Ayrshire  
F51



## Pandora's drums

Unique and atmospheric music recorded in the early 1900s – the days before 78s.

**£11.99**

Available exclusively from  
**Electronics World**

21 tracks – 72 minutes of recordings made between 1900 and 1929. These electronically derived reproductions are no worse than – and in many cases better than – reproductions of early 78rev/min recordings – some are stunning...

All tracks on this CD were recorded on DAT from cylinders produced in the early 1900s. Considering the age of the cylinders, and the recording techniques available at the time, these tracks are of remarkable quality, having been carefully replayed using modern electronic technology by historian Joe Pengelly.

### Use this coupon to order your copy of Pandora's drums

Please send me ..... CD(s) at £11.99 each including VAT plus £1.50 carriage per order, for which I enclose:

Cheque   
Credit card details  tick as appropriate

Name

Address

Phone number

Total amount £.....

Make cheques payable to Cumulus Business Media  
Or, please debit my credit card.

Card type (Master/Visa)

Card No

Expiry date

Please mail this coupon to *Electronics World*, together with payment. Alternatively fax credit card details with order on 020 8643 8952.


Address orders and all correspondence relating to this order to Pandora's drums, Electronics World, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ

### Track

- 1 Washington Post March, Band, 1909
- 2 Good Old Summertime, The American Quartet 1904
- 3 Marriage Bells, Bells & xylophone duet, Burckhardt & Daab with orchestra, 1913
- 4 The Volunteer Organist, Peter Dawson, 1913
- 5 Dialogue For Three, Flute, Oboe and Clarinet, 1913
- 6 The Toymaker's Dream, Foxtrot, vocal, B.A. Rolfe and his orchestra, 1929
- 7 As I Sat Upon My Dear Old Mother's Knee, Will Oakland, 1913
- 8 Light As A Feather, Bells solo, Charles Daab with orchestra, 1912
- 9 On Her Pic-Pic-Piccolo, Billy Williams, 1913
- 10 Polka Des English's, Artist unknown, 1900
- 11 Somebody's Coming To My House, Walter Van Brunt, 1913
- 12 Bonny Scotland Medley, Xylophone solo, Charles Daab with orchestra, 1914
- 13 Doin' the Raccoon, Billy Murray, 1929
- 14 Luce Mia! Francesco Daddi, 1913
- 15 The Olio Minstrel, 2nd part, 1913
- 16 Peg O' My Heart, Walter Van Brunt, 1913
- 17 Auf Dem Mississippi, Johann Strauss orchestra, 1913
- 18 I'm Looking For A Sweetheart And I Think You'll Do, Ada Jones & Billy Murray, 1913
- 19 Intermezzo, Violin solo, Stroud Haxton, 1910
- 20 A Juanita, Abrego and Picazo, 1913
- 21 All Alone, Ada Jones, 1911

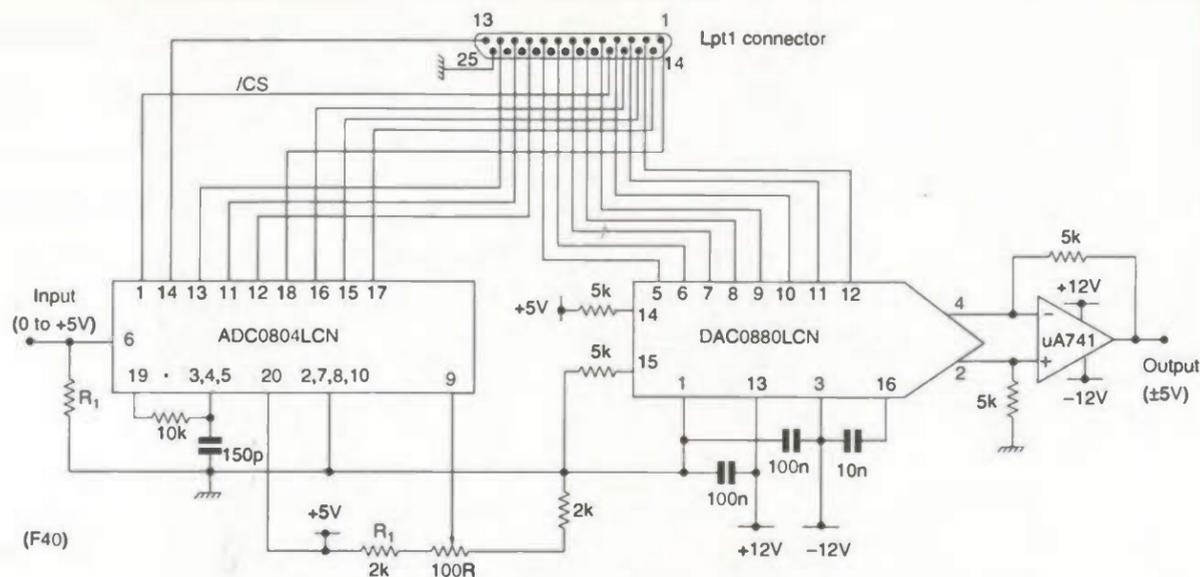**Total playing time 72.09**

21 tracks – 72 minutes of music.  
Published by *Electronics World*. All recordings reproduced by Joe Pengelly.



### Analogue interface circuit for a PC's parallel port

The bi-directional parallel interface, or LPT port, of an IBM PC compatible can be used for many applications.

One such application is to interface with the analogue world. This requires a-to-d and d-to-a converters, as shown. With this circuit, a PC can be used to sense an analogue voltage or output an analogue voltage each with 8-bit resolution. It uses an ADC0804LCN and a DAC0800LCN.

The D-to-A converter connects to the data lines of the port and is

configured to give ±5V output with the use of operational amplifier 741. The a-to-d converter is configured to accept 0 to +5V input.

Offset voltage of the a-to-d converter can be adjusted by the 100Ω potentiometer. It is set in the middle for 0V offset. An a-to-d start of conversion cycle can be started by sending H→L→H at its pin 1, CS.

The circuit can be operated from the PC's power supply. However, -12V is not available directly from the PC's power supply, so a separate supply must be used.

Simple test programs written in QuickBasic are shown. Addresses of data, status and control ports of the LPT 1 are 378<sub>16</sub>, 379<sub>16</sub> and 37A<sub>16</sub> respectively. A start-of-conversion cycle for the A-to-D converter is achieved by sending H→L→H to bit 3 of the control port. After the conversion, data is available at the control and status port.

Data bits 0 to 2 are available at the address 37A<sub>16</sub>, while data bits 3 to 7 are available at the address 379<sub>16</sub>. Bit data is extracted using an AND operation. Bit 0 and 1 of the control port and bit 7 of the status port are inverted.

In the first program shown, the XOR operation is used to correct this inherent inversion. Data output of control and status port are combined to get the converted output. Converted output is then scaled to display it on the screen.

A listing for generating a sinusoidal analogue voltage is shown in the second listing. Any data sent at the data port of the LPT 1 is converted into analogue voltage between +5V and -5V. This simple circuit can be used for many applications.

M Tariq Iqbal  
Rawalpindi  
Pakistan  
F40

#### QuickBasic program for recording and display a-to-d converter input.

```

SCREEN 12
10 h = 0
CLS
FOR y = 0 TO 640
h = h + 1
OUT &H37A, 8
OUT &H37A, 0
OUT &H37A, 8
x1 = INP(&H37A)
x1 = (x1 AND 7) XOR 3
x2 = INP(&H379)
x2 = (x2 AND 248) XOR 128
x = x/+x2
v = x/25.5 - 5
PSET (h, 240 - 240 * v / 5)
NEXT y
GOTO 10
    
```

#### QuickBasic program for generating sinusoidal output.

```


10 FOR i = 0 TO 360
pi = 3.14
x = 127 * SIN(pi * i/180) + 128
OUT &H378, CINT(x)
NEXT i
GOTO 10
    
```

### Mains voltage detector

This simple tester was developed to check for open circuit bulbs on Christmas tree lights. It is also useful for detecting live mains cables. By running the probe over an insulated cable the LED will illuminate when mains is present. If built on stripboard the gate/probe should be low capacitance to the surrounding copper. The battery can be permanently connected.

R A J Humphrey  
Abingdon  
Oxfordshire  
F41

Simple circuit detects live wires.

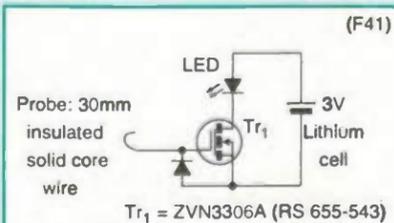

## 12V DC motor controller outputs PWM

This pwm controller provides speed control from zero to maximum angular velocity for any motor up to 250W. It provides a smooth, progressive control, for drills, kiddie cars, golf trolleys, models, robots, etc.

Below 7kΩ of control potentiometer resistance, Tr<sub>3</sub> and Tr<sub>4</sub> conduct, turning the Tr<sub>1,2</sub> constant current sink and IC<sub>1</sub> 'on'. A small potential across C<sub>3</sub> causes Schmitt trigger IC<sub>1</sub> to oscillate with a very short 'on' period. Transistor Tr<sub>5</sub>'s base is thus toggled about its emitter potential, and its collector current is amplified by Darlington Tr<sub>6</sub> to drive two 25A output transistors.

The control potentiometer track may be physically cut at 30° below maximum resistance to guarantee an electronically 'off' setting.


As the potentiometer resistance is further reduced, the voltage across C<sub>3</sub> and thus the IC<sub>1</sub> conduction period,

increases. At minimum resistance, IC<sub>1</sub>, and thus the output transistors, latch fully 'on'. An antilogarithmic potentiometer has produced very smooth and gradual clockwise power control, although ordinary 10kΩ log pots suit direct twist grip or pedal control.

All components fit in a 100 by 75 by 30mm alloy box; clip the power resistors and transistors to it. Fit additional output devices in parallel to increase power drive.

A 20:1 motor gearbox ratio with golf-trolley sized wheels should keep speed on the footpath legal. A 24Ah battery and 180W motor easily does the round on hilly golf courses.

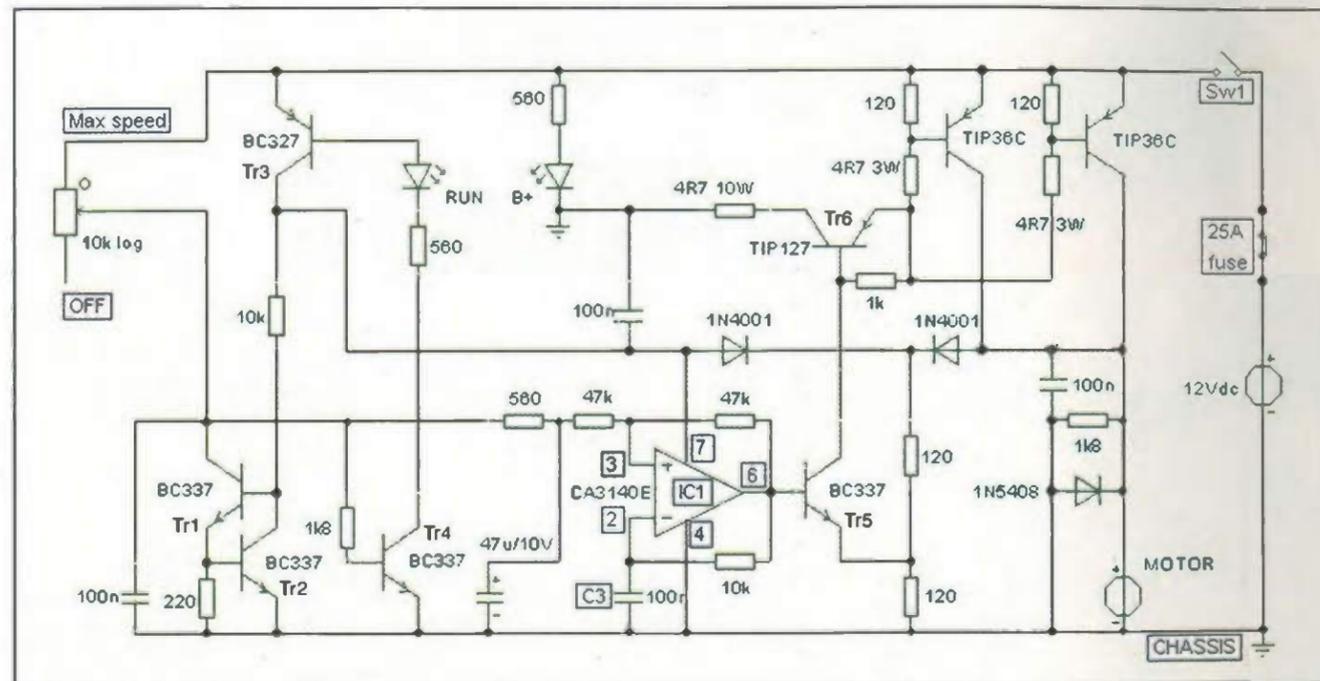Graham Maynard  
Newtonabbey  
Northern Ireland  
F49



### Minimal audio oscillators

These two oscillators took inspiration from the circuit ideas in the August 2000 issue. One was a telephone earpiece oscillator by D.M. Bridgen and the other a ceramic oscillator by C. J. D Catto.


Using reverse-biased n-p-n transistors it is possible to design basic oscillators with just three components. The earpiece oscillator operates between 8 and 16V with a frequency of 1800Hz at 12V.

The ceramic oscillator exploits its intrinsic capacitance and operates between 9.5 and 20V with a frequency of 1000Hz. This

latter oscillator draws very little power despite a sound level comparable to the earpiece oscillator.

You may try other n-p-n transistors, although I found that not all of them would oscillate. The base lead is normally left unconnected but it could be used to modulate the generated sound.

Dom Di Mario  
Milan  
Italy  
F44

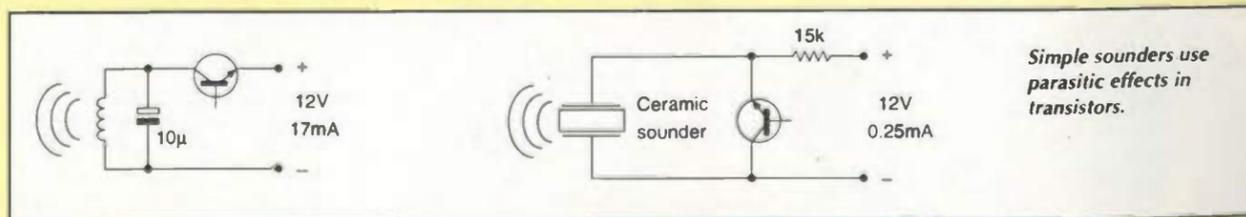

## Restoring Baird's Image



Donald F McLean

Hugh Mobberley reviews Don McLean's recent book on the work of Baird.

# Restoring Baird's image

November this year will mark the 65th anniversary of what is commonly regarded as the start of BBC Television in 1936. However, most of us are unaware that BBC Television started with regular scheduled broadcasting over four years before – in August 1932 – on the 30-line television system developed by John Logie Baird in the late 1920s.

Why is this so rarely mentioned? Part of it may be to do with the sheer complexity of television's development: the story has been oversimplified to maintain the general

public's attention. Part of it may also be to do with Baird's reputation, which steadily declined into the 1960s. Most likely though, it has to do with the sheer scale of the technological development of high definition television overshadowing all the earlier pioneering work.

So says a new book by Donald McLean, 'Restoring Baird's image,' published by the Institution of Electrical Engineers. This book makes an authoritative case for changing our thinking on early television in Britain, from the work of Baird all the way to the start of the 1936 high-definition service.

The author's credentials come from his unique restoration of several contemporary videodisc recordings made of 30-line television. These discs, covering the years 1927 to 1935, provide new reference points for the pioneering achievements of Baird and the quality of television programming in those early days. No images from these discs have previously been seen, with the later recordings of BBC TV

*Baird's early concept for a videodisc player and display. This would have been an alternative money-earner for Baird – if it had worked.*

entirely unknown until the late-1990s.

The author's work of restoring these discs forms the core of the book. Written in terms that a layman can easily follow, the story of the restoration reads like an archeological dig or a forensic analysis from a detective story. The book allows us to share with the author his genuine excitement in seeing, for the first time, video images of Baird's well-known 'Stookie Bill' ventriloquist's dummy from 1927, of the high-kicking Paramount Astoria Girls from 1933 and of the contralto, Betty Bolton.

Historical images from the dawn of television are one thing, but the book goes one major step further. Embedded in the distortion and revealed by computer-based signal analysis, are the telltale signs of the type of camera and equipment that Baird used and the reasons why the recordings were unsuccessful.

It would be a mistake to judge this book solely on the restoration of the early videodiscs. The double meaning of the book's title, 'Restoring Baird's Image' covers both the literal restoration of video recordings and the figurative restoration of not only the image and stature of Baird but also of the engineering achievements of the 30-line Baird era. What makes this book a fascinating read is its historical

coverage of the first decade of television.

Written in a conversational style, the book opens up this complex period in television's early history. The book goes a long way to help the reader appreciate the significance of these recordings and the era in which they were made.

It starts by taking us on an objective introduction to television's early history, identifying mechanically scanned television as another valid form of imaging that is of far more use today than it has ever been. A chapter on the development of videodisc and videotape recording – a rare sight in any television history book – describes how the 30-line recordings happen to be made 25 years before videotape and nearly 50 years before the videodisc player.

The achievements in the 30-line TV broadcast period before 1936 are quite a revelation. After sixty years of believing that no video recording of 30-line BBC TV existed, several discs turned up around five years ago. These video recordings were made on domestic aluminium disc audio recorders from 'off-air' broadcasts.

Akin to finding the proverbial needle in a haystack, the author has identified one of the discs as being a television special – the world's first television revue – transmitted by the BBC on 21st April 1933. Together with the other recordings, the book convincingly presents the evidence that 30-line BBC TV was in no way amateur, but was as professional and professionally produced as the later 405-line service became.

The book closes with a critical eye turned to the historians and documentary makers who have modified the history of television over the years. What separates this book from others covering the same period is its uniqueness and originality – it has both a new story to tell and illustrates an old story in a new and entirely authoritative way. Support from the leading experts on Baird, Ray Herbert and on videotape recording Martin Salter, assures the book's historical accuracy.


There are some 150 figures in the book, including 60 previously unpublished historic photographs and over 120 30-line images – the largest collection in any one publication. This is a TV historian's delight providing a refreshing 'new look' history in both words and pictures. The book's well-kept

A visit to the author's website at <http://www.dfm.dircon.co.uk> reveals many of the restored video clips from the videodiscs which it was not possible to include in his book.

secret is that the author has painstakingly cleaned up the historic photographs, removing crease marks, scratches, dust specks and mould.

The rarity of many of these pictures together with the high quality of restoration and reproduction makes this, for just the photographs alone, an attractive book to buy.

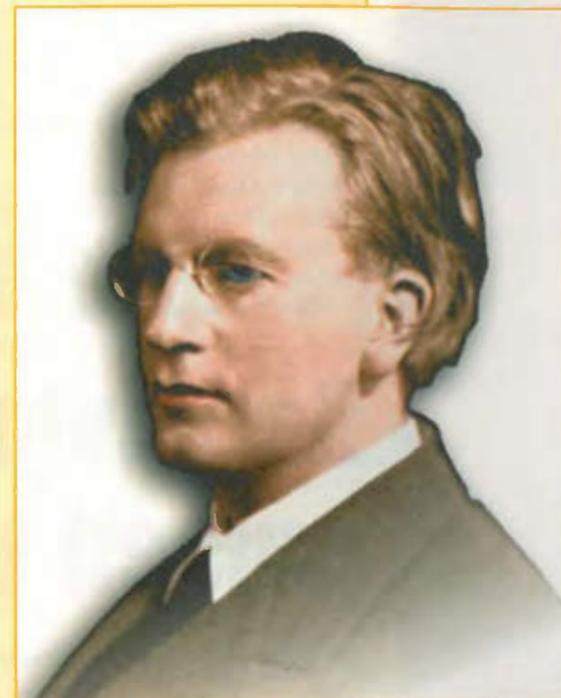To quote from the Foreword, John Trenouth of the National Museum of Photography Film and Television, describes the author's work as "an outstanding example of industrial archaeology."




John Logie Baird

*One of the book's hidden secrets: not content with restoring the early videodiscs, the author has also restored all the historical photographs in the book.*

A copy of Restoring Baird's Image can be obtained by sending a cheque for  
 UK Price £32.00 Europe £34.00  
 ROW £36.00  
 To Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ.

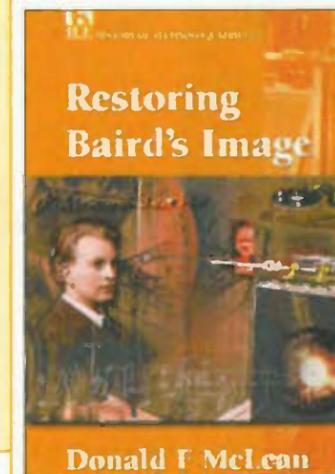Cheques should be made payable to Cumulus Business Media



### Winners!

The third winning entry from our ZXF36L01 design competition, announced in the March 2001 issue. All three winners will be receiving a voucher, redeemable at Farnell Electronic Components. Winner David Flatt receives a voucher for £500, the runners up, Mike Button and S. Vijayan Pillai, will receive vouchers of £100 each.

Many thanks to all of you who entered. We hope to publish some of those entries in the near future. All entrants will receive a cheque covering the cost of the Zetex development system. For more details on the ZXF36L01 filter/mixer, take a look at the March 2001 issue.

## Receiving multi-band pulsed ultrasonics

When receiving ultrasonic signals, band limiting helps reduce noise problems. With a wideband receiver, multiple bands are normally used, ramping up the number of components needed. £100 Farnell voucher winners **S. Vijayan Pillai** and **S. Subash** have devised a method for reducing the number of components using the mixer and oscillator features of the ZXF36L01 at the front-end of an ultrasonic receiver.

In an ultrasonic system, where a pulsed transmission of narrow band signal is involved, band-limiting the received signal reduces noise problems. Normally, band limiting is achieved by splitting the band right from the hydrophone level. This involves more hardware and sensors.

Wide-band hydrophones with built-in amplifiers are available covering 2 to 80kHz. One example is a wide-band ultrasonic sonar system whose useful range extends from 2 to 80kHz.

In the scheme described here, a ZXF36L01 does the band sampling. As a result, only one sensor and one a-to-d conversion are necessary.

Output from this system is in band-serial, bit-parallel form. The expected signal has a minimum pulse duration

of 5ms. Band processing in time is done for 2 to 85kHz, as shown in the Table.

Band sampling is done at every 0.5ms. The first 1.5ms is used for the lowest band and is separately processed. Since the converted band is limited to 19kHz, the sampling frequency of 64kHz is sufficient. A multi-channel processing scheme can be applied to the digital signal, Fig. 1.

Both mixer and band-pass filter can be realised using one ZXF36L01. An outline of the implementation is shown in Fig. 2.

For:

$$F_o = 14\text{kHz}, R = 10\text{k}\Omega, C = 1000\text{pF}$$

select  $R_f$  and  $R_i$  for a Q of 1.4. These components are

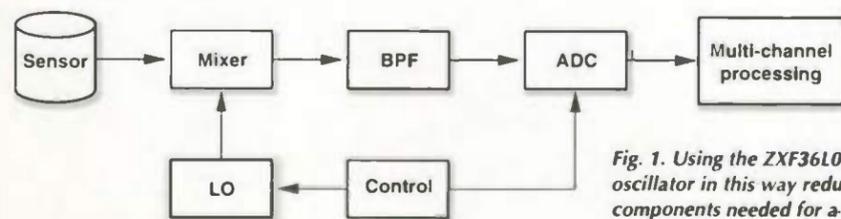


Fig. 1. Using the ZXF36L01 as a mixer and local oscillator in this way reduces the number of components needed for a multi-band sonar receiver.


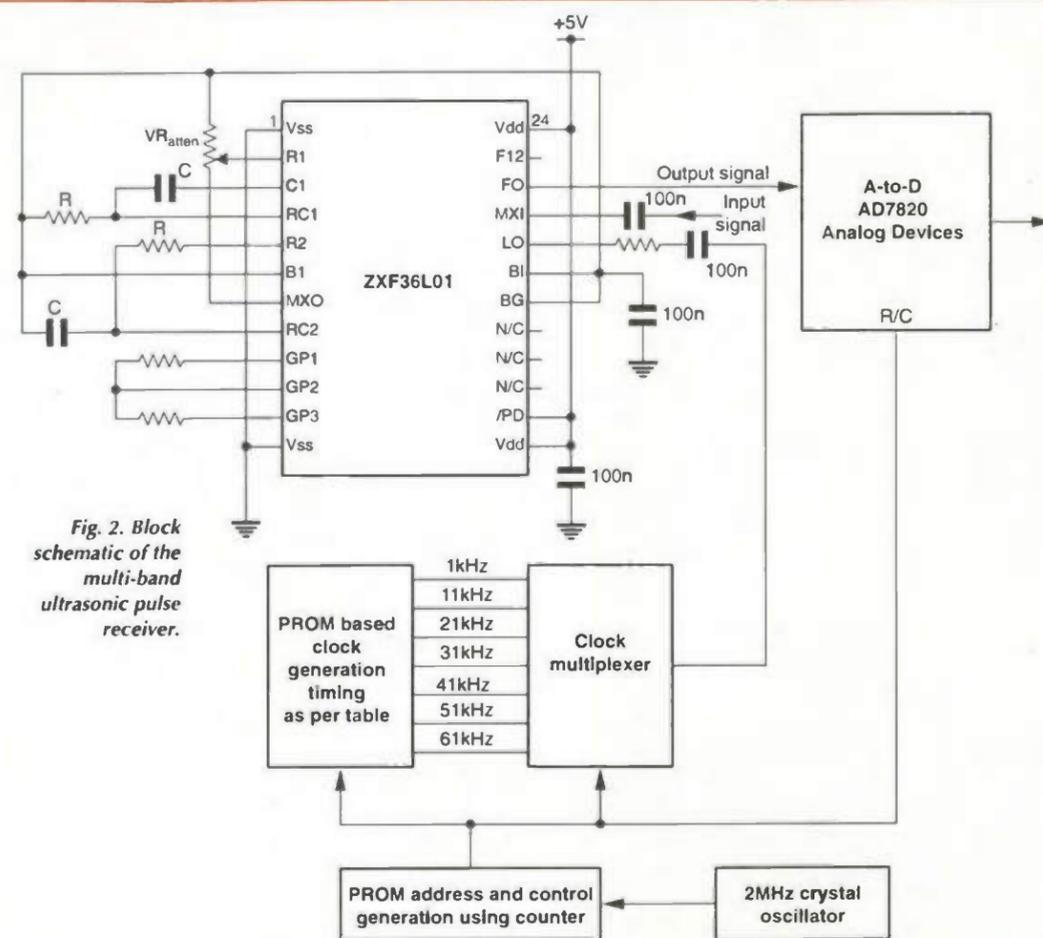


Fig. 2. Block schematic of the multi-band ultrasonic pulse receiver.

Launched this year, the ZXF36L01 is a versatile high-Q band-pass filter requiring a minimum of external components. In addition to the variable-Q analogue filter there is also a mixer block, making the device suitable for a wide range of applications. A designer's kit is available from Farnell and you can find full data on the device on Zetex's web site <http://www.zetex.com/pdf/ics/zxf36101.pdf>.

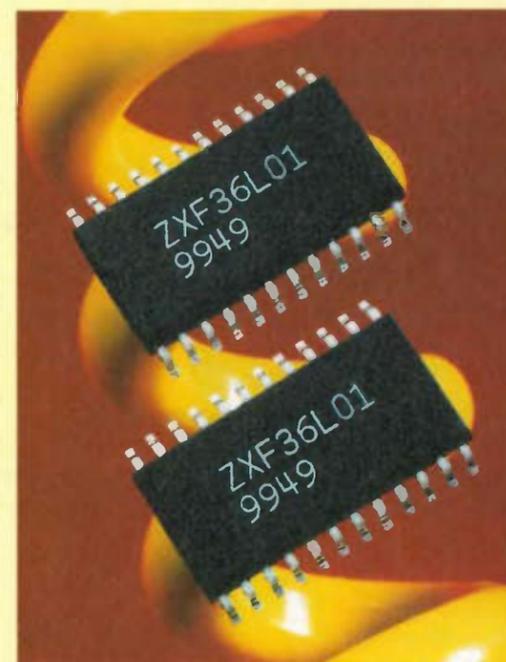

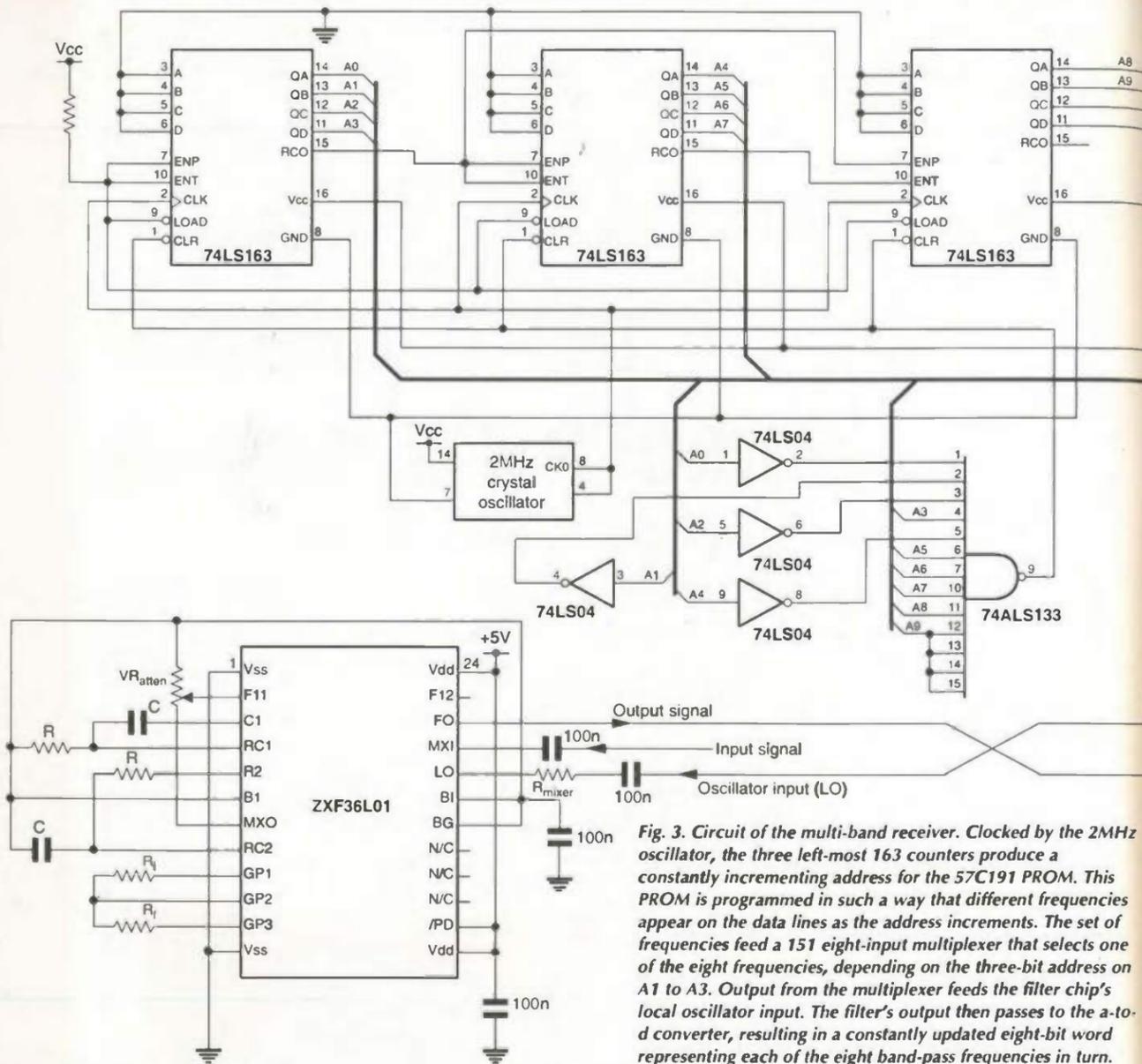


Fig. 3. Circuit of the multi-band receiver. Clocked by the 2MHz oscillator, the three left-most 163 counters produce a constantly incrementing address for the 57C191 PROM. This PROM is programmed in such a way that different frequencies appear on the data lines as the address increments. The set of frequencies feed a 151 eight-input multiplexer that selects one of the eight frequencies, depending on the three-bit address on A1 to A3. Output from the multiplexer feeds the filter chip's local oscillator input. The filter's output then passes to the a-to-d converter, resulting in a constantly updated eight-bit word representing each of the eight band-pass frequencies in turn.

shwon in Fig. 3. Since the local-oscillator clock is direct TTL output, use a value of 1kΩ for  $R_{mixer}$ . Chose  $R_{atten}$  depending up on the signal input.

Table. Band processing in time for 2 to 80kHz.

Time (ms)	Band (kHz)	LO (kHz)	Band shifted to (kHz)	Filter	Filter $Q_{eff}$
0-0.5	2-10	X	2-10	X	X
0.5-1	10-20	1	9-19	14	1.4
1-1.5	20-30	11	9-19	14	2.5
1.5-2	30-40	21	9-19	14	3.5
2-2.5	40-50	31	9-19	14	4.5
2.5-3	50-60	41	9-19	14	5.5
3-3.5	60-70	51	9-19	14	6.5
3.5-4	70-80	61	9-19	14	7.5

PROM frequency synthesiser

The PROM is a WS57C191B. This is a standard 24pin DIP slim package manufactured by Waferscale Integration, Inc. It is used as a frequency synthesiser.


An address is fed to the PROM once per microsecond and the three interlinked 74163 counters are cleared at every 1000μs. They cycle from 0 to 1000, addressing 1000 unique locations in the PROM.

If, for example, 1kHz at pin 9 of the PROM is needed, logic zero is stored in the first

$$\frac{1000000}{2 \times 1000} = 500$$

locations and then logic one to next 500 locations at the LSB (output O0) bit position of the PROM.

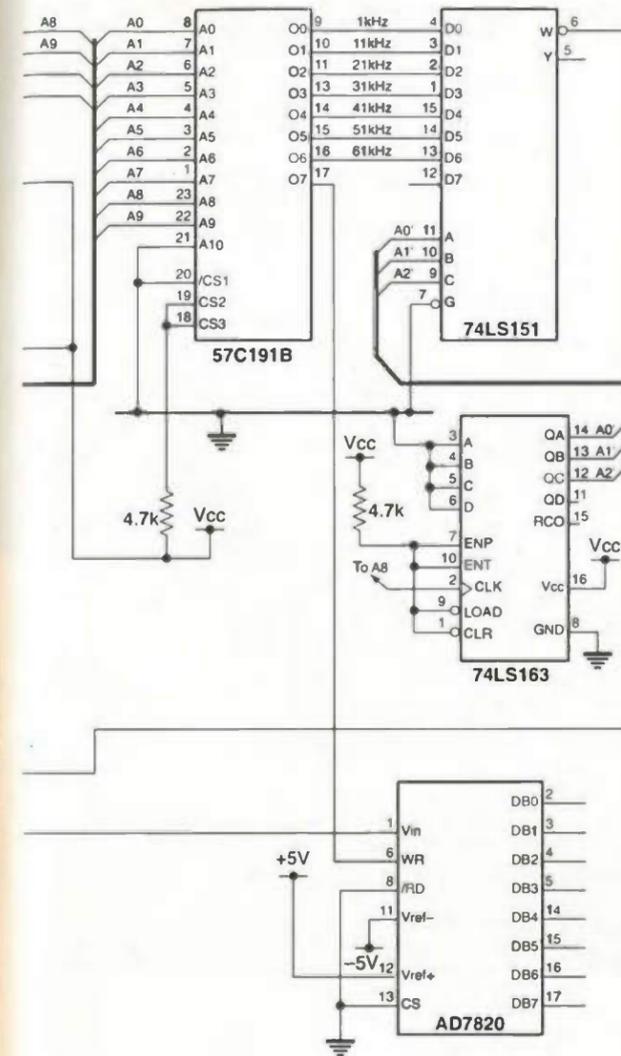Similarly if 11kHz is needed at pin 10, store logic zero for the first,



$$\frac{1000000}{2 \times 11000} = 45$$

locations, logic one in the next 46 locations, logic zero in the next 45 locations, logic one in the next 46 locations, and so on until 1000 locations are filled at the O1 output bit position of the PROM.


Other frequencies can be created at outputs O2 to O7 of the PROM in the same way. At the O7 bit position, the frequency to be generated is 64kHz, which is given as a sampling clock to the a-to-d converter.

## Make sure of your copy of *Electronics World*

It can be difficult finding a copy of *Electronics World* at local newsagents. The number of magazines being published keeps increasing, which means that newsagents have less shelf space for the display of particular titles. Specialist magazines in particular get crowded out.

There's a solution to the problem. Most newsagents provide "shop-save" and/or home-delivery services. There's no charge for a shop save. You simply ask your newsagent to order a copy for you: it will be kept on one side each month ready for you to collect. Home-delivered copies are ordered in the same way, but generally incur a delivery charge.

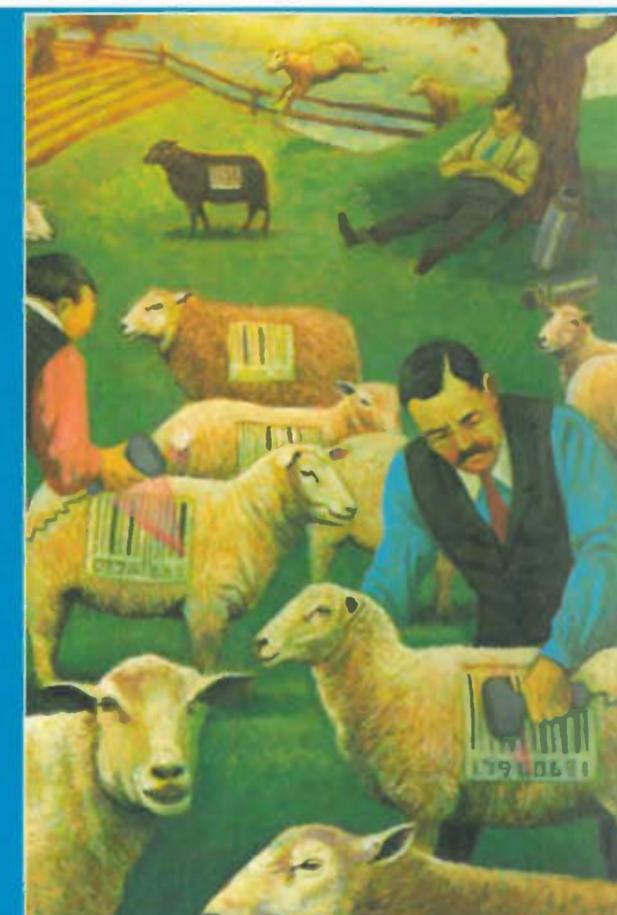A newsagent can order any magazine for you, whether or not the shop normally stocks it. If you buy your copies of *Electronics World* from a newsagent and want to make sure you get every issue, just ask at the counter.



# Self on Audio

**Douglas Self**

The cream of 20 years of Electronics World articles (focusing on recent material)

A unique collection of design insights and projects - essential for all audio designers, amateur and professional alike.

Scientific electronics based on empirical data

Douglas Self has been writing for Electronics World and Wireless World over the past 20 years, offering cutting-edge insights into scientific methods of electronics design.

This book is a collection of the essential Electronics World articles, covering twenty years of amplifier technology but with a very strong bias towards more recent material. The articles include self-build projects as well as design ideas and guidance for the professional audio designer. The result is a unique collection of design insights and projects - essential for all audio designers, whether amateur or professional.

Contents: Introduction; PRE-AMPLIFIERS: An advanced preamplifier MRPI; High-performance preamp MRP4; Precision preamp MRP10; Moving-coil head amp; Preamp '96 I; Preamp '96 II; "Overload Matters" (RIAA overload); Balanced line inputs and outputs, part 1; Balanced line inputs and outputs, part 2; POWER AMPLIFIERS: FETs less linear than BJTs; Distortion in power amplifiers 1-8; Distortion residuals; Trimodal part 1, 2; Load-invariant power amp INVAR.DOC; Common-emitter amps; Two-stage amplifiers; SPEAKERS: Excess speaker currents; Class distinction (amp classification); Relay control; Power partition diagrams; Audio power analysis.

ELECTRONICS  
WORLD



Self  
on  
Audio  
DOUGLAS SELF

Douglas Self has dedicated himself to demystifying amplifier design and establishing empirical design techniques based on electronic design principles and experimental data. His rigorous and thoroughly practical approach has established him as a leading authority on amplifier design.

Readership: Audio electronics enthusiasts;  
Professional amplifier designers;  
Power amp users  
Paperback  
Pages: 416pp

**UK Price: £26.50 Europe £27.50 ROW £28.50**

Return to Jackie Lowe, Cumulus Business Media  
Anne Boleyn House, 9-13 Ewell Road, Cheam,  
Surrey, SM3 8BZ

Please supply the following title:

**SELF ON AUDIO**

Total \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Telephone \_\_\_\_\_

Method of payment (please circle)

Mastercard/Visa/Cheque/PO

**Cheques should be made payable to  
Cumulus Business Media**

Credit card no. \_\_\_\_\_

Card expiry date \_\_\_\_\_

Signed \_\_\_\_\_

## LANGREX SUPPLIES LTD

PHONE 020 8684 1166 FAX 020 8684 3056  
DISTRIBUTORS OF ELECTRONIC VALVES  
TUBES AND SEMICONDUCTORS AND I.C.S.  
1 MAYO ROAD • CROYDON • SURREY CR0 2QP  
24 HOUR EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS  
email: langrex@aol.com

AZ31	£ p	KT66 Special	20.00	SZ4GT	3.00	GUBA	1.50
CL33	8.00	KT88 Special	20.00	6AQ5	2.00	6V6G	10.00
E88CC	15.00	N78	8.00	6AR5	6.00	6V6GT	6.00
E180F	8.50	OA2	3.00	6AS7G	7.50	6X4	3.00
E910F	3.50	OB2	3.00	6AU6GT	4.00	6X5GT	3.00
EAB08	20.00	OC3	3.00	6AU6	2.00	12AT7	3.00
EB91	4.00	OD3	3.00	6AW8A	4.00	12AU7	3.50
EBF80	1.50	PCF80	2.00	6B4G	22.00	12AX7	5.00
EBF89	1.50	PCL82	2.00	6BA6	1.50	12AX7A	7.50
EBL31	1.50	PCL85/805	2.50	6BE6	1.50	12AX7WA	6.00
ECC35	25.00	PCL86	2.50	6BH6	2.00	12BA6	2.00
ECC33	12.00	PD500	8.00	6BO7A	2.00	12BE6	2.00
ECC81	12.00	PL36	3.00	6BR7	4.00	12BH7	10.00
ECC82	3.00	PL81	2.00	6BR8	4.00	12BY7A	7.00
ECC83	5.00	PL504	3.00	6BW6	4.00	12DW7	15.00
ECC85	3.00	PL508	3.00	6BW7	3.00	12E1	10.00
ECC88	5.00	PL509/519	10.00	6BX7GT	7.50	13E1	85.00
ECC808	6.00	PL802	4.00	6BZ6	3.00	572B	27.50
ECF80	15.00	PY500A	3.00	6C4	2.00	805	45.00
ECH35	1.50	PY800/801	1.50	6C88A	3.00	807	7.50
ECH42	3.50	QOV02-6	12.00	6DC6G	5.00	811A	10.00
ECH81	3.00	QOV03-10	3.00	6CL6	3.00	812A	55.00
ECL82	3.00	QOV03-20A	10.00	6CG7	7.50	813	27.50
ECL86	5.00	QOV06-40A	12.00	6CH6	3.00	833A	85.00
ECLL800	5.00	U19	8.00	6CW4	6.00	866A	20.00
EF37A	25.00	UABC80	1.60	6DQ5	17.50	872A	30.00
EF39	3.50	UCH42	5.50	6DO6B	10.00	931A	25.00
EF40	2.75	UCL82	2.00	6F8G	8.00	2050A	12.50
EF86	4.00	UCL83	2.00	6FQ7	7.50	5687WB	6.00
EF91	5.00	UF89	4.00	6GK6	4.00	5751	6.00
EF183/4	2.00	UL41	12.00	6J5G	6.00	5763	8.00
EL33	2.00	UL84	3.00	6J5M	4.00	5814A	5.00
EL34	15.00	UY41	4.00	6J7	3.00	5842	12.00
EL34G	5.00	UY85	2.00	6JB6A	27.50	6072A	6.00
EL36	5.00	VR150/30	3.00	6J6C	27.50	6080	8.00
EL41	3.50	VR150/30	3.00	6J58C	27.50	6146B	15.00
EL84	3.00	Z759	10.00	6K6GT	4.00	6201	8.50
EL95	2.00	Z803U	15.00	6L6G	15.00	6336A	35.00
EL360	2.00	2D21	3.50	6L6GC	17.50	6550A	25.00
EL509/519	15.00	3B28	12.00	6L6WGB	10.00	6883B	15.00
EM34	7.50	4CX250B	45.00	607	3.00	7025	7.50
EM81/4/7	25.00	5R4GY	7.50	6SA7	3.00	7027A	28.00
EN91	5.00	5U4G	10.00	6SC7	3.00	7360	28.00
EZ80/EZ81	7.50	5U4GB	10.00	6SG7	3.00	7581A	15.00
GZ32	5.00	5V4G	5.00	6SL7	3.00	7586	15.00
GZ33/37	8.50	5Y3GT	2.50	6SK7	3.00	7587	20.00
KT61	15.00	SZ3	5.00	6SL7GT	5.00		
		SZ4G	6.00	6SN7GT	7.50		

OPEN TO CALLERS MON-FRI 9AM-4PM. CLOSED SATURDAY  
This is a selection from our stock of over 6,000 types. Please enquire for types not listed.  
Obsolete items are our speciality. Valves are new mainly original British or American brands.  
Terms CWO/min order £10 for credit cards.  
P&P 1-3 valves £2.00. 4-5 valves £3.00  
Add 17.5% VAT to total including P&P



CIRCLE NO.118 ON REPLY CARD

## RAEDEK ELECTRONICS

Raedek Electronics Co.  
Unit 12, Avenue Fields Industrial Estate  
Stratford Upon Avon CV37 0HT, United Kingdom  
Telephone: +44 (0) 1789 209294 Fax: +44 (0) 1789 295757  
email: sales@raedek.com www.raedek.com

Avionics  
Broadcast  
Industrial  
Marine  
Medical  
Military  
Telecoms  
etc ...



ABB  
Amperex  
Burl  
EEV  
Eimac  
GE  
ITT  
Marconi  
Motorola  
Mullard  
Thomson  
Toshiba  
etc ...


Electron Tubes • R.F. Power Transistors  
Integrated Circuits • Magnetrons  
Cathode Ray Tubes • Microwave Diodes  
Thyristors • Tube Sockets

*Many 1000s of current and obsolete  
manufactured devices in stock*

CIRCLE NO.117 ON REPLY CARD

# Free Guide to Circuit Design Solutions

Get your  
**FREE** Guide  
today!

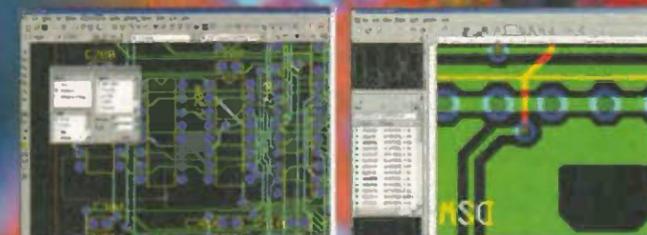

**multiSIM 2001**  
Schematic Capture, Simulation & Programmable Logic

**ultiBOARD 2001**  
Powerful PCB Layout

**ultiROUTE**  
Advanced Autorouting & Autoplacement

More electronics professionals choose Electronics Workbench than any other circuit design software. Find out why in this free guide.

Call our technical specialists on 01462 480055 for your **FREE** copy.

**ADEPT** Adept Scientific plc,  
Amor Way, Letchworth, Herts SG6 1ZA  
Tel: 01462 480055 Fax: 01462 480213 Email: ewb@adeptsience.co.uk  
WebStore: www.adeptstore.co.uk Website: www.adeptsience.co.uk

Copyright © 2001 Adept Scientific plc. All rights reserved. All trademarks acknowledged.

CIRCLE NO.110 ON REPLY CARD

**TELNET SPECIAL OFFERS**

**Special Offer**  
Telnet Suppliers and Buyers of Quality Test and Measurement Equipment at AFFORDABLE Prices.

**Challenge**  
To view a special offer for an appointment -  
Tel: 0144 8024 7165 (9.00 - 5.00)  
Fax: 0144 8024 7165 (9.00 - 5.00)  
Tel: 0144 8024 7165 (9.00 - 5.00)

**Special Offer**  
Telnet Suppliers and Buyers of Quality Test and Measurement Equipment at AFFORDABLE Prices.

# WEB DIRECTIONS

**PROTEUS VSM Models**

Proteus VSM is a powerful simulation tool for PCB design. It allows you to simulate your PCB design before it is manufactured, saving time and money. The software is easy to use and provides a wide range of simulation options.

Put your web address in front of 18,298 electronic fanatics.

Electronics World acknowledge your company's needs to promote your web site, which is why we are dedicating 3 pages in every issue to WEB ADDRESSES.

Linage only will cost £150 + vat for a full year.

Linage with colour screen shot will cost £350 + vat for a full year, this will include the above plus 3cm shot of your web site which we can produce if required.

To take up this offer or for more information call  
**Pat Bunce**  
Tel 0208 643 6207

E-mail  
p.bunce@cumulusmedia.co.uk

**ACQUIVISION**  
<http://www.acquivision.com>

AcquiVision solutions, including XY-Plotting, Oscilloscopes (with FFT), Data Logging and Custom Software, have been getting the most from computers since 1994. Download software. Telephone (01903)830502.

**AQUILA VISION**  
<http://www.aquila-vision.co.uk>

Aquila Vision specialises in supplying and supporting Embedded Microprocessor Development products from PICs to DSPs. We also stock robotics boards, Linux and general interest CD-ROM's.

**ALCATEL COMPONENTS**  
<http://www.components@alcatel.de>

**ASHWELL ELECTRONICS**  
<http://www.ashwell-hq.com>

Ashwell provide technical support for Apex Microtechnology op-amps and DC/DC'S; Aeroflex; EMP filtered connectors; M S Kennedy; Mintech obsolescence; NSC Mil/Aero; Teledyne Relays and isocom mil/optocouplers.

**ARCOM**  
<http://www.arcomcontrols.com/ew/>

A leading international supplier of communication and control technology to industry, Arcom provides leading edge solutions through a comprehensive range of market leading products.

**A.R.S.**  
<http://www.ars-surplus-stock.com>

We buy electronic, electrical, computer and test equipment. Visit our website or e-mail us at [info@ars-surplus-stock.com](mailto:info@ars-surplus-stock.com) Telephone us on 01271 867285

**BROADCASTING COMMUNICATIONS SYSTEMS**  
[www.broadercasting.co.uk](http://www.broadercasting.co.uk)

WINRADIO now brings you a complete choice in personnel computer controlled radio scanning and reception solutions • Broadcast • Media • Monitoring • Professional Amateur Radio communications

**BEDFORD OPTO TECHNOLOGY LTD**  
<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and custom, LED bargraphs, circuit board indicators, stand offs, transmissive/reflective switches, baseefa optocouplers tubular and surfacemount, pannel mount LED assemblies.

**CONCEPT ELECTRONICS**  
<http://www.conceptkey.co.uk>

Concept Keyboards are specialists in the design and manufacture of customer specified membrane panels and keyboards, and electronic design. Concept's membrane manufacture is supported by a full electronic production facility to provide a complete turnkey keyboard and electronics service, fully accredited to ISO9001.

**CONTROL SOLUTIONS**  
[www.controlsolutions.co.uk](http://www.controlsolutions.co.uk)

Data acquisition and control for beginners, hobbyists, and professionals. Perform mathematical and logical operations on data in real time. Email: [info@controlsolutions.co.uk](mailto:info@controlsolutions.co.uk)

**COOKE INTERNATIONAL**  
<http://www.cooke-int.com>  
[info@cooke-int.com](mailto:info@cooke-int.com)

Test & Measuring Equipment Operating & Service Manuals.

**CROWNHILL ASSOCIATES LTD**  
<http://www.crownhill.co.uk>

Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.

**DANIEL MCBREARTY**  
<http://www.danmcb.demon.co.uk/k/eng.html>

Experienced engineer based in London, specialist in audio and control systems. Available for design, project engineering or general consultancy. Background of high-quality work.

**DESIGNER SYSTEMS CO.**  
<http://www.designersystems.co.uk>

Electronic product design company with over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.

**ECM SELECTION**  
<http://www.ecmsel.co.uk>

For the pick of the UK's Top High-Tech Software and Hardware career opportunities - from fresh Grad/PhD to Senior Engineer/Manager - £22,000 - £70,000

**EDWIN PCB DESIGN SOFTWARE**  
<http://www.swifteurotech.co.uk>

Swift Eurotech supply the best-selling EDWIN CAD/CAE system for PCB design, including schematics, simulation and PCB design. Discounts up to 60% for non-commercial users.

**ELECTRONICS AND COMPUTING PRINCIPLES**  
<http://www.eptsoft.com>

Studying electronics or computing or just want to keep up-to-date in an easy and enjoyable way, then this fully interactive software is for you.

**EQUINOX TECHNOLOGIES UK LTD**  
<http://www.equinox-tech.com>

Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

**FARADAY TECHNOLOGY LTD**  
<http://www.faradaytech.co.uk>

Over 17 years experience in the design and manufacture of high quality passive filters and delay lines. Used in Broadcast, Telecommunications, Medical, Multimedia, and computer industries. Currently exporting worldwide

**FIELD ELECTRIC LTD**  
<http://www.fieldelectric.co.uk>

Field Electric Ltd has been successfully trading since 1958 in the re-sale of used test & measurement equipment & computer hardware. We buy and sell in small or bulk quantities and can source equipment to particular requirements. Visit our web site or call 44 01837 83736.

**FELLER UK**  
<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

**FLASH DESIGNS LTD**  
<http://www.flash.co.uk>

Flash supply low cost AVR ISP programmers (£39), MINI-ICE starter kits (from £69), Portable Easy-ICE emulators (from £199), ICE Adapters & 'C' compilers for any ATMEL AVR,

MCS51, Dallas, Hitachi M8 microcontroller. Download FLASH NEWS now. Watch out for Special Offers'. ARE YOU developing code in a Flash?

**GOOT PRODUCTS**  
<http://www.kieagoot.co.uk>

Kiea Trading Company is the sole agent of Goot products. We specialise in supplying the soldering and desoldering product range manufactured by Goot Japan for the UK market. Goot uses advanced production technology to manufacture high quality soldering iron products for industrial, professional and general purpose use.

**HSPS LTD**  
<http://dSPACE.dial.pipex.com/hsp/>

FILTER DESIGNER - Advanced analog and digital filter design software for the PC. - Standard and Professional versions. - Free download of Evaluation version.

**HTB ELEKTRONIK**  
<http://www.htb-elektronik.com>

We are selling second-hand test & measurement equipment and accessories for over 10 years, from all leading manufacturers.

**LABCENTER**  
<http://www.labcentre.co.uk>

Download evaluation versions of our unique Proteus VSM mixed mode SPICE and CPU simulator, and also the full range of Proteus PCB Design products. Register the Proteus Lite shareware versions online for as little as \$20.

**LOW POWER RADIO SOLUTIONS**  
<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and Micrel. Applications for telemetry, video and remote control.

**LEVY/LATHAM GLOBAL**  
<http://www.levylatham.com>

U.S. Military Surplus meters, plug-ins, test sets, oscilloscopes, power supplies, signal generators, spectrum analyzers and radio components from Tektronix, Hewlett Packard, Sony, Phillips and more!

**MATRIX MULTIMEDIA LTD**  
[www.matrixmultimedia.co.uk](http://www.matrixmultimedia.co.uk)

Matrix Multimedia publishes a number of highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

**NORCALL**  
<http://www.norcall.co.uk>

Suppliers and repairers of MOBILE RADIO equipment  
SALES  
HIRE  
REPAIR  
Huge stocks of used radios and spares  
Pye Philips Simoco Icom Kenwood Standard Clearstone Maxon Yaesu Key Midland.  
WE CAN PROGRAM ANYTHING  
24hr Service

**OMEGA RESEARCH LTD**  
<http://www.omega-research.co.uk>

\*SMD prototyping adapters. Unique, flexible, low cost adapters to allow bench working with SM devices. Range suits most devices down to 0.5mm pitch.\*

**PCA:PHILIP COLLINS & ASSOCIATES PTY. LTD**  
<http://www.pca.cc>

PCA manufactures Radphone 2000DX remote control systems for shortwave broadcasters and government agencies wanting worldwide control of communications receivers and transceivers from any tone phone.

**POLY-FLEX CIRCUITS LTD**  
<http://www.polyflex.com>

Design, manufacture and population of printed polyester flexible circuits, including Flip Chip on Flex providing practical, low cost, reliable solutions for today's small lightweight products.

**QUASAR ELECTRONICS**  
[www.quasarelectronics.com](http://www.quasarelectronics.com)

Over 250 electronic kits, projects and

ready built units for hobby, educational & industrial applications. TEL: 01279 306504, FAX: 07092 203496 or EMAIL: [ewsales@quasarelectronics.com](mailto:ewsales@quasarelectronics.com)

**QUILLER ELECTRONICS**  
<http://www.quiller.com>

100+ pages of detailed technical information on Schrack Relays, MEC Switches, Hirose Connections.

**RADIOMETRIX**  
<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use.

**RADIO-TECH LIMITED**  
<http://www.radio-tech.co.uk>

Radio modules, modems, telemetry, audio transmitters, pagers, antenna, remote controls and much more. All UK designed and manufactured.

**RALFE ELECTRONICS**  
professional test & measurement

[www.ralfe-electronics.co.uk](http://www.ralfe-electronics.co.uk)

**RD RESEARCH**  
<http://www.looking.co.uk/spice>

Analogue and digital SPICE modelling software. Full details available on this site. Available on a 30 day evaluation basis.

**RS COMPONENTS LTD**  
<http://rswww.com>

The award winning on-line service from RS - 110,000+ products available  
- Technical data library  
- Stock availability check  
- Integrated on-line purchasing  
- Order by 8pm - with you tomorrow.

**SOFTCOPY**  
<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of

Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

**SESCOM, INC.**  
http://www.sescom.com



SESCOM, INC. is a 30-year manufacturer of audio "problem solvers" and transformers. We also offer easily-fabricated aluminum enclosures for small production runs and prototypes.

**STAFFORDSHIRE WIRELESS COMPANY**  
http://www.staffs-wireless.com

Wireless, communication, test equipment, bought and sold for very competitive prices visit our web site or telephone John on 01889 569928 or 0973 296461.

**SUPRA AUDIO CABLES**  
http://www.jenving.se



Jenving Technology AB is the manufacturer of Supra Audio Cables. OEM productions are also accepted.

**TEMWELL CORPORATION**  
http://www.temwell.com.tw

Manufacturer & Exporter of Heical BPF Filter, 30 Watts BPF Power Filter and Handset/Base Station Duplexers

**TEST EQUIPMENT SOLUTIONS**

http://www.TestEquipmentHQ.com



Quality second user test equipment with full warranty and support. All types of equipment from all leading

manufacturers including general purpose, communications and industrial test.

**TELNET**  
http://www.telnet.uk.com

Top quality second-user Test and Measurement Equipment  
eMail telnetkm@msn.com

**TELONIC**  
http://www.telonic.uk.com



Telonic, specialists in laboratory AC & DC Power Supplies, Electronic AC & DC Loads, Electrical Safety Testing and complete test systems. Plus RF Filters, Attenuators, Diesel Engine Smoke Measurement, Quartz Crystal Microbalances.  
Tel +44 (0) 118 9786911

**THOSE ENGINEERS LTD**  
http://www.spiceage.com



Working evaluations of SpiceAge mixed-mode simulator, Spicycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.

**THERMOSPEED**  
http://www.thermospeed.co.uk



Temperature and pressure, control and instrumentation. Full on-line purchasing.  
\* Overnight ex-stock delivery  
\* Create your own hotlist  
\* Download datasheets  
\* Full technical support


**TOTAL ROBOTS**  
http://www.totalrobots.co.uk

Robot Kits and Control Technology products, including OOPic the first Object-Oriented Programmable Integrated Circuit. Secure on-line ordering and fast delivery.

**TRIDENT MICROSYSTEMS LTD**  
http://www.trident-uk.co.uk

Visit the Trident website for details and datasheets on their entire LCD and printer product range. Download data and subscribe for our regularly updated newsletter.

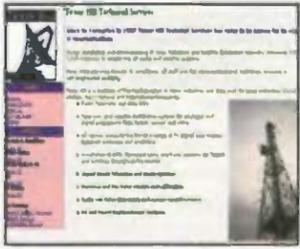**TOWER HILL TECHNICAL SERVICES**  
http://www.towerhillaerials.com



Everything you need for DIY Satellite & TV aerial installation. The one stop shop for TV, FM, Satellite, Amateur Radio PMR Aerials, Distribution Equipment, Cable & Accessories.


**TECHNICAL AND SCIENTIFIC SUPPLIES**  
http://www.technicalscientific.com

Suppliers of pre-1985 equipment and components.  
- Test/Measurement equipment  
- Valves and semiconductors  
- Transducers and pressure gauges  
- Scientific books and catalogues  
- Manuals and data sheets

**VANN DRAPER ELECTRONICS LTD**  
http://www.vanndraper.co.uk

Test equipment from Grundig, Kenwood, Hitachi, Fluke, Avo, Glassman, Advance in a comprehensive site including oscilloscopes, multimeters, power supplies, generators, counters, soldering, digital tv etc.

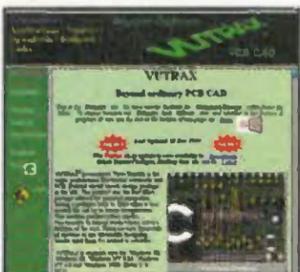**VUTRAX PCB DESIGN SOFTWARE**  
http://www.vutrax.co.uk



VUTRAX electronic schematic and pcb design system for Windows 95, 98 NE, NT and 200. Limited Capacity FREE version downloads available, all upgradeable to various customised levels.

**WOOD & DOUGLAS**  
http://www.woodanddouglas.co.uk

Wood & Douglas Ltd is the leading independent British designer and manufacturer of quality radio products for international telemetry, data, voice & video wireless communications.

**WARWICK WIRELESS LTD**  
http://www.radiotelemetry.co.uk



Free data on Radio Modems, Radio Telemetry, Radio Modules and Wireless Video systems. The licence exempt radios can transmit data from 1 to 20Km at baud rates of 19.2Kbaud to 128Kbaud. The UK based Company can offer customised derivatives of their products as well as turnkey RF Systems.

**UK ELECTRICAL DIRECT**  
http://www.uked.com

For a comprehensive on-line directory, buyers guide and resource locator for the UK Electrical Industry look at this site. Many of the companies listed have links to their own web sites, making this a one-stop shop for a huge amount of information.

**UK MAILING LIST GROUP**  
http://www.egroups.com/list/uk tvrepair

Following on from the newsgroup discussion last month there is a UK Email group for TV technicians where you can send an Email to everyone in the group. There's just over 30 people in the group at present. For more details and how to register look at the egroup home page. Just a general comment though - you do have to be careful who you give your Email address to so that you can avoid "spamming" - that is getting lots of unwanted Email about dubious Russian site (amongst others).

**REPAIRWORLD**  
http://www.repairworld.com

Repairworld is a sophisticated US based fault report database which is updated bi-weekly. It operates on a subscription basis and describes itself as an "affordable solution for all technicians". You can see some samples of the material for free, monitors, VCR, DVD and Camcorders being of particular relevance to UK users. The site also provides a "chat room".

**Ian Hickman describes a simple opto-electronic link with enough bandwidth to carry speech. It was designed so that a group of students could make it up in a couple of hours. In its basic form, the link's working distance is limited, but it is easily modified for building-to-building use - or even further.**

## Beginners' corner

# An optical speech link

This simple all analogue opto-electronic link conveys speech from a transmitter station, via a pulse modulated light beam, to a receiver, as in Fig. 1.

At the send end, the output of a microphone is amplified, and then applied to a pulse generator arranged as a modulator. The pulse train output of the modulator carries the speech signal as variations in mark/space (on-off) ratio. This mark/space modulated speech signal drives a light-emitting diode.

At the receive end, a photodiode detects the light pulses and produces a corresponding output - albeit tiny. This is amplified by an op-amp, connected as a transresistance amplifier. It is then further amplified by a second inverting op-amp stage.

Output from the second amplifier is applied to a low-pass filter. This filter acts as a demodulator, thus recovering the original speech signal.

For convenience, the output was monitored on an existing laboratory amplifier or "squawk box" - one of those endlessly useful pieces of kit that's a must in any electronics laboratory.

### The transmitter circuit

To feed the transmitter, Fig. 2, I used a very ordinary moving-coil microphone with an output resistance of 2000Ω. It was connected directly to the non-inverting input of an op-amp, one section of a TL084 quad op-amp.

A single op-amp would of course have sufficed. However, a quantity of quad op-amps had been made available for the students to experiment with under the RFEEI scheme, described in an earlier article.

With a 10MΩ feedback resistor, the voltage gain of the op-amp was 1000000÷2000=×5000, or 74dB. Open-loop gain of the TL08x series devices is typically ×200000, and in any case not less than the ×25000 minimum figure, so the actual gain is very close to the theoretical figure.

Besides amplifying the signal by the stated amount, of course, it also amplified the op-amp's input offset voltage by the same figure. As it happened, the op-amp used had a very small offset voltage, but the maker's maximum figure for the device is 15mV. Such a worst-case

op-amp would not be usable in the circuit as shown, as its output would be 'stuck' hard at the level of one or other supply rail.

The speech signal output from the op-amp was applied, via 100kΩ resistor R<sub>2</sub>, to the pulse generator/modulator. This modulator used one section of a CD40106 hex inverting Schmitt trigger.

Voltage at the inverter input, pin 1, rises as R<sub>3</sub> charges C<sub>1</sub> up, towards the supply voltage V<sub>cc</sub>. When the voltage reaches the trigger's upper threshold, the output at pin 2 switches abruptly from V<sub>cc</sub> to 0V (ground). Capacitor C<sub>1</sub> is then discharged via R<sub>4</sub> and D<sub>1</sub>, until the voltage at pin 1 falls to the lower threshold. At this point, the output switches back to V<sub>cc</sub>, the level of the supply at pin 14, and the action repeats.

The result is a pulse train at about 18kHz, with a mark/space ratio of about 2:1. This frequency is barely out of the audio range, but certainly beyond my hearing - and, I suspect, beyond that of most if not all of the students.

Fed via R<sub>2</sub>, the speech signal voltage at the output of the op-amp

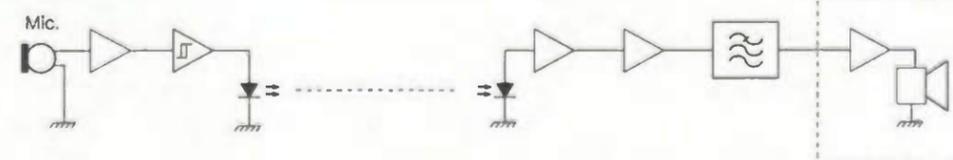


Fig. 1. Outline of an opto-electronic speech link. Speech from the microphone is amplified then modulated before being applied to the transmit LED on the left. Very small signals received via the photodiode feed a transresistance amplifier, which in turn feeds a second amplification stage before demodulation.

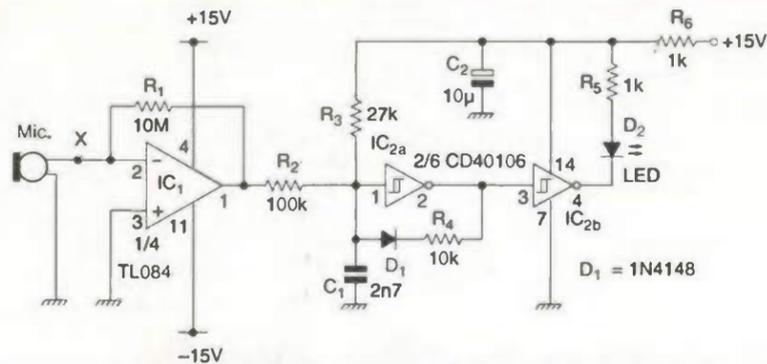


Fig. 2. Opto-link transmitter circuitry with, from left to right, the microphone and its amplifier, the modulator, and finally the transmitter LED together with its buffer/driver.

affects both the pulse-repetition frequency, or prf, and the mark-space ratio. When the voltage rises, the prf increases and the mark-space ratio decreases. When it falls, the prf decreases and the mark-space ratio increases. The change in frequency is immaterial, as far as operation of the link is concerned, the useful information being carried by the mark-space ratio.

The modulated pulse train is applied to another section of the CD40106. This device is used as a buffer to drive the light emitting diode  $D_2$ , the current being limited by series resistor  $R_5$ .

**At the receiving end**

At the receiver, Fig. 3, the photodiode  $D_3$  is aligned with the transmitter's light emitting diode  $D_2$ , so as to detect the light pulses. These

are amplified by op-amp  $IC_{3a}$ , connected as a transresistance amplifier. In this configuration, the photo-current generated by the diode is balanced by the current fed back to the inverting input via  $R_7$ .

Increasing the value of  $R_7$  gives a greater output voltage for a given amount of light falling on the diode. There is a limit to how much  $R_7$  can be increased though. The self capacitance of the photo-diode and the op-amp's input capacitance, together with  $R_7$ , form a low-pass filter. This filter action limits the circuit's frequency response.

Further gain is provided by  $IC_{3b}$ . This amounts to 40dB or  $\times 100$ , defined by the ratio of  $R_9$  to  $R_8$ . Output from  $IC_{3b}$  is applied to the simple first order low-pass filter formed by  $R_{10}$  and  $C_4$ , the cut-off frequency being about 5kHz. This

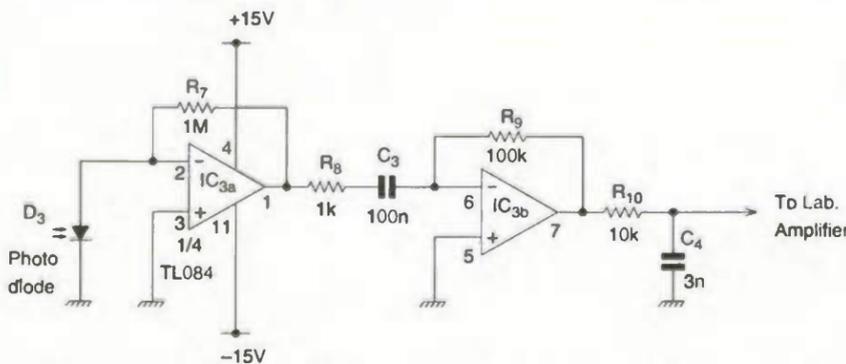


Fig. 3. Receiver circuitry for the optical speech link. The signal from an ordinary photodiode is amplified in two stages. A simple low-pass filter provides demodulation, final output being the original speech signal. This signal is still at a low level so further amplification is needed before a loudspeaker can be driven.

largely smoothes out the 18kHz pulses, leaving a waveform whose instantaneous value reflects the current mark-space ratio, i.e. the original speech waveform. This signal was then applied to the lab. amplifier.

**The ins and outs of 'system integration'**

The students worked in two groups. One group built up the kit of Fig. 2, the other that of Fig. 3. The circuits were built up on experimenters' plug-board, with component leads bent-over and plugged in wherever convenient.

I suggested that each circuit block be built up and got working in turn, rather than connecting up the whole circuit, and then trying to get it working. Thus in Fig. 2, the pulse generator of  $IC_{2a}$  was built first, then the  $IC_{2b}$  circuitry was added.

Next, the microphone and  $IC_1$  were connected up, and the resultant offset at pin 1 measured. As this was only a volt or so, the circuit was deemed to work. Adding  $R_2$  completed the transmitter section. Had the output offset been excessive, a capacitor of, say, 100nF, would need to be inserted at point X.

Similarly, at the receive end,  $IC_{3a}$  and the photo-diode were connected up, and operation checked by alternately shielding the diode from room lights, and flashing a torch at it. The  $IC_{3b}$  circuitry was then added, and then the low-pass filter.

Finally, with the lab. amplifier connected, the operation of the system overall was checked. Speaking into the microphone at one end of the link produced clear and distinct speech out of the lab. amplifier at the other; indeed, if the gain of the lab. amplifier was set too high, the system would 'sing round', as the microphone was able to 'hear itself' from the other end of the link.

An ordinary high-brightness RED diode was used for the transmitter. The photo-diode was a standard small silicon variety. With the aid of a simple lens, the range could be increased to the length of two laboratory benches.

**Increasing the range**

Various steps are available for increasing the range. The most obvious is to increase the drive to the LED, by reducing the value of  $R_5$ . This is possible, if the other unused inverters in the CD40106 are

connected in parallel with  $IC_{2b}$ .

Brighter LEDs than that used are also now available. The other way of increasing range is to arrange that more of the light emitted by the LED falls on the active area of the photo-diode, as detailed below.

With a wireless communication system, the range is determined by the available 'effective radiated power' at the transmitter, and the sensitivity at the receiver. The effective radiated power at the transmitter can be increased, in the desired direction of communication and at the expense of other directions. This can be done using a transmitting antenna with directional gain.

Likewise, at the receiver, a further improvement can be achieved by using a directional antenna aligned with the transmitter.

At frequencies in the HF band, up to 30MHz, it is difficult to achieve a large improvement with directional antennas, as they would need to be very large. At VHF and UHF directional gains of 6 to 15dB are possible with Yagi antennas - more with antenna arrays.

At microwave frequencies, where dish antennas are used, gains of around 40dB can be employed. Even higher gains are possible at optical frequencies. The equivalent of a directional antenna here can be either a refractor (a lens), or a reflector.

Suitable high-quality optics are in fact available, for a very modest price, now that camcorders have rendered 8mm cine cameras obsolete. Somewhere lurking in a cupboard I have a Bolex cine camera with a two-lens turret (Kern-Paillard normal and telephoto). This took over from a Bell and Howell camera with a three-lens turret (Taylor Hobson normal, telephoto and wide angle, also lurking).

The telephoto lenses in particular, Yvar 1:2.8 and Serital 1:1.9, offer the possibility of spectacular signal gain, permitting building-to-building communication. The disadvantage is that alignment them becomes critical.

Such communication should be possible - even in daylight - thanks to the remarkable linearity of silicon photodiodes used in the photoconductive mode as in Fig. 3, rather than photovoltaic mode.

Simple ac coupling of the photo-diode amplifier output may be adequate to reject the constant background output due to daylight.

When seeking maximum range though, a high value feedback resistor is involved so the background light may saturate the op-amp.

In this case, the scheme shown in Fig. 4 can be used<sup>1</sup>. This scheme rejects the unwanted output. The auxiliary op-amp monitors the output, and feeds back a current cancelling out the large constant photo-diode current due to daylight, thus driving the average output voltage to zero.

The feedback is ineffective above a certain frequency - around 16Hz with the component values shown - and so the wanted pulse train carrying the desired intelligence is unaffected. ■

**Reference**

1. Burr-Brown Application Bulletin AB-061.

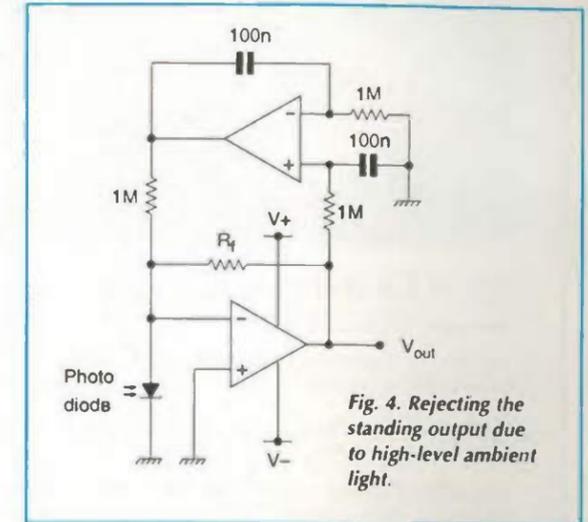


Fig. 4. Rejecting the standing output due to high-level ambient light.

**BOOK TO BUY**  
**Valve Radio and Audio Repair Handbook**



UK Price: £22.50 Europe £25.00 ROW £27.00  
\*\* Price includes delivery and package \*\*

Return to Jackie Lowe, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ

Please supply the following title:  
**Valve Radio and Audio Repair Handbook**

Name \_\_\_\_\_ Total \_\_\_\_\_  
Address \_\_\_\_\_  
Postcode \_\_\_\_\_  
Telephone \_\_\_\_\_

Cheques should be made payable to Cumulus Business Media  
Method of payment (please circle)  
Access/Mastercard/Visa/Cheque/PO  
Credit \_\_\_\_\_ card  
no. \_\_\_\_\_  
Card expiry date \_\_\_\_\_



## 20% discount for EW readers

Temperature controlled soldering stations



Vann Draper Electronics Ltd  
The test & measurement specialists  
www.vanndraper.co.uk

Grundig, Kenwood, Hitachi, Fluke, Avo, Advance

Use this coupon for your order

Please supply me:

- ..... SL20 soldering station(s) at £55 inc vat & del
- ..... SL30 soldering station(s) at £65 inc vat & del
- ..... Extra 0.8mm bit(s) at £1.65 inc vat & del
- ..... 1.6mm bit(s) at £1.65 inc vat & del
- ..... 3.2mm bit(s) at £1.65 inc vat & del

Name:

Address:

Tel No:

Total £

Cheques payable to Vann Draper Electronics Ltd or debit my visa, mastercard or switch card:

Card type:

Card No:

Expiry date:

Switch Iss No:

Signature:

Overseas readers can still obtain this discount but carriage charges vary according to country. Please telephone, fax, email or write to Vann Draper.

Vann Draper is offering over 20% discount for a limited period to readers of Electronics World magazine on their temperature controlled soldering stations.

The SL20 bar graph display soldering station normally sells at £69.33 and is available to readers of TV at only £55 fully inclusive of vat & delivery.

The SL30 digital display version is normally priced at £81.08 but for readers of TV the price is just £65 fully inclusive.

Both soldering stations feature 24V 48W elements for rapid heating and have full electronic temperature control between 150C and 420C (SL20), 160C and 480C (SL30).

The SL20 and SL30 are supplied ready to use complete with a 48W iron, 0.8mm long life bit, mains lead, operating instructions and a 12 month guarantee.

To order simply post the coupon to Vann Draper Electronics Ltd at Stenson House, Stenson, Derby DE73 1HL. Alternatively - Tel 01283 704706, Fax 01283 704707 or Email sales@vanndraper.co.uk

CIRCLE NO. 121 ON REPLY CARD

As an advertiser you can be certain that your sales message is going to be read by decision-making electronics professionals with the power to purchase your products.

The pre-paid rate for semi-display setting is £17 per single column centimetre (maximum 4cm). Box number £22 extra. All prices plus 17½% VAT. All cheques, postal orders etc to be made payable to Reed Business Information. Advertisements together with remittance should be sent to Electronics World Classified, Cumulus Business Media, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8DZ. Tel: 020 8722 6028. Fax: 020 8770 2016

## Service Link

### FOR SALE

#### RF DESIGN SERVICES

All aspects of RF hardware development considered from concept to production.

WATERBEACH ELECTRONICS

www.rlaver.dial.pipex.com

TEL: 01223 862550  
FAX: 01223 440853

#### Test Equipment



Service Manuals. Contact

www.cooke-int.com  
Tel: +44 01243 55 55 90

Very Good Condition  
Stabilock 4031 - £1,500  
Stabilock 4040 - £1,300  
Tek 3001 GPX Logic Analyzer - £1,300  
Hitachi VC-6175 Store O'scope - £700  
Tek 2235 100 MHz O'scope - £600  
Tel: 0779 6865 500

### ARTICLES WANTED

#### BEST CASH PRICES PAID

For all valves KT88 PX4 and other audio types  
Wide range of valves and CRT stocked  
Tel: 01403 784961  
Minimum Order UK - £100+VAT+Freight

Billington Export Ltd Fax: 01403 783519  
Email: sales@bel-tubes.co.uk  
Sussex RH14 9EZ  
Visitors by appointment

#### TMS77C82NL (40 pin DIL)

Any quantity considered  
Tel: 020 8930 0943  
Fax: 020 8933 2996

As an advertiser you can be certain that your advertisement is going to be read by DECISION-MAKING ELECTRONICS PROFESSIONALS with the POWER TO PURCHASE your products.

Why not let Electronics World help you?

Call Pat Bunce  
Tel: 020 8722 6028  
Fax: 020 8770 2016  
E-mail: P.bunce@cumulusmedia.co.uk

### ARTICLES WANTED

#### TOP PRICES PAID

For all your valves, tubes, semi conductors and ICs.

#### Langrex Supplies Limited

1 Mayo Road  
Croydon, Surrey CR0 2QP  
TEL: 020 8684 1166  
FAX: 020 8684 3056

#### 19" Rack Enclosures

New and Used most sizes  
16U to 50U side and rear panels  
mains distribution  
19" Panel mounts  
optima eurocraft

Prices from £45 + vat  
M&B Radio  
86 Bishopsgate Street  
Leeds LS1 4BB  
Tel. 0113 2702114  
Fax. 0113 2426881

### SERVICES

#### From Concept TO Production 48 HOUR SERVICE

Electronic design and manufacturing services for the new millennium:

- Embedded monitoring & control
- PSTN telephones and test equipment
- Datacom interfacing, line driving etc
- Switch Mode & linear PSU and battery management
- Gas detection systems
- Printed Circuit Board design
- Technical documentation, schematic layout & language translation
- Wireless telemetry systems
- Audio & Video processing
- GSM telemetry via SMS or data (TCP/IP)
- DVD player control systems
- GPS positioning systems
- Specialist cable looms
- Small, medium & large scale manufacturing

Email: sales@designersystems.co.uk  
Tel/Fax: +44 (0) 1872 223306



for more information see our web site @ http://www.designersystems.co.uk

#### T & M EQUIPMENT



- ADRET 740A signal generator 0.1-1120MHz £1000
- ANRITSU ME520B digital transmission analyser with MH370A jitter mod' oscillator £4000
- ANRITSU ML93A optical power meter with MASA power sensor £500
- IFR (MARCONI) 2610 true rms voltmeter £500
- IFR (MARCONI) 2955 mobile radio test set
- IFR (MARCONI) 2022C 10kHz to 1GHz synthesized signal generator
- NARDA 8305 broadband isotropic radiation monitor 0.3-18GHz £500
- RACAL DANA 1992 frequency counter 1.3GHz £500
- RACAL 6102 gsm test set £1000
- RHDDE AND SCHWARZ UAF video analyser £4000
- SCHAFFNER 2006/203A/222A line voltage simulator/interference simulator £1000
- SCHAFFNER 2006 mainframe £500
- WANDEL AND GOLTERMANN PF4 bit error rate tester (BN911.01. Option 00 01) £1500
- WAVETEK 1080 sweep generator 1-1000MHz £500
- WAVETEK 4106GPP handheld GSM mobile phone test set £500
- WILTRON 6640B sweep generator 26.5-40GHz £2500

#### • ralfe electronics •

Unit 1 Olds Close •  
Olds Approach •  
Watford • Herts WD1 8RU •  
England •  
TEL (+44) 01923-721396  
FAX (+44) 01923-721402  
EST 45 YRS



#### AGILENT TECHNOLOGIES



- 1145A active probe 2-channel (list 3725) £350
- 3336A level generator £1000
- 2148 pulse generator £1500
- 10715A digital generator £1000
- 346A noise source £850
- 8904A synthesizer function generator £1000
- 8018A serial data generator £1000
- 8175A digital signal generator (order pods separately) £2500
- 83440C lightwave detector 20GHz 1300/1550nm £2000
- 85033D 3.5mm calibration kit 30kHz to 6GHz (list 2381) £1500
- 85037B N-type calibration kit (list 1578) £850
- 85053B 3.5mm ventilation kit £2000
- 85056D 2.4mm economy calibration kit (list E4904) £2500
- 85056K calibration kit (list E381) £3500
- 85132F 7mm to 3.5mm flexible test port cable set (list E2682) £1750
- 85132F 2.4mm flexible test port cable set (list 4248) £2500
- 8594E 2.9GHz spectrum analyser options 041/01/105 (list E11k) £7500
- 8657A synthesised signal generator 0.1 - 1040MHz £2000
- 8657B synthesised signal generator 0.1 - 2080MHz £4000
- 8903B/10/S1 audio analyser £2000
- 8903E audio analyser £1250
- 8922 E, F, G and H gsm test sets, each £1000
- E1413C a/d converter (VXI based) (list 4932) £1500
- E1415A algorithmic closed loop controller (VXI based) (list E5221) £2000
- E1610A VXI card 34Mb/s line interface for BSTS £2500
- E1697A VXI card 155Mb/s optical line interface £5000
- E5200A broadband service analyser, options /02/05/1/22/122/138/138/139/139 £5000
- J2171A ethernet interface module £1500
- J2215A FDDI multimode test set £1000
- J3911A multiprotocol token-ring Lanprobe £2000
- J3914A E1 WanProbe £2000
- J3921A E3 ATM probe £6500
- J3335A Telegra D analyser /201/202 options (list E13250) £6500
- J3972A 3c/S/TM-1 performance enhanced ATM probe £6500
- R85026A 26.5 - 40GHz waveguide detector £650



Certificate No. 95/013

ISO9002 ACCREDITED STOCKIST  
MEASUREMENT & TEST EQUIPMENT


#### NEW INTO STOCK THIS MONTH, AGILENT UNITS

- 8714ES/100 3GHz network analyser, option 100 (fault location) (List over £18000) £13500
- 8722ET network analyser 50MHz - 40GHz, with options 010 (time domain) and 1D5 (Hi-stab) (List > £57k). £45000.
- 8653ES network analyser with 006 nad 010 (6GHz + time-domain options) (List £32k) £25000.

All above supplied with new Agilent calibration and 1 year warranty.

All equipment sold calibration-checked by independent laboratories and carries un-conditional refund and 90-day guarantees.  
TEST EQUIPMENT WANTED.  
TOP PRICES PAID FOR PROFESSIONAL HIGH-END UNITS  
AGILENT TECHNOLOGY SPECIALISTS.  
FOR COMPLETE STOCK LISTING PLEASE CHECK OUR WEBSITE  
www.ralfe-electronics.co.uk

CIRCLE NO. 122 ON REPLY CARD

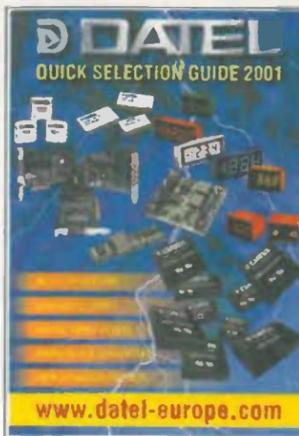

**DATEL**  
INNOVATION and EXCELLENCE  
Your professional partner for...

- DC/DC Converters
- Digital Panel Meters
- Data Acquisition Components
- Data Acquisition Boards

Request our Quick Selection Guide or visit our website:  
[www.datel-europe.com](http://www.datel-europe.com)

Date UK Ltd.,  
Campbell Court Business Park  
Bramley, Tadley, Hampshire, RG26 5EG  
Tel: 01256 880444, Fax: 01256 880706

[www.datel-europe.com](http://www.datel-europe.com)

CIRCLE NO.123 ON REPLY CARD



**DAQ Designer™ 2001**

National Instruments new DAQ Designer™ 2001 is a FREE CD that helps engineers and scientists interactively configure custom measurement systems. DAQ Designer™ 2001 includes the capability to recommend real-time data acquisition and motion control hardware and software.

Phone: 01635 523545  
Fax: 01635 524395  
E-mail: [Info.uk@ni.com](mailto:Info.uk@ni.com)  
Web: [www.ni.com/uk](http://www.ni.com/uk)

CIRCLE NO.124 ON REPLY CARD



UNBEATABLE OFFER - SmartCard reader for just £10!

**ELECTRONICS WORLD**

September 2001 £5.99

**E-fraud exposed**  
Audio-visual router  
Impedance meter  
Under 10mV transformer  
IC resonant tank  
Hands-on DSP design  
Ethernet I/O interface

**Great ideas:**  
Low power 100W LED driver  
High speed 100MHz 100V MOSFET  
A simple and easy to use 100MHz 100V MOSFET  
A simple and easy to use 100MHz 100V MOSFET

**ELECTRONICS WORLD** covers topics of most interest to the readers. Every section of the magazine is of interest and value to the Electronics Professionals who buy Electronics World every month. Your advertisement will appear in an environment which captures and holds the readers interest.

For further information call Pat Bunce  
Tel 020 8643 6207  
Fax 020 8770 2016  
E-mail: [P.bunce@cumulusmedia.co.uk](mailto:P.bunce@cumulusmedia.co.uk)

**ELECTRONICS WORLD** covers topics of most interest to the readers. Every section of the magazine is of interest and value to the Electronics Professionals who buy Electronics World every month. Your advertisement will appear in an environment which captures and holds the readers interest.

For further information call Pat Bunce  
Tel 020 8643 6207  
Fax 020 8770 2016  
E-mail: [P.bunce@cumulusmedia.co.uk](mailto:P.bunce@cumulusmedia.co.uk)



**EED**  
ENERGY EFFICIENT DEVICE

**Energy Efficient Devices (EEDs):**  
Central Semiconductor's new family of Energy Efficient Devices (EEDs) are designed to reduce the power requirements necessary for today's portable electronic products.

With VF as low as 0.35V, Central's Schottky Rectifiers are the perfect solution for battery powered hand-held applications such as PDAs, pagers, laptops and cell phones.

In addition, the Low Leakage 200 Volt diodes and Ultra Low Leakage diodes provide design engineers with yet another tool for controlling size, power management, and battery conservation.

Central Semiconductor is dedicated to complete customer satisfaction, perfect quality, on-time delivery, and reasonable prices. Visit our website at [www.centraisem.com](http://www.centraisem.com) for current information on all devices manufactured by Central.

Tel: 01420 542500 Email: [sales@mbcomponents.co.uk](mailto:sales@mbcomponents.co.uk)

**MB COMPONENTS**  
Semiconductor Corp. THE FUTURE OF SMD

Low V <sub>f</sub> Schottky Rectifiers	
CMSH1-20AL	1.0 Amp series SMA
CMSH0-20L	2.0 Amp series SMB
CMSH3-20L	3.0 Amp series SMC
CSH05-35L	5.0 Amp series DPAK
CSH010-45L	10 Amp series
Low Leakage High Voltage Diodes	
CMPD0001	Single
CMPD0001A	Dual Common Anode
CMPD0001C	Dual Common Cathode
CMPD0001B	Dual In Series
CMPD0001D	SOT-23
Ultra Low Leakage Diodes	
CMPD0001	Single
CMPD0001A	Dual Common Anode
CMPD0001C	Dual Common Cathode
CMPD0001B	Dual In Series
CMPD0001D	SOT-23
CMPD0001E	Single
CMPD0001F	Single

CIRCLE NO.125 ON REPLY CARD

**ADVERTISERS' INDEX**

ADEPT SCIENTIFIC..... 719	MILFORD INST..... 653
BETA..... 686	NUMBER ONE SYSTEMS..... 671
CONFORD ELECTRONICS..... 686	PICO..... 657
CRICKLEWOOD..... 693	RAEDEK..... 719
CROWNHILL..... IBC	RALFE ELECTRONICS..... 726
DISPLAY ELECTRONICS..... 691	RD RESEARCH..... 653
EPTSOFT..... OBC	SEETRAX..... 657
JOHNS RADIO..... 681	STEWART OF READING..... 693
JPG ELECTRONICS..... 693	TELNET..... IFC
LABCENTER ELECTRONICS.. 650	TIE PIE..... 697
LANGREX..... 719	VANN DRAPER..... 726
	WEB PAGES..... 720, 721, 722

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

**READER INFORMATION SERVICE**

For more information about any of the products or services in this issue of **ELECTRONICS WORLD**, simply ring the relevant enquiry number. Enquiry numbers may be found at the bottom of each individual advertisement.

101	102	103	104	105	106	107	108	109	110	111
112	113	114	115	116	117	118	119	120	121	122
123	124	125	126	127	128	129	130	131	132	133
134	135	136	137	138	139	140	141	142	143	144
145	146	147	148	149	150					
						500	501	502	503	504
505	506	507	508	509	510	511	512	513	514	515
516	517	518	519	520	521	522	523	524	525	526
527	528	529	530	531	532	533	534	535	536	537
538	539	540	541	542	543	544	545	546	547	548
549	550	551	552	553	554	555	556	557	558	559
560	561	562	563	564	565	566	567	568	569	570
571	572	573	574	575	576	577	578	579	580	581
582	583	584	585	586	587	588	589	590	591	592
593	594	595	596	597	598	599	600			

Name \_\_\_\_\_

Job title \_\_\_\_\_

Company Address \_\_\_\_\_

Telephone \_\_\_\_\_ SEPTEMBER 2001

Only tick here if you do not wish to receive direct marketing promotions from other companies.

**Newsagent order form**

Pass this order form to your newsagent to ensure you don't miss the next issue of *EW*.

To .....  
(name of Newsagent)

Please reserve me the October issue of *Electronics World* and continue to order every month's issue until further notice

Name.....  
Address.....  
.....  
.....

Thank you

**Subscribe today!**

Guarantee your own personal copy each month

**Save on a 2 year subscription**

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

**Subscribe today!**

Guarantee your own personal copy each month

**Save on a 2 year subscription**

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

SEE OVER!

**ELECTRONICS WORLD**  
Reader Information Service  
Cumulus Business Media Limited  
Perrymount Road  
Haywards Heath  
Sussex RH16 3DH

PLEASE  
AFFIX  
STAMP

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

**SUBSCRIPTION CARD**

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ \_\_\_\_\_ made payable to Reed Business Information. Please charge my Mastercard/Visa/Amex account.

With £ \_\_\_\_\_ Expiry Date \_\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_

Job Title \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Country \_\_\_\_\_

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
<b>Airmail</b>	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:  
**ELECTRONICS WORLD**  
P.O. Box 302  
Haywards Heath,  
West Sussex RH16 3DH UK.

**CREDIT CARD HOTLINE**  
Tel: +44 01444 445566  
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

**ELECTRONICS WORLD**  
INCORPORATING WIRELESS WORLD

**SUBSCRIPTION CARD**

Please enter my subscription to ELECTRONICS WORLD. I enclose Cheque/Eurocheque to the value of £ \_\_\_\_\_ made payable to Reed Business Information. Please charge my Mastercard/Visa/Amex account.

With £ \_\_\_\_\_ Expiry Date \_\_\_\_\_

Signature \_\_\_\_\_

Name \_\_\_\_\_

Job Title \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Tel: \_\_\_\_\_ Country \_\_\_\_\_

SUBSCRIPTION RATES	
UK 1 year	£36
UK 2 years	£58
UK 3 years	£72
Student rate (proof required)	£21.30
<b>Airmail</b>	
Europe 1 year	£51
Europe 2 years	£82
Europe 3 years	£103
Rest of the world 1 year	£61
Rest of the world 2 years	£98
Rest of the world 3 years	£123
Surface mail 1 year	£41

Post to:  
**ELECTRONICS WORLD**  
P.O. Box 302  
Haywards Heath,  
West Sussex RH16 3DH UK.

**CREDIT CARD HOTLINE**  
Tel: +44 01444 445566  
Fax: +44 01444 445447

Please tick here if you do not wish to receive direct marketing-promotion from other companies

**SMART CARD SOLUTIONS**

Crownhill Associates  
smart electronic solutions

Visit our web site: [www.crownhill.co.uk](http://www.crownhill.co.uk)



**ChipDrive Starter pack**

ChipDrive Microh - serial port card terminal  
Samples of Smart cards (6 cards)  
Source code examples on CD ROM (VB3,4,5,6, Delphi & C)  
Windows API Description, Windows DLL Documentation on CD ROM (PDF format)

**£69.95** +vat



**SmartCard Programmers from £9.99**

**29.95** +vat

**SIM Card Editor for Mobile Phones**

This advanced editor allows the user to modify, copy and print data held on any GSM SIM card. No longer do you have to battle with complicated programming sequences on the numeric keypad of your mobile phone. Simply connect the SIM card READER WRITER to your PC, install the easy to use software to:

- View and Print a detailed card profile
- Edit, Delete or Add phone book entries
- Edit, Delete or Add SMS messages
- PIN administration. Enable and Up-Date PIN1/2, unlock PIN's, Display the error counter for each PIN
- Archive SIM Card data to hard drive, copy Save and restore complete card data sets.
- Copy SIM card data from card to card
- Charge Control. set up charge counter limit, display current charge value, setup displayed price per unit.
- View and change preferred service providers

Includes:  
SIM Card Reader Writer  
Mini SIM Adapter  
Software on CD-ROM  
OnLine user Guide and Help  
Requires Windows 95/98, NT, 2000 & Pentium Class PC

CIRCLE NO. 102 ON REPLY CARD

32, Broad Street, Ely  
Cambridge, CB7 4AH

Tel: +44 (0) 1353 666709  
Fax: +44 (0) 1353 666710

All prices exclude VAT postage and packing

# 'Electronics and Computing Principles V7'

## '95, '98, NT or 2000 Principles V7'

Interested in PIC micro controllers, this is the software for you!

Electronics and Computing Principles V7

DC AC Electrical Semi-Conductors Op-Amps Maths Digital Computing Testing Micro PIC@ Toolbox Lab Index SAQ Window

PIC@ INTRODUCTION: Code example 'Configuring the Ports'

PIC@ ARCHITECTURE: PIC16F84 Block Diagram

PIC@ BYTE-ORIENTATED INSTRUCTIONS: MOVF f,d: Move f.

Syntax [label] MOVF f,d

Encoding (f) (d) (d) (d) (d) (d) (d) (d)

Description: The contents of register f are moved to destination 'd'. If 'd' is 0, destination is W register. If 'd' is 1, the destination is file register f itself. d = 1 is useful to test a file register since status flag 'Z' is affected.

Example: MOVF FSR, 0. Before Instruction: FSR = ABh, W = FFh. After Instruction: FSR = ABh, W = ABh.

Voltage Conversion:  $V = \frac{255}{VDD} \times (RA0/AN0 \times Vref) = 229 \times '11100101'$

RETLOW k: Return Literal to W.

Visit [www.eptsoft.com](http://www.eptsoft.com) or telephone for full details, including a description by Robert Penfold.

Electronics and Computing Principles V7 comprises more than a thousand main topics, covering AC and DC theory, Transistors, Op-Amps, Electrical, Digital techniques, Micro processors and Mathematics. PLUS: Components and Equipment Picture dictionary, SAQ's, Electronics toolbox etc, and more...

Also included is an enormous amount of interactive technical information about PIC micro controllers and the full instruction set.

Schools, colleges and industry use V7 alongside their own programmers enabling students and engineers to play with ALL the Byte, Bit and Literal instructions to explore their effect. V7 is listed on the Microchip university web site as a training resource for PICs.

FREE programming software to accompany EPV7 is available from the Microchip web site. Details provided.

Personal user £99.95 +VAT  
Education\* £299.95 +VAT  
(\* Includes unlimited multi-user site licence.)

For beginners our PIC topics start with an interactive introduction to the PIC program structure and basic operation with a summary of the complete instruction set and code examples.

PIC16F84 Architecture is shown whereby a context sensitive description of its action is displayed. Every PIC operation is discussed (even the more advanced are explained). Just as it occurs inside a PIC, we show it in colour on the screen.

PIC16C71 A/D functions are given the same treatment, along with a full explanation of the A/D conversion process, even the calculations.

A visually attractive set of Windows designed to help you quickly and easily get started in the development of your own PIC programs.

More than 80 PIC topics and it's still only a tiny part of the complete V7 package.

eptsoft limited. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.  
Tel: +44 (0)1376 514008. Fax: +44 (0)870 0509660. Email: [info@eptsoft.com](mailto:info@eptsoft.com).  
Switch, Delta, Visa and MasterCard accepted.  
No additional postage or airmail charges.