

Electronics World's renowned news section starts on page 5

# ELECTRONICS WORLD

NOVEMBER 2002 £2.95

## Digital I/O using USB

**Low power  
CMOS sensors**

**Capacitor  
sound part 4**


**RF Auto  
transformers**

### Circuit ideas:

**PIC  
programming  
solution**

**PIR  
enhancement**

**TDA7000  
signal strength  
display**

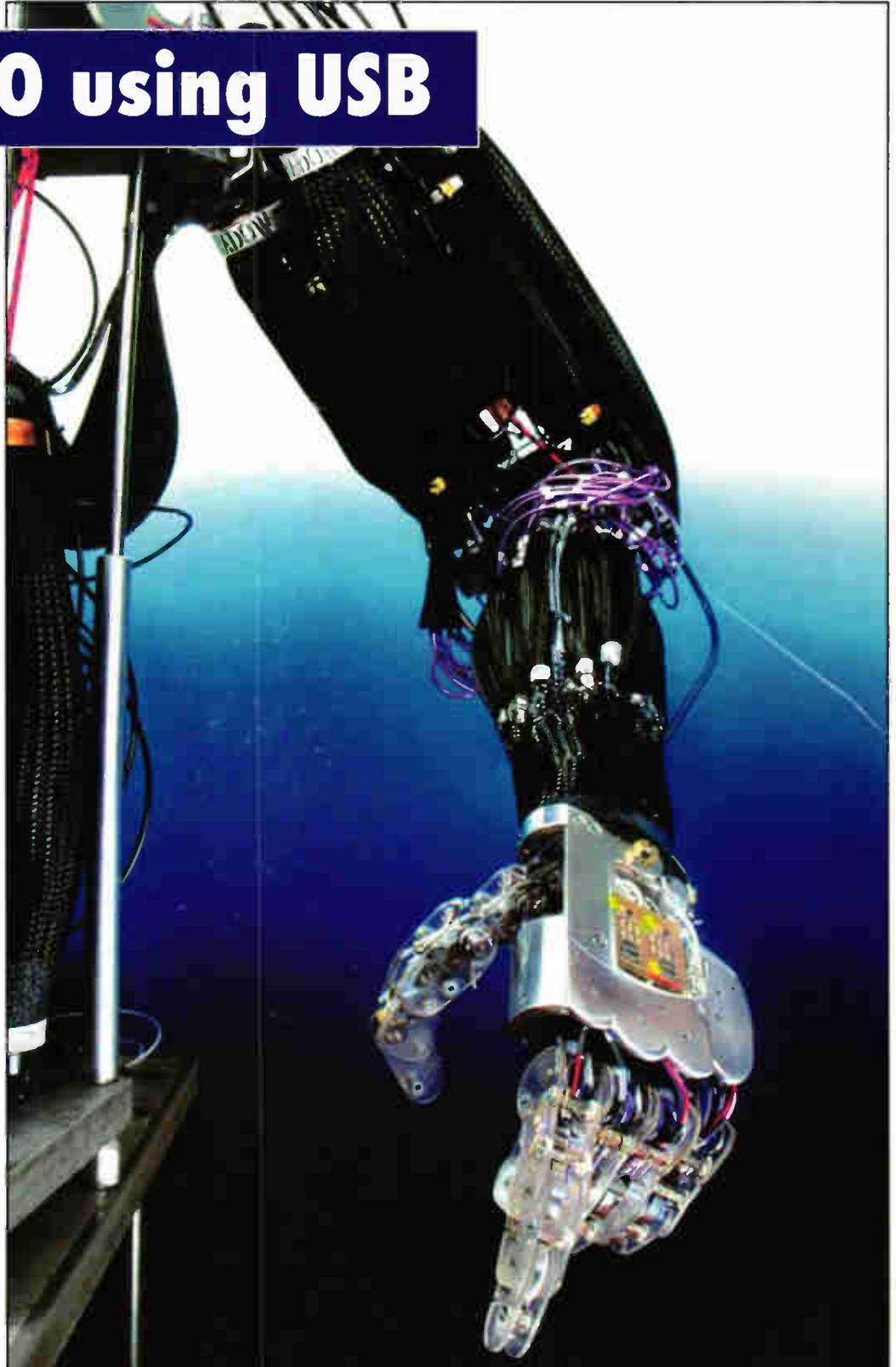

9 770959 833080

# Telnet

## Quality second-user test & measurement equipment

Amplifier Research 30W1000 Amplifier 30watt 1-1000MHz	£4750
Hewlett Packard 3314A Function Generator 20MHz	£1250
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	£2250
Hewlett Packard 3325B Synthesised Function Generator	£3250
Hewlett Packard 3326A Two-Channel Synthesiser	£3000
H.P. 4191A R/F Imp. Analyser (1GHz)	£4995
H.P. 4192A L.F. Imp. Analyser (13MHz)	£4000
Hewlett Packard 4193A Vector Impedance Meter (4-110MHz)	£3000
Hewlett Packard 4278A 1kHz/1MHz Capacitance Meter	£3750
H.P. 53310A Mod. Domain Analyser (opt 1/31)	£6750
Hewlett Packard 8349B (2 - 20 GHz) Microwave Amplifier	£2500
Hewlett Packard 8904A Multifunction Synthesiser (opt 2+4)	£1950
H.P. ESG-D3000A 3GHz Signal Gen	£6995
Marconi 6310 - Prog'ble Sweep gen. (2 to 20GHz) - new	£2500
Marconi 2032 10KHz-5.4GHz Sig. Gen.	£6995
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£2995
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£4750
R&S SMG (0.1-1GHz) Sig. Generator (opts B1+2)	£2750
Fluke 5700A Multifunction Calibrator	£12500
Fluke 5800A Oscilloscope Calibrator	£9995
H.P. 8341B Synth. Sweep Gen. (20GHz)	£15000
H.P. 4284A Precision LCR meter	£6500
H.P. 3458A DMM (8.5 digits)	£3750
Tek 371A Programmable Curve Tracer	£15000

### OSCILLOSCOPES


Gould 400 20MHz - DSO - 2 channel	£695
Gould 1421 20MHz - DSO - 2 channel	£425
Gould 4068 150MHz 4 channel DSO	£1250
Gould 4074 100MHz - 400 Ms/s - 4 channel	£1100
Hewlett Packard 54201A - 300MHz Digitizing	£750
Hewlett Packard 54502A - 400MHz - 400 MS/s 2 channel	£1600
Hewlett Packard 54520A 500MHz 2ch	£2750
Hewlett Packard 54600A - 100MHz - 2 channel	£675
Hewlett Packard 54616B 500MHz - 2Gs/s 2 Channel	£2500
Hewlett Packard 54810A 'Infinium' 500MHz 2ch	£3500
Hitachi V152/V212/V222/V302B/V302FV353F/V550BV650F	from £1100
Hitachi V1 100A - 100MHz - 4 channel	£750
Intron 2020 - 20MHz. Dual channel D.S.O (new)	£450
Iwatsu SS 5710/SS 5702 -	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lecroy 9314L 300MHz - 4 channels	£2750
Meguro MSO 1270A - 20MHz - D.S.O. (new)	£450
Philips 3295A - 400MHz - Dual channel	£1400
Philips PM3070 - 100MHz - 2 channel - cursor readout	£650
Philips PM3392 - 200MHz - 200Ms/s - 4 channel	£1750
Philips PM3094 - 200MHz - 4 channel	£1500
Tektronix 468 - 100MHz D.S.O.	£500
Tektronix 2213/2215 - 60MHz - Dual channel	£300
Tektronix 2220 - 60MHz - Dual channel D.S.O	£850
Tektronix 2221 - 60MHz - Dual channel D.S.O	£850
Tektronix 2235 - 100MHz - Dual channel	£500
Tektronix 2245A - 100MHz - 4 channel	£700
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2440 - 300MHz/500MS/s D.S.O.	£2100
Tektronix 2445 - 150MHz - 4 channel +DMM	£850
Tektronix 2445/2445B - 150MHz - 4 channel	£800
Tektronix 2465/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 7104 - 1GHz Real Time - with 7A29 x2, 7B10 and 7B15	from £1950
Tektronix TAS 475 - 100MHz - 4 channel	£850
Tektronix TDS 310 50MHz DSO - 2 channel	£750

### SPECTRUM ANALYSERS

Advantest 4131 (10kHz - 3.5GHz)	£3750
Advantest/TAKEDA RIKEN - 4132 - 100KHz - 1000MHz	£1350
Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£750
Farnell SSA-1000A 9KHz-1GHz Spec. An.	£1250
Hewlett Packard 182T Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2000
Hewlett Packard 853A Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2500
Hewlett Packard 3582A (0.02Hz - 25.5kHz) dual channel	£1500
Hewlett Packard 3585A 40 MHz Spec Analyser	£3000
Hewlett Packard 3561A Dynamic Signal Analyser	£3500
Hewlett Packard 8560A (50MHz-2.9GHz) High performance with Tracking Generator option (02)	£5500
Hewlett Packard 8567A -100Hz - 1500MHz	£3400
Hewlett Packard 8590A (opt 01, 021, 040) 1MHz-1.5MHz	£2500
Hewlett Packard 8596E (opt 41, 101, 105, 130) 9KHz - 12.8GHz	£9950
Hewlett Packard 8713C (opt 1 E1) Network An. 3 GHz	£6000
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£4995
Hewlett Packard 8753A (300KHz - 3GHz) Network An.	£3250
Hewlett Packard 8753B+85046A Network An + S Param (3GHz)	£6500
Hewlett Packard 8754A - Network Analyser 4MHz - 1300MHz)	£1500
Hewlett Packard 8756A/8757A Scaler Network Analyser	from £900
Hewlett Packard 70001A/70900A/70906A/70902A/70205A - 26.5 GHz Spectrum Analyser	£7000
IFR A7550 - 10KHz-GHz - Portable	£1750
Meguro - MSA 4901 - 30MHz - Spec Analyser	£600
Meguro - MSA 4912 - 1MHz - 1GHz Spec Analyser	£750
Tektronix 492P (opt 1,2,3) 50KHz - 21GHz	£3500
Willtron 6409 - 10-2000MHz R/F Analyser	£1250
Tektronic 2782 (100Hz-33GHz) Spec. An.	£9995

### Radio Communications Test Sets

Anritsu MT 8801C Radio Comms Analyser 300kHz - 3GHz (opt 1,4,7)	£6500
Hewlett Packard 8920B (opts 1,4,7,11,12)	£6750
Marconi 2955	£1250
Marconi 2955A	£1750
Marconi 2955B/60B	£3500
Marconi 2955R	£1995
Racal 6111 (GSM)	£1250
Racal 6115 (GSM)	£1750
Rohde & Schwarz CMD 57 GSM test set (opts B1/34/6/7/19/42/43/61)	£7995
Rohde & Schwarz CMT 90 (2GHz) DECT	£3995
Rohde & Schwarz CMTA 94 (GSM)	£4500
Schlumberger Stabilock 4031	£2750
Schlumberger Stabilock 4040	£1300
Wavetek 4103 (GSM 900) Mobile phone tester	£1500
Wavetek 4106 (GSM 900, 1800, 1900) Mobile phone tester	£2000

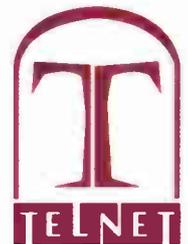

### MISCELLANEOUS

Ballantine 1620A 100Amp Transconductance Amplifier	£1750
EIP 545 Microwave Frequency Counter (18GHz)	£1000
EIP 548A and B 26.5GHz Frequency Counter	from £1500
EIP 575 Source Locking Freq.Counter (18GHz)	£1200
EIP 585 Pulse Freq.Counter (18GHz)	£1200
Genrad 1657/1658/1693 LCR meters	from £500
Gigatronics 8541C Power Meter + 80350A Peak Power Sensor	£1495
Gigatronics 8542C Dual Power Meter + 2 sensors 80401A	£1995
Hewlett Packard 339A Distortion measuring set	£750
Hewlett Packard 436A power meter and sensor (various)	from £750
Hewlett Packard 3335A - synthesiser (200Hz-81MHz)	£1995
Hewlett Packard 3457A multi meter 6 1/2 digit	£850
Hewlett Packard 3784A - Digital Transmission Analyser	£3750
Hewlett Packard 37900D - Signalling test set	£2950
Hewlett Packard 4274A LCR Meter	£2000
Hewlett Packard 4276A LCZ Meter (100MHz-20KHz)	£1400
Hewlett Packard 5342A Microwave Freq.Counter (18GHz)	£850
Hewlett Packard 5350B 20KHz Microwave Freq.Counter	£2000
Hewlett Packard 5385A - 1 GHz Frequency counter	£495
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6060A and B Electronic Load 300W	from £750
Hewlett Packard 6622A - Dual O/P system p.s.u.	£1250
Hewlett Packard 6624A - Quad Output Power Supply	£2000
Hewlett Packard 6632A - System Power Supply (20v-5A)	£695
Hewlett Packard 8350B - Sweep Generator Mainframe	£1500
Hewlett Packard 8642A - high performance R/F synthesiser (0.1-1050MHz)	£2500
Hewlett Packard 8656A - Synthesised signal generator	£750
Hewlett Packard 8656B - Synthesised signal generator	£995
Hewlett Packard 8657A - Synth. signal gen. (0.1-1040MHz)	£1500
Hewlett Packard 8657B - 100MHz Sig Gen - 2060 MHz	£3950
Hewlett Packard 8657D - XX DQPSK Sig Gen	£3950
Hewlett Packard 8901B - Modulation Analyser	£2250
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1000
Hewlett Packard 11729B/C Carrier Noise Test Set	from £2500
Hewlett Packard 53131A Universal Frequency counter (3GHz)	£850
Hewlett Packard 85024A High Frequency Probe	£1000
Keithley 228A Prog'ble Voltage/Current Source IEEE.	£2000
Keithley 237 High Voltage - Source Measure Unit	£4500
Keithley 238 High Current - Source Measure Unit	£4500
Keithley 486/487 Picoammeter (+voltage source)	£1350/£1850
Keithley 8006 Component Test Fixture	£1750
Marconi 2840A 2 Mbit/s Transmission Analyser	£1100
Marconi 6950/6960/6960A/6970A Power Meters & Sensors	from £400
Philips 5515 - TN - Colour TV pattern generator	£1400
Philips PM 5193 - 50 MHz Function generator	£1350
Philips PM 6654C System Timer Counter	£750
Sig. Gen. (100KHz-140MHz) AM/FM/CW	as new £650
Rohde & Schwarz FAM (opts 2,6 and 8) Modulation Analyser	£3750
Rohde & Schwarz NR/NRVD Power meters with sensors	from £1000
Schlumberger 1250 Frequency Response Analyser	£2250
Tektronix 1720 Vectorscope	£1150
Tektronix 1735 Waveform Monitor	£1150
Wavetek 178 Function generator (50MHz)	£750
Wayne Kerr 3245 - Precision Inductance Analyser	£1850
Bias unit 3220 and 3225L Cal.Coil available if required.	(P.O.A)
Wayne Kerr 3260A + 3265A Precision Magnetics Analyser with Bias Unit	£5500
Wayne Kerr 6245 - Precision Component Analyser	£2250
W&G PCM-4 PCM Channel measuring set	£3750

All equipment is used - with 30 days guarantee and 90 days in some cases

Add carriage and VAT to all goods.

Telnet, 8 Cavans Way, Binley Industrial Estate,

Coventry CV3 2SF.

Tel: 02476 650 702

Fax: 02476 650 773

Web: [www.telnet.uk.com](http://www.telnet.uk.com)

Email: [sales@telnet.uk.com](mailto:sales@telnet.uk.com)

# CONTENTS

NOVEMBER 2002

VOLUME 108

NUMBER 1799

## 3 COMMENT

Recession bites

## 5 NEWS

- Scientists explain metal superconductor
- Bristol bins its batteries
- Graphics adds stength to ARM



- Fingerprints get embedded
- Liquid spray-cooling



- Cheap computer nears production
- Disc drive makers go for terabytes
- Ribbons make light work
- Go low for low
- Robot arm uses air muscles

## 12 LOW-VOLTAGE LOW POWER CMOS INTEGRATED

**Giuseppe Ferri and Nicola C. Guerrini** propose some integrated interfaces for capacitive, resistive and temperature sensors designed with portability in mind.

## 22 WIDE DIGITAL I/O FROM THE USB PORT

Intrigued by **Colin Attenborough's** recent article on digital i/o using the USB port, but don't like PLDs? Read on, as with this article Colin shows how the PLD can be swapped for four standard CMOS ICs, with increased word width as a bonus.

## 27 NEW PRODUCTS

The month's top new products.

## 34 CIRCUIT IDEAS

- PIC programming solution
- PIR enhancement
- TDA7000 signal strength display

## 40 CAPACITOR SOUND

This month, **Cyril Bateman** concentrates on the difficult area of 100nF to 1 $\mu$ F,



which usually for size and cost reasons means using metallised PET products

## 52 RF AUTO-TRANSFORMERS LINE DEVICES MODELLED USING SPICE


**Nic Hamilton** (G4TXG) proposes an improved model for the small-signal RF auto-transformer with a ferrite core and illustrates it by building a SPICE model for a typical small signal RF transformer.

## 24 LETTERS

- MFB (or not?)
- No conspiracy
- Shock hazard
- Wien revisited
- CPU architecture
- More thoughts
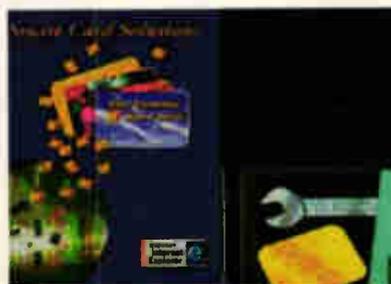
## 60 WEB DIRECTIONS

Useful web addresses for electronics engineers.



Cover Illustration: Robot arm from the Shadow Robot Company, see page 10.

December issue on sale 7 November

# PROTEUS

## VSM

Virtual System Modelling


Build It In Cyberspace

[www.labcenter.co.uk](http://www.labcenter.co.uk)

CIRCLE NO. 105 ON REPLY CARD

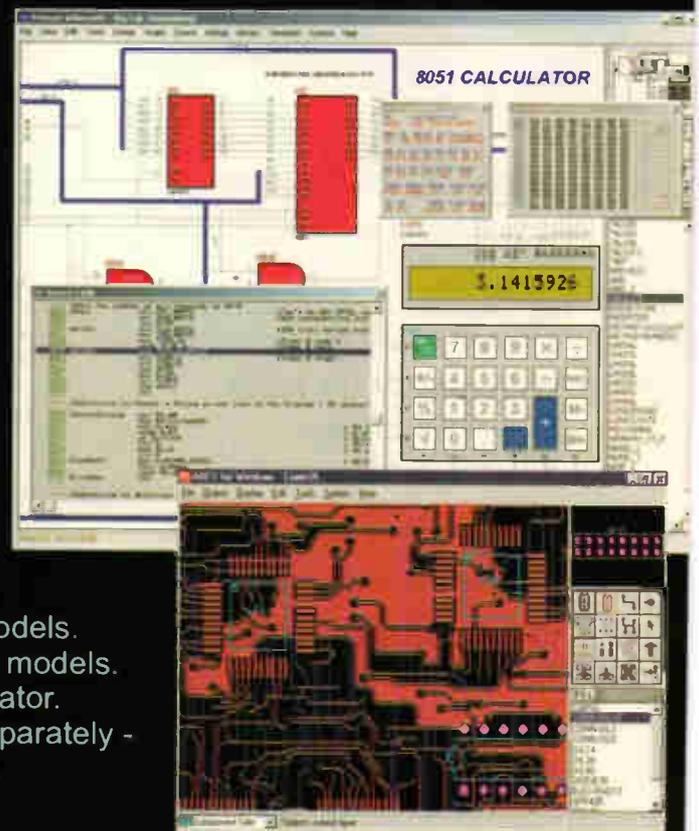**Develop and test complete micro-controller designs without building a physical prototype. PROTEUS VSM simulates the CPU and any additional electronics used in your designs. And it does so in real time. \***

- CPU models for PIC and 8051 and series micro-controllers available now. 68HC11 coming soon. More CPU models under development. See website for latest info.
- Interactive device models include LCD displays, RS232 terminal, universal keypad plus a range of switches, buttons, pots, LEDs, 7 segment displays and much more.
- Extensive debugging facilities including register and memory contents, breakpoints and single step modes.
- Source level debugging supported for selected development tools.
- Integrated 'make' utility - compile and simulate with one keystroke.
- Over 4000 standard SPICE models included. Fully compatible with manufacturers' SPICE models.
- DLL interfaces provided for application specific models.
- Based on SPICE3F5 mixed mode circuit simulator.
- CPU and interactive device models are sold separately - build up your VSM system in affordable stages.
- ARES Lite PCB Layout also available.



labcenter  
E l e c t r o n i c s

\*E.g. PROTEUS VSM can simulate an 8051 clocked at 12MHz on a 300MHz Pentium

Write, phone or fax for your free demo CD - or email [info@labcenter.co.uk](mailto:info@labcenter.co.uk).  
Tel: 01756 753440. Fax: 01756 752857. 53-55 Main St, Grassington. BD23 5AA.

**EDITOR**  
Phil Reed  
p.reed@highburybiz.com

**CONSULTANT**  
Ian Hickman

**CONTRIBUTING EDITOR**  
Martin Eccles

**EDITORIAL ADMINISTRATION**  
Jackie Lowe  
020 8722 6054

**EDITORIAL E-MAILS**  
j.lowe@highburybiz.com

**GROUP SALES**  
Reuben Gurunlian  
020 8722 6028

**ADVERTISEMENT  
E-MAILS**  
r.gurunlian@highburybiz.com

**EDITORIAL FAX**  
020 8722 6098

**CLASSIFIED FAX**  
020 8722 6096

**PUBLISHING DIRECTOR**  
Tony Greville

**MANAGING DIRECTOR**  
Roy Greenslade

**ISSN 0959-8332**  
**SUBSCRIPTION QUERIES**  
Tel (0) 1353 654431  
Fax (0) 1353 654400

**Disclaimer**  
We work hard to ensure that the information presented in *Electronics World* is accurate. However, *Electronics World's* publisher - Highbury Business Communications - will not take responsibility for any injury or loss of earnings that may result from applying information presented in the magazine. It is your responsibility to familiarise yourself with the laws relating to dealing with your customers and suppliers, and with safety practices relating to working with electrical/electronic circuitry - particularly as regards electric shock, fire hazards and explosions.

*Electronics World* is published monthly. Orders, payments and general correspondence to **Jackie Lowe, Highbury Business Communications, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ.**  
**Newstrade:** Distributed by COMAG, Tavistock Road, West Drayton, Middlesex, UB7 7QE Tel 01895 444055.  
**Subscriptions:** Wyvern Subscription Services, Link House, 8 Bartholomew's Walk,

Ely Cambridge, CB7 4ZD. Telephone 01353 654431. Please notify change of address.  
Subscription rates 1 year UK £38.00 2 years £61.00 3 years £76.00. Europe/Eu 1 year £54.00 2 years £86.00 3 years £108.00 ROW 1 year £63.00 2 years £101.00 3 years £126  
**Overseas advertising agents:** France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business

Publishing Ltd, 475 Park Avenue South, 2nd Fl New York, NY 10016 Tel: (212) 679 8888 Fax: (212) 679 9455  
**USA mailing agents:** Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.  
**Printed by** Polestar (Colchester) Ltd,  
**Filmsetting by** G&E 2000  
A1 Parkway, Southgate Way, Orton Southgate, Peterborough, PE2 6YN

  
**HIGHBURY**  
**Business Communications**  
A SUBSIDIARY OF HIGHBURY HOUSE COMMUNICATIONS PLC

## Recession bites

I have to say that I think the recession and effects of the terrorist attacks on the US are making themselves felt in the electronics industry. Certainly, anybody who is in the entertainment electronics business will be having a hard time.

Why do I say this? I have literally just returned from the International Broadcast Convention in Amsterdam where the mood was one of 'let's hope it can't get any worse'. The lack of spending on the high street affects the companies making the direct sales of home electronics which in turn affects the media companies whose lives depend on manufacturers and suppliers advertising (which fuels TV and radio stations and even magazines like this one.)

The good thing about the exhibition was that the 'time wasters' did not show up and so the quality of visitor was very high. But only things that could save operating costs were being taken seriously at the show, as with all those channels to fill and a shrinking advertising pot - something's got to give.

I think that is true of all manufacturing at the moment, even in non-electronic circles. Ways are having to be found that enable cheaper (and possibly better) products, whether it be a TV programme or a process controller. Slicker manufacturing, lower waste and less labour costs are the vogue.

One of my annoyances at these international industry events (certainly in Europe) is that you never see any government representation. You don't get government ministers (and I'm not just talking about Britain) looking around or even opening a show. There is a creative TV show that happens in Edinburgh every year. For the last two years, the minister responsible for the broadcast industry has snubbed it with the most lame of excuses. What is it about governments that makes them think they can make decisions about industries without (it appears) knowing a whole lot about them?

The equivalent US broadcast show (NAB) at least attracts some government dignitary (I remember Ronald Reagan opening one year) and you see government agencies wandering around the show. Not that that means that good decisions are made. Witness the amazing mess the FCC (broadcast's governing body in the US) has made regarding the introduction of high definition television and digital broadcasting.

Despite my rants above, there was some good news. As I said, processes that save overheads were seriously being looked at, especially if the ROI (return on investment) was short. And some US friends reported that the telecoms industry was picking up again - a bit too late for Marconi - but I expect a lot of you that work in that part of electronics will be breathing a small sigh of relief.

My last rant this month is the imposition by Europe of an Electronic Data Protection Directive that basically forces businesses to retain electronic data for a longer period of time. ISPs, internet companies and telecoms firms will have to keep records of emails and web caches. At the moment it does not extend to the contents - although the UK government can gain access to this in special circumstances. All this is not going to be paid for by governments, but rather indirectly by you and me in our internet charges. This is seriously going to hamper the roll-out of broadband - which just may have been something to hike the electronics industry out of its doldrums. I, for one, do not want people to know what I watch or surf to - if only to keep the target advertisers (and hence lots of junk mail) away from my mail box. And I don't see why I should have to pay for my ISP to store loads of stuff that I don't want it to.

And the UK government wants its citizens to file their tax returns via the internet by 2010 or get fined £3,000.

Phil Reed, Editor.



# THE IEC 320 CONNECTION



CALL OUR SALES HOTLINE

**020 8905 7273**



24 HOUR DELIVERY SERVICE

OLSON ELECTRONICS LIMITED  
OLSON HOUSE, 490 HONEYPOT LANE, STANMORE, MIDDX HA7 1JX  
TEL: 020 8905 7273 FAX: 020 8952 1232  
e-mail: sales@olson.co.uk web site: <http://www.olson.co.uk>

GB 1907

## Scientists explain metal superconductor

The discovery early last year that magnesium diboride ( $MgB_2$ ) is a superconductor at 39° kelvin opened up the possibility for cheap superconductors. It also left many scientists puzzled as to the mechanism that allowed the material to superconduct at such a relatively high temperature.

However, researchers at the Lawrence Berkeley National Laboratory and the University of California at Berkeley claim to have figured out  $MgB_2$ 's properties.

"Structurally, magnesium diboride is almost as simple as pencil lead, graphite," says Professor Steven Louie from Berkeley Labs. "It consists of hexagonal honeycombed planes of boron atoms separated by planes of magnesium atoms, with the magnesiums centred above and below the boron hexagons."

Louie and his team used a theory called Bardeen-Cooper-Schrieffer

(BCS) to study the material, showing how electrons combine to form pairs, which leads to superconductivity. To form the pairs, electrons exchange a phonon.

With  $MgB_2$  it seemed that different types of electron were involved in the pairing. Looking at the material's graphite-like planar structure, electrons in the boron plane of the

$MgB_2$  form different pairs to electrons out of the plane of the material.

The differing pairs are nicknamed red and blue electrons. The difference is helping to explain some of the somewhat bizarre properties shown by  $MgB_2$ . Both types of pairs are destroyed if the temperature exceeds 39°K, and the material ceases to superconduct.

## Bristol bins its batteries

Bristol City Council has begun a scheme to recycle batteries, removing potential toxic chemicals from household waste.

Although not the first recycling proposal for batteries in the UK, it is the first to collect batteries alongside household rubbish, rather than having battery banks scattered around the city.

The scheme will include rechargeable batteries which have

outlived their usefulness.

Britain has been slower than other countries to catch on to the idea of separate collections for householders. The Netherlands, Germany, Switzerland and Japan all collect batteries separately from domestic refuse.

It has been calculated that something approaching a billion batteries are sold in the UK every year.

## Graphics adds strength to ARM

Coming to a handheld computer or smartphone near you are 3D graphics such as these pictured.

Cambridge processor firm ARM spent the summer showing off the graphics capability it gained by licensing technology from Imagination Technologies.

ARM is using Imagination's PowerVR MBX core, which uses a tile-based approach to rendering 3D scenes, making it suitable for varying sizes of display.

When combined with an ARM9 processor, the MBX core could easily

render images onto screens ranging from 320x240 pixels up to full PC-type displays.

"Our objective with Imagination is to create a standardised graphics platform for a number of different markets," said Noel Hurley, manager for consumer entertainment at ARM. The firm expects the combined technologies to be designed into third generation mobile phones, in-car systems and even set-top boxes.

ARM has developed a range of MBX cores, each targeting different applications. A 3G phone processor

would be able to render some one million triangles/s, while a set-top box version could handle 2.5 million, said Hurley.

"It's a Sega Dreamcast type of performance," he said.

In order to download games to a mobile handset in reasonable time, ARM has teamed up with Superscape, another UK firm. It has developed a way of drastically reducing file sizes for 3D gaming.

*Images output direct from a test rig combining an ARM processor and 3D graphics core.*



## Fingerprints get embedded

A Lithuanian firm has developed a fingerprint sensing system aimed at embedded devices.

Neurotechnologija said its FingerCell design is aimed at providing controlled entry to doors, gates and computers. It can be used for both verification of a user or identification, the firm said.

The board is based around a 206MHz StrongARM processor, while the sensor itself is supplied by Authentec.

Software, which takes up some 512kbyte of space on the board, is supplied by the firm in ANSI C format.

"Developing a superior embedded biometric identification system is a long and expensive undertaking. Our FingerCell EDK greatly shortens the




process," said Dr Algimantas Malickas, Neurotechnologija's chief executive.

The false rejection rate is claimed to be three per cent, while false acceptance rate is said to be 0.001 per

cent. The system can learn and store a new print in under one second.

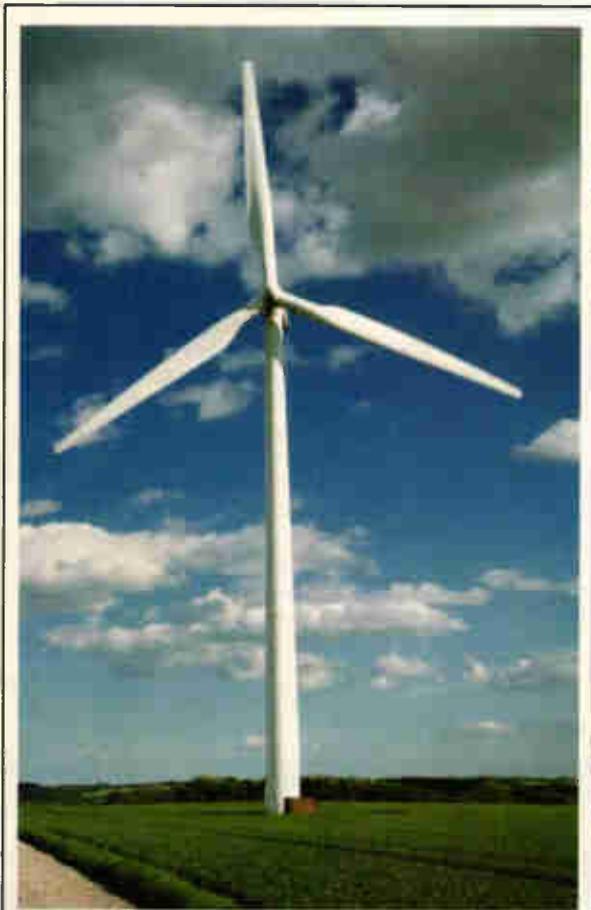Evaluation software and a sample fingerprint database can be downloaded from the firm's site at [www.neurotechnologija.com](http://www.neurotechnologija.com)



*Ben & Jerry's, the ice cream company, is to offset CO<sub>2</sub> emissions at its Vermont factory by supporting the construction of a wind turbine in South Dakota. Through an organisation called NativeEnergy's 'WindBuilders Business Partner' program, the machine will be erected on the Rosebud Sioux Tribe Wind Turbine Project - the first Native American owned and operated large-scale wind turbine in the USA. The turbine is expected to be working by November. [www.nativeenergy.com](http://www.nativeenergy.com)*

## Linux runs on Xbox

A group of German programmers have managed to boot a version of the Linux operating system on Microsoft's Xbox gaming console.


The addition of a \$30 chip to allow the machine to run unsigned code, leaves Xbox ready for Linux, the team said. Linux can be booted from flash or, more likely, from a CD inserted in the console.

Since Xbox contains an Intel processor, hard disc and DVD drive, it is perfect for use as a very low cost

PC, although not running any Microsoft applications.

Although the operating system is running, the team has yet to add drivers for the full video and audio systems. It plans to do this next, along with drivers for standard keyboard and mouse.

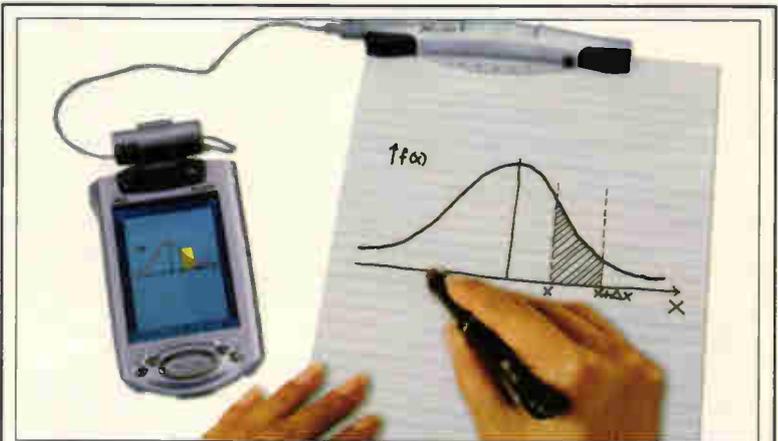The Xbox could be used as a PC, web server or as a node in a cluster. Being Linux, the operating system can be downloaded and copied freely. [xbox-linux.sourceforge.net](http://xbox-linux.sourceforge.net)



*If you think on paper, but work on computer, Seiko could have just the gadget for you.*

*InkLink, as it is called, is a pocket-sized device designed to transcribe handwritten notes and drawings to a PDAs or computer as they are written with a special pen.*

*Palm, Pocket PC and Windows are supported and data is transferred*

*through infra-red or USB.*

*Proprietary software, InkNote Manager, allows users to cut, copy, paste, e-mail and store handwritten notes as .ink vector files, but also allows the files to be exported in .bmp, .png, and .jpg formats.*

*The unit is 193 x 74 x 143mm and weighs 143g. Price is £99. [www.seikosmart.com](http://www.seikosmart.com)*

## Gentle spray cools better than air or water

As conventional heatsinking approaches its limits, two teams of US researchers are investigating a modified form of spray cooling for over-hot electronics.

While people have been blowing air at, spraying liquid over, and pumping water through hot assemblies for years, these latest efforts micro-spray the semiconductor dies directly.

At University of California, Los Angeles, Professor Elliott Brown found liquid spray-cooling could improve the performance of insulated gate bipolar transistors (IGBTs) in motor drives by as much as 34 per cent. "Significantly greater power than can be achieved with the same chips using conventional cooling," said Brown.

Over at HP Labs, Chandrakant Patel, principal scientist at HP's Thermo-Mechanical Architecture Lab, is cooling chips by spraying them from ink-jet-like nozzles.

According to Patel, existing chip power densities span 40 to 70W/cm<sup>2</sup>, but parts of PC processor chips will reach 200W/cm<sup>2</sup> within four years. Conventional heatsinking cannot deal with this, he said, and liquid-cooling based on low-boiling point materials

runs out at 100W/cm<sup>2</sup> as bubbles form over hotspots.

Spray cooling is already known, but Patel asked: "Wouldn't it be nice if we could put just enough fluid on the chip so that it goes 'psst' and vaporises without formation of any bubbles"?

And this is what he is doing.

Back at UCLA, Brown's research is with power transistors.

Above temperatures of 150°C, said UCLA, transistor life falls and at 200°C they cease to function.

As well as IGBTs, Brown looked at mosfets in 500MHz rf power amplifiers where spraying "was an order of magnitude more effective at removing heat".

In a 60W radio frequency power amplifier, spray-cooling disbursts about 20W of heat, he said.

Whereas HP is using special insulating low-boiling point liquids, UCLA researchers found that water is the best at their temperatures. As the water goes straight on the die, its top surface is coated with a conformal dielectric.

The UCLA nozzle is a 4.86x1.53mm block of silicon with a 28x18 hole matrix "to exactly match



the layout of the active cells", Brown said.

35µm jets are formed by reactive-ion etching to produce very smooth sidewalls.

Both cooling systems could be neatly packaged as closed systems with the chips they service. [www.hpl.hp.com/news/2002/apr-jun/cooling\\_demo.html](http://www.hpl.hp.com/news/2002/apr-jun/cooling_demo.html)

## Cheap computer nears production

Simputer, the computer-for-India, is nearing limited production.

"We have made considerable progress in the development of a new version of the Simputer which has several interesting features that help in product expansion and connectivity," said Shashank Garg, v-p of product development at Encore Software in Bangalore.

Encore is one of the original contributors to the development of the Simputer and also one of the earliest commercial licensees of the Simputer platform.

The computer now has a CompactFlash socket through an optional docking cradle "that could be used for CF-II compliant cards such as a flash card or a Wireless LAN (Wi-Fi) interface. We also offer a choice of colour or monochrome LCD displays," said Garg.

Originally envisaged as a computer for people who cannot read, Simputer uses specially-written Information Mark-up Language (IML). "It could well be

Standard Simputer evaluation kits			
Model	Display	ram Mbyte	flash Mbyte
ESKIT-3216M	mono	32	16
ESKIT-3216C	colour	32	16
ESKIT-6432M	mono	64	32
ESKIT-6432C	colour	64	32

called an Illiterate Mark-up Language," said the Simputer Trust.

Customised devices will be available for large volume customers and "our current plan calls for launching 200 evaluation kits by the middle of August, and a subsequent launch of 1,000 Simputers, before large scale production starts", said Garg.

Orders for the kits are now being accepted with delivery within eight to ten weeks of receipt, claimed Garg.

[www.ncoretech.com](http://www.ncoretech.com)  
[www.simputer.org](http://www.simputer.org)



## Disc drive makers go for Terabytes

UK hard disc technology developer NanoMagnetics has taken another step forward in its work on nanoparticulate magnetic films, by storing 12Gbit of data per square inch.

The latest announcement doubles the density of nanoparticulate systems. "A doubling in areal recording density in just over six weeks highlights the strength of this team and the promise of this technology," said Dr Eric Mayes, the company's co-founder and chief technology officer.

The areal density record for this

type of material does not match that achieved today by commercial hard discs, but the materials have fewer theoretical limits on density.

Nanoparticulates, in theory at least, should not be affected by the so-called 'superparamagnetic' limit that will soon be causing problems for conventional magnetic thin films.

The Bristol-based firm believes its technology will lead to discs that store 100 times more data, with drives able to store Terabytes of information.

Not to be outdone, hard drive

manufacturer Seagate recently outlined its bid to escape the superparamagnetic limit. It will use heat assisted magnetic recording (HAMR) on future disc drives.

HAMR also uses a particulate structure, with ordered arrays of iron-platinum particles spread across the disc. It heats the area of the disc being written, which makes it more stable, and subsequent cooling is claimed to stabilise the data.

Seagate also expects to reach densities of around 50Gbit/inch<sup>2</sup> with this technique.

## Tiny ribbons make light work of displays

Sony is to take forward the grating light valve (GLV) display device invented by California-based Silicon Light Machines, now owned by Cypress Semiconductor.

GLV is a micromachined technology that can achieve a contrast ratio of 3,000:1, claims Sony, making it ideal for projection display

products including large-screen TVs.

So far the company does not have hard plans to make finished products.

"We don't have any specific product schedule applying grating light valve display device so far. Currently, Sony is seeking the possibility to introduce this display device as a device itself in next two years," said Sony spokesman Shinji Obana.

The active part of a GLV pixel is six shiny metal ribbons mounted side-by-side facing the same way.

In the relaxed state the ribbons form a highly reflective rectangular mirror.

In the active state, every second ribbon is attracted out of the mirror plane by up to half a wavelength. When fully activated, destructive interference occurs in the light and


the pixel reflects hardly any light.

Partial operation, which can be achieved to any degree, produces grey-scales.

Sony's prototype device is 34 x 6 x 2mm, having 1,080 pixels (6,480 ribbons) in one long line. Red, green and blue lasers scan the grating to produce 1,920 x 1,080 high-definition colour images.

Sony has been working with Silicon Light Machines for a while, with the original aim of developing mass-produced display products.

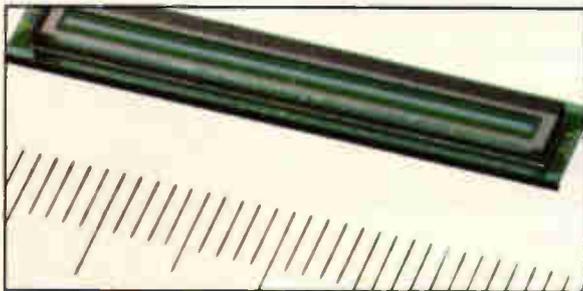Since then, in order to make sure the device succeeds, Sony has worked to develop micromachining technology to allow it to make the GLVs as well as developing other components including the laser sources.



## Swiss go low for flow

A Swiss firm has developed a liquid flow meter capable of measuring flows as low as 150nanolitre/minute.

Sensirion's device uses the

calorimetric principle to measure mass flow. A temperature sensor measures the calorific change from a constant temperature source.

The speed of the liquid through the pipe directly affects the calorific change between the temperature heads. Knowing the cross-sectional area of the pipe allows mass flow to be calculated from the flow rate.

The use of this technique, rather than impeller type systems, means the system can handle bi-directional flows.

The device is also non-invasive to the liquid flow. Sensirion said it can be used to measure viscous materials or those containing contaminants.

At the heart of the device is a CMOS chip which integrates the sensing elements, analogue to digital converter and basic signal


processing functions.

Combining all the essential functions on one chip makes the sensor ten times smaller and around 25 times lighter than competing systems, the firm claimed. It is also said to be 100 times more responsive. Response time is down to 20ms, the firm claimed.

Sensirion has already started selling products based around the sensor, the first being the ASL1430. It has either a 10 to 500[μl]/min range or a 5 to 1,000[μl]/min range. Accuracy is claimed to be better than 1.3 per cent.

Supply voltage is between 7 and 18V. The sensor will typically draw 20mA at 9V. The data output is RS232 compliant.

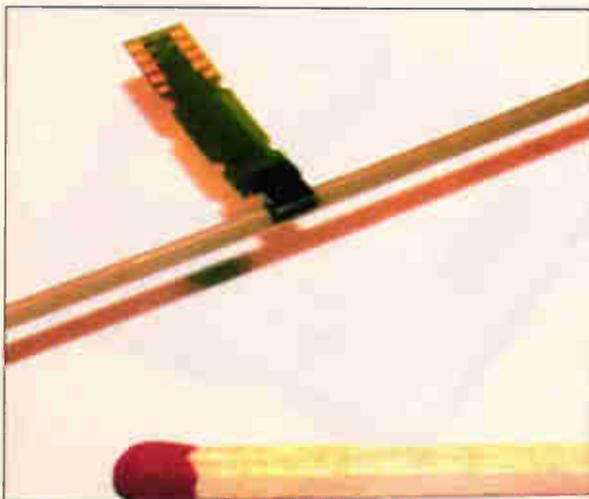Evaluation kits comprising the sensor, PC software, cables and fittings is priced at €3,000.



**QUASAR ELECTRONICS LIMITED**

(Dept EW), PO Box 6935, Bishops Cleeve, CM23 4WP  
**TEL: 01279 467799 FAX: 07092 203496**

ADD £2.00 P & P to all orders (1<sup>st</sup> class Recorded £4, Next day (Insured £250) £7, Europe £5.00, Rest of World £10.00). We accept all major credit cards. Make cheques/PO's payable to Quasar Electronics. Prices include 17.5% VAT. MAIL ORDER ONLY FREE CATALOGUE with order or sent 2 x 1" class stamps (refundable) for details of over 150 kits & publications.



**Enhanced 'PICALL' ISP PIC Programmer**

Kit will program virtually ALL 8 to 40 pin serial and parallel programmed PIC microcontrollers. Connects to PC parallel port. Supplied with fully functional pre-registered PICALL DOS and WINDOWS AVR Software packages, all components and high quality DSPTH board. Also programs certain ATMEL AVR, SCENIX SX and EEPROM 24C devices. New devices can be added to the software as they are released. Blank chip auto detect feature for super-fast bulk programming. Hardware now supports ISP programming. \*A 40 pin wide ZIF socket is required to program 0.3" devices (Order Code AZIF40 @ £15.00).



Order Ref	Description	inc. VAT ea
3144KT	Enhanced PICALL ISP PIC Programmer	£64.95
AS3144	Assembled Enhanced PICALL ISP PIC Programmer	£74.95
AS3144ZIF	Assembled Enhanced PICALL ISP PIC Programmer c/w ZIF socket	£89.95

**ATMEL 89xxxx Programmer**

Powerful programmer for Atmel 8051 micro controller family. All fuse and lock bits are programmable. Connects to serial port. Can be used with ANY computer and operating system. 4 LEDs indicate programming status. Programs 89C1051, 89C2051, 89C4051, 89C51, 89LV51, 89C52, 89LV52, 89C55, 89LV55, 89S8252, 89LS8252, 89S53 & 89LS53 devices. NO special software needed - uses any terminal emulator program (built into Windows).

Order Ref	Description	inc. VAT ea
3123KT	ATMEL 89xxxx Programmer	£29.95
AS3123	Assembled 3123	£44.95

Atmel 89Cx051 and AVR programmers also available.

**PC Data Acquisition & Control Unit**

Use a PC parallel port as a real world interface. Unit can be connected to a mixture of analogue and digital inputs from pressure, temperature, movement, sound, light intensity, weight sensors, etc. (not supplied) to sensing switch and relay states. It can then process the input data and use the information to control up to 11 physical devices such as motors, sirens, other relays, servo motors & two-stepper motors.



**FEATURES:**

- 8 digital Outputs: Open collector, 500mA, 33V max
  - 16 Digital Inputs: 20V max. Protection 1K in series, 5.1V Zener to ground.
  - 11 Analogue Inputs: 0-5V, 10 bits (5mV/step)
  - 1 Analogue Outputs: 0.2.5V or 0-10V. 8 bit (20MV/step.)
- All components provided including a plastic case (140mm x 110mm x 35mm) with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo). with screen printed front and rear panels supplied. Software utilities & programming examples supplied.

Order Ref	Description	inc. VAT ea
3093KT	PC Data Acquisition & Control Unit	£99.95
AS3093	Assembled 3093	£124.95

**ABC Mini 'Hotchip' Board**




ABC Starter Pack

Currently learning about microcontrollers? Need to do something more than flash a LED or sound buzzer? The ABC Mini 'Hotchip' Board is based on Atmel's AVR 8535 RISC technology and will interest both the beginner and expert alike. Beginners will find that they can write and test a simple program, using the BASIC programming language, within an hour or two of

connecting it up. Experts will like the power and flexibility of the Atmel microcontroller. as well as the ease with which the little Hot Chip board can be "designed-in" to a project. The ABC Mini Board 'Starter Pack' includes just about everything you need to get up and experimenting right away. On the hardware side, there's a pre-assembled micro controller PC board with both parallel and serial cables for connection to your PC. Windows software included on CD-ROM features an Assembler, BASIC compiler and in-system programme. The pre-assembled boards only are also available separately.

Order Ref	Description	inc. VAT ea
ABCMINISP	ABC MINI Starter Pack	£59.95
ABCMINIB	ABC MINI Board Only	£34.95

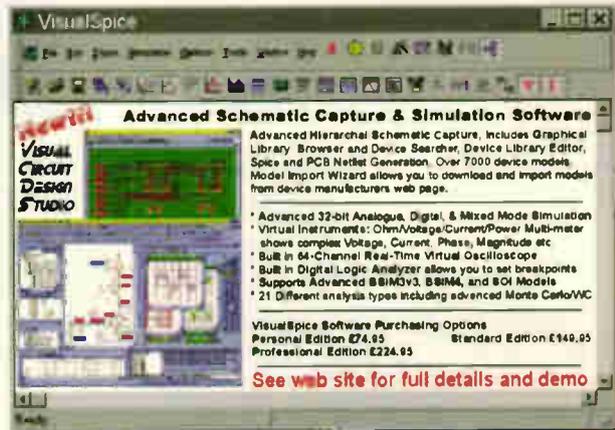**Advanced 32-bit Schematic Capture and Simulation Visual Design Studio**



**Serial Port Isolated I/O Controller**

Kit provides eight relay outputs capable of switching 5 amps max and four optically isolated inputs. Can be used in a variety of control and sensing applications including load switching, external switch input sensing, contact closure and external voltage sensing. Programmed via a computer serial port, it is compatible with ANY computer & operating system. After programming, PC can be disconnected. Serial cable can be up to 35m long, allowing 'remote' control. User can easily write batch file programs to control the kit using simple text commands. NO special software required - uses any terminal emulator program (built into Windows). Screw terminal block connections. All components provided including a plastic case with pre-punched and silk screened front/rear panels to give a professional and attractive finish (see photo).



Order Ref	Description	inc. VAT ea
3108KT	Serial Port Isolated I/O Controller Kit	£54.95
AS3108	Assembled Serial Port Isolated I/O Controller	£69.95

Full details of these items and over 200 other projects can be found at [www.QuasarElectronics.com](http://www.QuasarElectronics.com)



## Robot arm uses air muscles

North London robot R&D firm Shadow Robot Company has received £75,000 from lottery-funded NESTA (National Endowment for Science, Technology and the Arts) to develop a robot that can perform tasks for disabled people.

Shadow aims eventually to produce a multi-functional robot that can be guided, trained and programmed to carry out a wide variety of useful tasks for the disabled.

Shadow already has 'air muscles' - tubes which shorten as air is pumped in - which have been used in a fully functional analogue of the human hand.

"Systems based on the hand have the potential to make significant social contributions by enabling and empowering people through the creation of assistive devices," said Shadow.

The device the firm intends to develop will have a hand and arm on a wheeled base, with remote control and camera systems, so a user can



guide the robot through simple tasks.

For example, the company envisions a user sending the robot to the bathroom to fetch a drink of water.

Initially the robot will be stupid but "over time, open-source software will be developed to perform more complex tasks automatically".

The Shadow Robot Company is a group of inventors working towards the long-term goal of producing a useful humanoid robot. MD Richard Greenhill, has been working in the robotics field since 1981 and in 1987 he set up the Shadow Robot Project where a group of enthusiasts would meet once a week to build a bipedal robot.

In 1997, the Shadow Robot Company was established to carry out robotic research and prototyping. Since then the company has received a number of contracts to build robots, including the BBC's Tomorrow's World and a Scandinavian toy manufacturer. [www.shadowrobot.co.uk](http://www.shadowrobot.co.uk)



## A soft touch makes sleek products.

Hampshire-based touch switch company Quantum Research Group has announced a six-channel device.


Called QT160, the chip includes a Risc processor which analyses signals to detect touch electrostatically through glass (up to 10cm thick), plastic, stone, ceramic, or even wood. It can also turn conductive objects into touch sensors.

"It not only allows manufacturers to create sleek touch controls, but also offers a practical way to create sealed, IP67 rated keypads," said the company.

The device requires only one capacitor per channel to function. Each of the 6 channels operates independently and sensitivity can be set per channel by changing the capacitor.

Adjacent key suppression blocks response from weaker responding keys and accepts only the dominant key - to solve the problem of large fingers on tightly spaced keys or water films over several keys.

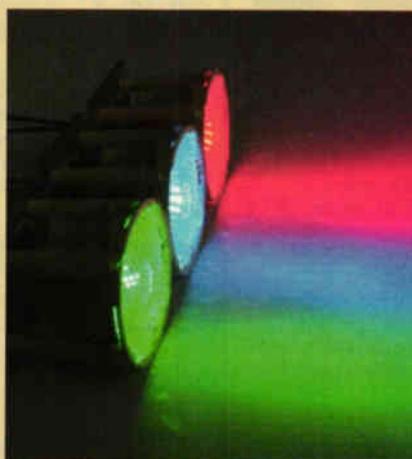The E160 evaluation board, pictured, demonstrates all these capabilities.



The Italian branch office of US optical company Fraen has developed a family of lenses suitable for Lumileds' Luxeon range of high-intensity LEDs.

The family currently has four lenses - Luxeon calls them 'collimators' - Narrow (6 to 10°), Middle (25 to 30°), Wide (40 to 45°) and Elliptical (10x20 to 12x25°). In each, the actual angle depends on the Luxeon model combined with the lens. Fraen claims they are "available for all the Lumileds Luxeon version: batwing 1W, Lambertian 1W and also for the new 5W Leds". The naked lenses may be combined with Fraen's universal lens holder for convenient mounting and alignment, said the company. [www.fraen.com](http://www.fraen.com)

## GIANT 10" 7 SEGMENT DISPLAYS

A bulk purchase enables us to bring to you these GIANT 10" segment digital displays at a now affordable price!! The 10" character size gives exceptional readability at long distances and enables a host of applications including score boards, digital clocks, counters, event timers etc. As the units are a simple electromechanical device and operate from 12V DC, simple switching via switches, relays, PIC or PC may be used to control single or multiple digits. Units feature integral Zero Power memory which greatly simplifies design. For an excellent DIY practical article, see the May issue of **Everyday & Practical Electronics**' magazine. Ideal School / College construction project. Supplied in good RFE condition, complete with data sheet.

Less than 30% of makers price! **Only £29.95(B)** or 4 / **£99.00(D)**

Order RW44      Order PH26



## THE AMAZING TELEBOX

Converts your colour monitor into a **QUALITY COLOUR TV!!**

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully unbreakable off air UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PIP (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

**TV SOUND & VIDEO TUNER**  
CABLE COMPATIBLE™

TELEBOX ST for composite video input type monitors **£36.95**  
TELEBOX STL as ST but fitted with integral speaker **£39.50**  
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner **£69.95** or overseas PAL versions state 5.5 or 6 MHz sound specification.  
For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Telebox's, code (B)

**NEW** State of the art PAL (UK spec) UHF TV tuner module with composite TV pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 60 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £39.95 code (B)**  
See [www.distel.co.uk/data\\_my00.htm](http://www.distel.co.uk/data_my00.htm) for picture + full details

## HARD DISK DRIVES 2fi" - 14"

fi" TOSHIBA MK1002MAV 1.1Gb laptop (12.5 mm H) **New £59.95**  
fi" TOSHIBA MK4313MAT 4.3Gb laptop (8.2 mm H) **New £105.00**  
fi" TOSHIBA MK6409MAV 6.1Gb laptop (12.7 mm H) **New £98.00**  
fi" TOSHIBA MK1814GAV 18 Gb laptop (12 mm H) **New £149.95**  
fi" to 3fi" conversion kit for Pc's, complete with connectors **£15.95**  
fi" COMPAQ 313706-B21 (IBM) 9 gb ULT/SCSI3 **New £199.00**  
fi" FUJI FK-309-26 20mb MFH I/F RFE **£59.95**  
fi" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE **£59.95**  
fi" CONNER CP3044 40 mb IDE I/F (or equiv.) RFE **£69.00**  
fi" QUANTUM 40S Prodrive 42mb SCSI I/F, New RFE **£49.00**  
fi" MINISCRIBE 3425 20mb MFH I/F (or equiv.) RFE **£49.95**  
fi" SEAGATE ST-238R 30 mb RLL I/F Refurb **£69.95**  
fi" CDC 94205-51 40mb HM MFH I/F RFE tested **£69.95**  
fi" HP 97548 850 Mb SCSI RFE tested **£99.00**  
fi" HP C3010 2 Gbyte SCSI differential RFE tested **£195.00**  
fi" NEC D2246 85 Mb SMD interface. **New £99.00**  
fi" FUJITSU M2322K 160Mb SMD I/F RFE tested **£195.00**  
fi" FUJITSU M2392K 2 Gb SMD I/F RFE tested **£345.00**

Many other floppy & H drives, IDE, SCSI, ESDI etc from stock, see website for full stock list. 22 on page ls code (C)

## TEST EQUIPMENT & SPECIAL INTEREST ITEMS

ITSUBUSHI FA3445ETKL 14" Ind. spec SVGA monitors **£245**  
ARNELL 0-60V DC @ 50 Amps, bench Power Supplies **£995**  
ARNELL AP3080 0-30V DC @ 80 Amps, bench Supply **£1850**  
INGSHILL CZ403/1 0-50V @ DC 200 Amps - NEW **£3950**  
w to 400 kW - 400 Hz 3 phase power sources - ex stock **EPOA**  
IM 8230 Type 1, Token ring base unit driver **£760**  
ayne Kerr RA200 Audio frequency response analyser **£2500**  
IFODEC 1U, 24 port, RJ45 network patchpanels. #TH93 **£49**  
COM 16670 12 Port Ethernet hub - RJ45 connectors #LD97 **£69**  
COM 16671 24 Port Ethernet hub - RJ45 connectors **£89**  
COM 16700 8 Port Ethernet hub - RJ45 connectors NEW **£39**  
IM 53F5501 Token Ring IC5 20 port lobe modules **EPOA**  
IM MAU Taken ring distribution panel 8228-23-5050N **£45**  
IM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE I/O **£550**  
LLGON 8360.11805-1880 MHz hybrid power combiners **£250**  
end DSA 274 Data Analyser with G703(2M) 64 i/o **EPOA**  
arconi 6310 Programmer 2 to 22 GHz sweep generator **£4500**  
arconi 2022C 10KHz-1GHz RF signal generator **£1550**  
P1650B Logic Analyser **£3750**  
P3781A Pattern generator & HP3782A Error Detector **EPOA**  
P621A Dual Programmable GPIB PSU 0-7 V 160 watts **£1800**  
P626A Rack mount variable 0-20V @ 20A metered PSU **£475**  
S54121A DC to 22 GHz four channel test set **EPOA**  
P8130A opt 020 300 MHz pulse generator, GPIB etc **£7900**  
P A1, A0 8 pen HPGL high speed drum plotters - from **£550**  
P DRAFTMASTER 1 8 pen high speed plotter **£750**  
P 3-G Brookdeal 95035C Precision clock in amp **£1800**  
ithley 590 CV capacitor / voltage analyser **EPOA**  
ical ICR40 dual 40 channel voice recorder system **£3750**  
skers 45KVA 3 ph On Line UPS - New batteries **£4500**  
erson AP130 2.5KVA industrial spec. UPS **£1499**  
ann Tally MT645 High speed line printer **£2200**  
tel SBC 486/133SE Multibus 486 system, 8Mb Ram **£945**

## IC's - TRANSISTORS - DIODES

OBSELETE - SHORT SUPPLY - BULK  
**10,000,000 items EX STOCK**  
For MAJOR SAVINGS  
CALL or see web site [www.distel.co.uk](http://www.distel.co.uk)  
**COMPUTER MONITOR SPECIALS**

**Legacy products**  
**High spec genuine multisync.**  
CGA, EGA, VGA, SVGA

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, test switching and LOW RADIATION MPR specification. Fully guaranteed, in EXCELLENT little used condition. Tilt & Swivel Base **£4.75**

VGA cable for IBM PC included. **Only £129 (E)** Order as CG73

External cables for other types of computers available - CALL

**Generic LOW COST SVGA Monitors**  
We choose the make, which includes Compaq, Mitsubishi, IBM, etc. Supplied ready to run with all cables, Standard RTB 90 day guarantee.

14" <b>£59.00</b> order TD84	15" <b>£69.00</b> order TG21	17" <b>£79.00</b> order TJ66
------------------------------------	------------------------------------	------------------------------------

Supplied in good used condition. Shipping code (D)

## VIDEO MONITORS

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed. Dimensions: W14" x H12" x 15" D. **Only £99.00 (D)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13" D. 240 V AC mains powered. **Only £79.00 (D)**

## INDUSTRIAL COMPUTERS

Tiny shoebox sized industrial 40 Mhz 386 PC system measuring only (mm) 266 w x 88 h x 272 d. Ideal for dedicated control applications running DOS, Linux or even Windows I Steel case contains 85 to 265 V AC 50 / 60 Hz 70 Watt PSU, a 3 slot ISA passive backplane and a Rocky 318 (PC104) standard, single board computer with 8 Mbyte NON VOLATILE solid state 'Disk On Chip' RAMDISK. System comprises: Rocky 318 (PC104) SBC ISA card with 40MHz ALI 386SX CPU, 72 pin SIMM slot with 16 Mbyte SIMM, AMI BIOS, battery backed up real time clock, 2 x 9 pin D 16550 serial ports, EPP/ECP printer port, mini DIN keyboard connector, floppy port, IDE port for hard drives up to 528 Mbyte capacity, watchdog timer and PC/104 bus socket. The 8 Mbyte solid state 'disk on a chip' has its own BIOS, and can be formatted, formatted & booted. Supplied BRAND NEW fully tested and guaranteed. For full data see featured item on website. Order as QG36 100's of applications inc: **Only £99.00 (D)**  
firewall, routers, robotics etc

Unless marked NEW, items in this section are pre owned.

HP6030A 0-200V DC @ 17 Amps bench power supply **£1950**  
Intel SBC 486/125C08 Enhanced Multibus (MSA) New **£1150**  
Nikon HFX-11 (Ephiphot) exposure control unit **£1450**  
PHILIPS PM5518 pro. TV signal generator **£1250**  
Motorola VME Bus Boards & Components List. SAE / CALL **EPOA**  
Trio 0-18 vdc linear, metered 30 amp bench PSU. New **£550**  
Fujitsu M3041R 600 LPM high speed bench printer **£1950**  
Fujitsu M3041D 600 LPM printer with network interface **£1250**  
Siemens K4400 64Kb to 140Mb demux analyser **£2950**  
Perkin Elmer 299B Infrared spectrophotometer **£500**  
Perkin Elmer 597 Infrared spectrophotometer **£3500**  
VG Electronics 1035 TELETEXT Decoding Margin Meter **£4250**  
LightBand 60 output high spec 2u rack mount Video VDA's **£395**  
Sekonic SD 150H 18 channel digital Hybrid chart recorder **£1995**  
B&K 2633 Microphone pre amp **£300**  
Taylor Hobson Tallysurf amplifier / recorder **£750**  
ADC SS200 Carbon dioxide gas detector / monitor **£1450**  
BBC AM20/3 PPM Meter (Ernest Turner) + drive electronics **£75**  
ANRITSU 9654A Optical DC-2.5G/b waveform monitor **£5650**  
ANRITSU ML93A optical power meter **£990**  
ANRITSU Fibre optic characteristic test set **EPOA**  
R&S FTDZ Dual sound unit **£650**  
R&S SBUF-E1 Vision modulator **£775**  
WILTRON 6630B 12.4 / 20GHz RF sweep generator **£5750**  
TEK 2445 150 MHz 4 trace oscilloscope **£1250**  
TEK 2465 300 MHz 300 MHz oscilloscope rack mount **£1955**  
TEK TD380 400MHz digital realtime + disk drive, FFT etc **£2900**  
TEK TD524A 500MHz digital realtime + colour display etc **£5100**  
HP3585A Opt 907 20Hz to 40 MHz spectrum analyser **£3950**  
PHILIPS PW1730/10 60KV XRAY generator & accessories **EPOA**  
VARIACS - Large range from stock - call or see our website **£325**  
CLAUDE LYONS 12A 240V single phase auto. volt. regs **£325**  
CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs **£2900**

## 19" RACK CABINETS

Europe's Largest Stocks of  
quality rack cabinets,  
enclosures and accessories.  
Over 1000 Racks from stock

This month's special  
**33 / 42 / 47 U - High Quality**  
**All steel Rack Cabinets**

**BIG £ SAVER**

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue, some grey available - CALL - Can be supplied in many other configurations.



<b>33U</b> Order as BC44 External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 1/2" W) Only <b>£245</b>	<b>42U</b> Order as DT20 External dimensions mm=2019H x 635D x 603 W. (79.5" H x 25" D x 23 1/2" W) Only <b>£345</b>	<b>47U</b> Order as RV36 External dimensions mm=2235H x 635D x 603 W. (88" H x 25" D x 23 1/2" W) Only <b>£410</b>
---	---	---

Call for shipping quotation

## COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power I A quality product featuring a fully cased COLOUR CCD camera at a give away price! Unit features full auto light sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data, 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.

Order as LK33 **ONLY £79.00 or 2 for £149.00 (B)**



## SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. **ONLY £89.00 (B)**  
ENCARTA 95 - CDROM, Not the latest - but at this price! **£7.95**  
DOS 5.0 on 3fi" disks with concise books c/w QBasic. **£14.95**  
Windows for Workgroups 3.11+ No Disc 6.22 on 3.5" disks **£55.00**  
Windows 95 CDROM Only - No Licence **£19.95**  
Wordperfect 6 for DOS supplied on 3fi" disks with manual **£24.95**

shipping charges for software is code B

## SOLID STATE LASERS

Visible red, 670nm laser diode assembly. Unit runs from 5 V DC at approx 50 mA. Originally made for continuous use in industrial barcode scanners, the laser is mounted in a removable solid aluminium block, which functions as a heatsink and rigid optical mount. Dims of block are 50 x 50 x 15 mm. Integral features include over temperature shutdown, current control, laser OK output, and gated TTL ON / OFF. Many uses for experimental optics, comms & lightshows etc. Supplied complete with data sheet.


Order as TD91 **ONLY £24.95 (A)**

## DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock - Call or see our web site.
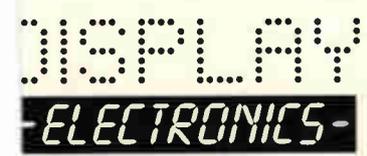
## RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site [www.distel.co.uk](http://www.distel.co.uk) for more information. Many obsolete types from stock. Save ££££'s



**ALL MAIL TO**  
Dept W, 29 / 35 Osborne Rd  
Thornton Heath  
Surrey CR7 8PD, UK  
Open Mon - Fri 9.00 - 5:30

**18 Million Items On Line Now!**  
Secure Ordering, Pictures, Information  
**www.distel.co.uk**  
email = [admin@distel.co.uk](mailto:admin@distel.co.uk)

**ALL ENQUIRIES**  
**0208 653 3333**  
FAX 0208 653 8888



All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £100. Cheques over £100 are subject to 7 working days clearance. Carnage charges (A)=£3.50, (B)=£6.50, (C)=£10, (D)=£15.00, (E)=£18.00, (F)=CALL. Allow approx 3 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale which can be viewed on our website and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 2002. E & O E.

# Low-voltage low-power CMOS integrated architectures for sensor interfaces

**Giuseppe Ferri and Nicola C. Guerrini propose some integrated interfaces for capacitive, resistive and temperature sensors designed with portability in mind.**

In this work we shall propose some integrated interfaces for capacitive, resistive and temperature sensors. The topologies have been developed in CMOS technology that give the possibility of being included in portable systems where the sensor and the related electronics can be located. In applications like these, it is mandatory that circuits work at low supply voltages, with reduced power consumption and can therefore be supplied by a single-cell battery for all its lifetime (e.g., from 1.5V down to 1.2 V).

We have designed, as a 'general purpose' sensor front-end, a low-voltage low-power CMOS operational amplifier. In particular the amplifier shows low input noise and offset and the following main features: rail-to-rail input voltage range with constant  $g_m$ , full output voltage range, good DC voltage gain, high CMRR and PSRR. And special attention has been paid in the parasitic elements, which can affect sensor measurement.

The circuit interfaces have been developed considering the type of sensor and including where possible the cited amplifier. For capacitive sensors, in particular, the capacitive value is often converted to a frequency value through an oscillator configuration. Resistive sensors have interfaces mainly based on bridge circuits.

We propose a topology that recalls the Wheatstone bridge, but the branch resistances have been implemented

by MOS transistors. With respect to the traditional passive bridge, this circuit improves sensitivity and resolution. An alternative topology using a phase shifter allows us to avoid the offset and calibration problems belonging to the bridge solution. Other resistive interfaces can be realised by means of the same operational amplifier used for capacitive sensor interfaces, where the sensing element is the resistance instead of the capacitance.

In all the proposed schemes, particular attention has been dedicated to the sensor constraint verification and in particular all the topologies have to show a very low dependence on supply discharges and temperature variations.

Finally, temperature sensors have also been considered. In alternative to traditional topologies, which sense the base-emitter differences in bipolar transistors, a low-voltage low-power bridge structure has been implemented, in CMOS technology, which gives an output voltage proportional to the temperature. A high linearity for a large temperature range variation is guaranteed and resolution is one order of magnitude lower than that of commercial digital thermometers.

## Introduction

Modern microelectronic technology is capable of integrating a large amount of transistors on a single chip at reasonable costs. This enables the fabrication of highly complex electronic functions, amongst which are signal processing and data recording, etc. In this sense, it is necessary that the nature of the signal is electrical. Non-electrical information has to be converted through the use of sensors and actuators.

The integrated circuit technology has been continuously pushed towards the fabrication of devices operating with lower and lower operating supply voltages. The reason for

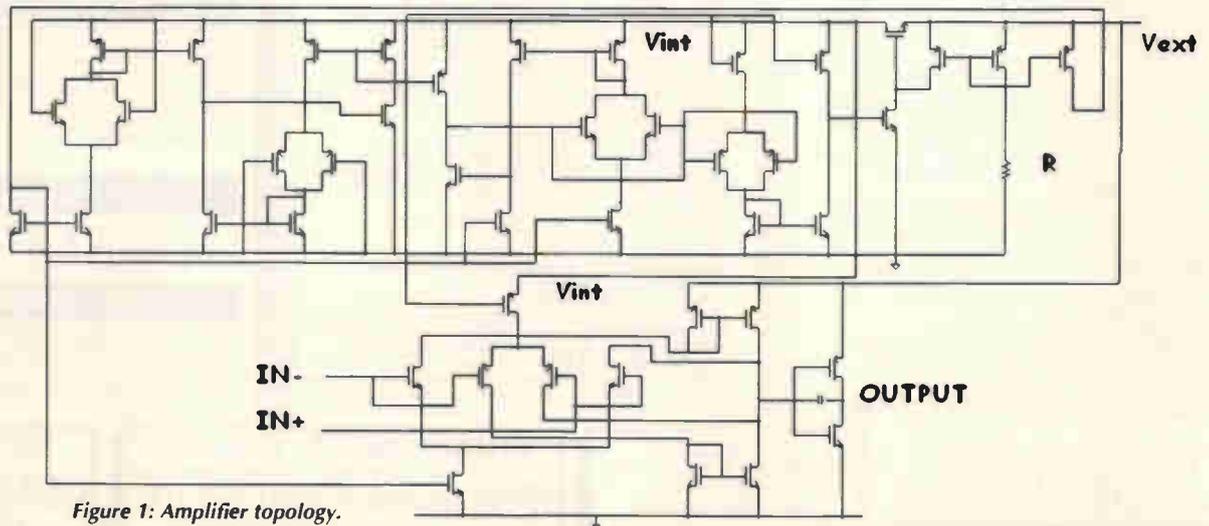


Figure 1: Amplifier topology.

this trend is mainly the increasing use of battery-operated portable electronics and wireless systems, which call for low power consumption, small size and low weight. Especially important is the need to reduce power dissipation in modern analogue and digital systems, which plays an important role in determining this trend. Also, a further push is due to the cultural scientific interest in exploring the technological and physical limits of the integrated devices.

Low-voltage, low-power structures find a natural but fundamental application in sensors and microsystems. In this field, there have not been any particular design constraints in the past, but actually new markets are moving towards the concept of portable and miniaturised products and the low-power solution is mandatory also for sensors and microsystems interfaces.

Hence, mixed analogue and digital electronics are becoming more and more important for sensors, because the chip-scale integration can be utilised for combining, on the same chip, existing standard IC processes, the sensing elements (if of silicon-type) and the processing electronics to fabricate 'smart sensors'. This is exalted by the fact that actually the same materials (silicon, polysilicon, aluminium and dielectrics) are used to fabricate the majority of sensors and electronic circuits.

In this way, CMOS has been proved to be the main sensor technology, because it is able to match the reduction of the technological costs with the design of new low-power interfaces.

Obviously, the first sensor interface has to be analogue, because of the analogue nature of the signal coming from the sensor. Moreover, analogue signal processing offers high functional density and an ability to interface directly the analogue real world of sensors. However, an A/D conversion of the output signal is also possible, so as to improve the quality of data display. In this case, owing to the sensor nature, no particular speed constraints are necessary. Traditional analogue-to-digital converters can be quite good for the purpose.

## Sensors

Sensors are physical devices which transfer information from six different energy domains (chemical, optical, mechanical, thermal, magnetic and electrical) into an electrical one, providing a broad variety of electrical signals, which are normally analogue.

With respect to electronic circuits integrated on the same chip, sensors are normally divided into two groups: *active* sensors, which give an output current or voltage, and *passive* sensors, which modify their internal parameters if an external force is applied.

In the first case, resistive bridges or magnetically sensitive transistors can be interfaced to signal processing and conditioning circuitry such as low-noise voltage or current amplifiers. The basic parameters of the passive sensors (the capacitance and the resistance) can be either directly measured or integrated with the sensor and some controlling topologies such as oscillators, bridges, charge amplifiers and switched-capacitor circuits.

In Table 1, typical electrical outputs from sensors are shown.

Output signals coming from sensors have the following characteristics: low-level signals, relatively slow sensing parameter variation and the need of initial calibration for long-term drift (it means they generally can be time-variant). For this reason, in order to save the results from measuring errors, the design of low-noise low-offset signal amplifiers with low parasitic transistors is essential. Another important parameter to be considered is the electrical impedance of the sensor, which determines the

**Table 1**

type of signal	typical range	type of sensor
voltage	$\mu\text{V}$	thermopiles, pyro, piezo
current	$\mu\text{A}$ -mA	pyro, magnetic
capacitance	fF- $\mu\text{F}$	humidity, gas, pressure
charge	pC	piezo
resistance	m $\Omega$ -M $\Omega$	pressure, chemical (gas)

frequency measurement range. The main sensor characteristics can be summarized in two parameters :

Sensitivity = electrical output variation / non-electrical parameter variation

Resolution = minimum detectable non-electrical parameter value in conditions of unitary signal-to-noise ratio.

Sensitivity has to be the highest possible and it has to be evaluated in the typical variation range of the non-electrical parameter. Possibly, it has to be linear and this means that its value does not depend on the working operating point. On the contrary, resolution has to be minimised and is definitively the most important sensor characteristic.

In the following sections, after the description of a low-voltage low-power integrated amplifier, to be used as a general purpose scheme for the sensor interface, examples of capacitive, resistive and temperature sensor interfaces working at low supply voltages with low power consumption will be presented, with the aim of helping the reader towards the concept of standard interface. Unfortunately, the literature suffers from the lack of universal interfaces to be utilised in a broad variety of sensing systems and also commercial integrated circuits are either for very specific applications or very complicated with a heavy digital elaboration part.

## Low voltage low power 'general purpose' amplifier

The proposed amplifier<sup>1</sup> can operate with a 1.5 V supply voltage (the minimum being 1.2 V) and the circuit architecture has been designed to obtain low offset, low input noise, rail-to-rail input and output common mode range and low power consumption. The amplifier topology (whose simplified schematic is in Fig. 1) has been also optimised for the lowest supply voltage compatible with the technology used (Mietec 0.7 $\mu$  with threshold voltages of about 0.75V). The circuit has also been redesigned at a 0.5 $\mu$  technology, and power dissipation has been reduced at less than 200 $\mu\text{W}$ .

The input and output full swing characteristic has been obtained in order to have a high signal-to-noise ratio when the amplifier is used in a follower configuration or in front-end circuits, where the signal comes directly from the sensor. This means that the range of the sensor response is not absolutely limited by the amplifier.

The amplifier topology differs from other literature solutions (working at higher supply voltages) for its constant- $g_m$  input stage that ensures a constant gain-bandwidth product over the input common mode voltage and, consequently, simpler frequency compensation. In Table 2 its main experimental characteristics are shown.

Particular attention has been paid in the design of the amplifier input stage, especially concerning its noise and offset and the input transistors have been designed to operate in weak inversion condition (WI).

In order to have low input noise, a study about the input

**Table 2**

Amplifier characteristics	Measured values
Input stage swing	rail-to-rail (from $V_{SS}$ to $V_{int} + 0.5V$ )
Output stage swing	rail-to-rail
Equivalent input voltage noise	10 nV/ $\sqrt{Hz}$ (@ 1kHz)
Input offset voltage	typ. = 0.2mV ; 3 $\sigma$ value = $\pm 0.08mV$
Input transconductance	constant ( $\Delta g_m$ MAX=6 %)
Gain Band Width (GBW)	1.3MHz (PM = 64°)
Low frequency gain	84dB
Power Consumption	0.46mW
Slew Rate	1V/ $\mu s$
Distortion THD (1Hz, $V_{pp}=60\%V_{AL}$ )	-40dB
CMRR	56dB @ 10Hz ; 52dB @ 100kHz
PSRR+	48dB @ 10Hz ; 26dB @ 100kHz
PSRR-	51dB @ 10Hz ; 32dB @ 100kHz
Chip area	1.2mm <sup>2</sup>


transistor condition has been done. In particular, the two noise contributions have been considered: thermal (inversely proportional to the input transconductance  $g_m$ ) and flicker (inversely proportional to MOS sizes and frequency, and consequently dominant at low frequencies):

$$\overline{dv_n^2(f)} = \frac{8kT}{3g_m} df + \frac{KF_F}{WLC_{ox}^2} \frac{df}{f}$$

where  $k$  is the Boltzmann constant,  $T$  the absolute temperature (in K),  $g_m$  the input transistor transconductance,  $KF_F$  the Spice flicker noise parameter,  $C_{ox}$  the oxide capacitance, and  $W$  and  $L$  the width and length of the input transistor.


The minimisation of the noise depends on the input transistor condition. In strong inversion (SI) there is a particular relation between  $W$  and  $L$ . In the case of WI, the previous function is typically minimised using the highest values of  $W$ . Unfortunately high values of  $W$  give high values of related parasitic capacitances. Of course, the design, in terms of noise minimisation, can be also optimised at the sensor working frequency.

Concerning the offset, an auto zero technique<sup>2</sup> which measures the systematic offset and subtracts it, has been considered. The basic idea of auto zero is the sampling of the unwanted quantity (noise and offset) which is then subtracted from the instantaneous value of the contaminated signal either at the input or the output of the op-amp. This cancellation can also be done at some intermediate node between the input and the output of the op-amp, using an additional input port defined as the nulling input and identified with the letter N in the schematic of Fig. 2.

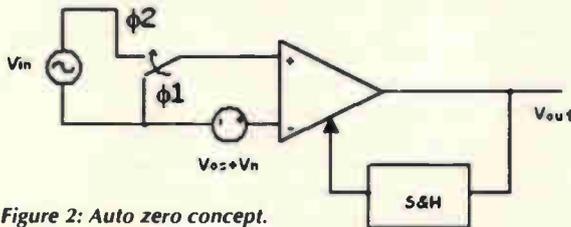

**Figure 2: Auto zero concept.**

If the noise is constant over time (like a DC offset) it will be cancelled, as is needed in a high precision amplifier or high resolution comparator. If the unwanted disturbance is a low frequency random noise (for example,  $1/f$  noise), it will be high-pass filtered and thus strongly reduced at low frequencies, but at the cost of an increased noise floor due to aliasing of the wideband noise inherent to the sampling process.

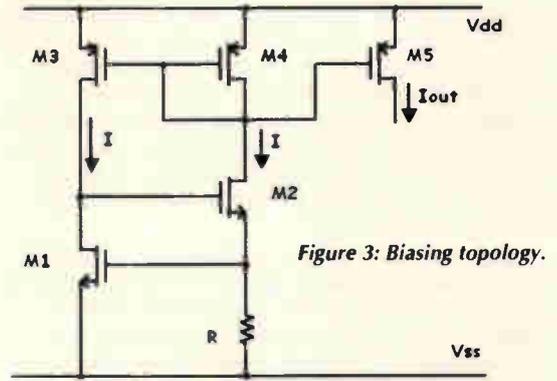

**Figure 3: Biasing topology.**

The auto zero process requires at least two phases: a sampling phase ( $\phi_1$ ) during which the offset voltage  $V_{OS}$  and the noise voltage  $V_N$  are sampled and stored, and a signal processing phase ( $\phi_2$ ) during which the offset free stage is available for operation.

The principle can be used not only to cancel the amplifier offset but also to reduce its low frequency noise. It should be noted that the effect of the auto zero is equivalent to subtracting from a time varying noise a recent sample of the same noise. For DC or very low frequency noise this results in a cancellation, so auto zero effectively high-pass filters the noise.

Particular attention has been paid to the layout design (a common centroe scheme) that helps to reduce the random offset coming from the technological spread of integrated transistors.

Finally, another important consideration has to be the biasing of the amplifier and of all the circuits to be used in sensor interfaces. It is important to implement a biasing current independent of the supply voltage variations<sup>3</sup>, so as to avoid performance reduction when the supply battery discharges. Fig. 3 shows this topology. It is easy to prove that:

$$IR = V_{GS1} = V_{t1} + \sqrt{\frac{2I}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}}$$

from which, if the transistor is working in WI, we can write :

$$I = \frac{V_t}{R}$$

The current  $I$  is independent of the supply voltage and depends very slightly on the temperature. It is mirrored into  $I_{out}$  (see Figure 3) with a unity gain mirror factor.

With commercial products, they typically have no supply voltage operation and so cannot be used in portable applications. For example, the National Semiconductor LM9044, a 'Sensor Interface Amplifier' is fabricated in bipolar technology. The amplifier is absolutely not low-voltage, because the supply voltage is  $\pm 60V$  and the power consumption is 1.3W. Dallas-Maxim Semiconductors seem to be the most suitable among the commercial companies. In particular the MAXIM452 is a 'sensor signal conditioner', formed by a processor with DAC and operational amplifier incorporating a temperature sensor. The supply voltage is 5V and power consumption is 10mW. Another interesting product is a current-sense amplifier for portable applications, namely the MAXIM4172, whose supply is 3V and power dissipation is 2.4mW. But this product is not specific for sensors. If you want more information, you can consult the web site: <http://www.maxim-ic.com>.

**Low voltage low power capacitive sensor interfaces.**

Capacitive sensors have been proved to be good transducers for signal conditioning electronics with reduced current consumption. In fact, they have a high impedance up to reasonably high measurement frequencies and high signal levels.

The capacitive sensors are often interfaced with read-out electronics that performs a capacitance-to-frequency conversion (as with oscillators and phase shifters). The topologies have to respect the following constraints: high dynamic range, good linearity and precision, low input noise and offset, long-term temperature stability, reduced area, low effect of parasitic capacitances and calibration and compensation of the transducer characteristics. These constraints have to be satisfied by interface circuits which, if designed with low-voltage low-power techniques, can be utilised in portable, remote and wireless systems for industrial, biomedical, automotive and consumer applications, where a great need of reliable and miniature sensor systems emerges.

The first two examples here presented will consider the application of the amplifier described in the previous section as a read signal amplifier in capacitive sensors, whose use is rather spread in many sensing systems.

The proposed interface architectures (an oscillator and a phase shifter) have been implemented with low-voltage and low-power constraints. The frequency of the signal at the output of the amplifier allows it to determine the value of the sensor, this frequency being inversely proportional to the capacitance. An automatic storage of the oscillation frequency has also been performed, using a frequency counter controlled by a PC via a GPIB (General Purpose Interface Bus) gate.

Figure 4 shows the topology of a traditional Schmitt trigger, utilized in an oscillator configuration, for the determination of the capacitance values<sup>4</sup>.

These values can be determined by reading the frequency of the oscillator, according to the following relation (if  $R_1=R_2$ ):  $f_{osc} @ 1 / (2.2R C_{sen})$ . The circuit has been tested for three decades of capacitance variations (from 1nF to 1µF), which it translates to a frequency span of three decades (from about 20Hz to 20kHz). The frequency values have been stored and elaborated in a personal computer by a GPIB interface. The sensitivity is about 100fF/Hz. Precise values of resistance (in particular of R) have been utilised and non-linear effects (among which the temperature) have been verified to be negligible in the frequency determination.

Figure 5 shows another topology developed to determine the capacitance values<sup>4</sup>. The main block is the traditional phase shifter, realised with the described

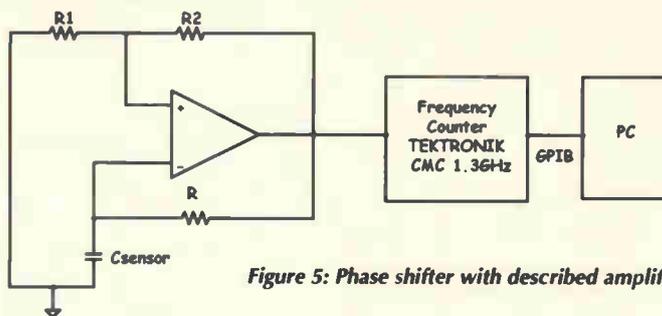


Figure 5: Phase shifter with described amplifier.

amplifier. The input signal is a sinusoidal voltage whose frequency has been set to the initial calibrated value. At the frequency of  $f_0=1/(2\pi RC_{sen})$ , the output of the amplifier is shifted  $-90$  degrees with respect to the input. Then, input and output curves have been sent to two Schmitt triggers, in order to obtain square-waved voltages. Hence, these signals are directed to a traditional EX-OR gate, supplied at low voltages, and used to automatically detect the frequency  $f_0$ . In fact, when the EX-OR gives an output signal at a frequency equal to  $2f_0$  with a duty cycle of 50%, the inputs of the EX-OR are in the  $-90^\circ$  shifting condition. In this manner, reading  $f_0$ , we know the capacitance sensor value. The values of the frequencies at the output of the amplifier and of the EX-OR have been stored in a PC by a GPIB.

The main problem related to the proposed topologies concerns the detection of small capacitance values. In this case, the key aspect of the problem is related to the sensing system, where the sensitivity to parasitic, interconnection wires and noise has to be the lowest. Other applications of the OTA can be easily realized in other sensing systems, as in resistive sensors.

A third capacitive sensor topology has been considered, formed by an oscillator<sup>5</sup>. This topology does not utilise the

Figure 6: Oscillator block diagram.

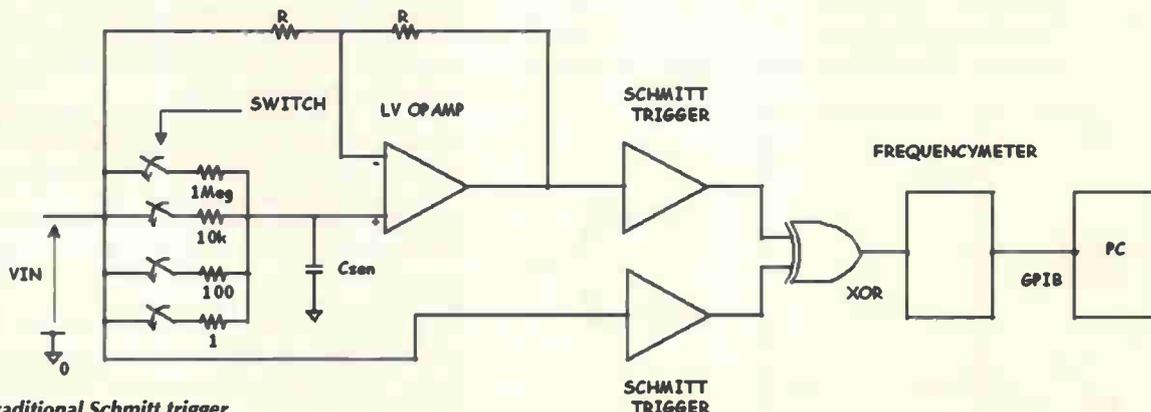
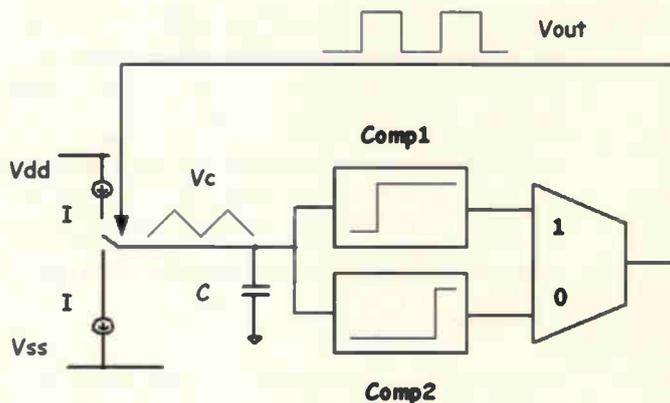


Figure 4: Traditional Schmitt trigger.

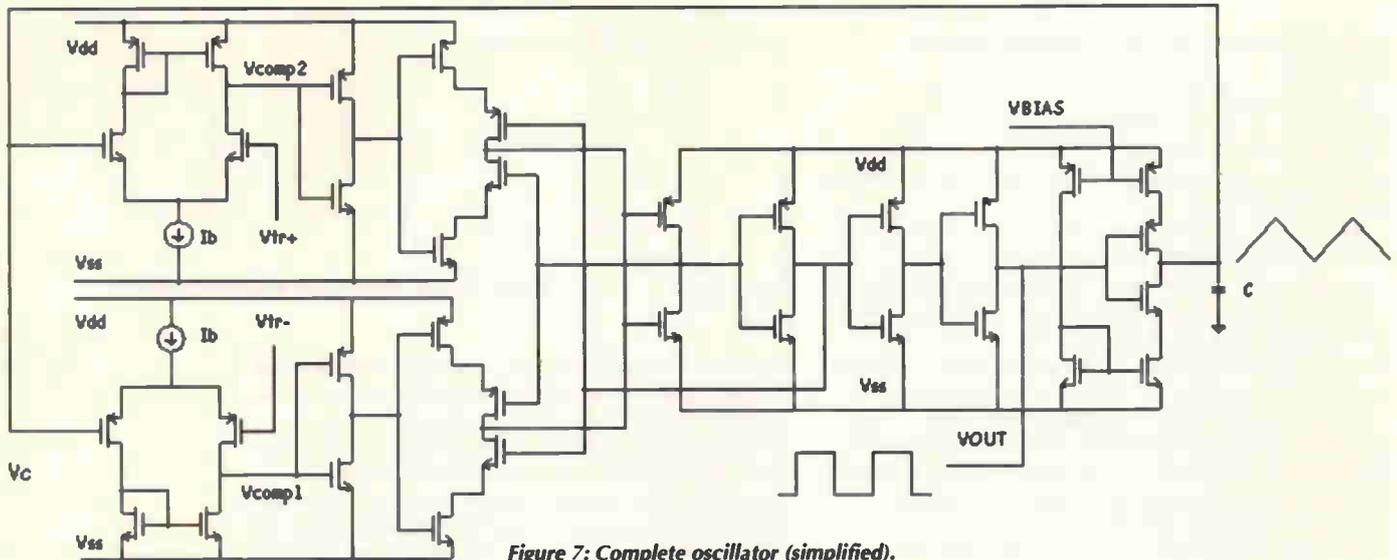


Figure 7: Complete oscillator (simplified).

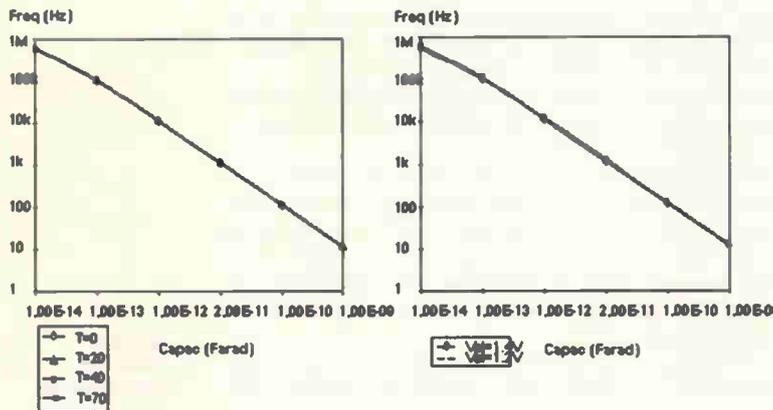


Figure 8: Frequency vs sensor capacitance.

amplifier to overcome the amplifier's imperfections. In order to understand the working principle, let us consider Fig.6 that shows the oscillator block scheme. The sensor capacitance C is charged and discharged with the constant currents I. The output voltage  $V_{out}$  drives the switch. The hysteresis comparator has been designed with two traditional comparators having different threshold voltages  $V_{tr+}$  and  $V_{tr-}$ . The aim of the comparator is to convert the triangular voltage  $V_C$  on the capacitor in a squared-wave, whose duty cycle is set by the choice of the current sources values. The output frequency is the following:

$$f = \frac{I}{2(V_{tr+} - V_{tr-}) C}$$

where the current I has been set to 20nA (by the use of suitable current mirrors) and the quantity in brackets is about 0.9 V, with the utilised technology. This solution can be particularly attractive because it gives an output frequency independent of resistive values. The outputs of

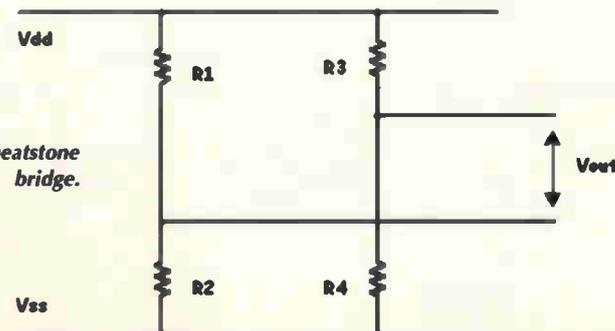


Figure 9: Wheatstone bridge.

each comparator are sent to a two-input multiplexer with the output fed back to the strobe terminal. By doing so, it can be easily shown that for  $V_C$  decreasing, the output of the multiplexer is determined by comp1, whereas for  $V_C$  increasing, it is determined by comp2.

The simplified schematic of the complete oscillator is in Fig. 7. Comparators are formed by simple differential structures. The p-type pair (lower), driven by  $V_{tr-}$ , is related to  $V_{comp1}$ , while the n-pair (upper), driven by  $V_{tr+}$ , generates  $V_{comp2}$ . The bias voltage controls the current sources, which charges and discharges C. Indeed, if  $V_{out}$  is high, the capacitance is discharging; on the contrary, if  $V_{out}$  is low, C is charging.

Figure. 8 shows the output frequency vs. sensor capacitance, at different temperatures (left) and supply voltages (1.4V and 1.2V, right). The circuit shows a very low power consumption (23µW) and a reduced dependence on supply voltage and temperature (0.06%/mV and 0.12%/°C, respectively). The flicker noise contribution has been reduced by the use of high area input transistors.

### Low voltage low power resistive sensor interfaces

Resistance variations are often measured interfacing the sensor element in the Wheatstone bridge configuration Fig. 9, where the sensor is one of the four branches of the bridge<sup>6</sup>. If the relative variation of the sensor resistance is less than 5%, an almost linear relation between the voltage output and the sensor variation exists. If  $V_{cc}$  is the total supply voltage, in this basic Wheatstone bridge, the sensitivity, defined as the ratio between the differential output voltage and the relative variation of the sensor resistance, is equal to  $V_{cc}/4$ . It has to be noted that this sensitivity can be increased if a differential stage is cascaded to the bridge output.

A novel circuit topology is presented here, based on the conversion of the passive resistances into active resistances, thus obtaining an improved performance.

The circuit here proposed makes use of CMOS elements in parallel to the resistances in each branch of the bridge. The conceptual scheme is shown in Fig. 10. The circuit is symmetrical in order to achieve a high CMRR performance and at the two outputs a common mode feedback circuit (CMFB) has been included to fix the output voltage at the half of the total supply, guaranteeing the maximum output dynamic range. The circuit has been designed to work with a low voltage supply (1.2V) and it also has low power consumption. As an example, the

performances of the CMOS bridge have been evaluated in two cases considering the bridge working with sensors of 10kΩ and 1MΩ respectively. Table 3 summarises the main circuit performances. In order to evaluate the advantages of the proposed topology, the sensitivity and the resolution have been evaluated and compared with those exhibited by the corresponding passive Wheatstone bridge. The sensitivity is 40 times better in the case of a sensor of 1MΩ and 120 times greater in the case of the sensor of 10kΩ, while the resolution has been improved by almost two orders of magnitude.

Another resistive sensor interface is shown in Fig. 11. Based on a phase shifter<sup>7</sup>, two equal source currents loads and unloads the capacitance, C. The output inverter, formed by transistors MPout and MNout, ensures a square wave at the output. If these transistors have the same β, the output delay  $T_d$  will be given by:

$$T_d = \frac{V_{sup} C}{2I}$$

being  $V_{sup}$  the total supply voltage. The delay time corresponds both to the capacitive loading time (from the negative supply to  $V_{sup}/2$ ) and to the unloading time (from the positive supply to  $V_{sup}/2$ ).

The proposed circuit performs a maximum delay time of a quarter of the input period (that means a 90° shift), achievable only with ideal current sources. However, the technological spread and the temperature dependence make it impossible to obtain a symmetrical output voltage even if the condition on equal β of transistors Mnout and Mpout is verified. For this reason and with the aim to increase the output shift, two equal phase shifters of Fig. 10 type can be cascaded. Calling with  $V_{th}$  is the inverter transition threshold voltage, the first shifter gives a delay of

$$\frac{C}{I} (V_{th} - V_{SS})$$

while the second shifter delay is

$$\frac{C}{I} (V_{DD} - V_{th})$$

This allows a total delay independent on  $V_{th}$  whose value is exactly the double of the previous delay. As a consequence, its maximum theoretical value is 180°.

In Fig. 12 we propose a circuit that allows the control of the delay time (and, consequently, of the shift) by the use of a trimmed resistance. Its delay time is proportional to the resistance value, as follows:

$$T_d = \frac{(R1 + R2)C}{R2} R_{sensor}$$

The measure of the delay time is directly proportional to the value of the sensor resistor. It is also

Table 3

	Sensor Resistance= 10kΩ	Sensor Resistance=1MΩ
Supply voltage	1.2V	1.2V
Power dissipation	254μW	113μW
Sensitivity	1.2mV/Ω	11.8μV/Ω
(corresponding passive bridge)	(0.01mV/Ω)	(0.3μV/Ω)
Resolution	$5.45 \cdot 10^{-5} \Omega/(Hz)^{1/2}$	$2.6 \cdot 10^{-3} \Omega/(Hz)^{1/2}$
(corresponding passive bridge)	$(4 \cdot 10^{-3} \Omega/(Hz)^{1/2})$	$(4.2 \cdot 10^{-1} \Omega/(Hz)^{1/2})$

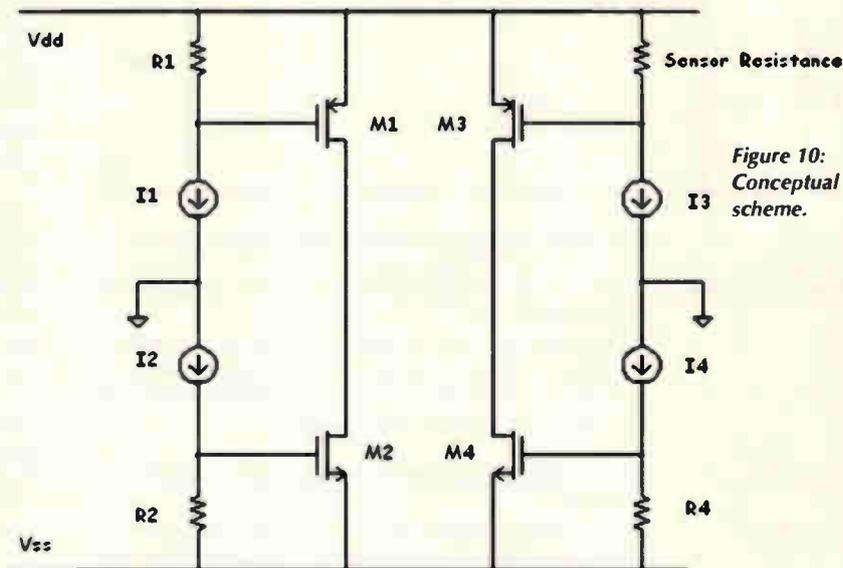


Figure 10: Conceptual scheme.

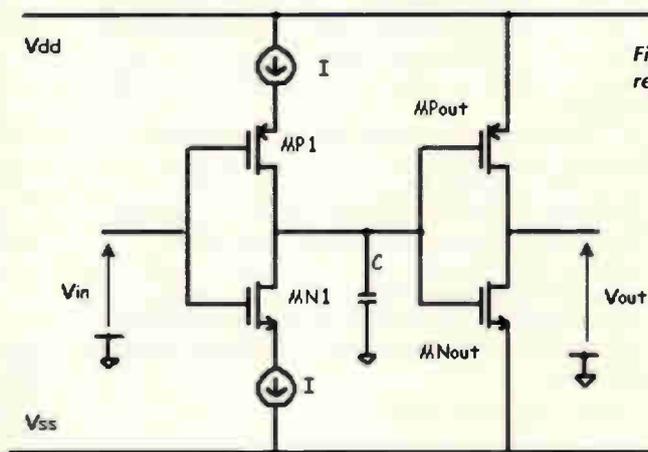


Figure 11: Phase shifter resistive interface.

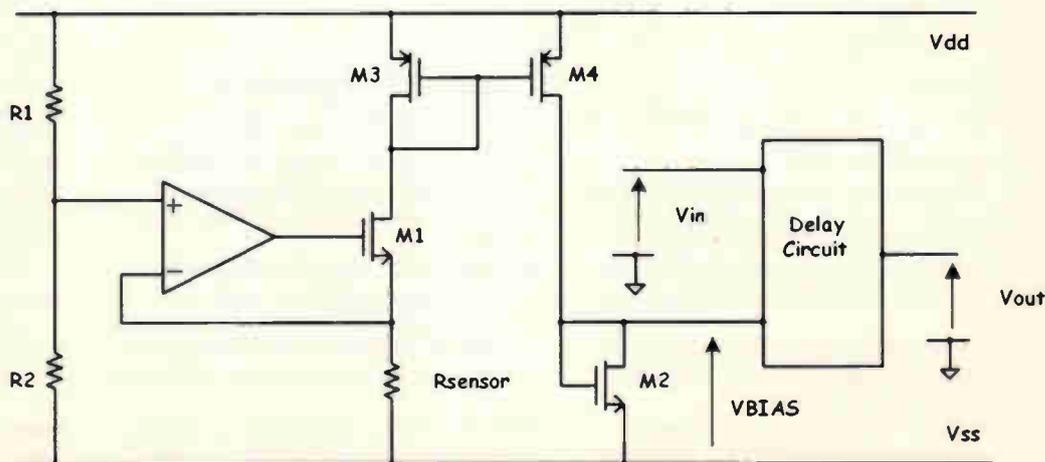


Figure 12: Controlling delay time.

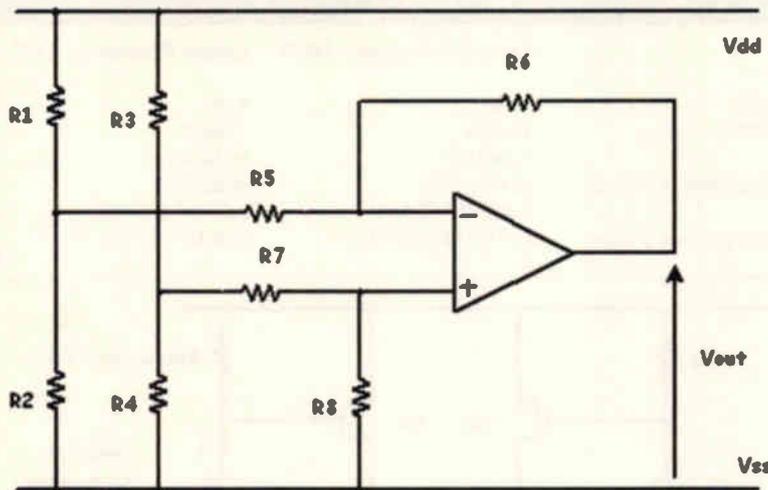


Figure 13: Introducing a differential amplifier.

possible to change the presented topology through the conversion of the shifter into an oscillator. In this case, once more the output frequency is inversely proportional to the sensor value.

Obviously, the first two topologies with the amplifier described in the previous section can be utilised to have a resistive sensor interface where the sensing element is the resistance instead of the capacitance.

**Low voltage low power temperature sensor interfaces**

Traditional temperature sensors make use of bipolar technology integrated in a chip. They normally sense the difference of two base-emitter voltages, biased by different currents, to detect temperature variation. To improve the sensitivity of this circuit they need a differential amplifier at the output. Unfortunately bipolar technology is very costly, so they actually have to be substituted by cheaper solutions.

A temperature sensor can be designed in a CMOS standard process (Mietec 0.7µ)<sup>8</sup>. It makes use of a temperature sensitive Wheatstone bridge, of Fig. 9 type. The bridge is fabricated using polysilicon resistor layers of positive first order temperature coefficients (a1 = 620ppm/°C) to fabricate opposite resistors R1 and R3 and of negative temperature coefficients (a2 = -2100ppm/°C) to fabricate R2 and R4. In this manner, the output voltage of the bridge will be proportional to temperature variation as follows:

$$V_{out} = \frac{1}{2}V_{cc} (a_1 - a_2) T$$

being Vcc the supply voltage and:

$$R_1 = R_3 = R_0 (1 + a_1 (T - T_0));$$

$$R_2 = R_4 = R_0 (1 + a_2 (T - T_0))$$

The output voltage is independent on the values chosen for the resistances. The circuit has been powered at low voltage supply (1V). The output sensitivity is about 1.3mV/°C. Resolution is 10<sup>-5</sup>°C, considering a 10kΩ resistance at room temperature. The introduction of a differential amplifier Fig. 13, which improves the circuit sensitivity, opens an interesting problem from the noise matching point of view. Using this logic, it is possible to determine the temperature range where the complete system has the best noise performance.

The total output noise depends on both the resistances' noise (thermal) and the amplifier noise (thermal and flicker). Noise calculation is fundamental to determine the system resolution. An accurate evaluation of the noise brings us to the conclusion that noise is generally given from external resistances if the described amplifier is used<sup>9</sup>.

A suitable design implies the possibility of having a high linearity for a large temperature range variation. A 0.01°C resolution, one order of magnitude lower than commercial digital thermometers (e.g., National Semiconductor LM 35 and all the other related ICs, whose minimum resolution is 0.5°C at 25°C), can be achieved even if for a confined range of temperature (0-40°C).

**Conclusion.**

This paper has been written with the aim to give to the *Electronics World* reader some basic concepts about sensor interfacing.

The main aspects can be summarised as follows:

- 1) Get information about the sensor peculiarities (e.g., non-electrical characteristics, variation range, ...) and if it is resistive, capacitive, etc., and choose an interface topology to work at the best sensor operating frequency, so as to obtain high sensitivity and low resolution.
- 2) Use a good CMOS technology with low spread of technology parameters.
- 3) Use a low-voltage low-power interface design: the interface will become of a portable kind.
- 4) Minimize the effect of the interface in terms of noise, offset, and make the circuit insensitive to supply and temperature variations.

As it is clear from the considerations in the paper, it is very difficult to design a standard sensor interface, but the proposed amplifier can certainly constitute a general-purpose interface to be used in capacitive and resistive sensor applications. ■

**References**

[1] G. Ferri, W. Sansen: "A rail-to-rail constant-g<sub>m</sub> low-voltage CMOS operational transconductance amplifier" - *IEEE Transactions on Journal of Solid-State Circuits* - vol.SC-32 n.10, Oct. 1997, pp.1563-1567.  
 [2] C. Enz, G. Temes: "Circuit techniques for reducing the effects of op-amp imperfections" - *Proc. IEEE* vol.84 n.11, Nov.1996, pp.1584-1614  
 [3] P. Gray, Hurst, Lewis, Meyer: "Analysis and design of analogue integrated circuits", Wiley Ed, ISBN 0-471-32168-0  
 [4] G. Ferri: "Novel low voltage low power topologies as sensor interfaces" - *Sensor and*

*Transducers Conference MTEC '99*, Birmingham, Feb. 17-18 1999  
 [5] G. Ferri, P. De Laurentiis: "A novel low voltage low power oscillator as a capacitive sensor interface for portable applications" - *Sensors and Actuators A*, vol.76 pp.437-441, 1999.  
 [6] G. Ferri, A. D'Amico, C. Di Natale: "A CMOS Low Voltage Circuit Improves Wheatstone Bridge Sensitivity and Resolution", *Proc.IV Conference AISEM (Associazione Italiana Sensori e Microsistemi)*- 1999, pp.403-407.  
 [7] G. Ferri: "Low voltage low power Integrated phase shifter as resistance sensor transducer" -

*ANALOG INTEGRATED CIRCUITS AND SIGNAL PROCESSING* Vol. 27 n. 3, June 2001, pp. 219-228.  
 [8] G. Ferri, R. Mazzone, A. D'Amico, C. Di Natale: "Noise characteristics in low voltage CMOS integrated temperature sensor" - *Proceedings XIII EUROSENSORS 12-15 Sept. 1999 The Hague* pp. 557-560.  
 [9] G. Ferri, A.D'Amico, C. Di Natale: "Noise considerations in low voltage CMOS integrated temperature sensors" - *Sensors and Actuators A* vol.85, n.1-3, 25 August 2000, pp.232-238.

**Other references.**

In the following, in order to help the reader to be

better informed in sensor interface design, a long list of further references is given.

**1990:**

R. Puers, E. Peeters, A. Vandenbossche, W. Sansen : "A capacitive pressure sensor with low impedance output and active suppression of parasitic effects" - *Sensors and Actuators*, vol. A21-23, (1990) - pp.108-114.

R.W. Time: "A field focusing capacitance sensor for multiphase flow analysis" - *Sensors and Actuators*, vol. A21-23, (1990) - pp.115-122.

**1991:**

J. Gattestad, H. Jacobsen, P. Ohlckers : "A front-end CMOS circuit for a full bridge piezo-resistive pressure sensor" - *Sensors and Actuators A*, 25-27 (1991) 859-863.

**1992:**

H. Huijsing : "Integrated smart sensors" - *Sensors and Actuators*, vol. A 30 - 1992 - pp.167-174.

F.R. Riedijk, J.H. Huijsing : "An integrated absolute temperature sensor with sigma-delta A-D conversion" - *Sensors and Actuators*, vol. A 34 - 1992 - pp.249-256.

**1993:**

R. Puers : "Capacitive sensors : when and how to use them" - *Sensors and Actuators*, vol.A 37-38, (1993) - pp.93-105.

H. Baltes : "CMOS as sensor technology" - *Sensors and Actuators* vol. A 37-38, 1993, pp.51-56.

I. Filanovski, H. Baltes : "Analog Integrated Sensors", in: M. Ismail, H. Fiez: *Analog VLSI Signal and Information Processing*, pp.506-546, Mc.Graw-Hill, 1993.

**1994:**

P. Wouters, M. De Cooman, R. Puers : "A multipurpose CMOS sensor interface for low power applications" - *IEEE Journal of Solid State Circuits* vol.SC-29 n.8 - Aug.1994, pp.952-956.

H. Dudaicevs, M. Kandler, Y. Manoli, W. Mokwa, E. Spiegel : "Surface micro-machined pressure sensors with integrated CMOS read-out electronics" - *Sensors and Actuators A* 43 (1994) pp.157-163.

J.Lin, S.Moeller, E.Obermeier : "SC signal processing circuitry for capacitive chemical microsensors" - *Proc.IMCS* (International Meeting on Chemical Sensors) 1994, Roma, pp.1180-1183.

P.Wouters, M.De Cooman, R.Puers : "A multipurpose CMOS sensor interface for low power applications" - *IEEE Journal Solid State Circuits* vol.SC-29 n.8 - Aug.1994, pp.952-956.

**1995:**

M. Schmidt, E. Spiegel, H. Dudaicevs, Y. Manoli, W. Mokwa: "Readout electronics for wide temperature range with integrated surface micro-machined capacitive pressure sensor" - *Proceedings ESSCIRC (European Solid State Circuit Conference) 1995*

S. Tedja, J. Van der Spiegel, H.H. Williams: "A CMOS low noise low power charge sampling integrated circuit for capacitive detector/sensor interfaces" - *IEEE Journal of Solid State Circuits* vol.30 n.2, pp.110-119, Feb.1995.

F. Maloberti, H. Baltes, P. Malcovati : "Sensor interfaces", in *Sensors for Domestic Applications*, Ed. D'Amico, Sberveglieri, pp.201-216, World Scientific, 1995.

C. Canè et al. : "A technology for the monolithic fabrication of a pressure sensor and related circuitry" - *Sensors and Actuators*, vol.A 46-47, 1995, pp.133-136.

O. Paul, H. Baltes : "Novel fully CMOS-compatible vacuum sensor" - *Sensors and Actuators*, vol.A 46-47, 1995, pp.143-146.

J.Weber et al. : "A monolithically integrated sensors system using sensor-specific CMOS cell" - *Sensors and Actuators*, vol.A46-47, 1995, pp.137-142.

J. Gakkestad, P. Ohlckers, L. Halbo : "Effects of process variations in a CMOS circuit for temperature compensation of piezo-resistive pressure sensors" - *Sensors and Actuators A* - vol.48 (1995) - pp.63-71.

G. Van der Horn, J.H. Huijsing : "Smart temperature sensor with integrated bit stream calibration" - *Proceedings ESSCIRC '95*, pp.234-237.

A. Bakker, J.H Huijsing: "Micropower CMOS smart temperature sensor", *Proc. ESSCIRC Conference 1995*, 238-241.

M. Schmidt, E. Spiegel, H. Dudaicevs, Y. Manoli, W. Mowka: "Read-out electronics for wide temperature range with integrated surface micro-machined capacitive pressure sensor" - *Proc.ESSCIRC 1995*, pp.230-233.

**1996:**

M. Grigorie, C. de Raad Iseli, F. Krummenacher, C. Enz : "A circuit for the temperature compensation of capacitive sensors" - *Proceeding ISCAS (IEEE International Conference on Circuits and Systems)'96*.

H.C. Hsiek, C. Wu, F. Jih, T. Sun, H. Chang: "A new CMOS readout circuit design for the IR FPA with adaptive gain control and current-mode back-ground suppression" - *Proceeding ISCAS (IEEE International Conference on Circuits and Systems)'96*.

B.E. Boser, K.W. Markus: "Emerging technologies" - *Proceeding ISCAS (IEEE International Conference on Circuits and Systems)'96*.

H. Baltes, A. Haberli, P. Malcovati, F. Maloberti: "Smart sensor interfaces" - *Proceeding ISCAS (IEEE International Conference on Circuits and Systems)'96*.

E.D. Joseph, B.K. Kar, R. Rohrkemper, M. Ger: "Design and noise analysis of an automotive accelerometer" - *Proceeding ISCAS (IEEE International Conference on Circuits and Systems)'96*.

H. Yamasaki : "The future of sensor interface electronics" - *Sensors and Actuators A* - vol.56, 1996, pp.129-133.

H. Baltes: "Future of IC microtransducers" - *Sensors and Actuators A* - vol.56, 1996, pp.179-192.

G. Ferri, M. Faccio, G. Stochino, A. D'Amico, P. Vilmercati: "A low voltage band-gap reference circuit for sensor applications" - *Sensors and Microsystems - Proceedings I Congresso AISEM (Associazione Italiana Sensori e Microsistemi)* - 1996 - pp.374-378.

**1997:**

F. Beckmann, J. Marschner, T. Hofmann, R. Laur: "Analysis of complex impedances in CMOS technology for chemical sensor applications" -

*Sensors and Actuators A*,62 (1997) 734-738.

L.K. Baxter : *Capacitive sensors: design and application*. IEEE Press, NY 1997.

G. Ferri: "Low voltage low power CMOS front-ends for capacitive sensors" - *2<sup>nd</sup> IEEE CAS Region 8 Workshop on Analogue and Mixed Design* - Baveno (PV), 12-13 Sett.1997.

G. Ferri : "A Low-Voltage CMOS Operational Transconductance Amplifier for Capacitive Sensor Applications" - *Sensors and Microsystems - Proc. Second Italian Conference of Sensors and Microsystems*, Roma, Feb.1997.

F. Alesii, M. Faccio, G. Ferri, A. D'Amico, G. Stochino: "Low-Voltage Rail-to-Rail Bipolar Operational Amplifier for Resistive Sensor applications" - *Artificial and Natural Perception - Proc. Second AISEM (Associazione Italiana Sensori e Microsistemi) Conference - 1997* - pp.378-382.

7A. D'Amico, C. Di Natale, M. Mariucci, G. Baccarani, M. Faccio, G. Ferri, F. Maloberti, P. Malcovati, G. Stochino: "Active capacitance multiplication for sensor application" - *Sensors and Microsystems - Proc. Second Italian Conference of Sensors and Microsystems*, Roma, Feb.1997 - pp.371-377.

B. Boser : "Capacitive interfaces for monolithic integrated sensors" - *Proc.AACD (Advances on Analogue Circuit Design) Conference 1997*, Baveno, 1-3 April 1997.

B. De Geeter, O. Nys, G.P. Bardyn: "A high temperature micropower capacity pressure sensor interface circuit" - *Analog Integrated Circuit and Signal Processing*, Vol.14 pp.179-191, 1997.

X. Li, G.W. De Jong, G.C.M. Meijer, F.N. Toth, F.M.L. Vandergoes: "Low cost CMOS interface for capacitive sensors and its application in a capacitive angular encoder" - *Analog Integrated Circuit and Signal Processing*, Vol.14 pp.223-233, 1997.

M. Pedersen, M. Meijerink, W. Olthuis, P. Bergveld: "An IC-compatible polyamide pressure sensor with capacitive readout" - *Sensors and Actuators A*,63 (1997) 163-168.

F. Van der Goes, G.C.M. Meijer: "A universal transducer interface for capacitive and resistive sensor elements" - *Analog Integrated Circuit and Signal Processing*, Vol.14 pp.249-260, 1997.

P. Passeraub, P. Besse, C. De Raad, R. Popovic: "A differential relaxation oscillator as a versatile electronic interface for sensors" - *Sensors and Actuators A*58, 1997 (141-148).

Y. Sun, X. Sun, B. Sun, Q. Meng: "Electric drift of the bridge offset for pressure sensor and its utilization" - *Sensors and Actuators A* 58, 1997 (249-256).

T. Smith, J. Bardyn, B. DeGeeter, O. Nys: "Low power capacitive sensor interfaces" - *Proc. AACD (Advances on Analogue Circuit Design) Conference 1997*, Baveno, 1-3 April 1997.

R. Puers, P. Wouters: "Adaptable interface circuits for flexible monitoring of temperature and movement" - *Analog Integrated Circuit and Signal Processing*, Vol.14 pp193-206, 1997.

S.H. Khadouri, G.C.M. Meijer, F.M.L. Van der Goes: "A CMOS interface for thermocouples with reference-junction compensation" - *Analog*

- Integrated Circuit and Signal Processing*, Vol.14 pp.235-248, 1997.
- B.J. Hosticka, W. Brockherde, D. Hammerschmidt: "Silicon sensor systems", *Analog Integrated Circuit and Signal Processing*, Vol.14 pp.261-273, 1997.
- J. Bryzek, A. Rastegar: "Advances in state of art in smart sensor signal conditioning" - *Proc.AACD (Advances on Analogue Circuit Design) Conference 1997*, Baveno, 1-3 April 1997.
- B. Hosticka: "Integrated sensor systems in CMOS technology" - *Proc.AACD (Advances on Analogue Circuit Design) Conference 1997*, Baveno, 1-3 April 1997.
- A. Haberli, H. Baltes: "Compensation and calibration of IC microtransducers" - *Proc.AACD (Advances on Analogue Circuit Design) Conference 1997*, Baveno, 1-3 April 1997.
- J. Bausells, J. Carrabina, A. Merlos, S. Bota, J. Samitier: "Mechanical sensors integrated in a commercial CMOS technology - *Sensors and Actuators A*,62, 1997, pp. 698-704.
- G.C.M. Meijer, F.M.L. Van der Goes: "Low-cost smart sensor interfaces" - *Proc.AACD (Advances on Analogue Circuit Design) Conference 1997*, Baveno, 1-3 April 1997.
- 1998:**
- M. Tuthill: "A switched current switched capacitor temperature sensor in 0.6µm CMOS" - *IEEE Journal of Solid State Circuits* Vol. 33 n.7 July 1998 pp. 1117-1122
- B. Wang, T. Kajita, T. Sun, G. Temes: "High accuracy circuits for on chip capacitive ratio testing and sensor readout" - *IEEE Trans. on Instrum. and Measurement* Vol. 47 n. 1 Feb. 1998 pp. 16-20
- M. Grigorie, C. de Raad, F. Krummenacher, C. Enz: "Active temperature compensation for capacitive sensor interfaces" - *Proceedings ESSCIRC 98*
- G.Ferri, P.De Laurentiis, S. Pennisi: "A 1.4 V oscillator for CMOS capacitive sensor interfaces"- *Proc. Eurosenors '98*, Southampton, 13-17 Sept. 1998, pp.887-890.
- 1999:**
- C. Hierold et al. " Low power integrated pressure sensor system for medical applications " - *Sensors and Actuators 73 (1999)*, vol. A73, n. 1-2, pp. 58-67.
- T. D'Alessio: " Measurement errors in the scanning of piezo-resistive sensors arrays" - *Sensors and Actuators 72 (1999)*, vol. A72, n. 1 , pp. 71-76.
- J. C. Lotters, W. Olthuis, P. H. Veltink, P. Bergveld: "A sensitive differential capacitance to voltage converter for sensor applications" - *IEEE Trans. on Instrum. and Measurement* Vol. 48 n. 1 Feb. 1999 pp. 89-96
- H. J. Weller, D. Setiadi, T. D. Binnie: "Implementation of an integrated charge sensitive amplifier for pyroelectric infrared sensors" - *Proceedings XIII EUROSENSORS 12-15 Sept. 1999* The Hague pp. 545-548
- 2000:**
- Y. Qiu, C. Azeredo Leme, J. E. Franca: "CMOS Humidity Sensor with calibrated Voltage Output" - *Proceedings XIV EUROSENSORS 27-30 August 2000* pp.75-78
- M. Cole et al.: "Active bridge polymeric resistive device for vapour sensing" - *Proceedings XIV EUROSENSORS 27-30 August 2000* pp.895-898
- N. Yadzi, A. Mason, K. Najafi, K. D. Wise: "A generic chip interface for capacitive sensors in low power multiparameter Microsystems" - *Sensors and Actuators (84) 2000* pp. 351-361
- S. Vlassis, S. Siskos: "A signal conditioning circuit for piezo-resistive pressure sensors with variable pulse-rate output" - *ANALOG INTEGRATED CIRCUITS AND SIGNAL PROCESSING* Vol. 23 n. 2, May 2000, pp. 153-162
- 2001:**
- G. Amendola, G. N. Lu, L. Babadjian: "Signal processing electronics for a capacitive microsensor" *ANALOG INTEGRATED CIRCUITS AND SIGNAL PROCESSING* - Vol.29, n. 1-2, Oct Nov 2001, pp.105-120.
- C. Ribio, S. Bota, J. Macias, S. Sannitier: "Modelling, design and test of a monolithic integrated magnetic sensor in a digital CMOS technology using a switched current interface system" - *ANALOG INTEGRATED CIRCUITS AND SIGNAL PROCESSING* Vol. 27 n. 1-2, April May 2001, pp. 115-126
- Y. Ha, M. C. Li, A. Q. Liu: "A new CMOS buffer amplifier design used in LV MEMS interface circuits" - *ANALOG INTEGRATED CIRCUITS AND SIGNAL PROCESSING* Vol. 27 n. 1-2, April May 2001, pp. 7-18
- S. Chatzandrolis, D. Tsoukalas: "Capacitance to frequency converter suitable for sensor applications using telemetry" - *ANALOG INTEGRATED CIRCUITS AND SIGNAL PROCESSING* Vol. 27 n. 1-2, April May 2001, pp. 31-38
- C. C. Guo, P. Schmitt, G. Deptuch, Y. Hu: "A fully integrated low noise and low power BiCMOS front-end readout system for capacitive detector" - *ANALOG INTEGRATED CIRCUITS AND SIGNAL PROCESSING* Vol. 28 n. 3, Sept 2001, pp. 211-224.

**Use this coupon to order your copy of Pandora's drums**

Please send me ..... CD(s) at £11.99 each including VAT

Cheque   
 Credit card details  tick as appropriate

Name  
 Address

Phone number  
 Total amount £.....

Make cheques payable to TELEVISION  
 Or, please debit my credit card.

Card type (Master/Visa)  
 Card No  
 Expiry date


Please mail this coupon to TELEVISION, together with payment. Address orders and all correspondence relating to this order to Pandora's drums, Television, Highbury Business Communications, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ

# Pandora's drums

Unique and atmospheric music recorded in the early 1900s - the days before 78s.

Available exclusively from **Electronics World** **£11.99**

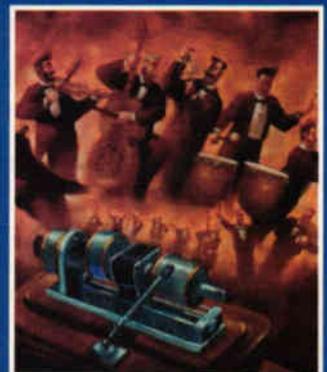All tracks on this CD were recorded on DAT from cylinders produced in the early 1900s. Considering the age of the cylinders, and the recording techniques available at the time, these tracks are of remarkable quality, having been carefully replayed using modern electronic technology by historian Joe Pengelly.



21 tracks - 72 minutes of recordings made between 1900 and 1929. These electronically derived reproductions are no worse than - and in many cases better than - reproductions of early 78rev/min recordings - some are stunning...

## £1 BARGAIN PACKS

**PIEZO ELECTRIC SOUNDER**, also operates efficiently as a microphone. Approximately 30mm diameter, easily mountable, 2 for £1. Order Ref: 1084.

**LIQUID CRYSTAL DISPLAY** on p.c.b. with i.c.s. etc. to drive it to give 2 rows of 8 figures or letters with data. Order Ref: 1085.

**30A PANEL MOUNTING TOGGLE SWITCH**. Double-pole. Order Ref: 166.

**SUB MIN TOGGLE SWITCHES**. Pack of 3. Order Ref: 214.

**HIGH POWER 3in. SPEAKER**. 11W 8ohm. Order Ref: 246.

**MEDIUM WAVE PERMEABILITY TUNER**. It's almost a complete radio with circuit. Order Ref: 247.

**HEATING ELEMENT**, mains voltage 100W, brass encased. Order Ref: 8.

**MAINS MOTOR** with gearbox giving 1 rev per 24 hours. Order Ref: 89.

**ROUND POINTER KNOBS** for flatted 1/4in. spindles. Pack of 10. Order Ref: 295.

**REVERSING SWITCH**. 20A double-pole or 40A single pole. Order Ref: 343.

**LUMINOUS PUSH-ON PUSH-OFF SWITCHES**. Pack of 3. Order Ref: 373.

**SLIDE SWITCHES**. Single pole changeover. Pack of 10. Order Ref: 1053.

**PAXOLIN PANEL**. Approximately 12in. x 12in. Order Ref: 1033.

**CLOCKWORK MOTOR**. Suitable for up to 6 hours. Order Ref: 1038.

**HIGH CURRENT RELAY**, 12V d.c. or 24V a.c., operates changeover contacts. Order Ref: 1026.

**3-CONTACT MICROSWITCHES**, operated with slightest touch, pack of 2. Order Ref: 861.

**HIVAC NUMICATOR TUBE**, Hivac ref XN3. Order Ref: 865 or XN11 Order Ref: 866.

**2IN. ROUND LOUDSPEAKERS**. 50Ω coil. Pack of 2. Order Ref: 908.

**5K POT**, standard size with DP switch, good length 1/2in. spindle, pack of 2. Order Ref: 11R24.

**13A PLUG**, fully legal with insulated legs, pack of 3. Order Ref: GR19.

**OPTO-SWITCH** on p.c.b., size 2in. x 1in., pack of 2. Order Ref: GR21.

**COMPONENT MOUNTING PANEL**, heavy Paxolin 10in. x 2in., 32 pairs of brass pillars for soldering binding components. Order Ref: 7RC26.

**HIGH AMP THYRISTOR**, normal 2 contacts from top, heavy threaded fixing underneath, think amperage to be at least 25A, pack of 2. Order Ref: 7F243.

**BRIDGE RECTIFIER**, ideal for 12V to 24V charger at 5A, pack of 2. Order Ref: 1070.

**TEST PRODS FOR MULTIMETER** with 4mm sockets. Good length flexible lead. Order Ref: D86.

**LUMINOUS ROCKER SWITCH**, approximately 30mm square, pack of 2. Order Ref: D64.

**MES LAMP HOLDERS** slide on to 1/4in. tag, pack of 10. Order Ref: 1054.

**HALL EFFECT DEVICES**, mounted on small heatsink, pack of 2. Order Ref: 1022.

**LARGE MICROSWITCHES**, 20mm x 60mm x 10mm, changeover contacts, pack of 2. Order Ref: 826.

**COPPER CLAD PANELS**, size 7in. x 4in., pack of 2. Order Ref: 973.

**100M COIL OF CONNECTING WIRE**. Order Ref: 685.

**WHITE PROJECT BOX**, 78mm x 115mm x 35mm. Order Ref: 106.

**LEVER-OPERATED MICROSWITCHES**, ex-equipment, batch tested, any faulty would be replaced, pack of 10. Order Ref: 755.

**MAINS TRANSFORMER**, 12V-0V-12V, 6W. Order Ref: 811.

**QUARTZ LINEAR HEATING TUBES**, 360W but 110V so would have to be joined in series, pack of 2. Order Ref: 907.

**REELS INSULATION TAPE**, pack of 5, several colours. Order Ref: 911.

**LIGHTWEIGHT STEREO HEADPHONES**. Order Ref: 989.

**THERMOSTAT** for ovens with 1/4in. spindle to take control knob. Order Ref: 857.

**MINI STEREO 1W AMP**. Order Ref: 870.

**BT TELEPHONE EXTENSION WIRE**. This is a proper heavy duty cable for running around the skirting board when you want to make a permanent extension. Four cores properly colour coded, 25m length only £1. Order Ref: 1067.

**VERY THIN DRILLS**. 12 assorted sizes vary between 0.6mm and 1.6mm. Price £1. Order Ref: 128.

**EVEN THINNER DRILLS**. 12 that vary between 0.1mm and 0.5mm. Price £1. Order Ref: 129.

**MES BATTEN HOLDER**. Pack of 6. Order Ref: 26.

**SCREW DOWN TERMINAL**. Can also take 4mm plug. Mounts through metal panel with its own insulators and 2 quite hefty nuts for securing the cable. Pack of 3. Order Ref: GR42. Only red ones available.

**1000 WATT FIRE SPIRALS**. Useful if you are repairing old types of porcelain body heaters. pack of 4. Order Ref: 223.

## SELLING WELL BUT STILL AVAILABLE

**IT IS A DIGITAL MULTITESTER**, complete with backrest to stand it and hands-free test prod holder. This tester measures d.c. volts up to 1,000 and a.c. volts up to 750; d.c. current up to 10A and resistance up to 2 megs. Also tests transistors and diodes and has an internal buzzer for continuity tests. Comes complete with test prods, battery and instructions. Price £6.99. Order Ref: 7P29.

**INSULATION TESTER WITH MULTIMETER**. Internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges: AC/DC volts, 3 ranges DC milliamperes, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P4.



**REPAIRABLE METERS**. We have some of the above testers but slightly faulty, not working on all ranges, should be repairable, we supply diagram, £3. Order Ref: 3P176.

**BT TELEPHONE EXTENSION WIRE**. This is proper heavy duty cable for running around the skirting board when you want to make a permanent extension. Four cores properly colour coded, 25m length only £1. Order Ref: 1067.

**HEAVY DUTY POT**. Rated at 25W, this is 20 ohm resistance so it could be just right for speed controlling a d.c. motor or device or to control the output of a high current. Price £1. Order Ref: 1/33L1.

**1mA PANEL METER**. Approximately 80mm x 55mm, front engraved 0-100. Price £1.50 each. Order Ref: 1/16R2.

**D.C. MOTOR WITH GEARBOX**. Size 60mm long, 30mm diameter. Very powerful, operates off any voltage between 6V and 24V D.C. Speed at 6V is 200 rpm, speed controller available. Special price £3 each. Order Ref: 3P108.

**FLASHING BEACON**. Ideal for putting on a van, a tractor or any vehicle that should always be seen. Uses a Xenon tube and has an amber coloured dome. Separate fixing base is included so unit can be put away if desirable. Price £5. Order Ref: 5P267.

**MOST USEFUL POWER SUPPLY**. Rated at 9V 1A, this plugs into a 13A socket, is really nicely boxed. £2. Order Ref: 2P733.

**MOTOR SPEED CONTROLLER**. These are suitable for D.C. motors for voltages up to 12V and any power up to 1/6h.p. They reduce the speed by intermittent full voltage pulses so there should be no loss of power. Made up and tested, £18. Order Ref: 20P39.

**BALANCE ASSEMBLY KITS**. Japanese made, when assembled ideal for chemical experiments, complete with tweezers and 6 weights 0.5 to 5 grams. Price £2. Order Ref: 2P44.

**CYCLE LAMP BARGAIN**. You can have 100 6V 0.2A MES bulbs for just £2.50 or 1,000 for £20. They are beautifully made, slightly larger than the standard 6.3V pilot bulb so they would be ideal for making displays for night lights and similar applications.

**SOLDERING IRON**, super mains powered with long-life ceramic element, heavy duty 40W for the extra special job, complete with plated wire stand and 245mm lead. £3. Order Ref: 3P221.

YOU WILL RECEIVE THIS MONTH'S 14-PAGE LIST OF BARGAINS WITH YOUR GOODS IF YOU ORDER. IF NOT, PHONE OR WRITE FOR THIS LIST.

### RELAYS

We have thousands of relays of various sorts in stock, so if you need anything special give us a ring. A few new ones that have just arrived are special in that they are plug-in and come complete with a special base which enables you to check voltages of connections of it without having to go underneath. We have 6 different types with varying coil voltages and contact arrangements.

Coil Voltage	Contacts	Price	Order Ref.
12V DC	4-pole changeover	£2.00	FR10
24V DC	2-pole changeover	£1.50	FR12
24V DC	4-pole changeover	£2.00	FR13

Prices include base

**MINI POWER RELAYS**. For p.c.b. mounting, size 28mm x 25mm x 12mm, all have 16A changeover contacts for up to 250V. Four versions available, they all look the same but have different coils:

6V - Order Ref: FR17	24V - Order Ref: FR19
12V - Order Ref: FR18	48V - Order Ref: FR20


Price £1 each less 10% if ordered in quantities of 10, same or mixed values.

**RECHARGEABLE NICAD BATTERIES**, AA size, 25p each, which is a real bargain considering many firms charge as much as £2 each. These are in packs of 10, coupled together with an output lead so are a 12V unit but easily dividable into 2 x 6V or 10 x 1.2V £2.50 per pack, 10 packs for £25 including carriage. Order Ref: 2.5P34.

**4 CIRCUIT 12V RELAY**. Quite small, clear plastic enclosed and with plug-in tags. £1. Order Ref: 205N.

**NOT MUCH BIGGER THAN AN OXO CUBE**. Another relay just arrived is extra small with a 12V coil and 6A changeover contacts. It is sealed so it can be mounted in any position or on a p.c.b. Price 75p each, 10 for £6 or 100 for £50. Order Ref: FR16.

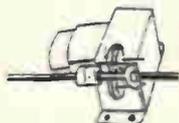**1.5V-6V MOTOR WITH GEARBOX**. Motor is mounted on the gearbox which has interchangeable gears giving a range of speeds and motor torques. Comes with full instructions for changing gears and calculating speeds, £7. Order Ref: 7P26.



## £1 BARGAIN PACKS

**FIGURE 8 FLEX**, figure 8, flat white PVC, flexible with 0.4 sq mm cores. Ideal for speaker extensions and bell circuits. Also adequately insulated for mains lighting, 12m coil. Order Ref: 1014.

**SOLENOID COIL**, 6V DC or 12V AC, only needs a plunger which could be a nail, you would then have a really efficient solenoid. Pack of 10. Order Ref: 1/L2.

**ONE OHM 20W RESISTOR**. Made for the Admiralty in 1952 but being wirewound is probably just as good as when new. Pack of 2. Order Ref: 7/19R4.

**COLVERN 5K POT**. Totally enclosed with good length spindle. Pack of 2. Order Ref: 7/19R5.

**DITTO** but 20k. Pack of 2. Order Ref: 7/19R6.

**PHILIPS TRIMMER CAP**. Sometimes called the beehive trimmer as this is in two sections, the top being on a threaded rod. Capacity is altered by twisting along the rod. Pack of 2. Order Ref: 7/19R19.

**THREE BOOKS: The Mullard Uniles Handbook, Practical Electronic Projects and Short Wave Receivers for Beginners**. Order Ref: 400.

**SMITHS COOKER CLOCK**. Their Ref OCU9900/1 in its own metal case but without a face plate, still in maker's packing. Order Ref: 2/17L7.

**SUPERIOR FERRITE ROD AERIAL**. This is an extra special 1/2in. diameter rod so the long and medium wave coils are extra robust. Order Ref: D203.

**DOLLS HOUSE SWITCH**. A very neat white body with red control tag. Pack of 2. Order Ref: 57.

**MAINS RELAY**. Plugs into octal base, double-pole changeover contacts which look OK for up to 10A. Order Ref: 7TOP14.

**THERMAL DELAY SWITCH**. Length of delay depends upon the voltage applied to its heater coil which causes the 10A contacts to open. This again plugs into octal base. Order Ref: 7TOP15.

**TINY MAINS MOTOR**. This is only 2in. square, the shaded pole type with good length of 1/8in. spindle. Order Ref: 7/1R7.

**COMPUTER DUST COVER**. Made for Altai, these dust covers are a special opaque plastic measuring 22in. long, 14in. wide and 6in. deep, nicely boxed. Order Ref: D204.

**PROJECT BOX**. Conventional plastic construction, colour is beige and size approximately 250mm x 130mm x 50mm deep. Divides into 2 halves, held together by screws. Ventilators in the top and bottom corners, but these are quite a decoration and give the box a pleasing look. Order Ref: D201.

**LIMITED SPACE LIGHT SWITCH**. It is only about 2in. x 1in. brown Bakelite but rated at 15A 250V. It is easy to fix in a small space. Its operating toggle is labelled off for up and on for down. Pack of 3. Order Ref: 1/11R27.

**IN-LINE FUSE HOLDERS**. Just cut the wire and insert, fully insulated. Pack of 4. Order Ref: 969.

**MINI MONO AMP**. 3W into 4 ohm speaker or 1W into 8 ohm. Order Ref: 495.

**15V DC 150mA PSU**. Nicely cased. Order Ref: 942.

**6V 1A MAINS TRANSFORMER**. Upright mounting with fixing clamps. Pack of 2. Order Ref: 9.

**SUCK OR BLOW OPERATED PRESSURE SWITCH**, or it can be operated by any low pressure variation such as water level in tanks. Order Ref: 67.

**12V SOLENOID**. Has good 1/2in. pull or could push if modified. Order Ref: 232.

**NEON INDICATORS**. In panel mounting holders with lens. Pack of 6. Order Ref: 180.

**12V ALARMS**. Make a noise about as loud as a car horn. Use one lead and case for DC, all brand new. Pack of 2. Order Ref: 221B.

**PANOSTAT**. Controls output of boiling ring from simmer up to boil. Order Ref: 252.

**OBLONG PUSH SWITCHES**. For bell or chimes, these can switch mains up to 5A so could be foot switch if fitted in pattress. Pack of 2. Order Ref: 263.

**MIXED SILICON DIODES**. Pack of 25. Order Ref: 293.

**SHADED POLE MAINS MOTOR**. 1/4in. stack so quite powerful. Order Ref: 85.

### TERMS

Send cash, uncrossed PO, cheque or quote credit card number, if ordered is £25 or over deduct 10% but add postage, £3.50 if under 2 kilo, £6 if under 4 kilo.

**J & N FACTORS**  
 Pilgrim Works (Dept.E.E.)  
 Stairbridge Lane, Bolney  
 Sussex RH17 5PA  
 Telephone: 01444 881965  
 E-mail: jnfactors@aol.com

# Wide digital I/O from the USB port

**Intrigued by Colin Attenborough's recent article on digital i/o using the USB port, but don't like PLDs? Read on, as with this article Colin shows how the PLD can be swapped for four standard CMOS ICs, with increased word width as a bonus.**

**S**ome months ago, I showed how a module using the FT8U245AM chip could be used in a simple 16-bit i/o interface connected to the USB port of a PC. While the design used few chips (input/output buffers and a PLD), and, with parallel data handling in the PLD, was fast, it was not easily adaptable to word widths greater than 16 bits. Wider words would demand more PLD pins, with an increase in cost for the PLD.

These shortcomings led me to consider sacrificing speed for the ability to cope with wider words. In a design using a PLD, it is prudent to add buffers to protect the PLD from the outside world. If we use shift registers rather than simple buffers, then serial data to and from the registers reduce pin count on the PLD. Going further, I realised that the control logic between the USB module and the registers could be accommodated in four standard CMOS ICs – the PLD could be discarded. The approach works for any reasonable word widths – just add a register at input and output for each 8-bit increase of word width.

## USB module pin functions

As well as the 8 data bi-directional data lines, the USB module has four data control lines. At a high-to-low transition on the NOT\_WR input, data are read from the data lines into the transmit FIFO in the module's FT8U245AM chip. The NOT\_TXE output goes high while the FIFO is entering the data; while NOT\_TXE is high, there must be no more high-to-low transitions on NOT\_WR. For data output from the module, each byte written into the module causes a high-to-low transition on the NOT\_RXF output. External circuitry must respond by dropping the NOT\_READ input for at least 50ns and then raising it again; NOT\_RXF will rise in response. While NOT\_READ is low, the bi-directional data lines assume a low impedance output state; at all other times, they are high impedance inputs.

Figures 1 and 2 show the circuit of the interface in a 16-bit form. The output registers, 74HC595 (Figure 2), are dual-rank; data are shifted serially along an input register by clock pulses on SCK, and then transferred to the output

by a pulse on RCK. The input registers, 74HC589 (Figure 2), are also dual-rank; a positive going edge on RCK transfers input data to a parallel register, a negative-going pulse on \*SLOAD transfers it to a serial output register, from where it is shifted out serially by clock pulses on SCK.

Six of the eight data lines of the USB module are used to control data transfer to the interface. (The allocation of function to line is arbitrary.)

D0: Transfer data from parallel to serial section (\*SLOAD input of 74HC589s)

D1: Strobe data into output registers (RCK input of 74HC595s)  
Load from-world data into parallel registers (RCK input of 74HC589s)  
Reset counter for input shift pulses

D2: Serial data to output (SER input of 74HC595)

D3: Clock for output data (SCK input of 74HC595)

D4: Serial data from world (SER\_OUT output of 74HC589)

D7: Start input of data

When sending data from the PC to the interface, the NOT\_RXF output of the USB module gives a high-to-low transition for each byte sent. A delay circuit, consisting of inverter U1f, C1, R1 and Schmitt NAND gate U2a gives an immediate high-to-low transition on the NOT\_RXF input, which lasts for a period defined by C2, R2, (and the threshold voltages of U2a). Inverter U1e disables the output of the input shift register while the outputs of the USB module are active – this avoids contention due to two outputs at the same point possibly trying to pull in opposite directions.

Reading data from the interface to the PC involves


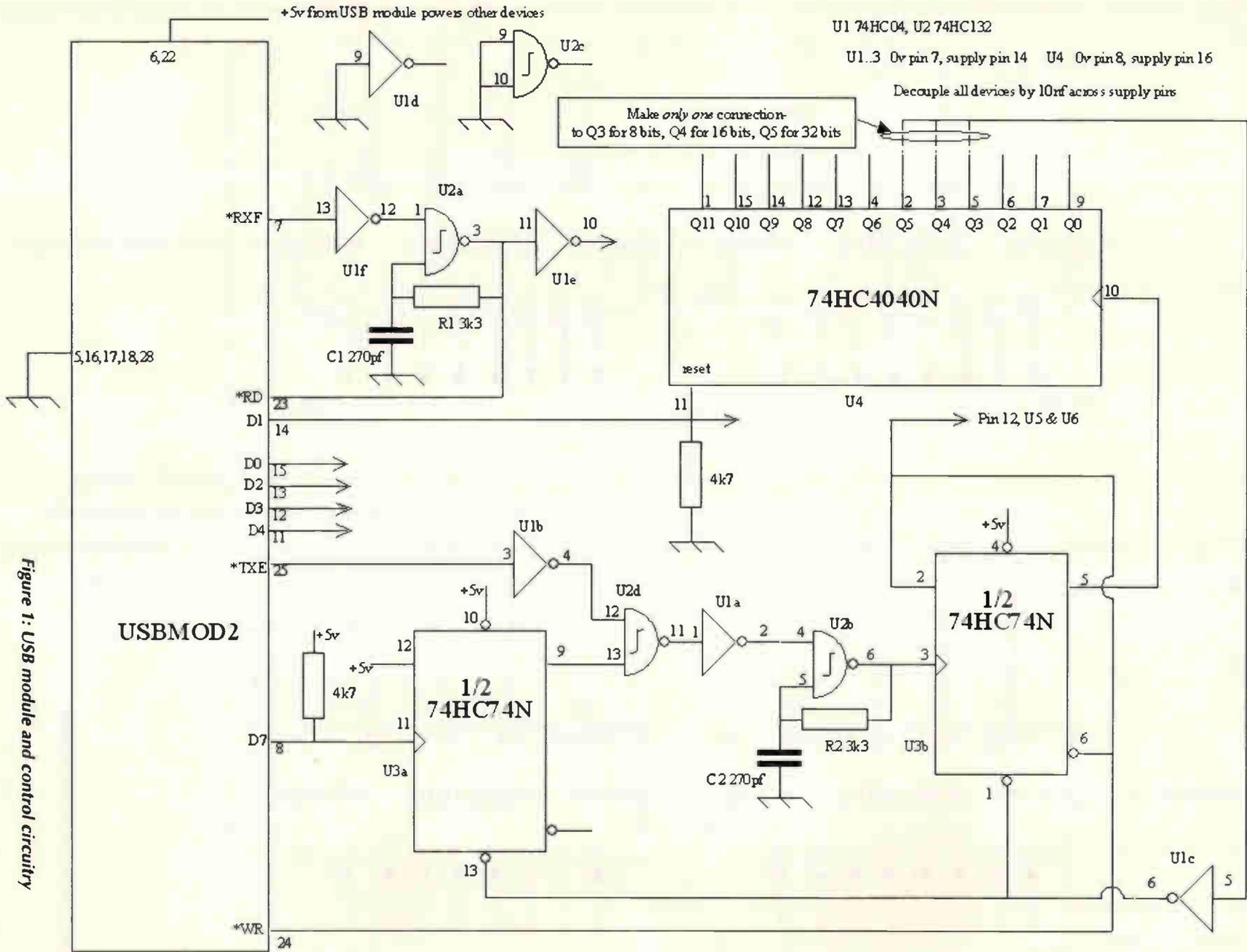


Figure 1: USB module and control circuitry

Figure 2: Input and output registers

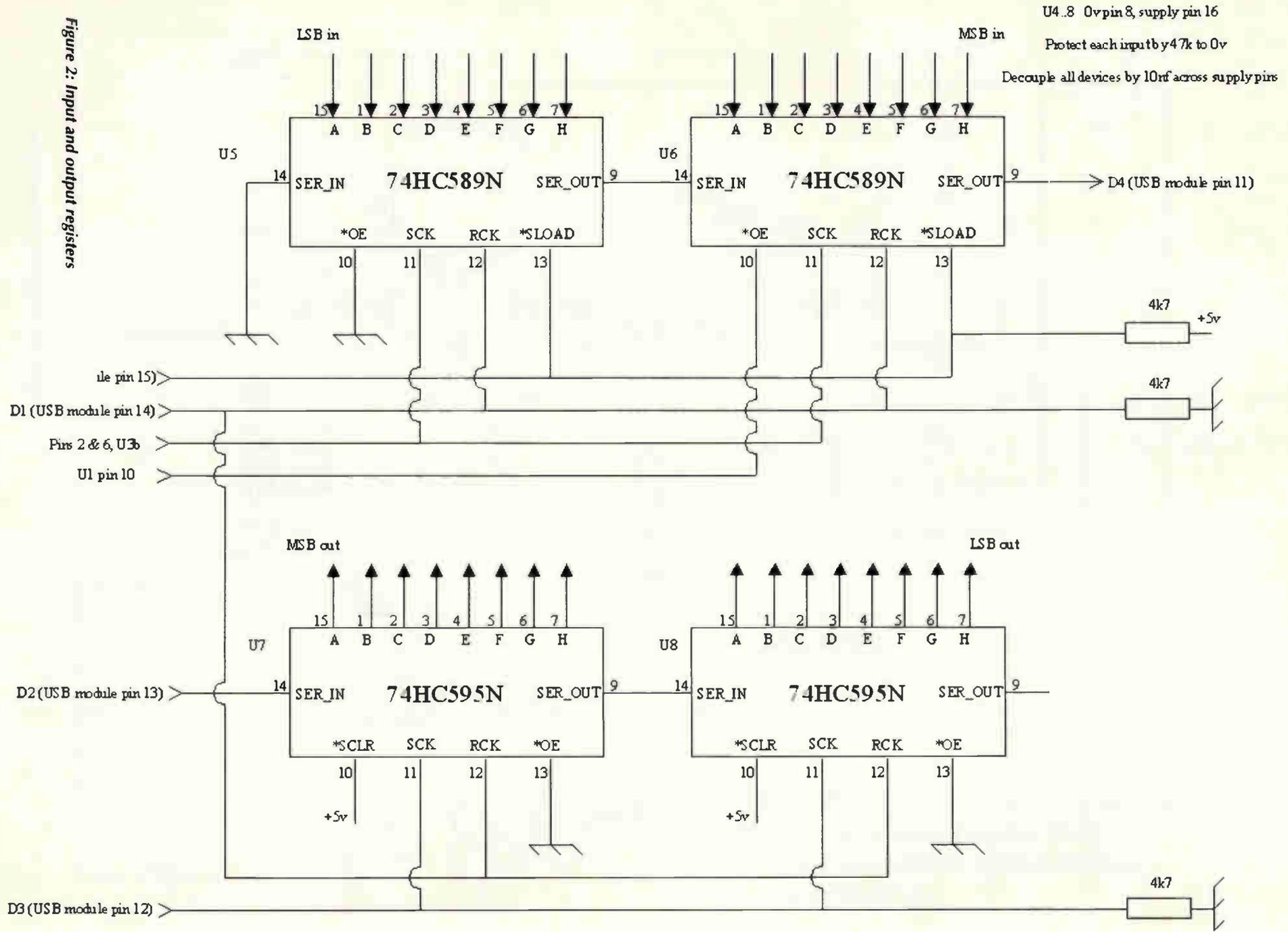

pulsing the \*SLOAD and RCK inputs of the 74HC589 devices to get input data into their shift registers. For an interface with an n-bit wide word, n clock pulses must then be applied to the USB module's NOT\_WR input. This process is initiated by a low-to-high transition on the clock input of the D flipflop U3a, putting a logic '1' on the Q output and enabling the oscillator consisting of C2, R2, and Schmitt NAND gate U2b. U1a, U1b and U2d inhibit the oscillator when NOT\_TXE is at logic '1'. The D flipflop, U3b, divides the oscillator frequency by two, providing antiphase drive to the USB module's NOT\_WR input, and to the counter U4. When the selected output of the counter goes high, both sections of U3 are reset via U1c, inhibiting the oscillator.

Some of the USB module data lines need pull-up or pull-down resistors. D0 (\*SLOAD) and D7 (start input of data) need pull-ups, as the signals they drive are active low; D1, D3 and D4 need pull-downs. D2 must not be pulled in either direction – each data bit for output is put on D2 for two successive writes, and the shift clock is raised for the second of these writes. The system relies on the data line maintaining its state between the two writes – which it does easily, but only if the data line isn't pulled either up or down.

### A question of timing

The circuit contains two timings set by analogue components – the delay circuit around U2b for writing to the interface, and the oscillator around U2b for clocking data into the USB module. The period of the delay and the frequency of the oscillator are not closely defined due to wide variations in the threshold levels of the Schmitt trigger gates U2a and U2b. However, the values shown gave periods on the prototype about ten times longer than the minimum values required by the USB module and so should be 'safe'.

Different word widths affect both software and hardware. In the Visual Basic source code, look for the definition of N\_BYTES – set it to 1, 2 or 4 for 8, 16 or 32-bit word widths. (If you want, say, 64 bits, then you'll have to provide more check boxes to define the output data and display the input data a different way.) Setting N\_BYTES sets up other program parameters, which ensure the correct width of the displayed form, the correct number of check boxes for input data, and the correct length of the strings that communicate data to and from the USB module. (That's why there are three compiled versions for 8, 16 and 32 bits.)

The effects on the hardware of different word widths are twofold. The figures show a 16-bit system; for wider words, insert additional 74HC595s between pin 14 of U7 and pin 13 of the USB module, and additional 74HC589s between pin 9 of U6 and pin 11 of the USB module. The number of clock pulses fed to the NOT\_WRITE input of the USB module must also be correctly set by using the appropriate output of the counter U4. Remember that U4's Qn output goes high after 2n pulses have been applied. (Actually, the system will work if, say, a word width of 16 is used but 32 NOT\_WRITE pulses are applied; the extra pulses are ignored once the expected word length has been shifted in, but this slows the system avoidably.) If you try to read a 16-bit input word when Q4 has been set up to give eight pulses, you'll get a 'timeout' error in a message box.

### The USB module

My previous article used the DLP\_USB01 module from DLP Design; this one uses the USBMOD2 from GigaTechnology.com Pty. Both can be obtained from Alpha Micro Components ([www.alphamicro.net](http://www.alphamicro.net)). My use of the GigaTechnology device here does not imply any criticism of the DLP module. The DLP device contains an EEPROM that stores the USB serial number, product description and other strings. The GigaTechnology device does not include such an EEPROM, but its omission does not affect the operation of the unit described here.

The DLP module is on two rows of 0.1" separated pins, the rows being 1" apart. It can be soldered into a perforated board. The GigaTechnology device is suitable for plugging into a 32-pin 0.6" pitch IC socket. (No, me neither; I used a 40-pin socket and did gentle violence with a very small saw.)

Of course, if you want to use a PLD (or a PIC) then the functions of U1, U2, U3 and U4 can be implemented in a single package. "This is left as an exercise for the student".

### Software

The Visual Basic code provides a GUI to allow setting of the outputs and reading of the inputs. Changing a tick box to alter an output line generates a character string reflecting the tick box states; this string is sent to the USB module, providing clock, data and strobe pulses to the output registers. Pressing the "Read" button also sends a string of characters to the USB module, which latch data into the input registers and clock U3a, allowing the U2b oscillator to run and clocking in data from the input registers.

A dynamic link library provides the functions that interface Visual Basic to the USB driver; the DLL is in the same directory as the other source files.

### What's on the disc

The disc contains three directories:

- Vb Source- the source code for readers with Visual Basic, who can examine and modify the program.
- Compiled- containing three subdirectories, Install8, Install16 and Install32, for readers without Visual Basic.
- Driver- containing a zipped version of the driver that must be installed before the USB module can be driven.


The D10202 file in the Driver directory should be unzipped and stored in a directory somewhere. (You'll find it also contains the dynamic link library- this is already embedded in the compiled versions of the code. It's also included among the source code files.) When you plug in the USB module for the first time, the system will search for a driver; browse your way to where the driver has been unzipped and it will be installed.

The driver file was downloaded from the FTDI website [www.ftdichip.com](http://www.ftdichip.com); it works entirely satisfactorily, but readers may wish to check for an updated version. ■

### Acknowledgements

The author is grateful to his employers, Cambridge Consultants Limited, for permission to publish this article.

# BOOKS TO BUY

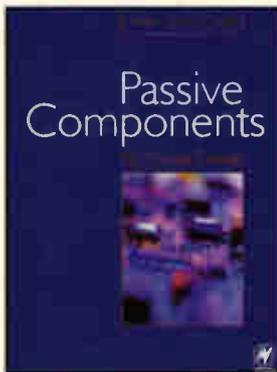


## PASSIVE COMPONENTS FOR CIRCUIT DESIGN

Passive Components for Circuit Design is a unique introduction to this key area of analog electronics designed for technician engineers and anyone involved in circuit design. The coverage encompasses all component types capable of power amplification: resistors, capacitors, transformers, solenoids, motors and transducers. The behaviour of the components is explored along with the different types available and the principles of circuit design. Tolerances, stability, variation with temperature, reliability and manufacturing standards are all covered. Reading this book will improve your skills in component selection and analog circuit design. These are essential skills not only for the analog designer, but for all circuit designers, professional or amateur.

**Contents:** Preface; Fundamentals; Fixed resistors; Variable resistors, potentiometers and diodes; Capacitors; Inductors and inductive components; Inductive devices; Transducing components; SMT; Hardware; Index

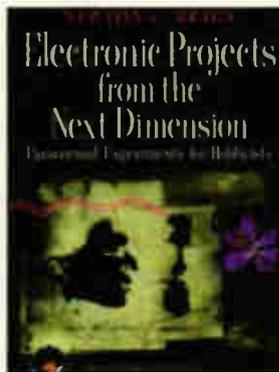**Readership:** Technician engineers, circuit designers, advanced hobbyists  
**Pages:** 304pp  
**Price:** UK £23.00  
 Europe £24.00  
 ROW £27.00




## ELECTRONIC PROJECTS FROM THE NEXT DIMENSION

For years paranormal scientists have explored the detection and documentation of spirits, auras, ESP, hypnosis, and many more phenomena through electronics. Electronic Projects from the Next Dimension provides useful information on building practical circuits and projects, and applying the knowledge to unique experiments in the paranormal field. The author writes about dozens of inexpensive projects to help electronics hobbyists search for and document their own answers about instrumental transcommunication (ITC), the electronic voice phenomenon (EVP), and paranormal experiments involving ESP, auras, and Kirlian photography.

Although paranormal studies are considered esoteric, Electronic Projects from the Next Dimension teaches the technical skills needed to make devices that can be used in many different kinds of experiments. Each section indicates how the circuit can be used in paranormal experiments with suggestions about procedures and how to analyze the results.

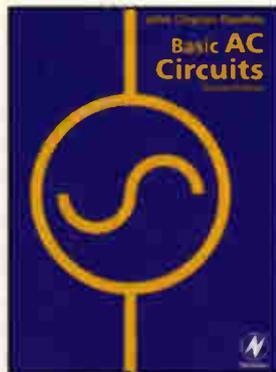**Contents:** White noise generators for use in instrumental transcommunication (ITC) and electronic voice phenomenon (EVP) experiments; Practical circuits for image experimentation, such as a




## BASIC AC CIRCUITS

This is the step-by-step approach for beginners. This self-paced individualized learning tool covers concepts, terms, and the mathematics required to understand AC circuit problems. It has been designed to improve analysis techniques for prediction and control development.

**Readership:** Beginners meeting AC circuits for the first time: students; technicians  
**Pages:** 921pp  
**Price:** UK £34.00  
 Europe £36.00  
 ROW £38.00

wireless sparkling image generator, horizontal bar generator, brontophic sound, magnetic field generator, high-voltage generators (Kirlian Machine's I & II); Paranormal skills experiments with temperature change, polygraph, electro-shock, random number generation, UFO detection, and ghost-finding.

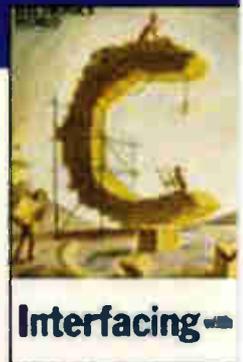**Readership:** Hobbyists, Electronics Enthusiasts  
**Pages:** 256pp  
**Price:** UK £28.00  
 Europe £30.00  
 ROW £37.00



## Interfacing

### INTERFACING WITH C

A practical and painless way of becoming an expert C programme New edition also covers C++ and the Windows environment Get up to speed with the essential maths needed for C without having to buy a university maths text!

**Price:** UK £20.00  
 Europe £22.00  
 ROW £24.00

Post your completed order form to:-

**Jackie Lowe,  
 Highbury Business Communications,  
 Anne Boleyn House, 9-13 Ewell Road,  
 Cheam, Surrey, SM3 8BZ**

### How to order

Book Title \_\_\_\_\_

I enclose a cheque/bank draft for £ \_\_\_\_\_  
 (payable to *ELECTRONICS WORLD*)

Please charge my credit/charge card

Mastercard  American Express  Visa  Diners Club

Credit Card No: \_\_\_\_\_ Expiry Date: \_\_\_\_\_

Signature of Cardholder \_\_\_\_\_

Cardholder's statement address: (please use capitals)

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Post Code \_\_\_\_\_ Tel: \_\_\_\_\_

# NEW PRODUCTS

Please quote *Electronics World* when seeking further information

## Mosfet with 2.3m $\Omega$ on-resistance

Philips Electronics is offering a family of Mosfets for automotive applications. The TrenchMOS family is designed to reduce on-resistance and offer better switching for high-current applications such as electronic power assisted steering (EPAS), integrated starter alternator (ISA) and other major motor drive applications. Called the High Performance Automotive (HPA) family, devices are available in all of the common automotive breakdown voltage grades of 30, 40, 55, 75 and 100V and are qualified to the automotive electronics standard AEC Q101 for automotive discrete semiconductors.

Philips Electronics  
Tel: +44(0) 3140272 2091  
[www.semiconductors.philips.com](http://www.semiconductors.philips.com)

## Flash micro for motor control

Motorola has introduced the 68HC908MR8 flash microcontroller, optimised for motor control systems. It offers extended data retention of the

embedded flash memory to typically 100,000 write/erase cycles and 50 year data retention (running at 55°C). As a result, most embedded systems that require non-volatile storage of temporary or changing data no longer need separate electrically erasable programmable read only memory (EEPROM) chips. Features include PWM modules optimised for motor control, analogue-to-digital converters (ADC), on-board voltage regulation and asynchronous serial communications interface (SCI). The micro is available in 28-pin PDIP, 32-pin QFP and 28-pin SOIC packages.

Motorola  
Tel: +44(0) 1355 565000  
[www.motorola.com](http://www.motorola.com)

## Handy tool for crimping

Tyco Electronics is offering the Pro-Crimper 11 and PEW 12 hand tool frames. Both tools are designed for low production volumes or repair functions. Providing ratchet action with emergency release, the hand tools accept a variety of pinned or shouldered dies, enable



crimping of multiple terminals with one die set, and incorporate a lightweight, ergonomic design. Also included in the range is the Pneumatic 626 system, which is suitable for both bench and hand held applications, and includes a flexible head that can be rotated to any angle. Designed to crimp terminals of 6 to 26 AWG, the system is available in two force levels (for UL and CSA approved applications), operates with a 110V or 240V power supply, and provides hand or foot actuation.

Tyco Electronics  
Tel: +44(0) 1237 428601  
[www.tooling.tycoelectronics.com](http://www.tooling.tycoelectronics.com)

## Nonvolatile memory features unlimited endurance

The FM18L08 is the world's first commercial nonvolatile memory to feature unlimited endurance. Accelerated characterization of the FM18L08's underlying FRAM

technology guarantees virtually unlimited read/write endurance. FM18L08 eliminates the reliability concerns, functional disadvantages and system design complexities of battery-backed SRAM. With its unlimited access cycles, it provides any combination of volatile and nonvolatile storage, replacing both SRAM and EEPROM in the end system with no disadvantages. All FRAM 3-volt products include the unlimited endurance feature, and they are FM24CL64, FM24CL16, and the FM25CL64.

Ramtron  
Tel: +44(0) 1444 473555  
[www.ramtron.com/products](http://www.ramtron.com/products)

## Digital audio compression aims to 98 per cent

A digital data compression algorithm from APT (Audio Processing Technology) is based on ADPCM principles, but uses 4 equally divided sub-bands, predictive analysis and backward adaption. Called Enhanced apt-X, the developer claims it can return 98.5 per cent of the original content after the first encode/decode process. Subsequent passes are truer to the first process as the predictive element becomes more exact. With an end-to-end theoretical processing delay 1.9ms at 48kHz sampling frequency, additional features include immunity to bit errors, embedded synchronisation word pattern in

the event of drop out and ancillary data for information relating to the program content. Embedded design support includes DSP from Motorola, Texas Instruments, Analog Devices, VHDL/Verilog and Windows/Linux operating systems. The company has dedicated a developers section on its website which provides full on-line documentation and source downloads in the form of an SDK (Software Development Kit) for C++, Delphi and VB6 applications.

APT  
[www.aptx.com](http://www.aptx.com)

## Indicator for bright lights

The 154 series right-angle mounting status indicator from Marl is available with a range of T-1 3/4, 5mm LED elements. The lens assemblies are colourless for better on/off contrast ratio, and what the



supplier calls secret-unit-lit functionality, makes the product suitable for direct viewing in high ambient light conditions, or through a transparent/translucent front panel screen. Colour range includes red (3,750mcd), yellow (4,500mcd), green (6,000mcd), blue (2,000) and white (800mcd). Other features include dovetail interlocking to enable stacking and customised lead lengths.

Marl  
Tel: +44(0) 1229 582430  
[www.marl.co.uk](http://www.marl.co.uk)



Please quote *Electronics World* when seeking further information

**10Gbit/s opto transceiver goes for record**

Pulsar Electronics is offering a 10Gbit/s physical layer (PHY) device from US firm Mysticom, which the supplier claims features the industry's lowest power and best bit error rate (BER). Based on a patent-pending architecture that incorporates what the firm called an all-digital receiver, the Mysticom MY3004 reduces BER by two orders of magnitude compared with conventional transceivers. Adaptive line-conditioning software is supported which means the device automatically adjusts signal parameters whenever system configurations change. In addition, the device supports a variety of frame formats that allow it to be used as an Ethernet, InfiniBand, or Fibre Channel Transceiver. Packaged in a 17x17mm ball grid array the device is a four-channel 3.125 Gbit/s serialiser/deserialiser (SerDes) device with an XAUI/XGMII HSTL 1.5 volt compliant interface. It features a power consumption of 1.1W equating to 200mW per channel

and selectable 8B/10B encoding/decoding with timing options which provide hook up to upstream Asic, FPGA or other devices. It supports source-centred and flexible source-synchronous timing.  
*Pulsar Electronics*  
 Tel: +44(0) 1296 670922  
 www.mysticom.com

**Siroyan signs up to ewb-based SoC evaluation**


IP company Siroyan has added its scalable DSP technology to SOCworks, the web-based SoC evaluation and simulation environment from Sonics. Under the terms of the agreement, SoC designers will get free access to Siroyan's recently launched SRA328 DSP core to assess performance and interoperability. SOCworks is an online environment that is designed to offer services for the locating and evaluating commercially available semiconductor IP cores by enabling their remote assembly into models of targeted SoC applications for full chip data flow simulations. Siroyan's OneDSP architecture uses instruction-level parallelism to

provide up to 32 execution-unit clusters to be implemented by the licensee with either 32 or 64-bit data paths. At 200MHz, OneDSP will scale from 400 MMACs, with just the master cluster deployed, through to 25.600 MMACs, with a full complement of 32 clusters.  
*Siroyan*  
 Tel: +44(0) 118 949 7028  
 www.sonicsinc.com

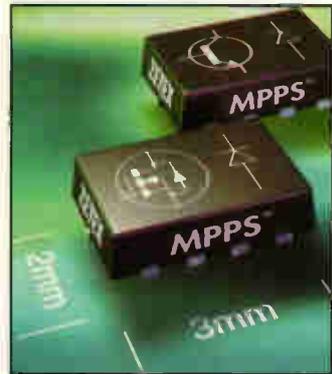**Transistor/Schottky pairs in a smaller device**

These six transistor/Schottky diode pairings are the first devices to be made available in Zetex's miniature package power

solutions (MPPS) range, which it claimed offers board space saving of 88% over alternative SM8 packaged products. Through a reduction in thermal and electrical resistance, the 0.9mm high MLP832 packaged products are characterised by high power dissipation and cooler running. As a result, current handling can be increased by a minimum of 300%. One NPN and three PNP bipolar combination products are offered, featuring a low saturation transistor and a 1A fast switching Schottky barrier diode with a VR of 40V at 1A and the range includes 12, 20 and 40V rated PNP parts and a 20V NPN.  
*Zetex*  
 Tel: +44(0) 161 622 4444  
 www.zetex.com



**PCB prototyping tool supports IP re-use**

Zuken has upgraded its Hot-Stage virtual prototyping tool to enable electrical constraints to be defined and reused within a schematic capture environment. Version 4.03 enables definition of high-level meta-constraints for complete signal paths within the schematic, each constraint being capable of application to hierarchy levels. The tools have always allowed users to establish electrical and physical constraints from a central database of information, but only logical attributes could be defined within the schematic. Effective IP re-use requires the ability to capture not only logical net constraints, but also the constraints associated with electrical nets and complete timing paths. At the schematic level, engineers have always been able to specify delays for logical nets N1 and N2, but have not been able to specify overall path delays. Such low-level attribute definition leads to over-constrained routing, particularly in high-speed designs.  
*Zuken*  
 Tel: +44(0) 1454 207800  
 www.zuken.com

**Optical test for 300 DWDM channels**

Rohde & Schwarz is offering an optical measuring instrument through its relationship with Advantest, which has the capability of simultaneous measurements on up to 300 dense-WDM channels. Measuring both emission wavelengths and power levels, the Q8331

allows the simultaneous measurement of up to 300 channels at an average measurement speed of only 0.5s. The signals are displayed on the screen as a function of wavelength (similar to the display of the current wavelength fluctuation on a spectrum analyser) or in

the form of numerical lists. The instrument has a measurable wavelength range of 1270nm to 1680nm and a measurement accuracy of  $\pm 1$  ppm at a display resolution of 0.1pm.  
*Rohde & Schwarz*  
 Tel: +44(0) 1252 818888  
 www.rohde-schwarz.com




**75A Current sensor**

Allegro Microsystems has developed a current sensor based on a precision linear Hall-effect integrated circuit coupled with a

# High Resolution Oscilloscope

- High speed 5GS/s dual channel oscilloscope
- 50MHz, 80dB dynamic range spectrum analyser
- PicoScope & PicoLog software supplied FREE
- Plug into any desktop or laptop PC
- High resolution - 12 bits
- Large 128K memory
- 1% DC accuracy

**NEW**  
Product  
Range

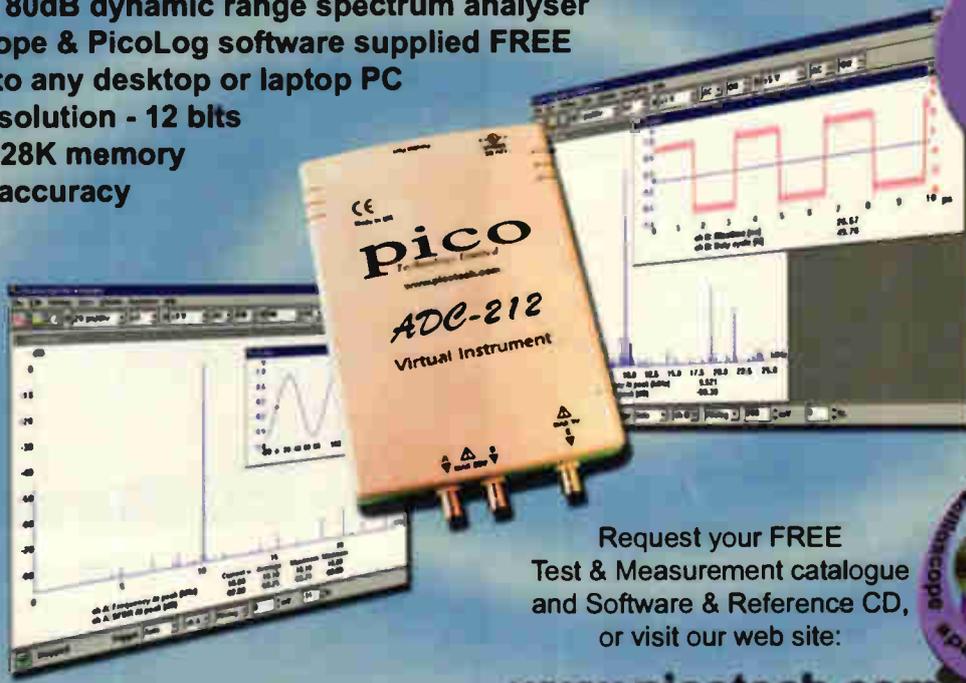

Request your FREE  
Test & Measurement catalogue  
and Software & Reference CD,  
or visit our web site:


[www.picotech.com](http://www.picotech.com)



**PICO**  
Technology Limited


Tel: +44 (0) 1480 396395 Fax: +44 (0) 1480 396296 E-mail: [post@picotech.com](mailto:post@picotech.com)

## TAKE YOUR PIC!

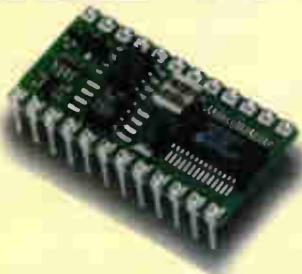

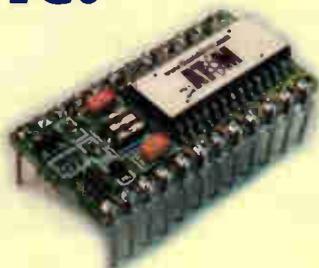**Parallax BASIC Stamp2**

- Very easy to use
- No programmer required
- 500 lines Interpreted BASIC
- Windows Environment
- 16 I/O lines
- 4000 lines/sec
- 24-pin DIP package
- Ready-to-go module
- £39.00 each



**BASICMICRO ATOM**

- Easy to use
- No programmer required
- Compiled BASIC
- 99.99% Stamp2 Compatible
- Uses 16F876
- Very fast
- Interrupts/PWM/Timers/ADCs
- 32 bit Maths-Int/Floating Point
- £45.00 each



**BASICMICRO Compiler**

- Full spec BASIC Compiler for PICs
- Windows Environment
- 99.99% Stamp2 Compatible
- Requires programmer
- We use it!
- Full Debug facility
- Supports all 14-bit PICs (inc 16F84/87X/628 etc)

[www.milinst.com](http://www.milinst.com)

Milford Instruments Limited, Tel 01977 683665, Fax 01977 681465, [sales@milinst.com](mailto:sales@milinst.com)


Please quote *Electronics World* when seeking further information



magnetic circuit optimised to maximise device sensitivity. The entire assembly is housed in a package configuration with automotive or industrial applications in mind. The first device based on the design is the ACS750, which will measure currents of up to  $\pm 75A$  with an accuracy better than 1% and linearity better than 0.5% said the supplier. The sensor is designed for through-hole PCB mounting, with the power leads electrically isolated from the sensor leads. The power leadframe used for current sensing is designed for low power loss, and has an internal resistance of less than  $1m\Omega$ . The sensor exhibits a low thermal drift of offset voltage ( $\pm 0.008\%$ ) and of sensitivity ( $\pm 0.01\%$ ) and has a response time of  $23\mu s$ .  
**Allegro Microsystems**  
 Tel: 0033 450 512359  
 www.allegromicro.com
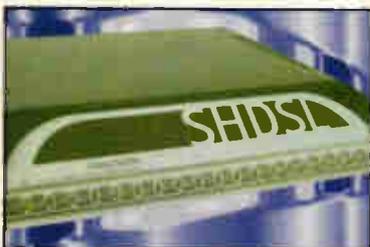
### SHDSL modem puts 2.3Mbit/s on unshielded cable

The Microtel Crocus SHDSL modem uses single-pair high-bit-rate digital subscriber line technology to provide full duplex transmission at up to 2.3Mbit/s over a single two-wire unconditioned unshielded twisted-pair cable. Operation is



based on the new G.SHDSL standard for higher speeds and longer loop ranges, and the variable line transmission rate can be increased to 4.6Mbit/s using a two-pair version of the modem. The use of TC-PAM (trellis-coded pulse-amplitude modulation) is designed to ensure spectral compatibility with other transmissions in the same bundle, so that the risks of crosstalk and intermodulation effects are minimised. It is manageable under HP OpenView, and is supplied with advanced free maintenance software.

**Microtel**  
 Tel: +44(0) 1322 552020  
 www.microtel.co.uk


### RF screening of radiated emissions

Microponents has patented its RF screening system to provide designs with radiated emissions compliance. The system, which is aimed at small-scale electronics manufacturers, allows engineers to build screening enclosures of various sizes, shapes and heights. A design feature is the way in which a profile can be formed whilst maintaining the 2.54mm spacing to fit on development boards. Other features are multi-fence heights, assembly without tools and solderability.

**Microponents**  
 Tel: +44(0) 121 3800100  
 www.microponents.com
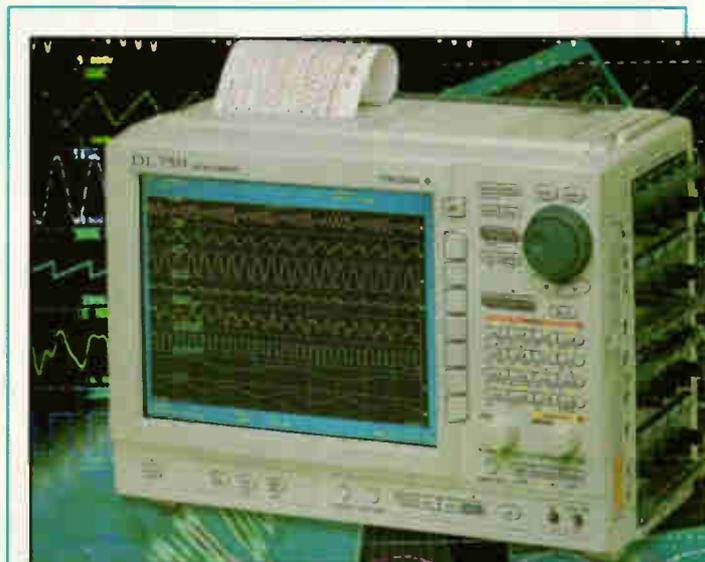
### Development kit with a view

Impact Memec is offering the LabVIEW development kit from Xicor for evaluating and developing systems incorporating the firm's programmable mixed-signal devices. The development environment uses low-level device drivers to allow programmability of specific features such as voltage gains, comparator threshold levels and other key analogue parameters. The kit includes schematics for the hardware interface that is connected via a PC parallel port. The software operates with any PC running Microsoft Windows.  
**Impact Memec**  
 Tel: +44(0) 1296 336100  
 www.impact.uk.memec.com



### Waveform analyser has gigaword of memory

The DL750 ScopeCorder from Yokogawa is a portable waveform measuring instrument that combines recorder and oscilloscope technologies. The instrument's exceptional memory length of up to one gigaword coupled with 10Msamples/s sampling makes it suitable to the capture and analysis of high-speed signals over long time periods of up to ten days. It can act as an oscilloscope for capturing instant events and as a data recorder for prolonged trend measurement. A dual-capture function allows the instrument to capture slow trend data and

high-speed events simultaneously, while a high-speed processing facility called Giga-zoom can process the entire 1 gigaword of data stored in the memory and display it. The instrument can capture data on up to 16 analogue channels plus one 16-bit logic input. Data is sampled at up to 10Msamples/s with 12 bits A/D resolution via a 2-channel isolated input module, or at 1Msamples/s at 16 bits using a high-sensitivity (1mV/div) input module.  
**Yokogawa**  
 Tel: +44(0) 1494 459200  
 www.matron.co.uk

### Audio DAC works off 3V

Wolfson Microelectronics has introduced a family of audio DACs that can run at supply voltages down to 3V. The first device, the WM8726, is a 24-bit, 192kHz stereo DAC which is targeted at applications such as digital TV and digital set top boxes, home theatre systems, MP3, CD and DVD players. The WM8726 is a pin compatible upgrade to the Scottish firm's WM8725, featuring on-chip digital volume control, improved linearity and a data interface that supports industry-standard DSP data

formats. The device has a signal-to-noise ratio (SNR) of 100dB and Total Harmonic Distortion (THD) at -95dB. It is available in a 14-pin SOIC package.  
**Motorola**  
 Tel: +44(0) 1355 565000  
 www.mototrola.com

### Low profile PCI cards have 2 or 4 ports

Brain Boxes are offering two low-profile PCI communications cards. The two port and four port cards are less than 85mm in height. The cards follow a one port version released to coincide with the launch of low profile PCI as a standard in February 2000. Low profile PCI is similar

## SPECIAL OFFERS



**ONLY £425**

TEKTRONIX 2232 Digital Storage Scope. Dual Trace 100 MHz, 100ms with probes. £925  
 H.P. 54501A Digitizing Oscilloscope 100MHz, 4Ch £425  
 H.P. 3312A Function Gen 0.1Hz-13MHz AM/FM Sweep/Tri/Gate/Burst etc. £300  
 FARNELL Oual PSU XA35-2T 0-35V 0-2A Twice OMD LCO Display. £180  
 CIRRUS CRL254 Sound Level Meter with Calibrator, 80-120dB, LEO. £150  
 EDDYSTONE 1002 Receiver 150kHz-30MHz + Broadcast FM. £125  
 FARNELL AHM255 Automatic Mod Meter 1.5MHz-2GHz Unused. £300  
 FARNELL OSG1 Low Frequency Syn Sig Gen 0.001Hz to 99.9kHz, Low Distortion TTL/Square/Pulse Outputs etc. £95  
 FLUKE 8060A Handheld True RMS OMM 4 1/2 digit As new £150 Used £95  
 BECKMAN HD110 Handheld 3 1/2 digit OMM, 28 ranges with battery, leads and carrying case. £40

H.P. 3310A Function Gen 0.005Hz-5MHz Sine/Sq/Tri/Ramp/Pulse. £125  
 FARNELL FLMA Sine/Sq Oscillator 10Hz-1MHz low distortion, TTL Output, Amplitude Meter. £125  
 H.P. 545A Logic Probe with 546A Logic Pulsar and 547A Current Tracer. £90  
 FLUKE 77 Multimeter 3 1/2 digit Handheld. £60  
 FLUKE 77 SERIES II. £70  
 HEME 1000 LCO Clamp Meter 0-1000A In Carrying Case. £60

Racal 9008 ONLY £95  
 Automatic Modulation Meter AM-FM 1.5MHz-2GHz

Oatron 1061 £150  
 High Quality 5.5 Digit Bench Multimeter True RMS/4 wire Res/Current Converter/IEEE

Oatron 1061A £225  
 High Quality 6 1/2 digit Bench Multimeter True RMS/4 wire/Current Converter

Racal Receiver RA1772 £250  
 50kHz - 30MHz LEO Display Basically Working.

## STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
 Telephone: (0118) 9268041 Fax: (0118) 9351696  
 www.stewart-of-reading.co.uk

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

## MARCONI 2019A



AM/FM synthesised signal generator 80kHz - 1040MHz  
**NOW ONLY £400**

MARCONI 893C AF Power Meter, Sinad Measurement. Unused £100 Used £60  
 MARCONI 893B - No Sinad. £30  
 MARCONI 2610 True RMS Voltmeter Autoranging 5Hz-25MHz. £195  
 GOULD J3B Sine/Sq Osc. 10Hz-100kHz Low distortion £75-£125  
 AVO 8 Mk6 in Ever Ready Case, with leads etc. £80  
 Others Avos. from £50  
 GOODWILL GVT427 Oual Ch AC Millivoltmeter 10mV In 12 Ranges Freq 10Hz-1MHz. £100-£125  
 SOLARTRON 7150 OMM 6 1/2 digit True RMS - IEEE £95-£150  
 SOLARTRON 7150 PLUS £200

**HIGH QUALITY RACAL COUNTERS**  
 9904 Universal Timer Counter, 50MHz. £50  
 9916 Counter, 10Hz-520MHz. £75  
 9916 Counter, 10Hz-560MHz, 9-digit. £125  
 WAYNE KERR B424 Component Bridge £125  
 RACAL/AIM 9343M, LCR Oatbridge, Digital Automeasurements of R.C.L.O.D. £200  
 HUNTRON TRACKER Model 1000. £125  
 MARCONI TF2015 AM/FM sig gen. 10-520MHz. £175  
 FLUKE 8050A 4.5 Digit, 2A True RMS. £75  
 FLUKE 8012A 3.5 Digit, 2A. £40

SOLARTRON 7045 Bench Multimeter £30  
 4.5 Digit Bright LED with Leads ONLY

Portable Appliance Tester Megger Pat 2 ONLY £180

H.P. 6012B OC PSU 0-60V; 0-50A 1000W. £1000  
 FARNELL AP60/50 1KW Autoranging. £1000  
 FARNELL H60-50 0-60V 0-50A. £750  
 FARNELL H60/25 0-60V; 0-25A. £400  
 Power Supply HPS3010 0-30V, 0-10A. £140  
 FARNELL L30-2 0-30V; 0-2A. £80  
 FARNELL L30-1 0-30V, 0-1A. £60  
 Many other Power Supplies available.  
 Isolating Transformer 240V In/Out 500VA. £40

## GOULD OS 300 OSCILLOSCOPE



DUAL TRACE 20MHz TESTED WITH MANUAL **£95**

### OSCILLOSCOPES

TEKTRONIX TD3350 Dual Trace 200MHz 16S unused. £1500  
 TEKTRONIX TDS320 Oual Trace 100MHz 500MS. £1200  
 TEKTRONIX TDS310 Oual Trace 50MHz 200MS. £950  
 LECROY 9400A Oual Trace 175MHz SG/S. £750  
 HITACHI VC6523 Dual Trace 20MHz 20MS etc unused. £500  
 PHILIPS PM3092 2+2Ch 200MHz Delay. £900 As New £950  
 £700 As New £800  
 TEKTRONIX TAS465 Dual Trace 100MHz Delay etc. £750  
 TEKTRONIX 2465B 4Ch 400MHz Delay Cursors etc. £1500  
 TEKTRONIX 2465 4Ch 300MHz Delay Cursors etc. £900  
 TEKTRONIX 468 Oig Storage Oual Trace 100MHz Delay. £450  
 TEKTRONIX 466 Analogue Storage Oual Trace 100MHz. £250  
 TEKTRONIX 485 Dual Trace 350MHz Delay Sweep. £550  
 TEKTRONIX 475 Oual Trace 200MHz Delay Sweep. £350  
 TEKTRONIX 2465B Dual Trace 100MHz Delay Sweep. £325  
 TEKTRONIX 2215 Oual Trace 60MHz Delay Sweep. £250  
 PHILIPS PM3217 Dual Trace 50MHz Delay. £200 - £250  
 GOULD DS1100 Oual Trace 30MHz Delay. £125  
 HAMEG HM303.6 Dual Trace 35MHz Component Tester. As new. £240  
 HAMEG HM303 Oual Trace 30MHz Component Tester. £200

### MANY OTHER OSCILLOSCOPES AVAILABLE

MARCONI 2022E Synthesised AM/FM Sig Gen £525 - £750  
 10kHz - 1.01GHz LCD Display etc.  
 H.P. 8657A Syn 100kHz - 1040MHz Sig Gen. £2000  
 H.P. 8658B Syn 100kHz - 990MHz Sig Gen. £1250  
 H.P. 8656A Syn 100kHz - 990 MHz Sig Gen. £995  
 RAS APN62 Syn 1Hz - 260kHz Sig Gen. £425  
 Balanced/Unbalanced Output LCO Display  
 PHILIPS PM5328 Sig Gen 100kHz - 180MHz with 200MHz Freq Counter IEEE. £550  
 RACAL 9081 Syn AM/FM Sig Gen 5kHz - 1024MHz £250  
 H.P. 3325A Syn Function Gen 21MHz. £600  
 MARCONI 6500 Amplitude Analyser. £1500  
 H.P. 4192A Impedance Analyser. £5000  
 H.P. 4275A LCR Meter 10kHz - 10MHz. £2750  
 H.P. 8903A Oistortion Analyser. £1000  
 WAYNE KERR Inductance Analyser 3245. £2000  
 H.P. 8112A Pulse Generator 50MHz. £1250  
 MARCONI 2440 Freq Counter 20GHz. £1000  
 H.P. 5350B Freq Counter 20GHz. £2000  
 H.P. 5342A 10Hz - 18GHz Freq Counter. £800  
 H.P. 1650B Logic Analyser 80 Channel. £1000  
 MARCONI 2305 Mod Meter 500kHz - 2GHz. £750  
**RADIO COMMUNICATIONS TEST SETS**  
 MARCONI 2955/2955A. £1500  
 Rohde & Schwarz CMT 0 1 - 1000MHz. £2000  
 Schlumberger 4040. £900

### USED EQUIPMENT - GUARANTEED. Manuals supplied.

This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

## JUST IN

H.P. 6063B DC Electronic Load 3-240V/0-10A 250W P.O.A. £400  
 H.P. 66312A PSU 0 - 20V/0-2A £400  
 H.P. 66311B PSU 0 - 15V/0-3A £400  
 H.P. 663090 PSU Dual 0 - 15V 0-3A/0-12V 0-1.5A. £750  
 H.P. 6632B PSU 0 - 20V/0-5A. £590  
 H.P. 6623A PSU Triple Output ranging from 0-7V 0-5A to 0-20V 0-4A £850  
 H.P./Agilent 34401A DMM 6 1/2 digit. £400/£450  
 H.P. 3478A OMM 5 1/2 digit. £275  
 FLUKE 45 OMM Oual Display. £400  
 KEITHLEY 2010 DMM 7 1/2 digit. £950  
 KEITHLEY 617 Programmable Electrometer. £1250  
 H.P. 4338B Millichrometer. £1500  
 RACAL Counter type 1999 2.6 GHz. £500  
 H.P. Counter type 53131A 3GHz. £850  
 H.P./Agilent 33120A Function Gen/ARB. £900/£1000  
 100microHz - 15MHz  
 SONY/TEKTRONIX AFG320 Arbitrary Function Gen. £1250  
 H.P. 8904A Syn Function Gen OC - 600kHz £1000/£1250  
 BLACK STAR JUPITOR 2010 Function Gen 0.2Hz - 2MHz with Frequency Counter. £140  
 H.P. 8116A Pulse Generator 1mH-50MHz. £1950  
 H.P. 6657B Syn Signal Gen 0.1-2080MHz. £2500  
 CO-AXIAL SWITCH 1.5GHz. £40  
 IEEE CABLES. £10

### SPECTRUM ANALYSERS

H.P. 8561B 50Hz - 6.5GHz. £5000  
 H.P. 8560A 50Hz - 2.9GHz Synthesised. £5000  
 H.P. 8594E 9kHz - 2.9GHz. £4580  
 H.P. 8591E 1MHz - 1.8GHz 75 ohm. £2750  
 H.P. 853A with 8559A 100kHz - 21GHz. £1750  
 H.P. 8558B with Main Frame 100kHz - 1500MHz. £750  
 H.P. 3585A 20Hz - 40MHz. £2500  
 H.P. 3580A 5Hz - 50kHz. £900  
 ADVANTEST R4131B 10kHz - 3.5GHz. £2750  
 EATON/Aitech 757 0 001 - 22GHz. £750  
 MARCONI 2382 100Hz - 400MHz High Res. £2000  
 MARCONI 2370 30Hz - 110MHz. £500  
 H.P. 182 with 8557 10kHz - 350MHz. £500  
 H.P. 141T Systems  
 8553 1kHz - 110MHz. £750  
 8554 500kHz - 1250MHz. £750  
 8555 10MHz - 18GHz. £1000  
 H.P. 8443 Tracking Gen/Counter 110MHz. £250  
 H.P. 8444 Opt 059. £750  
 B & K 2033R Signal Analyser. £650  
 H.P. 8754A Network Analyser 4MHz - 1300MHz. £1250  
 H.P. 3577A Network Analyser 5Hz - 200MHz. £3000  
 H.P. 53310A Modulation Domain Analyser Opt 001/003. £5000  
 ONO SOKKI Portable FFT Analyser. £1500  
 H.P. 8720C Microwave Network Analyser 50MHz-200GHz. £12500

# Professional PCB Layout & Mixed Mode Simulation at Computer Store Prices!!

From Only

**£97**

## NEW Easy-PC V6.0

Easy-PC for Windows V6.0 is released with now even more time saving features:

- On-line design rules checking
- Single 'shot' post processing for all your output files
- PCB Footprint & SCM Symbol Wizards for fast creation
- Import DXF files from your mechanical drawings
- and many more new features!

## Spice Based Simulator

Easy-Spice is a powerful A/D mixed mode simulator with superior convergence and functionality.


- Easy-Spice is integrated with Easy-PC Schematics
- Supplied ready to use with SPICE libraries and models
- Easy to learn and use and supplied with a full manual

For more information or for a demo copy call us on +44 (0)1684 773662 fax +44 (0)1684 773664

or E-mail [info@numberone.com](mailto:info@numberone.com)

or download a demo copy from [www.numberone.com](http://www.numberone.com)

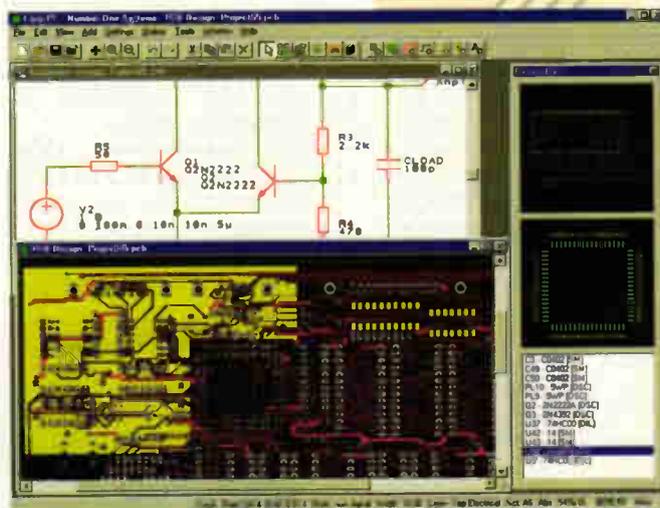Number One Systems, Oak Lane, Bredon, Tewkesbury, Glos, GL20 7LR



## NEWPRODUCTS

Please quote *Electronics World* when seeking further information

to PCI in terms of electricals, signals, and drivers, but possesses a more compact form factor with a shorter raw card and new mounting bracket. The two new cards are backward compatible with standard PCI brackets. Both new cards are offered with a customer support package including a three year warranty.

*Brain Boxes*

Tel: +44(0) 151 220 2500

[www.brainboxes.com](http://www.brainboxes.com)

### Small package buck voltage regulator

A buck regulator in a package claimed to be 36% smaller than the commonly used TO-263 (D2PAK) is available from Micrel Semiconductor. The MIC4685, a member of SuperSwitcher family, is a 200kHz, PWM buck regulator housed in a 7-lead SPAK package. The device has an input

voltage range of 14V to 34V, and a 3A output current. Output voltage is adjustable down to 1.25V. Features include a cycle-by-cycle current limit, frequency foldback short circuit protection, and thermal shutdown. Samples are available from stock, and production quantities are on a 12 week lead time. Efficiency is over 85% and a typical shutdown current is 150µA.

*Micrel Semiconductors*  
[www.micrel.com](http://www.micrel.com)

### 1.5Gbit/s serial connectors

Honda is offering a family of 1.5Gbit/s serial ATA connectors. The company also expects to release 3Gbit/s and 6Gbit/s versions by 2004 and 2007 respectively which it said is in line with the projected rollout of the serial data interface standard. They are designed to support the bandwidths which will be required in RAID arrays and multimedia PCs for transferring data between high capacity HDDs and to CD-ROM/DVD drives with read/write capabilities. Features include a passive locking system and a polarisation feature, as well as hold downs to improve retention to the PCB. The serial ATA

interface is specified for cable runs of up to 100cm. It has been implemented on a cable-mount signal connector, a combined PCB mount connector and a 7-pin PCB mount signal connector.

*Honda*

Tel: +44(0) 1793 523388

[www.hondaconnectors.co.uk](http://www.hondaconnectors.co.uk)

### EMC horn antenna for 18GHz

A double-ridge horn antenna has been added to the range offered by Schaffner. The BHA9118 is suitable for applications such as RF and EMC measurements to MIL, SAE, IEEE, IEC and FCC standards. The 1GHz to 18GHz antenna is a linearly polarised broadband unit is capable of

250V/m, at one metre. The design is rugged and corrosion-resistant, and can be used to receive and transmit. A precision N-type connector is used to provide low VSWR and high power handling capability. Each antenna is individually calibrated, following ANSI 063.5 traceable to national standards. The antenna is supplied with a calibration certificate that contains the measured antenna factor data certifying precise antenna performance.

*Schaffner*

Tel: +44(0) 1306 710205

[www.schaffner.com](http://www.schaffner.com)

### Power Mosfets cut on-resistance by 40 per cent

International Rectifier has introduced the 100V, IRFB4710 and IRFS4710 HEXFET power Mosfets that it claimed increase power density in 48V input, half- or full-bridge topologies used in the top-end DC-DC converters required for telecoms and datacomm systems. The IRFB4710 device is rated at 75A in the TO-220 package, or 30% higher current than previous generation devices. The Mosfets have a 40% lower on-resistance, or RDS(on), than previously available devices. According to



### 32-bit superscalar embedded processor

Hitachi has announced two SH-4 32-bit superscalar Risc embedded microprocessors that offer higher frequency and a new cache architecture for multimedia applications, car information systems and networking applications. The devices include a superscalar architecture, full floating point engine, SIMD (Single Instruction Multiple Data) acceleration for 3D and DSP, and 16-bit fixed instruction length for low memory footprint. The SH7751R offers an integrated PCI controller while the SH7750R has a 64-bit SDRAM interface for increased memory bandwidth. Both offer increased performance (430MIPS/1.7Gflops) and higher frequency (240MHz) than existing SH-4 devices, with 64-bit bandwidth to provide a memory throughput up to


120MHz SDRAM access at a peak of 960Mbyte/s. The new cache architecture from direct map to 2-way set associative reduces the cache miss and increases the real time capabilities. Operating at 1.5V, they have four additional DMA channels (eight in total), support a temperature range from -40 to +85°C, and provide 16kbytes instruction and 32kbytes data

cache memory. The devices support the complete multimedia software stack which includes operating systems, JavaVM, browser, e-mail, OSGI, VoIP, H.323 suitable for Java-based embedded applications, Internet appliances and Multimedia interactive TV.

*Hitachi*

Tel: +44(0) 1628 585161

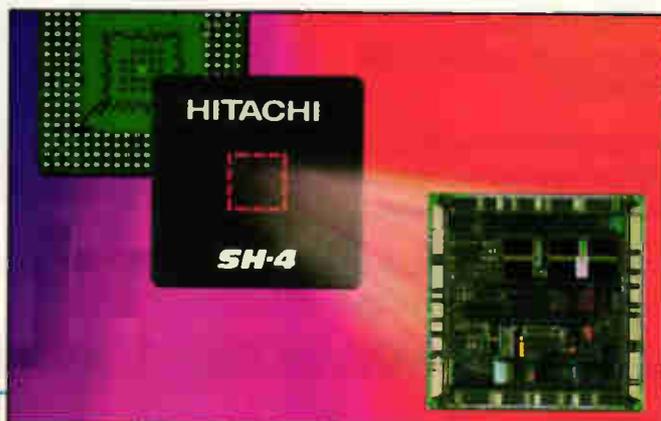[www.hitachi-eu.com](http://www.hitachi-eu.com)



the supplier, in-circuit testing shows that four IRFB4710s run 20°C cooler at 350W compared to industry-standard devices. The IRFS4710 MOSFET, in a D2Pak package is optimised for 100 to 300W, board mounted power systems. The IRFB4710, in a TO-220 package is designed for 3kW to 5kW shoe-box type power supplies used in wireless base stations.

*International Rectifier*

Tel: +44(0) 20 8645 8003

[www.irf.com](http://www.irf.com)



# CIRCUIT IDEAS

## Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity. Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly. Where software or files are available from us, please email Jackie Lowe with the circuit idea name as the subject.

Send your ideas to: Jackie Lowe, Highbury Business Communications, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8BZ email [j.lowe@highburybiz.com](mailto:j.lowe@highburybiz.com)

## An on line programming adapter solves PIC programming pins problem


The most important secret in embedded processors is on line programming. It is done either with a ROM emulator or with a flash programming. These methods allow programming and testing in real

devices. Sometimes all the programming pins of the processor are used by an external load. Then on line programming does not work. Also an on line programmer prevents operation of some processor pins. I

faced this problem in my last project, namely a 12" LED display for horse races. ULN2803 in RB7 and RB6 prevented the on line programming. After I had added some booster resistors the programmer worked, but it prevented normal operation of the circuit.

The solution is to automatically switch the on line programmer on and off. This circuit works on any PIC programmer. The circuit uses a standard 12 volt 2 pole DIP relay to switch programming pins RB7 and RB6 on and off with 5V from the programmer. Diode D1 prevents circuit power to switch the relay on with normal power supply. D2 separates the reset circuit from programmer. I used a LED in series with the relay to get a visual indication and to reduce 5V loading. I found that a 12V relay works with 3V and 18mA! The R1 and R2 add some boost to the programmer for external loads. The resistors are automatically switched off after programming. Using PC software I can switch the programmer 5V on. I do not need any other power supply for testing. Which is very convenient for field programming! I used a small utility box with two DB9 connectors to build this very useful programmer adapter. When needed, I simply put this adapter in series of my normal PIC programmer.

**Pekka Ritamaki**  
Tampere,

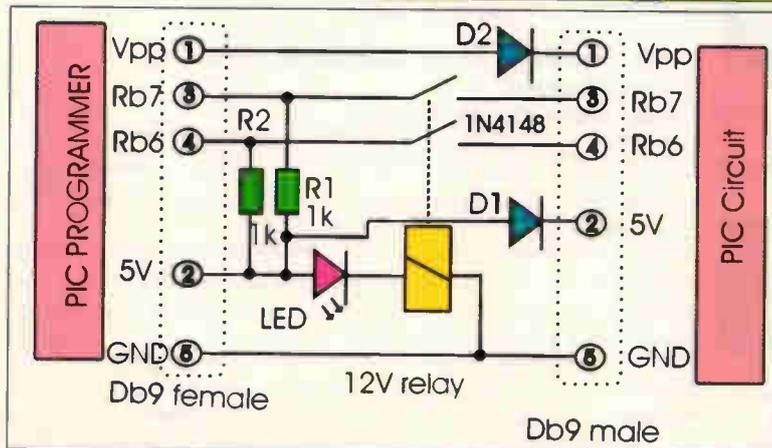

# PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

- Prototypes at a fraction of the cost
- Industry standard quality
- Tooling and setup included
- Follow up series runs
- Any contour
- CAM / CAD consulting
- Fr4 1.6mm, 35µm Cu

**PRICE EXAMPLE**  
**1 EUROCARD DS/PTH**  
 + Tooling  
 + Photoplots  
 + VAT  
 = **£ 29.89\***

\*Sterling rates may vary. Price = € 49

**FREE** (with stock test)

**Freephone 0800-389 8560**

Tel: +353 (0)61 701170  
 Fax: +353 (0)61 701164  
 E-Mail: sales@pcbpool.com

Simply send your files and order ONLINE:  
**WWW.PCB-POOL.COM**

Protel orcad EDWIN GraphiCode

## The Stereo Headphone Amplifier Box

Balanced or unbalanced line inputs to stereo headphone output

Professional portable units operating from an internal PP3 battery or external mains adaptor



\* Precision transformerless differential left and right inputs \*  
 Wide range of headphone drive impedances \* High common mode rejection \* Low noise and distortion \* Low quiescent power consumption for extended battery life \* Extensive RFI protection

The Balance Box (mic/line amplifier) – The Phantom Power Box – The OneStop DIN rail mounting radio frequency interference filter and voltage transient protector for voltage and current loop process signal lines

Conford Electronics Conford Liphoad Hants GU30 7QW

Information line 01428 751 469 Fax 751223

E-mail: contact@confordelec.co.uk

Web http://www.confordelec.co.uk/

### T & M EQUIPMENT

AGILENT TECHNOLOGIES (HEWLETT PACKARD)



8563ES/02/06/010 network analyser with 006 & 010 (6GHz + time-domain options) (list £32k) £20000  
 All above supplied with new Agilent calibration & 1 year warranty.

• **ralfe electronics** • *exclusively professional T&M*  
 Unit 1, Olds Close, Olds Approach • WATFORD Herts WD1 8RU • ENGLAND  
 Tel (+44) 0 1923 721396 • Fax (+44) 0 1923 721402

EST 45 YRS



### AGILENT TECHNOLOGIES



8720C/011 20GHz network analyser	£12500
16534A digitising oscilloscope card	£2500
16702A logic analyser system mainframe (E865)	£4000
33120A 150MHz function generator	£850
37724A / 37776A SDH/PDH test set with optical (1310nm) plug-in	£2000
437B microwave power meter (requires additional sensor)	£1000
4386B /010/06 spectrum/network impedance analyser (E5-25k)	£15000
53310A modulation analyser /01030 (>10k)	£9000
54835A infinium oscilloscope 5GSa/sec 4 channel (E16k)	£9000
85053B 3.5mm ventilation kit	£2000
85096D 2.4mm economy calibration kit (list £4904)	£2500
85132F 7mm to 3.5mm flexible test port cable set (list £2862)	£1750
85133F 2.4mm flexible test port cable set (list 4249)	£2500
89441A 2.65GHz vector signal analyser, many options listing at >50k 2 in Stock	£ call
8164A lightwave measurement system with 81640A / 072 tunable laser module	£15000
8164A lightwave measurement system with 81680A / 072 tunable laser module	£15000
86142B /004/006 optical spectrum analyser (>£37k)	£15000
8657B synthesised signal generator 0.1 – 200MHz	£3000
8722E/010/05 40GHz network analyser (list >£58000)	£90000
89003B /10/51 audio analyser	£2000
89004A function generator	£1000
8970A noise figure meter with 346A noise source	£3000
88350A 300kHz - 9GHz network analyser (48k)	£25000
E4432B 250kHz-3GHz signal gen with /1ES/UNS/AJ/47/UN6/UND (E29k)	£16000
E4437B 250kHz-4 GHz signal gen with UN6/UN6/UND (27k)	£17500
E5200A broadband service analyser, options /02/05/1/22/122/138/138/139/139	£5000
J2171A ethernet interface module	£1500
J3458A fast ethernet lanprobe option 201 OR 202 and ANS	£2000
J3911A multipoint telnet-ring Lanprobe	£2000
J3921A E3 ATM probe	£6500
J535A Telegra D analyser 201 / 202 options (list £1325k)	£6500

## HEWLETT PACKARD 8563A

Low phase-noise, high specification microwave spectrum analysers.  
 300kHz-22GHz £6500 each.



8722E/010 40GHz network analyser  
 £30,000. (LIST >58k)

All equipment sold calibration-checked by independent laboratories and carries un-conditional refund and 90-day guarantees.

**TEST EQUIPMENT WANTED.**

TOP PRICES PAID FOR PROFESSIONAL HIGH-END UNITS  
**AGILENT TECHNOLOGY SPECIALISTS.**  
 FOR COMPLETE STOCK LISTING PLEASE CHECK OUR WEBSITE  
**www.ralfe-electronics.co.uk**



£50 winner

# Two-wire PIR enhancement

What follows is a low cost and novel means of removing the need for the six-wire bundle currently used to connect to PIR and other detectors in domestic and commercial alarm applications. The bundle is replaced with a more easily routeable two-wire solution. This circuit also offers certain anti-tamper enhancements over the existing six-wire designs.

Driven by the need to route wiring to a new PIR for my home alarm system, this circuit allows the use of single twisted pair to provide the full PIR functionality, which usually requires a three-pair solution.

In normal operating conditions, standard wired PIR detectors exist in one of the following three different current states:

- Idle – requiring about 15mA for the detector circuitry.
- Alarmed – about 70mA. Alarm relay closed, 50mA flows in alarm loop, plus idle current.
- Tampered, where wire has been cut – 0mA.

These values are based on an ageing Wickes system.

A simple current window detector is used in the circuit described here to distinguish between these states. Selection of  $R_1$  and  $R_2$  determines the window of normal operation. Nominally, a current of 15mA is required by my PIR in its non-triggered state, but this will vary according to the detector type used.

In this design, upper and lower thresholds have been set to give roughly an 18mA window of normal operation (8- 26mA).

Resistor  $R_1$  and the  $V_{be}$  of  $Tr_1$  determine the upper threshold while the lower threshold is set by a

combination of  $Tr_2$ ,  $R_1$  and the  $R_5/R_6$  divider.

In the idle state,  $Tr_1$  and  $Tr_2$  are not conducting and a current of about 15mA flows through  $R_1$ . When triggered, the PIR alarm relay (relay contacts in series with 200Ω) switches in and a total current of more than 70mA flows. The resulting voltage across  $R_1$  switches  $Tr_1$  into conduction, driving  $Tr_3$  which draws current via  $R_9$  (200Ω in this case to simulate the PIR alarm relay) triggering the alarm circuit of the original three-wire circuit.

If there's no common ground between the power and alarm circuits, a relay could be used in place of  $Tr_3$ .

In the event that the two-wire loop is cut, or the PIR case is opened causing the anti tamper switch to break the circuit, no current will flow and  $Tr_2$  conducts. This causes the normally-closed relay  $RL_1$  to become open circuit.

Resistor  $R_4$  provides a little hysteresis and additional base drive to  $Tr_2$ . An open circuit at  $RL_1$  triggers the anti-tamper circuit of the original alarm circuit. For a number of reasons, including absence of a common ground with the power circuit, a simple relay contact in the existing loop was used to convey the tampering signal.

In the event that an attempt is made to tamper with the PIR or its connecting wires by bypassing them, cutting them, or other means, current drawn will fall outside its operating window and  $Tr_1$  or  $Tr_3$  will conduct, stimulating an alarm. This scheme offers potentially greater tamper resistance than the original design.

Diode  $D_1$ , together with  $R_1$ , helps reduce voltage drop across the circuit to ensure continued operation of the

PIR power circuits under alarm or other high current conditions.

Values shown give a normal operating window of between about 8mA and 26mA, which gives good immunity to false alarms. The debouncing feature of the parent alarm system itself and  $C_1$  and  $C_2$  complement this. As current in the alarm or tamper states are considerably outside the normal window of operation, switching is quick and reliable.

Maximum current delivered by the combined alarm circuit and power circuit of the parent system is understood to be no more than 100mA per port. Resistors  $R_{1,2}$  should have enough dissipation handling capability to cater for a long-term short-circuit tamper.

Careful selection of  $R_5/R_6$  could reduce current taken by the circuit to a few milliamps in current-sensitive applications.

## Rewiring of PIR detectors


In order to use the circuit described, it is necessary to carry out some simple rewiring of the detectors as shown in the diagram. This rewiring can be carried out simply at the screw terminal connectors of the PIR.

The anti tamper switch on the case of the sensor should be connected in series with the parallel combination of PIR power circuit and the alarm circuit.

In order to reduce maximum current drawn via the alarm relay of the PIR and hence through  $R_1$ ,  $D_1$  and  $R_2$ , an additional resistor has been added in series with the alarm contacts of the PIR. A value of 200Ω has worked well.

The alarm contact of the PIR used, remains in conduction for about three

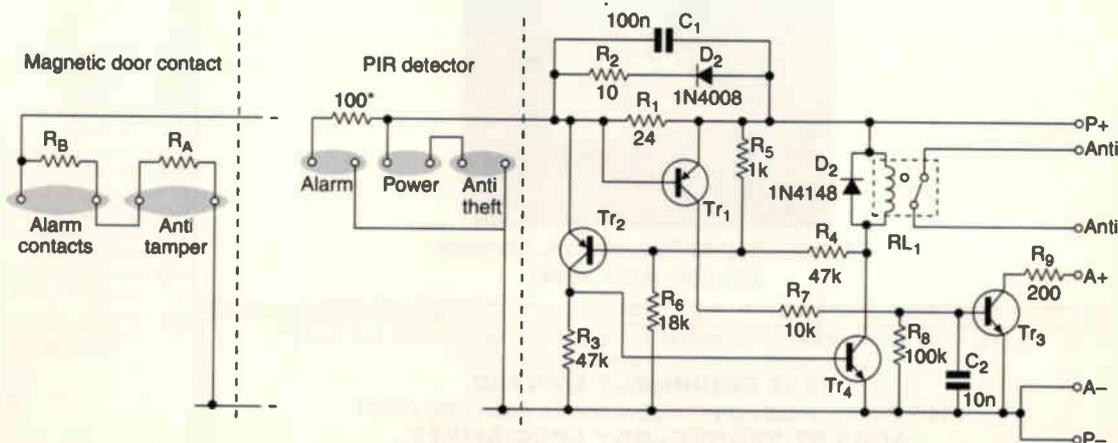*This interface reduces the number of wires needed to connect a PIR sensor from six to two. Transistors  $Tr_{1,2}$  are BC212L while  $Tr_{3,4}$  are BCW34. Line P+ is the positive alarm system supply connection and P- is the negative line. The alarm connections are A+ and A- and the two conductors marked 'Anti' are the anti-tamper circuit connections.*



# FRUSTRATED!

## Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).

2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD  
 ADC AN AM AY BA BC BD BDT BDV BDW BDX BF  
 BFR BFS BFT BFW BFX BFY BLX BS BR BRX BRY BS  
 BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY  
 BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS  
 DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA  
 KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB  
 MC MDA J MJE MJF MM MN MPS MPSA MPM MPST  
 MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB  
 SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD  
 STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB  
 TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA  
 UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN  
 ZTX + many others

We can also offer equivalents (at customers' risk). We also stock a full range of other electronic components. Mail, phone, Fax, Credit Card orders & callers welcome.



## Cricklewood Electronics Ltd

40-42 Cricklewood Broadway, London NW2 3ET  
 Tel: 020 8452 0161 Fax: 020 8208 1441  
 www.cricklewoodelectronics.co.uk  
 E-mail: sales@cricklewoodelectronics.com



SCHEMATIC SIMULATION PCB AUTOROUTING CAD/CAM DESKTOP MANUFACTURE

From £49\*



# Be The First



"a quantum leap"  
Release 12/97

Users all over the world are discovering Electronic Design Studio 3 (EDS 3), with its modern user interface and powerful tool set. And now with the launch of the Standard version of EDS, prices start at just £49\*.

All versions of EDS include fully integrated schematic and PCB design with autorouting and simulation built in. The powerful editing tool set including the Project management system are also included.

More advanced versions include copper pour with support for unlimited zones, cross-probing, heirarchical and multi-sheet design, rip up and retry routing, extensive CAD/CAM options and our new Desk Top Manufacturing (DTM) system.

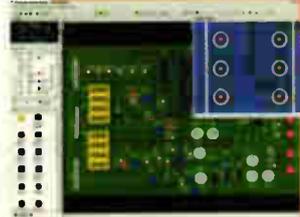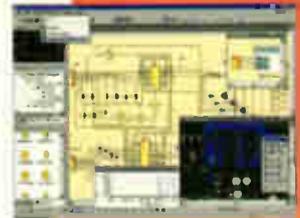Call us know for a free information pack, or try the online trial version at [www.dotqr.com](http://www.dotqr.com)



## electronic design STUDIO

	Standard	Personal	Advance	Ultra
Schematic Design & Capture	✓	✓	✓	✓
SPICE/XSPICE Simulation	✓	✓	✓	✓
Vipar II Autorouter	✓	✓	✓	✓
Realtime Connectivity Checking	✓	✓	✓	✓
Power rail and bus support	✓	✓	✓	✓
Multiple Sheet Schematics	✓	✓	✓	✓
CAD/CAM R-2470X and Drill	✓	✓	✓	✓
Copper Pour with unlimited Zones	✓	✓	✓	✓
Shape based Design Rule Checks	✓	✓	✓	✓
Rip up and retry Autorouter	✓	✓	✓	✓
Cross probing, Net Styles and Tags	✓	✓	✓	✓
Heirarchical Schematics	✓	✓	✓	✓
1mm resolution, Unlimited Layers, auto mitre	✓	✓	✓	✓
Desk Top Manufacturing option	✓	✓	✓	✓
Polyblend system (punch holes in copper, etc)	✓	✓	✓	✓

Send me Price includes UK P&P and VAT. Other variants available. Pin limits may apply.

- EDS 3 Standard 300 at £65       EDS 3 Personal 300 at £91  
 EDS 3 Advance 1000 at £299       EDS 3 Ultra at £476

Name/Address

Card Number

Expiry

Signature



Phone/FAX 01422 255010/255014

www.dotqr.com

Copyright © 2002 Quickroute Systems. E.&O.E.  
 \*Price excludes VAT and P&P.



## WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES (using a video capture card)



"Liesgang diav" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see [www.diatv.co.uk](http://www.diatv.co.uk)

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye).....£37.00 + vat = £43.48

30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole.....£35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses.....£32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle.....£15.97 + vat = £18.76

VSL4022F 4mm F1.22 63x47 degrees viewing angle.....£17.65 + vat = £20.74

VSL6022F 6mm F1.22 42x32 degrees viewing angle.....£19.05 + vat = £22.38

VSL8020F 8mm F1.22 32x24 degrees viewing angle.....£19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle.....£26.43 + vat = £31.06

VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle.....£77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat

1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.5Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily..... £7.46+vat = £8.77



Please add 1.66 + vat = £1.95 postage & packing per order

## JPG ELECTRONICS

Shaws Row, Old Road, Chesterfield, S40 2RB

Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch

Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

seconds following each triggering, after which the PIR is inactive for about three seconds before being rearmed.

**Door/window magnetic reed contacts**

Re-wiring of door contacts is also necessary in order to provide a three-state system and allow full operation of the current-window circuit. Fortunately this is easily achieved at

the screw terminal connectors by adding two resistors in the  $R_A, R_B$  positions shown in the diagram.


For optimum system performance, the resistors chosen should ensure that no more than a few milliamps of current flows. Resistors  $R_1, R_5$  and  $R_6$  should be scaled accordingly.

This arrangement also provides improved anti tamper resistance when compared to the original system for installations using reed type contacts

as this circuit will trip the alarm when a short circuit is used to bypass anti tamper circuits.

If necessary, the circuit can also be locally powered to allow expansion of an alarm system without placing additional demand on the central system's power circuits.

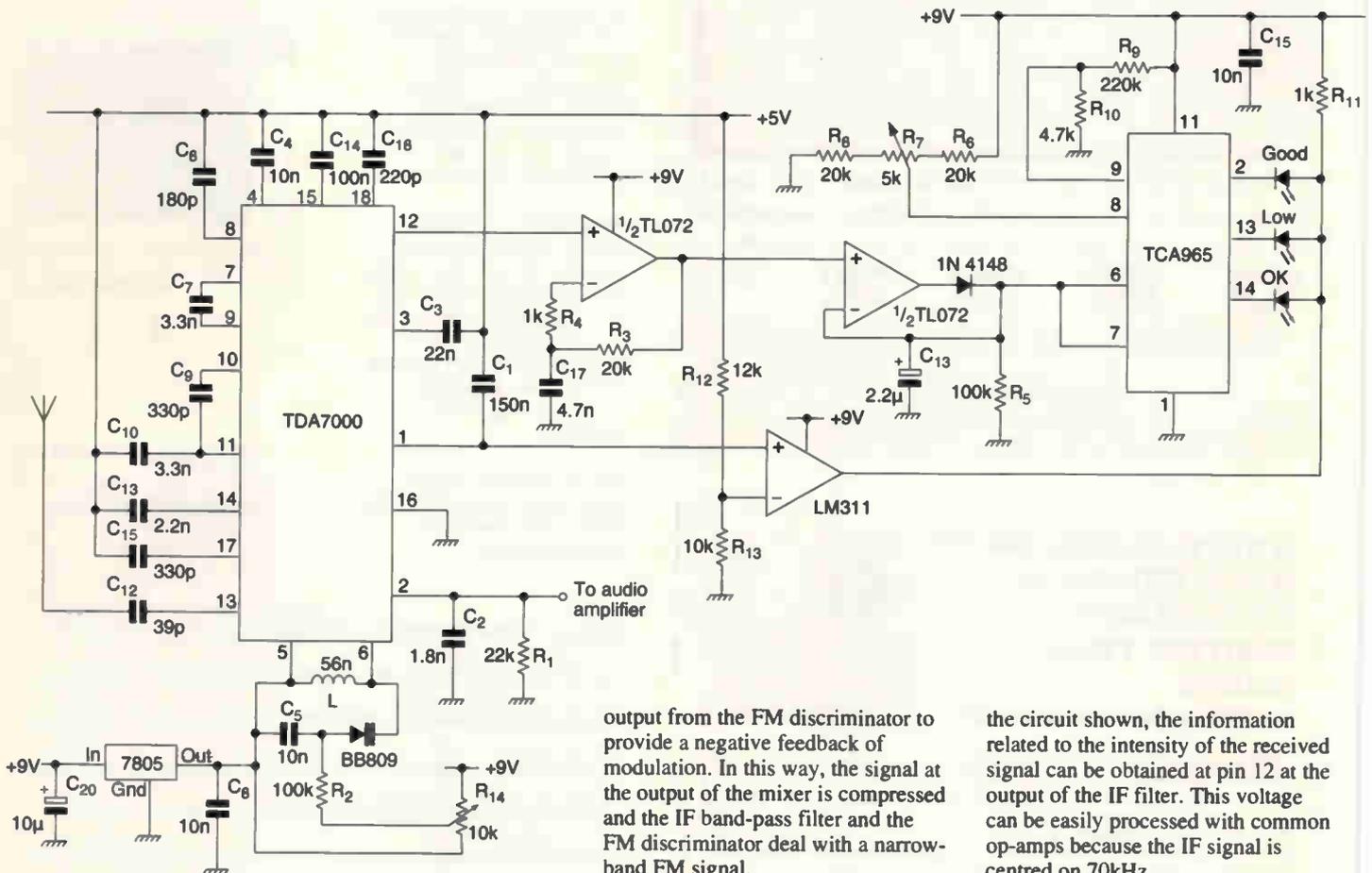**Ian Jennings**  
Caldicot  
Monmouthshire  
UK



**Improve the TDA7000 receiver with a signal-strength display**

Philips' TDA7000 integrates a monophonic FM radio receiver all the way from the antenna to the audio output. Only one tuneable LC circuit for the local oscillator, a few capacitors, two resistors and a potentiometer to control the variable-capacitance diode tuning need to be added to the IC to make a complete receiver.

The 7000 has a frequency-locked-loop structure. The basic idea is simple. Local oscillator output is frequency-modulated by filtered

output from the FM discriminator to provide a negative feedback of modulation. In this way, the signal at the output of the mixer is compressed and the IF band-pass filter and the FM discriminator deal with a narrow-band FM signal.

For a compression factor  $K=3$ , the original FM bandwidth is reduced to  $180/3=60\text{kHz}$ . The IF can be as low as  $70\text{kHz}$  so neither ceramic filters nor complex LC tanks are necessary to realise the IF filter. A simple active filter with operational amplifiers fulfils the task.

The IC incorporates a correlation muting system that suppresses interstation noise and spurious responses due to detuning. The muting circuit is built around a second mixer. Its output is available externally at pin 1 and can also be used to drive a tuning indicator.

If your application demands a high performance FM radio you can add a signal-strength display to the 7000. In

the circuit shown, the information related to the intensity of the received signal can be obtained at pin 12 at the output of the IF filter. This voltage can be easily processed with common op-amps because the IF signal is centred on  $70\text{kHz}$ .

Voltage at pin 12 is DC coupled to an amplifier. Next, an envelope detector built around the TL082 gives a DC voltage analogue to the received signal strength. This voltage is compared in the Siemens TCA965 window discriminator with a voltage derived from  $R_6, R_7$  and  $R_8$  – the window centre – and  $R_9, R_{10}$  for the window half width.

Three LEDs show the result of the comparison – 'low', 'OK', or good – but only when the tuning is correct. When it is, the voltage at pin 1 reaches its maximum value and the comparator LM311 enables the TCA965.

**José Ma Miguel-Lopez**  
Barcelona, Spain

# Self on Audio

## Douglas Self

The cream of 20 years of Electronics World articles (focusing on recent material)

A unique collection of design insights and projects - essential for all audio designers, amateur and professional alike.

Scientific electronics based on empirical data

Douglas Self has been writing for Electronics World and Wireless World over the past 20 years, offering cutting-edge insights into scientific methods of electronics design.

This book is a collection of the essential Electronics World articles, covering twenty years of amplifier technology but with a very strong bias towards more recent material. The articles include self-build projects as well as design ideas and guidance for the professional audio designer. The result is a unique collection of design insights and projects - essential for all audio designers, whether amateur or professional.

**Contents:** Introduction; PRE-AMPLIFIERS: An advanced preamplifier MRPI; High-performance preamp MRP4; Precision preamp MRP10; Moving-coil head amp; Preamp '96 I; Preamp '96 II; "Overload Matters" (RIAA overload); Balanced line inputs and outputs, part 1; Balanced line inputs and outputs, part 2; POWER AMPLIFIERS: FETs less linear than BJTs; Distortion in power amplifiers 1-8; Distortion residuals; Trimodal part 1, 2; Load-invariant power amp INVAR.DOC; Common-emitter amps; Two-stage amplifiers; SPEAKERS: Excess speaker currents; Class distinction (amp classification); Relay control; Power partition diagrams; Audio power analysis.

ELECTRONICS  
WORLD



Self  
on  
Audio  
DOUGLAS SELF

Douglas Self has dedicated himself to demystifying amplifier design and establishing empirical design techniques based on electronic design principles and experimental data. His rigorous and thoroughly practical approach has established him as a leading authority on amplifier design.

Readership: Audio electronics enthusiasts;  
Professional amplifier designers;  
Power amp users  
Paperback  
Pages: 416pp

**UK Price: £26.50 Europe £27.50 ROW £28.50**

Return to Jackie Lowe, Highbury Business Communications  
Anne Boleyn House, 9-13 Ewell Road, Cheam,  
Surrey, SM3 8BZ

Please supply the following title:

**SELF ON AUDIO**

Total \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

Telephone \_\_\_\_\_

Method of payment (please circle)


Mastercard/Visa/Cheque/PO

**Cheques should be made payable to  
Electronics World**

Credit card no. \_\_\_\_\_

Card expiry date \_\_\_\_\_

Signed \_\_\_\_\_

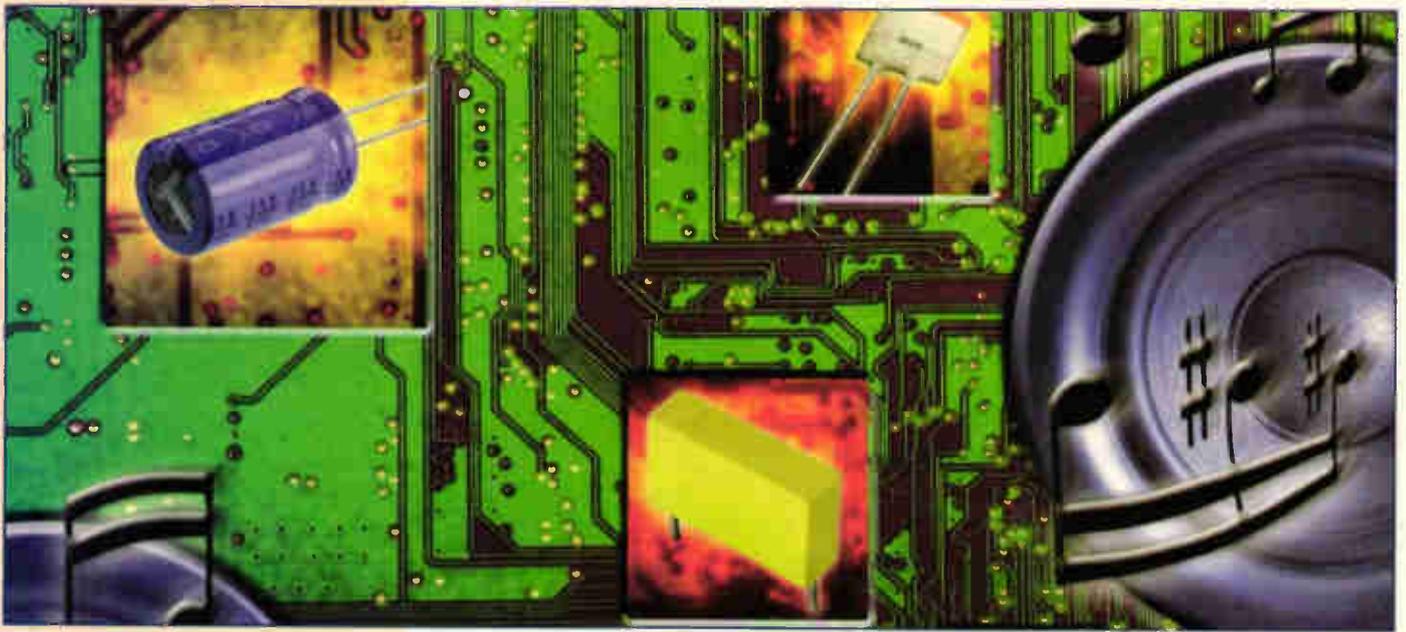

# Capacitor sound 4

**This month, Cyril concentrates on the difficult area of 100nF to 1µF, which usually for size and cost reasons means using metallised PET products**

**R**eaders of my previous articles will have seen that many capacitors do introduce distortions onto a pure sine wave test signal. In some instances distortion results from the loading the capacitor imposes onto its driver. In others, the capacitor generates the distortion within itself.<sup>1</sup>


Capacitors are not categorised for distortion in manufacture, so a distorting capacitor would not be accepted as reject by its maker. Using my easily replicated test method, capacitor distortions can now be measured, surpassing speculation. Equipment designers can now select capacitors for each circuit requirement.

For capacitances of 10nF and smaller, the safe solution is to use COG ceramic or extended foil/film capacitors. Made with Polystyrene or Polypropylene dielectrics and with leadwires soldered or welded directly to the extended foil electrodes. Avoiding altogether capacitors made with metallised film dielectrics.

These idealised choices minimise all measurable distortion products. While this presents a counsel of perfection, as an engineer I believe prior knowledge of the best and worst extremes should form part of any compromise.

Such near ideal capacitors are not easily

*Figure 1: Distortion measurement of a 100nF 50 volt COG ceramic, using 100Hz and 1kHz signals at 4 volts with 18 volt DC bias. With no bias this multilayer capacitor measured just 0.00004%. Second harmonic was -131.7dB, other harmonics remained as shown.*

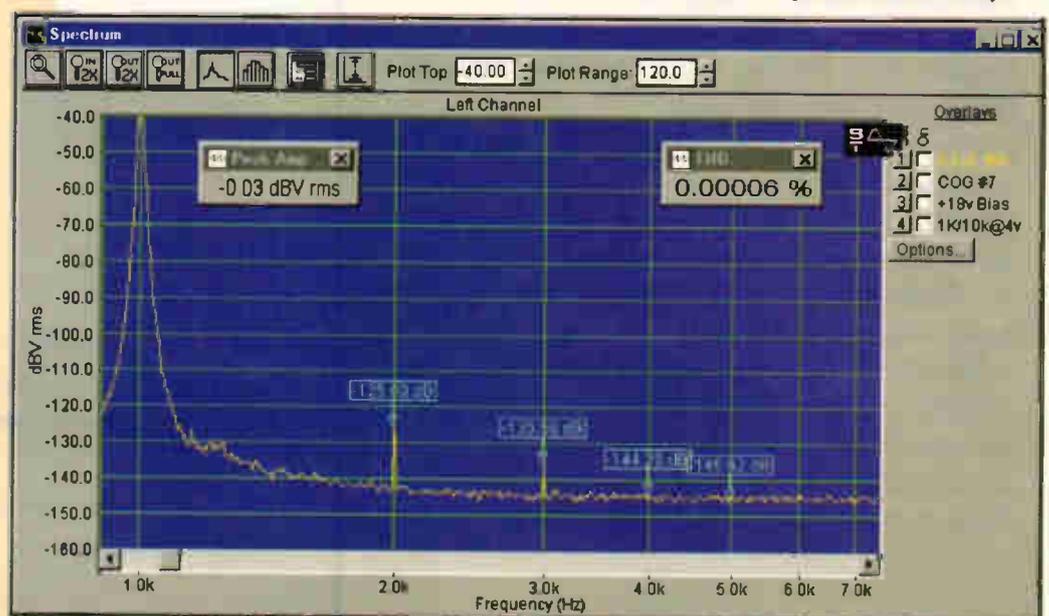

available in acceptable sizes or costs for higher capacitance values. Finding suitable low distortion 0.1 $\mu$ F and 1 $\mu$ F capacitors proved almost impossible. High 'k' BX, X7R, W5R and Z5U capacitors produce far too much distortion for our needs.<sup>1</sup>


Multi-layer ceramics of 100nF 50 volt manufactured in COG, produce little distortion, with and without DC bias, but are not easily available in small quantities. Fig. 1

### The worst capacitor?

A 100nF ceramic disc capacitor is still available. Having the thinnest possible high-k dielectric it provides the worst possible distortion. Despite this, a number of papers found on the internet choose to use this style on which to base their ceramic capacitor measurements and opinions.<sup>2</sup>

Originally called a 'transcap', it pre-dated all low cost 0.1 $\mu$ F film capacitors by many years. It was developed as the smallest, lowest possible cost capacitor, used in pocket transistor AM radios.

A conventional high 'k' ceramic, re-sintered in a reducing atmosphere, becomes a semi-conducting disc measuring a few Ohms resistance. The outer few surface molecules are re-oxidised when the electrode silver is fired in air, to become the dielectric. If sectioned, you will find a black disc, apparently made from charcoal. Using a high power microscope, you may just see an extremely thin, much lighter coloured dielectric layer covering the outer surfaces.<sup>3</sup>

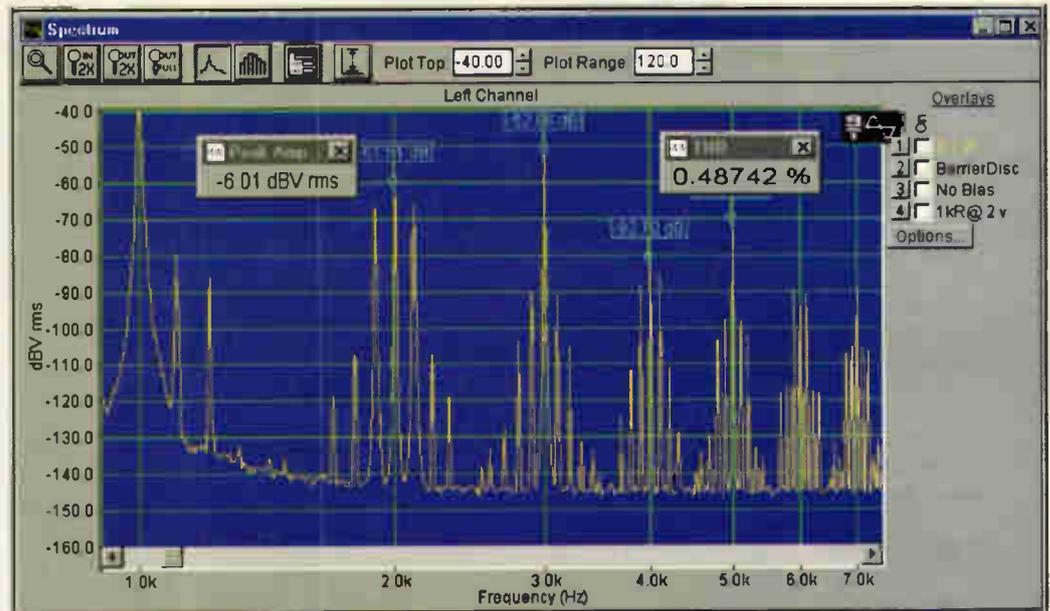

Such devices have no place in any audio system. So take care if offered a small ceramic disc, having significantly greater capacitance than found in conventional disc capacitors.<sup>4</sup> Fig. 2

### Electrolytics

Tantalum or aluminium electrolytic capacitors are available in these values and form the subject of my next article. Meanwhile we will investigate the options available in film capacitors.

Very low distortion foil and film, Polypropylene (PP) and Polyethylene terephthalate (PET) capacitors are available but are large and usually expensive. The lowest

cost, smallest size capacitors, are made with metallised PET.

### Metallised PET capacitors

In the drive, some thirty years ago, to size and cost reduce the 0.1 $\mu$ F capacitor, two problems had to be addressed:

1) First was to produce satisfactory quality, extremely thin metallised PET. In 1978, the Dupont 'Mylar'® capacitor film became available at a thickness of 1.5 microns, some 20 times thinner than human hair.

2) The second was to develop low labour cost methods to wind small capacitor elements. For capacitor makers this was difficult because of the high cost and large numbers of

*Figure 2: The worst distortion of more than 2000 capacitor measurements. The test voltage had to be reduced to two volts AC with no DC bias, to avoid harmonics overloading my soundcard.*

## Metallised film dielectrics

All common film capacitor dielectrics, other than Polystyrene, can be metallised, to produce a negligibly thick electrode. This metallised coating, usually aluminium, is produced by evaporating metal ingots inside a vacuum chamber. The film is stretched taut and passed through the chamber at controlled speed. To prevent overheating, the film passes over refrigerated rollers.

The metallised coating is so thin, it is transparent. Thickness is monitored by measuring resistance, typically a few Ohms per square, of the metallised surface.

PET and PPS films are easily metallised and provide good adhesion to an evaporated aluminium coating. Untreated Polypropylene has a smooth, waxy surface, which inhibits adhesion.

Various pre-treatments have been applied to PP to improve electrode adhesion. These include mechanical roughening and exposure to high voltage ionisation fields. However, a

metallised electrode is often applied to a higher resistance value, i.e. thinner, onto PP than other films.

Contact to the metallised electrode is made by spraying minute metal particles, evaporated inside a high temperature spray gun, onto each end of the capacitor winding. This is known as a 'Schoop' connection. The volume of air needed to propel the metal particles ensures the film surface is only exposed to relatively cool metal and so does not melt.


This 'schoop' metal spray end connection is also used to manufacture some makes of foil and film capacitors and those with double-sided metallised carrier film electrodes. The conductive end spray, short circuits together all turns of a wound capacitor, ensuring minimal self-inductance.

When sufficient 'end spray' thickness has been applied, the capacitor leadwires are attached, usually by soldering or electrical

resistance 'welding.' Properly applied this 'schoop' end spray provides a good connection to the electrodes, able to carry significant current. The extremely thin metallised film electrodes obviously cannot handle high currents. When overloaded, visible electrode 'edge burning' occurs, ultimately leading to an open circuit capacitor.

The resistance of the metallised electrode combined with aluminium's temperature coefficient of 0.0039, results in a non-linear resistance. This may at least partially explain some of the larger third harmonic distortions. One simple indicator of the current carrying ability of the 'schoop' end connection into the electrodes used, can be seen in the peak current ratings claimed for the capacitor. For example a 10nF metallised PET capacitor might be rated for 30v/ $\mu$ sec, foil and PET has a much higher current carrying ability, being rated as high as 1000v/ $\mu$ sec.

Figure 3: Finalised measurement system using two test signals, 100Hz and 1kHz, to measure capacitor intermodulation and harmonic distortion, with and without DC bias voltage. The capacitor under test is mounted directly onto the DC bias buffer network. The red crock clip and screened cable supply the 100Hz signal. All screening case lids must be fitted while measuring distortion.

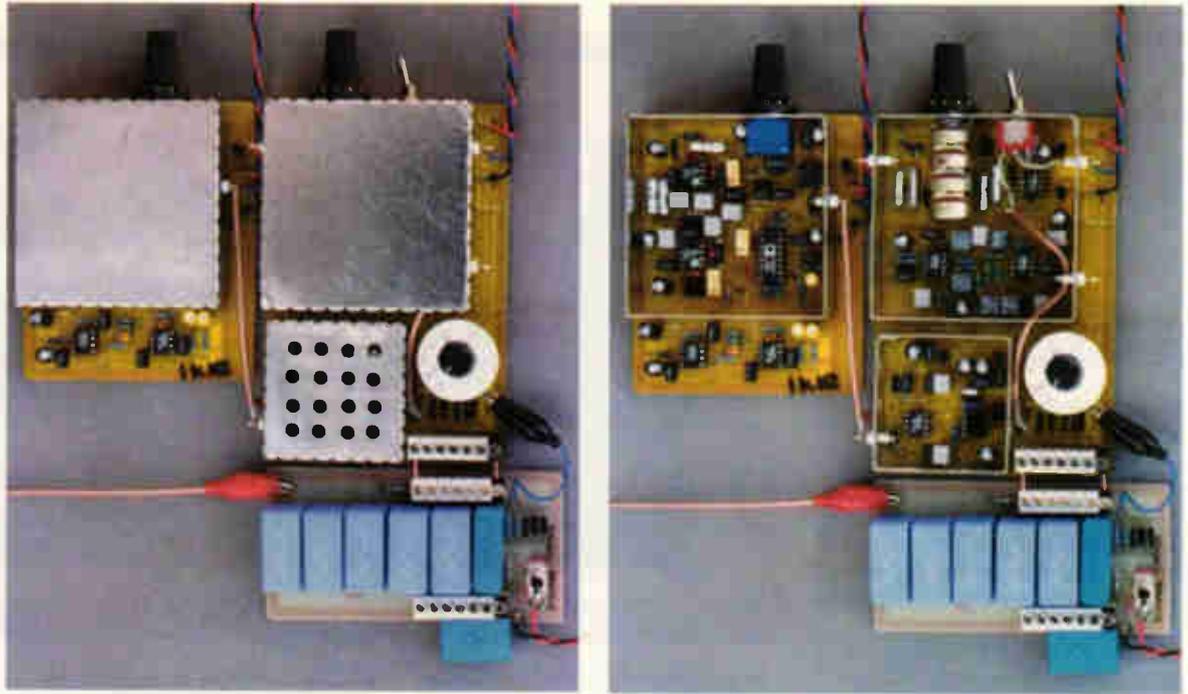

automatic winding machines needed to produce capacitors in volume. The major German capacitor makers were leading these developments. Wima with others, worked to develop intricate machines capable of automatically winding individual small capacitors. The Siemens company, now Epcos, sought a different solution, their so-called 'stacked' capacitor. Despite their name, stacked film capacitors are first wound onto a large diameter wheel, to make a 'mother' capacitor. When all possible

processing stages are complete, this 'mother' is sawn into short lengths, each a discrete capacitor element.<sup>5</sup> During my initial distortion measurements on metallised PET capacitors, I was curious as to whether these two processes would result in different distortion characteristics. Concentrating my measurements on known wound BC Components type 470 and known stacked Epcos capacitors, I did find differences. The stacked film capacitors usually exhibited an increased third harmonic, compared to this wound type. My

initial stocks were too small to be statistically valid, so more capacitors were purchased.

**Wound v Stacked metallised PET**

At this time I measured distortion using only a single pure 1kHz tone and no DC bias. With 4 volts dropped across the capacitor, my equipment noise floor was below -140dB. Loaded with a 0.5% metal film resistor, distortion measured 0.00005%. Similarly the best capacitors typically measured 0.00006%, with second harmonic better than -125dB, third and higher harmonics better than -130dB.

Measuring 25 type 470 capacitors I found three having more than ten times higher distortion. Even harmonics were little changed, but third harmonic increased to -100dB, fifth to -115dB. Measuring another 25 capacitors I found two with high distortion. I set a good/bad limit at -120dB, any harmonic exceeding this level being viewed as bad.

The next step was measuring 25 stacked capacitors and I found most measured as bad. Distortions varied from 0.00034% to 0.0018% and many displayed -90dB third harmonics.

Was this difference genuine or was my sample still not statistically significant? Measuring more capacitors, I found some also having increased second harmonic distortions. I had anticipated finding third harmonic variations but did not understand these second harmonic problems.

PET of course has significant



Figure 4: With no bias, this exceptionally good 0.1µF 63 volt type 470 metallised PET capacitor from BC Components, with magnetic leadwires, measured just 0.00004% distortion. With 18 volts DC bias, the second harmonic increased 22dB from -133.3dB to -111.4dB (distortion increased six times.) Intermodulation products are just visible, either side of 2kHz.

**Figure 5: Distortion measurement of a typical MKS2, with no DC bias measured just 0.00007%. With 18 volts DC bias the second harmonic increased 31dB from -128.3dB to -96.4dB. Intermodulation products and other harmonic levels did not change.**



dielectric absorption, typically 0.5%.<sup>6</sup> Several capacitors, pre-selected as good and very bad distortion, were accurately measured for capacitance and  $\tan\delta$  at 1kHz using my precision bridge, initially unbiased then with 30 volts DC bias. The biggest capacitance change found was less than 0.01% and with  $\tan\delta$  values remaining constant regardless of bias voltage, seemed to rule out any dielectric absorption effects.

Somewhat puzzled, I decided to expand my distortion measurements, changing the measurement stimulus in small steps and varying one test parameter only at a time. I would also look for intermodulation using two test frequencies and explore the affects of change of DC bias voltage. I had no choice but start again, repeating almost 1000 single frequency distortion measurements already saved to disk, both of film and electrolytic capacitors.


#### Revised measurements

To prove my DC bias buffer contributed no distortion, I measured my near perfect  $1\mu\text{F}$  KP capacitor. Using 6 volt test signals at 100Hz and 1kHz and 50 volts DC bias, its distortion measured 0.00006%. This DC bias buffer was then used for all measurements. Fig. 3.


A 'good'  $0.1\mu\text{F}$  63v type 470 wound capacitor,  $\tan\delta$  0.00337, measured similar distortion when tested with no DC bias.

Intermodulation was just visible either side of the second harmonic. With 18 volt DC bias, second harmonic increased by 22dB and distortion to 0.00027%. Fig. 4.

A batch of Wima MKS2 wound capacitors consistently show increased intermodulation products and third and fifth harmonics. Typical no bias distortions measured around 0.0001%. With 18 volt DC bias the

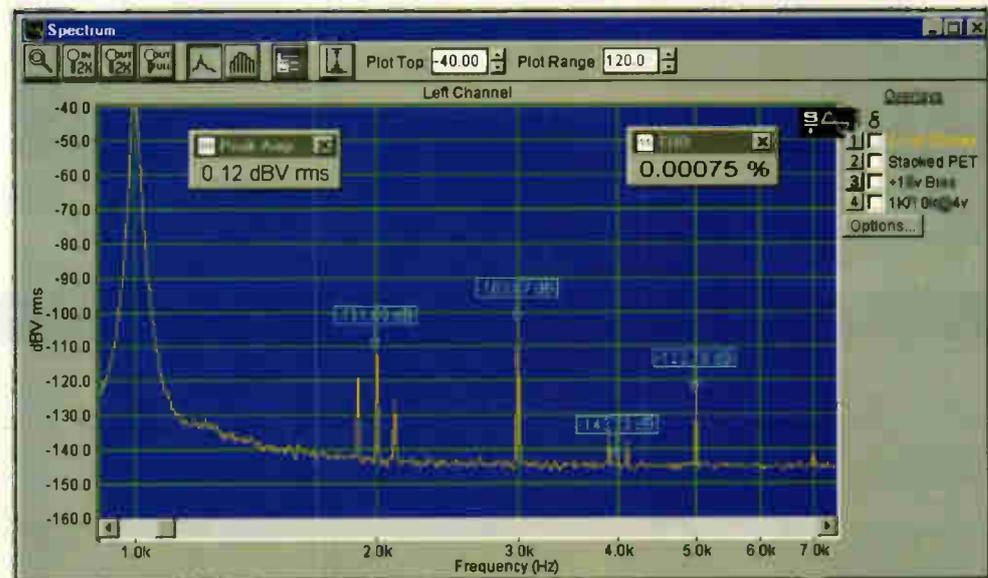

**Figure 6: A  $0.1\mu\text{F}$  100 volt stacked metallised PET, with magnetic leadwires, displays increased odd harmonics and intermodulation components. The second harmonic of this much larger capacitor made with thicker PET, increased less with DC bias, compared to figures 4 and 5.**

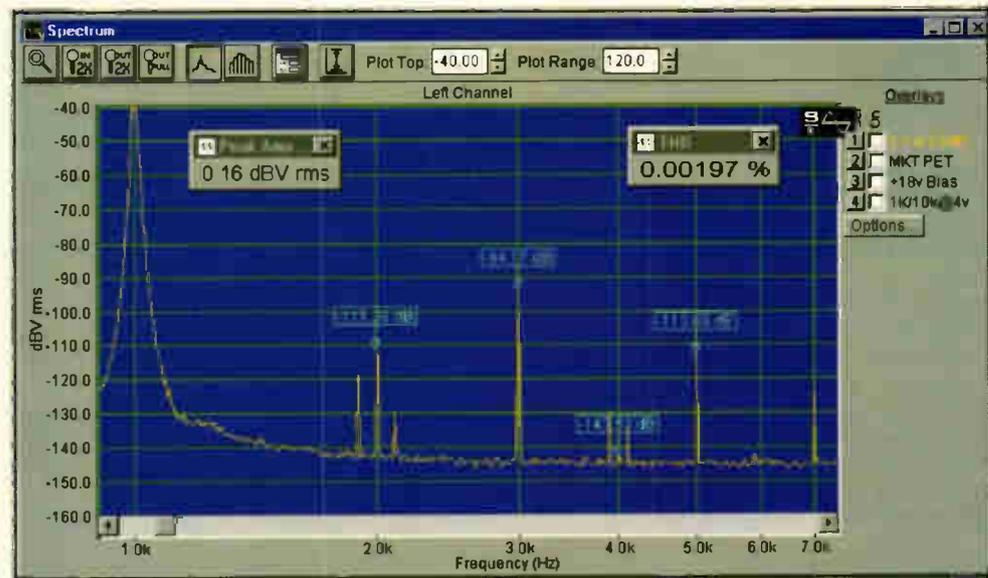

**Figure 7: A different maker's very much smaller, 63 volt stacked metallised PET capacitor with copper lead wires exhibits worse distortions than those shown in figure 6. Notice however a family likeness of distortion components, similar to figure 6 but quite different from figure 4.**

second harmonic increased by 32dB and distortion measured 0.00151%. With a  $\tan\delta$  of 0.00272, this capacitor was dismantled to confirm it was wound construction. Fig. 5

A much bigger, 100 volt rated, uncased stacked capacitor with  $\tan\delta$  0.00352, shows a very high third harmonic level and increased intermodulation products, typical of

the construction. Made using thicker dielectric, its second harmonic increased by 16dB when biased with 18 volts. Due to its third harmonic, high distortions were measured with and without bias. Fig. 6

Third and odd harmonics vary with AC test signal, but DC bias from 0 volts to 30 volts, has almost no affect. These enormous changes in second harmonic, tested with and without bias, clearly result from the DC bias, dielectric thickness and dielectric absorption. (see box Dielectric Absorption.)

Uncertain of their construction, I ordered just ten MKT capacitors (Farnell 814-192) and all behaved similarly. Exceptionally high distortion with and without bias, dominated by the near -90dB third and -113dB fifth harmonics. With  $\tan\delta$  0.00371, this capacitor was dismantled to confirm it was stacked construction. Fig. 7

With such large variations in harmonic distortion, it seemed all small metallised PET capacitors should be distortion tested, to avoid building obviously 'bad' capacitors into the signal paths of audio equipment

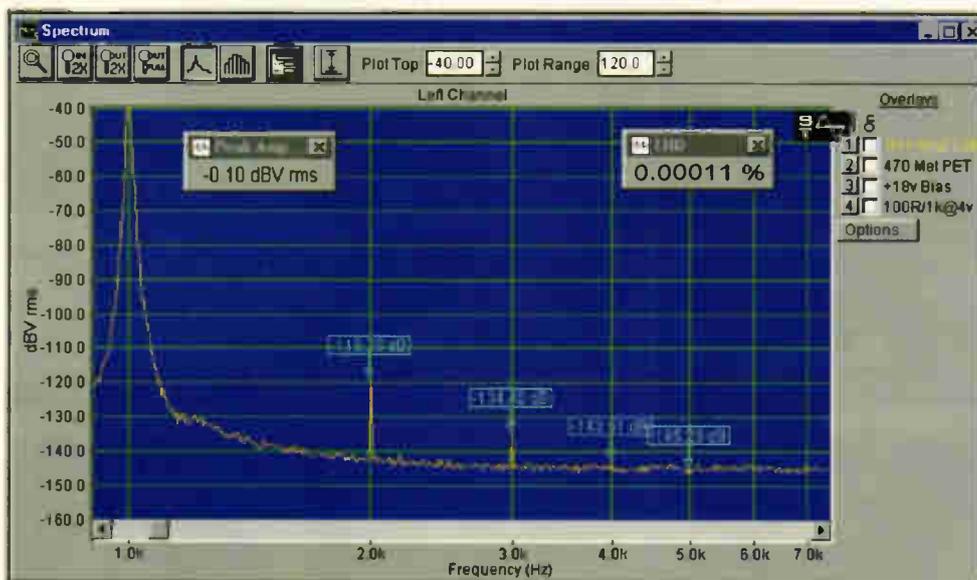


Figure 8: The first of two plots which explore the effect an increase in metallised PET film thickness might have on distortions. With no bias, distortion of this 100 volt capacitor measured 0.00006%, second harmonic -126.2dB. With DC bias, second harmonic increased by 7dB and distortion to 0.00011%

## Dielectric Absorption

Two major dielectric characteristics exist, polar and non-polar. By polar I am not referring to an electrolytic capacitor, but to the way the dielectric responds when subject to voltage stress. This stress relates to the voltage gradient across the dielectric and not just the applied voltage. In other words it is stress in volts per micron, which matters.

Non-polar dielectrics, for example vacuum and air, are little affected by voltage stress. Solid dielectrics which behave in a similar fashion are termed 'non-polar'. Most solid dielectrics and insulators however are affected to some extent, increasing roughly in line with their dielectric constant or 'k' value. This 'k' value is the increase in measured capacitance when the chosen dielectric is used to replace a vacuum or more usually, air.

When a dielectric is subject to voltage stress, electrons are attracted towards the positive electrode. The electron spin orbits become distorted creating mechanical stress and a so-called 'space charge' within the dielectric. This mechanical stress produces some heat rise in the dielectric and a power loss, called dielectric loss. Non-polar dielectrics exhibit very small power or dielectric losses. Polar dielectrics are

much more lossy. Having been charged to a voltage, it takes much longer for the electron spin orbits in a polar dielectric to return to their original uncharged state. Polar dielectrics produce easily measured 'dielectric absorption' effects.

Dielectric behaviour with voltage depends on the voltage gradient, in terms of volts/micron as well as on the characteristics of the dielectric. Its effects are more readily apparent with very thin dielectric. The lowest voltage, 50 and 63 volt rated metallised PET film capacitors are often made using 1 micron or thinner film. As will be seen in my next article, the dielectric used to make small low voltage electrolytics is perhaps one hundred times thinner. Consequently we should anticipate increased effects from dielectric absorption.

Foil and film capacitors cannot 'self heal' so must be made using relatively thick dielectric films. As a consequence we find that foil and film PET capacitors can provide low distortion, even when subject to DC bias voltages.

Dielectric absorption is usually measured by fully charging the capacitor for several minutes to a DC voltage, followed by a rapid discharge into a low value resistor for a few seconds. The capacitor is then left to rest for some time

after which any 'recovered' DC voltage is measured. The ratio of recovered voltage to charge voltage is called dielectric absorption.

So how might dielectric absorption affect the distortion produced by a capacitor? Many fanciful descriptions can be found, describing smearing, time delays and compression. My AC capacitance and distortion measurements, simply do not support these claims. The main characteristic I have found, which clearly relates to dielectric absorption, is the magnitude of the second harmonic. This does increase with applied AC or DC voltage stress and especially so with thin materials, having known higher dielectric absorption. For example, the PET (Polyethylene Terephthalate) and PEN (Polyethylene Naphthalate) dielectric films have almost identical characteristics except for dielectric absorption. Comparative distortion measurements with and without DC bias, made on metallised PEN and metallised PET capacitors, show that PEN capacitors do produce much larger second harmonics. The PEN material at 1.2%, has almost three times greater dielectric absorption than PET<sup>6</sup>

### The 1 $\mu$ F problem

To approach our idealised capacitor we need the small size provided by metallised PET, the low distortions found using Polypropylene and low cost. These qualities could be approached using metallised Polycarbonate, but Polycarbonate capacitors have become extremely expensive. With the production of Bayer Makrofol Polycarbonate film having ceased, metallised Polycarbonate capacitors may disappear.

A great many 0.1 $\mu$ F metallised PET capacitors had been measured, without finding clear reasons for their widely differing distortions. Would measurements at 1 $\mu$ F help?

I decided to measure the same make and style, rated at both 63 volt and 100 volt, to explore the D. Self comment that 63 volt capacitors exhibit ten times more distortion than

100 volt.<sup>7</sup> Provided the maximum capacitance possible at these voltages in both case sizes is obtained, dielectric absorption effects related in volts per micron to the differing film thickness used should be observed. It seemed probable that the 63 volt capacitor would exhibit increased second harmonic compared to the 100 volt version.

I choose to measure the 470 style capacitors, because 0.47 $\mu$ F at 100 volt and 1 $\mu$ F at 63 volt, were the maximum capacitances available in the case size. I soldered together several pairs of 0.47 $\mu$ F to produce near 1 $\mu$ F 100 volt capacitors.

Measured within a few minutes of each other, with no bias voltage, the 63 volt and 100 volt capacitors measured almost identically, with distortion at 0.00007% and 0.00006% respectively.

Re-measured with 18 volt DC bias, the third and higher harmonics were unchanged but second harmonic levels increased for both voltage ratings. Second harmonic for the 63 volt capacitors increased by +12.5dB, the 100 volt capacitors by +7dB, giving measured distortions of 0.00024% and 0.00011% respectively. Fig. 8 These figures equate well with the expected differences in film

### Technical Support

Interested readers are free to build a system for personal use or educational use in schools and colleges. Commercial users and replicators should first contact the author.

A professionally produced set of three FR4 printed circuit boards, with solder resist and legends, for the 1kHz signal generator, the output buffer amplifier/notch filter/pre-amplifier and the DC bias buffer network, comprising a 'with DC bias, single frequency, distortion test system'. Complete with component parts lists and assembly notes, the set of three boards costs £32.50.

Post/packing to UK address £2.50. Post/packing to EU address £3.50, rest of world £5.50.

As a service to Non-UK readers, but only if ordered together with the above PCBs, I can now supply one four gang potentiometer with each set of boards, re-tinned and tested, for an additional £5.00 inclusive of postage.

Falcon Electronics (EW September) has these potentiometers in stock.

Postal Orders or Cheques, for pounds sterling only, to C. Bateman, 'Nimrod' New Road, ACLE, Norfolk NR13 3BD England.



Figure 9: Distortion of the 63 volt capacitor, same make comparison with figure 8. With no bias, distortion measured just 0.00007% with second harmonic at -124.9dB. With DC bias, second harmonic increased by 12.5dB. At 0.00024%, distortion is double that of the 100 volt capacitors.

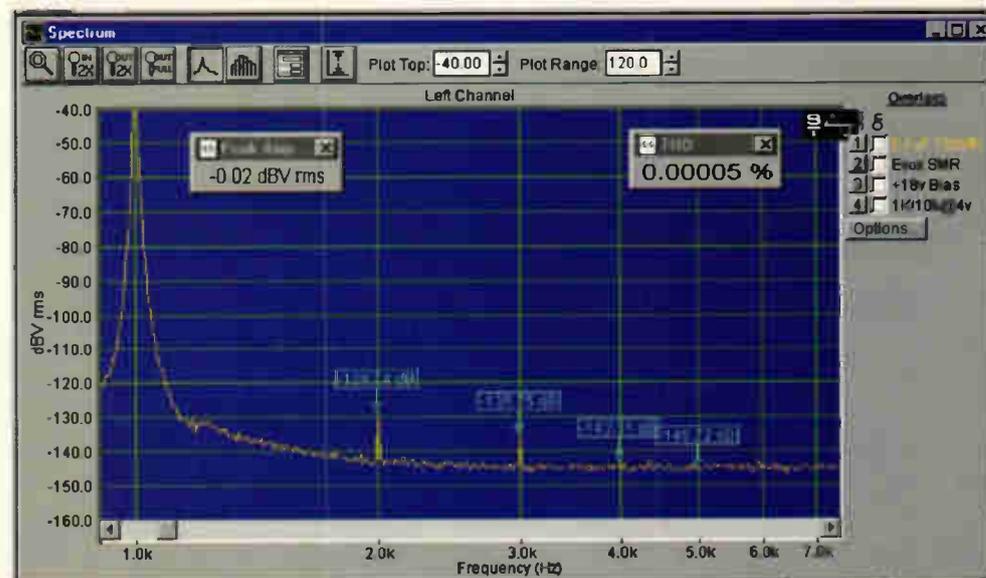


Figure 10: This 0.1 $\mu$ F 100 volt Evox Rifa SMR capacitor, provides a superb low distortion performance with or without DC bias, even as high as 30 volts and no intermodulation products were seen.

thickness and confirmed the effect dielectric absorption has on second harmonic distortion. (see box Dielectric Absorption.) Some factor other than rated voltage, must account for Douglas's reported observation. **Fig. 9**

Further measurements on 1µF metallised PET capacitors, using 25 pieces of the wound type 470, and a similar quantity of stacked film capacitors, revealed nothing new. Distortion patterns established by the smaller capacitors were being repeated. I also had 10 pieces of wound capacitors type 370, dated 1995. These produced harmonic

levels with and without bias remarkably similar to those measured on the MKS2 types.

**Possible mechanisms**

These tests clearly illustrate how audible problems can exist using metallised PET capacitors in low distortion audio. I now sympathise with listeners who complain about amplifier sounds, when using metallised PET capacitors.

Lacking the facility to assemble test capacitors using known differences in materials and processes, I can only speculate as to possible reasons for the different third harmonic distortion

levels I found. These may result from differences in manufacture of the basic film or the vacuum deposition of the metallised electrodes, processes that vary from maker to maker.

It might even be as simple as the electrode metallisation thickness used. Perhaps thickness gives the wrong impression, this aluminium coating is so thin, like mirror sunglass lenses, it is quite transparent. Its thickness is measured in Ohms/square, typically some 2 to 4 Ohms.

One convenient explanation for these differences might be the use of copper versus magnetic leadwires. Not so, the lowest distortion, type 470 metallised PET capacitors tested use magnetic leads whilst the worst distortion stacked types used copper.

More likely are differences in the metal compositions and spray application methods used, to produce the 'schoop' end connections.<sup>5</sup> Aluminium metallised electrode has an electro-chemical potential of +1.66 volt, magnetic leads +0.44 volt, copper wires -0.337 volt. For the 'schoop' connection, a variety of other metals are used, having intermediate, mostly positive potentials. Possible 'Seebeck' effects should not be ignored. (see box Metallised film dielectrics.)


**Intermodulation distortion**

From many measurements using AC voltages from 0.5 to 6 volts, intermodulation products are produced in metallised PET capacitors according to the level of third harmonic the capacitor produces. For example a 'bad' capacitor exhibits intermodulation when subject to much less than 1 volt AC. A capacitor developing smaller third harmonic, shows no visible intermodulation until its AC voltage exceeds 3 volts. **Fig. 4**

The best metallised PET capacitors produced almost no distortion with no DC bias, but when used to block DC, second harmonic distortion increased rapidly with increasing DC bias voltage. Depending on circuit arrangements, many capacitors could produce audible distortions. Perhaps this should not surprise us.

Audiophiles have claimed to be able to 'hear' PET capacitors for many years.

I believe that for 0.1µF to 1µF values, metallised PET capacitors should first be distortion tested. Because of their rapid increase in second harmonic with DC bias, they should not be used with significant DC bias, relative to their rated voltage, in high quality audio equipment. Having so far failed to find a physically small, economic,

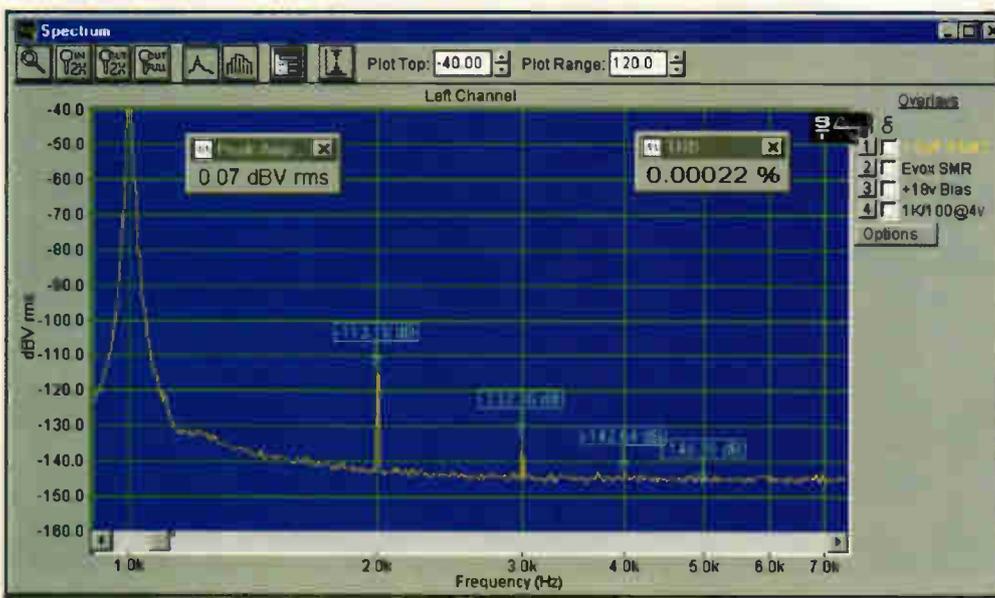

**Figure 11:** Little larger than their 0.1µF, this 1.0µF 63 volt SMR capacitor from Evox Rifa behaves impeccably with or without DC bias up to 10 volts. With increased DC bias its second harmonic does increase but no intermodulation products were seen.



**Figure 12:** If you have room for a capacitor with 22mm lead spacing, this 1.0µF 250 volt Epcos with DC bias voltage, distorts less than most capacitors with no bias.

low distortion solution, is one possible?

### Polyphenylene Sulphide

A much better but little used, slightly more expensive dielectric has been available for many years.<sup>8</sup> It is available metallised down to 1.2 microns and with a 'k' of 3, it provides capacitors slightly larger than metallised PET.<sup>6</sup> It has many other benefits. Usable to 125°C, it provides a near flat temperature coefficient and  $\tan\delta$  slightly higher than metallised Polypropylene. It has a small dielectric absorption of 0.05%, better than Polycarbonate and ten times better than PET.

Like Polycarbonate, Polystyrene and COG ceramic, it provides superb long-term capacitance stability, changing only 0.3% maximum in 2 years. It seems Polyphenylene Sulphide (PPS) should provide acceptable size, low distortion capacitors.

I used 0.1 $\mu$ F 50 volt, 5mm centres Evox Rifa SMR metallised PPS capacitors, in my  $\tan\delta$  meter assemblies. Measurements of 25 pieces displayed extremely low distortion. This stock was purchased from RS, who has dropped the product from its catalogues, so I sought another stockist. The Farnell web site recently listed a small selection of Evox Rifa Polyphenylene Sulphide capacitors. Maximum stock value in 5mm lead spacing is 10nF, with up to 1 $\mu$ F at 63 volt in 10mm centres and at 100 volt in 15mm. The largest value, 3.3 $\mu$ F at 63 volt, has 15mm centres.

The 0.1 $\mu$ F 100 volt SMR produced superb results with and without DC bias voltage. Fig. 10 The 1 $\mu$ F 63 volt produced superb results if biased to less than 10 volts but with increasing bias, second harmonic distortion increases. The larger 1 $\mu$ F 100 volt should be less sensitive. Fig. 11 Both SMR types tested have small case size and 10mm lead spacing.

### Bigger the better?

Another new Farnell line is Polypropylene capacitors from Epcos (Siemens). The second harmonic of the 1 $\mu$ F 5% 250v B32653, with 22mm centres, changes little with DC bias up to 30 volts, distortion is then 0.0008%, a superb performance. Fig. 12 The 0.1 $\mu$ F 5% 400v 15mm centres B32652, measured 0.0005% with 30 volts DC bias. Fig. 13 Distortions from these 0.1 $\mu$ F and 1 $\mu$ F Epcos capacitors were not bettered by any similar sized capacitor I tested. With double the PCB footprint of the SMR types they may not fit your space. No

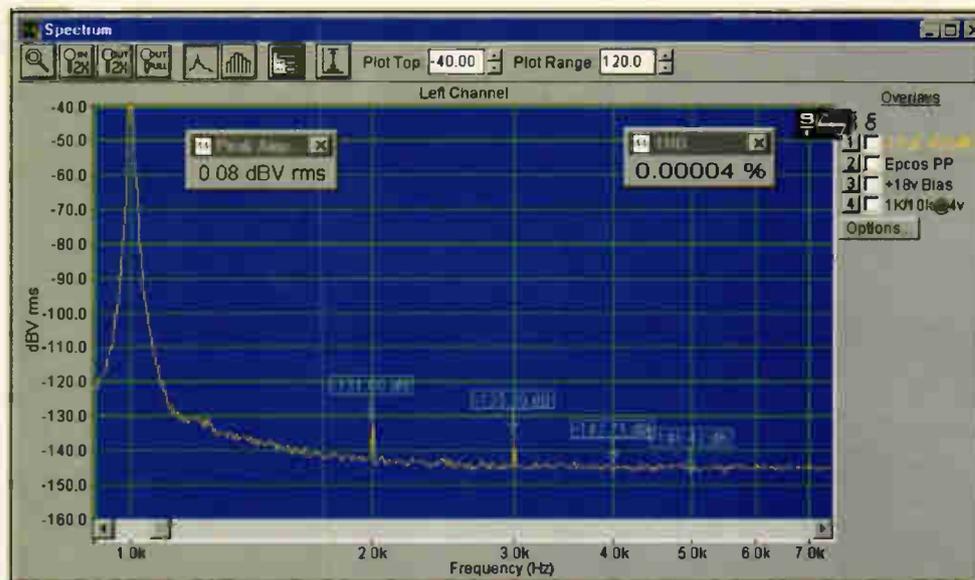


Figure 13: As good as Polystyrene? Distortions from this Epcos 15mm lead spacing 0.1 $\mu$ F 400 volt capacitor barely change even with 30 volts DC bias.

doubt these new lines will appear in the Farnell catalogue.

### Maintaining designed performance

Having measured several hundred metallised PET capacitors, I found many with extremely low distortions if measured without DC bias. I also found far too many showing very bad distortions, both DC biased and unbiased, yet metallised PET capacitors continue to be used in the signal paths of high quality audio amplifier designs.

To ensure the claimed performance of a published audio circuit can be repeated, the designer should declare the make, model and rated voltages of the capacitors. Simply stating ceramic, film etc. is totally unacceptable. These tests illustrate how a capacitor with an acceptable single frequency distortion test, can produce significant intermodulation on audio when presented with multiple frequencies.

Many years ago Ivor Brown presented the case that amplifier tests should comprise three test signals. This seems to have been completely ignored, at least in EW amplifier design articles.<sup>9</sup> Single tone 1kHz amplifier harmonic distortion tests ignore distortions caused by the rising impedance of capacitors at low frequencies. It is now clear that large amplitude bass notes and drum beats in music can result in peculiar intermodulation distortions, in an otherwise apparently good amplifier.

For my part I shall disregard any published audio designs which do not

report low frequency intermodulation distortion claims or low frequency harmonic distortion results, especially if the capacitors used are not properly chosen and adequately defined.

In my next article we introduce that most complex of capacitors, the electrolytic, then explore which produces the least distortion at 1 $\mu$ F, a metallised film or an electrolytic capacitor. ■

Some of the illustrations in last month's article were accidentally reduced too much, resulting in some of the text bordering on being illegible. Those diagrams are repeated over the next pages in larger form. Apologies.

### References.

1. Capacitor Sounds parts 1,2,3 C. Bateman EW July, September, October 2002
2. Picking Capacitors. W. Jung, R. Marsh Audio Magazine Feb/March 1980.
3. Barrier Layer Dielectrics. International Conference on Components. June 1961.
4. Decoupling Ceramic Disc 0.1mF 50 volt Maplin part BX03D
5. Understanding capacitors - Film. C. Bateman EW May 1998 p.391
6. Film Capacitors 2000. Evox Rifa AB., Kalmar, Sweden.
7. Precision Preamplifier '96. D. Self EW July/August 96 p.545
8. Capacitor Resistor Technology Symposium 1987 The Components Technology Institute.
9. Trial by three tones, I. Brown. EW Feb 91 page 131

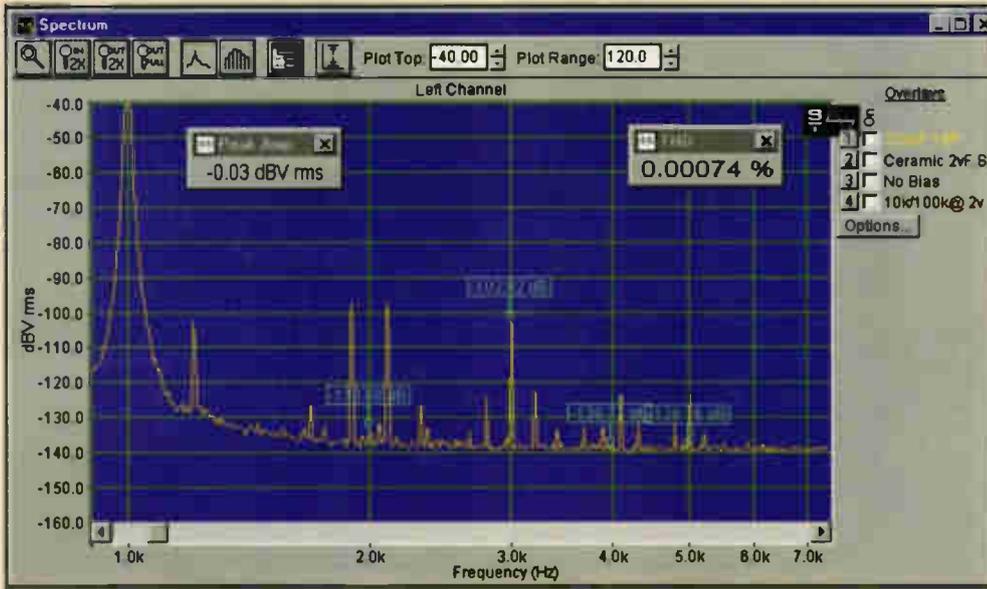


Figure 1: Y5P is a medium 'K' class 2 ceramic. Tested with two signals, 100Hz and 1kHz at 2 volts amplitude, with no bias network, it produces many new intermodulation distortion frequencies.


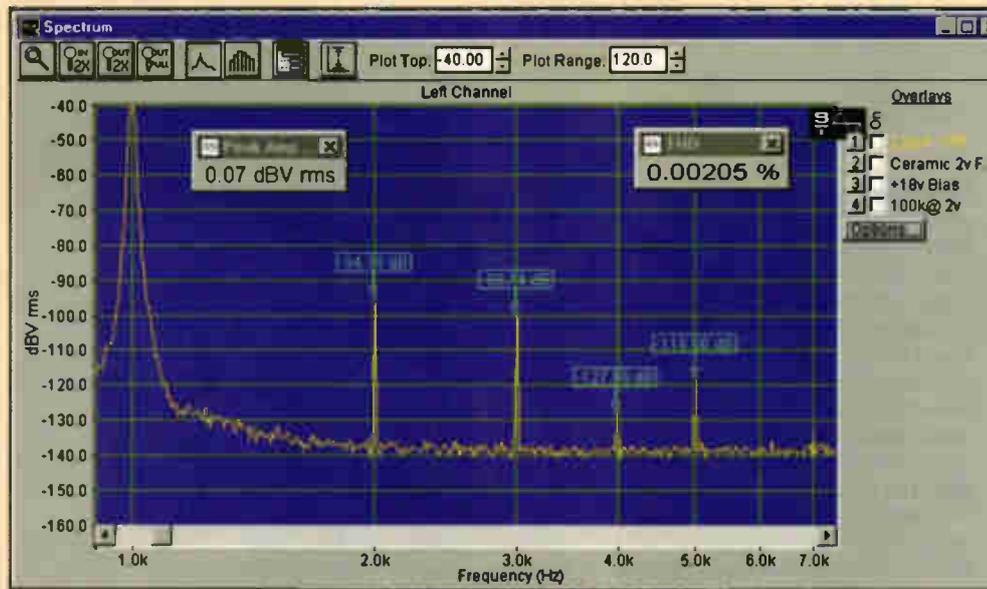


Figure 2: The figure 1 capacitor tested using 1kHz only with 18 volt DC bias. Compared to its 0 volt bias test, second harmonic has increased 23dB, a 14 times distortion increase.

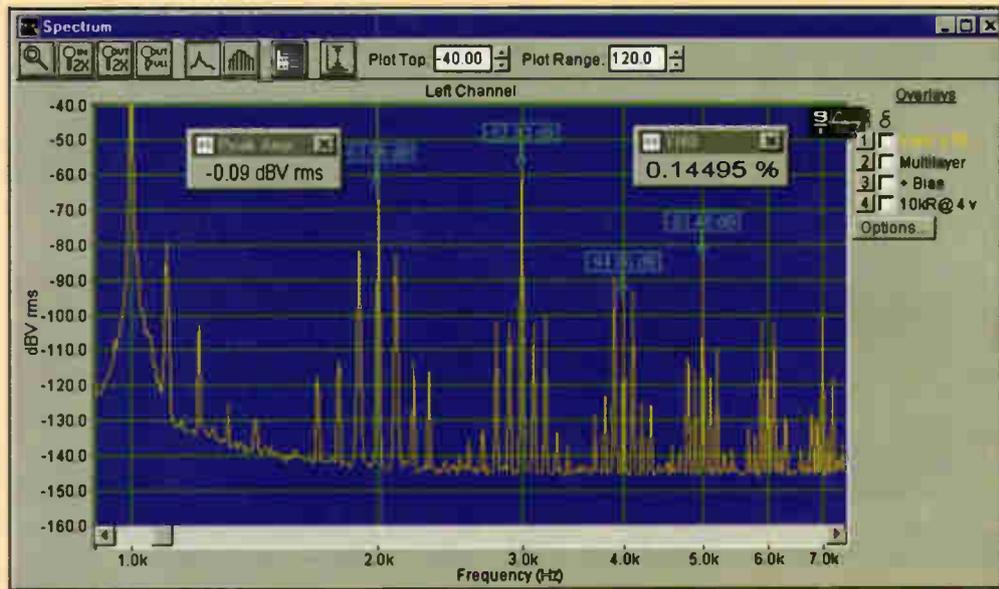

Figure 5: Distortion measurement of a Class 1 ceramic using 100Hz and 1kHz signals at 4 volts and 18 volt DC bias. With no bias this tiny 10nF 50 volt COG multilayer capacitor measured just 0.00006%. Second harmonic was -128.5dB, the other levels remained as shown.

**Figure 6:** A Class 2 X7R 10nF capacitor from the same maker as figure 5 and tested the same. This test dramatically shows the impact an increase in both  $\tan\delta$  and dielectric absorption have on capacitor distortions.



**Figure 7:** This now discontinued Philips extended foil/Polystyrene 1% axial lead capacitor, with 4 volt signals and 18 volt DC bias, shows negligible distortion. With test signals increased to 6 volt and DC bias to 30 volt second harmonic increased less than 4dB and distortion to 0.00007%.

There was no visible intermodulation.



**Figure 8:** The makers replacement extended foil/Polypropylene shows the same 0.00005% distortion but second harmonic is 1dB worse. With test signals increased to 6 volts and DC bias to 30 volts second harmonic increased just over 5dB, distortion to 0.00008%. Again, no visible intermodulation.





Figure 9: The small Wima FKP2 foil/Polypropylene capacitor shows similar performance except for 2dB increased second harmonic. Distortion just 0.00008% with 6 volts stimulus and 30 volts DC bias.

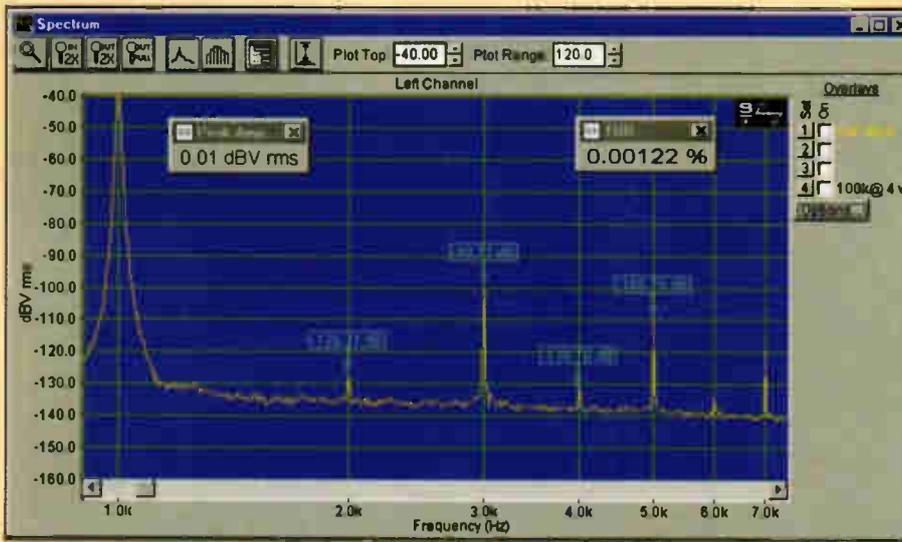


Figure 10: Despite cleaning and re-tinning its oxidised lead out wires, this 1nF Mica capacitor, tested using 1kHz only at 4 volts and no bias, clearly has an internal non-ohmic connection problem.

Figure 11: Tested with no bias, this 0.1µF MKS2 metallised PET capacitor measured 0.00016% with clearly visible intermodulation products. With 1B volts DC bias, the second harmonic increased dramatically, from -119.0dB to -92.9dB and harmonic distortion to 0.00225%.


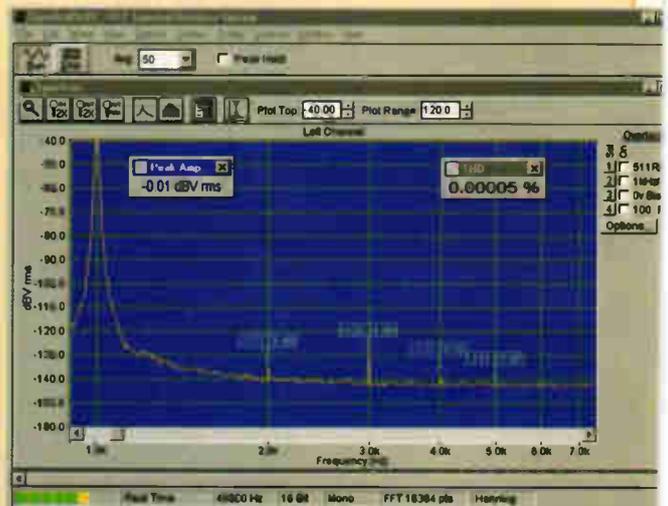


Figure 12: The Plus232 software shows a green then yellow signal strength meter, bottom left, changing dramatically to red at the soundcard overload level. My 'standard' measurement settings can be seen. Loaded with a 511Ω resistor, all harmonics are well below 0.5 ppm distortion.
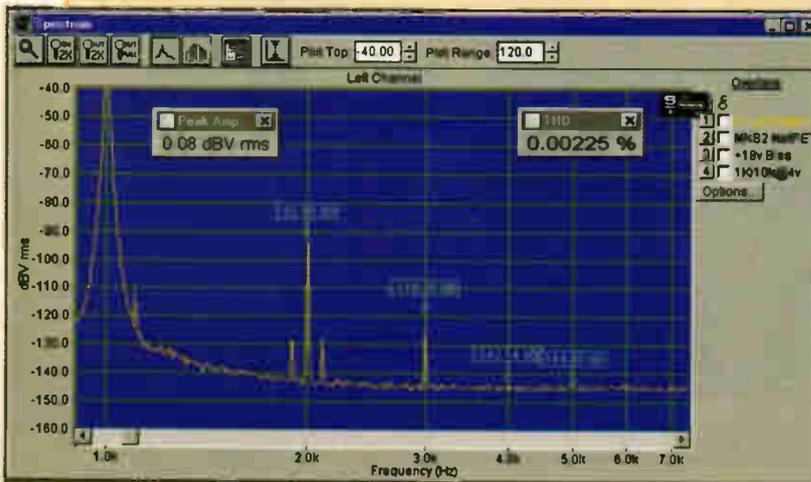
# RADIO MODEMS WIRELESS CCTV RADIO MODULES



**No Licence**

**Range up  
to 20Km**

**Data Rates  
up to  
50Kbps**

[www.radiotelemetry.co.uk](http://www.radiotelemetry.co.uk)

**Warwick Wireless Ltd**

The Manor, Aston Flamville, LE10 3AQ

Tel: +44 (0) 1455 233616

Fax: +44 (0) 1455 233179

**SMALL SELECTION ONLY LISTED – EXPORT TRADE AND  
QUANTITY DISCOUNTS – RING US FOR YOUR  
REQUIREMENTS WHICH MAY BE IN STOCK**

**Ring for Latest Reduced Prices on this advert**

## EXAMPLES OF SPECIAL OFFERS

GOVERNMENT INTENSIFIER NIGHT SIGHTS tested £300 each  
MARCONI TF2019A SIGNAL GENERATOR AM/FM 80kcs-1040  
MCS, off the stack as come and seen untested £190 – or tested  
basic working £300 – or normal Johns Radio workshop test with  
warranty £380. All supplied with instruction book – qty available.

TEK 2445A OSCILLOSCOPE – 4 CH – 150 MCS with instruction  
book, off the stack as come and seen untested £250 each or  
tested basic working £350 – Johns Radio workshop test with  
warranty plus two probes and instruction book £400

TEK 2465-2465A-2465B etc available

RACAL DANA 1992 COUNTERS 1.3GHZ tested from £250

RACAL DANA 1999 COUNTERS 2.6GHZ tested from £400

H.P. 53131A COUNTERS 3.0GHZ tested from £750

BENCH + RACK POWER SUPPLIES large range qty from £10

H.P. POWER UNITS 66311B-66312A-66309D in large qties from  
£250

H.P. 8922 RADIO TEST SETS TYPE G-H-M-M010 with HP83220 A  
OR E GSM CONVERTOR from £500-£1,000 options available  
including Spectrum Anz. quantity in stock.

Most previous advertised items available in stock.

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS, PRICE IS EX WORKS. SAE  
FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS,  
AVAILABILITY OR PRICE CHANGE. VAT AND CARRIAGE EXTRA. ITEMS MARKED TESTED  
HAVE 30 DAY WARRANTY. WANTED: TEST EQUIPMENT-VALVES-PLUGS AND SOCKETS-  
SYNCHROS-TRANSMITTING AND RECEIVING EQUIPMENT ETC.

**Johns Radio, Whitehall Works, 84 Whitehall Road East,  
Birkenshaw, Bradford BD11 2ER.  
Tel: (01274) 684007. Fax: 651160**

**A QUANTUM LEAP IN  
EMBEDDED CONTROLLERS**

# Quick FIRE

**SUPERCONTROLLERS**

**Our range provides:-**

- **The fastest 68000 based  
Core up to 66 Mhz.**
- **Extensive I/O:- Serial,  
IrDA, SPI, I<sup>2</sup>C, Analogue,  
Timers/Counters, RTC, etc.**
- **Large Memory Capacity:-  
Flash, SRAM, DRAM.**
- **Supports:-  
Mono & Colour LCD's,  
Touch Panels & Keypads,  
Very Low Power.**

**ALSO LOW COST**

## DEVELOPMENT

- **Target easily & quickly.**
- **Full ANSI 'C' compiler, assembler  
& linker all Windows32 based.**
- **Source Level Debug.**
- **Full Driver Support with  
Libraries.**
- **Real Time Multitasking OS with  
a free run time licence.**
- **Free Unlimited email support.**

[www.cms.uk.com](http://www.cms.uk.com)

see our web site for full details

**CAMBRIDGE MICROPROCESSOR SYSTEMS LTD**



Unit 17-18 Zone 'D' Chelmsford Rd. Ind. Est.  
Great Dunmow, Essex CM6 1XG

Telephone: **01371 875644**

email: [sales@cms.uk.com](mailto:sales@cms.uk.com)

# RF Auto-transformers - Transmission Line Devices modelled using SPICE

**Nic Hamilton (G4TXG) proposes an improved model for the small-signal RF auto-transformer with a ferrite core and illustrates it by building a SPICE model for a typical small-signal RF transformer.**

The usual model for RF transformers is the same as the model used for low frequencies. Although the model is fine for 50 and 60Hz, it provides inaccurate results at RF and offers no enlightenment on the way the transformer works. I'll start by putting the transmission line into the transmission line transformer and modelling the turns.

I have a PC based on a P2 233MHz processor and this is now slow by modern standards, yet it can run a SPICE simulation of the frequency response of a circuit with hundreds of components in a reasonable time. I am also interested in RF. There are plenty of models around for surface mounted transistors and most passive components, but many circuits use transformers, and when I take a twin-hole 'Balun' core (also known as pig-nose, dual-

aperture, double-aperture or binocular) and thread through a few turns of wire, how do I model it, and how do I use the model to optimise the transformer design? This is not just an idle curiosity: RF transformers appear in baluns, hybrid couplers, mixers, low-noise amplifiers, wide-band data circuits and switched-mode power supplies. Measurements show that Balun cores give a wider bandwidth than similar transformers wound on toroids and that 'monofilar' RF auto-transformers give a wider bandwidth than similar transformers using multi-filar windings with defined impedances<sup>1</sup>.

### Why use an auto-transformer?

RF auto-transformers are usually used as impedance matching devices. Impedance matching can also be achieved using networks containing capacitors and inductors, transmission lines, resistors, or a mixture of these. The transformer's main advantage is that it works over a wider bandwidth with less loss than the other options. Impedance matching has two effects. It minimises the transmission loss (can give insertion gain), and it maximises the return loss (minimises VSWR).

The transmission loss is usually the more important of the two, but consider the following illustration. Connecting 50Ω coaxial cable to 75Ω cable in an otherwise matched system will cause a 1.5:1 VSWR and a transmission loss. Ask most non-specialist engineers in the street for an estimate of this loss and the most frequent answer is 3dB, but in fact the loss is only 0.177dB. Therefore, using a matching transformer in this circuit could give an insertion gain of 0.177dB. However, the loss of the transformer is likely to be 0.2dB anyway, so there would be little point in using a transformer to minimise insertion loss.

But, if the 50Ω to 75Ω cable join occurs in a long run that connects to a TV, and if the source and load impedances are not perfectly matched to the cables, ghosting could occur on the picture due to the signal reflected from the join. A pair of resistors in an L configuration could be used to achieve a perfect broadband match, but the additional loss of the resistor network would be almost 6dB. In this case, the use of an auto-transformer would be justified.

### What is the 'usual' auto-transformer model?

Figure 1 shows the lumped element equivalent circuit of an impedance matching transformer. In this model, the source impedance  $R_S$  and load impedance  $R_L$  are matched by a perfect transformer with an appropriate turns ratio. Imperfections associated with this transformer are present in both the primary and the secondary windings, but for convenience, are collected on the primary side of the transformer.  $L_P$  is the inductance of the primary winding, and  $R_P$  is the associated core loss.  $L_L$  is the leakage inductance representing the imperfect coupling of the primary and secondary windings, and  $R_W$  is the winding

Fig. 1. Lumped equivalent circuit of an impedance matching transformer

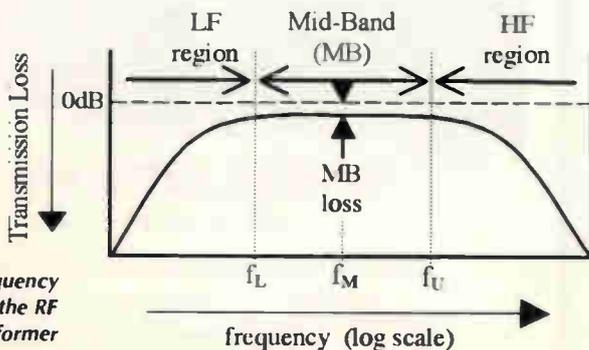
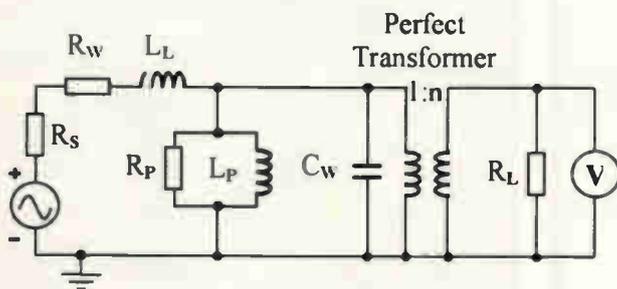


Fig. 2. Frequency response of the RF transformer

resistance.  $C_w$  is the winding capacitance.

**Figure 2** shows the frequency response that results from this model. The  $L_F$  droop below  $f_L$  is due to the low reactance of  $L_p$  compared with  $R_S$ , the MB attenuation is due to  $R_p$  or  $R_w$ , and the HF droop above  $f_U$  is attributed to the high reactance of  $L_L$  compared to  $R_S$ , or to the low reactance of  $C_w$ .

For a given frequency response,  $f_L$  and  $f_U$  are defined by the transformer's maximum allowable VSWR or insertion loss. Where insertion loss is the prime concern, flatness of the frequency response is important, and  $f_L$  and  $f_U$  may be set at the frequency where the insertion loss rises by 1, 2 or 3dB in excess of the Mid Band loss. But remember that, ultimately, most matching transformers must have an insertion gain to be useful.

**What's wrong with the 'usual' model?**

The primary winding inductance is represented by  $L_p$ , a single lumped inductor. An assumption inherent in all lumped elements is that the current flow into a component is equal to the current flow from it. For  $L_p$ , this is true at DC, and is a reasonable approximation up to  $f_M$ . But at frequencies higher than  $f_M$ , the electrical length of the winding is no longer small compared to a wavelength, and the current flow in the primary winding is no longer uniform in magnitude and phase along the winding's length. This defect, with others, gives the 'usual' model several shortcomings:

- a) The values of the components of the model change with frequency. For example, the winding resistance depends on the skin effect, which is a function of frequency.
- b) Above  $f_U$ , the model's HF attenuation increases continuously as frequency is increased. Real transformers have additional HF pass-bands with a transmission loss only slightly greater than the MB loss.
- c) The 'usual' model's phase response is hopelessly wrong at the high end of the MF region. This can be very important, for example, in modelling amplifiers with transformer feedback.
- d)  $f_U$  depends on  $L_L$ , the leakage inductance. This element, which is so vital to the transformer's performance, is not predictable for the RF transformer.
- e) Impedance matching transformers tend to suffer from increased VSWR near  $f_U$ . A recognised way of curing this is by placing a low value capacitor in parallel with the transformer's low impedance winding. The 'usual' model predicts that a lower value capacitor could be equally well connected in parallel with the high impedance winding. In fact, placing a capacitor there degrades the transformer's performance.

In spite of this, the 'usual' model does have several useful features, which will be retained in the development of the SPICE model.

**Transmission lines: the heart of a better transformer model?**


The 'usual' model fails because it uses a lumped inductor to simulate a winding that is not electrically short compared to a wavelength. The way forward must be to use transmission line theory. Consider an RF transformer with a 2:1 turns ratio consisting of just two turns wound on a large twin-hole core. The winding of this transformer will be two wires lying side by side. The obvious deduction is that a useful starting point for a model would be a parallel wire transmission line of length equal to one turn.

Similarly, a transformer with three turns could be based on three transmission-lines, each representing the characteristic impedance between each possible pair of

turns. A four-turn transformer would have six transmission lines, and an n-turn transformer would have  $n(n-1)/2$  transmission lines. So a model of a transformer with 8 turns could have 28 transmission lines. I tried this model<sup>2</sup>. It was relatively successful, but as the number of turns is increased, the number of transmission lines in the model gets rapidly out of hand. A transformer with 12 turns would have 66 transmission lines. And the 'characteristic impedances' of these transmission lines will be far from equal, and impossible to calculate if the windings are not laid perfectly.

**The basis of the new model**

Instead of modelling each transmission line between each turn, the model I now suggest uses a transmission line to represent the characteristic impedance  $Z_0$  between one turn and the generality of the other turns. These other turns could be considered to be similar in effect to the outer conductor of a coaxial cable as shown in **Fig. 3**.

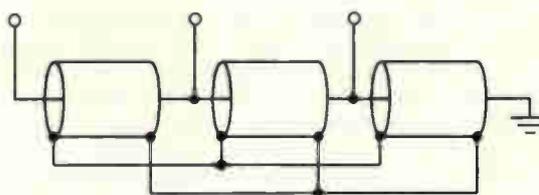

*Fig. 3. Transmission line model of a three turn transformer*


In this model, one transmission line represents one turn. However each turn has two coupling mechanisms. Firstly, each turn is a transmission line causing extra time delay. This forces the current in the individual turns out of phase with each other. Secondly, each turn is coupled to the rest by the traditional 'Faraday' transformer action of the core. This tends to force the phases of the currents in the individual turns together.

There are two ways of modelling transmission lines in SPICE.

- a) Use the SPICE transmission line model. I used SPICE 2G.6, 3F4 and 3F5. While the latter were OK, the implementation of SPICE 2G.6 that I used had a faulty model. The transmission line could be connected to give power gain<sup>2</sup>.
- b) Use a lumped element low pass filter model. This uses inductors and capacitors of sufficiently small value that the HF cut-off frequency is above the highest frequency of interest. This gives models with hundreds of components that take too long to run.


**SPICE transmission lines work as a transformer**

The SPICE transmission line model simulates only the energy flowing in either direction between the conductors of the line - it does not simulate energy flow external to the line. **Fig. 4** shows an equivalent circuit of the half of the SPICE transmission line model that propagates signals from left to right. The other half of the equivalent circuit is a superimposed mirror image of the circuit that allows signals to propagate from right to left. Notice that the input is isolated from the output. This is a form of transformer action.

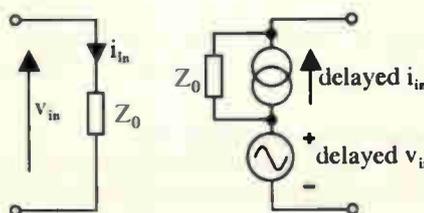


*Fig. 4. The forward transmission element of the SPICE transmission line model.*

Fig. 5. The perfect transformer in the centre can be rotated by 90° leaving the RF performance of the circuit almost unchanged.

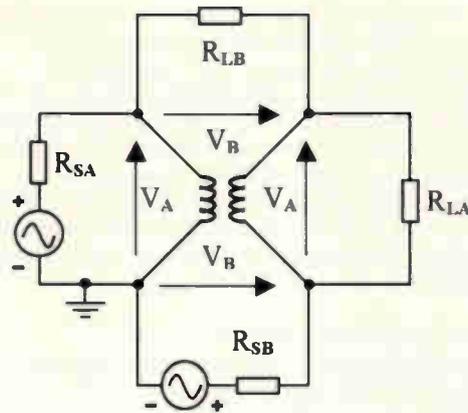

A perfect 1:1 transformer is shown at the centre of Fig. 5. The normal 'Faraday' transformer action propagates energy from left to right. However energy will also propagate from the bottom to the top of Fig. 5 by what Sevick<sup>3</sup> has called the Guanella mode. A little thought shows that the transformer could be rotated by 90°. leaving the circuit's performance unchanged except in the matter of DC connections, and a slight difference in phase delay. This is a very useful technique for visualising and analysing RF transformers. Take Fig. 3. treat the transmission lines as transformers and apply a 90° twist.

Fig. 6. The three turn transmission line transformer with lines represented by 1:1 transformers with a 90° twist.

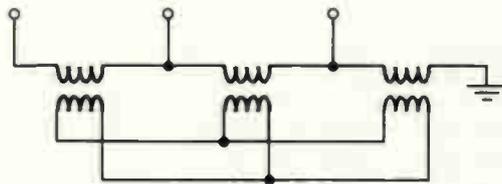

The result is Fig. 6, which illustrates the way the transmission line transformer works; the three 'secondary windings' are wired in parallel. This ensures that each turn or 'primary winding' is coupled to the next.

**Frequency response of the transmission line model**

Examine Fig. 3, and assume that there are no secondary connections, so that the whole transformer operates as a choke. At some frequency, the electrical length of the three turns added together comes to a quarter wavelength. At this frequency, the transformer will present a short-circuit. Furthermore, as this frequency is approached, the transformer becomes increasingly inductive. This presents a practical limit to  $f_U$ , unless the higher frequency passbands are to be exploited.

To model the turns, the winding length must be known, and this depends on the shape and size of the magnetic core. Core shapes are derived from the fundamental relationship between the current flow and the lines of magnetic flux. In the transformer, both the winding length and the magnetic path length must be minimised. This can be achieved in one of two basic ways:


- a) Toroidal flux lines and a radial winding, as in the toroidal core.
- b) Toroidal winding with radial flux lines, as in the pot core.

The double-aperture core can be regarded as a pot core with the sides removed for access, and it is ideal for use as a transformer core.

**Description of the transformers**

I took Siemens-Matsushita B62152A8X30 cores (available from RS, etc.). These double-aperture ferrite cores are

Fig. 7. Measurement of Insertion Loss spectrum of two transformers connected back-to-back  
a) Step-down circuit with low centre impedance  
b) Step-up circuit with high centre impedance

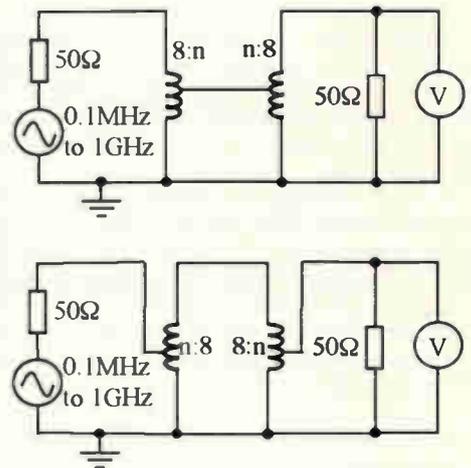

small: 3.6x2.5x2.1mm. and the holes have a diameter of just 0.8mm. I threaded 8 turns on each core. The average DC resistance of the transformers' 8 turns was 0.049Ω, and by comparing this with the resistance of 1 metre of wire, I deduced that the mean winding length was 71mm. Each connection wire was about 6mm long. I wound 10 such auto-transformers, two each with a turns ratio of 8:1, 8:2, 8:3, 8:4 and an 8-turn choke with no tap point.

I connected each pair of transformers at the low impedance side, as shown in Fig. 7a, and measured the insertion loss spectrum. The 8:7, 8:6 and 8:5 transformers were the 8:1, 8:2 and 8:3 transformers with the end connections reversed. I halved the insertion loss of the circuit to give the transmission loss of one transformer. The results are shown in Fig. 8a. I repeated the process, but connecting the high impedance side as shown in Fig. 7b giving the results in Fig. 8b. These are the graphs that the model must reproduce. However, I found later that the high frequency attenuation peak in Fig. 8a was to be due to a spurious resonance of the test jig at 474MHz; it should be ignored.

**Discussion of results**

Note that the high frequency cut-off  $f_U$  of the transformer depends on the transformer's turns ratio. This is a characteristic of all auto-transformers, and is similar to LC matching circuits, where the greater the impedance ratio to be achieved, the narrower the bandwidth of the resulting impedance match.

The SPICE transmission line is specified by two fundamental parameters: the time delay  $t_d$  and the characteristic impedance  $Z_0$  of the line. SPICE works in capitals, so these are entered as  $T_D$  and  $Z_0$ . However, when the transmission line under consideration is short compared to a wavelength, an odd effect occurs, and the effects of  $t_d$  and  $Z_0$  become related as shown in Fig. 9. Conduct the following thought experiment to demonstrate the truth of this. Consider a section of transmission line with  $t_d=1ps$  and  $Z_0=5Ω$  in series with a 50Ω circuit. At low frequencies, the insertion loss of the 5Ω line will be negligible, but the insertion phase shift and group delay will be measurable. Because of the 10:1 VSWR at each end of the 5Ω line, the signal is reflected repeatedly between the ends, and a small amount of signal leaks from the ends at each reflection. The result is that the insertion group delay of the 5Ω 1ps line is about 5ps. Halving  $Z_0$  to 2.5Ω halves the signal leakage, and so doubles the insertion group delay to about 10ps. So, providing the line is very short compared to a wavelength, the insertion group delay is the only important parameter. This delay can be achieved by an infinite number of different values of  $t_d$

and  $Z_0$ . However, of the two parameters,  $t_d$  is much the easier to estimate in a transformer, and the correct high frequency response will depend on selection of the correct value of  $Z_0$ .

**Setting the delay  $t_d$  for the lines**

The time delay  $t_d$  of the line is determined by its electrical length. The physical length of the 8-turn winding in each transformer is about 0.072m. Assuming that the signal travels at the speed of light, the time delay is  $0.072/3 \times 10^8 = 240$ ps, and the delay of each turn is  $240/8$ (30ps). However, the SPICE transmission line has an alternative method of defining the time delay. This is achieved by setting two sub-parameters: F and  $N_L$ . F is the frequency in Hz and  $N_L$  is the normalised electrical length of the transmission line with respect to wavelength in the line at frequency F. It all sounds very complex. But, by using an alternative definition where F is the propagation velocity in metres/second, then  $N_L$  is the physical length of the line in metres. As  $N_L$  is a parameter that must be entered into the model elsewhere, it is attractive to use this definition. So the problem is to find the propagation velocity. The signal travels down the transmission line at

the speed of light only if the transmission line is:

- a) suspended in a vacuum, and the relative permittivity  $\epsilon_r=1$ .
- b) has no magnetic materials nearby, and the relative permeability  $\mu_r=1$ .

( $\epsilon_r$  is also known as the relative dielectric constant. This is a poor name because if  $\epsilon_r > 1$ ,  $\epsilon_r$  is not a constant, it is a function of frequency). If the dielectric is other than air, the signal travels at less than the speed of light by a factor equal to the square root of  $\epsilon_r$ . The more slowly the signal travels, the greater the electrical length of the cable compared to its physical length. Take an example. A coax cable has a polythene dielectric.  $\epsilon_r=2.3$ . In this cable, the electrical length will exceed the physical length by a factor of  $\sqrt{2.3}=1.52$ . This assumes that  $\mu_r=1$ , which, in the case of the RF transformer, it does not. Most of the dielectric between the conductors is air with  $\epsilon_r = 1$ . The other dielectric is the thin 'enamel' coating which insulates the wire, which has  $\epsilon_r=5$ . Let's assume that the overall  $\epsilon_r=1.44$  and  $\mu_r=1$ , and therefore the velocity ratio is 1.2. So  $F=3 \times 10^8/1.2=2.5 \times 10^8$ .  $N_L$ , the length of each turn, is  $0.072/8=0.009$  metres. So  $t_d$ , had it been entered in that format, would have been  $0.009/2.5 \times 10^8=36$ ps.

**Setting  $Z_0$  for the lines**

Assume for a moment that  $Z_0$  is set purely by the geometry of the windings. There is an approximation for finding the  $Z_0$  of a transmission line with two parallel enamelled wires in contact<sup>4</sup>. This indicates that  $Z_0$  will be greater than  $50\Omega$ . There is also an approximation to find  $Z_0$  for a transmission line consisting of a conductor in the centre of a square of four similar conductors<sup>5</sup> carrying an equal share of the return current. This approximation indicates that  $Z_0$  should be less than  $150\Omega$ .

At this point, I have a confession to make. Given a

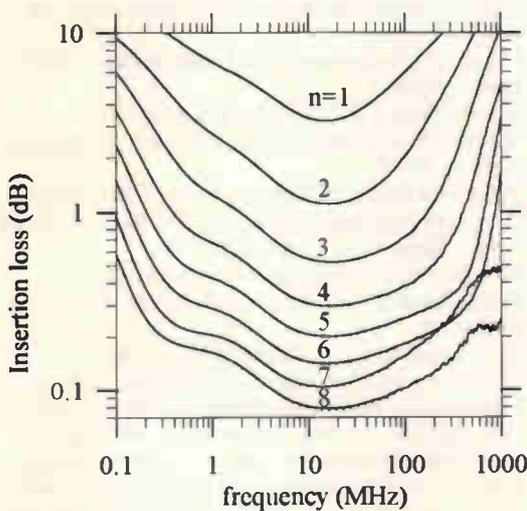
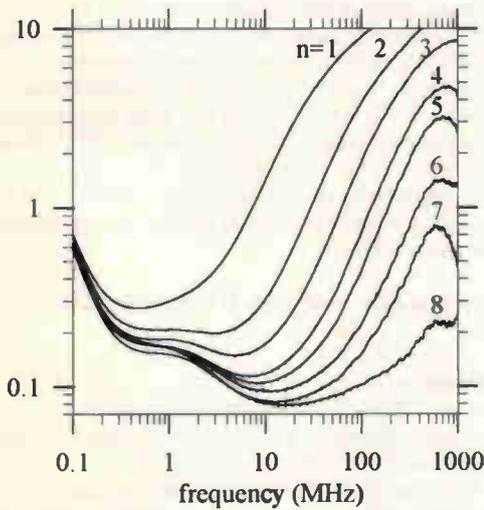


Fig.8. Insertion Loss spectrum of one transformer measured in back-to-back circuits of Fig 7  
 a) Loss of a step down transformer  
 b) Loss of a step up transformer

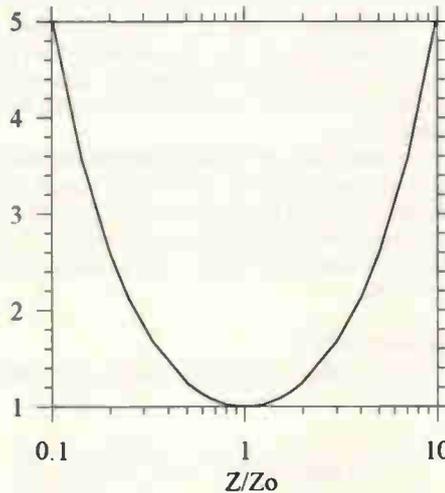


Fig. 9. The additional delay factor of a short transmission line characterised by  $Z$  &  $t_d$ , inserted in a line with characteristic impedance  $Z_0$


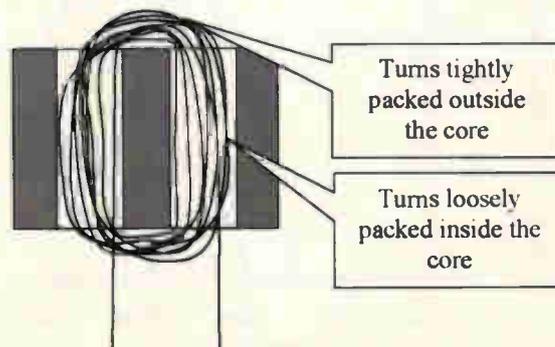


Fig. 10. Eight turns hand wound on a small core. What is  $Z_0$ ?

**Fig. 11. SPICE model of a loss-free auto-transformer. Turns have  $F=2.5E8$   $NL=0.009$   $Z_0=100$  and connection wires have  $F=3.0E8$   $NL=0.006$   $Z_0=150$**

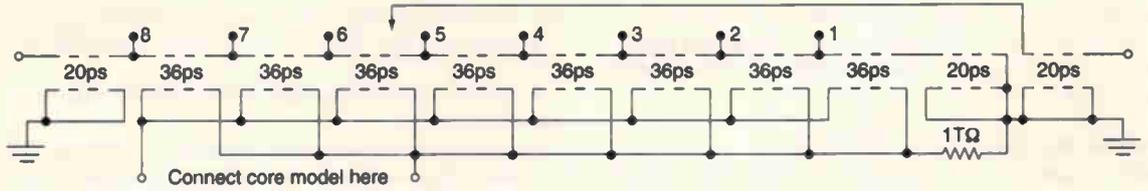

transformer, I cannot think of a way of determining a value for  $Z_0$  for use in the transformer's SPICE model. There are many difficulties:

a) The simple formulae for impedance of multi-wire lines are based on one signal conductor and several return conductors. These return conductors all carry the same voltage and current. This condition does not apply inside a transformer.

b) Fig. 10. shows that  $Z_0$  is not constant over one turn. Even if it were constant, the average impedance would be impossible to calculate.

c) We have had to assume that  $\epsilon_r=1.44$ . The choice of  $\epsilon_r$  also affects  $Z_0$ .

d) For the turns on the outside of the windings, the core must have a significant effect, as ferrite's  $\epsilon_r$  and  $\mu_r$  are both very large.

e) In the model, the transmission line represents both the phase delay of the turn and the mutual coupling of the turn with the transformer core. It is not clear to me how the magnetic coupling should be reflected in the impedance chosen for the transmission lines.


f)  $Z_0$  is a simple real number independent of frequency only if the line has no loss. Although the line has loss, the assumption is one that is frequently made (e.g. 50Ω cable).

However, experiment with different values of  $Z_0$  in the model shows that  $Z_0$  does not have a great effect on the loss predicted by the transformer model. The predicted loss increases as  $Z_0$  increases, and this is more noticeable near 2:1 turns ratio than at very large or very small ratios.  $Z_0=100\Omega$  gives a reasonable fit to the data. This is a good enough value to start from, but does not take into account the winding losses.

The connection wires are modelled as transmission lines. They are 6mm long and in air, so  $F=3 \times 10^8$  and  $NL=0.006$ . The equivalent value of  $t_d$  would be 20ps. The impedance of the connection wires is high because they are a long way from the ground-plane relative to the diameter of the wire. Say 150Ω.

**Results from SPICE**

Fig. 11. shows a simple model of a transformer. The core

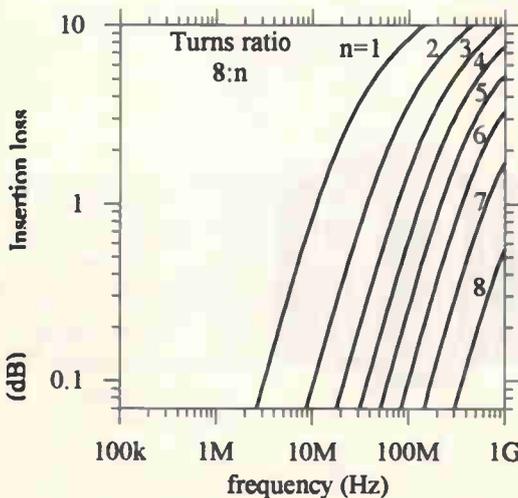

**Fig 12. Simulated insertion loss spectrum of the loss-free step-down transformer in Fig 11**

model will be discussed later, but an ideal core with no loss and an infinite inductance per turn is modelled by leaving the core model connections open-circuit. If two of such transformer models are connected back to back as in Fig 7, the simulator gives Fig. 12, which has a high-frequency performance similar to the measured values shown in Fig 8a.

The simulation results in Fig. 12 are for transformers with no resistive elements, and so represents a theoretical limit to auto-transformer performance. If you want the transformer to work at higher frequencies than Fig. 12, changing the core material is fruitless. You must either shorten the winding length, use filter matching techniques<sup>6</sup>, or abandon the simple auto-transformer and use something more complex with multiple transformers. Examples include a chain of auto-transformers with a smaller impedance ratio, diplexers to route the signal to multiple transformers with different frequency responses, or transformers wound with defined transmission line impedances<sup>7,8</sup>. Sevick<sup>3</sup> has named these types Guanella transformers. Guanella transformers have their optimum performance when the transmission-lines are a quarter of a wavelength long, and this performance is extended to lower frequencies by ferrite loading of the secondary transmission line. ■

*In the next part, I will show how to model the ferrite core loss.*

**References**

1. Alex J. Burwasser: 'Wideband Monofilar Autotransformers' RF Design, 1981 Part 1 Jan/Feb pp38-44 Part 2 March/April pp20-29.
2. N.C. Hamilton, 'RF transformers considered as transmission line devices', Proceedings of IEE Conf. on Radio Receivers and Associated Systems, 1995, pp. 109-113.
3. J Sevick: 'Transmission Line Transformers', (ARRL, 1990, 2nd edn.)
4. John H. Broxon II & Douglas K. Linkhart: 'Twisted-Wire Transmission Lines', RF Design, June 1990, pp 73-75.
5. 'Reference Data for Engineers: Radio, Electronics, Computer, and Communications', (7th Edition) Ed. EC Jordan, Sams, 1985, Chapter 29 p21
6. E.C. Snelling: 'Soft Ferrites: Properties and Applications', (2nd Edition), Butterworth, 1988, pp206-213
7. S.E. London and S.V. Tomashevitch: 'Line Transformers with Fractional Transformation Factor', Telecomms & Radio Engineering, Vol 28/29, April 1974, pp. 129-131. See also Donald A. McClure: 'Broadband Transmission Line Transformer Matches a Wide Range of Impedances' (in 2 Parts), RF Design, Part 1, Feb 1994, pp. 62-66 Part 2, May 1995, pp. 40-49. (Errata: May 1994 p16, Jun 1995 p12, Nov 1995 p18)
8. R. Williams, D.A. Grant and J. Gowar: 'Use of Multielement Transformers in Quasiresonant Converters', IEE Proc. B, Electr. Power Appl., Nov 1993, Vol. 140 No 6, pp 357-361

# LETTERS

## to the editor

Letters to "Electronics World" Highbury Business Communications,  
Anne Boleyn House, 9-13 Ewell Road, Cheam Road, Surrey SM3 8BZ  
e-mail [j.lowe@highburybiz.com](mailto:j.lowe@highburybiz.com) using subject heading 'Letters'.

### MFB (or not?)

Jeff Macaulay's article (Sept. 2002) offers an interesting way of improving the performance of a traditional woofer and I would not seek to belittle that. However, I do not accept that the technique described can be classified as motional feedback, because all of the necessary steps are not present.

At no point is there an analogue of the back emf of the drive unit. At no point is this subtracted from the input signal to produce a cone velocity error. There is no high loop gain applied to a cone velocity error and no compensation to obtain stability. As there is no motional feedback, there is no extension of the frequency response. This is evident from the fact that external equalisation is needed.

Negative output impedance is one way of increasing damping, but I can (and do) increase the damping of woofers by fitting stronger magnets. I doubt that I would be allowed to claim this as motional feedback.

**John Watkinson**  
Reading, UK.

*Expect to hear more of John's ideas in the future - Ed*

### No conspiracy

I believe the debate about radiation from mobile phones (and overhead power lines) has been compromised by the silly ideas put forward as possible modes of action. Let us be clear that the radiation quanta are of far too low energy to cause any chemical reaction (you need light for that, which is why we see in the band we do); there is no chance of building up cyclotron resonance in hydroxyl ions (for example) as their motion is being continually randomised by thermal agitation; and the tissue temperature rise is negligible compared to that produced by a hot bath or even a hot cup of tea. It is not therefore surprising that studies looking for physical changes such as

cancer produce at best indeterminate and statistically dubious results, nor that the village of Wychbold (slap bang underneath the 500kW Droitwich transmitter) does not seem to be a cancer hotspot. I think it entirely possible, however, that just as mobile phone interference causes my CD player's processor to crash, it may equally well disrupt the tiny electrical signals in the brain and effectively cause part of the brain to crash. Psychological and psychosomatic effects are therefore much more obvious. It is also the case that the brain's response to 50Hz fields is considerably enhanced by stimulants such as amphetamine and its relatives, popular among the 'rave culture' but probably not among 'bio-EMC' researchers. It might prove profitable to correlate amphetamine-induced psychoses with living under power lines.

**Pigeon**  
By email

### Measuring low distortion

While I applaud the attempts to use low cost measurements whenever they are adequate for the task in hand,

I fear this is not so with the Richard Black attempts to measure speaker cable distortions.

Before attempting any serious distortion measurements, especially those planned for publication, one should first attempt to quantify the level of distortion that might be expected. Then add a safety margin, typically 10dB, as an absolute minimum should be provided.

In like fashion any signal source used must also be of lesser distortion, since any attempt to quantify small distortion differences, swamped by much larger distortions, is unrealistic.

Researching back publications, in measurements reported by G. Millard (BBC engineering), carbon-film resistors typically exhibit THD around -120dB -130dB, mostly third harmonic and intermodulation around -100 to -120dB.

Using my equipment I too have measured similar values with carbon film but even with a dynamic range of -140dB cannot satisfactorily measure differences in metal film resistors. For that much lower distortion equipment, or a different measurement, is required.

Surely one must assume that all

### Shock hazard

I welcome the full debate my letter on the shock hazard of 1mA has brought. I expected (and hoped) another reader would find a standard (the IEC 60479) bringing real authority to the debate. My top the of head and practical observation guesses were in the right ballpark, if a bit high on the Ventricular Fibrillation threshold.

Obviously individuals should always be protected from the chance of electric shock by suitable barriers and by limiting powers and energy to as low a level as practically possible.

In my work we follow EN60204 "Safety of Machinery, Electrical Equipment of Machines" which generally requires a double barrier between the user and live parts. Covers require tools to remove them and interlocks cut the power to exposed parts or

secondary insulation (such as terminal block covers) prevents in inadvertent contact. Many items in the domestic environment fall well short of this goal. On the subject of safety, the dangers of UV light are perhaps understated (Tiaraju Vasconcellos "Wager's Ozoniser" (August 2002) and Jose A.Senna "Another UV source for EPROM erasing" (September 2002)). The short wavelength UV from an unshielded mercury vapour lamp quartz arc tube is readily damaging to the eyes, like viewing a welding arc. The outer filter glass bulb should never be removed. Such lamps always have outer glass bulbs or are operated in enclosures with further glass filters. Today UV concerns extend to quartz halogen lamps also and the popular 20 and 50W dichroic low voltage spotlights now have glass filters.

**Paul Bennett MIEE CEng, UK**

copper based cables will produce less third harmonic distortion than the best resistor?

I can find no statement as to exactly which soundcard or even test voltages he used. Most modern cards are 16 bit only but a select few are 20 bit or better. The dynamic range of an unaided 16 bit card is not sufficient, which is why I had to spend time and money developing a notch filter/preamplifier.

For my initial experiments, in August 2001, I did try using my Soundblaster 1024 Live card with the signal generators in 'Cool Edit', to measure capacitors. These signals are far from distortion free and all attempts failed. Noise and distortion from the generator far exceeded and clouded those I was attempting to measure. I also tried measuring intermodulation distortion differences, using these signals. To say the results I found were utterly confusing would be an understatement.

From my experiences I suspect that Black's attempts to measure cable distortions using his system were doomed to failure from the beginning. Perhaps he also was making the wrong measurements.

Even using the much-vaunted AP test set would not, I believe, be sufficient to measure distortions in speaker cables.

Failure to measure differences using a test method may prove comforting but it does not prove that cable distortions or differences will not be found in more realistic tests.

To paraphrase a sentence from my first Capacitor sounds article "truly audible differences must be both understandable and measurable. Understanding in terms of construction. Measurements may however require a change in measurement technique."

From my earlier work on speaker cables I know that audible distortion differences certainly do occur with change in cable construction. Measuring them is quite another matter.

I also have some comments on last month's letters. John Jardine makes the point he would like to see all schematics redrawn; Martin Eccles frequently did get schematics redrawn. As a contributor I have suffered many hours trying to identify and remedy errors in redrawn schematics, often in barely legible Faxed proof copies. I accept the present arrangement of posting hardcopy proofs is easier but even so I for one shudder each time I receive a redrawn schematic for corrections, so would certainly not welcome such a move as routine.

Having regularly submitted many exceptionally well developed constructional and measurement projects, all complete with PCB layouts, I would hope the quality of the schematics I submit as HPGL plot files should be acceptable. If not and the decision is to redraw all with no increase in page rate, then for me no more schematics unless very small and simple. End of project design publication in EW for me.

As to the Michael Edinger letter, I suspect he wrote that quickly with little thought as to practicality. While I cannot speak for Mr. Black, I suspect that like me he is freelance and not an EW employee. In which case all expenditure in time, materials and travel must be recouped from the modest EW page rate.

From experience, especially of my recent projects, which so many readers have admired, that quality of article cannot be cost effective for one person, yet alone two sharing the page rate and incurring extra expenses. While suitable recompense can overcome many problems that also would seem unlikely.

As to his suggestion of downloading PCB drawing BMP files, no way, even compressed the file sizes would be enormous. He may have a broadband access, most do not. As to hardware, even a modest PCB would require using screen resolutions of 1800 x 1200 as a minimum. I do not have such capability and to reduce eyestrain always prefer to work at 800 x 600 resolution.

I could output 'Gerber' but how many readers can accept Gerber, I suspect none. It might be feasible to output a compressed PCL file, but again how many can read and print PCL. As to PDF, from PCB software that requires a number of file conversions again with the creation of errors.

I can speak on this with some authority, since of late I have spent considerable time trying to find how best to output such files from a Windows machine to CD Rom. If any reader has a proven practical method that does not cost an arm and a leg, I would like to be so advised.

He like many others also seems over enamoured of common simulators. I wrote my first dedicated simulator way back in 1983. Since then I have used Touchstone and Hewlett Packard's Microwave Design system running under Unix, also many variations of Spice both DOS and Windows as well as a Microwave version of Spice from Compact Software. For most of my published projects I used Microcap6.

While usable models for transistors and ICs are freely available and can provide reasonably accurate results, as soon as a design involves capacitors larger than a couple of hundred pF or inductors more than a couple of hundred  $\mu$ H, goodbye accuracy, especially calculating distortion and frequency response, even at audio frequencies.

Perhaps if he too purchased a copy

## CPU architecture

A fast, agile computer is essential for the function of modern defensive weapons such as an anti-missile. A simple homing warhead in an anti-missile might be foxed by an incoming target that employs counter-measures. Counter-counter-measures are difficult.

In my work for spastics, I have examined numerous computer architectures in the course of my study. The biggest problem that I have encountered is in the realm of input-output. It is in the pursuit of an improved connection between input-output and a computer's software core that I wish to suggest the 'differentiated multi-processor'. A classical multi-processor consists of a handful of similar cores tightly connected using shared memory. It seems to me that the performance of this system can be improved by individualising each core according to function. That is the basic idea.

To give an example of how such a

computer might be implemented, take the M68000 microprocessor family. The 32-bit 68020 member of the family is a particularly interesting microprocessor core because of its exceptional support for high-level language. I am particularly referring to its firmware support for modules, the CALLM and RETNI instructions. Using dual-port RAM memory, which is now freely available, it does seem to be feasible to connect the high-speed computation-oriented 68020 directly to other M68000 family members as a tightly-coupled multi-processor. Hardware 8-bit data bus communication, to simplify the wiring, would be feasible because the 68020 offers dynamic data bus sizing, while there are still M68000 family members, akin to the old 68008, that can be hard wired for 8-bit, operation. But so what? It is plain to me that here is a way round that perennial old problem with microprocessors, package pin-out restriction. Enough said!

**Allan Campbell**  
Newcastle, UK

of the SPICE2 document ERL-M250 from Berkeley as I did many years ago, he might find it illuminating.  
**Cyril Bateman**  
 UK

We often have to re-draw circuit diagrams, not because the author has made a mess of it, but usually because the original design software will not export to something other than a bitmap (usually via MS Paint). This normally produces 'jagged' resistors, gaps in the lines connecting components and the text is far too small to be read if printed. Complex circuit diagrams that go through a manual re-draw process have to be checked, which of course takes time. Each author is different, which can make proofing a time consuming process. In an ideal world, the circuit software would output a standard DXF file, which could then be just tweaked, MS Equation Editor would allow you to export its funny little text box pictures into something normal

and above all the Mac (and Quark layout software) would recognise a whole lot more than it does at present. And I could just email a PDF file to the author to print, correct and re-scan to be sent back to me. - Ed

### Spectrum pricing

Dr Rudd is correct in his observation that auctions are normally designed to maximise revenue. But that is not the same as realising the full economic value of the spectrum. When the objectives of the 3G auction were announced to the House of Commons on May 18th 1998, the words used were: 'realise the full economic value to consumers, industry and the taxpayer.' What the taxpayer has gained has been lost by industry and/or consumers. (Even the taxpayers' gains are short term. To properly take into account tax revenues over the 20 year licence period would lead to a very different auction design.) Since the most

profitable bidders will win, an auction will normally maximise industry profit, but intervention is needed if you want to include consumer benefit in the maximisation (unless you have perfect competition!) As this was not done it could be argued that the auction was the wrong tool for the stated objective. Neither did it comply with the EU Licensing Directive, which requires 'due weight to be given to maximise benefits to users' and 'ensure optimal use'. I covered this in more detail in an article in the June issue of Land Mobile.

Dr Rudd also comments on the practice of reserving bands for specific services. While it is true that this can raise prices in certain bands, it will reduce others and increase choice. Overall, intelligent band planning will have a net positive effect on consumer benefits. ■

**James Page**  
 Manager, Radio Regulations,  
 Nokia UK Ltd.

### Wein revisited

I read with some interest Cyril Bateman's article about Capacitor Sound in the July issue. In particular, his modification of the Wien-bridge oscillator described by John Linsley Hood caught my eye.

The two amplifier version of the wien-bridge oscillator seems to have a rather chequered history and to have been independently discovered several times. The occasions that I know (and I don't pretend to be an expert on the matter) are 1959 by Hewlett Packard<sup>1</sup>, 1960 by W. Woodman of Nash and Thompson<sup>2</sup>, an unknown date probably in the 1960's by Peter Baxandall<sup>3</sup> and 1981 by John Linsley Hood<sup>4</sup>. Intriguingly, the earliest version had equal output voltages as utilised by Cyril.



One advantage of the circuit is that the outputs from the two amplifiers are in antiphase. By making the two voltages equal, a balanced output can be obtained. In the days of valves, this was then an ideal way to drive a push pull output stage. I believe this was why HP adopted it on their 1959 oscillator. The block diagram in fig. 1, with the bridge redrawn to show its balanced nature, illustrates their circuit. (Actually their bridge circuit was rather more complicated as complex RC circuits were used to enable 20Hz to 20kHz to be covered without band switching.)


**P.F. Gascoyne**  
 Wantage, Oxon. UK

#### References:


1. New kind of Audio Oscillator. Robert F. Scott. Radio Electronics Jan 1959 p58.
2. Letter to the Editor. W. Woodman. Wireless World Dec 1960 p610.
3. Private communication from J. Linsley Hood.
4. Wien-bridge oscillator with low harmonic distortion. J L Linsley Hood. Wireless World May 1981 p51.

## New kind of AUDIO OSCILLATOR

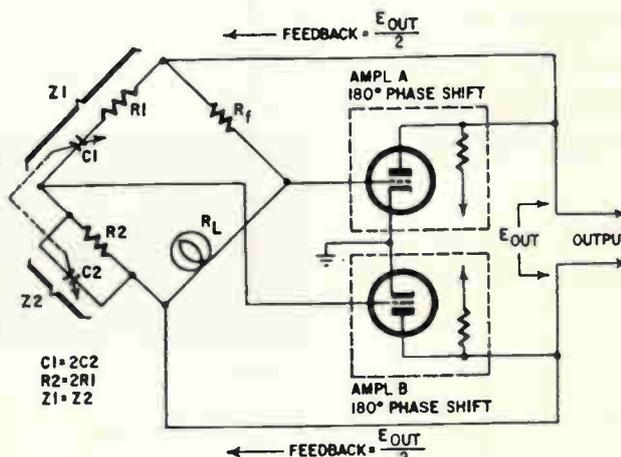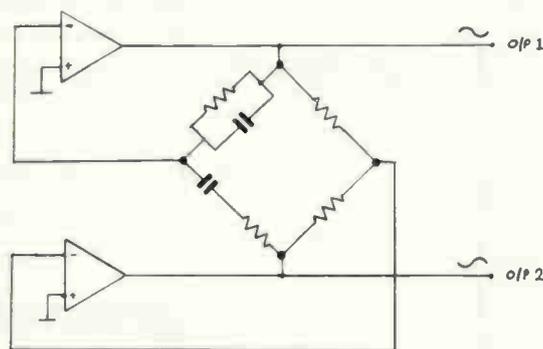

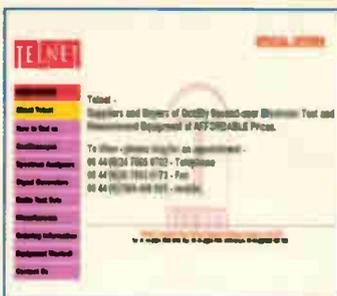

# WEB DIRECTIONS

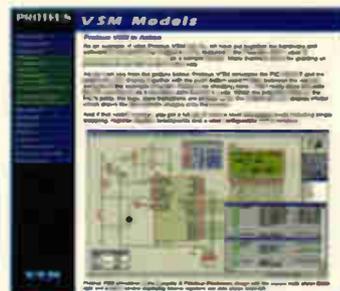

Put your web address in front of 18,000 electronic fanatics.

Electronics World acknowledge your company's needs to promote your web site, which is why we are dedicating over 3 pages in every issue to WEB ADDRESSES.

Linage only will cost £150 + vat for a full year.

Linage with colour screen shot will cost £350 + vat for a full year, this will include the above plus 3cm shot of your web site which we can produce if required.

To take up this offer or for more information telephone  
**Reuben Gurunlian**  
Tel 0208 722 6028

E-mail  
r.gurunlian@highburybiz.com

## ANASOFT LTD

<http://www.anasoft.co.uk>

SuperSpice, the affordable, mixed-mode windows circuit simulator. Wrote by an analogue design engineer for those Teletubbies who like keeping things simple.

## BEDFORD OPTO TECHNOLOGY LTD

<http://www.bot.co.uk>

Optoelectronic products UK design development manufacture standard and custom, LED bargraphs, circuit board indicators, stand offs, transmissive/reflective switches, baseafe optocouplers tubular and surface mount, pannel mount LED assemblies.

## CRICKLEWOOD ELECTRONICS

<http://www.cricklewoodelectronic.co.uk>

Cricklewood Electronics stock one of the widest ranges of components, especially semiconductors including ICs, transistors, capacitors, all at competitive prices.

## COMPONENT KITS

<http://www.componentkits.com>




"Component Kits LLC manufactures and distributes Electronic Component Kits used for professional engineering design, prototype, University lab, and hobbyist uses.

Visit our website to review our current product line, request our Free CD-ROM, or join our newsletter."

## COOKE INTERNATIONAL

<http://www.cooke-int.com>

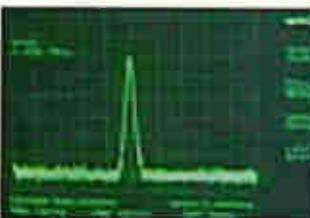

[info@cooke-int.com](mailto:info@cooke-int.com)

Test & Measuring Equipment  
Operating & Service Manuals.

## CROWNHILL ASSOCIATES LTD

<http://www.crownhill.co.uk>



Crownhill supply low cost development tools for use with Micro-Controllers and Smart Cards. Products include Smart Card development tools, Smart cards, Micro Development tools and Bespoke Design Services.

## DB TECHNOLOGY

<http://www.dbtechnology.co.uk/>



EMC Testing and Consultancy.  
Anechoic chamber and open area test site.

- Compliance Tests
- Rapid, accurate pre-compliance tests.
- Fixes included. FCC Listed.
- Flexible, hourly booking available.

## DESIGNER SYSTEMS CO.

<http://www.designersystems.co.uk>



Electronic product design company with over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.

## EAGLE PCB DESIGN SOFTWARE

<http://www.puresoft.co.uk>

- Professional PCB design made easy!
- Fully functional freeware download.



- Schematics, Layout & Autorouting.
- Free tech support

## EDAForce

<http://www.edaforce.co.uk>

EDAForce is a division of the independent specialist recruitment consultancy TelecomForce. We specialise in placing engineers and engineering managers, either contract or permanent, in the role that is right for them. Visit the web site, email us on [ew@edaforce.co.uk](mailto:ew@edaforce.co.uk) or call +44(0)1628 850273 to find out how we could help you.

## EQUINOX TECHNOLOGIES UK LTD

<http://www.equinox-tech.com>



Equinox Technologies UK Ltd., specialise in development tools for the embedded microcontroller market.

## FELLER UK

<http://www.feller-at.com>

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

## FIELD ELECTRIC LTD

<http://www.fieldelectric.co.uk>

Field Electric Ltd has been successfully trading since 1958 in the re-sale of used test & measurement equipment & computer hardware. We buy and sell in small or bulk quantities and can source equipment to particular requirements. Visit our web site or call 44 01837 83736.



### FUTURE TECHNOLOGY DEVICES INTL. LTD.

<http://www.ftdichip.com>

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s. Complete with PC drivers these devices simplify the task of designing or upgrading USB peripherals

### J W HARDY COMMUNICATIONS


<http://www.jwhardy.co.uk>



R.F. Network Specialist. Shop online - for R.F.network components. We supply a full range of TV, radio reception equipment to receive analogue/digital signals from both terrestrial and satellite sources. We provide a free planning service for your R.F. networks, MATV and SMATV etc

### LABCENTER

<http://www.labcenter.co.uk>

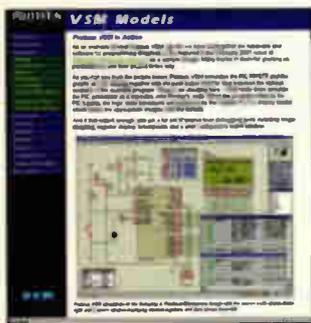

Download evaluation versions of our unique Proteus VSM mixed mode SPICE and CPU simulator, and also the full range of Proteus PCB Design products. Register the Proteus Lite shareware versions online for as little as £20.

### LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS markets low power radio transmitters, receivers and transceiver modules manufactured by ourselves, Radiometrix, Circuit Designs, RDT and

Micrel. Applications for telemetry, video and remote control.

### MAGNIFICO (The Magnifier Company)

<http://www.magnifyingglasses.co.uk>



The best online selection of magnifiers and low-vision aids, including hand-held, hands-free, illuminated, magnifying stands, fresnel sheets and inspection loupes.

### MAPLIN ELECTRONICS

<http://www.maplin.co.uk>



A fully secure and interactive internet ordering system from Maplin Electronics, the specialist electronic retail and mail order company to business and retail consumers alike. 15,000 products available on line.

### MATRIX MULTIMEDIA LTD

[www.matrixmultimedia.co.uk](http://www.matrixmultimedia.co.uk)



Matrix Multimedia publishes a number of highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

### NORCALL Ltd

<http://www.norcall.co.uk>

e-mail [Norcall@aol.com](mailto:Norcall@aol.com)  
Suppliers programmers and repairers of new and refurbished two-way radio equipment. Retuning and recrystalling service available. All types of batteries chargers and aerials supplied.

### QUASAR ELECTRONICS

[www.quasarelectronics.com](http://www.quasarelectronics.com)

Over 250 electronic kits, projects and ready built units for hobby, educational & industrial applications.



TEL: 01279 467799, FAX: 07092 203496 or EMAIL: [ewsales@quasarelectronics.com](mailto:ewsales@quasarelectronics.com)

### PHAEDRUS LTD

[www.phaedrusltd.co.uk](http://www.phaedrusltd.co.uk)

Manufacturer and supplier of low cost general purpose and serial I/O digital modules and accessories. PC based software for data logging and control applications.

### RADIOMETRIX

<http://www.radiometrix.co.uk>



Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use. They comply with European harmonised standards EN300 220-3 and EN301 489-3 and are CE certified by an independent Notified Body.

### RADIO-TECH LIMITED

<http://www.radio-tech.co.uk>

Radio modules, modems, telemetry, audio transmitters, pagers, antenna, remote controls and much more. All UK designed and manufactured.

### RALFE ELECTRONICS

professional test & measurement



[www.ralfe-electronics.co.uk](http://www.ralfe-electronics.co.uk)

### RIMO-AKD-PP

<http://www.art-decade.com>

We provide the following services: Systems design, test & analysis. Software design & coding. Avionics design. Document technical review, authoring & proof reading. Rig design. Hardware design.



### RD RESEARCH

<http://www.spice-software.com>

B2 Spice offers powerful simulation software for professional engineers and education establishments. All the software is available on a 30 day trial basis and comes with free technical support.

### SOFTCOPY

<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

### TEMWELL CORPORATION

<http://www.temwell.com.tw>

Manufacturer & Exporter of Heelical BPF Filter, 30 Watts BPF Power Filter and Handset/Base Station Duplexers

### TELNET

<http://www.telnet.uk.com>



Top quality second-user Test and Measurement Equipment  
[eMail:sales@telnet.uk.com](mailto:eMail:sales@telnet.uk.com)

### TELONIC

<http://www.telonic.co.uk>



Telonic, specialists in laboratory AC & DC Power Supplies, Electronic AC & DC Loads, Electrical Safety Testing and complete test systems. Plus RF Filters, Attenuators, Diesel Engine Smoke Measurement, Quartz Crystal Microbalances.  
Tel +44 (0) 118 9786911\*



### TEST EQUIPMENT SOLUTIONS

<http://www.TestEquipmentHQ.com>  
 Test Equipment for rental or second user sale at the industry's lowest prices. All types of equipment from all leading manufacturers including general purpose, communications and industrial test. Items fully refurbished with 1 year warranty. Rental rebate given on purchases.

### THOSE ENGINEERS LTD

<http://www.spiceage.com>  
 Working evaluations of SpiceAge mixed-mode simulator, Spicycle PCB design tools and Superfilter demo (synthesises passive, active, digital filters). Tech support, sales links and price list.



### TECHNICAL AND SCIENTIFIC SUPPLIES

<http://www.technicalscientific.com>  
 Suppliers of pre-1985 equipment and components.  
 - Test/Measurement equipment  
 - Valves and semiconductors  
 - Transducers and pressure gauges  
 - Scientific books and catalogues  
 - Manuals and data sheets

### TOTAL ROBOTS

<http://www.totalrobots.co.uk>  
 Robot Kits and Control Technology products, including OOPic the first Object-Oriented Programmable Integrated Circuit. Secure on-line ordering and fast delivery.

### ULTRACOM

<http://www.ultracom.fi>  
 Ultracom specializes in the design and manufacture of data radio products including Radio Modules, Radio Modems, Filters and Antennas for real-time data communication. In addition to our standard RF-products we provide tailored solutions for customers wireless communications requirements. Our wireless data radios are used in the most varied applications: transferring environmental data in tropical conditions, locating moving targets, remote-control of cranes, controlling pump stations in waterworks, monitoring real estates, transferring data in public transportation information systems.

There are countless applications, what are yours?

### VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>



Vutrax electronic schematic and pcb design system for Windows 95/98, ME, NT, 2000, XP and Linux. Limited Capacity FREE version downloads available, all upgradeable to various customised level.

### WARWICK WIRELESS LTD

<http://www.radiotelemetry.co.uk>  
 Free data on Radio Modems, Radio Telemetry, Radio Modules and Wireless Video systems. The licence exempt radios can transmit data from 1 to 20Km



at baud rates of 19.2Kbaud to 128Kbaud. The UK based Company can offer customised derivatives of their products as well as turnkey RF Systems.

### WILMSLOW AUDIO

<http://www.wilmslow-audio.co.uk>



"Uk's largest supplier of high quality loudspeaker kits and drive units. Comprehensive range of components and accessories, including damping products, connectors and grilles materials. Demonstration facilities available.

## WEB DIRECTIONS

Put your web address in front of 21,000 Electronics fanatics. Electronics World acknowledges your companys need to promote your web site, which is why we are now dedicating page's in every Issue to WEB ADDRESSES. This gives our readers the opportunity to look up your companys name, to find your web address and to browse the magazine page to find new sites. We also understand that cost is an important factor, as web sites are an added drain on budgets. I am sure you will agree these rates make all the difference

### FOR 12 ISSUES:

Lineage only will cost £150 for a full year just £12.50 per month. This includes your companys name, web address and a 25 word description.  
 Lineage with colour screen shot will cost £350 for a full year just £29.17 per month. This will include the above plus a 3cm screen shot of your site, which we can produce if required.  
 To take up this offer or for more information ring on 0208 722 6028.  
 E-mail: [r.gurunlian@highburybiz.com](mailto:r.gurunlian@highburybiz.com)

Company Name	Web address



**Electronics World reader offer:**  
**x1, x10 switchable**  
**oscilloscope probes,**  
**only £21.74 a pair,**  
**fully inclusive\***

\*Additional pairs as part of the same order, only £19.24 each pair.

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to **Probe Offer, Jackie Lowe, Highbury Business Communications, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey, SM3 8BZ**

Readers outside Europe, please add £2.50 to your order.

Please supply the following:

**Probes**

Total \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Postcode \_\_\_\_\_ Telephone \_\_\_\_\_

Method of payment (please circle)

**Cheques should be made payable to Electronics World**  
 Access/Mastercard/Visa/Cheque/PO

Credit card no \_\_\_\_\_

Card expiry date \_\_\_\_\_ Signed \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Please allow up to 28 days for delivery

**Specifications**

**Switch position 1**  
 Bandwidth DC to 10MHz  
 Input resistance 1MΩ – i.e. oscilloscope i/p  
 Input capacitance 40pF+oscilloscope capacitance  
 Working voltage 600V DC or pk-pk AC

**Switch position 2**  
 Bandwidth DC to 150MHz  
 Rise time 2.4ns  
 Input resistance 10MΩ ±1% if oscilloscope i/p is 1MΩ  
 Input capacitance 12pF if oscilloscope i/p is 20pF  
 Compensation range 10-60pF  
 Working voltage 600V DC or pk-pk AC

**Switch position 'Ref'**  
 Probe tip grounded via 9MΩ, scope i/p grounded

As an advertiser you can be certain that your sales message is going to be read by decision-making electronics professionals with the power to purchase your products.

The pre-paid rate for semi-display setting is £17 per single column centimetre (maximum 4cm). Box number £22 extra. All prices plus 17 1/2% VAT. All cheques, postal orders etc to be made payable to Highbury Business Communications Ltd. Advertisements together with remittance should be sent to Electronics World Classified, Highbury Business Communications Ltd, Anne Boleyn House, 9-13 Ewell Road, Cheam, Surrey SM3 8DZ.  
Tel: 020 8722 6028. Fax: 020 8770 2016.

# Service Link

## ARTICLES WANTED

### TOP PRICES PAID

For all your valves, tubes, semi conductors and ICs.

### Langrex Supplies Limited

1 Mayo Road, Croydon, Surrey CR0 2QP  
TEL: 020 8684 1166 FAX: 020 8684 3056

### BEST CASH PRICES PAID

For all valves KT88 PX4 and other audio types

Wide range of valves and CRT stocked

Tel: 01403 784961

Billington Export Ltd.  
Fax: 01403 783519  
Email: sales@bel-tubes.co.uk  
Sussex RH14 9EZ  
Visitors by appointment

**Rack Enclosures**  
New and Used - most sizes  
16U to 50U side and rear panels  
mains distribution  
19" Panel mounts  
optima eurocraft  
  
Prices from £45 + vat  
**M&B Radio**  
86 Bishopsgate Street, Leeds LS1 4BB  
Tel. 0113 2702114 Fax. 0113 2426881

## FOR SALE

### RF DESIGN SERVICES

All aspects of RF hardware development considered from concept to production.

### WATERBEACH ELECTRONICS

www.rlaver.dial.pipex.com  
TEL: 01223 862550  
FAX: 01223 440853

### PRINTED CIRCUIT BOARDS

**DESIGNED & MANUFACTURED**   
• Prototype or production quantities  
• Fast turnaround available  
• PCBs designed from circuit diagrams  
• Almost all computer files accepted  
• PCB assembly - mechanical assembly  
• Full product design-manufacture-test-repair  
Unit 5, East Belfast Enterprise Park  
308 Albertbridge Rd, Belfast BT5 4GX  
TEL 028 9073 8897 FAX 028 9073 1802  
info@agarcircuits.com

## SERVICES

### P&P ELECTRONICS

Design of Electronic Systems by Degree Qualified Engineer  
**01924 402931**

### POWER SUPPLY DESIGN

Switched Mode PSU  
Power Factor Correction  
*designed to your specification*  
Tel/Fax: 01243 842520  
e-mail: eugen\_kus@cix.co.uk  
**Lomond Electronic Services**

## SERVICES

### From Concept To Production

48 HOUR SERVICE

Electronic design and manufacturing services for the new millennium:

- Embedded monitoring & control
- PSTN telephones and test equipment
- Datacom interfacing, line driving etc.
- Switch Mode & linear PSU and battery management
- Gas detection systems
- Printed Circuit Board design
- Technical documentation, schematic layout & language translation
- Wireless telemetry systems
- Audio & Video processing
- GSM telemetry via SMS or data (TCP/IP)
- DVD player control systems
- GPS positioning systems
- Specialist cable looms
- Small, medium & large scale manufacturing

Email: sales@designersystems.co.uk  
Tel/Fax: +44 (0) 1872 223306



for more information see our web site @ <http://www.designersystems.co.uk>

Need a Remote Control manufactured?

## You can get it from Wallis!

We are a manufacturer and distributor of replacement remote controls and, specialise in providing Fast and Low-Cost solutions for OEM customers.

For further information, please contact us.

Wallis Remotes, A109 Riverside Business Centre, London, SW18 4UQ  
(Tel) 020 8870 3388 (Fax) 020 8870 9988  
(email) sales@wallis-universal.co.uk

**PCBs** Conv/PTH/Multi-Layer/Flexible • UK & Far East production  
• CAD Layout • Electronic Design • Assembly (prototype & production)  
• SMD m/c assy @ 18,500 cps/hr

Deliveries from **24hrs**

Prototype PTH PCBs from just **£40.00**



Tel: 01635 40347

Newbury Electronics Ltd  
Faraday Road Newbury Berks RG14 2AD  
Fax: 01635 36143  
e-mail: circuits@newbury.tcom.co.uk  
<http://www.newburyelectronics.co.uk>

Visit

[www.pcbtrain.com](http://www.pcbtrain.com)

The low cost source for prototype PCBs from 1 to 6 layers

## WANTED

### WANTED Surplus or Obsolete Electronic Components

Turn your excess stock into instant cash!

SEND OR FAX YOUR LIST IN STRICTEST CONFIDENCE

Will collect anywhere in the UK




**Mushroom**  
COMPONENTS

6a St.Marys St, Bedford, Bedfordshire, MK42 0AS  
Tel: 01234 363611 Fax: 01234 326611  
E-mail: sales@mushroomcomponents.com  
Internet: [www.mushroomcomponents.com](http://www.mushroomcomponents.com)

For a FREE consultation on how best to market your products/services to a professional audience contact REUBEN on 020 8722 6028

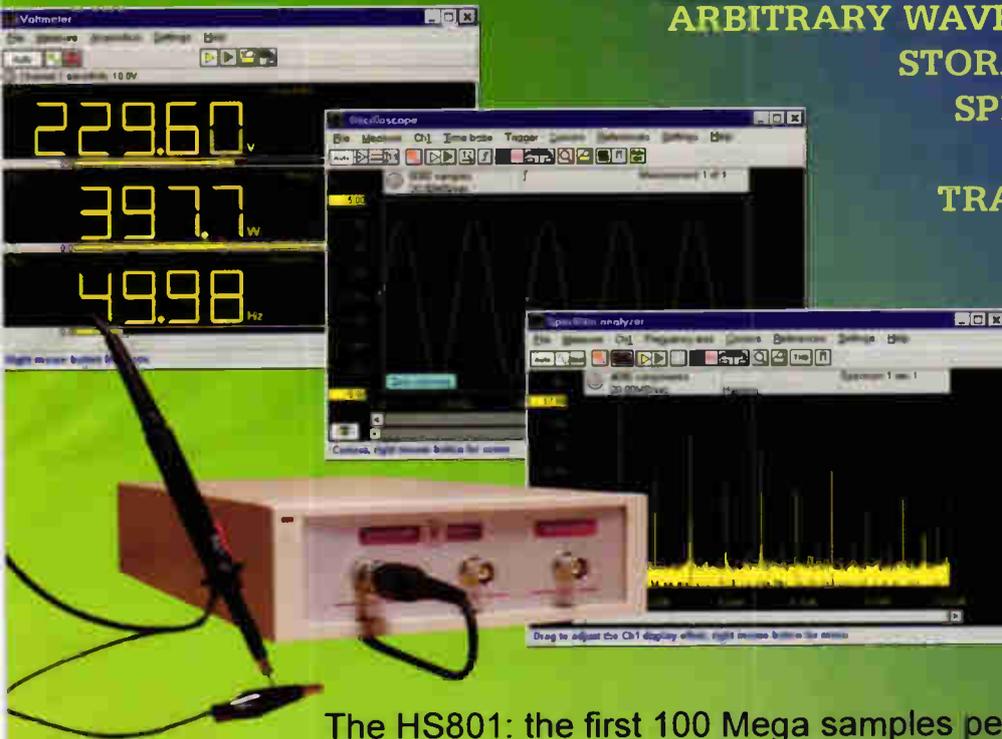**ARBITRARY WAVEFORM GENERATOR-  
STORAGE OSCILLOSCOPE-  
SPECTRUM ANALYZER-  
MULTIMETER-  
TRANSIENT RECORDER-**



The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (Arbitrary Waveform Generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.

- The versatile software has a user-defined toolbar with which over 50 instrument settings quick and easy can be accessed. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.
- When a quick indication of the input signal is required, a simple click on the auto setup button will immediately give a good overview of the signal. The auto setup function ensures a proper setup of the time base, the trigger levels and the input sensitivities.
- The sophisticated cursor read outs have 21 possible read outs. Besides the usual read outs, like voltage and time, also quantities like rise time and frequency are displayed.
- Measured signals and instrument settings can be saved on disk. This enables the creation of a library of measured signals. Text balloons can be added to a signal, for special comments.
- The (colour) print outs can be supplied with three common text lines (e.g. company info) and three lines with measurement specific information.
- The HS801 has an 8 bit resolution and a maximum sampling speed of 100 MHz. The input range is 0.1 volt full scale to 80 volt full scale. The record length is 32K/64K samples. The AWG has a 10 bit resolution and a sample speed of 25 MHz. The HS801 is connected to the parallel printer port of a computer.
- The minimum system requirement is a PC with a 486 processor and 8 Mbyte RAM available. The software runs in Windows 3.xx / 95 / 98 or Windows NT / 2000 / XP and DOS 3.3 or higher.

TiePie engineering (UK), 28 Stephenson Road, Industrial Estate, St. Ives, Cambridgeshire, PE17 3WJ, UK  
Tel: 01480-460028; Fax: 01480-460340

TiePie engineering (NL), Koperslagersstraat 37, 8601 WL SNEEK The Netherlands  
Tel: +31 515 415 416; Fax +31 515 418 819

Web: <http://www.tiepie.nl>

**Reliability**

**COMPUTER CONTROLLED MEASURING INSTRUMENT**



**atlas**  
component analyser

Check your  
semi's

**£50!**

fully inclusive UK price  
Great overseas price too!



**NOW MEASURES  
TRANSISTOR LEAKAGE!**

- Automatic component identification
- Pinout identification
- Transistor gain measurement
- MOSFET gate threshold measurement
- PN junction characteristics measurement
- Shorted Junction identification
- Transistor leakage measurement
- Just connect the part anyway round and press the button!

**Supports:**

- Bipolar transistors.
- Darlington transistors.
- Diode protected transistors.
- Resistor shunted transistors.
- Enhancement mode MOSFETs.
- Depletion mode MOSFETs.
- Junction FETs.
- Low power triacs and thyristors.
- Diodes and diode networks.
- LEDs (+tricolours)

The Peak Atlas is analysing...

Two terminal bicolour LED

NPN bipolar Darlington

Diode protection between C-E

Resistor shunt between B-E

Current gain Hfe=126

Enhancement mode N-Ch MOSFET

Gate Threshold Vgs=3.47V

RED GREEN BLUE Base Emit

B... La ... 77V

... ..

... ..

**If you don't love it, you get your money back!**

Buy online!

**Test CAT 5/5e/6 Connections**

Just plug one end of your cable into the Atlas IT and the other into the Atlas Terminator and press "test". In seconds the unit will identify the cable type (straight through, crossover or token ring) and verify every connection. If there are any faults then they are clearly explained on screen.


Socket testing is possible too thanks to the special patch cables included in the outfit.

Swapped lines, missing lines, shorted lines are all uniquely identified together with the full connection pattern!

What's more, if you want to know how to make up a special network cable, the Atlas can instruct you, even down to cable colours!

The Atlas IT is supplied with 2 non-ID terminators, 2 patch cables, spare battery, carry case and user guide.

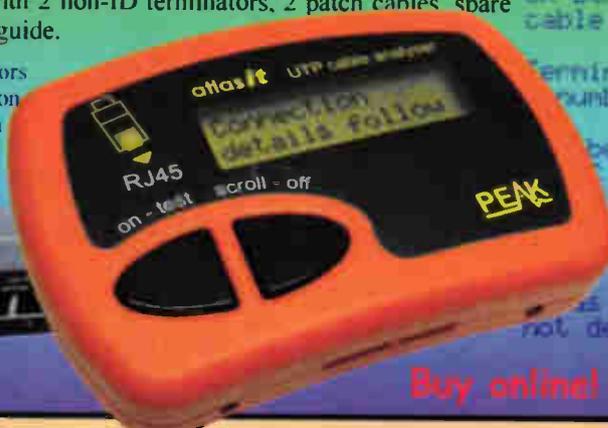Also available are ID terminators enabling cable-run identification together with full connection mapping and testing. Up to 24 IDs available



Buy online!

supplied in carry case

OK Cross-Over cable (PC-PC)

Connection details follow

Term) 12345678  
Atlas) 86145278

Shorted lines detected! 4 & 5

OK Straight Thru cable (PC-Hub)

Terminator ID number 04

be conn... or Hub

lines led

as Term not detected.

**atlasit**  
network cable analyser

**£79!**  
fully inclusive UK price



Visit [www.peakelec.co.uk](http://www.peakelec.co.uk) to download the data sheets, user guides and copies of independent reviews.

You can pay using a cheque, postal order, credit or debit card and even pay securely online. Please contact us for overseas or volume orders - you will be pleasantly surprised.

Also available from

**Farnell**

**MAPLIN ELECTRONICS**

**PEAK**  
electronic design ltd

Atlas House, Kiln Lane  
Harpur Ind. Est., Buxton  
Derbyshire, SK17 9JL, UK

[www.peakelec.co.uk](http://www.peakelec.co.uk)  
[sales@peakelec.co.uk](mailto:sales@peakelec.co.uk)

Tel. 01298 70012 Fax. 01298 70046

