

ELECTRONICS WORLD



NOVEMBER 2003 £3.25

RTTY decoder




16 MW switch

Accurate time
measurement

Project: Scanning
force microscope

Reader offer
serial I/O card

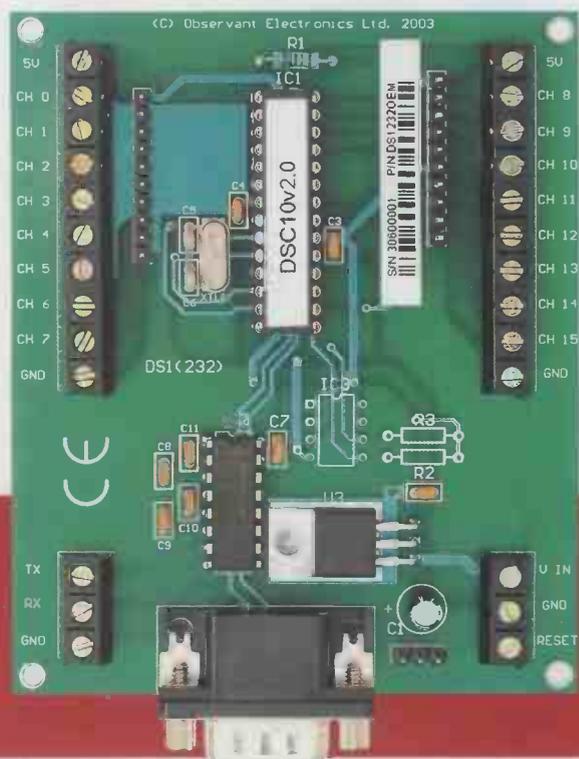

Hewlett Packard 3314A Function Generator 20MHz	£750
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	£1950
Hewlett Packard 3325B Synthesised Function Generator	£2500
Hewlett Packard 3326A Two-Channel Synthesiser	£2500
H.P. 4191A R/F Imp. Analyser (1GHz)	£3995
H.P. 4192A L.F. Imp. Analyser (13MHz)	£4000
Hewlett Packard 4193A Vector Impedance Meter (4-110MHz)	£2900
Hewlett Packard 4278A 1kHz/1MHz Capacitance Meter	£3500
H.P. 53310A Mod. Domain Analyser (opt 1/31)	£3950
Hewlett Packard 8349B (2 - 20 GHz) Microwave Amplifier	£2000
Hewlett Packard 8508A (with 85081B plug-in) Vector Voltmeter	£2500
Hewlett Packard 8904A Multifunction Synthesiser (opt 2+4)	£1750
H.P. ESG-D3000A 3GHz Signal Gen	£6995
Marconi 6310 - Prog'ble Sweep gen. (2 to 20GHz) - new	£2500
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£2995
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£3750
R&S SMG (0.1-1GHz) Sig. Generator (opts B1+2)	£2500
Fluke 5700A Multifunction Calibrator	£12500
Fluke 5800A Oscilloscope Calibrator	£9995

OSCILLOSCOPES

Gould 400 20MHz - DSO - 2 channel	£695
Gould 1421 20MHz - DSO - 2 channel	£425
Gould 4068 150MHz 4 channel DSO	£1250
Gould 4074 100MHz - 400 Ms/s - 4 channel	£1100
Hewlett Packard 54201A - 300MHz Digitizing	£750
Hewlett Packard 54502A - 400MHz - 400 MS/s 2 channel	£1600
Hewlett Packard 54520A 500MHz 2ch	£2750
Hewlett Packard 54600A - 100MHz - 2 channel	£675
Hewlett Packard 54810A 'Infinium' 500MHz 2ch	£2995
Hitachi V152/V212/V222/V302B/V302F/V353F/V550BV650F	from £1200
Hitachi V1 100A - 100MHz - 4 channel	£750
Intron 2020 - 20MHz. Dual channel D.S.O (new)	£450
Iwatsu SS 5710/SS 5702 -	from £125
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lecroy 9314L 300MHz - 4 channels	£2750
Meguro MSO 1270A - 20MHz - D.S.O. (new)	£450
Philips 3295A - 400MHz - Dual channel	£1400
Philips PM3070 - 100MHz - 2 channel - cursor readout	£650
Philips PM3392 - 200MHz - 200Ms/s - 4 channel	£1750
Philips PM3094 - 200MHz - 4 channel	£1500
Tektronix 468 - 100MHz D.S.O.	£500
Tektronix 2213/2215 - 60MHz - Dual channel	£300
Tektronix 2220 - 60MHz - Dual channel D.S.O	£850
Tektronix 2221 - 60MHz - Dual channel D.S.O	£850
Tektronix 2235 - 100MHz - Dual channel	£500
Tektronix 2245A - 100MHz - 4 channel	£700
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2445 - 150MHz - 4 channel -DMM	£850
Tektronix 2445/2445B - 150MHz - 4 channel	£800
Tektronix 2465/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 7104 - 1GHz Real Time - with 7A29 x2, 7B10 and 7B15	from £1950
Tektronix TAS 475 - 100MHz - 4 channel	£850
Tektronix TDS 310 50MHz DSO - 2 channel	£750
Tektronix TDS 520 - 500MHz Digital Oscilloscope	£2500

SPECTRUM ANALYSERS

Advantest 4131 (10kHz - 3.5GHz)	£3750
Advantest/TAKEDA RIKEN - 4132 - 100kHz - 1000MHz	£1350
Anritsu MS2613A 9kHz - 6.5GHz Spectrum Analyser	£4950
Ando AC 8211 - 1.7GHz	£1750
Avcom PSA-65A - 2 to 1000MHz	£2500
Farnell SSA-1000A 9kHz-1GHz Spec. An.	£1250
Hewlett Packard 182T Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2000
Hewlett Packard 853A Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2500
Hewlett Packard 3582A (0.02Hz - 25.5kHz) dual channel	£1500
Hewlett Packard 3585A 40 MHz Spec Analyser	£3000
Hewlett Packard 3561A Dynamic Signal Analyser	£3500
Hewlett Packard 8568A - 100kHz - 1.5GHz Spectrum Analyser	£3500
Hewlett Packard 8590A (opt 01, 021, 040) 1MHz-1.5MHz	£2500
Hewlett Packard 8596E (opt 41, 101, 105,130) 9kHz - 12.8GHz	£9950
Hewlett Packard 8713C (opt 1 E1) Network An. 3 GHz	£6000
Hewlett Packard 8713B 300kHz - 3GHz Network Analyser	£5000
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£4995
Hewlett Packard 8753A (3000KHz - 3GHz) Network An.	£3250
Hewlett Packard 8753B+85046A Network An + S Param (3GHz)	£6500
Hewlett Packard 8754A - Network Analyser 4MHz - 1300MHz)	£1500
Hewlett Packard 8756A/8757A Scaler Network Analyser	from £900
Hewlett Packard 8757C Scalar Network Analyser	£3500
Hewlett Packard 70001A/70900A/70906A/70902A/70205A - 26.5 GHz Spectrum Analyser	£7000
IFR A7550 - 10KHz-GHz - Portable	£1750
Meguro - MSA 4901 - 30MHz - Spec Analyser	£600
Tektronix 492P (opt1,2,3) 50KHz - 21GHz	£3500
Wiltron 6409 - 10-2000MHz R/F Analyser	£1250
Tek 496 (9KHz-1.8GHz)	£2500

Radio Communications Test Sets

Hewlett Packard 8920B (opts 1,4,7,11,12)	£6750
Hewlett Packard 8922M + 83220E	£2000
Marconi 2955	£1250
Marconi 2955A	£1750
Marconi 2955B/60B	£3500
Marconi 2955R	£1995
Motorola R2600B	£2500
Racal 6111 (GSM)	£1250
Racal 6115 (GSM)	£1750
Racal 6103 (opts 1, 2)	£5000
Rohde & Schwarz SMFP2	£1500
Rohde & Schwarz CMT 90 (2GHz) DECT	£3995
Rohde & Schwarz CMTA 94 (GSM)	£4500
Schlumberger Stabilock 4015	£3250
Schlumberger Stabilock 4031	£2750
Schlumberger Stabilock 4040	£1300
Wavetek 4103 (GSM 900) Mobile phone tester	£1500

MISCELLANEOUS

Ballantine 1620A 100Amp Transconductance Amplifier	£1250
EIP 545 Microwave Frequency Counter (18GHz)	£1000
EIP 548A and B 26.5GHz Frequency Counter	from £1500
EIP 575 Source Locking Freq. Counter (18GHz)	£1200
EIP 585 Pulse Freq. Counter (18GHz)	£1200
Fluke 6060A and B Signal Gen. 10kHz - 1050MHz	£950
Genrad 1657/1658/1693 LCR meters	from £500
Gigatronics 8541C Power Meter + 80350A Peak Power Sensor	£1250
Gigatronics 8542C Dual Power Meter + 2 sensors 80401A	£1995
Hewlett Packard 339A Distortion measuring set	£600
Hewlett Packard 436A power meter and sensor (various)	from £750
Hewlett Packard 438A power meter - dual channel	£1750
Hewlett Packard 3335A - synthesiser (200Hz-81MHz)	£1750
Hewlett Packard 3457A multi meter 6 1/2 digit	£850
Hewlett Packard 3784A - Digital Transmission Analyser	£2950
Hewlett Packard 37900D - Signalling test set	£2500
Hewlett Packard 34401A Multimeter	£500
Hewlett Packard 4274A LCR Meter	£1750
Hewlett Packard 4275A LCR Meter	£2750
Hewlett Packard 4276A LCZ Meter (100MHz-20KHz)	£1400
Hewlett Packard 5342A Microwave Freq. Counter (18GHz)	£850
Hewlett Packard 5385A - 1 GHz Frequency counter	£495
Hewlett Packard 6033A - Autoranging System PSU (20v-30a)	£750
Hewlett Packard 6060A and B Electronic Load 300W	from £750
Hewlett Packard 6622A - Dual O/P system p.s.u	£950
Hewlett Packard 6624A - Quad Output Power Supply	£1750
Hewlett Packard 8350B - Sweep Generator Mainframe	£1500
Hewlett Packard 8642A - high performance R/F synthesiser (0.1-1050MHz)	£2500
Hewlett Packard 8656A - Synthesised signal generator	£750
Hewlett Packard 8656B - Synthesised signal generator	£995
Hewlett Packard 8657A - Synth. signal gen. (0.1-1040MHz)	£1500
Hewlett Packard 8657B - 100MHz Sig Gen - 2060 MHz	£3950
Hewlett Packard 8657D - XX DQPSK Sig Gen	£3950
Hewlett Packard 8901B - Modulation Analyser	£1750
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1000
Hewlett Packard 11729B/C Carrier Noise Test Set	from £2500
Hewlett Packard 53131A Universal Frequency counter (3GHz)	£850
Hewlett Packard 85024A High Frequency Probe	£1000
Hewlett Packard 6032A Power Supply (0-60V)-(0-50A)	£2000
Hewlett Packard 5351B Microwave Freq. Counter (26.5GHz)	£2750
Hewlett Packard 5352B Microwave Freq. Counter (40GHz)	£5250
Keithley 220 Programmable Current Source	£1750
Keithley 228A Prog'ble Voltage/Current Source IEEE.	£1950
Keithley 237 High Voltage - Source Measure Unit	£3950
Keithley 238 High Current - Source Measure Unit	£3750
Keithley 486/487 Picoammeter (+volt.source)	£1350/£1850
Keithley 617 Electrometer/source	£1950
Keithley 8006 Component Test Fixture	£1750
Marconi 2840A 2 Mbit/s Transmission Analyser	£1100
Marconi 6950/6960/6960A/6970A Power Meters & Sensors	from £400
Phillips 5515 - TN - Colour TV pattern generator	£1400
Phillips PM 5193 - 50 MHz Function generator	£1350
Phillips PM 6654C System Timer Counter	£750
Panasonic VP 8175A Sig. Gen. (100KHz-140MHz) AM/FM/CW	as new £650
Rohde & Schwarz FAM (opts 2,6 and 8) Modulation Analyser	£2500
Rohde & Schwarz NRV/NRVD Power meters with sensors	from £1000
Tektronix 1720 Vectorscope	£950
Tektronix 1735 Waveform Monitor	£1100
Tektronix AM503 - AM503A - AM503B Current Amp's with M/F and probe	from £800
Wayne Kerr 3245 - Precision Inductance Analyser	£1750
Bias unit 3220 and 3225L Cal.Coil available if required.	(P.O.A)
Wayne Kerr 3260A + 3265A Precision Magnetics Analyser with Bias Unit	£5500
W&G PCM-4 PCM Channel measuring set	£3750

All equipment is used - with 30 days guarantee and 90 days in some cases.

Add carriage and VAT to all goods.

1 Stoney Court, Hotchkiss Way, Binley Industrial Estate
Coventry CV3 2RL ENGLAND

Tel: 02476 650 702

Fax: 02476 650 773

Web: www.telnet.uk.com

Email: sales@telnet.uk.com

3 COMMENT


Wireless, wireless everywhere

5 NEWS

- 16MW switch is fastest yet
- UK lags in Pb-free race
- Casimir force measured
- Robots swarm maps and searches



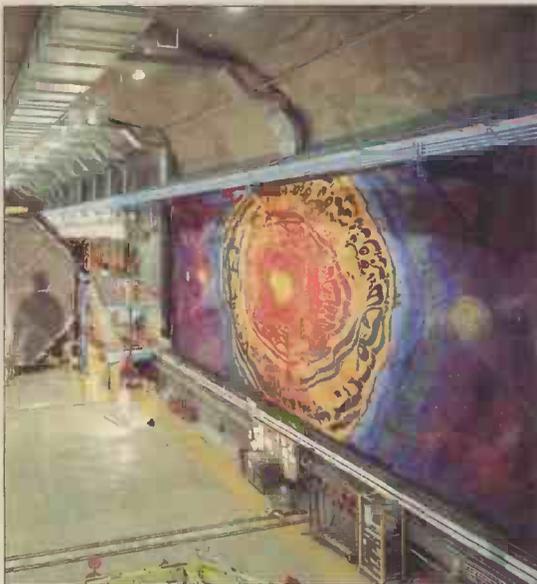- UK starts ceramic antenna research
- Second-generation DRM broadcast receiver
- Giant detector comes online



- Physics turns schoolkids off
- One step closer to SkyNet
- Chip de-thumps headphones
- Smart sand is more than silica

12 RTTY DECODER

Roger Thomas shares his love of long-range radio with this novel RTTY (teletype) decoder

22 THE MACROSCOPE

A practical project to produce a home-made scanning force microscope by Giacomo Torzo, Barbara Pecori, Pietro Scatturin and Giorgio Delfitto.

29 NEW PRODUCTS


The month's top new products.

38 CIRCUIT IDEAS

- Bipolar reference generator from a printer port
- Current-to-current converter
- Using multiple-purpose timer chip to build inverting SMPS

44 CAPACITOR & AMPLIFIER DISTORTIONS

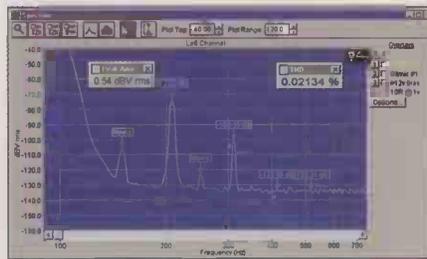Cyril Bateman continues using his 'de facto' distortion analyser with more practical measurements



51 LETTERS

- Historic receivers
- 1000lines, Green
- Content and focus
- Automotive audio systems
- De-bounce II
- Design for EMC
- Errors, nonsense and 'The question'
- Google search
- Understanding ADCs

56 TIME MACHINE

Accurate time measurement on a budget by John Morrison

60 WEB DIRECTIONS

Useful web addresses for electronics engineers.

READER OFFER
Buy a discounted, software configurable serial I/O card, courtesy of **Observant Electronics**.



Quasar Electronics Limited
 PO Box 6936, Bishops Stortford,
 CM23 4WP
 Tel: 0870 246 1826
 Fax: 0870 460 1046
 E-mail: sales@quasarelectronics.com

Add £2.00 P&P to all UK orders. 1st Class Recorded - £4.
 Next day (insured £250) - £7. Europe - £5. Rest of World - £10.
 We accept all major credit/debit cards. Make cheques/PO's
 payable to Quasar Electronics Limited.
 Prices include 17.5% VAT. MAIL ORDER ONLY.
 Call now for our FREE CATALOGUE containing details of
 over 300 electronic kits, projects and modules.



QUASAR 0871 CREDIT CARD SALES 717 7168 electronics

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, unipolar/bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (6A/100V)

Control the speed of almost any common DC motor rated up to 100V/5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15VDC. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£12.96**
 Assembled Order Code: AS3067 - **£19.96**

NEW! PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9V DC. PCB: 80x50mm. Kit Order Code: 3179KT - **£9.96**
 Assembled Order Code: AS3179 - **£16.96**



PC Controlled Dual Stepper Motor Driver

Independently control two unipolar stepper motors (each rated up to 3 Amps max.) using PC parallel port and software interface provided. Four digital inputs available for monitoring external switches and other inputs. Software provides three run modes and will half-step, single-step or manual-step motors. Complete unit neatly housed in an extended D-shell case. All components, case, documentation and software are supplied (stepper motors are NOT provided). Dimensions (mm): 55Wx70Lx15H. Kit Order Code: 3113KT - **£16.96**
 Assembled Order Code: AS3113 - **£24.96**



NEW! Bi-Polar Stepper Motor Driver

Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer. Supply: 8-30V DC. PCB: 75x85mm. Kit Order Code: 3158KT - **£12.96**
 Assembled Order Code: AS3158 - **£26.96**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU203 £9.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12VDC/6mA (standby). Two and Ten channel versions also available. Kit Order Code: 3180KT - **£41.96**
 Assembled Order Code: AS3180 - **£49.96**



Computer Temperature Data Logger

4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables. Kit Order Code: 3145KT - **£22.96**
 Assembled Order Code: AS3145 - **£29.96**
 Additional DS1820 Sensors - **£3.96 each**



NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130x110x30mm. Power: 12VDC. Kit Order Code: 3140KT - **£39.96**
 Assembled Order Code: AS3140 - **£69.96**




Serial Isolated I/O Module

PC controlled 8-Relay Board. 115/250V relay outputs and 4 isolated digital inputs. Useful in a variety of control and sensing applications. Uses PC serial port for programming (using our new Windows interface or batch files). Once programmed unit can operate without PC. Includes plastic case 130x100x30mm. Power: 12VDC/500mA. Kit Order Code: 3108KT - **£64.96**
 Assembled Order Code: AS3108 - **£64.96**



Infrared RC Relay Board

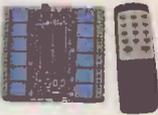Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12VDC/0.5A
 Kit Order Code: 3142KT - **£41.96**
 Assembled Order Code: AS3142 - **£69.96**



PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) **£16.00**
 18V DC Power supply (PSU201) **£6.96**
 Leads: Parallel (LEAD108) **£4.96** / Serial (LEAD76) **£4.96** / USB (LEADUAA) **£4.96**

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied complete with 40-pin wide-slot ZIF socket, box and Windows Software. Kit Order Code: 3128KT - **£49.96**
 Assembled Order Code: AS3128 - **£64.96**



Enhanced "PICALL" ISP PIC Programmer

Will program virtually ALL 8 to 40 pin PICs plus a range of ATMEL AVR, SCENIX SX and EEPROM 24C devices. Also supports In System Programming (ISP) for PIC and ATMEL AVRs. Free software. Blank chip auto detect for super fast bulk programming. Requires a 40-pin wide ZIF socket (not included). Kit Order Code: 3144KT - **£64.96**
 Assembled Order Code: AS3144 - **£69.96**



ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16-18VDC. Kit Order Code: 3123KT - **£29.96**
 Assembled Order Code: AS3123 - **£34.96**



NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Ideal for field use. Header cable for ICSP. Free Windows software. See website for PICs supported. ZIF socket not incl. Supply: 18VDC. Kit Order Code: 3149KT - **£29.96**
 Assembled Order Code: AS3149 - **£44.96**



www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

EDITOR**Phil Reed****p.reed@highburybiz.com****CONSULTANT****Ian Hickman****CONTRIBUTING EDITOR****Martin Eccles****EDITORIAL E-MAILS****EWeditor@highburybiz.com****EDITORIAL ADMINISTRATION****EWadmin@highburybiz.com****GROUP SALES****Reuben Gurunlian****01322 611292****ADVERTISEMENT****E-MAILS****r.gurunlian@highburybiz.com****CLASSIFIED FAX****01322 616376****PUBLISHING DIRECTOR****Tony Greville****ISSN 0959-8332****SUBSCRIPTION QUERIES**

Tel (0) 1353 654431

Fax (0) 1353 654400

Disclaimer

We work hard to ensure that the information presented in *Electronics World* is accurate. However, *Electronics World's* publisher - Highbury Business Communications - will not take responsibility for any injury or loss of earnings that may result from applying information presented in the magazine. It is your responsibility to familiarise yourself with the laws relating to dealing with your customers and suppliers, and with safety practices relating to working with electrical/electronic circuitry - particularly as regards electric shock, fire hazards and explosions.

Wireless, wireless everywhere.....

And half of it doesn't work. I reported a few months ago about the trouble I was having with getting a simple Bluetooth connection going between my laptop and a GPRS phone. Well, I have to admit defeat - the Nokia and Belkin softwares combine to be the most hideous piece of code and I'm now using infra-red.

The point of this, as I said at the time, is that we as engineers need to make this kind of technology accessible to the average member of the public for it to be successful, so that lots of people buy it and in the long term to keep us all in a job.

I've just had a similar 'radio' experience by putting in a Wi-Fi network at home. In fact, setting up the network and even the ADSL router was extremely easy. The software and instructions from the 'black box' maker (D-Link) and the installation instructions from my ISP (Pipex) combined on this occasion to make the project go very smoothly.

I look forward to more 'public' Wi-Fi points opening up in the future - although the small bandwidth allocated thus far is getting very cluttered. It will be wonderful, though in the not too distant future to be able to hook up to a proper, high-speed network, just using the adaptor in the laptop as opposed to hooking into other (not very reliable) networks. The hugely indebted G3 franchise holders could also learn a lesson or two. Whilst they are scrabbling around looking for a 'killer app' - the business community needs high-speed data on the move and is willing to pay for it. Sending your mates stupid videos or watching sports highlights on the phone is not going to do repay the huge fees these networks have had to shell out

to unscrupulous governments selling off bandwidth. But the plus side is that the proliferation of all this mobile networking can only help our industry back on its feet.

More housekeeping

As I reported last month, we are still experiencing problems with our admin without a new 'Jackie'. Readers who have been waiting for our offers will be pleased to hear that they have all been dispatched (in fact, by the time you read this I will be sunning myself in Rhodes and you will have received your goods. And of course look out for a new reader offer for those who were unlucky in our competition last month. You can buy an Observant Datastation development kit for £20 off (see page 42).

Phil Reed

New editorial and advertising address

The Highbury Business Communications office previously at Cheam, Surrey has moved to Swanley in Kent. All correspondence intended for the editorial and advertising departments should be addressed to:

Electronics World,
Highbury Business Communications,
Nexus House,
Azalea Drive,
Swanley,
Kent, BR8 8HU

The switchboard phone no. is
01322 660 070
Advertising sales (Reuben Gurunlian)
Tel 01322 611292
Fax 01322 616 339

Electronics World is published monthly. Orders, payments and general correspondence to Jackie Lowe, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU

Newstrade: Distributed by COMAG, Tavistock Road, West Drayton, Middlesex, UB7 7QE Tel 01895 444055.

Subscriptions: Wyvern Subscription Services, Link House, 8 Bartholomew's Walk, Ely Cambridge, CB7 4ZD. Telephone 01353 654431. Please notify change of address.

Subscription rates
1 year UK £38.95 O/S £64.50
US\$100.62 Euro 102.55

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar (Calchester) Ltd,
Filmsetting by Impress Repro By Design
A1 Parkway, Southgate Way, Orton Southgate,
Peterborough, PE2 6YN



HIGHBURY
Business Communications

A SUBSIDIARY OF HIGHBURY HOUSE COMMUNICATIONS PLC

THERE IS INTERESTING NEWS

THE FIRST USB 2.0
100 MS/S, 12-16 bit
MEASURING INSTRUMENT
IN THE WORLD

PC CONTROLLED MEASURING INSTRUMENT
COMPLETE PACKAGE STARTING AT £ 435

OSCILLOSCOPE


FFT ANALYSER

VOLTMETER

RECORDER

The Handyscope 3 is a powerful and versatile two channel measuring instrument with an integrated function generator.

- USB 2.0 connection (USB 1.1 compatible)
- sample speed up to 100 MHz per channel
- 8 to 16 bit resolution (6 μ Volt resolution)
- 50 MHz bandwidth
- input sensitivity from 200 mVolt up to 80 Volt
- large memory up to 131060 samples per channel
- four integrated measuring devices
- spectrum analyser with a dynamic range of 95 dB
- fast transient recorder up to 10 kHz
- several trigger features
- auto start/stop triggering
- auto disk function up to 1000 files
- auto setup for amplitude axis and time base
- auto trigger level and hysteresis setting
- cursor measurements with 21 read-outs
- very extensive function generator (AWG) 0-2 MHz , 0-12 Volt

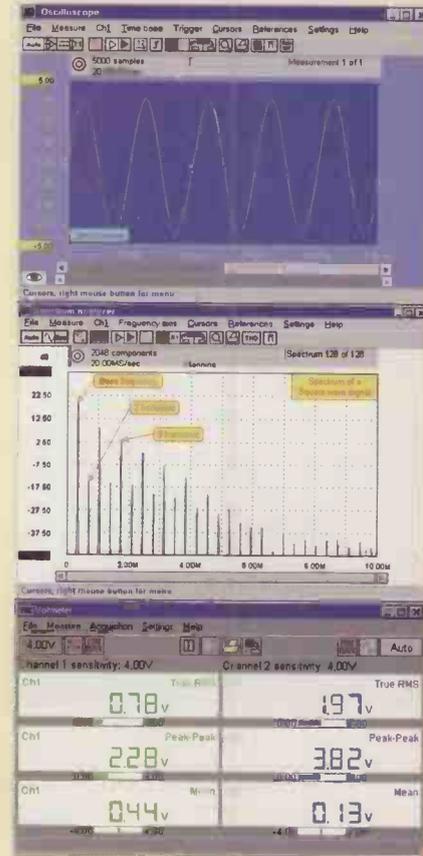

for more information, demo software, software, source code and DLL's visit our internet page: <http://www.tiepie.nl>



TiePie engineering (NL)
Koperslagersstraat 37
8601 WL SNEEK
The Netherlands
Tel: +31 515 415 416
Fax: +31 515 418 819

TiePie engineering (UK)
28, Stephenson Road, St. Ives
Cambridgeshire, PE17 3WJ, UK
Tel: 01480-460028
Fax: 01480-460340

16MW switch is fastest yet

Researchers at the US Virginia Tech have developed a high-power semiconductor switch.


Called an emitter turn-off thyristor (ETO), it operates without snubber circuits and can be controlled fibre-optically.

"An optical pulse is applied to turn on current flow. It can conduct 10,000 amps of current and will withstand 16MW of instantaneous power," said Professor Alex Huang of Virginia's electrical engineering department.

For continuous operation, the ETO can carry 1.5kA (at 125°C) and block

6kV. Switching time is 5µs, on or off. "This switch allows us to advance very high power converters from a line speed of 60Hz to 3kHz switching at the same power level," said Huang. "This speed allows you to chop the voltage into whatever shape you need."

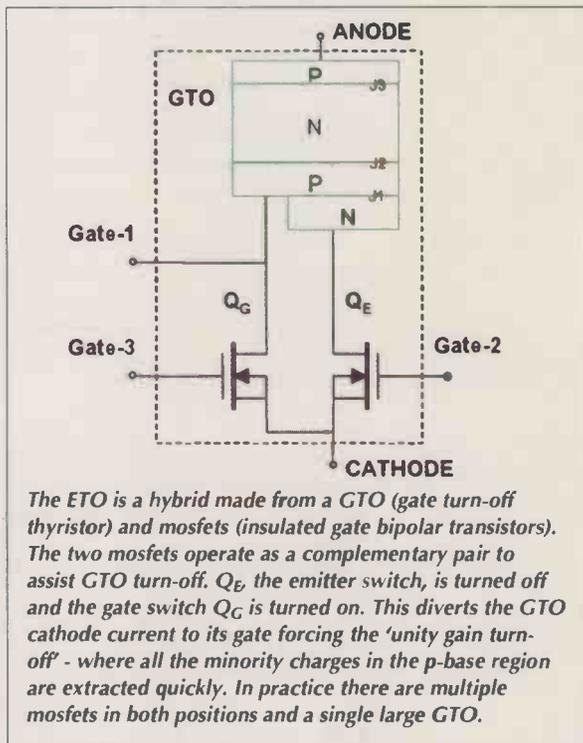Present technology is the GTO (gate turn-off thyristor). "The GTO is reliable and inexpensive, but requires a snubber capacitor to protect it in the turn-off process," said Virginia, "The snubber uses significant power itself and increases the size of the switch."



The ETO is a hybrid made from a GTO (gate turn-off thyristor) and mosfets (insulated gate bipolar transistors). The two mosfets operate as a complementary pair to assist GTO turn-off. Q_E , the emitter switch, is turned off and the gate switch Q_G is turned on. This diverts the GTO cathode current to its gate forcing the 'unity gain turn-off' - where all the minority charges in the p-base region are extracted quickly. In practice there are multiple mosfets in both positions and a single large GTO.



UK lags in Pb-free race

The British electronics industry has its head in the sand over the ban on lead-based solders and components, said ERA Technology.

The Surrey-based research firm has surveyed the UK electronics industry to find how ready it is to make the transition from tin/lead solders to lead-free solders, and lead-free components

"Only three per cent of companies have developed lead-free products, only nine per cent of companies have started trials

with lead-free solders and 50 per cent of companies admit they don't understand the impact of banning lead-based solders," said ERA.

The EU 'Restriction of use of certain Hazardous Substances' (RoHS) directive bans lead from many finished electronic and electrical products from July 1st 2006.

"While the deadline may seem a long way off, there are currently no lead-free solders that are direct replacements for use in all existing products," said ERA,

"All lead-free solders are different in their properties and the way they need to be used."

Over 150 small, medium and large size companies were questioned by ERA. "These were a broad cross-section of the country's electronics industry, which means the findings are truly representative," said ERA. "The good news is that 87 per cent of the sample at least knew about the RoHS directive, and half had contacted one supplier." www.era.co.uk/product/lead-free-survey.htm to buy the report.

Casimir force measured

Physicists in the US have made a more accurate measurement of the Casimir force, that pushes together objects at close separations. The work could result in better photonic mirrors and nanomachines.

"The Casimir force is not a new discovery," said Purdue University's Professor Ephraim Fischbach. "Its effects on machines are essentially negligible until you start building at

the nanoscale. When the teeth of two tiny gears come together, for example, the Casimir force could push them together so strongly that they would stick and freeze up."

First predicted by Hendrik Casimir of Philips Research Labs in 1948, the force is due to the fact that objects close together cannot fit any photons, real or virtual, between them. Thus photons striking the outside of the

objects push them together.

In experiments the forces have been measured at up to 1nanonewton, or 100µ dynes. Purdue's work has proven the theory within one per cent of experiment, which should lead to better modelling.

"It is not often you get to unify theory and practice this closely," said Fischbach.

Robot swarm maps and searches

US research institute SRI has made 100 Centibots to map and search unknown spaces.

"As totally self-contained, untethered entities, these robots can determine their own location and plan their own path, process images they see, make decisions based on a continually expanding knowledge base, and negotiate with other robots when teamwork is required," said SRI's Artificial Intelligence Center.

There are two types of Centibot. Mapping robots with laser range finders enter an area first, followed by a larger second wave of tracking robots that search.

As they move, the robots create an adhoc 802.11 (WiFi) network to enable all machines to stay in touch with the control centre which directs the swarm.

The robots run the Debian distribution of Linux and use a software control system developed the Artificial Intelligence Center that was first created as an integrated architecture for robot perception and action.

Processing power comes from 1GHz mini-ITX size PC motherboards from VIA - which recently launched a Robotics Initiative "in response to the



inexorable melding of mechanical robots and the PC architecture", it said.

The Centibots project is sponsored

by the US military Defense Advanced Research Projects Agency (DARPA). www.ai.sri.com/centibots www.viaarena.com

UK starts ceramic antenna research

Leatherhead technology firm ERA Technology has begun a research programme on antenna technology using ceramic structures.

"The new technology will combine the efficiency and bandwidth of conventional antennas with the compactness of current ceramic designs," said the firm.

ERA will use the low temperature co-fired ceramic (LTCC) process to create complex 3D structures.

The technique could also lead to low cost phased arrays, said the firm, by combining conductors and active circuits in the same ceramic block.

"This new technology is a real breakthrough because of its versatility, compact size and low manufacturing cost," said Dr Robert Pearson, head of ERA's antenna business.

"In military applications, it offers favourable radar and electromagnetic

compatibility characteristics and therefore can be used as a fundamental building block on a range of future military platforms. As a bonus, the construction technique also offers exceptionally high temperature performance, making it ideal for fast jets and missiles.

Operating bandwidths will be better than ten per cent, claimed ERA, while the antennas could be configured as multiband devices.


A Cambridge University researcher has found that coating carbon nanotubes with conducting polymers could lead to supercapacitors that rival existing technology.

Dr Mark Hughes from the department of materials science and metallurgy found that both of the two materials have desirable properties and has worked on merging them.

Carbon nanotubes have high conductivity and a large surface area, while the conducting polymers, such as polypyrrole, can be oxidised and reduced easily and quickly, allowing many charge and discharge cycles.

When combines, these two materials offer a high capacitance material of more than 2.6Fcm^2 .

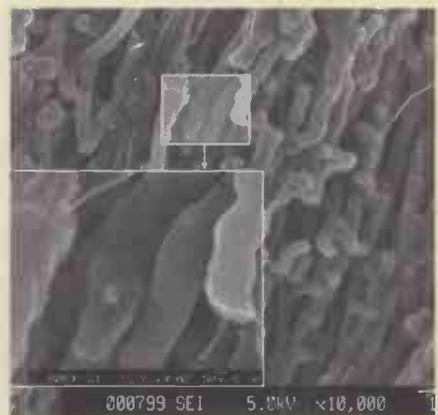The capacitance is more than double that of either material on its own, said Hughes.



These SEM images show (a) randomly oriented and (b) aligned composites of carbon nanotubes and polypyrrole.

Second-generation DRM broadcast receiver

A second-generation DRM (Digital Radio Mondiale) receiver has been announced by Coding Technologies.

A joint venture with Munich-based product design house Mayah, the radio is smaller (21 x 7 x 13cm) than the 29 x 7 x 19cm \approx 1,000 first-generation design, will be cheaper, said Coding, and also receives standard AM transmissions.

DRM is the digital transmission standard chosen by most of the world's broadcasters to replace analogue AM on shortwave, mediumwave and longwave.

Coding is the company behind the audio compression technology which makes it possible to fit good quality audio into the limited spectrum normally allocated to an AM broadcast channel - hence its interest in popularising the format by developing receivers. "Now that many radio stations already broadcast a full DRM programme daily, these first mass-produced receivers will open the path to the end consumer for affordable access to Digital Radio Mondiale broadcasts," said Coding.

Called Spectral Band Replication

(SBR), Coding's technology allows a fictitious but realistic spectrum from 7kHz upwards to be generated from an audio signal low-pass filtered to below 7kHz, plus some 'helper' information.


Part of the helper information is the shape of the discarded upper spectrum and SBR generates harmonics of the low-pass filtered signal to fit the original upper spectrum profile. Other helper information describes significant signals above 7kHz which were not harmonically related to lower frequencies.

The sub 7kHz signal is compressed using standard MPEG 4 AAC audio compression.

The whole scheme is called aacPlus, where the Plus is SBR. "aacPlus delivers streaming and downloadable 5.1 multi-channel audio at 128Kbit/s, CD-quality stereo at 48Kbit/s, excellent quality stereo at 32kbit/s, and excellent quality for mixed content at 20Kbit/s mono and below," said Coding.

www.mayah.com

www.codingtechnologies.com

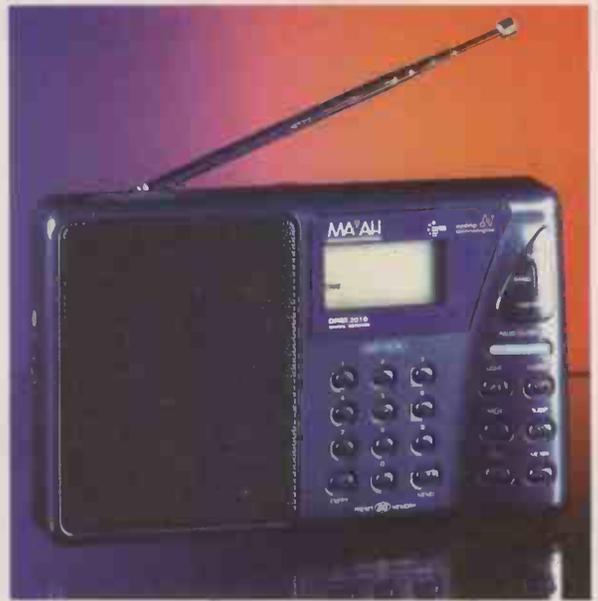

What does it sound like?

Electronics World heard a demonstration of aacPlus audio.

It is much more like the sound of FM on VHF or MP3-encoded material than AM on MW. The simulated upper frequencies don't sound synthetic to the casual listener - although more experienced people might of course be able to spot the difference between FM and aacPlus on MW.

Giant detector comes online

UK scientists have started receiving data from the 6,000 ton MINOS detector located in an iron mine in northern Minnesota.

Minos - the Main Injector Neutrino Oscillation Search - hopes to gain more understanding of the neutrino mass.

"The MINOS detector in Soudan, Minnesota, together with the new Fermilab neutrino beam line, will provide a detailed look at the secrets behind neutrino

oscillations," said Dr Raymond Orbach, director of the US department of energy's office of science.

MINOS is over 30m in length and took more than four years to build. Its 486 steel plates are each about 7m high and are coated with scintillating plastic.

The detector is said to be able to tell the difference between neutrino and anti-neutrino interactions. Eventually neutrinos

'made' in Illinois will be sent through 450 miles of the earth directly to MINOS. Out of one trillion neutrinos per year, only about 1,500 will collide with an atomic nucleus in the detector.

Scientists hope to discover more about the three known types of neutrino - electron, muon and tau - and how they switch from one to another as they move through space and matter.



1kW output from fibre laser

A fibre optic laser with an output power exceeding 1kW has been developed by Southampton Photonics (SPI) and Southampton University's Optoelectronics Research Centre (ORC).

While higher power fibre lasers have been reported, these are (optically) less pure multi-mode systems.

"Breaking the kW barrier with a

single fibre having high beam quality is a milestone thought to be virtually unattainable just a few years ago," said David Payne, SPI's chairman and director of the ORC.

SPI uses a cladding pump technique for its fibre lasers, which allows a multi-mode source to produce single-mode output. Light from a diode stack is launched into the inner cladding of a double-clad single-

mode fibre. The pump light propagating through the inner cladding excites the rare-earth elements in the core, in this case ytterbium, producing single mode light at 1090nm.

The firm has quadrupled its output power of these lasers since February. It will produce commercial versions for industrial and aerospace applications.

FogScreen is a walk-through display made of fine mist. "The key features are that the screen is flat and thin, enabling high-quality projections," said the Finish firm. "It feels like nothing and does not make things wet."



Book-sized PC for servers

Taiwanese PC component maker VIA has introduced a new series of motherboards in the 17 x 17cm mini-ITX format, aimed at networked systems "enabling the development of a wide variety of networking applications including servers, firewalls, and routers", said VIA.

Called the EPIA CL-Series, the boards have dual 10/100 Mbit/s LAN controllers, six USB 2.0 connectors for peripherals, four serial COM ports for older peripherals, support for LVDS embedded LCD panels and a PCI slot for expansion.

The soldered-in processor is VIA's own x86-compatible range including the fanless 677MHz Eden (CL6000), the 800MHz C3 (CL8000) and the CL1000 that uses VIA's top-end 1GHz Nehemiah chip.

All boards have a hardware MPEG-2 decoder and integrated graphics core.

www.via.com.tw

Physics turns schoolkids off

A-level entries for physics and other science subjects have fallen again, according to figures from the Institute of Physics.

The number of students taking A-level physics dropped by three per cent this year.

On the positive side, said the IoP, the ten year trend which has seen entries dropping from 60,000 to 30,000 is slowing.


The IoP blamed subjects such as

law and media studies for the declining fortunes of science subjects. In its promotion of the hard sciences it points to evidence that science graduates "have higher salaries than arts and humanities graduates in later life".

A shortage of physics teachers is being addressed by a £750,000 investment from the IoP in supporting development of teachers of 11 to 14-year olds.

Future Electronics is offering a development kit for low power radios using the 433, 868 and 915MHz frequencies. The radios make use of the Xemics XM1202

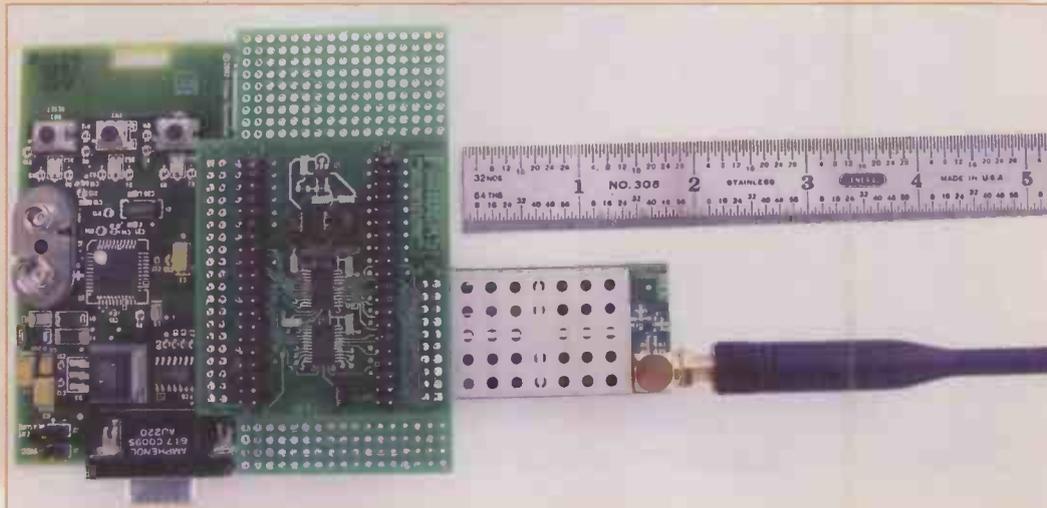RF transceiver module and Motorola's '908 microcontroller. The combination allows 'drop-in' designs to be created that will meet FCC/CE/ETSI certification, said Future. The module takes RS232 data and transmits over the RF link at between 4.8kbit/s and 76.8kbit/s. Output power can be programmed up to 15dBm (31.5mW).



112003



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ

Prices Exclude Vat @17.14%
UK Carriage £1.50 (less than 1kg)
£3.50 greater than 1kg

Cheques / Postal orders payable to
ESR Electronic Components
PLEASE ADD CARRIAGE & VAT TO ALL ORDERS

See Next / Last Months Ad. for ELECTRONIC COMPONENTS

PCB Production - Development
0.1" Copper Stripboard

Size	Tracks/Holes	£0.24
25 x 64mm	9T / 25H	£0.24
64 x 95mm	24T / 37H	£0.87
95 x 127mm	36T / 50H	£1.41
95 x 432mm	36T / 170H	£4.39
100 x 100mm	39T / 38H	£1.40
100 x 160mm	39T / 63H	£1.80
100 x 500mm	39T / 199H	£6.20
119 x 455mm	46T / 179H	£5.40

Stripboard track cutter
Solderless Breadboard
Tie Points & Size Power Rails
390 81 x 60mm 2 £2.75
840 175 x 67mm 2 £4.86
740 175 x 55mm 1 £4.03
640 175 x 42mm 0 £3.08

Many other sizes available,
also jump wires & matrix board.

PCB Production - Drafting Materials
A4 Artwork Film (per 10 sheets)
Clear Manual Film £1.25
Clear Laser Film £1.75
White HQ Laser Film £4.62

Etch Resist Pens
"Dalo" Pen £2.70
"Sigaretter" Fine Pen £0.88

Etch Resist Transfers
Seno mixed DIL pads £2.24
Seno mixed Rnd pads £2.24
Alfac mixed pads £1.84
Alfac mixed lines £1.84
Transfer Spatular £1.25

We carry the full range of Seno & Alfac PCB transfers, see our catalogue for full details.

Soldering Irons
We carry in stock a wide range of soldering iron and soldering accessories. Irons from 12 to 100 Watts.

15W 240V Low cost	£2.80
20W 240V Basic	£3.74
25W 240V Ceramic	£14.05
30W 240V Basic	£4.68

Solder Pumps
Basic 165 x 18mm £2.85
Antistatic 195mm £3.92
Antex Mini 198mm £6.02
Antex Pro 210mm £10.26

Soldering Station
A 48W adjustable temperature soldering station with a rotary dial, LED Temperature metering, on-off switch, iron holder and tip cleaning sponge. This station features accurate heat sensing for instant compensation & stable temperatures. Adjustable temperature range of 150 - 420°C. Low voltage iron with Silicone cable.
Supply: 240V, Iron: 24V 48W
Model 167-540 £44.50

Soldering Station
A 48W adjustable temperature soldering station with a rotary dial, Digital Temperature Indication, on-off switch, iron holder and tip cleaning sponge. This station features accurate heat sensing for instant compensation & stable temperatures. Adjustable temperature range of 150 - 480°C. Low voltage iron with Silicone cable.
Supply: 240V, Iron: 24V 48W
Model 167-570 £58.75

CCTV - Complete Systems
We carry the full range of Micromark Black & White and Colour CCTV systems for the home or office.

These complete easy install systems are supplied complete with power supply, cables and all fixings. Simple plug-in connections, for use with any TV or Video with a scart socket.

Black & White Systems from £22.97

CCTV - Black & White Module
A miniature CMOS camera module with a 3.6mm F2 Lens, video output & power via connectors provided.
Specs (660-800)
Power: 12Vdc 50mA
Video System: CCIR
Pixels: 352 x 288
Min Illumination: 0.5Lux
Video Output: 1 Vpp, 75Ω
Dims: 35 x 35 x 28mm 20g **£17.93**

PCB Production - Processing Equipment
We carry a large range of the photographic & chemical processing equipment for PCB production, a full list with full technical specifications is available in our catalogue or visit our web site.

UV Exposure units
2 x 8W Tubes, 6 min timer
229 x 159mm working area
Model 332-002 £88.78
4 x 15W Tubes, 7 1/2 min timer
330 x 260mm working area
Model 332-004 £194.51

Chemical Processing
Low cost plastic tray £1.50
Process tanks feature electrically operated pumps and/or heaters with thermostat control, suitable for boards upto 320 x 260mm.
Universal Tank with heater
Model 333-007 £161.60
Bubble etch Tank with heater & bubble pump.
Model 333-004 £198.50

Any of these items, carriage £5.50

PCB Production - Tools
Drill Bits
HSS parallel shank bits available in sizes from 0.3mm to 2.0mm
0.3-0.95mm in 0.05mm steps £0.60ea £4.00/10
1.0-2.0mm in 0.1mm steps £0.40ea £3.60/10
HSS Reduced Shank (2.35mm) bit available in sizes from 0.6mm to 1.7mm in 0.1mm steps £0.84ea £7.60/10
Reground Tungsten carbide reduced shank (3.2mm) available in sizes from 0.6 to 1.6mm in 0.1mm steps £1.90

Drilling Machines
Expo reliant 12V drill, 3.8mm capacity, 8400rpm £12.78

Minicraft MX1 230V, 8000 - 21000rpm with chuck & collet.
Model EPE270-390
Normal price £48.51

**** SPECIAL OFFER PRICE £31.02 ****

Servisol Products
Aerosols

200ml Switch Cleaner	£1.96
200ml Freezer	£3.97
400ml Foam Cleanser	£2.13
400ml Cleaner / lubricant	£2.79
75ml Vide Head Cleaner	£1.94
200ml Aero Klene	£2.85
200ml Aero Duster	£4.66
250ml Cold Clean	£3.14
200ml Label remover	£3.52
400ml Isopropyl alcohol	£3.36

Tubes
25g Heatsink Compound £2.60
50g Silicone grease £2.50

NEW CATALOGUE OUT NOW
available from www.esr.co.uk

Educational Kits
These kits are an ideal way to start your interest in electronics. They feature re-usable components which are attached via springs & wires and easy step by step guides to make a range of exciting projects. The 300-in-1 features a breadboard for more complex circuits.

30-in-1	£12.80
50-in-1	£16.80
150-in-1	£22.00
300-in-1	£55.20

Panel Meters
High quality analogue panel meters, class 2, zero point correction, mirror scale and wired for panel illumination. Meter size 46 x 60mm, Cutout size: 38mmØ.

Range	Int Ω	All meters £5.89 each 6V Lamps £1.23 /pair
0-500µA	6k5	
0-100µA	1k0	
0-500µA	430Ω	
0-1mA	200Ω	
0-10mA	20Ω	
0-50mA	1Ω2	
0-100mA	0.265	
0-500mA	0.12	
0-1A	60mΩ	
0-3A	20mΩ	
0-5A	12mΩ	
0-15A	4mΩ	
0-10V	10k	
0-15V	15k	
0-30V	30k	
±50µA	1k9	

CCTV - Colour Module
A miniature colour CMOS camera module with a 3.6mm F1.2 Lens, video output & power via connectors provided.
Specs (660-842)
Power: 12Vdc 150mA
Video System: PAL
Pixels: 628 x 582
Min Illumination: 3Lux
Video Output: 1 Vpp, 75Ω
Dims: 28 x 28 x 28mm 20g **£36.33**

PCB Production - Laminates
Copper clad - paper
Single sided low cost paper composite board

100 x 160mm Board	£0.44
100 x 220mm Board	£0.62
160 x 233mm Board	£1.02
220 x 233mm Board	£1.40
8" x 12" Board	£1.70

Copper clad - glass fibre
Single & Double 1.6mm 305g/m²

100 x 160mm Single	£0.85
100 x 220mm Single	£1.18
160 x 233mm Single	£2.29
220 x 233mm Single	£2.88
8" x 12" Single	£3.44
100 x 160mm Double	£0.88
100 x 220mm Double	£1.25
160 x 233mm Double	£2.30
220 x 233mm Double	£2.90
8" x 12" Double	£3.50

Photoresist Coated
1.6mm 35 micron Pre-coated with a high quality photoresist layer. Available in low cost paper composite or Glass fibre, Single & Double sided. Other sizes also available.

Size	Paper		Glass Fibre	
	Single	Double	Single	Double
4 x 6"	£1.47	£1.82	£1.89	£2.17
6 x 12"	£4.20	£5.04	£5.60	£6.23
8 x 12"	£6.30	£7.70	£8.40	£9.38
10 x 12"	£8.19	£10.01	£10.78	£11.83
12 x 12"	£8.26	£10.08	£10.99	£12.25
100 x 160mm			£2.38	£2.66
203 x 114mm			£3.01	£3.43
220 x 100mm			£3.08	£3.71
233 x 160mm			£4.83	£5.32
233 x 220mm			£6.83	£7.70

PCB Production - Chemicals

100ml Aerosol Photoresist spray, covers 2m ²	£4.25
50g Powder developer, makes 1lt	£1.09
500g Powder developer, makes 10lt	£7.08
250g Ferric Chloride Pellets, makes 500ml	£1.68
500g Ferric Chloride Pellets, makes 1lt	£3.04
2.5kg Ferric Chloride Pellets, makes 5lt	£9.84
1.1kg Clear Fine etch crystals, makes 5lt	£17.58
90g Tin Plating Powder, makes 1lt	£11.58
200ml Aerosol Flux spray	£3.41
110ml Aerosol PCB Laquer spray	£3.63

Magnifying Desk Lamp
A high quality scratch resistant magnifying glass fitted to a balanced swivel arm and desk mount. An integral fluorescent tube provides illumination.
Magnification: 3x Lens: 120mmØ
Tube: 22W Daylight simulation.
Model: 028-205 £28.80

Tools - Cutters & Strippers
We carry a wide range of specialist tools for the electronics industry including:

Side Cutters

130mm Low cost	£1.99
115mm Draper	£2.38
115mm Box Jointed	£4.26
145mm Long reach	£3.40

Wire Strippers
130mm Low cost £2.30
150mm Draper 5mmØ £5.86

Tools - Ratchet Crimping Pliers
High quality ratchet crimping pliers for various terminals including Automotive, Data, Power and Data connections.

Red / Blue / Yellow	£15.80
BNC / TNC RF series	£15.19
RJ11/12 Data Series	£22.32
RJ45 Data Series	£21.20
RJ11/12 & 45 Series	£13.00

CKO Tools Crimp Pliers
Green/Red/Blue £24.38
Red/Blue/Yellow £21.42
0.24-2.5mm² crimps £24.35
0.5-6.0mm² crimps £24.35
Non insulated crimps £24.38

Cable - Ribbon
7/0.127mm Grey ribbon cable on a 0.05" 1.27mm pitch with a red identifying stripe. Supplied by 305mm (1ft) or on full 30.5m (100ft) reels.

Size	per 305mm	per Reel
10 Way	£0.10	£5.36
14 Way	£0.14	£7.50
16 Way	£0.16	£8.58
20 Way	£0.20	£10.70
26 Way	£0.26	£13.94
34 Way	£0.34	£18.22
40 Way	£0.40	£21.44
50 Way	£0.50	£26.80
60 Way	£0.64	£33.92
IDC Crimp tool		£11.80

CAT5e Networking
UTP Cable
305m Box, conforms to CAT5E 100MHz standard, ETA verified TIA/EIA 568-B.2

Only £25.99 per box exc carriage.

RJ45 Outlet Kit
Backing Box
2 Gang Plate
RJ45 Module
Blank Module
Colour coded id inserts.
special price £3.14

Tools
Plastic punch down tool & cable stripper £1.42
Professional punch down IDC & trim tool £8.50

NOW in Stock
Patch & Cross-over leads from £0.50, Full range of outlet modules/keystone outlets & accessories.

One step closer to SkyNet

US computer scientists are to test a prototype of Cyberinfrastructure, the technology which will eventually support its inter-supercomputer data grid.

The prototype, NPACI Grid, is from the US National Partnership for Advanced Computational Infrastructure and will connect its main resource sites: at the San Diego Supercomputer Center (SDSC), the Texas Advanced Computing Center (TACC) in Austin, TX, and the University of Michigan, Ann Arbor.

It will then be extended to the California Institute of Technology, Pasadena.

"NPACI Grid is a production,

heterogeneous national Grid consisting of interoperable software, scientific applications, and hardware resources," said the organisation. "It unifies mature software infrastructure efforts through the development of the interoperable, tested and hardened 'NPACKage' deployed at all resource sites."

Other parts of Cyberinfrastructure development are US National Science Foundation's NSF Middleware Initiative (NMI) and TeraGrid/ETF project.

The hardware resources in the NPACI Grid are a 1.7Tflop AIX cluster, Blue Horizon at SDSC, a 435Gflop AMD based Linux cluster

at the University of Michigan and three large shared-memory server nodes at TACC delivering 1.16Tflop.

Smart sand is more than silica

Grains of sand might be worth a second glance if research at five of Scotland's leading universities comes to fruition.

A team from the universities of Edinburgh, Glasgow, Napier, St Andrews and Strathclyde has just won a £1.3m grant to develop networked computers as small as sand grains.

The project, called Speckled Computing, aims to integrate modest amounts of digital signal processing, an RF transceiver, power source and sensors.

Professor DK Arvind, director of Edinburgh's Institute for Computing Systems Architecture, said the project will proceed in two stages: "The aim is to produce these specks in a millimetre cubed of semiconductor." There is an intermediate stage of 5mm³ in two years, with the final mm³ in four years."

Although each device will not have large amounts of processing power, because they are networked they will form a distributed system.

Arvind said the power source will be a photovoltaic cell, made using a gallium arsenide process. The radio will also use GaAs, while digital sections will use CMOS. The two sections will be bonded together.

Qinetiq wins windfarm funding

Defence technology research firm Qinetiq has won funding from the DTI to develop 'stealthy' wind turbine blades.

Qinetiq hopes that by modifying their glass fibre reinforced polymer construction, it can reduce the unwanted radar reflections from the blades.

Air traffic control, marine navigation, weather monitoring and Ministry of Defence systems are all affected, it said.

NOI Scotland with work with Qinetiq on the blades. The firm, originating from Germany, has technology for building 50m, resin-infused blades suited to offshore turbines producing 2MW more more.


"This is an excellent example of how the results of military research can be exploited

for civil gain," said Steve Appleton, the Qinetiq technical leader of the DTI project.

The UK Government has set ambitious targets for clean energy production, with ten per cent of the countries energy to come from sustainable sources by 2010, and 20 per cent by 2020.

Despite our constant complaints about wind, the UK has only the eighth largest amount on installed wind generating power in the world at 570MW. Germany tops the list with 12,000MW, while the US has 4,700MW and Spain 5,000MW.

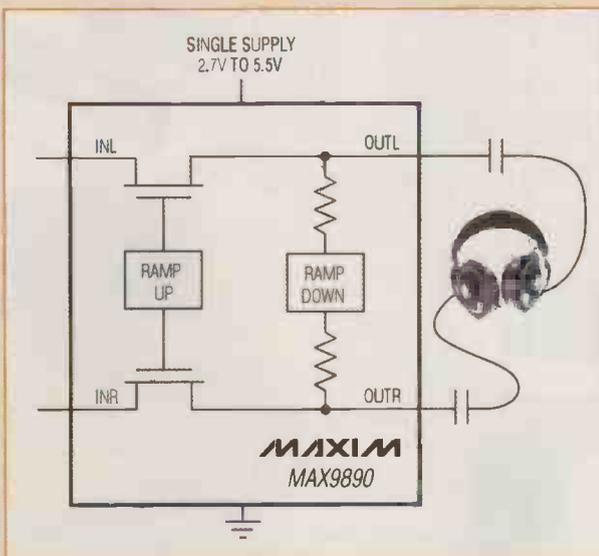According to the British Wind Energy Association, last year over a quarter of all proposals for windfarm developments were the subject of objections from radar operators.



Chip de-thumps headphones

Maxim has revealed a novel chip which removes switch-on clicks and thumps from headphones.

The MAX9890, as it is called, is placed between amplifier and headphone socket and open-circuits both left and right paths until transients are under control.

The device requires only one additional 0.1µF capacitor and deals with switch-off transients as well.


Applications in portable equipment such as notebook, phones, DVD players and PDAs are foreseen, particularly where an existing model has a click problem, or the thump-prone audio amplifier is part of a larger chip which cannot be designed out.

There are two versions. The MAX9890A for use with DC-blocking capacitors of up to 100µF and the 9890B for capacitors up to 220µF

Supply is 2.7V to 5.5V, 23dB of click-and-pop suppression is provided, supply current is 20µA and added THD+N is under 0.006% into a 32Ω load. Package is either 1.5 x 1.5 x 0.6mm (9-pin) or an 8-pin 3 x 3 x 0.8mm.

PROTEUS

The Complete Electronics Design System

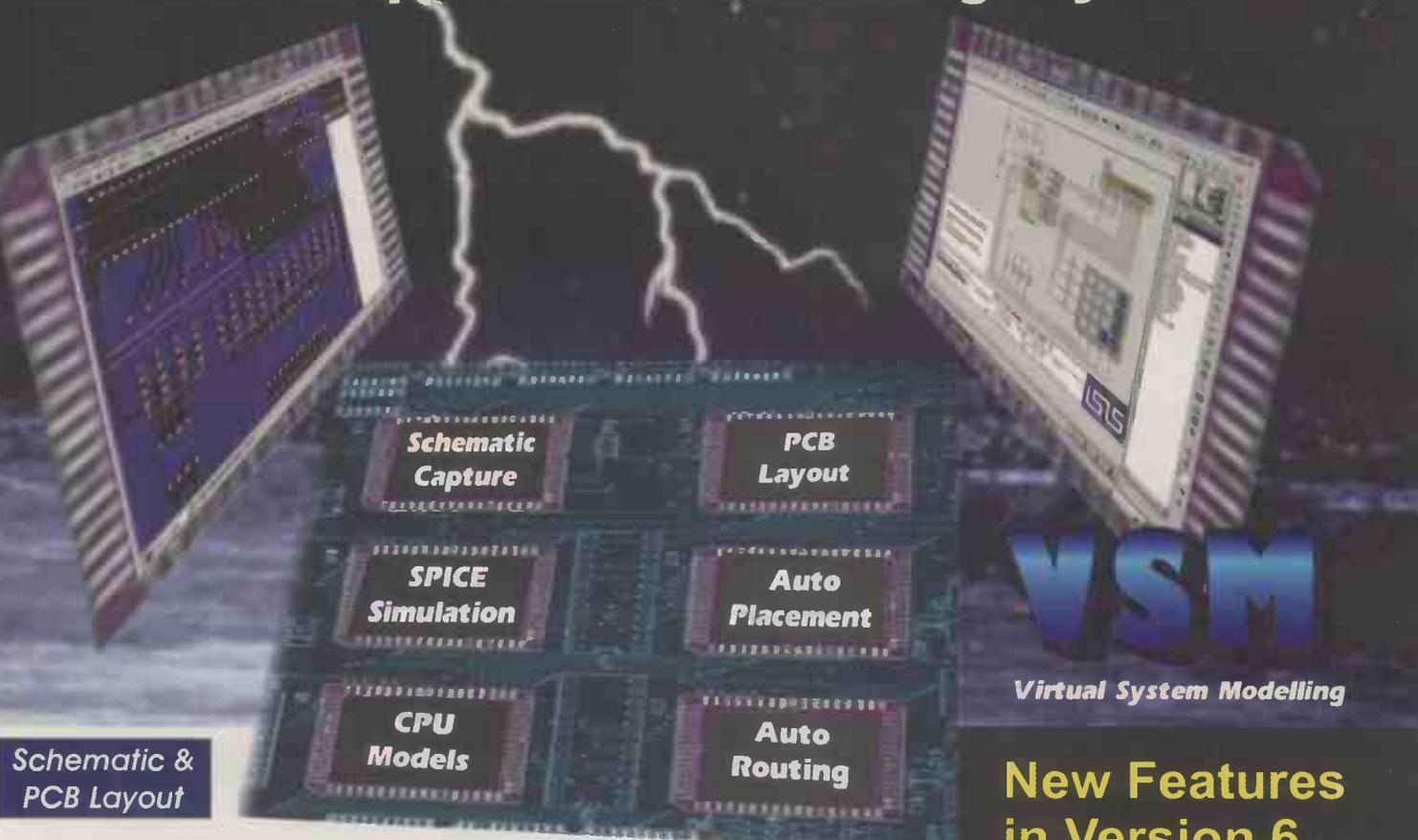

Schematic & PCB Layout

Schematic Capture

PCB Layout

SPICE Simulation

Auto Placement

CPU Models

Auto Routing

VSM
Virtual System Modelling

New Features in Version 6

- Powerful & flexible schematic capture.
- Auto-component placement and rip-up/retry PCB routing.
- Polygonal gridless ground planes.
- Libraries of over 8000 schematic and 1000 PCB parts.
- Bill of materials, DRC reports and much more.

- Drag and drop toolbars.
- Visual PCB packaging tool.
- Improved route editing.
- Point and click DRC report.
- Multiple design rules (per net).
- Multiple undo/redo.

Mixed Mode SPICE Circuit Simulation

- Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- 6 virtual instruments and 14 graph based analysis types.
- 6000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

Call Now for Upgrade Pricing

Proteus VSM - Co-simulation and debugging for popular Micro-controllers

- Supports PIC, AVR, 8051, HC11 and ARM micro-controllers.
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Provides source level debugging for popular compilers and assemblers from Crownhill, IAR, Keil, and others.

**Works with
PIC Basic Plus
from Crownhill
Associates**

labcenter

Electronics
53-55 Main Street, Grassington. BD23 5AA

Tel: 01756 753440
Fax: 01756 752857

Contact us for
Free Demo CD

www.labcenter.co.uk
info@labcenter.co.uk

RTTY Decoder

Radio Teletype (RTTY) is a direct machine-to-machine communications mode and has been in existence since the 1930's. The commercial use of RTTY on short wave has declined having been replaced with more robust transmission modes, however radio amateurs still use RTTY. Roger Thomas has designed an ingenious decoder

To encode and transmit text characters two different audio frequencies are transmitted. These two audio frequencies are commonly referred to 'mark' and 'space', where mark is usually the higher frequency. The most common audio frequencies used within Europe are 1275Hz (space) and 1445Hz (mark) and the difference between the two audio frequencies is called the 'shift'.

Most amateur radio transmissions use 170Hz audio shift, but shifts of 425Hz or 850Hz are used on other bands. It is possible for the transmission to be 'up side down' with the space frequency higher than the mark frequency, changing the receiver's side band settings and re-tuning will correct this. American amateur stations use a different set of audio frequencies (2125Hz and 2295Hz) but as the shift is still 170Hz this does not pose any problems with tuning or decoding.

Transmission speed is specified in baud, where baud is defined as the number of signal changes per second. Amateur RTTY transmissions in Europe are normally 45 or 50 baud but other speeds including 75 and 110 baud are used on other commercial bands. Although 45/50 baud transmission may seem very slow in comparison to computer modems, it is fast enough for a typed conversation. A 45/50 baud RTTY transmission equates to approximately 66 words per minute.

RTTY text characters are encoded using ITA2 (International Telegraph Alphabet Number 2) code, which uses five bits for each character. With only five bits per character, the maximum number of unique patterns is only 32. To enable RTTY to transmit the full alphabet two different character tables are used, one for letters (all letters are in upper case) and one for figures (which includes punctuation). A letters or figures control character determines which table to use when printing the received character. Control and space characters are represented in both tables to reduce then number of times the letters or figure control character needs to be transmitted. RTTY signals do not have any error detection capabilities.

RTTY is relatively simple to decode in software, but the different combinations of transmission speed and shift means that it is impossible to decode every combination. The PIC program as given is designed to decode both 45 and 50 baud RTTY using 170Hz shift as

this is the most common amateur radio signal, but both speed and shift parameters can be changed within the program.

RTTY is an asynchronous mode, which means that there is no common time frame between the station transmitting text and station receiving. In front of every 5 bit character is a single start bit (at space frequency) that makes the receiving printer ready for the incoming transmission. The five character data bits are transmitted, followed by a 'stop bit' which may be of a longer duration (one or one and a half units) and is transmitted at mark frequency. A useful feature to overcome the problem of noise or corrupt characters incorrectly signifying use of the figure table is to automatically revert to the letters table on receiving a space character.

Using start/stop bits means that after the receiving printer had printed out a character it was then waiting for the start bit of the next character. Thus synchronisation is not needed between sender and receiver.

RTTY uses the ITA2 (International Telegraph Alphabet 2) character set, sometimes called Baudot code (named after Emile Baudot), and is listed in Fig. 2. Where there is no designated character assigned (figure shift F, G, H) I have used characters from the teleprinter set.

Fig. 2. RTTY text characters.

letter	figure	RTTY	value
A	-	00011	3
B	?	11001	2
C	:	11101	14
D	\$	01001	9
E	3	00001	1
F	!	01101	13
G	&	11010	26
H	#	10100	20
I	8	00110	6
J	*	01011	11
K	(01111	15
L)	10010	18
M	.	11100	28
N	,	01100	12
O	9	11000	24
P	0	10110	22
Q	1	10111	23
R	4	01010	10
S	"	00101	5
T	5	10000	16
U	7	00111	7
V	=	11110	30
W	2	10011	19
X	/	11101	29
Y	6	10101	21
Z	+	10001	17

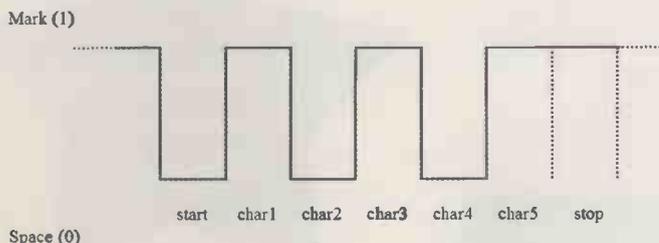


Fig. 1. RTTY Character 'Y' or '6'.

Fig. 3. RTTY control characters.

RTTY	function	value
11111	letters shift	31
11011	figures shift	27
01000	carriage return	8
00100	space	4
00010	line feed	2
00000	blank	0

RTTY software description

The advantage of using a Microchip PIC 16F84 18-pin microcontroller is that it is electrically erasable and therefore re-programmable using a low cost PIC programmer. This allows experimentation with different RTTY decode algorithms or variable values.

RTTY assembler code is ready for the Microchip MPLAB assembler, part of the MPLAB development software. This software is freely available from the Microchip web site (www.microchip.com). Type in the assembler code in the same sequence as it is presented and you should end up with a working RTTY decoder program to burn into a 16F84 microcontroller. The assembler code is in upper case and to help understand the assembler code appropriate extracts from the source program are included. Feel free to alter and improve the assembler code.

Define variables routine

The first part of the decoder program defines the PIC registers, the names of the variables used and where the variable value is to be stored in memory. The STATUS register contains various flags including C (carry), Z (zero), RPO (register banks select). The C flag is set (logic 1) if the result of an arithmetic operation produces a carry-out condition (i.e. most significant bit set). The Z flag is set if the operation result is zero.

Likewise the FLAGS byte contains Boolean flags for LTRS, BUSYFLAG, CONVFLAG, TOPLINE. BINCHAR is the binary representation of the received RTTY character. The config command instructs the assembler on the internal PIC fuse settings (power-up timer enabled, watchdog disabled, crystal oscillator selected).

Start routine

When power is applied to the PIC microcontroller it immediately starts program execution at address zero, this location has a jump instruction to the START routine. ORG assembler command instructs the assembler to generate code from the address given.

```
ORG 0
goto START
```

Interrupt routine

The rising edge of the received audio waveform on PIC port pin RBO causes an interrupt. When an interrupt occurs the PIC automatically runs interrupt service code located at address 4. This block of code saves the current PIC status and then calls routine INTERRUPT. After returning from executing the INTERRUPT code the registers are restored to their previous values and the RETFIE (return from interrupt) instruction allows the PIC to resume execution as if the interrupt had not occurred.

```
ORG 4 ; interrupt
MOVWF IRQW
SWAPF STATUS,W
BCF STATUS,RPO
MOVWF IRQS
MOVF STACK0,W
MOVWF IRQSTK
CALL INTERRUPT ;
MOVF IRQSTK,W
MOVWF STACK0
SWAPF IRQS,W
MOVWF STATUS
```

```
SWAPF IRQW,F
SWAPF IRQW,W
RETFIE
```

Conversion tables

The character data to convert received RTTY characters into the equivalent ASCII characters for display is stored in look up tables. How this table is derived is quite simple, for example the RTTY 'E' character has a value of 1 (binary 00001), therefore 'E' is located in the 1st position of the table called letters. RTTY character 'A' has a value is 3 (binary 00011) so is located in the 3rd position in the table, and so on for the rest of the RTTY character set. An asterisk character is used where there is a non-print control character defined for that

Fig. 4. Defining the PIC variables used in the RTTY decode program.

```
; Radio Teletype (RTTY) program.
; Written by Roger Thomas.

list p=16F84
__config H'3FF9'

; PIC register definitions
RTCC EQU D'1' ; timer
STATUS EQU D'3' ; status flags
C EQU D'0' ; carry
Z EQU D'2' ; zero
RPO EQU D'5' ; page select
PORTA EQU D'5' ; lcd port
RA0 EQU D'0' ; lcd_RS line
RA1 EQU D'1' ; lcd_E line
RA2 EQU D'2' ; lcd_RW line
PORTB EQU D'6' ; lcd data port
RBO EQU D'0' ; audio input
RB4 EQU D'4' ; lcd DB4
RB5 EQU D'5' ; lcd DB5
RB6 EQU D'6' ; lcd DB6
RB7 EQU D'7' ; lcd DB6
INTCON EQU D'11' ; register
IRQ_RBO EQU D'1' ; interrupt flag
IRQ_TIMER EQU D'2' ; interrupt timer
OPT EQU D'1' ; option register

; program definitions
STACK0 EQU D'12' ; temp use
STACK1 EQU D'13' ; temp use
STACK2 EQU D'14' ; temp use
STACK3 EQU D'15' ; temp use
STACK4 EQU D'16' ; temp use
IRQW EQU D'17' ; interrupt
IRQS EQU D'18' ; interrupt
IRQSTK EQU D'19' ; interrupt
RTCCVAL EQU D'20' ; timer value
VALRTCC EQU D'21' ; timer value
CHAR EQU D'22' ; output character
SAVECHAR EQU D'23' ; temp save CHAR
TEMP EQU D'24' ; store temp value
LCDPOS EQU D'25' ; lcd cursor position
MARKCOUNT EQU D'31' ; mark frequency count
SPACECOUNT EQU D'32' ; space frequency count
BITCOUNT EQU D'33' ; which bit of binchar
BINCHAR EQU D'26' ; binary RTTY char
CHAR1 EQU D'0' ; bit 1 RTTY character
CHAR2 EQU D'1' ; bit 2 RTTY character
CHAR3 EQU D'2' ; bit 3 RTTY character
CHAR4 EQU D'3' ; bit 4 RTTY character
CHAR5 EQU D'4' ; bit 5 RTTY character
FLAGS EQU D'27' ; Boolean byte
LTRS EQU D'0' ; letter/figure shift
BUSYFLAG EQU D'1' ; lcd busy flag
CONVFLAG EQU D'2' ; data convert flag
TOPLINE EQU D'3' ; top or bottom line
```

Fig. 5. look up tables.

```

; display message
    RETLW D'82'    ; R
    RETLW D'84'    ; T
    RETLW D'84'    ; T
    RETLW D'89'    ; Y
    RETLW D'32'    ; _
    RETLW D'68'    ; D
    RETLW D'69'    ; E
    RETLW D'67'    ; C
    RETLW D'79'    ; O
    RETLW D'68'    ; D
    RETLW D'69'    ; E
    RETLW D'82'    ; R
    RETLW D'32'    ; _

; letters look up table
    RETLW D'37'    ; % (0)
    RETLW D'69'    ; E (1)
    RETLW D'42'    ; * (2)
    RETLW D'65'    ; A (3)
    RETLW D'32'    ; _ (4)
    RETLW D'83'    ; S (5)
    RETLW D'73'    ; I (6)
    RETLW D'85'    ; U (7)
    RETLW D'42'    ; * (8)
    RETLW D'68'    ; D (9)
    RETLW D'82'    ; R (10)
    RETLW D'74'    ; J (11)

    RETLW D'78'    ; N (12)
    RETLW D'70'    ; F (13)
    RETLW D'67'    ; C (14)
    RETLW D'75'    ; K (15)
    RETLW D'84'    ; T (16)
    RETLW D'90'    ; Z (17)
    RETLW D'76'    ; L (18)
    RETLW D'87'    ; W (19)
    RETLW D'72'    ; H (20)
    RETLW D'89'    ; Y (21)
    RETLW D'80'    ; P (22)
    RETLW D'81'    ; Q (23)
    RETLW D'79'    ; O (24)
    RETLW D'66'    ; B (25)
    RETLW D'71'    ; G (26)
    RETLW D'42'    ; * (27)
    RETLW D'77'    ; M (28)
    RETLW D'88'    ; X (29)
    RETLW D'86'    ; V (30)
    RETLW D'42'    ; * (31)

; figures look up table
    RETLW D'37'    ; % (0)
    RETLW D'51'    ; 3 (1)
    RETLW D'42'    ; * (2)
    RETLW D'45'    ; - (3)
    RETLW D'32'    ; _ (4)
    RETLW D'34'    ; " (5)
    RETLW D'56'    ; 8 (6)

    RETLW D'55'    ; 7 (7)
    RETLW D'42'    ; * (8)
    RETLW D'36'    ; $ (9)
    RETLW D'52'    ; 4 (10)
    RETLW D'42'    ; * (11)
    RETLW D'44'    ; , (12)
    RETLW D'33'    ; ! (13)
    RETLW D'58'    ; : (14)
    RETLW D'40'    ; ( (15)
    RETLW D'53'    ; 5 (16)
    RETLW D'43'    ; + (17)
    RETLW D'41'    ; ) (18)
    RETLW D'50'    ; 2 (19)
    RETLW D'35'    ; # (20)
    RETLW D'54'    ; 6 (21)
    RETLW D'48'    ; 0 (22)
    RETLW D'49'    ; 1 (23)
    RETLW D'57'    ; 9 (24)
    RETLW D'63'    ; ? (25)
    RETLW D'38'    ; & (26)
    RETLW D'42'    ; * (27)
    RETLW D'46'    ; . (28)
    RETLW D'47'    ; / (29)
    RETLW D'61'    ; = (30)
    RETLW D'42'    ; * (31)

; end of tables
    
```

particular position. For example, RTTY character 2 (binary 00010) is a line feed control character. There is a similar table for numbers and punctuation.

These look up tables (including the RTTY LCD message) are stored sequentially in memory in ascending order located after the interrupt handler routine.

Audio conversion

To calculate the specific mark and space audio frequencies that the RTTY program has to respond to the following formula is used, assuming a 4MHz clock crystal. The actual timer frequency used is the 4MHz clock divided internally in the microcontroller by four.

$$\frac{\text{clock frequency} / 4}{\text{frequency Hz}} = \frac{4,000,000 / 4}{\text{space Hz}} = \frac{1,000,000}{1275} = 784.3$$

$$\frac{\text{clock frequency} / 4}{\text{frequency Hz}} = \frac{4,000,000 / 4}{\text{mark Hz}} = \frac{1,000,000}{1445} = 692$$

These numbers cannot be represented by the RTCC (Real Time Clock Counter) timer which is 8 bit (0 to 255 range), thus the clock used by the RTCC has to be divided by 4 using the internal prescaler.

$$\text{space} = \frac{1,000,000}{1275} = \frac{784}{4} = 196$$

$$\text{mark} = \frac{1,000,000}{1445} = \frac{692}{4} = 173$$

Fig. 6. valRTCC centre values

space	mark	shift
1275Hz = 196	1445Hz = 173	170Hz
1275Hz = 196	1700Hz = 147	425Hz
1275Hz = 196	2125Hz = 118	825Hz

Start routine

The START routine is always called whenever the PIC is reset. START routine calls INITVAR, INITPORT, INITLCD, and DISPLAY. After this the prescaler ratio is set (using bits PSx defined

in the OPTION register). The PSA bit is set to 0, which assigns the prescaler to the timer rather than the watchdog timer. RB0 interrupt is selected and enabled in the INTCON register.

```

START CALL INITVAR ; initialise variables
      CALL INITPORT ; initialise PIC ports
      CALL INITLCD ; initialise display
      CALL DISPLAY ; display RTTY message
      BSF STATUS,RP0
      BCF OPT,5 ; PIC clock as source
; prescaler (4000000 / 4) by 4
      BSF OPT,0 ; PS0
      BCF OPT,1 ; PS1
      BCF OPT,2 ; PS2
      BCF OPT,3 ; PSA
; use RB0 as interrupt source
      BCF STATUS,RP0
      BSF INTCON,4 ; IRQ RB0 enable
      BSF INTCON,7 ; interrupt enable
    
```

Loop routine

After initialising various options within the PIC microcontroller the program sits in the loop checking the CONVFLAG Boolean flag. This flag is set (true) in the INTERRUPT routine to indicate whenever new data is available and this flag is tested using the BTFSS instruction (Bit Test File, Skip if Set). If CONVFLAG is false then the next instruction GOTO LOOP is executed. If the result of the BTFSS is true the GOTO LOOP instruction is ignored and the CALL CONVERT is executed. File is Microchip terminology for what everyone else calls a register.

```

LOOP BTFSS FLAGS,CONVFLAG
     GOTO LOOP
; if convflag = true then
     CALL CONVERT
     GOTO LOOP
    
```

Initialise routine

INITVAR (initialise variables) routine sets various variables to zero using CLRF (Clear Register File) single instruction. INITPORT (initialise port) routine configures the various port pins

that are attached to the LCD display as outputs using the BCF (Bit Clear File). Port pin RBO is set as an input using BSF (Bit Set File) instruction; this is the PIC pin that the RTTY audio is connected to.

```

INITVAR          CLRF   MARKCOUNT ; = 0
                CLRF   SPACECOUNT ; = 0
                CLRF   LCDPOS ; = 0
                CLRF   BITCOUNT ; = 0
                CLRF   BINCHAR ; = 00000
                CLRF   FLAGS ; bits = false
; topline = true
                BSF    FLAGS,TOPLINE
; ltrs = true
                BSF    FLAGS,LTRS
                RETURN

INITPORT         BSF    STATUS,RP0 ; page 1
                BCF    PORTA,RA0 ; output
                BCF    PORTA,RA1 ; output
                BCF    PORTA,RA2 ; output
                BCF    PORTB,RB4 ; output
                BCF    PORTB,RB5 ; output
                BCF    PORTB,RB6 ; output
                BCF    PORTB,RB7 ; output
                BSF    PORTB,RB0 ; input
                BCF    STATUS,RP0 ; page 0
                RETURN

```

Read timer interrupt routine

In the following interrupt routine, the 8-bit RTCC counter value is assigned to RTCCVAL variable. The timer overflow flag is set if the counter has reached 255 (maximum byte value) and has started counting again. The status of this flag is checked and if the timer overflow flag is true then the program will ignore the timer value as it is invalid.

The RTCC count is then cleared and starts to automatically count up from zero and the flags indicating an interrupt condition are cleared. After this call the PIC re-loads the previously saved information and resumes processing from where it was before the interrupt had occurred.

```

interrupt:
if irq_timer = false then
begin
    RTCCval = rtcc ; read 8 bit timer value
    convflag = true ; set data ready flag
end
clr(rtcc) ; zero 8 bit timer
irq_RB0 = false ; clear interrupt flag
irq_timer = false ; clear interrupt flag

INTERRUPT
    BTFSC   INTCON,IRQ_TIMER
    GOTO    INVALID ; timer overflow
; RTCCval = rtcc (read 8 bit timer value)
    MOVF    RTCC,W
    MOVWF   RTCCVAL
; convflag = true set data ready flag
    BSF    FLAGS,CONVFLAG
INVALID   CLRF   RTCC ; zero 8 bit timer
; irq_RB0 = false (clear interrupt flag)
    BCF    INTCON,IRQ_RB0
    BCF    INTCON,IRQ_TIMER
    RETURN

```

Convert RTTY mark audio

Within the routine, CONVERT the MarkCount and SpaceCount variables translates a sequence of mark or space frequency into either a 1 or 0 by counting the number of consecutive pulses received.

With reference to the line if (valRTCC >= 161) and (valRTCC <= 185), the two numbers set the mark frequency (1445Hz) capture range as 1553Hz to 1352Hz. Any number received within this range will be treated as a mark frequency and will increment the MarkCount variable accordingly. Variable bit count is used to keep track of which bit within the BINCHAR variable is to be used. After receiving a predetermined number of mark frequencies (26) a '1' is added to the BINCHAR variable by making the relevant charX bit within BINCHAR to '1'. BINCHAR (binary character) becomes the binary representation of the received RTTY character.

The start bit of a RTTY character is always a space frequency, so if a mark frequency is detected as the first bit received this will be ignored and the bitcount is set back to zero. This helps prevent random noise generating random text. A RTTY station will send a continuous mark tone if there is no text ready to transmit.

```

; Mark - 1445Hz
if (valRTCC >= 161) and (valRTCC <= 185) then
begin
    inc(MarkCount) ; MarkCount = MarkCount+1
    if MarkCount >= 26 then
    begin
        clr(SpaceCount) ; SpaceCount = 0
        clr(MarkCount) ; MarkCount = 0
        inc(bitcount) ; bitcount = bitcount+1

        select bitcount
        case 1 : clr(bitcount); waiting for space
        case 2 : char1 = 1 ; set bit to 1
        case 3 : char2 = 1 ; set bit to 1
        case 4 : char3 = 1 ; set bit to 1
        case 5 : char4 = 1 ; set bit to 1
        case 6 : char5 = 1 ; set bit to 1
        Text
        end select
    end if
end if

; clear data ready flag
CONVERT     BCF    FLAGS,CONVFLAG
; valRTCC = RTCCval
    MOVF    RTCCVAL,W
    MOVWF   VALRTCC
; Mark - 1445Hz
; if valRTCC >= 161 and <= 185 then
    MOVF    VALRTCC,W
    MOVWF   STACK0
    MOVLW   D'161'
    SUBWF   STACK0,W
    CLRW
    BTFSC   STATUS,C
    ADDLW   D'255'
    MOVWF   STACK4
    MOVF    VALRTCC,W
    SUBLW   D'185'
    CLRW
    BTFSC   STATUS,C
    ADDLW   D'255'
    ANDWF   STACK4,W
    BTFSC   STATUS,Z
    GOTO    SPACEF
; MarkCount = MarkCount+1
    INCF    MARKCOUNT,F
; if MarkCount >= 26 then
    MOVF    MARKCOUNT,W
    MOVWF   STACK0
    MOVLW   D'26'
    SUBWF   STACK0,W
    BTFSS   STATUS,C
    GOTO    SPACEF

```

```

    CLRFB    SPACECOUNT    ; = 0
    CLRFB    MARKCOUNT    ; = 0
    INCF     BITCOUNT,F    ; +1
; bit 1 waiting for space
BIT1  MOVF   BITCOUNT,W
      SUBLW  D'1'
      BTFSS  STATUS,Z
      GOTO   BIT2
      CLRFB  BITCOUNT
      GOTO   ALLDONE
BIT2  MOVF   BITCOUNT,W
      SUBLW  D'2'
      BTFSS  STATUS,Z
      GOTO   BIT3
      BSF    BINCHAR,CHAR1 ; set bit
BIT3  MOVF   BITCOUNT,W
      SUBLW  D'3'
      BTFSS  STATUS,Z
      GOTO   BIT4
      BSF    BINCHAR,CHAR2 ; set bit
      GOTO   ALLDONE
BIT4  MOVF   BITCOUNT,W
      SUBLW  D'4'
      BTFSS  STATUS,Z
      GOTO   BIT5
      BSF    BINCHAR,CHAR3 ; set bit
      GOTO   ALLDONE
BIT5  MOVF   BITCOUNT,W
      SUBLW  D'5'
      BTFSS  STATUS,Z
      GOTO   BIT6
      BSF    BINCHAR,CHAR4 ; set bit
      GOTO   ALLDONE
BIT6  MOVF   BITCOUNT,W
      SUBLW  D'6'
      BTFSS  STATUS,Z
      GOTO   ALLDONE
      BSF    BINCHAR,CHAR5 ; set bit
      CALL   TEXT

```

```

      BTFSC  STATUS,C
      ADDLW  D'255'
      MOVWF  STACK4
      MOVF   VALRTCC,W
      SUBLW  D'212'
      CLRW
      BTFSC  STATUS,C
      ADDLW  D'255'
      ANDWF  STACK4,W
      BTFSC  STATUS,Z
      GOTO   ALLDONE
; SpaceCount = SpaceCount +1
      INCF   SPACECOUNT,F
; if SpaceCount >= 24 then
      MOVF   SPACECOUNT,W
      MOVWF  STACK0
      MOVLW  D'24'
      SUBWF  STACK0,W
      BTFSS  STATUS,C
      GOTO   ALLDONE
      CLRFB  MARKCOUNT ; = 0
      CLRFB  SPACECOUNT ; = 0
; bitcount = bitcount+1
      INCF   BITCOUNT,F
; if bitcount = 6 then
      MOVF   BITCOUNT,W
      SUBLW  D'6'
      BTFSS  STATUS,Z
      GOTO   ALLDONE
      CALL   TEXT
      ALLDONE    RETURN

```

Convert RTTY space audio

Using valRTCC numbers of 181 to 212 gives a frequency capture range of 1381Hz to 1179Hz and any number received within this range will increment the SpaceCount variable. The relevant BINCHAR bit variable is already '0' so the space routine does not need to change BINCHAR but still needs to increment variable bitcount to point to the next bit.

```

; Space - 1275Hz
if (valRTCC >= 181) and (valRTCC <= 212) then
begin
  inc(SpaceCount) ; SpaceCount = SpaceCount +1
  if SpaceCount >= 24 then
  begin
    clr(MarkCount) ; MarkCount = 0
    clr(SpaceCount) ; SpaceCount = 0
    inc(bitcount) ; bitcount = bitcount+1
    if bitcount = 6 then
    begin
      Text
    end
  end
end

; Space - 1275Hz
; if valRTCC >= 181 and <= 212 then
SPACEF MOVF   VALRTCC,W
        MOVWF  STACK0
        MOVLW  D'181'
        SUBWF  STACK0,W
        CLRW

```

Text output routine

After receiving five bits (BITCOUNT = 6) the Text routine is called (stop bits are ignored). Within the Text routine the value of BINCHAR (binary char) is checked for a control character such as carriage return, line feed or letter/figure shift.

If a space character is received (BINCHAR value equals 4), this forces the program to use the letters table then the space character is sent to the display. As the display is only two lines, any carriage returns or line feeds received result in the display cursor being moved to the beginning of the top line but the existing text is not erased.

If the received character (char) is not a control character then it is converted into an ASCII character based on a look up table and sent to the display. For example, if the binary sequence of the BINCHAR variable is 01010 then the decimal equivalent is (msb first) $0+8+0+2+0 = 10$. The look up (read) routine is used to access the tenth item in the letters table and returns the character 'R' in the char variable. The appropriate table (letters or numbers) is selected by the Boolean value of the LTRS variable.

Char variable is used in the TEXTLCD routine that handles sending this value to the display. The TEXTLCD routine also keeps track of where the cursor is (LCDPOS) and will move from the end of the top line to the first position on the bottom line when appropriate (TOPLINE flag).

If the value of char is 255 then we have received a non-print character and the second half of the routine is not called.

```

Text:
clr(bitcount)
char = '?'
select binchar
  case b'00100' : ltrs = true ;space forces letter shift
  case b'01000' : clr(lcdpos) ;carriage return
                  char = b'10000000' ; cursor to top line
                  CommandLCD
                  topline = true ; lcd top line
                  char = 255
  case b'00010' : clr(lcdpos) ; line feed
                  char = b'10000000' ; cursor to top line

```

```

        CommandLCD
        topline = true ; lcd top line
        char = 255
    case b'11011' : ltrs = false ; figure shift
        char = 255
    case b'11111' : ltrs = true ; letters shift
        char = 255
end select

if char <> 255 then ; 255 = non-print character
begin
    if ltrs = true then
    begin
        read(letters,binchar,char)
        TextLCD
    end
    else
    begin
        read(numbers,binchar,char)
        TextLCD
    end
end
clr(binchar) ; = b'00000'

```

```

TEXT CLRf BITCOUNT ; = 0
MOVW D'63'
MOVWF CHAR ; char = '?'
MOVf BINCHAR,W
SUBLW D'4' ; space ?
BTfSS STATUS,Z
GOTO CR
BSF FLAGS,LTRS
GOTO TEXT1

; carriage return ? (4)
CR MOVf BINCHAR,W
SUBLW D'8'
BTfSS STATUS,Z
GOTO LF
CLRf LCDPOS

; char = b'10000000'
; cursor to top line
MOVW D'128'
MOVWF CHAR
CALL COMMANDLCD

; topline = true
BSF FLAGS,TOPLINE
MOVW D'255'
MOVWF CHAR
GOTO TEXT1

; line feed ? (2)
LF MOVf BINCHAR,W
SUBLW D'2'
BTfSS STATUS,Z
GOTO FS
CLRf LCDPOS

; char = b'10000000'
; cursor to top line
MOVW D'128'
MOVWF CHAR
CALL COMMANDLCD

; topline = true lcd top line
BSF FLAGS,TOPLINE
MOVW D'255'
MOVWF CHAR
GOTO TEXT1

; figure shift ? (27)
FS MOVf BINCHAR,W
SUBLW D'27'
BTfSS STATUS,Z
GOTO LS

```

```

BCF FLAGS,LTRS
MOVLW D'255'
MOVWF CHAR
GOTO TEXT1
;letter shift ? (31)
LS MOVf BINCHAR,W
SUBLW D'31'
BTfSS STATUS,Z
GOTO TEXT1
BSF FLAGS,LTRS
MOVLW D'255'
MOVWF CHAR

```

```

; if char <> 255 then
TEXT1 MOVf CHAR,W
MOVWF STACK0
MOVLW D'255'
SUBWF STACK0,W
BTfSC STATUS,C
GOTO ENDTXT
BTfSS FLAGS,LTRS
GOTO NUMBER

; if ltrs = true then
; char = read(letters,binchar)
MOVLW D'31'
MOVWF STACK0
MOVLW D'0'
MOVWF STACK1
MOVf BINCHAR,W
MOVWF STACK2
CLRf STACK3
CALL READ
MOVWF CHAR
CALL TEXTLCD
GOTO ENDTXT

; if ltrs = false then
; char = read(numbers,binchar)
NUMBER MOVLW D'63'
MOVWF STACK0
MOVLW D'0'
MOVWF STACK1
MOVf BINCHAR,W
MOVWF STACK2
CLRf STACK3
CALL READ
MOVWF CHAR
CALL TEXTLCD
ENDTEXT CLRf BINCHAR ; = b'00000'
RETURN

```

RTTY element timing

For 45 baud RTTY each element (bit) of the character is 22ms long, for 50 baud each element is 20ms long.

Fig. 7. Integer values for MarkCount and SpaceCount.

45 baud	1445 * 22ms = 31 (mark)
	1275 * 22ms = 28 (space)
50 baud	1445 * 20ms = 28 (mark)
	1275 * 20ms = 25 (space)
75 baud	1445 * 13ms = 18 (mark)
	1275 * 13ms = 16 (space)

A compromise has to be reached between the theoretical and actual number chosen for the mark and space comparison count. Too small a number and one bit may be interpreted as two consecutive bits or two consecutive bits misread as three bits. Too large and a poor quality RTTY signal may never reach the required number. If the parameters are too exact then the PIC program will only accept RTTY that is 'perfect'. Ideally we want the software to respond to both 45 and 50 baud. With all these numbers there will be small variations due to interrupt latency.

Fig. 8. Summary of LCD commands.

instruction	R S	R W	D 7	D 6	D 5	D 4	D 3	D 2	D 1	D 0	instruction description
clear display	0	0	0	0	0	0	0	0	0	1	clears display and cursor to home position
cursor home	0	0	0	0	0	0	0	0	1	X	returns cursor to home position
entry mode set	0	0	0	0	0	0	0	1	1	S	I - sets cursor move direction (0 = decrement, 1 = increment) S - shift display
display control	0	0	0	0	0	0	1	D	C	B	D - on/off of display C - cursor on/off B - blink cursor character
cursor/display shift	0	0	0	0	0	1	S	D	X	X	S - sets cursor move or display shift D - shift direction (1=right or 0=left)
function set	0	0	0	0	1	D	N	F	X	X	D - interface data length (4 or 8 bit) N - number of display line (1 or 2 lines) F - character font (0=5x10 or 1=5x7)
read busy flag	0	1	B	x	x	x	x	x	x	x	B - busy flag 1 = busy 0 = not busy
move cursor	0	0	1	a	a	a	a	a	a	a	move cursor to address aaaaaaa a = 0 line 1, position 1 a = 64 line 2, position 1
write character	1	0	d	d	d	d	d	d	d	d	write character ddddddd to display at current cursor position

To change the frequency range the valRTCC values need to be altered within the assembler program. Selecting too narrow a frequency range may make tuning difficult and not all amateur transmissions have exactly the right shift. Frequency drift within the receiver itself may need to be taken into consideration. Making the frequency range wider makes tuning easier and increases the chance of receiving less than perfect RTTY, however noise and co-channel interference could introduce errors.

RYRYRY

As the letter R is alternating between space and mark (01010) and the letter Y alternates between mark and space (10101) these two characters are sometimes used alternately (RYRY) when calling CQ. This distinctive pattern helps receiving stations to tune to the transmissions. Numbers 4 and 6 will appear if the figure table is being used.

LCD display

A low cost 16 character, two-line LCD is used to display the received RTTY text. The vast majority of these are based around the Hitachi HD44780 (or compatible) display controller. The display is initialised by calling routine InitLCD, the device is set for 4 bit data transfer, 2 display lines, 5x7 font, cursor on and character blink off.

Using a LCD connected to a PIC is a low cost and convenient method of displaying text, both the display and PIC circuit will run off a +5 volt regulated supply.

Although the interface to the LCD is 4 bits it may seem odd for the first three instructions sent (routine InitLCD) to set the data bus interface to 8 bits. The reason for this is that with a four bit interface there is no mechanism to tell the LCD which four bits is being sent (i.e. upper or lower nibble). If the LCD misses a nibble it will be out of sync for all the following data. During initialisation this will cause the LCD to be set in the wrong mode. Sending the 8 bit mode command (the four unconnected bits DB0 to DB3 will be correctly read) makes sure that everything is working correctly before the transfer mode is switched to four bits.

Fig. 9. LCD address of each display character position.

position	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
line 1	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
line 2	64	65	66	67	68	69	70	71	72	73	74	75	76	77	78	79

Fig. 10. Initialise LCD.

```

INITLCD
; char = b'00110000' 8 bit mode
    MOVLW    D'48'
    MOVWF    CHAR
    CALL     INILCD
; char = b'00110000' 8 bit mode
    MOVLW    D'48'
    MOVWF    CHAR
    CALL     INILCD
; char = b'00110000' 8 bit mode
    MOVLW    D'48'
    MOVWF    CHAR
    CALL     INILCD
; char = b'00101000'
; 4 bit, 2 lines, 5x7 font
    MOVLW    D'40'
    MOVWF    CHAR
    CALL     COMMANDLCD
; char = b'00011000'
; cursor move, right shift
    MOVLW    D'24'
    MOVWF    CHAR
    CALL     COMMANDLCD
; char = b'00001110'
; display+cursor on,blink off
    MOVLW    D'14'
    MOVWF    CHAR
    CALL     COMMANDLCD
; char = b'00000100' entry mode
    MOVLW    D'4'
    MOVWF    CHAR
    CALL     COMMANDLCD
; char = b'00000001' clear display
    MOVLW    D'1'
    MOVWF    CHAR
    CALL     COMMANDLCD
    RETURN

COMMANDLCD
    CALL     WAIT    ; is lcd busy ?
    BCF     PORTA,RA2
    BCF     PORTA,RA0

```

```

; send routine to output 4 bits
CALL SEND
; swap over lower 4 bits
SWAPF CHAR,F
CALL SEND
RETURN

INILCD CALL WAIT
BCF PORTA,RA2
BCF PORTA,RA0
CALL SEND
RETURN

```

Displaying RTTY text

The text and data is transferred to the display four bits at a time (routine send). The variable LCDPOS (LCD cursor position) is to make sure that we have not passed the end of the display line. If you are using a LCD that can display more than 16 characters then change this number. If the cursor is at the end of the line then the output character is stored and the Boolean flag is checked to see if the display is using the top or bottom display line. The appropriate command is then sent to the LCD to use the other display line and the cursor set to the first position before restoring the character and sending that to the LCD.

The higher four bits are sent first then the four lower bits. The swap command is used to exchange the lower and upper 4 bits of the byte, hence the output routine (SEND) is called twice.

Fig. 11. LCD text output routines.

```

TextLCD:
if lcdpos > 15 then ; end of lcd line ?
begin
  clr(lcdpos) ; position 0
  savechar = char ; temp save char
  if topline = false then
  begin
    char = b'10000000' ; cursor to top line
    CommandLCD
    topline = true
  end
  else
  begin
    char = b'10000000'+64 ;cursor to bottom line
    CommandLCD
    topline = false
  end
  char = savechar ; restore original value
end
call wait ; is lcd busy ?
RA2 = 0 ; 0 - writing to lcd
RA0 = 1 ; 1 - data register
call send ; output upper 4 bits
swap(char) ; swap lower/upper 4 bits
call send ; output upper 4 bits
inc(lcdpos) ; next lcd position

TEXTLCD MOVF LCDPOS,W
SUBLW D'15' ; LCD
BTFSC STATUS,C
GOTO LINE
; if lcdpos > 15 then
CLRF LCDPOS ; position 0
; savechar = char
MOVF CHAR,W
MOVWF SAVECHAR
; if topline = false then
BTFSC FLAGS,TOPLINE
GOTO BOTTM

```

```

; char = b'10000000' cursor to top line
MOVLW D'128'
MOVWF CHAR
CALL COMMANDLCD
BSF FLAGS,TOPLINE
GOTO REST

; char = b'10000000'+64
; cursor to bottom line
BOTTM MOVLW D'192'
MOVWF CHAR
CALL COMMANDLCD
BCF FLAGS,TOPLINE

; char = savechar
; restore original value
REST MOVF SAVECHAR,W
MOVWF CHAR

; is lcd busy ?
LINE CALL WAIT
BCF PORTA,RA2
BSF PORTA,RA0

; send output upper 4 bits
CALL SEND

; swap lower/upper 4 bits
SWAPF CHAR,F
CALL SEND

; next lcd position
INCF LCDPOS,F
RETURN

```

```

SEND
; RB4 = char AND b'00010000'
MOVF CHAR,W
ANLW D'16'
BTFSS STATUS,Z
BSF PORTB,RB4
BTFSC STATUS,Z
BCF PORTB,RB4

; RB5 = char AND b'00100000'
MOVF CHAR,W
ANLW D'32'
BTFSS STATUS,Z
BSF PORTB,RB5
BTFSC STATUS,Z
BCF PORTB,RB5

; RB6 = char AND b'01000000'
MOVF CHAR,W
ANLW D'64'
BTFSS STATUS,Z
BSF PORTB,RB6
BTFSC STATUS,Z
BCF PORTB,RB6

; RB7 = char AND b'10000000'
MOVF CHAR,W
ANLW D'128'
BTFSS STATUS,Z
BSF PORTB,RB7
BTFSC STATUS,Z
BCF PORTB,RB7

; RA1 = 1 (enable high to low)
BSF PORTA,RA1
; RA1 = 0 (data valid)
BCF PORTA,RA1
RETURN

```

Port A (bits 0 to 2) is used to provide the LCD control lines and port B (bits 4 to 7) is used as the four bit data bus. The Enable control line (RA1) is used to inform the display that data is available by taking the line high then low.

Fig. 12. Summary of LCD control lines.

PIC	name	function	
RA2	lcd_rw	read/write	0 - write, 1 - read
RA1	lcd_e	enable	1/0 data available
RA0	lcd_rs	register select	0 instruction register 1 display register

These LCD displays are slow in comparison to the operation of a PIC micro-controller and require time to complete commands. These range from 40ms to 60ms when sending data and up to 2ms for clearing the display. Worst case delays have to be assumed to ensure that the command has been completed, which may make the program wait unnecessarily before communicating with the display.

By polling the display's busy flag to see if it can accept data means that the PIC program can send data to the display without using software time delays. To enable the PIC to send text to the display as fast as possible the LCD's internal busy flag is read in routine wait. This requires the port to switch from output to input. Busy flag is contained in the status byte as the most significant bit (the rest of the status information is ignored).

Fig. 13. LCD wait routine.

```
wait:
RA2 = 1          ; 1 - reading from lcd
RA0 = 0          ; 0 - instruction register
input(RB4)      ; make port pin input
input(RB5)      ; make port pin input
input(RB6)      ; make port pin input
input(RB7)      ; make port pin input
busyflag = true ; is lcd busy ?
while busyflag = true ; 1 = busy 0 = ready
    RA1 = 1      ; read data high to low
    busyflag = RB7 ; read msb bit
    RA1 = 0      ; receive upper 4 bits first
    RA1 = 1      ; not interested in lower 4
    RA1 = 0      ; ignore rest of status byte
loop ; if busy keep in the loop
output(RB4)     ; make port pin output
output(RB5)     ; make port pin output
output(RB6)     ; make port pin output
output(RB7)     ; make port pin output
WAIT BSF PORTA,RA2 ; reading lcd
BCF PORTA,RA0 ; instruction register
BSF STATUS,RP0
BSF PORTB,RB4 ; pin input
BSF PORTB,RB5 ; pin input
BSF PORTB,RB6 ; pin input
BSF PORTB,RB7 ; pin input
BCF STATUS,RP0
BSF FLAGS,BUSYFLAG
; while busyflag = true (1 = busy 0 = ready)
BUSY BTFSS FLAGS,BUSYFLAG
GOTO READY
; if busy keep in loop
BSF PORTA,RA1
; busyflag = RB7
BTFSC PORTB,RB7
BSF FLAGS,BUSYFLAG
BTFSS PORTB,RB7
BCF FLAGS,BUSYFLAG
BCF PORTA,RA1
BSF PORTA,RA1
BCF PORTA,RA1
GOTO BUSY
READY BSF STATUS,RP0
BCF PORTB,RB4 ; pin output
BCF PORTB,RB5 ; pin output
BCF PORTB,RB6 ; pin output
BCF PORTB,RB7 ; pin output
BCF STATUS,RP0
RETURN
```

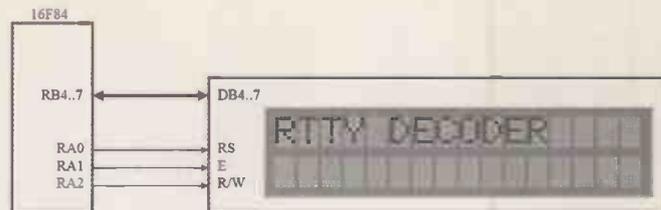


Fig. 14. LCD wiring diagram.

Fig. 15. PIC connection list.

RA0	17	-	output to lcd RS line
RA1	18	-	output to lcd E line
RA2	1	-	output to lcd R/W line
RB4	10	-	data bus to lcd DB4
RB5	11	-	data bus to lcd DB5
RB6	12	-	data bus to lcd DB6
RB7	13	-	data bus to lcd DB7
Vdd	14	-	power supply +5v
Vss	5	-	power supply 0v
mclr	4	-	power supply +5v
RB0	6	-	audio input
osc2	15	-	4 MHz crystal
osc1	16	-	4 MHz crystal

Fig. 16. LCD pin description.

Vss	1	-	ground
VDD	2	-	+5v
VO	3	-	contrast voltage
RS	4	-	register select line
R/W	5	-	read/write line
E	6	-	enable line
DB4	11	-	data bus 4
DB5	12	-	data bus 5
DB6	13	-	data bus 6
DB7	14	-	data bus 7
Vled	15	-	back lighting (optional)
Vled	16	-	back lighting (optional)

Fig. 17. Component list.

R1	-	120kW
R2	-	1kW
R3	-	47kW
VR1	-	47kW linear (audio)
VR2	-	47kW linear (lcd contrast)
C1, 4	-	100nF ceramic
C2, 3	-	10uF electrolytic
C5, 6	-	33pF ceramic
TR1	-	BC549 or similar
IC1	-	PIC 16F84
IC2	-	74LS14 (hex buffer)
X1	-	4MHz crystal
LCD	-	16 by 2 line display

Circuit description

The circuit can be built using strip board with the majority of connections between the display and the PIC. LCD displays either have a single line of 14 pin holes or a double row of seven pins holes. If the display has a back lighting option then there will be 16 holes.

The LCD display may need a potentiometer (20-50 kW) to set the contrast voltage. This potentiometer should be connected between the positive supply rail and ground, connect the wiper to the LCD contrast pin (usually pin 3). If after reset no message is visible then this setting may need to be altered. Once this potentiometer is set for the best viewing angle it should not need to be altered again. For simplicity this contrast line can be connected direct to 0v line but the viewing angle may not be optimal.

The circuit should be connected to a +5 volt regulated supply. Display and PIC circuit will consume around 8-10mA but this rises

considerably if display back lighting is used. The amount of current depends on the type of back lighting, the display that I have (manufactured by Anders) has two side type LEDs and consumes over 50mA when using the back lighting option.

Display routine

When power is first applied to the circuit, the PIC program should display 'RTTY DECODER' message, demonstrating that the program and display has been initialised correctly. The READ routine gets the appropriate character from the look up table.

```
display:
temp = 0
while temp <= 11 ; 11 characters in text
  read[ready,temp,char]
  TextLCD    ; char = ready[temp]
  inc(temp)  ; next character
loop
```

```
DISPLAY CLRF  TEMP ; =0
; 11 characters in text
DISP1  MOVF  TEMP,W
        SUBLW D'11'
        BTFSS STATUS,C
        GOTO  DONE
; char = read(ready,temp)
        MOVLW D'18'
        MOVWF STACK0
        MOVLW D'0'
        MOVWF STACK1
        MOVF  TEMP,W
        MOVWF STACK2
        CLRF  STACK3
        CALL  READ
        MOVWF CHAR
        CALL  TEXTLCD
; next character
        INCF  TEMP,F
        GOTO  DISP1
DONE RETURN
```

```
; Read from table
READ   MOVF  STACK0,W
        ADDWF STACK2,f
        BTFSC 3,2
        INCF  STACK1,f
        MOVF  STACK1,W
        ADDWF STACK3,W
        MOVWF D'10' ; PCLATH
        MOVF  STACK2,W
        MOVWF D'2'  ; PCL
        END
```

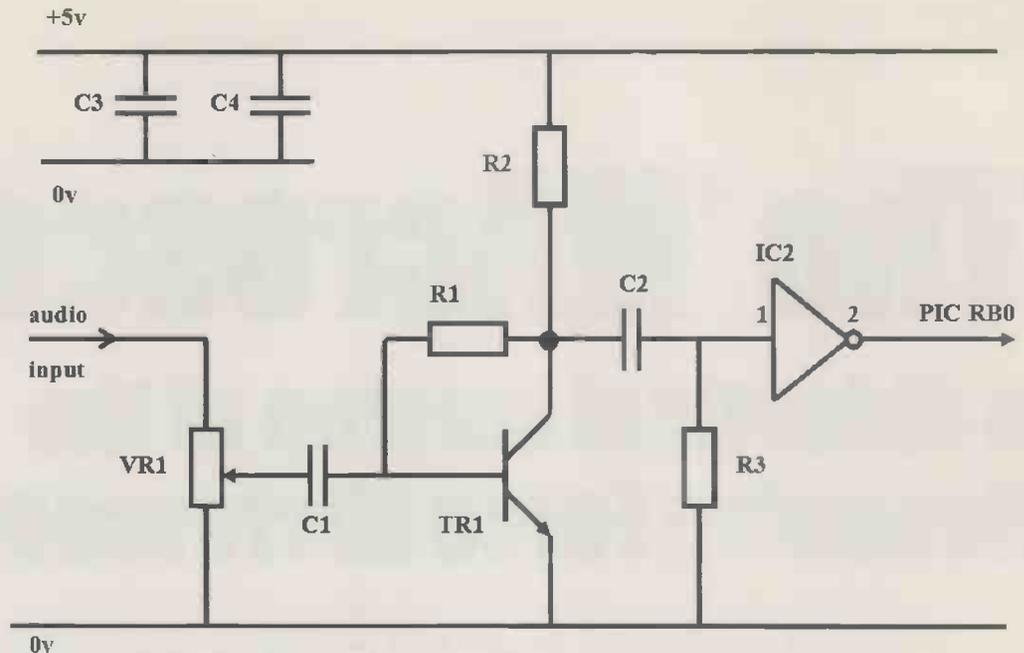


Fig. 18. interface circuit.

Interface circuit

The transistor interface circuit is designed to be connected to the loudspeaker or headphones output of the receiver. Connection to the receiver is by screened audio cable, soldered either side of VR1 potentiometer. Set the potentiometer and volume control as appropriate when the radio is receiving RTTY for correct reception and comfortable listening level.

The transistor circuit changes the shape of the audio sine wave into a square wave. Using the 74LS14 buffer guarantees a constant amplitude TTL signal so that the audio edge properly triggers the PIC interrupt. The 74LS14 buffer has a Schmitt trigger type input which ensures a clean output signal and makes the interface less sensitive to noise. I used a BC549 npn transistor (plastic version of BC109) in the prototype but any general purpose npn transistor will do. Ideally, the interface circuit should be housed in a metal box to prevent any radio signals generated by the PIC from being picked up by the receiver. Take care with the input level to prevent excessive signal input. Although some clipping of the audio signal does not affect the operation of the PIC as it is triggered on the waveform edge.

To check the operation of the circuit in the absence of a RTTY signal, find a clear steady tone and tune very slowly until a row of % characters appear on the display (BINCHAR value of 0 being received). Under normal operations this display would signify that the tuning is close but incorrect. The frequency is being processed as a space frequency but a steady tone being transmitted by a RTTY station should be a mark frequency. The stronger and clearer the radio signal is the more RTTY will be correctly decoded.

Despite more 'modern' forms of data communications, there are still many RTTY signals to be heard on the amateur bands. A few radio amateurs continue to use mechanical printers but the majority use a computer and software. Indeed it is because RTTY signals can be produced and decoded entirely by computer software, and ease of operation, which has contributed to its continued use. ■

The 'MACROSCOPE': a didactical version of the Scanning Force Microscope

A homemade device that mimics, at macroscopic level, the behaviour of an SFM (Scanning Force Microscope) that may be used for didactic purposes aimed at clarifying genesis and meaning of electronic micrographs. Giacomo Torzo, Barbara Pecori, Pietro Scatturin and Giorgio Delfitto¹ elucidate

Our world is full of images. Some of them, like the image of a coin, are part of a general background knowledge and, appearing 'natural', do not raise any curiosity about the mechanisms generating the image. But if we try to find out the value of a coin inside our pocket by hand inspection only, the process involved in our fingers collecting data and our brain transforming data into a 'coin image' is different from the usual way of transforming the eye's signals into images. It is more similar to the process used in modern scanning force microscopy (SFM).

These considerations brought us to design a device that

could be used, even by students with a poor physics background, to help understanding the basic processes through which images are normally built from electric signals acquired by sensors. The basic idea is to use a device working at macroscopic level with techniques similar to those used investigating the microscopic world.

How are topographic images produced?

Electronic images may be of a different type. The simplest is the 'bit-mapped' one, i.e. *matrix of dots* of different colours that may be printed or displayed on a computer screen. Each pixel is a numeric value in the matrix stored in the computer memory.

Topographic images are special images, that give a quantitative representation of the surface of an object, where the colour of each pixel 'measures' the distance z from a geometric plane parallel to the average surface of the object ($z=z_0$).

If we pick up only a row of the matrix, we obtain a vertical cross-section of the topographic image.

By plotting this set of numbers versus their position along x , with segments joining the nearby dots, we get an x -line profile. Putting in the same plot all the x -line profiles corresponding to the various y positions (each one shifted upward of the same quantity Δz) we obtain a 3D representation of the surface that is named 'wire-frame'. The azimuthal 'angle of view' of this 3D image is determined by the shift value Δz , while a polar rotation of the angle of view may be obtained by applying a shift Δx to each x -line profile.

In Fig. 1. we report an image obtained with commercial SFM operating at constant force² (square matrix of 256x256 pixel where lighter dots indicate larger z values): the single atomic layers in a Gallium Arsenide single crystal substrate are evident, as well as some Indium

Fig. 1. SFM image of InAs nanoislands on GaAs substrate (3x3mm)



Arsenide nanostructures (white dots) grown onto the substrate by Metal Organic Vapor Phase Epitaxy.

Working principle of the 'macroscope'

Our device is based on the technology of 'stylus profilometers'. The commercial profilometers work in one dimension, generating a line-profile of the investigated sample, while our device must scan a surface by moving the probe along a series of parallel lines (the raster scanning normally used by SFM when storing bitmapped images in a matrix). A simple software for real time data acquisition may be used to build a profilometer by using as a vertical displacement probe (z-axis) a tip soldered at the end of a cantilever whose deflection is measured by strain gauges and as a horizontal displacement sensor (x-axis) a micropositioner whose driving screw rotation angle is measured by a potentiometer

Our device is able to record two series of values (vectors) corresponding to the signal $V^z=V(z)$ of the vertical displacement of the tip following the sample topography and to the signal $V^x=V(x)$ of the potentiometer measuring the displacement along the x axis. On the computer screen it is therefore possible to trace the plot $V_z=f(V_x)$ reproducing the sample profile along a line parallel to x.

A series of scans (each one made for a different position along y-axis) contains information on the whole sample surface, but if we placed them all together in the plot $V_z=f(V_x,y)$ the result would be unreadable, due to the overlap. We therefore used a simple 'trick' in order to make visible the sample topography and to produce a 'pseudo-3D' image. The trick consists of mounting the sample onto a tilted plane so that every displacement along the y-axis produces a vertical shift $\Delta V^z=V(\Delta y \tan \alpha)$

The tip-cantilever system (z-axis displacement sensor) is mounted on a metal holder that may be moved along the y-axis by rotating a driving screw, while the sample-holder performs the x-axis scan. The x-axis movement is obtained using a cheap trolley (a Domino 50, produced by Schluderbacker) whose knob is ganged to the axis of a potentiometer by means of a pulley.

The maximum scan width is limited by the range of x and y screws (in our case about 20mm in both directions). A sketch of the device is shown in Fig. 2.

The Z-detector

The strain gauge is made of a thin film resistance incorporated into a plastic strip to be glued to the object whose strain has to be measured. Applying to the film a tensile (compressive) strain increases (decreases) its resistance. The change in resistance ΔR is proportional to the relative length change $\epsilon=\Delta L/L$, with a gauge factor $G=(\Delta R/R)/\epsilon \approx 2$. By gluing two identical strain gauges to an elastic cantilever and by connecting them in a Wheatstone bridge with two fixed resistors R, we obtain a force sensor (see Fig. 4. and Text Box 2).

Fig. 4. The Wheatstone bridge configuration of the strain gauges resistances R^1 and R^2 , and sketch of the cantilever geometry. The actual probe is a needle soldered at one end of the cantilever.

When the tip is pushed upward, with a vertical shift Δz , the cantilever deflection produces the relative change $+\epsilon$ in lower strain gauge and $-\epsilon$ in the upper one. The value of the shift may be written (see Text Box 2) $\Delta z=\epsilon(2L^2/3a)$, where a is the cantilever thickness and L its length, so that the relative resistance change is $\Delta R/R=G\epsilon=\Delta z(3a/L^2)$. For example for $L=30$ mm, $a=0.3$ mm, we get $(\Delta R/R)/\Delta z=10^{-4}mm^{-1}$, a sensitivity comparable with the thermal drift of metallic resistances $\beta=(\Delta R/R)/\Delta T=10^{-4}C^{-1}$.

This explains why we use two strain gauges instead of

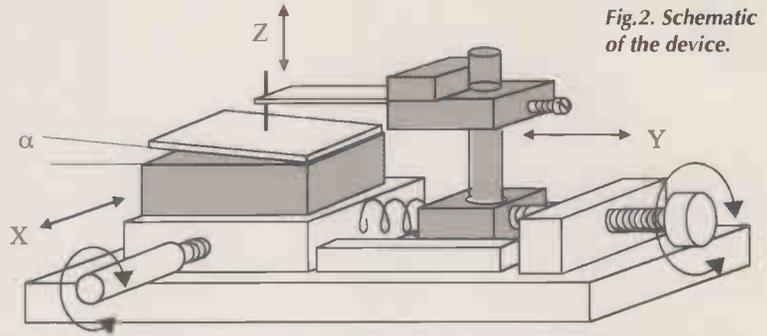


Fig.2. Schematic of the device.

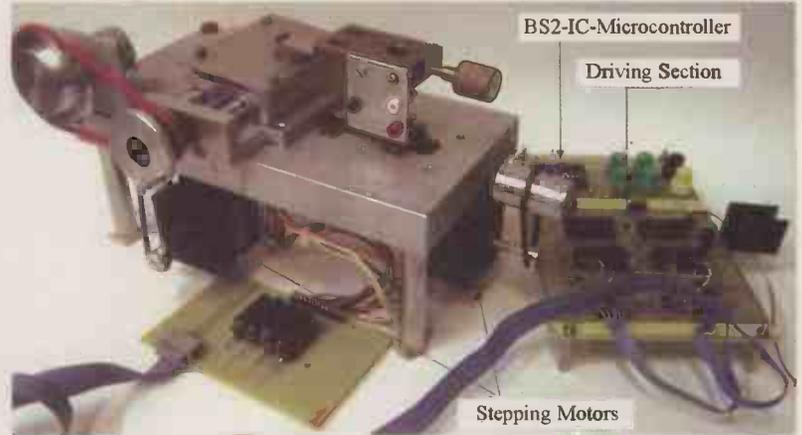



Fig. 3. A picture of our device.

one: besides the gain of a factor of two in sensitivity, with matched gauges we make the system unaffected by thermal drifts. The voltage V^A at the strain gauge's midpoint depends on the bridge bias voltage V^B and on the values of the two resistances $(R-\Delta R)$ and $(R+\Delta R)$: $V^A=V^B/2+V^B\Delta R/2R$. The fixed resistor's midpoint voltage is $V^B=V^B/2$, so that the bridge output signal is $\Delta V=V^A-V^B=V^B\Delta R/2R=V^B\epsilon$.

For example, with $V^B=1V$ and $\Delta z=0.1$ mm we get a signal $\Delta V=1$ mV, requiring a gain of about 1000 in order to match the input voltage range of the used interface (0-5V). The signal measuring horizontal displacements is provided by a potentiometer, biased at 5V, driven by a pulley linked to the micrometer axis through a rubber band. Typical resolution of a Helipot (10 turns potentiometer) is of the order of 10^{-4} , introducing an uncertainty smaller than that due to the ADC (10 bits): e.g. with a trolley moving 2mm per each turn of the driving screw, the 5mV sensitivity gives a theoretical resolution of 20mm, better than the limit imposed by the curvature radius of the thinnest usable needles.

The signal conditioning circuit is shown in Fig. 5. It consists of an active bridge, built around IC3, biased by IC1, a REF03 2.5V voltage reference buffered by IC2. The output V_z is amplified to obtain a signal suitable to the input range of our Data Acquisition System (0-5V). One

Fig. 4. The Wheatstone bridge configuration.

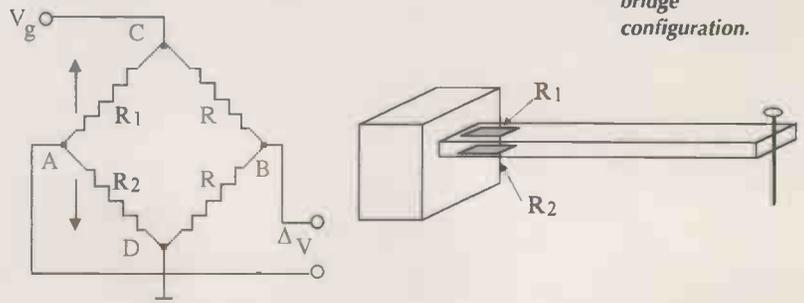

The BASIC Stamp II code for the stepping motors controller

STEP31.BS2

```

dx      var          bit
sx      var          bit
ay      var          bit
by      var          bit
au      var          bit
i       var          word
j       var          byte

input 0      'Pin 5 of BS2-IC; RIGHT BUTTON
input 1      'Pin 6 of BS2-IC; LEFT BUTTON
input 2      'Pin 7 of BS2-IC; UP BUTTON
input 3      'Pin 8 of BS2-IC; DOWN BUTTON
input 4      'Pin 9 of BS2-IC; AUTO SCAN BUTTON
output 8     'Pin 13 of BS2-IC;  $\overline{CK}$ 
output 9     'Pin 14 of BS2-IC; CW/ $\overline{CCW}$ 

signal
output 10    'Pin 15 of BS2-IC; ENABLE signal for horizontal displacement
output 11    'Pin 16 of BS2-IC; ENABLE signal for vertical displacement
dx=0
sx=0
ay=0
by=0
au=0
low 10
low 11

loop:
  button 0,0,255,1,dx,0,skip1
  gosub dex

skip1:
  button 1,0,255,1,sx,0,skip2
  gosub six

skip2:
  button 2,0,255,1,ay,0,skip3
  gosub aly

skip3:
  button 3,0,255,1,by,0,skip4
  gosub bay

skip4:
  button 4,0,255,1,au,0,skip5
  gosub aut

skip5:
  goto loop

dex:
  high 10
  high 9

dex1:
  button 0,0,255,1,dx,1,dex2
  low 10
  return

dex2:
  pulsout 8,100
  goto dex1

six:
  high 10
  low 9

six1:
  button 1,0,255,1,sx,1,six2
  low 10
  return

six2:
  pulsout 8,100
  goto six1

aly:
  high 11
  high 9

aly1:
  button 2,0,255,1,ay,1,aly2
  low 11
  return

aly2:
  pulsout 8,100
  goto aly1

bay:
  high 11
  low 9

bay1:
  button 3,0,255,1,by,1,bay2
  low 11
  return

bay2:
  pulsout 8,100
  goto bay1

aut:
  for j=1 to 20
  high 10
  low 9
  for i=1 to 4100
  pulsout 8,100
  next
  return

next
low 10
pause 100
high 11
for i=1 to 77
pulsout 8,100
next
low 11
pause 100
high 10
high 9
for i=1 to 4100
pulsout 8,100
next
low 10
pause 100
high 11
low 9
for i=1 to 217
pulsout 8,100
next
low 11
next
return

```

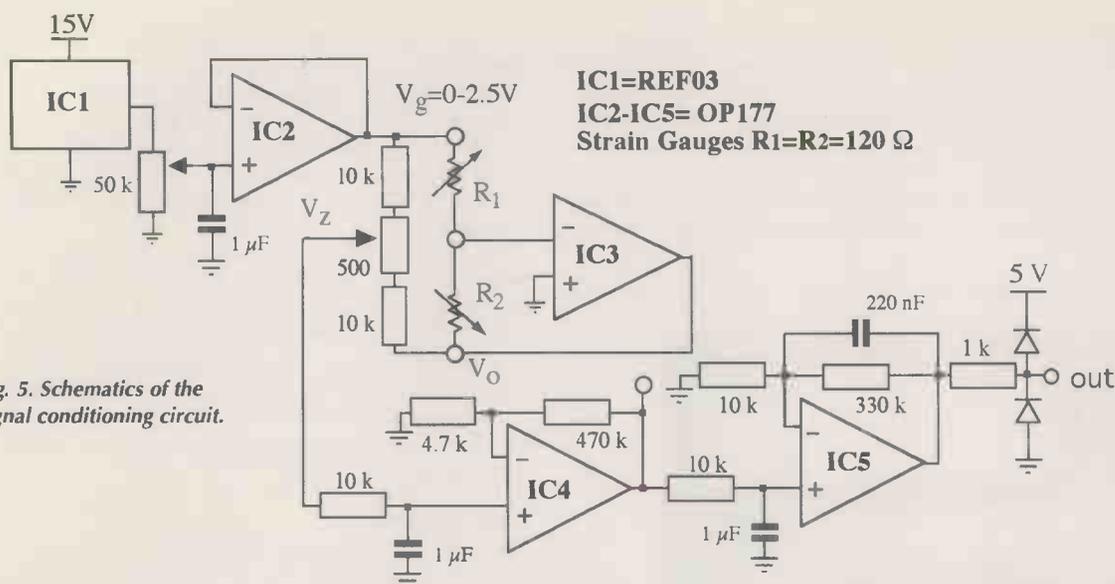


Fig. 5. Schematics of the signal conditioning circuit.

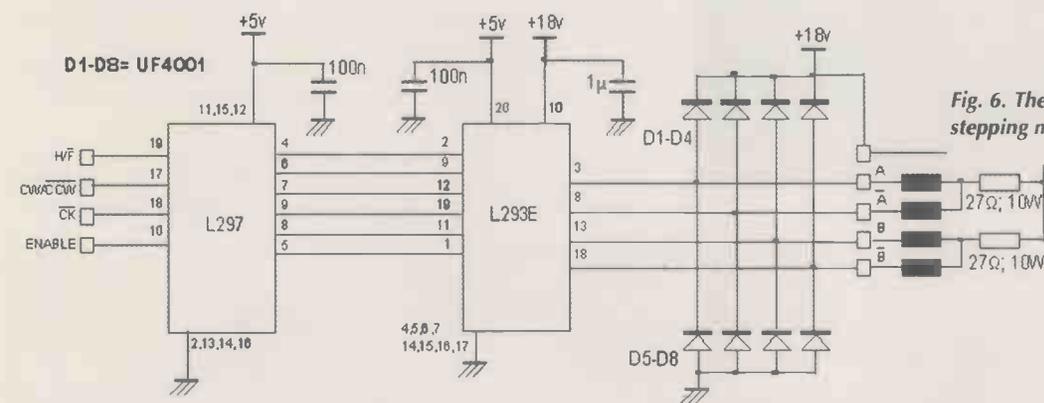


Fig. 6. The simple schematics of the stepping motors drivers.

arm of the bridge is made of the two strain gauges (120Ω) and the other one is made of two fixed resistors (10kΩ) and a balancing potentiometer (500Ω), which allows zeroing of the system before starting scanning a sample.

The strain gauges midpoint is kept at virtual ground by the operational amplifier IC3. The bridge is therefore biased by two signals: V_g and $V_O = -(R_2/R_1) V_g$, where $R_2 = R + G\epsilon$ and $R_1 = R - G\epsilon$ are the gauge resistances and $G\epsilon = \Delta R/R$ their relative resistance changes. The output signal $V_z \approx (1/2)(V_g + V_O) \approx 2\epsilon V_g$, taken at the sliding contact of the potentiometer, is amplified by IC4 and IC5: a differential amplifier is not necessary to amplify the bridge output voltage V_z , given that it is referred to

ground. As IC2-IC5 we have used four OP177 precision low voltage offset and low drift op-amps.

The stepping motors controller

To make the displacements automatic in the x and y axis during the sample scan, we have used for our device a BS2-IC (BASIC Stamp II produced by Parallax, Inc. <http://www.parallaxinc.com>), a simple and versatile PIC based microcontroller with a BASIC interpreter on board. The BASIC Stamp II program is shown in Text Box 1.

The BASIC Stamp II has 16 Digital I/Os that can be software configured as input or output. We needed five inputs, to sense the state of five buttons (UP, DOWN,

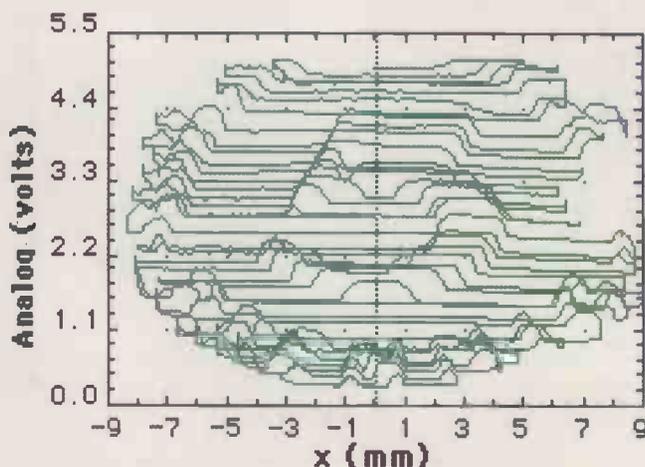
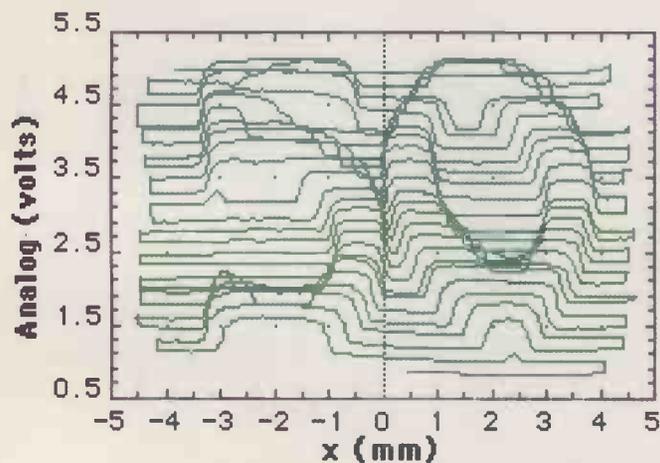


Fig. 7. Profiles of 50 and 5 Pfenning coins.

LEFT, RIGHT, AUTO SCAN), and 4 outputs, to drive the stepping motors. A sixth button, connected to the RESET pin of the BS2-IC makes possible to stop the scan process.

Figure 7 shows the interface circuit that we have used to drive each stepping motor. It is composed by an L297, that integrates all the control circuitry required to control bipolar and unipolar stepping motors, and by an L293E, a quad push-pull driver capable of delivering output currents

to 1A per channel. Both pins 17 (CW/CCW; clockwise/counterclockwise) of the two L297s are connected together. The same for pins 18 (CK).

The CW/CCW and CK signals are generated by the BS2-IC pins 14 and 13 (P8 and P9, respectively). The ENABLE signals, for the two L297s come from pins 15 and 16 (P10 and P11) as can be seen in the programme (Text Box 1).

H/F (half step or full step) is directly connected to the 'high' logic state. The interface output signals A, \bar{A} , B, \bar{B} , drive the windings of the stepping motors. We chose the model 15PM-K004 low cost, unipolar, small angle motors by MINEBA CO. LTD. Their holding torque is 650gcm and their current per winding is 0.36A with 8.6V applied. The 27Ω power resistors between the windings common leads and the 18V power supply are necessary to set the current at the correct value.

Some images

To give an idea of the capabilities of this device we present in figure 7 some images of coins obtained using 40 lines of 100 points per line; with a sampling frequency of about 4 points per second a total acquisition time of about 10 minutes is required.

A photo of the sample coins (50, 5 and 1 Pfennig, chosen for their small diameter and simple design) is shown in Fig. 8.

The images shown in figure 7 were taken using a wool-needle, with a not too sharp tip (whose radius of curvature R=0.28 mm is shown in figure 9a), thus reducing the risk

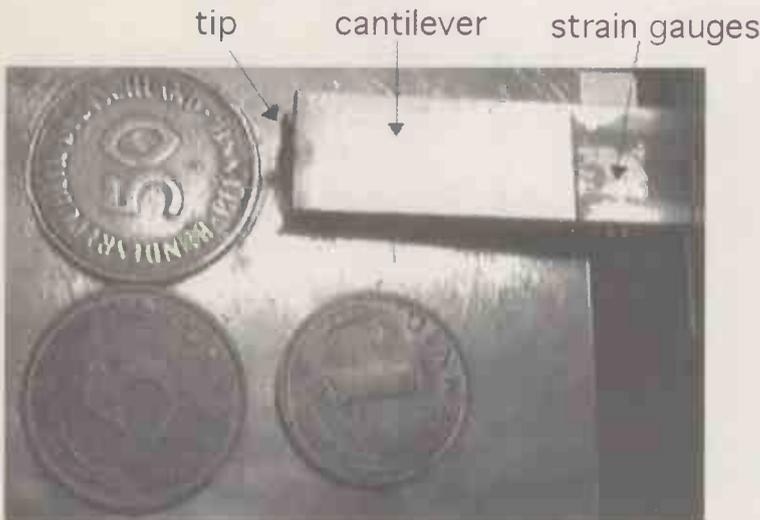


Fig. 8. The sample coins and the cantilever.

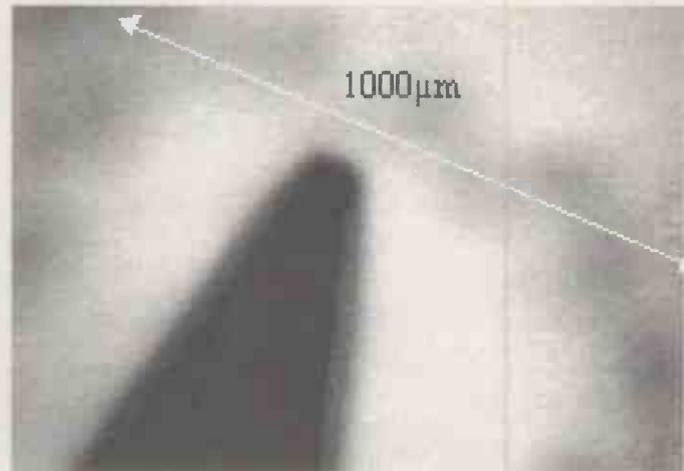
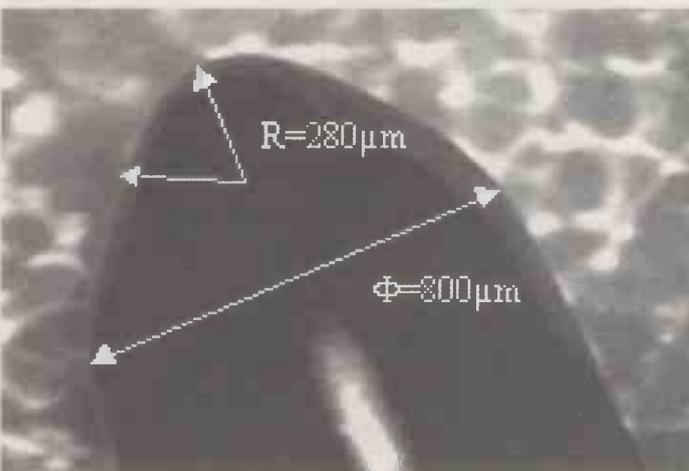


Fig. 9. Photomicrographs of a wool-needle tip (a) and of a sewing-needle tip (b).

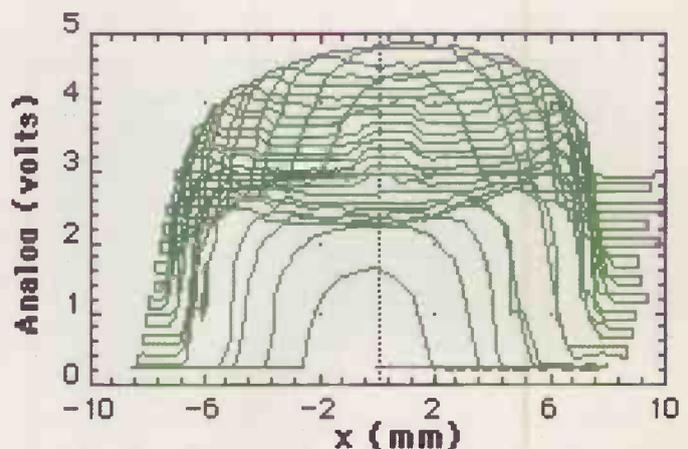
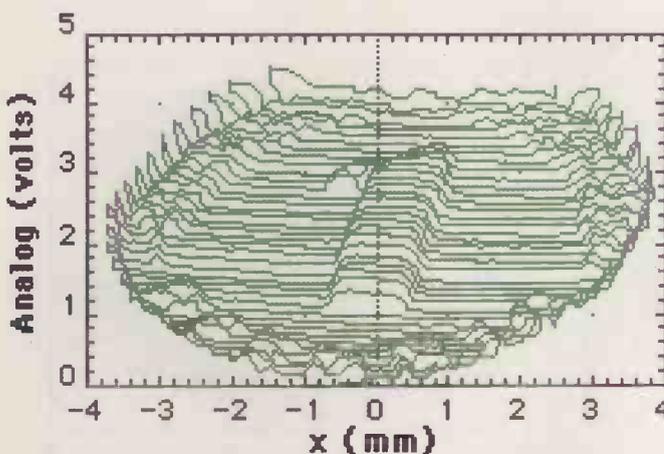


Figure 10: Images of the same sample (1 Pfennig coin) taken with different tips (see text)

of chokes and lateral deflections of the cantilever when crossing sharp steps on the sample. Our device is affected by this problem because it does not have the feedback mechanism that allows SFM to work at constant force: in that case when the tip meets a sample relief, the sample holder is suitably displaced along z to keep constant the cantilever deflection.

Obviously the lateral resolution is better the smaller the tip radius of curvature. To show this effect, that in the language of probe microscopists is named 'tip convolution'¹, we recorded two images, shown in figure 10, of the same sample first using a sharper sewing-needle ($R=0.08\text{mm}$) and then a ball-bearing sphere ($R=1.5\text{mm}$) as probe tips.

Using a curvature radius larger than the coin thickness, we can detect the sample borders (the tip can cross steps slightly smaller than R), but we spoil our lateral resolution. Using a smaller curvature radius we get better resolution, but the probe-sample interaction becomes important (note that in our devices the applied force increases with Δz), so that at the scan end the sample results are slightly damaged (see Text Box 2). The images shown in figures 7 and 10 report the x -axis calibrated in mm. How did we calibrated it? We simply measured the change ΔV^x corresponding to a known displacement Δx to calculate the conversion factor $K^x = \Delta x / \Delta V^x (\text{mm/V})$. To calibrate the y -axis we measure the change in the V^z signal produced by a known

shift Δy along a flat region of the sample surface: the conversion factor is $K^y = \Delta y / \Delta V^z (\text{mm/V})$.

For the z -axis we have $K^z = K^y \tan \alpha$, where α is the tilt angle between the sample surface plane and the x - y scan plane. ■

References

- 1 Giacomo Torzo: Dipartimento di Fisica, Università di Padova, INFN and CNR
Barbara Pecori: Dipartimento di Fisica, Università di Bologna
Pietro Scatturin: Dipartimento di Fisica, Università di Padova
Giorgio Delfitto: Dipartimento di Fisica, Università di Padova and INFN
- 2 For a bibliography on SFM see the websites:
<http://www.park.com/spmguide/contents.htm>, or
<http://www.spm.genebee.msu.su>, or the book Yaminsky I.V., Elensky V.G. *Scanning Probe Microscopy: Bibliography (1982-1997)*. Moscow: Scientific World, 1997. (A Series: Scanning Probe Microscopy; Vol. 2)
- 3 See G.Torzo and D. Cerolini: *SFM image reconstruction reducing tip artifacts*, Microscopy and Microanalysis, May 2000.

Calculus of the strain ϵ produced by the cantilever deflection Δz

The strain in elastic bodies is described by the relation $\epsilon = 1/E \cdot (F/S)$ relating $\epsilon = \Delta L/L$ to the applied force F , the section S and the Young modulus E (for steel $E \approx 22 \cdot 10^6 \text{ N/cm}^2$).

We are looking for a relation between the displacement Δz of the free end of a cantilever and ϵ . Thinking the cantilever (horizontal in equilibrium) as a beam of fibres, a deflection produces an increase of the fibres length on the convex side and a decrease on the concave side, with respect to the median fibre. Now, the length dx of an arc P-Q (figure 11) of the median fibre may be written as product of the curvature radius ρ and angle α : $dx = \rho \alpha$.

The relative length change, at the generic distance y from the median fibre is therefore $\epsilon = \pm y/\rho$, corresponding to an applied tangent force $dF = E dS (y/\rho)$, where $dS = b dy$ is the cross section of the fibre. A cantilever deflection corresponds to an applied torque given by the integral:


$$\Gamma = \int y dF = \int y^2 (E/\rho) dS = (E/\rho) j$$

$$\text{where } j = \int y^2 dS = a^3 b / 12.$$

Because the angle between tangents to the fiber in P and Q is α , the differential contribution to vertical displacement is $dz = x dx / \rho$, where x is the distance of P from the cantilever end (tip position). By substituting ρ we get $dz = (\Gamma/Ej) x dx$. Neglecting the cantilever weight, the equilibrium between applied torque F_x and the restoring elastic torque Γ gives $F = (Ej) x^2 dx$. The total displacement is obtained by integrating along the cantilever length: $\Delta z = (F/Ej) L/3 = (F/E)(4L^3/ba^3)$.

The strain ϵ changes along x growing with curvature $1/\rho$, reaching a maximum close to $x=L$, where the gauges are glued. Here $\epsilon = \pm (a/2)/\rho = \pm (a/2)(\Gamma/Ej)$, and the torque is $\Gamma = FL$. From $\Delta z = (F/Ej)L/3$ we get $(FL/Ej) = \Delta z/(3/L^2)$ and finally $\epsilon = \pm (a/2)(FL/Ej) = \Delta z(3a/2L^2)$. Higher sensitivity ($\sigma = \epsilon/\Delta z$) can be attained by increasing thickness a and reducing length L , but this also increases the tip to sample force $F = \epsilon E a^2 b / 6L = E \Delta z b a^3 / 4 L^3$. With $a=0.3\text{mm}$, $b=10\text{mm}$, $L=30\text{mm}$, the applied force with a deflection of 1mm is $0.25\text{N} \approx 25\text{g}$, already sufficient to slightly scratch a metal with a sharp needle.

Fig. 11. Schematics of the cantilever deflection.

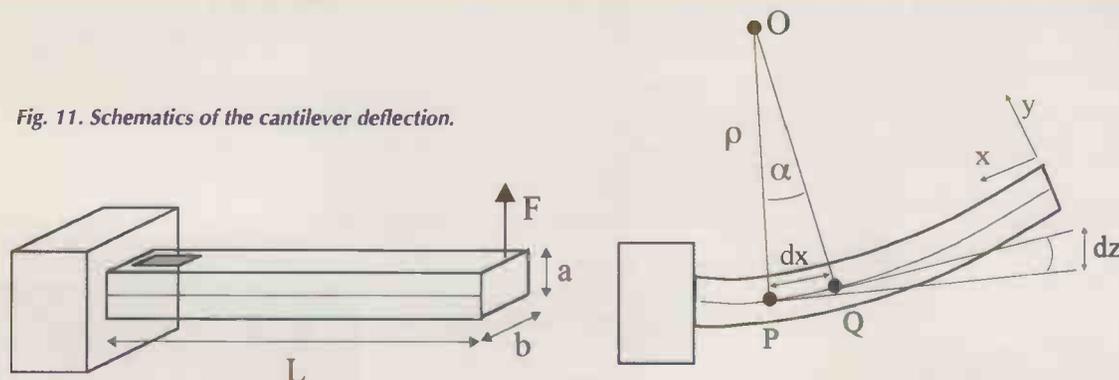

£2 BARGAIN PACKS

30A 600V BRIDGE RECTIFIER. Order Ref: 2P474.
 10 HOOK-UP LEADS. Assorted colours terminating with insulated crocodile clips each end, each lead length 36cm. Order Ref: 2P459.
 PHILIPS STEPPER MOTOR. 12V 7.5 degrees. Order Ref: 2P457.
 32µF 250V A.C. CAPACITOR. Order Ref: 2P452.
 4µF 440V A.C. CAPACITOR. Order Ref: 2P454.
 VERY POWERFUL MOTOR. Operates off 6, 9 or 12V D.C. 2 1/2in. long, 1 1/2in. diameter. Order Ref: 2P456.
 HIGH VOLTAGE STRIPPER. Contains many items for 10kV working. Order Ref: 2P388.
 GALVANISED EQUIPMENT BOX. 150mm square without lid. Order Ref: 2P391.
 4 r.p.m. GEARED MAINS MOTOR. 115V but supplied with mains adaptor. Order Ref: 2P393.
 TWIN 50pF AIR-SPACED TUNING CAPACITOR, the veins wide spaced so suitable for transmitting. Order Ref: 2P394.
 20 R.P.M. GEARED MAINS MOTOR. 115V but supplied with mains adaptor. Order Ref: 2P396.
 20µF 375V CAPACITOR. Aluminium cased. Order Ref: 2P406.
 9V-0V-9V MAINS TRANSFORMER. 25VA, upright mounting with fixings. Order Ref: 2P408.
 COPPER CLAD BOARD. Size 15in. x 10in. x 1/16in. thick for making p.c.b.s etc. Order Ref: 2P409.
 20W TWEETER. 4in. x 4in. 8 ohm by Goodmans. Order Ref: 2P403.
 BATTERY CHARGER METER. 0A-3A. Order Ref: 2P366.
 W-SHAPED 30W FLUORESCENT. Philips, ideal name plate illuminator. Order Ref: 2P372.
 DIMMER SWITCH. Standard size flush plate, state colour - red, yellow, green or blue. Order Ref: 2P380.
 TELEPHONE EXTENSION LEAD. 12m with plug end, socket ends. Order Ref: 2P338.
 FIGURE-8 FLEX. Mains voltage, 50m. Order Ref: 2P345.
 INFRA-RED UNIT. As fitted TV receiver. Order Ref: 2P304.
 L.C.D. CLOCK MODULE with details of other uses. Order Ref: 2P307.
 AM/FM RADIO RECEIVER with speaker but not cased. Order Ref: 2P308.
 2A MAINS FILTER AND PEAK SUPPRESSOR. Order Ref: 2P315.
 45A DP 250V SWITCH: on 6in. x 3in. gold plate. Order Ref: 2P316.
 SOLAR CELL. 3V 200mA, 5 of these in series would make you a 12V battery charger, £2 each. Order Ref: 2P374.
 PERMANENT MAGNET SOLENOID. Opposite action, core is released when voltage is applied. Order Ref: 2P327.
 HEATER PAD. Not waterproof. Order Ref: 2P329.
 DISK DRIVE. Complete less stepper motor, has all the electronics to control stepper motor. Order Ref: 2P280.
 15V 320mA A.C. POWER SUPPLY. In case with 13A base, ideal for bell or chime controller. Order Ref: 2P281.
 POWERFUL MAINS MOTOR with 4in. spindle. Order Ref: 2P262.
 20M 80 OHM TV COAX. Order Ref: 2P270.
 6-DIGIT COUNTER. Mains operated. Order Ref: 2P235.
 13A ADAPTORS. Take two 13A plugs, pack of 5, £2. Order Ref: 2P187.
 3-CORE 5A PVC FLEX. 15m. Order Ref: 2P189.
 MAINS TRANSFORMER. 15V, 1A. Order Ref: 2P198.
 7-SEGMENT NEON DISPLAYS. Pack of 8. Order Ref: 2P126.
 MODERN TELEPHONE HANDSET. Ideal office extension. Order Ref: 2P94.
 13A SWITCH SOCKET on satin chrome plate. Order Ref: 2P95.
 500 STAPLES. Hardened pin, suit burglar alarm or telephone wire. Order Ref: 2P99.
 ROTARY SWITCH. 40A with porcelain pointer control knob. Order Ref: 2P419.
 AIR-SPACED TUNING CAP with one section 350pF, the other 250pF, with 1/4in. spindle and slow motion drive. Order Ref: 2P422.
 DITTO but 150pF and 300pF. Order Ref: 2P423.
 TRANSMITTER TUNER. 2 gang, wide spaced. Order Ref: 2P425.

ENGINEERS BENCH PANEL

This has 2 x 13A mains sockets which are switched and illuminated, thus saving you having to keep pulling out the plugs. Nicely cased. Only £2. Order Ref: 2P461.

SELLING WELL BUT STILL AVAILABLE

HIVAC NUMICATOR TUBES, £1 each, £85 per 100.

IT IS A DIGITAL MULTI-TESTER, complete with backrest to stand it and hands-free test prod holder. This tester measures d.c. volts up to 1,000 and a.c. volts up to 750; d.c. current up to 10A and resistance up to 2 megs. Also tests transistors and diodes and has an internal buzzer for continuity tests. Comes complete with test prods, battery and instructions. Price £6.99. Order Ref: 7P29.



INSULATION TESTER WITH MULTIMETER. Internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges: AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P4.

REPAIRABLE METERS. We have some of the above testers but slightly faulty, not working on all ranges, should be repairable, we supply diagram, £3. Order Ref: 3P176.
 BT TELEPHONE EXTENSION WIRE. This is proper heavy duty cable for running around the skirting board when you want to make a permanent extension. Four cores properly colour coded, 25m length only £1. Order Ref: 1067.

HEAVY DUTY POT. Rated at 25W, this is 20 ohm resistance so it could be just right for speed controlling a d.c. motor or device or to control the output of a high current. Price £1. Order Ref: 1/33L1.

1mA PANEL METER. Approximately 80mm x 55mm, front engraved 0-1000. Price £1.50 each. Order Ref: 1/16R2.

D.C. MOTOR WITH GEARBOX. Size 60mm long, 30mm diameter. Very powerful, operates off any voltage between 6V and 24V D.C. Speed at 6V is 200 rpm, speed controller available. Special price £3 each. Order Ref: 3P108.

FLASHING BEACON. Ideal for putting on a van, a tractor or any vehicle that should always be seen. Uses a Xenon tube and has an amber coloured dome. Separate fixing base is included so unit can be put away if desirable. Price £5. Order Ref: 5P267.

MOST USEFUL POWER SUPPLY. Rated at 9V 1A, this plugs into a 13A socket, is really nicely boxed. £2. Order Ref: 2P733.

MOTOR SPEED CONTROLLER. These are suitable for D.C. motors for voltages up to 12V and any power up to 1/6hp. They reduce the speed by intermittent full voltage pulses so there should be no loss of power. Made up and tested, £18. Order Ref: 20P39.

BALANCE ASSEMBLY KITS. Japanese made, when assembled ideal for chemical experiments, complete with tweezers and 6 weights 0.5 to 5 grams. Price £2. Order Ref: 2P44.

CYCLE LAMP BARGAIN. You can have 100 6V 0.2A MES bulbs for just £2.50 or 1,000 for £20. They are beautifully made, slightly larger than the standard 6.3V pilot bulb so they would be ideal for making displays for night lights and similar applications.

SOLDERING IRON, super mains powered with long-life ceramic element, heavy duty 40W for the extra special job, complete with plated wire stand and 245mm lead, £3. Order Ref: 3P221.

RELAYS

MINI POWER RELAYS. For p.c.b. mounting, size 28mm x 25mm x 12 mm, all have 16A changeover contacts for up to 250V. Four versions available, they all look the same but have different coils:


6V - Order Ref: FR17 24V - Order Ref: FR19
 12V - Order Ref: FR18 48V - Order Ref: FR20
 Price £1 each less 10% if ordered in quantities of 10, same or mixed values.

RECHARGEABLE NICAD BATTERIES. AA size, 25p each, which is a real bargain considering many firms charge as much as £2 each. These are in packs of 10, coupled together with an output lead so are a 12V unit but easily dividable into a 2x 6V or 10 x 1.2V. £2.50 per pack, 10 packs for £25 including carriage. Order Ref: 2.5P34.

4 CIRCUIT 12V RELAY. Quite small, clear plastic enclosed and with plug-in tags, £1. Order Ref: 205N.

NOT MUCH BIGGER THAN AN OXO CUBE. Another relay just arrived is extra small with a 12V coil and 6A changeover contacts. It is sealed so it can be mounted in any position or on a p.c.b. Price 75p each, 10 for £6 or 100 for £50. Order Ref: FR16

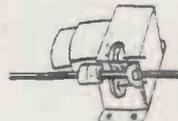1.5-6V MOTOR WITH GEARBOX. Motor is mounted on the gearbox which has interchangeable gears giving a range of speeds and motor torques. Comes with full instructions for changing gears and calculating speeds, £7. Order Ref: 7P26.



FOR YOU

Latest newsletter and very useful free gift with chance to earn £100. Just send us 2 first class stamps to cover postage.

£2 BARGAIN PACKS

24V STEREO POWER SUPPLY. Mullard. Order Ref: 2P80.
 UP TO 90 MIN 25A SWITCH. Clockwork. Order Ref: 2P90.
 POWERFUL MAINS MOTOR. 1 1/2in. stack, double spindle. Order Ref: 2P55.
 SPEED CONTROL FOR MODELS. 6V-12V variable p.s.u., also reverse. Order Ref: 2P3.
 MAINS TIME AND SET SWITCH. 25A, up to 6 hours delay. Order Ref: 2P9.
 MOTORISED 6 MICROSWITCHES but motor 50V A.C. Order Ref: 2P19.
 TWIN EXTENSION LEAD. Ideal lead lamp, Black & Decker tools, etc., 20m. Order Ref: 2P20.
 MAINS COUNTER. Resettable, 3 digit. Order Ref: 2P26.
 ILLUMINOUS PANEL, 16 x 16V bulbs to light coal effect heater, etc. Order Ref: 2P317.
 TIME AND SET SWITCH. 15A mains. Order Ref: 2P104.
 D.C. VOLT REDUCER. 12V-6V, fits into car lighter socket. Order Ref: 2P318.
 CAPACITOR, VARIABLE. For tuning AM/FM with 1/4in. spindle. Order Ref: 2P269.
 CAPACITOR, VARIABLE. 0.0005 solid dia. 1/4in. spindle. Order Ref: 2P268.
 COPPER CLAD BOARD. 15 x 10 x 1/16 for p.c.b. Order Ref: 2P409.
 25V-0V-25V MAINS TRANSFORMER. 1 1/2A. Order Ref: 2P410.
 20V-0V-20V DITTO. Order Ref: 2P411.
 80mm x 46mm 65mm METAL PROJECT BOX with rubber feet, supplied as flat pack. Order Ref: 2P412.
 24V 1A MAINS TRANSFORMER. Order Ref: 2P413.
 12V 2A MAINS TRANSFORMER. Order Ref: 2P414.
 80 OHM COAX. Extra thin, 15m. Order Ref: 2P417.
 A.C. 250V CAPACITOR. 20µF. Order Ref: 2P427.
 12V P.S.U. 800mA D.C. with pins for shaver socket. Order Ref: 2P428.
 MAINS MOTOR WITH GEARBOX giving 6 revs per hour. Order Ref: 2P430.
 CLOCKWORK TIMESWITCH with scale settable up to 6 hours. Order Ref: 2P432.
 OLD TIME RADIO CASE for the Good Companion. Order Ref: 2P436.
 4 OHM TWEETER. 20W, by Goodmans. Order Ref: 2P437.
 OLD TYPE 15A ROUND PIN PLUGS. Order Ref: 2P438.
 BT ENGINEER'S PHONE. Unused but missing some parts, ideal for stripping. Order Ref: 2P439.
 FLUORESCENT TUBE CHOKE. 65W or 80W. Order Ref: 2P440.
 MINI MOTOR WITH GEARBOX, giving 16 r.p.m. Order Ref: 2P442.
 ICESAT. Cuts in just above freezing. Order Ref: 2P443.
 BALANCE KIT with gram weights for chemical experiments etc. Order Ref: 2P444.
 Vu METER. 40mm square. Order Ref: 2P445.
 SLYDOK FUSE. 30A. Order Ref: 2P447.
 KV CAP. 1µF 1500V. Order Ref: 2P448.
 9V P.S.U. 1A D.C., plugs into 13A socket. Order Ref: 2P450.
 6-CORE 3AFLEX. 15m. Order Ref: 2P451.

SOME BUY ONE GET ONE FREE OFFERS

CUPBOARD ALARM. Activated by light. When set, this alert is designed to let you know when small hands open medicine cabinets, drawers, desks or other places they shouldn't. Price £3. Order Ref: 3P155.

WATER LEVEL ALARM. When water reaches its sense head its internal alarm sounds. It is a ready-built unit which you can fix above where you want to know the water has risen. It then sounds its internal alarm. Needs only a battery. Price £3. Order Ref: 3P156.

DYNAMIC MICROPHONE. 500 ohm, plastic body with black mesh head, on/off switch, good length lead and terminated with audio plug. Price £1. Order Ref: 2P220.

TERMS

Send cash, uncrossed PO, cheque or quote credit card number. If order is £25 or over deduct 10% but add postage, £3.50 if under 2 kilo, £6 if under 4 kilo.

J & N FACTORS

Pilgrim Works (Dept.E.E)
 Stairbridge Lane, Bolney
 Sussex RH17 5PA
 Telephone: 01444 881965

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

White LEDs have 35mcd brightness

Rohm has expanded its family of miniature surface mount white chip LEDs with three devices that combine high brightness with low typical and maximum forward voltage (V_F) ratings of 3.0V and 3.3V respectively. Designed to provide enhanced PCB mounting flexibility, the new parts have dimensions down to 1.6 x 0.8 x 0.55mm and are ideal for consumer and telecom applications, said the supplier. Typical brightness levels for the



new devices are in the region of 35mcd at a forward current (I_F) of 5mA. Maximum I_F is rated at 20mA, while each LED will handle a peak I_F of 100mA (pulse duration 30ms).
Rohm
www.rohm.co.uk
Tel: +44(0) 1908 282284

2-2-2 DDR Dram

Smart Modular Technologies owned by Solectron, now has low latency PC2100 registered double data rate (DDR) memory modules aimed at increasing memory speeds in high performance computing and server applications. The line-up features a 2.1 Gbyte/s data throughput and CAS latency timings of 2-2-2 (CAS) delay,

RAS-to-CAS delay, pre-charge). Intel has validated the devices on a Xeon-based Prestonia server reference platform featuring the Plumas-533 chipset (533MHz, front side bus).
Smart
www.smartm.com
Tel: +44(0) 1928 735651

Voltage regulator can be buck or switch

Semtech has a low-voltage current-mode regulator controller that can be configured into a buck, buck-boost



(inverter) or zeta (step-up or step-down) switching-regulator topology. The SC4508 is for driving p-channel power Mosfets to supply up to 6A output current. It accepts inputs from 2.7 to 15V. Its programmable switching frequency, up to 1.5MHz, allows for small capacitors and coils. Output voltage is programmable, through a resistor divider over positive voltages from $V(\text{Ref})$ to $0.9 \times V_{in}$ or, on the negative side, from -1 to -200V. It typically draws about 3mA in normal operation, which drops to 200 μ A in shutdown mode.
Semtech
www.semtech.com

MPC5200 PowerPC gets RTOS support


Green Hills Software is supporting Motorola's MPC5200 PowerPC processor with its Integrity RTOS, multi integrated development environment and C, C++ and Misra C compilers. This software is for developers of embedded systems for mobile and fixed applications in

telematics, gateways, industrial control and electronic and medical instruments. The deterministic RTOS builds on the hardware memory protection facilities of the MMU. It provides a firewall between the kernel and user tasks that prevents errant or malicious code from corrupting user data, the kernel, inter-process communications, device drivers and other tasks. It also runs with interrupts continuously enabled, guaranteeing access to the CPU and memory for critical tasks, even during RTOS system calls. The 400MHz device delivers



Ethernet connector

Pulse has a range of IEEE 802.3af compliant Power over Ethernet (PoE), 10/100BASE-TX transformer modules, specifically designed for mid-span PoE applications. The use of products H1180, H1183 and H1197 upgrades an existing Ethernet connection to a power over Ethernet compliant system, allowing a remote device to receive power and data over the same unshielded twisted pair (UTP) cable. The H1180, H1183 and H1197 are placed in parallel (in-line) with the existing UTP Ethernet cabling architecture. Their high input impedance makes each transformer appear transparent to the existing Ethernet system,

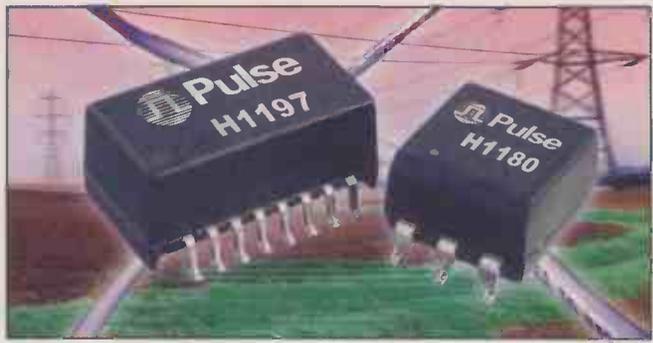

instantly upgrading the connection, said the company. This upgrade thus reduces cost and time-to-market for establishing a PoE-enabled system. The components can deliver 15W of power to a remote device located 100m away, making them suitable for remote power-feeding applications

such as security camera equipment, wireless networking systems, remote sensors and transducers, and VoIP phones. The modules deliver a minimum of 1,000Vrms isolation and 350mA capability.
Pulse
www.pulseeng.com
Tel: +44(0) 1483 401700

NEWPRODUCTS

Please quote *Electronics World* when seeking further information

760Mips and consumes less than 850mW.

Green Hills Software
www.ghs.com

Headphone amp for single-cell designs

National Semiconductor is offering a version of its Boomer stereo headphone amplifier to operate from a one cell 1.5V battery. The LM4916 is unity gain stable. It is a mono differential output (for bridged loads or BTL) audio power amp and a single-ended stereo headphone amp. Operating from a 1.5V supply, the mono BTL mode delivers 85mW into an 8Ω load at 1 per cent THD+N.



In single-ended stereo headphone mode, the amp delivers 14mW per channel into a 16Ω load at 1 per cent THD+N.

National Semiconductor
www.national.com

Resolver-to-digital converter option improves accuracy

Data Device has announced an option for its RD19230FX resolver-to-digital monolithic converter that provides an accuracy of one arc minute. Resolver-to-digital converters take analogue AC inputs from resolvers, which are rugged angular transducers, and convert them to digital angular format. The device also provides programmable 10, 12, 14 and 16-bit resolution, dual



bandwidth and tracking rates, +5V only input power, internal synthesised reference, and A quad B encoder emulation. Applications include motor control, radar antenna position, machine tool control, robotics and process control. Available with operating temperatures of -40 to +85°C (FX-205) and 0 to 70°C (FX-305), the converter is in a 10 by 10mm, 64-pin, plastic quad flat pack.

Data Device
www.ddc-web.com
Tel: +44(0) 1631 567 5600

5V reference accurate to ±0.5mV

Xicor has introduced 5V reference devices which it claims offer a guaranteed absolute initial accuracy as low as ±0.5mV, straight-line temperature coefficients of 5ppm/°C, and a long-term stability of 10ppm/1000 hours.



Power consumption is 500nA of supply current. Both devices feature a noise voltage figure of 30μV p-p (0.1 to 10Hz), and an operating temperature range of -40 to +85°C. They are the first devices in an extensive family of precision voltage references manufactured using Xicor's proprietary FGA technology, which the firm claims achieves performance levels that exceed conventional burid-zener and band-gap technologies.

Xicor
www.xicor.com
Tel: +44(0) 1993 700544

Tiny dual PLL runs up to 6GHz

Fujitsu Microelectronics Europe has announced the MB15F7xUV series, sub-miniature dual PLL frequency synthesisers for high frequency mobile comms. The design of the PLLs enables the devices to be housed in the industry's smallest PLL enclosure, claims the firm, an 18-pad 'bump chip carrier' measuring 2.4 x 2.7 x 0.45mm. Fabricated in Fujitsu's 0.35μm BiCMOS, the family is capable of operating from 2.4 to 3.6V. Fujitsu Microelectronics
Tel: +44(0) 049 6103 6900

Modular PSUs with increased output

Astic Power has added new output power ratings to its MOP modular power supply series. The existing four MP models now deliver an extra 200W of output power at high line voltage when compared to their universal voltage ratings. Four chassis sizes are available. These enable installed output modules to deliver maximum power levels of 600W, 800W, 1,000W and 1,200W to their designated loads when operated at high line. Each chassis can be configured with almost any combination of more than 25 commercial-off-the-shelf output modules to provide a variety of output voltage combinations from 2V to 60V with output current capacities from 0.5A to 120A. Each chassis can accommodate up to seven output

Power supply packs it with plug-in modules

A configurable power supply that packs up to 700W into a chassis that measures 266.7 x 127 x 63.5mm has been introduced by XP. The F7 modular AC-DC power unit uses plug-in modules to provide up to nine floating outputs between 1.9 and 150V DC. Outputs can be connected in series or parallel, the latter using active current sharing. The rugged design has a universal AC input with integral power factor correction and 40A maximum peak inrush current. The outputs are adjustable by ±5 per cent and have maximum ripple and noise of 50mV or 1 per cent peak-to-peak,

whichever is greater. Line regulation is typically 0.1 per cent and load regulation is 1 per cent maximum for single output modules and 2 per cent for dual or triple output modules. It has over-voltage protection at 115 to 140 per cent of nominal, depending on the individual module and output, and overload protection which operates at 140 per cent of nominal rating. The signal set includes a TTL-compatible inhibit function, DC OK signal, power fail indication and a 5V 1A housekeeping rail.

XP
www.xppic.com
Tel: +44(0) 1271 856666



FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV
BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
MC MDA J MJE MJE MM MN MPS MP5A MP5H MP5U
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
ZTX + many others

Please ask for our Free CD Rom STOCK LIST.
WE STOCK A MASSIVE RANGE OF COMPONENTS!

Mail, phone, Fax, Credit Card orders & callers welcome.



Connect

Cricklewood Electronics Ltd

40-42 Cricklewood Broadway, London NW2 3ET


Tel: 020 8452 0161 Fax: 020 8208 1441

www.cricklewoodelectronics.co.uk

E-mail: sales@cricklewoodelectronics.com

ROLL-YOUR-OWN

minimal embedded Linux system

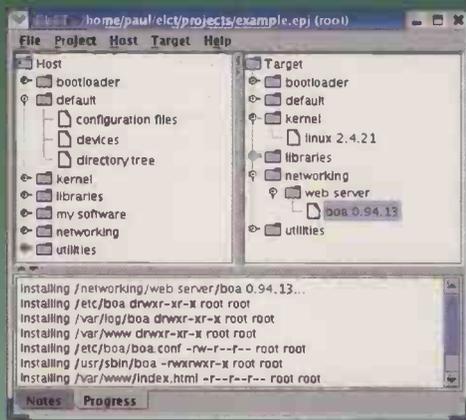

Embedded Linux Configuration Tool

Select the software to include in your target project. Use ELCT to launch source configuration programs, compile source, check for library dependencies and install to the target.

Included on the ELCT CDROM is enough open source software for you to roll-your-own minimal Linux system.

See our website for more details.

£135
excl. VAT

Ashdown Electronics Ltd

www.ashdownelectronics.com

sales@ashdownelectronics.com

Telephone 01342 315656



A QUANTUM LEAP IN EMBEDDED CONTROLLERS

Quick FIRE

SUPERCONTROLLERS

Our range provides:-

- The fastest 68000 based Core up to 66 Mhz.
- Extensive I/O:- Serial, IrDA, SPI, I²C, Analogue, Timers/Counters, RTC, etc.
- Large Memory Capacity:- Flash, SRAM, DRAM.
- Supports:- Mono & Colour LCD's, Touch Panels & Keypads, Very Low Power.

ALSO LOW COST

DEVELOPMENT

- Target easily & quickly.
- Full ANSI 'C' compiler, assembler & linker all Windows32 based.
- Source Level Debug.
- Full Driver Support with Libraries.
- Real Time Multitasking OS with a free run time licence.
- Free Unlimited email support.

www.cms.uk.com

see our web site for full details

CAMBRIDGE MICROPROCESSOR SYSTEMS LTD



Unit 17-18 Zone 'D' Chelmsford Rd. Ind. Est.
Great Dunmow, Essex CM6 1XG

Telephone: **01371 875644**

email: sales@cms.uk.com

NEWPRODUCTS

Please quote *Electronics World* when seeking further information

modules. The modules are suited to computing, networking, office systems and data communications.

Astec Power

www.astecpower.com

Tel: +44(0) 031 24372 3212

Mobile test platform for 3G troubleshooting

Tektronix has available a mobile protocol test platform equipped with application software to test complex third-generation (3G)

and existing second-generation (2G, 2.5G) mobile networks. According to the company, the test platform and supporting application software allows operators to resolve service degradation warnings within minutes with multi-interface call trace and automatic UMTS configuration. The real-time troubleshooting capabilities of the application software should also allow technicians to automatically configure monitoring parameters, correlate data coming from multiple interfaces and locate the root cause of faults while sustaining high data capture rates. Technologies supported include UMTS, CDMA2000, cdmaOne, EDGE, GPRS and GSM.

Tektronix

www.tektronix.com

Tel: +44(0) 01344 392241

Power rocker switches

The CG and CL series of panel mount power rocker switches from ITT Industries, are targeted at small appliances, instrument panels, industrial controls, floor care products, and computers and peripherals. The CG series can be supplied with a two tone actuator or can be illuminated



with white, red, amber, or green actuators. Additionally, the actuators can be marked. The CL series feature a positive detent and were designed for easy snap-in mounting. With constant ratings of 16A at 125VAC or 10A at 250VAC, both series have UL and CSA approvals. The CG series also have VDE approval.

ITT Industries

www.ittcannon.com

Tel: +44(0) 01 617 969 6600

Kits adapt test equipment for cars

Fluke has introduced two kits aimed at technicians working on automotive systems. Designed for use with any handheld Fluke ScopeMeter, the kits include suitable shielded and heat resistant test leads, probes and clips together with PC

compatible software. The SCC128 Auto Kit is designed for use with a 20MHz or 40MHz bandwidth, 5000 counts true-RMS 120 Series ScopeMeter, and the SCC198 Auto Kit for use with a ScopeMeter from the up-to-200MHz and 2.5Gsample/s 190 Series. Both kits contain FlukeView for Windows software and an optically isolated connecting cable. A library of named test set-up waveforms and measurements can be built up and uploaded to the ScopeMeter for comparison in the field. Captured waveforms, screens and measurement data can be downloaded to a PC for archiving, printing or importing into reports.

Fluke

www.fluke.co.uk

Tel: +44(0) 20 7942 0700

Custom oscillators up to 2.4GHz

RFX use PLL techniques to produce custom oscillator modules, with frequencies up to 2.4GHz, from a high base oscillator. The oscillators may be locked to an internal or external high precision reference resulting in a very high precision clock. Jitter levels of 0.5ps can be achieved together with excellent phase noise and low ageing characteristics producing accuracies to 0.005ppm max./day. Modules are available with ECL or sine wave output. Applications are communications equipment, instrumentation and system synchronisation.


RFX

www.irfx.co.uk

Tel: +44(0) 01506 873797

Battery-backed PSU has modbus functions

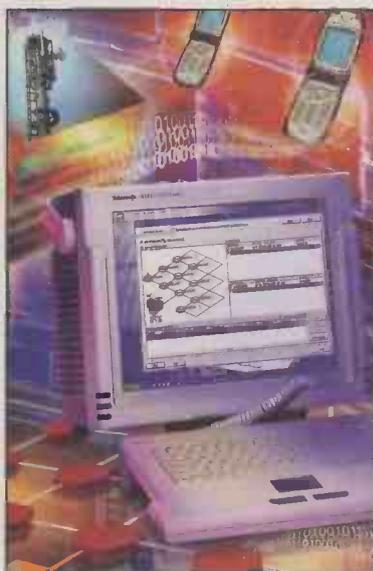The Oracle 111 200 battery-backed switch-mode power supply from VXI Power has a built-in RS232/RS485 interface with modbus functionality, so it can be controlled or monitored remotely. As well as logging data on historical holdup events, the PSU lets the user monitor parameters such as system load



Smallest single-gate logic devices

Toshiba claims to have the smallest single-gate logic device. The logic-MOS (LMOS) device comes in a


miniature style FSV package measuring 1.0 by 0.48mm. According to the supplier, board-mounting area can be

76 per cent less than previous generation USV (SOT353) alternatives and over 60 per cent less than miniature ESV packages. The TC7SHxx devices operate with a supply voltage between 2 and 5.5V and offer a typical propagation delay of 3.7ns. Output current is 8mA, with power dissipation 50mW. All devices incorporate input power down protection as standard. The range includes two-input NAND, two-input AND, two-input NOR, two-input OR and two-input EX-OR single-gate logic functions, as well as various inverter and buffer options.

Toshiba

www.toshiba.com

Tel: +44(0) 049 211 5296 254

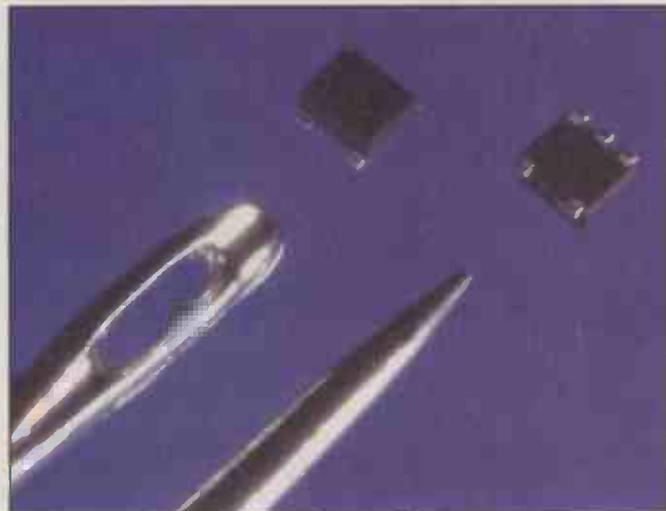

Please quote *Electronics World* when seeking further information

or battery test cycles. The power supply incorporates a two-stage charger with power shift software to reduce battery recharge time. Operating from an 85-264V AC autoranging input, the PSU is available in 12 and 24U versions.

VXI Power
www.vxipower.com
Tel: +44(0) 1522 500511

Devices allow digital Internet link

Epson has introduced the SIS61000 and SIS65000 TCP/IP network device products to let users develop and connect digital electronics to the Internet. The SIS61000 is an open-platform network controller that provides a development environment with the source code disclosed. The SIS65000 is a network controller that lets a camera network be built simply by connecting camera modules. Applications are in white goods, intelligent building, industrial and manufacturing control,

transaction and payment terminals, POS, Soho, laboratory measurement equipment, sensors and monitoring, remote data collection equipment, network cameras, video projectors and protocol converters such as serial-to-Ethernet. The SIS61000's network connection is via simple command operations using the firm's network control procedure. It controls devices from the network via general-purpose I/O pins¹2C bus, and is usable as a main processor thanks to its ARM720T with unified cacheCPU and open hardware and open software. The SIS65000 is a dedicated network camera controller. Based on the SIS61000, it is further outfitted with a camera interface and JPEG encoder. Pictures can be transmitted at up to 7.5fps in VGA size. Features include PC-less Internet camera function capability, compatibility with various camera modules, up to VGA size and rewritable JPEG encoder table. Energy-

saving is done by using a timer or other device for intermittent starting or stopping. A wireless LAN interface is supported.

Epson
www.epson-electronics.de
Tel: 49 8914 005363

White LED for high end lighting

Vishay Intertechnology has added to its TLCx5100 LED series with the TLCW5100, a 5-mm white LED for high-end lighting applications. The TLCW5100 is a clear, non-diffused LED with 0.33 chromaticity and typical luminous intensity of 4000 mcd. The LED has a 9° angle of intensity and an untinted plastic lens. The TLCx5100 series serve as energy-saving alternatives to incandescent lamps in a broad range of applications.

Vishay
www.epson-electronics.de
Tel: 49 7131 67 2831

Humidity controllers blow hot and cold

Available from distributor Switchtec, Vemer measurement and regulation controllers for temperature, humidity and pressure can be used for most industrial applications, but particularly the air conditioning, heating and refrigeration industry. Such applications include chill cabinets as used in delicatessens and supermarkets. The controllers offer mounting options including 72 x 72mm,

32 x 74, panel, and DIN mount. Models with highly visible displays are available comprising three digit, seven segment units. Additionally, one, two or four relay output versions are available for controlling multiple external devices and equipment. Thermoresistances NiPt cover the range -20°C to +400°C, thermoresistances NTC from -40°C to +110°C, and thermocouples JK (Fe-Co and Cr-Al) from -200°C to +1200°C
Switchtec
www.switchtec.co.uk
Tel: +44(0) 1785 818600

Ferrite for transformers


TDK Electronics Europe GmbH has started mass production of its PC95 ferrite core material for use in power supply transformers. The PC95 ferrite addresses the increase in demand for smaller and higher efficiency transformers used in DC-DC converters and inverters, as well as the need to comply to a broader range of temperature conditions. Designed for use in near-optimal conditions over a broad temperature range of 25°C to 120°C, the PC95 is for use in conventional switching power supplies, as well as in the main transformers of DC-DC converters of electric automobiles.

TDK
www.tdk.de
Tel: 49 211 9077 183

Boxes suit handheld or desktop devices

Serpac's range of enclosures has been updated with the S, SL and A series cases for housing handheld, portable and desktop devices, and consisting of two or four piece

design., assembled with four or six self-tappingscrews. The top panel of the SL series is inclined for improved ergonomics when used on a desk, said the supplier. The enclosures come with or without a battery compartment for a 9V PP3 cell. All ranges are made in ABS plastic (UL94 HB) in standard colours of black, grey or almond. Other colours are available on demand. As an option, the S series top panel can be recessed for mounting a membrane keypad or a product label. All include internal screw bosses for mounting PCBs. Accessories include a pocket clip that is welded to the base, replacement A series end panels in infra-red, clear and red Plexiglass, and black or clear self-adhesive feet
Serpac
www.serpac.co.uk
Tel: +44(0) 1489 583858

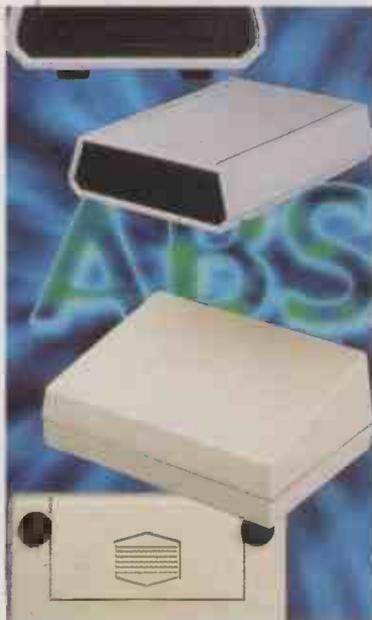

OLSON

UK's NO.1 IEC CONNECTION



CALL OUR SALES HOTLINE

020 8905 7273



24 HOUR DELIVERY SERVICE



OLSON ELECTRONICS LIMITED
OLSON HOUSE, 490 HONEYPOT LANE, STANMORE, MIDDX HA7 1JX
TEL: 020 8905 7273 FAX: 020 8952 1232
e-mail: sales@olson.co.uk web site: http://www.olson.co.uk

Please quote *Electronics World* when seeking further information

Processor with IPsec accelerator

Renesas Technology has announced the SH7710 32-bit Risc microprocessor with an IPsec accelerator for fast encryption and communication processing. The device also has



two on-chip Ethernet controllers that enable connection to two Ethernet LANs. Both peripherals make it suitable for security enabled devices for networks such as VPN dedicated boxes, home gateway servers, surveillance cameras and IP phones. The SH7710 is based on a SuperH Risc SH3-DSP CPU core that operates at up to 200MHz and achieves a processing capability of 260Mips. The on-chip DSP supports various kinds of

middleware, such as a voice codec and echo canceller, and enables fast execution of multimedia related processing such as VoIP. The IPsec accelerator implements security in the IP or network layer and supports Des and 3Des encryption and decryption methods and MD5 and SHA-1 authentication data generation methods. As well as the encryption circuitry, buffer memory and dedicated data transfer DMACs are provided, allowing data transfer directly between external memory and the buffer memory, and between the buffer memory and encryption circuitry, without CPU load and enables communication processing to be executed at speeds upwards of 20 Mbit/s with a VPN configuration when using 3Des processing. Evaluation boards – such as the Hitachi ULSI Systems' Solution Engine and Renesas Technology's E10A simple emulator – are supported as development environment tools. User development of various protocol stacks is supported by the third-party providers.

Renesas Technology
www.renesas.com
Tel: +44(0) 1628 585100

Claim for smallest Schottky diode

The IRI40CSP Flipky device in a standard ball-grid array (BGA) package occupies 2.25mm². According to the supplier, this is 86 per cent smaller than the standard SMA package. The 1A, 40V Schottky diode is a four-ball, 1.5 x 1.5mm device with a height of less than 0.8mm.

The BGA package enables size reduction and better heat transfer away from the die junction to the circuit board. Since this device is made with chip scale packaging, it dissipates heat directly from the die into the air, increasing thermal efficiency. Thermal resistance junction-to-ambient is 75°C/W maximum and thermal resistance junction-to-PCB is typically 55°C/W.

International Rectifier
www.irf.com
Tel: +44(0) 208 645 8003

Filterless class D audio amplifier

Maxim Integrated Products is offering a filterless class D audio amplifier. The Max9712 offers class AB circuit design with no output filters and class

AB audio performance (0.06 per cent THD+N), with 90 per cent class D efficiency, says the company. The device uses a modulation scheme that meets FCC radiated emissions standards without the need for an output filter or ferrite beads. It operates over a 2.4 to 5.5V supply, has a fixed gain of 12dB and produces up to 500mW per channel into an 8Ω load. High 70dB PSRR at 217Hz allows operation directly from a single lithium-ion cell without the need for additional supply conditioning. It includes four clocking options to optimise the noise spectrum for a given application. These include three internally generated clock rates and a fourth unique external-clock mode, letting the user control the exact placement of the switching energy. Multiple device scan operate in a master-slave configuration. It comes in 12-pin UCSP (1.5 x 2 x 0.6mm), ten-pin DFN (3 x 5 x 1 mm) packages.

Maxim
www.maxim-ic.com
Tel: +44(0) 118 930 3388

Circular Dins for automotive use

ITT Cannon's APD circular DIN72585 connectors are for automotive, transport and industrial environments, including those subject to shock and vibration. Available in one, two, three, four, six and seven way configurations, the connectors come with a bayonet coupling or as a flanged version. The one way circular connector can handle up to 245A using a 50mm square wire cross section. The dual way has two cavities that can accommodate 16mm square wire cross section with a current capability of 74A. Two, three and four contact connectors have a maximum current rating of 30A, while six and seven way products handle 16A.

ITT Canon
www.ittcannon.com
Tel: 49 7151 699 252


Thermistors are linear

Betatherm has introduced what it believes is the world's first standard linear series of NTC thermistor probes. Betalinear thermistors, available from Sequoia Technology are based on a combination of precision resistors and thermistors, which

together generate a linear response to temperature. The linear composite typically consists of two or three sensor elements; the most popular being 36K53A1, which uses two thermistor elements (30K5 and 6K3) and appropriate resistors to

give a linear output between 0 and 100°C. The circuit designs can accommodate various circuit mounting options. These include custom probe assemblies for the thermistor sensing elements and mounting precision resistors at board level in a control module. It is also possible to package the thermistors and resistors that form the linearisation circuit into one probe construction. The networks are suitable for temperature measurement and control from -30 to +100°C and can be configured in either resistance or voltage mode where they can provide up to ten times the voltage output of a thermocouple sensor.

Betatherm
Tel: 353 91 753238

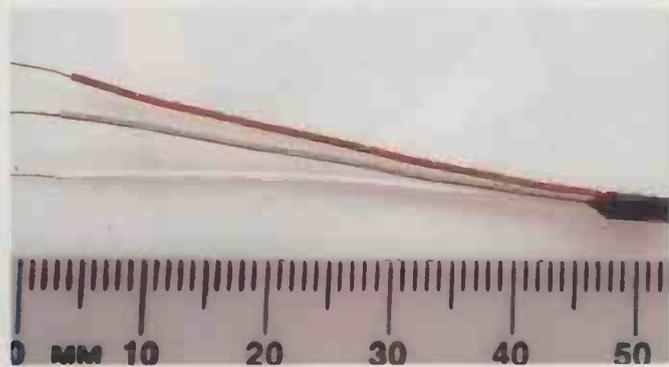



WELDEX 2003

WELDCOME. 11-14 November 2003
National Exhibition Centre Birmingham, UK

11-14/NOVEMBER/03

Join us at Weldex 2003

The international welding, joining, cutting and fabrication exhibition
co-located with Manufacturing Week INSPEX, Tooling and CIM (T.E.A.M)

Weld class event

At Weldex 2003 you will experience, first hand, the very latest products, services and technologies in welding, joining, cutting and fabrication. As the largest international show of its kind in the UK, Weldex 2003 represents a unique opportunity to make contact with some of the biggest and best names in the business, from all over the world.

Weldex 2003 is the event in the UK welding calendar

Whether you are selling, buying, learning, or just staying in touch, Weldex 2003 is the place to do good business in the UK. So make a date to join us at the NEC, Birmingham, 11 - 14 November 2003.

For tickets and early registration visit: www.weldexpo.com or call
Nichola Mitchell: +44(0)1322 660070 **NOW!**

To find out who's exhibiting at Weldex 2003 contact: Karin Allfree or Isobel Roberts:
+44(0)1322 660070

WEEX/VAD/HHC/IPG

Supported by:



American Welding Society



Official sponsoring publications:

ENGINEERING
DISTRIBUTOR



Quality Today

weldex news

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem – provided it has a degree of ingenuity. Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Don't forget to say why you think your idea is worthy.

Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best – but please label the disk clearly. Where software or files are available from us, please email Jackie Lowe with the circuit idea name as the subject.

Send your ideas to: *Phil Reed, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU*
email ewcircuit@highburybiz.com

Bipolar reference generator from a printer port

Using a small and low cost circuit Fig. 1. with simple control software, you can extend the utility of your PC's printer port for yet another purpose. With your printer port, you can implement a versatile programmable bipolar reference generator by using this circuit. Built using a few readily available low cost components, the circuit occupies a very small space and can be easily attached to the printer port of your PC. You can effectively use this programmable reference generator as a 'stable reference source' for testing your circuits without going for a big, mains powered general-purpose reference generator or any PC add on cards. Further, with this design, you need not turn pots or set thumb wheel switches for setting or changing the reference output to any desired value. All you need to do is just enter the desired voltage and the PC does the rest to set the reference output to the desired bipolar value!

As shown in Fig.1. the circuit uses a low power, programmable 13-bit DAC (IC1, MAX5130), a

programmable inverting amplifier (IC2, OP07) and a polarity control switch (IC3, MAX4541CPA). The PC, depending on the reference output required by the user, controls the DAC using three-wire serial interface. Thus the data lines D₀ to D₂ of the data port (0x378h) of printer interface are used by the PC for sending the Chip Select (/CS), data (DATA) and clock (CLK) signals to the DAC. Depending on the data sent by the PC, the DAC produces a voltage output in the range of 0-4.0955 volts in 8192 steps with a step resolution of 0.5mV. Thus data of 0x4000h to the DAC produces the DAC output of 0.00volts while the data of 0x5fffh results in the DAC output of 4.0955volts. Using the 2.5 volts internal reference available in the DAC itself, the output of the DAC and the data input are related as per the following equation:

$$V_{out} = \pm (2.5 * (DATA/8192) * GAIN)$$

where DATA is the decimal equivalent of binary data sent to the DAC and GAIN is the gain of the DAC's

Continued over page

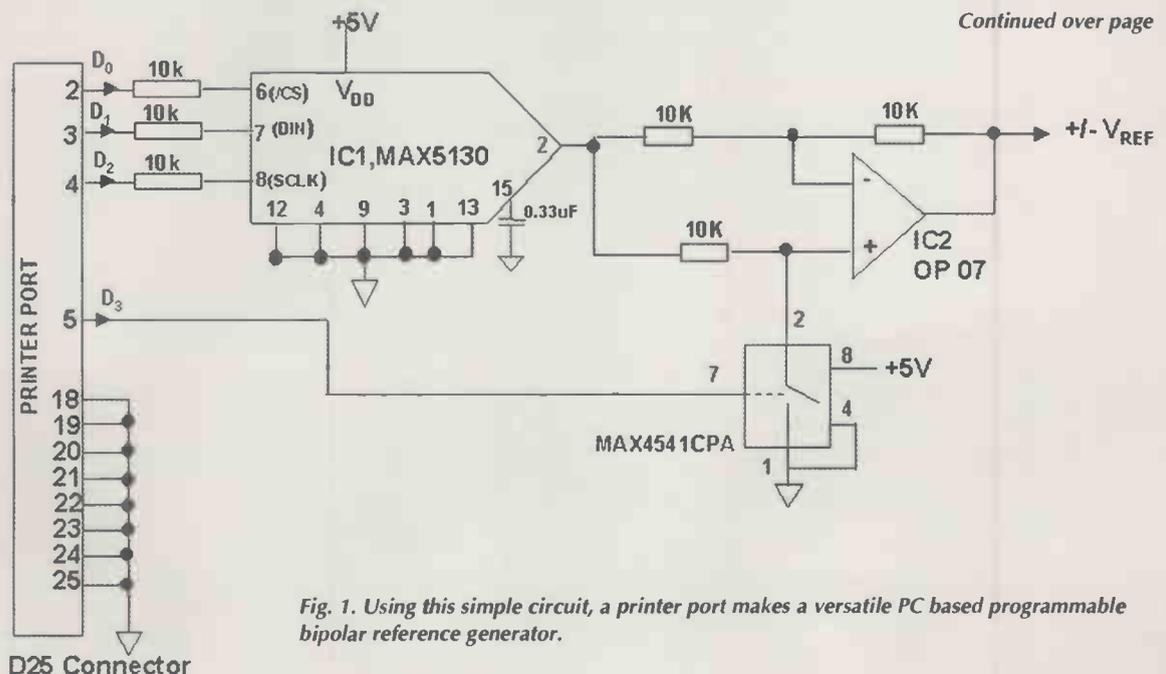


Fig. 1. Using this simple circuit, a printer port makes a versatile PC based programmable bipolar reference generator.

Listing 1

```
/**Turbo C program for "Printer port implements a programmable bipolar reference generator***/
```

```
*****Author: K.Suresh, MSD, IGCAR, Kalpakkam, Tamil Nadu, India 603102*****/
```

```
#include<stdio.h>
#include<conio.h>
#include<math.h>
#include<bios.h>
#include<dos.h>
```

```
#define CLK1 0x04 /* Clock Pulse High*/
#define CLK0 0xfb /* Clock Pulse Low*/
#define CS1 0x01 /* Chip Select high to deactivate DAC*/
#define CS0 0xfe /* Chip Select low to activate DAC*/
#define DATA 0x02 /* Data Pulse High*/
#define DATA0 0xfd /* Data Pulse low*/
#define PLUSVREF 0x00 /*Vref =positive*/
#define MINUSVREF 0x08 /*Vref=negative*/
```

```
int c[16],dport,ACTUALDATA,out,k; /*Global Declarations*/
float Vref ;/*Desired Reference output*/
```

```
void d2b(unsigned int x, int*c)/*Routine for Decimal to Binary Conversion*/
```

```
{
int i;
for(i=0;i<=15;i++)
*(c++)=(x>>1) & 0x1;
}
```

```
float SETREF(void) /*Routine for getting the required reference output from the user*/
```

```
{
int Vin;
printf("\n Enter the desired reference output Vref( -4.0955 V to 4.0955V):");
scanf("%f",&Vin);
while((Vin<-4.0955)|| (Vin>4.0955))
{
printf("\n ERROR!!! Vref Out of Range(-4.0955 V to 4.0955V)!");
printf("\n Press any key to continue");
getch();
printf("\n Enter the desired reference output Vref( -4.0955 V to 4.0955V):");
scanf("%f",&Vin);
}
Vref=Vin;
printf("\n Your Desired Reference is %f\n",Vref);
return Vref;
}
```

```
void SETPOLARITY( float Vref ) /* Routine for setting the Vref Polarity*/
```

```
{
if (Vref<0.0)
{
out|=MINUSVREF;
outportb(dport,out); /* Set the Vref polarity as negative*/
}
else
{
out|=PLUSVREF;
outportb(dport,out); /* Set the Vref polarity as positive*/
}
}
```

```
void CLOCK_DAC(void)/*Routine for clocking the DAC*/
```

```
{
out|=CLK1;
outportb(dport,out);/*Setting the clock high*/
```

```
delay(1);
out&=CLK0;
outportb(dport,out);/*Setting the clock low*/
delay(1);
}
```

```
void LOAD_DACDATA(int*c)/*Routine for loading actual data into the DAC*/
```

```
{
out|=CS1;
outportb(dport,out);/*Chip Select high to disable DAC*/
delay(1);
out&=CS0;
outportb(dport,out);/*Chip Select low to enable DAC*/
delay(1);
printf("\nDATA loaded into the DAC=");
for(k=15;k>=0;k-)
{
out|=c[k];
outportb(dport,out);
printf("%d",c[k]<<1);
delay(1);
CLOCK_DAC();
}
out|=CS1;
outportb(dport,out);
delay(1);
}
```

```
main()
```

```
{
int v,inc;
float y;
unsigned int x;
double fraction, integer, number;
clrscr();
printf("\tPrinter Port as a Programmable Frequency Generator");
printf("\n\t\t\t by\n");
printf("\tK.Suresh,MSD,IGCAR,Kalpakkam,TamilNadu-603102,India");
dport= peek(0x40,8);/*Check up for availability of Printer Port*/
if (dport==0)
{
printf("\n\n LPT NOT AVAILABLE! EXITING.....");
exit(1);
}
printf("\n\nAddress of the printer port found =0x%X",dport);
SETREF();
out=0x00;
SETPOLARITY(Vref);
y=(Vref*8192)/(2.5*1.6384);
v=y/1;
number=y;
fraction = modf(number, &integer);
if (fraction<0.44)
inc=0;
else inc=1;
ACTUALDATA=16384+v+inc; /*Actual data including the Control Word for DAC*/
d2b(ACTUALDATA,c);
LOAD_DACDATA(c);
return 0;
}
```

internal amplifier, usually set to 1.634.

Normally the DAC output is unipolar (positive) only. As is normally done, you can also operate the DAC in bipolar mode with internal reference with an additional op amp as specified in the device data sheet. But here the range of the output is limited to $-2.499V$ to $+2.499V$ (for MAX5130) only. However, the present design enables you to overcome this and get an extended range of reference of $-4.0955V$ to $+4.0955V$ with a step resolution of $0.5mV$. As shown in the Fig. 1, you can achieve this extended bipolar output by using the programmable inverting amplifier (IC2) and the polarity control switch (IC3) combination. Depending on the control signal output at Pin 5 (D_3 of Data Port 0x378), the polarity control switch is either closed (D_3 =logic 1) or open (D_3 =logic 0). This makes the programmable inverting amplifier function either as a unity gain inverting amplifier or as a unity gain buffer. If a positive reference output is required, the switch is opened by sending $0V$ ($<0.8V$, logic 0) at D_3 making IC2 work as a unity gain buffer. Then the DAC positive output is buffered by IC2 before being available at the output as $+V_{REF}$. When a negative reference output is needed, the switch is closed by sending a $+5V$ (logic 1) at D_3 and the positive DAC output is amplified by IC2 with a gain of -1 . The desired $-V_{REF}$ is now available at the output. Thus by controlling the 16-bit data sent to the

DAC and the polarity control switch, the programmable reference generator can be made to output any user desired output.

The control software for this bipolar reference generator written in Turbo C is given in Listing 1. The software obtains the desired V_{ref} from the user, checks the set value lying within the range of $-4.0955V$ to $+4.0955V$. If it lies within the range, the program proceeds further. However, if the set value lies outside the allowed range, an error message warns the user about the over range and asks the user to input a correct V_{ref} . When the desired V_{ref} lies within the allowed range, the program first sets the polarity of the desired V_{ref} by sending appropriate logic signal at pin 5 of the printer port and then calculates ACTUALDATA to be sent to the DAC. The d2b routine converts the ACTUALDATA into 16-bit binary data. The program then enables the DAC ($/CS$ = low) and then serially clocks the binary equivalent of ACTUALDATA, starting from MSBit to LSBit, one by one, to the data pin of the DAC. With LSB set at the data pin, the low to high transition of the clock latches the ACTUALDATA completely into the DAC. Now the user set V_{ref} is available at the output!

K. Suresh
Kalpakkam
Tamil Nadu

Current-to-current converter

A current to current converter may often be needed if you have a fixed reference current source of current of the order of say, tens of microamperes and would like to have a current higher or lower than this for your application and to switch or change the direction of the input reference current.

Non inverting Current-to-current converter

You can build a programmable current source of any value higher than input current just by adding two resistors R_1 and R_2 to a unity gain buffer/voltage follower as shown in Fig 1. a & b.

The input current I_1 , from an external current source that is to be scaled up flows through R_1 (assuming that the bias current of the op amp is negligible) and creates a voltage drop I_1R_1 across R_1 . Since the voltage follower has a severe negative feedback, the error voltage across its

inverting and non-inverting input terminals should ideally be zero. Therefore the potential at the output of the op amp has to be same as the potential at the non-inverting input. Since one end of R_1 and R_2 are tied together, the potential across R_2 has to be same as the potential across R_1 .


$$\text{Potential across } R_2 = I_2R_2 = I_1R_1$$

The output current is sum of the input current flowing through R_1 and the current supplied by the op amp flowing through R_2

$$I_0 = I_1 + I_2 \\ = I_1 + (I_1R_1) / R_2 = I_1 (1 + R_1 / R_2)$$

$$I_0 = I_1 (1 + R_1 / R_2)$$

The current gain is always greater than unity, which means that the output current to the load R_L is always

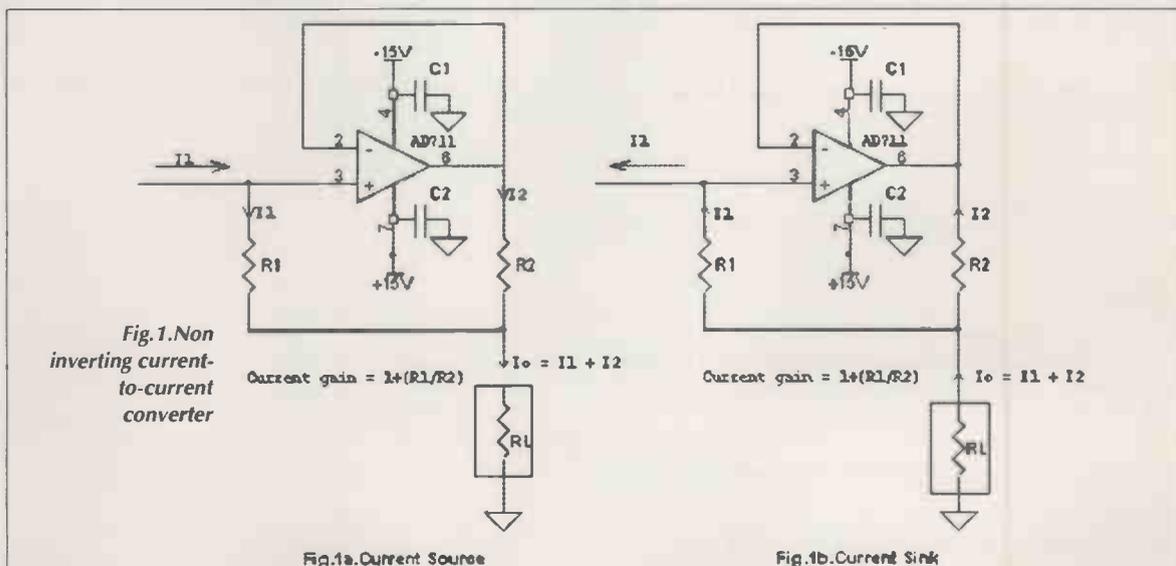

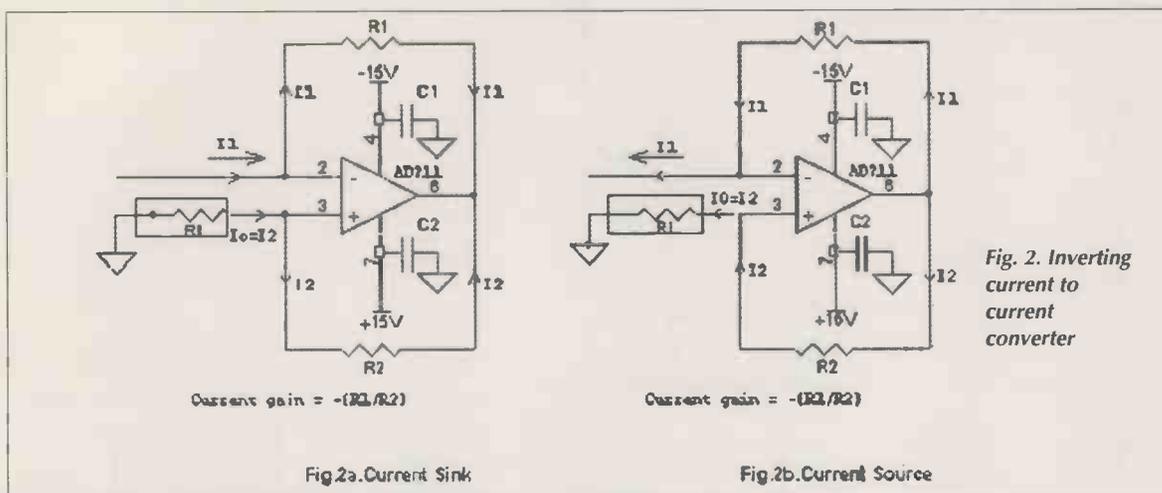


Fig. 2. Inverting current to current converter

greater than the input current. The direction of the current that is delivered to the load is same as the direction of the input current.

The bias current of the op amp determines the minimum value of input reference current that can be handled. An FET op amp with very low input bias current and offset voltage would be a suitable choice for this application. C1 & C2 are the recommended decoupling capacitors for the op amp.

Inverting current-to-current converter

Fig. 2. is another current-to-current converter where output current to the load RL can be greater or lesser or equal to the input current with the direction of the output current changed.

The input current from a current source (assuming that the bias current of op amp is negligible) flows through R1 and creates a voltage drop $I_1 R_1$ across the feedback resistor R1. The negative feedback forces the potential across inverting and non-inverting input to be zero. Therefore the potential across R2 has to be the same as the potential across R1.

$$I_1 R_1 = I_2 R_2$$

If the bias current of the op-amp is negligible, the current through the resistor R2 and the current through the load RL is same.

$$I_0 = I_2$$

$$I_0 = I_1 (R_1/R_2)$$

An input current I_1 that is sourced out from a current source causes a current I_0 to sink into the load RL and vice versa as shown in the Fig.2. a & 2b. Therefore I_0 may be written as

$$I_0 = -I_1 (R_1/R_2)$$

The bias current of the op-amp determines the minimum value of input reference current that can be handled. An FET op amp with very low input bias current and offset voltage would be a suitable choice for this application. C1 & C2 are the recommended decoupling capacitors for the op amp.

V. Manoharan
Kochi
Kerala
India

Using Multiple-purpose Timer Chip to Build Inverting SMPS

Both positive and negative supply voltages are usually required for driving most op-amp. circuits, RS-232 line drivers, A/D and D/A conversion circuits, etc. As the power requirement of these circuits is generally small, an inverting regulator that generates negative supply from the positive one is a preferable alternative rather than employing a full line dual power supply. Despite the fact that this task can be easily accomplished by using a single-chip charge-pump, building an inverting switched mode regulator using an off-the-shelf multiple-purpose chip is interesting as it incorporates the educational aspects of understanding the principles of switched mode power supply.

The circuit being described in this article uses the popular 555 timer chip as a controller for inverting switched mode power supply to generate -5V from +5V supply. The timer is configured as an astable multivibrator with timing controlled by R_1, R_2, C_1, V_{CC} , and upper threshold voltage V_{TU} . The output high time of the timer is determined by the time required to charge C_1 from $-V_{TU}$

to V_{TU} through V_{CC}, R_1 , and R_2 that can be expressed by:


$$t_{hi} = \ln \left[\frac{V_{CC} - \frac{1}{2} V_{TU}}{V_{CC} - V_{TU}} \right] (R_1 + R_2) C_1$$

The V_{TU} itself depends on $V_{CC}, 3 \times 5 k\Omega$ internal resistors of the timer chip, feedback circuit R4, and VA through following equation.

$$V_{TU} = V_{CC} - 5K\Omega \frac{V_{CC} (R_4 + 10K\Omega) + 10K\Omega V_A}{15K\Omega R_4 + 5K\Omega 10K\Omega}$$

The output low time of the timer is determined by the time required to discharge C_1 from V_{TU} to $-V_{TU}$ through R_2 and the internal discharge transistor of the chip which can be expressed by:

$$t_{lo} = \ln(2) R_2 C_1$$

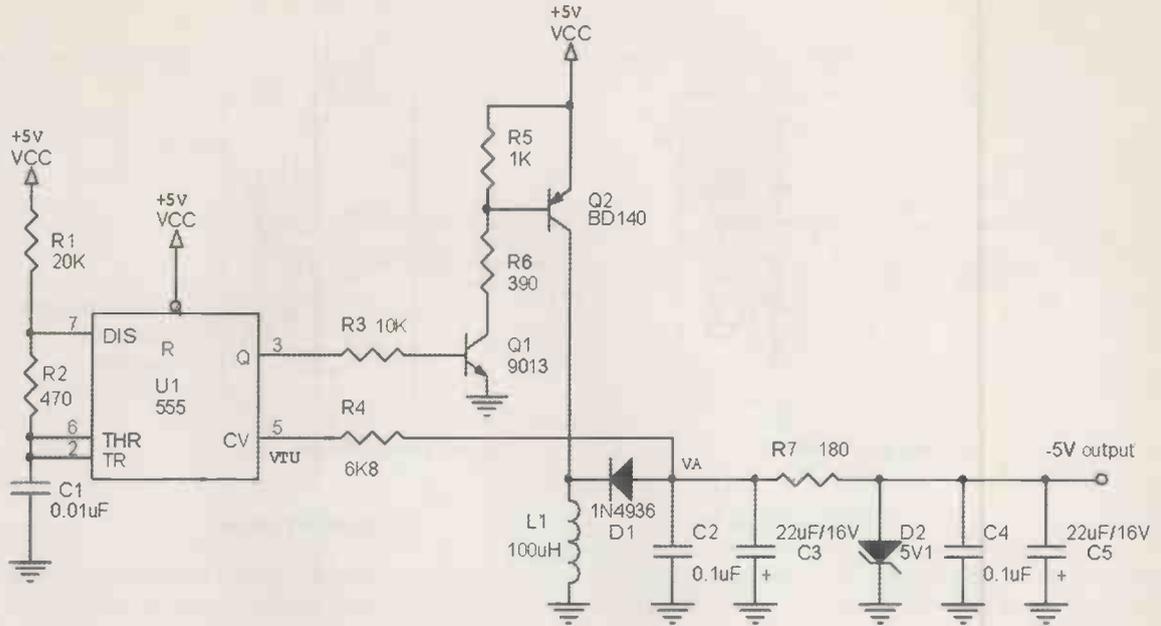

The buck-boost switched mode regulator circuits consist of Q_2 , L_1 , D_1 , C_2 , and C_3 . When the output of the timer chip is high during t_{hi} , Q_1 and Q_2 will be turned on and energize inductor L_1 . When the output of the timer chip is low during t_{lo} , Q_1 and Q_2 will be turned off and L_1 releases its energy to C_2 and C_3 through D_1 and thus generates negative voltage V_A . The value of V_A depends on V_{CC} , and also the on and off time of Q_1 through following relation.

$$V_A = -V_{CC} \frac{t_{hi}}{t_{lo}}$$

As t_{hi} itself depends on V_A , the timer chip serves as an active low pulse position modulator that regulates the output voltage. If V_A decreases (becomes less negative), VTU will increase and yield larger t_{hi} that implies higher energy to energize the inductor. This increase in t_{hi} will then restore the intended value of V_A back. The opposite story will take place when V_A increases. Additional ripple filtering and voltage regulation are then carried out by R_7 , D_2 , C_4 , and C_5 .

Henri P. Uranus
Enschede Netherlands

Electronics World reader offer:

Save £20 on a DataStation™ development kit and get free delivery!*

Get a DataStation plus development board and cable for just £99 +VAT (Normally priced at £119.50 + delivery).

DataStation™ is a 16 channel, software configurable I/O module offering more than 500 samples per second and 391 different I/O configurations from a single product. This unrivalled flexibility makes DataStation suitable for virtually any PC driven monitoring or control application. Please send your completed coupon and payment to:

EW Reader Offer

Observant Electronics Ltd.
Unit F2b, Avonside Enterprise Park,
Melksham, Wiltshire SN12 8BS

Alternatively call 01225 704631
or fax your order to 01225 708618.

*Note: free delivery is only available within the UK. For delivery outside of the UK please add £2.50.

Offer valid until 28th November 2003



Specifications:

Max Analogue Inputs:	6
ADC resolution:	8 or 12-bit selectable
Sample Rate:	> 500 samples per second
Max PWM outputs:	2
Max PWM resolution:	10 bits
Max Digital inputs:	16
Max Digital outputs:	16
Interface:	RS-232
Supply Voltage:	7 to 35v dc
Supply Current:	15mA typical
Dimensions:	99 x 82 mm



Electronics World reader offer:
x1, x10 switchable
oscilloscope probes,
only £21.74 a pair,
fully inclusive*

*Additional pairs as part of the same order, only £19.24 each pair.

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to
Probe Offer, Jackie Lowe, Highbury Business Communications, Nexus House, Azalea Drive, BR8 8HU

Readers outside Europe, please add £2.50 to your order.

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment *(please circle)*

Cheques should be made payable to Electronics World

Access/Mastercard/Visa/Cheque/PO

Credit card no _____

Card expiry date _____ Signed _____

Please allow up to 28 days for delivery

Specifications

Switch position 1

Bandwidth	DC to 10MHz
Input resistance	1M Ω – i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC

Switch position 2

Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10M Ω \pm 1% if oscilloscope i/p is 1M Ω
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC

Switch position 'Ref'

Probe tip grounded via 9M Ω , scope i/p grounded

Capacitor & Amplifier Distortions

Cyril Bateman uses his real-time distortion measuring system to investigate capacitor distortions in audio power amplifiers

Assembled using polar aluminium electrolytic capacitors for C1, 3, 9 and 11, my workhorse 100 watt Maplin Mosfet amplifier, tested at 1kHz and 25 watts into an 8Ω load, measured -81.5dB second harmonic, -91.4dB third harmonic, clearly meeting its claimed less than 0.01% distortion¹.

Fig. 1.

Replacing the four polar aluminium electrolytic capacitors in this schematic, with the same value and voltage rating bi-polar electrolytics and no other changes, amplifier distortion improved dramatically, becoming -92.1dB second and -94.3dB third harmonic, re-measured a few minutes later. This article is

based on more than eighty distortion measurements, taken while investigating the possible reasons for these improvements.

In the past, many amplifier designers have stated that provided the capacitance value is chosen to ensure only a small AC signal voltage drop can appear across capacitors at the lowest frequencies, then capacitor distortion can be ignored.

My original *Capacitor Sounds* series² found measurable distortions occurring in un-biased polar aluminium electrolytic capacitors tested at 0.1 volt AC, my smallest practical test voltage. With signals this small, second harmonic of the lowest distortion 100μF 25 volt DC


rated polar capacitor I tested, measured -99.5dB with 6 volt bias and -94.4dB with 12 volt bias. Using 0.2 volt AC and larger test voltages, second and third harmonic distortions in polar aluminium electrolytic capacitors increase dramatically, measured with and without DC bias voltage.

Tested using a 1 volt signal, this capacitor's third harmonic remained close to -100dB, with no bias its second harmonic was -93.2dB, increasing to -77.9dB at 6 volt bias and -72.9dB with 12 volt bias. Application of a very small, optimal bias, typically less than 3 volts DC, to selected capacitors may minimise the second harmonic, however for every electrolytic capacitor I tested, further increase of bias voltage resulted in increased second harmonic distortion.

Contrary to the popular belief that a polar aluminium electrolytic capacitor should be biased to 50% rated voltage for minimal distortion, my measurements show that second harmonic distortion can only be minimised by using very small or no DC bias. Any further increase in DC bias increases the second harmonic generated by the capacitor. Application of DC bias at 50% of the capacitor's rated voltage as shown in the figure, results in exceptionally large second harmonic distortions, even for this, the lowest distortion, the best polar capacitor, of those measured. Fig. 2.

At very low frequencies, as capacitor impedance increases, signal

Fig. 1. Schematic circuit of my Maplin Mosfet 100W amplifier, redrawn for convenience using my Microcap MC6 circuit simulator.

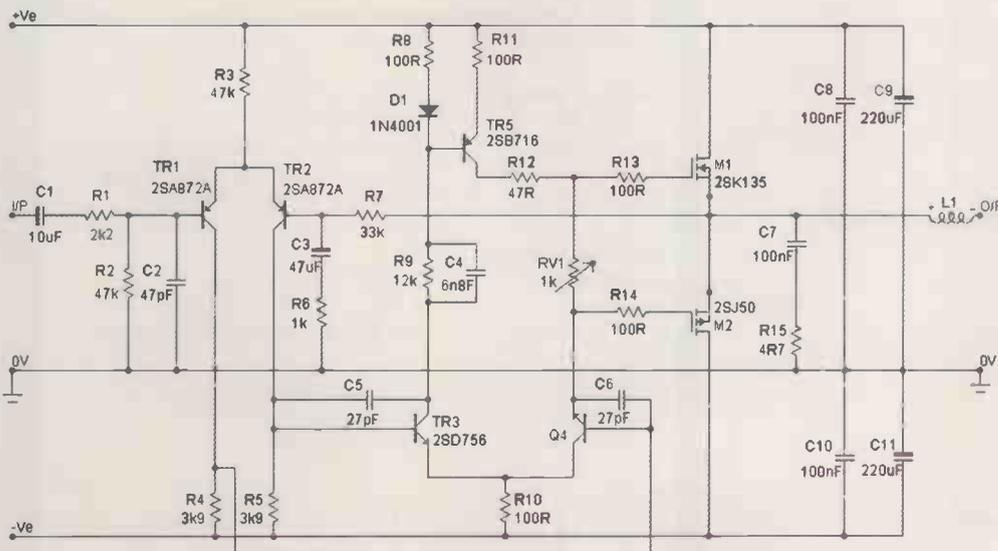

voltages could occur in the circuit sufficient to generate measurably increased distortion. However at my 1kHz distortion measurement frequency, all four capacitors have low impedance, so are subject only to small AC signal voltage drops, apparently not sufficient to explain my measured reduction in distortion when replaced by the same value and voltage bi-polar types.

At a given test frequency, capacitor distortions do vary with capacitor AC signal levels and DC bias voltage, but for my Maplin amplifier comparison tests, nominal capacitance values were unchanged so both sets of polar and bi-polar capacitors experienced the same signal voltages. Why should simply changing these capacitors from polar to bi-polar types, provide such benefit?

Capacitor C3 conditions

I ran a few simulations to identify the capacitor most likely to influence this amplifier's distortion. As in many power amplifiers, a 47 μ F polar aluminium electrolytic capacitor, C3, is used in the feedback network, to roll off amplifier gain at low frequencies, minimising DC offset at its output. With 33k Ω for R7 and 1k Ω for R6, this capacitor is presented with a high impedance for charge and discharge currents. My original *Capacitor Sounds* measurements used lower impedances. Might this high impedance condition affect the capacitor's distortion contributions?

It seemed possible that distortions generated in the capacitor result from two mechanisms, a current dependant component in addition to the voltage component already identified. Throughout that series, I related distortions measured in capacitors to their signal and bias voltages, using test circuit source impedance some two thirds that of the capacitor's at 1kHz for values to 1 μ F, 100Hz for 1 μ F and larger values.

I expected to find some third harmonic current dependency from non-ohmic resistances in the capacitor internal connections. Second harmonic distortions in capacitors result from dielectric absorption effects, DC bias and test voltage level, so I wondered whether a change of measuring current with constant bias and test voltage, would reveal changes also in the second harmonic?

In my original *Capacitor Sounds* series I described test equipment designed and built to measure capacitor distortion at 100Hz and 1kHz. For another project last year I

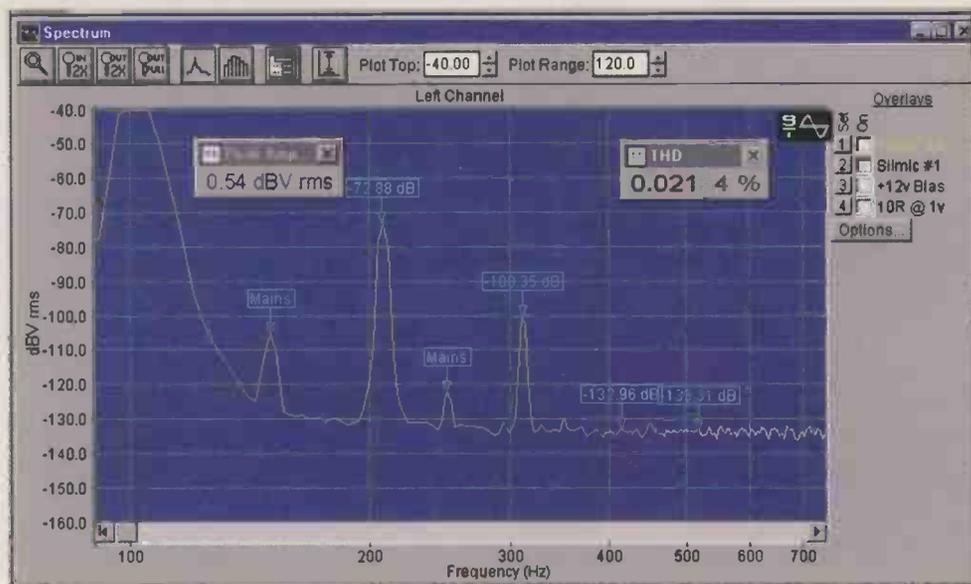


Fig. 2. Distortion results for a Silmic 100 μ F 25 volt rated polar aluminium electrolytic capacitor, with 12 volt DC bias and tested using 10 Ω source impedance generating 1 volt across the capacitor. With no bias, second harmonic distortion for this capacitor was -93.2dB and -77.9dB with 6 volt bias.

assembled a 5kHz test oscillator, buffer amplifier, notch filter/preamplifier, using 1kHz PCBs with smaller tuning and filter capacitors.

Following a few tests, I found this equipment could develop an undistorted 0.5 volt 5kHz signal across my 1 μ F FKP reference capacitor using 100 Ω source impedance. I could measure distortions produced by a 1 μ F polar aluminium electrolytic capacitor at three test frequencies, 100Hz, 1kHz and 5kHz, using 100 Ω source impedance, increasing capacitor test current from 314 μ A at 100Hz to 15.7mA at 5kHz at constant test voltage. Perhaps that would clarify any capacitor current dependant component.

Using 100 Ω source impedance and no bias, I adjusted test levels to develop a 0.5 volt AC voltage across the capacitor at each frequency. Second harmonic distortion increased by 8dB and third harmonic 4.3dB with this change of capacitor current. Clearly both second and third harmonic distortions do increase with capacitor current and AC voltage drop.

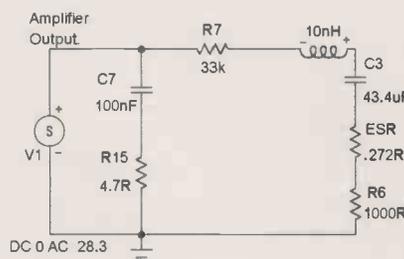


Fig. 3. To simplify my simulations, I extracted the C3 and C7 capacitor sub circuits from the Figure 1 schematic and used the amplifier output voltage as my calculation stimulus. Much simpler, quicker and less prone to simulation errors than when modelling the amplifier.

Second harmonic distortion increases rapidly with DC bias voltage.

Circuit conditions

A few simulation runs using measured capacitance and ESR values by frequency, would establish the voltage and current for capacitor C3, from 10Hz to 20kHz and beyond. Analogue behavioural modelling techniques could be used, but determining the capacitor model can be time consuming and many readers may not have a suitable simulator. Far simpler and quicker - make several frequency runs using measured values for a specific frequency in turn, noting the result for that frequency. This method is practical using the simplest simulator.

Table 1: With 0.5 volt AC test voltage, 100 Ω source impedance and no bias, I found second and third harmonic distortion increasing with capacitor current. Clearly both second and third harmonic distortions do increase with capacitor current, voltage drop and second harmonic with DC bias.

Frequency	Impedance	Test Current	Second Harmonic	Third Harmonic	% T.H.D.
100Hz	100 Ω	314 μ A	-107.8dB	-115.7dB	0.00047%
1kHz	100 Ω	3.14mA	-102.4dB	-111.6dB	0.00083%
5kHz	100 Ω	15.7mA	-99.8dB	-111.4dB	0.00117%

Table 2: Measured values of a 47µF 50 volt Panasonic 'S' bi-polar aluminium electrolytic capacitor as used for C3, with results from my eight simulation runs

Measured Values.				Simulation Results.	
Frequency	Capacitance	Actual ESR	Impedance.	Voltage drop	C3 Current
10Hz	49.08µF	25.74Ω	325.29Ω	270.82mV	832.0µA
20Hz	48.54µF	12.97Ω	164.52Ω	138.02mV	832.03µA
100Hz	45.41µF	1.862Ω	35.09Ω	29.28mV	832.31µA
300Hz	44.24µF	0.575Ω	12.01Ω	10.07mV	832.33µA
1kHz	43.40µF	0.272Ω	3.67Ω	3.05mV	832.35µA
3kHz	42.74µF	0.210Ω	1.26Ω	1.05mV	832.35µA
10kHz	41.71µF	0.191Ω	0.426Ω	0.35mV	832.35µA
30kHz	40.00µF	0.182Ω	0.225Ω	0.18mV	832.35µA


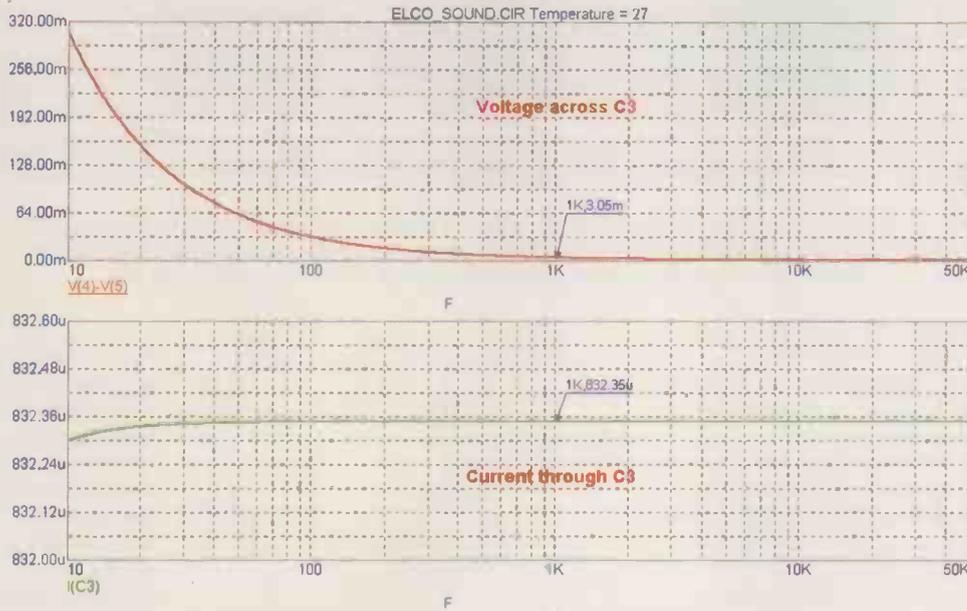


Fig. 4. One of eight simulations needed to accommodate C3 measured parameters by frequency, showing the 1kHz results. Voltage across C3 reduces with frequency but current through C3 remains almost constant regardless of frequency.

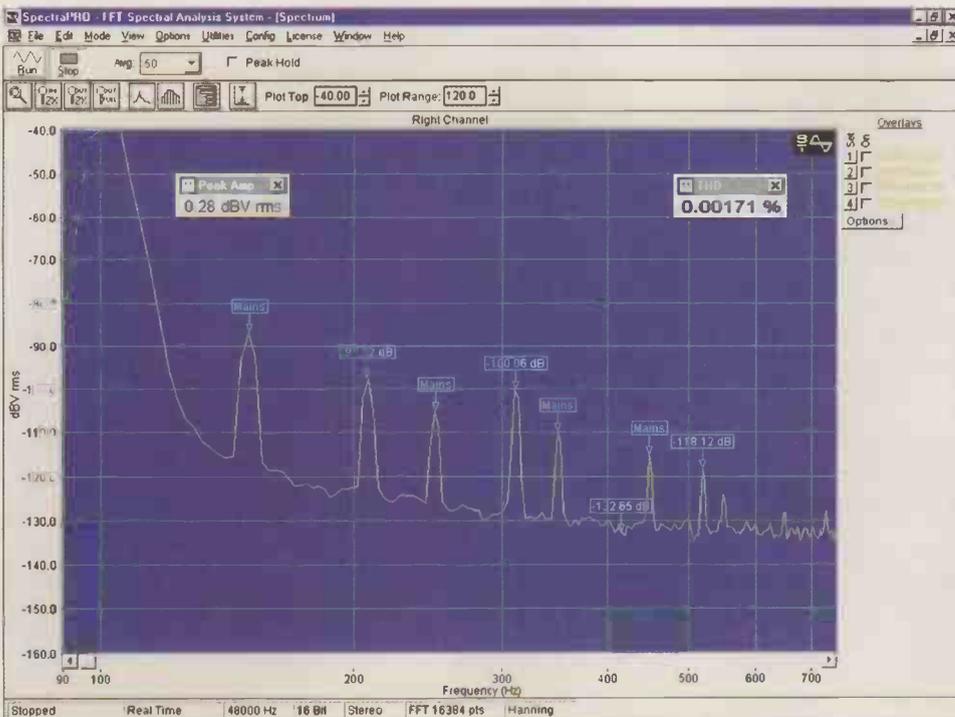

I extracted the feedback resistor network with this capacitor from the main circuit and used the amplifier's output voltage for 100 watt into 8Ω as the stimulus. I measured a radial lead, 47µF 50 volt Panasonic 'S' bi-polar electrolytic, the type used when exchanging the capacitors, for capacitance and ESR by frequency. Self resonance was 300kHz, so estimating 10nH for its self inductance, typical of many radial lead aluminium electrolytics in a 20 × 10mm case, completed the model. Fig. 3.

Using my Hewlett Packard reference test jig and Wayne Kerr B6425 precision digital LCR meter, I measured this capacitor from 10Hz to 30kHz, for capacitance value and ESR. These pairs of values were inserted into the model in turn for each of eight simulation runs, noting the voltage drop across the capacitor model, from the negative side of the 10nH to the junction of ESR and R6, also C3 through current.

For each run, similar voltage and current plots were observed with subtle changes at the frequency of interest, for the capacitor parameters used. Clearly capacitor signal voltage does reduce with increasing frequency but capacitor current remains almost constant, generating a near constant level of current dependant distortion. Fig. 4

Protection Diodes

Most published amplifiers using a polar aluminium electrolytic capacitor for this C3 position add a diode or pair of diodes in parallel, to

Fig. 5. A Rubycon YXF 47µF 25 volt rated polar aluminium electrolytic capacitor tested at 100Hz and 200mV with diodes. Without diodes, third harmonic was -122.67dB, a more than 20dB improvement. At this test voltage, low level AC mains harmonics cannot be eliminated, for clarity test frequency was 103.8 Hz and mains peaks labelled.

protect the capacitor should the amplifier 'go DC' with its output voltage 'stuck' to a supply rail. It has often been claimed such diodes do not distort at the capacitor's signal voltage levels, but I wondered if that were correct. Using a pair of 1N4448 diodes and my 1 μ F FKP reference capacitor, I made measurements at 1kHz with 100 Ω source impedance and test voltages of 75mV, 100mV, 150mV and 200mV, comparing distortion results with and without diodes.

Measured with diodes, third harmonic distortion was visible at -110dB for the 75mV test, increasing to -100dB for 100mV and -84.9dB tested at 200mV, when a fifth harmonic at -100dB was seen. These harmonics result from the diodes conducting slightly at these test voltages since without diodes, my FKP reference capacitor was distortion free.

I measured distortions at 100Hz, with and without diodes, for a variety of 47 μ F and 100 μ F polar aluminium electrolytic capacitors, rated at 25 volt and 50 volt, comparing these results with those for the same value bi-polar electrolytics. The results were overwhelmingly conclusive. At 200mV with diodes, third harmonic distortion increased by 20dB with polar and bi-polar capacitors. At 100mV I found smaller increases of third harmonic, depending on the level of distortion generated by the capacitor without diodes. Tested at 0.1 volt with diodes, this capacitor generated -96.8dB second and -108.2dB third harmonic distortion. Fig. 5.

I question whether these protection diodes are necessary for polar aluminium electrolytic capacitors in this circuit. They certainly are not needed using a bi-polar aluminium electrolytic capacitor of rated voltage similar to the amplifier's power supply voltage. That capacitor will happily survive indefinitely, regardless of whether the amplifier has 'gone DC' or is working correctly. More important it will generate almost no measurable distortion. Fig. 6.

All polar aluminium electrolytic capacitors inherently include a reverse polarity diode³ so should an amplifier 'go DC', reverse polarising the capacitor by more than 1 volt, capacitor reverse leakage current increases causing a voltage drop across R7. With \pm 50 volt power supplies and 10k Ω for R7, current cannot exceed 4.8mA. This reverse current may degrade the capacitor which should be replaced during

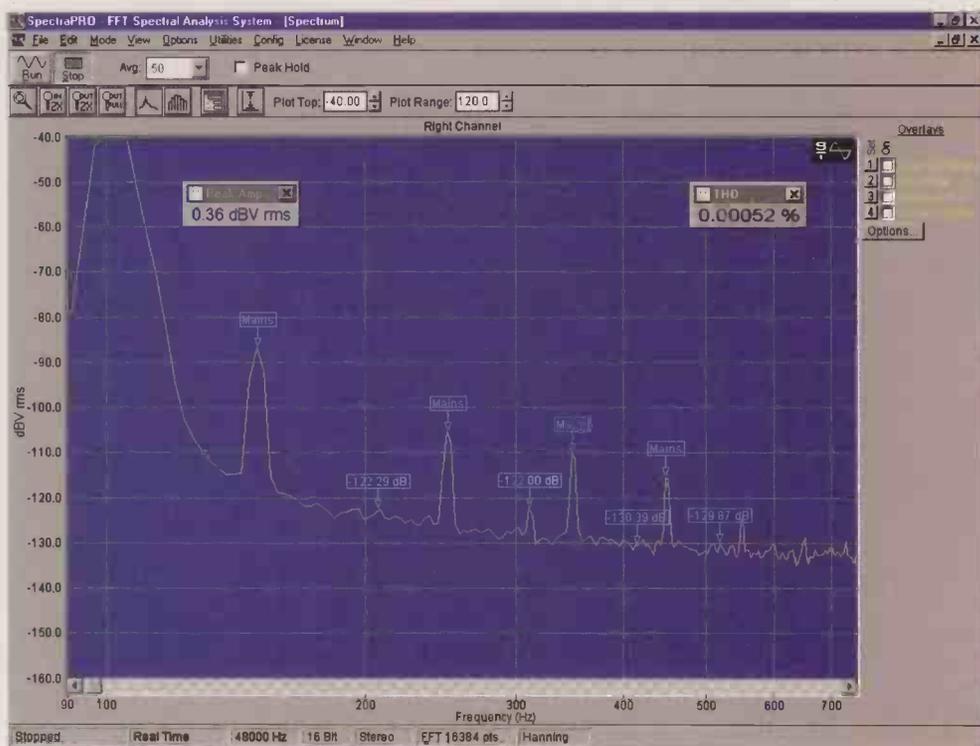


Fig. 6. Without diodes, but otherwise exactly as Figure 5, this Panasonic 'S' 47 μ F 50 volt bi-polar aluminium electrolytic capacitor shows the distortion reduction available by changing a polar capacitor for a bi-polar type. With diodes, third harmonic increased more than 20dB to -99.24dB, further proof of the diode effect.

repair, but is most unlikely to result in capacitor failure.

Zobel circuit

Many designers have expressed concern to me about the output stage CR Zobel network, that the signal voltage across resistor R15 with this resistor's voltage coefficient might generate audible distortion. With C7

and R15 already modelled, we can quickly explore this Zobel network.

With typical component values of 0.1 μ F and 4.7 to 10 Ω , the 0.1 μ F capacitor sustains almost all the amplifier output voltage at least to 10kHz and is more highly stressed than the resistor. At higher frequencies, resistor voltage increases but capacitor voltage reduces little.

Technical support

Full details of the 'Real Time' hardware test method and my original *Capacitor Sounds* low distortion oscillator, buffer amplifier, notch filter/preamplifier and DC bias assemblies, complete with parts lists, assembly manuals and full size printed circuit board drawings, as .PDF files arranged for easy viewing of the figures, on screen or hardcopy, are provided in my CD.

This CD includes updated and much expanded re-writes with very many more figures, of my first series *Capacitor Sounds* articles, supported now by some ninety capacitor distortion measurement plots as well as articles from this new *Capacitor SoundsII* series.

Also included are PDF re-writes of my earlier *Understand Capacitors* series together with articles on how to diagnose failed printed board mounted capacitors and essential low cost capacitor measurement methods, more than twenty popular articles.

This CD costs £15 Sterling inclusive of post & packing.

I can also supply sets of three professionally manufactured printed circuit boards, FR4 with legend and solder resist also four gang potentiometers, as described in my original *Capacitor Sounds* articles.

One set of boards costs £27.50 but due to weight, post and packing is extra.

Four gang potentiometer if ordered together with PCBs costs £5.00.

Post packing UK and EU £3.50

Rest of World £7.50

Send cheques or postal/money orders in Pounds Sterling only to:-

C. Bateman.

'Nimrod' New Road. ACLE. Norfolk. NR13 3BD.

England.

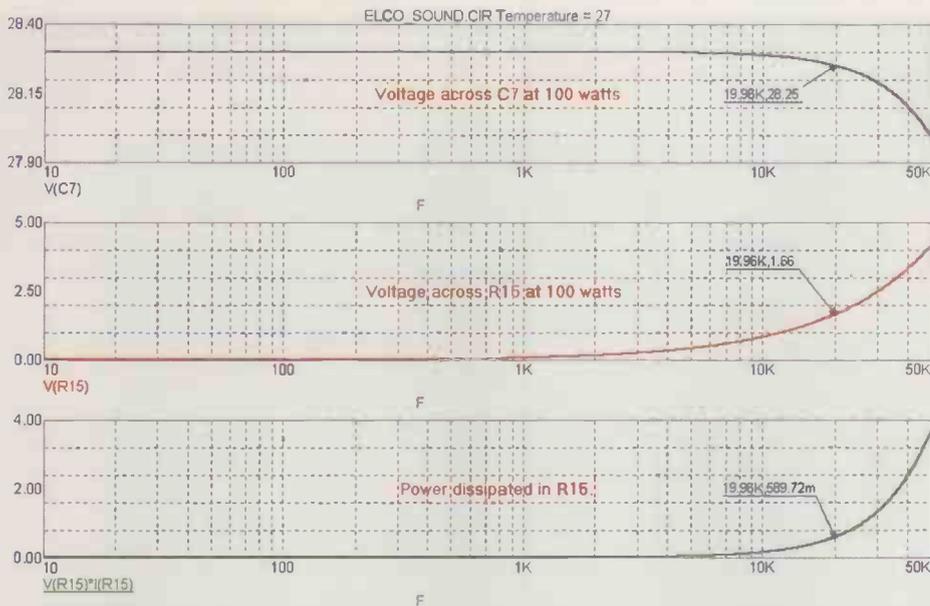


Fig. 7. Using the Figure 3 simulation circuit to analyse for C7, we see the capacitor is highly stressed not resistor R15 and badly chosen C7 can generate large distortion. When an amplifier is used for high frequency sinewave tests with or without load, this capacitor frequently fails open, disabling the Zobel, the amplifier may oscillate. Yet R15 is frequently specified as 3 watt rating and C7 ignored.

Fig. 8. Actual measured distortion of the 'stacked' metallised PET capacitor in the Self Blameless 50 watt class B design, at 8 watts power in an 8Ω load. Distortion will increase rapidly with increasing power output.

With 100 watts output into 8Ω at 20kHz, the capacitor must still withstand more than 28 volts while the resistor is subject to less than 2 volts or 0.6 watts. At such voltage a metallised PET capacitor can generate significant distortion. Fig. 7. My test equipment cannot generate that voltage so I measured C7 distortions using an eight volt signal and 100Ω source impedance, equivalent to 8 watts power output, representative perhaps of normal

listening. I measured a 0.1μF 'stacked' metallised PET capacitor, the unused spare for my 'Self' amplifier. At 8 watts output this capacitor generated -113.5dB third and -126.3dB fifth harmonic, distortions which would be reflected into the feedback network. Fig. 8.

Apart from this distortion, at 20kHz and 100 watts, this capacitor is subjected to more than twice the permitted sine wave rating for an Evox-Rifa MMK 0.1μF 63 volt

metallised PET capacitor while almost any resistor easily manages the less than 2 volt and 0.6w R15 dissipates. To minimise distortion in normal use and survive no-load sine wave testing, the capacitor choice for this network is important. I prefer a foil and Polypropylene or Polyphenylene Sulphide capacitor.

Input capacitor C1

Many designs use an unbiased 10-22μF polar aluminium electrolytic capacitor, C1, to input the signal and block unwanted DC from entering the power amplifier, assuming that if sized to ensure minimal signal voltage across the capacitor at low frequency, low distortion is guaranteed. That may well be correct provided the capacitor is not subjected to DC bias. More than a few volts bias will result in second harmonic distortion which will be amplified.


I believe a polar aluminium electrolytic capacitor is false economy since quite small metallised PPS or PET capacitors are available. Polypropylene capacitors produce much lower distortion but are larger and expensive. An inexpensive bipolar electrolytic is small and produces little distortion unless subject to significant DC bias voltage. For the best performance use a film capacitor.

Class B bias stability networks

Many power amplifiers include another significant capacitor we should explore. Typically a 10-47μF is used to bypass the signal across the bias current stabilisation network. For values up to 22μF the lowest distortion most economic choice is a metallised PET style, closely followed by the 'double bi-polar' electrolytic capacitor⁴. For larger values, unless cost and size is no object, chose this electrolytic.

Many readers are familiar with the Douglas Self 'Blameless 50 watt class B' design, published in *Electronics World* February 1994. I have a pair, assembled on printed boards purchased from the magazine, which measured some 2.6 volts of DC bias voltage across their 47μF polar aluminium electrolytic capacitor C4, the bias current stabilisation network bypass capacitor.

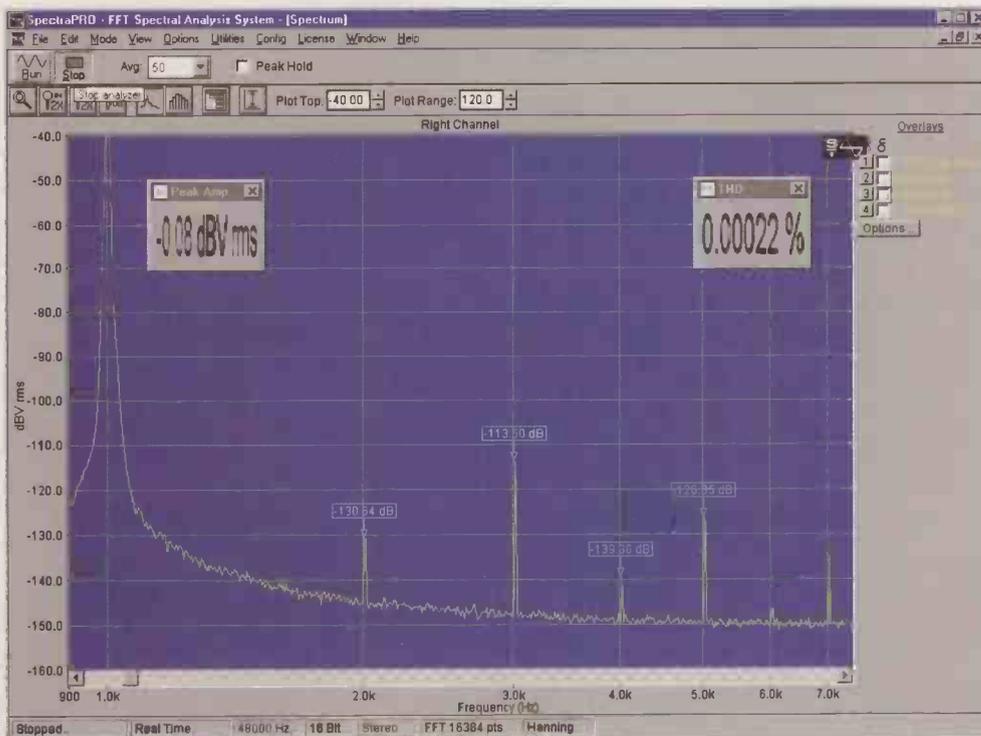Measurements of the AC voltage across C4, with the amplifier driven to 50 watts into 8Ω shows its AC voltage increasing significantly with frequency. At low frequencies, while the amplifier still has substantial open loop gain, this voltage remains small. As the amplifier open loop



gain reduces with increasing frequency, C4 is subjected to a significant signal voltage. At 10kHz I measured 1.15 volt AC using an AC coupled DVM to ignore the DC voltage. Any polar aluminium electrolytic capacitor subject to such AC voltage will generate very large second and third harmonic distortions.

The very best and quite expensive, specialist polar aluminium electrolytic capacitor of those I tested at 1 volt, generated some -93.2dB second and -100dB third harmonic with no bias. With 6 volt DC bias distortions increased dramatically, the second harmonic now -77.9dB. With 12 volt bias second harmonic increased tenfold to -72.9dB. Other polar aluminium electrolytics generated even more distortion when tested using a 1 volt signal.

The only cost effective, low distortion solution for this 1 volt signal level and DC bias voltage, is to use two double capacitance, 63 volt rated bi-polar aluminium electrolytic capacitors connected in series, the 'double bi-polar' configuration recommended in the last article of my first *Capacitor Sounds* series, *Electronics World* January 2003. Measured using 1 volt and no DC bias, this 'double bi-polar' capacitor combination measured -117dB second and -123dB third harmonic. With 6 volt bias, second harmonic became -102dB and -97.2dB biased to 12 volt DC as shown in this plot. An almost twenty times smaller distortion than measured using the best polar capacitor I tested, with or without bias. **Fig. 9**

Contrary to common belief, using an electrolytic well below its rated voltage does no harm, in fact it is beneficial, reducing leakage current, like choosing a more expensive, professionally rated, long life capacitor. Production electrolytic capacitors rated at 25-63 volt, provide better performance than lower and higher voltage types. In past years 'underrunning' was frowned on because some badly designed electrolytes degraded the aluminium oxide dielectric. Subsequent application of rated voltage resulted in leakage current exceeding the maker's claim. Installed in circuit and under-run for some time, a capacitor would not usually become subjected to rated voltage. Under-running never was a problem, rather a misunderstanding of capacitor and circuit behaviour.

Valve amplifiers

To date I have avoided discussing

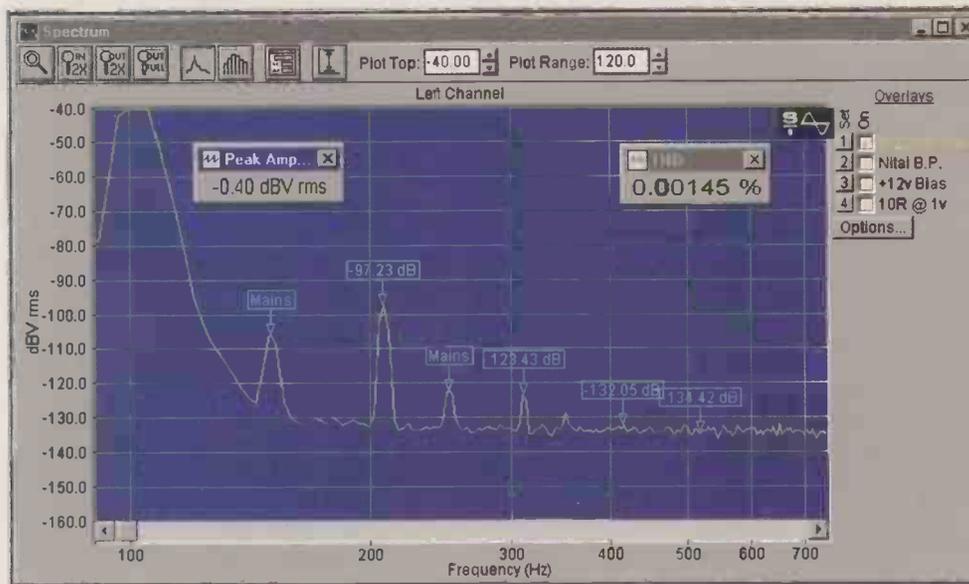


Fig. 9. Two 220 μ F 63 volt Nitai bi-polar capacitors in series made this 100 μ F "Double bi-polar" capacitor. Measured using a 1 volt AC and 12 volt DC bias as Figure 2, it generates almost twenty times less distortion. Second harmonic measured -101.75dB with 6 volt bias, -117dB unbiased.

valve amplifiers because I do not possess one and so cannot make any confirming measurements. However, I believe the DC blocking AC signal coupling capacitor used between a valve anode and subsequent grid, subjected to large DC bias and AC signals, can create distortion.

I decided to measure a specialist metallised Polypropylene 1 μ F 630 volt MKP capacitor⁵ and the 1 μ F paper capacitor reported in my August article, using a 6 volt test signal, the largest very low distortion signal I can generate across a 1 μ F capacitor using 100 Ω source impedance, with DC bias from 0 to 100 volt, then compare the results.

The MKP capacitor performed as well as expected, second harmonic increasing from -132dB with no bias to -123dB with 100 volt DC bias, a superb result. In contrast the paper capacitor behaved rather less well, illustrating perhaps why second harmonic distortion often dominates a valve amplifier output.

With no DC bias, second harmonic of this paper capacitor measured -128.8dB but biased to 30 volts DC its -116.5dB second harmonic was worse than the MKP at 100 volts. Biased to 100 volts this paper capacitor performed badly, generating an enormous -108dB second harmonic. Third harmonic for both capacitors changed little with bias, staying close to -130dB. Second harmonic distortion for this and similar paper capacitors increases with DC bias or AC signal voltage. **Fig. 10.**

Power Rail Capacitors

The four polar electrolytic capacitors I exchanged for the bi-polar types included two 220 μ F power rail capacitors which are irretrievably linked with the power supply so cannot easily be evaluated in isolation. I plan to explore these as part of a future article.

In my next article, the last for this series, I measure distortions in low-level IC op-amp circuits and include a novel circuit technique that allows a modest op-amp to produce lower than usual distortion driving a low impedance load. In response to reader's requests, I also include a brief look at possible resistor and potentiometer distortions.

Conclusion

Having examined a variety of capacitor styles and their audio frequency distortions over the past two years, it is perhaps appropriate with the benefit of hindsight to summarise some findings.

For low level and pre-amplifier circuits but ignoring supply rail decoupling, most capacitors used will be small value and many will need

Table 3: AC and DC voltages measured on C4, with the amplifier set to generate 50 watts into 8R. This amplifier was assembled using printed circuit boards purchased from *Electronics World*.

Frequency	100Hz	1kHz	10kHz
DC bias volts	2.6v	2.6v	2.6v
AC signal voltage	0.095v	0.158v	1.15v

FFT Software

Throughout my *Capacitor Sounds* series except the first two articles, I used the SpectraPlus232 software for my distortion plots. This software is easy to set up and has served well. However some readers have asked whether lower cost software might be used, since a full set of options can become expensive.

I have now found two alternatives. Provided the reader can accept not having the on screen THD% display, all other facilities I used are provided by purchasing only the Spectra base module, almost halving the cost. The on screen THD% option can be purchased later.

My second alternative is 'WinAudioMLS Pro', I evaluated version 1.66, a new version having its microphone correction ability updated for use with my test equipment, or a conventional microphone. It can be obtained from the Dr. Jordan web site.

As standard this software provides a THD+N display and cursor controlled readout of harmonic levels. It accepts the microphone correction file, essential when using my notch filter/preamplifier assembly. In addition to all the features needed for my measurements it also provides an MLS measuring facility. This can be used to measure loudspeaker and room responses as well as the impedance and phase of low impedance components, especially those used in loudspeakers. All this for less cost than for the basic SpectraPlus232 module, makes this software well worth your evaluation.

This software also has a range of additional upgrade options, but I found the base WinAudioMLS Pro version with their THD% option, sufficient for my needs.

Contact

WinAudioMLS Pro
<http://www.dr-jordan-design.de>
 SpectraPlus232
<http://www.soundtechnology.com>

1% tolerance. For values up to 47nF we have a choice of near perfect, very low distortion, extended foil and Polystyrene or extended foil and Polypropylene capacitors, available at 1% in both axial lead and 'tombstone' styles. COG ceramic capacitors at 5% tolerance, as low cost discs for small values and multi-layer capacitors to 100nF, are distributor items. Larger capacitance values and closer tolerances are manufactured. COG ceramic provides low distortion, unsurpassed capacitance stability with voltage, temperature, time and frequency, the almost perfect capacitor.

For values of 100nF and above, we could use multiples of the above types but foil and Polypropylene styles are available to 10 μ F, regardless of DC bias they assure very low distortion. Metallised PPS types produce little distortion unless subject to significant DC bias. Available to 10 μ F and 1% tolerance, PPS capacitors provide excellent temperature and long-term capacitance stability in smaller case sizes than Polypropylene types.

Power amplifiers needing larger value signal path capacitors, should use bi-polar aluminium electrolytic capacitors, avoiding the conventional polar aluminium electrolytic capacitor for audio signals. With signal voltages across a large

capacitor of 0.5 or more volts, the 'double bi-polar' aluminium electrolytic capacitor, two double value conventional bi-polar aluminium electrolytic capacitors in series, is demonstrably the most economic low distortion choice. Many writers advocate using lesser value film capacitors, to bypass a polar aluminium electrolytic capacitor to reduce its distortion. My measurements show this has little effect, compared to using the bi-polar style, which produces much lower distortion at less cost.

Distributor stocks of bi-polar aluminium electrolytic capacitors rarely exceed some 470-1000 μ F at low voltage, this results from customer demand and not capacitor technology, manufacturers will respond to market demand as will distributor stockholdings.

More than 30 years ago I developed a range of bi-polar or *reversible* electrolytic capacitors up to 10,000 μ F at 63 volt and the Erie Company manufactured many thousands. The largest example which I still have today, a 2,000 μ F 100 volt in a 115 x 45mm case, was developed as the output coupling capacitor for a very high power audio amplifier. ■

References

1. Capacitor SoundsII. C. Bateman. *Electronics World*, October 2003.
2. Capacitor Sounds. C. Bateman. *Electronics World*, July, September 02, through January 03
3. Understanding Capacitors - Electrolytics. *Electronics World*, June 1998.
4. Double bi-polar aluminium electrolytic capacitor. *Electronics World*, January 2003. Patent application GB 0227606
5. Audio-Grade Polypropylene axial capacitor. Maplin Electronics part no. KR78K.

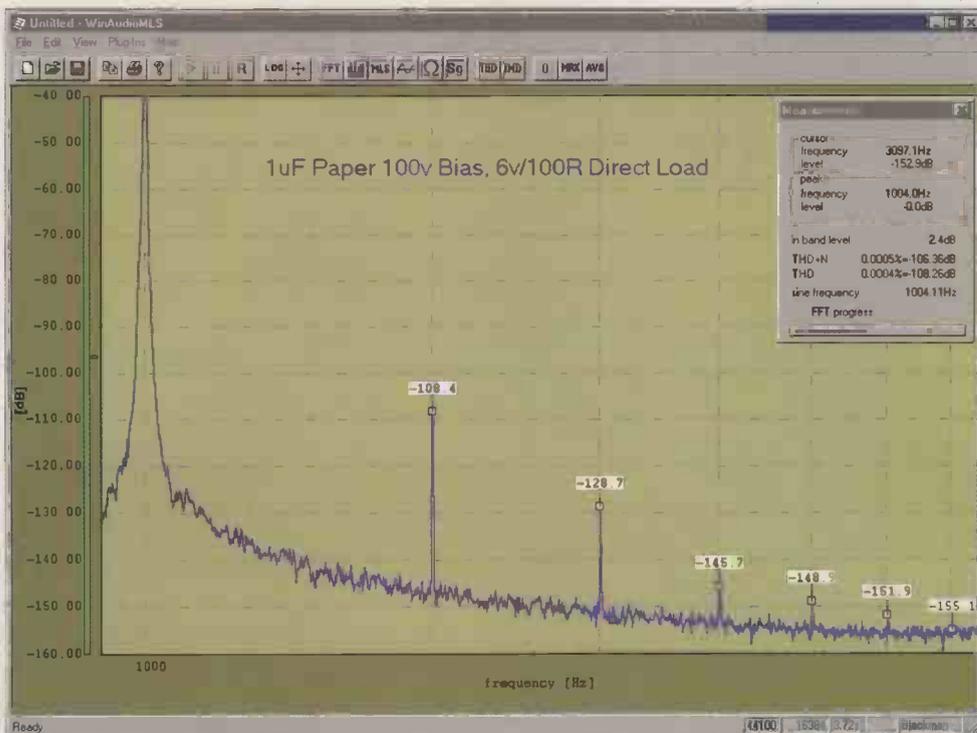


Fig. 10. A typical 1 μ F paper capacitor, with 6 volts AC at 1kHz and 100 volt DC bias, produced this excessively large second harmonic distortion. The 630 volt 1 μ F MKP Polypropylene capacitor was five times better with second harmonic - 123dB, third - 130dB, just 0.00008% distortion. This plot was measured using the Dr.Jordan software, the SpectraPlus232 gave almost identical results.

LETTERS

to the editor

Letters to "Electronics World" Highbury Business Communications,
Nexus House, Azalea Drive, Swanley, Kent, BR8 8Hu
e-mail EWletters@highburybiz.com using subject heading 'Letters'.

Historic receivers

I was reading the article by Jeremy Stevens on 'Receivers of the Third Reich', which I found most interesting, but the marking of the capacitors reminded me of a similar situation in British military radio history.

Many years ago, I was employed by a TV sales and service company owned by an ex-army (probably REME) officer who had served in WW2. He loaned me some books entitled "Handbook of Wireless Telegraphy", the Admiralty Radio Handbook, published by HMSO in 1938. These tomes covered every detail of technology at the time, in fascinating detail.

The thing which sticks in my mind the most is that all capacitor values (or condensers, as the term was then) were given in 'jars'. Somewhere there was a note explaining that "the jar is now obsolete as the service unit, having been replaced by the Farad and sub-multiples thereof." Despite this statement, all the worked examples are done in terms of jars! Fortunately a colleague has the same manuals, and has loaned them to me to do this little piece of research.

The jar, based on early capacitors built in 'standard' Leyden jars was equivalent to 1000cm. It goes on to give conversion factors to and from micro-Farads where $1\mu\text{F} = 900 \text{ jars}^1$. The same paragraph states that a cm (centimetre, yes really) is that value of capacitor which when charged with 1 Electro Static Unit of charge, has a potential of 1 ESU of PD (voltage) between its plates. Further references define the ESU for charge and ESU potential difference.

Charge is defined in terms of force in dynes exerted between two unit charges at 1cm distance in *vacuo*. This evaluates as 1 coulomb = 3×10^9 ESU. The ESU² of PD is defined in terms of coulombs and ergs, and

evaluates to 300volts³.

For the younger reader, the Leyden jar is a bit like a square glass jam-jar with a lift out metal centre and a metalised outer shell. The unit can be charged, separated, handled, then re-assembled and discharged. The only time I have ever seen one was in my physics lessons at school, where the thing was charged from a Van-der-Graaf generator, duly dismantled (using a long, insulated rod) and played with by the whole class, ultimately to be re-assembled and then discharged with an impressive 'crack'.

It was used to clearly demonstrate that the charge was stored in the dielectric, in this case, the glass. The metal parts from a fully discharged jar were then assembled around a previously charged and dismantled glass jar, with the same satisfying result.

Following on from the great EMC debate, most of us appreciate the thinking behind the CE marking of electronic equipment, but it is ludicrous to try to implement the regulations imposed in the manner that they have been. With so many loopholes and escape clauses, a carefully worded paragraph in the CE statement will let most things off the hook.

The tests applied can be quite selective. For example, electrically a kettle has a resistive element, is unlikely to be susceptible to RF emissions (short of a nuclear explosion) and providing that the switch has some spike suppression, is unlikely to emit much radiation. Is this device justified in being subjected to a full product spec EMC test similar to that for a complex multi-way fire alarm system?

Similar reasoning can be applied for a 'likely use' aspect of a piece of equipment. A simple battery and bulb torch may carry a CE mark. If one were to build a similar torch, but

using an inverter and white LEDs, should this have the same or a more stringent test applied? These decisions are left to the manufacturer, but if we get it wrong what then? Fines, confiscation of equipment, each director held singly and jointly at fault. What a minefield!

The great CE con is in full swing

1000 lines, Green

Leslie Green's article on Calculus was well written. The answers had 3 typos.

(1) answer 1 is 26.66 V / microsecond

(2) head of answer 3) missing

(3) answer 4) mean power in resistor is 25.75 W

George Barnes

Hunter Institute

Newcastle TAFE

Australia

Green II

Leslie Green's article on basic maths is admirable. Perhaps someone should likewise take up cudgels on behalf of logarithms. It's quite amazing (to the calculator-bound majority) what can be done with mental arithmetic and logarithms.

I should like, if I may, to propose a small clarification. 'RMS power' is of course calculable but is, as the article states, neither valid nor useful. What's invariably meant is quite simply average power. Voltage or current is measured as Root Mean Square and is then squared in the process of calculating power. 'Root mean' squared becomes simply mean, a.k.a. arithmetic average. I suspect that to most of us plain 'average' simply sounds instinctively too vague, accurate thought it may be!

Re: Catt etc., please keep this stuff coming. It clearly makes a lot of us think and that's no bad thing! But could letter-writers on audio please read Doug Self's articles (or books) before armchair theorising? Usual disclaimers - I've never met him etc. etc. - but he's already invented the wheel and credit to him for telling us exactly how.

Richard Black

London

UK

now. Have you found a piece of equipment with a mains lead attached lately? It would appear that if the unit radiates undesirable RF signals from the lead, then technically it fails the EMC emissions test. On the other hand, if the lead can be unplugged, and the lead is CE marked (and most mains leads are fairly benign when not plugged in or connected only to a resistive load after all) then they are classed as separate items, and the unit with no lead can be certified. Hence the rise in equipment supplied with 'kettle' leads. Of course, having connected them together and switched on the unit, does the whole assembly fail to comply, and who could be held responsible for any undue emissions? Both the device and lead are CE marked and therefore can be supplied legally, but who is at fault - the customer? "I know nuffink, Guv! That's how it came in the box!"

Similar reasoning is applied to 'plug top' power supplies. On its own, the PSU passes the relevant tests for its class of equipment. Similarly, on its own, the powered

equipment passes, except for radiation from the power lead. So: fit a DC socket and CE label, and supply a CE marked PSU. Job done!

Perhaps the faceless men in Brussels should stick to defining the size of the Euro-apple, or the colour of the standard Euro-tomato, or even the shape of the standard Euro-car, and let our industry do what it does best - make working, reliable products with minimal interference radiation and absorption problems.

After all is said and done, Joe Public will let us know, for certain, that his new video, TV, computer, radio etc. does not work, so we have to design in interference suppression anyway.

As for EMC susceptibility, again J.P. will avoid the radio that he has heard will only receive Radio 2 LW if it is in a steel shed down the garden!

References taken from "Handbook of Wireless Telegraphy Volume 1" published by HMSO 1938
 paragraph. 167
 paragraph. 95
 paragraph. 102
Andrew Denham
By email

relatively fleeting coverage in Letters. With the many skilled writers and contributors at the disposal of *EW*, I could imagine some lively, interesting and engrossing articles. There is no other technical journal that does this that I know of.

Looking back and doing a brief check of my library, between 1957 and when *WW* became *E&WW*, the things most evident were its thickness and the relatively constant proportionality of articles to total pages along with the preponderance all thing British. In 1978 there were 128 pages and 44 of them were technical, in 1986 perhaps the publisher was hard up as it only had 96 pages and a similar proportion of technical, and in more recent times 2002 there were 55 pages of which 25 were technical. The other notable aspect is the value for money - this appears not to have markedly changed in relation to technical content. Say 40 pages for £2.95, which equates well to the costs of living during the past 20 years or so - in May 1981 it was 60 pence. Also noteworthy in terms of value for money is my current issue (July) of the journal, for of its 64 pages, no less than 40 are technical if you count the letters! Value increased?

However, looking back again over that period, there seems not to be any replacements for regular small feature writers like 'Vector', 'Cathode Ray' and SW Amos or indeed the Lab Technician/projects manager. I note that many technical magazines have their own Lab and most have articles written from, or at least verified from their specific labs. Perhaps *EW*'s lab would have a lot to do with proving some of the letter discussions as mentioned. It could also enhance the credibility of some projects and become a reference point for those seeking advice on a project.

One of the dangers of change from a readership point of view, might be evident if the journal were to become too market oriented, by having larger numbers of advertisements or become a medium for specialised promoters like test gear manufacturers. For me, the current exposure of such material is now borderline. I know it helps to pay the bills, but we the readers, should not have that foisted upon us simply because of costs. I would be one of those who would approve an increased subscription rather than see the magazine degrade in that way. As an aside to this issue, are there any possibilities of any kind of relatively neutral

More history

I thoroughly enjoyed reading the well researched and illustrated historical article in the August 2003 *EW* issue on the VE301 valve radio receivers of the Third Reich. It is revealing to look back at the often elegant techniques used to solve design problems despite the limitations of the components available at the time. What is also striking is that the valve design goals were achieved with a very low component count - size and cost prevented 'Norwegian coast' designs (apologies to the late D. Adams!).

The nostalgic days of World War II were well before my time. I passed my formative years in the transition from valve to semiconductor technology in the 1960's and remember well the problems these fragile germanium newcomers provoked - do you remember the OC series ??? It is amusing now to look at such details as the influence of valve chassis design culture on the early attempts at portable transistor radios, each stage often being an isolated island of components as if there was a phantom valve base. Compare that to a smd digital pcb of today!

There is much wealth and wisdom in the fascinating legacy of a century of electronics development. The scope for further historical articles drawn from this heritage can only be limited by your enthusiasm to print them, so please, more of that kind of thing!

Peter Sullivan
 Geneva
 Switzerland

I am actively looking at doing some more historical articles as it has proved very popular. Watch this space, and yes I remember them well! - Ed.

Content and Focus

I have been reading *WWW*, *E & WW* and now *EW* as my magazine of choice since 1957 and have seen many changes in its presentation and content! Normally I'm one of the silent majority, but now feel the need to comment on this apparently vexatious matter. My latest copy is July due to normal subscription delays to NZ, so I hope that my comments are still appropriate.

Whilst I accept that change is constant and that any magazine, journal or periodical must adapt to survive, there are, I submit, some notable aspects that must never be seen as compromised. These would include technical accuracy and timeliness. Two areas that *EW* seems to handle well I think. There also, seems to be a fair balance between non-computer based and computer based articles or those with a high degree of academy. If there's a lacking in any way, for me, it would be in the areas of 'High End' projects, especially those of the calibre of Cyril Bateman's "Capacitor Sound", or Doug Self's Audio projects and J.L. Hood's work.

An area that *EW* can serve well is to support solid discussion on the many contentious issues often given only a

technical sponsorship?

There would I suggest, be a quite a large readership who read this Journal, purely for its technical content and detailed approach without ever making a project, often using it to keep up to date by, or as reference. For these readers the broadest technical content will always be welcomed and to limit it by concentrating on what is purely vogue or topical might not be useful.

In general, I applaud *EW* for its breadth and depth and hope that it will continue to maintain its standards and even improve upon them with a resident Laboratory and Manager.

Terry Bicknell
Waikanae
New Zealand

Glass Houses

I would not judge Alan Bate MIEE as suitably qualified to comment on the contributions of others (Letters, *EW*, September 2003). I base this judgement on his description of a simple(sic) two-gate latch. He explains its operation using three statements - and all three are wrong. The latch (as drawn) does not set at power up - it resets. The latch does not change state as soon as contact A momentarily opens - it changes state when contact B momentarily closes. The latch has not already set by the time the switch pole is contacting B - it is still reset.

In the same issue R Harris concludes his(?) letter berating *Electronics World* for '... rather sloppy English ...' (citing a recent spelling error). However, his previous paragraph ends with a far worse example of sloppy English - '... any potential contributors out there.' The grammar is passable but the word 'potential' makes no sense at all, the correct word is 'prospective'. This is because we are all potential contributors by virtue of being able to write in English but, since most of us are insufficiently informed on the subject matter, we would first require a considerable period of study, so few of are prospective contributors.

I don't object to criticism but I do think that it should be properly informed.

Richard Burfoot
Yate
Bristol
UK

Automotive audio systems

I have enjoyed very much Mr. Catt returns in March issue and that *Electronics World* is appealing. Not a subscriber as yet but a buyer at the bookstand. When is the time that some writers will contribute to the automotive audio systems? The in-car-entertainment; manufacturer basics, like DIN connectors used and to interface such a task. Computer has so much learning criterion than I will see in automotive audio system. In bookstores are many computer books than any other books on the stand. Where is auto audio? Thank you for the great work.

Tony Neiburg
St. Paul
Minnesota
US

Sounds like a gauntlet being thrown down to me - Ed

De-bounce II

With reference to Alan Bate's comments on Deng Yong's switch de-bouncing circuit (Letters, September 2003), would it be stating the obvious to point out that Mr Yong's circuit will work with a simple ON/OFF switch, whereas the standard bistable circuit requires a two-way switch? The more complex circuit would be useful when adding-on circuitry to an existing piece of equipment, or in situations where a two-way switch is not feasible.

Ronald Ogilvie
Killearn
Stirlingshire
UK

Design for EMC

In his letter "Student knowledge and EMC" (*EW* Sept. 03), Cyril Bateman identifies one of the most significant sources of interference - EMC filters. These devices are designed to reflect unwanted energy back into the conductors. Since this energy is not dissipated in the conductor resistance, it radiates into the environment and reappears as unwanted interference. The culprit circuit may be immune, but what about other equipment in the vicinity of the supply line?

Mr. Bateman treats the topics of 'student knowledge' and 'EMC' as two entirely separate issues; thereby highlighting the fact that no one

Bateman in error - shock

Your current EMC debate is unlikely to resolve satisfactorily when even (respected) Cyril Bateman seems to be in error. In his letter of your September issue he states, "An EMC filter in contrast, while it may still produce 50dB attenuation, dissipates almost no energy." Well, no, actually. A correctly designed EMC filter absorbs energy with a frequency proportionality inherent of ferrite loss characteristics, and after ferrimagnetic resonance the impedance becomes ostensibly resistive. Check out 'Ferroxcube' (now Yageo apparently) publications for elucidation. Of course pure reactance can play a part whereby the energy is reflected back to from whence it came, hopefully a sealed unit, but this is a very dangerous practice upon which to rely. My July 2001 article "Elastic Capacitors" alludes to the pitfall, as does Cyril, of the dubious practice of slapping in inductors in the blind belief that it will probably help.

The efficacy of the absorption is easily demonstrated. For instance, many years ago I designed a switcher of only a few watts and cleaned the spikes with a ferrite bead. It got reasonably warm. On a more recent 60 watt design, I burned a finger tip on an inappropriately selected filter ferrite when searching for what was smelling, and no it wasn't copper loss.

Regarding Cyril's appraisal of domestic washing machines having included EMC filter solutions for the last 30 years, I don't think my last machine was aware of this. My scope protested audibly when the thyristor spike generator kicked in. Could have fried pies on the radiation.

A S Robertson
Girvan
Ayrshire
Scotland

really expects young graduates to have any useful knowledge of electromagnetic compatibility. It is assumed that such knowledge can only be gained the hard way - through experience.

This situation exists in spite of the need for a clear understanding of the phenomena by anyone who designs or uses electronic equipment. If no one is provided with the basic analytical tools when they are introduced to the subject, then very few are likely to discover those tools for themselves when faced with a real problem, especially when the budget is tight and the timescale is limited.

The young engineer is confronted with a virtual mountain of literature on the subject of EMC and is all too easy a prey for those who provide courses and seminars of dubious value at extortionate prices. The result is a sense of extreme frustration. Ivor Catt indicated this in his article in the March 03 issue of *EW*.

The nub of the problem is the fact that EMC requirements are not subjected to a rigorous analytical process; in sharp contrast to other design requirements such as system function, response time, stability, power consumption, reliability, mass, size and cost. Admittedly, there are useful hints, tips, and fixes to be

found in some books on the market. But such advice can hardly be classed as analytical.

However, it is not particularly difficult to create a circuit model of the configuration under review, analyse the electromagnetic coupling between independent circuits, and validate the results using simple

bench tests. When the coupling mechanism is understood, it can be controlled.

Such an approach was introduced to readers of *Electronics World* in the August 1998 issue by the article 'Grounding on a different plane', and developed in subsequent articles. For those who have no time

Errors, nonsense and 'The Question'

It's not only my handwriting that gives rise to errors. John Barrow explained in his article 'Glitch' (*New Scientist*, 7th June 03) that superior intelligences in a multiverse model – an extension of DeWitt's 'many worlds' interpretation (1973) are not immune from this phenomenon. Not only are they inevitable; they are necessary: for economical reasons (in terms of computing resources needed) and for survival (IGUS Information Gathering and Utilising System, Gell-Mann and Hartle, 1989). Paul Davies believes that "our living in a fake, simulated reality is a nonsense", although the model is popular with many theorists.

If qPCs (quantum personal computers) become available we won't even need to switch them on – or buy them! Whether or not we'll need VDU/WP/email with this set-up is beyond my ken. Perhaps Ivor could explain?

Sébastien's observation that "0.5% distortion is more appealing than (nearly) none at all" is something to think about, especially when you consider all the time and effort that has been devoted to eliminating it!

When you wrote that you "will draw a line under the EMC debate" at the end of Ivor's letter about the Catt Anomaly, I got a bit confused! No big deal.

The EMC debate has had a good airing and probably deserves a rest, but the same can't be said of the 'Catt Anomaly' which may be closely associated with one of the strangest problems that has cropped up in theoretical analysis to date, that is: - time reversal, or 'time runs backwards'. Martin Gardener has tackled this problem in his latest book "Are Universes thicker than blackberries?"

The idea stems from the work of Kornhuber (1976) and Libet (1979), which Roger Penrose discusses (at the end of his books) in conjunction with consciousness and language. The main findings are that (i), a and individual's brain response precedes a stimulus; and (ii), there is a 'dead time' of about 0.5 second. Little or no mention has been made to the relationship between 0.5s and 2Hz –

except in *EW!* The findings of brain research – in some cases, using electrical probes – was summarised by Susan Greenfield in *The Mind Game* (BBC 2 TV) in 2002: -

- (i) time runs backwards
- (ii) all history is pre-recorded in the brain
- (iii) the brain samples the record at intervals to create a sense of time, objective or whatever?

These ideas are not new! (vide refs 2,4)

One of the most exciting developments comes from the findings of Vitor Ramachandran, who appeared in *The Mind Game*. In the last of the *Reith Lectures* (BBC Radio 4) for 2003, he suggested that "the origin of cognition lies in the sounds found in the language centre of the parietal lobe.... and probably, quite a small number". Curtius listed 664 basic phonemes (roots and stems) of which 17.3% involve Kappa and most conform to Zipf's law and Shannon's Eutropic order for intelligent interaction. 'Kai' is the locative pronoun from the Skt. 'kas', still used in Cyprus, which lends itself to the Latin 'que' (kwā); Italian lost the 'w' whilst German and English lost the 'k'.

Tracing 'kai', 'su' and 'tu' to its roots is easy – 'Bruton' (fermented wine) is more involved. If it's from Sanskrit 'brahm', by loss of aspirate (h), it should have carried the meaning 'whirring whirling motion' rather than 'whirring sound' or 'breath'. Hebrew, however, uses HeBeL and HeVeL for 'whirring whirling motion' in Ecclesiastes 1:2 "Vanity of vanities... all is vanity" (KJ), but retains 'h' in BaHiR (Job 37:21) for 'bright light'. Sanskrit 'ruk' (light) softened in Greek to 'luk' and further in Italian to 'luce', but is retained in 'ēlēcktron' (amber, shining metal), although Curius associated a different provenance! Why?

One reason might be the mechanism which Rama' described: leakage from the parietal areas into other sensory and brain areas (synaesthesia), as for example, in the case of 'The man who couldn't tell the difference between his wife and his hat' (Oliver Sachs patient). The leakage might

be quite common, however, even in 'normal' people! – including physicists. If this mechanism is coupled with the 'many-minds interpretation' of Everett, elaborated by David Deutsch (in 1985) in a bifurcating model, as against the many worlds interpretation of DeWitt (multiverses), which Paul Davis thinks is nonsense, it's possible to see how the contradictions in modern physics may be resolved. This will create problems, however, for electronics theory where frequency and time are inversely related in standard models, which brain researchers assume! In bifurcating brain processes, period doubling is 'perceived' as frequency doubling. This is 'real time'.

To a certain extent, the reasoning in 'The Question' and in Nigel Cook's articles (*The Electronic Universe*) about 'awareness' of an open circuit are soundly based – it's not nonsense. Electrons, photons, beables (John Bell's), Hu particles are aware. That's what many leading physicists believe. David Bolm and Basil Hiley discuss this in 'The Undivided Universe', Routledge, (1993) in chapters 13, 14 and 15.

Lit

- 1 George Curtius *Principles of Greek Etymology*, 5th edition, 2 vols English translation, A.S. Wilkins, E.B. England, Pub.: John Murray, London.
- 2 Gershom Scholem, *Origins of the Kaballah* (1962), English translation (1987) Princeton University Press, Ch 2 *The Book BaHir*.
- 3 David Bohm and Basil J. Hiley *The Undivided Universe, An ontological interpretation of quantum theory*, Pub: Routledge, (1993), London.
- 4 John Berges *Hidden Foundations of the Great Invocation*, Pub: Planetnetwork, NJ, USA.

G3OMD

Tony Callegari BSc., MPHIL., (Lond)
Much Hadham
Hertfordshire
UK

A model handwritten letter complete with an 'error code' column! My wife much appreciated it! – Ed.

to go hunting for back issues, the information is available at the website www.designemc.info.

The suggestion that any EMC problem could be analysed by any electronics engineer will be greeted with extreme scepticism; especially by those who have been steeped in the propaganda that it is an arcane subject whose secrets are available only to the gifted few. However, anyone who overcomes this scepticism will be able to visit the site. It contains an e-mail address for any comment.

Ian Darney
Kingswood
Bristol
UK

Google search

Ivor Catt suggested (*EW* Sept 2003 p.57) a Google search on "Pepper FRS". I did this and am pleased to have taken his advice; I spent the next three days virtually glued to my screen! Incredible stuff.

Charles Coultas
Wokingham
Berkshire

Self replies

In answer to William C. Cross' letter last month - if I understand this suggestion correctly, it could indeed be set up to make the input FET drains track the gates and so render non-linear capacitance here innocuous. This does however still leave you with the greater non-linearity of a FET input stage to grapple with, plus the need to use expensive dual devices to cope with the input offset voltages.

Douglas Self
London
UK

Meaningless algebra

I must apologise that until now I have not had time to respond to Mr. Koren's letter published in the August *EW*.

That someone can dismiss algebra as 'meaningless' needs no observation from me but Mr. Koren's misunderstanding regarding experimental error does need comment. Since he has declared his algebraic scepticism, let us work in the numeric field.

Suppose a Wheatstone Bridge uses all 1% resistors and in a particular job is balanced at 4321 ohms. At most this value could be 4364.21, an inflation of 43.21 ohms. Of this the

Understanding ADCs

I am referring to the article "Understanding inputs to ADCs" by Mr. Daniel Malik in the June 2003 issue.

In the example given of the change in potential (voltage) when a 5pF charged condenser (capacitor) is connected in parallel with a discharged 0.5pF. It is stated that the potential will drop to 95% of its original value.

My calculations below disagree. Assuming the condenser was originally charged to 1V.

$C_t + C_p = 5\text{pF}$ (charged to $U = 1\text{V}$)

$C_x = 0.5\text{pF}$ (discharged, connected in parallel)

$Q = U \cdot C$ $Q = 5e-12\text{ C}$ (original and final total charge)

$U' = Q / (C_t + C_p + C_x)$ $U' = 5e-12 / 5.5e-12$ $U' = 0.91\text{V}$ (final potential)

Also it is stated that $1/2(C_t + C_p) \cdot U^2 = 1/2(C_t + C_p + C_x) \cdot U'^2$. This implies that the energy is preserved after connecting the charged and discharged condensers in parallel. To the best of my knowledge, this not so.

I have not read the whole article, so I cannot comment any further.

George Nole
Wyaliba NSW Australia

error in the thousands is 40, in the hundreds is 3, in the tens is 0.2 and the units contribute 0.01.

However, if only 10% resistors can be found for use in the units decade, the 1 ohm resistor could have a maximum value of 1.1, which would now contribute 0.1 ohms to the total of 4364.3. Thus the overall accuracy would change from 1% to a maximum percentage error of 1.002%, i.e. practically no change at all.

Consequently there is every reason to have high specification resistors in the upper decades while lower tolerance components can be used in the units decade since they will contribute less

significantly to errors overall.

It is with this in mind that manufacturers of test gear which use digit displays often declare their equipment to be '1% accurate, plus or minus one digit'.

The only time that using 10% resistors in the units decade would be significant is when the bridge is balanced at 000X (X between 1 and 9) but this would represent poor use of the divide-by-1000 facility designed as part of the bridge circuit in the published article.

David Ponting
Clutton
Bristol UK


July cover

No doubt you have been asked this many times, but I haven't spotted any reference.

What is the location of the spectacular storm photo (cover and inside article) in the July issue?

Alan Watling
Colchester
Essex
UK

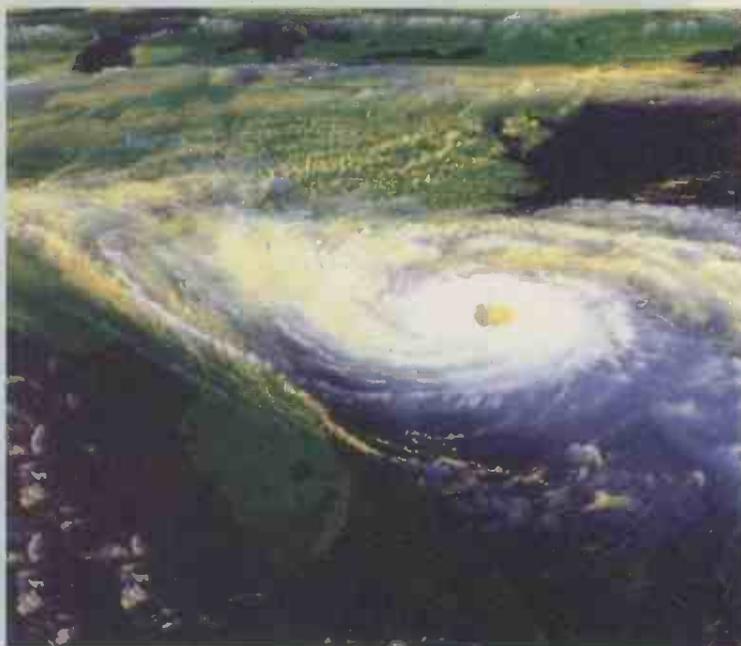Unfortunately, the image came from a generic picture CD that did not have any info as to the whereabouts of the satellite -Ed



TIME MACHINE

Accurate time measurement on a budget by John Morrison

When trying to calibrate a watch or any other device that produces a one cycle per second pulse it becomes very difficult, if not impossible, to measure and adjust using standard 'off the shelf' equipment. The oscilloscope is of no use as the graticule spacing resolution is unreadable when trying to calibrate to 0.001 of a second in the 0.2 – 0.5 scale. A similar problem occurs with the frequency meter, as frequencies below 10Hz cannot normally be measured.

However it is possible to make a low cost unit that can measure 1Hz to a resolution of 1000th of a second.

Measurement basics

If the pulse to be measured is used to turn a fixed frequency count on then off at, for example, 2000cps, then the count available at the end of one second should be 2000.

If the pulse to be measured produces a count that is above or below the 2000 expected - then the pulse is either slower or faster than one second. Note: a slow pulse will give a number greater than 2000.

By using a homemade pick-up coil and an op amp, pulses can be detected from most quartz clocks that have hands. These clocks operate by pulsing a small solenoid at one-second intervals.

The pulse to be measured may not be an exact square wave, as in the clock example, so the unit must take

this into account.

The pulse width shown in Fig 1(B) is 1 second overall, but looks very different to A.

To measure the counter is cleared every time the pulse goes low. There is no stop counter.

Some sort of display is required to show the results of the measurement. Using a 4-digit display would be overkill. A 10 segment Bar graph display is cheaper and produces an easier to understand readout.

The unit could be produced using several discrete devices including decimal counters, and IC gates but a

better way is to replace most of these with just one microcontroller. The other advantage with this approach is that any frequency can be measured with extreme accuracy, simply by changing the software.

Micro-controller

There are many cheap micro-controllers on the market. This design needs one that can drive LEDs directly, has an internal timer and a prescaler. The one chosen meets this specification, a Microchip 16F84. This controller also has re-programmable code memory and is cheap and readily available.

If you have never worked with micro-controllers, this is an ideal choice as there is a huge amount of information and examples on the microchip website www.microchip.com

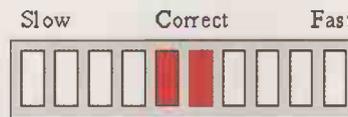


Fig. 2. 10 segment bar graph display.


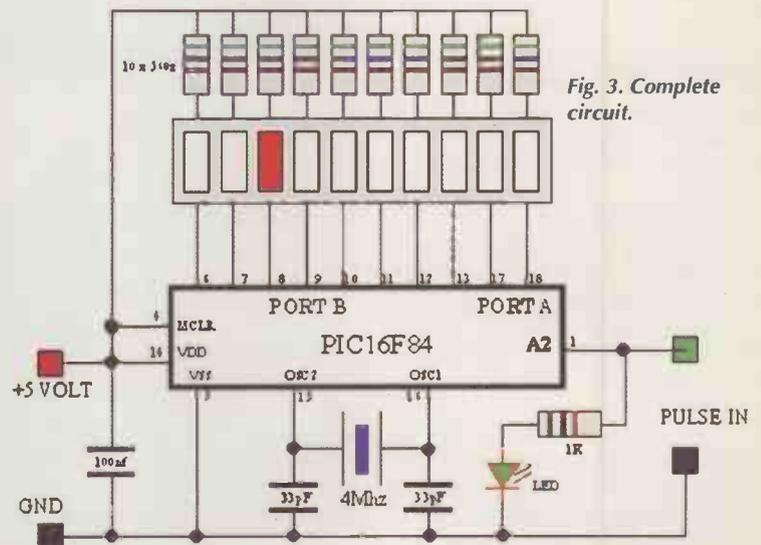


Fig. 3. Complete circuit.

ELECTRONICS WORLD

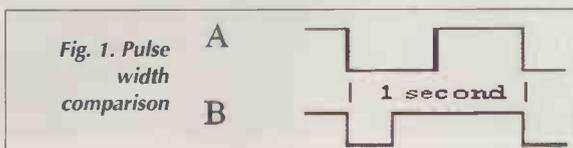

The world's leading electronics magazine, **Electronics World** is a technology-transfer magazine for the global electronics industry. It covers research, technology, applications, products and patents in areas such as audio, R.F., components, CAD design, circuit building, PC & Micro based products, tests & measurement, semiconductors, power sources and much, much more.....

A trustworthy source of reference each month for keeping ahead with the latest news and technical developments in the electronics industry.

As the longest established magazine in the industry - 80 years experience serving the electronics market, **Electronics World** is the leading technical journal for electronics professionals and high-level enthusiasts.

Make sure you receive your regular monthly copy by subscribing today.....



Complete and fax the coupon to: +44 (0) 1353 654400

I wish to subscribe for one year to **Electronics World** (12 Issues) 1 year

UK £38.95

O/S £64.50

US\$100.62

Euro 102.55

Please tick preferred method of payment

I enclose a cheque payable to Highbury Business Communications Ltd

Please invoice me Purchase No

(NB Purchase order must be included to validate invoice)

Please charge my: Master Card/Visa/Amex/Diners Club/Switch/Delta (please circle)

Card No _____

Expiry Date _____

(Switch/Delta Only) Valid from / Issue Number

Signature _____

Date _____

Name _____

Job Title _____

Company _____

Address _____

Postcode/Zip _____

Country _____

Telephone/ Fax _____

E-mail _____

Please tick here if you do not wish to be contacted by other businesses either by
Mail Telephone Fax E-mail

Please return to: Highbury Subscription Services, Link House,
8 Bartholomew's Walk, Ely, Cambridgeshire CB7 4ZD, UK.
Email: wss@wyverncrest.co.uk (Quote Ref: EW1)



HIGHBURY
Business Communications
A SUBSIDIARY OF HIGHBURY HOUSE COMMUNICATIONS PLC

The Electronics World Book Service offers access to our team of specialist publishing experts. We can order any book or CD-ROM currently in print from *War And Peace* to the *Reference Data for Engineers*. All books are delivered free of charge within the UK unless otherwise stated. Contact us at the numbers below:

Telephone: **01737 812727** or **01737 812676**

Fax: 01737 813526

Email: salesteam@boffinbooks.demon.co.uk

HIGH SPEED DIGITAL DESIGN
Howard W Johnson & Graham Martin
Re-issue
Focusing on the field of knowledge lying between digital and analog circuit theory, this text sets out to help engineers working with digital systems shorten their product development cycles and help fix their latest design problems. It covers signal reflection and crosstalk.



820 pages ▲ HB
Code PEAR 0 13 395724 1 **£44.99**

RF CIRCUIT DESIGN: THEORY & APPLICATIONS
Reinhold Ludwig; Pavel Bretchko
This practical guide introduces RF circuit design fundamentals while emphasizing a circuit based approach. It provides MATLAB routines to carry out simple transmission line computations and uses a PC-based commercial RF circuit simulation tool to demonstrate actual circuit behaviour.



Oct 1999 ▲ 656 pages ▲ HB
Code PEA 0 13 095323 7 **£35.99**

THE ART OF ANALOG LAYOUT
Roy Alan Hastings
This text aims to provide students with a broad understanding of the issues involved in successfully laying out analog-integrated circuits - ranging from the mechanics of layout to essential information about many related areas, such as device physics, processing and failure modes and effects.



Oct 2000 ▲ 559 pages ▲ HB
Code PEAR 0 13 087061 7 **£30.99**

DESIGN-FOR-TEST: FOR DIGITAL INTEGRATED CIRCUITS AND EMBEDDED CORE
Alfred L Crouch
An introduction to the basic concepts of Design-For-Test, an area in chip design.



July 1999 ▲ 350 pages & CD-ROM
Code PEAR 0 13 084827 1 **£59.99**

ELECTRONIC PROJECTS FROM THE NEXT DIMENSION: PARANORMAL EXPERIMENTS FOR HOBBYISTS
Newton Braga
A guide to making and using paranormal research electronics. It describes practical electronic circuits to be used in experiments involving instrumental transcommunication (ITC), the electronic voice phenomenon (EVP), and paranormal experiments involving ESP, auras, and Kirlian photography. White and pink noise generators for use in instrumental transcommunication (ITC) experiments; Kirlian photography; plasma experiments; extrasensory perception testers; magnetic fields sensors.



Nov 2000 ▲ 256 pages ▲ PB
Code H80 7506 7305 2 **£28.50**

BASIC AC CIRCUITS
Clay Rawlins
A step-by-step approach to AC circuits for beginners, providing thorough coverage of theory and practice. The text provides individualized learning goals covering electronics concepts, terms and the mathematics required to understand AC circuit problems.



2nd Edition ▲ Oct 2000 ▲ PB
Code H80 7506 7173 4 **£34.50**

INTERFACING WITH C
Mike James & Howard Hutchings
An exploration of interfacing personal computers using C. An introduction to C; loops and data conversion; data acquisition using C; essential mathematics; convolution; digital filters; Fourier transforms; correlation; Kalman filters; data conversion; investigating the spectral and time-domain performance of z-transforms using computer-managed instruction; introducing audio signal processing using C; standard programming structures. Dewey: 005.71262



2nd edition ▲ Dec 2000 ▲ 308 pages
Code HB 0 7506 4831 7 **£20.50**

SELF ON AUDIO
Douglas Self
This work offers a collection of *Electronics World* articles, including self-build projects. It aims to demystify amplifier design and establish empirical design techniques based on electronic design principles and experimental data.



Jul 2000 ▲ 256 pages ▲ PB
Code H80 7506 4765 5 **£28.50**

BUILD AND UPGRADE YOUR OWN PC
Ian Sinclair
This third edition of *Build and Upgrade Your Own PC* is based around building and upgrading to the very latest systems running processors with speeds over 2.0 Ghz and ultrafast buses. It also covers upgrading to Windows XP and Windows Me.



3rd edition ▲ Jul 2002 ▲ 335 pages ▲ PB
Code HB 0 7506 5758 8 **£22.50**

PRACTICAL ELECTRONICS HANDBOOK
Ian Sinclair
A collection of all the key data, facts, practical guidance and circuit design basics needed by a spectrum of students, electronics enthusiasts, technicians and circuit designers. It provides explanations and practical guidance, and includes new sections on SHF techniques and intruder alarms.



5th edition ▲ Feb 2000 ▲ 571 pages ▲ PB
Code HB 0 7506 4585 7 **£16.99**

ANALOG CIRCUIT TECHNIQUES WITH DIGITAL INTERFACING
Trevor Wilmshurst
Aimed at junior undergraduates, this textbook offers comprehensive coverage of analogue electronic circuit design with two full chapters devoted to the use of SPICE in circuit simulations. programmes leading to IEng MSc Electronic conversion type courses.



Mar 2001 ▲ 320 pages ▲ PB
Code H80 7506 5094 X **£19.99**

ELECTRONICS FOR SERVICE ENGINEERS
Joe Cieszynski & Dave Fox
From simple mathematics and circuit theory to transmission theory and aerials, this text provides the range of knowledge required to service electronic and electrical equipment. Questions and worked examples illustrate the concepts described in each chapter.



Mar 1999 ▲ 294 pages ▲ PB
Code H80 7506 3476 6 **£20.99**

FABRICATING PRINTED CIRCUIT BOARDS
Jon Varteresian
Engineers are often faced with the need for small quantities of a certain board design for construction of a small number of devices. This book describes the process of making a printed circuit board, from the conversion of a schematic diagram into a board layout to the making of the board itself.



Jul 2002 ▲ 251 pages ▲ PB
Code HB 1 878707 50 7 **£21.99**

REFERENCE DATA FOR ENGINEERS: RADIO, ELECTRONICS, COMPUTERS AND COMMUNICATIONS
Mac E Van Valkenburg
Written by professionals for professionals, this title is a complete reference for engineers, covering a broad range of topics. As well as addressing radio technology data, this reference volume covers digital electronics, computers and communications.



9th edition ▲ Aug 2001 ▲ 1568 pages
HB & CD-ROM
Code H80 7506 7291 9 **£90.00**

PRACTICAL RF HANDBOOK
Ian Hickman
A hands-on-guide for engineers, technicians, students and enthusiasts working in RF design, this comprehensive text covers all the key topics in RF, including: analogue design principles; transmission lines; transformers; couplers; amplifiers; oscillators; modulation; and antennas.



3rd edition ▲ Feb 2002 ▲ 289 pages
150 line drawings ▲ PB
Code HB 0 7506 5369 8 **£19.99**

NEWNES TELEVISION AND VIDEO ENGINEER'S POCKET BOOK
Eugene Trundle
This text provides a pocket tool for service engineers. It presents a range of essential information in a compact form, covering television reception, satellite and cable television, video recorders, colour camera technology, teletext and fault-finding.



3rd edition ▲ Oct 1999 ▲ 512 pages ▲ HB
Code HB 0 7506 4194 0 **£17.99**

**BEBOP TO THE
BOOLEAN BOOGIE**

Clive Maxfield

Comprehensive introduction to contemporary electronics - friendly, funny and quirky. Whether you're an engineer, hobbyist, or student who needs a thorough and up-to-date electronics reference or a non-technical person who wants to understand more about this electron dance that has seemingly taken over the world, this book is the answer. Hundreds of diagrams that clarify even the most difficult subjects.

2nd Edition ▲ Jan 2003
Code HB0 7506 7543 8 **£27.50**



**NEWNES GUIDE TO
DIGITAL TV**

Richard Brice

Covering all aspects of digital television (terrestrial, satellite and cable), this text has been updated with developments since the 2000 edition. Foundations of television; digital video and audio coding; digital signal processing; video data compression; audio data compression; digital audio production; digital video production; the MPEG multiplex; broadcasting digital video; consumer digital technology; the future.

2nd edition ▲ Sep 2002 ▲ 304 pages ▲ HB
Code HB0 7506 5721 9 **£24.99**



**NEWNES
DICTIONARY OF
ELECTRONICS**

SW Amos & R S Amos

Aimed at engineers, technicians and students working in the field of electronics, this dictionary provides clear and concise definitions, including TV, radio and computing terms, with illustrations and circuit diagrams.

4th edition ▲ March 2002 ▲ 394 pages ▲ PB
Code HB0 7506 5642 5 **£12.99**



**RSGB RADIO AND
ELECTRONICS
COOKBOOK**

Radio Society of Great Britain

Only a basic knowledge of electronics is assumed for this collection of electronics projects, and it is ideal for all electronics and DIY enthusiasts and experimenters. Designed by the RSGB, the UK radio amateurs federation, the projects are clearly explained step by step.

Nov 2000 ▲ 336 pages ▲ PB
Code HB 0 506 5214 4 **£17.99**



**ELECTRONIC
SERVICING AND
REPAIRS**

Trevor Linsley

Updates the previous text taking into account changes in the City and Guilds courses 2360 and 2240. Also features hardware topics, testing and fault diagnosis, PLCs and CAD software, and new chapters. Health and safety; electronic component recognition; electronic circuit assembly techniques; electronic semiconductor devices; electronic circuits in action; testing electronic circuits; digital electronics; electrical circle theory; electronic systems; communication systems; security systems; sensors and transducers.

3rd edition ▲ Aug 2000 ▲ 261 pages
Code HB 0 7506 5053 2 **£18.99**



**DIGITAL LOGIC
DESIGN**

Brian Holdsworth & Woods

This undergraduate text on digital systems covers first and second year modules and HND units, and can also be used as a reference text in industry. Updated topics in the fourth edition include: EBCDIC, Gray code, practical applications of flip-flops, linear and shaft encoders and memory elements.

4th edition ▲ Aug 2002 ▲ 448 pages
Code HB 0 7506 4582 2 **£19.99**



**NEWNES
INTERFACING
COMPANION:
COMPUTERS,
TRANSDUCERS, INSTRUMENTATION
AND SIGNAL PROCESSING**

Tony Fischer-Cripps

Provides the fundamentals of electronics, transducers, computer architecture and interfacing techniques needed to use a simple PC or PLC-based system for the collection of data previously only obtainable from expensive dedicated equipment.

Aug 2002 ▲ 320 pages ▲ HB
Code HB 0 7506 5720 0 **£24.99**



**NEWNES RADIO
AND RF
ENGINEERING
POCKET BOOK**

Steve Winder & Joseph J Carr

With a mass of information and data for students, radio and telecommunications engineers, RF circuit designers, radio hobbyists and technicians, this guide covers all aspects of radio and communications engineering from low frequencies to microwaves, with an emphasis on mobile communications.

3rd edition ▲ Jul 2002 ▲ 352 pages ▲ HB
Code HB 0 7506 5608 5 **£16.99**



**ROBOTICS,
MECHATRONICS,
AND ARTIFICIAL
INTELLIGENCE:
EXPERIMENTAL CIRCUIT BLOCKS
FOR DESIGNERS**

Newton C Braga

This work simplifies the process of finding basic circuits to perform simple tasks, such as how to control a DC or step motor, and provides instruction on creating moving robotic parts, such as an "eye" or an "ear".

Nov 2001 ▲ 317 pages ▲ PB
Code HB 0 7506 7389 3 **£21.99**



**EMBEDDED
MICROPROCESSOR
SYSTEMS: REAL
WORLD DESIGN**

Stuart Ball

Providing an introduction to the design of embedded microprocessor systems, this edition covers everything from the initial concept through to debugging the final result. It also includes material on DMA, interrupts and an emphasis throughout on the real-time nature of embedded systems.

3rd edition ▲ Nov 2002 ▲ 368 pages ▲ PB
Code HB 0 7506 7534 9 **£35.00**



**POWER SUPPLY
COOKBOOK**

Marty Brown

Providing an easy-to-follow, step-by-step design framework for a wide variety of power supplies, including linear, switching and quasi-resonant switching. There is also discussion of design topics such as magnetics, feedback loop compensation design and EMI/RFI control in straightforward terms.

2nd edition ▲ Jun 2001 ▲ 336 pages ▲ HB
Code HB 0 7506 7329 X **£24.99**



**MIXED-SIGNAL
AND DSP DESIGN
TECHNIQUES**

Walt Kester

Mixed-signal processing implies the use of analogue and digital in the same system; this is a specialized type of signal processing that requires a high level of experience and training. This book focuses primarily on signal processing hardware - how it works, how to interface it, and design it.

Oct 2002 ▲ 336 pages ▲ PB
Code HB 0 7506 7611 6 **£39.99**



**UNDERSTANDING
AUTOMOTIVE
ELECTRONICS**

W B Ribbens

Covering the most recent technological advances in operation and troubleshooting of electronic systems and components, including low-emission standards, on-board diagnostics and communications, digital instrumentation, and digital engine control. A practical text, suitable for the automotive technical student, enthusiast, or professional who wants to upgrade his or her background in electronic systems found in the automotive.

6th ed. Dec 2002
Code HB 0 7506 7599 3 **£24.99**



**DESIGNING
EMBEDDED
INTERNET DEVICES**

Brian DeMuth & Eisenreich

This guide to designing internet access and communications capabilities into embedded systems takes an integrated hardware/software approach, using the Java programming language and industry-standard microcontrollers. The CD-ROM has Java source code and a version of the text.

Aug 2002 ▲ 320 pages
PB & CD-ROM
Code HB 1 878707 98 1 **£35.00**



**PIC IN PRACTICE:
AN INTRODUCTION
TO THE PIC
MICROCONTROLLER**

David W Smith

An exploration of the PIC microcontroller, designed to be used at a variety of levels. It introduces the reader to the range of tasks the PIC can perform and makes use of readily available components. The PIC used in the examples is the re-programmable EEPROM 16C84/16F84.

Apr 2002 ▲ 261 pages ▲ PB
Code HB 0 7506 4812 0 **£14.99**



If you are ordering by credit card, need further information, or would like to use our search facilities call
01737 812727 Fax 01737 813526.
The order/helpline is open from 9am to 5pm, or leave your order on our out of hours answerline or email us at salesteam@boffinbooks.demon.co.uk.

When placing orders please quote
• Name • Address (home & delivery) • Daytime telephone number • Debit/Credit card number • Expiry date
• Details of order. Please note that prices may change, but are correct at time of going to press.


Boffin Books Ltd., 24 Walton Street,
Walton-on-the-Hill, Tadworth, Surrey KT20 7RT, UK

ELECTRONICS WORLD ORDER FORM

Please order or search the following:

Code	Description	Qty	Price
POSTAGE & PACKING FREE IN THE UK*			TOTAL
Name		Daytime Tel	
Address			
Postcode			
Delivery address (if different)			
Postcode			
I enclose a cheque/postal order value £ _____ payable to 'Boffin Books Ltd'			
Please debit my Access/Visa/Switch/Delta card		Issue number (Switch only) _____	
Card Number _____		Expiry Date _____	
Signed _____		email:salesteam@boffinbooks.demon.co.uk	

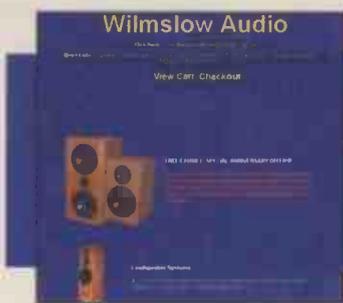*Postage charges outside the UK available upon request or email to salesteam@boffinbooks.demon.co.uk
Send order form to: Boffin Books Ltd., 24 Walton Street, Walton-on-the-Hill, Tadworth, Surrey KT20 7RT, UK



WEB DIRECTIONS



Put your web address in front of 18,000 electronic fanatics. *Electronics World* acknowledge your company's needs to promote your web site, which is why we are dedicating 2 pages in every issue to **WEB ADDRESSES**.

Linage only will cost £150 + vat for a full year.

Linage with colour screen shot will cost £350 + vat for a full year, this will include the above plus 3cm shot of your web site which we can produce if required.

To take up this offer or for more information telephone

Reuben Gurnlian


Tel 01322 611292

E-mail

r.gurnlian@highburybiz.com

ANASOFT LTD


<http://www.anasoft.co.uk>

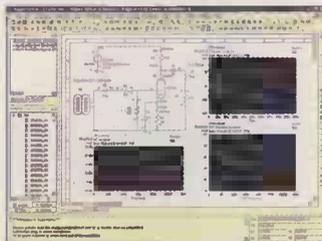

SuperSpice, the affordable, mixed-mode windows circuit simulator. Wrote by an analogue design engineer for those Teletubbies who like keeping things simple.

CHARLES HYDE & SON Ltd


<http://www.charleshyde.co.uk>

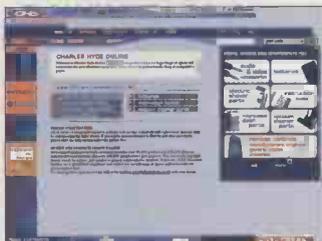

Search for both original and copy spare parts in our extensive database covering Akai, Alba, Bush, Ferguson, Goldstar, Hitachi, LG, Marantz, Matsui, Nokia, Saisho, Sanyo, Sony, Sharp, Thomson, Panasonic, Philips, Samsung, Tascam, Teac, Toshiba, Yamaha and many more. In addition huge ranges of Lasers, Loptos, Remote controls and Semiconductors may be accessed.

CHYGWYN

<http://www.chygwyn.com>

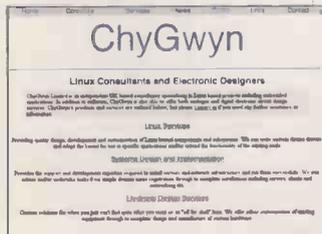

ChyGwyn Limited offers electronic design and embedded software development for remote monitoring, embedded appliances, set-top boxes and similar devices. We are experts in customisation of Linux and write device drivers for custom hardware.

CONFORD ELECTRONICS

<http://www.confordelec.co.uk/index.shtml>

Lightweight portable battery/mains audio units offering the highest technical performance. Microphone, Phantom

Welcome to our range of professional audio and process control products

Just select the products that interest you from the following descriptions

Our standard equipment provides wide variety offering the highest technical performance and rigidity of operating in an industrial PCB layout or industrial PC application. All data from our extensive Trade Programme (available products list) are based on current regional prices. Some of our standard products have not yet been priced and are available on request.

© The Release Box

Microchip is the latest amplifier for balanced or unbalanced signals

- Precision line loading transformer balanced input and output
- Single balanced transformer balanced input and output
- Two channel balanced input
- High Common Mode Rejection

Power and Headphone Amplifiers. Balanced/unbalanced signal lines with extensive RFI protection.

CRICKLEWOOD ELECTRONICS

<http://www.cricklewoodelectronic.co.uk>

Cricklewood Electronics stock one of the widest ranges of components, especially semiconductors including ICs, transistors, capacitors, all at competitive prices.

DB TECHNOLOGY

<http://www.dbtechnology.co.uk/>



EMC Testing and Consultancy. Anechoic chamber and open area test site.

- Compliance Tests
- Rapid, accurate pre-compliance tests.
- Fixes included. FCC Listed.
- Flexible hourly booking available.

DESIGNER SYSTEMS CO.

<http://www.designersystems.co.uk>



Electronic product design company with over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.



EAGLE PCB DESIGN SOFTWARE

<http://www.puresoft.co.uk>

- Professional PCB design made easy!
- Fully functional freeware download.
- Schematics, Layout & Autorouting.
- Free tech support

EasySync

<http://www.easysync.co.uk>



EasySync supplies a wide range of USB-RS232 and USB-RS422/485 converters. It also specialises in USB test and measurement devices.

FELLER UK


<http://www.feller-at.com>



Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

FUTURE TECHNOLOGY DEVICES INTL. LTD.


<http://www.ftdichip.com>

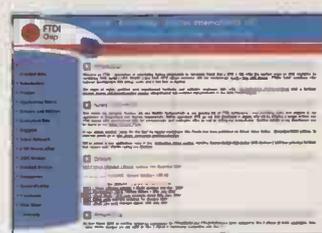

To reserve your web site space phone Reuben Gurunlian

Tel: 01322 611292


Fax: 01322 616376

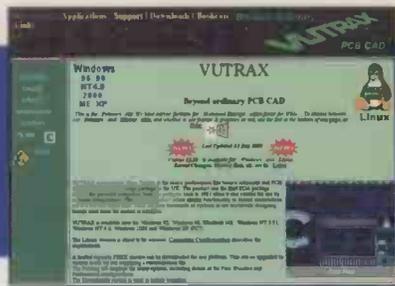

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s. Complete with PC drivers these devices simplify the task of designing or upgrading USB peripherals

GREENWELD

<http://www.greenweld.co.uk>

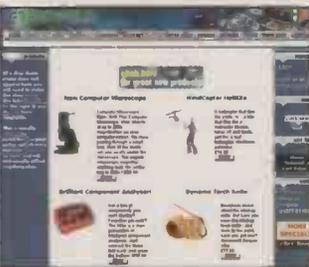


Audio ● Batteries & Chargers ● Books ● Communications ● Computer ● Cable ● Capacitors ● Car Equipment ● Craft Goods ● Disco Equipment ● Enclosures ● Electrical ● Fuses ● Graphic supplies ● Hardware ● Instrumentation ● Kits ● Lighting Mechanical ● Optical ● Photographic ● Power supplies ● Transformers Resistors ● Semiconductors ● Software ● Soldering Irons ● Surplus goods ● Switches ● Relays ● Telephone Accessories ● Tools ● Plus much more.

Whether your interest is in electronics, model engineering, audio, computer, robots or home and leisure products (to name just a few) we have a wide range of new and surplus stock available.

J W HARDY COMMUNICATIONS

<http://www.jwhardy.co.uk>

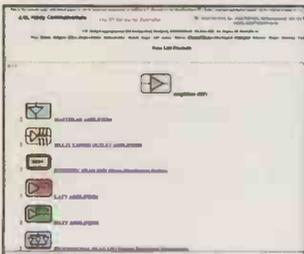

R.F. Network Specialist. Shop online - for R.F. network components. We supply a full range of TV, radio reception equipment to receive analogue/digital signals from both terrestrial and satellite sources. We provide a free planning service for your R.F. networks, MATV and SMATV etc

LOW POWER RADIO SOLUTIONS

<http://www.lprs.co.uk>

LPRS produces radio modules with embedded "easy-Radio" software protocols for short range radio applications. We also represent Circuit Design narrow band modules in the UK.

MATRIX MULTIMEDIA LTD

www.matrixmultimedia.co.uk



Matrix Multimedia publishes a number of highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).


NORCALL Ltd

<http://www.tetra-com.co.uk>

e-mail Norcall@aol.com
Suppliers programmers and repairers of new and refurbished two-way radio equipment. Retuning and recrystallising service available. All types of batteries chargers and aerials supplied.

QUASAR ELECTRONICS

www.QuasarElectronics.com

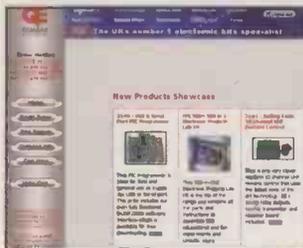

Over 300 electronic kits, projects and ready built units for hobby, education and industrial applications including PIC/ATMEL programming solutions. Online ordering facilities.
Tel: +44 (0) 870 246 1826
Fax: +44 (0) 870 460 1045
Email: sales@QuasarElectronics.com

RADIOMETRIX

<http://www.radiometrix.co.uk>

Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB



mounted miniature transmit, receive and transceiver modules for OEM use. They comply with European harmonised standards EN300 220-3 and EN301 489-3 and are CE certified by an independent Notified Body.

SOFTCOPY

<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

TECHNICAL AND SCIENTIFIC SUPPLIES

<http://www.technicalscientific.com>

Suppliers of pre-1985 equipment and components.

- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

TELEVES

<http://www.televes.com>

Tel: 44(0) 1633 875821
email hbotas@televes.com
Televes website was launched as an easier way to keep in contact with our World-wide Network of Subsidiaries and Clients. This site is constantly updated with useful information/news plus you can download info on our range: TV Aerials & accessories, Domestic and Distribution amplifiers, Systems Equipment for DTT and Analogue TV, Meters and much more.

TEST EQUIPMENT SOLUTIONS

<http://www.TestEquipmentHQ.com>


Test Equipment for rental or second user sale at the industry's lowest prices. All



types of equipment from all leading manufacturers including general purpose, communications and industrial test. Items fully refurbished with 1 year warranty. Rental rebate given on purchases.

TELONIC

<http://www.telonic.co.uk>

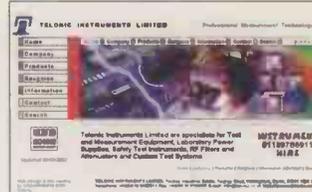

Telonic specialists in laboratory AC & DC Power Supplies, Electronic AC & DC Loads, Electrical Safety Testing and complete test systems. Plus RF Filters, Attenuators, Diesel Engine Smoke Measurement, Quartz Crystal Microbalances.
Tel +44 (0) 118 9786911

TOTAL ROBOTS

<http://www.totalrobots.co.uk>



Robot Kits and Control Technology products, including OOPIC the first Object-Oriented Programmable Integrated Circuit. Secure on-line ordering and fast delivery.

TELNET

<http://www.telnet.uk.com>



Top quality second-user Test and Measurement Equipment
eMail sales@telnet.uk.com

ULTRA-CREA OY

<http://www.ultra-crea.fi>




Our business idea is to provide our customers complete service, i.e. design from the customer specification to the delivery of finished and tested products.

Our offerings are as follows:

- RF transmission line filters from 100MHz to 3GHz
- Special antennas to frequencies as above
- Transmitter and Receiver modules
- RF-subunits such as amplifiers, oscillators, directional couplers etc.

VUTRAX PCB DESIGN SOFTWARE

<http://www.vutrax.co.uk>

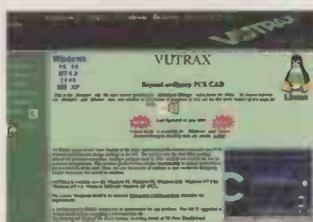

Vutrax electronic schematic and pcb design system for Windows 95/98, ME, NT, 2000, XP and Linux. Limited capacity FREE version downloads available, all upgradeable to various customised level.


WILMSLOW AUDIO

<http://www.wilmslow-audio.co.uk>



"UK's largest supplier of high quality loudspeaker kits and drive units. Comprehensive range of components and accessories, including damping products, connectors and grilles materials. Demonstration facilities available.

Ten year index: new update

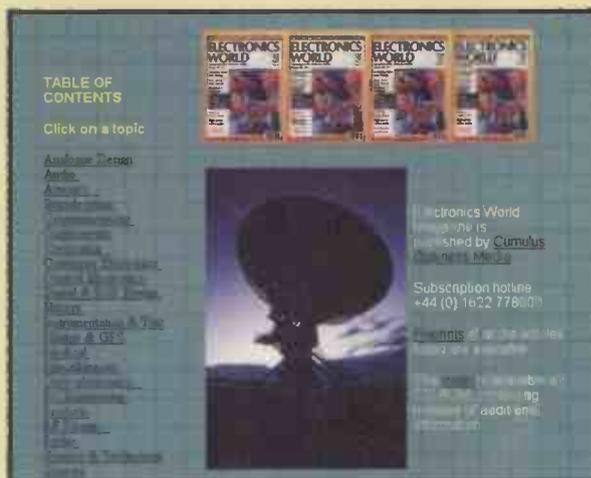

www.softcopy.co.uk

Photo copies of *Electronics World* articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy *Electronics World* indexes on paper for volumes 100, 101, and 102 are available at £2 each, excluding postage.

Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications - including a synopsis for each.

The *EW* index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format.

Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Ordering details

The *EW* index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders

Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquires about photocopies etc please send an sae to SoftCopy Ltd.

**Send your orders to SoftCopy Ltd,
1 Vineries Close, Cheltenham GL53 0NU.**

Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

Easy-PC for Windows

World Beating Value in PCB Design Software


from
£97

High performance Windows based PCB Design Capture, Simulation and Layout software at prices you'd expect from your local computer store!



NEW! in Easy-PC 7

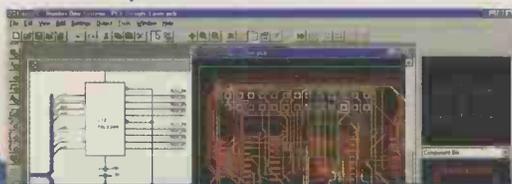- Library Databook
- Step and repeat plotting
- Swap Connection Mode
- Dimensioning
- Copy to Metafile
- plus much more.....



Stop press... by customer demand, now with **Tsien Boardmaker 2** design import...

Number One Systems delivers true 32 bit Windows software applications including features that a few short years ago would only have been available in software tools priced in the thousands!

Test drive Easy-PC and Easy-Spice for yourself and be prepared to be amazed at the super value...

Call for a brochure, price list and demo CD
on +44 (0)1684 773662 or email sales@numberone.com

No1 Number One Systems

Number One Systems
Oak Lane, Bredon
Tewkesbury, Glos GL20 7LR
United Kingdom

or download from
www.numberone.com

High Resolution Oscilloscope

- High speed, 5GS/s dual channel oscilloscope
- 50MHz, 80dB dynamic range spectrum analyser
- PicoScope & PicoLog software supplied FREE
- Plug into any desktop or laptop PC
- High resolution - 12 bits
- Large 128K memory
- 1% DC accuracy

NEW
Product
Range



Request your FREE Test & Measurement catalogue and Software & Reference CD, or visit our web site:

www.picotech.com/scope129



Tel: +44 (0) 1480 396395 Fax: +44 (0) 1480 396296 E-mail: sales@picotech.com

PICO
Technology Limited

Service Link

ARTICLES WANTED

BEST CASH PRICES PAID

FOR VALVES KT88, PX4 AND MOST AUDIO/OTHER TYPES.

Tel: 01403 784961

Billington Export Ltd.
Sussex RH14 9EZ
Fax: 01403 783519
Email: sales@bel-tubes.co.uk
Visitors by appointment

TOP PRICES PAID

For all your valves, tubes, semi conductors and ICs.

Langrex Supplies Limited
1 Mayo Road, Croydon, Surrey CR0 2QP
TEL: 020 8684 1166 FAX: 020 8684 3056

FOR SALE

RF DESIGN SERVICES

All aspects of RF hardware development considered from concept to production.

WATERBEACH ELECTRONICS

www.rlaver.dial.pipex.com
TEL: 01223 862550
FAX: 01223 440853

FOR SALE

PRINTED CIRCUIT BOARDS

DESIGNED & MANUFACTURED  **agar** Circuits

- Prototype or production quantities
- Fast turnaround available
- PCBs designed from circuit diagrams
- Almost all computer files accepted
- PCB assembly - mechanical assembly
- Full product design-manufacture-test-repair

Unit 5, East Belfast Enterprise Park
308 Albertbridge Rd, Belfast BT5 4GX
TEL 028 9073 8897 FAX 028 9073 1802
info@agarcircuits.com

RADIO COMMUNICATIONS TEST SET

SCHLUMBERGER
STABILOCK 4040 0.4 - 960mhz
In good working order
\$750

ANALOGUE & DIGITAL SERVICES

Unit 1, Aghanloo Ind Est,
Limavady, NI
Tel: 02877764676
john@analogueanddigital.co.uk

SERVICES

POWER SUPPLY DESIGN

Switched Mode PSU
Power Factor Correction
designed to your specification

Tel/Fax: 01243 842520

e-mail: eugen_kus@cix.co.uk

Lomond Electronic Services

WESTDALE ELECTRONICS

We would welcome the opportunity of quoting for your requirements.

If you have a problem with your semiconductors or relays, give us a call and we will locate them for you.

We also have access to Inventory Stateside ie

Current, Obsolete, MII, Spec

Call: Bryan on -

Tel/Fax:

0115 9402127



SERVICES

From Concept To Production

48 HOUR SERVICE

Electronic design and manufacturing services for the new millennium:

- Embedded monitoring & control
- PSTN telephones and test equipment
- Datacom interfacing, line driving etc.
- Switch Mode & linear PSU and battery management
- Gas detection systems
- Printed Circuit Board design
- Technical documentation, schematic layout & language translation
- Wireless telemetry systems
- Audio & Video processing
- GSM telemetry via SMS or data (TCP/IP)
- DVD player control systems
- GPS positioning systems
- Specialist cable looms
- Small, medium & large scale manufacturing

Email: sales@designersystems.co.uk

Tel/Fax: +44 (0) 1872 223306



for more information see our web site @ <http://www.designersystems.co.uk>

PCBs Conv/PTH/Multi-Layer/Flexible • UK & Far East production

- CAD Layout • Electronic Design • Assembly (prototype & production)
- SMD m/c assy @ 18,500 cps/hr

Deliveries from

24 Hrs

Prototype PTH PCBs from just

£40.00


Tel: 01635 40347

Newbury Electronics Ltd
Faraday Road, Newbury Berks RG14 2AQ
Fax: 01635 36143
e-mail: circuits@newbury.tcom.co.uk
<http://www.newburyelectronics.co.uk>

Visit:

www.pcbtrain.com

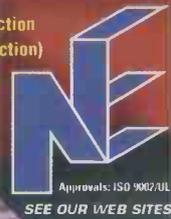The low cost source for prototype PCBs from 1 to 6 layers



WANTED

WANTED Surplus or Obsolete Electronic Components

Turn your excess stock into instant cash!

SEND OR FAX YOUR LIST IN STRICTEST CONFIDENCE

Will collect anywhere in the UK



Mushroom
COMPONENTS

28 College Street, Kempston, Bedfordshire, MK42 8LU

Tel: 01234 363611 Fax: 01234 326611

E-mail: sales@mushroom.co.uk

Internet: www.mushroom.co.uk

Service Link

A thousand applications ONE SOLUTION!

Introducing DataStation™ a 16 Channel, mixed-signal, software-configurable serial I/O controller.

Greater than 500 samples per second, 391 different I/O configurations from one single product!


With up to:

- 6 Analogue Inputs
- Selectable ADC resolution
- 2 PWM Outputs
- 16 Digital Inputs
- 16 Digital Outputs
- RS-232 interface

Typical Applications:

- Machine control
- Industrial automation
- Environmental monitoring
- Robotics

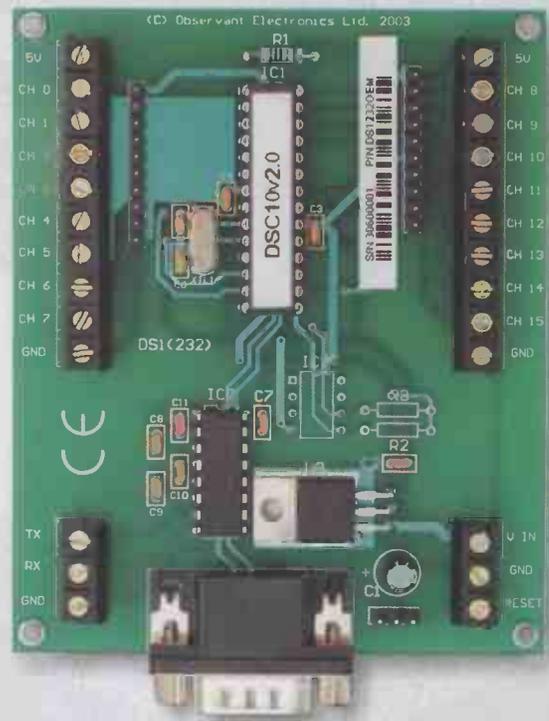This unrivalled flexibility allows designers to meet the needs of virtually any application with just one product, helping to reduce development costs and time-to-market significantly.



£89.00
plus VAT

(Significant discounts for higher volumes)

To find out more or buy online visit: www.ObservantWorld.com



Unit F2b, Avonside Enterprise Park,
New Broughton Road, Melksham,
Wiltshire. SN12 8BS. U.K.

Telephone: 01225 704631

Facsimile: 01225 708618

www.ObservantWorld.com


Email: enquiries@ObservantWorld.com

The Simple Solution!

FlexIt

AVR Controller Development System

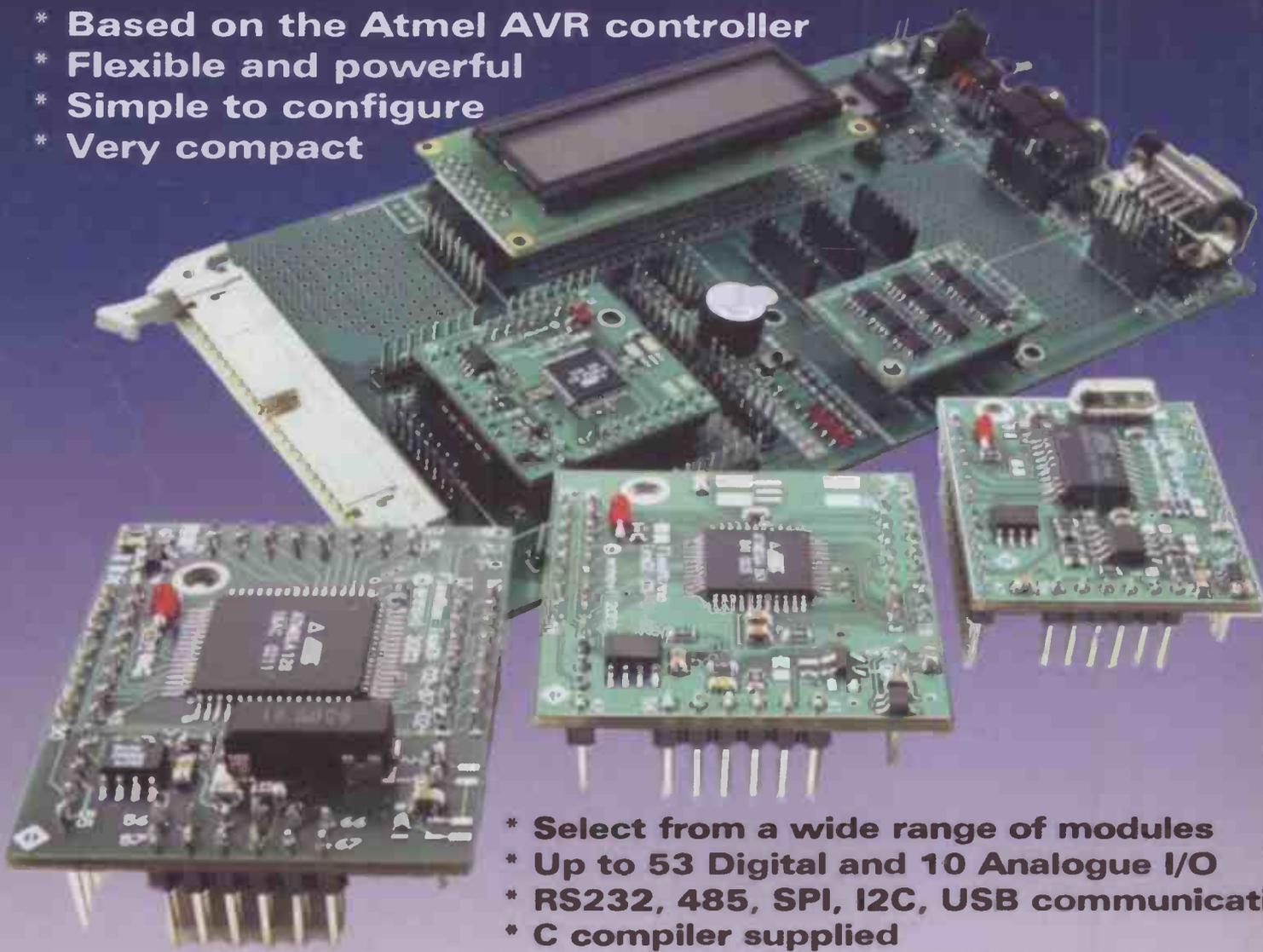- * Based on the Atmel AVR controller
- * Flexible and powerful
- * Simple to configure
- * Very compact



- * Select from a wide range of modules
- * Up to 53 Digital and 10 Analogue I/O
- * RS232, 485, SPI, I2C, USB communication
- * C compiler supplied
- * Compatible with most AVR dev. tools
- * In-system programmable
- * Free Atmel debug simulator available
- * Peripheral drivers and libraries supplied
- * Increasing range of expansion modules
- * Full website support

Check out FlexIt at www.ennovi.co.uk

ennovi Ltd
Dynamic Design

+44 (0)1425 478884
sales@ennovi.co.uk

Precision measurement
Embedded control
Intrinsic safety
Internet embedded systems
USB interface

