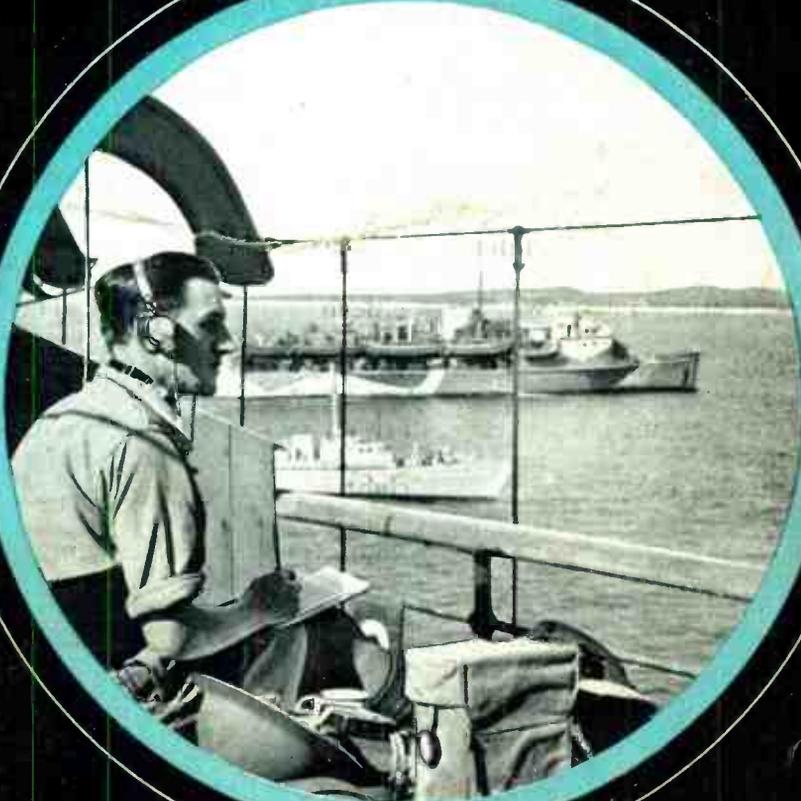


Wireless World

RADIO • ELECTRONICS • ELECTRO-ACOUSTICS



SEPT. 1943

1/3

Vol. XLIX. No. 9

"ASYMMETRICAL" CONTRAST EXPANSION



**T H E R E I S N O S U B S T I T U T E
F O R
E N G I N E E R I N G E X P E R I E N C E**

*

And this is obviously a matter of extent, intensity and time.

Take Electrical condensers for instance—simple in conception maybe—but demanding infinite experience and skill, to satisfy the exacting operating conditions of modern requirements. The fulfilment of these has meant the whole time occupation of highly skilled specialists, working at high pressure, in this way to earn, along with their countrymen in other spheres, the right of survival.

What a wealth of experience and technical excellence will be available to all, when happier times arrive ; and nowhere more than in Dobilier Condensers.

DUBILIER
CONDENSER CO. (1925) LTD.



*Experts and
Experimenters Agree . . .*

for **ACCURACY** rely on

AVO PRECISION
MEASURING
INSTRUMENTS
Regd. Trade Mark BRITISH MADE



The Model 7 Universal AvoMeter (illustrated) is a compact combination electrical measuring instrument of B.S. 1st Grade accuracy. Its 50 ranges cover A.C. and D.C. amperes and volts, resistance, capacity, audio-frequency power output and decibels. No external shunts or series resistances. Protected by automatic cut-out against damage through overload.

Some delay in delivery of Trade Orders is inevitable, but we shall continue to do our best to fulfil your requirements as promptly as possible.

In every sphere of electrical test work . . . in the laboratory, the workshop, the service engineer's bench or "out on a job," . . . the word "AVO" is synonymous with instruments of precision.

The "AVO" range embraces instruments for every essential electrical test. By reason of their reliability and maintained accuracy, even under the most searching of workshop conditions, they are frequently used as a standard by which other instruments are judged.

Write for literature fully descriptive of any "AVO" instrument in which you are interested.

Sole Proprietors and Manufacturers:

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT Co., Ltd., Winder House, Douglas St., London, S.W.1


Telephone: VICTORIA 3404/7

*On all the Seven Seas
Condensers are at work*

TRADE **HUNTS** MARK
The
Home of Condensers

ADVT. of A. H. HUNT LTD., LONDON, S.W.18. EST. 1901

**WHARFEDALE
FACTORY SPEAKERS**

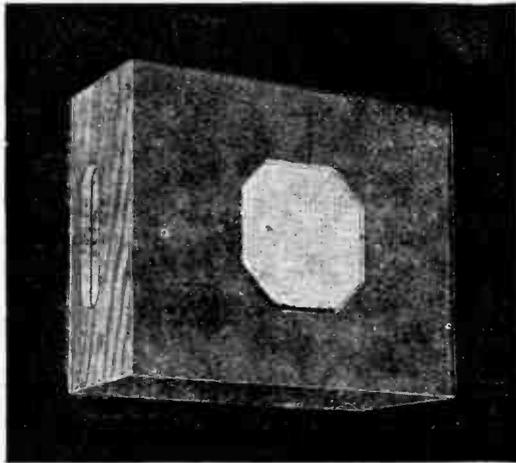

SIZE: 15½" by 12½" by 6½"

DELIVERY 3 to 4 WEEKS for PRIORITY ORDERS ONLY.

With 10" Bronze Unit 65/- Transformer - - - 7/6 extra
 With 10" Golden Unit 95/- Truqual Volume Control 6/6 "
 Remote Volume Control 17/- "

WHARFEDALE WIRELESS WORKS

SOLE PROPRIETOR: D. E. BRIGGS

HUTCHINSON LANE, BRIGHOUSE, YORKS.


PHONE: BRIGHOUSE 50.

GRAMS: "WHARFDEL."

WRITE FOR
CATALOGUE
W.O./330

ADASTRA
RADIO MASTS
POLES LTD TYBURN RD ERDINGTON,
BIRMINGHAM. 24.

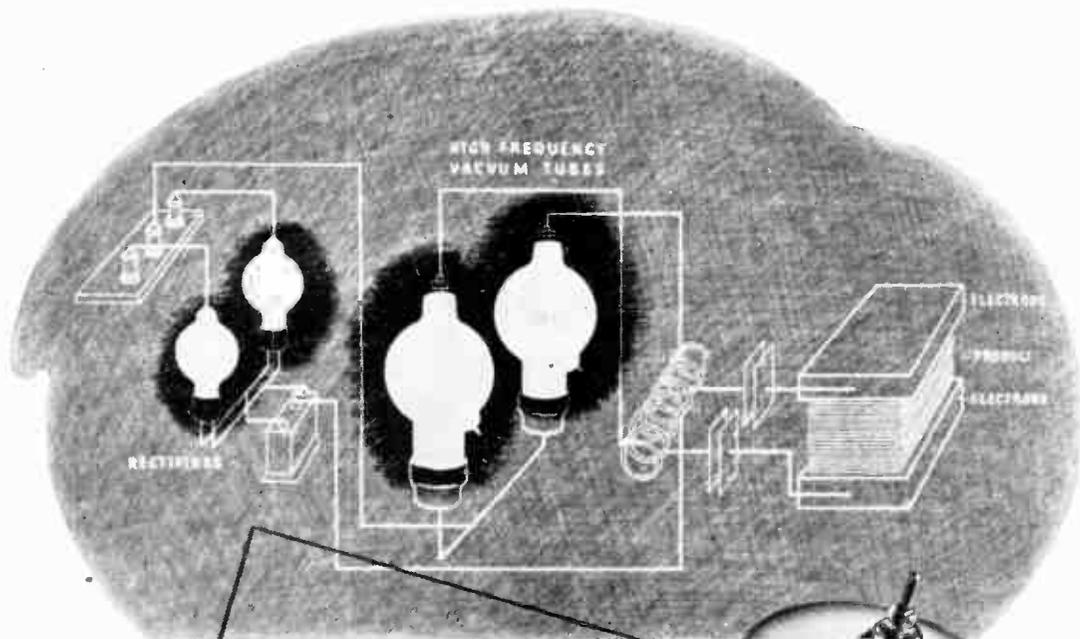Enquiries should be accompanied by Government Priority Reference



ELECTRONIC BRIEFS: Electrostatic Heating


High frequency electrostatic heating is simply the use of electricity to create friction between the molecules of a substance. The generation of heat in non-metallic substances by molecular friction is accomplished by the application of high frequency currents. The equipment used employs the basic electronic circuit used in radio transmitters. The output of the power amplifier is connected direct to the material to be heated exactly as the output of a transmitter is connected to antenna and ground. The energy is sufficient to cause the molecules within the material to distort and rub against one another very rapidly. The friction thus caused creates heat within the material.

As with all things in the field of electronics, Electrostatic heating is wholly dependent upon the vacuum valves employed. Eimac valves are first choice of the world's leading engineers, first in the key sockets of the important new developments in electronics. You'll get long life, dependability and superior performance with Eimac valves in the key sockets. Today Eimac valves are proving their superiority in the most gruelling test—WAR.



EITEL-McCULLOUGH, INC.
SAN BRUNO, CALIFORNIA

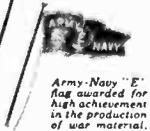Export Agents: **FRAZAR & HANSEN,**
301 Clay St., San Francisco, California, U. S. A.




Follow the leaders to
Eimac
VALVES

SENSITIVITY

IN THE AIR ON THE LAND ON THE SEA UNDER THE SEA

in Electrical Measuring Instruments

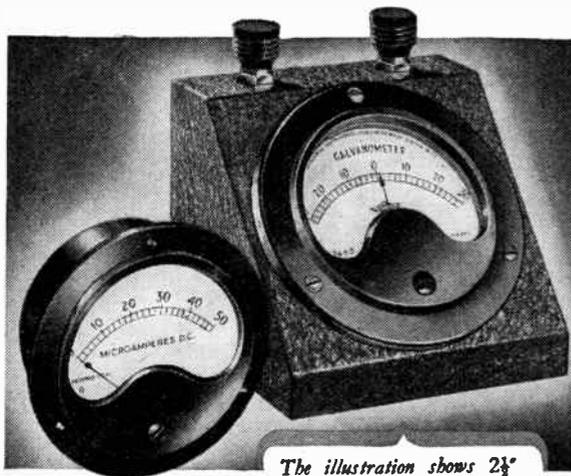The development of plant and apparatus needing highly sensitive indicating devices, is one of the features of modern times. Too often, however, increased sensitivity is obtained at the expense of robustness and consistent accuracy. M.I.P. instruments are designed for the situation that requires sensitivity coupled with long working life.




The illustration shows $2\frac{1}{2}$ " Galvanometer in desk type stand and $2\frac{1}{8}$ " flush type D.C. Microammeter.

Consult us for low-range Milliammeters, Microammeters, and Galvanometers.

**MEASURING INSTRUMENTS
(PULLIN) LTD.**
ELECTRON WORKS, WINCHESTER ST., ACTON, W.3

MALLORY VIBRATORS

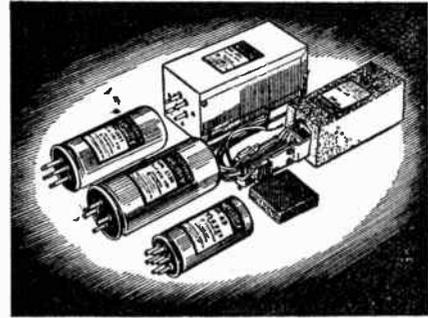

IDEAS WILL POP FOR YOU

In the crucible that is war production, ideas pop into reality in bewildering numbers. Co-operative progress in techniques, in chemical, metallurgical and electrical applications of materials, has contributed astounding gains to man's control over Nature's resources. Comparatively few can have more than a vague notion of industrial accomplishment for the war effort. But the discoveries that have mechanised warfare and conquered the air, that have developed transportation and supplies to marvellous wartime results, represent ideas that will pop into an amazing variety of commercial contributions to post-war living standards.

P. R. MALLORY & CO. INC.
INDIANAPOLIS, INDIANA, U.S.A.
RADIO AND ELECTRONICS DIVISION

Represented exclusively in Gt. Britain by
FRANK HEAVER LTD., Kingsley Road, Bideford, N. Devon, Eng.

**IDENTIFICATION
LABELS** FOR CABLES
& PIPELINES
(M.A.P. APPROVED) AID APPROVAL No 2583/A2

TRANSMITTER

Indelibly printed on white or coloured fabric for use in conjunction with transparent adhesive tape.

• Guaranteed 2/3 day delivery service.

P. P. PAYNE & SONS LTD
HAYDN ROAD NOTTINGHAM Phone: 64335
BUSH HOUSE LONDON Phone: TEMple Bar 6356


THE SYMBOL OF RELIABILITY

We quote (and substantiate on test) figures giving the sensitivity, selectivity and general performance of the "358X" receiver. But this is only half the story. Service requirements dictate the highest reliability, made possible in this receiver by many years experience in the design and production of specialised radio components and apparatus. The continuous reliability exemplified by the "358X" is the outcome of efficient overall design allied with extreme attention to electrical and mechanical detail. Complete technical details available in 30 page Instructional Booklet on "358X" including all circuit values. Price 2/6, post free.

EDDYSTONE '358X'



Communication Receiver

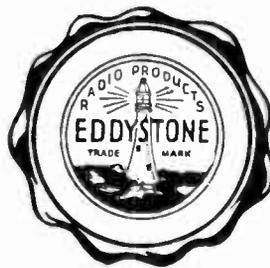

WEBB'S RADIO

14, SOHO ST. OXFORD ST. LONDON W.1. Telephone GERRARD 2089

SHOP HOURS: 10 a.m. to 4 p.m.

SATURDAYS, 10 a.m. to 12 noon.

*British Aircraft
Use*



*FOR QUICKER, EASIER,
CABLE & PIPE LINE MARKING*

DURABLE - LEGIBLE - INDELIBLY PRINTED IN ANY COLOUR
CAN BE USED WITHOUT TOOLS - RESISTANT TO FLUIDS AND HEAT

HERTS PHARMACEUTICALS LTD. WELWYN GARDEN CITY

**WAXES
OKERIN**

AND
DIELECTRIC MATERIALS

Cable, Condenser, Coil, Transformer and Resistance
Impregnating, dipping, sealing, filling and finishing.

A.I.D. and C.I.E.M.E. TYPE AP-
PROVED WAXES to meet both
ARCTIC and TROPICAL conditions.

TELEPHONE : WEST DRAYTON 2189

**ASTOR BOISSELIER
& LAWRENCE LTD**

MIDDLESEX OIL & CHEMICAL WORKS

WEST DRAYTON, MIDDLESEX

ROLA

LOUD
SPEAKERS

THE WORLD'S FINEST REPRODUCERS

TRANSFORMER
LAMINATIONS


Core Widths $\frac{3}{8}$ " to 1 $\frac{1}{2}$ " (E's and I's.)

EIGHT STOCK SIZES

A Comprehensive Bulletin together with details of Associated Covers
and Clamps with design data will be sent to manufacturers on request.

BRITISH ROLA LIMITED

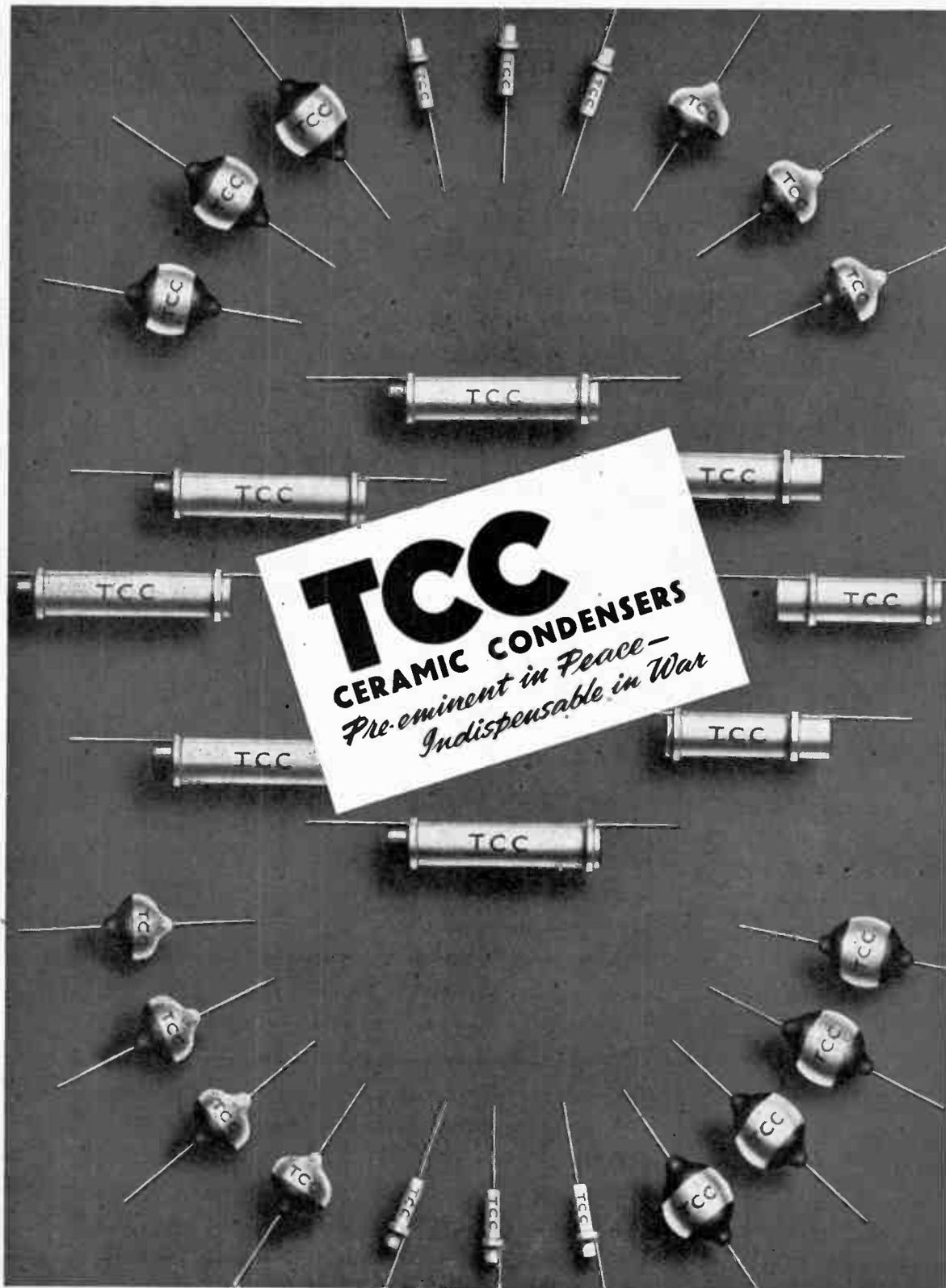MINERVA ROAD · PARK ROYAL · N.W.10 · WILLODEN 4322



ADVERTISEMENT OF THE TELEGRAPH CONDENSER CO., LTD.

The glory of the future..



... when the tank gives pride of place to the "family 'bus" and engines of war to the instruments of peace, Goodmans will be able, once more, to give the connoisseur Loudspeakers that open up new possibilities in high fidelity reproduction.



GOODMANS

Makers of

HIGH GRADE LOUDSPEAKERS

Priority Orders only can be accepted

GOODMANS INDUSTRIES, LTD., LANCELOT ROAD, WEMBLEY, MIDDLESEX

M.R. SUPPLIES

offer from stock the following brand new RADIO, ELECTRICAL and INDUSTRIAL EQUIPMENT of our usual dependable quality. All prices nett cash.

TOGGLE PRESSES (by S.T.C.). Senior and new Minor models here in stock. Double-acting, precise tool, suitable for all small pressing operations in many trades. Senior, weight 30 lbs., pressure 1½ tons, £30 nett. Minor, weight 80 lbs., pressure ½ ton, £23 nett. (Supplied by us to many important users.)

SYNCHRONOUS TIME SWITCHES, 200/250 v. 50 c. Capacity, 10 amps. Precision made, complete movements, without housing. Fitted with removable solar device which automatically adjusts the positions of the riders to switch "on" at dusk and "off" at dawn (or vice versa), with instant pre-set for any month and for B.S.T. and B.D.S.T. This device can be readily dispensed with, if not required, using the two spare riders provided. Full instructions supplied. Self-starting, silent and brand new. 72/6. Also special model in 4in. by 4in. by 5in. weatherproof cast iron housing, same voltage and capacity, with fully enclosed gearing, 97/6. A real opportunity for factory, laboratory and domestic use in process timing, time signalling, blackout warning, alarm clock, switching radio, etc.

LONDEX RELAYS, 200/250 v. A.C. 2-watt coil, with triple-pole change-over 6-amp. high tension switching, 42/6. Also U.S.A. make, enclosed, with 4/12 v. D.C. coil (250 m.a.) with 6-amp. single-pole "make" switch, 6/6.

ROTHERMEL-BRUSH PIEZO-CRYSTAL MICROPHONES. Continuation of our very popular offer of these specially housed D.104 Microphones. Fitted knuckle-joint for angle adjustment and direct-fixing mounting boss (½in. thread). Response level to about 8,000 c/s. Sensitivity—50 db, with about 6in. screened lead, 75/-; Suitable Floor Stands, chromium, folding to 2ft. ext. to 5ft. 6in., 37/6

ROTHERMEL-BRUSH MINIATURE MICROPHONES (Piezo-Crystal). Only 1½in. dia. and capable of very high performance. In aluminium housing with short screened lead but no front grille. Made for deaf-aids but perfect for all other microphone uses, cardiophones, piano and guitar retester, etc., and useful in research dep'ts., 27/6.

TRANSFORMER BOBBINS, Prim. 200/400 v., sec's—350/250 75 m.a., 4 v. 3 a., 4 v., 4 a. Core opening 1½ by 1½in. by 1½in. through. Semi-standard replacement for many sets incl. Marconi, Pye, Lissen, etc. Here is the solution to re-wind problem, 18/6.

BATTERY CHARGER KITS, Comprising S.T.C. 2-amp. Metal Rectifier and appropriate 220/240 v. Mains Transformer, the pair, 32/6. (Or with high-grade 0/2.5 Ammeter by Ferranti, Weston, etc., 59/6.) Diagram supplied.

ROTHERMEL PIEZO-CRYSTAL PICKUPS. Limited delivery of the latest black bakelite model at pre-war price, plus P.T.; total, £3.18.9. Early application advised.

PUBLIC ADDRESS SPEAKERS. Latest model G.E.C. comprising 10-watt P.M. Projector Unit (16 ohms imp.) with built-in line transformer, and 42in. round all-metal Horn, £10.5.0. (Carr. 7/6 extra.) Also G.E.C. INDUSTRIAL SPEAKERS in 9in. metal drum with front and rear grille and built-in multi-transformer, handling 5 watts, 45/- (Packing and carriage, 2/-)

STAGE DIMMERS. Constantly rated and both with carbon break flicker switch and "off" position. For controlling staled load from full bright to blackout at 220/240 v. With screw motion drive and hand-wheel, 1,000 watts, £6.8.0. 1,500 watts, £7.15.0. (Part carr. 5/- in returnable case.)

RAINBOW HEADPHONES, new, 2,000 ohms, with headband, 25/- pair. Also same make, second-hand, 2,000 ohms, 3/9 each single phone.

CENTRALAB VOLUME CONTROLS. Following range only: 5,000, 10,000, 50,000, 250,000, 500,000 ohms and 1 megohm. Less switch, 3/11. With switch, 5/3.

Please include sufficient for postage and packing. Excess refunded.

M.R. SUPPLIES, 68, New Oxford Street, London, W.C.1.


(Telephone: MUSeum 2958)

IMHOF'S • INSTRUMENT CASES • IMHOF'S
IMHOF'S • INSTRUMENT CASES • IMHOF'S


If you use
QUALITY
Instrument
Cases
it's a fine idea to let
IMHOF'S Engineering Division
help you. Priority orders
only just now

Contractors to the Admiralty, Air Ministry, M o S.

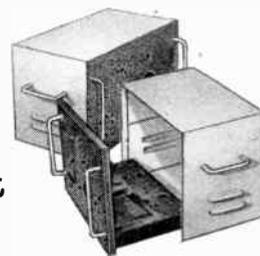IMHOF'S ENGINEERING DIV.
Alfred Imhof, Ltd., 112-6 New
Oxford Street, London, W.C. 1
Telephone: MUSeum 5944



Value proved by long service

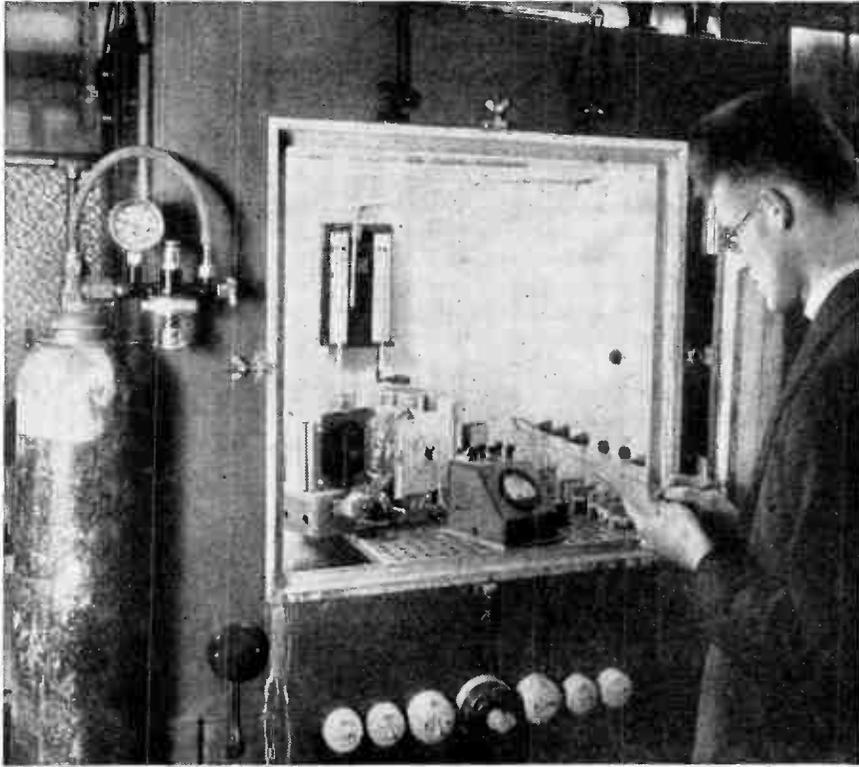

Osram Valves

MADE IN
ENGLAND

Ever since the advent of radio Osram Valves have been closely connected with all the progressive stages of development in radio science. Intensive research still goes on, and improvements in design and technique to keep pace with the advancing times will ultimately be of benefit to all.

Advt. of The General Electric Co. Ltd., Magnet House, Kingsway, London, W.C.2

LONDON CENTRAL RADIO STORES

Please see last month's advertisement on page 12 for

COMPONENTS & ACCESSORIES which are still available

also our classified advertisement on page 27 of this issue.

.....

For future Radio Bargains
—SEE NEXT ISSUE—

Owing to paper rationing the Publishers are unable to give us our usual space this month.

23, LISLE STREET, LONDON, W.C.2

'Phone: GERrod 2969

ROGERS

Postwar industry will be making wider use of industrial electronic technique developed during recent years. In this work Rogers Radio Tubes—the tubes which opened the way to all-mains wireless—have played and will play a recognised part. Rogers with an established reputation for quality, produce all standard types of radio receiving tubes, power tubes for radio transmission, audio frequency amplification and industrial electronic applications generally. At present engaged solely on official work, they look forward to future co-operation over a wide field of industry.

ROGERS RADIO TUBES LTD.

TORONTO (ONTARIO) CANADA

*A subsidiary of BROADCAST RELAY SERVICE LIMITED,
VICTORIA STATION HOUSE, VICTORIA ST, LONDON, S.W.1.*

On National Service WITH... 



**ROYAL ORDNANCE
FACTORIES** ★



**AIRCRAFT
WORKS** ★



**ASSEMBLY
PLANTS** ★



**SCIENTIFIC
INSTRUMENT
MAKERS** ★

... IN FACT, wherever a high-grade light lubricating and penetrating oil is required

THREE-IN-ONE OIL 

is 'on the job'. 301 uses in Factory, Workshop and Office.
Enquiries to:

Sole Manufacturers: **A. S. BOYLE CO. LTD.**, Chenies Street, London, W.C.1
Trade Distributors: **ROLLINS & SONS (Ldn.) LTD.**, 107 Fleet Street, London, E.C.4


War-time installations show more conclusively than ever that

you can

trust

TRIX

30-watt Amplifier with Radio.

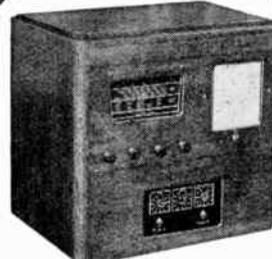

**Quality
SOUND
Equipment**

There are TRIX amplifiers from 5-5000 watts.
Send for details.

To priority order only

TRIX ELECTRICAL CO. LTD., 65, Bolsover St., London, W.1.
'Phone: EUS 5471/2. *Grams: Trizadio, Weedo, London.



SILVERED MICA CONDENSERS



*Overshadow
all others in
quality and
performance*

Incessant progress in methods of manufacture and research linked with the most thorough mechanical and electrical inspection, are reasons for the outstanding superiority of U.I.C. Silvered Mica Condensers. Available in all standardized sizes. Suitable for tropical and arctic conditions. Type approved.

UNITED INSULATOR CO. LTD
 12-22, LAYSTALL ST LONDON, E.C.1
 Tel: TERminus 7383 (5 lines)
 Grams: Calanel, Smith, London

THE PIONEERS OF LOW LOSS CERAMICS

HE WHO SITS BACK

SLIDES BACKWARD



A frank statement
about **ULTRA** service . . .

"An expert is a man who says, 'it can't be done'." The old joke is still alive.

But we are not that sort of experts. Nor, we hope, are you. Between us we have made and sold hundreds of thousands of **ULTRA** sets. Still, it has to be admitted that if we answer "Sorry—impossible" whenever listeners ask for service, the joke will boomerang back upon us.

Let us first make sure there isn't something we can do. **ULTRA** spare parts are coming through—slowly, but they're coming. We can answer questions and make suggestions. Now and then we can accept a set or two for overhaul—perhaps you can, too.

So even the war hasn't absolutely transfixed us. And, when we remember that *anything* more than complete apathy is gratefully received by listeners these days, any sincere efforts we make are sure to keep **ULTRA** as high as it has always been in public estimation. That's how we see the situation—and you will see by our advertisements in the Press, that we have the courage of our convictions—and faith in your support.

**LISTENING
MUST GO ON!**

ULTRA ELECTRIC LIMITED, WESTERN AVENUE, LONDON, W.3



Westinghouse
Rectifiers

for **Outstanding reliability**
Highest efficiency

Performance proved by 17 years'
continuous service all over the World

WESTINGHOUSE BRAKE & SIGNAL'CO. LTD.
PEW HILL HOUSE, CHIPPENHAM, WILTS.

HIVAC
THE SCIENTIFIC
VALVE
BRITISH MADE

Specialists in
**MIDGET
VALVES**

HIVAC LIMITED
Greenhill Crescent,
Harrow on the Hill, Middx.

Telephone: Harrow 0895

◆ LINAGLOW LIMITED ◆

Radios

7-Valve Superhet Receiver—Specification :

3-WAVEBAND 15/52, 200/550, 800/2,000 metres. Separate tone and volume control, gramophone pick-up connections.

Circuit in brief: Triode Hexode Freq. Changer followed by 465KC I.F. Stage which includes a High Efficiency Iron-cored 2nd I.F. Quality Diode Detector feeding Triode Amplifier followed by Phase Inverter and two 6V6 valves in Push Pull giving a Power Output of 8.5 watts. Contained in very well finished walnut veneered cabinet. 200/250 A.C.

Vertical Model, illustrated **29½ guineas**

(Dim. 20in. x 16in. x 10in.)

Horizontal Model **33 guineas**


(Dim. 24in. x 12in. x 11in.)

These radio sets can be heard in our showrooms.

30-Watt P.A. Amplifier.

A High Quality Amplifier, using finest components and Red "E" Valves. Circuit: High Resistance input feed through two separate input sockets or through pre-amplifier socket into two series connected valves with tone and volume control followed by twin valve acting as Amplifier and Phase Inverter feeding into two High Wattage Output Pentodes connected in Negative feed back. Class A B Circuit: 200/250 volts A.C. chassis finished in dark grey. 16 gauge steel. Brand new pre-war manufacture. Amplifier is fitted with Multi Ratio Output Transformer to take from one to forty-four 5,000 ohm speakers also 15 ohm speaker and 600 ohm line. Separate Stand-by Switch.

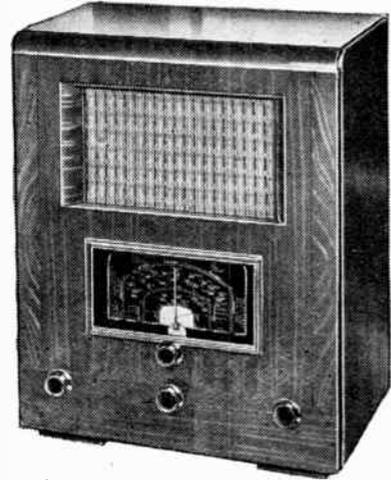Amplifier with valves suitable for gram. microphone and radio inputs **Price \$35 10 0**
 Amplifier with valves and 20in. Horn P.A. Speaker and output transformer **Price \$45 0 0**



VOLTAGE DROPPING RESISTORS AND LINE CORD REPLACEMENTS

suitable for every make of radio receiver, comprehensive ranges mentioned below.

- 950 ohm .2 amp. Chassis mounting, heavy duty on porcelain former, 2 adjustable tapings, 9/8 each; as above, 800 ohm, .3 amp., 8/6 each.
 - .3 amp. 675 ohm, tapped 100, 100, 425 and 50 ohms, suitable for Ekco and other makes, 4/- each.
 - .2 amp. 840 ohm, tapped 100, 100, 475, 115 and 80 ohm, for Ekco, etc., 4/-.
 - .2 amp. 945 ohm, tapped 100, 100, 100, 545 and 100 ohm, for Halcyon, etc., 4/6.
 - .2 amp. 810 ohm, tapped 60, 105, 85 and 260 ohm, for Coeser, etc., 4/6.
 - .2 amp. 680 ohm, tapped 150, 360, 120 and 30 ohm, for Pilot Little Maestro, etc., 4/6.
 - .3 amp. 547 ohm, tapped 80, 80, 387 ohm, for Ferranti, etc., 7/6.
 - .3 amp. 1,014 ohm, tapped 82, 82, 320 and 530 ohm, for Double Decca, 7/6.
 - .3 amp. 781 ohm, tapped 45, 45, 332, 146 and 193 ohm, for Ferguson, etc., 9/6.
 - .3 amp. 823 ohm, tapped 45, 45, 290, 166 and 277 ohm, for Ferguson, etc., 9/6.
 - .3 amp. 680 ohm, tapped 150, 360, 120 and 30 ohm, for Pilot Major Maestro, etc., 8/6.
- SPECIAL HEAVY DUTY RESISTORS**, 5-watt, for bias, etc., all values from 25 to 2,000 ohm, with copper clips, 1/9 each. Similar to above, but 10 watt, 2/3.
- 50 ohm centre tapped Resistor, tapped at 25 ohm, for pilot lamps, 2/-.
- .3 amp. **LINE CORD RESISTOR**, 360 ohm, 6/6; .3 amp. **LINE CORD RESISTOR**, with slider, any resistance obtained up to 750 ohm, 7/8.
- SPECIAL MULTI-LINE CORD RESISTOR**, 5 tapings 50 ohm, 1 tapping 750 ohm, with slider, .2 amp., 8/6.

- RADIO MECHANIC'S TOOLS**. Set of 3 screwdrivers, bright steel shaft, insulated handles, also set of 3 Box Spanners, 2, 4 and 6 B.A. with Tommy Bar, at 10/6 complete set.
- FIXED CARBON RESISTORS**. Wire ends, assorted and useful values. ½-watt, 24/-; ¼-watt, 30/-; 1-watt, 36/- per 100. Minimum orders 50 assorted.
- LINE CORDS**. 3 Way, 360 ohms, 8/6; 480 ohms, 11/-; 600 ohms, 13/6.
- TUBULAR PAPER CONDENSERS**. 350-500 v., D.C. working. .0005, .001, .003, .0008 mfd., 4/- doz.; .001, .0015, .002, .003, .004, 6/- doz.; .01, .025, .03, .05 mfd., 7/- doz.; .08, .1 mfd., 12/- doz.; .15, .2, .25, .3 mfd., 15/6 doz.; .5 mfd., 18/- doz.; or assorted parcel of 50 for 27/6. Minimum orders, 1 doz., any type.

- LOUDSPEAKER TRANSFORMERS**. Philips Pentode 45 m.a., 5/6; Heavy Duty Multi-ratio, 100 m.a., 12/6; Heavy Duty Pentode, 100 m.a., 10/6; Universal Output and Push-Pull, 100 m.a., 12/6; Push-Pull Output, 120 m.a., 15/-.
- MAINS TRANSFORMERS**, 200/250, 350-0-350, 4 v., 6 amp., 4 v., 3 amp., 120 m.a., or 6.3 v., 3 amp., 5 v., 2 amp., 37/6 each.
- LOUDSPEAKERS**. Rola P.M., 3 ohm voice coil without transformer, 5in., 21/-; 6in., 22/6; 8in., 25/6. Any of the above can be supplied with pentode output transformer at 10/6 extra. With multi-ratio at 12/6 extra.
- 5in. GOODMAN P.M. LOUDSPEAKER**. Extra heavy magnet for Midgets and communication Sets. Price 25/6 each.
- DPDT SWITCHES**. Panel mounting, P.O. type, 2/6 each.
- VOLUME CONTROLS**. 5,000, 10,000, 25,000, 50,000, 100,000 ohm; ½, 1, 1 and 2 megohm, without switch, 4/9 each. As above, with switch, 6/9 each.
- CYCLE DYNAMOS**. Complete with brackets for fitting and leads. Special Offer, 18/9 each.
- AUTO-TRANSFORMERS**. Step up or down, 110/210/220/240 v., 100-watt, 32/6.

- VALVES**
LEASE-LEND AMERICAN TYPES AT B.O.T. CONTROLLED RETAIL PRICES. FOR REPLACEMENT PURPOSES ONLY.
- 1H5, 6F6, 6J5, 12P5, 18P5, at 9/2; 1A5, 1C5, 1N5, 1T5, 5Y3, 2A2Z, 3E2Z, 3E2Z, at 11/-; 6Q7, 12Q7, 12SQ7, at 11/7; 1A7, 6F6, 6T7, 6K7, 12K7, 12K7, 12K7, 12K7, 20A6, 25L6, 35L6, 36, 42, 50L6, at 12/10; 6A6, 6X47, 12A8, 12B47, at 14/-; 25A7, 38L7, 70L7, 83, at 15/6. * 6V6 at 12/10.
- Also British Valves at Manufacturer's List Prices. AC/ME, at 10/6; U6, U7, at 11/-; TDD4, at 11/7; AO/VF2, CL4, EF39, KTW61, VP41, at 12/10; AC/TF, BOB3, FC19, X63, X65, at 14/-; KT39C, at 14/8; H236, at 18/6.
- All above prices include Purchase Tax. All Orders taken in Strict Rotation.
- Cash with Order. Add 3d. per valve postage.
- * POST OFFICE PERMIT MUST BE OBTAINED TO PURCHASE THIS VALVE.

- FLAT FLEX**. 8-way, 14/36, 18/20ft. length, suitable for amplifiers, extension speakers, remote control and many other purposes. Finest quality pre-war manufacture, 7/8 per coil.
- I.F. COILS**. 20 hys., 100 m.a., brand new, 16/9.
- ALUMINIUM SCREENED AERIAL COILS**. Bargain Offer, 6 assorted for 15/-.
- WALNUT VENEERED LOUDSPEAKER CABINETS**. Modern design, fitted silk and bafls, 35/-.
- Modern design, fitted silk and bafls, 35/-.
- Modern design, fitted silk and bafls, 35/-.
- VALVE HOLDERS—AMPHENOL TYPE**. International or Maida Octal, chassis mounting, at 1/- each.

- SCREENED INTERLACED FLEXIBLE MICROPHONE CABLE**, Single. Special Offer, 9d. per yd. Pre-war Super Quality, 1/3 per yd.
- HEAVILY NICKEL-PLATED BEST QUALITY BOILING RINGS** on Patent Swivel Base, ideal for anything not in a hurry, 200/250 volts AC/DC, suitable for canteens, hospitals, etc., 21 17s. 6d. Blue cellulose finish, 21 6s., including purchase tax.

SPECIAL OFFER OF SERVICE KITS, as follows :

- No. 1.**—1 8 x 8 mfd. tubular can-type electrolytic condensers, 500 v.d.c.w., 25 assorted silver mica wire-end condensers, 25 assorted ½, 1- and 1-watt carbon wire-end resistors, 25 assorted 1-, 2- and 3-gang I.F. and aerial trimmers. £1 7s. 6d. per kit.
- No. 2.**—3 8 x 8 mfd. tubular can-type electrolytic condensers, 500 v.d.c.w., 100 assorted silver mica wire-end condensers, 100 assorted ½, 1- and 1-watt carbon wire-end resistors, 50 assorted 1-, 2- and 3-gang I.F. and aerial trimmers, 50 assorted wire-end tubular paper condensers, 3 assorted volume and tone controls. £4 12s. 6d. per kit.
- No. 3.**—3 8 x 8 mfd. tubular can-type electrolytic condensers, 500 v.d.c.w., 1 8 mfd. tubular can-type 500 v.d.c.w., 1 25 mfd. x 25 v., 1 50 x 50 mfd. x 12 v., 1 50 x 50 x 2-550 v., 1 32 mfd. 360 v., 1 5 x 5 x 35 v., 200 assorted silver mica wire-end condensers, 200 assorted ½, 1- and 1-watt carbon wire-end resistors, 100 assorted 1-, 2- and 3-gang I.F. and aerial trimmers, 100 assorted wire-end tubular paper condensers, 6 assorted volume and tone controls, 3 lengths 2-way 360-ohm line cord. 28 8s. per kit.
- No. 4.**—12 8 x 8 mfd. tubular can-type electrolytic condensers, 500 v.d.c.w., 4 8 mfd. tubular can-type 500 v.d.c.w., 1 16 x 8 mfd. 550 v. Block, 1 16 x 16 mfd. 500 v., 1 50 mfd. x 20 v., 2 32 mfd. aluminium can-type, 350 v.d.c.w., 1 50 x 50 x 2—15/550 v., 1 5 x 5 x 35 v., 1 50 x 50 x 12 Mallory type condenser, 500 assorted silver mica wire-end condensers, 500 assorted ½, 1- and 1-watt carbon wire-end resistors, 250 assorted 1-, 2- and 3-gang I.F. and aerial trimmers, 100 assorted wire-end tubular paper condensers, 50 assorted wire-end wire-wound resistors, 15 assorted volume and tone controls with and without switch, 1 pentode output transformer, 1 multi-ratio output transformer, 1 push-pull output transformer, 3 rolls insulating tape, 6 assorted line cord replacement resistors, 6 lengths 2-way 360-ohm line cord. 28 10s. per kit.


◆ PLEASE NOTE ◆

Owing to staff shortage and volume of orders we are unable to accept C.O.D. orders until further notice.
CASH WITH ORDER ONLY.
 No pre-forma invoices.

◆ **POST ORDERS** to Dept. M.O.1,
3 HAMPSTEAD LANE, N.6.

◆ **CALLERS** to Show Rooms,
61 HIGHGATE HIGH ST., N.6
 Phone: MOUntrivw 9432.

Ensure the most successful results

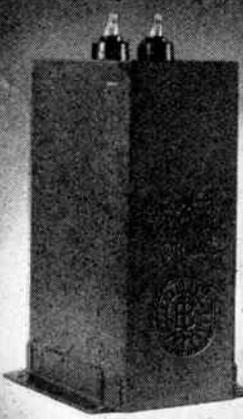

USE

B.I.
CONDENSERS

BRITISH INSULATED CABLES LTD.
Head Office, PRESCOT, LANC. Telephone, PRESCOT 3111.

When they have finished their vital war service



DAGENITE AND **PERTRIX**

—the dependable BATTERIES will again be available to all

FOR RADIO, CARS, MOTOR CYCLES, COMMERCIAL VEHICLES, AIRCRAFT, ETC

Sales Concessionaires: **HOLSUN BATTERIES LTD.**
137 Victoria Street, London, S.W.1.

D10b.

LOOKING AT THEM—



FROM EVERY VIEWPOINT—
these 3 New types of Raymart Valveholders have put the finishing touch to our present-day range of Ceramic Valveholders which for reason, efficiency and service meet all modern requirements.

TYPE VH8
Mazda Octal
1/3 each.


TYPE VA8
International Octal
1/3 each.

TYPE VH9
British "E" type
1/9 each.

Write for further details, or refer to our advertisement on page 24 of June issue. Enquiries invited from Government Departments, Traders and Servicemen. We have a civilian allocation.

RAYMART
48, HOLLOWAY HEAD, BIRMINGHAM, 1
Telephone: Midland 3254.

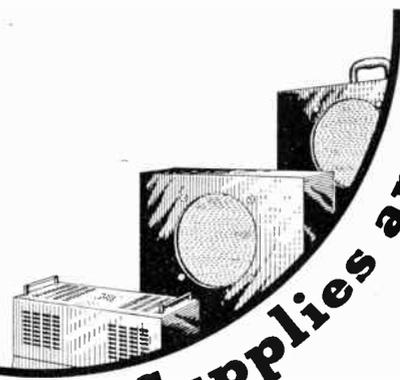Yes! Supplies are cut but not the quality



There is only one thing that is static in the dynamic range of R·S Sound Equipment—its indisputable quality. Progress and experience provide the inevitable improvements in design and technique... urgent demands in many directions curtail supplies. But through it all quality has the last word, which is why we ask you to tell those of your customers who have R·S Sound Equipment to look after it well.—It is not easy to come by. If it is your desire to sell an unusually good Sound System, we will gladly send you fullest details of the very limited range still available in exchange for a penny stamp.

R·S
Amplifiers Limited

3-4, Highfield Road, Shepperton, Middx.
Tel.: Walton-on-Thames 1019.

WHY ERSIN MULTICORE

the Solder wire with 3 cores of non-corrosive ERSIN FLUX is preferred by the majority of firms manufacturing the best radio and electrical equipment under Government Contracts.



WHY THEY USE CORED SOLDER

Cored solder is in the form of a wire or tube containing one or more cores of flux. Its principal advantages over stick solder and a separate flux are :

- (a) it obviates need for separate fluxing
- (b) if the correct proportion of flux is contained in cored solder wire the correct amount is automatically applied

to the joint when the solder wire is melted. This is important in wartime when unskilled labour is employed.

WHY THEY PREFER MULTICORE SOLDER. 3 Cores—Easier Melting

Multicore Solder wire contains 3 cores of flux to ensure flux continuity. In Multicore there is always sufficient proportion of flux to solder. If only two cores were filled with flux, satisfactory joints are obtained. In practice, the care with which Multicore Solder is made means that there are always 3 cores of flux evenly distributed over the cross section of the solder,


so making thinner solder walls than single cored solder, thus giving more rapid melting and speeding up soldering.

ERSIN FLUX

For soldering radio and electrical equipment non-corrosive flux should be employed. For this reason either pure resin is specified by Government Departments as the flux to be used, or the flux residue must be pure resin. Resin is a comparatively non-active flux and gives poor results on oxidised, dirty or "difficult" surfaces such as nickel. The flux in the cores of Multicore is "Ersin"—a pure, high-grade resin subjected to chemical process to increase its fluxing action without impairing its non-corrosive and protective properties. The activating agent added by this process is dissipated during the soldering operation and the flux residue is pure resin. Ersin Multicore Solder is approved by A.I.D., G.P.O., and other Ministries where resin cored solder is specified.

PRACTICAL SOLDERING TEST OF FLUXES

The illustration shows the result of a practical test made using nickel-plated spade tags and bare copper braid. The parts were heated in air to 250° C, and to identical specimens were applied 1/2" lengths of 14 S.W.G. 40/60 solder. To sample A, single cored solder with resin flux was applied. The solder fused only at point of contact without spreading. A dry joint resulted, having poor mechanical strength and high electrical resistance. To sample B, Ersin Multicore Solder was applied, and the solder spread evenly

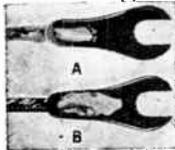

over both nickel and copper surfaces, giving a sound mechanical and electrical joint.

ECONOMY OF USING ERSIN MULTICORE SOLDER

The initial cost of Ersin Multicore Solder per lb. or per cwt. when compared with stick solder is greater. Ordinary solder involves only melting and casting, whereas high chemical skill is required for the manufacture of the Ersin flux and engineering skill for the Multicore Solder incorporating the 3 cores of Ersin Flux. However, for the majority of soldering processes in electrical and radio equipment Multicore Solder will

show a considerable saving in cost, both in material and labour time, as compared either with stick solder or single cored solder. Cored solder ensures that the solder and flux are put just where they are required, and by choice of suitable gauge, economy in use of material is obtained. The quick wetting of the Ersin flux as compared with resin flux in single core resin solder ensures that with the correct temperature and reasonably clean surface, immediate alloying will be obtained, and no portions of solder will drop off the job and be wasted. Even an unskilled worker, provided with irons of correct temperature, is able to use every inch of Multicore Solder without waste.

ALLOYS

Soft solders are made in various alloys of tin and lead, the tin content usually being specified first, i.e. 40/60 alloy means an alloy containing 40% tin and 60% lead. The need for conserving tin has led the Government to restrict the proportion of tin in solders of all kinds. Thus, the highest tin content permitted for Government contracts without a special licence is 45/55 alloy. The radio and electrical industry previously used large quantities of 60/40 alloy, and lowering of tin content has meant that the melting point of the solder has risen. The chart below gives approximate melting points and recommended bit temperatures.

ALLOY Tin Lead	Equivalent B.S. Grade	Solidus C.°	Liquidus C.°	Recommended bit Temperature C.°
45/55	M	183°	227°	267°
40/60	C	183°	238°	278°
30/70	D	183°	257°	297°
18.5/81.5	N	187°	277°	317°

VIRGIN METALS—ANTIMONY FREE

The wider use of zinc plated components in radio and electrical equipment has made it advantageous to use solder which is antimony free, and thus Multicore Solder is now made from virgin metals to B.S. Specification 219/1942 but without the antimony content.

IMPORTANCE OF CORRECT GAUGE

Ersin Multicore Solder Wire is made in gauges from 10 S.W.G. (.128"—3.251 m/ms) to 22 S.W.G. (.028"—.711 m/ms). The choice of a suitable gauge for the majority of the soldering undertaken by a manufacturer results in considerable saving. Many firms previously using 14 S.W.G. have found they can save approximately 33 1/3%, or even more by using 16 S.W.G. The table gives the approximate lengths per lb. in feet of Ersin Multicore Solder in a representative alloy, 40/60.

S.W.G.	10	13	14	16	18	22
Feet per lb.	23	44.5	58.9	92.1	163.5	481

CORRECT SOLDERING TECHNIQUE

Ersin Multicore Solder Wire should be applied simultaneously with the iron, to the component. By this means maximum efficiency will be obtained from the Ersin flux contained in the 3 cores of the Ersin Multicore Solder Wire. It should only be applied direct to the iron to tin it. The iron should not be used as a means of carrying the solder to the joints. When possible, the solder wire should be applied to the component and the bit placed on top, the solder should not be "pushed in" to the side of the bit.



ERSIN MULTICORE SOLDER WIRE is now restricted to firms on Government Contracts and other essential Home Civil requirements. Firms not yet using Multicore Solder are invited to write for fuller technical information and samples.

MULTICORE SOLDERS LTD., BUSH HOUSE, W.C.2. 'Phone Temple Bar 5583/4

Electronic Engineering Services, Ltd.

24 STANLEY ROAD HEATON MOOR
STOCKPORT
TELEPHONE HEATONMOOR 3107

FOR
AMERICAN EQUIPMENT

TRANSMITTERS AND RECEIVERS: A WIDE RANGE OF BOTH A.M. AND F.M. AVAILABLE. SPECIAL U.H.F. HIGH GRADE EQUIPMENT BUILT TO SPECIFICATION.

INSTRUMENTS: TEST GEAR OF NON-STANDARD TYPE BUILT TO SPECIFICATION.

MIDGET COMPONENTS: VALVES, CRYSTAL EARPHONES, VARIABLE & FIXED CONDENSERS, RESISTORS, CHOKES, ETC.

GENERAL: WE WELCOME ENQUIRIES FOR EQUIPMENT AND COMPONENTS UNOBTAINABLE IN THIS COUNTRY.

PRIORITIES ESSENTIAL.

Precisely!



for accurate testing it must be

TAYLOR METERS

Write for complete details to:
TAYLOR ELECTRICAL INSTRUMENTS, Ltd., Montrose Av., Slough, Bucks
Telephone: Slough 21381 (4 lines).

Greenwood

CELESTION



LOUDSPEAKERS

As in the past, so in the future, the highest possible quality of reproduction will emanate from Loudspeakers bearing the name

CELESTION

The Foremost Name in Sound Reproduction.

(At present supplied against Priority Orders only.)

CELESTION LTD.

Acoustical Engineers
KINGSTON-UPON-THAMES, SURREY.

Telephone: KINGSTON 5626-7-8




Audio Amplifiers and Sub-assemblies to critical standards




In addition to Standard Amplifiers the activities of Acoustical include Special Amplifiers for Industrial Applications, Microphones, Transformers, Coil Winding, Sheet Metal Work, Stampings, Switch Assemblies, etc.



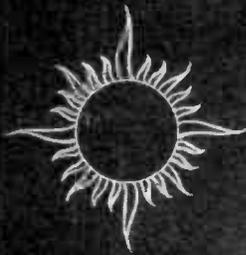ACOUSTICAL
MANUFACTURING Co. LTD.
HUNTINGDON - TEL: 361



SYMBOLS OF PRECISION

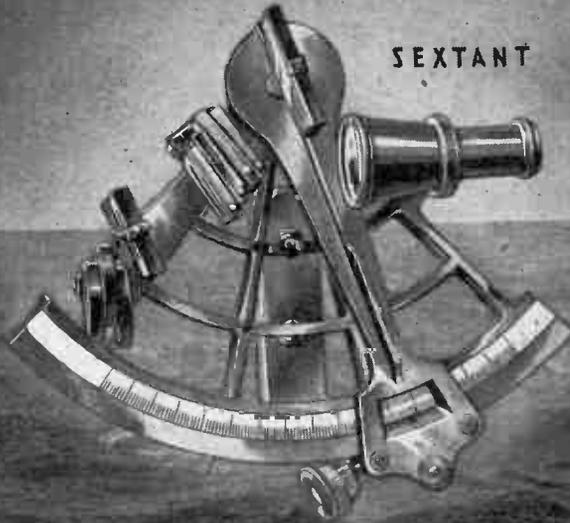

SEXTANT



MAZDA

**RADIO
VALVES**


THE EDISON SWAN ELECTRIC CO. LTD.



155, CHARING CROSS RD., LONDON, W.C.2

For full particulars write to Technical Service Department

B

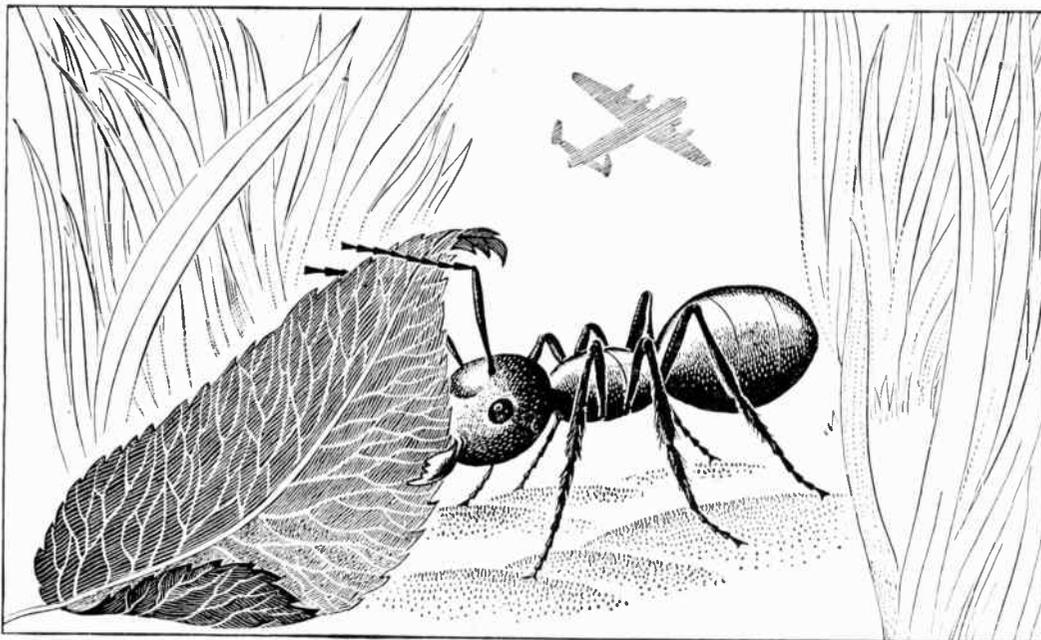

Resource

WE are less industrious than the ant, but more inventive. We have learned to think ahead, and by applying our inventiveness to the anticipated needs of the future we can ensure for mankind a more abundant leisure in the post-war world.

Creative technology is to-day at full flood. The widespread use of Simmonds AEROCESSORIES means that more units of production are being manufactured by fewer people from less material in shorter time. Their continued and expanded use after the war will increase the manifold fruits of industry in the new age.

S I M M O N D S

In high service to
AERONAUTICAL, INDUSTRIAL & MARINE
Construction

THE SIMMONDS NUT · PINNACLE NUT · SPIRE NUT · SIMMONDS INSTRUMENTS,
 CONTROLS AND ELECTRONIC PRODUCTS · FRAM OIL AND ENGINE CLEANER

SIMMONDS AEROCESSORIES LTD.
 GREAT WEST ROAD, LONDON

A COMPANY OF THE SIMMONDS GROUP

LONDON MELBOURNE MONTREAL PARIS NEW YORK

Wireless World

Radio • Electronics • Electro-Acoustics

33rd YEAR OF PUBLICATION

SEPTEMBER 1943

Proprietors :
ILIFFE & SONS LTD.

Managing Editor :
HUGH S. POCOCK,
M.I.E.E.

Editor :

H. F. SMITH.

Editorial, Advertising
and Publishing Offices :

DORSET HOUSE,
STAMFORD STREET,
LONDON, S.E.1.

Telephone :
Waterloo 3333 (35 lines).

Telegrams :
"Ethaworld, Sedist, London."



**PUBLISHED
MONTHLY**

Price : 1/3

(Publication date 25th
of preceding month)

Subscription Rate :
Home and Abroad
17/- per annum.

EDITORIAL. Against Wired Broadcasting ..	255
USE OF VALVES. By J. R. Hughes, A.M.I.E.E.	256
RECORD TRACKING	260
WIDE-RANGE R-C OSCILLATOR. By T. A. Ledward, A.M.I.E.E.	263
CONTRAST EXPANSION UNIT. By D. T. N. Williamson	266
DESIGN OF SIMPLE OHMMETERS—2 By F. Livingston Hogg	269
CALCULATING COUPLING COEFFICIENTS. By S. W. Amos, B.Sc.(Hons.)	272
"WIRELESS WORLD" BRAINS TRUST..	274
RESEARCH AND PRODUCTION	275
NEWS IN ENGLISH FROM ABROAD ..	276
WORLD OF WIRELESS	277
RANDOM RADIATIONS. By "Diallist" ..	280
LETTERS TO THE EDITOR.. .. .	282
RECENT INVENTIONS	286

Branch Offices :

COVENTRY :
8-10, Corporation Street.
Telephone : Coventry 5210.
Telegrams :
"Autocar, Coventry."

BIRMINGHAM :
Guildhall Buildings,
Navigation Street, 2.
Telephone :
Midland 2971 (5 lines).
Telegrams :
"Autopress, Birmingham."

MANCHESTER :
260, Deansgate, 3.
Telephone :
Blackfriars 4412 (4 lines).
Telegrams :
"Iliffe, Manchester."

GLASGOW :
26B, Renfield Street, C.2.
Telephone : Central 4857.
Telegrams : "Iliffe, Glasgow."



As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.

"HYPERLOY"

TRANSFORMERS AND CHOKES

A range of high-performance, space-saving Components designed to meet the most exacting requirements of modern Electronic and Communications equipments.

- Small in size
- Weighing only 2 oz.
- Meeting the most rigid Tropical Specification
- Easily mounted in any position
- Manufactured in a variety of windings to meet many diverse applications


★ Owing to wartime restrictions on supply of raw materials, it is not possible to supply Wearite Components for purposes other than those connected directly with the war effort.

WRIGHT & WEAIRE LTD.

HIGH ROAD, TOTTENHAM, N.17

Telephone: TOTTENHAM 3847-8-9



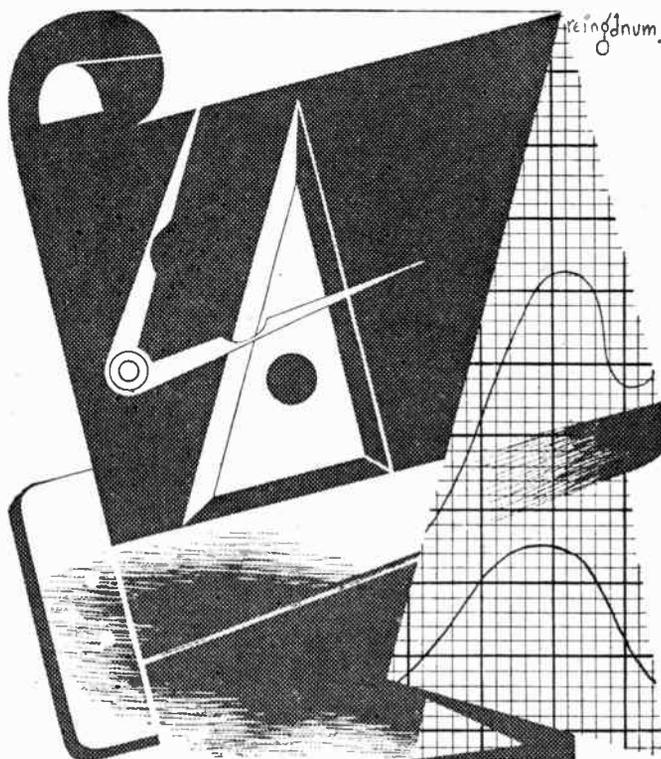

PLANNING

Through the whole wide sweep of Philips activities in the field of electricity there is evidence of inspired planning . . . not for the moment only, but also for those needs which will depend on discoveries and developments yet to emerge from the laboratory and the drawing board.

PHILIPS



INCANDESCENT AND DISCHARGE LAMPS • FLUORESCENT LIGHTING • RADIO RECEIVERS AND TRANSMITTERS • COMMUNICATIONS EQUIPMENT • THERMIONIC VALVES AND OTHER DEVICES • X-RAY EQUIPMENT FOR ALL PURPOSES • ELECTRO-MEDICAL APPARATUS • ARC AND RESISTANCE WELDING PLANT AND ELECTRODES • MAGNETS AND MAGNETIC DEVICES • SOUND AMPLIFYING INSTALLATIONS

PHILIPS LAMPS LIMITED, CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2 (125H)

Wireless World

Radio • Electronics • Electro-Acoustics

Vol. XLIX. No. 9

SEPTEMBER 1943

Price 1s. 3d.

Against Wired Broadcasting

Explaining Our Attitude

LAST month we stated our reasons for opposing the big-scale introduction of wired broadcasting and, since then, have received a large number of letters on the subject. Naturally, most wireless men object to the introduction of a system that threatens the expansion of their technique, and so support our attitude. But a surprisingly large number of readers feel that the technical arguments for the wire are so strong that it should be given a trial. That might come later, but we strongly contend that the immediate post-war period is not the appropriate time to make such a sweeping change. It seems necessary to amplify the reasons already given for this view.

In explaining the attitude of *Wireless World* it would be well to re-state, as concisely as possible, our main grounds for objection. Politically, an isolationist wired system is wrong for a post-war world of which the future is generally thought to depend on international co-operation; also a wired system is, under post-war conditions, too dangerous a weapon to place ready-made in the hands of a possible enemy of our liberties. Remember that Hitler came to power by exploiting mass psychology through the loud speaker, consolidated his power through broadcasting, and then introduced the *Volksempfänger*, which gave him some of the advantages of a watertight distribution system for canalising public opinion. Economically, wireless is not yet developed to such an extent that it can afford to dispense with the stimulus and the financial contributions of radiated broadcasting. It was stated only a few weeks ago that broadcast receivers accounted for 80 per cent. of the output of the pre-war British wireless industry, leaving only 20 per cent. for transmitters and general communication equipment. Any country adopting the wire would fail to keep pace with those retaining radiating systems.

Letters expressing contrary views are published elsewhere in this issue, and we can best substantiate our opinions by replying to specific points.

"There has never been any suggestion that the household set should be 'purged' or that a ban should be placed on foreign listening," says a

reader. Exactly; but if the G.P.O. undertook broadcast distribution over the telephone wires one can imagine that the extent of radio listening would soon become negligible, without any need for a ban. To boost its new venture the G.P.O. would have at its command the B.B.C. microphone, the most powerful instrument of publicity in the country, and the great mass of the public could hardly fail to succumb. The B.B.C. would probably be only too willing to lend itself to the campaign. Indeed, certain sections of the Corporation, remembering with acute discomfort the embarrassment caused by competitive broadcasting from Radio Normandie and Luxembourg, would welcome anything that removed a threat to its monopoly. Incidentally, we would hazard a guess that this broadcasting to Britain from abroad, which also tended to cut across the P.M.G.'s communication monopoly, was responsible for first inclining the official mind towards wired broadcasting.

International Broadcasting

Several readers suggest that there is no essential difference between the present (or even the pre-war) Government control of broadcasting and the control that might be exercised over a wire system. So far as internal broadcasting is concerned, that is true, but, from the international point of view there is all the difference in the world between a watertight wired system and a radiating system, where a turn of the dial can bring in outside opinions not subject to internal control.

Other readers, while admitting our statement that the pre-war public judged its broadcast receivers by their ability to receive distant stations, deny that it made any real use of that facility. That, also, is true, but it is beside the point. What is described as the "magic of distance" started the public interest in radio, and wired broadcasting would be too prosaic to sustain that interest.

The public did not listen consistently to foreign stations because real international broadcasting had hardly begun; it has not yet achieved, as a world unifying force, even a small fraction of what we hope and think it eventually will. •

USE OF VALVES

What is "Good Practice"?

By J. R. HUGHES,

A.M.I.E.E.,

(British Radio Valve Manufacturers' Association)

THE recently issued War Emergency British Standard B.S. 1106 sets out a code of good practice in respect of the use of radio valves; by due regard to its provisions optimum operating conditions and good valve life can be ensured. This article, which is a survey of some of the basic theoretical considerations which form the justification for the Code of Practice, explains the reasons for the recommendations made in the Code.

Only a small part of the Code of Practice deals with the more general and perhaps more obvious aspects of valve use. The major part is devoted to information and advice on specific points, much of which appears not to be generally known or for which the reasons are imperfectly understood.

Valve Ratings.—The manufacturers' published data includes a number of "Ratings" which must be considered as limiting values. It must not be assumed that any one of them may be exceeded because others are not approached. To take as an example a rectifier, the ratings would normally include the maximum input voltage and the maximum DC output current. The use of an input voltage lower than the rated maximum cannot justify a DC output current higher than the rated maximum.

A radio valve is a complicated structure, the design of which must always be a compromise between a number of physical, mechanical and chemical considerations. For instance, the design features which determine the input voltage rating of a rectifier are not the same as those which determine the output current rating. The permissible maximum current may be limited by anode dissipation or by cathode emission or both, whilst the permissible maximum input voltage may be limited by inter-electrode spacing, as well as by the anode dissipation. Evidently then, the different ratings of the

valve are interdependent to some degree, but certainly not interchangeable in any simple manner.

Many valves include among their ratings the maximum frequency of operation. A variety of different factors may call for this rating, such as the eddy-current heating of the valve electrodes and connections, the dielectric loss heating of the glass seal through which the electrode connections pass, the loss of valve efficiency due to transit time (i.e., the time taken by an electron to travel from the cathode to the anode), or, in the case of a mercury vapour rectifier, the time necessary for the ionised vapour to de-ionise. It will be evident that it may be possible in some cases to raise the frequency of operation above the rated maximum if other ratings of the valve are appropriately reduced, whereas in other cases the frequency limit will be an absolute limit which may not be exceeded in any circumstances. Accordingly, the advice of the manufacturer should always be taken when contemplating the use of a valve at a frequency in excess of the rating.

Heater Voltages and Currents.

—The Code of Practice stipulates that in general the heater voltage should not vary more than 7 per cent. each way from the rated value and that in some cases the regulation must be even closer. Moreover, emphasis is laid on the lesser-known requirement that "low heater voltages are as much to be avoided as high voltages. . . ."

In a valve the emitted electrons collect round the cathode to form a space charge. This space charge acts as a kind of reservoir from which the electrons constituting the space current of the valve are drawn. In practice the valve will be designed so that the space current (which is made up of the

anode current and the screen currents if any) will be far below the total possible cathode emission.

The cathode emission, however, is a high-order function of the cathode temperature, which in its turn is a function of the heater voltage. Thus a comparatively small drop in the voltage gives rise to a considerable drop in the cathode emission.

If the valve is, for example, an output valve, the total cathode emission under the reduced temperature conditions may be insufficient to maintain the anode current, and in this event the grid voltage/anode current characteristic will not be linear and distortion will result. In the case of a rectifier, the consequences of too low a voltage are somewhat different but no less serious. Here the decrease of emission will give rise to an increased voltage drop across the valve and this will raise the power dissipated in the valve. The point is considered at greater length later in this article, but it can be said that one consequence of this increased dissipation may be the release of residual gas from the electrodes, and this in turn will result in a still further decrease in emission. Thus a vicious circle is established which will ultimately destroy the valve or its associated equipment. Even if the normal anode current of the valve is fairly small and the total emission is adequate to maintain the anode current, the operation of the cathode at too low a temperature is still undesirable, for another reason.

It should be appreciated that the condition of the cathode coating is largely determined by the processing which takes place in manufacture and that this processing is designed to distribute the active element through the thickness of the coating and in its surface. The maintenance of the emission during the useful life of the valve is dependent upon the surface of the coating being continually replenished by active material migrating to the surface. This migration is dependent upon temperature, and the operation of

the cathode at too low a temperature may result in its rapid deactivation and the consequent shortening of the valve life.


On the other hand, it should not be supposed that the main risk arising from the use of too high a voltage is that the heater may burn out. If the cathode is operated at an unnecessarily high temperature, excessive evaporation (sublimation) of the emissive coating will take place. Not only does this shorten the life of the cathode coating but it results in excessive deposition of the active material upon the grid and other electrodes. Some of the undesirable consequences of such deposition are considered more fully later in this article, particularly in relation to grid emission.

A further point which is often overlooked is the undesirability of connecting valve heaters in series, unless they have been specially designed for this purpose, as, for example, in the case of AC/DC valves. Normally the manufacturer's data will make clear whether a valve is designed for constant voltage or constant current operation, but in cases of doubt it is wise to make specific enquiries of the manufacturer if series operation is desired. If several valves designed for constant voltage operation are connected in series (thus giving the same value of current through all the heaters), and if one should have a resistance slightly greater than the others, the power dissipated in that one heater will be greater. The heater material has a large positive resistance/temperature coefficient, and thus the resistance and hence the temperature, of the heater which is already running hotter than the others, will rise further still. In this way a small percentage change in the supply voltage can result in a considerably larger percentage change in the voltage across one of the heaters which are connected in series across the supply.

Mounting. — The Code of Practice recommends very strongly that valves should be mounted vertically with the base downwards. It is a not uncommon practice to squeeze valves into odd corners by mounting them out of the vertical, and it is also true that in many cases no

apparent harm results. In the case of mercury vapour rectifiers, no exception to the recommendation for vertical mounting is admissible since it is essential that liquid mercury should be prevented from collecting on the electrodes or on the upper portions of the bulb. Even with other valve types mounting out of the vertical is not to be recommended; partly on the grounds of heat distribution, partly because of the risk of electrodes becoming displaced and so causing changes of characteristics, and partly because of the possibility of the valve being more susceptible to vibration and so causing microphonic noise.

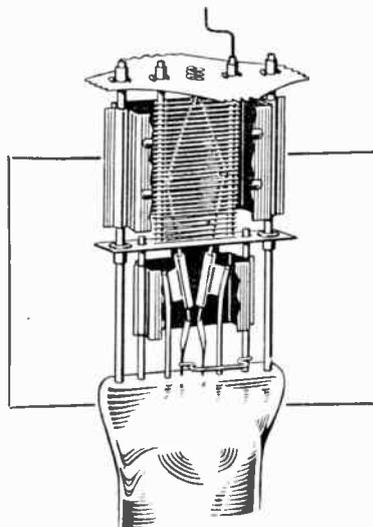Amongst receiving valves, rectifiers or output valves run rather hot and an unequal distribution of the total heat may easily result in part of the valve structure reaching an excessive temperature. One common consequence of running a valve in an inverted position is that the increase in temperature loosens the base.



Part section of a valve employing flat grid structure.

Directly-heated valves with their relatively long and thin filaments are likely to be rather more troublesome so far as electrode sagging is concerned than are indirectly-heated valves where the cathode is of more rigid construction. Valves having a flat grid structure rather than a circular structure may also be more prone to this trouble if the valve is not vertical. In both these cases the difficulty can be mini-

mised by mounting the valve in such a way that the plane of the filament or grid is vertical even if the valve itself is not vertical.

In the case of valves in mobile or portable equipment the arrangement should be such that the valves are vertical when the apparatus is in its usual operating position.

• Heater - Cathode Insulation.

—Indirectly-heated valves with automatic bias or in cathode-follower or phase splitting circuits, provide some examples of applications calling for an appreciable potential difference between the cathode and the heater. BS.1106 deprecates the use of standard indirectly-heated valves in circuits where this potential difference exceeds 100 volts.

The cathode assembly of an indirectly-heated valve consists of a small metal tube on the outside of which is sprayed the emissive coating and inside which the heater wire is inserted. The insulation between the heater and the metal tube is normally effected by spraying the heater with an alumina cement before insertion. It is a relatively thin coating and undue liberties should not be taken with it. In valves specially designed for operation under conditions where a high potential difference is to be maintained between the heater and the cathode, additional precautions are taken during manufacture both in regard to the insulating material and its subsequent processing.

The insulation resistance between the heater and the cathode is dependent upon the cathode temperature and also upon the potential difference and the sense or polarity of this potential. The capacity between the heater and the cathode, too, is a somewhat erratic quantity since the heater is liable to move within the cathode under the influence of temperature changes. For these reasons the heater-cathode impedance should not be included in radio-frequency circuits where high stability is required.

It is worth bearing in mind that one of the consequences of a potential difference between the cathode and the heater may be the attraction of electrons from the cathode coating to the heater. Since the heater normally has an alternating potential applied to it

Use of Valves—

any electron current between heater and cathode may be modulated by this potential and so cause the introduction of hum. It is preferable, therefore, that any potential difference should maintain the heater negative with respect to the cathode, but it should be appreciated that it is similarly undesirable for the heater to be appreciably negative with respect to the grid.

Electrode Temperatures and Gas Release.— With the exception of mercury vapour rectifiers and a few other special valve types the majority of radio valves are "hard," i.e., the bulb contains the minimum of gas. If gas enters the bulb or is freed from within the bulb, the valve is said to have gone "soft" and the effect on the valve's characteristics will be very great indeed. These effects arise from the gas molecules being broken up as the result of collisions between them and the electrons flowing in the normal way from the cathode to the anode. The gas is then said to be ionised and there will be present ions carrying positive or negative charges. Many of the positive ions move to the cathode, and under the influence of the potential existing between the anode and the cathode their velocity when they arrive at the cathode may be sufficient to cause considerable damage by the bombardment of the emissive surface. Apart from this point the mere presence of positive ions in the vicinity of the cathode has the effect of partially neutralising the space charge and the effect of this will be to increase the anode current which, as we shall see, may result in the release of further quantities of gas.


It is very exceptional for gas to be able to enter a "hard" valve as a result of any sort of leakage, but the valve electrodes and the electrode supports are metallic and will contain a certain amount of occluded gas which may be driven from "solution" by an excessive increase of temperature.

This point is taken care of in fixing the valve ratings, and several of the recommendations in the Code of Practice are also based upon it. For instance, the Code emphasises the need to avoid the use of valves "... as oscillators or under any other circuit conditions which result in appreciable grid current unless such a requirement is covered by the specification. . . ." The grid current referred to here is, of course, the so-called "grid positive current" formed by a flow of electrons from the cathode to the grid when the instantaneous grid potential is allowed to become positive, or insufficiently negative, with respect to the cathode. This grid current necessarily dissipates power at the grid and the consequent rise in temperature of the grid may result in gas release. Moreover, apart from the temperature rise, the bombardment of the grid by the arriving electrons may also contribute to the release of occluded gas from the grid surface.

Control of Screen Voltage.— The avoidance of gas release is also one of the explanations of another interesting recommendation

recommendation in question reads: "It is desirable that the resistances used in the supply network for voltages on screen grids of multi-electrode valves should be kept as low as possible. Aligned grid valves operating with the screen voltage substantially lower than the anode voltage should derive the screen supply from a potentiometer network. Unaligned grid valves, other than frequency changers, may derive the supply by means of a series resistance."

Small manufacturing variations in the positioning of the electrodes in aligned grid valves result in rather wide variations of screen current from one valve to another. Thus the replacement of a valve in a circuit where the screen supply was derived through a series resistance rather than from a potentiometer might cause the screen voltage to depart greatly from the designed value. This would cause a marked change in performance and the rise in anode current might result in raising the anode temperature to a value at which appreciable gas release takes place. Unaligned grid valves employing a suppressor grid are not normally so critical in this respect.

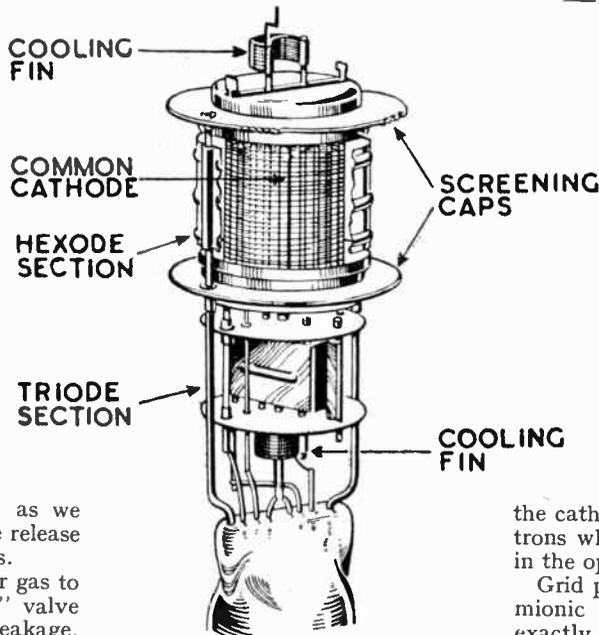

Illustrating the use of grid cooling fins in a representative triode-hexode frequency changer.

Grid Primary Emission.

—In any simple consideration of the operation of a radio valve, it is assumed that the cathode is the sole source of the electron stream. Ideally, the control grid of a valve when operated under "Class A" conditions would neither collect nor lose electrons, and the input resistance of the valve would be infinity. In practice these simple conditions do not hold exactly and the valve electrodes other than the cathode can and do emit electrons which produce irregularities in the operation of the valve.

Grid primary emission is a thermionic emission occurring in exactly the same way as, but fortunately to a much lesser degree than, the thermionic emission from the cathode. It will be appreciated that the valve grids, and more particularly the first or control grid, are heated by ther-

in BS.1106, which is probably very far from generally known. The

mal radiation from the cathode and that this effect is increased by reflection and radiation from the surfaces of the other electrodes. The resultant grid temperature under certain conditions may be sufficient for appreciable electron emission to take place.

Since grid primary emission is thermionic in character, its prevention or reduction is evidently in part a question of grid cooling. The valve will have been designed in such a manner that, under the conditions permitted by the ratings, the grid or grids will operate at a temperature at which grid primary emission is not troublesome. The cooling of the grid is effected partly by conduction through the grid supports and partly by radiation from the grid or from special cooling fins which may be provided. The efforts of the valve designer will be defeated if a valve is used under conditions where more heat is dissipated on the grid than has been allowed for in design, and this adds further weight to those clauses of the Code of Practice which are concerned with the avoidance of the use of valves under conditions where electrode temperatures may rise unduly.

It was mentioned, earlier in this article, that an excessive cathode temperature could result in the evaporation (sublimation) of the emissive coating of the cathode and its deposition upon the other electrodes of the valve. If a grid becomes contaminated the possibility of primary emission is very greatly increased since the contaminated surface has a greater thermionic emissivity than the original clean metallic surface.

The electrons so emitted will tend to pass to an electrode carrying a more positive potential. In general, this electrode will be the anode, but in any event the stream of electrons leaving the grid will constitute a current which, under the normally accepted convention, flows from the grid to earth through the external path. Such grid current is called "grid negative current" to distinguish it from the "grid positive current" which flows from earth to the grid through the external path whenever the grid potential permits the collection of electrons from the cathode stream.

This flow of grid negative current may set a limit to the resistance which may be connected between the grid concerned and the cathode, since the flow of grid negative current through the external resistance gives rise to a voltage drop which, in the case of a control grid, would offset the bias potential by a value proportional to the external grid resistance. This point explains the necessity for keeping such external resistance as low as possible.

Although it does not occur as a result of grid primary emission, it is necessary to consider here the case of grid negative current arising from another cause, and generally referred to as "gas current." It has been mentioned already that a small residual quantity of gas may be present in the bulb and further gas is liable to be released by an increase in temperature of the valve electrodes. Collision between the electrons from the cathode and gas molecules results in ionisation of some of the latter, which become positively charged and will travel to the grid and other negatively charged surfaces. The arrival of positively charged ions at the grid can be regarded as constituting a grid negative current comparable with the loss of electrons from the grid. It has already been pointed out that the flow of grid negative current offsets the bias potential on the valve to an extent determined by the external resistance of the grid circuit. The reduction of bias voltage increases the anode current and this will raise the temperature of the anode. A vicious circle may therefore be established in which the flow of gas current in the grid circuit causes an increase in temperature of the anode and so results in the release of more gas and consequently in an increase in the gas current itself. This danger of the valve "running away" is obviously dependent upon the external grid resistance and may be avoided by ensuring that this resistance is as small as possible.

These considerations requiring a low external resistance apply equally to all valve grids, but the Code of Practice is more specific in the case of the first or control grid and quotes recommended maxima which should not be ex-

ceeded. For voltage amplifying valves, the figures are $1M\Omega$ when automatic bias is used and $0.5M\Omega$ with fixed bias, but in the case of output valves having an anode dissipation of 10 watts or over, these limiting resistances are still further reduced to $0.5M\Omega$ when automatic bias is used and $0.1M\Omega$ with fixed bias. Output valves generally run rather hotter and have a larger grid surface, and for these reasons grid emission is likely to be greater and the external resistance must be correspondingly reduced.

The distinction which is made between the permissible external grid resistances with automatic bias and with fixed bias arises from the fact that, as mentioned already, the flow of gas current offsets the bias potential and, in turn, may bring about a still further increase in gas current. If, however, automatic bias is used, the increase of anode current arising from the offsetting of the bias voltage will cause a compensatory increase of bias voltage. Because of this the conditions are more stable than when fixed bias is used, and the employment of larger values of grid resistance is justified.

(To be concluded.)

AMERICAN AMATEUR'S HANDBOOK

THOUGH the handbook issued annually by the American Radio Relay League is primarily intended for the amateur transmitters that constitute the membership of the League, it has, in the course of the 20 years of its existence, tended to reach an ever-widening public. The 1943 edition, which has expanded to 600 pages, is useful as a source of information on many technical matters besides those primarily affecting the amateur.

The "Radio Amateur's Handbook" may be briefly described as a non-mathematical general textbook of the theory, design and operation of wireless communication equipment, plus much specialised information for the amateur transmitter. Copies are obtainable to order (price 10s. 6d) through the Radio Society of Great Britain, New Ruskin House, Little Russell Street, London; W.C.1.

RECORD TRACKING

Weight Required to Keep the Needle in the Groove

THERE is general agreement among gramophone quality enthusiasts that a light needle-pressure is desirable from the point of view of reducing wear on the surface of the groove and thus preserving the low noise level of the newly pressed record. In the early days a weight of 5 oz. was regarded as the minimum which would ensure adequate tracking and prevent the needle from riding up the sides of the groove. This was equivalent to a pressure at the needle point of the order of 30 tons per square inch, and it is not to be wondered at that records showed distinct signs of deterioration after only one playing.

Excessive mass and damping of the moving parts in the older pick-ups was undoubtedly the chief reason for this unsatisfactory state of affairs, and designers soon turned their attention to the

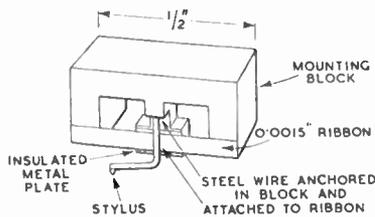


Fig. 1. General construction of frequency-modulation pick-up.

problem of lowering the lateral mechanical impedance at the needle point. Miniature needle-armature and moving-coil systems made their appearance, and the average weight required for tracking fell to about 1½ oz. (40 grams).

Needle-point impedance is not the only factor determining the downward pressure; the form and fit of the groove and needle profiles are of equal importance. It is for this reason that experiences differ and controversy still centres on the relative merits of light and heavy pick-up heads, spring or counterbalance adjustment of pressure, etc.

A useful contribution to our knowledge of this subject comes from a recent paper by Beers and

Sinnett.* In the course of an investigation into the possibility of using a frequency-modulated system of record reproduction the authors developed a miniature


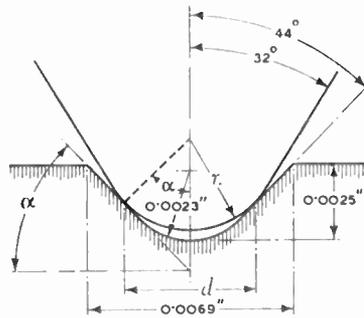


Fig. 2. Section of stylus in record groove showing tracking diameter d and wedging angle α .

variable-capacity pick-up (Fig. 1) and the following facts were given in justification of a choice of 0.003in. for the radius of the sapphire stylus.

For proper tracking the stylus must have sufficient vertical force exerted upon it to overcome the vertical component of force due to the lateral velocity of the modulated record groove. Calculations have been made which show the vertical forces exerted upon styli of various radii when seated in a standard groove having an 88-deg. included angle, a 0.0023in. radius cutting stylus and a groove width at the top of 0.0069in. In addition to the vertical forces, consideration has also been given to the variations to be expected in pinch effect with different sizes of reproducing styli.

Fig. 3. Variation of tracking diameter and wedging angle with radius of stylus.

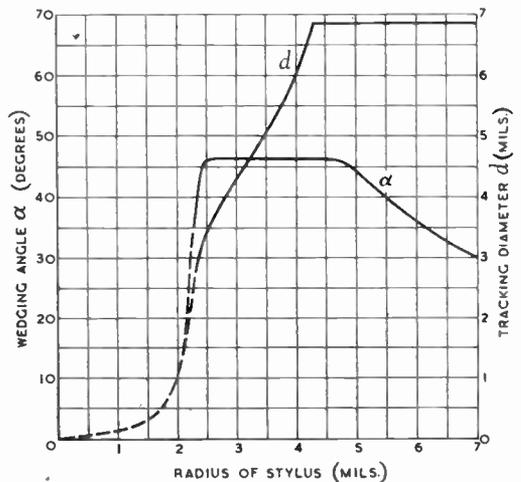

*"Some Recent Developments in Record Reproducing Systems" by G. L. Beers and C. M. Sinnett. *Proc. I.R.E.* Vol. 31, April 1943.

Fig. 2 illustrates a stylus seated in a record groove of the above dimensions. Two important factors which change with the diameter of the stylus are: the tracking diameter d and the wedging angle α . Tracking diameter d has a direct bearing upon both pinch effect and the high-frequency response and should be kept as small as possible. On the other hand, wedging angle α which determines the tendency of the stylus to climb the groove wall, should be made as large as possible for a specified groove. From this it is obvious that a compromise must be made. Fig. 3 shows the variations in d and α with stylus radius; and from observation it can be seen that the stylus radius should not be less than 0.0025in. or greater than 0.0042in. Furthermore, since the curve for angle α is flat from a stylus radius of 0.0025in. to 0.0042in. and the curve for diameter d is rising rapidly over this range it appears desirable, when record-groove variations are considered, to use a stylus radius of about 0.003in. The importance of the tracking diameter d and the wedging angle α is further emphasised by the curves in Fig. 4. This figure shows, in curve form, the two factors $\cot \alpha$ and $d \tan \alpha$, which have a direct

bearing upon the vertical force due to lateral velocity and pinch effect, respectively. It will be

observed that the curve for $\cot \alpha$ approaches infinity for a stylus smaller than 0.0023in. radius, decreases rapidly to about 0.0025in. radius and then remains essentially flat to 0.0042in. At the same time, however, $d \tan \alpha$, the factor governing the pinch effect, increases rapidly from a 0.0023in. radius to a 0.0042in. radius and then decreases. Observation of these two curves provides a further confirmation that a stylus radius of 0.003in. is the best compromise from the standpoint of overall performance.

Z_L = impedance of stylus and pick-up moving system in a lateral direction.


v_L = velocity of recording.

α = angle at which stylus would ride up groove wall.


Utilising the above equation and the previously determined values for the lateral impedance and the curve for angle α , it is possible to calculate the tracking weight required to overcome the vertical force due to

mentioned were not included in the calculations, the curve shapes are similar, indicating that the choice of a 0.003in. stylus is a desirable compromise. . . .

Fig. 6 shows the tracking weight required for a frequency-modulation pick-up as compared

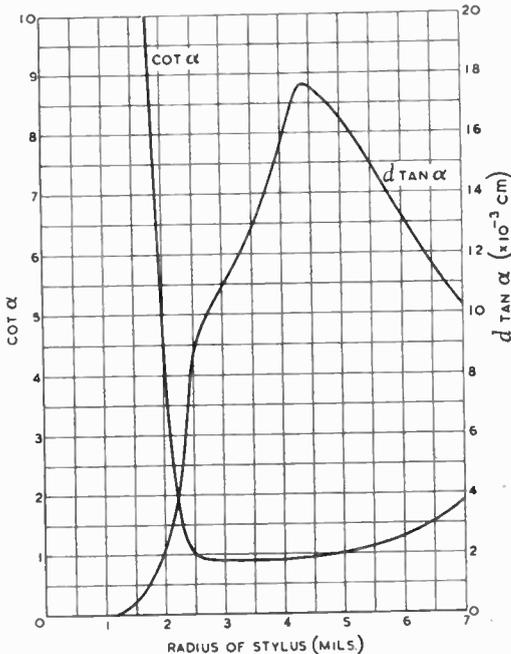

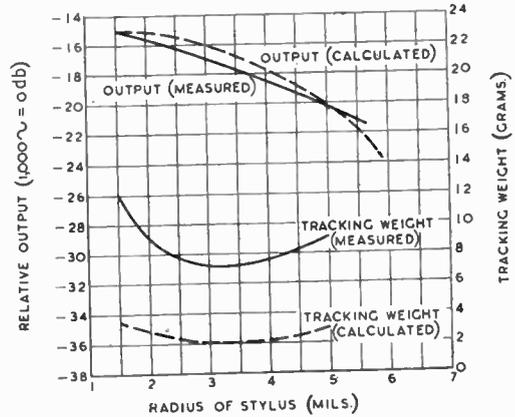(Left) Fig. 4. Effect of stylus radius upon factors governing tracking weight and "pinch effect."



(Above) Fig. 5. Calculated and measured tracking weights required by and relative outputs obtained from frequency-modulation pick-up for a wavelength of 0.0053 inch at 7,000 c/s.

with three other types of phonograph pick-ups. Curve (A) is a conventional crystal pick-up having a normal tracking weight of 70 grams. Curve (B) is a transcription-type magnetic pick-up with a normal tracking weight of 45 grams. Curve (C) shows the tracking-weight characteristic of a recently developed crystal pick-up which operates at a normal tracking weight of 28 grams and curve (D) shows the tracking-weight characteristic of the frequency-modulation pick-up normally operated with a tracking weight of 18 grams."

A few remarks on the nature of the "pinch effect" referred to in the foregoing extract may not be out of place here. It arises from the fact that commercial record masters are cut with a chisel-shaped stylus which vibrates with its flat forward face always at right-angles to the mean axis of the record groove. As a result, the width at the top of the groove, and consequently the angle between the walls of the groove, is reduced when the cutter is in lateral motion—the faster it moves sideways the narrower the groove. Maximum groove width in a sine wave is found at the peaks when the lateral motion is momentarily zero, and the minimum width appears half-way between these points as the cutter is passing the mean position with peak lateral

In the above equations and those which follow, such factors as the elasticity of record materials and the effective damping of the mechanical system are not included. For this reason the calculated performance characteristics do not provide all the information that might be desired, but they do give a general indication of the performance which can be expected. Expressed mathematically, the conditions for tracking a laterally cut record exist when

$$E_v = Z_L v_L \cot \alpha$$

where

E_v = minimum vertical force acting on the stylus which will ensure proper tracking.

lateral velocity as the stylus radius is varied.

As the stylus radius is increased, it is apparent that for a given groove velocity the output to be obtained at high frequencies will decrease. Calculations have been made of the expected loss in high frequencies and Fig. 5, shows the correlation between calculated and measured loss in response at 7,000 cycles as the stylus radius is increased. Also shown in the same figure are calculated and measured curves for the tracking weight required for different styli at 7,000 cycles. It will be noted that while the actual weights required are somewhat higher than the calculated values, because the factors previously

Record Tracking—

velocity. Fig. 7 shows a plan view of a groove of exaggerated amplitude to make this point clear. The sections are enlargements to scale of the groove shape at minimum and maximum width and show the lift imparted to the needle point.

The vertical needle movement passes through a complete cycle between the two peaks (half a wavelength) of the original lateral wave so the frequency of the vertical movement is twice that of the recorded frequency. Obviously the mass of the pick-up head will not permit it to follow this "hill-and-dale" motion, and if the needle suspension is "solid" in a vertical direction, the needle will either plough the groove out to a constant width or remain floating in a mean position, not having time to fall into contact with both walls between the lifts it receives from successive pinches.

The effect is greatest near the centre of the record, where the vertical vibrational velocity may rise to nearly half the lateral velocity at high frequencies. On the other hand, the amplitudes involved are small, so that the range of movement required is less than that which must be allowed for in a lateral direction. It is essential, however, that the vibrational impedance to vertical motion should be kept low.


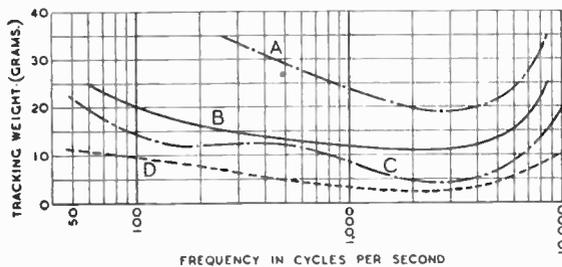


Fig. 6. Comparison of tracking weights required for various pick-ups. (A) Conventional crystal pick-up. (B) Transcription type magnetic pick-up. (C) Special crystal pick-up. (D) Frequency-modulation pick-up.

In the pick-up in Fig. 1 the requisite vertical compliance is provided by bending of the bottom horizontal portion of the steel wire, while the lateral compliance is due partly to bending and partly to torsion of the vertical part to which the ribbon is attached. Changes in capacity between the ribbon and the insu-

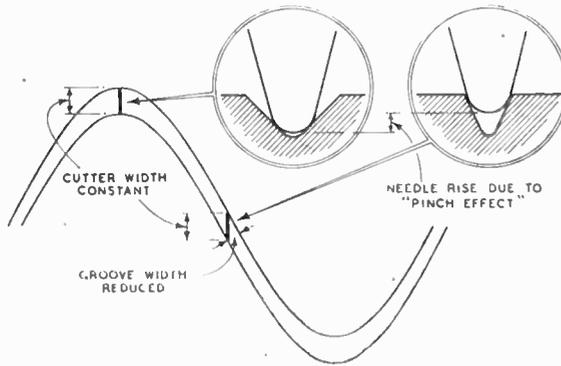lated metal plate are made to vary the frequency of a 6SA7 type electron coupled 30 Mc/s oscillator. A simple resonant circuit is used to convert the oscillator frequency variations to amplitude modulation, the circuit being tuned so that the mean oscillator



frequency falls at the 70 per cent. response point on one side of the resonance curve and the output applied to the diode of a 6R7 valve the triode section of which also supplies the first stage of AF amplification.

The change in diode current is proportional to the displacement of the stylus, and in this respect the system described differs fundamentally from other pick-ups which give an output proportional to the RMS velocity of the stylus. As a consequence, the response characteristic taken with a standard gliding tone test record shows a response level up to 500 cycles and then falling steadily at a rate of about 4 db per octave. Treble compensation would be required in place of the usual bass lifting circuit if the system is to be used on existing records, and the authors point out that to obtain the fullest benefit from the system, records "with a high-frequency accentuation characteristic which is comparable to that used in transcriptions" are desirable.

They conclude: "Experimental records of this type have been

made. The surface noise obtained from these records with the frequency-modulation reproducing system was reduced to the point where it was not objectionable to the most critical listeners.

Although the calculations and measurements which have been given are confined primarily to 78 revolutions-per-minute records, the same performance advantages are retained in a frequency-

Fig. 7. Illustrating the origin of the "pinch effect."

modulation reproducing system designed for transcriptions."

PHONETIC ALPHABET

For British and American Forces

THE combining of the British and American Forces in a growing number of theatres of war necessitated the revision of many of the rules of procedure in wireless telegraphy and telephony.

For obvious reasons it is not permissible to publish the various changes introduced. It is, however, possible to give the revised phonetic alphabet now used by the Allied Forces to avoid confusion between similarly sounding letters in telephony.

In the first column are the new code-words, those in the second column were the most frequently

A	Able	America	Able
B	Baker	Boston	Boy
C	Charlie	Canada	Cast
D	Dog	Denmark	Dog
E	Easy	England	Easy
F	Fox	France	Fox
G	George	Germany	George
H	How	Holland	Have
I	Item	Italy	Item
J	Jig	Japan	Jig
K	King	Kentucky	King
L	Love	London	Love
M	Mike	Mexico	Mike
N	Nan	Norway	Nan
O	Oboe	Ontario	Oboe
P	Peter	Portugal	Pup
Q	Queen	Quebec	Quack
R	Roger	Radio	Rot
S	Sugar	Santiago	Sale
T	Tare	Turkey	Tare
U	Uncle	University	Unit
V	Victor	Victoria	Vice
W	William	Washington	Watch
X	X-ray	X-ray	X-ray
Y	Yoke	Yokohama	Yoke
Z	Zebra	Zanzibar	Zed

used by British amateurs prior to the war, while the third column gives those used by American amateurs.

WIDE-RANGE R-C OSCILLATOR

From 16 to 18,000 c/s with Nearly Constant Amplitude

AN audio-frequency oscillator based on the multivibrator circuit, with modifications to give sine wave output, was described by the writer some years ago* and different forms of RC oscillator have been developed by others. A careful consideration of the principle of operation of the writer's original circuit has enabled him greatly to improve the practical form of this oscillator while retaining, in essential details, the simplicity of the basic circuit.

The oscillator in its new form gives a continuous frequency range in three stages, covering 16 c/s to 18,000 c/s with nearly constant amplitude.

The basic circuit of this type of oscillator is shown in Fig. 1. It will be seen that this is a 2-valve resistance-coupled amplifier circuit in which the second valve is coupled back to the first as in a multivibrator, but the amount of feedback is controlled by means of a potentiometer R₂ and there is a resistance R₁ in series with the grid of V₁. This resistance R₁, while it forms no part of the ordinary multivibrator circuit, is an essential element in the present AF oscillator, as will be seen from the explanation which follows.

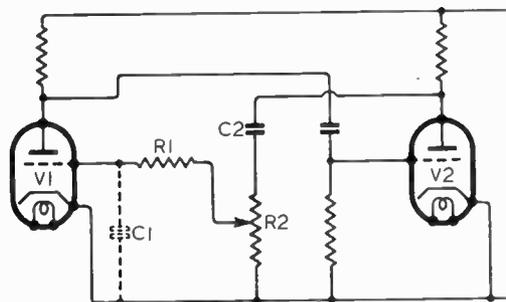


Fig. 1. Basic circuit of the oscillator.

Fig. 2 shows the feedback section of the circuit of Fig. 1. The oscillation frequency is determined by the values of the two condensers and two resistances shown in Fig. 2. R₁ is the resistance in series with the grid of V₁, while C₁ is the total capacitance across the grid and cathode, including the effective internal

By T. A. LEDWARD,
A.M.I.E.E.

capacitance due to the Miller effect. C₂ and R₂ form the output circuit of V₂.

Fig. 3 (a) is the vector diagram of voltages for the input circuit of V₁, E₀ being the applied voltage derived from the output circuit of V₂. E_{R1} is the voltage drop in the grid series resistance R₁, and E_{C1} is the voltage across the grid capacitance C₁, or, in other words, the true grid voltage of V₁.

The forward coupling from V₁ to V₂ is so designed that the phase angle between the anode voltage of V₁ and the grid voltage of V₂ will be negligibly small at all frequencies within the range of oscillation required. Then the anode voltage of V₂ will be in phase with the grid voltage of V₁. This is shown by the vector E_{A2} of Fig. 3 (b) in phase with E_{C1} of Fig. 3 (a).

This anode voltage E_{A2} is applied across C₂ and R₂ (Figs. 1 and 2). The vectors E_{C2} and E_{R2}, Fig. 3 (b), represent the respective voltages across these components. The relative amplitudes of these voltages, as compared with those of Fig. 3 (a) will of course, depend upon the amplification, and the position of the potentiometer tap that will just maintain oscillation will be such that the voltage at this tap is just equal to the grid input of V₁ required to produce it. In other words, the ratio of the tap volts to the anode volts will be equal to the amplification ratio of the two-valve combination. The potentiometer resistance can, therefore, be quite a small part of the total resistance R₂, a separate fixed resistance being added to make up whatever total value may be required.

It is clear that when oscillation

occurs E_{R2} and E₀ will be in phase, as E₀ is derived from a tapping on R₂.

$$\begin{aligned} \therefore \theta_1 &= \theta_2 \\ \therefore E_{R1}/E_{C1} &= E_{C2}/E_{R2} \\ \therefore R_1/X_1 &= X_2/R_2 \end{aligned}$$

where X₁ and X₂ are the reactances of C₁ and C₂.

$$\therefore X_1 X_2 = R_1 R_2 \dots (1)$$

$$\therefore \omega^2 C_1 C_2 R_1 R_2 = 1 \dots (2)$$

where $\omega = 2\pi f$

$$\therefore f = 1/2\pi\sqrt{C_1 C_2 R_1 R_2} \dots (3)$$

where f is the oscillation frequency.

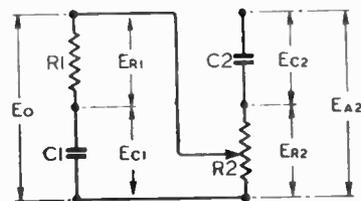


Fig. 2. Equivalent circuit of the feedback section of Fig. 1.

In the original design the capacitance C₁ was the effective grid capacitance of V₁ only, but a study of the principle of operation shows that considerable practical advantages are obtained by making C₁ = C₂ and R₁ = R₂. Equation (3) then reduces to

$$f = 1/2\pi CR \dots (4)$$

where C = C₁ = C₂ and R = R₁ = R₂.

Further, as C₁ = C₂, then X₁ = X₂, so that equation (1) becomes X² = R²

$$\therefore X = R.$$

This result means that provided the oscillation frequency is varied by varying both C₁ and C₂ together and keeping them equal, the frequency will always be such that X = R. Now let Z = the impedance of either of the circuits C₁, R₁ or C₂, R₂ (which, of course, are equal) then

$$Z = \sqrt{R^2 + X^2}$$

$$\text{but } X = R$$

$$\therefore Z = \sqrt{2}R = 1.414R.$$

In other words, unless R is changed, the impedance remains constant.

The practical significance of this result is that if R₁ = R₂ and C₁ = C₂ and the oscillation frequency is varied by varying both C₁ and C₂ together, while R₁

*Wireless World, May 14th, 1937.

Wide-range R-C Oscillator—

and R₂ remain constant, the oscillation amplitude will remain constant. This statement, of course, assumes a constant amplification ratio at all frequencies.

A further advantage of ganging C₁ and C₂ is that a wide range is covered in a single sweep.

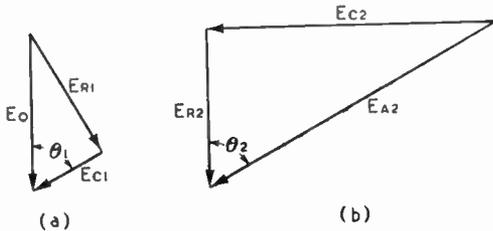


Fig. 3. Vector diagrams illustrating operation of the oscillator.

The complete circuit of a practical audio-frequency oscillator, constructed on the principles outlined above, is shown in Fig. 4.

While the foregoing equations for frequency give a useful approximation to the actual conditions in the practical oscillator, they would need some rather complicated modification if the effect of all refinements included in the practical apparatus were to be taken into account. For instance, some means of applying grid bias to the valves must be

included and the best method in this case is to use cathode resistors without the usual large by-pass condensers. The absence of these condensers assists the attainment of good wave form and lowers the minimum frequency obtainable with a given value of R. In order to extend the range at the upper end of the scale, however, a small by-pass condenser is connected across the cathode resistor of V₁. This condenser has practically no effect at the bottom end of the scale, but the effect is very marked at the top end, so that the combined effect of cathode resistor and

small by-pass condenser is to appreciably widen the whole frequency range. For the attainment of good wave form on range 3, it was found undesirable to make R₁ less than 70,000 ohms. A value of R₂ equal to 40,000 ohms, in conjunction with other details shown, then gave the required range.

The variable condensers C₁ and C₂ are each of 0.0015μF maximum capacitance. Each is obtained by paralleling the three sections of a 0.0005μF 3-gang

condenser, and the two 0.0015μF condensers thus formed are mechanically coupled in tandem, but insulated electrically from one another.

The two three-way switches A and B, which change the resistance values, are operated together to give the following three frequency ranges:—

- (1) 16 to 300 c/s
- (2) 250 to 3,500 c/s
- (3) 1,200 to 18,000 c/s

The Yaxley type of switch is very convenient and satisfactory for this purpose.

The frequency is continuously adjustable over each of these ranges by the condenser control. The potentiometers P₁, P₂ and P₃ control the amplitude of oscillation and each one is normally pre-set by trial to give the same amplitude for each range. It is then possible to cover the whole range of frequency without very much change of amplitude. P₁, the low-range amplitude control, is not connected as a potentiometer, but as a series resistance. This is in order that the spindle may be earthed to avoid hand-capacity effects, which might otherwise be noticeable owing to the high resistance between spindle and earth. Slight changes of frequency occur if the oscillation amplitude controls are altered,

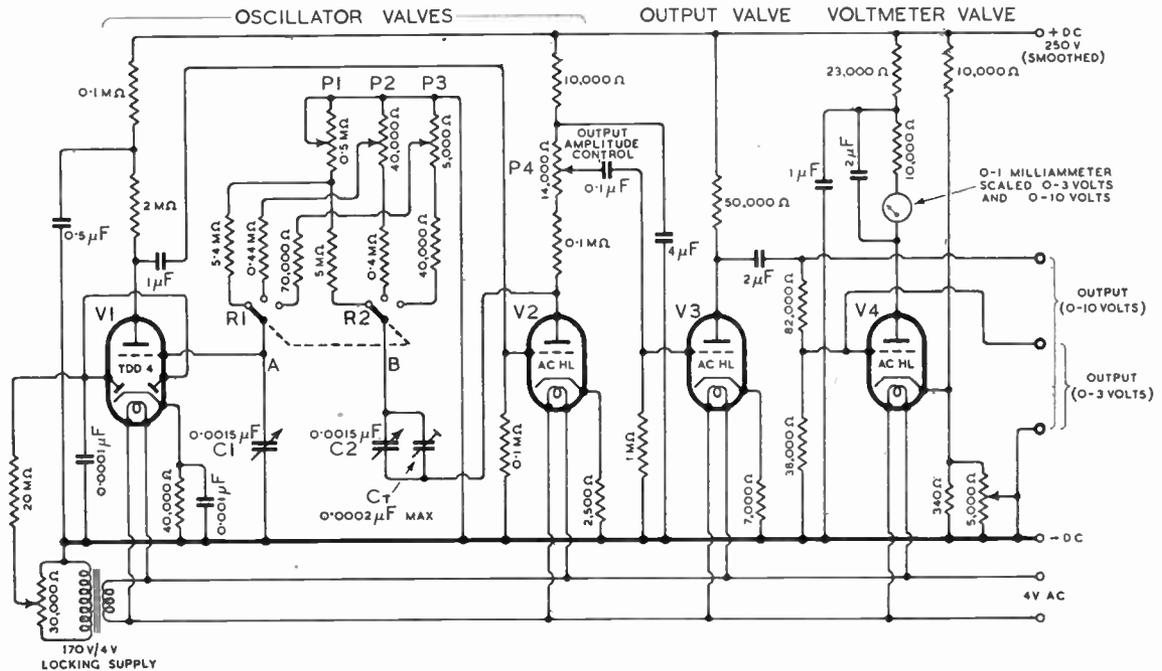


Fig. 4. Complete circuit of the oscillator described.

but as these are normally maintained at a fixed setting, this is of no importance. A separate control for output amplitude is provided which does not affect frequency.

As previously stated, once the controls have been set the oscillation amplitude changes very little over the whole frequency range. The amount of variation that takes place is shown in Fig. 5. In order to maintain such constant amplitude it is necessary, as already explained, to maintain the equality of C_1 and C_2 . In the case of C_1 the effective grid capacitance of V_1 is added to external stray capacitance in

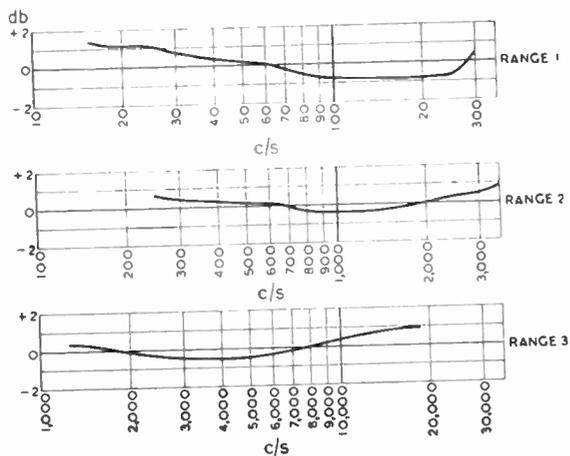


Fig. 5. Amplitude characteristics for the three ranges (odb. is equivalent to 8 volts RMS across 120,000 ohms.)

parallel with C_1 and it becomes necessary, therefore, to provide an additional trimmer condenser across C_2 . The trimmer is marked C_T in Fig. 4 and should be adjusted on trial until the amplitude is found to be constant at different frequencies. In the writer's instrument the necessary trimmer capacitance was found to be approximately $0.000115 \mu F$. Another condition for constant amplitude is that the oscillation should not be too weak. The potentiometers give a smooth control of amplitude and it is found that the best setting is that which gives the maximum amplitude that can be attained without distortion being discernible on a cathode ray screen.

It will be noticed that change of frequency range is effected by changing the values of resistances R_1 and R_2 by means of switches A and B. A change of resistance

would change the oscillation amplitude if the potentiometer setting were unchanged; that is why three separate potentiometers are required, the appropriate one for each range being selected by the switching operation.

It has been stated that the coupling between the anode of V_1 and the grid of V_2 should be so designed as to give a very small phase angle at the lowest frequency. Such a condition minimises the effect of this coupling on the oscillation frequency or change of amplitude. But it is desirable that this coupling should impose a fairly high damping effect on the anode of V_1 . A fairly low resistance and large capacitance are therefore indicated. The damping introduced by this coupling and the high value of anode resistor of V_1 gives a smooth control of oscillation at low amplitudes. The high value of cathode resistor for V_1 is suited to the anode resistor. The grid swing of V_1 is very small, but that of V_2 is much greater and more normal values of anode and cathode resistors are needed for V_2 . Negative feedback is, of course, present in both valve circuits, owing to the absence of large by-pass condensers.

An output valve V_3 is coupled to V_2 in such a way that negligible load is imposed on the oscillator circuit. The diagram will make this clear without detailed explanation, but it may be pointed out that control of output amplitude is by means of the potentiometer P_4 , which controls the input to V_3 . This arrangement allows the output circuit impedance to remain constant at all amplitudes. It also minimises any distortion in V_3 , because the lower the amplitude, the lower the input to V_3 .

A voltmeter valve V_4 indicates output volts on the instrument G , which is a 0-1 milliammeter suitably calibrated. The valve is operated as an anode-bend recti-

fier, and, at normal oscillator amplitude it has no effect on the output wave form.

Initial tests are made with the aid of an oscillograph to determine the maximum output voltage that can be obtained without distortion in the oscillator itself.

No reference has so far been made to the fact that V_1 is a double-diode-triode. The diode section is a refinement which assists in providing means for locking any multiple of 50 c/s to the mains frequency (assuming 50 c/s to be the mains frequency). This means that if the oscillation frequency is adjusted to be very nearly equal to any harmonic of 50 c/s, the locking control will pull it into step and hold it at the harmonic frequency. This is accomplished by connecting one or both diodes to the mains supply through a high resistance. It is convenient to provide a variable voltage for this purpose in the manner shown, as the voltage required increases with increase of frequency. The locking is effective up to about 2,000 c/s, but above this a higher locking frequency than 50 would be desirable.

Briefly, the locking action may be explained as follows: Once per cycle of 50 c/s mains voltage a rectified pulse flows through the cathode bias resistor and momentarily increases the negative bias. This action is similar to increasing the value of the bias resistance and tends momentarily to lower the oscillation frequency, hence the effect of "pulling into step." If the pulse were strong enough the oscillation would cease once every cycle of the locking frequency.

Effective screening should be provided for the whole of the apparatus, as the pick-up from AC fields may otherwise be troublesome, and, of course, suitable screening will ensure that the output of the oscillator will be confined to the output terminals.

Institute of Physics.—At the annual general meeting of the Institute of Physics, held recently, the following were elected to take office on October 1st, 1943: President, Sir Frank Smith; vice-presidents, E. R. Davies, Dr. W. Makower and T. Smith; hon. treasurer, Maj. C. E. S. Phillips; hon. secretary, Prof. J. A. Crowther; ordinary members of the Beard, Prof. J. D. Cockcroft, D. C. Gall, Dr. H. Lowery, D. A. Oliver, A. J. Philpot and R. S. Whipple. A record increase in membership of the Institute is reported.

CONTRAST EXPANSION UNIT

Design Giving Unequal "Pick-up" and "Decline" Delays

By

D. T. N. WILLIAMSON

IT is well known that in broadcasting and recording sound it is necessary to reduce the contrast between the loudest and softest passages. The maximum permissible signal level is rigidly determined by the power-handling capacity of the equipment, and if the full range of contrast is handled the minimum will approach closely the residual noise level, which is obviously undesirable. Thus, if the difference in level between the maximum permissible signal and the residual noise is, say 70 db., and it is desired to maintain a difference between the inherent noise and the minimum signal of 25 db., then it is clear that an original having a contrast range of 60 db. must be compressed to a maximum of 45 db. This is at present usually achieved by manual control at the source, but automatic means will no doubt gradually find favour.

To reproduce such a signal realistically it is desirable that the reproducer should restore the original range. To achieve this it is necessary to arrange that the gain of the reproducing amplifier varies with the variations in *intensity* of the signal. A steady signal requiring a constant gain consists, however, of cyclic variations at audio-frequency, and if the gain were to alter instantaneously it would follow these cyclic variations and alter the waveform of Fig. 1 (a) to that

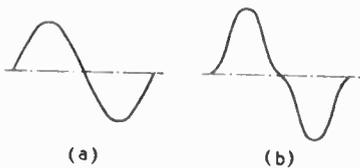


Fig. 1. Waveform distortion produced by instantaneous gain alteration.

of Fig. 1 (b), producing objectionable distortion. It follows, therefore, that it is necessary to introduce some form of time delay to prevent the gain of the amplifier fluctuating at a frequency comparable with the lowest to be reproduced.

By the introduction of this time delay, the rate of change of gain of the amplifier is reduced. If the rate of rise is reduced, a signal of the type shown at Fig. 2 (a)—that is, a transient—is altered to that at Fig. 2 (b), resulting in poor

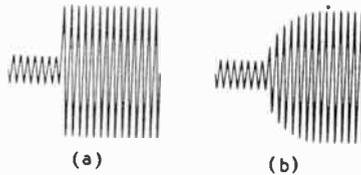


Fig. 2. Effect on a rising transient of time delay in the application of volume expansion.

transient response. On the other hand, if the rate of fall of gain is reduced, the signal of Fig. 2 (a) is unaffected, as it ceases instantaneously; the way in which the gain varies after this is obviously of no importance. The signal of Fig. 3 (a), however, will be distorted to that at Fig. 3 (b).

In general, in acoustics the maximum rate of decay of a signal is considerably less than the maximum rate of rise, e.g., a note of a pianoforte is as in Fig. 4. Also, any reverberation which may be present still further tends to reduce the rate of decay. It is thus apparent that the gain of the amplifier should increase very rapidly, and fall at a relatively low rate determined by the lowest frequency required to be reproduced. This rapid increase will cause some waveform distortion of transients, but this will occur over so short a period as to be inappreciable.

In the usual form of contrast expansion equipment the rates of rise and fall of gain are approximately equal, and a compromise has to be adopted between high rate of change to obtain satisfactory transient response and low rate of change to avoid waveform distortion. The performance of this type of equipment is mediocre, and has given contrast expansion a totally undeserved

reputation for transient and amplitude distortion.

The use of manual control of compression leads to anomalies when automatic expansion is in operation. In particular, when the intensity of a loud passage is reduced, the level is not immediately restored at the end of the passage, and so reverberations are kept at the same relative level as the parent sound. Thus, when contrast expansion is introduced, the contrast between the passage and its reverberation is increased, which results in an undesirable attenuation of the echo. This can be avoided by decreasing the rate of fall of gain, holding the rate of gain near its maximum for the duration of the echo. A time of decay of gain of about one second proves very satisfactory in all respects, and gives the added advantage that "flutter" does not occur due to large fluctuations of gain when reproducing music such as the final bars of the Beethoven 5th Symphony, i.e., loud chords separated by short time intervals.

Contrast expansion is most conveniently achieved by means of a variable-gain amplifier, the control voltage being derived from the signal. As is well known, expansion must be carried out at a very low signal level, as attempts to control the gain of a valve handling a large signal will result in distortion. A separate amplifier must, therefore, be provided to obtain a suitably large

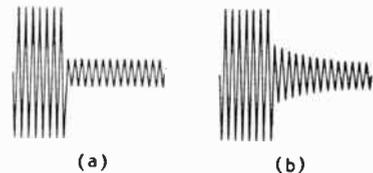


Fig. 3. Distortion produced by time delay in a falling transient.

voltage which is then rectified and fed to the controlled stage through a filter network, by means of which the time delay is introduced.

Fig. 5 shows the basic arrangement of the rectifier and delay circuit. A unidirectional voltage proportional to the instantaneous

value of the signal is developed across R_1 by the amplifier and rectifier. The rectifier should be full-wave to ensure that the whole waveform appears across R_1 with the negative half-cycles inverted, giving a unidirectional voltage which pulsates in a similar manner to the original signal as in Fig. 6 (b). This voltage is in opposition to the standing voltage S , giving a resultant voltage between A and B of the form shown in Fig. 6 (c). This procedure is necessary because variable-gain amplifiers require for control purposes a negative voltage which decreases as the amplification is required to increase. The resultant voltage is applied to the circuit consisting of R_2 , V and C_1 . Under no-signal conditions the voltage between A and B is S , and C_1 will be charged to this



Fig. 4. Waveform of a struck string.

value. On receipt of a signal the resultant voltage AB falls during the first quarter-cycle. C_1 will almost simultaneously discharge through the diode V , as the time-constant of C in conjunction with the conduction resistance of V is made small compared with the time of a quarter-cycle. During the next quarter-cycle the voltage across AB will rise, but now the diode is non-conductive and the condenser can charge only through R_2 , which is of high value to give a time-constant long in comparison with the period of a cycle. C_1 thus has insufficient time to acquire any further appreciable charge before the next fall in resultant voltage, and its voltage remains practically steady until a change in signal level occurs. The control voltage for the variable-gain amplifier is taken from C_1 , and is of the form shown at Fig. 6 (d).


It is apparent that as R_1 and the resistance of the supply S are in series with the diode to form the discharge circuit of C_1 , their values must be kept as low as possible to give a high rate of discharge.

Fig. 7 shows the circuit of a contrast expansion unit which embodies the foregoing principles. Dealing first with the control equipment; V_4 , the control amplifier, is a single high-slope output tetrode designed to develop a rectified voltage of some 30 V peak in the load resistance R_{14} . It will be adequately loaded by the output of a crystal pickup, but if the output of the preceding equipment is low, an additional stage of amplification must be provided. The standing voltage is obtained by the drop across R_{17} .

R_{15} and R_{16} , in conjunction with C_8 , determine the time of fall of gain, and as previously stated, this should be about one second. Insulation difficulties limit the resistance in parallel with the diode to about $4M\Omega$, and with this value, C_8 should be $0.25 \mu F$, giving a time-constant of one second. Some degree of control over the rate of fall of gain is desirable, and for this reason R_{15} is made variable. R_{16} sets a lower limit for this delay, to ensure that distortion does not occur.

It is the writer's experience that a time constant of about one millisecond is satisfactory for the discharge circuit which determines

Fig. 5. Basic arrangement of rectifier and delay circuit.

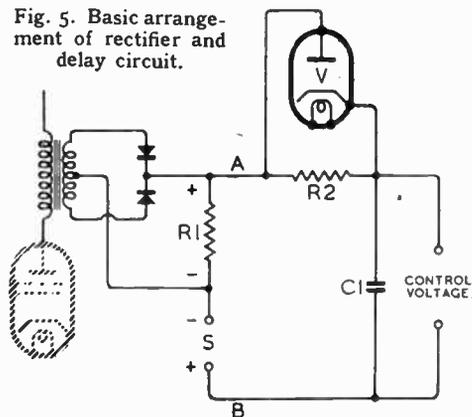

the rise of gain; this necessitates that the total resistance of the discharge circuit should not be greater than $4,000\Omega$. The characteristic of a diode is, of course, non-linear and graphical methods

are required to determine exactly the discharge time of the condenser, but a sufficiently close approximation may be obtained by

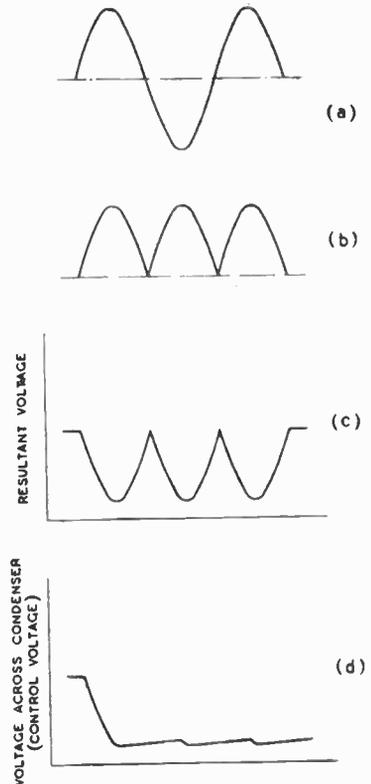


Fig. 6. How the controlling voltage is derived from the signal.

assuming a mean value of resistance over the working range. The diode used is a power-rectifier type, and its resistance over the range in use should be considerably less than $4,000\Omega$.

The use of an extremely high rate of gain causes difficulties in the amplifier. The rise in anode current which accompanies an increasing gain gives a violent transient. In the case of a single controlled valve this appears superimposed on the output signal, and causes an objectionable noise. The use of a push-pull controlled stage is necessary to eliminate this effect, the transients, which are in the same phase in each valve, cancelling each other, provided balance is correct. The push-pull connection is also advantageous in reducing distortion in this stage, where it is most likely to be present. It is advisable to precede this stage with a phase-splitter, as it is difficult otherwise to provide means for varying the

Contrast Expansion Unit—

signal inputs of both signal and control amplifiers without unbalancing the push-pull arrangement.

It is impracticable to use resistance coupling from the output of the push-pull stage to the input of the main amplifier (unless this is of a type requiring a split phase

The following procedure is essential for correct operation and should be carefully observed. With the sliders of R₁₂ and R₁₇ at the chassis ends, R₁ is adjusted in conjunction with the volume control of the main amplifier so that the latter will just be fully loaded with the loudest

to be at cathode potential. Any further alteration in volume level should be made by means of R₁, rather than with the volume control of the main amplifier, as the former reduces the signal to be handled by the controlled stage.

Equipment on the lines indicated has been used by the writer

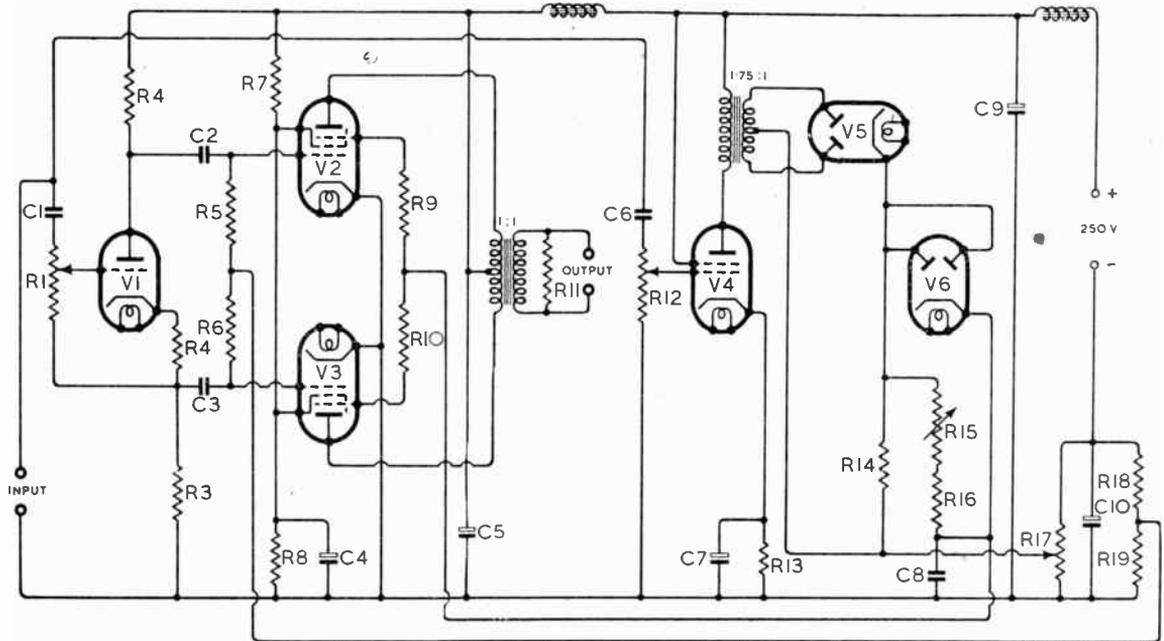


Fig. 7. Contrast expansion unit embodying the principles described in the text. Component values given below.

input isolated from earth), and a transformer must be used. This should introduce negligible distortion, however, as it has no resultant DC magnetisation and will only be called upon to handle signals of the order of one volt. It may be of the nickel-core type.

The method of controlling the amplification of the valves gives some scope for experiment. Variation of the control grid potential is not to be recommended, as it is difficult to arrange matters so that the grid bias is not decreased below the limit for distortionless operation by an unexpectedly large signal. An auxiliary control electrode is therefore desirable and the suppressor grid of a pentode proves satisfactory for this purpose, although other multi-electrode valves may, of course, be utilised. R₉ and R₁₀ are included to prevent the suppressor grids being driven positive. The bias for the signal grids is obtained from R₁₇ by the potential divider R₁₈ and R₁₉.

expected signal. R₁₇ is then adjusted to give the desired increase in contrast. For convenience, it may be calibrated in db. R₁₂ is advanced until the loudest signal just causes the suppressor grids

for a considerable period, and has given very satisfactory results. The distortion of the first cycle or so of transients which theoretically occurs is completely inaudible, due perhaps to the inability of the ear to perceive changes of very short duration.

Quality of recorded music reproduced by this equipment is greatly enhanced and a considerable improvement results from the apparent reduction in surface-noise which takes place due to the expansion process.

THE WIRELESS INDUSTRY

A NEW illustrated leaflet describing four Rothermel-Brush crystal pick-ups, their accessories and method of mounting, has been issued by R. A. Rothermel, Ltd., Canterbury Road, London, N.W.6.

Instrument wires covered with a new plastic enamel having improved mechanical and electrical properties are described in List NSW₂ issued by British Insulated Cables, Ltd., Prescott, Lancs. The new wires will be known under the name of "Bicolon."

COMPONENT VALUES

Resistances

R1	1 MΩ	R11	0.1 MΩ
R2	1,000Ω	R12	1 MΩ
R3	25,000Ω	R13	100Ω
R4	25,000Ω	R14	500Ω
R5	0.25 MΩ	R15	4 MΩ
R6	0.25 MΩ	R16	0.5 MΩ
R7	2,500Ω	R17	250Ω
R8	10,000Ω	R18	20,000Ω
R9	0.1 MΩ	R19	3,500Ω
R10	0.1 MΩ		

Condensers

C1	0.01 μF	C6	0.02 μF
C2	0.1 μF	C7	50 μF
C3	0.1 μF	C8	0.25 μF
C4	4 μF	C9	8 μF
C5	8 μF	C10	50 μF

Valves

V1	Osram MH4	V4	Osram KT41
V2, V3	Mazda AC/SP1	V5, V6	Mullard AZ3

Development and Research




INTENSIVE research is constantly proceeding in the Standard Laboratories and, wherever practicable, each new development is incorporated in every Brimar Valve leaving the Factory.

BRIMAR
BVA
VALVES

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.

NEVILLE'S

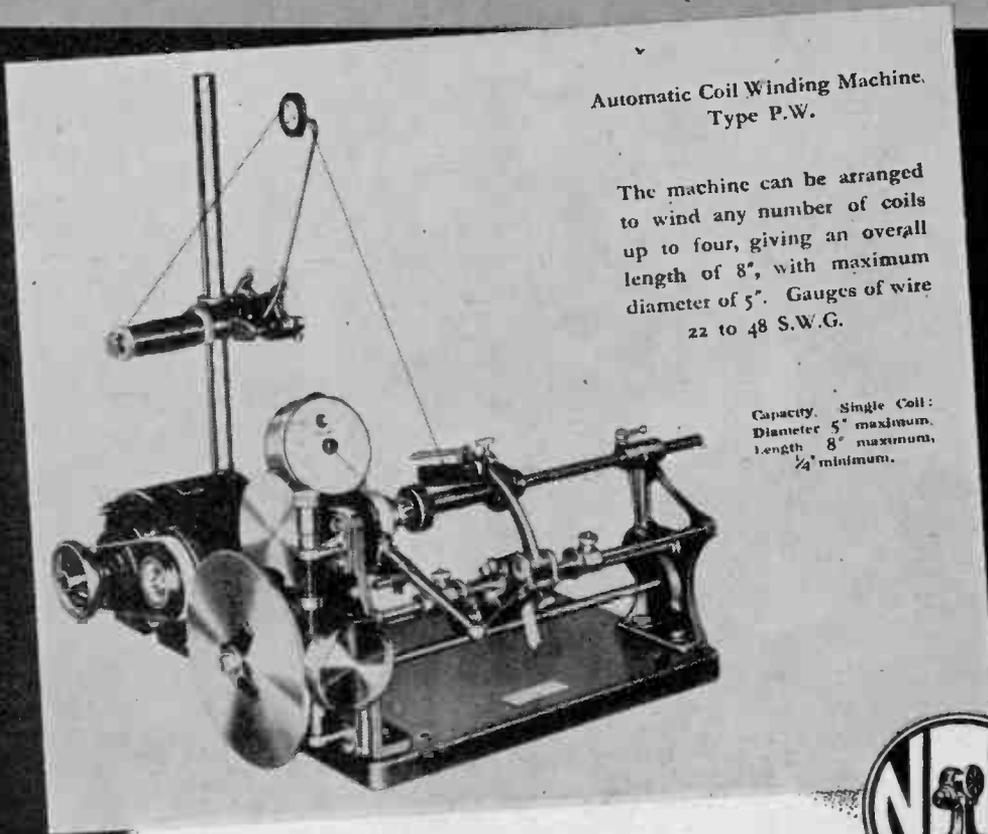

Automatic Coil Winding Machine.
Type P.W.

The machine can be arranged to wind any number of coils up to four, giving an overall length of 8", with maximum diameter of 5". Gauges of wire 22 to 48 S.W.G.

Capacity. Single Coil:
Diameter 5" maximum.
Length 8" maximum.
1/4" minimum.



Specialists

IN THE DESIGN AND MANUFACTURE
OF COIL WINDING MACHINES

NEVILLE'S (LIVERPOOL) LIMITED
SIMMONDS TOWER · GREAT WEST ROAD · LONDON

A DIVISION OF THE SIMMONDS GROUP
LONDON · MELBOURNE · MONTREAL · PARIS · NEW YORK · LOS ANGELES

DESIGN OF SIMPLE OHMMETERS

2.—Formulae and Practical Hints for Designing a Low Ohmmeter

By F. LIVINGSTON HOGG

(Concluded from page 227 of the August, 1943, issue)

WE want the Low Ohmmeter to overlap with the High Ohmmeter described in the last issue. We also want to be able to measure low resistances such as of earth bonding points, soldered joints, etc. This means that 0.1 ohm must be a good sizable reading, and that 0.01 ohm should be seen though not measured accurately. These requirements can be met by three ranges with mid-scale values of 0.5, 5 and 50 ohms.

When the external resistance to be measured is very low, the meter reading will be in error by an amount equal to the resistance of the leads to the prods from the meter circuit. This means that it is necessary to deduct the lead resistance from the scale reading each time a low value is taken. As the lead resistance may easily be 0.05 ohm or so, and a bad joint may be less than 0.1 ohm, this is very inconvenient. There is, however, a simple dodge which gets over this difficulty. Referring to Fig. 5, the circuit supplying power, i.e. E and R_2 is connected across R, and the measuring circuit R_3 and M is connected as closely as possible to the same spot. The common resistance which causes trouble is then very much lower. If heavy brass prods are used, this residual error can be made less than 0.01 ohm.

The final circuit is shown in

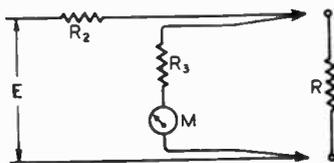


Fig. 5. Errors are reduced if separate leads are used for connecting the meter and battery circuits to the test prods.

Fig. 6, and in simplified form for calculation in Fig. 7. R_{35} is inserted to represent the switch contact and connecting lead resistance. Equating volt drops again we can write down:—

$$E = (I_7 + I_8 + I_9) R_{31} + I_9 \cdot R_{32} \dots \dots (8)$$

$$I_9 \cdot R_{32} = (I_7 + I_8) R_{33} + I_8 \cdot R_{34} \dots \dots (9)$$

$$I_8 \cdot R_{34} = I_7 \cdot R_{35} + I_6 \cdot R_{36} \dots \dots (10)$$

$$I_6 \cdot R_{36} = (I_7 - I_6) R \dots (11)$$

From these we get:—

$$I_7 = I_6 \left(1 + \frac{R_{36}}{R} \right) \dots (12)$$

$$I_8 = \frac{I_6}{R_{34}} \left(R_{35} \left(1 + \frac{R_{36}}{R} \right) + R_{36} \right) \dots \dots (13)$$

$$I_9 = \frac{I_6}{R_{32}} \left[R_{33} \left(1 + \frac{R_{36}}{R} \right) + \left(1 + \frac{R_{33}}{R_{34}} \right) \left(R_{35} \left(1 + \frac{R_{36}}{R} \right) + R_{36} \right) \right] \dots (14)$$

Now by equating the resulting value of E obtained from these with the value obtained by substituting for the known case $I_6 = I_{\max}$ when R is infinite, we get

$$\left(\frac{I_{\max}}{I_6} - 1 \right) \left\{ 1 + \frac{R_{36} \left[\frac{R_{31}}{R_{34}} + \left(1 + \frac{R_{31}}{R_{32}} \right) \left(1 + \frac{R_{33}}{R_{34}} \right) \right]}{R_{31} \left(1 + \frac{R_{35}}{R_{34}} \right) + \left(1 + \frac{R_{31}}{R_{32}} \right) \left[R_{33} + R_{35} \left(1 + \frac{R_{33}}{R_{34}} \right) \right]} \right\} \dots \dots (15)$$

This fearsome equation is found on inspection to be our old friend (2) in substance, and, neglecting for the moment the effect of variation of R_{31} , we see that if we choose our values correctly we can use a pre-calibrated scale again.

It is a great convenience to have a constant setting adjustment for all ranges. There are two obvious methods of doing

this. If current consumption is not important, the scheme shown in Fig. 7 can be used. R_{32} serves to keep the current drain, and therefore the voltage V, constant between ranges. Alternatively three separate controls could be used. We will take the former case, which is a little more awkward to calculate, for our example. It is convenient to supply the necessary voltage from dry cells. If we do this we must remember that during the useful life of the cell the voltage will fall from about 1.5 to 0.8 volts.

We will assume that V the working voltage is 0.7 volt. The meter will be 1 mA full-scale. Its resistance is not likely to be much over 40 ohms, and R_{36} includes this meter resistance. R_{35} , the switch and lead resistance is unknown, but it is

unlikely to be over 0.1 ohm. It has an appreciable effect on the $\times 1$ range. We will assume that it is 0.1 ohm, and then we can build it up to this value of test.

R_{31} , which is the setting up control, will be taken as 3 ohms for calculation.

We start by calculating R_{36} on $\times 100$, as then R_{34} is infinite. If V is 0.7 volt, and I_{\max} is 1 mA, then $R_{33} + R_{35} + R_{36}$ is 700 ohms. This is the elementary case of Fig. 1 (b), with $R_3 = R_{36}$ and $R_2 = R_{33} + R_{35}$. Then if the mid-scale value of R is

Design of Simple Ohmmeters

50 ohms, we can see that, from (2), R_{36} is 54.2 ohms, and R_{33} is 645.7 ohms. R_{32} cannot be calculated accurately at this stage.

For ranges $\times 1$ and $\times 10$ it is convenient to write down:—

$$V = (I_7 + I_8)R_{33} + I_8 \cdot R_{34} \quad (16)$$

Substituting values of I_7 and I_8 ,

$$V = I_6 \cdot R_{33} \left(1 + \frac{R_{36}}{R} \right) + I_6 \left(1 + \frac{R_{33}}{R_{34}} \right) \left[R_{35} \left(1 + \frac{R_{36}}{R} \right) + R_{36} \right] \quad (17)$$

And when $I_6 = I_{\max}$, and R is infinite

$$V = I_{\max} \left[R_{33} + \left(1 + \frac{R_{33}}{R_{34}} \right) (R_{35} + R_{36}) \right] \quad (18)$$

Here only R_{33} and R_{34} are unknown. With small inaccuracy we can take the mid-scale values of R , and solve. However, for best accuracy the figures thus found can be tried and adjusted, together with R_{32} , as necessary until, on substitution in (15), at say mid-scale, the error is negligible. The results are tabulated in Fig. 7.

To evaluate R_{32} it is simplest to calculate $I_7 + I_8$ on range $\times 1$. This gives us the maximum open circuit current, which is also the

The results for our particular example are given in the table in Fig. 7.

We have now to decide on the maximum value of R_{21} . Our working current is 128.4 mA, and we have to drop a maximum of 0.8 volt, so that a variable resistance covering the range 0 to 7 ohms or so will suffice. It will be noticed that on range

$\times 1$, R_{34} is shown as two resistances in parallel, R_{28} and R_{29} . This is for convenience in adjustment, as it is difficult to adjust a low resistance. R_{28} may be made about 0.45 ohm, and R_{29} about 10 ohms. R_{29} is adjusted on test to give the correct value for the combination.

The construction of the instrument is quite straightforward. S_3 and S_4 are ganged break-before-make Yaxley type switches. It was expected that

fore any adjustment is tested.

The current can conveniently be taken from two bell type dry cells in parallel. These are switched by means of a double-pole switch, as shown in Fig. 6, to prevent one cell from discharging through the other when off load. The prods may be 1/4 in. brass rods covered with sleeving, with gramophone needles soldered in for contact points.

The lining up problem is rather more difficult than on the High Ohmmeter. A good method involves the use of two standard resistances on each range. (It will be found that shunts from high-grade meters are useful for this purpose.) One can, with some loss of accuracy, use one resistance on each range, about mid-scale, and use open circuit as the other value. In any case it is very difficult to do without a good Wheatstone Bridge. As the values are somewhat low, special care has to be taken when measuring by indirect methods. A DC voltmeter reading 0.7 volt, and a milliammeter covering 128 mA are also desirable.

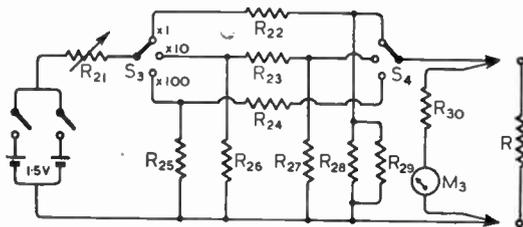



Fig. 6. Circuit diagram of practical Low Ohmmeter. $R_{21} = 0$ to 7 ohms; $R_{22} = 5.03$ ohms; $R_{23} = 63.3$ ohms; $R_{24} = 645.7$ ohms; $R_{25} = 5.49$ ohms; $R_{26} = 5.92$ ohms; $R_{27} = 5.9$ ohms; $R_{28} = 0.45$ ohms; $R_{29} = 10$ ohms (approx.); $R_{30} = 54.2$ ohms; $M_3 = 0$ to 1 milliamp.

setting-up condition. Then if we subtract the values of $I_7 + I_8$ on the other two ranges from this value we get the corresponding values of I_9 . For this condition the general equations are:—

$$I_7 = I_6 \quad \dots \quad (19)$$

$$I_8 = \frac{I_6}{R_{34}} (R_{35} + R_{36}) \quad \dots \quad (20)$$

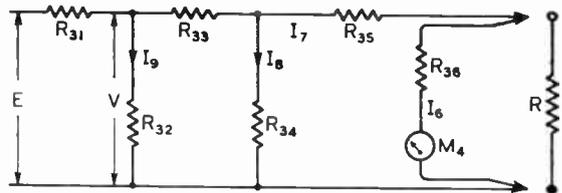the switch contact resistance would be so variable that it would cause serious trouble, but this has not been found to be so in practice. It is extremely important to wire up with very heavy connecting wire, and make really first-class soldered joints. Owing to the thermo-electric effect, it is necessary for each joint to become cold be-



RANGE	RESISTANCE OHMS					MILLIAMPERES OHMS		
	R_{31}	R_{33}	R_{34}	R_{35}	R_{36}	$I_7 + I_8$	I_9	R_{32}
$\times 100$	3	645.7	∞	0.1	54.2	1	127.4	5.49
$\times 10$	3	63.3	5.9	0.1	54.2	10.2	118.2	5.92
$\times 1$	3	5.03	0.426	0.1	54.2	128.4	-	∞

Fig. 7. Simplified circuit with values obtained by calculation.

The procedure may be as follows. On range $\times 100$, set V to 0.7 volt, and adjust R_{24} to give full scale deflection on open circuit. Measure a known resistance and adjust R_{30} until the correct reading is obtained. Repeat until both results are obtained without readjustment. Similarly adjust R_{23} and R_{27} , and then R_{22} and R_{29} . So far

R_{35} has been neglected; this affects range $\times 1$ only. Having lined up R_{28} and R_{29} , measure the current taken from the battery on open circuit, with V at 0.7 volt. If the current is lower than 128.4 mA, then the lead from S_4 arm to the prod should be made of slightly higher resistance, and vice versa. Finally, the instrument is set up

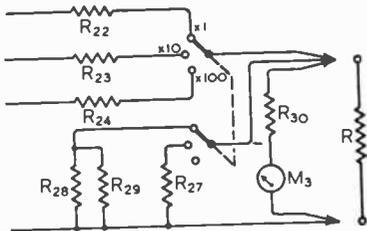


Fig. 8. Circuit modification for eliminating the effect of lead resistance.

on open circuit on range $\times 1$, and then R_{26} and R_{25} are adjusted on ranges $\times 10$ and $\times 100$ to give exactly full-scale deflection without altering R_{21} . If two standard resistances are available for each range, they should be used instead of one resistance and the open circuit condition, the latter being used as an additional check. In practice, if the resistances have been reasonably accurately made and connected up, it will be found necessary to adjust only R_{30} , R_{27} and R_{29} .

The accuracy of this instrument depends even more than the High Ohmmeter on the care and accuracy with which it is made and adjusted. In general, the greatest inaccuracy is on the lowest range, where it is of the least consequence in general radio work. For instance, neglecting the adjustment of R_{35} will cause a mid-scale error of not more than 10 per cent. on 0.5 ohm. The effect of R_{21} is not great, and is worst on the lowest range. The formulae given enable the probable errors to be estimated for any given case, according to circumstances.

Whereas it was found essential to use the protective device on the meter on the high ohm instru-

ment, the need is not nearly so great on the Low Ohmmeter, and it has therefore been omitted.

It should be pointed out that the Low Ohmmeter may have a quite noticeable temperature coefficient on the lowest range, as there is a considerable proportion of copper in some of the low-resistance circuits.

There are numerous deviations from the design given which may sometimes be preferable. For instance, the effect of R_{35} can be to all intents and purposes eliminated by adding a further switch bank, and making the lead to one prod threefold, as shown in Fig. 8.

These instruments are intended for fault-finding and similar purposes, and not to give a high accuracy of measurement. They are, however, much more accurate and useful than

many of the universal meters on the market, because they are designed specifically for the purpose.

There is no fundamental reason why the two instruments should not be combined, with a shunt across the meter for the low ohm ranges. It is also possible to extend the High Ohmmeter ranges down lower, but it is recommended that this be done by shunting the meter and not by reducing the voltage further. The microammeter when shunted will probably be very sluggish.

The work of designing these instruments was done by the writer assisted by his colleagues, when he was with Messrs. Standard Telephones and Cables Ltd., New Southgate, London, to whom acknowledgment is therefore due.

American Valve Designations

Interpreting the Type Numbers

IN spite of the fact that a large number of American "Lend-Lease" valves are now available in this country, it seems that many wireless users do not appreciate the meaning of the numbers allotted to the various valve types.


Most current American receiving valves are designated according to a system standardised by the American R.M.A. in 1933. The type number is divisible into four groups having the significance shown in the sketch.

Group 1.—The figure(s) indicates the actual heater voltage, ignoring fractions of a volt, *except* in the case of 2-volt valves, where 1 is used for all voltages below 2.1, and 2 is used for voltages between 2.1 and 2.9 volts. This convention originated from the necessity of distinguishing between the 2.0 and 2.5-volt series.

Group 2.—Type letters were assigned to valves as they were introduced, starting at A for any type except rectifiers, and from Z working backwards for rectifiers. Double letters are now being used for many new valves. If the first letter of a two-letter group is "S" it indi-

cates the single-ended version of an existing type. Thus the 6SJ7 is similar to the 6J7 but its working grid is brought out to a pin in the base instead of to a top cap.

Group 3.—In earlier types this

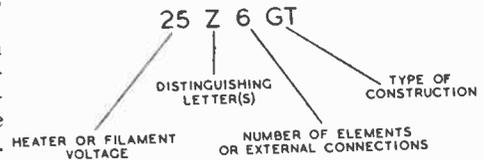

number referred to the number of useful elements; thus a battery triode would be indicated by 3 (filament, grid and anode), but in later types it refers to the number of external contacts—two for heater, one for cathode, etc.

Group 4.—This gives the type of envelope and base; thus M = metal envelope, octal base; G = glass envelope, octal base; GM = metal-coated glass envelope, octal base; GT = short glass envelope, octal base; GL = integral glass envelope and loktal base; ML = integral metal envelope and loktal base; LM = metal envelope and loktal base; LT = glass envelope and loktal base; GB = integral glass envelope and base.

CALCULATING COUPLING COEFFICIENTS

Useful Formulae for Finding the Optimum Spacing of IF Transformer Windings

THE sensitivity and selectivity of a superheterodyne receiver depend to a very large extent on the characteristics of its IF transformers and consequently considerable care is necessary in the design of these if a satisfactory performance is desired.

Nearly all IF transformers are of the type illustrated in Fig. 1, i.e., they consist of two wave-wound coils coupled, by means of the mutual inductance existing between them, to give a bandpass effect. The effective bandwidth so obtained depends on the coefficient of coupling between the

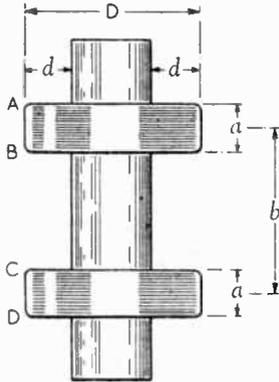


Fig. 1. Type of construction generally used for IF transformers. The calculation of k between the windings is discussed in the text.

windings, being given approximately by the expression $\Delta f = f_0 k$ where Δf = bandwidth in kc/s, f_0 = intermediate frequency in kc/s, and k = coefficient of coupling between the windings.

Now the performance of such an IF transformer with respect to voltage step-up and selectivity depends also on this coefficient of coupling and is best understood by reference to the curves of Fig. 2, which are based on those given in an article by Reed*. From these it is clear that there is one value of k which gives maximum voltage amplification. This value, known

* "The Design of HF Transformers" by M. Reed. *Wireless Engineer*, p. 349, July 1931.

By S. W. AMOS, B.Sc. (Hons.)

as optimum coupling, is given by

$$k = \frac{1}{\sqrt{Q_1 Q_2}}$$

in which Q_1 and Q_2 are the effective Q values ($\frac{\omega L}{R}$) of the two windings. If

$Q_1 = Q_2 = 100$, values which are quite common in IF transformers, then the optimum value of k is 0.01.

Optimum coupling, however, gives a poor performance with respect to selectivity, as will be seen from Fig. 2. In fact these two qualities are mutually conflicting, that is to say, increase in gain is generally only possible by sacrificing selectivity and vice versa. There is, however, one value of k , actually equal to half optimum coupling, which gives 80 per cent. of the maximum possible voltage gain and the same percentage of the maximum possible selectivity, which represents an extremely good compromise. This article is devoted to the derivation and some applications of a compara-

two inductances L_1 and L_2 is defined by the relationship $k = \frac{M}{\sqrt{L_1 L_2}}$, where M is the mutual inductance between the windings. In the case of an IF transformer $L_1 = L_2$, and we have thus—

$$k = \frac{M}{L_1} \dots \dots (1)$$

Before we can calculate k , therefore, we must know the value of M . Assume, in Fig. 1, that the space BC has been wound into an inductance with the same type of construction and number of turns per unit length, etc., as for the coils AB and CD. Let the inductances of AB and CD, etc., be represented by L_{AB} and L_{CD} , etc. Then the value of M between the coils AB and CD is given by $M = \frac{1}{2}(L_{AD} + L_{BC} - L_{AC} - L_{BD}) = \frac{1}{2}(L_{AD} + L_{BC} - 2L_{AC})$, since $L_{AC} = L_{BD}$ in an IF transformer.

From expression (1) k is therefore given by—

$$k = \frac{L_{AD} + L_{BC} - 2L_{AC}}{2L_{AB}} \dots (2)$$

Let the dimensions of each winding be as indicated in Fig. 1 and let the number of turns per unit

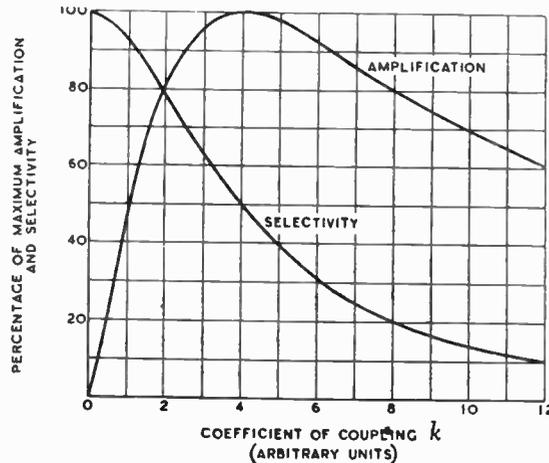


Fig. 2. Curves showing the effect of varying k on the voltage gain and selectivity of an IF transformer.

tively simple formula for calculating the coefficient of coupling for an air-cored IF transformer (or any other coil assembly which consists of two similar coils mounted on the same former).

The value of k between any

length on each be n . Now Reyner's formula* for the inductance of a multilayer coil with an air core is

$$L = \frac{0.2N^2 D^2}{3.5D + 8l} \times \frac{D - 2.25d}{D} \mu H,$$

* See "Radio Communication," by J. H. Reyner. Vol. 1. Edition 7. p. 29.

where D = overall diameter of coil in inches, d = depth of winding in inches, l = length of winding in inches, and N = total number of turns on the coil.

Consider the coil AB. In this $N = na$ and consequently its inductance may be written $L_{AB} = \frac{0.2n^2a^2D^2}{3.5D + 8a} \times \frac{D - 2.25d}{D}$, which we will rewrite as $L_{AB} = \frac{0.2n^2a^2D^2h}{3.5D + 8a}$ where $h = \frac{D - 2.25d}{D}$.

Similar results may be obtained for L_{AD} , L_{BC} and L_{AC} . Substituting these values in (2) above, and putting $c = b - a$ and $e = b + a$, we have—

$$k = \frac{0.2n^2D^2h \left(\frac{c^2}{3.5D + 8c} + \frac{e^2}{3.5D + 8e} - \frac{2b^2}{3.5D + 8b} \right)}{2 \times \frac{0.2n^2D^2a^2h}{3.5D + 8a}}$$

$$= \frac{3.5^2D^2(3.5D + 8a)}{(3.5D + 8b)(3.5D + 8c)(3.5D + 8e)}$$

$$= \frac{1 + \frac{2.3a}{D}}{\left(1 + \frac{2.3b}{D}\right)\left(1 + \frac{2.3c}{D}\right)\left(1 + \frac{2.3e}{D}\right)} \dots (3)$$

As we have already seen, in IF transformers generally the degree of coupling is small ($k = 0.01$ was quoted earlier) and this is achieved by making b much greater than a . By doing this, c , b and e become approximately equal and the expression for k may be written—

$$k = \frac{1 + \frac{2.3a}{D}}{\left(1 + \frac{2.3b}{D}\right)^3} \dots (4)$$

From this we can see that k is independent of the number of turns on the coils.

As an example of the use of this formula we will calculate the value of k for a typical IF transformer. The component has $a = 0.25$ in., $b = 1.25$ in. and $D = 0.5$ in. Substituting these values in (3)—

$$k = \frac{2.15}{6.75 \times 5.6 \times 7.9} = 0.0072$$

Substituting in (4)—

$$k = \frac{2.15}{(6.75)^3} = \frac{2.15}{307.8} = 0.0070.$$

The difference between these two values of k due to neglecting a in comparison with b in (4) is seen to be small, about 3 per cent.

It is a comparatively simple matter to derive an expression showing the percentage error introduced by the use of the approximate expression (4). Division of (4) by (3) gives—

$$\frac{\left(1 + \frac{2.3c}{D}\right)\left(1 + \frac{2.3e}{D}\right)}{\left(1 + \frac{2.3b}{D}\right)^2}$$

$$= 1 - \left(\frac{2.3a}{D}\right)^2$$

$$= \frac{\left(1 + \frac{2.3b}{D}\right)^2}{\left(1 + \frac{2.3b}{D}\right)^2}$$

Hence the percentage error

$$= 100 \left(\frac{2.3a}{D + 2.3b} \right)^2$$

Substituting the values appropriate to the above example, namely, $a = 0.25$ in., $b = 1.25$ in., and $D = 0.5$ in., we get—

Percentage error

$$= 100 \left(\frac{2.3 \times 0.25}{0.5 + 2.3 \times 1.25} \right)^2$$

= 3 per cent.

Investigation of the expression for the percentage error shows that this will not exceed about 4 per cent. provided b is more than four times a . The value of the ratio b/D does not seem to affect the error very much.

By rearrangement formula (4) enables us to design an IF transformer to have a particular value of k , thus—

$$b = 0.4375D \left(3 \sqrt[3]{\frac{1 + \frac{2.3a}{D}}{k}} - 1 \right) \dots (5)$$

We will assume that a , n and D have been fixed to give the required inductance for each winding and that the Q values of each coil, under actual working conditions, have been measured as 100. We have already shown that $k = 0.01$ for optimum amplification in these circumstances. We will suppose that the values of a and D are 0.3 in. and 0.6 in. respectively. Substitution of these values and that of k in expression (5) gives $b = 1.30$ in.,

We have already seen that the best performance is given by making k half the value for optimum amplification, i.e. 0.005 in this case. Substituting this amended value of k in (5) gives $b = 1.72$ in.

It is important to see that the values of Q which are used in calculating k should be those which obtain when the transformer is damped as in the receiver. The secondary winding of an IF transformer which feeds a diode is effectively shunted by a resistance equal to half the value of the diode load resistance. If the load is 100,000 ohms, a likely value in a high-quality superhet, this damping may be serious enough to reduce the Q of the secondary winding to half its normal value. This increases the value of k necessary to secure optimum performance and so decreases the value of b .

EXTENDING EDUCATIONAL OPPORTUNITIES

Brit.I.R.E. Annual Report

THE Annual Report of the British Institution of Radio Engineers lays stress on the fact that the advancement of radio depends upon increased educational facilities; it is a primary post-war objective of the Institution to work for the extension of present opportunities.

Many other aspects of post-war wireless have been considered by the Institution during the year under review, and a meeting has been held with the Post-War Planning Committee of the R.M.A.; liaison with the appropriate committees of other associations is foreshadowed. It is hoped that initial steps taken to bring into being a National Certificate in Radio Engineering will prove fruitful. During the year the Institution was invited to join the Parliamentary and Scientific Committee.

In all, 444 applications for membership of all grades have been received, of which 343 have been accepted (including 40 transfers to higher grades). It has been decided that first-class passes in the City and Guilds Radio Communications Grades 2 and 3 examinations, as well as a pass in Technical Electricity Grade 2, will exempt candidates from the Institution's Graduateship examination. The entire list of examinations carrying exemption has now been revised, as has also the Institution's own syllabus; as a general result, a higher standard of knowledge is called for.

“Oddness” of Standard Voltages

QUESTION No. 14.—Why was the “odd” voltage of 132,000 adopted for the main transmission lines of the Grid System?

[This matter was originally brought up by our contributor “Diallist.” Though the question deals with the raw material of wireless rather than with wireless itself, it has raised much interest, and explanations have been offered by many of “Diallist’s” correspondents. The question is now passed to our “Brains Trust,” and it is suggested that the “oddness” of supply voltages generally has its origin rather earlier in electrical history than is ordinarily believed.—ED.]

C. R. COSENS, of the Engineering Laboratory, Cambridge, provides an interesting and plausible explanation of why the extremely “odd” factor of 11 came to enter so widely into transmission and supply voltages.

IT is doubtful if the explanation given by “Diallist” is tenable; it seems unlikely that the extra 10 per cent. in voltage over the round hundred is to allow for a 10 per cent. drop in the mains. The explanation given to me by an early experimenter seems much more probable. It is as follows:—

Before the adoption of the volt, ampere, etc., as official units—and this was within living memory—EMF or PD was specified as due to so many cells of a given type (Smee, Bunsen, etc.). The chief engineering use of electricity in early days was for line telegraphy (remember that The Institution of *Electrical Engineers* was originally The Institution of *Telegraph Engineers*). The most common telegraph battery was composed of Daniell cells, which had a reasonably constant EMF, and it became customary to specify electrical pressures as equivalent to so many Daniell cells; in fact, the *daniell* very nearly attained the unofficial position now officially occupied by the *volt*. We find in the early literature of electricity such expressions as “an EMF of 50 Daniells.”

When, in 1882, it was decided to adopt a practical system of

units based on the absolute c.g.s. electromagnetic system of Gauss, with powers of 10 as conversion factors, the factor adopted for EMF was 10^{-9} , so that the new unit—the volt—should be roughly of the same magnitude as the unofficial “Daniell.” In terms of the new unit, the EMF of the Daniell cell was found to be about 1.1 volts.

But, before this, dynamos had begun to be used for generating electricity, previously only obtainable from primary batteries. The engineers adopted a round number, 100 or 200, of the then commonly used Daniell cells as their “mains PD.” When the volt arrived in 1882 they did not alter the supply pressure, but kept it at the same value of “100 Daniells,” and just re-christened it as “110 volts.” The era of DC supply, say, 1880 to 1920, saw almost all supply companies giving DC at 110 and 220 volts; there were some three-wire systems of 220-440 volts, and some tramway systems were 550 volts DC.

By about 1890 the Board of Trade had made regulations; amongst others that no conductor in a private house might be more than 250 volts PD above or below earth. Apparently the belief was held that a fatal shock could not occur on less than 250 V, though in this they were mistaken. Hence, when AC came into use, there was a tendency to go as close to this as was possible, and leaving a margin of 10 volts for possible excess over “declared” value, we often got 240 V AC; this was in “single phase” days.

Round about 1900, three-phase AC became more common; with an earthed neutral, the line-to-neutral PD might by law be as much as 250 V, giving a line-to-line voltage of 433. But many supply companies preferred to have a good round number, namely, 400 V, for the line-to-line voltage; then the line-to-neutral, as supplied to a dwelling-house, became $400/\sqrt{3} = 231$ volts.

An additional reason against the suggestion that the early en-

gineers allowed 10 per cent. for “mains drop” is found in the clause in early electricity Acts which allowed supply companies to vary the PD at the customer’s terminals by not more than ± 2 per cent. of the declared value. The penalty for greater variation was £5 a day, half of which was to go to the consumer who complained. Incidentally, it may be doubted if any supply company ever kept mains variations within anything like ± 2 per cent., so it is curious that no consumer ever availed himself of this source of income—£2 10s. a day or £912 10s. a year for life! It appears that no action under this clause ever came before the courts. Some 20 years ago the clause was dropped—presumably because the Government, themselves having assumed responsibility for the Grid, thought they might become liable! Variations of 5 per cent. or 6 per cent. are now “allowed,” but as there is no penalty for infringement, supplies very often show variations even greater than the extended allowance.

ELECTRICAL INDUSTRIES RED CROSS FUND

CONTRIBUTIONS to this Fund are still urgently required, and those firms that have not yet responded to the recent circular letter from the organisers are asked to give sympathetic consideration to the renewed appeal. The total of covenanted subscriptions and donations now amounts to about £16,500. Among the latest list of donations from wireless firms and firms with wireless interests are: Gem Mill (Ferranti, Ltd.), £14; Westinghouse Electric International Company, £7; Enfields Radio Services, £5 5s.; Ultra Electric, Ltd., £4 6s.

Information can be obtained from the Joint Secretaries of the Fund, c/o The E.D.A., 2, Savoy Hill, London, W.C.2. Contributions should be sent direct to the Electrical Industries' Red Cross Fund, St. James's Palace, London, S.W.1.

WASTE PAPER

ALTHOUGH the response to appeals for waste paper, books, etc., has been good, there is still a wide gap between the amount of recovered salvage and the country's needs, which are thousands of tons in excess of the weekly salvage collections.

RESEARCH AND PRODUCTION

Prospective and Retrospective

"FOR a period after the war—a period possibly of at least some years—a measure of Government control of industry, including the radio industry, is likely to be necessary." Mr. Garro-Jones, Parliamentary Secretary to the Ministry of Production, made this remark when speaking on "Radio Research and Production Before, During and After the War," at a recent meeting of the Radio Industries Club.

During his speech he drew some interesting comparisons between the pre-war and present position of the industry. In pre-war days about 80 per cent. of the 80 specialist firms comprising the radio industry, which had an annual turnover of about £25,000,000, was devoted to the production of broadcast receivers. The remaining 20 per cent. was devoted principally to the production of broadcasting transmitters and telecommunications apparatus. The ratio of skilled to unskilled labour in firms producing broadcast sets was of the order of 1:30, and in the firms

producing communications equipment it was about 1:10.

Four years of war have seen a very great transformation in the industry. Virtually the whole of the present output, which is many times greater than before the war, consists of operational equipments for the Armed Forces. "In fact," said Mr. Garro-Jones, "production of broadcast receivers for civilian use has been curtailed to such a degree that the manufacture of additional receivers for British homes is now becoming an urgent matter." Many types of apparatus which are now produced for the Fighting Services are very different in

character from pre-war productions. A higher degree of technical skill in production is therefore necessary in a large number of cases (for example, in many radiolocation equipments the required percentage of skilled/unskilled labour was at one time of the order of 1:4 and is still of the order of 1:8).

Mr. Garro-Jones said the radio laboratories of the defence services, though under-staffed, under-equipped and under-financed, had done solid work, of a development rather than a research kind, on equipment which, like much of the military equipment here and in Germany,



{SHIP-TO-SHORE communication between landing parties and headquarters vessels is essential in invasion. A Signals Section on the Sicilian beach is shown establishing communication with a Signals station afloat (see our cover illustration). Complete stations mounted in "prams," as shown left, were brought ashore during the landings

was doomed to be obsolete before the great clash came. Radiolocation was, he said, by far the most important national asset ever to emerge from the National Physical Laboratory. It was a natural but not inevitable synthesis of techniques developed within the Radio Research Board's programme. It revived the laboratories of the defence services. The wisdom of Sir Edward Appleton and of Sir Henry Tizard and his colleagues of the Tizard Committee, supported as they were by the Government and its highest advisers, not only contributed to

Research and Production—

save our country, but to the reshaping and enlargement of the radio industry.

A "common meeting ground for the service man and the scientist" is now provided by the Operational and Technical Committee of that "still young organ of the War Cabinet," the Radio Board. "Our radio world," said Mr. Garro-Jones, who is chairman of the Production, Planning and Personnel Committee of the Radio Board, "is a technical democracy in which the civilian junior scientific officer hears directly from the Admiral's mouth what he wants, and the Air Marshal hears from the junior civilian's mouth what he ought to want and why."

Referring to the post-war application of new devices such as radiolocation, which, incidentally, is now officially given the American name "radar," the speaker pointed out that in the civil aviation and mercantile marine fields many radio aids to navigation, etc., can only be fully effective if introduced on an international basis and with international agreement not only in regard to wavelengths, etc., to be employed, but also in regard to standardisation of the facilities. Technical progress on ultra-short wavelengths, resulting from wartime research and development, has opened up the possibility of new national broadcasting services of a quality which was unobtainable in the overcrowded

pre-war long-wave and medium-wave broadcast bands.

FM AND FOLIAGE

MEASUREMENTS taken in Milwaukee, Wisconsin, have shown that the foliage on trees has an adverse effect on the reception of frequency-modulated transmissions.

The president of FM Broadcasters, Inc., states it has been proved that within the 1 mV/m service area of an FM station there was a fall in signal strength during the summer of an average of 15 per cent. where receivers were installed in houses completely surrounded by trees. Outside the ½ mV/m area the drop in signal strength is said to average as much as 50 per cent. The strength of the signal increased considerably during the autumn and winter.

NEWS IN ENGLISH FROM ABROAD**REGULAR SHORT-WAVE TRANSMISSIONS**

Country : Station	Mc/s	Metres	Daily Bulletins (BST)	Country : Station	Mc/s	Metres	Daily Bulletins (BST)	
America				India				
WKR D	5.985	50.12	0600, 0700, 0800, 0900	VUD3 (Delhi) ..	7.290	41.15	0800, 1300, 1550	
WLWO (Cincinnati) ..	6.080	49.34	0600, 0700	VUD4	9.590	31.28	0800, 1300, 1550	
WBOS (Hull)	6.140	48.86	0900, 1000‡	VUD3	15.290	19.62	0800, 1300	
WCBX (Brentwood) ..	6.170	48.62	0500	Mozambique				
WGEA (Schenectady) ..	6.190	48.47	0515, 1000‡	CR7BE (Lourenco Marques)	9.830	30.52	1155, 1712, 1915	
WKTM	6.370	47.10	0600, 0700, 0800, 0900	Newfoundland				
WLWO (Cincinnati) ..	7.575	39.60	0900	VONH (St. John's) ..	5.970	50.25	2315	
WKR D	7.820	38.36	0000, 0100, 0200, 0300, 0400, 0500, 1000‡, 1100, 1200, 2300	Spain				
WCRC (Brentwood) ..	9.650	31.09	0600	EAQ (Aranjuez) ..	9.860	30.43	1815	
WNBI (Bound Brook) ..	9.670	31.02	0000	Sweden				
WKR D	9.897	30.32	2100	SBU (Motala)	9.535	31.46	2220‡	
WKR X	9.897	30.32	0100	Switzerland				
WCRC (Brentwood) ..	11.830	25.36	1100, 1200, 2045	HER3 (Schwarzenburg) ..	6.165	48.66	2150	
WGEA (Schenectady) ..	11.847	25.33	1200, 1300, 1500‡, 1600, 1700	HER4	9.535	31.46	2150	
WKR D	12.967	23.14	1300, 1500‡, 1600, 1700, 1800	Syria				
WLWO (Cincinnati) ..	15.250	19.67	1400, 1500, 2200	Beirut	8.035	37.34	1820	
WCBX (Brentwood) ..	15.270	19.65	2045	Turkey				
WGEO (Schenectady) ..	15.330	19.57	1100, 1200	TAP (Ankara)	9.465	31.70	1800	
WRUV (Boston)	17.750	16.90	1500‡, 1600	U.S.S.R.				
WLWO (Cincinnati) ..	17.800	16.85	1700, 1800, 1900, 2000	Moscow	5.890	50.93	2100, 2200	
Algeria					6.980	42.98	1800, 2200, 2300	
Algiers	8.965	33.46	1600, 1700, 1800, 2100, 2200		7.300	41.10	1800, 2000, 2100, 2200	
	12.110	24.77	1700, 1800, 2100		7.330	40.93	2000, 2100, 2200	
Australia					7.560	39.68	2100	
VLG3 (Melbourne) ..	11.710	25.62	0800		10.445	28.72	1240	
VL12 (Sydney)	11.872	25.27	0800		11.830	25.36	1600, 1700	
Brazil					12.190	24.61	1240	
PRL8 (Rio de Janeiro)	11.715	25.61	2030‡		15.230	19.70	1240, 1515	
China					15.750	19.05	1240	
XGOY (Chungking) ..	9.635	31.14	1500, 1700, 2130	Vatican City				
Egypt					HVJ	5.970	50.25	1915
Cairo	5.785	51.85	1125, 1740	MEDIUM-WAVE TRANSMISSIONS				
	7.510	39.94	1125, 1740	Ireland				
French Equatorial Africa					Radio Eireann ..	565	531	1340‡, 1845, 2210
FZI (Brazzaville) ..	11.970	25.06	2045					

It should be noted that the times are BST one hour ahead of GMT. The timing of some of the bulletins may be changed to compensate for the reversion to BST. ‡ Sundays excepted.

WORLD OF WIRELESS

B.B.C. CONSTITUTION

REFERENCE was recently made in the House of Commons to the constitution of the B.B.C. and the lack of effective Parliamentary control over its activities and organisation. In reply, the Minister of Information said the charter of the B.B.C. was approaching its end [actually December, 1946] and Members would do a great deal of good in pressing for a "complete examination of the whole set-up of the corporation." He added: "While it had made many mistakes, it was the best broadcasting organisation in the world, and the European section had fulfilled the best hopes."

FREQUENCY ALLOCATIONS

THE use of ultra-high-frequencies for the U.S. airways communications instead of the 200 to 400-kc/s band is foreshadowed in a recent statement issued by the Office of War Information regarding the post-war reorganisation of American airways.

It is pointed out by the Civil Aeronautical Authority that the immediate post-war problem of the airways will be "to rebuild the [communication] system by substituting ultra-high-frequencies for the old standard intermediate frequencies."

The proposed change is bound to have repercussions on existing ser-

vices in the UHF band and also on the anticipated extension of FM broadcasting.


Commenting on the proposal, our American contemporary *Broadcasting* points out that whilst the 200 to 400-kc/s band is well suited for broadcasting there is some inclination towards a greater use of the top end of the frequency spectrum for post-war broadcasting. The situation will also be aggravated by the proposed use of UHF relay stations for FM networks.

It is obvious from this and other recent statements on the post-war allocation of frequencies that it will be necessary to have an international telecommunications conference to settle this vexed question. The last telecommunications conference was held in Cairo in February, 1938.

"FATHER OF RADIOLOCATION"

THE Honorary Degree of Doctor of Laws was recently bestowed upon Sir Edward Appleton, K.C.B., F.R.S., Secretary to the Committee of the Privy Council for Scientific and Industrial Research, by Lord Cecil, Chancellor of Birmingham University.

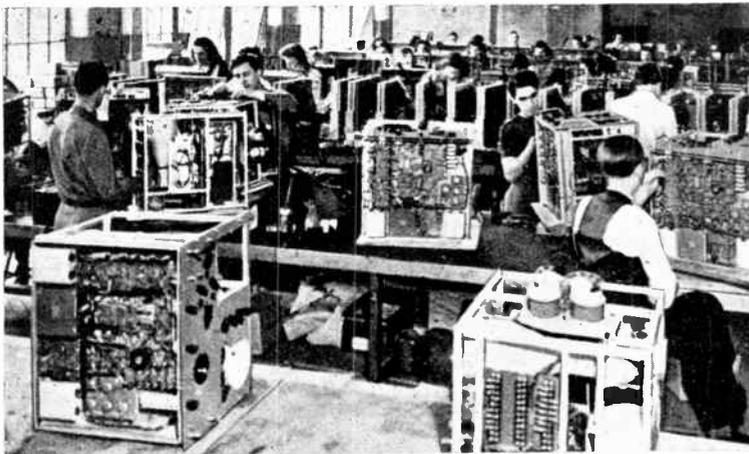At the investiture, Prof. Ritchie, the University's Public Orator, welcomed Sir Edward as the one "responsible for the whole of the Government activities in research in physical sciences." He said: "As the result of his dealings with



RADAR equipment for the U.S. Navy in process of production at a General Electric factory in New England. This is the first photograph to be released from the States showing, with any degree of clarity, the construction of radar sets.

OF OUR
ABILITIES
AND
FACILITIES
WE GIVE
GLADLY



PARAMOUNT above all else is the necessity of meeting urgent and immediate demands for the protection of cherished liberty.

Astatic's engineering and manufacturing facilities are therefore first at the disposal of Allied Governments.

Astatic will be ready to serve you again with high quality piezo-electric devices when the "All Clear" of Victory sounds.

Register your name with our Representative for your future benefit.


ASTATIC

THE ASTATIC CORPORATION
YOUNGSTOWN, OHIO, U.S.A.
TORONTO, CANADA.

—Exclusively Represented by—
Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon

G. I.

VICTORY PRODUCTION

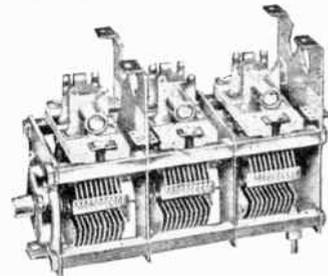

WHEN the mission of complete victory is accomplished, General Instrument will help "Win the Peace" by making the best use of still greater knowledge and experience in the manufacture of variable condensers and drives.

THE GENERAL INSTRUMENT CORPORATION
ELIZABETH, N.J., U.S.A.

—Exclusively Represented by—
Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon

World of Wireless—

the upper air, Sir Edward Appleton became the father of radiolocation. It was a relatively simple step to pass from the observation of reflecting layers in the upper atmosphere to the detection of aircraft. . . . The methods of radiolocation differ only in detail from those devised by Sir Edward from the study of a purely scientific problem. In other words, he is among the few, the glorious few, who won the Battle of Britain."

SHORT WAVES FROM NORTH AMERICA

ACCORDING to the latest figures given in the States, there will probably be 36 short-wave broadcasting stations radiating programmes overseas by July, 1944. In June, 1942, there were only 14 transmitters in use.

The power of some of the new transmitters, which are being erected as quickly as manufacturing facilities permit, will be as high as 250 kW.

Originally it was planned to employ 22 transmitters on the East Coast and 14 along the Pacific Coast, but later developments of war may necessitate a change being made.

The 22 new transmitters planned for erection during the next year are being allocated to the seven companies operating the existing stations.

NEWS IN MORSE

FOLLOWING requests from readers for details of the schedule of transmissions of news bulletins in morse, we are giving below the latest information regarding these broadcasts from the G.P.O. stations, which, although intended for overseas listeners, may, under suitable conditions, be heard in this country.

The call signs, which include two new ones—GCP and GBC5—and the wavelengths employed for these transmissions are:—

GIA: 15.27 m.	GIM: 23.13 m.
GAD: 15.40 m.	GCP: 27.86 m.
GBI: 20.47 m.	GHI: 28.17 m.
GID: 22.13 m.	GAY: 33.67 m.
GBC5: 34.56 m.	

The times (GMT) of the broadcasts and the transmitters radiating them are:—

0048: GBC5, GIJ.
0030: GIA, GID, GHI.
1302: GAD, GIA, GID.
1602: GAD, GIA, GID.
1800: GIM, GCP, GAA.
2000: GIM, GBC5.

In addition to the above, the B.B.C. radiates bulletins in morse at 0030, 0100 and 0130 (GMT) in English, German and French respectively. These transmissions are radiated on a number of wavelengths in the 49-, 41- and 31-metre bands.

Wireless World**AMERICA'S BLUE NETWORK**

IT is learned that the American chain of broadcasting stations originally operated by the National Broadcasting Company as the Blue Network has been sold by Radio Corporation of America, the parent company, to Edward J. Noble, millionaire candy manufacturer. Temporarily known as the Blue Network Company Inc., it includes 157 medium-wave broadcasting stations. Three of these transmitters, WJZ, New York, WENR, Chicago, and KGO, San Francisco, are owned by the company, the remainder being affiliated on a time basis.

The company proposes having news reporters in Cairo, Algiers, Stockholm, Moscow, and Ankara. George Hicks is the European manager, with offices at 2, Mansfield Street, London, W.1.

AWARDS TO RADIO OFFICERS

LOYD'S War Medal for "Bravery at Sea," which is struck in silver with a ribbon of blue and silver, is bestowed upon officers and men of the Merchant Navy and Fishing Fleets in cases of exceptional gallantry at sea in time of war. The latest list of awards includes the names of Radio Officer Ernest Sturdy (deceased) and Radio Officer Thomas Simkins. Radio Officer Sturdy remained in his cabin to send out a distress message after his ship was torpedoed. The ship sank quickly and he was drowned. Radio Officer Simkins' ship was hit and set on fire by Japanese bombers in Far Eastern waters. During the attack Radio Officer Simkins showed fearlessness in climbing the ship's mast to renew the aerial, which had been destroyed.

The George Medal has been awarded to Chief Radio Officer Donald Wilfred Dennis who, when his ship was torpedoed and set on fire, volunteered to release the only undamaged boat. Although he was

badly burned, he crawled through the flames on his hands and knees and released the falls. Throughout he displayed outstanding courage and fortitude; but for his brave act the boat would not have got away and there would have been few, if any, survivors.

The King has approved the appointment as a Member of the Order of the British Empire (Civil Division) of Chief Radio Officer Bert King, who displayed outstanding courage and devotion to duty, remaining on board his torpedoed ship until it sank.

FM PROGRESS

AMERICANS' confidence in the future of FM broadcasting is shown by the number of applicants for FM transmitting licences.


In addition to the 50 or more stations already operating and those for which construction permits have been granted although they are not yet in operation, there have been applications for licences for the erection of 40 more.

A number of stations already in use are operated by educational authorities. The transmissions from the station operated by the San Francisco Board of Education are received by 80 schools in the San Francisco area.

FLYING FORTRESS RADIO

THE successful daylight sorties over Germany of Flying Fortresses of the U.S. Eighth Army Air Force operating from this country makes it opportune to give a few details of the planes' radio equipment.

The radio operator, who, because he is a trained gunner and has a 0.5 calibre machine-gun in his cabin, is sometimes referred to as a radio gunner, has to operate a comprehensive array of apparatus. It includes duplicate "command" transmitters and receivers for inter-communication between planes in the formation and what is known as a liaison set, which is for communication with the base from which the plane is operating.

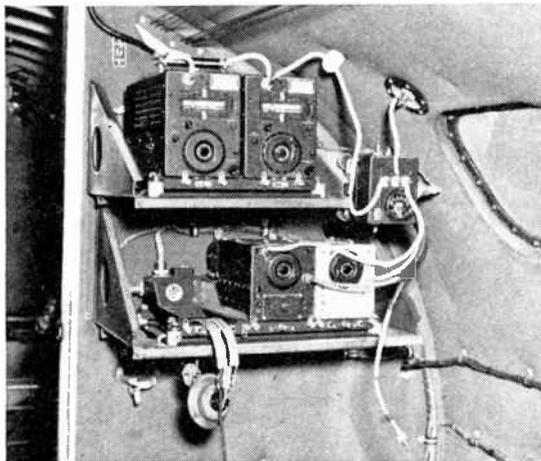

A CORNER of the operator's quarters in a Flying Fortress showing the duplicated transmitters (top) and receivers (bottom) for inter-communication between planes in the formation. The unit on the right is the aerial switching relay.

There is also the usual blind-landing apparatus, crew intercommunication gear, and radio compass. In addition there is a UHF combined transmitter-receiver.

The operator's job is largely one of listening, but he has to be capable of sending morse at 16 w.p.m.

All aviation communications equipment is maintained by personnel of the U.S. Signal Corps attached to the Eighth Air Force Service Command.

POST-WAR PLANNING

A POST-WAR planning committee, with terms of reference covering radio manufacturing and research, was proposed by the U.S. Radio Manufacturers' Association at its recent annual conference. The necessity for a comprehensive plan embracing all radio services, both transmitting and receiving, was emphasised by J. L. Fly, chairman of the Federal Communications Commission. "After this war," he said, "we must ensure that all phases of radio will be re-established on a firm and spacious foundation. Not the least challenging of our ultra-modern developments is the opening of the limitless ranges of the higher frequencies. We cannot satisfy all the demands for frequencies and yet the problem must be constantly considered."

U.S. VALVE POSITION

A WEAKNESS in the method of distribution has allowed large quantities of valves manufactured for the express purpose of maintaining civilian sets in the States to fall into the hands of set manufacturers with the result that there has been an acute shortage of replacement valves for the public.

In an unsuccessful endeavour to stop the leakage, valves were marked "MR" (maintenance and repair). The latest order makes it illegal for "MR" valves to be used for any other purpose than for the maintenance and repair of civilian sets.

According to the U.S. Radio Manufacturers' Association, some 2,000,000 valves were manufactured monthly during the beginning of this year for civilian requirements.

IN BRIEF

"Picture by Wireless."—A radio photo-telegraphic service between London and Montreal was opened a few days before the arrival of the Prime Minister and his party in Canada. Cable and Wireless are operating the terminal on this side of the Atlantic, and the Canadian Marconi Company that on the other side.

Canadian Wireless School Subsidised.—The Minister of Munitions in the Canadian House of Commons obtained approval for a sum of approximately £25,000 for the subsidisation of

radio operator students taking a course at a school operating in association with the University of Toronto. Students receive a small salary when taking the course.

Second-hand Sets in Canada.—An order issued by the Wartime Prices and Trade Board in Canada establishes a maximum selling price schedule for used receivers and valves. The dealer must guarantee every used set sold and prices are based on the age and type of set. The price charged for a used valve must not be more than 25 per cent. of the price charged in the same district for the same kind of valve when new.

B.B.C. News on Short Waves.—It should be noted that the times given in this schedule of B.B.C. transmissions of news in English on short wavelengths, which will be operative when this issue of *Wireless World* appears, are BST (one hour ahead of GMT).

0015†	...	25.53, 25.68, 30.53, 31.32
0200	...	25.53, 25.68, 30.53, 31.32, 42.46
0345	...	25.08, 30.53, 30.96, 31.32, 41.96, 42.13, 42.46, 48.43, 49.10
0530	...	25.68, 30.53, 30.96, 31.32, 42.13, 48.43, 49.10
0605 }	...	16.92, 19.01, 25.38, 25.47, 25.53,
0715 }	...	25.68, 30.53, 31.25, 31.55, 42.13
0830	...	16.92, 19.01, 25.53, 25.68, 30.53, 31.55, 42.13
0900	...	24.80, 25.58, 31.12, 31.25, 31.32, 31.61, 31.75, 31.88, 41.01, 41.32, 41.90, 42.46, 48.43, 49.59, 49.98
0958	...	16.92, 19.44, 19.60, 19.91, 25.53, 25.68, 31.55
1200 }	...	13.97, 16.64, 16.79, 16.84, 19.44,
1400 }	...	19.60, 19.91, 25.53
1600	...	13.97, 16.64, 16.79, 16.84, 16.92, 19.44, 19.46, 19.60, 24.02, 25.68, 31.55
1700	...	16.59, 16.64, 16.92, 19.66, 25.53
1745	...	25- and 49-m bands
1900	...	16.92, 19.60, 19.82, 25.20, 25.53, 31.75, 42.46
2145	...	16.92, 19.66, 25.20, 25.53, 30.53, 31.25, 31.41, 31.55, 31.88, 41.40, 41.75, 41.96, 42.46, 48.98, 49.42, 49.92
2245†	...	25.53, 25.68, 30.53, 31.32
2300	...	31.25, 42.46
2345	...	25.53, 25.68, 30.53, 31.32

† Sundays only. ‡ Sundays excepted.

Institution of Electrical Engineers.—It is proposed by the committee of the South Midland Centre of the Institution to form a Wireless Group. A questionnaire is being circulated to members of the Centre to ascertain their interest in wireless or high-frequency engineering, and whether they would be prepared to support the idea of a Wireless Group and attend meetings. Particulars may be obtained from H. Hooper, Hon. Secretary, 65, New Street, Birmingham.

Radio Relays.—An increase of 12,871 subscribers in the three months to March 31st last is revealed by latest radio relay statistics. At this date there were 447,944 subscribers.

Canada and Radio.—As a result of a survey of radio in the Dominion of Canada, it is estimated that 1,900,000 homes out of 2,700,000 own receivers.

Brit.I.R.E. Officers.—The appointment of the new officers of the British Institution of Radio Engineers, as given in our August issue, does not become effective until the annual general meeting. The meeting has been arranged for 6.15 on Thursday, September 16th, at the Institution of Structural Engineers, 11, Upper Belgrave Street, London, S.W.1.

RANDOM RADIATIONS

By "DIALLIST"

Utility Sets

SO far I have made no comment on the proposed utility broadcast receivers that may be one of the features of life in wartime, but I feel now that I would like a word or two. There is much to be said both for and against the scheme. Its main "pros" are that it offers a way of providing the public with respectable quantities of receivers at moderate prices, and that these simple, more or less standardised sets should make the problems of servicing and of component replacement easier than they are now. The "cons"? Well, the utilities naturally won't be high-class performers as regards either sensitivity or quality of reproduction. Some manufacturers fear that once the public finds that such cheapish sets are good enough for bringing in the news bulletins and some entertainment from the local station, it will never go back to the better set when it is available again. I don't believe a word of that. For more than a dozen years many manufacturers have, in my view, taken an unwise line in educating the public not *up* but *down* to the kind of set that was selling at from £8 to £12 or thereabouts before the war. And a large section of the public showed that it wanted something better, refusing to go as far down the slippery slope as some sections of the industry would have led them. Moreover, a set with poor sensitivity and selectivity, though it may answer during the war, will hardly be good enough afterwards. Any retailer will tell you that the first question he is asked about a set by nine prospective buyers out of ten is: How many foreign stations will it bring in? The fact that the enquirer, having turned from a prospective into a real purchaser, seldom listens to anything but the local station after the first month has passed is neither here nor there; sensitivity and selectivity are the qualities of a wireless set uppermost in the mind of the man-in-the-street, and he's jolly well going to have them when he buys his peacetime receiver.

No Harm Done

All things considered, then, the utility set is no more likely to influence post-war tastes than the utility suit. The man-in-the-street will regard it as just as much of a wartime makeshift. As soon as may be after peace has returned, his two-valve utility set will follow the depocketed jacket and the turn-up-

less trousers of his utility suit to the jumble sale. What we need now—and the need is growing daily as more and more ancient receivers become beyond repair—is a set that can be provided in large quantities by such semi-skilled labour as is available in the factories. Numbers are the great thing, and in wartime we can't have sufficient quantities of the more elaborate sets that would normally be produced. In the ordinary way I'm all against lowering the price and the performance of sets: I do not much mind whether the manufacturers turn out station-getters or not so long as they don't try to make the public believe that wireless reproduction must have no top and a carpet-beater bass; but in wartime I am quite prepared to accept the utility set as a temporary expedient, believing, as I do, that when happier days return it will pass, leaving behind it as few regrets as will soya-bean sausages, wooden-soled shoes, five-inch socks, and all the other minor horrors of war.

□ □ □

Early Complex Valves

A CORRESPONDENT reminds me that one of the reasons for the production of two-in-one and three-in-one valves in the mid-nineteen-twenties was the queer royalty system for wireless sets which then prevailed. He is quite right: I had clean forgotten what was perhaps the main reason why, in its early days, popular wireless reception developed along such different lines here and in the U.S.A. Any British set that you bought had to add to its price a royalty of so much per

valve holder. Motor cars were handicapped in much the same way by the horse-power tax. Neither of these things obtained in America. Over there cars rated at 20-30 horse-power were the popular models. Here manufacturers strove to get the last ounce out of small engines. Similarly, quite early American domestic receivers contained numerous valves, whilst two or three, all working fit to bust, were for a long time the rule here. Then the Loewe Company had the brilliant idea of fitting two or more electrode assemblies, with coupling resistances and condensers, all into one gigantic bulb which could be inserted into a single holder. Later we continued to suffer badly from the same few-valve-holder complex, even when this form of royalty had gone: we designed valves with slopes like the side of a house and continued to work them all out: seldom, in fact, can so much have been done for so many by so few. Later still we went all complex-valve minded, largely because the ordinary man was afraid of the expensive replacements that might be needed if he bought a set containing more than four valves, excluding the rectifier. I hope sincerely that after the war we shall enter an era of bigger and better sets, containing simpler valves and more of them.

□ □ □

Grid System Voltages

EVERY month brings me a goodish number of letters from readers, all of them interesting and most of them helpful. But never before has there been such a mass

Books issued in conjunction with "Wireless World"

	Net Price	By Post
FOUNDATIONS OF WIRELESS, by A. L. M. Sowerby. Third Edition, revised by M. G. Scroggie ...	6/-	6/4
TELEVISION RECEIVING EQUIPMENT, by W. T. Cocking ...	10/6	10/10
RADIO LABORATORY HANDBOOK, by M. G. Scroggie. Second Edition ...	12/6	12/11
WIRELESS SERVICING MANUAL, by W. T. Cocking. Sixth Edition ...	7/6	7/10
HANDBOOK OF TECHNICAL INSTRUCTION FOR WIRELESS TELEGRAPHISTS, by H. M. Dowsett and L. E. Q. Walker. Seventh Edition ...	27/6	28/1
WIRELESS DIRECTION FINDING, by R. Keen. Third Edition ...	30/-	30/7
RADIO INTERFERENCE SUPPRESSION, by G. W. Ingram ...	5/-	5/4
LEARNING MORSE. 335th thousand ...	6d.	7½d.
INTRODUCTION TO VALVES, by F. E. Henderson ...	4/6	4/10
VALVE REPLACEMENT MANUAL, by A. C. Farnell and A. Woffenden ...	6/-	6/2

Obtainable from leading booksellers or by post from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1

of correspondence as was evoked by my innocent query, "Why was 132 kV adopted as standard for the main transmission lines of the Grid System?" Since I wrote on this subject last month, more letters have come in, and more information can be pieced together. First of all, the most economical way of sending power over long distances is to use the three-phase system. For industrial purposes a three-phase supply at 400 volts is required; for household heating, lighting and so on one phase of a star system is used, and the voltage here is, of course $400/\sqrt{3}$, or 230 volts. In order that 400 volts may be ensured in the final distribution lines it is necessary to allow an ample margin in main and subsidiary transmission lines. Ten per cent. had been found by experience to meet requirements here. Hence, though 10,000 was the nominal voltage of short-distance transmission lines, 30,000 or 60,000 that of secondaries, and 120,000 that of main grid lines, the working voltages were fixed at 11,000, 33,000 or 66,000 and 132,000 respectively.

How It Works Out

For certain main alternators a voltage of 6,600 had been found to be a satisfactory figure. A twenty-fold step-up by means of transformers gave the main transmission line voltage of 132,000, or 120,000 plus ten per cent. Before the Central Electricity Board came into being there were already lines with voltages of 66 kV, 33 kV and 11 kV in existence, and integral transformation ratios enabled these to be brought into the system. Thus the apparently odd figure of 132 kV, with its factors of $4 \times 3 \times 11$ is seen to have been the result of careful calculation. It is curious that, though I have more than once put the question to electrical engineers and have heard it discussed between them, I never had a completely satisfactory answer until readers of *Wireless World* took a hand.


Early History

Having just had a few days of blissful and blessed leave at home I have been able to get at some of my reference books and to dig out some rather interesting facts. Apparently the highest transmission line voltage used in this country prior to 1922 was some 40 kV. In 1926 this had risen to 66 kV, used by the County of Durham Electric Supply Company. Much higher voltages had been used to cover the greater distances that had to be spanned in other parts of the world. Until the suspension type of insulator was introduced 66 kV was the upper limit; but by 1911

100-110 kV lines were in operation in Canada, the United States and Germany. In the next five years systems with voltages up to 165 kV were developed in many countries. By 1926 the U.S.A. had four 220-kV lines built or building and a fifth planned. The Boulder Dam line is designed for 276 kV. A line voltage of 132 kV was in use in Sweden and in Australia before our system was established. Two factors have contributed in recent years to the solution of the problem of sending electric power economically over great distances: improvements in insulators and improvements in conductors. In the early days of electric power transmission the "pin" type insulator limited the line voltage, as I have mentioned, to about 66 kV. Copper conductors were used in all lines and with such a voltage they had to be of large sectional area in order to avoid undue losses. This meant that what may be called the economic radius of a generating station was comparatively small: if transmission lines were made longer, overhead costs made it impossible to supply power at a price attractive to the user. Improvements in the design and construction of insulators more than trebled the maximum safe line voltage, with a consequent reduction in the sectional area of conductors, though it must be remembered that for a given high-tension voltage the thickness of the conductors cannot be reduced below a certain definite figure if serious losses from corona effects are to be avoided. Then came the invention of the steel-cored aluminium conductors. Not only is this cheaper than copper, but it has also greater tensile strength: spans can be longer and, therefore, fewer pylons are needed.

The Future

In days to come I have no doubt that electric power will be conveyed economically over far greater distances than we wot of to-day. Possibly such a development won't affect this small country enormously—though one wonders what bearing it may have on the future of the electric scheme for the Highlands of Scotland, which can rely on vast and hitherto untapped resources of water power. But in many other parts of the world it may lead to developments undreamt of to-day. Even here it may bring us to utilise for heating, lighting and industrial purposes sources of power that are at present running to waste. Have you, in your travels in these islands, ever seen the Falls of Lora at Connell Ferry, near Oban? There must be a vast amount of power available here.

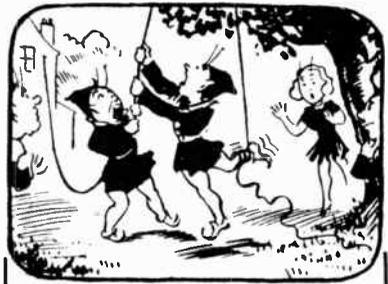

THE "FLUXITE QUINS" AT WORK

"Now don't lark about!" hollered EE;
 "This aerial's mixed up with the tree.
 There'll be work for FLUXITE,
 When this wire is fixed right;
 But for goodness' sake—leggo of me!"

See that FLUXITE is always by you — in the house — garage — workshop — wherever speedy soldering is needed. Used for over 30 years in Government works and by leading engineers and manufacturers. Of all Ironmongers—in tins, 8d., 1/4 and 2/8.

Ask to see the FLUXITE SMALL-SPACE SOLDERING SET—compact but substantial—complete with full instructions, 7/6.

TO CYCLISTS! Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 1/6, or filled, 2/6.



ALL MECHANICS WILL HAVE

FLUXITE

IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT" SOLDERING and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d. each.

FLUXITE LTD.

(Dept. W.W.), Bermondsey Street, S.E.1

Letters to the Editor

In Support of the Wire • 10 kc/s Separation?

Wire versus Wireless

HAVING had some years' experience in broadcast relay over wires, which is akin to wired broadcast, besides in radio service and sales and, at present, radio manufacturing, perhaps I may be permitted to make a few observations on the subject?

First, neither your Brains Trust members nor your Editorial provide very solid arguments against P. P. Eckersley's proposals. You all seem concerned with the fact that wired broadcast will be controlled by the Government or other dictatorial body (surely this is true of open broadcast at present?) and, judging by some of your remarks, none of you seem to have much faith in the democratic Governments *you* will elect in this "new" world!

Secondly, much is made, by those in favour of open broadcasting, of the enormous number of programmes available on an all-wave set (with or without interference, fading, etc.!). (Yes, Madam, Timbuctoo easily on an indoor aerial!) Go into nine houses out of ten (ours included) on any day and what will you find grinding out of the loud-speaker? Either the Home or the Forces programme! As far as I can see, it makes little difference whether the Home or Forces is coming over the air or by wire—except that by wire the reception would, in many cases, be better.

Thirdly, I think I detect, in those who argue against wire broadcasting, a somewhat shaky feeling as to what would happen to the radio receiver market and their future positions, should wire broadcasting come to stay. Personally, I think anything would be better than the Awful Mess that was known as the "Radio Trade" in the latter pre-war years!

Fourthly, to summarise: in my opinion Eckersley has stated well the case for wire broadcasting, but there are, of course, difficulties in initiating the service and, for the immediate future, it seems to me the best thing is (as usual) compromise. Provide receivers which operate on either wired or

Pick-up Filters

open broadcast, also television, reducing, where possible, the number of radiating broadcast stations on the various wavebands. D. W. HEIGHTMAN.

Clacton-on-Sea, Essex.

I READ last month's Editorial, and also the views of your "Brains Trust" on that much mooted question "Wired Broadcasting—or Not"! In the first place I am disappointed that the Brains Trust feature should be used for political discussions, not because it was any the less interesting, but while I respect the technical opinions of your contributors, I feel that they are in no way qualified to talk politically. In fact, having read what they have to say, I am more than ever inclined to think favourably of the scheme as outlined by P. P. Eckersley.

Two red herrings would appear to have crossed the path of unbiased technical discussion on this subject, namely: (a) What effect will the introduction of wired wireless have on receiver sales? and secondly: (b) We shall be entertained, educated and "propagated" on the lines laid down by the Government, and that we are to be precluded from hearing the numberless contrasting views put out by the rest of the nations of the world.

With regard to (b)—what utter nonsense!

I cannot see why *both* systems should not exist side by side. I think, moreover, that if some of the programmes were transferred "underground," that more room would be available in those already overcrowded wavebands for that "infinite variety of programme material which will emanate . . . after the war." (And with a better chance of hearing it too!)

Perhaps your contributors would show how "the Government" does not now influence the matter radiated by that great monopoly, the British Broadcasting Corporation; or rather, which

is perhaps more important, how we should be any the worse off politically if the B.B.C. did feed some of their programmes over wires instead of "over the air."

There has never been any question that ordinary radio broadcasting should be given up for wire broadcasting even less so that the household set should be "purged" and a ban placed on foreign listening. Coming back again to the first bogey, I believe that the system should be introduced and that manufacturers should produce a unit to detect the "wired" signals, employing the ordinary household set as an amplifier. In due course a set could be sold which would combine the detection and tuning unit with the normal all-wave receiver.

No! I cannot see any justification for the sombre views expressed on the outcome of the effects, both politically and technically, of the introduction of "wired wireless."

J. GIBBONS-PARTRIDGE.
Lower Castlereagh, Co. Down.

I CONSIDER your attack on the G.P.O. and your arguments against "wired wireless" entirely ill considered; your Editorial and "Brains Trust" contributions carry all the stamp of Left Wing hysteria. There is no connection between a Nazi workshop and a democratic home. In a democracy a person is free to buy the form of broadcasting receiver he fancies, and can subsequently switch off any programme he dislikes, so that if his receiver emits unwanted opinions or noises, he has the remedy!

Furthermore, to state that distance-getting is the greatest "magic" of broadcasting receiving is entirely to ignore the facts. My experience in hundreds of homes has proved to me that the public in general do not "listen-out." The station-getting facilities were entirely wasted. When Radio Normandie and Luxembourg were available, seven out of ten sets appeared to be permanently tuned to them; two of the other three listeners were con-

cerned mainly in not missing Henry Hall's programme, and the odd one was generally a quality fan who used Continental programmes only when there were no "Proms." Short waves were not understood, and in any case were too difficult for most people.

In conclusion, I affirm that the public can get all they want, including quality, from wired broadcasting without paying exorbitant prices for complicated competitive apparatus they cannot use, and I think it is this fact that is causing misgivings amongst those mainly concerned with unloading so-called "new" models year by year by means of the "hot salesmanship" of which you accuse the G.P.O.

H. F. LESLIE.

London, N.W.7.

Post-war Broadcasting

I WOULD like to put forward a suggestion which I have never seen mentioned so far. It is simply to standardise the spacing of transmitters in Europe at 10 kilocycles.

The advantages of this are many. First, perhaps most important, heterodyne interference is almost entirely eliminated—as anyone who has operated a receiver in the U.S.A. or Australasia can testify. Chance heterodynes between transmitter harmonics, etc., are never less than 10 kc/s. Secondly, the fidelity of the reception can be slightly improved. Thirdly (another important reason), it would bring Europe into line with the U.S.A., Canada, South and Latin America, Australia and New Zealand. About two-thirds of the world's transmitters are located in these countries, which all have 10-kc/s spacing. Fourthly, since we already think in decimal terms of kilocycles, megacycles, etc., it would be much more convenient if the stations were spaced decimally, and had frequencies such as 660, 1210, 9,340 kc/s. Fifthly, it would simplify the calibration of receivers and identification of transmitters. This may seem an unimportant point, but if a dial is divided by radial lines, each spaced 10 kc/s, as they often are, then a station will always be tuned in on one of these lines. Then, if an unknown transmission is received, its *exact* frequency

can be read off even if the receiver is mis-calibrated by ± 3 or even ± 4 kc/s, since its frequency will be that of the nearest 10-kc/s mark. At present the dial must be calibrated accurately to ± 0.4 k/c (or 400 cycles) at least, to find the exact frequency of a station.

Now, if ever, is the time to prepare for this change—a change which is essential if post-war broadcasting is to run smoothly.

P. D. THOMAS.

Ayr.

"Visual Frequency Comparison"

WE notice that the August issue of *Wireless World* contains an article describing the use of a "magic eye" tuning indicator as a frequency comparator. We would like to place on record that this method has been used in our GM2304 audio oscillator since early 1938.

A. W. RUSSELL,


The Mullard Wireless Service Co., Ltd., Measuring Apparatus Section. London, W.C.2.

[It should perhaps have been emphasised that the use of a magic eye for frequency comparison is in itself not novel. Implied claims for the novelty of the method described by our contributor rest on the inclusion of means for obtaining reliable indications up to the 12th harmonic. —ED.]

"Static Charges on Records"

MY note on this subject (p. 165, June *Wireless World*) has provoked a number of enquiries regarding the best method of overcoming the difficulty of the removed coating thread tending to fly up against the cutting-head, causing tangling with the stylus, etc. The recognised means of thread control are, of course (a) hand-brush, (b) automatic brush or chip-chaser, (c) suction device (see p. 137, May, 1941, *Wireless World*), and a method, used in some professional studios, of covering the blank about five minutes before being cut, with a solution consisting chiefly of distilled water, and leaving to dry. To facilitate coating the blank evenly, it is necessary to reduce the surface tension of the water, and to give it conducting properties, other ingredients have to

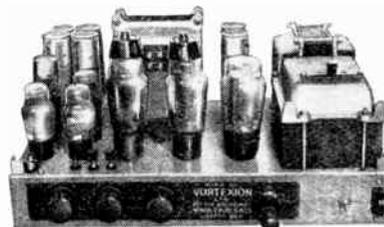The Improved VORTEXION 50 WATT AMPLIFIER CHASSIS



The new Vortexion 50 watt amplifier is the result of over seven years' development with valves of the 6L6 type. Every part of the circuit has been carefully developed, with the result that 50 watts is obtained after the output transformer at approximately 4% total distortion. Some idea of the efficiency of the output valves can be obtained from the fact that they draw only 60 ma. per pair no load, and 160 ma. full load anode current. Separate rectifiers are employed for anode and screen and a Westinghouse for bias.

The response curve is straight from 200 to 15,000 cycles. In the standard model the low frequency response has been purposely reduced to save damage to the speakers with which it may be used, due to excessive movement of the speech coil. Non-standard models should not be obtained unless used with special speakers loaded to three or four watts each.

A tone control is fitted, and the large eight-section output transformer is available in three types: 2-8-15-30 ohms; 4-15-30-60 ohms or 15-60-125-250 ohms. These output lines can be matched using all sections of windings and will deliver the full response to the loud speakers with extremely low overall harmonic distortion.

PRICE (with 807 etc. type valves) £18.10.0
Plus 25% War Increase

MANY HUNDREDS ALREADY IN USE
Supplied only against Government Contracts

VORTEXION LTD.

257, The Broadway, Wimbledon, S.W.19

Phone: LIBerty 2814

Letters to the Editor—


be added. These can be a proprietary detergent, e.g., "Aqua-sol" (1 drop in 0.25 pint), or a minute quantity of high-grade soap (the residual saponified oil that will appear on the record surface, although not improving its appearance, may actually prove useful as a slight lubricant); plus a trace of colloidal graphite. Exact formulæ have not been published, but experiments on the lines indicated (I acknowledge gratefully Dr. C. G. Lemon's advice in this connection) will prove well worth while. This treatment must be applied only to lacquer-coated blanks, never gelatinous coatings. Incidentally, some recordists use a hard stream of cold water for removing dust or foreign matter from the blank surface, rather than the usual brush, when the best medium—compressed air—is not available.

Finally, may I suggest that, following on the recent interesting pick-up designs, a fruitful field for experimentation is the design and construction of high-quality electro-magnetic and crystal disc cutting-heads? Details of a really good head design would be greatly appreciated by recordists.
DONALD W. ALDOUS.
Torquay, Devon.

Pick-up Filter Circuits


I WAS very interested by Mr. Brierley's article in your April issue on a filter for use with a high-quality pickup. Such a filter would also be useful in a local-station receiver to remove 9 kc/s heterodyne whistles, especially if the resonant frequency of one shunt arm is made 9 kc/s. However, in its present form it has several disadvantages, particularly its bulk, the compromise between hum and screening, and the difficulty in obtaining the wire at the present time.

By using a low-impedance filter

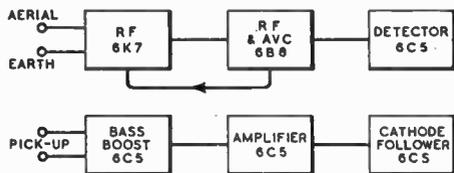

all these disadvantages are overcome. It can then be worked from an "infinite impedance" detector, the output impedance of

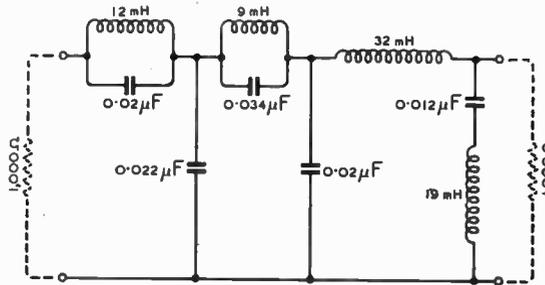which is about 600Ω for an ordinary medium amplification factor triode. The "Gram." side would pass through a bass compensator and an amplifier into a cathode follower and thus to the filter.



Suggested filter for 1,000-ohm load.

This has the additional advantage that the gramophone amplifier can be kept entirely separate from the rest of the circuit if required, the low impedance preventing any pick-up in the long leads.

I have calculated the values for a filter fulfilling these requirements, but unfortunately I cannot at present undertake any practical experiments, and I should be very glad to have any readers' opinions. The suggested circuit is also shown, it being arranged that the filter can be shorted out when on radio, but is permanently in on gramophone. M. E. FELIX.
Cranwell.

Frequency Modulation

THE advocates of the frequency modulation system for normal broadcast reception continually stress its main advantages as being absence from interference noises, and better quality reproduction, and it has been put over on these grounds in America. The writer, who has been interested in obtaining what we used to call "nearly perfect reproduction" for a number of years, would like to suggest that we are still a very long way, at

amplitude modulation system now in use, and that, therefore, this claim for frequency modulation, which is due entirely to the use of short waves which are equally applicable to amplitude modulation, is in the nature of a red herring.

It is to be observed, too, that in this country the writer's experience shows that outside interference with reception is rarely serious except when listening to distant stations, for which purpose, of course, the frequency modulation system is unsuitable.

JOHN BAGGS.
Saddleworth, Yorks.

SERVICE-MEN'S EXAMINATION

Draft Syllabus Issued

AS we first reported some months ago, plans have been made for the conduct of an examination in wireless maintenance and repair. To this end, the Radio Trades Examination Board was formed, with the function of conducting the examinations and awarding Radio Servicing Certificates to successful entrants. The Board comprises three representatives each of the Radio Manufacturers' Association, the Scottish Radio Retailers' Association, the Radio and Television Retailers' Association and the British Institution of Radio Engineers.

A draft syllabus of the proposed examination has now been issued by the Technical Committee of the Board and is printed below.

Part 1.—Fundamental Principles of Radio.—(1) Current/Voltage relationships in AC and DC circuits. (2) Theory of magnetism: magnetic screening. (3) Laws of induction: mutual and self-inductance. (4) Elec-

trostatics: electrostatic screening. (5) Resonance: series and parallel resonant circuits. (6) Modulation, methods of. (7) Thermionic valves. (8) Rectifiers: rectification and detection. (9) Electro-

magnetic waves; simple wave theory. (10) Aerials and transmission lines. (11) Amplifiers and oscillators. (12) Receiver circuit practice. (13) Reproducers and electrical pick-ups.

Part 2.—Practical Applications.—

(1) Principles and use of test meters: resistors; rating and coding. (2) Permanent and electro-magnets, and their uses. (3) Transformers, RF, IF, AF, and mains. (4) Condensers, variable and fixed. (5) Tuned circuits and alignment. (6) Diode, triode, tetrode, pentode and frequency-changing valves: gas-filled types. (7) Copper-oxide and selenium rectifiers: methods of rectification; simple filters; battery-charging plant. (8) Receiver power supplies. (9) Wave propagation: interference and its suppression. (10) Aerial installation and coupling devices. (11) RF, IF, and AF amplifier circuits. Degeneration and regeneration: negative feed-back, oscillators. (12) Public-address and relay practice; methods of mixing; reflex circuits. (13) Receivers: TRF, supersonic heterodyne and super-regenerative. (14) Automatic gain control; tuning indicators; automatic frequency control; automatic tuning devices. (15) Tone control and correction circuits; noise suppression circuits. (16) Loudspeakers, microphones and gramophone pick-ups. Methods of matching.

Part 3.—Practical Examination.—

(1) Soldering technique. (2) Care and maintenance of tools and instruments. (3) Valve testing (HT, LT and GB supplied). (4) Correction of typical receiver faults, which may include realignment. Circuit diagrams, chassis layouts and oscillators supplied. (5) Testing components.

AIR RAID WARNINGS

Valve Equipment for "Imminent Danger" Signals

TO meet the danger from surprise enemy attacks the local authorities at Hove have installed their own system for warning the townspeople. This consists of a valve-generated signal tone which may be distributed from an 800-watt amplifier to loudspeakers in various parts of the town. The valves are kept running continuously and facilities are provided for checking valve efficiency.


The amplifier may be used to reinforce normal Home Office "Alert" and "All Clear" siren tones and also for police announcements, but the Imminent Danger Signal automatically takes priority over any other input.

The equipment was made by the G.E.C. and supplied and installed by Broadcast Amplifiers, Ltd., 17, Preston Road, Brighton.

GOODS FOR EXPORT

The fact that goods made of raw materials in short supply owing to war conditions are advertised in this journal should not be taken as an indication that they are necessarily available for export

COMMUNICATIONS DEPEND...

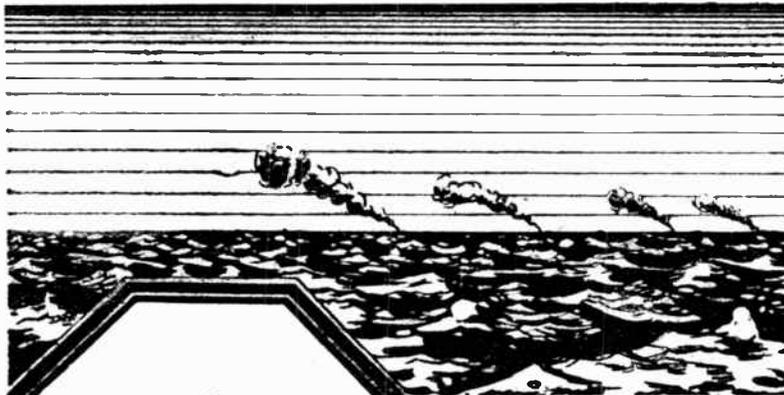

ON SMALL PARTS...

IN countless instances quite intricate pieces of apparatus are wholly dependent on the proved reputation and reliability of their component parts.

All products from the House of Bulgin are pre-eminent for superior design and workmanship and every article bearing our Trade Mark has to pass exacting and exhaustive tests during the course of its production.

We ask the kind indulgence of the Trade on delivery until peaceful conditions return.

The Choice of Critics

BULGIN

FOR

JACKS

A Large and comprehensive range of Jacks, standard to B.S.S. 666, fixing with single $\frac{3}{8}$ " hole to panels 0.036—0.250" thick; single-, double-, and triple-pole, with and without switching. Only $2\frac{1}{2}$ " max. rear depth. Panel-area taken up = $\frac{2}{16}$ " x $\frac{3}{8}$ " average. Best bakelite insulation, nickel-silver leaves, silver switching-contacts.

"The Choice of Critics"

BULGIN

REGISTERED • TRADE • MARK

A. F. BULGIN & CO. LTD., BYE PASS RD., BARKING,

TEL.: RIPPLEWAY 3474 (4 lines).

ESSEX

RECENT INVENTIONS

FRAME AERIALS

THE presence of a mass of powdered iron inside the field of a frame aerial is stated to increase the pick-up and sharpen the directivity of the aerial, provided the spacing of the windings is suitably correlated with the "grain" of the powdered magnetic material.

The magnetic "core" is preferably arranged symmetrically about the axis of rotation of the frame, though some degree of asymmetry may be deliberately introduced in order to correct for the quadrantal or like error due to the presence of a nearby conductor.

In one arrangement the core consists of a hollow cylinder, built up of a number of rings, set close to the frame windings and concentric with the aerial shaft. Alternatively, the core may consist of a hollow sphere of powdered material about which the frame windings are mounted to rotate.

Standard Telephones and Cables, Ltd. (communicated by W. J. Polydoroff). No. 551546. (Addition to 524492.)

FREQUENCY MODULATION

THE repetition frequency of a multivibrator oscillator, comprising a pair of cross-coupled valves, depends upon the time constant or resistance-capacity value of the coupling circuits. Since this includes the anode-cathode resistance of each of the valves, any factor which varies the valve resistance will alter the output frequency of the oscillator as a whole. If then the multivibrator is normally designed to oscillate at a carrier-frequency, the application of a signal voltage to the anode or grid circuit, or to one of the electrodes of each of the valves, will give a frequency-modulated signal.

The signal input may be applied through parallel amplifiers to the anode or grid resistances or directly to the screen grids of each of the valves forming the multivibrator pair. The frequency-modulated output is taken off from a coil which is inserted between the two anode resistances and centred-tapped to the common high-tension supply.

Marconi's Wireless Telegraph Co., Ltd. (Assignees of G. L. Usselman). Convention date (U.S.A.) October 30th, 1940. No. 552039.

TUNING TO FM SIGNALS

A VISUAL tuning indicator is generally required to ensure the accurate adjustment of the circuits when receiving frequency-modulated signals, particularly when these are transmitted on the ultra-short wave-band.

In order to allow of accurate tuning by the ear alone, the set is fitted, according to the invention, with a magnetic relay which automatically keeps the signal channel to the loudspeaker open-circuited until the threshold of accurate resonance has been reached, whereupon the relay is closed to allow the required signals to come through. Incidentally, the

A Selection of the More Interesting Radio Developments


arrangement also serves to cut out undesirable inter-station "noise."

The relay is subjected to the pull of two coils arranged in opposition. One coil is fed with rectified grid current from the limiter valve, and the other coil is energised from the frequency discriminator circuits. As the point of accurate resonance is approached, the current through the second coil falls off, and the pull of the first coil predominates, thereby bringing the loud-speaker into action.

Marconi's Wireless Telegraph Co., Ltd. (Assignees of D. E. Foster). Convention date (U.S.A.) October 25th, 1940. No. 552462.

AUTOMATIC CONTROL

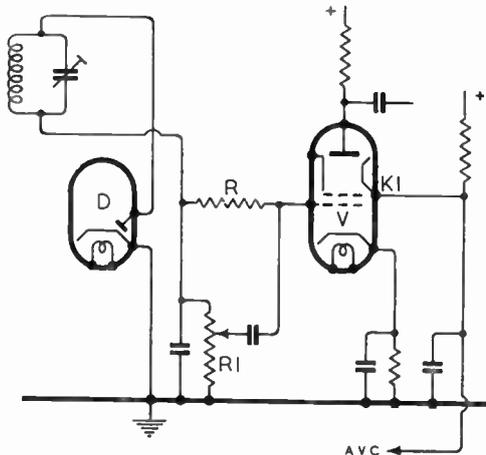PROVISION is commonly made in a wireless receiver to develop a control voltage which can be used either for AVC, or for adapting the



Secondary emission control circuit.

bandwidth of the set to the prevailing interference, or for automatic tuning, or for expanding or compressing the frequencies in the AF stage. The derived voltage is preferably amplified in order to improve the effective control. As it is necessary to maintain correct polarity, this usually involves the addition of at least one phase-reversing valve.

To simplify the phasing problem, use is made of an amplifier comprising a secondary-emission cathode.

As shown in the figure, the valve V contains an electrode K1, the emission from which varies with the intensity of its bombardment by the main discharge through the valve. The control voltage is generated by a diode D, coupled as usual to the IF stage (not shown), and is applied through a re-

sistance R to the control grid, which also receives rectified signal voltages from a tapping on a resistance R1. The potential of K1 varies with the secondary emission from it. This depends upon the electron impact of the main discharge stream, which, in turn, is controlled by the applied grid voltage. The signal output is taken from the anode, and the AVC voltage from the electrode K1.

For "contrast" control, K1 is directly coupled to the screening grid of the last LF amplifier.

Philips Lamps, Ltd. (communicated by N. V. Philips Gloeilampenfabrieken). Application date July 29th, 1941. No. 551981.

SHORT-WAVE SIGNALLING

SHORT-WAVE signals reach their destination by alternative paths which vary in length according to the manner in which the radiated energy is reflected from the ionosphere.


When sending morse signals by the known method of using "spacing" and "marking" pulses which differ slightly in carrier-frequency, the phase-differences mentioned above produce beat-notes at the beginning and end of each significant pulse, which tend to blur the definition of the morse.

To overcome this difficulty a momentary "overswing" above and below the normal frequency is deliberately introduced in transmission, at the beginning and end of each marking and spacing wave respectively and for a period which corresponds approximately to the longest time-delay which is likely to be produced as a result of the multipath propagation of the signals.

This increases the average frequency of the undesired beat-notes during their persistence, and, in the simplest form of the invention, allows them to be more easily filtered out. Alternatively, it permits of a higher keying speed for a given ratio of signal strength to beat interference.

Marconi's Wireless Telegraph Co., Ltd. (Assignees of C. W. Hansell). Convention date (U.S.A.) November 23rd, 1940. No. 552068.

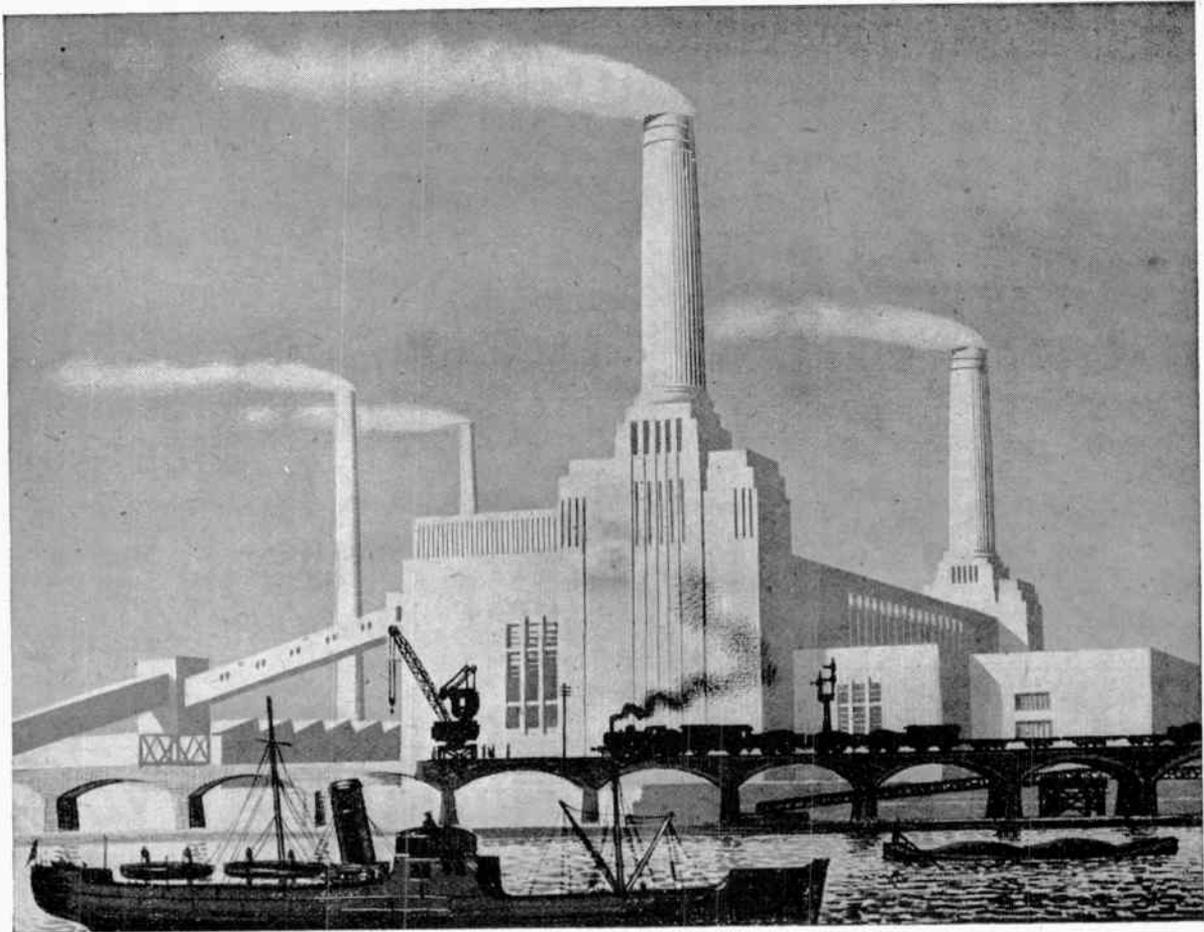The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.



Valves and Chimneys

White vapour issuing from industrial chimney-stacks is a sign of an efficient combustion system; black smoke indicates incomplete combustion, and shows that fuel is going to waste.

Many industrial concerns now make use of an electronic device consisting of an arrangement of valves and a light sensitive cell, which is capable

of giving a record of smoke density, or of regulating the combustion process to ensure maximum efficiency.

This is another example of the ever-increasing usefulness of the thermionic valve—not only contributing to greater industrial efficiency, but also foreshadowing far-reaching benefits to the community.

MULLARD

THE MASTER VALVE

A Valve for Every Purpose

DOMESTIC · COMMERCIAL · INDUSTRIAL · SCIENTIFIC · MEDICAL · EXPERIMENTAL
 THE MULLARD WIRELESS SERVICE CO. LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2. (58)



TYPE: V.S.3
VOLTS: 230 A.C.
OUTPUT: 1.25 K.V.A.

The "Brimain" Power Unit is a robust and sturdy Petrol Electric Generator designed specially for the provision of power and light for the operation of 16 mm. Projectors—Sound or Silent—where light load surge and instability are liable to damage valuable equipment. The output is ample for all standard projectors. Full details gladly sent on request.

BRIMAIN Power Units

BRITISH FILMS LTD., 199, PICCADILLY, LONDON, W.1.
Tel.: Regent 2828. Works: 260, High Road, Balham, London, S.W.
Tel.: Battersea 8506.

IF ITS TRANSFORMERS OR CHOKES

Let the manufacturers of VARLEY products assist you.

SEND US YOUR ENQUIRIES.

Standard units available up to $\frac{1}{2}$ K.W.
or to your specification.

OLIVER PELL CONTROL LTD
CAMBRIDGE ROW, BURRAGE ROAD, WOOLWICH, LONDON SE



**SCIENCE IS BEHIND
THIS HIGH SPEED SOLDER**

Approved by the Ministry of Aircraft
Production and used in countless factories.

Superspeed
CORED SOLDER

H. J. ENTHOVEN & SONS LTD.
230 THORNTON ROAD, WEST CROYDON, SURREY
THORNTON Heath 2462



**It's
happening
in
Radio,
too!**

Between Verdun and Tunisia is a great advance in weapons and technique. But while paratroopers fight in the public eye, the radio war goes on "behind the scenes." The benefits of modern development will not be seen until domestic radio sets are built again. Masteradio are looking ahead to that happy time and invite you to register NOW without obligation for post-war priority, stating home or car radio interest. Write: Masteradio, Ltd., Watford, Herts.

Masteradio
IS LOOKING AHEAD

★ One of a Series of Advertisements
appearing in the National Press

MASTERADIO LIMITED • WATFORD • HERTS


MUSIC WHILE YOU WORK

**FOR BUILDINGS UP TO
5,000 SQ. FT.**

EARLY DELIVERY

R. M. ELECTRIC LTD.

TEAM VALLEY
GATESHEAD, II

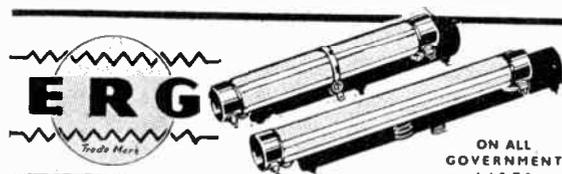

ON ALL
GOVERNMENT
LISTS

Resistors

MANUFACTURED BY

ERG RESISTORS LIMITED
1021a, FINCHLEY ROAD, LONDON, N.W.11

CLASSIFIED ADVERTISEMENTS. Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 5-6 words. Each paragraph charged separately. Press Day: October issue, first post Monday, September 13th, one day earlier at branch offices. Box Numbers 5 words, plus 1/- Deposit System: particulars on request. No responsibility accepted for errors.

MORE & BETTER TRANSFORMERS

Modern transformer technique is essentially the province of a specialist. Nothing can replace intimate practical experience supplemented by scientific study and positive research.

The solution of individual problems has for many years formed a part of our normal day's work. The production in quantity of PARTRIDGE TRANSFORMERS has been built upon the unique knowledge thus accumulated.

If transformers are employed in the equipment you manufacture, we shall be glad to give you the advantage of our experience and to offer the same efficient service that has won the confidence of the Government Experimental Establishments and of the Leading Industrial Organisations.

N. Partridge

Transformer Manufacturer,
76-78, PETTY FRANCE, LONDON,
S.W.1. Telephone: ABBey 2244.

ARMSTRONG SERVICE

OUR Service Department is still at your service.

Despite the many changes caused by over three years of war, and the difficulties in material and valve supplies, we have managed to maintain a very large proportion of Armstrong Chassis in good working order.

IN ADDITION to practically all Armstrong Chassis, including very old models, we can now undertake the repair and overhaul of many other makes of receivers, including American types.

ARMSTRONG MANUFACTURING CO.
WALTERS ROAD, HOLLOWAY, LONDON, N.7
Phone: NORth 3213

NEW RECEIVERS AND AMPLIFIERS

DEGALLIER'S, Ltd.—See advert. under "Repairs and Service." Sorry no sales. [1938]

HIGH fidelity ac/dc amplifiers, 18 watts, U.D.O. mixing input channels, bass and treble controls, input and output transformers, octal base valves, complete chassis; 18gns.—Below.

30-WATT ac amplifiers, complete in chassis form or multiple rack assemblies to 150 watts, for P.A. and industrial installations; early deliveries.—Below.

DANCE and stage transportable amplifying equipment, comprising amplifier as above, m/c microphone, adj. stand, 2 auditorium speakers, cables; 36gns.—Broadcast and Acoustic Equipment Co., Ltd., Broadcast House, Tombland, Norwich. [1980]

V.I.F. superhet receivers. Advance details: DRX 14A. 20-120mc., DRX14 B. 50-200 mc., employing a new variable inductance tuning system, very robust construction; sensitivity better than 5 microvolts; 7 valves, excluding rect.; a.c. mains or batt. operation; meter on panel checks stages during operation, and gives signal strength indication; designed to minimise service troubles; avail. only for priority orders; full details.—Denco, Old Rd., Clacton-on-Sea. Tel. 151. [1950]

£24 only, new 7-valve "Wireless World" Quality amplifier with tone control stage, 2 watt push-pull triode output, price includes Super Quality 12in permanent magnet speaker with large matched output transformer and all valves; as above, but with 15 watt tetrode output and super power cinema speaker with 18in cone, £29; ideal for quality reproduction; limited number available.—Bakers Selhurst Radio, 75, Sussex Rd., South Croydon. [1955]

RECEIVERS, AMPLIFIERS—SECOND-HAND SKY Champion, splendid condition, first owner; offers.—F. L. Nunn, 8, Blinco Grove, Cambridge. [1975]

HALLICRAFTER'S Skyriver Marine Model S22, superheterodyne ac/dc 8-valve receiver, cost £50 (receipt shown), almost unused; offers wanted; South Scotland; buyer collects.—Box 2922, c/o *Wireless World*. [1942]

HALLICRAFTER Super Skyriver, 5x23, with matched speaker, new 1940 and unused since March, 1941, owner on service overseas, perfect condition; what offers? Glasgow district.—Box 2930, c/o *Wireless World*. [1981]

BAKER'S W.W. 7-valve quality amplifier, tone control stage, 8 watts push-pull output, transformer, large energised speaker, all valves, as brand new, solidly built box baffle included, carriage paid passenger; £20, no offers.—Commander Morton, Naval Centre, Cambridge. [1945]

Wanted

HALLICRAFTER or similar receiver, also Avometer for cash.—Blake, 47, Essex Park, Finchley, N.3. [1954]

WE Offer Cash for Good Modern Communication and All-Wave Receivers.—A.C.S. Radio, 44, Widmore Rd., Bromley. [1541]

LATEST Model G.E.C. No. 4018 radio-gramophone for use on 230 volt a.c., also hypersensitive H.M.V. or Marconi pick-up and arm; scratch filters; state model, price, age, etc.—Box 2916, *Wireless World*. [1931]

WANTED, large model American communications receiver such as Hallicrafters, National Hammerlund, R. M. F. Howard, R.C.A., etc., etc., for work of immediate importance; best price paid.—Reply 26, The Granpiana, Western Gate, London, W.6. [1926]

LONDON CENTRAL RADIO STORES will pay good prices for receivers, radio-grams, amplifiers, dynamos, converters, test equipment, electric gramophone motors, and all radio and electrical accessories.—London Central Radio Stores, 23, Lisle St., London, W.C.2. Gerrard 2969. [9836]

HALLICRAFTER'S communication receivers SX-17, SX-24, SX-25, SX-28 or Model DD-1, each with matched speaker for operation on 230 volts a.c.; also R.M.E. 70 receiver with matched speaker for use on 230v a.c. and R.M.E. DM-36 band expander; state age, conditions and price to Box 2919, *Wireless World*. [1934]

MORSE EQUIPMENT

FULL range of transmitting keys, practice sets and equipment for Morse training.—Webb's Radio, 14, Soho St., London, W.1. Tel. Gerrard 2089. [9553]

TEST EQUIPMENT

CAMBRIDGE Unipivot patt. L. 220 ma.f.s.d., 500 meg. res., hand calib.; offers.—Box 2925, c/o *Wireless World*. [1962]

AVO valve tester, as new, can be seen by appointment; what offers?—Apply F. C. Davies, 75, Helix Rd., Brixton, S.W.2. [1943]

Advertisers and buyers are reminded that under Defence Regulations 1939, Statutory Rules and Orders 1940, Number 1689, a permit (T 99 G) must be obtained before sale or purchase of certain electrical and wireless apparatus, particularly such valves and apparatus as are applicable to wireless transmission.

THE RADIO INSTRUMENT CO.

Manufacturers and Distributors of Radio Components. MAINS TRANSFORMERS. Primary, 0.210/230/250 v. Secondaries 350-0-350v. (except Z types).

Type
A 80ma. 4v. 2a. and 4v. 4a. CT. 25/-
B 80 ma. 5v. 2a. and 6.3v. 4a. CT. 25/-
S 80ma. 4v. 2a. and 4v. 2a. and 4v. 4a. CT. 28/-
T 100ma. 4v. 2a. and 4v. 2a. and 4v. 2a. and 4v. 4a. CT. 32/6.

X 120ma. 4v. 3a. and 4v. 6a. CT. 35/-
Y 120ma. 5v. 3a. and 6.3v. 6a. CT. 35/-
Z 120ma. 500/0/500 4v. 3a. and 4v. 6 amp. 39/6.
ZA 120ma. 500/0/500 5v. 3a. and 6.3v. 6 amp. 39/6.

OUTPUT TRANSFORMER. Primary 120ma., 12 ratio. Four secondary windings. Suit single or push pull connection, triodes or pentodes. Outputs in excess of 50 watts can be obtained, low percentage of distortion due to high primary inductance. Exceptional "top" without harmonics. For multiple speakers and huge output. Full data chart on request. 39/6.

DELIVERY of all transformers is regulated by the Essential Works Contracts. Quote priority numbers when available.

CHOKES. Smoothing, C11 80ma., 5/6. CH2 100ma., 17/6. CH3 200ma., 22/6. DC Resistance of all above types 500 ohms. FR2 type field replacement choke 2,000 ohms, 17/6.

MAINS CHOSES for insertion of mains leads, 2 amp. capacity, 2/9. (Condensers for above, 1 mfd. 2.250v. test, 1/9.)

AUTO TRANSFORMERS. 60 watt types, 22/6.

SPEAKER REPLACEMENT BOBBINS. Centre tapped Power/Pentode. Standard Rola and Celestion, Goodmans stock. 2/9 each. 30/- doz.

VOLUME CONTROLS. All values, long shafts, less sw. 4/-, with sw. 5/6.

SWITCHES. Toggle, SP2/11 DPDT, 3/6. Wave change 6-bank 4-wave, 8/6.

ROTHEMEL SENIOR PICK-UPS. Ebony bakelite, 23/18/9 incl. tax.

SPEAKERS. A limited number. EIGHT-INCH PM. Units by famous maker. Large, powerful magnet with special high flux. Fitted with Pentode Matching trans., 29/6.

VALVES. Large stock of pre-war types. Write for lists.

MAIL ORDERS. Please include postage. C.O.D. available.

All enquiries for new lists must be accompanied by 2jd. stamp.

For full details of our products, write:—

THE RADIO INSTRUMENT CO.

294, THE BROADWAY, BEXLEYHEATH, KENT

L.R.S. STUART PUMPS

As supplied to Govt. Dept. & County Councils



These Centrifugal Pumps are ideal for Machine Tool Cooling and all pumping purposes—hot or cold water. Supplied complete with foot-valve, strainer and hose union. Suitable rubber hose available from stock.

No. 10. 100 gals. per hour. Carr. 2/- extra. 25 2 6

No. 11. 280 gals. per hour. Carr. 2/- extra. 26 6 0

No. 12. 560 gals. per hour. Carr. 3/- extra. 27 12 0

Please send 2jd. stamp for specification.

The **STUART AUTOMATIC FLOAT SWITCH** is the best method of controlling water—Post Paid level. Price complete with all fittings ... 26 6 0

LONDON RADIO SUPPLY CO.

Est. 1925
Ardingly Road, Balcombe, Sussex



FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I. C. S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 38, International Buildings, Kingsway, London, W.C.2
Please explain fully about your instruction in the subject marked X.

Complete Radio Engineering
Radio Service Engineers
Elementary Radio Television
And the following Radio examinations:
British Institution of Radio Engineers
P.M.G. Certificate for Wireless Operators
Provisional Certificate in Radio Telephony and Telegraphy for Aircraft
City and Guilds Telecommunications
Wireless Operator & Wireless Mechanic, R.A.F.

Name..... Age.....
Address.....

Trained men get GOOD JOBS

Now is the time to prepare yourself for the future. There will be splendid opportunities for technically trained men to secure well-paid employment, or start radio businesses of their own.

Even if you know nothing about radio, we can train you. Our specialised method of Home-Study Tuition is a proved success. Hundreds of our students now doing important work owe their progress solely to our training.

Post coupon now for free details of our Home-Study Courses in:

- Radio Reception, Transmission, Servicing, Television, Radio Calculations, Mathematics.

T. & C. RADIO COLLEGE, 2, THE MALL, EALING, W.5

(Post in unsealed envelope, 1d. stamp.)

Please send me free details of your Home-Study Mathematics and Radio Courses.

NAME.....
ADDRESS.....
W.W.21

TEST equipment kits; limited stocks still available; please state requirements, enclosing a.s.c.—MacLachlan & Co., Strathyre, 1961

TESTSCOPE, used everywhere by radio service engineers, makes 20 important tests; send for interesting leaflet "R.I."—Hunbaken, Manchester, 1. [1074]

FERRANTI electrostatic, 0-150v, with special metal case, £5/10; Mazda T11, 30/-; h.f. vacuum tester, 40/-; wanted F.M. oscillator (H-h.f.)—Box 2928, c/o *Wireless World*. [1972]

OSCILLOSCOPE, Mullard, wide band horiz. and vert. amplifiers, sweep frequency 25-25kc, usual controls, has had only very occasional use in private laboratory, perfect order, £30; television tube, 12in, Mullard, brand new, complete with e.h.t. trans., rectifier, h.t. supply and rectifier T/B valves, focusing and deflection coils, £20.—234, Green End Rd., Cambridge. [1974]

SECONDARY frequency standard d.f.s., 1a, an inexpensive, compact and useful piece of equipment for every radio laboratory or test bench; provides spot frequencies every 100kc and 100kc from 100kc to 50mc; quartz crystal frequency stabilisation, a.c. mains operated; uses include receiver calibration, frequency measurement, signal generation, etc.; priority only. Denco, Old Rd., Clacton-on-Sea. [1952]

Wanted
AVOMETER, any cond., would buy or repair for owner.—Box 2921, c/o *Wireless World*.

NEW MAINS EQUIPMENT
VORTEXION mains transformers, chokes, etc., are supplied to G.P.O., B.B.C., L.P.T.B.; why not you? Imitated but unequalled; orders only be accepted against Government contracts.
VORTEXION, Ltd., 257, The Broadway, Wimbledon, London, S.W.19. Lib. 2814.

GRAMOPHONE EQUIPMENT
COILS for filters, tone controls, etc., all types transformers for "W.W." circuits accurately wound.—R. Clark, 69, Longley Ave., Alperton, Middx. [1953]

Wanted
WANTED, Quality 12in. P.M. speaker, a.c. turntable, swing records.—Fiddian, A.M.E.S., Salcombe Rd., West Alvington, Nr. Kingsbridge, S. Devon. [1978]

A.C. or a.c.-d.c. electric gramophone record player for operation on 230v supplies, 12in turntables, supersensitive pick-ups, scratch filters, single or dual instruments with fade-out controls if two turntables, etc.; stato model, age, condition, price.—Box 2918, *Wireless World*. [1933]

WANTED, record player (230 ac or ac/dc), preferably with automatic changer, hypersensitive pick-up essential; also modern dual-turntable playing desk with fade-outs, etc., and matched hypersensitive pick-ups; super-quality amplifier and matched speakers also considered.—Box 2931, *Wireless World*. [1982]

NEW LOUSPEAKERS
£3/15 only. Brand new Super Quality triple cone permanent magnet speaker, made by Bakers Selhurst Radio, the pioneer manufacturers of moving-coil speakers since 1925; wide frequency range, even response, ideal for quality reproduction; limited number available under list price; send 2/6 stamp for leaflet describing above and giving constructional details of infinite baffle cabinet; every music lover interested in realistic reproduction should write for leaflet now, £8/15 only, brand new super power cinema p.m. speaker with 18in cone, will handle 20 watts C.D.O., ideal for quality p.a. equipment.—Bakers Selhurst Radio, 75, Sussex Rd., South Croydon. [1956]

SECONDHAND LOUSPEAKERS
GOODMAN Infinite Baffle speaker; £12.—Box 2927, c/o *Wireless World*. [1965]

Wanted
GOODMANS 12in p.m. speaker; 50% above list.—Hett, 59, Lindum Rd., Cleethorpes. [1970]

ROLA G.12, Magnavox 66, or 12in Goodman speaker, P.M., 15ohms; price, cond.—Rees, The Sands, Fairlie, Ayrshire. [1935]

NEW COMPONENTS
DENCO, low loss components, using Polystyrene insulation, include variable condensers, midget variable condensers, air-spaced trimmers, compression type trimmers, coils and coil formers, I.F. transformers, r.f. chokes, small stand-off insulators and special components and equipment to Government specification; for priority requirements only; details on request.—Denco, Old Rd., Clacton-on-Sea. [1951]

"UNIVERSAL CIRCUITS"

by R. S. Roberts, M.Brit.I.R.E., A.M.I.R.E.

Three folders and a thirty-six page booklet, presenting the main principles of radio circuit operation in a concise and convenient form for the pocket.

- I. The Transmitter
- II. The T.R.F. Receiver
- III. The Superheterodyne Receiver

By means of hinged flaps, the charts give a large number of recognised alternatives for each stage. To assist the student in memorising and understanding these, a logical five-colour scheme has been adopted throughout.

"Grid Leak" says: "The Charts and Notes are really intended for students and teachers of radio, but are extremely useful to every radio engineer."

Price complete 6/3 post free, from
The Bookstall
NORTHERN POLYTECHNIC
HOLLOWAY, LONDON, N.7

COVENTRY RADIO

MAINS TRANSFORMERS. 350-0-350v, 120ma, 4v.5a.; 4v.3a.; or 6.3v.4a.; 5v.3a. Half shrouded or open, 262 type 25/6
I.F. TRANSFORMERS. 465 k.c., screened 7/6
COILS. Aerial, H.F. or Osc., short, med. or long wave. P. type Each 2/6
P.M. SPEAKERS. Rola or Celestion.
COMPONENTS. Large assorted stock. Condensers, Resistors, Switches, Transformers, Valve Holders, Wire, Sleeving, Flex, etc.
5,000 B.V.A. VALVES in Stock.

Quotations, stamped envelope please.
COVENTRY CO. EST. 1925
191, DUNSTABLE ROAD, LUTON.
'Phone: LUTon 2677.



For high quality loud speakers when the good times come again.

The Courts, Silverdale, London, S.E.28. 'Phone: SYD 6666.
VOIGT PATENTS LTD.

GECALLOY RADIO CORES

MAIN ADVANTAGES

- Greater magnification.
- Higher selectivity.
- Small size.
- Reduced costs.
- Robust construction.
- Simple adjustment.
- Non-rusting.

Salford Electrical Instruments Ltd.
PEEL WORKS, SILK STREET, SALFORD, 3
Telephone: BLAckfrans 6688 (6 lines)
Proprietors: The General Electric Co. Ltd., of England



CONSTRUCTORS' KITS

See July issue for illustration and details of Constructors' A.C. and Battery 3-v. Kits. Delivery approximately one month.

COILS. Aerial and osc. iron core. Superhet coil unit, 6 push buttons, adjustable permeability tuning, complete with button. New. Colour coded circuits supplied, **£11/0/-**.

Midget Aerial and Osc. Superhet. 465-k/cs. three wave-band coils, mounted on panel, new, **12/6** each. Also Short-Wave Coils on Paxolin Formers 10-50 metres approx., **1/6** each. Midget Medium Wave only, **1/6** each. Aerial and HF Transformer, with reaction, colour coded connections, **6/6** per pair.

IF TRANSFORMERS. 450/470 k/cs iron core permeability tuned, centre tapped, first-class component, new, **12/6** per pair.

MAINS VOLT DROPPING RESISTORS. 2 amp. 1,000 ohms, 2 variable sliders, **4/6**; 3 amp. 750 ohms, 1 variable slider, **6/-**.

10-WATT WIRE-WOUND RESISTORS, 2,000, 500 and 150 ohm, 2/6 each.

PADDERS. Twin ceramic .0003 mfd. (max.) and .0006 mfd. (max.), **1/6** each.

CHASSIS. Undrilled steel, painted, new, **10 1/2 x 8 x 2 1/2 in.**, **7/6**; **8 x 6 x 2 1/2 in.**, **4/6** each. Drilled for 3-v. **8 x 6 x 2 1/2 in.**, **5/6**.

WESTECTORS. Type W6, **5/-** each.

SWITCHES. New, Yaxley type midget, single bank, single pole, 4-way, **2/9** each. Single bank, 3-pole, 3-way, **3/6** each; 3-bank, 2-pole, 4-way screened, **7/6** each; 4-pole, 3-way, midget, **4/6** each.

PARALLEL FEED TRANSFORMERS. Midget. Colour coded circuit, **6/-**. H.F. Choke Amplion, **2/8** each. Short-wave double wire wound Filament Choke for electronic reaction coupling, **2/-** each.

VALVE HOLDERS, 4-, 5-, 6-, 7-pin Paxolin, 6d. International Octal, moulded bakelite, **9d.** each. Short-wave Ceramic 5- and 7-pin, **1/8** each.

CONDENSERS. Tubular, .0005 mfd. to .005, **6d.** each; .02 to .1, **9d.** each. Mica, .01, .001 mfd., 2,200 volt test, **1/8**. Silver mica, .00015, .0002, .0005 mfd., .00005 mfd., **9d.** each.

VOLUME CONTROLS. 1/2 and 1/4 meg., with switch, **6/6** each. 50,000 ohms less switch, **4/-** each.

VARIABLE CONDENSERS. Single .0005 mfd., 2-speed drive with pointer, knob and dial, no escutcheon required. Single hole fitting for portables, crystal sets, etc., **6/-**. .0003 mfd. reaction condensers, **2/8** each. Short-wave Tuning Condensers, 30 mfd., **2/6**.

SPEAKER OUTPUT TRANSFORMER. Heavy duty Pentode, **10/-** each.

PAXOLIN. Polished, flat, strong, **18 x 2 1/2 x 3/32nds** approx., **1/6** each. Soldering Tags, **3d.** dozen. Terminal Strips, from **3d.** to **9d.** Eyelets, **1/2** to **1/6** gross. Resistors, 1/2-watt, **6d.**; 1-watt, **1/-** each, most values available. Spiro Clips, 2 a 1d. Flexible Coupling Joints, large, **1/-**. Dial Lamp Holders, **6d.** each. A, A1, E Panels, **6d.** Systoflex, coloured, **4d.** per yd. length.

A good selection of shop-soiled and odd components available to callers only. Cheap.

Licence to export to Northern Ireland and Irish Free State. Please add postage for enquiries and mail orders. C.O.D. orders accepted.

51-52 CHANCERY LANE.
LONDON, W.C.2. Telephone **HOLBORN 4531.**

COMPONENTS—SECOND-HAND, SURPLUS
LONDON CENTRAL RADIO STORES offer the finest radio and electrical bargains.
ELECTRIC soldering irons, 200-250v, 75 watts; **12/6**; post **8d.**
PUSH-BUTTON mechanism only unit, complete with buttons; **4/6**; post **9d.**
T.C.C. condensers, 0.1mfd 5,000v, dc wkg.; **9/6** each; post **8d.**
SCREENED cable, fine quality, heavy duty, 15 strands, 30 gauge, 5mm rubber covering, with two layers of Empire tape, **1/9** yd.
RUBBER covd. flex, wire, tinned copper, approx. 17 strands, 9ft. lengths; **3d.** yd.
PHILCO bleeder resistances, in metal cans, 100, 150, 250ohms; all **10w**; **2/6**; post **3d.**
TUBULAR condensers, 0.5mfd, 500v working; **2/6**; post, etc., **4d.**
MULLARD EASO diodes, 60mm x 12mm overall, 6.3v heater at 15a; **10/6**; post **3d.**
POTENTIOMETERS, carbon: 700,000ohms, less switch, **3/6**; 100,000ohms, with 2-pole m and b switch, **4/6**; post **8d.**
LONDON CENTRAL RADIO STORES, 23, Lisle St., London, W.C.2. Gerrard 2969. [1977]

QUANTITY useful components, Browns' phones, Avionior, etc.; details on request.—Box 2924, c/o *Wireless World*. [1959]
COIL formers, ceramic ribbed, 2 1/2 x 1 1/2 in., with 5-hole bases, without fitting; 5/- per doz., post free.—A.C.S. Radio, 44, Widmore Rd., Bromley, Kent. [1949]

FERRANTI A.F.5c; A.F.5; Browns' "A" type headphones; set 4-gang Nicore tuning coils; offers; other components, Eddystone coils, etc.; stamp for list.—Brownson, 144, Makepeace Ave., Highbury, N.6. [1967]

LASKY'S RADIO, 370, Harrow Rd., Paddington, W.9, offer for sale the following condensers: 0.15mfd 2,000v at **1/6** each, 0.02mfd 2,000v at **1/-** each, 0.23mfd 2,000v at **1/6** each, 0.05mfd 2,000v at **1/-** each, 0.002mfd 2,000v at **1/-** each, 2mfd cond., 700v, at **2/6** each; 50mfd 12v tubular, 16/- doz, 25mfd 25v tubular, 18/- doz; 0.1mfd 350v tubular, 6/- doz; 10mfd 25v tubular, **1/6** each; speakers, speaker output transformers from **6/-**; 6 1/2 in. Rola speakers, less transformers, at **17/6**, plus postage; 8in Rola speakers, less transformers, at **21/-**, plus postage; 5in Rola speakers, less transformer, **17/6**, plus postage; 8in Rola speakers, with transformers, **27/6**; 10in Rola speaker, less trans., **31/6**, plus postage; terms cash with order or c.o.d. Send us your requirements. [1737]

COULPHONE Radio, New Longton, nr. Preston.—New goods only. Tungram valves, mains transformers, 350v 120mA, 4v 8A, 4v 2 1/2A, 4v 1 1/2A, 33/6; 350v 120mA, 6.3v 3A 5v 3A, 32/6; Celestion, 8in p.m., with trans., 24/6; Rola p.m., less trans., 5in 20/-, 6 1/2 in 22/-, 8in 24/-, 10in 28/6; cored solder, 4/6 lb; tinned copper wire, 2/3 1/2 lb; 2mm Systoflex, 3d. yd; Barrettor resistors, 6/-; line cord replacement resistors, 800 ohm 2 adj. taps, 6/9; Paraflex L.F. trans., 4:1, 4/9; 50 mfd 12v, 1/9; 25 mfd 25v, 1/9; Erie resistors, 1w 9d, 1/2w 6d, 1/4w 4d; Pushback wire, 100ft 6/-; switch cleaner, 2/3 bott.; output trans., 1/6; Bell trans., 6/6; valveholders, 7d per pin; Stanelco cl. soldering irons, 21/-; tubular and mica condensers, V controls, with sw., 5/9, less sw. 4/9; s.a.e. for stock list. [1856]

SOUTHERN RADIO'S wireless bargains: Screws and nuts, assorted gross of ea. (2 gross in all), **10/-**; soldering tags, including spade ends, **6/-**; Philco 3-point car aerials, excellent for short wave and home aerials, **7/6**; limit tone arms, universal fixing for all types of sound boxes and pick-up heads, **10/-**; Ace P.O. microphones, complete with trans., ready for use with any receiver, **7/-**; metal panels, undrilled rigid, 18 1/2 x 8 1/2 in., 2/6; circular magnets, very powerful, 1 1/2 in diameter by 3/8 in thick, **1/6** each, 15/- per dozen; Erie resistances, brand new, wire ends, all low value from 0.8 ohms upwards, a few higher value are included in ea. parcel, 1/4, 1/2, 1 and 2-watt, 100 resist. for 30/-; Multicon Master mica condensers, 28 capacities in one, from 0.0001, etc., etc., 4/- each. Special assorted parcel for Service men: 100 Erie resistances (description above), 24 assorted tubular condensers, 6 reaction condensers, 0.0001, 12 lengths insulated sleeving, 75ft push-back connecting wire, soldering tags, screws, wire, etc., 65/-, all brand new. Crystals (Dr. Cecil), 6d, with cat's whisker, 9d; complete crystal detectors, 2/6; 75ft wire for aerials, etc., 2/6; 25 yds push-back wire, 5/-; Telsen reaction condensers, 0.0001, 1/9 each; Telsen large disc drives, complete with knob, etc. (boxed), type W184, 2/6 ea.; insulated sleeving, assorted, yd lgths, 3/6 dozen; single screened wire, doz. yds, 10/-; speaker units, unshrouded, Midget type, 4/-; metal cased condensers, 0.1+0.1+0.1, 2/6; many bargains for callers—Southern Radio Supply Co., 46, Lisle St., London, W.C.2. Gerrard 6653. [1845]

PREMIER RADIO

METERS

Q-100ma. Moving Iron AC or DC, Bakelite Case, flush mounting, 2 1/2 in. diameter. Price **12/6** each.
Frontier 1-valve de Luxe Battery Model S.W. Receiver, complete with 2-volt valve, 4 coils covering 12-170 metres. Built on steel chassis and panel, **55/-**, including tax.

I.F. TRANSFORMERS, IRON CORED
450-473 kcs., plain and with flying lead, **5/6** each.

NEW PREMIER S.W. COILS

4- and 6-pin types, now have octal pin spacing and will fit International Octal valve holders.

4-PIN TYPE		6-PIN TYPE	
Type	Price	Type	Price
04	9-15 m. 2/6	06	9-15 m. 2/6
04A	12-26 m. 2/6	06A	12-26 m. 2/6
04B	22-47 m. 2/6	06B	22-47 m. 2/6
04C	41-94 m. 2/6	06C	41-94 m. 2/6
04D	76-170 m. 2/6	06D	76-170 m. 2/6
04E	150-350 m. 3/-		
04F	250-550 m. 3/-		
04G	490-1,000 m. 4/-		
04H	1,000-2,000 m. 4/-		

OCTAL HOLDERS
New Premier 3-Band S.W. Coil, 11-25, 26-38 38-86 m., 4/9.
Rotary Wave Change Switch, to suit above, 1/6.
Bakelite Dielectric Reaction Condensers.
0001 mf. 1/3 0005 mf. 2/8 0005 mf. 2/9 each
0003 mf. Differential 2/11 each
2-gang 0005 mf. Condensers, with trimmers 5/6 each

H.F. CHOKES

S.W. H.F. Choke, 10-100 m. 1/3
Standard H.F. Choke 1/6
Binocular H.F. Choke 1/8

SHORT WAVE CONDENSERS

Trolit insulation. Certified superior to ceramic. All-brass construction. Easily ganged.
15 mfd. 2/11 100 mfd. 3/11
25 mfd. 3/3 160 mfd. 4/8
40 mfd. 3/3 260 mfd. 5/8
Brass Shaft Couplers, 1/4 in. bore . . . 7/4 each
Flexible Couplers, 1/4 in. bore . . . 1/2 each
7-pin Chassis Chassis mtg. English fitting Valve Holders, 1/8 each.
Amphenol Octal Chassis mounting Valve Holders. International type, 1/3 each; English type, 1/3 each.

RESISTANCES

Mains Resistances, 660 ohms .3A Tapped, 360 x 180 x 60 x 60 ohms, 5/6 each.
1,000 ohms, 2A Tapped, 900, 800, 700, 600, 500 ohms, 5/8 each.
1 watt all values, 5d. each.
1 watt all values, 7d. each.
4 watt from 60 to 2,500 ohms, 1/- each.
9 watt from 100 to 2,500 ohms, 1/6 each.
15 watt from 100 to 10,000 ohms, 2/- each.
25 watt from 100 to 20,000 ohms, 2/9 each.

SWITCHES

QMB, panel mounting, split knob type, 2 point on/off, 2/- each.
Double pole on/off, 3/6 each.

VOLUME CONTROLS

Carbon type, 20,000, 50,000, 1 meg., 1 meg. and 2 meg., 3/9 each. 5,000, 10,000 and 1 meg., 4/6 each.
Wire Wound Type, 5,000 and 10,000 ohms, 5/6 each.
Valve Screens for International and U.S.A. types, 1/2 each.

Resin-Cored Solder, 7/4d. per coil.
Push-Back Connecting Wire, 2/4d. per yard.
Systoflex Sleeving, 2 mm., 2/6 per doz yards.
Screened Braided Cable, Single, 1/3 per yard

MOVING COIL SPEAKERS

Rola 5 in. P.M. Speaker, 3 ohms voice coil, 21/-
Rola 8 in. P.M. Speaker, 3 ohms voice coil, 25/-
Rola 8 in. P.M. Speaker, 3 ohms voice coil, 25/-
Above Speakers are less output transformer.

Send for details of our Morse Equipment, Valves, and other Accessories available.

ALL ENQUIRIES MUST BE ACCOMPANIED BY A 2/- STAMP.

PREMIER RADIO CO.


ALL POST ORDERS TO:

JUBILEE WORKS, 167, LOWER CLAPTON ROAD, LONDON, E.5. (Amherst 4723.)

CALLERS TO:

JUBILEE WORKS or 169, FLEET STREET, E.C.4. (Central 2833.)

F.W.S.CO.

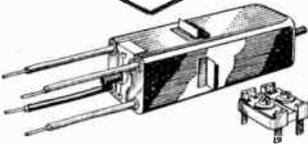

Sickness Midget Transformer and Trimmer.

OUR greatly increased manufacturing facilities in the War effort, coupled with our added production knowledge, will materially benefit you 'when Victory is won.' Quality has always been the dominant consideration in the design—in the choice of materials and in the method of manufacture of our products; and we look forward with confidence to the day when we shall once again continue our relationship with the Radio Industry of Great Britain with greater cordiality than ever before.

**I.F. TRANSFORMERS
AERIAL AND OSCILLATOR COILS
TRIMMER AND PADDER CONDENSERS
'SILVERCAP' CONDENSERS
COIL FORMS, etc.**

Register your name with our Representative for your future benefit.

**The F. W. SICKLES Co.
CHICOPEE, MASS., U.S.A.**

Exclusively Represented by
**Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon**

AFTER THE WAR!

The advance in Radio Technique after the war will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook. Full details are given of A.M.I.E.E., A.M.Brit.I.R.E. City & Guilds Exams., and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc., etc.

We Guarantee "NO PASS—NO FEE"

Prepare for to-morrow's opportunities and post-war competition by sending for your copy of this very informative 112-page guide NOW—FREE.

**BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY (Dept. 388)
17, Stratford Place, London, W.1**



**W. BRYAN SAVAGE
LTD.**

Expert assistance in the solution of problems relating to

● **TRANSFORMERS, CHOKES**

● **AMPLIFIERS
● POWER UNITS**

and Specialised Equipment

embodying

ELECTRONIC CONTROL

**WESTMORELAND RD., N.W.3
COLINDALE 7131**

**G. A. RYALL, 69, Wharfedale Gardens,
Thornton Heath, Surrey.**—Please note new temporary address; mail order only.

ERIE resistances.— $\frac{1}{2}$ W. 680 ohms 3/ doz.; Erie 2W, 150, 3,900, 140,000, 270,000, 3 1/6; Erie 3W, 6,800 ohms, 2 1/6 T.C.C. 0.1 non-inductive tubular condensers, in paxolin tubes, type 330, 350v wks, 6/6 dozen, 75/- gross.

SLOW motion (epicycle) drives, in well-finished brass, ratio 8-1, shaft $\frac{1}{2}$ in long, $\frac{1}{4}$ in dia., drilled to take pointer, 1/3 each. **PAXOLIN** strip, $\frac{1}{2}$ in wide, 12 in lengths, 3 1/6 and 100 25/-; short lengths cut group board size, 6 1/3.

TB wave traps, iron core, suitable medium and long wave, 1/3 each; thimble top caps, 24 1/3; insulating tape, black, 1/3 lb; Wearite switches, ebonite with silver-plated contacts, for 2Hf and band pass with dial lights, 1/6 each.

YAXLEY switch screens, size approx. 4in \times 3 $\frac{1}{2}$ in, drilled with mounting flange, 3 for 1/3. [1957]

SOLDER tags, 2/6 per gross; copper earth rods, 2/3 each; twin leads, suitable for 'phones, 1 yard in length, 6d. each; list 1d.; c.w.o. or c.o.d.—Box 2926, c/o Wireless World. [1964]

7-VALVE m. and l.w. s.h. basic kit, 10in spkr., crystal twtr., mains t., choke, gang condr., dial, 3 coils, 2 i.f.s., valves, sockets, cans, £6 9-valve s.w., s.h., basic kit, mains t., chokes, Trilomat condrs., plug-in coils, 3 i.f.s. valves, ceramic sockets, cans, £6; 1-valve 12-550 metres battery basic kit, £2.—Calver, 109, Collingwood, Dolphin Sq., S.W.1. [1960]

BATTERY charging.—Metal rectifiers, 6v 0.5amp, 6/3; 12v 0.5amp, 11/6, postage 3d.; 12v 3amp, 34/6; special transformer for same, 23/6, postage 10d.; metal rectifier, 6v 2.5amp, 15/6, with special transformer and ballast bulb 42/6, post 10d.; also transformer, rectifier and ballast bulb for 2v, 6v, lamp, 29/6; ditto, 1.5amp, 35/-, postage 10d.; transformer and rectifier for 2v 0.5amp charger, 14/6, post 7d.; ditto 2v 0.3amp, 11/6; instrument type rectifiers for meters, 1ma 18/6, 5ma 15/6, 10ma and 50ma 14/6, new goods, good make, postage 3d.; one milliamp full scale meters, $\frac{3}{4}$ in dia, flush mounting, 65/-; Rothermel bakelite crystal pickups, latest model, 78/6; famous Rothermel Bullet microphones, for stand mounting, new ultra mount, black crackle, finished housing, really good tonal quality, at a modest price, £3, stands in stock; also few only D.104 microphones, £4/15; miniature deaf-aid mikes, crystal, 42/6, post 6d.—Champion, 42, Howitt Rd., London, N.W.3. [1976]

Wanted

WANTED, Partridge transformers, types IV60, IV240, 45W0.—11, Hillbury Rd., London, S.W.17. [1969]

"SKYROD" aerial, complete with accessories as supplied by Messrs. Belling and Lee, Ltd., for chimney stack anchorage; state price and condition.—Box 2917, Wireless World.

DYNAMOS, MOTORS, ETC.

ALL types of rotary converters, electric motors, battery chargers, petrol-electric generator sets, etc., in stock, new and second-hand.

WARD, 37, White Post Lane, Hackney Wick, E.9. Tel. Amherst 1393. [0518]

MOTOR alternator, input 110v dc, output 230v 600 cycles, 1,850 watts, £17/10; Crypto commutating rectifier, input 230v ac, output 15v 5a dc, with switchboard, £15/10.—Below.

ROTARY converters, dynamos, ac and dc motors, lighting sets, all voltages and sizes up to 5kw; hundreds in stock.—Harris, Strouds, Bradfield, Berks. [1958]

FOR sale, E.D.C. rotary converter, 100 volts d.c. to 230v a.c., 50 cycles, 0.391 amps. in perfect order with maker's suppressors and screening box.—Offers to R. Morrison, Har-mullock, Bridge of Weir, Renfrewshire. [1927]

LT. dynamos for charging. Lucas-Rotax, 6-12v 8 amps dc, 3rd brush, weight 11lb, size 8in \times 4 $\frac{1}{2}$ in, unused ex W.D. cost £10, to clear 17/6 each; ht and lt G.E.C. double current 6v and 600v, 17lb, ditto, 27/6; all carr. paid England and Wales.—Electradix, 214, Queenstown Rd., Battersea, S.W.8. [1748]

VALVES

GOOD stocks of valves, retail; state types wanted.—A.C.S. Radio, 44 Widmore Rd., Bromley, Kent. [1948]

IF you cannot obtain that wireless valve, try Dowsett and Co., Ltd., 48, Grove Rd., Eastbourne. Stamp reply. [1929]

OUR adaptors will help in replacing un-obtainable valves; send 7d. for interesting booklet on valve replacements; trade enquiries invited.—V.E.S., Radio House, Ruislip. [1885]

HILL AND CHURCHILL BOOKSELLERS SWANAGE DORSET


ENGLISH & AMERICAN
BOOKS IN STOCK ON
RADIO AND
TELECOMMUNICATION

CATALOGUE ON APPLICATION

LONDEX for RELAYS

for A.C. and D.C.

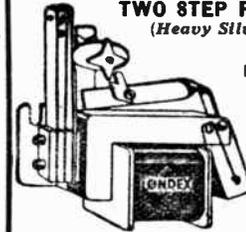**TWO STEP RELAY LF/F8
(Heavy Silver Contacts)**



First Impulse
"ON." Second
Impulse "OFF."

Also Aerial
Change-over
Relays.

Ask for
leaflet 88A/WW

LONDEX LTD
MANUFACTURERS OF RELAYS
MERLEY 207 MERLEY ROAD, LONDON S.E.20 (PHONE: 2731)

R. K. Dundas

LIMITED

Experimental and Aeronautical
Engineers and Scientific Instrument
Makers. Manufacturers of Precision
Mechanical, Electro-Mechanical and
Thermionic Instruments. Electro-
Medical and Industrial Apparatus,
Time Interval Measurement and
Counters, DC Amplifiers and
Recorders. Specialised Design
Enquiries Welcomed

THE AIRPORT, PORTSMOUTH

Telephone: 74874.

SPEAKER REPAIRS by Specialists

Any make, British
or American

Best Service

Moderate Charges

TRADE ONLY

Also Components for Service Men at keenest prices. List 1d.

A. W. F. RADIO PRODUCTS 'Phone: 11632
13, Lilycroft Road, Bradford, Yorks.

Radio Service

REWINDS. Mains 25/-. Output from 6/-.
Field Coils, 9/-. PROMPT DELIVERY.

VALVES (B.V.A.). Send for list—good selec.
PHILIPS D.C. CONVERTERS—Bought
—Sold—and Exchanged.

S.A.S. to:—

A.D.S. Co. ASTON, BIRMINGHAM, 6
261/3/5, Lichfield Road,

LASKY'S RADIO

for
Valves, Speakers, Condensers and ELECTROLYTICS

WE HAVE A LARGE SELECTION OF ENGLISH AND U.S.A. VALVES IN STOCK as per example.

1A5, 5Z3, 5Z4, 6A5, 6P6, 6K6, 6K7, 6E8, 1C6, 6Q7, 12A5, 12Q7, 12R7, 2B16, 25Z6, 6B8, 32L7, 36L6, 36Z4, 32Z6, 50L6, 70L7, 117Z6, 80, 6X6, 12B8, 12F6, 6J7, etc., etc. All at B.O.T. Fixed Retail Prices Plus Tax. English AC, AC/DC & Battery Valves as follows: U50, HL4, HL13, MV8PEN, VP4, SP4, FC4, MU14, X65, MU12, U12, ECH3, DW4/600, EBL1, PC2, U06, X65, KTW61, KT65, WD40, TDD4, etc., etc. Speakers, Speaker Transformers, Volume Controls, with and without switch. Roia F.M. Speakers in stock: 5", 6", 8", 10", with or without Transformer.

The following List of Components and Condensers in Stock.

U.S.A. Octal Base Valve Holders, 8d. each	7/6 doz.
Wander Plugs, assorted, 8d. each	2/6 "
Assorted Volume Controls, less Switch	2/9 each
Iditto, with Switch	4/9 "
2 mfd. 700v. Block Paper Condensers	2/6 "
.15 mfd. 2,000v. Tubular Condensers	1/6 "
.02 mfd. 2,000v. ditto	1/- "
.25 mfd. 2,000v. ditto	1/6 "
.05 mfd. 2,000v. ditto	1/- "
.002 mfd. 2,000v. ditto	1/- "
50 mfd. 12v. ditto	16/- doz.
25 mfd. 25v. ditto	18/- "
.1 mfd. 350v. ditto	6/- "
10 mfd. 25v. ditto	1/6 each
2 mfd. 400v. Can Electrolytics	4/3 "
Toggle Switches	3/8 "
Spade Terminals for Accumulators, 9d. doz.	7/6 gross

Send us your requirements.

LASKY'S RADIO,

370, Harrow Road, Paddington, W.9.

Telephone: Cunningham 1979.

CASH WITH ORDER PREFERRED OR C.O.D.

MORSE CODE TRAINING

If you wish to become a proficient W/T Operator, or, if you are already an Operator and desire to increase your present sending and receiving speeds as well as to improve your technique, then apply for a copy of the Candler "Book of Facts."

Numerous students trained by the Candler system are now W/T Operators in the ARMY, NAVY, AIR FORCE and MERCHANT SERVICE, whilst many others are doing W/T work of national importance. Full details of the following Courses are given in the Candler "Book of Facts."

The JUNIOR Scientific Code Course for beginners teaches all the necessary code fundamentals scientifically.

The ADVANCED and High-Speed Telegraphing Course, for operators who want to increase their w.p.m. speed and improve their technique.

The TELEGRAPH Touch-Typewriting Course.

Fill in the Coupon and learn more about this highly efficient Candler method of Morse Code training in your own home.

Courses on Cash or Monthly Payment terms.

COUPON
Please send me a Free Copy of Candler "Book of Facts."

NAME
ADDRESS

Post Coupon in 1d. unsealed envelope to—
THE CANDLER SYSTEM CO. (Room 55W),
121 Kingsway, London, W.C.2
Candler System Co., Denver, Colorado, U.S.A. (943)

5000 valves, all types, including output, rectifiers, etc., s.a.e.—Davies, 28, Mount Vernon Crescent, Barnsley. [1848

WE have a large stock of new and boxed valves, all guaranteed, at retail prices, plus tax; also U.S.A. lease-lend types for replace., send your requirements.—Lasky's Radio, 370, Harrow Rd., Paddington, W.9.

1000 valves in stock: UU5, UU6, UU7, AC5/Pen, Pen45, Pen45DD, TH4B, AC/TP, TP1340, AC5/PenDD, 5Y3G, 6C6, 6D6, 36, 45, 75, 6Q7G, 12Z3, 12SQ7, 35L6, TH2321, CBL1, 6B7, DC/Pen, 6F6G, 6J8G, PM24A, FC2A, VP4A; send s.a.e. for valve and wireless parts lists, 2d.—Ransom, 9 & 34, Bond St., Brighton. Retailers not supplied. [1878

BRITISH and American valves, many types in stock; Midget coils, aerial and h.f. transformers, fitted trimmers, medium wave only, no reaction, for T.R.F. midgets, 8/6 pair; black instrument pointer knobs, 1/3; mains dropping resistances, speakers, condensers, volume controls, etc.; everything for the serviceman; stamped envelope with all enquiries, please.—O. Greenlick, 34, Bancroft Rd., Cambridge Heath Rd., London, E.1. Stepney Green 1334. [1963

DALE ELECTRIC COMPANY—A selection of some of the valves available: HL2, PM1HL at 5/10; 1115, 6C5, 6F5, 6H6, 6J5, 12F5, 12J5, 12SF5, AC/HL, HL13, MH4, at 9/2; AC/ME, 10/5, 1A5, 1C5, 1N5, 1T5, PM12M, PEN220, VP2, at 11/-; 75, 76, 6Q7, 12Q7, 12SQ7, PK4, at 11/7; ML4, at 12/2; 1A7, 6C6, 6D6, 6F6, 6K7, 6J7, 6U7, 12J7, 12S7, 25A6, 25L6, 35L6, 24, 30, 41, 42, 45, 46, 57, 58, 77, FC2, MK74, KT63, PENA4, VP13B, at 12/10; 2B7, 6A6, 6B5, 6B7, 6G5, 6K8, 12A8, 12SA7, FC4, at 14/-; 6F7, 6J8, 6P8, 12B8, 25A7, 70L7, 117Z6; at 15/3; 6L6, KT66, at 18/3; AC/PA, at 21/4; PX25, at 24/4; rectifiers, 25Z6, 5Z4, 80, U50, U31, IV3, MU14, MU12, at 1/-; U52, 5X4, 18/3; please add 6d. postage to all orders; enquiries s.a.e., please.—The Dale Electric Co., 13, Tretawn Gdns., London, N.W.7. [1968

Wanted

VALVES wanted, any quantity from one upwards; also test equipment, service sheets and spares.—J. Bull, 246, High St., Harlesden, N.W.10. [9732

REPAIRS AND SERVICE

TRANSFORMERS, motor rewinds, repairs of all descriptions to the wireless trade.—Marshall, 137, Windmill Lane, Nottingham.

MIDWEST, etc., the American experts.—Bennett's, 4, Humberstone Drive, Leicester. [1971

METROPOLITAN RADIO SERVICE Co. guarantee repairs to American and British receivers.—1021, Finchley Rd., N.W.11. Spe. 3000. [9641

MAINS transformers service, repairs, rewinds, or construction to specification of any type, competitive prices and prompt service.—Sturdy Electric Co., Ltd., Dipton, Newcastle-upon-Tyne. [9651

ACCURATE radio rewinds, mains transformers, fields o.p. transformers, etc., and all loudspeaker repairs.—Southern Trade Services, 297-299, High St., Croydon. [1715

ALL types of radio receivers serviced. Murphy and Pilot specialist; valves in stock; sound repairs for 13 years.—T. E. Feyrer, F.I.P.R.E., 50, Vine St., Uxbridge.

"SERVICE with a Smile."—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cords.—F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [1575

DEGALLIER'S, Ltd. "Service with a guarantee." If you cannot get your receiver serviced, let American specialists do the job; first-class workmanship only; specialising in Air-King, Belmont, de Wald, Challenger, Delco, Emerson, Ferguson, Garod, Hallcraft, Hammerland, Midwest, Majestic, Pilot, Stromberg, Carlson, Wells Gardner, etc.; also any British set. Remember, for 14 years we have handled American sets; this is self-explanatory; s.a.e. with all enquiries.—Degallier's, Ltd., 9, Westbourne Court, London, W.2. [1939

MISCELLANEOUS

RUBBER stamps up to your special requirements, and design, typical example, stamp showing name, address and profession; 9/6 post free.—V.E.S., Radio House, Ruislip. [1884

ENGINEERING firm requires the following work: process drilling, mechanical and radio assembly, coil winding.—C.B. Engineering Co., X.L. Works, Robin Hood Gate, Kingston Vale, S.W.15. Tel. Kingston 3587. [1930

GALPINS

ELECTRICAL STORES

"FAIRVIEW,"

LONDON ROAD, WROTHAM, KENT.

TERMS: Cash with Order. No C.O.D.

Regret Orders from Eire and Northern Ireland cannot be accepted.

KLAXON MOTORS, approx. 1/2 h.p., laminated fields, ball bearing, perfect mechanical condition, offered for rewinding only, windings not guaranteed. Price 10/- each, carriage paid.

KLAXON MOTORS, as above, with right angle drive, but need slight repair, mostly fields, open circuit, not guaranteed, laminated fields, 20/- each, carriage paid.

D.C. MOTOR, shunt wound, condition as new, high grade, ball bearing, 1/2 h.p., 110 volts. Price 40/-, carriage paid.

AUTO-TRANSFORMER, 2,000 watts, tapped 0-110-200-220-240 volts, as new. Price 29/-, carriage paid.

VOLTMETERS, 2 1/2 in. dia., panel mounting moving coil, modern type, by famous maker range 0-8v., F.S.D. 5 m.a. Price 32/6, post free.

AMP METERS, description as above. Ranges 0-1, 0-1 1/2 and 0-20 amps, F.S.D. 15 m.a. State which reading required. Price 25/- each, post free.

DUBILIER RESISTORS, new lead and wire ends, 2 watt, 30,000 ohm, 1/8 each or 15/- per doz., post free. Ditto, 1 watt, 5,000 ohm., 3/8 per doz., post free.

RESISTANCE MATS, size 8in. by 6in., set of four. 80, 80, 150 and 800 ohms, carry 1/2 to 1/2 amp. Price, set of four, 5/-, post free.

MOVING COIL MOVEMENTS, needing slight repair, modern type, famous makers, deflection 5 to 10 m.a. Price 15/-, post free.

RIGHT ANGLE DRIVE, mounted in gunmetal box, all ball bearing, 1/2 in. dia. shafts, as new. 12/- each, carriage paid.

RECORDING AMPMETER, in ironclad case, meter movement wants repair, no pen, clock perfect, range 0-3 amps. Price 27/-, carr. paid.

MOTOR-DRIVEN PUMP, for oil or water, motor 220v. D.C., 1 amp., 1,250 r.p.m., maker Keith Blackman. Price 28 10s., carr. paid.

200 AMP. KNIFE SWITCHES, S.P., D.T., in first-class condition. 15/- each.

200 AMP. CABLE, V.I.R., as new, rubber cover perfect, size 37/13, lengths 30 to 40 yds. Price in lengths, 5/- per yard, carr. paid.

DYNAMO, maker C.A.V., output 20 volts, 10 amps., speed 1,500 r.p.m., ball bearing. Price 25/-.

ROTARY CONVERTOR, D.C. to D.C., input 11 volts, output 1,100 volts, 80 watts, will operate successfully on 6 volt input. Price 50/-.

MASSIVE GUNMETAL WINCH, complete with long handle, for use with 1/2 in. dia. wire cable weight 50 lbs., condition as new. Price 23/- carriage paid.

ELECTRIC LIGHT CHECK METERS, well-known makers, first-class condition, electrically guaranteed, for A.C. mains, 200/250 volts 50 cy. 1 phase 5 amp. load, 10/- each; 10 amp. load, 12/6, carriage 1/-.

1/2 WATT WIRE END RESISTANCES, new and unused, assorted sizes (our assortment). 6/- per doz., post free.

SOLID BRASS LAMPS (wing type), one hole mounting, fitted double contact, S.B.C. holder, and 12 volt 16 watt bulb. Price 3/6 each, post free, or 30/- per doz., carriage paid.

TUNGSTEN CONTACTS, 1/2 in. dia., a pair mounted on spring blades, also two high quality pure silver contacts, 1/2 in. dia., also on spring blades, fit for heavy duty, new and unused. There is enough base to remove for other work. Price, the set of four contacts, 5/-, post free.

220 VOLT DYNAMO, 9 amp. output, by Lancaster Dynamo Co., shunt wound, speed, 600 R.P.M., condition as new. Price 210, carriage paid.

The Golden Fleece

When Jason set out with his Argosy in search of the Golden Fleece he did so with no greater determination than we at Gardners when we embarked upon the building of a range of quality transformers in our search for perfection. Although every Gardner product bears the stamp of this determination it is prominent indeed in our Small Power Transformers up to 4 kva. When next you need this type of component and a "Golden Fleece" quality is a "must," let your Argosy set sail in our direction.

We regret that at present Small Power Transformers are available for highest priority orders only.



GARDNERS RADIO LIMITED
SOMERFORD, CHRISTCHURCH HANTS G.6.



Designed by engineers for engineers, the Solon Electric Soldering Iron gives neater, cleaner, more efficient work in less time. The heating element is right inside the bit, giving constant heat at the point—where you want it. All internal connections housed at end of handle—away from heat and easy to get at. Complete with 6ft. of Henley 3-core flexible. Made for the following standard voltages:—100/110, 200/220, 230/250. Supplies are, of course, only available for essential war work. Early ordering is advisable as the demand is heavy.

Made in England

Model shown is a standard 125 watt round pencil bit Solon. Other sizes and types available.

SOLON
Electric
SOLDERING IRON FOR INDUSTRIAL USE

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
Engineering Dept., Milton Court, Westcott, Dorking, Surrey

CINE camera, 16mm. professional model, excellent sturdy mechanism, fitted powerful condenser, and arrangements for use as projector also, cost £75; first £25 secure.—234, Green End Rd., Cambridge. [1973]

ADVERTISER wishes to contact a few of the most eminent engineers in the country, or men who have held the highest appointments in prominent engineering concerns, to criticise manuscripts of a practical and technical nature dealing with civil, mechanical, electrical, aeronautical, automobile and radio engineering. Interesting work, non-repetitive, could be carried out leisurely in spare time. A high fee is offered.—Write in strictest confidence, stating position, salary, etc., to Box 2889, c/o *Wireless World*. [1821]

SITUATIONS WANTED

EXPERIENCED electronic physicist offers whole or part time services work of national importance; near London preferred.—Box 2929, c/o *Wireless World*. [1979]

TECHNICAL TRAINING

A.M.I.E.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes; for full details of modern courses in all branches of electrical technology, send for our 112-page handbook, free and post free.—B.I.E.T. (Dept. 388A), 17, Stratford Place, London, W.1. [1941]

GREAT possibilities exist for technically qualified engineers, key men in wartime and afterwards. Through the home-study courses of The T.I.G.B. take a recognised engineering qualification, such as A.M.I.Mech.E., A.M.I.E.E., A.F.R.Ae.S., A.M.I.Chem.E., C. and G., etc., in which examinations the T.I.G.B. students have gained 25 **FIRST PLACES** and hundreds of passes. Write today for "The Engineer's Guide to Success"—free—containing the world's widest choice of engineering courses covering all branches, including aeronautical, mechanical, electrical, wireless, chemical, etc.

THE TECHNOLOGICAL INSTITUTE OF GREAT BRITAIN, 82, Temple Bar House, London, E.C.4. [1403]

TUITION

LEARN Morse code the Candler way. See advertisement on page 29. [1922]

RADIO training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0611]

PERSONAL tuition required, practical and theoretical radio; N.W. district.—Box 2923, c/o *Wireless World*. [1946]

MORSE and wireless, evening tuition; pupils prepared for all Service exams; stamp.—Masters, 15, Wilmington Ave., W.4. [1928]

RADIO Engineering.—Television and Wireless Telegraphy, comprehensive postal courses of instruction. Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9 (Estd. 1906). Also instruction at school in wireless for H.M. Merchant Navy and R.A.F. [9249]

"ENGINEERING Opportunities."—Free 112-page guide to training for A.M.I.Mech.E., A.M.I.E.E., and all branches of engineering and building; full of advice for expert or novice; write for free copy and make your peacetime future secure.—B.I.E.T. (Dept. 387B), 17 Stratford Place, W.1. [1940]

A POSTAL training in electrical engineering—power or radiology; individual correspondence tuition by highly qualified engineers with wide teaching and technical experience. Elementary or advanced courses. Preparation for recognised examinations. Pre-service training specially arranged.—G. B., 18, Springfield Mount, Kingsbury, N.W.9. [1731]

THE Tuitionary Board of the Institute of Practical Radio Engineers have available home study courses covering elementary, theoretical, mathematical, practical, and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E., Service-entry and progressive exams; tuitionary fees—at pre-war rates—are moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, Bush House, Walton Avenue, Henley-on-Thames, Oxon. [1462]

PATENT NOTICES

THE proprietors of British Patent No. 505632, dated November 12, 1937, for Improvements in and relating to cathode-ray tubes, are desirous of entering into arrangements by way of a licence or otherwise on reasonable terms for the purpose of exploiting the above patent and ensuring its practical working in Great Britain.—Enquiries to Singer, Ehlerst, Stern and Carlberg, Chrysler Bldg., New York City, N.Y., U.S.A. [1845]

BOOKS, INSTRUCTIONS, ETC.

WANTED, "W.W." Nov. 9, 1934.—6, Brookbank Ave., London, W.7. [1947]

MARTIN'S HAVE IT

IN STOCK :

Mains Transformers. Well made Standard Replacements, 4-v. and 6.3-v., 87/6 each.
8 M.F.D. Gas Type, Dry, 450 V.W., 10/6 each.
.01 and .03 Tubular Fixed Condensers, 1,500 V.D.O., 8d. each.
.05 Tubular Fixed Condensers, 1,500 V.D.O., 1/8 each.
25 M.F.D. Tubular, 25 V.W., 2/6 each.
25 M.F.D., 12 V.W., 2/3 each.
.0001 Reaction Condensers, 2/- each. Boxed.
Yaxley Type Switches, 5-way, 1-bank, 2-pole, 3/6 each.
Resistors, 1 watt, 100 ohms to 2 meg., mixed, 72/- gross.
Resistors, 1 watt, 100 ohms to 2 meg., mixed, 63/- gross.
Dropper Resistors, wire wound, 1,000 ohms, variable superior type, fitted 2-hole fixing lug, 5/9 each.
10-watt Resistors, 800 ohms, wire wound, 2/6 each.
2-Gang Condensers, .0005, with slow-motion drive. Brand new. Boxed, 9/- each.
3-Gang Condensers, .0005, new, 7/- each.
Volume Controls and Tone Controls, all values, with switch, 6/6 each; without switch, 4/6 each.
Valve Holders, Octal Base, American, 8d. each.
Valve Holders, 7-pin British, 8d. each.
Replacement Valves for American Midsets, and British receivers, nearly all types in stock—all at controlled prices.

MARTIN'S (Edmonton) LTD.

3/4, The Broadway, Edmonton,
London, N.9. TOTtenham 4188.

THE NORTHERN POLYTECHNIC, HOLLOWAY ROAD, N.7.

Department of Radio and Musical
Instrument Technology.

Head of Department :
S. A. Hurren, M.C., F.Brit.I.R.E.

Full-time Day Courses in RADIO TECHNOLOGY

in preparation for all
recognised qualifications in this subject
Practical laboratory and workshop experi-
ence provided.

Prospectus free on application to Secretary
New Term begins September 6th.

WARD ROTARY CONVERTERS

Petrol Electric Generating Plants, H.T.
Generators, D.C. Motors, Frequency
Chargers, etc., up to 25 K.V.A.

CHAS. F. WARD

37, WHITE POST LANE, HACKNEY WICK, E.9.
Phone: Amhurst 1393

TESTOSCOPE

Makes 30 im-
portant tests A.C./D.C.
Used everywhere by
Electricians, Wiremen and
Service Engineers. Interesting
booklet "R14" on testing, free. From
all Wholesalers or direct.


RUNBAKEN -- MANCHESTER -- I

"SYSTEMATIC RADIO SERVICING"

A method for organising the repair-shop, devised and employed by J. Bull. Also a catalogue of many Radio Service Aids including "History of Faults," "Job Cards," which almost repair the sets, "Valve Base Data Cards," and perhaps most important, a Rectifier which will replace any of the popular Universal valves such as 1Z23, 2Z25, 1D5, U30, 40SUA, etc. Price 1/7 p.f.

V.E.S.,

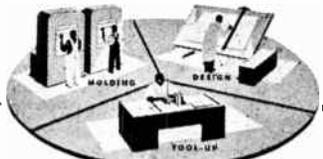(W) Radio House, Weltheone Drive, Ruislip, Mdx.



WHEN you think of plastic mouldings for post-war products we suggest you consult the Kurz-Kasch "Plastic Round Table"—a group of specialists in design, materials, tool-up and moulding. Kurz-Kasch can give you complete service under one roof, one responsibility.

Register your name with our representative now. He will forward you information of our products as soon as they become available.

KURZ-KASCH INC.
Moulders of Plastics,
DAYTON, OHIO
U.S.A.

Exclusively Represented by
Frank Heaver Ltd., Kingsley Road, Bideford, N. Devon

MODERN text books by Cainm, Dowsett, Termann, Sowerby, etc., required by wireless college for students' use.—Particulars and prices to Box 2920, c/o *Wireless World*. [1936

WEBB'S radio map of the world locates any station heard, size 40x30in. 4/6, post 6d., on linen, 10/6, post free.—Webb's Radio, 13, Soho St., London, W.1. Tel. Gerard 2089. [9947

CLASSIFIED ADVERTISEMENTS intended for the OCTOBER issue can be accepted up to First Post Monday, September 13th

RADIO VALVES AND COMPONENTS

AMERICAN TYPE VALVES 706, 6K7G, 12/8; 7A8, 8B9G, 6J8G, 14/-; 1F5G, 15, 11/-; 01A, 35/51, 33; 10/3; 1A4, 1B4, 0/-; 6Y5V, 16/-.

TUNGSRAM, DDT13, DDT13S, 11/3; TH29, 1X21, 13/9; P215, SP220, 6/-; H14, 0/2; DDT4, 11/3.

FERRANTI, SPTA, PTT, 10/6; VPT, 12/6.

BARRETTIERS, British glass type Atlas 150, 4-pin or side-contact equivalent to C1, C1C, C3, BR201, BR201S, 202, etc., 9/-.

FIXED CONDENSERS: Wire end tubular. .0002, .0003, .0005, .002, 6/- doz.; .0001 to .006, 4/- per doz.; Assorted, 0M4 or tag end. **FIXED RESISTORS**: Assorted, 1/- watt, 4/- doz.; 1-watt, 6/- doz.

AERIAL INSULATORS, Small egg, 2/6; medium reel, 3/- doz.; large shell, 4/- doz.

PHILCO Block-type Fixed Condensers, .0001, .0002, .00025, .0003, .002, 9d. ea.; .01, 1/-; .02, 1/3; .05, 1/6; .1, 1/9; .15, 2/-.

PHILCO: 2-band Aerial and RF Coils, 6/-; with Trimmers, 8/-; Cans, 2/-; 2-band 125 kcs. Oscillator Coils, 6/-; 3-band 451 and 465 kcs. Oscillator Coils, with Trimmers, 10/-; Cans, 2/-; IF Transformers, 260 kcs., 3/6; 125 kcs., 5/-; 451 and 465 kcs., 10/-.

STAND-OFF Beehive Insulators, 1/-; Slow-motion driving-head spindles, 3/6; Insulated Hooks (screw-in), short, 2/- doz.; long 3/6 doz. Slow-motion Discs, (old type), 2/6.

Terms—Cash with order, postage extra. Satisfaction guaranteed. Stamp with enquiries please.


E. H. ROBINS TRADING CO. LTD.,
44, Kyle Crescent South, Whitchurch, Glam.

• VALVES •

This is part of our current stock list of types available and many representing equivalents to numerous valves not mentioned; a stamped envelope will bring you any information about any other particular valve you may desire. If out of stock we may send equivalents. All at Board of Trade controlled prices. C.O.D.

ACPI, AC2Pen, ACSPI, AC6Pen, ACHI, ACHLDD, APP4E, ACHIM, ACME, AC-PA4, AC/P, AC04A, ACTH1, ACSPI, ACTH4, ACTP, ACVP2, AZ1, AZ31, B30, B63, CR220, CL53, CCH35, CL4, D41, D63, D13, DD14, DDT24, DD4D, DC3-H1, DD14, DC3-SG, DC/Pen, DCHL, DC8G, DD101, DD16, DL63, DDT4, DHD, DHT3M, DW2, EBC3, EBC33, EBL1, EBL31, ECH2, ECH3, ECH3E, F6E, F6E, F8N, F8F, F839, EK2, EK3, EL2, EL3, EL52, EL33, EL35, EM1, EM4, FC3A, FC4, FC13, FC13C, FV4-500, H12, H14ID, H124, H12, H14, H121DD, H122, H123, H123DD, H141, H141DD, H133DD, H1320, HP215, HP210, HR210, IW4-350, IW4-500, IRF120, K70B, KT24, KT32, KT33C, KT41, KT61, KT63, KTW61, KTW63, KTZ63, L63, LD210, LP2, LP220, M81, ME920, M14, MH41, M14A, M14, M14A, M14B, M8Pen, M8Pen, MH4105, MVS PenB, MX40, MX4, OM6, OM9, P2, PA20, Pen45, Pen46, Pen49E, PenA4, PenB4, Pen4DD, Pen4VA, PM12A, PM2BA, PM2BA, PM12M, PM2HL, PM22A, PPS-260, PPS-600, PP222, P220, PT2-K, P24, P225, QP25, 8215VM, SP2, SP2D, SF4, SF4B, SF13, SF13C, SF215, SF120, SP220, TD12A, TD14, TDD13C, TH2, TH4, TH4B, TH130, TH2IC, TH30C, TH41, TH233, TP26, TP1340, TT4, TX4, TX41, U5, U10, U17, U31, U60, U82, U8, U8, U8, U7, UY31, VMP4G, VMP4K, V048, VP2, VP2B, VP4A, VP13A, VP13K, VP21, VP23, VP41, VP133, VP210, V89, V824K, V814, W21, W40, WD40, X22, X24, X41, X63, X64, X61M, X65, Y61, Y63, Z14, Z21, Z22.

AMERICAN TYPES—01A, 1A4E, 1B4, 1B6-253, 1C5, 1D7, 1E7, 1F4, 1F7, 1H5, 1J5, 1J6, 1LA4, 1N6, 2A3, 2A6, 2A7, 2B6, 2B7, 2D4B, 2P, 2XP, 4D1, 4TH4, 5U4A, 5Y3, 5Y4, 6A3, 6A6, 6A8, 6A6G, 6B6, 6B7, 6B8, 6C5, 6C8, 6D5, 6D6, 6F6, 6F7, 6F8, 6F6, 6J7, 6K7, 6K8, 6L6, 6N6, 6Q7, 6P5, 6P7, 68Q7, 68K7, 68Q7, 6U5, 6V6, 6X6, 6Z3, 6Z5-1225, 7A7E, 7A8, 7B5, 7B6, 7B7, 7B7E, 7B8E, 7C5, 7C6, 7D3, 7D5, 8D2, 9A1, 9A2, 10B1, 11D3, 11D6, 12A, 12B, 12C, 12D, 12E, 12F, 12G, 12H, 12J, 12K, 12L, 12M, 12N, 12O, 12P, 12Q, 12R, 12S, 12T, 12U, 12V, 12W, 12X, 12Y, 12Z, 13A, 13B, 13C, 13D, 13E, 13F, 13G, 13H, 13I, 13J, 13K, 13L, 13M, 13N, 13O, 13P, 13Q, 13R, 13S, 13T, 13U, 13V, 13W, 13X, 13Y, 13Z, 14A, 14B, 14C, 14D, 14E, 14F, 14G, 14H, 14I, 14J, 14K, 14L, 14M, 14N, 14O, 14P, 14Q, 14R, 14S, 14T, 14U, 14V, 14W, 14X, 14Y, 14Z, 15A, 15B, 15C, 15D, 15E, 15F, 15G, 15H, 15I, 15J, 15K, 15L, 15M, 15N, 15O, 15P, 15Q, 15R, 15S, 15T, 15U, 15V, 15W, 15X, 15Y, 15Z, 16A, 16B, 16C, 16D, 16E, 16F, 16G, 16H, 16I, 16J, 16K, 16L, 16M, 16N, 16O, 16P, 16Q, 16R, 16S, 16T, 16U, 16V, 16W, 16X, 16Y, 16Z, 17A, 17B, 17C, 17D, 17E, 17F, 17G, 17H, 17I, 17J, 17K, 17L, 17M, 17N, 17O, 17P, 17Q, 17R, 17S, 17T, 17U, 17V, 17W, 17X, 17Y, 17Z, 18A, 18B, 18C, 18D, 18E, 18F, 18G, 18H, 18I, 18J, 18K, 18L, 18M, 18N, 18O, 18P, 18Q, 18R, 18S, 18T, 18U, 18V, 18W, 18X, 18Y, 18Z, 19A, 19B, 19C, 19D, 19E, 19F, 19G, 19H, 19I, 19J, 19K, 19L, 19M, 19N, 19O, 19P, 19Q, 19R, 19S, 19T, 19U, 19V, 19W, 19X, 19Y, 19Z, 20A, 20B, 20C, 20D, 20E, 20F, 20G, 20H, 20I, 20J, 20K, 20L, 20M, 20N, 20O, 20P, 20Q, 20R, 20S, 20T, 20U, 20V, 20W, 20X, 20Y, 20Z, 21A, 21B, 21C, 21D, 21E, 21F, 21G, 21H, 21I, 21J, 21K, 21L, 21M, 21N, 21O, 21P, 21Q, 21R, 21S, 21T, 21U, 21V, 21W, 21X, 21Y, 21Z, 22A, 22B, 22C, 22D, 22E, 22F, 22G, 22H, 22I, 22J, 22K, 22L, 22M, 22N, 22O, 22P, 22Q, 22R, 22S, 22T, 22U, 22V, 22W, 22X, 22Y, 22Z, 23A, 23B, 23C, 23D, 23E, 23F, 23G, 23H, 23I, 23J, 23K, 23L, 23M, 23N, 23O, 23P, 23Q, 23R, 23S, 23T, 23U, 23V, 23W, 23X, 23Y, 23Z, 24A, 24B, 24C, 24D, 24E, 24F, 24G, 24H, 24I, 24J, 24K, 24L, 24M, 24N, 24O, 24P, 24Q, 24R, 24S, 24T, 24U, 24V, 24W, 24X, 24Y, 24Z, 25A, 25B, 25C, 25D, 25E, 25F, 25G, 25H, 25I, 25J, 25K, 25L, 25M, 25N, 25O, 25P, 25Q, 25R, 25S, 25T, 25U, 25V, 25W, 25X, 25Y, 25Z, 26A, 26B, 26C, 26D, 26E, 26F, 26G, 26H, 26I, 26J, 26K, 26L, 26M, 26N, 26O, 26P, 26Q, 26R, 26S, 26T, 26U, 26V, 26W, 26X, 26Y, 26Z, 27A, 27B, 27C, 27D, 27E, 27F, 27G, 27H, 27I, 27J, 27K, 27L, 27M, 27N, 27O, 27P, 27Q, 27R, 27S, 27T, 27U, 27V, 27W, 27X, 27Y, 27Z, 28A, 28B, 28C, 28D, 28E, 28F, 28G, 28H, 28I, 28J, 28K, 28L, 28M, 28N, 28O, 28P, 28Q, 28R, 28S, 28T, 28U, 28V, 28W, 28X, 28Y, 28Z, 29A, 29B, 29C, 29D, 29E, 29F, 29G, 29H, 29I, 29J, 29K, 29L, 29M, 29N, 29O, 29P, 29Q, 29R, 29S, 29T, 29U, 29V, 29W, 29X, 29Y, 29Z, 30A, 30B, 30C, 30D, 30E, 30F, 30G, 30H, 30I, 30J, 30K, 30L, 30M, 30N, 30O, 30P, 30Q, 30R, 30S, 30T, 30U, 30V, 30W, 30X, 30Y, 30Z, 31A, 31B, 31C, 31D, 31E, 31F, 31G, 31H, 31I, 31J, 31K, 31L, 31M, 31N, 31O, 31P, 31Q, 31R, 31S, 31T, 31U, 31V, 31W, 31X, 31Y, 31Z, 32A, 32B, 32C, 32D, 32E, 32F, 32G, 32H, 32I, 32J, 32K, 32L, 32M, 32N, 32O, 32P, 32Q, 32R, 32S, 32T, 32U, 32V, 32W, 32X, 32Y, 32Z, 33A, 33B, 33C, 33D, 33E, 33F, 33G, 33H, 33I, 33J, 33K, 33L, 33M, 33N, 33O, 33P, 33Q, 33R, 33S, 33T, 33U, 33V, 33W, 33X, 33Y, 33Z, 34A, 34B, 34C, 34D, 34E, 34F, 34G, 34H, 34I, 34J, 34K, 34L, 34M, 34N, 34O, 34P, 34Q, 34R, 34S, 34T, 34U, 34V, 34W, 34X, 34Y, 34Z, 35A, 35B, 35C, 35D, 35E, 35F, 35G, 35H, 35I, 35J, 35K, 35L, 35M, 35N, 35O, 35P, 35Q, 35R, 35S, 35T, 35U, 35V, 35W, 35X, 35Y, 35Z, 36A, 36B, 36C, 36D, 36E, 36F, 36G, 36H, 36I, 36J, 36K, 36L, 36M, 36N, 36O, 36P, 36Q, 36R, 36S, 36T, 36U, 36V, 36W, 36X, 36Y, 36Z, 37A, 37B, 37C, 37D, 37E, 37F, 37G, 37H, 37I, 37J, 37K, 37L, 37M, 37N, 37O, 37P, 37Q, 37R, 37S, 37T, 37U, 37V, 37W, 37X, 37Y, 37Z, 38A, 38B, 38C, 38D, 38E, 38F, 38G, 38H, 38I, 38J, 38K, 38L, 38M, 38N, 38O, 38P, 38Q, 38R, 38S, 38T, 38U, 38V, 38W, 38X, 38Y, 38Z, 39A, 39B, 39C, 39D, 39E, 39F, 39G, 39H, 39I, 39J, 39K, 39L, 39M, 39N, 39O, 39P, 39Q, 39R, 39S, 39T, 39U, 39V, 39W, 39X, 39Y, 39Z, 40A, 40B, 40C, 40D, 40E, 40F, 40G, 40H, 40I, 40J, 40K, 40L, 40M, 40N, 40O, 40P, 40Q, 40R, 40S, 40T, 40U, 40V, 40W, 40X, 40Y, 40Z, 41A, 41B, 41C, 41D, 41E, 41F, 41G, 41H, 41I, 41J, 41K, 41L, 41M, 41N, 41O, 41P, 41Q, 41R, 41S, 41T, 41U, 41V, 41W, 41X, 41Y, 41Z, 42A, 42B, 42C, 42D, 42E, 42F, 42G, 42H, 42I, 42J, 42K, 42L, 42M, 42N, 42O, 42P, 42Q, 42R, 42S, 42T, 42U, 42V, 42W, 42X, 42Y, 42Z, 43A, 43B, 43C, 43D, 43E, 43F, 43G, 43H, 43I, 43J, 43K, 43L, 43M, 43N, 43O, 43P, 43Q, 43R, 43S, 43T, 43U, 43V, 43W, 43X, 43Y, 43Z, 44A, 44B, 44C, 44D, 44E, 44F, 44G, 44H, 44I, 44J, 44K, 44L, 44M, 44N, 44O, 44P, 44Q, 44R, 44S, 44T, 44U, 44V, 44W, 44X, 44Y, 44Z, 45A, 45B, 45C, 45D, 45E, 45F, 45G, 45H, 45I, 45J, 45K, 45L, 45M, 45N, 45O, 45P, 45Q, 45R, 45S, 45T, 45U, 45V, 45W, 45X, 45Y, 45Z, 46A, 46B, 46C, 46D, 46E, 46F, 46G, 46H, 46I, 46J, 46K, 46L, 46M, 46N, 46O, 46P, 46Q, 46R, 46S, 46T, 46U, 46V, 46W, 46X, 46Y, 46Z, 47A, 47B, 47C, 47D, 47E, 47F, 47G, 47H, 47I, 47J, 47K, 47L, 47M, 47N, 47O, 47P, 47Q, 47R, 47S, 47T, 47U, 47V, 47W, 47X, 47Y, 47Z, 48A, 48B, 48C, 48D, 48E, 48F, 48G, 48H, 48I, 48J, 48K, 48L, 48M, 48N, 48O, 48P, 48Q, 48R, 48S, 48T, 48U, 48V, 48W, 48X, 48Y, 48Z, 49A, 49B, 49C, 49D, 49E, 49F, 49G, 49H, 49I, 49J, 49K, 49L, 49M, 49N, 49O, 49P, 49Q, 49R, 49S, 49T, 49U, 49V, 49W, 49X, 49Y, 49Z, 50A, 50B, 50C, 50D, 50E, 50F, 50G, 50H, 50I, 50J, 50K, 50L, 50M, 50N, 50O, 50P, 50Q, 50R, 50S, 50T, 50U, 50V, 50W, 50X, 50Y, 50Z, 51A, 51B, 51C, 51D, 51E, 51F, 51G, 51H, 51I, 51J, 51K, 51L, 51M, 51N, 51O, 51P, 51Q, 51R, 51S, 51T, 51U, 51V, 51W, 51X, 51Y, 51Z, 52A, 52B, 52C, 52D, 52E, 52F, 52G, 52H, 52I, 52J, 52K, 52L, 52M, 52N, 52O, 52P, 52Q, 52R, 52S, 52T, 52U, 52V, 52W, 52X, 52Y, 52Z, 53A, 53B, 53C, 53D, 53E, 53F, 53G, 53H, 53I, 53J, 53K, 53L, 53M, 53N, 53O, 53P, 53Q, 53R, 53S, 53T, 53U, 53V, 53W, 53X, 53Y, 53Z, 54A, 54B, 54C, 54D, 54E, 54F, 54G, 54H, 54I, 54J, 54K, 54L, 54M, 54N, 54O, 54P, 54Q, 54R, 54S, 54T, 54U, 54V, 54W, 54X, 54Y, 54Z, 55A, 55B, 55C, 55D, 55E, 55F, 55G, 55H, 55I, 55J, 55K, 55L, 55M, 55N, 55O, 55P, 55Q, 55R, 55S, 55T, 55U, 55V, 55W, 55X, 55Y, 55Z, 56A, 56B, 56C, 56D, 56E, 56F, 56G, 56H, 56I, 56J, 56K, 56L, 56M, 56N, 56O, 56P, 56Q, 56R, 56S, 56T, 56U, 56V, 56W, 56X, 56Y, 56Z, 57A, 57B, 57C, 57D, 57E, 57F, 57G, 57H, 57I, 57J, 57K, 57L, 57M, 57N, 57O, 57P, 57Q, 57R, 57S, 57T, 57U, 57V, 57W, 57X, 57Y, 57Z, 58A, 58B, 58C, 58D, 58E, 58F, 58G, 58H, 58I, 58J, 58K, 58L, 58M, 58N, 58O, 58P, 58Q, 58R, 58S, 58T, 58U, 58V, 58W, 58X, 58Y, 58Z, 59A, 59B, 59C, 59D, 59E, 59F, 59G, 59H, 59I, 59J, 59K, 59L, 59M, 59N, 59O, 59P, 59Q, 59R, 59S, 59T, 59U, 59V, 59W, 59X, 59Y, 59Z, 60A, 60B, 60C, 60D, 60E, 60F, 60G, 60H, 60I, 60J, 60K, 60L, 60M, 60N, 60O, 60P, 60Q, 60R, 60S, 60T, 60U, 60V, 60W, 60X, 60Y, 60Z, 61A, 61B, 61C, 61D, 61E, 61F, 61G, 61H, 61I, 61J, 61K, 61L, 61M, 61N, 61O, 61P, 61Q, 61R, 61S, 61T, 61U, 61V, 61W, 61X, 61Y, 61Z, 62A, 62B, 62C, 62D, 62E, 62F, 62G, 62H, 62I, 62J, 62K, 62L, 62M, 62N, 62O, 62P, 62Q, 62R, 62S, 62T, 62U, 62V, 62W, 62X, 62Y, 62Z, 63A, 63B, 63C, 63D, 63E, 63F, 63G, 63H, 63I, 63J, 63K, 63L, 63M, 63N, 63O, 63P, 63Q, 63R, 63S, 63T, 63U, 63V, 63W, 63X, 63Y, 63Z, 64A, 64B, 64C, 64D, 64E, 64F, 64G, 64H, 64I, 64J, 64K, 64L, 64M, 64N, 64O, 64P, 64Q, 64R, 64S, 64T, 64U, 64V, 64W, 64X, 64Y, 64Z, 65A, 65B, 65C, 65D, 65E, 65F, 65G, 65H, 65I, 65J, 65K, 65L, 65M, 65N, 65O, 65P, 65Q, 65R, 65S, 65T, 65U, 65V, 65W, 65X, 65Y, 65Z, 66A, 66B, 66C, 66D, 66E, 66F, 66G, 66H, 66I, 66J, 66K, 66L, 66M, 66N, 66O, 66P, 66Q, 66R, 66S, 66T, 66U, 66V, 66W, 66X, 66Y, 66Z, 67A, 67B, 67C, 67D, 67E, 67F, 67G, 67H, 67I, 67J, 67K, 67L, 67M, 67N, 67O, 67P, 67Q, 67R, 67S, 67T, 67U, 67V, 67W, 67X, 67Y, 67Z, 68A, 68B, 68C, 68D, 68E, 68F, 68G, 68H, 68I, 68J, 68K, 68L, 68M, 68N, 68O, 68P, 68Q, 68R, 68S, 68T, 68U, 68V, 68W, 68X, 68Y, 68Z, 69A, 69B, 69C, 69D, 69E, 69F, 69G, 69H, 69I, 69J, 69K, 69L, 69M, 69N, 69O, 69P, 69Q, 69R, 69S, 69T, 69U, 69V, 69W, 69X, 69Y, 69Z, 70A, 70B, 70C, 70D, 70E, 70F, 70G, 70H, 70I, 70J, 70K, 70L, 70M, 70N, 70O, 70P, 70Q, 70R, 70S, 70T, 70U, 70V, 70W, 70X, 70Y, 70Z, 71A, 71B, 71C, 71D, 71E, 71F, 71G, 71H, 71I, 71J, 71K, 71L, 71M, 71N, 71O, 71P, 71Q, 71R, 71S, 71T, 71U, 71V, 71W, 71X, 71Y, 71Z, 72A, 72B, 72C, 72D, 72E, 72F, 72G, 72H, 72I, 72J, 72K, 72L, 72M, 72N, 72O, 72P, 72Q, 72R, 72S, 72T, 72U, 72V, 72W, 72X, 72Y, 72Z, 73A, 73B, 73C, 73D, 73E, 73F, 73G, 73H, 73I, 73J, 73K, 73L, 73M, 73N, 73O, 73P, 73Q, 73R, 73S, 73T, 73U, 73V, 73W, 73X, 73Y, 73Z, 74A, 74B, 74C, 74D, 74E, 74F, 74G, 74H, 74I, 74J, 74K, 74L, 74M, 74N, 74O, 74P, 74Q, 74R, 74S, 74T, 74U, 74V, 74W, 74X, 74Y, 74Z, 75A, 75B, 75C, 75D, 75E, 75F, 75G, 75H, 75I, 75J, 75K, 75L, 75M, 75N, 75O, 75P, 75Q, 75R, 75S, 75T, 75U, 75V, 75W, 75X, 75Y, 75Z, 76A, 76B, 76C, 76D, 76E, 76F, 76G, 76H, 76I, 76J, 76K, 76L, 76M, 76N, 76O, 76P, 76Q, 76R, 76S, 76T, 76U, 76V, 76W, 76X, 76Y, 76Z, 77A, 77B, 77C, 77D, 77E, 77F, 77G, 77H, 77I, 77J, 77K, 77L, 77M, 77N, 77O, 77P, 77Q, 77R, 77S, 77T, 77U, 77V, 77W, 77X, 77Y, 77Z, 78A, 78B, 78C, 78D, 78E, 78F, 78G, 78H, 78I, 78J, 78K, 78L, 78M, 78N, 78O, 78P, 78Q, 78R, 78S, 78T, 78U, 78V, 78W, 78X, 78Y, 78Z, 79A, 79B, 79C, 79D, 79E, 79F, 79G, 79H, 79I, 79J, 79K, 79L, 79M, 79N, 79O, 79P, 79Q, 79R, 79S, 79T, 79U, 79V, 79W, 79X, 79Y, 79Z, 80A, 80B, 80C, 80D, 80E, 80F, 80G, 80H, 80I, 80J, 80K, 80L, 80M, 80N, 80O, 80P, 80Q, 80R, 80S, 80T, 80U, 80V, 80W, 80X, 80Y, 80Z, 81A, 81B, 81C, 81D, 81E, 81F, 81G, 81H, 81I, 81J, 81K, 81L, 81M, 81N, 81O, 81P, 81Q, 81R, 81S, 81T, 81U, 81V, 81W, 81X, 81Y, 81Z, 82A, 82B, 82C, 82D,

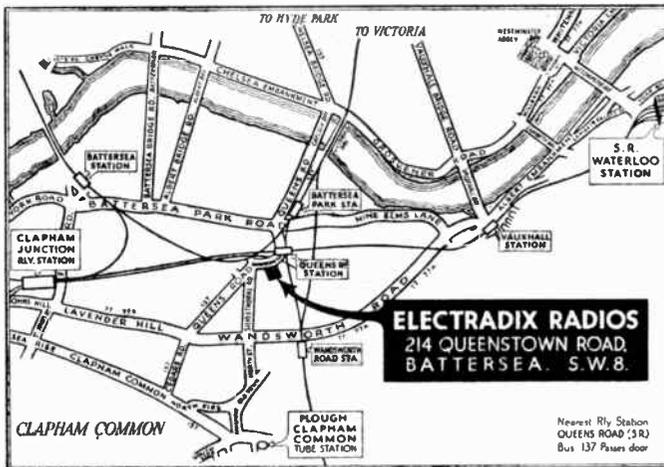

THERE IS NOTHING BETTER THAN SEEING THE GOODS

Whilst many readers of this journal have called, inspected and bought just the Radio, Electrical, Mechanical or Laboratory apparatus they desired, there must be hundreds of others who have not yet visited our New Showrooms. All are cordially invited. Come along. The time spent will be well worth while.

ELECTRADIX RADIOS offer exceptional bargains in:—

Morse Keys. Buzzers. Recorders. Relays. Wavemeters. Headphones. House-phones. Handcoms. Rheostats. Condensers. Dials. Transformers. Magnets. Turntables. Plugs. Sockets. Rotaries. Chargers. Mirror Galvos. Wheatstone Bridges. Resistor Boxes. Meggers. Radiogoniometers. Dynamos. Motors. Generators. Pumps. Circuit Breakers. Switches. Meters. Indicators. Engines. Motor Pumps. Petrol Electric Plants, etc., etc.

Telephone : MACaulay 2159.

Past

Starting with a lively interest in Sound Recording technique we concentrated on supplying readers with discs and the necessary small equipment. This early beginning rapidly developed and our activities soon embraced the Professional field.

Present

We have recently acquired new premises and all enquiries and correspondence should be addressed to:—

4 BITTACY PARK AVENUE, MILL HILL, N.W.7.

In addition to equipment previously advertised we now have completely mobile RECORDING AND SOUND AMPLIFYING EQUIPMENT available for hire in all parts of the country. Further details on application.

Enquiries are invited for all types of Sound Equipment.

We take this opportunity to apologise for any delay in the despatch of equipment owing to our present shortage of staff and the large amount of priority work which we have in hand.

Future

We are looking ahead and have already made our post-war plans. Our after-the-war address will be "The Elms," Warham Road, South Croydon, Surrey, where large studios with every modern facility for high quality recording will be available

SOUTHERN SOUND STUDIOS

4 Bittacy Park Avenue, Mill Hill, N.W.7

The Voice of the Services

SIGNALLING EQUIPMENT

LTD.

Specialists in Morse Equipment

Makers of Small Transformers, Heavy Duty Resistances, Plugs and Sockets, Fuse Holders, Electric Bells, Buzzers, and Switches. Also Plastic Mouldings, Coil Windings, Light Pressings, Turned Parts, and other components and accessories for the Wireless and Electrical Trades

Merit House, Southgate Road, Potters Bar

Phone : Potters Bar 3133. Telegrams & Cables : Sel, Potters Bar

BASICALLY BETTER...

Air Insulation
is the basic principle of

CO-AX

LOW LOSS CABLES

Unequaled

H.F. PROPERTIES

TRANSRADIO LTD. Inc. TELEQUIPMENT CO. 16 HIGHWAY, BEACONSFIELD.

The PYROBIT

ELECTRIC SOLDERING IRON — WIRELESS MODEL

THE LIGHTEST IRON ON THE MARKET

Weight 6 ozs. (without cable)


Tested and approved by most important users and Government Departments. All voltages from 12—250 v.

Stearite clad element inside the copper bit. Every part easily replaced—but the necessity seldom arises. Ask for Leaflets.

The AGRU ELECTRIC TOOL MFG. CO. LTD. 123 HYDE ROAD, ARDWICK, MANCHESTER, 12


Telephone : ARDwick 4284

Printed in England for the Publishers, ILLIFF AND BONS LTD., Dorset House, Stamford Street, London, S.E.1, by THE CORNWALL PRESS LTD., Paris Garden, Stamford Street, London, S.E.1. "The Wireless World" can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: Imperial News Co.; GORDON & GOTCH, Ltd. SOUTH AFRICA: Central News Agency, Ltd.; Wm. Dawson & Sons (S.A.), Ltd. UNITED STATES: The International News Co.

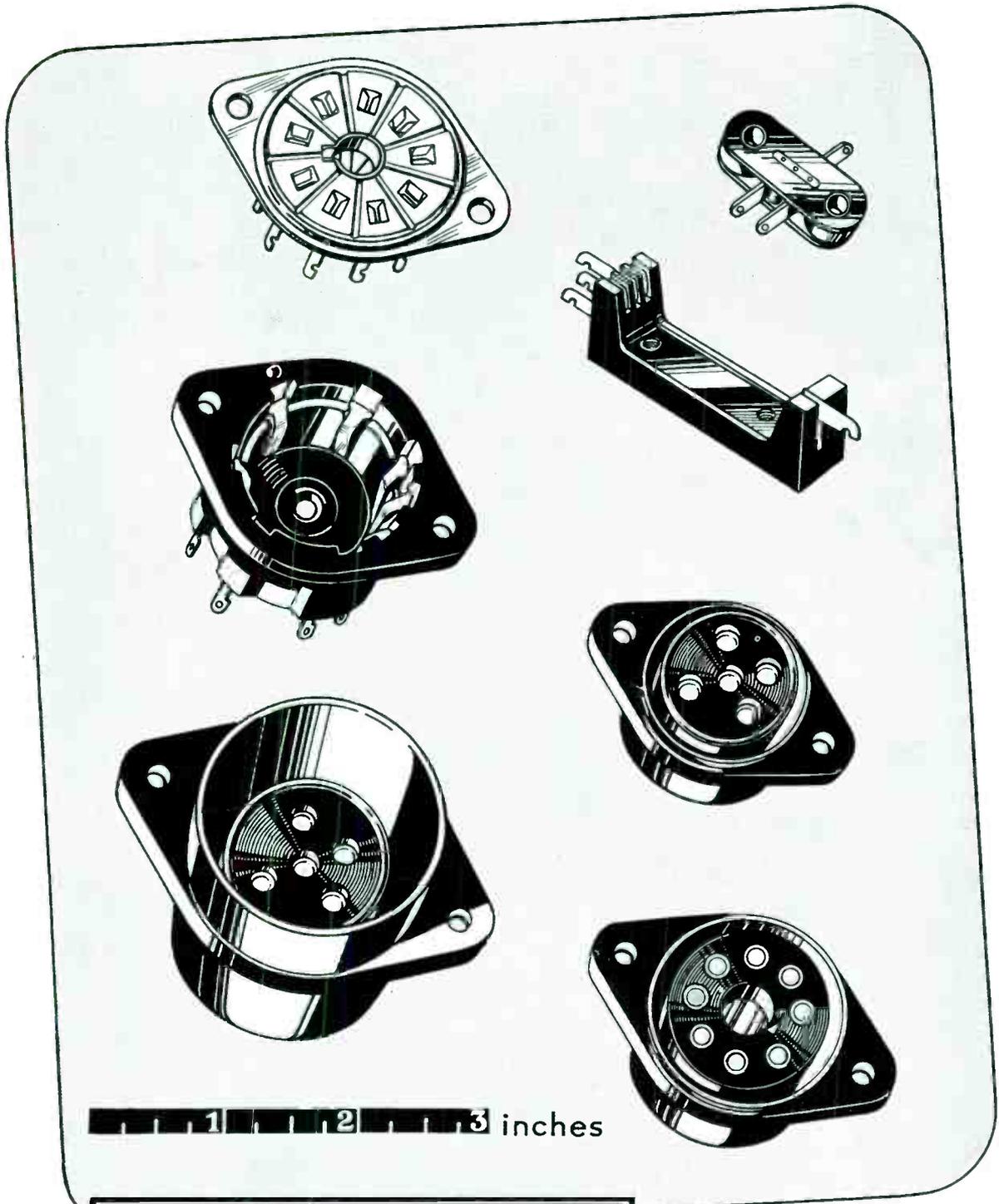

BELLING & LEE LTD
CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDDX

GA 8790

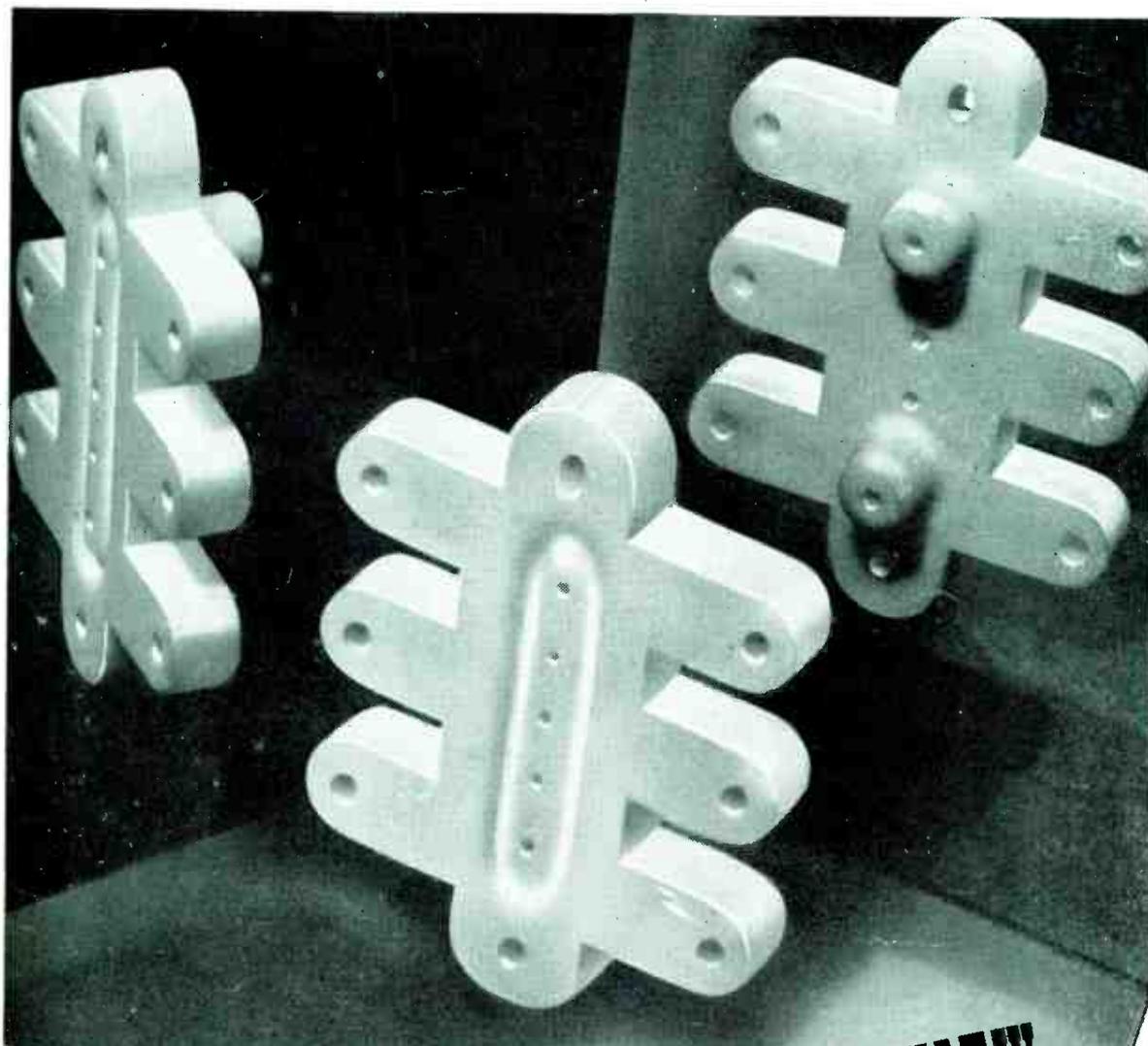

FROM EVERY POINT OF VIEW

Frequentite is the most suitable insulating material for all high frequency applications. Ten years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.



STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: Stourport-on-Severn, Worcester.

Telephone: Stourport 111.

Telegrams: Steatain, Stourport.

SP29