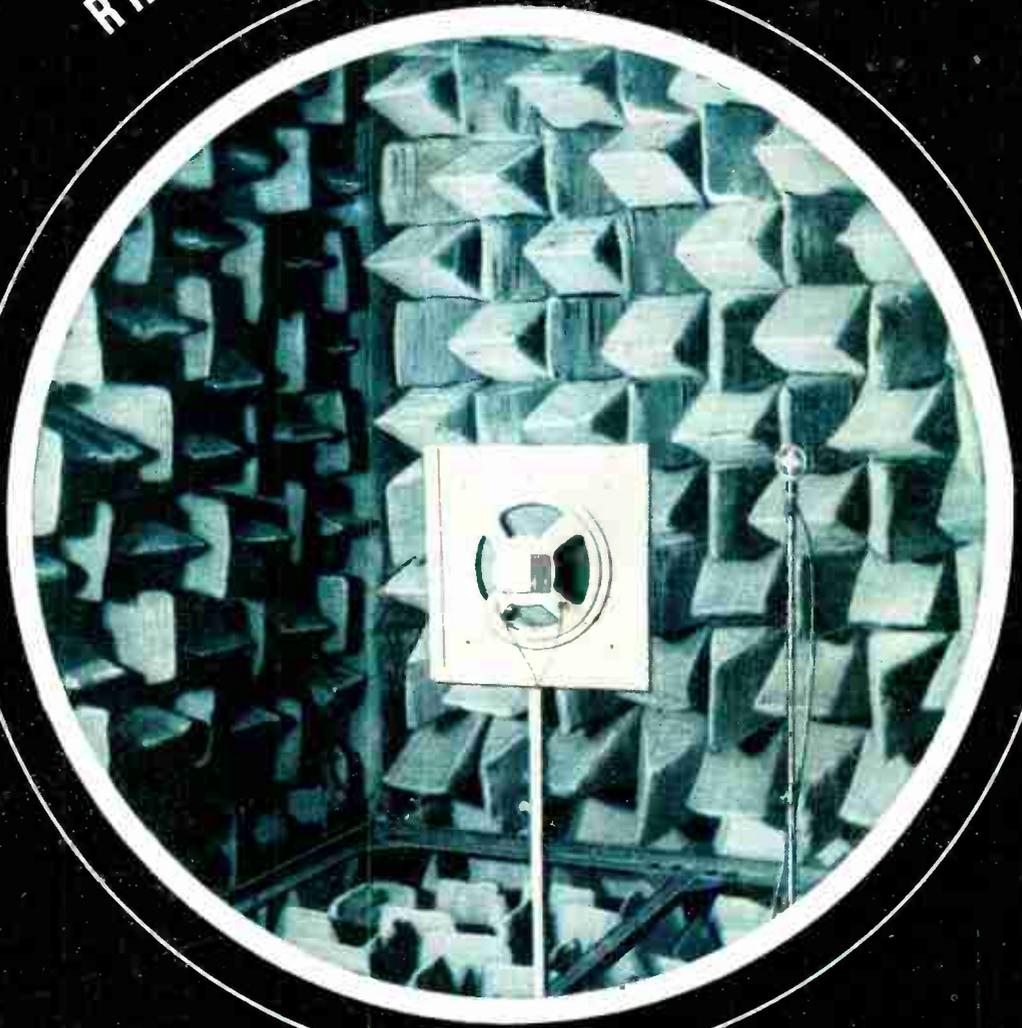


# Wireless World

RADIO AND ELECTRONICS



DEC. 1949


2/-

Vol. LV. No. 12

IN THIS  
ISSUE :

NEW NOISE-REDUCING CIRCUIT

# A PUBLICATION *for* RADIO ENGINEERS

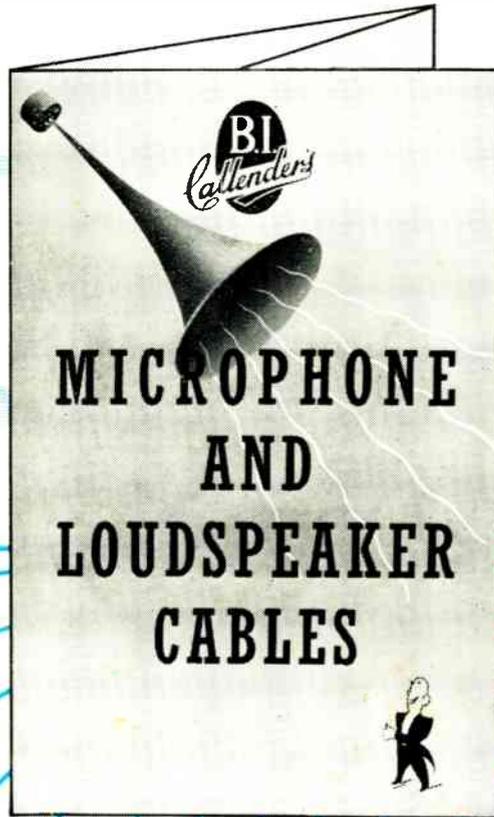

This folder contains useful information on the complete range of BICC cables and wiring accessories which have been specially designed for use with public address and paging systems.

Write to-day for Publication No. 245 I.

BRITISH INSULATED CALLENDER'S CABLES LIMITED  
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

*Fine Limits of Accuracy*



## VALVE CHARACTERISTIC METER

A comprehensive instrument built into one compact and convenient case, which will test any standard receiving or small power transmitting valve on any of its normal characteristics under conditions corresponding to any desired set of D.C. electrode voltages. A patented method enables A.C. voltages of suitable magnitude to be used throughout the Tester, thus eliminating the costly regulation problems associated with D.C. testing methods.


A specially developed polarised relay protects the instrument against misuse or incorrect adjustment. This relay also affords a high measure of protection to the valve under test. Successive settings of the Main Selector Switch enable the following to be determined :—

Complete Valve Characteristics including  $I_a/V_g$ ,  $I_a/V_a$ ,  $I_s/V_g$ ,  $I_s/V_a$ . Amplification Factor, Anode, A.C. Resistance, 4 ranges of Mutual Conductance covering  $m\mu/V$  figures up to 25  $m\mu/V$  at bias values up to  $-100V$ ., together with "Good/Bad" comparison test on coloured scale against rated figures.


"Gas" test for indicating presence and magnitude of grid current, inter-electrode insulation hot and cold directly indicated in megohms, separate cathode-to-heater insulation with valve hot. Tests Rectifying and Signal Diode Valves under reservoir load conditions, and covers all the heater voltages up to 120 volts.

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.  
WINDER HOUSE. DOUGLAS STREET. LONDON. S.W.1. Phone : VICTORIA 3404.9

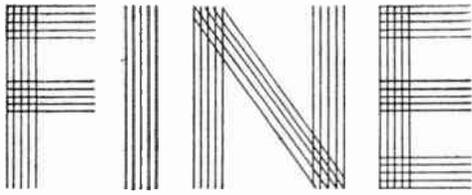*Avo Precision Electrical Testing Instruments*




# RESISTANCE WIRES

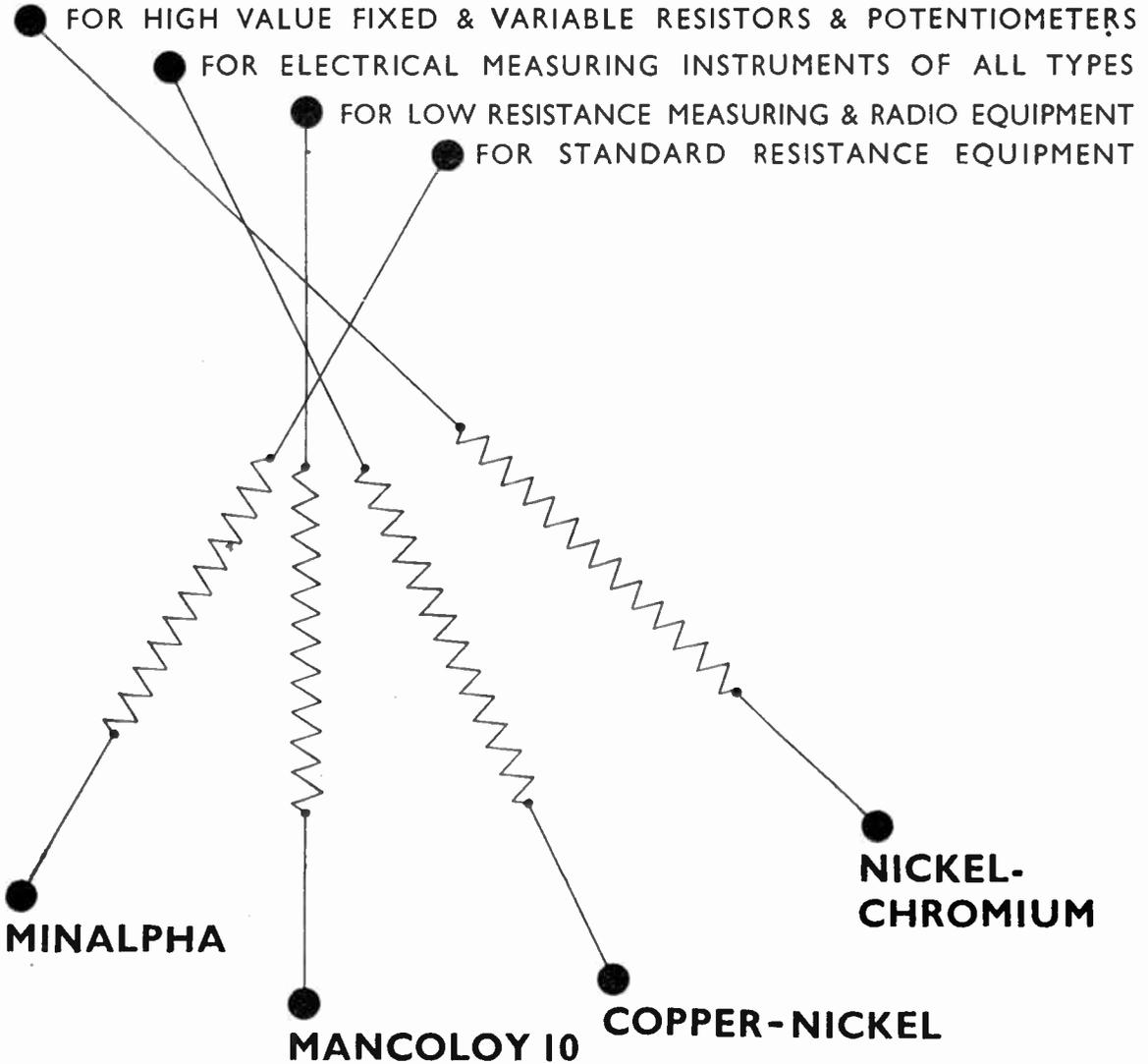

Comprehensive details of the properties of these alloys and of recommended uses of our precision-drawn resistance wires are given in Booklet 1440, freely available to you on request

**Johnson**   
**Matthey**

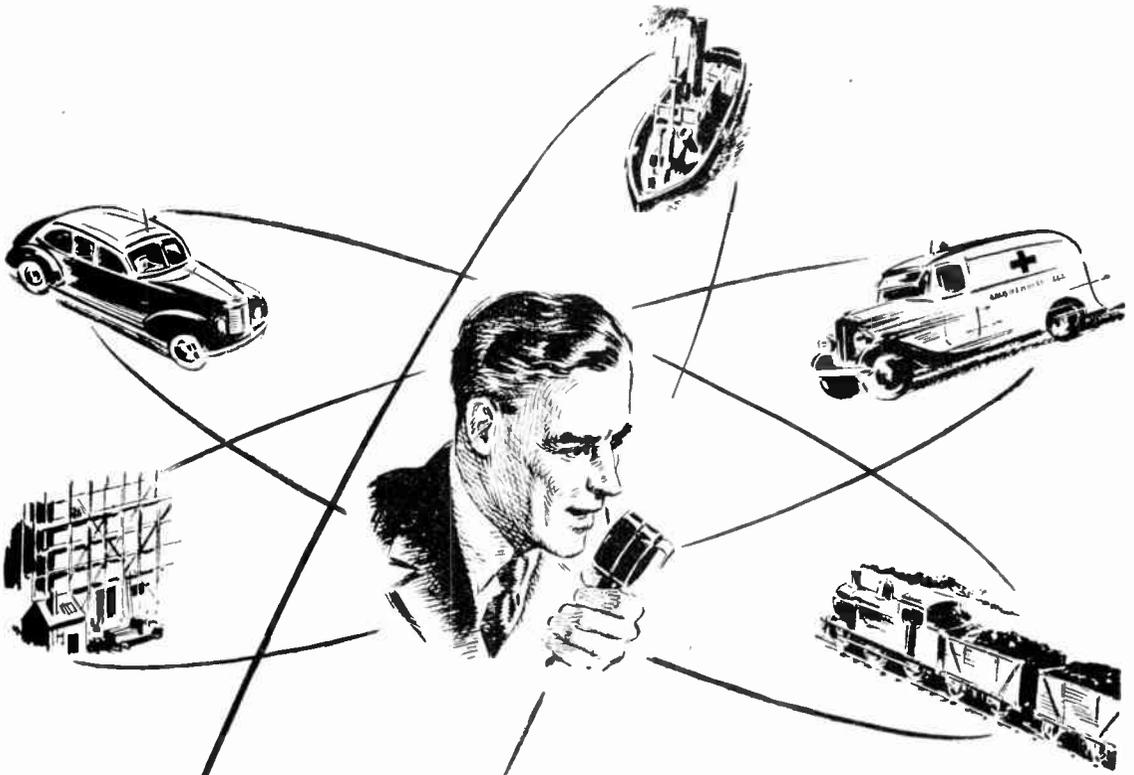JOHNSON, MATTHEY & CO., LTD., HATTON GARDEN, LONDON, E.C.1  
 Birmingham: Vittoria Street, Birmingham 1



# PYE

## *Business radio*

- Contracting Engineers
- Haulage Contractors
- Fire Services
- Doctors
- Ambulance Services
- News Editors
- Veterinary Surgeons
- Building Contractors
- Port and Harbour Authorities
- Private Hire Companies
- Airports
- Surveyors
- Railways
- Agricultural Engineers

Pye Ltd. announce a complete new range of "fixed" and mobile V.H.F. Radio-Telephone equipment for the Business Radio band 156-184 Mc/s, and for essential services in the 60-130 Mc/s band.

Combining the high performance made possible by modern V.H.F. Radio techniques with reliability and simplicity of operation, this new Pye equipment will meet the exacting needs of Government and Industry at home and overseas.

*Further details will be sent on request.*



PYE LIMITED • TELECOMMUNICATIONS DIVISION • CAMBRIDGE • ENGLAND

# 45!

## Right for Every pocket

# TRUVOX

Truvox speakers can be obtained from all good dealers. Full technical data and price lists of the complete Truvox range will be gladly forwarded upon request.


# 12" C.P.M.



Frequency range 60-8,000 c.p.s. bass resonance 65 c.p.s.; flux density 10,000 gauss; power handling capacity 10 watt (peak). Voice coil D.C. Resistance 2.6 ohms. The specification speaks for itself. The TRUVOX 12 inch C.P.M. speaker Model BX11, marks something of an economic revolution in the high quality reproduction of sound.

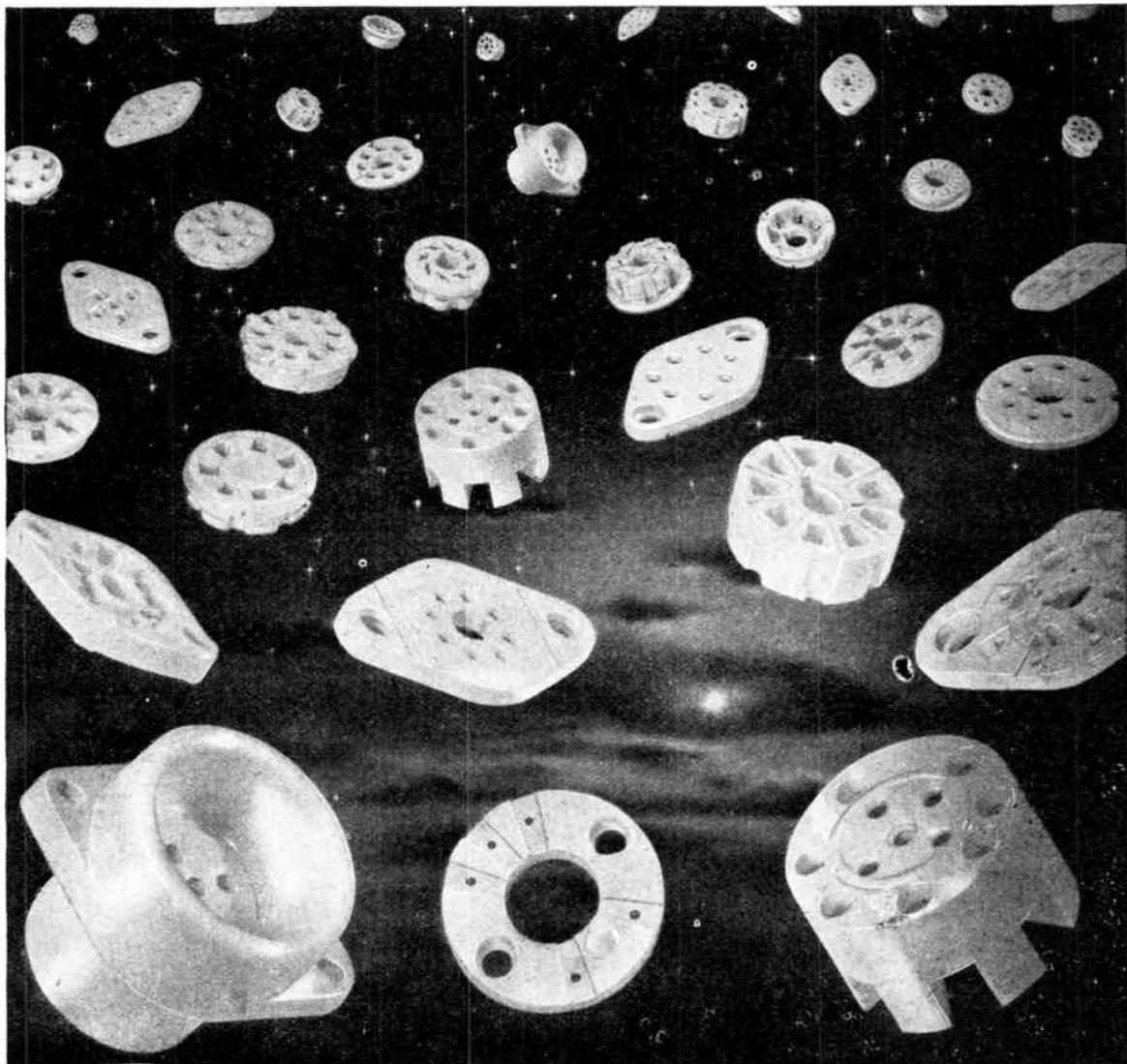**TRUVOX ENGINEERING CO. LTD., EXHIBITION GROUNDS, WEMBLEY, MIDDX.**

"JUNO" and "OCO" floor polishing machines are also manufactured by TRUVOX—send for details.



# CERAMICS

FOR VALVE HOLDERS  
and all radio components  
FREQUENTITE — FARADEx — TEMPRADEx

**STEATITE & PORCELAIN PRODUCTS LTD.**

Stourport on Severn, Worcester

Telephone: Stourport 111


Telegrams: Steatite, Stourport



S.P.55

**designed . . . .**

**with  
your  
specific  
needs  
in  
mind**

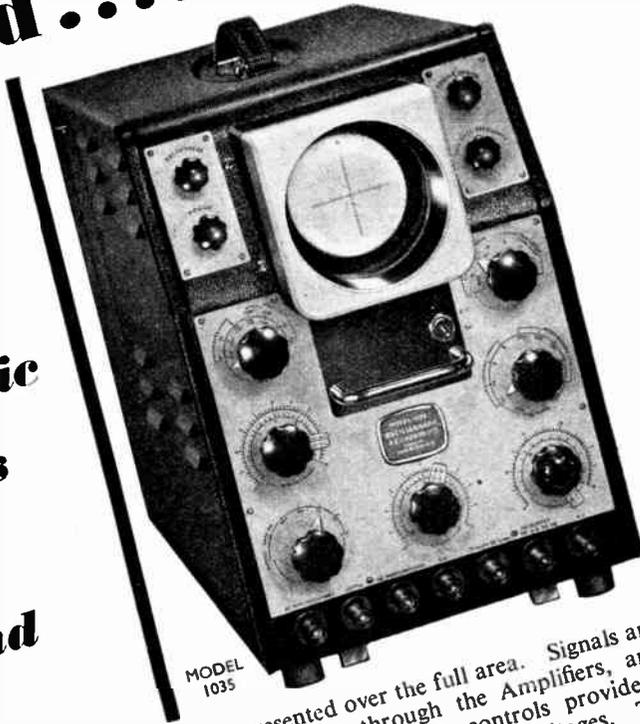

MODEL 1035

The Cossor general purpose Oscillograph is designed and built by electronic engineers who are themselves familiar with the everyday problems which technicians have to face. The instrument consists of a Double Beam Tube operated at 2kV., a Time Base, Y Deflection Amplifiers and Internal Power Supplies. The 90mm. screen is flat, and traces

are presented over the full area. Signals are normally fed through the Amplifiers, and the calibrated Y-Shift controls provide a measurement of the applied voltages. The Time Base operates repetitively, or by external trigger (for single stroke operation), or at trigger pulse repetition frequency for continuous scanning. A calibrated X-Shift Control is provided for the measurement of Time.



**Model 1428  
C A M E R A**

Specially developed for use with Cossor Oscillographs, it provides the simplest means of recording stationary or non-recurrent waveforms and slow transients by the moving film method on standard perforated 35 mm. film or paper. Of robust construction, it has provision for power drive by the Cossor Three-Speed Motor Attachment, Model 1429.

**COSSOR**  
**Double Beam**  
**OSCILLOGRAPH**

Further details obtainable on application to:—

**A. C. COSSOR LTD., INSTRUMENT DIVISION, Highbury, London, N.5**

CI11



Starring in the Samuel  
Coldwyn Technicolor  
Production  
"A Song is Born"

USING HIS

# Soundmirror

MAGNETIC TAPE RECORDER

*Made in England. Protected  
by British & Foreign Patents  
and Patents Pending.*

*Full details from the Manufacturers, or Demonstrations by  
Appointment.*

**THERMIONIC PRODUCTS LTD.**  
**MORRIS HOUSE, JERMYN STREET,**  
**HAYMARKET, LONDON, S.W.1**

Telephone: WHItchall 6422 (5 lines)

With this one compact and reasonably priced Instrument you are completely equipped for all Sound Recording and Reproducing.

The Soundmirror is a high-fidelity Instrument which records and reproduces on reels of inexpensive magnetic tape Speech, Music, and every other sound audible to the human ear. Each reel gives a half-hour's uninterrupted playing. Short recordings can be cut and joined together. Playback is immediate. Recordings are permanent or if desired, can be automatically erased as new items are recorded.

The Soundmirror is simple to operate—Single finger-tip control for Play, Record, Fast Re-wind or Fast Forward requirements.

Built-in jacks enable the Soundmirror to be used in conjunction with radio or public address equipment.

SALES AND SERVICE CENTRES: BIRMINGHAM · MANCHESTER · BRISTOL · LEEDS, etc.


# An entirely new development...

## THE METROVICK UNIVERSAL METER

This latest Metrovick product in the field of electronics gives the Electronic and Radio Engineer all he needs in a multi-range instrument for the measurement of current, resistance and voltage. In addition, provision for R.F. Voltages is made by the inclusion of a probe which employs a diode valve for rectification. All sections give indication on the same moving coil instrument, and a multiplier switch enables all the A.C. and D.C. ranges, except the 1000 volt scales to be trebled if required.

Though so compact, the instrument is robust enough to be used constantly under average conditions. It weighs only 17 lb., and is contained in an attractive steel case in cream or blue hard stoved enamel, fitted with leather carrying handle.

**TYPE 214**

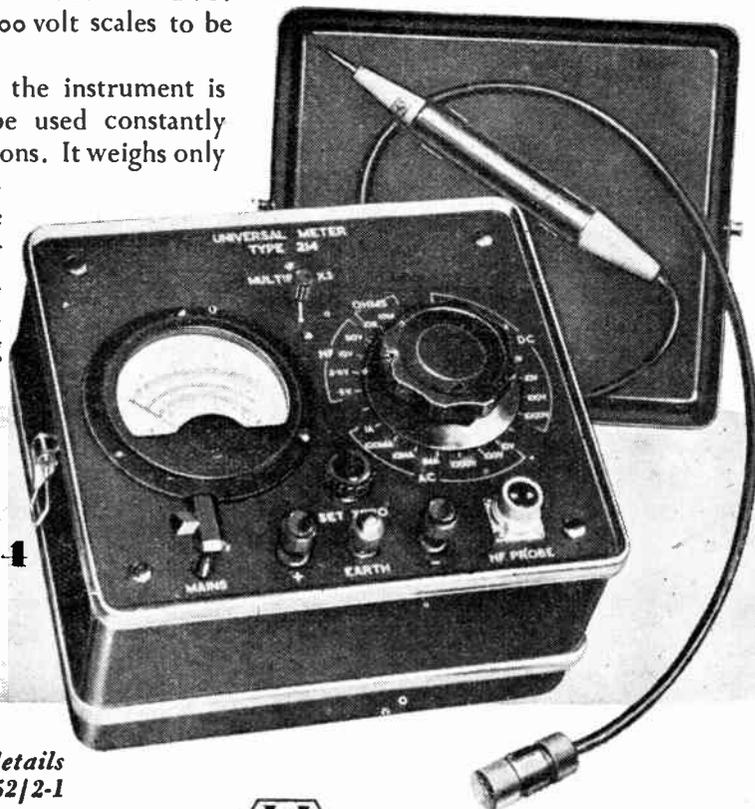


*Send for further details  
contained in leaflet 652/2-1*



**METROPOLITAN-VICKERS ELECTRICAL CO. LTD.**

TRAFFORD PARK, MANCHESTER 17

# in communications...

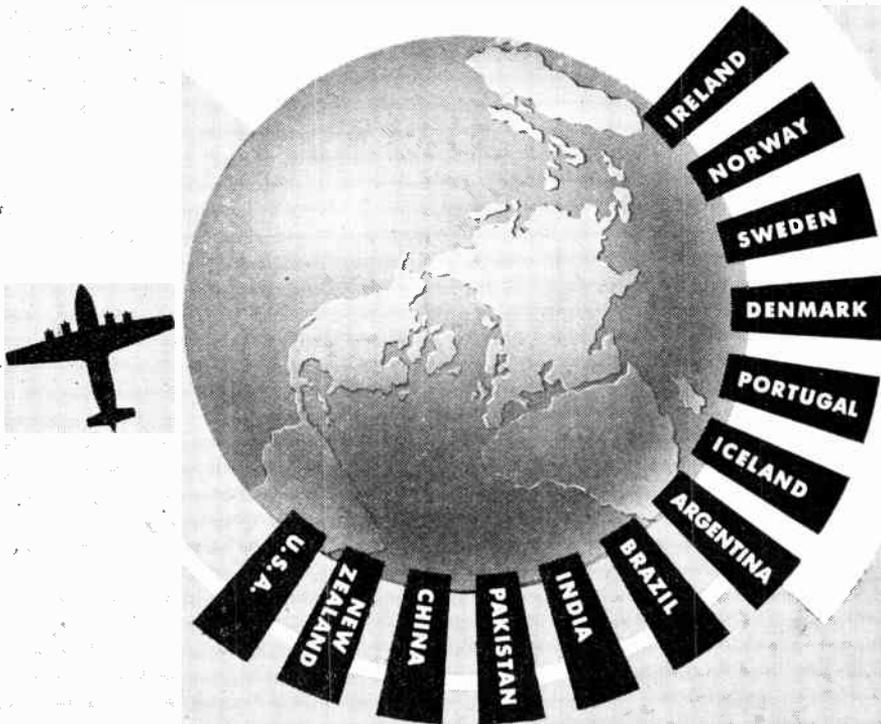

## WILCOX SERVES THE GOVERNMENTS OF THE WORLD

Wherever airplanes fly—wherever lives depend on reliable communications—you'll find WILCOX radio transmitting and receiving equipment. From the Scandinavian countries to New Zealand...from Portugal to Pakistan, the governments of the world select WILCOX because of its proven performance under all extremes of climate, temperature, and humidity.

As with many governments, WILCOX is being used by the United States government in the basic communication systems for the Air Force, Signal Corps, and the Civil Aeronautics Authority.

The governments of the world have spanned the globe with WILCOX communications. From the Berlin Airlift to the Orient...WILCOX equipments carry the messages that help keep freedom a vital force in the turbulent affairs of the world.

**WRITE TODAY...** for complete information on all types of point-to-point, air-borne, ground station, or shore-to-ship communications equipment.



## WILCOX ELECTRIC COMPANY


KANSAS CITY

MISSOURI, U.S.A.

# PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

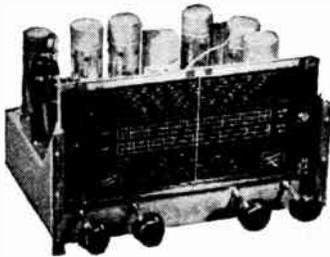**A NEW A.C. ALL-WAVE SUPERHET RECEIVER**



7 Valves (plus metal Rectifiers) for 200/250 volts; 40/60 cycle A.C. mains. 4 wavebands, 13.6-32, 51-200, 200-550 and 900-2,100 metres. Pick-up input. Uses 6K7, 6K8, 6K7, 6B8, 6J7 and 2-6V6 in push-pull, giving an output of 10 watts. Specially designed OP Transformer to match 6V6's to 3 and 15 ohm Speakers. Negative feedback is applied over 3 stages giving a high fidelity output. Completely wired and tested, £15/17/9. Our Universal model is still available at £15 built; or £13/8/- in kit form. All prices include Pur. Tax.

**H.T. METAL RECTIFIERS.**

230 v. 30 m/a., 2/6; 260 v. 30 m/a., 3/-; 300 v. 75 m/a., 4/-; 250 v. 120 m/a., 5/-.

**L.T. METAL RECTIFIERS.**

To charge. 2 v. Acc. at 1 a., 2/-; 12 v. Acc. at 1 a., 6/-; 24 v. Acc. at 6 a., 37/6.

**E.H.T. RECTIFIERS.**

J.50 400 v. at 2 m/a., 3/6 each, or 18/- for six.

**BATTERY CHARGERS.**

Input 100/250 v. A.C. Output 15 volts at 16 amps. Continuously variable metered output. Usual price £24. Our price £10/10/- each plus 10/- carriage.

**BATTERY CHARGER KITS.**

All incorporate Metal Rectifiers. Transformers are suitable for 200-250 v. A.C. 50 cycles.

Cat. No.	Price.
2002. Charges 6-volt Accumulator at 1 amp. Resistance supplied to charge 2 v. Accumulator	£1/2/6
2003. Charges 12-volt Accumulator 1 amp	£1/7/6
2004. Output 15 v. 4 a. Variable Resistance and Meter	£3/15/-
2005. Output 15 v. 6 a. Variable Resistance and Meter	£5/-
2007. Output 30 v. 5 a. Variable Resistance and Meter	£6/-
2009. Output 24 v. 3 a. Variable Resistance and Meter	£4/5/-

**COLLARO AUTOMATIC RECORD CHANGERS.**

Type RC500 R.m.-drive. Plays nine 10in. or 12in. records. A.C. 100/250 v., with High Fidelity Magnetic Pick-up, £10/15/-. With Crystal Pick-up, £11/8/4.

**COLLARO GRAMOPHONE UNITS.**

High grade Rim-drive Motors, complete with Pick-up and Automatic Stop-Start. A.C. 100/250. With Magnetic Pick-up, £5/3/2. With Crystal Pick-up, £5/17/7.

**CONRAD GRAMOPHONE MOTORS.**

A reliable Rim-drive Motor for A.C. 100/250 v. operation, £2/17/6.

**ALUMINIUM CHASSIS.**

16 S.W.G. Substantially made of bright aluminium with four sides.

Size	Price.
7in. x 3 1/2in. x 2 1/2in.	3/3
9 1/2in. x 4 1/2in. x 2 1/2in.	4/-
10 1/2in. x 8in. x 2 1/2in.	5/6
12 1/2in. x 9in. x 2 1/2in.	6/8
14 1/2in. x 9in. x 2 1/2in.	6/11
16 1/2in. x 8in. x 2 1/2in.	7/3
20in. x 8in. x 2 1/2in.	7/11
22in. x 10in. x 2 1/2in.	10/-
10in. x 9in. x 3in.	6/3
12in. x 10in. x 3in.	6/10
14in. x 10in. x 3in.	7/11
16in. x 10in. x 3in.	8/6
20in. x 10in. x 3in.	10/-

**NINE DETECTOR PANELS.** Include three 1T4 valves. 12-1 Midget Traps, three ceramic valveholders, 18 condenser and resistors, etc., 20/-. Without valves, 5/-.

**ELECTRON MULTIPLIER PHOTO CELL TUBES.** Type 931A. Brand new. Guaranteed, 30/-.

**CRYSTAL DIODES.** Type CV102, 3/6 each.

**MOVING COIL EARPIECES.**

Comprise a 1 1/2in. Moving Coil Loudspeaker fitted with noise excluding rubber caps. Make excellent Mikee. Phones or Speakers, 2/- each, 18/- doz.

**GOVERNMENT SURPLUS MAINS TRANSFORMERS.**

All are for use on 230 volt 50 cycle Mains.


Type	Price
42 500-0-500 v. 170 mA. 4 v. 4 a.	25/-
44 10 v. 5 a., 10 v. 5 a., 10 v. 5 a.	35/-
53 250-0-250 v. 60 mA., 5 v. 2 a., 6.3 v. 2-3 a.	15/-
54 275-0-275 v. 60 mA., 5 v. 2 a., 6.3 v. 2-3 a.	15/-
55 250-0-250 v. 100 mA., 5 v. 2 a., 6.3 v. 3-5 a.	17/6

**SUPER MOVING COIL MIKE AND STAND.** We have purchased the entire stock of a famous Manufacturer of PA Equipment at a very low price, and are offering a £5/5/- Super Moving Coil Mike, with a chromium plated folding stand to match. The list price of the stand was £3/3/-.

**WE OFFER THE PAIR AT 79/6. LESS THAN HALF THE USUAL PRICE.**

**THERE ARE THOUSANDS OF RADIO AND TELEVISION BARGAINS IN THE PREMIER CATALOGUE 3d.**

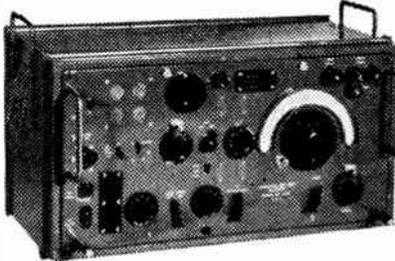**R107. ONE OF THE ARMY'S FINEST COMMUNICATIONS RECEIVERS. (See "W.W." August, 1945.)**



9 valves. R.F. amp. osc. Frequency Changer, 2 I.F.'s. (465 kc.), 2nd Detector, A.V.C. Af. amp. B.F.O. A.C. mains, 100-250 v. or 12 v. accum. Frequency range 17.5 to 7 mcs., 7.35 mcs. to 2.9 mcs., 3.0 to 1.2 mcs. Monitor L.S. built in. Complete. Write for full details. Price £12/12/-, plus 21/- carriage and packing.



**PREMIER MIDGET RADIO KIT.** Due to greatly increased production we are now able to offer this Kit at a greatly reduced price. Including an attractive Bakelite case, 12in. long x 5in. wide x 6in. high. The valve line up is 6K7, 6J7, 6V6 and a Selenium Rectifier in the A.C. model; and 6K7, 6J7, 25A6 and Selenium Rectifier in the A.C./D.C. model. Both are for use on 200 to 250 volt mains. The dial is illuminated, and the receiver presents a very attractive appearance. Coverage is for the medium and long wavebands. Complete kit of parts with cabinet and diagrams. £24/19/6, inc. Purchase Tax.

**PREMIER MIDGET SUPERHET KIT.** This powerful Midget Superhet Receiver is designed to cover the short-wave bands between 16 and 50 metres and the medium wavebands between 200 and 557 metres. Two models are produced, one for 200-250 volt A.C. mains, and the other for 200-250 volts A.C. or D.C. mains. Both are supplied with the same plastic cabinet as the TRF Receiver. The A.C. valve line-up is 6K8, 6K7, 6Q7, 6V6 and a selenium rectifier. The A.O./D.C. line-up is the same, with the exception of the output valve which is a 25A6. The dial is illuminated, making a very attractive receiver. Complete kit of parts with cabinet and diagrams. £26/19/6, inc. Purchase Tax.

**PLASTIC CABINETS,** as illustrated above. In Brown, 17/6. In Ivory, 22/6.

**METER KIT.**

**A FERRANTI 500 MICROAMP M/C METER,** with separate High Stability, High Accuracy, Resistors to measure, 15, 60, 150 and 600 volts D.C. Scale length 1 1/2in., diameter 2 1/2in. 10/- the complete kit.

**SECTIONAL WHIP AERIAL.** Seven sections which plug into each other making an aerial 14ft. long. Thinnest section 1/8in. diam., thickest section 1/2in. diam. Weather proof enamel. 3/6 each complete.

**INSULATED BASE** for above, 2/6 each.

Full Scale Deflection		Scale Marking	Scale Length	Movemen	Price
1 mA.	0-100	2 1/2in.	M/C D.C.	15/11	
1 mA.	0-1	2in.	M/C D.C.	7/6	
5 mA.	0-5	2in.	M/C D.C.	5/-	
50 mA.	0-50	2in.	M/C D.C.	10/6	
50 mA.	0-50	2in.	M/C D.C.	8/6	
150 mA.	0-150	2in.	M/C D.C.	6/-	
200 mA.	0-200	2 1/2in.	M/C D.C.	8/6	
2.5 Amp.	0-2.5	2in.	Thermo	5/-	
3 Amp.	0-3	1 1/2in.	Thermo	5/-	
3.5 Amp.	0-3.5	1 1/2in.	Thermo	5/-	
20 Amp.	0-20	2in.	M/C D.C.	7/6	
25 Amp.	0-25	2 1/2in.	M/C D.C.	£11	
40 Amp.	0-40	2in.	M/C D.C.	7/6	
20 v.	0-20	2in.	M/C D.C.	5/9	
40 v.	0-40	2in.	M/C D.C.	5/9	
200 v.	0-200	1 1/2in.	M/C D.C.	10/-	
5,000 v.	0-5,000	3 1/2in.	Elect	50/-	
500 u.a.	0-15 0-600	2 1/2in.	M/C D.C.	5/-	
500 u.a.	0-500	2in.	M/C D.C.	7/6	
500 u.a.	0-500	2 1/2in.	M/C D.C.	19/6	

**NEW 2-VOLT ALL WAVE KIT.** 16 to 2,000 metres. Switched Coil Pack ready wired and tested. 2 Mazda H123 Valves, 'Phones, H.T. and L.T. Batteries, Condensers, resistors, diagrams and steel case, all ready to assemble, £3/10/- including Purchase Tax.

**207, EDGWARE ROAD, W.2** Phone: AMBassador 4033 **BRANCHES AND AT —**

All POST ORDERS to 167, LOWER CLAPTON ROAD, LONDON, E.5. 'Phone: AMHerst 4723

Terms of Business: Cash with order or C.O.D. over £1. Send 2d. stamp for list.

**EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS**

# PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

You can build a commercial looking and working

## TELEVISOR WITH PREMIER KITS FOR

### £17.17.0

This Receiver consists of 4 units:

The Sound Receiver, Vision Receiver, Time Base and Power Pack. As is usual in all Premier Kits, every single item down to the last bolt and nut is supplied. All chassis are punched and layout diagrams and theoretical circuits are included.

The cost of the Kits of Parts is as follows:

VISION RECEIVER with valves, £3/13/6.  
Carriage 2/6.

SOUND RECEIVER with valves, £2/14/6.  
Carriage 2/6.

TIME BASE with valves, £2/7/6.  
Carriage 2/6.

POWER SUPPLY UNIT with valves, £6/3/-.  
Carriage 5/-.

#### THE TUBE ASSEMBLY UNIT.

Which contains the VCR97 Cathode Ray Tube and Socket, 6in. P.M. M.C. Loudspeaker with closed field for televisors, Tube Mountings, etc. £2/18/6. Carriage and packing 2/6.



A well-made pedestal cabinet in walnut is available at £5/10/- plus 10/- packing and carriage.

The Instruction Book costs 2/6, but is credited if a Kit for the Complete Televisor is Purchased.

Any of these Kits may be purchased separately; in fact any single part can be supplied. A complete priced list of all parts will be found in the Instruction Book.

20 valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver is a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

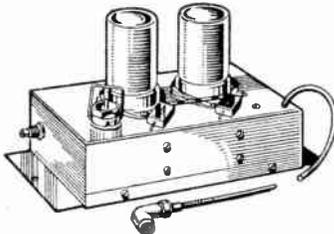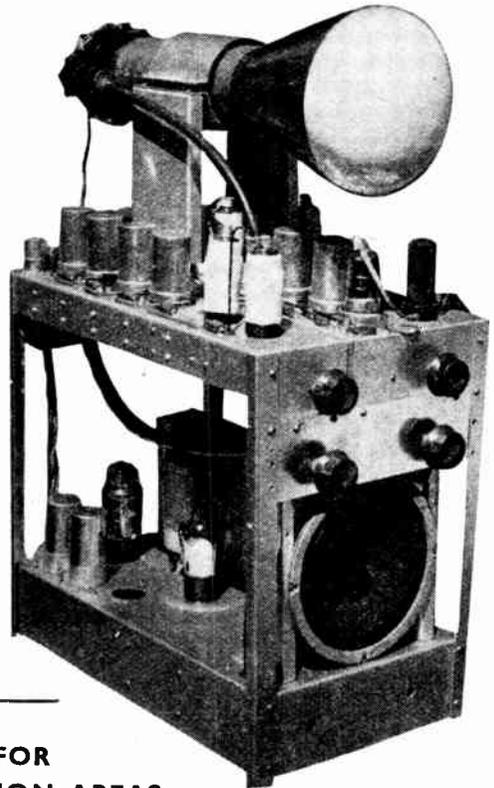Those wishing to build the MIDLAND version of this Televisor can obtain the complete kit with the exception of the coils and rejectors from stock. These will be available a few days after the commencement of full power transmission. The Coils and Rejectors are included in the price of £17/17/-.



#### PRE-AMPLIFIER FOR FRINGE RECEPTION AREAS

We can supply the complete kit of parts to make this wide band width Pre-Amplifier, using 2 EF54 Pentodes. Powered by the TV Kit, it is completely screened. With all parts, valves, chassis, diagrams, etc., 27/6. All parts available separately.

WORKING MODELS CAN BE SEEN DURING TRANSMITTING HOURS AT OUR FLEET ST. & EDGWARE RD. BRANCHES

AT  
-152-153, FLEET STREET, E.C.4 Phone: CENTral 2833

All POST ORDERS to 167, LOWER CLAPTON ROAD, LONDON, E.5. Phone: AMHerst 4723

Terms of Business: Cash with order or C.O.D. ove. £1. Send 21. stamp for list.


EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS



**NOW AVAILABLE FOR  
IMMEDIATE DELIVERY  
A REALLY VERSATILE  
WIRE RECORDER**

- ★ Completely self contained and portable with storage for microphone and leads. Weight 40lbs.
- ★ Records for one hour at one loading from microphone, gram or radio.
- ★ Uses large capstan and flywheel to reduce "wow" to a minimum. Rewinds at  $6\frac{1}{2}$  times forward speed.
- ★ Push button controlled for ease of operation.

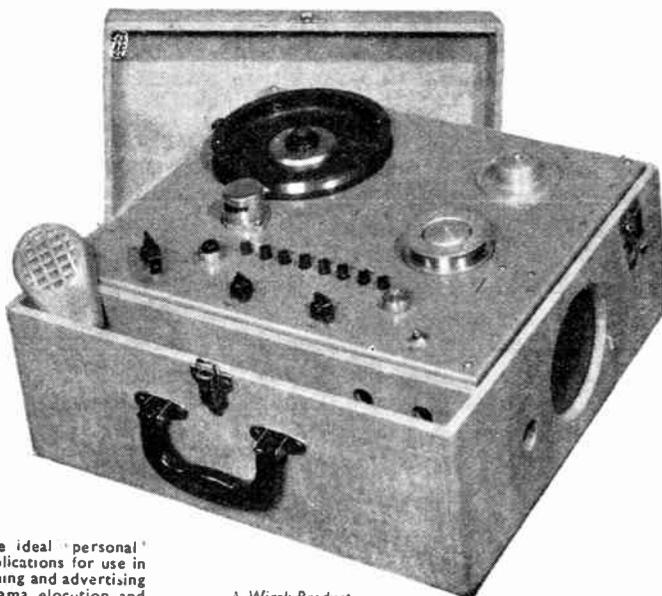This up-to-date instrument in its neat carrying case is the ideal 'personal' recorder for home or business use. It possesses unlimited applications for use in offices, universities and schools, hospitals and clinics, sales training and advertising departments and for professional artists and students of drama, elocution and music.



*A Wirek Product*


FOR DETAILS OF THIS UNIT AND OUR COMPREHENSIVE RANGE OF RECORDING EQUIPMENT AND ACCESSORIES PLEASE WRITE TO:—

**SIMON SOUND SERVICE, Recorder House, 48/50, George St., Portman Square, London, W.1.**

CABLE : *Simsale London.*

TELEGRAMS: *Simsale. Wesdo. London.*

TELEPHONE: *Welbeck 2371 (4 lines)*

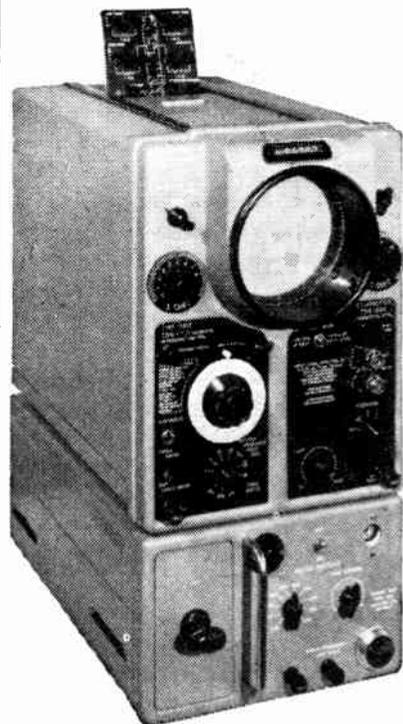

## A CALIBRATED WIDE RANGE OSCILLOSCOPE

with SIMPLE CONTROLS—LARGE SCREEN and the MEASURING FACILITIES OF A VALVE VOLTMETER

### THE NAGARD TYPE 103

**TIME BASES UP TO 1 Mc/s**  
with frequency and time measurement to an accuracy of 2%.

**VOLTAGE MEASUREMENT**  
10mV to 1,000V.

**D.C. AMPLIFIERS**

Zero frequency to 2.5 Mc/s at 1 cm mV R.M.S.

Zero frequency to 10 Mc/s at 1 mm/mV R.M.S.

AUTOMATIC SYNCHRONISATION

*Fully detailed information on request from:*

# **NAGARD** LTD

245, BRIXTON ROAD, LONDON, S.W.9

Phone: **BRIXTON 3550**

# \* Perfect Reproduction?

## THE LOUSPEAKER AND ITS ASSOCIATED POWER AMPLIFYING STAGE

We now come to the last and most important link in the chain of reproduction—the loudspeaker and its associated power amplifying stage. They cannot be considered separately since the amount of electrical power required obviously depends upon the efficiency of the loudspeaker itself. In fact, all one need say about the output stage is that it must be capable of giving an output of about 10 times that of normal listening level if it is to handle peaks of modulation. For good quality it is essential that the harmonic distortion and—more important, the intermodulation products shall be kept low even at full output.

There are no inherent difficulties in achieving this result though it is bound to be somewhat costly. For average loudspeakers a power of at least 15 watts will be required and to handle this without distortion involves a large output transformer and an expensive power supply.

When we come to the loudspeaker itself we are assailed by enormous difficulties, many of which are, as yet, unsolved. If we ask of our loudspeaker—as we academically should—that it shall provide a pressure distribution which is a faithful copy of the power applied to it; that it should do this over a range of frequencies from 30 c.p.s. to at least 15,000 c.p.s.; that it should add nothing of its own character, either by harmonic distortion or ringing to the desired reproduction, then we have to admit that we are nowhere in sight of this desirable end. In fact, it is only the coarseness of the ear as a measuring instrument which allows one to feel that present day reproduction can be extraordinarily good.

The magnitude of the problem can easily be seen by a brief examination of the two ends of the frequency scale. In the deep bass from 50 c.p.s. downwards we need a vibrator of very large area mounted in a truly gigantic baffle or cabinet to produce adequate sound. In the high frequencies, we require a tiny radiator to which must be added some diffusing mechanism if the radiation is to be spread over a wide angle. If

we could proceed regardless of cost, good results could be achieved from a series of loudspeakers, each carefully designed to cover a relatively narrow band of frequencies, the whole lot being fed from a suitable power dividing net work so that each loudspeaker is excited from handling those frequencies for which it is not adapted. The design of all the speakers would be controlled by one general principle, i.e. that its diaphragm size shall be small enough for it to behave as a piston over the range of frequencies which it is to produce.

The really remarkable thing is that almost any type of paper cone loudspeaker tends to produce the sort of response that we require for the following reason. Let us examine the behaviour of a paper cone, say, 8 in. in diameter when it is driven by the apex at frequencies from 50 cycles upwards. At the low frequencies the whole cone will move as one piece, provided, of course, that a suitable flexible surround is used. But it is easy to see that at some higher frequency the outer edge of the cone will fail to follow the movement of the centre—because, in fact, the frequency is so high that there is no time for the force applied at the centre to spread to the edge of the cone before the reversion of motion has started at the centre. In other words, the velocity of a sound wave in the cone material is too low.

As the applied frequency is increased still further a smaller and smaller portion of the cone faithfully follows the applied power whilst the annular area outside behaves in an almost unpredictable manner. If we could assume that this annular area remained at rest, then a plain paper cone loudspeaker would, to a first approximation, give a similar answer to a large number of separate loudspeakers of decreasing size, each fed from a frequency selective net work.

Unfortunately, the outer parts of a cone do not remain at rest. They continue to vibrate in various ways, sometimes in phase and sometimes in antiphase with the central portion so that the pressure measured at a distance from the loudspeaker is a resultant of a number of different movements. It is this that causes the response curve of a normal loudspeaker to be covered with peaks and troughs. Worse still, the rebellious parts of the cone which are failing to follow the central directive will continue to move if the applied force is suddenly removed; for a short while they will “ring” at their own natural frequency. Methods have been developed over the past few years of measuring the behaviour of loudspeakers by the application of transient inputs. A great deal can be learnt from the shape of the resultant pressure wave after the input has been removed.

It will be readily seen that the application of mathematics to such a complicated mechanical system as a paper cone is not likely to give useful results.

Loudspeaker development of this type calls for enormous numbers of painstaking experiments with different cone materials, different thicknesses, different shapes of cone, different surrounds—and hosts of other small details, each of which may be vitally important. By years of experience, certain broad generalisations can be found which reduce the almost infinite variety to more manageable proportions; even so the labour is immense.

Of course, there are some aspects of loudspeaker design which are more amenable. For example, if we confine our attention only to the centre portion of the cone and the driving coil, we can see that to avoid distortion the whole of the suspension must obey Hook's law over the largest excursions which are to be used. We must arrange that even at low bass frequencies the amplitude of movement of the cone does not produce non-linearity in the stress/strain relation of the surround and centre spider. Equally, the dimensions of the coil and the magnetic field must be chosen so that the average field strength through the coil shall be constant whatever the excursion. Some niceties in design are involved in securing this requirement for we may adopt several methods. The magnet gap may be made long, ensuring that the whole coil always operates in a uniform field, or the gap may be short so that the coil embraces the whole field, however far it moves. Both these methods are relatively easy but are uneconomic and inefficient and it is more usual for the coil length and distribution of the magnetic field to be chosen so that as one part of the coil moves out into a weaker field, another part compensates by moving into a stronger field.

From what has been said so far, it might be thought that we have only been considering normal moving coil loudspeakers such as are usually found in radio sets. Actually, this is not intended since the same fundamental considerations apply in all cases. It matters not what method of driving is chosen though a change of method will usually ease some parts of the problem and make others more severe.

We in Murphy Radio have spent an enormous amount of our research time on the problem of reproduction, and if we are honest, we must admit that the more we learn about it the more far off the final goal appears to be. We do, however, find great comfort when we come to compare the reproduction of today with what it was a few years ago. Although we are more dissatisfied now than we were then, it is quite obvious that our present standards are higher than in the past.

**murphy radio  
limited**

WELWYN GARDEN CITY, HERTS

C.B.C. 10

### \* Problems referred to in previous notes.

- Spatial Distribution of Sound.
- Echoes in the Listening Room.
- Limitations of Single Channel.
- Limitations of the Human Ear.
- Distortions and Faults caused by Apparatus.
- The Radio Link.
- Frequency Response.
- Non-Linearity.
- The Signal Rectifier.
- The A.V.C. Rectifier.

# Webb's RADIO

## A Christmas suggestion

—MORE ACCEPTABLE THAN—

### PURPLE NECKTIES WITH YELLOW SPOTS

Why not hint gently to Aunt Maud that you'd prefer Webb's Radio Globe of the World 50/- carriage paid (or 47/6 to callers). A handsome adjunct to either the parlour or radio shack.

### EDDYSTONE '5/10 METRE CONVERTERS'

Originally listed at £14, we have a few to offer at reduced price. The Converter will allow experimental reception of 5 and 10 metre signals on your receiver, also

#### TELEVISION SOUND

(Midland and London Frequencies)

Tested and new, with valves and instructions, £6.10.0

(Descriptive leaflet free on request.)

### NEW 'Leak' MOVING COIL PICK-UP

Call and hear this outstanding addition to our large range of disc reproducing apparatus. Price with ruby stylus and transformer, £14.10.8.

### COMMUNICATIONS RECEIVERS

We advise our friends that all stocks of Eddystone '640' receivers are now sold. The new Eddystone '750,' price £45, will be available soon, details free on request. As regards the Eddystone '680,' price £85, the outstanding performance of this specialised receiver has resulted in Export orders taking the bulk of production, but WEBB'S usually have a demonstration model and orders are being booked for rotational delivery. Also we often have interesting second-hand bargains in receivers of U.S.A. and British origin—enquiries invited, though Webb's offers do not remain long unsold!

Webb's Radio, 14, Soho St., Oxford St., London, W.1.

Phone: GERrard 2089. Shop Hours: 9 a.m.—5.30 p.m. Sats. 9 a.m.—1 p.m.

## A NEW

# FIELDEN TECHNIQUE

*in micro - measurement  
and control*

FOR ANY INDUSTRIAL OR RESEARCH  
PROBLEM RESOLVABLE INTO MINUTE  
ELECTRICAL CAPACITANCE CHANGE


ACTUATION BY PROXIMITY of solid or  
liquid conductors or insulators to an electrode  
terminating a co-axial cable.



**THE FIELDEN PROXIMITY METER—SENSITIVITY 0.01 mmf**—indicates minute capacitance changes, whether caused by very small mechanical displacement or dielectric change. It measures, for instance, strains in structures, it gauges components to less than 0.00001 in., monitors sheet,

foil and wire sizes, measures liquid and other levels precisely, monitors dimensions and compositions, compares dielectric properties of non-conducting, liquids etc. It does what is impossible mechanically and, in many fields, surpasses all other micro-measurement methods.

### THE FIELDEN TEKTOR—SENSITIVITY

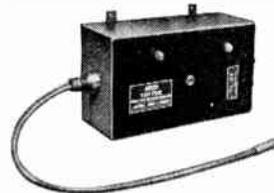

**0.25 mmf**—is a unique, stable, high-speed capacity relay which solves many problems of counting, temperature control, level control of liquids and solids, and so on where simple direct-switching is impossible.

Please send for specification FE/4 to the SPECIALISTS  
IN INDUSTRIAL ELECTRONIC EQUIPMENT

*Fielden*

**(ELECTRONICS) LIMITED**

HOLT TOWN - - - MANCHESTER

Telephone: ARDwick 2619.

# INSIDE INFORMATION

*about the switch that is superior*

We agree that there are cheaper 3 amp. toggle switches than the Cutler-Hammer types made by British N.S.F. — but there are none better. If super-reliability is the yardstick by which you choose a switch then this is the switch for you.

## NOTE THESE C-H FEATURES

- Self-aligning "wiping" moving contact.
- Spring-leaf fixed contacts.
- Long coil spring.
- One-piece moulded case.
- Welded terminal plates.
- Isolated toggle lever.
- Insulated terminal bridge.
- Quick make and break mechanism.

Nominal rating 3 amps, 250 volts—suitable for A.C. and D.C. service. Available in a wide range of single and double pole types operated by lever, plunger, slider or trigger, with screw or solder-lug terminals. Enquiries invited.

● Other British N.S.F. products include: 'Oak' Rotary, Push-button and Slider switches; Carbon and wire-wound potentiometers for Television and Radio applications; Paper Tubular Capacitors; Wire-wound resistors.



**BRITISH N.S.F. CO. LTD**  
**KEIGHLEY YORKS**

Phone: Keighley 4221/5. Grams: ENESEF, Keighley.

**LONDON OFFICE: 9 Stratford Place, W.1. Phone: Mayfair 4234.**

Licenses of Igranic Electric Co. Ltd. for the above products of Cutler-Hammer Inc. Milwaukee, U.S.A.

# Instruments of Precision



# PULLIN

*Precision-Built Electrical Measuring Instruments*



**MEASURING INSTRUMENTS (PULLIN) LTD**

ELECTRIN WORKS, WINCHESTER STREET, LONDON, W.3. Tel.: ACOm 4651/3 & 4995

## AUTOMATIC Choice!

The Collaro Automatic Microgram! . . . a portable electric gramophone comprising amplifier and automatic record changer, completely self-contained in one handsome carrying case.

Fitted with the new Collaro R.C. 500 Record Changer—a brilliant new 'Changer designed for reliability and extreme simplicity of operation—with crystal pickup, two-valve amplifier plus metal rectifier and 6½" speaker giving an undistorted output of 2-3 watts. All controls on the outside of the cabinet—and it's light enough to be instantly portable.



The Automatic Microgram

Retail Price  
£18.18.0  
Plus P.T.

# The COLLARO AUTOMATIC Microgram Portable Electric Gramophone


Trade enquiries to:—

**COLLARO LTD., RIPPLE WORKS, BY-PASS ROAD, BARKING, ESSEX**

Telephone: RIPPLEWAY 3333.

★ Ask your dealer to demonstrate the Collaro Automatic Microgram . . . and the Collaro "De Luxe" Microgram—the world's finest portable electric gramophone. Price £14. 14. 0d. plus P.T.

Telegrams: "KORLLARO, BARKING."

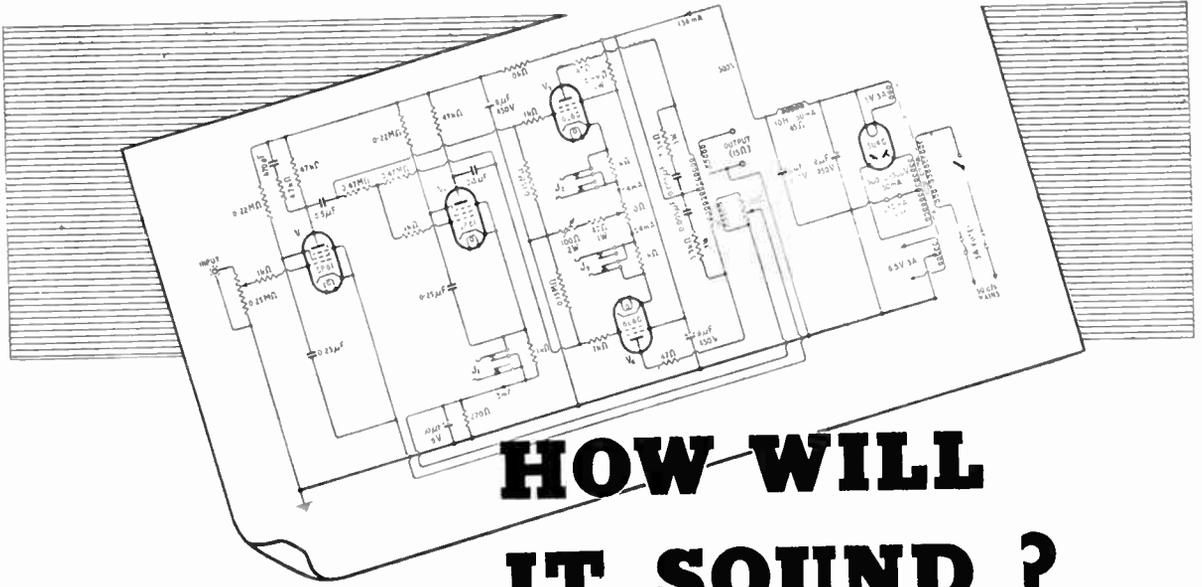


# HOW WILL IT SOUND ?

It may look O.K. on the blueprint, but the only thing that really matters is—how does it sound? Time and money are often spent by enthusiasts who

neglect the essential feature of all sound equipment—a high quality, reliable speaker—best of all, a VITAVOX. Consult us on your sound problems and remember—

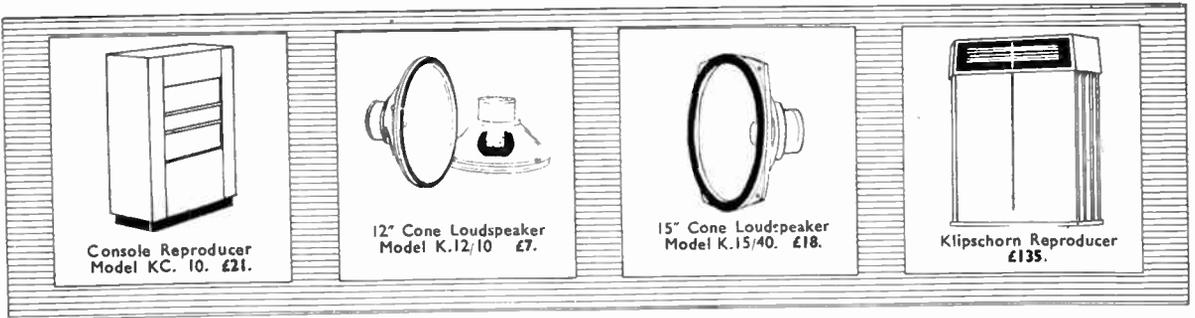**IT WILL SOUND BETTER THROUGH**  
**VITAVOX** **LOUDSPEAKERS**



Console Reproducer  
Model KC. 10. £21.

12" Cone Loudspeaker  
Model K.12/10 £7.

15" Cone Loudspeaker  
Model K.15/40. £18.

Klipschorn Reproducer  
£135.

*Fullest Information gladly sent on request*

## VITAVOX LIMITED

WESTMORELAND ROAD - LONDON - N. W. 9 - ENGLAND  
 Telephone: COLindale 8671/3      Telegrams: Vitavox, Hyde, London      Cables: Vitavox, London



## When Seeing is Believing

The man who says "I saw it with my own eyes" is simply endorsing the general conviction that seeing is believing. That is why you should insist on a demonstration with a Magnavista lens, for then you can see with your own eyes how greatly the image is enlarged, how brilliant the picture becomes, how wide an angle of view is secured, and seeing these things, you believe in the advantages of Magnavista viewing.

**PRICES**

Type	Tube	£	s.	d.
A.7 ... ..	6"	3	3	0
A.1, A.2, A.4, A.5, A.8, A.9, A.9a, A.10, A.11 and A.12 ... ..	9"	4	14	6
B.1, C.1 ... ..	10" & 12"	5	5	0
D.1 ... ..	15"	5	15	6
A.3 (Universal) ... ..	9"	6	16	6
B.2 (Universal) ... ..	10"	7	7	0
C.1x ... ..	12"	7	7	0

Subject to Trade Discount

MAGNAVISTA Magnification  
is Television Perfection

### METRO PEX LTD

Head Office:  
38, Gt. Portland St., London, W.1  
(\*Phone: Museum 9024-5)  
Midlands Depot:  
Kings Heath Stn., Birmingham, 14  
(\*Phone: Highbury 2765)

## T.P.R.I. COMPLETE PORTABLE RECORDER

EASIEST DISC RECORDER to operate.

NO EXPERT KNOWLEDGE REQUIRED.

PLUG IN AND RECORD

IMMEDIATELY, Speeches, Lectures, Meetings, Concerts and Special Radio Programmes.

The lightest and most compact Portable Disc Recorder including Amplifier, Speaker and high quality Microphone, in one Carrying Case, 14" x 15" x 10½". WEIGHT 37 lbs.



PRICE £85.0.0

ELECTRO SOUND SUPPLIES LTD.  
99, BELGRAVE ROAD, S.W.1

\*Phone: VIC 8814



As specified for conversion of the T.R.1196.

## OSMOR "Q" COILPACKS

No need to spend hours puzzling over coil and switching problems. Just 5 connections (1-hole fixing), and the job's done—quickly, efficiently and cheaply. Full-circuit layouts and instructions with every pre-aligned "Q" Coilpack. Portable Battery—Model now available.

Send stamp for free circuits and our new lists of coils, coil-packs and matched radio components, also "Bargain Bulletin."

OSMOR RADIO PRODUCTS LTD.

Dept. W.1.

BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON SURREY.

Telephone: Croydon 1220

# THE OSRAM MINIATURES are becoming more popular every day . . .



**OSRAM BATTERY  
MINIATURES "17" RANGE**  
Left to Right: The X.17 Frequency  
Changer; W.17 Vari-Mu H. F. Pentode;  
ZD.17 Diode Pentode; N.17 Output Pentode

## and here's why

These valves, now extensively used by set manufacturers, have been specially designed with a view to H.T. current economy. The filaments, intended primarily to operate from a dry cell, maintain adequate emission during the whole useful life of the cell. Mounted on the popular B7G miniature base, they are compact and extremely robust. Ideal for battery operation in portable equipment such as personal receivers.

# Osram

V A L V E S



THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2



Send for your copies to Dept. W. W. 12

WESTINGHOUSE ERAKE & SIGNAL CO., LTD., 82, YORK WAY, KING'S CROSS, LONDON, N.1

Why you should use...



- 1 Maximum "Wetting" Capacity.
- 2 Accelerated Fluidity.
- 3 Moderate soldering bit temperatures.
- 4 Mechanical bonding and perfect Electrical conductivity ensured.
- 5 Minimum amount of solder used per joint.
- 6 Residue sets hard, is non-corrosive, and of high dielectric strength.
- 7 No harmful fume deposits.
- 8 Continuous, unvarying core.
- 9 Even distribution of activator in core.
- 10 Approved by Air Ministry and General Post Office.

Supplied in a wide range of Gauges and Alloys on 1 lb and 7 lb reels, works coils, or as required. Prices on application.

Sole Manufacturers :

**H. J. Enthoven & Sons, Ltd.**

89, UPPER THAMES STREET, LONDON, E.C.4.  
Phone: Mansion House 4833. Works: Rotherhithe, Croydon, Derbyshire.

FOR QUICK DELIVERY  
AT  
REASONABLE PRICES  
OF  
RADIO & ELECTRONIC PRODUCTS  
(Wholesale Only)

Write or phone:—

**S. Szymanski**  
(pronounced SHE-MAN-SKEE)

ELECTRONIC ENGINEER & STOCKIST  
95 STRODES CRESCENT  
STAINES, MIDDLESEX  
Staines 3971

VALVES are our speciality—Probably the  
Largest Actual Stockist in England

EXPORT ENQUIRIES WELCOMED

First of an occasional series from Charles Amplifiers (Sales) Ltd.

## Facts On Figures

A fairly recent trend in High-Fidelity Reproduction has been the insistence on very low distortion figures. The general expression we use with both our "Concerto" and the "K.I." amplifiers is "Distortion below  $\frac{1}{2}$  per cent." although our production test figure averages 0.15 per cent. The reason for this figure is simple. It is extremely doubtful whether 1 per cent. of 2nd-harmonic distortion is ever audible with normal equipment. Cross-modulation occurring in the amplifier, the speaker (including its chamber or other mounting) and in the pickup is much more important and much research is still needed in this field.

There is really little doubt that any high-fidelity amplifier worthy of its name has inaudible distortion—and so far as harmonic distortion is concerned that is almost all that need be said. Except for one important point: our distortion figure holds good at all settings of the tone controls, and this is particularly significant if treble boost is required.


Furthermore, we have found time and time again that the choice of the type of tone control is most important. The enormous popularity of the "Concerto" is certainly due in part to the fact that it has two networks of bass boost; their effect can not only be seen on a meter, but the improvement is obvious on first listening. This is specially noticeable on recorded organ music and it may be for this reason that the "Concerto" was used by Mr. Alan Douglas when he gave a lecture at the Royal Academy of Music and demonstrated records of electronic organs.

Our range of equipment consists of amplifiers, speaker chambers and an excellent tuning unit which has just been redesigned and reduced in price. The units are all designed with an

eye on the users' requirements and our catalogue makes interesting reading. May we send you a copy?

Since Radiolympia we have been rather overwhelmed with enquiries and we have opened new offices for enquiries and demonstrations at the address shown below. Trade and export enquiries should be addressed to Charles Amplifiers Ltd., 1e, Palace Gate, London, W.8.

### The CONCERTO Amplifier

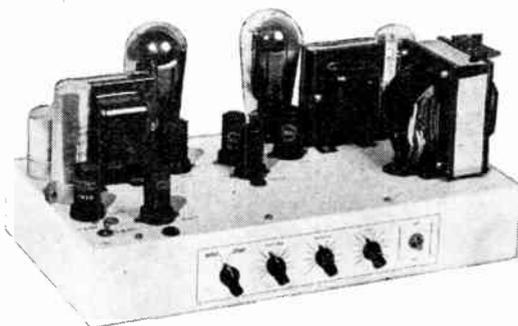

... acclaimed by music lovers for its exceptionally high fidelity, this magnificent amplifier covers all normal requirements for home or concert hall. Distortion level below 0.5 per cent. *Two channels* of bass boost ensure unusually smooth balance and depth. Designed for any type of pickup. Radio input socket provided. Two year guarantee. Price £27.10.0. Heavy perforated steel cover with bottom plate and rubber feet, 45/- extra. Delivery by passenger train, Carriage Paid. 10/- deposit (returnable) for crate.

Deferred terms now available.

Our Equipment is used abroad  
in:—

ARABIA	MALAYA
ARGENTINE	NIGERIA
AUSTRALIA	N. RHODESIA
EIRE	PAKISTAN
GERMANY	SUDAN
HONG KONG	TANGANYIKA
INDIA	U.S.A.

*Charles*  
**AMPLIFIERS**  
(SALES) LTD.

181c KENSINGTON HIGH STREET,  
LONDON, W.8. Phone: WESTern 3350.


Our products can also be seen and  
heard at:—

WEBB'S RADIO,  
SOHO STREET, LONDON, W.1  
UNIVERSITY RECORDING CO.,  
16 BURLEIGH PLACE, CAMBRIDGE  
also  
ERNEST BUCHAN,  
28 BELMONT STREET, ABERDEEN

EDX.22G



The best  
**HIGH**  
and  
**LOW**

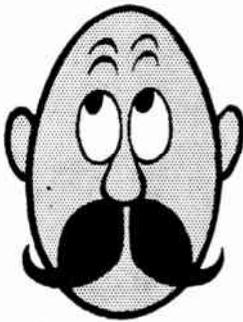


**Exide** AND **Drydex**

LOW TENSION ACCUMULATORS      HIGH TENSION BATTERIES  
for better battery radio reception

ISSUED BY THE CHLORIDE ELECTRICAL  
STORAGE COMPANY LIMITED
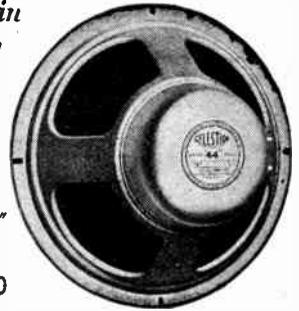
# CELESTION

The Foremost Name in  
Sound Reproduction



## MODEL P44.

- Overall Diameter 12- $\frac{3}{8}$ "
- Voice Coil Impedance  
ohms 3.0
- Magnet Pole Diameter 1 $\frac{1}{2}$ "
- Flux Density (Gauss) 10,000
- Total Gap Flux (Maxwells)  
60,000
- Peak Power Capacity 10W

The General Public should  
please order through their  
Local Dealers.

Manufacturers are invited  
to write for details of the  
full range of Celestion  
speakers.

**CELESTION LTD.** SUMMER ROAD,  
THAMES DITTON, SURREY

Telephone: EMBERBROOK 3402-5

## M.R. SUPPLIES Ltd.

for exclusive and completely reliable material. All prices nett.

**RECTIFIER UNITS.** For E.H.T., H.T., and L.T. (D.C.) supply. Unit "A" (E.H.T.), input 200/250 v. (10 v. taps) 50 c. 1 ph., output fully choke/capacity smoothed, 1,200 volts D.C. 200 mA. at 50 deg. C. ambient. In ventilated steel housing 19 in. by 18 in. by 9 in., approx. weight 60 lb., £7/10/- Unit "B" (H.T. and L.T.) input 200/250 v. (10 v. taps) 50 c. 1 ph. outputs 6.3 v. D.C. 13 amps and 220 v. D.C. 110 mA., both choke/capacity smoothed. In ventilated steel housing 19 in. by 18 in. by 12 in., approx. weight 60 lb., £8/10/-, or the pair for £15. These are new, slightly store soiled, in perfect electrical order. Prices are ex this address.

**E.H.T. TRANSFORMERS.** Primary 100/250 v. 50 c. 1 ph. (in 10 v. taps), secondary 2000/2000 v. (4,000 v. C.T.) 400 mA. (50 deg. C.), size 10 in. cube, enclosed with top terminal panel. Weight approx. 50 lb., £4/10/- (despatch 7/6).

**VOLTAGE CHANGING TRANSFORMERS (Portable).** 100, 110 v./200, 220, 240 v. (and vice versa) auto-wound, loading 1.25 kVA., in steel cabinet 9 in. by 8 in. by 6 in., with carrying handle. Just right for mobile cine work. Brand new, £4/15/- (despatch 5/-).

**ROTARY CONVERTERS (new)** Input 110 v. D.C., output 230 v. 50 c. 1 ph., 100-watts, under half current price, £5/17/6 (despatch 5/-).

**ELECTRIC BLOWERS.** For electronic and lamp cooling, air conditioning, drying, etc., 24 v. A.C./D.C., 6000 r.p.m., reasonably quiet in running. Small, efficient model, 5 in. by 3 in. overall, brand new in cartons, 18/6 (despatch 1/-).

**MINIATURE MICRO-AMMETERS.** 0/500 micro-amps, m/coil, only 1 1/4 in. dia., single hole mount, back terminals, new, boxed, 10/6 (despatch 6d.).

**MILLIAMMETERS.** Very special offer to clear overstocks. Brand new, m/coil 0/20 mA., 2 1/4 in. proj. panel, with back terminals, 5/- Here is a real opportunity which this announcement will clear. Also some 6 in. s/board meters, 0/30 volts (calibrated at 800 c. but suitable for 50 c.). First grade jewelled movement, to clear, 15/- each (despatch 1/6).

**F.H.P. MOTORS.** 200/250 v. A.C. Brand new shaded pole type, suitable for stirrers, tape recorders, cine projectors, etc., running torque 400 gram/Cms, 1200 r.p.m. Double-ended shaft, frame 3 in. by 3 in., ventilated enclosed, 29/6 (despatch 1/-).

**OPERATION COUNTERS.** (Mechanical). To 99,999, 7/6. **FOOTSWITCHES.** 1 make and 1 break when depressed, 15 amps, mains voltage, 6/- **THERMOSTATIC SWITCHES** (ex A.M.). On at 32 deg. F., off at 49 deg. F. (adjustable) capacity 1.5 amp mains voltage, 4/6 **THERMAL DELAY SWITCHES.** (Various) 4-volt, 4/6 **TUMBLER SWITCHES (Crabtree)** 2-pole, 15-amp., plated, 4/6 **MERCURY SWITCHES**, lined, 6/10 amps, with beaded leads, new 7/6. **HIGH-SPEED KEYING RELAYS** (Siemens—ZA 3193) Twin-coil, 2,000 ohms, new, 7/6. **P.O. RELAYS.** 2,000 ohms, 1 m. and 1 b., new, 4/6.

**STAGE LIGHTING DIMMERS.** Full-bright to blackout at stated load at 220/240 v. Sliding type, 100-watt, 32/6, 200-watt, 37/6, 500-watt, 50/- (despatch 2/-). Screw motion, with handwheel, 1,000-watt, £8/3/-, 2,500-watt, £9/5/- (despatch 5/-). All fully protected.

**SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS.** Ready for use with chromium bands (hrs. mins. sec.) to suit 5/7 in. clock, 200/250 v. 50 c. Size 3 1/4 in. dia., 2 in. deep, silent running, 37/- (despatch 9d.).

**ELECTRIC PUMPS.** The reliable Stuart range from stock. 220 250 v. 50 c. No. 10 (120 g.p.h.), £5 15/- (despatch 1/6). No. 12 (600 g.p.h.), £8/10/- (despatch 3/6). Larger models and Piston Pumps also available from stock. Details on request.

**HIGH DUTY BRONZE PUMPS** (ex-Admiralty), brand new. Power required to drive 1 h.p. Vane-type impeller, approx. 2,000 g.p.h., £8/10/- (despatch 4/6). (Illustrated lists of Pumps, Clock Movements, Variable Resistances and Dimmers, Transformers, etc. Please send stamp.

**M. R. SUPPLIES Ltd., 68, New Oxford Street, London, W.C.**  
Telephone: MUScum 2958




## men talk —

*said Desoutter's Little Horse —*  
of More productivity per *Man*.  
But who does the extra work?  
Horses of courses. Man with-  
out horsepower is but an ass.  
Can Man drive a screw at 3000  
r.p.m.? Or bite through duralu-  
min at 12 ft. per minute? If  
Man wants greater produc-  
tivity—to drill ten holes where  
he drilled one, to run ten nuts  
where he was slowly winding  
one—let him

## call up the little horses
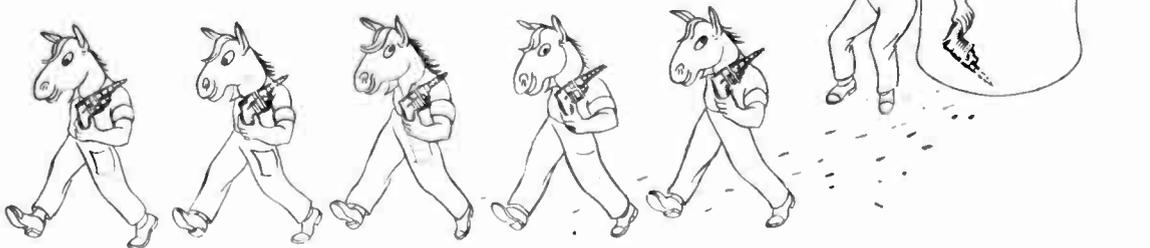
# DESOUTTER

*Specialists in Lightweight Pneumatic  
and Electric Portable Tools*



DESOUTTER BROS. LTD., THE HYDE, HENDON, LONDON, N.W.9. TELEPHONE: COLINDALE 6346-7-8-9. TELEGRAMS: DESPNUCO, HYDE, LONDON

CRC 206

# Are you building the 'VIEW MASTER'

— the Television Set you can build  
at home from standard parts

Here for the first time is a Constructor Envelope which by means of 8 full size drawings gives the clearest and most detailed stage-by-stage instructions for building a Television Receiver of the very latest type. Failure is impossible. The accompanying 32-page booklet not only explains how the set works and gives a complete breakdown of the circuit, but also includes a most lucid explanation of the whole principle of Television.

You can build the "View Master" with complete confidence, knowing that it has been designed by W. I. Flack, Fellow of the Television Society, and sponsored by nine\* of the leading British component makers. Two Models of the "View Master" are available: Model A for London area, Model B, (published early Dec.), for Sutton Coldfield area.

Constructor Envelopes price 5/- now on sale at your local Wireless Shops or direct (5/6 post free) from "View Master", 10, Norfolk Street, London, W.C.2.

\* Belling & Lee, Bulgin, Colvern, Morganite Resistors, Plessey, T.C.C., Wearite, Westinghouse, Whiteley Electrical.



- Uses 12" or 9" C.R. Tube.
- 12 Valves only.
- Magnetic Focussing.
- Metal Rectification throughout.
- Automatic Interference Suppression.
- Easily aligned without instruments.



BROWN—E.R.D. 13 inch Portable Disc Recorder  
An important S. G. Brown product

## Brown-E.R.D.

### DISC RECORDER

Incorporating the latest advances  
in Sound-on-Disc Recording

Write for interesting brochures presenting full technical details of this latest development in Sound-on-Disc recording. Also 17 inch models for the Professional user.

**S. G. BROWN LTD., Shakespeare St., WATFORD**

Established in Electro Acoustics and high precision Engineering for over 40 years. Manufacturers of the world-famous BROWN' Gyro Compass.

Telephone : Watford 7241

## High Fidelity Reproduction.



TYPE "K."

The S. G. Brown Type "K" Moving Coil headphones, with the following outstanding characteristics, supply that High Fidelity Reproduction demanded for DX work, monitoring and laboratory purposes, etc.

#### CHARACTERISTICS.

D.C. RESISTANCE, 47 Ohms.

IMPEDANCE 52 Ohms. at 1,000 c.p.s.

SENSITIVITY,  $1.2 \times 10^{-11}$  Watts at 1kc. —  $0.002 \text{ Dyn/cm}^2$

Descriptive Literature on request

PRICE £5.5.0 PER PAIR

Your Local Dealer can supply

For details of other S. G. Brown Headphones (prices from 30/- to 77/6) write for illustrated Brochure "W.W."

HEADPHONES WHICH UPHOLD BRITISH PRESTIGE

Telephone :  
Watford 7241

## S. G. Brown, Ltd.

SHAKESPEARE STREET, WATFORD, HERTS.

# NATIONAL PHYSICAL LABORATORY REPORT

On tests of 12 watt amplifier  
marked: "POINT ONE", TL/12, H. J. LEAK & CO. LTD.

Ref. E.388.150. Aug. 30th., 1949

**Test Conditions.** In all cases the input was applied to a 50 000Ω resistor connected to the amplifier by 3 feet of screened cable. The output load was in all cases a resistor of 18Ω and the output transformer secondary windings were connected for the "15Ω — 20Ω" condition.

**HARMONIC DISTORTION.**

0.03% for 10 watts output at 1,000 c/s.  
0.1% for 10 watts output at 60 c/s.  
2nd and 3rd harmonics predominated, and were approximately equal in magnitude.

**HUM AND NOISE.**

— 60 db. referred to 10 watts.

**SENSITIVITY.**

148 mV.r.m.s. input gave 12 watts output at 1000 c/s.

**LOAD DAMPING FACTOR.** (Load impedance/output impedance)

42 for 10 watts output at 1,000 c/s. (Output impedance 0.43Ω).  
45 for 2.5 watts output at 1,000 c/s. (Output impedance 0.43Ω).  
The output impedance was found to be substantially resistive.


**FREQUENCY RESPONSE.**

Gain relative to that at 1,000 c/s. measured at 7.5 watts output, including the losses introduced at the higher frequencies by the capacitance of the input cable shunting the input resistance of 50,000Ω.

c/s.	db.
20	+0.1
60—1,000	0
5,000	-0.1
10,000	-0.3
15,000	-0.4
20,000	-0.7

WRITE FOR BOOKLET W/TL/12 which explains how these amazing results are achieved.

THE  
**LEAK**  
DYNAMIC PICK-UP

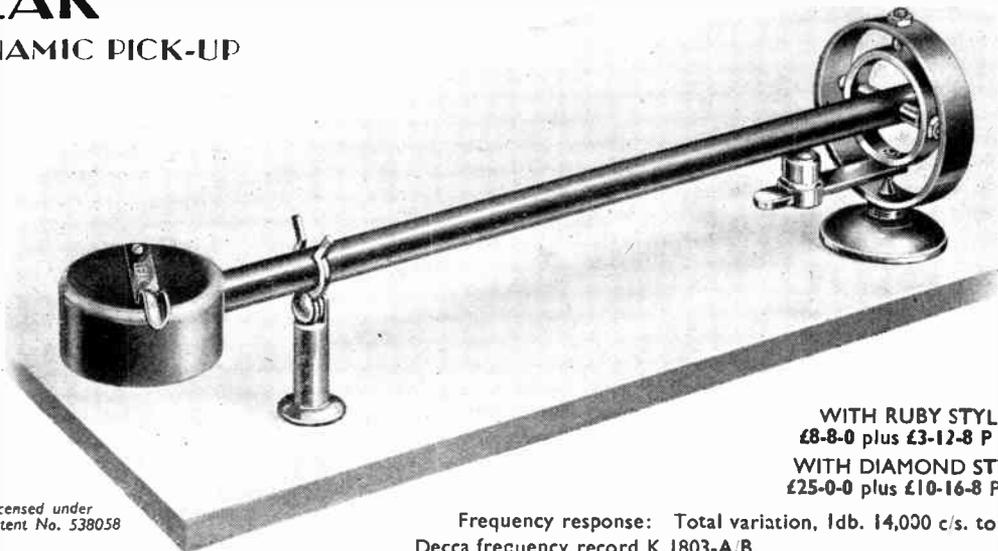

Licensed under  
Patent No. 538058

WITH RUBY STYLUS  
£8-8-0 plus £3-12-8 P. TAX  
WITH DIAMOND STYLUS  
£25-0-0 plus £10-16-8 P. TAX

Frequency response: Total variation, 1db. 14,000 c/s. to 40 c/s. from Decca frequency record K.1803-A/B.

In mechanical detail and electrical performance the LEAK DYNAMIC PICK-UP is as far ahead of other pick-ups as the LEAK "POINT ONE" TL 12 AMPLIFIER is ahead of other amplifiers.

WRITE FOR LEAFLET W/P.

**BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3**

Phone: SHEpherds Bush 5626.

Telegrams: Sinusoidal, Ealux, London.


Foreign: Sinusoidal, London


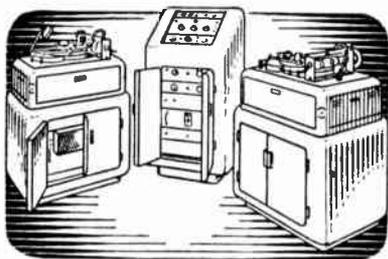
## DIRECT RECORDING ON DISK

**T**HE year 1930 marked a vital point in sound recording progress. It was then that Mr. C. E. Watts, founder of the M.S.S. Recording Co. Ltd., produced the first cellulose lacquer-coated disk—an achievement which paved the way to—indeed made possible—to-day's high-fidelity sound reproduction. That same pioneering spirit, consistently prompting every endeavour of the M.S.S. organisation, has produced a range of sound recording equipment which is acknowledged supreme wherever there is an appreciation of true fidelity in sound reproduction. Apart from its "quality" performance, every item of M.S.S. equipment—whether a complete recording channel or a cutter head—is built to a standard of technical excellence which assures long-maintained efficiency under the most exacting operating conditions. In this connection it is interesting to mention that the first disk recorder used by the B.B.C. for broadcast programmes and supplied by M.S.S. in 1933, is still in use in their training school.

*Illustrated below is a typical M.S.S. Studio Recording equipment, but the M.S.S. range includes Portable Studio Recording equipment, Portable Recorders for the professional and also home recording equipment. Full details will gladly be sent on request.*



**M.S.S. RECORDING CO., LIMITED**  
POYLE CLOSE, COLNBROOK, BUCKS  
Telephone: COLNBROOK 115

## RECORD PLAYERS

by

*Richard Allan*



C.D.M. With variable speed regulator, automatic start and stop, 12" cloth covered turntable. Price £15 : 1 : 0  
Tax Paid

R.D.M. (illus.) This powerful rim driven model is fitted with fool-proof start and stop mechanism beneath the unit plate. Price £12 : 0 : 8  
Tax Paid

C.D.U.M. Universal model operating on A.C. or D.C. Current. Price £20 : 15 : 8  
Tax Paid

FROM ALL  
GOOD DEALERS

*There is a most comprehensive range from which to choose*


**RICHARD ALLAN** RADIO LTD.

**BAFFLETTE HOUSE · BATLEY · YORKS**

*Makers of the famous BAFFLETTE Extension Speakers*

## "Cyldon" VARIABLE Capacitors

TRANSMITTING

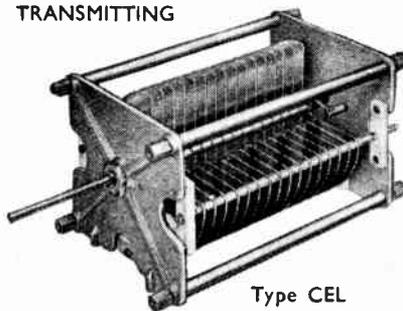

Type CEL

13½" long (excluding spindle). 8" wide. 7¼" high.  
Air gap .218" Range of max. capacities. 100—1000pF.

**MICA TRIMMERS to AIR DIELECTRIC**  
**HIGH-VOLTAGE** *Transmitting Capacitors*

**SYDNEY S. BIRD & SONS, LTD.**  
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX.  
Phone: Enfield 2071-2. Grams: Capacity, Enfield.



**VALVES** For **SPECIAL PURPOSES**


**6F33**

**RATING**

Heater Voltage (volts) ...	Vh	6.3
Heater Current (amps) ...	Ih	0.35
Maximum Anode Voltage (volts) ...	Va(max)	250
Maximum Screen Voltage (volts) ...	Vg2(max)	250
Mutual Conductance (mA/v) ...	gm	* 4.35
Inner μ ↑ ...	μgl2	* 38
Maximum Anode Dissipation (watts)	pa(max)	2.5
Maximum Screen Dissipation (watts)	pg2	0.8
Maximum Potential Heater/Cathode (volts DC) ...	Vh-k(max)	100

\*Taken at Va=200v; Vg2=100v; Vg1=-1.5v; Vg3=0v

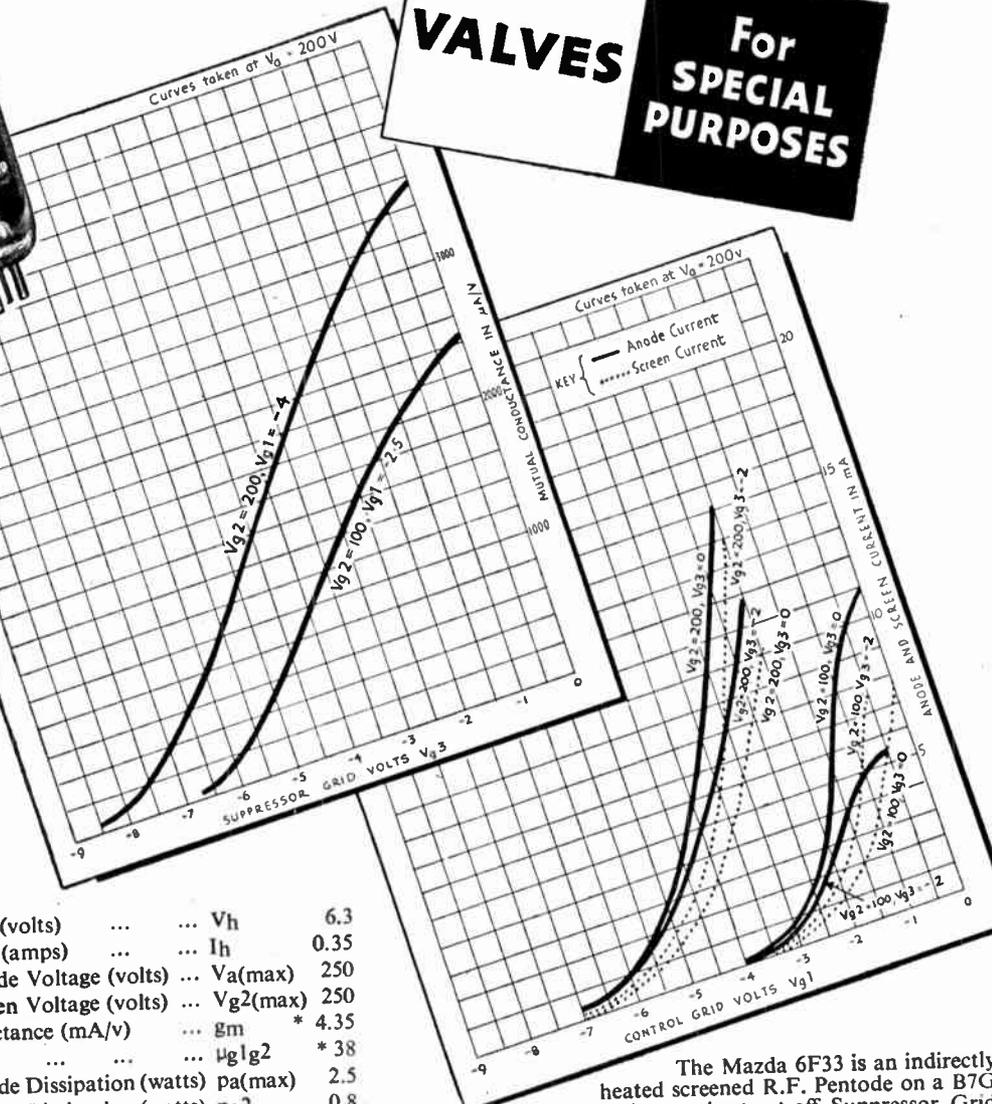f.t.e  $\frac{\delta V_{g2}}{\delta V_{g1}}$  with Ia constant



The Mazda 6F33 is an indirectly heated screened R.F. Pentode on a B7G base. It has a short cut-off Suppressor Grid characteristic which makes it particularly suitable for use in Modulator, Variable Reactance and Timing Circuits. In order that the Suppressor Grid may be driven positive, a diode has been tied to this grid. List Price 17/6d.

Further details will be supplied on application to the Radio Division.

**EDISWAN**  
**MAZDA**

**RADIO VALVES AND CATHODE RAY TUBES**

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS RD., LONDON, W.C.2.

RA13



**AMBASSADOR**  
OF GREAT BRITAIN  
REGD

OF particular interest to "Wireless World" readers are the Ambassador "849" and "949" (Export) series, featuring high fidelity push-pull output and twin speakers.

Literature is available on application.

AMBASSADOR RADIO — HUTCHINSON LANE — BRIGHOUSE — YORKS


You can have 100 gns.

## RADIO-GRAM

for less than one third of that amount with

"RUCO" FEEDER AND AMPLIFIER UNITS

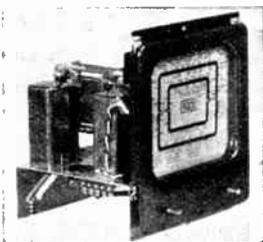Revive that old gram with a Ruco outfit and bring new life to your Radio and Record entertainment



Several types are available 9 to 3 wave bands single ended and push-pull output bandspread.ing pre R.F. amplification fly-wheel tuning etc., etc.

*Don't delay—*

WRITE NOW GIVING FULL DETAILS OF YOUR REQUIREMENTS

*Do you know that we are one of the largest manufacturers of Radio Feeder Units?*

**RUCO PRODUCTS**  
**197 Lower Richmond Road**  
**RICHMOND, SURREY**

'Phone PRO 7463.

*Special Waxes*  
FOR THE

## ELECTRICAL INDUSTRIES

Manufacturers of electrical and radio materials and components are invited to investigate

# OKERIN

WAXES AND DI-JELLS

for insulating, waterproofing, impregnating, sealing and finishing condensers, cables, transformers, batteries, resistances, etc.

*For technical data and samples please telephone TEMPLE BAR 5927*

Sales Department

**ASTOR BOISSELIER & LAWRENCE LTD**  
NOFOLK HOUSE · NOFOLK STREET · STRAND · W.C.2

Works and Laboratories: West Drayton Middlesex.

**We recommend this tube**

**because**

**It has a specially flat face.**

**It gives a bright,  
pleasantly coloured  
image.**

**Ferranti reliability  
ensures long life.**

**Freedom  
from ion burns.**

**The price is reasonable.**



## **FERRANTI CATHODE RAY TUBES**

There's a keen demand for this Ferranti T12/46 12" Television Tube, so place your order NOW!


**FERRANTI LTD MOSTON MANCHESTER 10; & 36 KINGSWAY LONDON WC2**

# CELESTION

The Foremost Name in  
Sound Reproduction
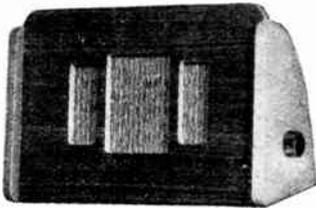
## “BAFFLE” SPEAKERS

It is worth considering that whichever CELESTION Extension Loudspeaker you purchase, you are certain of getting the accumulated experience of over 25 years specialisation in the design and construction of Loudspeakers. For appearance, perfect tonal quality and many years trouble free service, CELESTION Extension Loudspeakers are second to none.



**MODEL “FIVE B”**  
5in. P.M. SPEAKER

*Without transformer*  
Size: Height 8in.  
Width 11½in. Depth 5in

**PRICE 39/6**

**MODEL “SIX B”**  
6½in. P.M. SPEAKER

*Without transformer*  
Size: Height 9in. Width  
2½in. Depth 5½in.

**PRICE 49/6**

Both above models have Polished Walnut Baffle, cream sides and are fitted with Volume Controls.

## CABINET SPEAKERS

There are several excellent CELESTION Cabinet Model Extension Loudspeakers to choose from. The Senior 8, as illustrated has a cabinet of selected walnut veneer and the expanded metal grille is most attractive.


**SENIOR 8**  
8in. P.M. SPEAKER

*Without transformer*

Size: Height 10½in. Width  
12½in. Depth 5½in. Fitted  
with Volume Control.

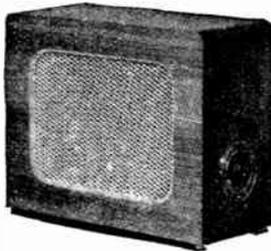**PRICE £4-5-0**

Price with Multi-Radio  
transformer £4-11-0



OUR NEW ILLUSTRATED BROCHURE AND PRICE LIST “B.C.” WILL BE SENT YOU ON REQUEST.

### SOLE DISTRIBUTORS

to the Wholesale and Retail Trades

*Cyril French Ltd.*

HIGH STREET, HAMPTON WICK,  
KINGSTON-ON-THAMES, SURREY

Telephone: KINGston 2240

## • CONSTANT VOLTAGE • POWER SUPPLY UNITS

### NEW SERIES 101

Our new Laboratory Power Supplies, Series 101, are based on our well-known Model 101-A, but incorporate a number of improvements and refinements.



DETAILS ON REQUEST.

**ALL-POWER TRANSFORMERS LTD.**

8a, GLADSTONE ROAD, WIMBLEDON, S.W.19

Tel.: LIBerty 3303.

## The Revolutionary GOLDRING

*Headmaster*

HYPERFIDELITY

**PICK-UP**



With an interchangeable Pick-Up Head for every type of record.

Supplied in attractive Display Carton complete with Goldring Tonaliser and Transformer



Goldring Products include:

PICK-UPS, PICK-UP HEADS,  
SAPPHIRE JEWEL POINT  
NEEDLES, AND RADIOGRAM  
ACCESSORIES.



Write for full Descriptive Lists and Technical Information:

**ERWIN SCHARF**

49-51a LEA VOR ROAD, LONDON, N.1

Telephone: CLISSOLD 3434

# *Play the Ace of Trumps against Ignition Noise*



Reduced List Price

**1/6** each




# ERIE
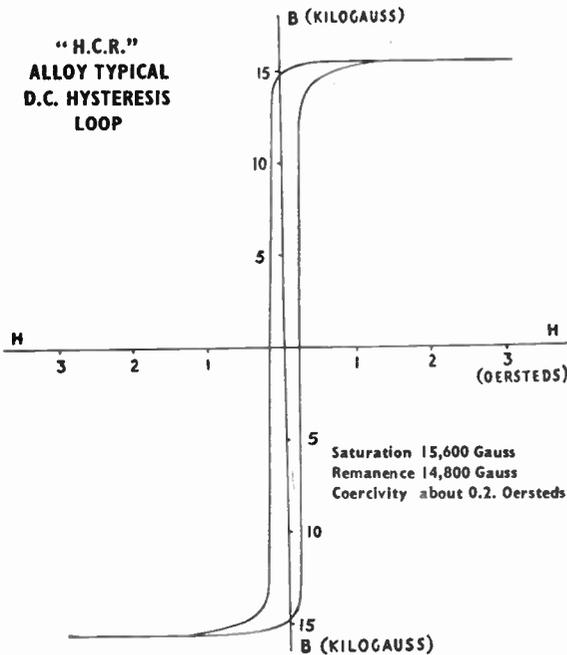
## TELCON'S LATEST MAGNETIC DEVELOPMENT



*is now available in commercial quantities*



The magnetic properties of this alloy make it suitable for mechanical rectifiers, magnetic amplifiers and special forms of reactors.



Full technical details on request from :-

**THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD.**  
 Founded 1864  
 Head Office: 22 OLD BROAD ST., LONDON, E.C.2. Tel: LONDON Wall 3141  
 Enquiries to TELCON WORKS, GREENWICH, S.E.10 Tel: Greenwich 3291

*Size counts!*

**THE SMALLEST SILVERED MICA CAPACITOR**

Our type IOB capacitors are now extensively used as a standard component for low capacitance values. Their small size offers the advantage of low stray capacitance and also allows a better spacing from coil assemblies where a high Q value must be maintained.

### STABILITY RADIO COMPONENTS LTD

14, NORMAN'S BUILDINGS  
 CENTRAL STREET, LONDON, E.C.1.

Telephone : CLErkenwell 5977/8

## THE SOUND MAGNET MAGNETIC TAPE RECORDERS

Orders are being taken against forward deliveries of model XL. £47/10/-. List.

Because of the abnormal demand for these machines, orders received from all over the world—our output is insufficient to meet immediate requirements—your early ordering is advised.

The new system of recording on Plastic Tape. Our SOUND MAGNET has these exclusive features, and many others.

Records any programme, music or speech.

Instant playback, no processing.

Clean erasure of unwanted material.

Tape can be cut and joined.

Three speeds, 3 3/4, 7 1/2, 15-inch per second.

Playing time, 1/4, 1/2, 1-hour from one reel.

Twin sound tracks double above times.

Supplied complete in handsome grained leathercloth cabinets.


**GENERAL LAMINATION PRODUCTS LTD.**  
 Dept. S.M., 294 BROADWAY, BEXLEYHEATH, KENT



# The longest Journey...
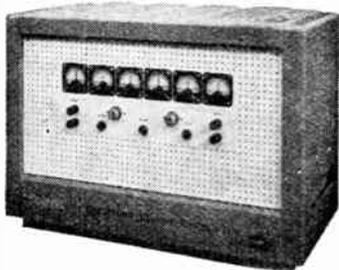
## begins with one step

'CINTEL' guarantees a step in the right direction where electronics are concerned. We illustrate three typical 'CINTEL' instruments from our wide range for the modern laboratory. Please write for further particulars.



CINTEL' MICROSECOND COUNTER CHRONOMETER

CINTEL' R.C. OSCILLATOR & AUTOMATIC FREQUENCY MONITOR



CINTEL' MUTUAL & SELF INDUCTANCE BRIDGE



## CINEMA - TELEVISION LIMITED

FOREMOST IN THE MANUFACTURE OF

- Counters & Chronometers
- Metal Detectors
- Oscilloscopes
- Proto-Electric Cells
- Cathode Ray Tubes
- Geiger-Muller Tubes
- Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S.E.26

Telephone: H1Ther Green 4600

Northern Agents:  
P. C. ROBINSON & PARTNERS LIMITED  
308 Deansgate, Manchester 3

Scottish Agents:  
ATKINS, ROBERTSON & WHITEFORD LIMITED  
100 Torrissdale Street, Glasgow, S.2



REGISTERED TRADE MARK

# THE MOBILE SIGNAL GENERATOR

FOR FIELD OR FACTORY

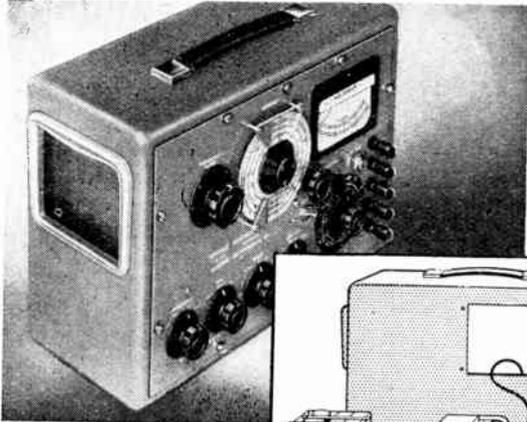


Diagram showing rear aperture and easily interchanged mains and battery units.


Originally styled for service in the front line, this mobile Marconi Signal Generator has proved itself supremely adaptable. Light and compact as an attaché case it is mains operated ordinarily but independent of power supplies when fitted with its special battery unit. Technically a triumph of ingenuity, it combines in so small a compass a SIGNAL GENERATOR with wide frequency coverage—70 kc/s to 70 Mc/s—OUTPUT POWER METER, up to 1 W with impedance matching — and CRYSTAL CALIBRATOR accuracy 2 parts in  $10^4$ . Accuracy of output and frequency calibration is above the average for so moderately priced an instrument. Please ask for further particulars of:

**The Portable Receiver Tester Type TF888**
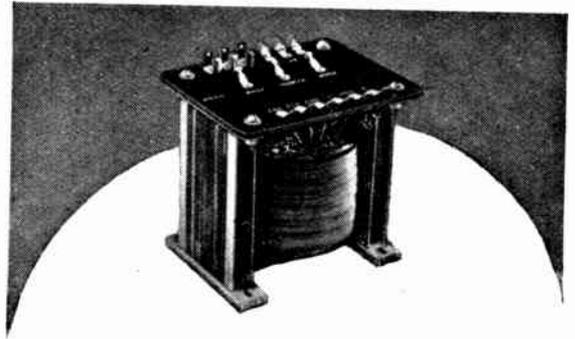
## MARCONI INSTRUMENTS LTD.

ST. ALBANS, HERTS. Telephone: St. Albans 6161/5

Northern Office: 30 Albion Street, Hull. Western Office: 10 Portview Road, Avonmouth. Southern Office & Showrooms: 109 Eaton Square, London, S.W.1. Midland Office: 19 The Parade, Leamington Spa.



## When an unusual Specification is required

We can give you the benefit of 20 years' experience in transformer construction and design. We do NOT mass produce. Every instrument is built to suit your most exacting individual specification.

Send your enquiries for the personal attention of our Mr. W. Bryan Savage.



SAVAGE TRANSFORMERS LTD.

NURSTEED ROAD, DEVIZES, WILTS

## "REPRODUCTION OF RECORDS"

by J. H. Brierley

Booklet. Price 3/6 (by post 3/11).

In this booklet inter alia is described a pre-amplifier incorporating all necessary equalising and variable tone control circuits that will fully load any standard amplifier if fed with an input of 5 mV., the noise and hum level being not higher than—60 db. at full gain.

Fullest practical details are given with photographic illustrations of the exact location of the components and method of wiring.

General principles are discussed with particular reference to the illogical and incorrect procedures that are always the root cause of difficulties associated with low output high fidelity pick-ups.

J. H. BRIERLEY (Gramophones & Recordings) LTD.

46, Tithebarn Street, Liverpool, 2

# LONDON CENTRAL RADIO STORES

**Government Surplus - Immediate Delivery from Stock**


**PHILIPS 6-VALVE COMMUNICATIONS RECEIVER**



16-50, 200-550 and 800-2,500 metres. R/F, F/C, 2 I.Fs. D.D.T. Pentode Output. Spin-wheel tuning. In black metal case with built-in speaker. Complete with power pack, AC 200-250 v. Can also be supplied with 12 v. D.C. power pack if required. **BRAND NEW-EX-GOVT. £17.10.0**

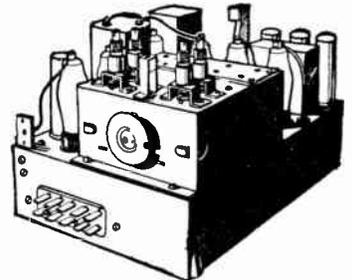**R.A.F. 6-VALVE SUPERHET RECEIVER UNIT No. 25**


All valves guaranteed. This unit is easily adapted to Short-wave reception for home use. In addition to two EF36, two EF39, one EK32 and one EBC33 valves, it contains 1 pr. 400 Kc/s iron dust I.F. Transformers, Mic. and phone output transformers, a number of resistances and fixed condensers of useful values, two 1 mid. 500 v. wkg. and four .1 tubular condensers, pot'meters, Int. Octal-Valve holders, Tuning Coil, etc., mounted on steel chassis 8½ x 6½ x 2½ in. **FREE circuit diagram 9in. x 19in.** showing all components, supplied with each set.



In new condition.

**22/6**

**TYPE 73A VISUAL UNITS.**

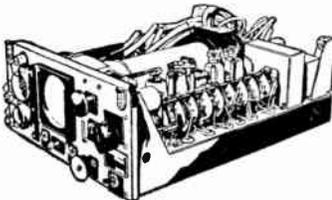


With 4in. Cathode Ray Tube, VCR138A, 4 SP61, 1 EB34 valves, potentiometers, etc. Complete on chassis, 16 x 12 x 5½ in. **35/-**

**EX-GOVT. SUPERHET UTILITY SET.** Medium Wave only. Valves - ECH35, EF39, EL33, DW4/350. P.M. Speaker. In pine wood cabinet 13½ x 12 x 6½ ins. In good condition. Carr. and pkg. 5/- **77/6**


**EX-R.A.F. TEST SET TYPE 202.** 7 EF50, 2 VR116, 1 5Z4G, 2 VR54 valves, electrolytic condensers, transformer, potentiometers, resistances and condensers. **60/-**

**BRAND NEW ACCUMULATORS.**

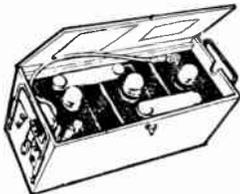

6 v., 85 a. Size 12 x 9 x 7in. Weight 45 lbs. British made. **£3.10.0**

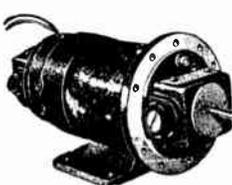**FRACTIONAL H.P. A.C. MOTORS**  
Converted from ex-Govt. Generators



Brush type 220-250 v. 50 cycles approx. 5,000 r.p.m. Overall diam. 10 x 4in. ½ in. spindle extends 1in. both ends. **21/-**

**COSSOR MODEL 900 TELEVISION, 15in. TUBE.**

with All-Wave Radio. Walnut Console Cabinet. In perfect working order. For callers only. **£85**

**HEADPHONES.** Low resistance with headbands, new, 4/8 pair New American midjet Reed type, 90 ohms, no headband, 3/8 pair. American light weight. Suitable for deaf aid, 7/8 pair. **BLOWER MOTORS.** 12-24 v., 17/6. 80 v., 15/-.

**2-VOLT VIBRATORS.** Self-rectifying. Output 200 v. at 60 mA., 7/6.

**VIBRATOR PACK.** Admiralty pattern, 12 v. D.C., 300 v., 100 mA. output, 30/-.

**POWER UNIT, Type 280.** Contains four VU133, one 5U4, one VR65 valves, 22/6.

**VISION UNIT, Type 182.** Complete with 6in. 617 CR. Tube, 2in. 139 CR. Tube, one 807, three VR65, one 6J5 valves. 0.5 milliammeter, condensers, etc. Suitable for Television, 55/-.

**VISION UNITS, Model 6A.** Consisting of 6in. VCR97 Electrostatic C.R. tube, 7 valves, including four EF50, potentiometers, resistances and other associated components. In metal cabinet 13 x 8 x 7in. These units are in perfect condition. Ideal for Television. 67/6.

**20-VALVE RECEIVER Type No. 3515.** Includes 13 Mc. strip suitable for Television sound or vision when used in conjunction with R.F. unit Type 25. Contains the following valves: 10 SP61, 5 EF36, 3 EBC33, 1 EB31, 1 Muzda A832, relays, condensers, resistances, etc. Brand new in metal case and supplied in wood transit case. 55/-.

The R.F. Unit Type 25 suitable for use with the above and for other television purposes is 12/6 extra.

**NEW MILNES H.T. UNITS** (everlasting) 120 v. 600 mA. Will charge from 6 v. accumulator. Callers only. 67/6.

**EX-R.A.F. CAMERA MOTORS.** 11mm. dia. 3in. x 2in. x 1½ in. 24 v. AC/DC. 8/6.

**EX-GOVT. TELEPHONE HAND SETS** (Sound Power). New stock. Self-energising. Need no battery or current, 7/6.

**1/30th H.P. MOTORS.** Constant speed. Double-ended spindles. 220-250 v. These motors are new, not surplus conversions and are suitable for 16 mm. projectors and many other purposes. AC/DC, with feet, 42/6. AC, without feet, 35/-.

**MOVING COIL HAND MICROPHONE.** Complete, 5/6.

**INSERTS, as above, 2/9.**  
**7-VALVE U.H.F. RECEIVER.** Type E1147A. Range approx. 200 megacycles (with 4 Acorn valves). A Real Opportunity. Beautifully constructed and fitted with micro-condenser drive. Valve types: two EF36, one EBC33, three 954 one 955. In black metal case, 8 x 7 x 6in. Set complete with valves. 30/-.

**EX-ARMY TEST SET-NEW, Type Demolition Mk. 1.** For circuit continuity and general testing. In hardwood carrying case, 42/-.

**FIVE-WAY RUBBER COVERED CABLE.** Suitable for lighting and other purposes. Per doz. yds., 6/-.


**EX-GOVT. 100W. COPPER AERIALS,** ebonite chain insulators, 30ft. guy rope, 4/3.

**PHOTO-ELECTRIC CELLS, Type GS16.** These cells are the gas-filled type with cesium Cathode. Made by Cintel. Minimum sensitivity 100A/lumen, working volts 100 D.C. or peak A.C. Projected cathode area 16 sq. cm. Suitable for 16 mm. Home Cinema Talkie equipment, Safety Devices, Colour and Photo-Matching, Burglar Alarms, Automatic Counting, Door Opening, etc. Brand new in original cartons. 42/6.

**PLEASE NOTE**

● All carriage paid unless otherwise stated. ● Carriage charges relate to British Isles only. ● We do not issue lists or catalogues. ● We have hundreds of items in stock too numerous to list, including Special Admiralty Transmitters, Receivers, etc., so when in Town pay us a visit.

**EX-R.A.F. TUNING UNIT TYPE 207A.**

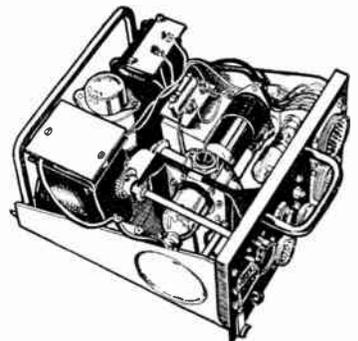

**BRAND NEW.** Includes Clystron valve, 3 Neon tubes CV71, 1 5Z4G and other useful components. As illustrated, plus metal cover. **21/6**

**NEW VCR97 CATHODE RAY TUBES, 37/6- R.C.A. CINEMA SPEAKERS.** 110 v. Complete with wood horns. 2ft flare. **£5.10.0**  
**12in. C.R. TUBES VCR140** Blue Screen, 90/-  
**WESTERN BALL MICROPHONE.** Manufactured by Standard Electric.

Suitable for broadcasting and recording. Moving Coil (Dynamic), Omni-directional. No energising necessary. High Fidelity. Coil Impedance 15 ohm, and will work very well in conjunction with an ordinary speaker transformer. **£4.17.6**



Is of the type used by many leading bodies, such as the B.B.C. and G.P.O. for high fidelity reproduction.


**EX-R.A.F. TUBULAR CONDENSERS.** .02 mid. 8 Kv. D.C. working, 8½ in., 4/-  
**4 MFD. CONDENSERS 2,000 v. D.C., 4/6.**

**LONDON CENTRAL RADIO STORES, 23, LISLE ST. (GERrard 2969) LONDON, W.C.2**

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.



# Leaders in their field

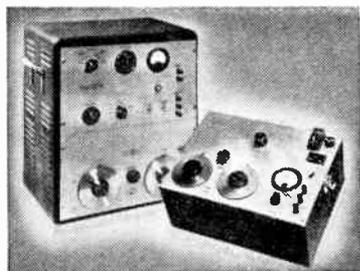

BEAT FREQUENCY OSCILLATORS & LABORATORY INSTRUMENTS




INDUSTRIAL SOUND INSTALLATIONS



PORTABLE AND MOBILE AMPLIFIERS



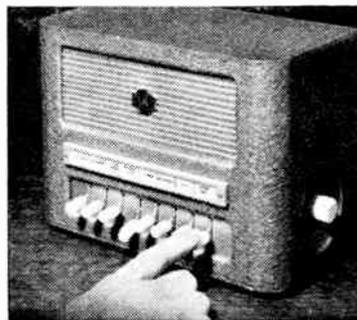
DIRECT DISC RECORDERS FOR HIGH FIDELITY DISC RECORDING



TELEMASTER INTER-OFFICE COMMUNICATION EQUIPMENT



G.U.2 GRAMOPHONE UNIT

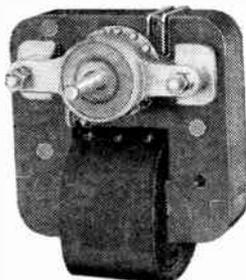

SHADED POLE MOTORS



T.U.2 TURNTABLE UNIT

## BIRMINGHAM SOUND REPRODUCERS LTD.

Telephone: Cradley Heath 6212

CLAREMONT WORKS, OLD HILL, STAFFS.

'Grams': 'ELECTRONIC' Oldhill, Cradley Heath

# Wireless World

RADIO AND ELECTRONICS

DECEMBER  
1949

39th YEAR OF PUBLICATION

Proprietors : ILIFFE & SONS LTD.  
Managing Editor : HUGH S. POCKOCK, M.I.E.E.  
Editor : H. F. SMITH

Editorial Advertising and Publishing Offices :  
DORSET HOUSE, STAMFORD STREET,  
LONDON, S.E.1.

Telephone : Waterlooo 3333 (60 lines).  
Telegrams : "Ethaworld, Sedist, London."

PUBLISHED MONTHLY

Price : 2/-

(Publication day : last Thursday of preceding month)

Annual Subscription : Home and Overseas, £1 6s. 0d.  
U.S.A. and Canada, \$11.00


Branch Offices :

Birmingham : King Edward House, New Street, 2.  
Coventry : 8-10, Corporation Street.  
Glasgow : 26B, Renfield Street, C.2.  
Manchester : 260, Deansgate, 3.

## In This Issue

OUR COVER : Anti-Echo Chamber (See Page 503)

EDITORIAL COMMENT .. .. .	46:
SUPPRESSED AIRCRAFT AERIALS By G. E. Beck .. .. .	46:
MEASURING TURNTABLE SPEED FLUCTUATIONS By E. W. Berth-Jones .. .. .	47:
TELEVISION RADIO RELAY .. .. .	47:
SHORT-WAVE CONDITIONS By T. W. Bennington .. .. .	47:
HIGH-QUALITY AMPLIFIER : New Version By D. T. N. Williamson .. .. .	47:
TEST REPORT : EKCO MODEL CR61 .. .. .	48:
WORLD OF WIRELESS .. .. .	48:
ELECTRONIC DIVERSITY SWITCHING By H. V. Griffiths and R. W. Bayliff .. .. .	48:
SUPPRESSING IMPULSE NOISE By D. C. Rogers .. .. .	48:
ELECTRONIC CIRCUITRY By J. McG. Sowerby .. .. .	49:
POINTER INSTRUMENTS By E. H. W. Banner .. .. .	49:
RECORDS UNDER THE MICROSCOPE .. .. .	49:
UNBIASED By Free Grid.. .. .	49:
THIS AND THAT By "Cathode Ray" .. .. .	49:
LETTERS TO THE EDITOR .. .. .	50:
RANDOM RADIATIONS By "Diallist" .. .. .	50:
RECENT INVENTIONS .. .. .	50:

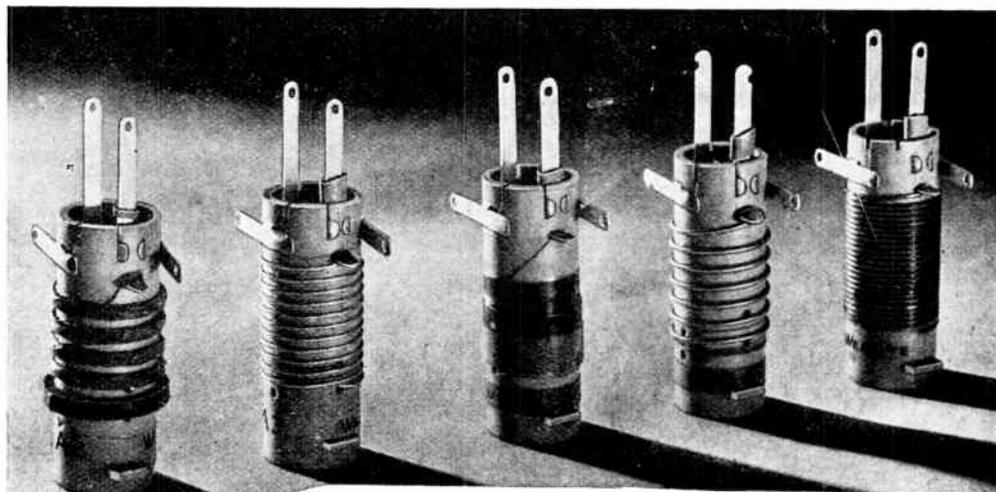

### WEARITE COIL PACKS "P" COILS


... for Aerial, R.F., and Oscillator Tuning and readily available in all ranges.

WRIGHT & WEARE LIMITED

138 Sloane Street, London, S.W.1.

Telephone : SLOane 2214/5.

Factory : South Shields, Co. Durham.

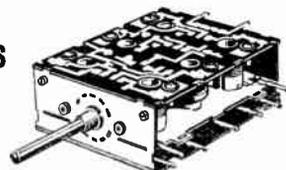

Send 6d. in stamps for the "Wearite" COILPACK Book of Technical Data and Circuits.



# Valves and their applications

## TELEVISION SYNCHRONIZING & TIME BASE CIRCUIT USING EF42, EGC34 & EL38. No. 3. SYNCHRONIZING PULSE SEPARATOR USING EF42.

The circuit of Fig. 1 with its associated waveforms in Fig. 2 will be recognised as part of the complete circuit in last month's issue of the "Wireless World".

The effectiveness of the time base synchronization profoundly affects the quality of the final picture. With the system of synchronization described in this series of reports a clean vertical edge and steady interlace are secured even in the presence of considerable interference, thus realising the full benefits of high definition obtained from specially designed signal circuits.

The process of synchronization is achieved in four major stages. In the first stage a slicing action takes place in which the composite video signal is truncated with the elimination of the picture signal and the tips of the synchronizing pulses which contain noise and interference.

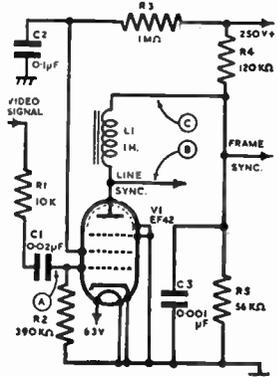


FIG. 1. CIRCUIT OF FIRST LIMITER IN SYNCHRONIZING PULSE SEPARATOR.

corresponding to the chain of eight frame pulses, is passed on and other pulses, corresponding to the line pulses, are eliminated.

In the circuits discussed these stages are somewhat inter-related but the conception of the four steps will assist in following the more detailed description of the circuits which is given in the additional notes and next month's advertisement.

The first limiter (see Fig. 1) has a double clipping action by driving the EF42 well into grid current on the tips of the pulses and having a sufficiently short grid base so that the base of the pulses and the vision signal are beyond cut-off. The inductor L1 causes the valve to bottom as if it had a very large resistive anode load which gradually decreases in value during the

In the second stage, the synchronizing pulses are fed to the line time base in such a way that the time base is synchronized or fired at the correct instants of time by the leading edges of the pulses.

In the third stage, amplitude differentiation of the line pulses and the chain of frame pulses is obtained. In the transmitted signal the differentiation is one of pulse length.

The fourth and final stage is a further slicing operation. The results of the third stage are sliced so that a single pulse of about 400μs duration,

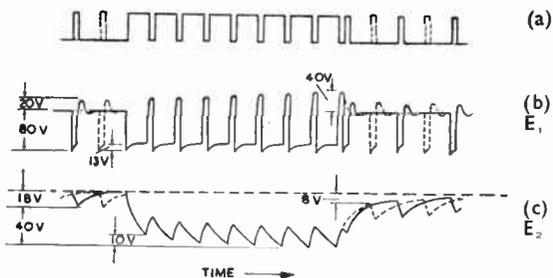


FIG. 2. WAVEFORMS OF POTENTIAL ASSOCIATED WITH THE FIRST LIMITER STAGE OF THE SYNCHRONIZING PULSE SEPARATOR.

- (a) Transmitted Synchronizing Pulses.
- (b) Waveform at Anode of Valve V1. (E<sub>1</sub>)
- (c) Waveform showing Amplitude Differentiation of Frame and Line Pulses (at point C, Fig. 1). (E<sub>2</sub>)

period of a synchronizing pulse. This has the effect of increasing the limiter base (the range of grid potential between cut-off and bottoming) during the pulse and the maximum amount of noise and interference is cut off at the beginning of the pulse period when the line blocking oscillator is fired and is taking current. If a large value resistor were used instead of an inductor to obtain this short limiter grid base the frame pulses would not be effectively developed across the capacitor C3 for lack of sufficient anode current. With the circuit employed large frame pulses are obtained, the amplitude of the first being practically equal to that of the last.



Reprints of this report from the Mullard Laboratories, together with a fuller description of the circuit, may be obtained free of charge from the address below.

MULLARD ELECTRONIC PRODUCTS LTD.,  
TECHNICAL PUBLICATIONS DEPARTMENT,  
CENTURY HOUSE, SHAFESBURY AVE., W.C.2  
(MVM108)

# Wireless World

VOL. LV. NO. 12

DECEMBER, 1949

RADIO AND ELECTRONICS

## Monthly Commentary

### G.P.O. AND INTERFERENCE

**A** CORRESPONDENT whose letter is printed elsewhere in this issue draws attention to a matter that has become of increasing importance since the Wireless Telegraphy Act was passed.

As everyone knows, the General Post Office has long undertaken to investigate complaints of interference with broadcast reception, and to give help, within its power, in removing the cause. It is less generally known that this help has been mainly restricted to dealing with interference affecting reception of B.B.C. stations, though we believe that no official pronouncement has been made to support the statement, quoted by our correspondent, that reception of foreign broadcast stations is no concern of the P.O. engineers.

Even before the passing of the Wireless Telegraphy Act such an attitude seemed hardly tenable, or at least highly arbitrary. In law, the listener pays his licence fee, not for the B.B.C. programmes, but for the use of a very small part of the Postmaster-General's monopoly in wireless telegraphy. If the licensee chooses to listen to foreign stations, he is surely entitled to equal protection within reason, though it would clearly be unreasonable to expect a signal of excessively low field strength to be effectively protected.

Although the Postmaster-General's obligations to protect his broadcast listener licensees may not be sensibly affected by the passing of the Wireless Telegraphy Act, his powers to afford effective protection are now greatly increased. These powers should, we submit, be wielded in such a way as to encourage the development of broadcast listening in every direction. The P.M.G. has always had authority to curb encroachments on the broadcast band by stations licensed by him, but it would seem that British beacon stations do at present interfere with the reception in this country of non-

B.B.C. stations. As to machine-made interference, it is hoped that the new powers of suppression will be wielded in such a way as to confer the greatest possible benefit to all, and not in a dictatorial or arbitrary manner.

### QUICK-TUNING SYSTEMS

**C**OMMENTING last month on the trend of design of broadcast receivers, as exemplified at the Olympia Exhibition, we referred to a tendency to provide the simplest possible form of tuning for the selection of B.B.C. programmes. This, as we said, is a change we have long expected to see. Domestic broadcasting is, at present, organized on a basis of three programmes—or two programmes for a large proportion of the population. Therefore there would seem to be a need for some quick and easy change-over device from one to the other, irrespective of the complexity or otherwise of the main tuning system of the receiver—and also irrespective of the skill of the user.

A surprisingly large number of readers seem to agree with the desirability of this innovation. A few of our correspondents, it must be admitted, chide us gently for detecting a summer when only one or two swallows in fact exist; they say, in effect, that the very small number of sets in which this feature is included hardly warrant its being hailed as a trend in design. Be that as it may, no dissentient voice is raised against the value of the feature, and our regular contributor, "Cathode Ray," suggests the general public lack the spirit to demand a facility of which he assumes the value to be self-evident. We think, now that the ordinary listener has been shown that switch selection of the main B.B.C. programmes is practicable, he will soon expect to find it in every type of receiver, at every price level.

# SUPPRESSED AIRCRAFT AERIALS

## Various Methods of Reducing "Drag"

By G. E. BECK, B.Sc., A.M.I.E.E.  
(Marconi's Wireless Telegraph Company)

TABLE OF AERONAUTICAL RADIO AND RADAR SYSTEMS

Service	Frequency Coverage Mc/s.	Type of Aerial
Automatic direction finding	0.15 to 2.0	Sense aerial and rotating loop.
M.F. weather reports and "Consol" navigation.	0.15 to 2.0	Reception only, omni-directional, vertically polarized.
H.F. communication	2.0 to 20.0	Transmission (150W) and reception, omni-directional.
V.H.F. communication.	118 to 132	Transmission and reception, vertical polarization.
Instrument landing system. Marker.	75	Reception, downward-looking.
Instrument landing system. Localizer.	108 to 118	Reception, omni-directional, horizontal polarization.
Instrument landing system. Glide path.	329 to 336	Reception, forward-looking, horizontal polarization.
Secondary radar homing system. (Rebecca).	208 to 234	Directional aerials for vertically polarized transmission and reception.
Radio altimeters.	1,600 to 1,700	Downward-looking, transmission and reception.
Cloud and collision warning radar.	10,000	Narrow rotatable beam transmission and reception.

ONE of the principal ways of improving the overall performance of aircraft—and hence increasing the payload of civil aircraft—is to reduce "drag" to a minimum, by eliminating or suppressing external fittings on wings and fuselage. Conventional radio and radar aerials have proved serious offenders in this matter of "drag," so that the immediate need has been to produce aerials which do not project beyond the normal skin of the aircraft. For example, by eliminating 1 lb of "drag" from a medium-sized airliner whose cruising speed is 230 knots, the pay-load can be increased by 20-30 lb, and this might well be achieved by replacing an existing external aerial with a suppressed aerial. Again, by suppressing all the aerials on a modern airliner it is possible to eliminate 25 lb or more of "drag." Apart from this, suppressed aerials have obvious mechanical advantages at high speeds, when it is difficult to secure such things as projecting rods or wires.

Types of aerial.—Aeronautical radio services use frequencies in a great many wavebands. Some idea of the complexity of the problem this presents to radio designers and engineers can be obtained from a study of the table. This table gives some of the services concerned, the frequency coverage of those services, and the types of aerial that the fre-


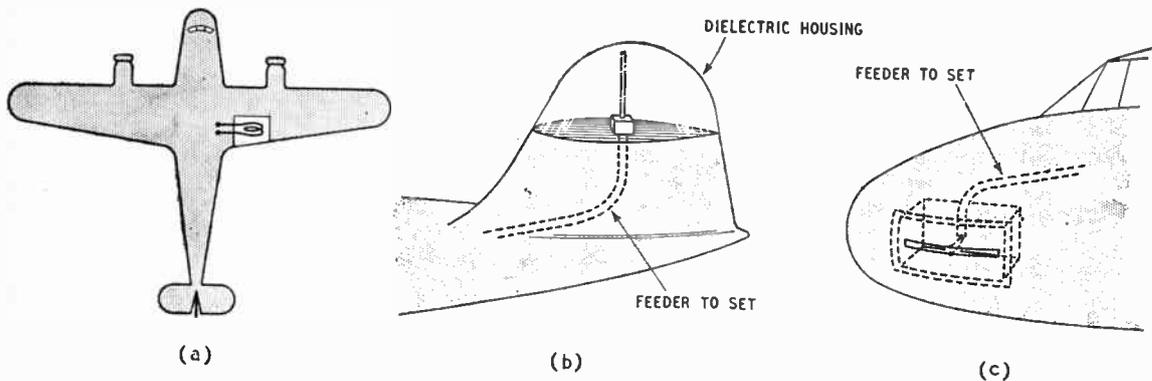
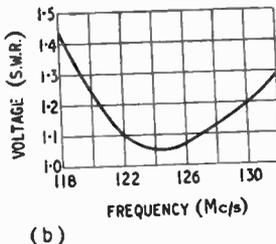


Fig. 1. Types of suppressed aerial : (a) wing radiator, (b) buried aerial, (c) slot aerial.

Fig. 2. Buried rod aerial for v.h.f. communication: (a) polar diagram, (b) measured bandwidth.

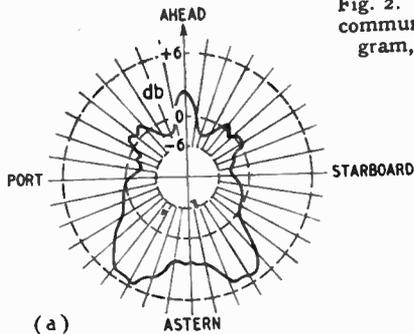

quencies demand. It is by no means a complete list, but all the items on it—or their equivalents—are required by aircraft flying on the international air routes of the world.

To cover such a wide range of frequencies it is obvious that the aerials of an aircraft must be of diverse forms, and some of the possibilities of suppressing these aerials are discussed below.

**Wing radiators (Fig. 1 (a)).**—Below 20 Mc/s the conventional aerials are trailing wires up to 200ft in length, or a fixed horizontal wire carried a few feet above the fuselage. The trailing type has a high loss resistance and the fixed wire a very low effective height, but it is not easy to produce as good a radiator within the aircraft structure. This structure is nearly always wholly metallic and the insulation of an appreciable part of it is not generally possible for mechanical or structural reasons.

One interesting approach to this problem is to excite the whole structure of the aircraft as an aerial. If the aircraft span is considered as a single "turn" secondary of a transformer whose primary is a small coil at the root of the wing, there will be some transference of energy which will be radiated. The same method can be applied to the excitation of the fuselage, and, if the wing and fuselage are energized in the correct phase relation, a "crossed dipole" system is produced from which the radiation pattern will be more or less uniform in azimuth.

Considerable success has been reported for this method over the frequency range for which the wing span is not less than 0.2 wavelengths (*loc. cit.*). Communication ranges equal to those

with a fixed wire aerial have been obtained, and the radiation pattern deviates from circular by less than ±2 db.

**Buried aerials (Fig. 1 (b)).**—Rod or loop aerials may sometimes be mounted in a way which does not cause any additional "drag" if a small part of the aircraft skin (such as the tip of a wing or a tail fin) is made from an insulating material. This is of value in the frequency band 100-200 Mc/s where an aerial approaching a quarter-wave in length can be housed inside a section not exceeding one or two feet long. Fig. 2 shows the polar diagram and measured bandwidth of a buried rod aerial for v.h.f. communication. It will be

seen that the polar diagram variations do not exceed ±6db and the voltage standing wave ratio is below 1.5:1 over the band. This compares favourably with an external aerial of the whip type.

Another example of a buried aerial is the rotating loop for medium-frequency direction finding. By the use of a dust-iron core sufficient pick-up is obtained from a shallow loop mounted in a tray below the aircraft skin. The skin of the aircraft is continued over the loop aperture with insulating material. The photograph (Fig. 3) also shows a symmetrical arrangement of rods inside the aperture which gives the vertical signal for sense determination.

All parts of the aircraft surface carry some mechanical stress and so the material for covering these aerials must possess good mechanical as well as electrical properties. This need is met by a laminate of woven glass cloth bonded together with a resin of good dielectric properties.

**Slot aerials (Fig. 1 (c)).**—It has been shown<sup>2</sup> that a rectangular slot cut in a metal plate will radiate if fed from an energized cavity placed behind it, or by a transmission line directly connected to opposite sides of the slot. The slot exhibits resonance similar to a half-wave dipole if it is a half-wavelength long at the operating frequency. If its width is small compared with a wavelength the radiation is polarized in a direction perpendicular to the length of the slot. (The slot is filled with a woven-glass type dielectric, otherwise the opening would defeat the purpose of suppressed aerials and create "drag.")

Radiation will take place from both sides of the sheet carrying the slot so that even when direct connection to the transmission line is used, as in Fig. 1 (c), a resonant cavity must be placed behind it to prevent unwanted radiation into the aircraft. The size of this cavity and the length of the slot which can be cut without weakening the structure make the applications to aircraft useful only for wavelengths less than 2 metres (frequencies greater than 15 Mc/s). A pair of directional receiving aerials formed by slots cut


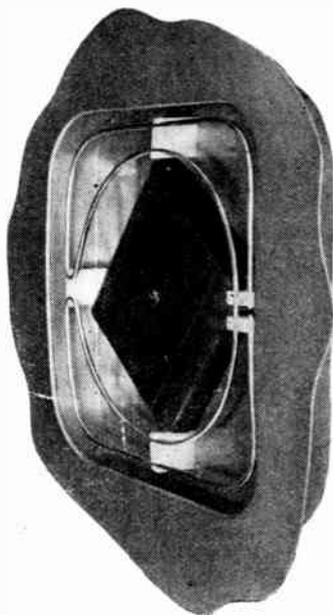


Fig. 3. Recessed iron-cored D/F loop and sense aerial; external view.
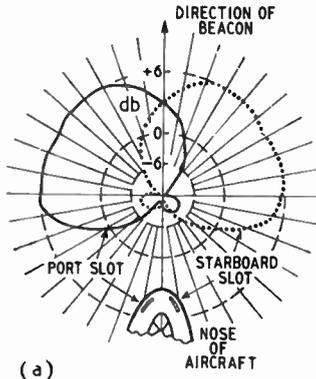
### Suppressed Aircraft Aerials—


either side of the aircraft nose will give an equisignal course for homing on a radar beacon (Rebecca-Eureka system). Fig. 4 shows the polar diagram and bandwidth of this type of aerial. The incoming signal energizes the slot which, in turn, energizes the cavity behind it. Within the cavity



an aircraft would be tested in the model at 2,400 Mc/s. The model can be raised sufficiently clear of the ground to simulate actual flying conditions. Fig. 5 shows such an arrangement.

A full-sized mock-up consisting of a framework formed in the shape of an aircraft nose is generally used to find the im-

Fig. 4. Directional slot aerial: (a) polar diagram, (b) measured bandwidth.

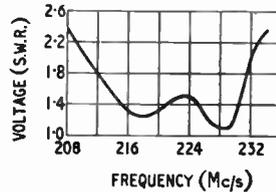

In all cases the performance of the suppressed aerials must not be inferior to that of the original external aerials which they are intended to replace, both as regards polar diagram and impedance variations within the specified frequency band. The most desirable terminal impedance depends on the particular equipment concerned, and so it is of the utmost importance that characteristics of aircraft aerials should be properly standardized throughout the radio industry if the aerials are to be suitable for any changes in equipment that may be required.

It should be pointed out, however, that already this matter has been greatly assisted by the publication of recommended aerial feeders and characteristics by the Air Radio Panel of the Radio Communication and Electronic Engineering Association<sup>3</sup>.

lies a probe which is energized by the cavity and provides receiver coupling.

**Design methods.**—One feature common to all these types of aerial is the dependence of aerial characteristics on the contours of the aircraft. The curvature of the metal skin surrounding a slot, the shape of a dielectric housing within which a rod aerial must be fitted, the presence of adjacent wings or tail fins; all have an effect on the aerial performance, so that the development of suppressed aerials must be based upon considerable experimental work.

A suppressed aerial which has been designed for one type of aircraft can rarely be used for any other type.

The final test of an installation is made on flight trials, but all the preliminary data can be obtained from experiments with models and full-size mock-ups of those parts of the aircraft which are concerned. The directional properties of an aerial can be gauged with considerable accuracy from a scale model of the aircraft and by using operating frequencies in proportion to the scale used.

Using a scale factor of 1/24, an aircraft of 100 ft wing span would be represented by a model a few feet across and an aerial intended to operate on 100 Mc/s in such

pedance characteristics of the aerials. The metal skin is represented by close-mesh wire netting over the framework. The figures thus obtained are those at ground level, but the change in impedance when flying is generally small enough to be neglected.

**Team work in design.**—Suppressed aerials are so much a part of the structure of an aircraft that the radio engineer and the aircraft designer must begin collaboration at a very early stage. The alternative designs which can be suggested, and the structural problems they raise, can be adequately resolved only while the aircraft is still on the drawing board. The possibilities of fitting suppressed aerials to machines which are already constructed are very limited.

This situation is now realized by the aircraft and radio manufacturers, and the aircraft of the future will carry suppressed aerials which are the result of good team work by the design staffs of both industries. Care must also be taken to see that potential users of the aircraft have been consulted at this early stage, so that the radio services they are likely to require may be catered for.

### References

- Johnson, W. A. "Recent developments of aircraft communication aerials." *J.I.E.E.*, Part IIIA, Vol. 94, p. 452, 1947.
- Booker, H. G. "Slot aerials and their relation to complementary wire aerials." *J.I.E.E.*, Part IIIA, Vol. 93, p. 620, 1946.
- Report of Sub Panel "H." (*Minutes of Air Radio Panel meeting, R.C. and E.E.A.*, 6.10.47).

Fig. 5. Scale model aircraft used for polar diagram measurements.



# MEASURING TURNTABLE SPEED FLUCTUATIONS

By E. W. BERTH-JONES, B.Sc.  
(E.M.I. Studios)

## *A Sensitive Method of Checking "Wow" and "Flutter"*

ONE of the most distressing forms of distortion which can occur in the reproduction of a sound recording, particularly a recording of music, is that caused by speed fluctuations. When this takes the form of slow cyclic variations, it is usually known as "wow," whereas rapid fluctuations are commonly referred to as "flutter." Erratic, non-cyclic speed changes are frequently called "watering."

The precise measurement of these variations in speed has offered considerable difficulty. The ear is particularly sensitive to this form of distortion, and anybody with a reasonably good sense of musical pitch will notice quite small variations, often as small as a tenth of one per cent, on a sustained note. In high-quality equipment it is commonplace to maintain speed constancy to within a twentieth of one per cent, and in order to measure the residual error with any accuracy, it is necessary to have a measuring instrument with a sensitivity of the order of one hundredth of one per cent, or one part in ten thousand.

Moreover, it is not sufficient to measure slow changes in the mean speed over a complete revolution. It is necessary to make the measuring period as short as possible in order to get accurate information of any rapid flutter which may occur, but this makes very severe demands upon the measuring apparatus. Fortunately, due to the inertia of the turntable, it is unlikely that speed changes will take place very rapidly, and a measurement averaged over one-tenth of a revolution would appear to give a satisfactory compromise.

A method which has met with some success employs a phonic wheel mounted concentrically with

the turntable, the teeth of which are used to generate an alternating electrical signal whose frequency will be proportional to the speed of rotation. This frequency may then be measured by bridge methods with the required degree of accuracy, and will be an indication of the speed. To attain an accuracy of one part in ten thousand, each tooth of the phonic wheel must be cut with this accuracy of tooth spacing, which makes the wheel a very costly item. With a wheel of normally realizable accuracy, the method is excellent, though expensive, for the measurement of "wow," but it is useless for the more subtle forms of "flutter."

### Change of Wavelength

For disc-recording purposes, a method which gives more reliable results at much lower cost consists simply of recording a continuous tone, at the same time playing back from a point slightly displaced from the point of application of the recording. It may safely be assumed that the oscillator producing the tone can be made to give a train of waves which are substantially identical in shape and spacing, to the required degree of accuracy. Methods of stabilizing oscillators have been described in the literature, and the problem becomes resolved into choosing the type which will maintain the required degree of constancy. The waveform is relatively unimportant, the governing factor being the precision of repetition.

The fundamental frequency of the reproduced wave may be measured as before, and if the speed is constant this will be identical with the oscillator frequency, since recording and re-

production are taking place at the same speed. If the rotational speed changes while the element is moving from the recording point to the reproducing point, the reproduced frequency will differ from that of the oscillator during the period of change. For instance, supposing that the disc is accelerating: the speed of an element when it passes the reproducer point will be higher than it was at the recording point, and the reproduced frequency will be correspondingly higher than that of the oscillator. This change in frequency can be made to give us a reading, not of the absolute speed, but of acceleration measured between recording and reproducer points. For normal cyclic variations, the amplitude of the speed change can be derived from this. It is unnecessary to measure the reproduced frequency directly. It may be compared with the original oscillator frequency on a ratio basis, or more conveniently on a difference basis, by means of beats. In the latter case, the beat frequency would be proportional to the acceleration.

Unfortunately, in practice, in any good recording system the accelerations to be measured have only a very low order of magnitude, so that a very high initial frequency has to be used in order to obtain a beat which will fall within a measurable range, and this high frequency may fall outside the limits of the recording system.

However, this method is capable of a modification which overcomes this limitation, and which can be made to yield a display which represents the speed deviation directly. For the purpose of this description, the method will be considered in its application to the measurement of flutter on

### Measuring Turntable Speed Fluctuations—

78 r.p.m. gramophone recording. It is a simple matter to adapt it to other problems.

The first requirement is an audio-frequency oscillator capable of supplying a tone of known frequency, constant to within a tolerance rather closer than the errors it is required to measure. This is fed through the recording channel to the cutter head, which is mounted in position on the recording lathe which is to be tested. A pickup is also mounted on the machine, in such a manner that it will track the groove cut by the recording head, at a distance of a few inches behind it, preferably adjustable. The output of this pickup is amplified until it can be matched in level with a second output tapped off from the recording channel. The recording machine is adjusted to run at correct mean speed, either by counting the number of revolutions in a given time, or by stroboscopic methods.

### Procedure

Cutting is now commenced, and the pickup is slipped into the groove, a little behind the recording point. Now if the turntable speed is constant, the output from the pickup will be, theoretically at least, a duplicate of the input wave, displaced from it only in time. Either by adjusting the oscillator frequency, or by moving the pickup mounting slightly, it is possible to arrange that both reach their maxima at the same moment, that is, they are in phase. Assuming no distortion of wave shape, the two outputs can be connected back-to-back, giving a resultant of zero.

Suppose now that the turntable speeds up, by a very small amount. Any individual wave peak, cut by the recording stylus, will now reach the reproducing point sooner, due to the increased speed of travel. This increase is very small, so that the saving in time is less than the duration of a single wave, but it is sufficient to ensure that the reproduced wave is now out of phase with the oscillator wave, and when the two are connected back-to-back, cancellation no

longer occurs. There is a residual resultant whose amplitude is a function of the change in speed, and which can be made to operate a meter. This is illustrated diagrammatically in Fig. 1.

Putting this in another way, supposing we set up the apparatus so that with correct mean turntable speed there are exactly 100 waves between recorder and reproducer points. If now the speed increases by, say, one tenth of one per cent, the wavelength will increase by one tenth of one per cent, and the length of 100 waves will increase by one tenth of one wave, which is  $36^\circ$  of phase difference, and easily measurable.

As an example of the dimensions involved, consider a gramophone recording turntable revolving at 78 r.p.m. The linear velocity of the groove under the needle point is given by

$$V = \frac{2\pi RN}{60} \text{ in/sec} \quad \dots (1)$$

where  $R$  is the radius of the groove, measured from the disc centre, and  $N$  is the speed in revolutions per minute. At a radius of about 4in, the linear velocity will be, say 30in/sec. If a 6,000 cycles per second tone is applied, then 6,000 cycles occupy 30in of arc on the disc, and the wavelength measured along the groove will be 0.005in. If now the spacing between recording and reproducing styli, again measured along the arc, is made exactly two inches, there will be exactly 400 waves between the two points, and the output will be in phase with the input.

Suppose now that the turntable speed is increased by, say, 0.01%, so that the linear velocity becomes 30.003in/sec. Now 6,000 cycles occupy 30.003in of arc, and the wavelength becomes 0.0050005in, so that there are now only 399.96 waves between the two points. The reproduced signal will be 0.04 of a wave in advance of the oscillator, which is a difference in phase angle of  $0.04 \times 360^\circ$ , equal to  $14.4^\circ$ , which is capable of giving a measurable output. At the present stage of the art, a speed fluctuation of 0.01%, which we have presumed, is generally considered to be quite inaudible.

It is worth noting here that this

measurement has been averaged over an arc of only 2in, on a circumference of 23.1in, that is, less than one-tenth of a revolution. The very high order of sensitivity of the method thus becomes evident.

### General Relationships

Generalizing from this example, it may be seen that, if we designate the number of waves between the two styli as  $W$ , and the distance along the arc in inches as  $D$ , then

$$W = D/\lambda \quad \dots (2)$$

where  $\lambda$  is the wavelength measured along the arc, in inches.

From (1) we have seen that

$$V = \frac{2\pi RN}{60}, \text{ and we have also}$$

$$V = f\lambda \quad \dots (3)$$

where  $f$  is the applied frequency.

Hence, the number of waves between the points is given by

$$W = \frac{60Df}{2\pi RN} \quad \dots (4)$$

Letting the suffix 0 denote the desired condition, for which the system is set up, we have  $N_0$  as the mean speed, in revolutions per minute, and  $W_0$  as the number of waves between the points when the speed is correct (which may be made any integral number of half wavelengths.)

The phase difference producing output, measured in degrees, will be the angle  $\phi$ , where

$$\phi^\circ = 360(W_0 - W) \quad \dots (5)$$

or, measured in radians

$$\phi_{\text{rad}} = 2\pi(W_0 - W) \quad \dots (6)$$

Substituting from (4), this latter becomes:—

$$\phi_{\text{rad}} = 60f \frac{D}{R} \cdot \left( \frac{1}{N_0} - \frac{1}{N} \right) \quad \dots (7)$$

$$= 60f \cdot \frac{D}{R} \cdot \frac{N - N_0}{NN_0}$$

$$= -\frac{6f}{10} \cdot \frac{D}{R} \cdot \frac{n}{N}$$


where 'n' is the percentage change in speed.

Since the actual change of speed is very small, it is permissible to write  $N_0$  for  $N$  in this equation, which then becomes

$$\phi_{\text{rad}} = -\frac{6f}{10} \cdot \frac{D}{R} \cdot \frac{n}{N_0} \quad \dots (8)$$

From equation (8) it will be seen that the phase angle changes in direct proportion to the percentage change of speed, so that any meter suitable for measuring the phase difference between the

Fig. 1. Illustrating the principle underlying the method of measurement.

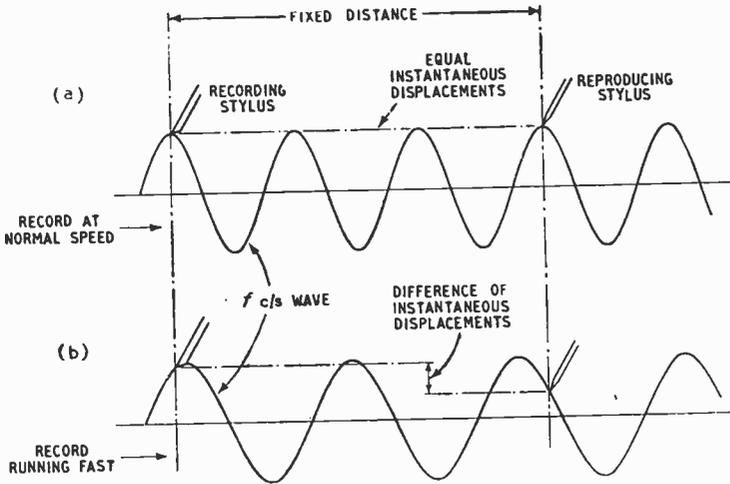

two waves may be calibrated directly in percentage change of speed.

If the phase change exceeds  $\pi$  radians (or  $180^\circ$ ), the output will commence to fall again, and it is not, therefore, possible to deal with phase variations greater than this. For illustration, Fig. 1(b) shows a phase change of about  $280^\circ$  from the peak of the third wave measured from the recorder point, which is the initial condition shown in Fig. 1(a). The meter reading for  $280^\circ$  ( $360^\circ - 80^\circ$ ) would be indistinguishable from that obtained for  $80^\circ$ , and the amount of flutter would therefore be underestimated. This can, however, easily be dealt with by reducing the oscillator frequency, so that the wavelengths become larger, and the phase changes proportionately smaller. For large amplitudes of flutter, therefore, we require a low frequency, and for high sensitivity a high frequency, as equation (8) suggests.

### Radial Tracking Essential

In practice, there remain several difficulties in the method outlined. For example, for a linear relationship between phase angle and percentage speed variation to be maintained, it is essential that the ratio  $D/R$  remains constant, unless readings are always taken at one particular radius. This involves precisely radial tracking of both recording and reproducing heads, which is difficult to achieve, and

which leads to mechanical complications at small radii. Also this method is confined to disc recorders.

It may, however, be extended and rendered almost universal in its application by the substitution of magnetic recording methods. If an annular magnetic track is substituted for the disc record, and the cutting head and reproducer are replaced by a magnetic recording head and replay head, the validity of the method remains unaltered. If, in addition, an erasing head is added, to wipe out the wave after it has passed the replay head, the same piece of track will return fresh and unmodulated under the recording head again and again, while the positions of the various components remain unchanged. With some forms of phase-meter the waveform from the replay head can be allowed to depart considerably from the sinusoidal shape, particularly near the peaks, and it is therefore quite permissible to use d.c. for erasing and for recording bias, with considerable simplification of equipment. A magnetic track may be deposited on the underside of a gramophone turntable, for instance, and the heads mounted below with their gaps arranged radially, and just clear of the track. In order to obtain a strong enough signal in spite of this clearance, the recording head may be heavily overloaded, again because we are indifferent to waveform. This arrangement may

be left *in situ*, and used to monitor the flutter on an attached meter while recording is in progress.

For the measurement of the phase changes in the laboratory, it is sufficient to feed the reproduced output to one input of a double-beam oscilloscope, the other input being fed from the oscillator output, and used to synchronize the time base. Then the difference in phase between the two traces can be read off the screen directly. If the gain of the oscilloscope is turned up so that the wave peaks fall outside the screen area, amplitude variations will be found to be less disturbing. For routine measurements, a phase-meter giving a direct scale reading has been devised, to simplify checking by non-technical operators.

### Sense Discrimination

As so far described, it will no doubt be noticed that there is no discrimination between acceleration and retardation. Both positive and negative speed changes will produce a positive reading on the meter. However, by using a slightly different oscillator frequency, we can arrange that the correct mean speed shows a phase-shift of  $45^\circ$ , instead of zero, and the meter will give a half-scale reading, which can be calibrated as zero fluctuation. Then a slightly lower speed will give a lower reading, and a higher speed a higher reading on the meter, thus showing whether any flutter which may be present represents an acceleration or otherwise.

One of the great advantages of this method is that the sensitivity of the system can be so easily varied, simply by changing the frequency of the applied tone. Further, the magnetic track method is capable of resolving very much smaller deviations than others hitherto used, and its low cost and absence of loading enable it to be fitted to every channel in a commercial recording system, and to be used during actual recording, instead of only as an occasional test.

For film recording, a magnetic

(Continued at foot of following page)

# TELEVISION RADIO RELAY

## London - Birmingham Link

**A** DEMONSTRATION of the London to Birmingham radio-relay link was given on 3rd and 4th Nov. Designed and constructed by the General Electric Co. to a performance specification of the Post Office, the link comprises two terminal stations and four relay stations at Harrow Weald, Dunstable, Blackdown and Rowley Regis. It provides a single-vision channel which can be used in either direction; that is, it can be employed to send a picture from London to Birmingham or from Birmingham to London. When the remaining equipment is installed two reversible channels will be available and then it will be possible to send pictures simultaneously in both directions.

It is claimed that this link is the first television relay link in the world which is installed on a permanent basis and which has been designed throughout with reliability as a prime consideration. Many other television relaying schemes have been tried, but all have been primarily experimental in nature.

In this link all apparatus is duplicated. There are duplicate transmitters, duplicate receivers and duplicate power supplies. In the event of a failure, therefore, the spare can be brought immediately into service with the briefest of interruptions.

The relay stations are un-

attended and are operated by remote control from London or Birmingham. In the event of a major fault in such a station the unit affected is automatically taken out of circuit and replaced by its duplicate. At the same time the terminal stations are automatically notified. The change-over from one unit to another at a relay station can also be carried out at any time by an operator at one of the terminal stations, who has only to press a button to effect the change. Even power failures are allowed for. The relay stations are normally fed from the grid; should the supply fail, a petrol-electric generator is automatically started up and the station is again operating within two minutes!

Because of the great flexibility of control provided, the control circuits are exceedingly complicated and embody some 3,000 relays! The radio side of the equipment almost tends to be buried in the welter of control and indicator equipment—which is a pity, since it is highly ingenious.

Transmission is carried out on about 30cm. Frequencies of 870 Mc/s and 890 Mc/s are used and a change from one to the other is made at each relay station. At the terminal station the v.f. signal, containing frequencies up to 2.7 Mc/s, is used to modulate a 34-Mc/s carrier in frequency, the deviation being  $\pm 1.5$  Mc/s.



A pair of mirrors at a terminal station

The modulated 34-Mc/s carrier varies in frequency between the limits of 32.5 Mc/s and 35.5 Mc/s and after amplification it modulates in amplitude a second carrier of, say, 904 Mc/s. The result is a 904-Mc/s carrier with sidebands centred on  $904 \pm 34 = 938$  Mc/s and 870 Mc/s. The sidebands vary in frequency in accordance with the vision signal over the range of  $\pm 1.5$  Mc/s or 936.5–939.5 Mc/s for one set and 868.5–871.5 Mc/s for the other. Band-pass and band-stop filters allow the 868.5–871.5-Mc/s band to pass to the aerial and prevent the other frequencies from doing so.


### I.F. Amplification

At a relay station the signal on, say, 870 Mc/s is received and passed to a crystal mixer and brought down to 34 Mc/s by the ordinary superheterodyne technique. It is then amplified in a somewhat elaborate i.f. amplifier of 10-Mc/s bandwidth which is provided with a g.c. Then, just as in a terminal station, it is brought back to signal frequency
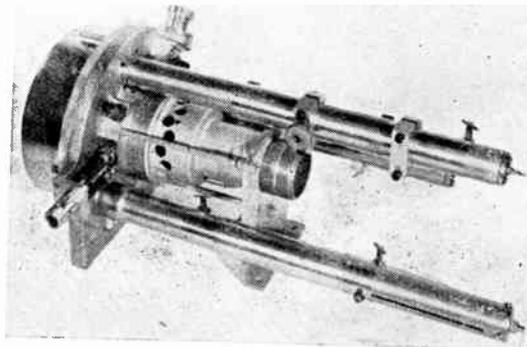
### Measuring Turntable Speed Fluctuations.

(Continued from foot of preceding page) track coated on to the film base allows fluctuations in speed of the film itself to be checked, and forms a valuable tool for the investigation of sprocket ripple.

A disc coated with magnetic material may easily be fitted to the sound drum of film recording systems, and the method is therefore equally applicable to this medium, or in fact to any problem involving the measurement of very small speed fluctuations.



Typical r.f. component.

by modulating an appropriate frequency. If the input is at 870 Mc/s, as in the example, the output is at 890 Mc/s and this can be obtained by modulating a 924-Mc/s carrier. At the next relay, the input is at 890 Mc/s and the output at 870 Mc/s, and so on. The arrangement is sketched in the block diagram.

The locally generated frequencies are derived from a crystal oscillator of high stability and by arranging for both signal frequencies to lie on the same side of the local frequencies, their frequency difference is virtually independent of any drift.


### Station Details

Coaxial circuits are used at signal frequency with triode valves. The transmitter output is 10W and the gain in a relay station is about 70db. Dipole aerials are used with reflectors, some 10ft by 14ft, giving about 28-db gain. The beam width to the half-power points is about 3° in elevation and 5° in azimuth. The reflectors are constructed of light alloy tubing and the tubes contain heating elements for de-icing.

During the demonstrations the relay stations had temporary masts for the aerials and all equipment was at ground level. In the final installation all equipment apart from power supplies will be at the mast head and feeder losses of some 12db at present existing will be eliminated. The final mast-head apparatus for the double link is to be four mirrors, four receivers and four transmitters, the two last being housed in a "room" about 9-ft square. The height of the masts vary from 60ft to 120ft in the different relay stations.

Two items of the equipment deserve especial mention; a filter and a switch. The former is a

combined band-pass and band-stop filter which provides 70-db discrimination between the wanted and unwanted frequencies in the amplitude-modulation process. It is built of co-axial resonant circuits and two of the filters are shown in the photographs. There are three sections to the filter, A, B and C. The long tubes control the band-stop characteristics and relatively very short tubes opposite them control the band-pass characteristics. The sections A and C are alike, but the middle one, B, is of smaller diameter and has one-half the characteristic impedance of the end sections. These tubes have inner conductors; however, the dielectric is not uniform but consists of alternate short sections of air and polythene. By adopting such a series of abrupt discontinuities in the dielectric the length of the section has been reduced from the 10-ft required with air to something like 18in only. Screw "trimmers" are provided at the ends for adjusting the precise characteristics. Similar "trimmers" are also provided on the short tubes controlling the pass-band.

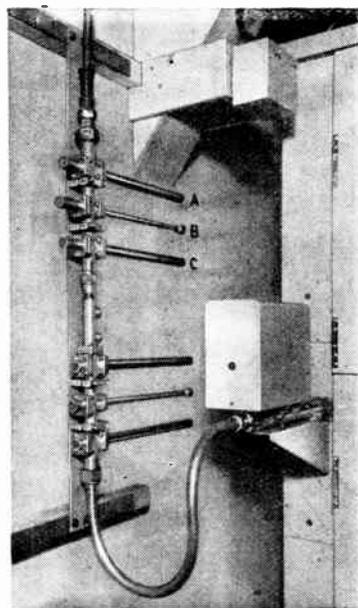

Two combined band-pass and band-stop filters are shown here.

it makes the input impedance tend to zero on the one hand and to infinity on the other. When the impedance is zero the line to which it is attached is short-circuited, whereas when it is infinity the line is unaffected by the stub.


The plungers in the stubs attached to the two lines move in opposite ways so that one line is blocked while the other is opened. Actually, two stubs  $\lambda/4$  apart are used on each line to increase the attenuation in the "closed" line and some 70db is attained.

These "switches" are motor-driven and are used to change over the r.f. sides of the transmitters and receivers. They are used on the one hand to bring the duplicate units into circuit in the event of a fault, and on the other hand, to reverse the aerials to change the direction of transmission. This last feature makes great demands on the switches, as the output of the transmitter and the input of the receiver are necessarily coupled by any leakage through them. Some 70-db attenuation between paths in the switch is obtained and with the special circuitry employed the attenuation between aerials is kept down to 140db.

During the demonstration a
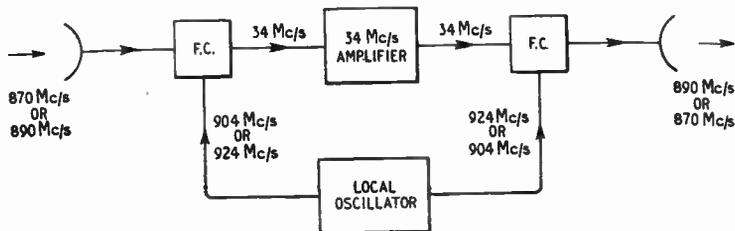
### "Contact-less" Switch

The switch operates at radio frequency to switch the coaxial circuits of the transmitters and receivers. It has no contacts and operates by moving plungers into coaxial stubs. Two input (or output) coaxial lines are T-junctioned to a single outlet (or inlet). At the proper distance from the T on each inlet line a stub is fitted. Now the input impedance of such a stub depends on its length and on its termination. In this case the termination is a movable plunger and in its two extreme positions




This block diagram illustrates the general arrangement of a relay station. The blocks labelled F.C. represent the frequency-changer on the receiving side and the modulation on the transmitting.
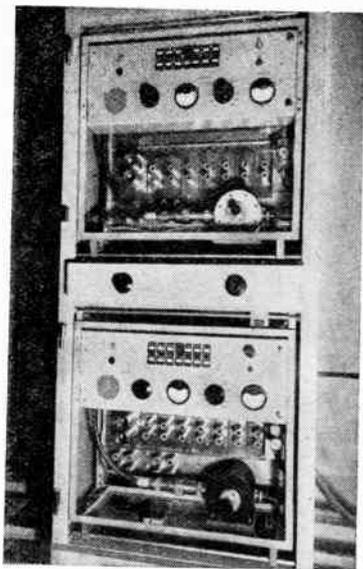
# SHORT-WAVE CONDITIONS

October in Retrospect : Forecast for December

By T. W. BENNINGTON (Engineering Division, B.B.C.)



The receiver and its spare with front covers removed.

picture originating in London was seen on a monitor tube in Birmingham and no visible form of distortion could be detected. The picture was free from noise and interference and the definition was indistinguishable from what one is accustomed to in London. There is no doubt whatever that when Sutton Coldfield relays a London programme, Midland viewers will be under no disadvantage compared with Londoners.

All concerned with the design, development and construction of this link deserve the highest praise for a fine achievement.

## EDUCATIONAL FILM

**Putting Free Electrons to Work,** a ten-minute film produced by Merton Park Studios Ltd. for the British Electrical Development Association, explains the thermionic effect and its application to the radio valve. A diagrammatic illustration is given of how electrons can be made to leave the surface of a conductor; then follows a simple explanation of the diode and triode, using conventional symbols. The photo-electric effect is similarly dealt with, and its application to the photo-electric cell. This film will be lent free, in either 16mm. or 35mm., to any responsible organization, on application to the General Manager and Secretary, British Electrical Development Association, 2 Savoy Hill, London, W.C.2.

**D**URING October the average maximum usable frequencies for these latitudes increased very considerably during the daytime, and decreased somewhat by night. This was in accordance with the normal seasonal trend, though, from the second week of the month onwards, the daytime increase was greater than had been expected. Daytime working frequencies were thus high: those as high as 28 Mc/s, for example, becoming regularly usable over most circuits. Night-time frequencies up to 9 Mc/s were still generally usable.

Sunspot activity was, on the average, slightly higher than during September, a fact which may account, in part, for the high m.u.f.s.

The rate of incidence of Sporadic E did not, as might have been expected, decrease very much compared with the previous month.

October was a very disturbed month, particularly during its latter part. Ionospheric storms, all of them relatively severe, occurred during the periods 5th-9th, 14th-18th, 23rd-26th and 27th-30th. During the latter three of these storms, on the nights 14th-16th, 22nd-24th and 27th, the Aurora

Borealis was widely seen in this country. Sixteen "Dellinger" fade-outs were reported as occurring during the month, the most intense being at 1406 on 2nd, 1318 on 8th, 1148 on 11th and 1145 on 13th.

Long-range tropospheric propagation occurred frequently between 1st and 10th of the month, and particularly on 6th and 7th, when Eiffel Tower television was widely received in southern England.


**Forecast.** — Day-time m.u.f.s in these latitudes during December should be somewhat lower than during November. This decrease is a usual feature at the extreme mid-

winter period, and it may, perhaps, be accentuated by decreasing sunspot activity. Night-time m.u.f.s should also decrease to their lowest winter values.

Long-distance working frequencies will still be relatively high by day, and those as high as 28 Mc/s should be regularly usable over most, but not all, circuits at the appropriate time of day, among which should be that to the eastern part of North America. At night only the lower short-wave frequencies will be generally usable, 7 Mc/s being about the highest regularly usable frequency for most circuits.

Ionospheric storms, though not usually particularly frequent during December, are apt to be troublesome after dark, because of the already low ionization prevailing during the winter night. At the time of writing it would appear that such disturbances are most likely to occur within the periods 1st-4th, 7th-9th, 16th-17th, 21st-22nd and 27th-30th.

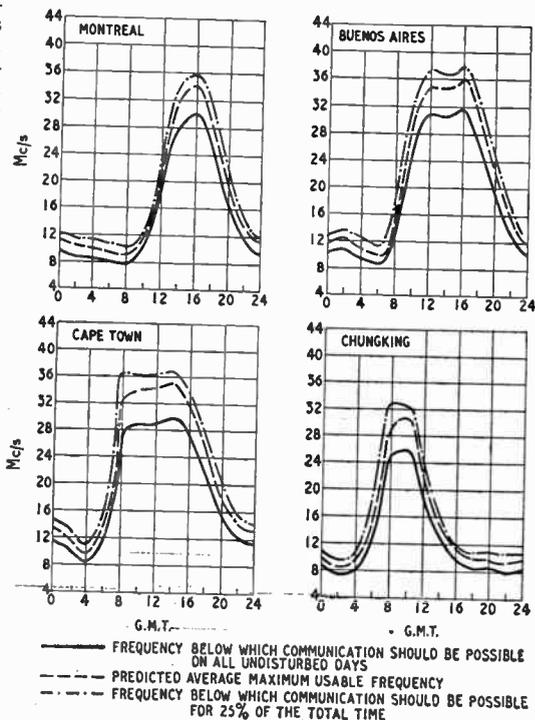The accompanying curves indicate the highest frequencies likely to be usable over four long-distance circuits.



# AT LAST— BETTER ALL-DRY MINIATURES

**1R5**  
Heptode Frequency  
Changer

**1S4**  
Battery Beam Tetrode

**1S5**  
Battery Diode Pentode

**3S4**  
Battery Beam Tetrode


**1T4**  
Battery Pent. Vari-Mu

**3V4**  
Battery Beam Tetrode

Type Number	Application	Heater		Anode Voltage Normal	Screen Voltage Normal	Grid Voltage Normal	Anode Current mA	Screen Current mA	Impedance Ohms	Mutual Conductance mA/V	Optimum Load Ohms	Power Output Watt
		Volts	Amps.									
1T4	Batt. Pent. Vari-Mu	1.4	0.05	90	67.5	0/-16	3.5	1.4	500,000	0.9	—	—
1R5	Heptode F.C.	1.4	0.05	90	67.5	0/-14	1.6	3.2	600,000	300*	—	—
1S4	Batt. Beam Tetrode	1.4	0.1	90	67.5	-7	7.4	1.4	100,000	1.58	8000	0.27
1S5	Batt. Diode Pentode	1.4	0.05	90	67.5	0	1.6	0.4	600,000	0.63	—	—
3S4	Batt. Beam Tetrode	1.4 2.8	0.1 0.05	90	67.5	-7	7.4	1.4	100,000	1.58	8000	0.27
3V4	Batt. Beam Tetrode	1.4 2.8	0.1 0.05	90	90	-4.5	9.5	2.1	100,000	2.15	10000	0.27

\* Conversion Conductance in Micromhos.

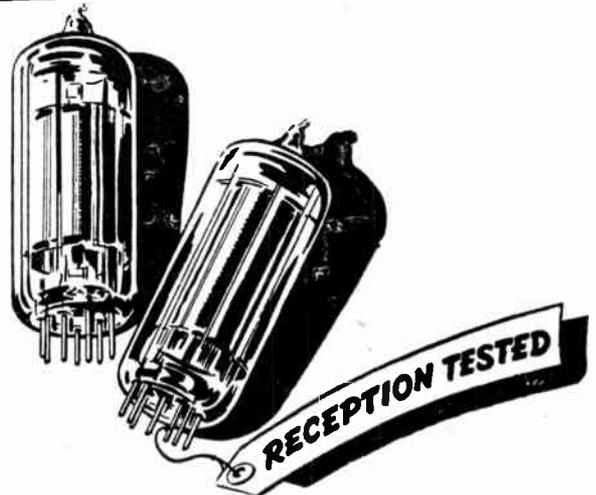**G**REATLY advanced engineering techniques have enabled us to produce *ALL-DRY* Miniatures that are better in every way. Every valve is individually **RECEPTION TESTED** and bears this identifiable seal. *BRIMAR ALL-DRY* Miniatures are suitable for every modern All-Dry Portable. Full details of their characteristics are shown in the table above.



**BRIMAR**  
ALL-DRY MINIATURES

**STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.**



## A new approach to "High Fidelity"...

and the coming of "New-True Fidelity"

PERHAPS no phrase in sound reproduction has been more loosely used in the past than "high fidelity." What some people would term high-fidelity reproduction caused others to shake their head. Obviously, ideas and ideals of fidelity were measured by differing standards. What, then, is "true fidelity"? Fortunately, this can accurately be measured and graphically expressed, but we have to seek the assistance of a very critical science—that of acoustics—which provides objective rather than subjective answers.

Here we are concerned more particularly with the reproduction of sound via an electrical pick-up. The authority of acoustic science has laid down a performance which it regards as ideal, but naturally, one that is unconcerned with the practical limitations which beset the manufacturer. For matters of cost and usage are no concern of the theorist. Indeed, the manufacturer could produce a pick-up with the approved ideal response, but such an instrument might cost, say, twenty-five guineas; and again it is conceivable that it would be so fragile as to preclude its use in the home. Further, even given a pick-up with the ideal response, and built on the most robust lines, its actual reproduction is still limited by the characteristics of commercial recordings. A practical pick-up must be capable of being used with a wide range of equipment, each item of which has its own idiosyncrasies. So the manufacturers' problems multiply, and a compromise of some kind is necessary.

### The Quest . . .

A year ago, however, after long experience in the design and mass production of pick-ups, Cosmocord Limited were convinced that an entirely new approach was essential. The easy way might have been to set a new, good, practical standard and say "This is high fidelity, and you ought to like it."

But the honest approach starts the other way round, viewing everything from the users point of view and the while, stimulating research at every step. That was the Cosmocord way.

### And the Conclusions . . .

The most important conclusions were:

- (1) That the average user does not want to spend time and money finding suitable equalising networks, etc. The pick-up must be a success from the word "go."
- (2) he wants his records to last—the pick-up must, therefore, cause the minimum possible wear.
- (3) he wants the pick-up to be robust enough to withstand even the most careless of handling.
- (4) and lastly, he wants the pick-up at a price he can afford.

Moreover, defects such as high tone-arm resonance, high needle-tip impedance and high tracking weight, excessive needle talk, reproduction of motor rumble and tracing distortion in the upper register, all these must be eliminated. So with these considerations in mind *acos* research set about developing the ideal pick-up—and the result is the GP.20.

### Stage by Stage Achievement

First the stiffness of the assembly was reduced until the pick-up satisfactorily tracked commercial records at seven grams. Then, because warped records or badly aligned turntables and badly sprung motors might cause the pick-up to jump grooves, the tracking weight was deliberately increased to 13-14 grams. This extremely low needle pressure, coupled with the use of a flexible, sprung permanent sapphire stylus, reduces record wear to an absolute minimum, thus ensuring vastly longer life to records. Further, this flexibility of the assembly makes the unit virtually damage-proof.

Needle talk, tracing distortion and distortion due to "pinch effect," were greatly reduced by increasing the vertical compliance of the assembly until it was little less than the lateral compliance. The outstandingly good frequency-response was achieved by making the crystal assembly appear as a terminated mechanical transmission line, and arranging that the terminating section would give pre-emphasis of approximately 6 db per octave above 1,000 cps. This resulted in the working pick-up characteristic from commercial recordings (turn over at 250 cps) being substantially flat from 20 to 250 cps, dropping approximately 6 db between 250 and 1,000 cps, and flat beyond that frequency up to 9 Kcs, the response falling above this frequency.

The pre-emphasis between 250 and 1,000 cps provides an automatic bass boost, *eliminating equalising circuits of any kind.* The frequency response was set flat to 9,000 cps, as being completely adequate to give the best reproduction from commercial records.

The output of the GP.20 is more than half a volt at 1,000 cps, and sufficient to load fully any domestic set or amplifier.

The tone-arm design is unique in that it is supported on a single needle point, thereby reducing lateral and vertical friction to the barest possible minimum. Torsional arm resonance is eliminated.

### Finally—the Cost . . .

Last, but not least, is the cost. The list price of the GP.20 in Great Britain is 50s. plus 21s. 5d. purchase tax. So *acos* research and *acos* mass production techniques, utilising the most efficient piezo-electric assembly, have produced an instrument comparable in price with ordinary pick-ups, but with a laboratory performance. Indeed a justification of the new approach to "high fidelity" reproduction, since it produced the GP.20 and achieved what we like to term "New-true Fidelity"—for that, assuredly, it provides

COSMOCORD LIMITED • ENFIELD • MIDDLESEX

# HIGH-QUALITY AMPLIFIER : New Version

(Continued from page 427 of November issue)

## Design for a Radio Feeder Unit

By D. T. N. WILLIAMSON

(Ferranti Research Laboratories)


THE preceding articles in this series have described amplifier, tone compensation and gramophone pre-amplifier units which are capable of driving a loudspeaker from the output of a pickup or a radio receiver. The design of a radio receiver which would be suitable for use under the varied reception conditions which exist in the populous parts of the country, and which at the same time could be constructed simply and with certainty of results, would be a difficult undertaking. In addition, such a receiver would be unnecessarily

complex for the needs of that section of the community which lives within the primary service area of high-powered twin-wave transmitters, and which desires only to receive transmissions from these by the simplest possible means.

In order that the units described in the series should form a complete domestic sound installation, it is proposed to outline the design of a small two-stage receiver suit-

able for the reception of medium-wave transmissions within the primary service area. The type of receiver to be described gives satisfactory results where the spacing between the carrier frequencies of the principal transmitters is high, say 200 kc/s. It is not suitable for use in districts where closely-spaced powerful transmissions exist, or where interference is severe. The receiver circuit is offered as an indication of the general lines on which to proceed, and is capable of being adapted to individual requirements and conditions.

Fig. 20. Circuit diagram of local station radio receiver. Positions of selector switches for pre-set tuning shown at X.

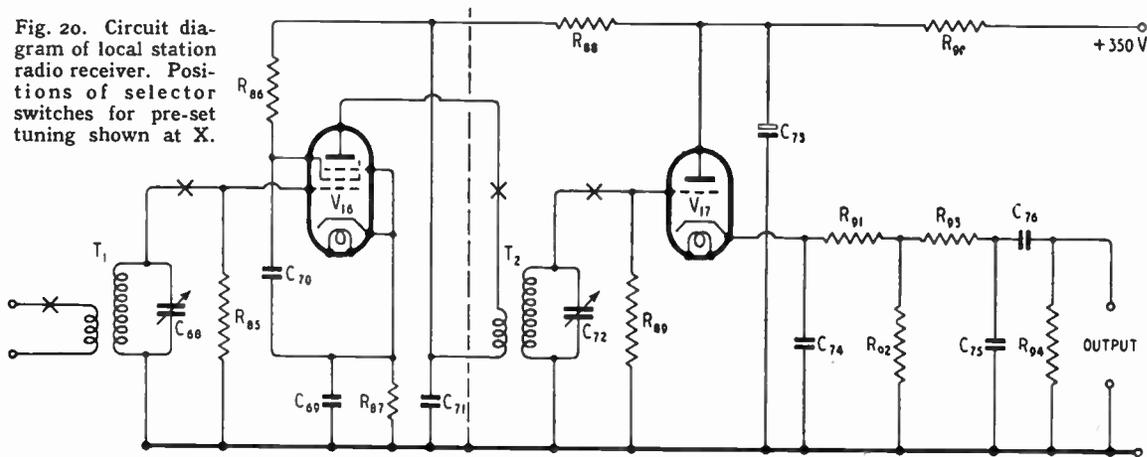

### COMPONENT VALUES FOR CIRCUIT OF FIG. 20

Component	Value	Rating	Type	Rating (V d.c. working)
R <sub>85</sub>	0.1 MΩ			
R <sub>86</sub>	0.1 MΩ	½ W		
R <sub>87</sub>	330 Ω			
R <sub>88</sub>	1.5 kΩ			
R <sub>89</sub>	0.1 MΩ	2 W		
R <sub>90</sub>	10 kΩ			
R <sub>91</sub>	47 kΩ			
R <sub>92</sub>	4.7 kΩ			
R <sub>93</sub>	22 kΩ			
R <sub>94</sub>	2.2 MΩ			
C <sub>68, 72</sub>	See text			
C <sub>69</sub>	0.1 μF		Paper	250
C <sub>70</sub>	0.1 μF		Paper	350
C <sub>71</sub>	0.1 μF		Paper	350
C <sub>73</sub>	10 μF		Electrolytic	450
C <sub>74</sub>	100 pF		Silvered mica	
C <sub>75</sub>	100 pF		Silvered mica	
C <sub>76</sub>	0.1 μF		Paper	500

All resistors may be ½ W rating, tolerance 20 per cent unless otherwise specified.

#### VALVES.

V<sub>16</sub> Mullard EF39, Osram KTW61. V<sub>17</sub> Mullard EF37.

**High-Quality Amplifier—**

The basic circuit, shown in Fig. 20, consists of an r.f. amplifier, transformer-coupled to a negative-feedback detector. Circuit values for a number of alternative tuning arrangements are given. Possibly the simplest scheme, from the point of view of construction, is to use a twin-ganged capacitor to cover the range, although by this method it is not easy to secure a uniformly good performance at each end of the medium-wave band. Alternatively the receiver may be pre-tuned, stations being selected by a push-button or rotary switch. The use of variable inductors in this arrangement provides a simple method of achieving a uniform selectivity and sensitivity over the range, with the disadvantage that two coils or tuned circuits must be provided for each station to be received. In the unlikely event of serious thermal drift, correction is easily applied by the use of negative temperature coefficient capacitors.

**R.F. Transformers.**—Winding data are given to enable r.f. transformers to be wound simply on standard formers without the use of a wave-winding machine. The correct number of turns are pile-wound in a random manner between thin Paxolin or cardboard cheeks, which serve to guide and support the edges of the winding. This gives an approximation to the performance of a wave-wound coil.

The table gives winding data for transformers to be used with a twin-ganged capacitor with a capacitance swing of 485 pF with trimmers, covering a frequency

Transformer	Winding	No. of turns	Inductance ( $\mu$ H)	Coefficient of coupling (approx.)
Aerial	Primary	35	30	0.35
	Secondary	95	160	
Coupling	Primary	60	80	0.65
	Secondary	95	160	

range of approximately 550-1,550 kc/s.

When separately-switched tuned transformers are to be used, the values of secondary inductance and tuning capacitance may be read from the curve of Fig. 21 against transmitter frequency. This curve has been computed for an L/C ratio of unity (L in  $\mu$ H, C in pF), which is nearly optimum. The number of turns necessary to produce the required inductance with the formers and dust-cores specified may then be obtained from Fig. 22. The dimensions of the coil formers and windings are shown in Fig. 23. When the capacitance is being chosen, allowance should be made for strays, which will probably be about 25 pF. The values used should therefore be less than those indicated by this amount. In practice the nearest standard value should be chosen, and allowance made in the value of inductance. Movement of the core will enable a variation of approxi-

mately  $\pm 18$  per cent to be made in the inductance.

**Construction.**—In order to preserve stability, precautions must be observed when constructing the receiver. The most likely cause of instability is the presence of undue stray capacitance between the anode and control grid of V<sub>16</sub>. The valve types used have an anode-grid capacitance of less than 0.003 pF, and a layout should be chosen which does not materially increase this figure. The design, based on this value, has a factor of safety of about 4. Although the valve is metallized, a screening can may be necessary to reduce leakage to the valve base. All

Fig. 21 (Below). Curve relating tuned circuit parameters and resonance frequency.



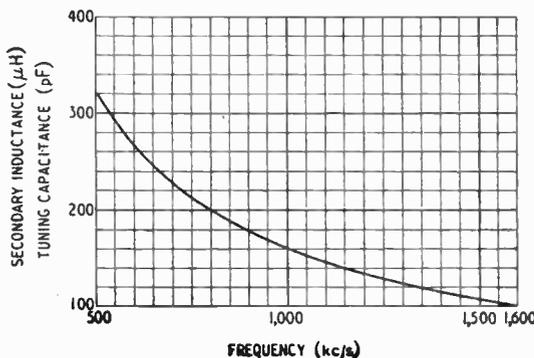
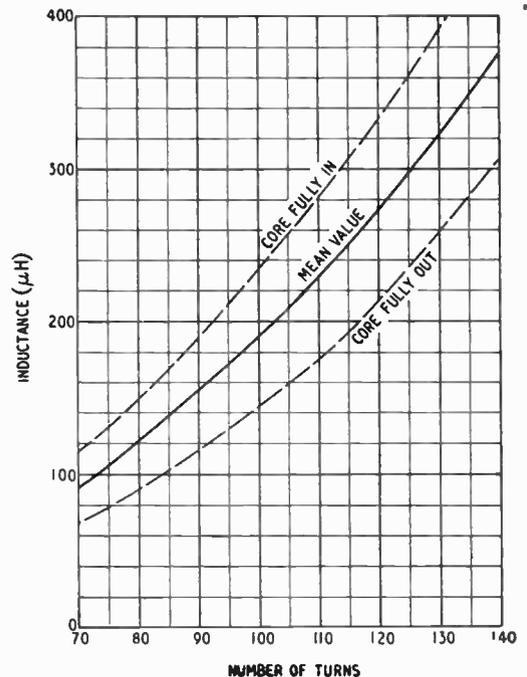


Fig. 22. Curve relating inductance and number of turns for windings discussed in text.

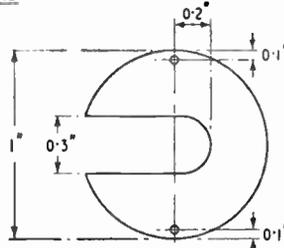


COIL FORMERS

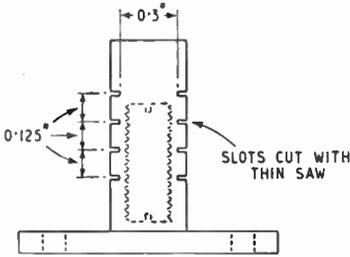


MATERIAL; 0.015" BAKELIZED FABRIC OR FAXOLIN

AERIAL TRANSFORMER

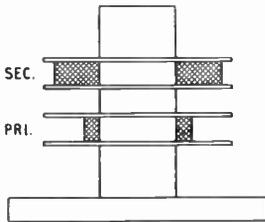

COUPLING TRANSFORMER


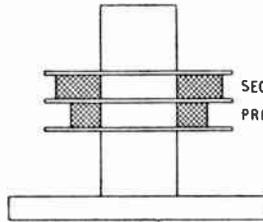


DATA FOR FIXED TUNING

- PRIMARY WINDING. (DIRECT AERIAL CONNECTION)  
1/3 NUMBER OF SECONDARY TURNS
- PRIMARY WINDING. (70Ω FEEDER)  
1/10 NUMBER OF SECONDARY TURNS
- SECONDARY WINDING. SEE TEXT

- PRIMARY WINDING.  
2/3 NUMBER OF SECONDARY TURNS
- SECONDARY WINDING. SEE TEXT

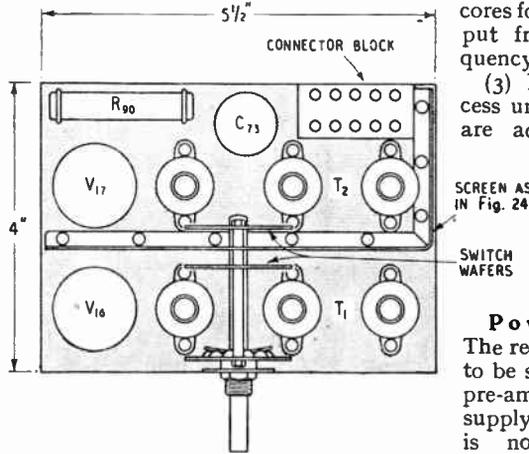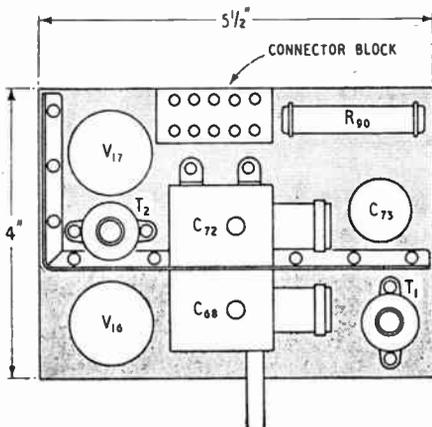components in the grid circuit should be kept above the chassis, and all components in the anode circuit below the chassis. Where components in the anode circuit, or in the following grid circuit must be brought above the chassis, as is the case when tuning is by means of a ganged capacitor, they



ALUMINIUM OR COPPER SCREEN EXTENDING BELOW CHASSIS AND 3/4" ABOVE CHASSIS WITH CUTOUT FOR GANGED CAPACITOR

CHASSIS 1/2" DEEP

Fig. 24. This diagram shows a plan view of top of chassis.

Fig. 23. Formers are standard moulded type, fitted with 8-mm threaded iron-dust cores. All coils are wound with Litz wire consisting of 7-9 strands of 45-48 s.w.g. enamelled copper wire.

must be screened carefully from the aerial circuits. Figs. 24 and 25 show suggested layouts for continuously variable and switched tuning arrangements.

**The Detector.**—To give low distortion, the detector requires to work at a fairly high signal level—say 5V r.m.s. output. As the receiver is intended to feed the tone compensation unit, which requires an input of only 200 mV peak, the output is taken from a tapping on the detector load resistance. This greatly reduces the a.c. loading on the detector and enables it to handle high modulation levels without distortion.

**Alignment Procedure.**—(1) Set ganged capacitor at a position about five degrees from the minimum capacitance end, and adjust trimmers for maximum output from the high-frequency 3rd Programme.

(2) Set capacitor about twenty degrees from maximum capacitance position and adjust dust-cores for maximum output from the low-frequency 3rd Programme.

(3) Repeat this process until both stations are accurately tuned.

Fig. 25. Plan view of top of chassis. Switched model.


**Power Supplies.**

—The receiver is intended to be supplied from the pre-amplifier power supply. The decoupling is not adequate to enable it to be fed from the main amplifier supply.

**Acknowledgment.** — The writer is indebted to Mr. A. T. Shephard of Ferranti, Ltd., for his assistance in the compilation of data for these notes.

**Note:** In the list of components below Fig. 15, page 424, of the November issue, the value of R69 should be 1 MΩ, not 0.47 MΩ. C56 should be 0.5 μF paper, 250 V d.c. working, ±20 per cent; C57, 50 μF, electrolytic, 12 V d.c. working, C64, 16 μF, electrolytic, 450 V working.

## TEST REPORT

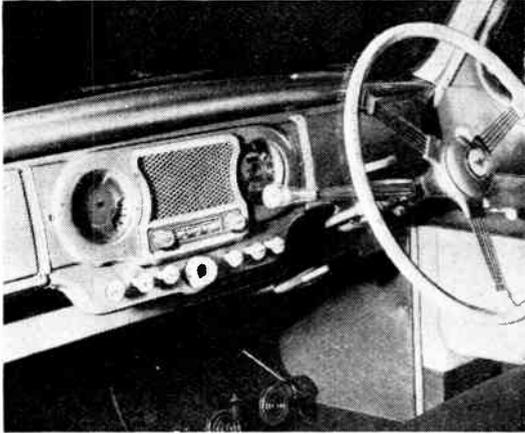

**D**ESIGNED primarily for the overseas motorist this car radio receiver is an eight-valve superheterodyne possessing a number of quite unusual features. Not the least is the exceptional wide range of wavelengths it covers, not necessarily continuously since no useful purpose would be gained, but by a judicious selection of the principal broadcast bands a coverage of from 19 metres to 1,800 metres is provided. Reception on the long waveband is, however, limited to a single pre-set station, but the user can choose which station he prefers.

### Bandspread

Tuning is not critical on any waveband, as the short wave ranges are, with one exception, restricted in coverage to a band of frequencies actually less than that on the normal medium waveband. Five free tuning ranges and four pre-set stations are selected by a nine-way rotary switch, which actuates a drum dial having the various ranges marked on it in megacycles as well as indicating which of the pre-set circuits are in use. The waveband table shows the sequence in which they appear, the ranges provided and their limits, also the actual coverage of each in kilocycles. The equivalent wavelengths in metres are included also.

While the three shortest wavebands have a very small coverage, the fourth, which is marked

"SW" on the dial, covers 40 to 90 metres (3.3 to 7.4 Mc/s) approximately. Broadcast stations are so widely scattered throughout this part of the short wave band that it would be extremely difficult, if not impossible, to select any one portion and bandspread it into a coverage of, say, 1,000 kc/s or less and take in all the stations likely to be required in various parts of the world.

Of the four pre-set positions one is for a long wave station and three are in the medium waveband. The positions on the dial are indicated in two ways; one is by an arrow-head pointing to a station name plate, the other by a small figure, 1 to 4 inclusive, which appears on the extreme right of the dial. These numbers correspond to similar numbers marked against the four pre-set adjustments on the receiver unit, being provided to act as a guide should it be required to change the pre-set stations at any time.

# EKCO MODEL CR61

## All-wave Car Radio with Permeability Tuning


Ekco model CR61, all-wave set fitted in the Austin Hampshire saloon. The loudspeaker grille is immediately above the tuning head.

The equipment is divided into four main units, the receiver, power unit, tuning head and loud-speaker. The use of two, or more, loudspeakers is quite feasible with this receiver and, indeed, the makers actually recommend it where facilities allow as a speaker in the back of the car is a great boon to rear-seat passengers. The set is well able to take the extra load as it gives about 4 watts output.
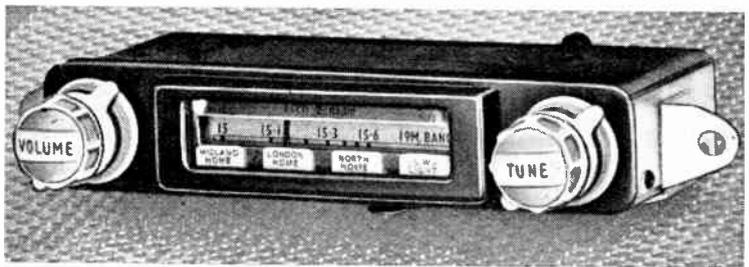
### The Circuit

The various units can be mounted separately or joined together to form a coherent whole of very compact form. When the items are separated it becomes necessary to mount the receiver and tuning head in reasonable juxtaposition as they are interconnected by shafts with flexible couplings. A considerable latitude is, however, possible in regard to their relative positions.

Eight valves of the latest all-glass type are used in the set which has an EAF42 r.f. amplifier, EC1142 frequency changer, EAF42 i.f. amplifier on 465 kc/s, and EAF42 functioning as detector, a.g.c. and first a.f. amplifier, EA50 noise limiter and a pair of EL42s in push-pull for the output stage. The eighth valve is an EZ41 rectifier which is in the



Close-up of the tuning head with the 19-m scale on the drum dial showing and below the four pre-set station name plates. Note the two sets of concentric controls.

power unit and provides h.t. in conjunction with a vibrator and transformer. The l.t. consumption is 3.4A at 12 volts. On a 6-volt supply it is 5.6A.

An interesting departure from the more orthodox practice is the use of permeability tuning for the variable, as well as for the pre-set, circuits. These are quite independent, being separate sub-assemblies and apart from other considerations the separate circuits help to lessen the risk of complete failure of the radio as it is possible for a defect to appear in one unit without putting the set entirely out of action. Either free tuning or pre-set operation would be available.

### Permeability Tuning

The free tuning system consists of six coils mounted in a screening box with six dust iron cores mounted on a carrier driven by a spindle, which is linked by shaft and flexible coupler to the tuning knob on the remote control unit. These six coils form the primary tuning elements of the receiver. One set of three is for medium wave tuning of the r.f., f.c., and oscillator, the remaining three being brought into circuit by the waveband switch initially for the 40- to 90-metre band (3.3 to 7.4 Mc/s) and subsequently as the tuning system for all the other short wave bands. As the switch is moved from one short wave position to another it switches loading coils in parallel with these primary circuits and as the variable elements of the tuned circuits are a part only of the total circuit inductances the coverages on the 19-m, 25-m and 31-m bands are restricted to the amounts given in the table.

Orthodox practice is adopted for the i.f. and noise limiter stages and these need no comment. A combined diode and r.f. pentode valve is unusual for the detector and first a.f. stage, but as a.g.c. is applied to the pentode portion a valve with variable-mu characteristics is needed.

Resistance-capacitance coupling links the a.f. amplifier with the push-pull output stage and an interesting feature of this part of the circuit is that one of the push-pull valves serves as a phase inverter for the other. A resistor of

WAVEBAND TABLES

Waveband	Frequency limits	Wavelength (approx.)	Coverage
19-metre	15.0 to 15.6 Mc/s	20 to 19.2 met.	600 kc/s
25-metre	11.6 to 12.3 Mc/s	25.8 to 24.4 met.	900 kc/s
31-metre	9.3 to 10.1 Mc/s	32.3 to 29.7 met.	800 kc/s
sw band	3.3 to 7.4 Mc/s	91 to 40.6 met.	4,100 kc/s
med. waveband	515 to 1,640 kc/s	583 to 183 met.	1,125 kc/s
Pre-set 1	1,000 to 1,540 kc/s		
Pre-set 2	790 to 1,220 kc/s		
Pre-set 3	550 to 880 kc/s		
Pre-set 4	167 to 245 kc/s		

1.8kΩ is included in the screen grid supply to one of the valves and this electrode is coupled via a 0.01-μF capacitor, to the input grid of the second push-pull valve. Signal voltages on the screen grid of the first valve being of opposite phase to those on its input grid gives the necessary phase inversion and it is only necessary to select component values that provide the required amplitude of signal to preserve the balance in the stage.

### Tone Control


Another interesting feature is the tone control system which is obtained by modifying the negative feedback circuit linking the anode of one output valve to the anode of the first a.f. amplifier.

Normally there is a fixed

amount of feedback via a 3.3 MΩ resistor and this is augmented by extra feedback applied over a frequency discriminating network that favours the upper register. A simple three-way switch, located in the tuning head, controls the amount fed back over this network.

In general a preponderance of treble is not unwelcome in a car as the rather confined space is inclined to over-emphasize the low notes. Possibly opinions will differ on this matter, but the range of control provided is quite sufficient to satisfy all tastes.

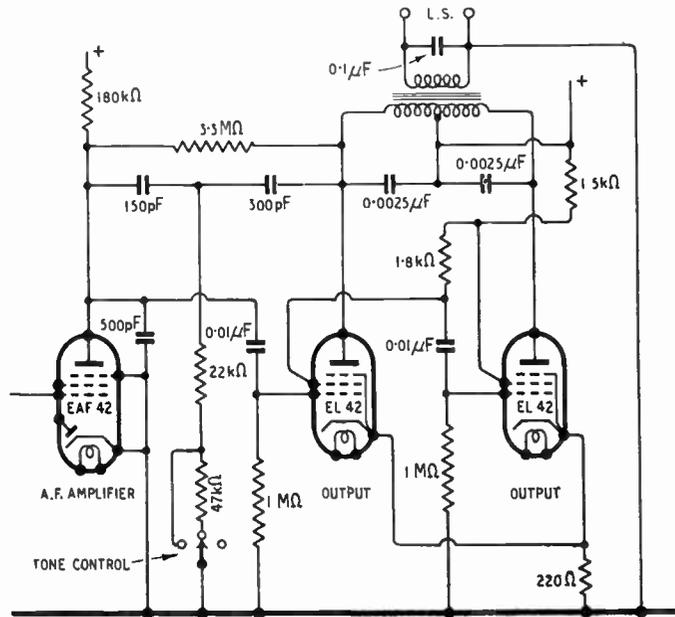The road test was made with a CR61 fitted in an Austin A70 Hampshire saloon. As shown in the illustration the tuning head and loudspeaker form an integral part of the instrument panel as in



Phase inverting output stage with negative feedback tone control used in the CR61 receiver.

**Ekco Model CR61—**

this case the fitting was carried out on the Austin production line. A telescopic aerial is mounted in an insulating bush just ahead of the near-side front screen pillar, its position being such that it is almost invisible from the driving seat and does not interrupt the view of the road.

On each side of the scale window in the tuning head are two concentric controls, the outer one on the right being for free tuning and its inner one is the three-position tone control. Of the left-hand pair the outer is a combined volume control and on-off switch, while its companion is the waveband switch.

Concentric controls are often a little awkward to manipulate unless one is very much larger than the other, but in this set the problem has been tackled in two ways. First, the inner controls are slightly larger, and secondly, they have two ears, which not only assist their operation but makes them easily distinguishable by feel, and is a great advantage for night driving.

As the suppression of interference is now well understood it is, perhaps, redundant to comment on the absence of interference by the ignition and the electrical accessory circuits. If the receiver be tuned to a blank spot on the dial then a faint background of engine noise is discernible and it

is just possible to hear the screen-wiper motor.

At times a little interference was noticed from passing lorries, buses and tramway cars, but in general, private cars caused surprisingly little interference. It may be that many private owners have fitted suppressors, but there is also the possibility that the anti-interference filters used in the CR61 contribute more than is realized to the suppression of interference picked up by the aerial.

**Performance**

Sensitivity and selectivity of the receiver are more than adequate for all normal requirements. On the road between London and the South Coast the main B.B.C.'s medium-wave stations were received with volume to spare, the Midland station, for example, providing an exceptionally good signal. The Light programme on 1,149 kc/s, which is often a little elusive on the South Coast at sea level, was received at good strength at all hours.

In the dense traffic of London Continental stations were well in evidence, but away from the Metropolis, especially on high ground, they were almost predominant. Judged on this basis there should be no difficulty in receiving the B.B.C.'s medium-wave stations almost anywhere on the Continent.

Turning to the short waves, all


four bands provided a plethora of signals, and the difficulty was not finding something to listen to, but in identifying those that were receivable.

On these bands the effect of fading began to be noticed, but through no defect in the a.g.c. system, which behaved as well as could be expected in the circumstances. A.g.c. is impotent when signals fade to almost inaudibility, but it did operate very well indeed on the rapid "flutter" type of fading encountered on the short waves. The flutter was, of course, audible by rise and fall of background noise, but taken by and large the signal remained reasonably steady.

The action of a.g.c. often became apparent on medium-wave stations when passing under bridges, between tall buildings and through avenues of trees, but during the whole of the test no single instance was recorded when a signal, normally of good programme value, was lost due to inadequate sensitivity or a.g.c. action.

Not the least important of the short-wave performance was the steadiness of the local oscillator after the receiver had reached its normal operating temperature. The bandspread tuning on the three shortest ranges undoubtedly contributes largely to the absence of drift, but even on the non-bandspread range of 3.3 to 7.4 Mc/s very little adjustment to tuning was needed. Incidentally, broadcast is not the only form of entertainment this Ekco set provides, as, if one's inclination leans towards amateur radio, the 3.3-7.4 Mc/s range offers a little diversion. On one occasion on the South Coast we overheard a two-way contact between a London and a Manchester amateur on the 40-metre band, both stations being strong enough to need toning down a little with the volume control.

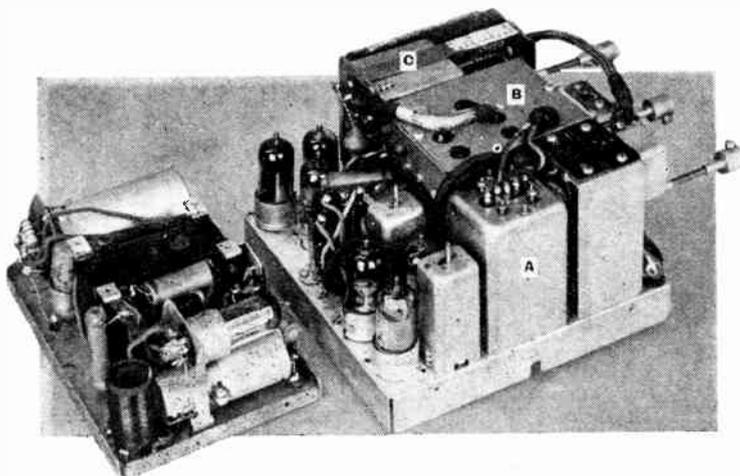The Ekco CR61 all-wave car radio receiver is, with good justification, termed a "luxury" model by the makers (E. K. Cole, Ltd., Southend-on-Sea, Essex). It is intended especially, though not exclusively, for the overseas motorist. The price of the set is £34 13s (exclusive of accessories), plus £7 10s 2d purchase tax on home sales.




Receiver and power units removed from their cases. The pre-set tuning coils (A), waveband switching and loading coils (B) and the primary tuning circuit (C) are contained in separate sub-assemblies on the receiver chassis.

# THE "BELLING-LEE" PAGE

## Providing technical information, service and advice in relation to our products and the suppression of electrical interference
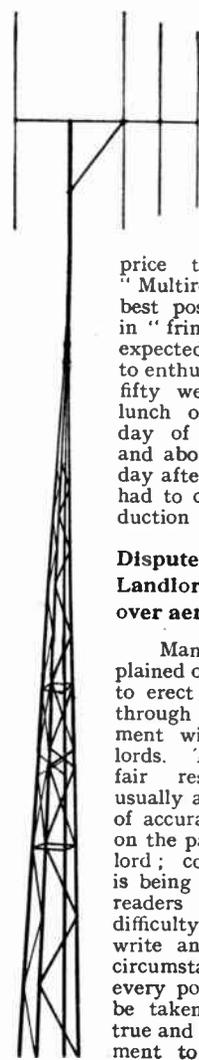
### Radiolympia Notes, Prices, etc.

The public and trade demonstrated their confidence and interest in "Belling-Lee" aerials at Radiolympia by continually surrounding our stand and we have learnt a great deal from their questions; number one outstanding item that is called to mind is the agreeable surprise registered by many visitors on hearing (a) the prices of aerials and (b) the cost of installations. Most of the people to whom the writer spoke, expected higher prices.



Number two is the interest in "fringe area" reception, and a surprising number of people think ten guineas plus the cost of a pole and erection is a very reasonable price to ask for a "Multirod" \*1 to give best possible reception in "fringe areas." We expected to sell a few to enthusiasts, but when fifty were sold before lunch on the opening day of the exhibition and about a hundred a day afterwards we have had to change our production arrangements.

### Disputes between Landlord and Tenant over aerials.

Many visitors complained of their inability to erect outside aerials through lack of agreement with their landlords. This is an unfair restriction, and usually arises from lack of accurate information on the part of the landlord; concerted action is being taken. If any readers are in this difficulty, do please write and give us the circumstances, when every possible step will be taken to present a true and unbiased statement to the landlord.

When the location is within eight to ten miles of a transmitter and interference is not severe it is likely that either a "Veerod," "Doorod" or "Viewflex" \*2 will serve adequately. All these are indoor types.

### Unsuitable aerial recommendations.

We have recorded some black marks; one is, a customer who lives within two miles of Alexandra Palace and whose dealer refused to guarantee satisfaction unless an "H" type "Viewrod" was installed; aerial plus installation costing twelve pounds. The customer was swamped with signal and had to be told to go back to the dealer and ask that an attenuator be fitted. Such an erection could only be justified if there was some **extraordinarily virulent** interference behind the aerial and in a straight line with the transmitter. Another is when a dealer was stated to have fitted "Doorods" by the "dozen" eight to ten miles from the transmitter, apparently without due regard to peculiarities of individual locations. This is unfair to the "Doorod," nor is the dealer being fair to his own reputation or to the receiver manufacturer. When asked if one could guarantee a "Doorod" or "Viewflex" within a few miles of a transmitter our general reply was that we could guarantee to position **any indoor aerial** (in relation to pipework, etc.) so that **little or no signal** could be picked up, but that these aerials should give every satisfaction if carefully sited and where interference is not too severe.

### Suppression and indoor broadcast aerials.

Many questions were asked about suppression: the first reply invariably went back in the form of another question; what aerial is being used? It is rarely worthwhile doing much about suppression unless at least part of the aerial is outside and standing away from the house. Such aerials are the "Winrod" and "Twinrod" \*3. It is not much use fitting a set lead suppressor when the only aerial is round the picture rail or under the carpet.

### The Post Office Exhibit.

We are indebted to the General Post Office for telling our story so very much better than we could ourselves. Of course we are "shareholders" and they are always most co-operative. We were particularly impressed by their model house, and by their demonstration of suppression of interference from motor car ignition systems. The motor car is the one really severe form of interference that is everywhere spoiling television, and actually hindering the sale of television receivers in towns over thirty miles from a transmitter. The trouble can be cured in 97 per cent of cases (independent statistics) for 1/6 per car.

### Motor ignition interference.

Surely your neighbours and tradesmen with vans would co-operate. It does not take a minute and does not affect the engine. A car with car radio has already been treated, so this covers most police cars, and army fighting vehicles.

Many public utility services and operators of large fleets of vehicles are co-operating. Are your local taxis suppressed? If you have neighbours with un-suppressed motor cars, you can obtain from us, or from the Television Society a few "courtesy" leaflets for distribution among them explaining the matter. It might be well worthwhile. The suppressors are usually obtainable from your radio dealer or garage.

### Types and Prices

\*1 "Multirod" with 9ft mast.  
£10/10/-. See illustration.

\*2 "Veerod" attic aerial, 25/-.

Twin. Coax.

"Doorod" indoor  
T.V. aerial .. 26/6 30/-

"Viewflex" all flex-  
ible dipole .. 17/6 21/-

\*3 "Twinrod" dual  
purpose aerial .. 29/- 32/6

Registration and patents applied for.

**BELLING & LEE LTD**  
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDD., ENGLAND



# Stentorian

## CONCENTRIC DUPLEX

A new quality speaker for the enthusiast

This twin "quality" reproducer, incorporating two independent speakers, is the latest application of the now well-known 'Series gap' magnet system, originated by W.B. engineers.


The centre pole is hollow, and forms the beginning of the pressure horn which loads the convex high-frequency diaphragm at the rear. In front this pole piece is surrounded by a separate gap, in which the low-frequency speech coil operates. The speaker should not be confused with the double-cone type.

There is no cross modulation, and the range very evenly covered (especially if a cross-over network is used) is from 50 to 14,000 c.p.s.

Although suitable for outputs up to 6 watts only, this small speaker is nevertheless a high-fidelity reproducer in the best sense of the word. You should try it.

**PRICE £6-6-0**  
complete with matching transformer and filter condenser.

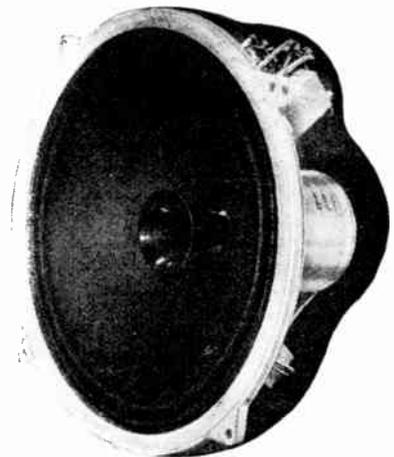Mounted in de luxe table cabinet - - - - £11-3-0  
Corner console twin speaker, less transformer - - £12-12-0



### SPECIFICATION

Series Gap Magnet of Alcomax 3.  
Cone: 10" diameter.  
Flux in L.F. gap, 12,000 gauss on 1" pole.  
Flux in H.F. gap, 13,000 gauss on 1" pole.  
Power handling capacity (both component speakers) 6 watts.  
Chassis material pressure die-cast from Mazak 3, non-magnetic and non-resonant alloy.

W.H. TELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS

# G.E.C. QUARTZ CRYSTAL UNITS

## For Reliable Radio Communications



From take-off to landing, the safety of passengers, cargo and machines is largely dependent on trouble-free radio communication.

Weather reports, conditions at terminal airports etc., must be reported to aircrews.

Navigation by radio beacons plays an important part in keeping the planes flying safely on their assigned routes.

Be sure, then, that the Quartz Crystal Units in your radio equipment are the best obtainable, for they are the most critical components.

Pioneering research and experience in making over a million units, ensure a product of the finest available quality at competitive prices. We can give rapid delivery for your urgent requirements.

When the requirement is exceptionally urgent, phone Middleton (Lancs.) 2424 or Temple Bar 4669 (London).



**SALFORD ELECTRICAL INSTRUMENTS LTD.** PEEL WORKS - SILK ST. SALFORD 3 - LANCs.

A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND

## WORLD OF WIRELESS

### New Television Advisers ♦ Aircraft Radiotelephony ♦ Amateur Show ♦ Television Servicing Certificate

#### Television Committee

[T was announced by the P.M.G., in reply to a question in the House on November 2nd, that the Television Advisory Committee had been reconstituted. He stated that, in view of the appointment of the Broadcasting Committee, under the chairmanship of Lord Beveridge, which was considering the wider aspects of broadcasting (including television), it had been decided to alter the Advisory Committee's terms of reference to "advise the Postmaster-General on current development problems of the B.B.C.'s television service."

In addition to Sir William Coates, who was recently appointed chairman, the membership of the Advisory Committee includes I. A. R. Stedeford, who is also a member of the Broadcasting Committee; Professor J. A. Ratcliffe, of Cavendish Laboratory; H. Townsend, Director of Telecommunications, G.P.O.; Sir William Haley, Director-General, B.B.C.; and an official of the Treasury. The secretary, H. Baker (G.P.O.), is also assistant secretary of the Broadcasting Committee.

Some misgivings have been voiced by the Radio Industry Council at the curtailing of the terms of reference, which were previously very wide. It has, however, been pointed out that complete liaison is being maintained between the two committees, and, moreover, that whereas the Beveridge committee will consider the long-term policies, the Coates committee will deal with current developments.

#### Civil Aviation Radio

THE Ministry of Civil Aviation recently introduced a v.h.f. radio-telephony system providing continuous coverage for all aircraft flying on the routes between Aberdeen and the Shetlands. The system, which employs seven stations, is designed to give coverage along the whole route. D.F. is provided on the communication frequencies.

This is the first part of a project to cover the whole of the British Isles with v.h.f. radio-telephony and direction finding. The intention is that this will supersede the existing system of m.f. and h.f. morse communication and direction finding.

The introduction of this plan will mean a reduction in the amount of equipment carried by aircraft flying on internal routes.

The plan provides for transmitters and receivers strategically located on high ground throughout Great Britain and part of Northern Ireland. The transmitters, operating on the multi-carrier principle, will be modulated from Air Traffic Control centres at Uxbridge; Barton Hill, near Preston; and Prestwick. The receiver outputs will, of course, be fed to the same centres.

#### Amateur Exhibition

THE third annual amateur radio exhibition, organized by the Radio Society of Great Britain, is being held at the Royal Hotel, Woburn Place, London, W.C.1, for four days from November 23rd. Admission to the show, which is open daily from 11 a.m. to 9 p.m., is by catalogue, price 1s.

The 24 exhibitors include the G.P.O. Engineering Department and the Air Ministry; eighteen manufacturers and four publishers. The manufacturers include Standard, Webb's, Quartz Crystal, Radiocraft, Oliver Pell, T. C. C. Philpott's Metalworks, Salford, Denco, Taylor, Cyril French, Imhof, Automatic Coil Winder, Southern Radio, Sangamo Weston, G.E.C., Woden and E.M.I.

We hope to give a review of the exhibits in our next issue.

#### Television Servicing

THE first examination for the Television Servicing Certificate, organized jointly by the Radio Trades Examination Board and the City & Guilds of London Institute, will be held on May 2nd and 4th

next year. The practical examination will be held at a later date. As London will be the only centre, it may be necessary to restrict the number of entries.

Admission to the examination is limited to candidates who have passed one of the following examinations:—

(a) The Radio Servicing Certificate Examination held jointly by the City & Guilds and the R.T.E.B.

(b) The Radio Servicing Examination held by the R.T.E.B. from 1941 to 1946.

(c) The examination in Radio Service Work of the City & Guilds held from 1938 to 1947.

(d) The "third year" examination in Radio Service Work of the Union of Lancashire and Cheshire Institutes.

(e) The examination in Radio Servicing held prior to 1944 by the Brit. I.R.E.

(f) The examination in Radio Servicing held prior to 1944 by the Scottish Radio Retailers' Association.

Regulations and entry forms are obtainable from the secretary of the R.T.E.B., 9, Bedford Square, London, W.C.1. The closing date for entries is December 15th.

#### PERSONALITIES

Sir Edward Appleton, until recently Secretary of the D.S.I.R. and now Principal and Vice-Chancellor of Edinburgh University, is to receive the honorary degree of Doctor of Laws from London University. From 1924 to 1936 Sir Edward was Wheatstone Professor of Physics at the University.

R. C. Wansbrough, M.A., M.I.E.E., M.Brit.I.R.E., who has been appointed personal assistant to E. J. Emery, managing director of E.M.I. Sales and Service, Ltd., recently retired from the R.A.F. with the rank of Air Commodore. Among the positions he held during his 30-odd years' service in the R.A.F. were those of Deputy Director of Radio Repairs (M.A.P.) and Director of Radio at the Air Ministry.

L. H. Bedford, O.B.E., M.A., B.Sc. (Eng.), of Marconi's, was elected president of the British Institution of Radio Engineers for a second year at the recent annual general meeting.



UN - RETOUCHE  
picture taken directly from the screen of a Wireless World superhet television receiver at Bath, some 100 miles from Alexandra Palace.

### World of Wireless—

Paul Adorian, a director of Redifon, and W. E. Miller, M.A., Editor of *The Wireless and Electrical Trader*, were re-elected vice-presidents.

L. Hotine, who joined the B.B.C. in 1923 and has been Senior Superintendent Engineer since 1943, has been placed in charge of that section of the Operations and Maintenance Dept. of the B.B.C. Engineering Division which consists of the studio, transmitter, recording and lines departments.

M. J. L. Pulling, M.A., M.I.E.E., has been appointed Senior Superintendent Engineer (Television) to take charge of the television side of the B.B.C. Engineering Division's work. He joined the Corporation in 1934 and became Superintendent Engineer (Recording) in 1941. He is a vice-president of the British Sound Recording Association. D. C. Birkinshaw, M.B.E., M.A., A.M.I.E.E., will continue as Superintendent Engineer (Television), to which post he was appointed in 1945 after 13 years' service with the Corporation. During the war he was engineer-in-charge of the Daventry short-wave station, prior to which he held a similar position at the London television station.

Harry A. Woodyer, who was until recently sales manager of Kolectric, Ltd., has been appointed managing director. He has been in radio for over 26 years, having been on the staffs of Dubilier and T.M.C., and from 1940 to 1946 was radio sales manager of Simmonds Aerocessories.

### OBITUARY

Walter G. Pye, who founded in 1899 the company of Cambridge instrument manufacturers bearing his name, died recently at the age of 80. He worked in the Cavendish Laboratory, Cambridge, prior to setting up in business. When W. G. Pye and Co. started manufacturing broadcast receivers, Pye, Ltd., was formed to develop this side of the business.

### IN BRIEF

**Licences.**—With increases of 65,250 and 8,850 sound and vision licences, respectively, during September, the totals at the end of the month were sound 11,920,600 and vision 171,000.

**Amateur Television.**—The Radio Society of Great Britain has asked the Postmaster-General for permission for selected amateurs to use television transmitting equipment within certain sections of the 420 to 460-Mc/s amateur band. The request has been refused.

**For the Blind.**—A Braille edition of the "Admiralty Radio Handbook" is in course of preparation by the National Institute for the Blind which, when completed, will comprise 18 volumes. It is also recorded in the annual report of the Institute that since its commencement in 1929 the "Wireless For The Blind Fund" has supplied 84,887 free sets. During last year 4,065 sets and relay installations were supplied. The response to last year's Christmas Day broadcast appeal was £30,596.

**Amateur Power.**—The Postmaster-General has granted permission for U.K. amateurs, other than those holding licences limiting power to 10 and 25 watts, to use a power of 150 watts on all amateur frequency bands above 28 Mc/s with the exception of the 420-460-Mc/s band on which the limit remains at 25 watts. The concession is for an experimental period of one year from October 18th.

**R.E.C.M.F. Exhibition.**—The ballot for stands at the exhibition of components, valves and test equipment, to be held at Grosvenor House, Park Lane, London, W.1, from April 17th to 19th next year was held on October 26th. There were nearly 100 applicants for space at this, the seventh show to be organized by the Radio and Electronic Component Manufacturers' Federation.

**Antarctic D.F.**—The two aircraft to be used to reconnoitre the ice fields and to guide the Anglo-Scandinavian Antarctic Expedition ship *Norsel* through them will be equipped with Marconi Type AD7092 automatic direction finders for guiding them back to the ship after reconnaissance. These have been fitted to obviate the errors which may be introduced in the planes' magnetic compasses when flying within the magnetic influence of the South Pole.

**Marconi marine radar equipment,** Radiolocator III, has been given the Ministry of Transport's "type approval" certificate which is granted after tests conducted to ensure efficiency, mechanical sturdiness and conformity with the M.o.T. specification.

**A Student's Guide** to the courses of study in engineering available in the Manchester district is published by the Manchester and District Advisory Council for Further Education. Particulars are obtainable from the Education Officer, Deansgate, Manchester, 3.

**Colour Television.**—At a meeting of the Institution of Electrical Engineers on October 31st, Dr. P. C. Goldmark gave a lecture on "The C.B.S. Colour Television System in the U.S.A." After dealing with the general history of colour television, Dr. Goldmark discussed the requirements of illumination, the choice of primary colours, and colour flicker. A demonstration of Pye three-colour television equipment, which is similar to the C.B.S. system, was given.

**"Radio Data Charts,"** which gives in graphical form most of the essential data for the design of receivers, has been revised and is again available from booksellers, price 7s 6d, or by post from our Publisher, price 7s 10d.

**"B.B.C. Year Book."**—The 1950 edition of this annual contains the usual wealth of information on the B.B.C. activities and an extensive reference section. This copiously illustrated 176-page book, costs 3s 6d.

**Plastics.**—In the book "Experimental Plastics for Students," by C. A. Redfern and A. Allcott, published for *British Plastics* by our Publisher (price 10s 6d), thirty-four experiments are described to give readers an appreciation of the principles involved in the production and moulding of plastic materials.

### EXPORTS

**Radio-Telephony in S.A.**—A u.h.f. radio-telephone link has been installed by Standard Telephones and Cables for the South African Post Office to extend communications between Port Elizabeth and Uitenhage—a distance of about fifteen miles. Half-wave dipoles (with directors) with corner reflectors are used at both stations. The "Standard" time-sharing multiplex system has been used which provides 24 channels and allows direct dialling between the telephone exchanges.



**Marconi Demonstrations.**—A week of demonstrations of television test equipment is being held by Marconi Instruments at their showrooms, 19, The Parade, Leamington Spa. During the week, which ends on November 26th, demonstrations are also being given by Marconi's W.T. Co. of a complete portable television camera chain. The showrooms are open from 10 a.m. to 5 p.m.

**Brazil.**—Tenders are being sought by the Rio Grande do Sul State Commission for Electric Energy for wired-wireless equipment, for use on the high-tension cables to provide a communication system between the main generating stations and the substations. The frequency to be used on the 66 kV lines will be between 90 and 150 kc/s. The audio-frequency equipment includes 50 telephones. A

**MAGNIFICATION** of dental operations to eight times life size were given, with the aid of Marconi portable television equipment working on a closed circuit with monitors in the lecture theatre, to those attending a recent function at the Royal Dental Hospital, London.

copy of the specification (in Spanish), Ref. CRE(IB) 31194/49, is available at the Commercial Relations and Exports Department, Board of Trade, Room 1080, Thames House North, Millbank, London, S.W.1, from whom further information is obtainable.

Pye Television is to make its debut in the United States. A complete transmitter, including cameras and monitoring equipment, for operation on the American 525-line standard has been shipped to the U.S. and is to be set up for demonstrations in Washington, New York and Chicago. The whole of the equipment is transportable in suitcase-size containers.

C. G. ALLEN, a director of McMichael's and a well-known amateur, was recently filmed talking to Henry Rieer, a South African amateur who frequently receives the London television transmissions. The film was televised and here is the un-retouched picture as received on the screen of a McMichael set.



**B.E.A.M.A. Catalogue.**—The first (1949/50) edition of this 868-page catalogue of the products of members of the British Electrical and Allied Manufacturers' Association has been issued by our Publisher for B.E.A.M.A. Thirteen thousand copies have been printed, ten thousand of which are being distributed overseas. The catalogue section, consisting of 740 pages, is printed in three colours. The buyers' guide and directory of addresses includes over ten thousand entries.

**Marconi Instruments.**—Two members of the staff of Marconi Instruments, Ltd., F. G. Cook, manager, instrumentation exports, and E. Garthwaite, development manager, are paying a six-weeks' visit to the United States to explore the possibilities of marketing Marconi test and measuring gear.

**Falkland Islands.**—An order for forty fixed-frequency transmitter-receivers to supplement the existing inter-island line communication system is to be supplied to the Falkland Islands authorities by Berry's (Short-Wave), Ltd.

**Decca.**—*Navigator*, the demonstration vessel of the Decca Navigator Co., has sailed for Holland and Belgium to demonstrate Decca radar equipment in those countries.

### CHANGES OF ADDRESS

**International Aeradio, Ltd.,** has moved its head office to Aeradio House, 40, Parker Street, London, W.1 (Tel.: Regent 5024). A subsidiary of the company has been formed in Karachi with the title International

Aeradio (Pakistan), Ltd. Technical training of aviation staff is being undertaken by the company on behalf of the Pakistan Government.

**Londex.**—Additional premises close to their present works at 207, Anerley Road, London, S.E.20, have been acquired by Londex, Ltd., manufacturers of remote-control equipment.

**Kolectric, Ltd.,** manufacturers of coil-winding machines, have opened offices and showrooms at 73, Uxbridge Road, London, W.5 (Tel.: Ealing 9096). All correspondence should now be sent to this address and not to the works at Grove Hill, Beverley, E. Yorks.

### MEETINGS

#### Institution of Electrical Engineers

**Radio Section.**—"Solar Radio-Frequency Radiation," by J. L. Pawsey, M.Sc., Ph.D., at 5.30 on December 7th.

"The Acoustics of Studios and Auditoria," by W. Allen, at 5.30 on December 19th.

**Discussion Circle.**—"The Electron Theory, Approach to Electro-magnetism," discussion opened by Prof. J. Thompson, D.Sc., M.A., at 6.0 on November 29th.

The above meetings will be held at the I.E.E., Savoy Place, London, W.C.2.

**Cambridge Radio Group.**—Address by R. T. B. Wynn, C.B.E., M.A., chairman of the Radio Section, at 6.0 on December 13th, at the Cambridge-shire Technical College.

**North-Western Centre.**—"Some Electromagnetic Problems," by Prof. G. W. O. Howe, D.Sc., LL.D., at 6.15 on December 6th, at the Engineers' Club, Albert Square, Manchester.

**North Lancashire Sub-Centre.**—"Some Electromagnetic Problems," by Prof. G. W. O. Howe, D.Sc., LL.D., at 7.0 on December 7th, at the North-Western Electricity Board Demonstration Theatre, North Road, Lancaster.

**South Midland Centre.**—Faraday lecture on "Radar," by R. A. Smith, M.A., Ph.D., at 6.0 on December 5th, at the Town Hall, Birmingham.

**South Midland Radio Group.**—"The Observation of Ionospheric Interactions," by D. A. Bell, M.A., B.Sc., F. J. Hyde, B.Sc., and C. C. Newton, at 6.0 on November 28th, at the James Watt Memorial Institute, Great Charles Street, Birmingham.

**British Institution of Radio Engineers London Section.**—"Electronics in Aircraft Design," by A. L. Whitwell, at 6.30 on December 15th, at the London School of Hygiene, Gower Street, W.C.1.

**Merseyside Section.**—"The Acceleration of Atomic Particles to High Energies," by J. D. Craggs, M.Sc., Ph.D., at 7.0 on December 7th, at the Accountants' Hall, Derby Square, Liverpool.

**North-Eastern Section.**—"A Review of the Basis of Electronics," by C. Laverick, at 6.0 on December 21st, at Neville Hall, Westgate Road, Newcastle-on-Tyne.

**Scottish Section.**—"Electronics in Industry," by A. A. M. Turnbull, at 6.30 on December 1st, in the Electrical Department, Glasgow University.

**South Midlands Section.**—"H.T. Supply for High Power Transmitters," by M. Lane, at 7.0 on December 15th, at the Technical College, The Butts, Coventry.

#### British Sound Recording Association

**London.**—"Some Aspects of L.F. Performance of Loudspeakers," by G. A. Briggs, at 7.0 on November 25th at the Royal Society of Arts, John Adam Street, W.C.2.

"Acoustics and the Film," by C. W. Glover and John McLaren, at 7.15 on December 7th at the G.B. Theatre, Film House, Wardour Street, London, W.1. (Joint meeting with the British Kinematograph Society.)

**Birmingham.**—Dr. L. E. C. Hughes will address a meeting at 2.15 on November 26th at the Imperial Hotel, Temple Street.

#### Institute of Navigation

"Navigational Systems and Instrumental Aids," by Dr. D. E. Adams and Dr. A. N. Uttley, at 6.0 on December 15th, at the Institution of Civil Engineers, Great George Street, London, S.W.1. (Joint meeting with the Royal Aeronautical Society.)

"Radar Charts," discussion opened by Lt. Cdr. P. G. Satow, D.S.C., R.N., on the adaptation of marine charts for use with radar, at 5.0 on December 16th, at the Royal Geographical Society, 1 Kensington Gore, London, S.W.7.

#### Institute of Physics

**Electronics Group.**—"The Nervous System as an Electrical Machine," by Dr. W. Grey Walter at 5.30 on December 13th, at the Institute's House, 47 Belgrave Square, London, S.W.1.

#### Radio Society of Great Britain

Annual general meeting at 6.30 on December 16th, at the I.E.E., Savoy Place, London, W.C.2.

#### Television Society

**Constructors' Group.**—"Baird Television Receivers," by P. Wigley, B.Sc., at 7.0 on December 8th, at the Cinema Exhibitors' Association, 164 Shaftesbury Avenue, London, W.C.2.

**Bedford Centre.**—"Television Aerial Problems," by E. M. Lee at 7.30 on December 14th, at the Flying Services Club, St. Mary's Street, Bedford.

**Bristol and S.W. Centre.**—"Television Aerials and Interference Problems," by E. M. Lee, on December 6th at the Royal Hotel, Bristol.

#### Guild of Radio Service Engineers

**Edinburgh Branch.**—"Radio Capacitors," by a member of T.C.C. staff, at 7.30 on December 15th, at Univ House, 4, Hillside Crescent, Edinburgh.

# ELECTRONIC DIVERSITY SWITCHING

(Concluded from Page 418 of November issue)

## Design and Operation of Triple Diversity System

**I**N the first part of this article the advantages of switched over combined-output methods in diversity reception were discussed, and an electronic switch for two receiving circuits was described. We shall now consider the extension of the method to three circuits.

Fig. 3 shows the full schematic of the triple-diversity version of the switch. It will be seen that three triode-hexode valves, instead of two, are used in the gate. Otherwise this part of the circuit

By **H. V. GRIFFITHS**  
and **R. W. BAYLIFF**

(Engineering Division, B.B.C.)

is identical with that used in the dual switch.

The discriminator contains duplicate circuits of the type used in the dual switch, together with additional circuits which interpret and rearrange the switching voltages developed by the four valves  $V_1, V_2, V_3$  and  $V_4$ . The three a.f.

signals from the diversity receivers are introduced into the three input channels, and the negative control potentials,  $E_1, E_2$  and  $E_3$ , are separated by the centre-tapped resistor combinations  $R_{35}-R_{36}, R_{45}-R_{46}$ , and  $R_{50}-R_{51}$ .  $E_1$  and  $E_2$  are applied through the cathode followers  $V_{10a}$  and  $V_{10b}$ , to the first pair of discriminator valves,  $V_1$  and  $V_2$ .  $E_3$  is similarly applied, through the cathode follower  $V_{11}$  to  $V_3$ , the first of the second pair of discriminator valves.  $V_4$  derives its control potential from

Values of Components used in Circuit of Fig. 3.

Component	Value	Rating	Component	Value	Rating	Component	Value	Rating
R <sub>1</sub>	510 kΩ	½ W	R <sub>32</sub>	15 kΩ	2 W	C <sub>3</sub>	8 μF	550 V
R <sub>2</sub>	510 kΩ	½ W	R <sub>33</sub>	100 kΩ	½ W	C <sub>4</sub>	8 μF	550 V
R <sub>3</sub>	100 kΩ	½ W	R <sub>34</sub>	50 kΩ	2 W	C <sub>5</sub>	50 μF	25 V
R <sub>4</sub>	15 kΩ	2 W	R <sub>35</sub>	39 kΩ	½ W	C <sub>6</sub>	5,000 pF	350 V
R <sub>5</sub>	47 kΩ	½ W	R <sub>36</sub>	39 kΩ	½ W			(mica)
R <sub>6</sub>	10 kΩ pot. linear (wire-wound)	2 W	R <sub>37</sub>	10 kΩ	½ W	C <sub>7</sub>	5 000 pF	350 V
R <sub>7</sub>	47 kΩ	½ W	R <sub>38</sub>	20 kΩ	2 W			(mica)
R <sub>8</sub>	150 Ω	½ W	R <sub>39</sub>	5 kΩ	2 W	C <sub>8</sub>	5,000 pF	350 V
R <sub>9</sub>	240 kΩ	½ W	R <sub>40</sub>	100 kΩ	½ W			(mica)
R <sub>10</sub>	240 kΩ	½ W	R <sub>41</sub>	100 kΩ	½ W	C <sub>9</sub>	0.1 μF	350 V
R <sub>11</sub>	15 kΩ	2 W	R <sub>42</sub>	240 kΩ	½ W	C <sub>10</sub>	0.1 μF	350 V
R <sub>12</sub>	100 kΩ	½ W	R <sub>43</sub>	600 Ω	½ W	C <sub>11</sub>	3,000 pF	350 V
R <sub>13</sub>	510 kΩ	½ W	R <sub>44</sub>	1.8 MΩ	½ W	C <sub>12</sub>	0.1 μF	350 V
R <sub>14</sub>	510 kΩ	½ W	R <sub>45</sub>	39 kΩ	½ W	V <sub>1</sub>	EF 55	
R <sub>15</sub>	20 kΩ pot. linear (wire-wound)	2 W	R <sub>46</sub>	39 kΩ	½ W	V <sub>2</sub>	"	
R <sub>16</sub>	510 kΩ	½ W	R <sub>47</sub>	100 kΩ	½ W	V <sub>3</sub>	"	
R <sub>17</sub>	4.7 kΩ	½ W	R <sub>48</sub>	240 kΩ	½ W	V <sub>4</sub>	6H6	
R <sub>18</sub>	20 kΩ pot. linear (wire-wound)	2 W	R <sub>49</sub>	1.8 MΩ	½ W	V <sub>5</sub>	EF 55	
R <sub>19</sub>	4.7 kΩ	½ W	R <sub>50</sub>	39 kΩ	½ W	V <sub>6</sub>	"	
R <sub>20</sub>	47 kΩ	½ W	R <sub>51</sub>	39 kΩ	½ W	V <sub>7</sub>	"	
R <sub>21</sub>	4.7 kΩ	½ W	R <sub>52</sub>	100 kΩ	½ W	V <sub>8</sub>	6J5	
R <sub>22</sub>	47 kΩ	½ W	R <sub>53</sub>	1 MΩ	½ W	V <sub>9</sub>	6H6	
R <sub>23</sub>	10 kΩ	1 W	R <sub>54</sub>	240 kΩ	½ W	V <sub>10</sub>	6SL7GT	
R <sub>24</sub>	20 kΩ pot. linear (wire-wound)	2 W	R <sub>55</sub>	1.8 MΩ	½ W	V <sub>11</sub>	6SQ7	
R <sub>25</sub>	240 kΩ	½ W	R <sub>56</sub>	1 MΩ	½ W	V <sub>12</sub>	6K8	
R <sub>26</sub>	15 kΩ	2 W	R <sub>57</sub>	1.5 kΩ	½ W	V <sub>13</sub>	6K8	
R <sub>27</sub>	47 kΩ	½ W	R <sub>58</sub>	15 kΩ	½ W	V <sub>14</sub>	6K8	
R <sub>28</sub>	10 kΩ pot. linear (wire-wound)	2 W	R <sub>59</sub>	6.8 kΩ	½ W	V <sub>15</sub>	6SN7GT	
R <sub>29</sub>	47 kΩ	½ W	R <sub>60</sub>	3.3 MΩ	½ W	T <sub>1</sub>	1 : 11.5	Line/grid
R <sub>30</sub>	240 kΩ	½ W	R <sub>61</sub>	1 MΩ	½ W	T <sub>2</sub>	"	"
R <sub>31</sub>	150 Ω	½ W	R <sub>62</sub>	1.5 kΩ	½ W	T <sub>3</sub>	"	"
			R <sub>63</sub>	220 Ω	½ W	T <sub>4</sub>	4.44 : 1	Anode/line
			R <sub>64</sub>	220 Ω	½ W	N <sub>1</sub>	Osglim "G"	
			R <sub>65</sub>	470 Ω	½ W	N <sub>2</sub>	"	
			C <sub>1</sub>	8 μF	550 V	N <sub>3</sub>	"	
			C <sub>2</sub>	500 pF	550 V (mica)			

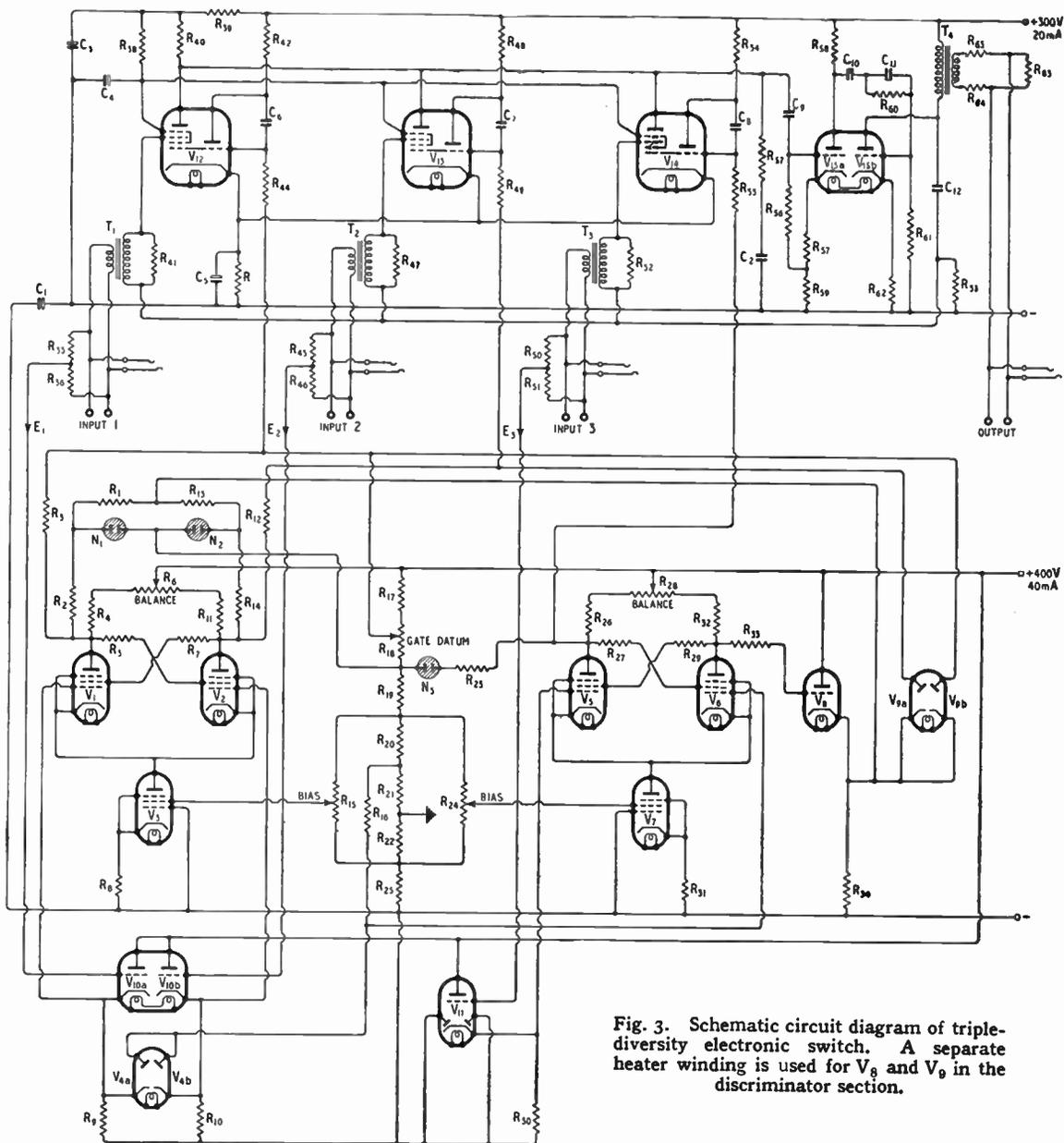


Fig. 3. Schematic circuit diagram of triple-diversity electronic switch. A separate heater winding is used for  $V_8$  and  $V_6$  in the discriminator section.

the anodes of the diodes,  $V_{4a}$  and  $V_{4b}$ , whose function is to select the "better," i.e., more negative, of the control potentials fed to  $V_1$  and  $V_2$ . Suppose, for example, that of the three signals No. 1 is the best ( $E_1$  is, say  $-12$  V); No. 2 is next best ( $E_2 = -10$  V); and No. 3 is worst ( $E_3 = -7$  V). The cathodes of the three cathode followers,  $V_{10a}$ ,  $V_{10b}$  and  $V_{11}$ , will then change by like amounts, so that  $V_1$ 's grid becomes 12 V negative with respect to its no-

signal value;  $V_2$ 's grid changes by  $-10$  V; and  $V_6$ 's grid changes by  $-7$  V. Of the two diodes  $V_{4a}$  and  $V_{4b}$ , the cathode of  $V_{4a}$  has changed by  $-12$  V, whilst that of  $V_{4b}$  has changed by  $-10$  V:  $V_{4a}$  conducts and its anode becomes equal in potential to its cathode;  $V_{4b}$  is cut off, because its anode is  $-2$  V with respect to its cathode. Therefore  $V_6$ 's control grid has a change of  $-12$  V impressed on it. The comparisons by the two discriminators are thus effected

as follows:  $V_1$  and  $V_2$  compare signals Nos. 1 and 2;  $V_8$  and  $V_6$  compare signal No. 3 with the better of Nos. 1 and 2.

For simplicity, the anode voltages of  $V_1$ ,  $V_2$ ,  $V_8$  and  $V_6$  will be considered merely as being either positive or negative with respect to the slider of  $R_{18}$ , i.e., the negative pole of the gate h.t. supply; the anode will be positive when the valve concerned is near cut-off; it will be negative if the valve is heavily conductive.

**Electronic Diversity Switching—**

Further, if one valve of a pair has its anode positive, then the other must be negative. Reverting now to the example used in the previous paragraph, where  $E_1$ ,  $E_2$  and  $E_3$  are  $-12$ ,  $-10$  and  $-7$  volts respectively, it will be seen that the  $V_1$ - $V_2$  pair are in the state where  $V_1$ 's anode is positive and  $V_2$ 's is negative; the  $V_5$ - $V_6$  pair are in the state in which  $V_5$ 's anode is negative and  $V_6$ 's is positive. The operation of the gate valves in these conditions is as follows:  $V_{12}$  will be turned "on" by the positive potential from  $V_1$  (thus signal No. 1—the best signal—is passed on to the output);  $V_{13}$  and  $V_{14}$  will be turned "off" by the negative potentials from  $V_2$  and  $V_5$  (hence signals Nos. 2 and 3 will be blocked). The resistors  $R_3$  and  $R_{12}$ , through which the switching voltages are fed to  $V_{12}$  and  $V_{13}$ , are small compared with  $R_{44}$  and  $R_{49}$  and so they do not appreciably alter the switching time constant.

The function of the cathode-follower buffer,  $V_8$ , and the diodes  $V_{9a}$  and  $V_{9b}$ , is to prevent the positive anode potential from  $V_1$  or  $V_2$  from being effective in turning "on"  $V_{12}$  or  $V_{13}$  if signal No. 3 happens to be the best one. It also avoids the faulty indication which would otherwise be given by one of the neon lamps,  $N_1$  or  $N_2$ . This action can best be illustrated by another example. Suppose that signal No. 3 is the best ( $E_3 = -15$  V); signal No. 1 is next best ( $E_1 = -10$  V); and signal No. 2 is the worst ( $E_2 = -6$  V). The  $V_1$ - $V_2$  pair operates in favour of  $E_1$ , i.e.,  $V_1$ 's anode is positive and  $V_2$ 's is negative; the  $V_5$ - $V_6$  pair operates in favour of  $E_3$  because  $V_5$  receives  $-15$  V ( $E_3$ ) and  $V_6$  receives  $-10$  V (the better of  $E_1$  and  $E_2$ ).  $V_5$ 's anode is, therefore, positive and  $V_6$ 's is negative. The cathode of  $V_8$  and hence the cathodes of the diodes  $V_{9a}$  and  $V_{9b}$  also will follow the potential of  $V_6$ 's anode and will become negative (with reference to the slider of  $R_{18}$ ). The positive voltage at  $V_1$ 's anode is prevented from turning  $V_{12}$  "on" by the negative voltage from  $V_{9b}$ . The presence of  $R_3$  increases the apparent impedance of the  $V_1$  source and enables the potential from  $V_{9b}$  to override

that from  $V_1$ . Thus both  $V_{12}$  and  $V_{13}$  are turned "off," and  $V_{14}$ , which is associated with the best signal, is turned "on" by the positive potential from  $V_5$ 's anode. The neon lamps  $N_1$  and  $N_2$  are each fed from two sources through high resistances. The potentials are such that the neons will light only if both sources are positive. Thus, in the last example, although  $V_1$ 's anode is positive and tends to strike  $N_1$  it is prevented from doing so by the negative supply, through  $R_1$ , from the cathode of  $V_8$ .  $N_2$  is also extinguished since it is driven from  $V_2$  anode (negative) through  $R_{14}$  and  $V_8$  cathode (negative) through  $R_{13}$ .  $N_3$  is, however, illuminated by the feed from  $V_5$  anode (positive) through  $R_{25}$ . This gives the correct indication, for gate-valve  $V_{14}$  is "open," signal No. 3 being the best.

The diodes  $V_{9a}$  and  $V_{9b}$  are necessary (as opposed to straight-through connections) in order that the negative potential from  $V_1$  or  $V_2$  can override, by cutting, off the appropriate diode, the positive voltage from  $V_8$  cathode when the best signal is either No. 1 or No. 2.

**Results in Service**

After more than two years' experience with the electronic switch it is considered that the switched diversity system is superior to combined diversity, the effects of selective carrier fading especially being less marked. The receivers and aerials must, however, be more strictly matched than is usually necessary with the combining system, and more frequent routine examinations of the radio—and intermediate—frequency amplifier alignment are necessary. This is because the rapid change-over enables the ear to detect very small differences of background noise, a disparity of as little as 2 db being perceptible when the signal/noise ratio does not exceed 20 db. For this reason, when aerials having widely different characteristics are used, in "polarization diversity," for example, with weak or moderate signals, the change-over is marked by an abrupt change in the background noise. In these conditions it is preferable to increase the mix period beyond the 50 milliseconds,

which was adopted on other grounds, to about 150 milliseconds by increasing the value of the capacitors  $C_6$  and  $C_7$  (Fig. 2) or  $C_6$ ,  $C_7$  and  $C_8$  (Fig. 3). The change-over is then less abrupt and will generally be inaudible. Although rapid selective fades may occasionally cause distortion, the results are still superior to those of combined diversity.

**"VIEW MASTER"**

THE "View Master" is a television receiver sponsored by several component manufacturers and intended for the home constructor. It is for the London area, and the constructional details and wiring drawings are obtainable from wireless dealers, price 5s.

The set has a gin tube with electromagnetic deflection. Two valves are used in each time base and e.h.t. is taken from the line fly-back. The receiver has three r.f. stages with coupled pairs of tuned circuits for the intervalve couplings. Noise limiters are included.

The h.t. supply comes straight from the mains via a half-wave metal rectifier, and a transformer is only included for the valve heaters. The set is thus suited to a.c. mains only.

The drawings supplied are very clear, and, if carefully followed, no constructional difficulty should be encountered. The receiver must be aligned for single-sideband reception of the sidebands remote from the sound channel, and the use of a signal generator for this is advised. A procedure is given, however, for alignment on a signal.

**NEWS FROM THE CLUBS**

**Basingstoke.**—At the meeting of the Basingstoke District Amateur Radio Society on December 9th the design and construction of communication receivers will be discussed. The meeting will be held at the British Workmen's Restaurant, Basingstoke, at 7.45. Sec.: L. S. Adams, 16, Brambls Drive, Basingstoke, Hants.

**Birmingham.**—A talk on loudspeakers, with demonstrations, will be given to members of the Slade Radio Society by A. E. Falkus of Reproducers and Amplifiers, Ltd., at the meeting on December 9th at 7.45 at the Parochial Hall, Slade Road, Erdington, Birmingham, 23.

**Northwich** employees of Imperial Chemical Industries have formed the Crescent Radio Society, which meets on alternate Tuesdays in the works conference room. Membership is limited to employees of I.C.I. Sec.: W. Houseman, 15, Snowdon Street, Barnton, Northwich, Cheshire.

# SUPPRESSING IMPULSE NOISE

## New Type of Eliminator Operating on Pulse Duration

By D. C. ROGERS, A.M.I.E.E.  
(Standard Telephones and Cables)

**I**MULSE noise consists of very short bursts of electrical energy originating from atmospheric disturbances, or from such devices as switches, motor commutators, etc. These pulses of energy have a duration nearly always substantially less than one microsecond, and hence less than the response time of the radio-frequency amplifiers of the receiver. They are, therefore, lengthened on their passage through the tuned amplifiers of the receiver and arrive at the detector with a duration which is dependent on the receiver bandwidth—in fact a duration which is of the order of twice the reciprocal of the receiver bandwidth. A further feature of these noise pulses, and one in which they differ from valve and circuit noise is that the interval between pulses is long compared with their duration at the output of the amplifier; in other words, they occur as separate pulses, and very rarely “overlap.”

Any circuit which is to discriminate against impulse noise must embody some means of distinguishing between the noise pulses and the desired modulation. In most circuits of the so-called

limiter type the noise pulses are distinguished by the fact that their amplitude is greater than that of the signal either before or after detection. For example, one well-known form of limiter is arranged to discriminate against any noise pulse whose amplitude exceeds twice the incoming carrier amplitude, this being the maximum value attained by the incoming signal at 100 per cent modulation. A circuit of this type cannot operate on pulses which have a small amplitude, but are nevertheless irritating to the listener.

### Bandwidth Considerations

The circuit to be described<sup>1</sup> uses the duration of the noise pulse instead of its amplitude to distinguish it from the desired modulation; it is therefore capable of discriminating against noise pulses, even when their amplitude is equal to or smaller than the incoming signal.

It has been mentioned that the duration of the noise pulse at the detector is dependent on the receiver bandwidth, and that it decreases as the bandwidth is increased. In order to be able to discriminate against noise pulses without distortion of the desired signal, it is necessary for the pulse to have a duration less than that of a half-cycle of the highest modulation frequency. This implies that the bandwidth of the section of the receiver prior to the detector

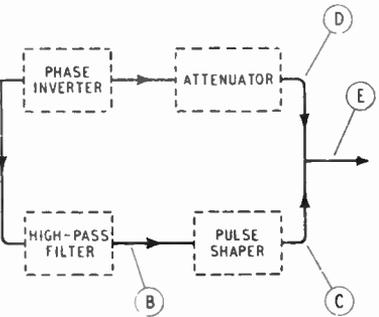


Fig. 2. Functional diagram of the circuit. The letters A, B, C, etc., refer to the points at which the waveforms of Figs. 1(a), (b), (c), etc., respectively, are observed.

should be greater than that needed for the reception of the transmitted modulation sidebands.

For this reason it will be seen that the use of the circuit is restricted to cases where selectivity is unimportant, and its application will generally be confined to frequencies above, say, 30 Mc/s. A typical case where it may be of use is in the sound section of a television receiver, where interference is frequently encountered from motor-car ignition and similar sources. It is not applicable to ordinary domestic broadcast receivers, or radio receivers of the “communication” type, where a high degree of selectivity is essential.

**Principle of Operation.** — The output of the receiver detector will consist of the desired modulation waveform, on which is superimposed a noise pulse, as shown in Fig. 1(a). The noise pulse may be analysed into a spectrum of frequencies extending from zero up to a maximum which is dependent on the receiver bandwidth, and, if this bandwidth is greater than that necessary to receive the transmitted carrier and sidebands, there will be noise components at frequencies correspondingly higher than the highest modulation frequency.

Referring now to Fig. 2, which

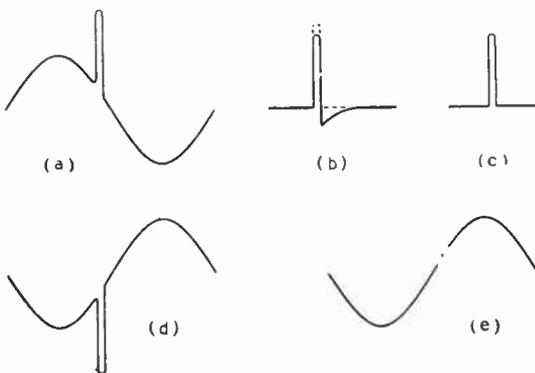


Fig. 1. Waveforms appearing at various points in Fig. 2

<sup>1</sup> Patents pending

**Suppressing Impulse Noise—** shows a block schematic diagram of the circuit, it will be seen that the output from the detector is fed into a high-pass filter. This filter transmits only those frequencies above the modulation band, and its purpose is to remove all modulation frequencies and the lower frequency components of the noise

The two outputs from the pulse shaper and attenuator are then combined, when the noise pulses, being in opposite sense, cancel completely, leaving the modulation free from noise as shown in Fig. 1(c).

**Circuit Variants.**—It will be apparent that it is possible to devise a variety of circuits

bandwidth of the receiver to the highest modulation frequency is so large that the filter can consist simply of a capacitance-resistance network shown by condenser  $C_1$  and resistor  $R_1$ ; two diodes are used to shape the pulse instead of one, as in Fig. 3, this arrangement presenting a higher impedance to the output of  $V_1$ . In both circuits the two output voltages are combined by applying them to opposite ends of potentiometer  $R_2, R_3$ , and taking the output from the junction of  $R_2$  and  $R_3$ . The ratio of  $R_2/R_3$  is adjusted so that the voltage from the anode of  $V_1$  suffers the requisite attenuation. (It should be noted that this method of combining the two voltages results in an additional loss of two-to-one in signal voltage.) The total resistance of this potentiometer can conveniently be about 1 megohm.

Suggested component values are shown in Fig. 4 for a modulation band of 10kc/s and a high-frequency bandwidth of, say, 200 kc/s.

There is an alternative method by which substantially the same principle can be applied. Referring again to Fig. 1(b), it will be recalled that the effect of removing the negative "overswing" from the noise pulse as it emerges from the high-pass filter is to restore to it the low-frequency

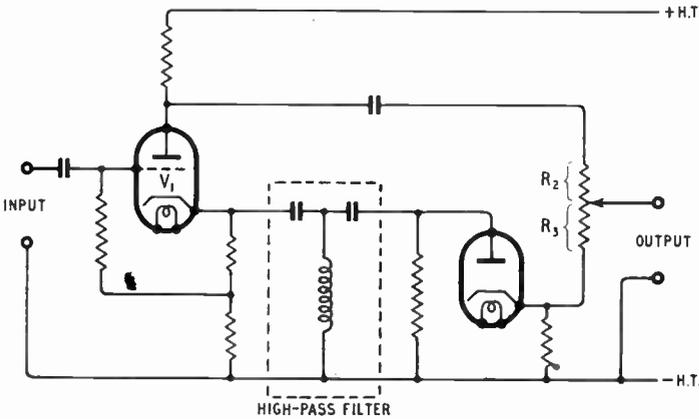


Fig. 3. Possible arrangement of a practical circuit.

pulse. This has the effect of distorting the noise pulse, as shown in Fig. 1(b). (The distortion can be seen by comparing with the dotted line in Fig. 1(b), which shows a noise pulse free from the modulation wave but undistorted.)

The distorted noise pulse then passes to the pulse shaper, where the overswing is removed, thus restoring the pulse approximately to its original shape, although with a slight loss in amplitude, as shown in Fig. 1(c).

The restoration of the pulse shape must clearly be equivalent to the re-insertion of the low-frequency components of the pulse, and, hence, the output from the pulse shaper consists of noise pulses of slightly smaller amplitude, but otherwise equivalent to those originally present in the detector output. A second output from the detector passes to a phase inverter, where the sense of the modulation wave and noise pulse is reversed, and thence to an attenuator which is arranged to give the same loss in amplitude as that suffered by the noise pulse in its passage through the filter and pulse shaper. The output from the attenuator is shown in Fig. 1(d).

which will perform the functions described above, differing, for example, in the form taken by the high-pass filter, the method of re-shaping the noise pulse, and the method of combining the output voltages. Two possible

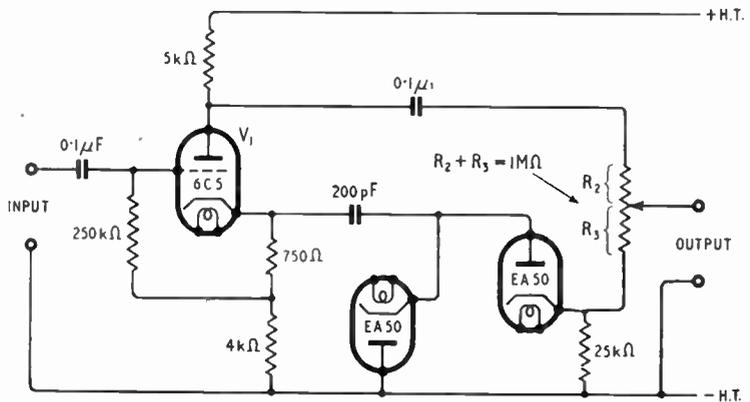


Fig. 4. An alternative circuit arrangement.

arrangements are shown in Figs. 3 and 4. In both these circuits the valve  $V_1$  performs the two functions of inversion of the signal, and provision of a low-impedance source to feed the high-pass filter. In Fig. 4 it has been assumed that the ratio of the high-frequency

components which were removed by the filter. It may be deduced, therefore, that this negative "overswing," i.e., that part of the waveform below the zero axis in Fig. 1(b), must contain the low-frequency components in anti-phase. Hence, if the pulse-

shaping circuit is arranged to remove the upper part of the waveform of Fig. 1(b), and the residue is then combined with the original

trates the small number of components with which the circuit can be built. For the successful operation of this circuit, however,

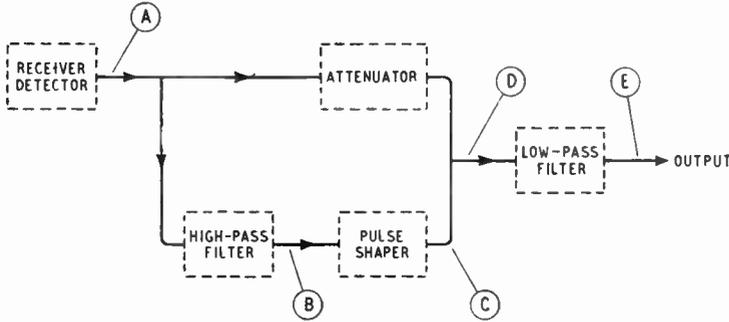


Fig. 5. Functional diagram of a variant of the circuit. The letters A, B, C, etc., refer to the points at which the waveforms of Fig. 6(a), (b), (c), etc., respectively, are observed.

waveform, this time without phase inversion, but with a suitable reduction in amplitude, the low-frequency components in the original noise pulse will be cancelled. The remaining high-frequency components can then be removed by a low-pass filter.

A functional diagram of this alternative arrangement and the waveforms appearing at various points in the circuit are shown in Figs. 5 and 6 respectively. A further note is necessary concerning the low-pass filter of Fig. 5. It is true that if the high-pass filter is designed to cut off at a frequency in the region of the upper limit of audibility, the noise components remaining at the output of the circuit will be above the audible range, and the loudspeaker, or indeed the human ear, would function effectively as a low-pass filter. However, any distortion taking place, due to valve non-linearity, in the amplifiers feeding the loudspeaker would result in the reintroduction of audible-frequency noise components. It is therefore very desirable that a low-pass filter should be provided to remove the high-frequency noise pulse components immediately after the combination of the original and re-shaped noise pulses, and before any further amplification takes place.

Again, it is possible to devise many circuits which will perform the functions indicated in Fig. 5. The circuit shown in Fig. 7 is of interest, however, since it illus-

trates the small number of components with which the circuit can be built. For the successful operation of this circuit, however, it is necessary that the output impedance of the detector be very low, possibly as little as 1,000 ohms, if the output waveform of the detector is not to be distorted

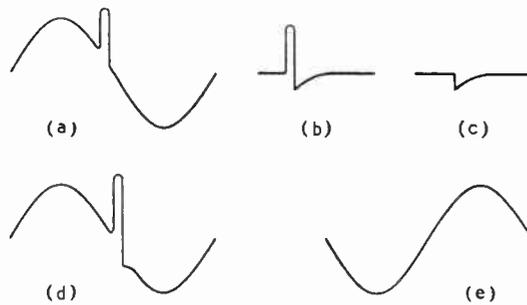


Fig. 6. Waveforms appearing at various points in Fig. 5.

by the severe loading imposed by the filter and diode combination. This low impedance will cause a considerable loss in gain, and in practice it would be preferable to use a cathode follower to feed the filter and diode.

It should be noted that in all the circuits described it has been assumed that the output from the receiver detector is in the positive sense. The necessary changes for negative output from the detector will be quite obvious.

**Experiment.**—A simple receiver, incorporating a circuit similar to that of Fig. 4, was built to test the effectiveness of the system. It consisted of two radio-frequency amplifier stages, a diode detector, audio-frequency amplifier and output stage. The

radio-frequency amplifiers were tuned to 41.5 Mc/s (the frequency of the sound transmission of the B.B.C. television service) and had a bandwidth of about 200 kc/s. Impulsive noise was generated by means of an ordinary spark coil located near the aerial. The reduction in noise output, as measured by an "average" type rectifier meter, was 24 db. Subjectively, the improvement was such that an almost unintelligible noise became a programme of reasonable entertainment value.

The circuit also operated satisfactorily on other interference, such as from motor car ignition systems, although precise measurements were not made.

On occasions bursts of interference have been observed on which the circuit has not been effective. Whilst it was not possible at the time to take oscillograms, it was presumed that this particular noise consisted of

pulses of much longer duration, and, hence, the high-class filter and pulse re-shaping circuits were not able to operate satisfactorily. Fortunately this form of interference was found to be comparatively rare.

**Conclusion.**—It is believed that this method of reducing the effect

of impulse noise in amplitude modulation receivers represents a new approach to the problem. It will be seen that the only restriction imposed on the noise amplitude is that it shall be large enough to operate the pulse-

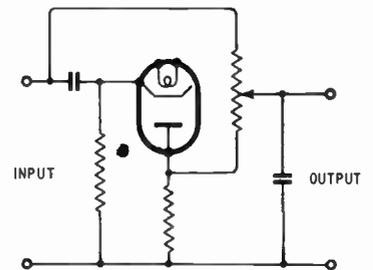


Fig. 7. A practical arrangement of Fig. 5.

shaping circuit correctly. No restriction exists on the ratio of the amplitudes of the noise pulse and the incoming signal.

In a recent article, Nicholson<sup>2</sup> suggests that frequency modulation offers little advantage over

<sup>2</sup> "Comparison of Amplitude and Frequency Modulation," M.G. Nicholson, *Wireless Engineer*, July 1947.

amplitude modulation if the two systems are compared under similar operating conditions. He himself describes a new noise limiter by means of which an amplitude modulation receiver may be made superior to one for frequency modulation in its ability to discriminate against impulse noise. The circuits de-

scribed here achieve a similar object and will normally entail the use of less additional components in the receiver. It is probable that the overall cost of an amplitude modulation receiver, incorporating these circuits, would be less than that of the equivalent frequency modulation receiver.

# ELECTRONIC CIRCUITRY

## Selections from a Designer's Notebook

By J. McG. SOWERBY (Cinema Television, Ltd.)

**PHASE** splitters are widely used in audio amplifiers and were treated in some detail in this journal<sup>1</sup> some time ago. The notes that follow are merely disconnected jottings on a few points which, although not original, may be of interest to some readers.

### Some Notes on Phase Splitters

One of the most widely used phase splitters is known as the "concertina" and is shown in Fig. 1(a). In this circuit a triode, V, has equal anode and cathode loads and these are effectively in series. Consequently, any signal current in the valve passes through both resistors and so equal output signal voltages are obtained at anode and cathode. The arrangement gives a gain of little less than one (usually about 0.9) between input and either output. It has the advantage that the balance of the output voltages depends only on the maintenance of equality of anode and cathode resistors. At (a) the bias for the valve is determined by  $R_b$ , which is small compared

with  $R_k$ . Consequently the cathode of V is positive to earth by anything up to 100 or more volts. This being so it seems logical to couple the grid of V directly to the previous anode as shown at (b), then the cathode potential of V will be very nearly the same as the anode potential of the previous stage. Besides saving three components the coupling eliminates any phase shift at low frequencies and this is often advantageous if V is within a feedback loop, as in Mr.

stage. The anode-cathode voltage of V is nearly  $V_{ak} = (V_b - 2V_a)$  where  $V_b$  is the supply h.t. potential. From this we see that it is reasonable to design for  $V_a = V_b/3$  or less. Even so, it is wise to ensure from the valve curves that no grid current flows in V even when  $V_a$  is 30% more than the design figure, making due allowance for the resultant reduction of  $V_{ak}$ . This arises because some variation in  $V_a$  is to be expected with time and with valve replacement.

Fig. 2(a) shows a cathode-coupled phase splitter in which the usual positive bias is supplied from a fixed potentiometer across the h.t. supply. A more economical arrangement is shown at (b)

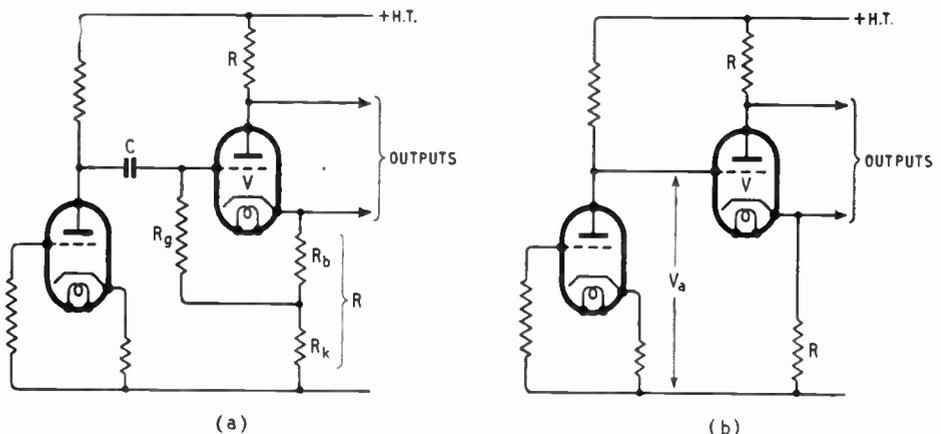


Fig. 1. "Concertina" phase splitter: (a) a.c. coupled, (b) direct coupled.

Williamson's amplifier<sup>2</sup>. To a sufficiently close approximation the current in V can be taken as  $i_a = V_a/R$  where  $V_a$  is the anode potential of the previous

using fewer components, in which the positive bias is the anode potential  $V_a$  of the previous stage. Both grids are obviously maintained at the same standing potential, but the signal is applied only to the grid of V, as the

<sup>1</sup> W. T. Cocking, *Wireless World*, Jan., Feb., March, April and May, 1948.

<sup>2</sup> D. T. N. Williamson, *Wireless World*, Aug. 1949, p. 282.

**Electronic Circuitry—**

"smoothing" circuit CR prevents the signal reaching the grid of  $V_2$ . Similar time constants are used in the two circuits, and at medium and high frequencies the performances are identical. At very low frequencies, however, CR in circuit (a) merely leads to attenuation of both outputs, whereas (b) reverts to a push-push output of low gain as the frequency approaches zero, because the grids of  $V_1$  and  $V_2$  both follow the anode potential of the previous stage, and are in phase with one another.

may have undesirable results on subsequent stages.

In designing the circuit of Fig. 2(b) the anode current of  $V_1$  or  $V_2$  may be taken to be  $V_a/2R_c$  and the anode-cathode potential of each valve will be  $V_{ak} = V_b - V_a(r + R_a/2R_c)$  nearly. Previous remarks concerning grid current in the circuit of Fig. 1(b) apply here too.

Some designers are disinclined to use the "concertina" and cathode-coupled circuits as both involve operating the cathode of a valve at a considerable potential to earth. A commonly used

necessary to make  $R_{a1}$  less than  $R_{a2}$  to obtain equality of output voltages. On analysis it turns out that

$$\frac{R_{a1}}{R_{a2}} = \left[ 1 - \frac{r_a + R_{a2} + 2R(r + r_a/R_{a2})}{r_a + R_{a2} + (\mu + 1)R} \right]$$

where  $\mu =$  amplification factor of either valve  
 $r_a =$  a.c. resistance

for equal signal output voltages.

In practice it is convenient to

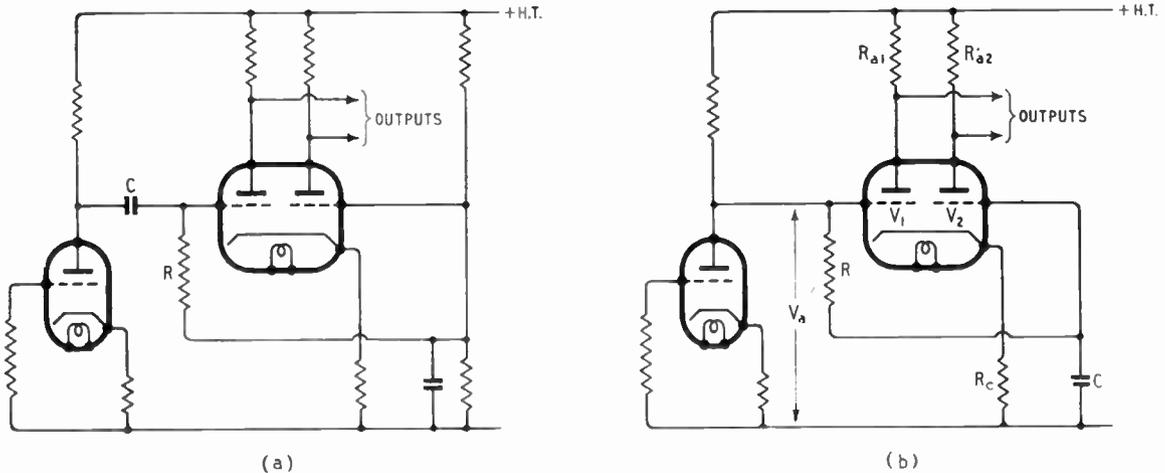


Fig. 2. Cathode-coupled phase splitter with two types of coupling.

An advantage of circuit (b) compared with (a) is that a large value of C can easily be used—say  $2\mu\text{F}$  or more. Such condensers are usually of the paper-block-in-metal-can type and if used in the circuit at (a) may lead to loss at high frequencies due to the additional stray capacitance at the grid of  $V_1$ . One such condenser measured by the writer recently had a condenser-can capacitance of more than 100 pF, and if such a condenser is fixed to an earthed metal chassis and used as a coupling condenser in (a), that 100 pF will appear between the grid of  $V_1$  and earth. In the circuit at (b) this condenser-can capacitance will only add to C, and so be slightly beneficial.

The circuit of Fig. 2(b) has a disadvantage inasmuch as variations in the h.t. supply potential may lead to a large push-push output from the splitter, and this

alternative is the "see-saw" circuit. Another circuit which might be regarded as a combination of the cathode-coupled and see-saw arrangements if available, however, and is shown in Fig. 3. It will be remembered that the cathode-coupled circuit of Fig. 2 tends to maintain equality of signal currents in the two valves, and that exact equality is approached as  $R_c$  is increased, eventually becoming exact when  $R_c$  is infinite. The circuit of Fig. 3 behaves in exactly the same way, provided that we substitute R for the  $R_c$  of Fig. 2. However, in this case there must always be some signal voltage across R (to operate the grid of  $V_2$ ) and this signal will be in phase with that obtained from the anode of  $V_1$ . Consequently, however large R may be made to achieve equality of signal currents in  $V_1$  and  $V_2$ , it will always be

make  $R_k$  the common bias resistance for the two valves; this largely controls the direct current through the two valves and hence through R. Next, R is made as large as possible having due regard for the voltage drop across it.  $R_{a2}$  is then fixed, and  $R_{a1}$  calculated. The time constant  $C_1 R_{g1}$  is calculated as for a normal amplifier stage, and it is preferable to make  $C_2 R_{g2}$  several times larger than  $C_1 R_{g1}$  to maintain a phase displacement of  $180^\circ$  between the output signals at low frequencies.

The gain from input to either output (when  $R_{a1}$  is properly chosen by means of the preceding equation) is

$$A = \frac{\mu R_{a1}}{r_a + R_{a1} + \frac{R_{a2} - R_{a1}}{R_{a2} + R} R}$$

Substitution of practical values indicates that this circuit yields a

gain approaching twice that for the ordinary cathode-coupled circuit of Fig. 2 when  $R_c = R$ , and the other constants are the same in both circuits. In this respect the splitter of Fig. 3 is more like the see-saw from which a correspondingly increased gain can also be obtained, and it also suffers from the disadvantage that any disturbances on the h.t. line are fed preferentially to one grid, so that the arrangement should be used only with a well-smoothed supply.

In using the circuit of Fig. 3 and see-saw circuits one point needs watching. A common bias resistor is quite in order as long as it is bypassed. If it is not, then as there is feedback from both anodes to one grid, and feedback from one valve to the other via the cathode resistor, an unfortunate accidental combination of stray capacitances may easily turn either circuit into a cathode-coupled multivibrator<sup>3</sup> at high frequencies. A relatively small cathode bypass capacitor will stop this trouble completely, but may also lead to a non-uniform

frequency response. By using a capacitor of more usual value—20 to 100  $\mu\text{F}$ —these faults are

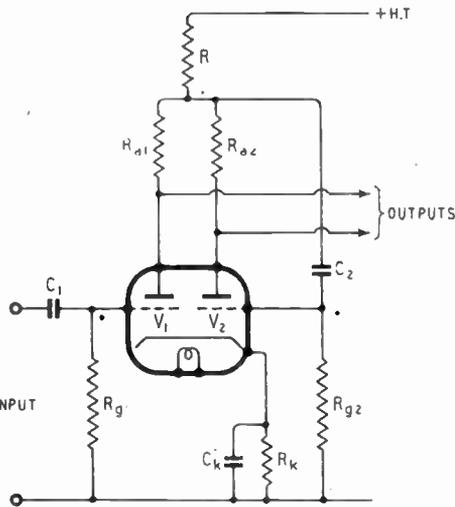


Fig. 3. Common-anode-coupled phase splitter. Typical values:  $V_1, V_2, = 6\text{SN}7, R_{g1} = R_{g2} = 1\text{M}\Omega, R_k = 1.8\text{ k}\Omega, R = 39\text{ k}\Omega, R_{a1} = 80\text{ k}\Omega, R_{a2} = 100\text{ k}\Omega, C_1 = 0.05\ \mu\text{F}, C_2 = 0.25\ \mu\text{F}, C_k = 20\text{-}50\ \mu\text{F}, \text{h.t.} = 350\text{V}$ . Gain (input to one output) = 17 (approx.).

both removed. If this is omitted and "multivibration" takes place, the amplitude may be quite low and of quite high frequency—100 kc/s or more—and so difficult to find except with an oscilloscope, of low input capacitance, or a high-impedance valve voltmeter,

this varies the leakage field used for focusing. Unequal adjustment to the screws tilts the core tube and so moves the picture on the tube and provides a shift control.

Because focus and shift are carried out by the same three screws the two are interdependent but, in practice, the adjustment is by no means difficult. The focus obtainable on a test was as good as with an electro-magnet and is free from "warming-up" drift. It is not, of course, free from any change brought about by variations of the tube e.h.t. supply. The magnet has a much larger external field than the usual electro-magnet and it may be necessary to take this into account if valves are mounted very close to it.

There are three types of magnet; the R17 at 21s for tetrode tubes, the R20 at 22s 6d for triodes at medium e.h.t. voltages and the R25 at 25s for triodes operating at high voltages. The makers are Electro Acoustic Industries, Ltd., Stamford Works, Broad Lane, Tottenham, N.15.

### Portable Radio-Amplifier

DESIGNED for use in small factories, schools, etc., the "Hadley" portable radio-amplifier is housed in a metal case 18in x 9in x 9in and provides facilities for relay-ing radio programmes, gramophone records and microphone announcements.



"Hadley" portable radio-amplifier.

There is a choice of four pre-selected radio programmes, and both radio and gramophone are automatically cut off when the microphone is switched on. A self-contained oscillator provides a push-button-controlled tone for time signals or fire alarms.


A small built-in loudspeaker unit with independent volume control is provided for monitoring.

The power output is 20 watts and the mains consumption is 120 watts at 200-250 V, 50-60 c/s. The price, including tax, is £52 7s 9d and the makers are Hadley Sound Equipment, 587-9, Bearwood Road, Smethwick, Birmingham, 17.

## NEW PRODUCTS
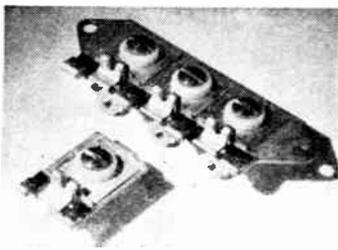
### Mica Trimmers

THE new "M" type trimmer introduced by the Plessey Company, Ilford, Essex, is of particularly robust construction and very stable in operation. The construction of the multiple units simplifies mount-



Single and multiple units of the Plessey "M" type trimmer.

ing and permits economy in space where a common earth is acceptable. Single capacitors are also available.

Best quality mica, with a power factor of approximately  $10 \times 10^{-4}$  measured at 1 Mc/s, is used and the insulation resistance is greater than 1,000 M $\Omega$  at 500 V d.c. Capacitance range is 5-65 pF.

### P.M. Focus Unit

THE Elac permanent magnet focusing unit replaces the commonly used electro-magnet for focusing the electron beam of a cathode-ray tube. It comprises a ring-type permanent magnet with fixed end cheeks and an inner core tube which is adjustable by three screws. Equal adjustments to the screws move the core tube along the axis and so vary the air gap between the tube and the front end cheek. In its turn

## Why we designed the

# STEREOPHONIC AMPLIFIER

In our search for really high quality we had already built an amplifier of .01 per cent. distortion and 40 times damping factor, which we believe is the finest straight amplifier in the world. Unfortunately we have been unable to obtain a single speaker which will faithfully reproduce the whole range, and when used to drive twin speakers via a cross-over network these introduced more distortion and peaks than could be tolerated. From this we drew the following conclusions.

The attainment of really high quality had always been marred by defects at the speaker end of the reproducer which were:—

- (a) The inability to cover the whole audio range with handling capacity of 8 to 10 watts at the lowest piano frequency of 26 cycles.
- (b) The interference caused by the Doppler effect, or where this has been minimised, the lack of speech coil feedback and damping at frequencies where that particular speaker should be silent.
- (c) The variation in acoustic power at the ends of the audio band, or the difference in efficiency of the two speakers when fed by cross-overs after the amplifier.
- (d) The resonance of the choke and condenser network at various frequencies which in one case gave a variation of 5 ohms to 105 ohms for a nominal 15 ohms impedance.

All these points were considered, and an amplifier was then designed and built to overcome all those deficiencies, the audible results exceeded expectations and a stereophonic effect was noticed on some records and the amplifier accordingly called "Stereophonic."

The requirements of triode cathode follower and 8 to 10 watts output is best met by PX4's, since their mains consumption is low compared to pentodes strapped as triodes and heater hum does not bother a cathode follower. A single valve is capable of the equivalent acoustic requirements at the higher frequencies. The cross-over is fitted in the middle of the amplifier where it is not concerned with power transfer and does not introduce resonance or distortion.

Superlatives fail in the description of the quality of reproduction from this new amplifier, but may we just say it gives the finest quality reproduction of any unit, some costing almost a thousand pounds, that we and many others have heard. This is due to the lack of resonances from the loud speakers, with the result that needle scratch is barely audible, even with the full audible frequency range.

Unlike most reproducers where bass is reduced to ensure good unmodulated treble it is possible in this case to retain the full richness of the bass without interfering in any way with the treble response, and the lowest organ note to the highest strings can be reproduced at the same time without modulation distortion. This high quality is maintained even at whisper strength to an abnormal degree.

In these few words we cannot convey just how good this quality of reproduction really is, but we do invite you to a demonstration, and if possible bring your own well-known test records, upon which to base your judgment

*Chassis complete with valves*

**Price 36½ gns.**

**VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19**  
Telephones LIB 2814 and 6242-3 Telegrams "Vortexion, Wimble, London"

# DECEMBER — MONTH OF GOOD CHEER

And why not? We are cheered by the knowledge that our products will bring pleasure to crowds of good people, the world over, and that is cheery compensation for our 20 years concentration on the design and production of Quality Equipment—not purely for the money, but for the sheer fun of producing something better.

May we also wish a Merry Christmas to all fellow enthusiasts?

**TONEMASTER AMPLIFIER**

**R-N-W PICK-UP**

**DX PLUS 2 RADIO UNIT**

**CONCERT GRAND—**

**SUPER LOUDSPEAKER**

They are sound by name  
and nature—  
uplifting in quality.

Write for details of our latest ideas—better still call at

OUR NEW OFFICE and SHOWROOM

125, OXFORD STREET, LONDON, W.1.

GERRARD  
8 7 8 2

## Sound Sales Limited



### PLAN YOUR CAREER

RADIO • TELEVISION  
and other INDUSTRIAL  
ELECTRONIC subjects  
ELEMENTARY & ADVANCED COURSES

**WRITE FOR FREE BOOKLET** summarising careers available in Electronics and giving particulars of Courses offered by E.M.I. Institutes.

The booklet contains full details of elementary and advanced HOME STUDY and DAYTIME courses in Radio, Television, Telecommunications and Industrial Electronics.

Courses ideal for those seeking recognised qualifications are also available.


Payment for tuition can be made in easy instalments if required.

Write to Dept. 16A

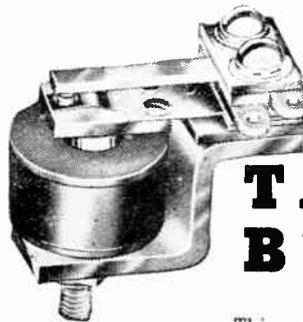**E.M.I. INSTITUTES**

43, GROVE PARK ROAD, LONDON, W.4. CHiswick 4417/8

Associated with  
"H.M.V."  
MARCONIPHONE  
COLUMBIA  
ETC.




### THE TAYLOR BUZZER

This small buzzer has a number of applications, such as continuity testing, a signal for telephones and communication circuits, or as a source of interrupted supply for bridge circuits.

It operates at approximately 500 cycles per second, and the consumption at 3 volts is very approximately 100 mA. Also it will operate satisfactorily from 4 volts A.C. 50 cycles.

**TAYLOR ELECTRICAL INSTRUMENTS LTD**  
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND  
Tulophone SLOUGH 21381 (4 lines) Grams & Cables TAYLINS, SLOUGH

E.147

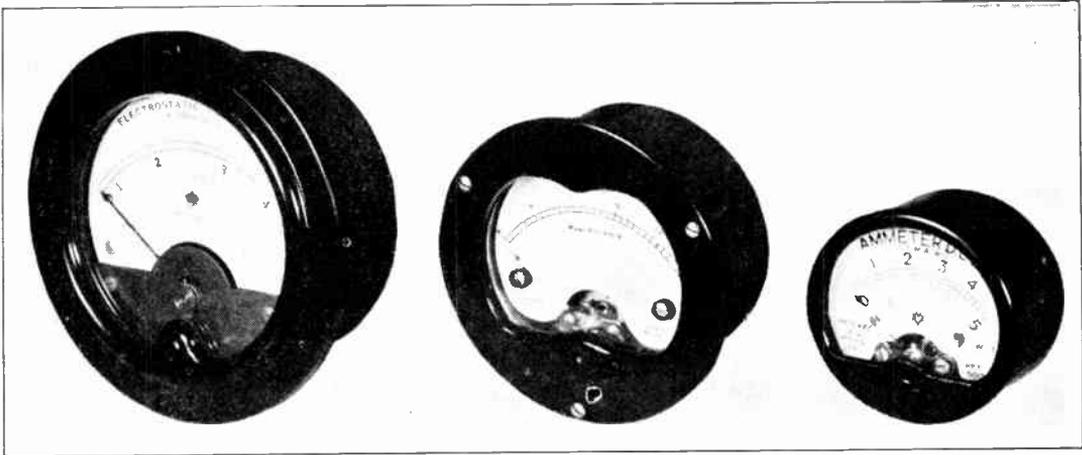

## POINTER INSTRUMENTS

### Types for Test Gear

By **E. H. W. BANNER**,  
M.Sc., M.I.E.E., F.Inst.P.

**I**NDICATING instruments of the pointer type are commonly incorporated in test gear, using the term widely to cover valve voltmeters, oscillators, bridges, attenuation meters, Q meters, output meters, etc. They are included for one of two purposes; they may provide the final means of indication, as in valve voltmeters, Q meters, etc., or they may be merely a means to an end such as assisting the correct setting of voltage and current in oscillators, bridges, etc. In the former case a larger size is normally required than in the second, where several instruments may be needed, all ancillary to the final measurement or other output.

Specifications for indicating instruments include B.S.89:1937 (now under revision).—This covers chiefly performance, but also includes desirable constructional and other features. Dimensions are not covered in it, but an inter-Service Specification, K.113, is largely complementary, and gives dimensions for overall size and fixings. This renders instruments interchangeable as regards mounting, while leaving individual designers free to modify the movement design as required.

An inter-Service Specification for hermetically-sealed instruments for use in all climates from tropical to arctic is in preparation and has been circulated in draft

form. Instrument sizes include 2, 2½ and 3½in, all in metal cases for flush mounting.

Tests specified include a full 84-day tropical cycle, involving dry and wet heat, dust, water immersion, mould growth, etc. Vibration and bumping tests are prescribed, as are many details of design and construction.

Another inter-Service specification dealing with equipment under extreme physical conditions is K.114, "Climatic and Durability Testing of Service Telecommunication Equipment."

The sizes in most demand for test gear are the so-called miniature series. These started with the 2½in (a nominal size), which is a compromise between small size and length of scale. The latter is just sufficient for a reading accuracy of 1 per cent of full-scale deflection near full scale. Next came variations up and down; a 3½in type which gives a better reading accuracy, as well as enhanced

scale visibility, and a 2in pattern. This has a lower reading accuracy and so is hardly good enough for first-grade accuracy, but it is of great application where small size is of more importance than accuracy. During the 1939-45 war Lipman, of Nalder Bros. and Thompson, Ltd., produced a sub-miniature design in which the permanent magnet is inside the moving coil, and only a small iron ring surrounds it. This is a 1½in instrument, and is extremely useful where minimum size and weight are the most important features and accuracy is second. Finally, an extension in the upward direction is the 4in, which really overlaps the former switchboard range of instruments, but is in a moulded case instead of metal as are most larger switchboard instruments. All these are round-pattern instruments, usually available for mounting either flush or projecting, flush being most common; the 4in may be in a square case or have a square flange on a round body, the latter also applying to the 2in.

In addition to the above sizes to K.113 another maker has for years supplied a nominal 2½in instrument which is larger than the K.113 dimensions, but which has the advantages of a longer scale—2½in—more room inside for additional ranges and higher self-contained ranges. It is even

Typical instruments of the 2in to 3½in types are illustrated above.

### Pointer Instruments—

possible to include an internal range-changing switch.

Shapes, other than round and square, include a sector  $2\frac{1}{2}$  in, projecting; and edgewise, horizontal and vertical mounting, flush. None of these is covered by K 113, but each has applications. Sector instruments have longer scale length for given area of instrument front than a corresponding round type. For minimum panel space, therefore, the edgewise pattern scores, but it has the limitation that it is necessary to use a smaller scale arc to avoid parallax.

The  $4\frac{1}{2}$  in type is not covered by any Specification. In some makes, however, it comprises a square flange, containing the pointer and dial, with a round body mounted flush in a hole which is standard for the  $3\frac{1}{2}$  in flush pattern. In this way it partly complies with K 113, and its mounting is interchangeable, except that the panel space is greater, which leads to wider spacing for adjacent instruments. The projecting pattern  $2\frac{1}{2}$  in and  $2\frac{1}{4}$  in sizes are also manufactured with a two-pin plug for socket mounting, which makes their rapid removal and changing easy. Illumination is provided in some instruments on the market. Generally, the lamp is external, with a window in the instrument case, and for ease of renewal this is preferable to an internal lamp. The  $4\frac{1}{2}$  in flange instrument mentioned above may be of this type, with a translucent dial.

For an instrument such as a valve voltmeter, where the instrument dial is the only part of real interest to the user, the  $4\frac{1}{2}$  in, or the  $3\frac{1}{2}$  in, are the two best sizes, for they give maximum scale length and reading accuracy. Many of these instruments are so mounted in output meters, Q meters, X-ray monitors, etc.

### Moving-coil Meters

The moving-coil type is nearly universal for direct-current measurements, but for high-voltage ranges the electrostatic voltmeter is often preferable, especially as it requires no current, and so has, in effect, infinite ohms-per-volt resistivity. Shunted

moving-coil instruments usually have a volt drop of 75 mV, in accordance with B.S. 89, but this is not necessarily the case for low ranges with internal shunts. As voltmeters, resistivities of 200 and 1,000 ohms per volt are common, with 5- and 1-mA movements respectively, but as microammeters down to  $5\mu\text{A}$  full scale are made by some firms, they may be made into voltmeters with resistivities up to 200 kilohms per volt.

Where mains voltage or current is to be measured, the moving-iron type of movement is the best, but it is not made in all the sizes and shapes given above. Minimum ranges for miniature instruments are about 1 A and 10 V; below these ranges rectifier instruments are available down to a few

microamps and 1.5 V, but the limitations, referred to later, should be noted. Also available with the moving-iron movement for mains use is the induction type, miniature sizes of  $2\frac{1}{2}$  and  $4\frac{1}{2}$  in being available in round-pattern cases. The great advantage of this type is, of course, the long scale arc of about  $330^\circ$ , which provides a scale length of  $5\frac{1}{2}$  in in the  $2\frac{1}{2}$  in instrument.



Marconi Instruments H.F. Circuit Magnification Meter using a square-face instrument for its built-in valve voltmeter.

For very high voltages the electrostatic type is again often to be preferred as for d.c.; it has a lower bulk than any electromagnetic type with its associated resistor or transformer. The current consumption of the electrostatic voltmeter on a.c. is also very small, depending on the capacitance, and this current is wattless.

At audio frequencies the rectifier instrument is supreme, with its wide frequency range up to about 100 kc/s. Rectifiers are being developed for the Mc/s range, apart from the use of crystal rectifiers for h.f. circuits. Ranges of microamps and milliamps are directly available and higher ranges by current transformers. Thermal instruments may also be used, with the advantage of independence of waveform, but their lack of robustness restricts their use when rectifier instruments will serve.

### High Frequencies

At high frequencies the thermal types have the field, with a very high upper frequency limit. They are nearly equally accurate on direct current, and completely independent of waveform, reading the true r.m.s. value. The thermocouple type is better than the old hot-wire type, although more expensive. Generally ranges from 10 or 20 mA upwards are available. All thermal instruments suffer from a lack of robustness due to the low overload capacity, as the working wire is heated to a temperature approaching its melting point at full-scale deflection.

There is a tendency on the part of many engineers to specify and use rectifier instruments for all a.c. circuits. But as already mentioned, moving-iron instruments are better for normal ranges at power frequency, partly because of the lower cost, but mainly because the rectifier instrument reads the mean value of the rectified current and as r.m.s. value is normally required, and the instrument is so calibrated, there is a waveform error which may be quite serious, although frequently overlooked. Further, the rectifier has an effect on the a.c. circuit, when the circuit is a low-power one, due to the resistance of the instrument varying with current and not remaining constant as for other types. At low currents the resistance, or impedance, is many times that at full-scale current. On the other hand, the advan-

tages include the good damping and snappiness of response of the moving-coil instrument, and lower consumption and lower minimum ranges than for other a.c. instruments. Most instruments of this type have a self-contained metal rectifier, either copper-oxide or selenium, but any moving-coil instrument may have an external rectifier. This is of use for the 1½ in instrument, where there is no room inside the very small case for a rectifier.

Other factors to consider in specifying a suitable instrument include whether the panel on which it is to be used is ferrous or non-ferrous. Most miniature instruments are in moulded cases and have no internal shielding, so that there is a tendency to stray field error. This may be shown up by a steel panel, hence the need for having an instrument

calibrated on a panel similar to that on which it is to be used. Electrostatic voltmeters may be similarly affected by electrostatic fields and a metal panel, not only a ferrous panel, will act as a screen and may affect the readings if it is not taken into account in the calibration. It may also be affected by local high-voltage fields.

Scales and scale marking require much care to ensure maximum legibility and to give all necessary information, while excluding extraneous matters of no interest to the user. B.S.89 lays down scale proportions, relative lengths of scale marks, etc. Scale factors of 2 and 5 are recommended as a compromise between the minimum number of ranges to overlap and the maximum percent scale reading for any numerical quantity. A scale factor of 3

is not recommended, although it has applications to cell-testers.

It is generally desirable to indicate on the scale the type of the instrument, or its range of measurement. A linearly scaled instrument marked "Milliamperes" and scaled 0-10 may be either moving-coil or rectifier, and so should be unmistakably marked which. Such an instrument could either be scaled "Milliamperes D.C." (or A.C.) or else a symbol showing d.c. or a.c. used, or the symbol for a rectifier instrument added, preferably both, as an a.c. ammeter may be moving-iron or rectifier and not always readily distinguishable by its scale shape. Symbols for this have been proposed for international use and have been adopted in some countries, and by some makers here, for many years. Their general employment is to be commended.

## RECORDS UNDER THE MICROSCOPE

### *Microphotography as an Aid to Research*

At a meeting of the British Sound Recording Association, on 21st October, C. E. Watts described the apparatus he uses to obtain the very instructive microphotographs of record grooves, cutters and styli for which he has acquired a well-deserved reputation.


By the use of polarized light and careful adjustment of the angle of incidence, it is possible to bring into relief any effects which may require prolonged and detailed examination; for example the angle of ejection of swarf from the cutter, its subsequent spontaneous expansion and the reasons for the generation of subsidiary shavings. Similarly, the walls of the groove can be examined for signs of wear, and the lines of contact (if any) between the needle tip and the groove walls during playback can be traced.

Mr. Watts has also devised a means of viewing the contact between stylus and groove under actual playing conditions, and he has stated that on loud passages "daylight" could be seen at these points for most of the time, even with the lightest of modern lightweight pickups. The only arrangement showing any semblance of continuous contact consisted of a fragment of sapphire broken from the extreme tip of a stylus and cemented to a segment of watch hair spring.

The surprising thing was that the lack of continuous contact did not seem to have any detectable effect on the quality of even the best recordings, as judged by critical and experienced listeners. It came as something of a shock to many of these people to be shown the movement of the stylus relative to the groove after having praised the

quality of a recording. Was it possible that the quality of modern disc recordings is better than the ear can appreciate.

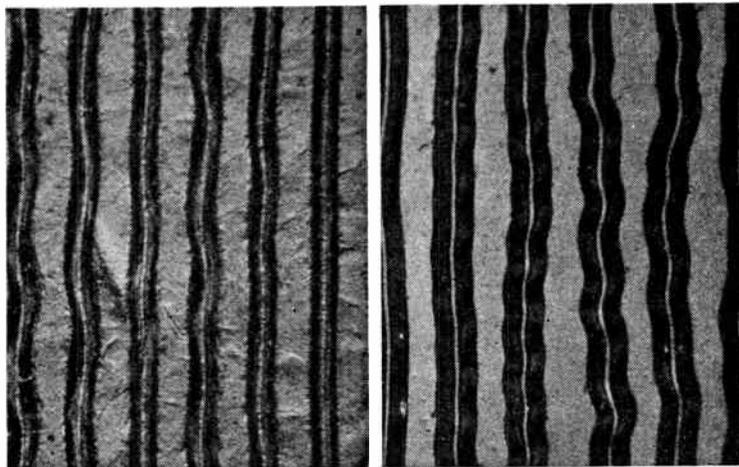That such a question should ever arise was in itself a tribute to the value of microphotographic methods in recording research, and provided the stimulus for continued investigation along these lines.



Two untouched microphotographs by C. E. Watts illustrating 50 years' progress in disc recording. On the left is an early Berliner pressing (circa 1899) and on the right a modern (1949) pressing.

# Unbiased

By FREE GRID

## On Exhibitions

COMPARISONS are said to be tedious but are none the less useful on that account, and in any case who am I to discard what great men like Attlee and Churchill both freely use? The comparison which I wish to draw is between the running of Radiolympia and two other exhibitions which happened to have their doors open at the same time as the wireless show. I refer, of course, to the exhibition of the Royal Photographic Society and to the Motor Show.

Now both these exhibitions, which I studied in some detail, fell lamentably short of Radiolympia in two opposite directions. In the case of the photographic exhibition there was on show the results given by the apparatus which the photographic industry makes and sells, but no attempt was made to show the apparatus itself. In the case of the Motor Show the apparatus was exhibited but results in the shape of free rides for all were singularly lacking. At Radiolympia, on the other hand, not only was the apparatus exhibited, but the results obtainable from it were demonstrated for all to see or hear, as the case may be.

It is true that in the case of the photographic show no sordid charge was made for admission but we were all invited to disclose our identity by signing the visitors book and a somewhat expensive catalogue was brought to our notice by the presiding goddess. Fortunately, I had Mrs. Free Grid with me and she quickly dealt with the goddess and took entire charge of the proceedings rather too thoroughly, in fact, as I was quickly piloted past photographs belonging to the "Sep-



Quickly Piloted.

tember Morn" school of art.


My object in going to the Motor Show, apart from comparing it with Radiolympia, was to choose a car for a grandson who is expected to enter this world shortly. My daughter and son-in-law have journeyed specially to the land of dollars for the event so that he will be entitled to American citizenship. On his arrival in this country with his parents, who will, of course, retain their British nationality, he will be able to have immediate delivery of as many new cars as he pays for provided that he makes no attempt to sell them. I, as one of his duly appointed chauffeurs, will have the use of one of them. The idea is Mrs. Free Grid's, but I cannot help feeling that there is a snag in it somewhere.

At any rate, after all this it was with a great sense of relief that I arrived at the well-organized and racket-free radio show in which both apparatus and the results they gave were freely exhibited, and the former freely sold to all without subterfuge.
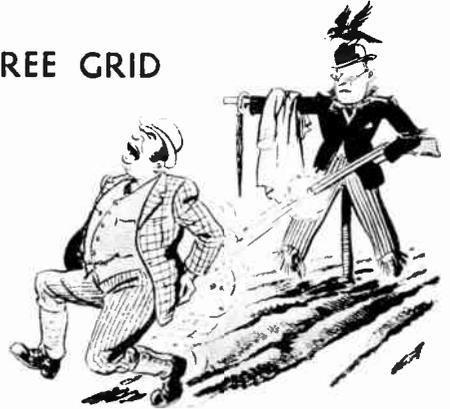
## Applied Science

ACCORDING to one of the more sober Sunday newspapers experiments are being made at one of our great airports to find a remedy for the danger caused by the collision of large birds with aircraft, which constitutes a very real menace. Apparently the trouble is particularly prevalent and exceptionally dangerous when aircraft are hurtling down the runway to take off or land.

A certain amount of success appears to have been had by taking advantage of the fact that birds, like dogs and certain other animals, can readily hear frequencies which are supersonic to human ears. Supersonic sounds, if I may use such a contradictory expression, are, therefore, generated which scare the birds without annoying the passengers. I cannot, however, see why a bird should be scared of a 20,000 c/s note and yet remain stolid and phlegmatic at hearing the appalling roar of the aircraft's engines, but doubtless my ignorance of ornithological psychology accounts for this. Unfortunately, the supersonic frequencies are disliked by dogs who set up a mournful





Painfully Pepered

howling which reminds superstitious passengers of banshees and causes those awaiting the departure of their planes to hurriedly cancel their passages.

Personally, I should have thought that the problem could have been solved by using simple radar beams which on striking the birds rebounded and thereby operated a series of shotguns suitably mounted in the nose of the plane and I offer this suggestion, without charge, to the harassed authorities. Doubtless they can improve upon it; but I do know what I am talking about as some time ago I was called into consultation by a farmer who was troubled with marauding birds. They treated the ordinary scarecrows with contempt and did the same even when loudspeakers, concealed in the clothing of each scarecrow and coupled to an outside in amplifiers housed in a nearby barn bellowed forth the B.B.C. Third Programme.


I quickly designed a series of radar scarecrows which were triggered off by the approach of intrepid and insolent birds, and in their turn triggered off a concealed shotgun. Unfortunately, the radar apparatus was no respecter or discriminator of persons and the farmer was well and painfully peppered one day when he approached too near one of them.

I offered to design for him and members of his staff a special I.F.F. unit which they could carry on their persons, the idea of this being that when a beam from a scarecrow struck them it caused an answering signal to be sent out which temporarily short-circuited the gun-operating mechanism. However, he was not long-sighted enough after the accidental peppering incident to proceed with the idea even though I pointed out to him that the radar scarecrow would deal impartially with either trespassers or birds.

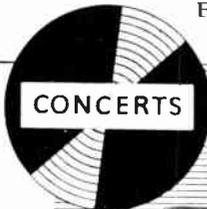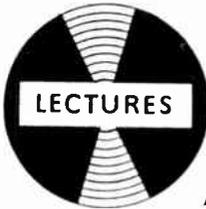

***If they are worth hearing . . .  
they are worth recording!***

Simple to operate and readily portable, the E.M.I. Portable Disc Recorder enables brilliant "on the spot" recordings to be made of outstanding events. Produced by E.M.I. technicians with 50 years' experience in recording, this new E.M.I. Portable Recorder is a remarkable technical achievement. Here in transportable form is a complete recording and play-back equipment designed to produce high quality recordings on lacquer blanks without demanding expert knowledge of recording technique. Operation is extremely easy and the equipment which is contained in three transportable cases needs 200/250 volts 50 cycles A.C. mains supply or a Car Battery and converter. Facilities for play-back and for sound amplification form an integral part of the Recorder. **RECORDING BLANKS:** EMIDISC Recording Blanks are ready for playback immediately after cutting. They are available in the following sizes—6", 10", 12", 16". **PROCESS BLANKS**—enabling the recording to be pressed in quantity, by E.M.I., are obtainable for 11", 12", 13", 17½" recordings.

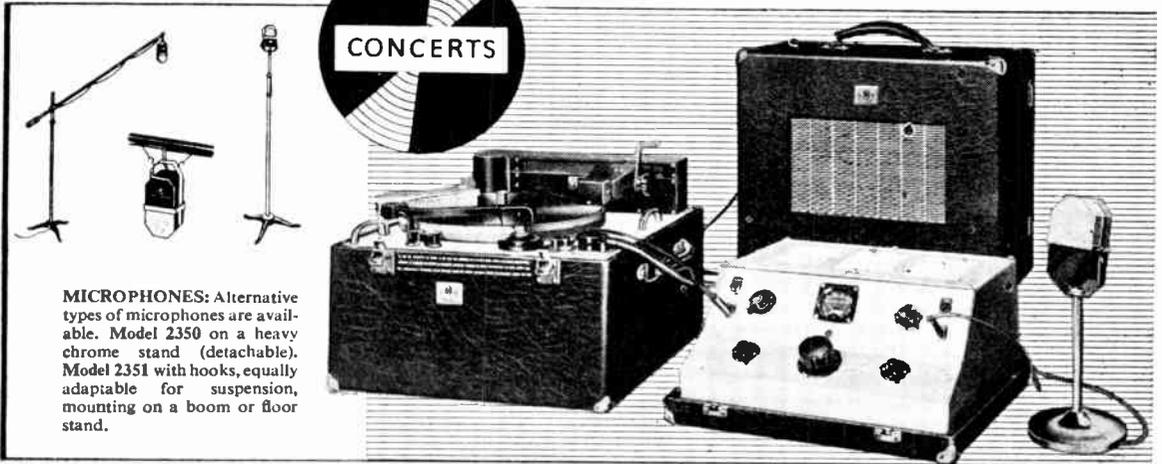


**MICROPHONES:** Alternative types of microphones are available. Model 2350 on a heavy chrome stand (detachable). Model 2351 with hooks, equally adaptable for suspension, mounting on a boom or floor stand.

*A descriptive leaflet giving full details of Model 2300, extra Microphones and Recording Blanks is available on request.*



**E.M.I. PORTABLE RECORDER** No. 2300

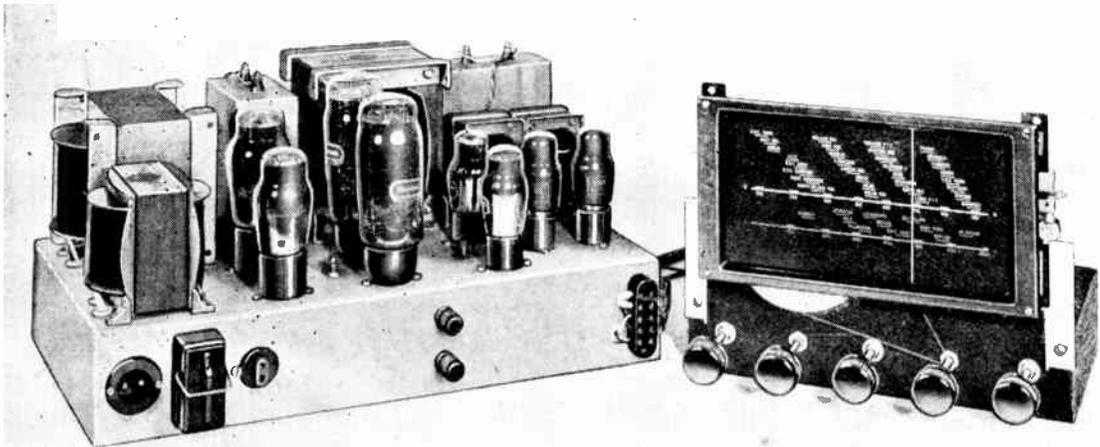**E.M.I. SALES & SERVICE LTD. HEAD OFFICE: HAYES, MIDDX.**



# GOODSELL

## HI-FIDELITY AMPLIFIERS

As described by D. T. N. Williamson in "Wireless World."

**ALSO HI-FIDELITY TUNERS & PRE-AMPLIFIERS**

Manufactured by **GOODSELL LTD., 40, GARDNER ST., BRIGHTON, SUSSEX** 'Phone : 6735

PRICES	
Amplifiers .. ..	from £19 19 0 } No Tax
Pre-Amplifiers ..	from £8 0 0 } Tax
Tuners with Pre-Amplifiers	£10 10 0 Plus Tax

Send for free illustrated brochure.

# LEARN MORE

**FREE BOOKLET**  
giving details of home study and daytime courses:—

**HOME STUDY**

- Practical Radio Receiver Servicing
- Basic Radio } for R.T.E.B.—
- Basic Television } "The practical man's diploma"

**DAYTIME**

- Principles and Practice of Radio—1 year
- Telecom. Engineering—2 years
- Electronics Engineering—3 years (including 1 year in E.M.I. Factories)

★ The value of E.M.I. Institutes correspondence courses is known the world over—large numbers of our students come from such widely scattered lands as India, Pakistan, Palestine, Ceylon and Europe.

Write to Dept. 16

## E.M.I. INSTITUTES

43, GROVE PARK ROAD, LONDON, W.4 Chiswick 4417/8

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.

E.148B

# BAKERS 'Selhurst' RADIO

PIONEERS OF MOVING COIL SPEAKERS SINCE 1925

NEW IMPROVED 1950 MODELS

## HIGH FIDELITY SPEAKERS

The World Famous 12" triple cone I2.B.

The standard 12" P.A. model I2.C.

The Cinema Model 18" "Duplex" C.T.

Write for illustrated list and technical details of SPEAKERS, TUNERS and AMPLIFIERS.

## BAKERS 'SELHURST' RADIO

Dingwall Road, Croydon  
Telephone: CROYdon 2271/2

# THIS and THAT

**B**ECAUSE it would have left the 1949 volume with its shirt hanging out, the Editor ruled against beginning my two-part treatise on filters in this December issue. And it may not be such a bad thing anyway; two big helpings of smoothing circuits followed without a break by a similar dose of filters might upset even hardened technical digestions. Something a bit lighter sandwiched between may be all to the good. Even Shakespeare admitted the need for comic relief.

Some time ago a correspondent made an extremely penetrating observation. He argued against the present G.P.O. practice of demanding a separate licence for car radio sets, not because it was an act of social injustice against the new poor, but (as he explained) on strictly technical grounds. By compelling the thrifty motorist to install his aerial under the running board or in some such inconspicuous part of the vehicle, it made mobile reception even worse than it need be. One more example, it would seem, of car design being influenced by the tax-gatherer rather than by the engineer.

## Sudden De-licencing

Talking about licences, have you realized that if you (or anyone else) charged for people to come into your house, say for the purpose of getting a good view of a procession from the upstairs windows, your wireless licence, even if you had bought it only yesterday, would forthwith expire? I confess I didn't until I took the unusual step of reading it. This is what it says: "M. Cathode Ray" (or words to that effect) "is hereby authorized . . . for a period ending on the date mentioned above or on any earlier date on which a charge for admission to the premises shall be made by the Licensee or any other person, to install and work apparatus for wireless telegraphy in the premises occupied by the Licensee

## "End-of-Term" Relaxation

By "CATHODE RAY"

. . . . There is nothing to limit this sudden de-licencing to situations where the mercenary activities of the Licensee have anything to do with "wireless telegraphy."

By the way, I suppose that to the legal mind it appears quite fitting to refer to the process that permits us to view our undeniably attractive television announcers as "wireless telegraphy." It reminds me of the enactment authorizing the closing of roads in the Isle of Man for the T.T. races, in which these thrilling events were defined as "the testing of light locomotives."

Such uses of words are quaint old legal customs at which we can smile tolerantly. But I don't feel at all the same about those commercial interests who, either from sheer ignorance or deliberately, try to make an impression on the gullible public by misusing scientific terms as names for their wares. With their high-pressure publicity they sometimes succeed in getting their counterfeit meanings into general circulation first, so that when the genuine article comes on the scene it is mistaken for an imposter. You know the sort of thing—somebody is not satisfied with selling suppressor resistors at the usual one and sixpence, so he calls them cyclotrons or isotherms and charges half-a-crown.

I see it is eleven years since I commented on the mentality of those who started the absurd habit—now thoroughly established—of classifying receivers into two kinds, television and radio. When a thing reaches a certain pitch of absurdity it becomes impossible to caricature it. So I pass on.

People say "What's the use of protesting about sloppy technical

language?' You can never change it once it's got a hold." But once upon a time the idea of substituting the new word "resistor" for the universally-used "resistance" seemed quite hopeless; yet it has been done. And "capacitor" is well on the way. There is still more justification for finding and putting into use a word to distinguish broadcast receivers and programmes without vision from those with.

Now that the radio industry has grown up there is much less about it to make fun of than when it was an adolescent. That is why I have of late years been driven to writing so much about solemn things like smoothing circuits and filters. However, there is one thing that makes me rock with mirth every time. It is the thought that several times every day, year in, year out, millions of the ever-patient British public grind away uncomplainingly at their tuning controls to change from Light to Home and Home to Light, when all they need do is to push a switch, if they had the spirit to demand it. It isn't even as if sets were so scarce that they were under the counter and the customer was always wrong. There is a buyer's market. But the buyer doesn't seem to have noticed it.

## Words and Music

Having from time to time chided the B.B.C. in these columns for maintaining approximately the same depth of modulation for announcements as for brass bands, mighty Wurlitzers, and massive orchestras, I was rather taken aback by published complaints from listeners to the effect that if the volume control was set right for speech, music was too loud. These complaints arose particularly during the summer, as an excuse for turning up the volume control to the discomfiture of the neighbours.

The only explanation that occurs to me is that while music continues to be generally regarded

**THIS and THAT—**

as something that must be allowed to go on, but not so loudly as to interfere with conversation, there are now many owners of receivers who have ceased to consider spoken broadcasts in that light and insist on actually listening to the words, presumably in the hope (analogous to that of football pool addicts) that some time, some day, someone in a variety programme may say something really funny. A contributory cause may well be that as a result of the popular demand for "mellow" tone, (in pre-war days, when buyers could and did demand), speech can't be followed unless turned well up. If it were not that it would send up the purchase tax too much, and

might interfere with export, manufacturers could incorporate a device for automatically cutting bass during speech and cutting top and most of the volume during music. The trouble would be that the B.B.C. is so seldom content to let us have them separately, so that the device would be in the same sort of dilemma as the chameleon who found himself on a tartan.

While on the subject of colour, my feeling is that though Hallows may wish to increase the number of frames per second in order to prevent things from looking as if they were leaning over when they flash across the television screen, my impression is that viewers couldn't care less. You may remember that focal-plane camera shutters were a success *because*

they did that, making racing cars look as if they really were racing. Television I think, is at the stage that . . . *teleaudition*, shall we call it? went through when theorists were insisting on the necessity for frequency characteristics level within a few per cent over the whole audible range, and whose efforts were received with such indifference by the listening public. Apart from a clear picture and a rather larger screen than they can get for the money, the only thing the viewing public know that they want is colour.

Well, if Hallows was (as he said) trailing his coat, I may almost be said to have been trailing several bags marked "Fully-fashioned Nylons." But next month, noses to the grindstone once more! Filters . . .

**NEW BOOKS**

**International Radio Tube Encyclopaedia.** Edited by Bernard B. Babani. Pp. 410+lxixiv. Barnards, Ltd., The Grampians, Western Gate, London, W.6. Price 42s.

THIS voluminous compilation of data on some 15,000 valves of many different countries starts off with four pages in English which explain the tabular matter contained in the body of the book. The following 80 pages repeat this in various languages—French, Italian, Spanish, Portuguese, German, Dutch, Swedish, Norwegian, Danish, Russian, Polish, Czech, Turkish and Hebrew.

The main tables cover receiving and transmitting valves, thyratrons, regulator and control valves, tuning indicators, c.r. tubes and photo-electric tubes.

Valves are arranged in numerical and alphabetical order of their type numbers, and in the case of receiving valves the information given comprises: type of cathode, class of valve, filament current and volts, anode and screen volts and currents, grid bias, cathode-bias resistor, a.c. resistance,  $g_m$ ,  $\mu$ , load resistance, power output, base connections and the makers' name.

British, American and Continental types are included as well as many British and American Service types.

The base connections are given with the valve characteristics, and drawings of the bases themselves are included at the end. Standard base designations are not always used. The B8B is not mentioned

but the B8G and octal, which are interchangeable with it, are given. The American UX bases are not so called but are given various unfamiliar names, such as US4E, US4N, USM4, USM7B, etc.

The book should be extremely useful to anyone who requires to find out the characteristics of a given valve, but does not meet the inverse requirement of indicating what valves have given characteristics.

W. T. C.

**Permanent Magnets.** By F. G. Spreadbury. A.M.Inst.B.E. pp. 280+viii. Sir Isaac Pitman & Sons, Ltd., Parker Street, London, W.C.2. Price 35s.

AS the author points out in his preface, permanent magnetism has been known for about 2,500 years, but only since 1910 has there been marked progress in the subject. Since then it has been so rapid that few have been able to keep up with it; yet permanent magnets are used on such a large scale for so many purposes that the need for a comprehensive and up-to-date book on the subject has become acute. The present work fills this need admirably.

Its substantial size is not due to a diffuse style—quite the contrary, for it is notably concise—but to its comprehensiveness. It is, moreover exceptionally self-contained, as the author has not followed the common practice of putting the onus on the reader of looking up innumerable references.

The chapter headings are: 1, Magnetism and the Permanent

Magnet; 2, Permanent-Magnet Materials; 3, Theory of Magnetism; 4, Magnetic Leakage; 5, Applications of Permanent Magnets; 6, Magnet Design; 7, Magnetic Measurements and Measuring Instruments; 8, Magnetization and Magnetizers; and 9, Demagnetization and Demagnetizers. There is, unfortunately, no reference to the rationalized m.k.s. system of units, c.g.s. units being used throughout. The author does not shirk mathematical proofs of his statements, including some that even the most sceptical might be prepared to take as read. In the last two chapters, particularly, all the factors involved are painstakingly investigated, and are illustrated by some examples of the author's design. Readers who may find some of the mathematics rather beyond them, or who are prepared to take the author's word for the findings, should have no difficulty in picking out what they want. Those who have not kept in close touch with the theoretical physics of magnetism will be fascinated by the account of some of the attempts, such as the Stern-Gerlach experiments, to solve the mysteries of permanent magnetism.

The practical problems of design, and especially those resulting from magnetic leakage, are clearly such as to call for specialized study and experience; but all radio engineers should be acquainted with them if only to know what it is reasonable to expect of the magnet designer. This book is an excellent reference for the purpose.

Though the price is perhaps rather high, it can be said that the standard of the book-production is on the same level. M. G. S.

**LETTERS TO THE EDITOR**

**Interference with Foreign Broadcasts ♦ Cathode-ray Tube Limitations ♦ Tone Control Circuits ♦ Record Reproduction ♦ Spoiling New Records**

**Beacon Interference**

MAY I add my astonished censure to "Mikrobe's" letter in your November issue on the subject of m.f. beacons in the broadcast band?

I say "astonished" as up until I saw "Mikrobe's" letter I hadn't the faintest notion what caused the interference and had vaguely attributed it to something quite illegitimate and "on the Continent." The idea that it emanated from authorities in this country didn't enter my head.

If you will permit me to say so, I cannot recall having seen this matter raised before in either the correspondence columns or the editorial of *Wireless World*, a fact (if true) which causes me considerable surprise.

With regard to the Wireless Telegraphy Act: does this provide for interference with foreign stations? When I asked the Post Office to investigate some particularly bad electrical interference (before the Act), the engineers ascertained the fact that the Home and Light carriers over-rode the interference, and left saying that proper reception of foreign stations was no concern of theirs.

C. E. KNIGHT-CLARKE.

London, S.W.19.

**C.R. Limitations**

IN reports on the performance of amplifiers the phrase "no distortion was visible on the screen of an oscilloscope" often occurs.

Many readers may have wondered what this statement really means, for there appears to be little published information on the minimum percentage of harmonic distortion which is visible by means of a c.r.o.

The results of rough tests to obtain some guidance on this point are given below:—

Harmonic	Minimum % visible
2nd .....	9%
3rd .....	4½%
4th .....	3½%
5th .....	1½%

These figures are probably rather low, as instantaneous comparison between the pure and distorted

waveforms was available. They refer only to the addition of one harmonic to the fundamental.


It would appear from these results that sometimes more faith than is justifiable is placed in the c.r.o. as an indicator of distortion.

E. W. ROYSTON.

Flixton, Manchester.

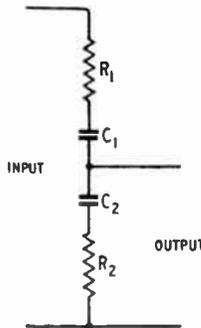**Tone Control Circuits**


IN the article on a High-Quality Amplifier in your October issue, D. T. N. Williamson describes a tone control circuit to provide continually variable treble and bass rise and fall. Whilst



the circuit shown will operate quite satisfactorily at the extremes of control settings, the slope of the rise and fall is by no means ideal at other settings of the controls.

Referring to the basic potentiometer circuit for bass control, Mr. Williamson short-circuits  $C_1$  and applies a variable resistance in parallel with  $C_2$  to provide variable bass boost. This arrangement controls the extent of the boost and does not affect the frequency at which it commences, nor its initial slope. At a low setting it will merely cause a step in the response curve.

Practical tests which we carried out in the development of similar circuits showed that a control which varies the slope of boost is very much to be preferred. Assuming the source impedance can be neglected and the ratio of the reactance of  $C_1$  to  $R_1$  is the same as  $C_2$  to  $R_2$ , then a variable resistance in parallel with  $C_1$  will shift the curve bodily along the frequency axis. If this is coupled with a variable resistance in parallel with  $C_2$ , then a close approach to a variable slope control can be obtained over the essential range.

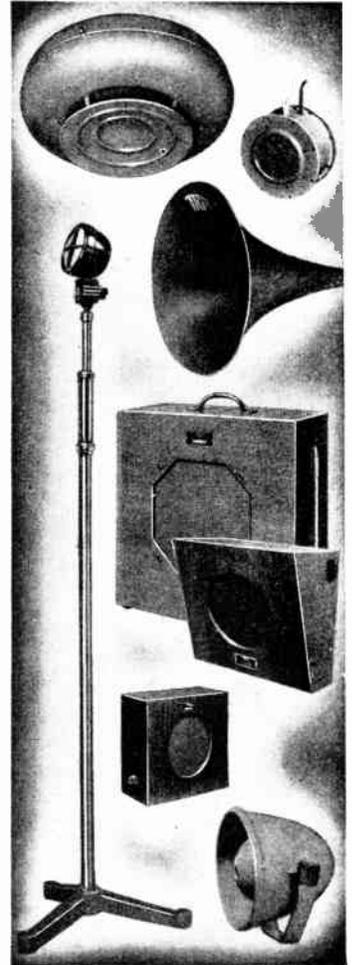

TRIX Loudspeakers and accessories are available in a variety of types to suit the needs of every Sound Installation. They are representative of a range of equipment noted for its robust construction and high standard of performance and reliability.

Full details of these accessories and the well-known series of TRIX Amplifiers, Gramo-Radio units, High Fidelity Reproducers and High Power Rack equipment are available on request.

THE TRIX ELECTRICAL CO. LTD.  
1-5 Maple Place, Tottenham Court Road,  
London, W.1. Phone: MUSeum 5817  
Grams & Cables: "Trixadio, Wesdo, London."

AMPLIFIERS · MICROPHONES · LOUDSPEAKERS

### Letters to the Editor—

If  $R_1$  is ten times  $R_2$ , then a good compromise can be obtained with a single logarithmic control for rise and fall with level response in the centre of the movement. Close-tolerance components are essential if kinks in the response are to be avoided.

Similar modifications to the treble control can be introduced, although for high frequencies a variable extent of rise and fall is usually more desirable.

Tone control should be applied with the greatest discretion, but a small amount of "compensation" correctly shaped can on occasions prove beneficial. The scale, perspective, or apparent distance of the programme is controlled at the studio and is (or should be) correct for average listening-room level. Variations from this optimum volume level will require only small correction for good balance, always assuming, of course, that the remainder of the equipment does not suffer from deficiencies.

P. J. WALKER.

The Acoustical Manufacturing Co.,  
Huntingdon.

**The Author replies:—**Mr. Walker's letter raises the interesting but vexed question of the most suitable type of bass accentuation. I feel that the answer to this question must depend upon individual circumstances, and that there is no unique solution.

Circumstances can be visualized where the "variable slope" method preferred by Mr. Walker would be distinctly advantageous, but, equally, there are occasions on which raising the general level below, say, 200 c/s can produce more pleasing results. Where the control is to be used solely for the correction of transmission defects, a third type of characteristic,

namely, a constant slope of, say, 6 db/octave, the cross-over frequency of which is variable, has much to recommend it. This type of characteristic is used for the treble control. Unfortunately, at low frequencies there is danger of overloading when a characteristic of this type is used for purposes other than the correction of deficiencies of the input.

Where circumstances warrant it, the circuit of Fig. 5 may readily be adapted, as shown in the accompanying figure, to incorporate the type of control recommended by Mr. Walker.

D. T. N. WILLIAMSON.  
Edinburgh.

### Record Reproduction

**I**N his article on "Pickup Design" Mr. Marshall rightly suggests that needle scratch is caused more by the rough composition of the material than by an abrasive put in the material by the manufacturer, as has been most popularly supposed in the past.

I should like, however, to draw attention to three points which appear to be somewhat misleading. In his reference to Fig. 4 (a) Mr. Marshall states that the groove is cut with a chisel-shaped edge and that as far as a spherical reproducing point is concerned will vary in width throughout the cycle. He then goes on to say "this is descriptively known as the 'pinch effect'; so that where the stylus is too small, over at least part of the cycle the stylus will lose contact with the groove walls." This latter remark may be true, but it cannot accurately be described as "pinch effect." The groove width varies when modulated, but although it can be smaller it will not usually be larger than the recording stylus size, even with maximum amplitude. "Pinch effect" is the inability of a reproducing stylus of normal dimensions correctly to trace this smaller groove width, causing a riding up of the stylus on the groove walls. A reproducing stylus of optimum dimensions will not be too small, but it may be subject to this "pinch effect."

My second point concerns Fig. 3, where Mr. Marshall says "It will be seen that point B . . . will only just fit this particular groove . . ." In fact, it will be seen that point B does not fit the groove, but rides on the bottom, a condition almost as bad as that shown in Fig. 3 (c). Most modern records of British manufacture have a groove width of 0.0067 in, a radius of 0.0015 to 0.0018 in, an angle of between 85 and 90 degrees, and a depth of 0.0027 in. It will usually be found that a re-

producing point with a radius of 0.0025 to 0.003 in will satisfactorily trace both old and new records.

Third, radius compensation is rarely, if ever, resorted to in commercial gramophone records in this country, although most 33½ r.p.m. transcription records use it to a greater or lesser degree. Amplitudes in the higher end of the frequency scale are so small that a "boost" in recording of, say, 6 db at 10,000 c/s can be tolerated, but the "boost" of between 15 and 30 db, which is so often found in American recordings, can be the cause of considerable distortion.

RICHARD W. LOWDEN.  
Farnborough, Wts.

### Spoiling New Records

**I**N view of the high quality (and cost!) of the modern gramophone record it is very galling to find that a new disc has been ruined by demonstration on obsolete reproducers such as are still to be found in many shops. I know of one, 1934 vintage, the needle of which is changed once a day, with luck!

Might I suggest to the makers that they put a proper seal on the envelopes so that one may be sure of a record in mint condition?

Returnable demonstration records would fill the gap until good reproducers are installed.

J. E. ELLIS.  
Harrow, Middx.

### "High-voltage Measurements"

**I** HAVE read with interest the article in the October *Wireless World* describing a peak voltmeter.


It may be of interest to know that the Osram U37 valve could be used with advantage in the circuit. It gives:

1. Instantaneous operation with a possibility of push-button control, due to its directly heated filament.
2. The possibility of using only one dry cell for filament heating.

F. E. HENDERSON.  
The General Electric Co.,  
London, W.C.2.
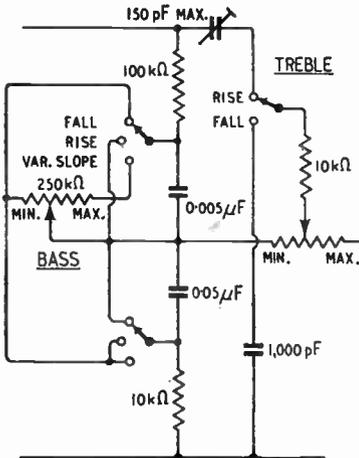
### "Q and L" Measurements

**I**N saying that my statement "Frequency is the most accurately-measurable quantity there is" was misleading in relation to the measurement of Q, W. T. Cocking (your November issue) has taken it out of its context. It occurred in a section devoted to the meaning and measurement of Q at such high frequencies that L and C are not separately measurable. So it was not quite the right text on which to hang his very instructive sermon on



OUR COVER

The acoustic characteristics of the anti-echo loudspeaker testing chamber at Plessey's, which is illustrated on our front cover, are comparable with those of free air. This erstwhile air-raid shelter has been lined with wedge-shaped blocks of sound insulating material to render it almost completely non-reflective. The free space area of the chamber is 12ft x 9ft x 6ft 9in.

the advantages of the capacitance-detuning method!

As regards even the general truth of the statement there can hardly be any question, for the accuracy with which frequency is known is several orders of magnitude better than that of any other quantity used in radio measurements. The G.P.O. reckon they have it within  $\pm 1$  in  $10^6$ , but what is more remarkable in its way is that any owner of a broadcast receiver has at his disposal one audio-frequency and several radio-frequency standards accurate to  $\pm 1$  in  $10^6$ . With quite cheap apparatus and a good deal of patience, these can be interpolated over the whole useful range of frequency in a positive manner—cheap, that is to say, when compared with the cost of a standard variable capacitance one thousand times less accurate.

For frequencies at which capacitance is measurable at all, I entirely agree with Mr. Cocking about the greater convenience of the apparatus for the capacitance-detuning method. But unless one cheats by buying two accurately calibrated variables, one of them reliable within 0.1 pF, how does one get these calibrations? Surely by a method based on known frequencies! The thing I dislike about capacitance measurements is the uncertainty of the absolute value, especially when there are several items in parallel, including a self-capacitance; and at the frequency of 40 Mc/s referred to by Mr. Cocking the errors due to distributed reactances and the necessary auxiliary measurements of L and  $C_0$  are usually regrettably large.

Mr. Cocking goes rather out of his way to make the frequency method look worse than it is. Anybody with the sense to use a separate low-reading capacitor for measuring  $\Delta C$  would hardly make the elementary blunder of trying to read  $\Delta f$  on the same frequency scale as  $f_1$ ! His point, of course, is that one might have to, for lack of the elaborate apparatus he describes. There are, however, reasonable methods of obtaining a known  $\Delta f$  without any

crystals or anything at all more elaborate than a fixed audio frequency that has been set to a multiple of the B.B.C.'s standard 440c/s broadcast daily. The horrid example of what would happen if one were to measure  $\Delta f$  as the difference between two nearly equal frequencies with errors of  $\pm 1\%$  and  $-1\%$  respectively is as unrealistic as measuring the height of a man by taking the difference between two independent measurements of height above sea level.

Incidentally, in view of Mr. Cocking's basis of distinction between Q-meters (direct-reading) and Q-measuring methods (which arrive at Q by calculation), it may be necessary for me to repeat that most so-called Q-meters do not give true Q without subsequent calculation. The practical significance of true Q having been called into question,\* a main point of my article was to reinstate it. Nobody appears to have questioned the reinstatement.

"CATHODE RAY."

\* *Wireless World*, June, 1949, p. 216.

MANUFACTURERS' LITERATURE

FOLDER (Y13, printed in three languages), describing "Solon" electric soldering irons, from W. T. Henley's Telegraph Works Co., 51 and 53, Hatton Garden, London, E.C.1.

Leaflet (CL534), giving details of "Tom Thumb" service replacement electrolytic capacitors, from A. H. Hunt, Bendon Valley, Garratt Lane, London, S.W.18.

Illustrated leaflets describing "Volmar" electric gramophones and record players, made by Industrial Sound Equipment and sold by the General and Overseas Trading Corporation, 6, Duke Street, London, S.W.1.

Catalogue of data sheets relating to the Type 103 cathode-ray oscilloscope made by Nagard, Ltd., 245, Brixton Road, London, S.W.9.


Catalogue (1D) of "Eclipse" permanent magnets from James Neill & Co., Napier Street, Sheffield, 11.

Details of Record "Major" insulation tester (500 V, range 0.50 M $\Omega$ ) from the Record Electrical Co., Broadheath, Altrincham, Cheshire.

Illustrated leaflet (No. 40), dealing with the new range of precision-ground ceramic radio coil formers, from Steatite & Porcelain Products, Stourport-on-Severn, Worcs.

Brochure describing television aerial service and new aerial types, from Valibus Aerials, 69, Hornsey Road, N.7.

A new conception in Television Aerials

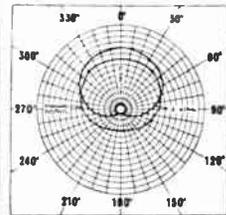

Horizontal Polar diagram at 45 Mc/s  
The Forward Gain of the "Antex" Aerial is 2db better than a standard "H" array.

THE "ANTEX" (REGD.)  
Greater Signal Strength  
Greater Noise Cut  
Less weight - Less Cost

Antiference research and engineering knowledge once more lead the way with this revolutionary new "ANTEX" (Regd.) Aerial. With front-to-back ratio of 22.0 db and a forward gain of 2 db when compared with the standard 'H' aerial, it brings a new level of quality to television reception.

The electrical and mechanical design of this aerial is protected by Prov. Pat. Nos. 35957/46 and 12178/49 and Regd. Design No. 859630.

FRONT BACK RATIO

Standard Dipole and Reflector ('H' array)— 7.5 db, "ANTEX" AERIAL ('X' array) — 22.0 db

MODEL XL for London ; XL/B for Birmingham, including 7-ft mast and chimney lashing equipment as illustrated. - - - £3-15-0

MODEL XW for London ; XW B for Birmingham, including 7-ft mast and wall mounting bracket - - - £3-0-0

ANTIFERENCE

LIMITED

67 BRYANSTON ST., LONDON, W.1.

# RANDOM RADIATIONS

By "DIALLIST"

## Capacitors as Dry Cells

YOU REMEMBER my recording a while ago instances of misbehaviour on the part of old paper-dielectric capacitors, which had so far forgotten their mission in life as to turn into dry cells, each with a definite polarity and terminal potential differences of from 0.1 to 0.4 volts? Several readers who have examined their stocks of old capacitors confirm that this kind of thing is by no means uncommon. In some instances capacitors tested with valve voltmeters with an input resistance of 20-50 MΩ have shown p.d.s as high as 3 volts. That these arise from genuine e.m.f.s and are not just static charges is proved by the fact they have a definite polarity and that they persist even after repeated short-circuitings of the terminals. I suggested, you may recall, that a capacitor mistaking its vocation in this way might give rise to some queer effects in a receiving set. A kind Irish reader sends me a record of one that did. In a t.r.f. battery set the manual volume control worked by varying the bias on the grid of the r.f. valve. Reception had become very weak and the v.c. was out of action; examination showed that its sliding contact had broken off. Tests disclosed a steady bias of 2V negative on the control grid—a surprising state of affairs, since the grid had apparently no d.c. connection to anything. Between the bottom end of the grid coil and the earthed chassis was a 0.5 μF paper capacitor. Due to the breakdown of the volume control it, too, was able to apply to the grid the whole of the 2V e.m.f. which it was found to be generating; and that was sufficient to reduce the set, with its pretty well worn out valves, almost to silence.

## Ingenious!

Another reader offers an explanation of the e.m.f.s from old capacitors recorded by the valve voltmeter which is at any rate highly ingenious. In capacitors of

old types, he writes, there is usually quite appreciable inductance. This, with the capacitance, would form a resonant circuit. The leads to the meter act as an aerial; oscillations at, or in the neighbourhood of the resonant frequency are picked up, a voltage appears across the circuit and is duly registered by the valve voltmeter. This e.m.f. varies from capacitor to capacitor because differences in their inductance and capacitance may sometimes produce a circuit resonating at a frequency quite close to that picked up by the meter leads and at other times one which is more or less "off tune" . . . . Ingenious, as I've said; but I'm afraid it won't work. Any capacitor, you see, which behaves in this way is invariably found to have a definite and fixed polarity; like a dry cell, it has its positive and negative terminals. If the resonant circuit explanation were correct, the meter reading would not be affected if the capacitor connections were reversed.

## It Doesn't Make Things Easy

WHAT A PITY it is that there can't be some kind of international uniformity in the use of the symbols—letters, figures, punctuation marks, lines, and so on—by means of which authors put their ideas on to paper and readers endeavour to discover what they are trying to convey. One is always coming across instances of the difficulties created—quite unnecessarily—by the lack of a single world-wide system in these things. When, for example, we express in figures two thousand six hundred and eighty-three point four seven we write 2,683.47; but in many other countries it appears as 2.683,47, the point and the comma having exchanged roles. A trillion with us is  $10^{12}$ ; elsewhere it may be  $10^{12}$ —it certainly is in France and I think in the United States. Our practice seems the more logical, for our trillion is the third power of a million; a quadrillion, the fourth

power, and so on. One of the most annoying bits of perversity I've come across is the habit at which at any rate some French publications have of turning the symbols for cell or battery upside down. I used to think that the use of a longish thin line for the positive end and of a short fat one for the negative end really was universal. The other day, though, I could not see from a circuit diagram in a French publication how a gadget containing two batteries could possibly work—until I realized that the short fat lines were there the positive ends of the batteries and the longer thin lines the negative.

## Radio Roundabout

FROM A MEDICAL READER comes a query about alleged effects of wireless waves on pigeons. It was solemnly stated, I gather, by someone at a meeting of medicos that carrier pigeons released near a certain transmitting aerial circle round it indefinitely when a particular wavelength is in use. He asks whether the report is fact or fiction. I have no hesitation in plumping for the latter. Tales of this kind are continually cropping up and, to the best of my knowledge, investigations have always shown them to be pure bunk. Carrier pigeons invariably circle when released, gaining height as they do so. It is some little time before they get their bearings and make a bee- (or pigeon-) line for home. Release a basketful near any high aerial mast and the odds are that they'll probably circle round it for a while. That, possibly, was the "proof" given to the lay journalist who wrote the original story. Experiments have been made in America with a view to discovering whether e.m. radiations of certain frequencies could have any effect on birds. The scale of the experiments was too small to be conclusive, but no definite or sustained effects were recorded. Actually, when you come to think of it, experiments of the same kind are conducting themselves on a vast scale on every day of the year in this country. Pigeon flying is a popular hobby, especially in the North. Enormous streams of migrant birds of many kinds pass into, through, and out of Britain. At any moment there must be radio, radar and television aeri-als radiating on wavelengths of every

order from centimetres to kilometres. Nobody to my knowledge has ever observed birds of any kind circling willy-nilly round any of these aerials.


**The Practical Aspect**

My correspondent wonders whether, if the story were true, the pigeons would fly always either right-about or left-about. I wonder, too! Presumably, those which were the subject of the alleged report described their circles in the horizontal plane. The radiations would most likely be vertically polarized. A really convincing demonstration could have been arranged by providing a change-over switch and an aerial for horizontal polarization as well. Flicking over the switch should then have caused the birds to describe circles in the vertical plane—which would have been well worth seeing!


**Some Television Station!**

BY THE TIME that these notes are printed the Sutton Coldfield television station is sure to have started test transmission, if it is to be ready (as doubtless it will be) for the opening ceremony on December 17th. I expect to hear of good reception at quite considerable distances at places on high ground. As the output power is just over twice that of the Alexandra Palace station, one would expect the service area to have a radius nearly one-and-a-half times as great in any event. I believe, though, that this radius may well turn out to be the best part of 60 miles in most directions. The station is well sited and some of the "fringe-area" receiving aerials now available are remarkably good performers. And I'm betting that soon after the station comes into action there'll be reports of consistently good reception at points 100 miles or even more away. Sutton Coldfield is a station for whose existence the country in general and the B.B.C. in particular may well feel that pats on the back are deserved. It is by far the most powerful television station in the world and I doubt whether there are many others anywhere which can as justly claim a vision modulation range of 2.75 Mc/s without appreciable amplitude—or phase—distortion. It's a fine Christmas present to Birmingham and the Midlands.


**More than a SWITCH — a SERVICE!**

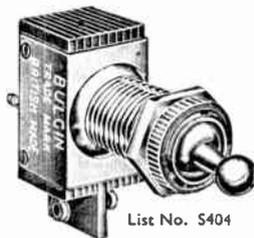

List No. S404

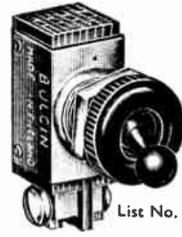

List No. S 478

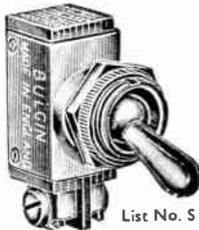


List No. S 259 P.D.



List No. S 365



LIST NO S 277

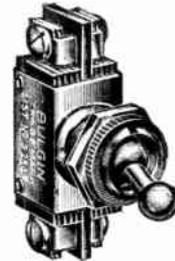

List No. S 264

**The experience of 25 years behind every switch!**

Famous 2-pole M.-B long bush Toggle Switch. This model is suitable for 6-250V. circuits; max. 1A, for all panels up to 9/16" thick. List No. S.404.

Pear dolly for easy operation; for circuits as above. All BULGIN switches are obtainable with a wide variety of dollies, fixing nuts, bushing rings, and finishes, on request. List No. S.258 P.D.

Double-pole general purpose M.-B. for similar circuits at 3A. max. Silver plated roller-action contacts. List No. S.277.

New version of long-popular single-pole M.-B model, for 6-250V., 3A. circuits. Note the insulated front ring, available on all switches at request. List No. S.478

Press ON; biased OFF. A popular model for 6-250V. circuits; max. 3A. List No. S 365. (Reversed action; List No. S.366)

Change-Over switch, single-pole. New version with terminals, for 6-250V. circuits; max. 2A. Guaranteed — as all BULGIN switches — for at least 25,000 operations! List No. S.264.



ILLUSTRATED COMPONENT CATALOGUE  
Price 1/-  
Post Free

"The Choice of Critics"



**A. F. BULGIN & CO., LTD.**  
**BYE PASS ROAD, BARKING, ESSEX**  
Telephone: RIPpleway 3474-8

# RECENT INVENTIONS

## A Selection of the More Interesting Radio Developments

### C - R Tubes

FOR producing a high-intensity electron beam one method is to heat a thermionic cathode by electronic bombardment; thereby high temperature operation may be secured while maintaining a long operating life, as well as other advantages. However, it is difficult to avoid disturbing effects due to secondary electrons resulting from the bombardment. These difficulties are avoided by the fact that bombardment is only effected periodically during the operating cycle by making the cathode periodically positive relative to the source of bombarding electrons; for television or oscilloscope use the bombardment is effected during the flyback intervals of a scanning process.

In a practical circuit a filament heater surrounds the cathode proper and the latter is coupled through a diode to a transformer energized from a time-base generator and arranged to make the cathode positive to the heater during the flyback, and thus effect the bombardment heating of the cathode during the same period.

*Cinema-Television, Ltd., and W. H. Buchanan. Application date, July 10th, 1947. No. 624,832.*

### F.M. Receivers

THE accurate tuning of f.m. receivers is difficult because there is usually an increased response on each side of

the correct position. To avoid this difficulty the amplitude limiter provides a muting voltage which is operative when the receiver is detuned from the signal.


In the circuit diagram *a* represents the i.f. amplifier, the output of which is fed to an amplitude limiter *V*<sub>1</sub>, and thence to the detector, e.g., the twin diodes *V*<sub>2</sub>. Negative voltage is applied to the grid and cathode of *V*<sub>1</sub>, the

screen of which is earthed. *V*<sub>3</sub> is an a.f. amplifier, which is fed from the diodes *V*<sub>2</sub>. The anode current of *V*<sub>1</sub> is a maximum for zero signal and decreases as the f.m. signal amplitude increases, due to grid rectification. This current produces a voltage across *R*<sub>1</sub> which is fed to the grid of *V*<sub>3</sub> through *R*<sub>2</sub> to mute the a.f. circuits. At the correct tuning point, however, the anode current of *V*<sub>1</sub> is so small that muting is ineffective and the receiver gives normal a.f. output.

*Marconi's Wireless Telegraph Co., Ltd. (assignees of A. Wright). Convention date (U.S.A.), November 6th, 1945. No. 625,449.*
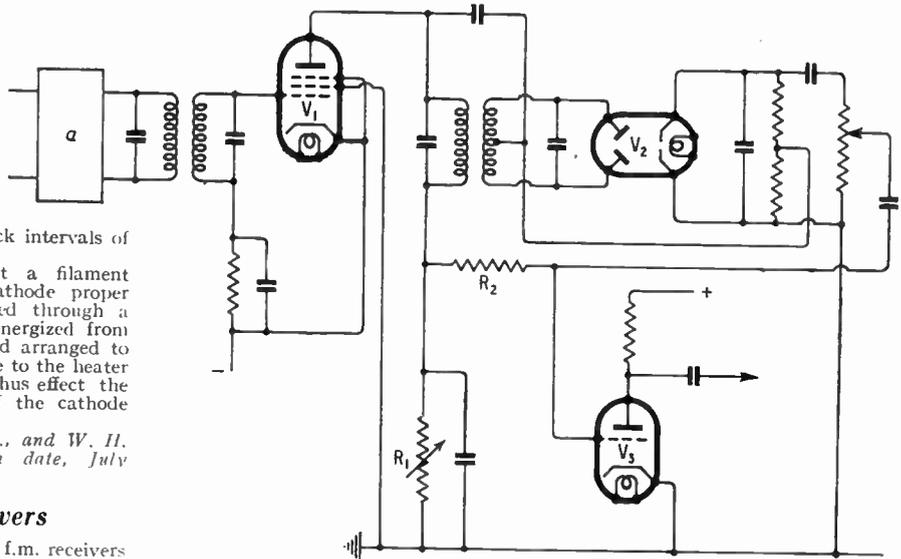
### Chassis Construction

IN unit chassis construction, e.g., for i.f. amplifiers and for other sec-



Muting circuit for f.m. tuning.



### Books Published for "Wireless World"

	Net Price	By post
RADIO DATA CHARTS, by R. T. Beatty, M.A., B.E., D.Sc., Fifth Edition—revised by J. McG. Sowerby, B.A., A.M.I.E.E.	7/6	7/11
GUIDE TO BROADCASTING STATIONS. Fifth Edition	1/6	1/7
RADIO VALVE DATA. Characteristics of 1,600 Receiving Valves	3/6	3/9
FOUNDATIONS OF WIRELESS. Fourth revised Edition, by M. G. Scroggie, B.Sc., M.I.E.E.	7/6	7/10
RADIO LABORATORY HANDBOOK. Fourth Edition, by M. G. Scroggie, B.Sc., M.I.E.E.	12/6	12/11
WIRELESS SERVICING MANUAL, by W. T. Cocking, M.I.E.E., Seventh Edition	10/6	10/10
TELEVISION RECEIVER CONSTRUCTION. A Reprint of 10 articles from "Wireless World"	2/6	2/9
WIRELESS DIRECTION FINDING. By R. Keen, M.B.E., B.Eng.(Hons.), Fourth Edition	45/-	45/9

A complete list of books is available on application

Obtainable from all leading booksellers or from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1.

tions of apparatus using thermionic valves, difficulties are sometimes met with when using valves having a base grid terminal. The construction described divides the valveholder between adjacent units. An i.f. unit might comprise a screening box having that part of the i.f. valveholder carrying all except the grid and anode terminals, the i.f. transformer and the part of the holder of the following valve containing the grid and cathode terminals. The holder parts match with other parts to form complete holders, when the units are assembled.

*Philips Lamps, Ltd. (Convention date (Netherlands), September 14th, 1943. No. 626,142.*

The British Abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 2/- each.

The sound reinforcement system

*at Radiolympia*

was engineered and installed by

***Standard***

**SPECIALISTS IN SOUND REPRODUCTION**

for over a quarter of a century

***Standard Telephones and Cables Limited***

(Registered Office: Connaught House, Aldwych, London, W.C.2)

**PUBLIC ADDRESS DEPARTMENT**

**Connaught House, Aldwych, London, W.C.2**

## When Quality Counts

... accuracy is demanded. When great pains are taken to ensure that calibration is 'spot on' it counts for very little if the frequency varies as the attenuator is adjusted. In the HOMELAB Signal Generator the attenuator is fed from a buffer stage: this isolates the oscillator from the output circuit and ensures that its inherently high frequency stability remains unimpaired. We think you will agree that this refinement in an instrument which covers from 100 kcs. to 130 mcs.,\* at such a modest price represents remarkable value for money. It has many other features which will interest you and we will gladly send full details on receipt of a S.A.F. Please include a P.O. for 2/6 if you require the circuit diagram.

\*On fundamentals, of course.



PRICE: £6 : 11 : 0 plus 5/- for packing and postage. Owing to the very large demand delivery is subject to some delay but all orders are dealt with in strict rotation. When our new showrooms are open we will be glad to receive callers and to demonstrate. In the meantime, orders by post only please.

**HELY-MANN ELECTRONICS LABORATORIES**  
116 GROVE ROAD LONDON, E.17.

*You simply must make a*

## WIRE OR TAPE RECORDER!

With very simple mechanism and your own amplifier you can record and playback speeches, radio programmes and family gatherings, or copy your friends' best records. Play them back time and time again, and then finally obliterate them and make a new recording using the same wire or tape.

We can supply all the necessary parts (including amplifier parts) from stock. The recorder need not cost more than about £16 with amplifier, or £20 for a super job using precision parts. Plenty of wire and tape in stock.

Send 5/- now for the complete Constructional Data, including price list of the necessary components.

**PARK RADIO of MANOR PARK**

(A division of Judge Industries)

676/8 ROMFORD ROAD, E.12

# RADIO SPARES

**MAINS TRANSFORMER**  
Potted—fully shrouded and impregnated, fitted primary screen. 280-0-280 at 150 mA., 6.3 v. at 10 amp. and 5 v. at 3 amp. Primary suitable for 50-cycle mains, 110-250 v., 27.6.

**MAINS TRANSFORMER**  
Half-shrouded drop-through type, 350-0-350 at 80 mA., 6.3 v. at 4 amp., 5 v. at 3 amp., primary tapped for 200-240, fitted primary screen and impregnated, 16 6.

**MAINS TRANSFORMER**  
260-0-260 at 60.70 mA., 6.3 v. at 3 amp., 5 v. at 2 amp., otherwise as above, 13.9.

**TUNING CONDENSER**  
Standard size 2-gang, .0005 long (2in. spindle), 3 6.

**AMPHENOL INTERNATIONAL**  
Octal valve holder, 6d. each.

**MIDGET TUNING CONDENSER**  
2-gang, .00035, fitted with trimmers, and complete with perspex dust cover, type used for tuning personal receivers, 6 6, plus 8d. postage.

**4-GANG TUNING CONDENSERS**  
.0005 each section, fitted trimmers—ceramic insulation, 29 6, plus 1 3 postage.

**ELECTROLYTIC CONDENSERS**

8 mfd. 350 v. ....	1 6
16 mfd. 350 v. ....	1 11
32 mfd. 350 v. ....	1 11
25 × 25 mfd. 200 v. ....	3 11
8 mfd. 150 v. ....	1 3
25 mfd. 25 v. ....	1 -
25 mfd. 50 v. ....	1 6
50 mfd. 12 v. ....	10d.
10 mfd. 25 v. ....	10d.
2 mfd. 450 v. ....	1 -
4 mfd. 450 v. ....	1 3
8 mfd. 450 v. ....	1 11
16 mfd. 450 v. ....	2 8
8 × 8 mfd. 450 v. ....	3 4
8 × 16 mfd. 450 v. ....	3 4
16 × 16 mfd. 450 v. ....	3 9
16 × 8 24 mfd. ....	4 2
8 mfd. 500 v. BR.850 ...	2 6
16 mfd. 500 v. BR.1650 ...	3 6

**P.M. SPEAKERS**

Size	With trans.	Less trans.
2½in.		10 6
3½in.		8 6
5in.	11 3	9 3
6½in.	12 6	10 6
8in.	14 6	12 6
10in.	21 6	
12in.		39 6

**MOVING COIL METERS**  
0-1 mA. 2½in., 12 6, 2in., 8 6.  
5-0-5 mA. 2½in., 10 6. 0-500 mA. 2½in., 15 -.

**FILAMENT TRANSFORMERS**  
6.3 v. 2 amp., 6 -.

**I.F. TRANSFORMER**  
465 kc/s, iron cored, 6/9 pr.

**OUTPUT TRANSFORMERS**  
Standard pentode matching midget, 3 6, small, 3 -, standard, 3/3. Push-pull matching, 4 -.

Multi-ratio, 4 6.  
6½in. **ENERGISED SPEAKER**  
700 ohm. field with output transformer, 'ROLA', 11 6.

# PARTS FOR MAGNETIC T.V.



**FRAME AND LINE COIL ASSEMBLY.**  
Perfectly made by a very famous maker, for standard type magnetic tubes, 9in., 10in., 12in. or 15in., we have a limited number only, the price is 16 6, and cannot be repeated once these are cleared, so please act quickly.

**PERMANENT MAGNETIC FOCUSING UNITS.** No current drain—for all makes of tubes—patented method of adjusting the gap, giving really clean pictures and even focus of whole of the tube free. Price 16 6 each.

**R. F. E. H. T. Non-Lethal**

**R.F. E.H.T.** We were so pleased with the quality of this unit that we have taken up the entire output of the manufacturer, the voltage can be adjusted to make it suitable for working 9in., 12in. or 15in. tubes, the unique design and vacuum impregnation combine to give a trouble-free unit which will give years of satisfactory service, and, of course, the big point about the R.F. E.H.T. is that it is not lethal, the size is only 4½ × 3½ × 4in., price, complete ready to operate, 65 -.

**£16 FOR A MAGNETIC TELEVISOR** (and H.P. terms if you wish), this we think you will agree a remarkable low price, even though the tube is not included, but the quality of the picture has not suffered, this was demonstrated to thousands of people at Radiolympia. We will demonstrate to you if you call. Full constructional data for novice or expert, 5 -. Explanatory leaflet free.


**P.M. FOCUSING for clear pictures**



## MISCELLANEOUS ITEMS

Blocking Osc. Transformer, 6/6. 9ft. dural. tube for aerial, 4 6.  
.1 mfd. 2.5 kV., 2 6. .1 mfd. 5 kV., 4 9. .02 8 kV., 3 9. .1 7 kV., 13 6. Vision Receiver strip (type 194), 45 -. Varley E.H.T. Transformer, 4 kV., 67 6. 2.5 kV., 27 6. B7C Valve Holder, 1/3. EF50 Valve Holder, 6d. Chokes, 200 mA. 10 henry, 10 -. 200 mA. 3 henry, 6 -. 80 mA. 10 henry, 4 6. 80 ohm. feeder, thin, 10d. per yd.; thick, 8d. per yd. Plastic 8 kV. Sleeving, 3 - doz. yds.

## OSCILLOSCOPE PARTS

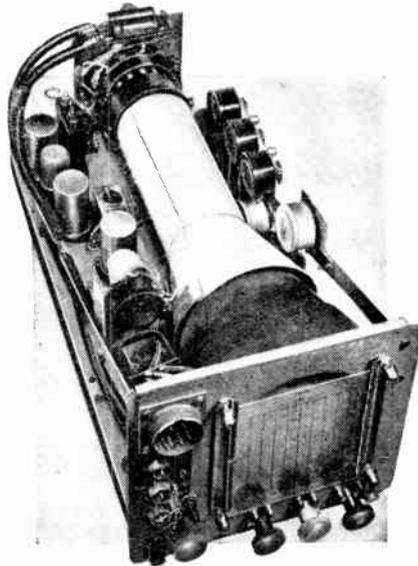

**TYPE 6 INDICATOR.** As specified for the "Wireless World" oscilloscope (reprint of data 9d.). Also for the "Inexpensive Televisor" (booklet 1 6), and the Mark I Televisor (constructors envelope, 2 6). These indicators are brand new, packed and sealed in manufacturer's original crates, they contain VCR97 Cathode Ray Tube, 4 EF50 valves, 3 other valves, and hundreds of useful components, including wire wound pots. Price is only £4/10/-, plus carriage and packing, 7 6.

# SPECIALS

## PARTS FOR PERSONAL RECEIVERS

New ex-W.D. chassis containing three B7G Valve Holders, resistors and other spares with valves type 1S4, and 2 1T4's, 29 6, complete with diagram of a midget receiver.  
**H.T. BATTERY UNITS,** 15 volts, but measure only 1½in. × 2½in. × ½in., 1/3 each; 10 for 10/-.  
**L.T. UNITS,** 3d. each; 2 6 dozen.  
**MIDGET .0005 TUNING CONDENSER,** 4 6 each.  
**MIDGET P.M. SPEAKER,** 2½in., 10/6.



## SHORTED TURNS COIL TESTER

You know that it is almost an impossibility to test for shorted turns in I.F. Transformers, Coils, L.T. Transformers, etc., with an ordinary ohmmeter. Our mains operated shorted turns coil tester will reveal these faults in a second. For one month only we are offering these to you at the remarkably low price of £5/10/- each.

## THE "SPEE-DEE" SIGNAL TRACER

A small metal case a few inches square, a flex terminating in a probe, a twin lead for connecting to either A.C. or D.C. mains, no switching, no tuning controls, and there you have the "SPEE-DEE" Signal Tracer. H.F., I.F., or L.F. checks—makes no difference: note frequency change is automatic. The fault is in the no-note stage. Yes, it's as simple as that. Price, with directions, £4, leaflet free.

## ELECTRIC HEATERS

Heavy cast iron work totally encloses the elements, so these are 100% safe even in confined spaces, just right for your radio den, garage, office, shop, etc. 900 watt (general) model, 19/6, plus 3/6, 250 watt (personal) model keeps legs and body warm for less than a farthing per hour, 23 6, plus 3 6.




## HOUSE TELEPHONES

Suitable for intercommunication between offices, workshops, stores, garages, big houses, kitchens, etc. Each station consists of normal size Bakelite handsets and desk or wall mounting cabinet with built-in selector switch, buzzer and push. All stations can communicate with one another independently. Each installation is absolutely complete and internally wired. 3-station installation complete with 50 yards 5-core cable £6/10/-. 4-station installation, complete with 50 yards 6-core cable, £8/10/-. 2-station installation, complete with 25 yards 4-core cable, £3/17 6.



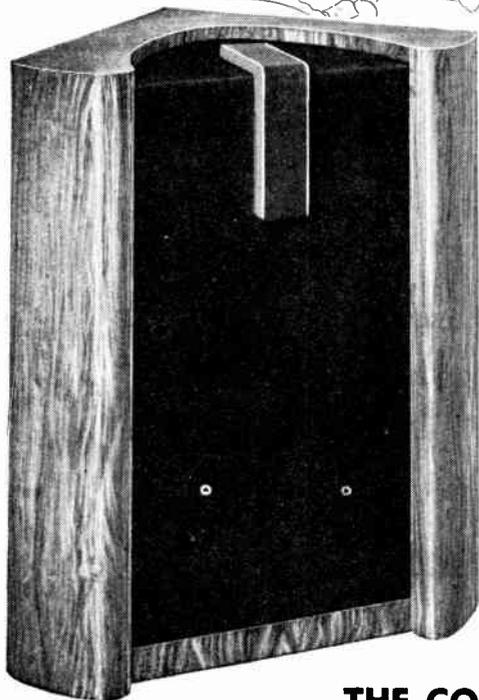**PRECISION EQUIPMENT (2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDLESEX**



## THE CORNER RIBBON LOUDSPEAKER

Details of this loudspeaker and its development are now available and will gladly be sent to you on receipt of a post card. In view of its specialised nature, the Corner Ribbon will not be released for random trade distribution. Enquiries may be placed initially through our normal distributors but subsequent demonstration and supply will be controlled from our laboratory in Huntingdon. Arrangements have been made for private test demonstrations in your own home by our own engineers at very low cost.

Price ex works £83 . 0 . 0

**ACOUSTICAL**  
MANUFACTURING CO LTD  
HUNTINGDON • HUNTS • TEL: 361

## TELEVISION WITHOUT TEARS

OUR Kit of Parts (down to the last nut and bolt) is proving doubly popular because (a) the price of £16/19/6 is amazingly low and (b) the explicit nature of our instructions and easy to follow point-to-point wiring diagrams ensures success for all. Its most convincing feature, however, is that the conversion of ex-government units is NOT involved.

The Televisor is built from standard radio components and assembled on two chassis, one for the Vision Receiver, Sound Receiver and Time Base, the other for the Power Supplies. It operates on A.C. Mains 200-250 volts.

If price is the primary consideration we can supply the Complete Kit for only £15 0s. 0d. The valves and C.R.T. are slightly used but guaranteed perfect in this case. The carriage charge on either Kit is 10s.

Price of the comprehensive point-to-point wiring diagrams and 17 pages of data is 5s. post free. May we urge you to send for these initially. If a Kit is subsequently purchased the 5s. will, of course, be credited. PLEASE SPECIFY LONDON OR SUTTON COLDFIELD WHEN ORDERING THIS DATA.

### NOTE THESE ★ FEATURES

- ★ No knowledge of television technique essential. All parts complete brand new and of the finest quality.
- ★ All parts may be purchased separately.
- ★ Rock-steady picture assured because six EF50 valves are used in the Time Base and Synch. Separator.
- ★ Unique "after-sales" service. Testing and alignment of receivers after completion of assembly undertaken for a nominal sum. WE GUARANTEE RESULTS.

Our Televisor is equal to many commercial models. Why not come along and see a demonstration during viewing hours?

### FURTHER BARGAINS!

**Mullard Resistance Capacity Bridge.** Absolutely brand new. Measures 10 pf. to 10 mfd. and 0.1 ohms to 10 megohms, A.C. Mains Operation, £8 19s. 6d., carriage paid.

**Indicator Unit Type 162.** Included in this equipment is a VCR517 6½in. C.R.T., a VCR139A 2½in. C.R.T., and the following valves: one 807, three SP61, four EA50, one 6J5 and a Klystron CV67. Also, incorporates an 0-1 mA meter and a 24 v. motor. ONLY £2 2s. 6d. plus 7s. 6d. carriage. Most wonderful value.

**Test Set 73.** This unit consists of a special purpose Oscilloscope with a 3½in. tube. Controls are Brightness, X and Y Shift, Focus, Amplifier, In/Out, Velocity, etc. The equipment is contained in a metal case size 19 x 12 x 8½in. and is complete with C.R. tube and all valves. Operates from A.C. Mains 230 v. 50 cycles. Supplied complete with comprehensive instructions for conversion to a standard oscilloscope, together with all the necessary parts for conversion. IN BRAND NEW CONDITION. Remarkable value at ONLY £7 19s. 6d. carriage paid.

**Receiver R1224.** Still going strong! A 5-valve battery superhet of outstanding performance and sterling quality, the R1224 makes an excellent communications receiver. Valve line-up: two of VP23, one FC2A, one HL2 and a 220PA. Frequency coverage 30-300 metres. Batteries required are H.T. 120 v., G.B. 9 v., and L.T. 2 v. Ideally suited for operation by trawlers and similar craft. May we suggest you submit your order promptly, as stocks are limited. Most reasonably priced at £4 19s. 6d., plus 7s. 6d. carriage and packing. Brand new and complete. Circuit diagram provided.

**Receiver Unit Type 71.** Will prove of interest to the Amateur. It is part of the TR1143 and tuned to the 124 Mc/s band. Contains eight valves, types; four EF50, two EF39, one EBC33 and one EL32. Numerous small components are included—four I.F. Transformers, etc. In excellent condition and offered at ONLY 19s. 6d., plus 3s. carriage and packing.

**Amplifier Unit 18/165.** A neat and compact equipment incorporating the following valves - two EF36, one EBC33, two EL32, together with microphone transformers, intervalve transformers, countless condensers and resistors, etc. A goldmine for only 19s. 6d. carriage paid. Shortage of space prevents us from listing more than a fraction of our tremendous stocks. In addition to "Surplus" items we also stock a comprehensive range of standard radio components, valves, 9in. and 12in. C.R.T.s and all parts for "Viewmaster," "Electronic Engineering," and other popular television kits.

More and more people are turning to us for expert advice and practical guidance. Why not call and discuss your problems with our fully competent technical staff? A cordial invitation extended to all.

Best Buy at Britain's



**CHARLES BRITAIN (Radio) Ltd.**

11, UPPER SAINT MARTIN'S LANE,  
LONDON, W.C.2

TELEPHONE 0545

3 minutes from Leicester Square Station (up Cranbourne Street)  
Shop Hours: 9-6 p.m. (9-1 p.m. Thursday). Open all day Saturday

# UNIVERSITY RADIO, LIMITED

## Offer Guaranteed Used Equipment at Attractive Prices

Decca Decalcan, 3 only, in perfect condition and working order. As new ..... £23 10 0

Collaro Microgram, 1948 model. Perfect. As new ..... £11 0 0

Pre-war Columbia Record Changer, in polished table cabinet. In almost new condition ..... £11 0 0

Collaro Record-changer Unit. As new ..... £9 0 0

Collaro Record-changer Unit, bar type. As new, each ..... £12 0 0

Collaro Record-player Unit, centre drive. As new, each ... £6 5 0

Garrard Auto-changer, Model RC65, fitted with Decca FFRR head. As new. AC mains ..... £15 0 0

Garrard Auto-changer, AC/DC, Model RC65/U-16C, in portable case. As new ..... £16 0 0

MSS Recorder Unit, 1948 model (disc). Complete less amplifier. As new, unused. 2 only ..... £35 0 0

German Recording Motor, with heavy 12in. turntable. Perfect

Another of similar make, complete with tracking-gear, less cutting-head. Perfect ..... £12 0 0

Marconi Console Radio, 1939 Model 564, 9 valve, 5 band (floor model). Complete with all valves, in perfect condition and working order ..... £35 0 0

Hallcrafters' SX28A, in perfect condition and working order, 110 to 250 AC ..... £40 0 0

AR88LF, one, as new, in original carton ..... £42 10 0

Another, perfect, less-valves..... £32 10 0

Another, complete at ..... £34 0 0

Eddystone 640, as new, with speaker, at ..... £22 10 0

Hambander, as new ..... £13 0 0

Eddystone 358X, with 8 coils and power-pack, in perfect condition and working order..... £25 0 0

BC348, converted for AC 200/250 volts. Perfect ..... £14 0 0

MCR-1, complete with power-pack, coils, phones, etc. As new ..... £8 0 0

S.T.C. Ex-W.D. Ball Mikes, 402C, moving coil, the finest make. Limited number only, each ..... £5 5 0

Avo Model D, Ex-W.D., equivalent to model 40. In perfect condition. As new ..... £8 10 0

E.D.C. Rotary Convertors, 220/240 DC to 230 AC 50 cycles, 1 phase, 120 watts, with Radio Filter Unit ..... £10 10 0

As above, 180 watts ..... £12 10 0

As above, 250 watts ..... £15 0 0

Rotary Converter, 24 volts DC to 230 AC 300 watts ..... £12 10 0

E.D.C. Rotary Converter, 230 DC to 230 AC, 50 watts ..... £4 10 0

Presto Portable Disc Recorder and play-back, with built-in amplifier, complete with valves. Ready for immediate use, and in perfect working order ..... £39 10 0

C.D.P. Disc Recording Unit, as new. Latest model, only 3 months old. Cost £39. Our price..... £27 0 0

Vortexion Recording Amplifier, Model AD47, as new. Complete with all valves ..... £28 10 0

Lexington Amplifier, as new, including pre-amplifier for M/C mike and pick-up. Cost £68. Our price ..... £19 10 0

### WE HAVE RECEIVED FURTHER SUPPLIES OF GOODS ADVERTISED IN PREVIOUS ISSUES

VG Tracking-gear, as new, a very fine job ..... £10 10 0

BSR Ampligram, Model AG4. As new ..... £22 0 0

H.M.V. Record-player (1949), table model, with built-in amplifier. As new ..... £15 10 0

Mullard Oscilloscope, in perfect working order. Cost £63 in 1946. A real bargain at ..... £17 10 0

United Electronics 15-watt AC/DC Amplifiers. Brand new, in sprayed metal cases. Moving coil mike and 'gram inputs. Complete with valves. £9 9 0

R.C.A. Amplifier Chassis, 50 watts, complete with valves. Four 6L6's in parallel push-pull. AC 110-volt operating. One only ..... £5 0 0

50-watt Amplifier, in metal case, 3 Mc. mike inputs and 'gram. input, 200/250 AC, complete with all valves. Two 807's in P.P. Built to former owner's specification ..... £10 0 0

12-watt Amplifiers, in wood cases, complete with valves, two 6V6's in P.P., with built-in M/C. mike transformer ..... £4 10 0

Pre-war "Wireless World" quality Amplifier and Radio Unit, in metal case, with separate unit for energising speaker field. Complete with all valves ..... £8 10 0

Pre-war Philco (U.S.A.), 6 valve, 6-volt car radio, complete and in good working order ..... £6 0 0

E.T.A. Wave Coil Winders. Hand wind—can be motorised. Complete with all accessories. As new, each ..... £22 0 0

Taylor Model 20A Circuit Analyser. As new ..... £11 0 0

Ladgear Electronic Fault-Tracer, 1948 model. As new... £18 0 0

Another, as above, with outer case slightly soiled, but internally perfect ..... £15 0 0

Taylor 65B Signal Generator. As new ..... £11 0 0

Avo 1948 Model Signal Generator. As new ..... £10 10 0

Avo Model 40. As new ..... £11 10 0

Avo Valve Testers, 1948, with roller panel. As new ..... £11 10 0

Hunt's Capacity and Resistance Bridge, Model CRB. As new ..... £11 0 0

Mullard Cap. and Res. Bridge. As new ..... £6 10 0

Avo Cap. and Res. Bridge. As new ..... £7 0 0

Thrush Cap. and Res. Bridge. As new ..... £7 15 0

Weston AC/DC Multi-range Test Meter, Model E665, 1,000 O.P.V., in perfect condition and working order..... £6 15 0

Weston All-wave Battery Oscillator, less batteries, with calibration charts. As new..... £6 10 0

G.B. Sound-on-Film Projector, 16 mm., Model L516. Complete in every detail, including large screen, spools, etc. In very good condition and working order. A real bargain at ..... £95 0 0

Lexington Radio Unit. As new £9 0 0

Recording Turntable, 12in. ... £2 0 0

Scott ex-W.D. Communication Receiver, 11 valves, 50 to 100 kc/s, 5 to 9 megs., 9 to 16 megs. Complete with valves. AC 200-250 volts. In perfect working order ..... £16 0 0

Magnavox 66 Speaker, with built-in output transformer, perfect ..... £4 0 0

1/2 h.p. Motors, 1 phase, 1248 revs., 220/250 volts AC. Various first-class makes. New, each... £4 10 0

Evershed's Bridge Meggers, 500 volts, with built-in resistance box. Perfect condition ... £15 0 0

Another, as new ..... £20 0 0

Goodmans 15 ohm, 12in. P.M. 20-watt Speaker. As new ..... £5 15 0

Goodmans 12in. P.M. Latest model As new ..... £4 10 0

Goodmans Axiom 12. As new £5 17 6

Goodmans Axiom 22. As new £9 10 0

Hartley-Turner, 1949 model P.M. Speaker. As new..... £6 0 0

Barker 148A Speaker. As new... £9 10 0

Vitavox 12in. P.M. Speaker. As new ..... £4 0 0

Tannoy 25-watt Amplifier, complete with valves. Two mike inputs. In metal and wood case, AC 200-250 volts. Perfect £10 0 0

B.T.H. RK Senior 5speaker. Mains energised. 15 ohm. speech coil. Perfect ..... £3 0 0

National H.R. O. Seniors, complete with 7 coils, power-packs. In perfect condition, some as new. From ..... £25 to £29 0 0


THE ABOVE ITEMS ARE ONLY A SMALL SELECTION FROM OUR EXTENSIVE STOCKS

We have other types of equipment arriving daily. We urgently need good used equipment, and will buy for spot cash. Bring, send or phone for offer.

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE PAID.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

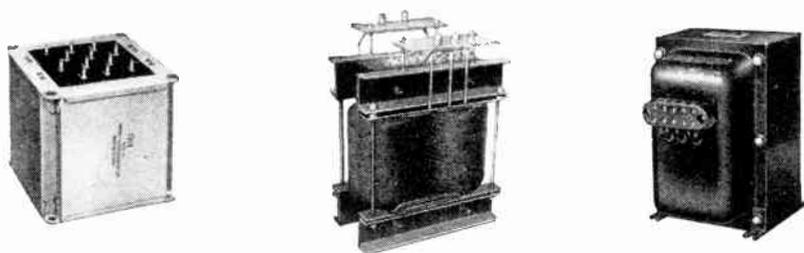'Phone GERrard 4447 and 8582. Hours 9 to 6. Thursdays 9 to 1.



**TRANSFORMERS WITH MAXIMUM EFFICIENCY · MINIMUM COST**

The Woden organization specialise in Quality Transformers for Radio, Television, Industrial Electronics, Amplifiers, Transmitters, etc., and are in heavy demand for the overseas market. A few of the prominent journals specifying Woden Components are "Wireless World" Williamson Amplifier, "Electronic Engineering" Home Built Televisor, "R.S.G.B." Modulator, etc. Special Types of Shrouded and Open Type Components have been produced at very keen prices to enable our clients to purchase a first class product to meet world competition. Why not send today for illustrated Catalogue and Price lists of our full range.

The Transformers illustrated from left to right are POTTED TYPE, compound filled, made in a very comprehensive range. Smart in appearance, impervious to moisture and silent in operation.

INDUSTRIAL TRANSFORMERS, either one, two or three phase open or protected, oil or air cooled. All types up to 100 K.V.A.

AUTO TRANSFORMERS, Single or Multiphase either step up or step down. Sizes from 60 V.A. to 50 K.V.A.

Your enquiries are invited for all types of Transformers also Amplifying Equipment.



**WODEN TRANSFORMER Co. LTD, MOXLEY ROAD, BILSTON, STAFFS.**

V.T.L.



UNBREAKABLE  
RUBBER MOULDED  
PLUG

MOULDED PLASTIC  
SOCKET

BERYLLIUM  
COPPER CONTACTS

*Control by*

**PAINTON**

& COMPANY LTD

KINGSTHORPE · NORTHAMPTON

# CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

## RECEIVERS OF THE AN/ARC-5 SCR-274-N 'COMMAND' SERIES

The Q. Fiver. R-23/ARC-5, B.C.453, I.F. 85 kcs., 550-190 kcs., 545-1,850 metres, or R-25/ARC-5, B.C.454, I.F. 1415 kcs., 3.0-6.0 mcs., 100-49 metres, or a few only: R-27/ARC-5, B.C.455, I.F. 2830 kcs., 6.0-9.0 mcs., 49-33 metres. Each a 6-valve superhet receiver, with valves: 2/125K7, 12K8, 125F7 or 125K7, 125R7, 12A6. The Receiver is totally enclosed, excepting the dynamotor (not supplied) for 24v. operation. Dimensions 11 x 5½ x 5in. Complete with circuit. Brand new in maker's cartons, or unused, good condition. Mainly R-23/ARC-5 and BC-453.

CLYDESDALE'S PRICE ONLY. **50/-** each. POST PAID

Or used, with case slightly dented, mainly BC-454, at 37/6 each, post paid. Set of Circuits for Command Equipment (SCR-274-H) at 4/6 or BC-453 1/3; BC-454 1/3; BC-455 1/3; BC-946 1/3; post paid.

## MEDIUM WAVE CONVERSION COIL ASSEMBLIES.

Cat. No. H67, for 85 kcs. I.F., BC-453. R23/ARC-5, or Cat. No. H68, for 1415 kcs. I.F., BC-454, R-26/ARC-5, or Cat. No. H69, for 2830 kcs. I.F., BC-455, R-27/ARC-5. Each unit comprised, Ae., H.F. and Osc., coils, wound on former 4½in. long, maximum diameter 1in. minimum diameter ½in., with circuit and data.

CLYDESDALE'S PRICE ONLY. **10/-** each. POST PAID.

### ★ STILL AVAILABLE.

★ Units of SCR-522, B.C.624 Receiver Chassis, with valves, etc., plus free gift B.C.625 Transmitter Chassis (partly stripped by B.O.T.) at 37/6.

★ R.14 B1 V.H.F. Receiver Unit at 99/6.

★ A.C. Power Unit Type 3 at 79/6, or both above items at £8.8.0.

★ Crystal Multiplier type MI-19468 at 39/6.

★ R-28/ARC-5 100-150 mcs. Receiver Unit at 37/6.

★ Bridge Megger 100 megs. at 1,000 v. at £35.

★ Wee Megger 20 megs. at 250 v. at £5 19. 6.

★ Battery Amplifier A.1368 at 11/6.

★ SCR-720 Blower, with shunt motor at 17/6.

★ Reflector Ariel (MX-137/A) at 5. 6.

As previously advertised, price includes carriage.

## BC-733-D CRYSTAL CONTROLLED RECEIVER UNIT.

Part of RC-103-A Beam Approach Equipment. Operates on frequencies 108.3, 108.7, 109.1, 109.9 and 110.3 mcs. with suitable crystals (not supplied).

Valve line-up:—3/717A, 2/125G7, 125Q7, 12A6, 12AH7GT, 2/125R7, operates from 14 v. or 28 v. dynamotor (not supplied) complete in black crackle finish metal case, dim:—overall length 14½ x 7.3/32 x 5in.

CLYDESDALE'S PRICE ONLY. **30/-** each. POST PAID

## R9/APN-4 RECEIVER UNIT.

Part of the "Loran" equipment, 4 preset frequency positions, three in band 1 (1.6-3.3 mcs.) and one in band 2 (7.6-11.7 mcs.), 15 valves, 4/65K7GT, 65A7, 65N7GT, 6H6, 65L7GT, 65J7GT, 3/GB4, 5U4G, 2/2X2, plus VR105 stabiliser. Slug tuned I.F. Trans. 1.05 mcs. In metal case 9 x 8 x 19½ in. height with 400 cs. power unit which also feeds Ind. Unit.

CLYDESDALE'S PRICE ONLY. **42/-** each. CARRIAGE PAID

## Ideal as SHORT WAVE CONVERTERS.

Brand new in maker's carton. R.F. Unit type 26 for 65-50 mcs., 5-6 metres. Variable tuning 2/VR135 (EF54), VR137 (EC52). Output approx. 7-8 mcs. in metal case 9½ x 7½ x 4½in.

CLYDESDALE'S PRICE ONLY. **35/-** each. POST PAID

ATTENTION PERSONAL SHOPPERS. NOW OPEN, bargain department, at No. 18, Bridge Street, large selection of items available too varied to list, (small quantities) all at Clearance Prices. Well worth a visit.

## HIGH VOLTAGE DYNAMOTOR UNIT PE-73-G.

Input 28 v. D.C., 19 amps. Output 1,000 volts D.C., .35 amps. 5,000 r.p.m., .35 KVA, 55°C. temperature rise, ½ hour time rating, with Dynamotor Contactor, and suppressed for Radio use. Dim: overall height 10 x 10½ x 6½in.

CLYDESDALE'S PRICE ONLY. **32/6** each. CARRIAGE PAID

### NOW READY

New Illustrated List No. 6 (152 pages). New applicants please send 6d. to cover distribution cost. Please print name and address.

## POWER UNIT 247.

For 230 v., A.C., 50 cycles. Output 600 v. at 200 mA. smoothed D.C. 6.3 v., A.C. 3 A. Complete power pack, with 5U4G rectifier, etc., built on metal tray 10½ x 9 x 1½in. with grey finish metal cover 11 x 9½ x 7½in., two chromium handles, red indicator and inspection door, giving access to rectifier and pilot bulb.

CLYDESDALE'S PRICE ONLY. **59/6** each. CARRIAGE PAID

with transit box.

Brand New, in maker's carton.

Ex-U.S.A.S.C.

## MASTER OSCILLATOR TYPE MI-19467-A.

A "ready-made" V.F.O. Unit, ranges 2-10 mcs. With 807 valve, grid current meter-E.C.O. circuit, variable inductances, calibrated micrometer controls, etc., in metal case 12 x 10 x 6ins. with Instruction Books.

CLYDESDALE'S PRICE ONLY. **79/6** each. CARRIAGE PAID.

## CAMERA CONTROL ELECTRICAL.

Type 35, No. 26, ref. 14A/2206. Input 24 volts, D.C. Time Interval selection switch, 2-51 seconds. One pulse per revolution. Exposure counter. Ideally suitable as the basis of an enlarger timer, data and circuit supplied. Also many other timing uses. In metal case 8 x 3½ x 4in. overall inc. controls. Supplied in padded wood transit box 8½ x 4½ x 5½in.

CLYDESDALE'S PRICE ONLY. **27/6** each. POST PAID

## PARAGON INTERVAL TIMER.

H.3 Time Delay Relay 110FB/260, 220v. A.C., 50-60 cs. 3.6 w. Suitable for time delays 0-10 seconds. 5.P.D.T. scale graduated in seconds. Automatically re-set when switched off. Dim: 3½ x 2½ x 2½in.

CLYDESDALE'S PRICE ONLY. **21/-** each. POST PAID

## EX. U.S.A.A.F. VACUUM PUMP 137J/3749.

With 24v. 11.2 amps. ½ H.P. Motor 6,600 r.p.m. Data (constant exhaust). 2,200 strokes per minute (running free). Pump capacity 10 cubic in.; pumping capacity (Air) 13 cubic feet per minute; pumping rate (water) 5½ gallons per minute (5/6 cubic feet per minute); Air pressure 36 lb. per sq. in.; water pressure 60 lb. per sq. in. (safe); water pressure 130 lb. per sq. in. (max.); eight ½ in. inlet valves; eight ½ in. outlet valves—internal. Whole assembly 12 x 7½ x 7in. shock mounted on board 14½ x 6½ x 2½in., accessories include: eight nozzles (various sizes), one with rubber tube, and Schween regulating valve.

CLYDESDALE'S PRICE ONLY. **40/-** each. CARRIAGE PAID

## Brand New, in maker's original carton. ADM. PATT. W7460 VIBRATORPACK.

H71. Input 12 volts, D.C. Output 300 v. 100 mA. unsmoothed.

Complete with 7-pin, reversible, synchronous vibrator, etc., in metal case 5½ x 4 x 5½in. overall, finish grey (similar to E954 in appearance).

CLYDESDALE'S PRICE ONLY. **21/-** each. POST PAID

## R.C.A. DRIVER TRANSFORMER (110K/117) XT.3202.

E562. C.T. Primary: Inductance 3.4 henries. Two Secondaries: Inductance 14 henries each. Ratio: whole primary to one secondary 1:2 approximately. Dimensions: Height 4½ x 3½ x 3½in., weight 6½ lb. Four hole fixing.

CLYDESDALE'S PRICE ONLY. **15/-** each. POST PAID


## Brand New. 2 VOLT, 7 A.H. ACCUMULATOR.

Lead acid type, non-spill top. Transparent plastic case, height 4½ x 3½ x 1½ in. Ideal for test sets or midjet radios.

CLYDESDALE'S PRICE ONLY. **3/11** each. POST PAID
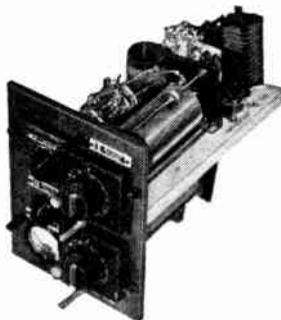
## CO-AXIAL CABLE, any length supplied.


12 mm. 52 ohms solid core at 6d. per yard Minimum 20 yards, 10/-, post paid.



Order direct from: **CLYDESDALE** SUPPLY 2 BRIDGE STREET GLASGOW - C.5

Phone: South 2706/9.

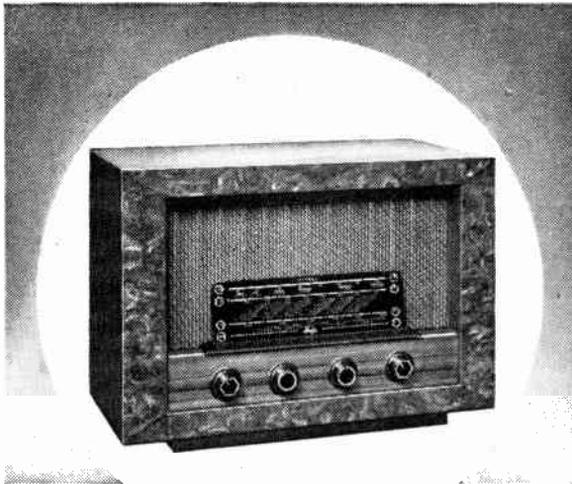Visit our Branches in Scotland, England and Northern Ireland.



## THIS SET

**will satisfy your expert judgment**

When you criticise a radio, you must in fairness, ask yourself: is this set as good as it could be for the price? When you examine a Sobell set, any Sobell set, we feel confident that you will agree that it gives superb value for the money. Look at Model 610, for instance. It is a typical model from the large Sobell range—a 6 valve, all-wave superhet with easily removable scale for new wavelengths, 10" speaker, and 6 watts push-pull output, A.C. mains, 200/250 volts. We invite you to check every component—circuits, signal rectification, tuning controls, the I.F. selectivity, the radio sensitivity. We know that you'll find them even better than you expected.

WITH

**2 years**

**FREE ALL-IN-SERVICE  
IN THE HOME**

★ *Valves and Cathode Ray Tubes are subject to the standard B.V.A. guarantee.*

Because you know much more about radio than the average man-in-the-street, we needn't stress the fact that we just couldn't afford to operate the Sobell 2 years free maintenance plan\* if our sets were not the good sets they are.


The Sobell dealer in your district will be glad to arrange a demonstration of any of the new models—one of which will suit your pocket, and give you the technical efficiency you so rightly demand—a set you will be proud to own.



**RADIO AND TELEVISION**

**SOBELL INDUSTRIES LTD., Langley Park, Slough, Bucks.**  
Tel.: Slough 22201/5

# A Pre-Fab Cabinet Widney

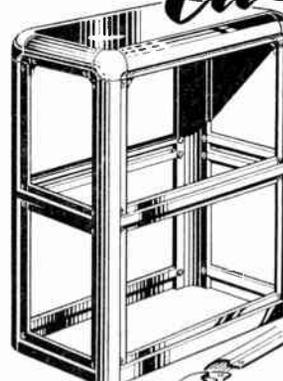

**- DORLEC  
REGD  
CABINET SYSTEM**

providing an easily constructed cabinet for manufacturers and laboratories. The range of extruded sections, corners and brackets now available enables a housing for individual designs to be easily erected.

Technical & Sales Agent  
**C. H. DAVIS**  
59, BROMPTON RD.  
LONDON, S.W.3


Write for Illustrated leaflet.



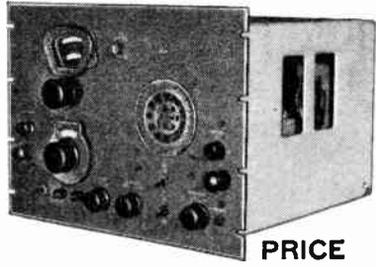**MANUFACTURERS**

**HALLAM SLEIGH & CHESTON LTD**  
WIDNEY WORKS · BIRMINGHAM · 4  
ESTABLISHED 1898  
Phone: Aston Cross 0914 (4 Lines) · Grams: Superfine, Birmingham, 4

**SPECIAL  
OFFER  
TO THE  
Enthusiast**



**PRICE  
£28.10**

Famous U.S.A. Radio Communications Receiver, Type BCL147A. This Receiver was one of the last types to be sent into this country for use with the Armed Forces and is a 13-Valve Superheterodyne of high efficiency covering from 1.5 to 30 m/cs in four bands, with a 5 per cent. frequency overlap between bands. Band division is 1.5 to 2.1 m/cs, 3.1 to 6.6 m/cs, 6.6 to 14.0 m/cs and 14.0 to 30.0 m/cs. Frequency calibration is accurate to within 1 per cent. of indicated value. The set has a built-in power pack for operation from 115 volts AC 50/60 cycles and we supply a suitable Auto Transformer to operate from standard 230-olt A.C. mains for use with each set. The Receiver employs two stages of R.F. Amplification with 455 KC's IF's which have an externally controlled band and sharp response switch. Valve Line Up: 1 6X17, 4 6XK7, 1 6X-A7, 1 6J5, 1 6HG, 1 6XJ7, 1 6XQ7, 1 6K6 or 6V6, 1 VR150 and 1 5U4G. The Handsome Front Panel is complete with Aerial Matching Control, Wave-band Switch, Tuning Control, AF Gain Control, HF Selectivity Control, BFO Control, Sensitivity Control, Power On/Off Switch, BFO On/Off Switch, AVC and Manual Control, Built-in Loudspeaker and Indicator Light Control. Size 19in. wide, 14in. high and 19in. deep.

Price includes suitable Auto Transformer, Packing in Wooden Crate, and Carriage Paid to your door.

**NO CARRIAGE OR PACKING CHARGES**

Carriage paid on all orders in U.K. For Fire and Export additional charges must be added or we will quote.

**WESTON PRODUCTS**  
(LIVERPOOL) LTD. • TEL: ROYal 5754/5.  
**71-GT-GEORGE STREET LIVERPOOL 1**



# Another **GOODMANS** Axiom

## HIGH (FIDELITY + POWER) <sup>Regd.</sup>

With an exceptionally high electro-acoustic efficiency, this new version of the well-known "Axiom Twelve" has been developed to satisfy the great demand for High Fidelity power reproduction.

Send for illustrated folder D129



**GOODMANS INDUSTRIES LTD.,**

Lancelot Rd., Wembley, Middx. Phone: Wembley 1200. Grams: Goodaxiom, Wembley

# AERIALITE

**makers of the world's best  
AERIALS & EQUIPMENT**

Introduce their **NEW**—



**AERIALITE ...**  
the most advertised  
aerials made!

According to statistics supplied by "The Statistical Review," Aerialite Aerials are easily the most extensively advertised aerials made. Our present campaign includes advertising in the "Radio Times," "Daily Express," "Daily Mail," "News Chronicle," "News of the World," "The People," "Sunday Express," "London Evening News," "The Star," "London Evening Standard," and the leading Midlands papers. The public are asking for "AERIALITE," —The Best!

**AERIALITE Ltd.**  
STALYBRIDGE, CHESHIRE

## AERIAL Fitting SERVICE

- Are you missing sales through the inability to fit an aerial? If so, cash in now on the **AERIALITE AERIAL FITTING SERVICE**. This new service by the World's Largest Makers of Aerials applies to the wide range of **AERIALITE TELEVISION** and **MASTATIC AERIALS**.
- We shall also be pleased to receive applications to join our organisation from dealers who have experience in aerial fitting.
- **EXAMPLE:** Fitting of our new Popular D.P.O. MODEL 52. You can supply this low-priced Television Aerial complete and erected for **£8.0.0** only. D.P.O. MODEL 52. Complete with 10ft. steel mast and Chimney Lashing Brackets, etc., **£4.10.0**. Complete Erection Costs, **£3.10.0**—Total Cost **£8.0.0**. Write today for full details.

*Make sure you can meet the demand!*



## 18 TOTTENHAM COURT ROAD, LONDON, W.1

Tel: MUSEum 2453

Tel: MUSEum 4539

Shop hours: Monday-Friday 9—5.30. Saturday 9—1

**FULL MAIL ORDER FACILITIES Please add postage**

### A.D.S. QUALITY AMPLIFIERS

Full constructional details of our 4½-watt inexpensive quality amplifier are now available, including circuit diagram and layout pictures. Postfree. 10s.

Complete set of components for above amplifier, including cabinet, chassis, knobs, etc. Carriage free, only £8/10/-.

Complete amplifier, constructed and tested Carriage free, only £9/9/-

### WILLIAMSON AMPLIFIER

Main transformer 425-0-425 volts 200 mA., 6.3 v. 4 a.; 6.3 v. 2 a.; 5 v. 3 a. Pri. 210 230, 250 volts 30 c.p.s. Size 4¼ x 4¼ x 4¼ high. (Postage 1/6). £3/10/-

Choke 10 Hry. 150 mA. Size 2½ x 3¼ x 3¼ in. high. Fully shrouded. (Postage 1/-) £1/5/-.

Choke 30 Hry. 40 mA. Size 2½ x 1¼ x 2¼ in. high. (Postage 1/-) 13/6.

### VIEWMASTER (post free).

Complete set of T.C.C. Condensers, £6/15/-.

Complete set of Bulgin components, 12/6.

Complete set of Westinghouse components, £3/2/6.

Complete set of Whiteley components, £6/5/-.

Appropriate Morganite Resistors from stock.

### “ WIRELESS WORLD ” TELEVISOR.

Complete set of TRF coils London area only, Bel Sound Products, £2 8 6. (Postage 9d.)

Complete set of Superhet coils London or B'ham, Bel Sound Products, £2/12/6. (Postage 9d.)

### “ ELECTRONIC ENGINEERING ” TELEVISOR.

Complete set of coils and chokes, Bel Sound Products, 15/-, Birmingham 18/6 (Postage 9d.)

Scanco Line Output Transformer. (Post 1/3). £1/5/6.

Scanco Scanning coils. (Post 9d.) £1/5/6.

Scanco Focus coils. (Post 1/6) £1/10/-.

Stewart 4 KV. EHT with 4VCT heater winding. (Post 1/6) £3/3/-.

Stewart 5 KV. EHT with 4VCT heater winding. (Post 1/6) £3/15/-.

Stewart Mains transformer to spec. (Post 1/6) £4/10/-.

Set of 4 Black knobs with gold lettering. (Post 6d.) 5/-.

### MASKS (Postage 6d.)

6in. stone, 7/10; 9in. black, 9/6; 9in. stone, 11/6; 12in. black, 18/-; 12in. stone, 21/6.

### LENS (Postage and packing 1/6 extra)

The latest oil filled plastic lens for all types of Television.

6in. type, £1/7/6.

9in. type, £3/15/-.

12in. type, £4/10/-.

12in. Television lens in attractive modern and adjustable floor mounting stand (wood finished dark oak), £5/10/6 (post 3/6).

12in. Television lens for table model television. Fully adjustable to suit all types. Stand constructed throughout with clear plastic, £5/19/6 (Post 3/6).

### CHOKES (Postage 9d. extra)

All wound to our own spec. and neatly finished.

10 Hy 75 mA 150 ohms, 4/9.

10 Hy 100 mA 300 ohms, 9/-.

15 Hy 80 mA 200 ohms, 9/-.

10 Hy 150 mA 200 ohms, 10/6.

### T.C.C.

.05mfd.	350 v.d.c. wkg.	Metalmite	CP35N	2/-.
.1 mfd.	350 v.d.c. wkg.	Metalmite	CP37N	2/3.
300 pF.	350 v.d.c. wkg.	Micadisc	CM30	1/6.
.1 mfd.	350 v.d.c. wkg.	Plecoack	CE30N	2/6.
.2 mfd.	350 v.d.c. wkg.	Plecoack	CE30P	2/6.
.20 mfd.	12 v.d.c. wkg.	Plecoack	CE30B	2/6.
.001 mfd.	6 KV.d.c. wkg.	Visconol	CP55QO	4/6.
.01 mfd.	5 KV.d.c. wkg.	Visconol	CP56QO	7/6.
.1 mfd.	2 KV.d.c. wkg.	Visconol	CP56X	7/6.
.1 mfd.	7 KV.d.c. wkg.	Visconol	CP58QO	15/-.

**RECEIVERS R.1355.** The ready made Vision and Sound receivers specified for "Inexpensive Television," a copy of which is supplied with each set. Receives London or Birmingham Television simply by plugging in the requisite R.F. Unit. ONLY 45/- (carriage 7/6).

**R.F. UNIT 26.** Used with the above receiver for Birmingham TV. BRAND NEW IN MAKER'S CARTONS. ONLY 35/- (postage 1/6).

**INDICATORS TYPE 6.** The Indicator Unit specified for "Inexpensive Television." Contains C.R. Tube VCR97, 4 valves EF50 and 2 EB34. BRAND NEW IN MAKER'S CRATES. ONLY 90/- (carriage 7/6).

**TRANSFORMERS** for the above Televisor have been specially made, as follows: Time Bases and Vision Transformer: 350-0-350 v. 160 mA., 5 v. 3 a., 6.3 v. 6 a., 6.3 v. 3 a.; ONLY 36/-.

Sound Receiver Transformer: 250-0-250 v. 100 mA., 5 v. 3 a., 6.3 v. 6 a.; ONLY 27/6. E.H.T. Transformer for VCR97 2,500 v. 5 mA., 4 v. 1.1 a., 2-0-2 v. 2 a.; ONLY 27/6. Complete price list of components for this televisor sent on request.

**RECEIVERS R.3170A.** Another Radar Unit popular with TV constructors working out their own design. Contains 15 valves as follows: 8 of EF50, 2 RL37, 1 RL16, 1 HV2, 1 R3, 1 EA50, 1 CV188, and a 30 m/cs I.F. Strip, etc. ONLY 59/6 (carriage 7/6).

**RECEIVER APW 4790A.** 1½-metre receiver containing 9 valves: 6 of SP61 and 1 each of RL7, RL16, EA50. Ideal for use as a Vision Receiver as it has 6 I.F.'s of 12 m/cs with 4 m/cs bandwidth. BRAND NEW, but some less coils which were not fitted by the makers when the contract finished. With these we supply 3 11 mm. formers enabling coils to be wound. ONLY 59/6 (carriage 5/-).

**INDICATORS TYPE 162B.** Contains 2 CR Tubes, a 6in. VCR517 and a 3in. VCR139, and 3 valves SP61, 4 EA50, 1 VR17, and a Klystron CV67. In addition is fitted with a .5 millimeter and a 12 v. blower. ONLY 67/6 (carriage 12/6).

**ADMIRALTY TRANSMITTER 7AD.** Contains valves 6V6G, VU111, CV73, and 2 of CV63, in addition to transformers, condensers, resistors, transmitting gear, etc. BRAND NEW. ONLY 19/6 (carriage 5/-).

**TRANSMITTER "PARCEL."** A beautiful assembly used in an R.A.F. Transmitter. Contains 2 large .0002 mfd. variable transmitting condensers, short wave coils, variable inductance, switching, 3 2½ in. knurled tuning knobs, 4 2½ in. bar knobs, etc., etc. BRAND NEW IN MAKER'S CARTONS. ONLY 10/- (carriage 3/6). C.W.O. Please.

S.A.E. for lists.

**U.E.I. CORP., The Radio Corner**  
138, GRAY'S INN ROAD, LONDON, W.C.1

(Phone: TERminus 7937)

Open until 1 p.m. Saturdays, we are 2 minutes from High Holborn (Chancery Lane Station), 5 minutes by bus from King's Cross.

# D.C.

## Voltage Changers

### BY VALRADIO

The introduction of D.C. Voltage Changers meets a long standing need by enabling users to obtain up to 2,000 volts D.C. from D.C. inputs of 6, 12, 24 or 32 volts. H.F. Suppression incorporated. L.F. Suppression optional. If required, tapings at 110 or 230 volts A.C. may be made (to special order) for gramophone motors. The output from these D.C. Voltage Changers is reliable and in the many cases where high D.C. voltages are required, Valradio Models will be found ideal. Details gladly sent on request.

6 V.D.C. Input/40 watts output.	6 V.D.C. /90 watts output.
12 V.D.C. input/80 watts output.	12 V.D.C./140 watts output.
24 or 32 V.D.C./90 watts output.	24 or 32 V.D.C./150 watts output.

£11.0.0

£14.14.0

**VALRADIO ALSO MAKE D.C.—A.C. Converters for A.C. outputs at standard voltages up to 400 watts: Frequency Changers, and heavy duty rectifier units, to deliver 50, 100, 200 or 300 watts.**

## VALRADIO

SPECIALISE IN POWER CONVERSION

VALRADIO LTD.


57, FORTRESS ROAD, N.W.5

\*Phone—Gulliver 5165
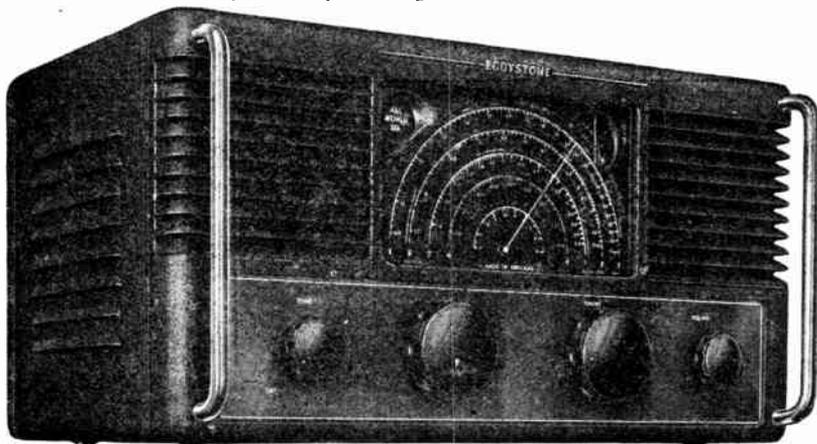
# THE NEW EDDYSTONE "ALL-WORLD 6" RECEIVER

A British Product

Specially designed for the remote Overseas listener



- ★ 6 volt Accumulator Operation
- ★ Low Current Consumption
- ★ Outstanding Performance

A wealth of practical experience in the design of shortwave receivers for tropical markets has been embodied in the Eddystone "All World Six" Receiver. It is designed to provide the remote "out-station" listener with a specialist built receiver capable of first-class performance and possessing the important feature of low battery consumption. Selectivity, sensitivity, quality of reproduction and performance on all wave bands, including the highest frequencies, will satisfy the most critical. Workmanship and quality of materials used are of the finest to ensure the highest degree of reliability. The wave range of the "All World Six" Receiver is continuous from 30.6 Mc/s to 484 Kc/s (9.8 to 620 metres). The current consumption is only 2.5 amperes from a 6 volt accumulator and no H.T. battery is required. This receiver is eminently suitable for those who, lacking electric supply mains, want performance equivalent to a mains-operated receiver, allied to the utmost economy in current consumption.

specialist built receiver capable of first-class performance and possessing the important feature of low battery consumption. Selectivity, sensitivity, quality of reproduction and performance on all wave bands, including the highest frequencies, will satisfy the most critical. Workmanship and quality of materials used are of the finest to ensure the highest degree of reliability. The wave range of the "All World Six" Receiver is continuous from 30.6 Mc/s to 484 Kc/s (9.8 to 620 metres). The current consumption is only 2.5 amperes from a 6 volt accumulator and no H.T. battery is required. This receiver is eminently suitable for those who, lacking electric supply mains, want performance equivalent to a mains-operated receiver, allied to the utmost economy in current consumption.

**PRICE: £37. 10. 0d. ex Works**



You are invited to write for descriptive literature and the address of your nearest Distributor to the sole manufacturers :

**STRATTON & CO., LTD., EDDYSTONE WORKS, WEST HEATH, BIRMINGHAM, 31**


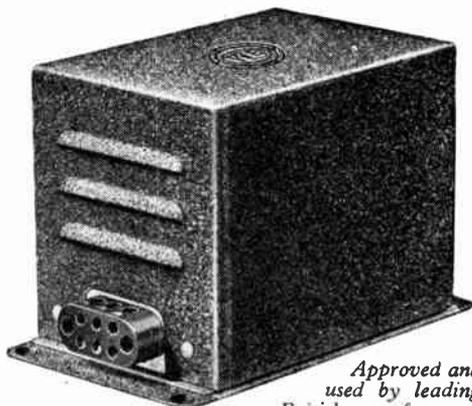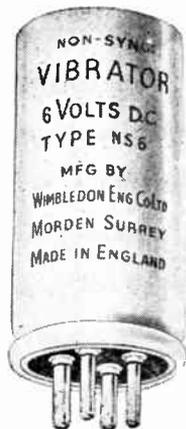
## It's got to be good

The heart of a Vibrator Power Unit (which supplies H.T. Current from low power D.C.) is the vibrator itself. Unless that gives a first class performance and goes on giving it for many, many hours, you have a heap of trouble on your hands. Hence the popularity of the "Wimbledon" Vibrator among many well known radio and electronic engineers. We have done a great deal of work on this Vibrator and we think it is just a little better than any other you can get. We are producing both synchronous and non-synchronous Vibrators and a complete range of Vibrator Power Units. Write for full details and judge them for yourself.



Approved and used by leading British manufacturers of car radio sets and receivers operated entirely from low voltage supplies.


### WIMBLEDON

ENGINEERING COMPANY · LTD

GARTH ROAD · LOWER MORDEN · SURREY · TEL: DERWENT 4814, 5010

CRCA

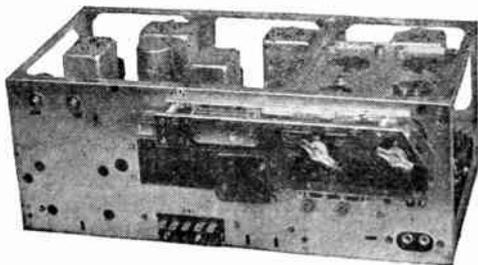
**2 METRE ENTHUSIASTS !!!**  
**BC624 Receivers part of SCR522. Brand New.**




Easily converted to cover 2 metre band. 10 valves. 9003 1st R.F., 9003 Mixer, 12AH7 Crystal Osc., 9002 Harmonic Gen., 9003 Harmonic Amp., 12SG7 1st I.F., 12SG7 2nd I.F., 12SG7 3rd I.F., 12CB 2nd Det., A.V.C. 1st audio, 12J5 2nd audio, I.F. 12 Mc/s. Power required 300 V. at 60 mA. and 12 V. 1.7 A. Drastically reduced. Few only. 19/6. Carr. 1/4d.

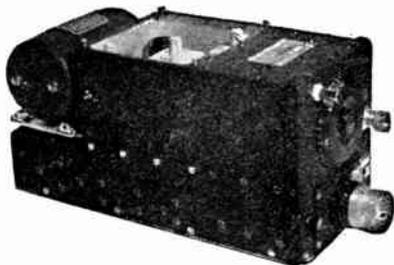**BC.306.**

**Antenna Units.** Size 16in. x 8in. x 8in. Black Crackle Cabinet. Aerial Loading Variometer 3 pole 5 way Ceramic Switch. 4 porcelain lead-through insulators. Precision slow motion dial. 3 6000 v. 80 mmf. block condensers. Brand New. 10/- each. Carr. 2/6.



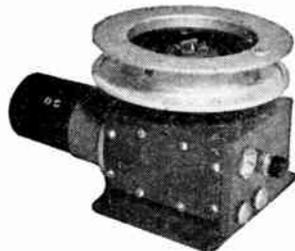**Receiver Type 26/ARCS.** 3-6 mc/s. 6 valves. 23 v. dynamotor fitted. Brand New in Original Sealed Cartons. Price 79/6 each. Carr. 1/4.



**Antenna Reels.** Type R1142A. Motorised 1/13 h.p. Motor. 28 v. 5 amps. 6in. Detachable Pulley. Elaborate Reduction Gearing. Instantaneous positive stop. Brand New in Sealed Cartons. each 30/-, Carr. 1/4.

**PROMPT DELIVERY AND SATISFACTION GUARANTEED AS ALWAYS**

**EXPORT ORDERS INVITED**

24\* stamped envelope must accompany all enquiries.

LISTS AVAILABLE

**H.P. RADIO SERVICES LTD.**

Britain's Leading Radio Mail Order House  
 Estd. 1935

**55 COUNTY ROAD, WALTON, LIVERPOOL, 4**

Tel.: Aintree 1445

Staff Call Signs, G3DGL, G3DLV

from the range of instruments

*The* **CONSTAC**  
 Constant Voltage Transformer

A versatile transformer which provides a fully stabilised 6.3v. heater supply in addition to a variety of stabilised H.T. outputs. Originally designed for use in E.I.L. instruments, the CONSTAC\* is now available to manufacturers of high-grade equipment.



TYPE A

\*Made under licence by  
 The Banner Electric Co., Ltd.

Input: 260 to 260 v., 50 c/s.  
 L.T. Output: 6.3 v., 2 A.  
 H.T. Output: 350 v., 25 mA  
 or 700 v., 15 mA or 35 v.  
 15 mA and 170 v. 25 mA.

**ELECTRONIC INSTRUMENTS LTD**  
 17 PARADISE ROAD · RICHMOND · SURREY



*Stars for Sale!*

**BUY ONE FOR XMAS!**

**COLLARO**



**AC 504 SINGLE RECORD PLAYER**

The most competitive unit in the market today. A powerful rim drive motor provides smooth running with constant speed. 10in. turntable, auto stop and magnetic P.U., conveniently mounted on unit plate. 200-250 v. A.C.

Price inc. P. Tax  
 £5/3/2  
 or with Xtal P.U.  
 £5/17/6

★ **WEARITE TAPE DECK**—Early delivery—Price £25. ★

**TELEVISION COMPONENTS**  
 B.T.H. Crystal Diodes C21.C. 11/3.  
 S.T.C. H4200 H.V. rectifiers. 28/-.  
 RELIANCE TV pots. 1k., 2k., 10k. 5/7.  
 DITTO. 80 pots, 150 k., 2 meg., 6/10.  
 DUBILIER mica condensers. .001/5,000v., 5/-; .002/5,000v., 6/-.  
 MORGAN "T" midget 1 watt. 4/8.  
 B.I. 23 uP/500v. electrolytic. 7/6.  
 B.I. 1/3,000v. moulded tubulars. 6/-.  
 T.C.C. Cathode rays. .001/5,000v. 4/8.  
 .01/5,000v., 7/8; .1/7,000v. 15/-.  
 MAZDA 9in. picture tube £11/6/10.  
 MULLARD 12in. Ditto. £15-2-5.  
 EDDYSTONE 28 + 26 pF stator 7/6.  
 T.C.C. Microdiscs. 500pF. 1/6.  
 T.C.C. Midget mica .001 CM20. 1/6.  
 T.C.C. .01/500v. midget tub. 643. 11d.  
 HUNTS .1/150v. midget tubular. 1/6.

T.C.C. Picopacks 1/350v., 2/150v., 20/12v. 2/6.  
 T.C.C. Metallites .002 CP308. 1/9; .005 CP328. 1/10; .01 CP338. 1/10; .01 CP32N. 1/8. .05 CP373. 2/1.  
 Also full range of parts for "Viewmaster", "Wireless World" and "Electronic Engineering" designs  
**BOOKS:** "Viewmaster" (London) 5/-; "EE" Home built TV (London) 2/6; "EE" Home built TV Birmingham, 4/6. Bernard's Hith Defective T.V. construction manual. 3/6.

**Grith RADIOCRAFT Ltd.**  
 69-71 CHURCH GATE, LEICESTER  
 PHONE 58971  
 CECOS C3471 G2R1

*just what we keep on saying—*

is drained.—P. G. E.

**Women's Voices**  
**ELIZABETH CHRISTINE BROWN** suggests that the reception of women's voices is worse than that of men's because they are pitched higher. Surely this is a reflection on the inability of most commercial wireless receivers to reproduce the top frequencies, on which the clarity of voices depends. Given a wireless adequate performance, I can assure her that women's voices are received as well as men's. It does seem to be the habit of many manufacturers to spend a disproportionately small amount of the cost of a set on the loudspeaker. After all it does make the noise.—R. C. Headington, Oxford.

Letter to  
**RADIO TIMES**  
 Aug. 12th 1949

*its the*  
**Loudspeaker**  
*that*  
**COUNTS!**

**REPRODUCERS AND AMPLIFIERS LIMITED**  
**FREDERICK STREET WOLVERHAMPTON ENGLAND**  
 Telephone Wolverhampton 22241      Telegrams "Audio Wolverhampton"



**RADIO EXCHANGE CO.**



**TELEPHONES D MK. V.** Self-contained telephones, with bell, buzzer, and standard P.O. type handset; ideal for all inter-com. purposes. **ONLY 27/6 ea.**

**AMPLIFIERS 185,** a small unit with 5 mains operated valves, comprising two audio amplifiers. (1) E14C 33 driven by EF35. (2) EF36 driving push-pull EL52's. Complete with circuit, for 17/6. Amplifier unit 18 is similar to above, but contains an additional valve, less circuit, 17/6.

**NOISE LIMITER KITS.** A complete noise limiter sub-assembly with diode valve, and all small parts. Comprehensive instruction booklet refers to a particular U.S. set, but enables you to fit this unit to ANY superhet. **ONLY 3/6.**


**RECEIVER TYPE 21.** Ex-Army receiver, functioning as a superhet from 4.2-7.5 Mc/s. and as a double superhet from 14-31 Mc/s. They use 6 VP29's and 3 11L23D11's, and require 120/100 v. H.T. and 6 or 3 v. L.T. Complete with circuit, 35/-.

**WESTERN ELECTRIC.** Wide band recording machines. A four-stage amplifier, using two stages of negative feedback, is used as a small S.R.E. pre-amp., or as a recording/playback amplifier. The motor and enamel oscillator, which also supplies a superoctic bias during recording, are built into this unit. The detachable head, with sufficient wire for 40/45 mins. recording, uses machine cut gears, incorporates timing and automatic switching mechanisms, and clamps on to the main unit.


The machine is capable of really high quality work, and is robustly constructed. Output, sufficient for driving a speaker, may be fed into a large amplifier. Input is 115 watts at 115 v., 50/60 cps. **OUR PRICE £37/10/-.**

A few, with slightly damaged contact strips and spilled wire. **ONLY £20.**

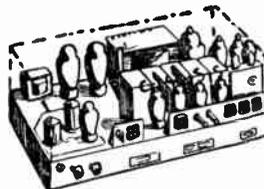**ELC RECEIVERS.** Ideal for television. 2 R.F. stages, 4 I.F. stages det. video amp. and cathode follower, plus additional stages suitable for time-base conversion, make this the ideal surplus television. A total of 17 valves! Why not make the "Radio Exchange Television set" at a cost of approx. £8. Receiver price, 30/-.



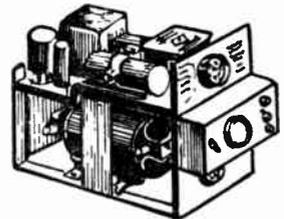**INDICATOR 188.** With a 3in. short persistence CRT, 4 8P81's and a host of pots, resistors, condensers, switches, etc., this is the ideal unit for converting into an oscilloscope. Brand new in sealed makers' cartons for £2.



**POWER UNIT TYPE 19.** This fine unit contains a motor generator, output 640 v. at 40 mA., and 275 v. at 110 mA., and a vibrator pack, with OZ4 rectifier. Unit is complete with all smoothing and input is 12 or 24 v. D.C. **TO CLEAR, 12/6.**

**IFP TRANS/RECEIVERS.** One of the R.A.F.'s best-known units, they can be converted for the 144 Mc/s band, or to provide a gold-mine of parts. Complete with 13 mains operated valves, and a 9 v. input rotary converter, which can be used as a mains motor. **ONLY 22/6.**

**J50 RECTIFIERS.** Ideal for use in voltage multiplying systems for T.V. or oscilloscopes. **OUR PRICE 2/6 ea.**

**MOVING COIL HEADPHONES,** complete with M/C milk; tested before despatch, and capable of providing **REAL** quality. **ONLY 6/6.**

**RADIO EXCHANGE CO., (W), 9 CAULDWELL STREET, BEDFORD. phone 5563** All goods sold as used unless otherwise stated.

**Wish all our friends, old and new, seasonal greetings**

**XMAS SPECIALS**

**FOR TELEVISION CONSTRUCTORS**

**7 DAYS APPROVAL OFFER. "THE VIEWMASTER."**

Complete assembly instructions for building a 9in. or 12in. tube television set. A 32-page booklet packed with information on construction and other necessary details is supplied together with 8 full size working drawings, and stage by stage wiring instructions.

This receiver incorporates a brilliant black and white picture, with all the latest developments, and can be built from standard components.

**PRICE 1/-.** Post free. The demand for this job has been terrific.

**A FULL SIZE TELEVISION FOR A MINIMUM OUTLAY OF CASH.**  
All components, valves, c.r. tube, etc., in stock.

**RADAR RECEIVER TYPE 3084A.**  
**BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL WOOD TRANSIT CASE.**  
Specifications: 14 brand new valves: 7 EF50; 2 VR136; 1 VR137; 1 HVR2; 1 R3; 1 V507; 1 RA50.  
Dozens of useful components, including an 80 volt A.C. motor used for aerials/winding, front panel tuning control, etc. With little modification this unit will be ideal for television reception. Also suitable for converting to a 2 metre receiver.  
Totally enclosed in metal case, size: 19in. x 8in. x 7in. Weight in case 40 lbs.  
**LASKY'S PRICE 59/6.** Carriage 5/- extra.

**CIRCUITS NOW AVAILABLE.**  
Circuit for the 3044A receiver. **PRICE 1/6,** plus 3d. postage.  
Converts on of the receiver type 3084A to television sound and vision reception.  
**PRICE 2/6** plus 3d. postage.

Full circuit diagram giving suggested sound and vision television receivers, time base and all associated circuits, power packs, etc., utilizing available ex Government equipment (3084A, VCR97, etc.). **PRICE 3/6,** plus 3d. post.

**PRICE FOR THE COMPLETE SET OF 3 CIRCUITS. 7/-.** Post free.

**CATHODE RAY TUBES TYPE VCR97. BRAND NEW EX. GOVERNMENT. FULLY GUARANTEED. SUPPLIED IN SPRUNG WOOD TRANSIT CASE.**  
Characteristics: Heater 4 volts 1 amp., H.T., 2.5 KV., maximum.  
**LASKY'S PRICE 35/-.** Carriage free.

**E.H.T. TRANSFORMER FOR THE VCR97 CATHODE RAY TUBE.**  
200-250 volts primary. Secondary 2.5 KV., 4 mA., 4 v. 1.1 a., 4 v. 1.5 a., C.T.  
**LASKY'S PRICE 35/-.** Post free.

**E.H.T. SMOOTHING CONDENSERS. 1 mid. 2.5 KV. working.**  
**LASKY'S PRICE 2/6** each. Post free.

**EX. A.M. RECEIVER TYPE 69.**  
Contains 10 valves: 4 VR58 and 6 EF50.  
Also motor generator with 27 volt input and 250 volts and 12.6 volts output. Dozen of components, resistances, coils, condensers, etc.  
**A GRAND BARGAIN AT LASKY'S PRICE OF 34/-.** Carriage 4/6 extra.

**BRAND NEW AND UNUSED I.F.F. RECEIVERS. SUPPLIED IN ORIGINAL CARTONS.**  
Each contains 8 new valves: 4 SP41; 1 EA50; 1 VR78; 2 CV6. Also hosts of components, coils, condensers, resistances, switches, etc. A motor generator which can easily be converted to a fractional horse power motor running off 230 volts A.C. or D.C.  
Type 3108 input 12 volts and output 480 volts. Type 3109 input 24 volts and output 490 volts.  
**LASKY'S PRICE 25/- EACH.** Carriage Paid anywhere in the U.K.

**EX. A.M. INDICATOR UNIT TYPE 184A.**  
Containing 17 valves, 2 c.r. tubes, components, etc.  
Valve line up: 5 EF50; 3 EB34; 3 SP61; 2 VR78; 4 EA50; also a 3in. cathode ray tube type VCR139 and one 6in. cathode ray tube type VCR517. Hundreds of other components, totally enclosed in black metal case, size 12in. x 9in. x 19in. Weight 40 lbs.  
**LASKY'S PRICE 59/6.** Carriage 7/6 extra.

**AMERICAN AIR CORPS RECEIVER TYPE BC624A.**  
11 valve superhet, frequency covers 100-156 Mc/s.  
Valve line up: 3 9003; 1 9002; 1 1208; 3 120G7; 1 12J5; 1 12AH7; 1 12H6.  
Dozens of useful components, coils, variable condensers, etc.  
Size: 15 1/2 in. x 7 1/2 in. x 6 in. Weight 28 lbs. Supplied less the buzzer  
This is the receiver in use of the SCR522.  
**LASKY'S PRICE 19/11.** Carriage 5/- extra.

**BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL CARTON.**  
**EX. A.M. UNIT TYPE 8621.**  
Containing 11 new valves: 2 5Z4G; 2 5U4G; 1 VU120; 1 6X50T; 2 EF50; 2 V870 (voltage stabilisers); 1 6V6G.  
Dozens of various components, including high voltage condensers, pot./meters, resistances, condensers (8 mid. 500 v.w.), chokes, etc.  
Totally enclosed in metal case, size: 12in. x 11 1/2 in. x 8in. Weight 40 lbs.  
**LASKY'S PRICE 49/6.** Carriage 5/- extra.

**POWER UNITS TYPE CP.11. NEW AND UNUSED.**  
200-250 volts 50 c.p.s. faned primary input. Contains 2 heavy duty mains transformers, 2 U50 rectifier valves, 3 cho. cs. condensers etc. Output 350 volt, 6 volts and 5 volts. **A GREAT BARGAIN AT LASKY'S PRICE 65/-.** Carriage and packing 7/6 extra.

Send a 2d. stamp with your name and address (in block letters please) for a copy of our current Lasky's Radio Bulletin.

# LASKY'S RADIO

370 Harrow Road, Paddington, London, W.9  
(opposite Paddington Hospital)  
Telephone: CUNningham 1979  
Hours Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. half day



## HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television include the following:

**Complete Radio Engineering Radio Service Engineers Radio Service and Sales Advanced Short-Wave Radio Elementary Electronics, Radar and Radio Television Technology**

And the following Radio Examinations:

**British Institution of Radio Engineers  
P.M.G. Certificates for Wireless Operators  
City and Guilds Telecommunications  
Wireless Operators and Wireless Mechanics, R.A.F.**

Write today for our FREE "Radio" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need of and the means of instruction

## International CORRESPONDENCE SCHOOLS

Dept. W.L.S., International Buildings, Kingsway, London, W.C.2

## MIDLAND INSTRUMENT CO.

For Govt. Surplus Stock, etc.

**TYPE 21 RECEIVERS**, 2-band, 4.2 to 7.5 and 19 to 31 mc/s, contains 11 valves, ARP12/VP23 (7), AR3/H12/D1D (4), one of each are spare, also Millory Type 650 6v. vibrator, 2 I.P. stages, 3-gang and 2-gang variable condensers in tandem to give separate R.F. sections for each waveband, slow motion drive and dial, volume, on/off and wave-change, etc. controls, chassis mounted with side protection frame, 9 1/2 x 8 1/2 x 6 1/2 in., operating data supplied. Brand spanking new. 37/6 post and packing 2/6 extra. **PACKARD BELL P&E-AMPLIFIERS**, Model K-1, contains 2 valves. 6SL7/GT and 25D7, input and output transformers, gain control, etc., operates from single battery supply 24v. at 4 amp., simple input, output and battery terminations, will raise electro magnetic, etc. microphones to L.S. level, in smart metal cases, 5 x 4 1/2 x 3 1/2 in., instructional booklet and accessories, brand new in sealed cartons, 15/-, post 1/-, ditto with 2 spare valves 25/-, post 1/-. **ROLLS PACKARD AIR COMPRESSORS**, piston type, develops 450 lbs. sq. in. at 1,200 r.p.m., bore 1 1/2 in., stroke 1 1/2 in. and 3/16 in., splined shaft fitting, superior make and finish, brand new boxed, 25/-, post 1/5. **3-22 CAMERAS**, fitted with lens 1 1/2 in. f/7.7. Dallan Tele-anamorphic lens unit, 3-speed louvre shutter, bright "dull" "fair", delayed action device and other incidentals, takes standard 120 roll film, brand new in wood transit cases, 55/-, carriage 5/-. **ROTARY CONVERTERS**, D.C. input 12v., A.C. output, 230v. 50 cycles, 80/100 watts, 50/-, carriage 5/-. **MAINS TRANSFORMERS**, input 230v. 50 cycles, output 50v. 11 amp., or with little alteration, 100v. at 5 1/2 amp., 25/-, carriage 5/-. **VENTA XIA EXHAUST FANS**, standard bakelite model, 24v. D.C., 30v. A.C. at 1 amp., in metal wall fixing casing, fitting 1/2 in. dia., front fitted louvers, back fitted adjustable louvers, 10in. deep overall, an exceptionally fine job, brand new boxed, 45/-, carriage 5/-. **CO-AX CABLE**, brand new 40ft. length, 1/2 in. diameter, 82 ohms impedance, suitable for television, fitted Pye socket, bargain offer, 7/6, post 1/-. **VR-97 C.R. tubes**, suitable for television, supplied brand new in special suspension crates, 35/-, carriage paid. Crates are charged 5/- extra, returnable. **MAINS MOTORS**, 200/250v. A.C./D.C., one end fitted enclosed fan blower, the other reduction gearbox, with 3 final 1/2 in. shaft drives of approx. 5, 25 and 125 r.p.m., fan blower can be removed for using initial drive of approx. 3,000 r.p.m., size overall 12in. long, 6in. wide, 4 1/2 in. high, special bargain offer, brand new, 35/-, post 1/4. **BURGESS MICRO SWITCHES**, make and break, 4 assorted, 6/-, post 9d. **WALBIE TALKIE AERIALS**, also copper collapsible, 9-sections, total 7 1/2 in. diameter, tapers to 3/32 in. Also makes a good fishing rod, 2/6, post 6d., 3 for 6/9, post 9d. **TELEPHONE SETS**, consists of 2 combined dual purpose phones and mikes, 25ft. twin connecting flex, provides perfect 2-way communication, self-energized, no battery required, complete ready for use, the perfect Christmas present, brand new boxed, 7/6, post 9d. **EX-U.S.A. GOVT. UNITS**, contains 12 valves, 6S17 (3), 6H5 (3), 7193 (3), also 2 relays, over 80 resistors and condensers, chokes, coils, volume control, etc., chassis mounted with louvre cover, size 12 1/2 x 8 x 6 in., as new, bargain, 15/-, post 1/4. **INDICATOR UNITS TYPE 198**, contains a VR-138 C.E. tube 3 1/2 in. diameter, 8 valves, VR165 (4), VR92 (3) and VR84, and a mass of other components, in metal cases, size 16 1/2 x 12 x 5 1/2 in., brand new in sealed cartons, 40/-, carriage 5/-. **FREQUENCY METERS TS-59/AP**, covers 341 to 1,000 mc/s with high precision cavity, 341 to 700, limits of 1 mfd. 700 to 1,000, limits of 2 mc/s., indicated on reed counter, fitted super 0-200 microammeter, crystal valve, auto serial, calibration sheets in hinged frame, smart crackle finish cases, 22 x 6 x 5 1/2 in., also super transit case, brand new, now in stock, 70/-, carriage 7/6. Also hundreds of other interesting items, send for current lists, 2d., with a.s.o., for those who have received our current lists, a supplement is now available, send a.s.o.

**MOORPOOL CIRCLE, BIRMINGHAM, 17**

Tel. HARborne 1308 or 2664

## The New **WESTON S75** Multi-Range Test Set



### 53 Ranges with Rotary Switch Selection

This new and uniquely comprehensive Test Set has 53 ranges for measuring A.C. and D.C. current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500 v. Selection is carried out by two 20-position switches. A fully protective safety device is fitted and is operative for forward or reverse overload. The 150-division 6in. scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89 covering first-grade instruments.

Full details of the ranges covered and of the complete specification will gladly be supplied on request.

**PRICE £65**

**SANGAMO WESTON LTD.**  
ENFIELD, MIDDX.

Tel.: Enfield 3434 (6 lines) and 1242 (4 lines)  
201 St. Vincent Street, Glasgow - - - Tel.: Central 6208  
22 Booth Street, Manchester - - - Tel.: Central 7904  
Millern House, Newcastle-upon-Tyne - - Tel.: Newcastle 26867  
33 Princess Street, Wolverhampton - - Tel.: Wolverhampton 21912

# INTRICATE PARTS



but not too  
intricate  
for

# Bullers

Made in Three Principal Materials

**FREQUELEX**

An insulating material of Low Di-electric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

**PERMALEX**

A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

**TEMPLEX**

A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.



**BULLERS LOW LOSS CERAMICS**

**BULLERS LTD.**, 6, Laurence Pountney Hill, London, E.C.4

Telegrams: "Bullers, Cannon, London"

K 5

Phone: Mansion House 9971 (3 lines)



**RS584 RECEIVER.** Comprising 16 EF50, EF36, ERC33, 2 EB34, 2 V473. In addition there is an I.F. strip, relays, motor-tuned dial, and countless other useful components. Absolutely brand new in sealed wooden crate. £5.5/- (plus 7/6 carriage and packing). Limited quantity only.

**A SIGNAL TRACER** at minimum cost. An easy-to-build unit that can be used for R.F., I.F. and Audio signal tracing, without any switching or tuning. Highly sensitive, easy-to-build, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain, 3-stage resistance-coupled audio frequency amplifier, with a 6-inch speaker in the Output of the Power Amplifier stage. We shall be pleased to supply a complete kit for the construction of the above, right down to the last nut and bolt, for the low price of £3 18 6. Concise instructions and circuits are supplied. If preferred, circuit and instructions only can be supplied for 1 6 post free. All items may be purchased separately. This is a highly efficient instrument, and a MUST for every radio man.

**P.M. SPEAKERS.** All are by leading manufacturers. Less Transformer—2 1/2 in., 15/-; 3 1/2 in., 9/-; 5 in., 10/-; 6 1/2 in., 12 6; 8 in., 15/-; 10 in., 23 6; 12 in., 37 6. With Transformer: 5 in., 12 6; 6 1/2 in., 15/-; 8 in., 17 6; 10 in., 25 6.

**BARGAIN PARCEL FOR MIDGET CONSTRUCTORS.** Comprising 1T4, 1S5, 1K5 and 1N4, 1.4 v. battery valves. Four ceramic valve-holders (or same). One pair midget "Wearite" I.F. Transformers, Type M400B. One 3 1/2 in. P.M. Speaker. One midist two-gang .000375 mid. with trimmers, vanes covered with perspex. All items absolutely brand new. The whole 57 6 only.

**PACKARD-BELL MICROPHONE PRE-AMPLIFIER TYPE K.** Complete with valves 6SL7GT and 2N07, relay, etc., etc., for 28 volt D.C. input. In metal box, size 5 in. x 4 in. x 2 1/2 in. Complete with leads, plugs, switch, two 2-way terminal blocks, and printed instruction and circuit manual. In original sealed carton, 14 6 only.

**WEB MEGGER,** by Evershed & Vignoles, Ltd. 20 megs at 250 v. Absolutely brand new in leather case. Limited quantity at only 25/15/- each, carriage free.

**VCR, 139A C/R TUBES.** Electrostatic 2 1/2 in., tested and guaranteed O.K. Only 12 6 each, plus 2 6 post and packing. Bases can be supplied at 2/- each. **D.C. AVO MINORS.** Special offer, limited quantity of these well-known instruments brand new and boxed, but slightly soiled. Not ex-Govt., 55/- only.

**RCA 931A PHOTO-ELECTRIC CELL AND MULTIPLIER.** For facsimile transmission. By the spot tele-line transmission and research involving low light-level 8-stage multiplier. Brand new and guaranteed. Only 30/-, Valve-holder for this cell can now be supplied at 4 6.

**TX VALVES,** Weeninghouse 813 at 50/-, 832 at 20/-, 866A at 15/-, Klystron 722A/B at 82 6. All brand new and boxed.

**TYPE BC 634A RECEIVERS.** Absolutely brand new by BENDIX, etc. Valve line-up: 12A17, 12X5, 3 12X67, 12Y9, 2 90Y3, 90Y2, making 10 valves in all. Frequency coverage 100-156 Mc/s. Can be supplied at the absurdly low price of 25/- (carriage and packing free).

**RECEIVER UNIT TYPE 159.** Size 8 in. x 6 1/2 in. x 4 1/2 in., containing VE91, VE92, CV66, VR65 and 24 v. selector switch. New condition, 15/-

**RECEIVER TYPE 25.** The receiver portion of the T/R 1196. Covers 4.3-6.7 Mc/s. and makes an ideal basis for an all-wave receiver, as per "Practical Wireless, August issue. Complete with valves types EF309, EF39(2), EK32 and EH323. Supplied complete with necessary conversion data for home use. Only 22 6. Chassis only, 8 6.

**INDICATOR UNIT TYPE 183.** Containing VCR 139A 3 1/2 in. tube, 3 VR65, 1 VR54, 1 VR92, 2 high-speed relays, volume controls and 101 res. and condensers. In new condition. Suitable for an oscilloscope. 35/-

**METER DISTRIBUTION BOARDS.** Comprising 0-300 v. M.I. Meter, 3 1/2 in. A.C./D.C. Input Plug and Socket, 3 Output Sockets, 3 porcelain fuses. Total size, 12 in. x 6 in. Brand new and individually boxed. 17 6.

**INTERNATIONAL RADIO TUBE ENCYCLOPEDIA.** Gives operating characteristics and base connections of over 15,000 valves. Includes all service types, transmitting Tubes, Thyratrons, C/R Tubes, Orthicons, Photo-Cells, etc., etc. Equivalents, Supplementary data, etc. In fifteen languages, fully cloth bound, 496 pages. Annual supplements will be issued. Price 42-/. Undoubtedly the finest of its type in the world.

Send stamp for current Component List. Probably the most comprehensive in the trade.

**5, HARROW ROAD, LONDON, W.2  
PADDINGTON 1008/9**

# "You're CERTAIN to get it at ARTHURS!"

★ **VALVES:** We have probably the largest stock of valves in the country. Send your enquiries. We will reply by return.

**AVO METERS IN STOCK**

Avo Model 7	£19 10 0
Avo Model 7, high resistance	£19 10 0
Avo Model 40	£17 10 0
Valve Tester	£16 10 0
Test bridge	£11 0 0
Avo Minor, AC/DC model	£8 10 0
Electronic Test Meter	£35 0 0
Signal Generator	£25 0 0

**DENCO COILS & COMPONENTS** in stock

**LATEST VALVE MANUALS**

- Mazda - 1/- ea.
- Mullard - 5/- ea.
- Brimar - 2/6 ea.
- Brimar Teletube Annual - 4/-
- Post 4d. extra

**ELECTRIC LAMPS, all types. TAYLORS METERS.** List on request.

DECCA PIC 'UPS	£6 14 6
DECCA HEAD lo. Garrard 24 11 0	
Adaptors	3 8

**LONDON'S OLDEST LEADING RADIO DEALERS**



EST. 1919

PROPS: ARTHUR GRAY, LTD. Terms C.O.D. or cash with order  
Our Only Address: Gray House, 150/152 Charing Cross Rd., London, W.C.2 TEMple Bar 3833 4 and 47 55  
**ELECTRICAL, TELEVISION & RADIO ENGINEERS.**

# TELE-RADIO (1943) LTD.


177, EDGWARE ROAD, LONDON, W.2  
AMB. 5393. PADD. 6116. PAD. 5606.

High Fidelity Williamson Amplifier	£26 10 0
Preamplifier Tone Control Unit, for above amplifier	£6 10 0
Rogers Development Junior Amplifier—frequency response flat within plus or minus .5 db from 20-20,000 cps. Output 8-10 watts	£19 10 0
Partridge Mains Transformer, for Williamson amplifier	£2 17 0
Partridge Chokes, for above amplifier, 25 H. 60 mA. and 13 H. 200 mA., 16.- and Partridge Williamson Output Transformer, as specified "W.W." of '47	£5 0 0
Punched Chassis, for "Williamson Amplifier"	£1 17 6
Matched Valves, in pairs, KT66, per pair	£1 16 6
Matched Valves, in pairs, 6L6, per pair	£1 16 6
Matched Valves, in pairs, PX4, per pair	£1 13 0
Matched Valves, in pairs, PX25, per pair	£2 14 4
Gram Record Changers, "Collaro"	£14 6 8
E.M.I. Record Changer	£10 10 8
Gram Record Changers, "Plassay"	£18 10 0
Paper Condenser, 4 mfd. 1,000 v. size, 5 1/2 x 4 x 1 1/2 in., 2/9 each or 3 for	7 0
Two Gang Tuning Condenser, 500 mmfd.	5 6
Electrolytic Condenser, 16 x 16 x 350 v., 4/9 each or five for	£1 1 0

When ordering please include sufficient for postage and packing.

THE VOICE OF AUTHORITY . . .

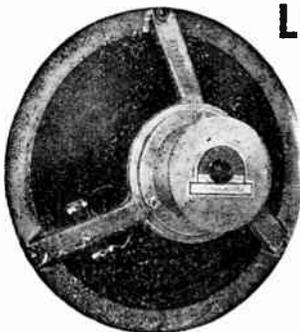The B.B.C. and the G.P.O. use the **GOLDEN (10 inch) LOUDSPEAKER**



**Price: 75/-**

Also available with wide response cone and cloth suspension in type GOLDEN/C5 at 85/-

During the past nine years hundreds of Wharfedale GOLDEN Units have been supplied to the B.B.C. and G.P.O. Selected by many discriminating users for its level response, the GOLDEN LOUDSPEAKER has a precision die-cast chassis, improved spider and Alcomax III Magnet increasing the flux density to over 13,000 lines. Speech coil 3 or 15 ohms impedance.

# Wharfedale Wireless Works

BRADFORD ROAD • IDLE • BRADFORD • YORKSHIRE

Telephone: Idle 461

Telegrams: W-oridel, Idle Bradford

## BOOKS THAT TELL YOU ALL YOU WANT TO KNOW ABOUT . . .

### The VOICE OF AMERICA

acclaims

#### "LOUDSPEAKERS."

Extract from announcement in "Radio & Television News," Sept., 1949.

Written by an English music lover turned so and expert, this little book is so good it has been selling like hot cakes for months. You'll find it the handiest, dandiest thing ever written on the subject of sound reproduction."

### SOUND REPRODUCTION

#### LOUDSPEAKERS

The Why and How of Good Reproduction by G. A. BRIGGS

Recognised as the standard work on the subject of Loudspeakers and the mechanics of faithful reproduction.

88 PAGES. 36 ILLUSTRATIONS. PRICE 5/- BY POST 5/3.

### SOUND REPRODUCTION

#### by G. A. BRIGGS

The latest book by the author of "Loudspeakers" has met with the tremendous success that greeted the previous publication. Contains new and valuable data on recording, accessories, pick ups, needles, frequency doubling, re-sonance, etc.

144 PAGES, 120 ILLUSTRATIONS, BOUND REXINE. PRICE 7/6. BY POST 8/-.

## A few examples of M.O.S. bargain offers..

### REMOTE CONTROL GROUND STATION.

A complete remote control morse device with heavy duty morse key, totally enclosed in moulded case, relay, 2 heavy duty on-off switches, resistors, transformer, etc., in teak cabinet. New. Only 7/6. (Carriage and packing 1/6.)

### THREE PHASE MOTORS.

Brand new 1/40th B.H.P. motors, designed for use on 50 volts, 50 cycles, 3 phase A.C. Speed 2,500-2,750 r.p.m. Spindle length 1 1/2 in., diameter 3/8 in. Price 25/- (carriage paid).

### ONLY 37/6. A.C. MOTORS.

A very robust 1/4 h.p. A.C. mains (220-250 v.), 2,000 R.P.M. motor fitted with a 4 in. grindstone at one end and a polishing mop at the other end. Complete with 3ft. three-way mains lead. Brand new. Grindstone and mop of finest quality. Supplied ready for use. (Add 5/- for carriage and packing.)

### FOOT CONTROL SWITCH.

Just what you have been waiting for . . . and offered at a fraction of the original cost. Made to Government specifications from heavy brass casting, accurately machined, will take the heaviest load, and can be used to control machinery, model engines, etc. Ideal for the amateur and professional photographer. ONLY 22/6 (carriage paid).



### VISION WITHOUT VEINATION... HEAD LAMP SETS.

Fits comfortably around the head in similar fashion to a miner's lamp, with long lead and battery box to clip on your belt or slip into your pocket. Leaves both hands free. Works off a standard 4.5 v. battery. Supplied complete with bulb, clips, headband, etc. New and unused, 3/11, post free. Or with battery ready for use, 7/11.

### FOLDING AERIALS.

A very useful aerial comprising seven sections of copper tube aerial, which extends to 14 feet. The aerial folds down to a compact parcel of approx. 2ft. length. Each section is permanently connected to the adjacent one by a flexible cable running through the centre of the tube. The aerial is assembled by push-fitting one section into another and the assembly is painted khaki green. We supply in addition a solid rubber insulated base into which the aerial fits. This base will fit anywhere as it is provided with a circular metal disc with 3 fixing holes. A connecting terminal is also provided. The WHOLE ASSEMBLY FOR ONLY 10/- post free.

### WIRELESS SET No. 19. SUPPLY

**UNITS No. 1.** Only 2 1/2 (carriage paid). The portable power unit for the renowned "19" set. Comprises a powerful rotary transformer with associated smoothing circuits, including electrolytic condenser. On-off control switch on front panel with fuses and signal lamp. Input 12 v. D.C. Outputs (a) 275 v. 110 mA. D.C.; (b) 500 v. 50 mA. D.C. Housed in a steel carrying case with handle. A useful supply for RX and TX.

### EDDYSTONE FLEXIBLE COUPLINGS.

Low-loss insulated type, 1/9 ea., or 18/- doz.

### POWER UNITS 32.

Input 12 v. D.C. Output 1,200 v. 200 mA. D.C. 240 watts. Ideal for conversion to fractional horse power motor for A.C. or D.C. mains. Unit incorporates starter and smoothing circuits. Brand new 21/- (carr. pd).

### TO CALLERS ONLY.

The famous TU9B and TU26B Transmitter Tuning Units, complete in outer case (17 1/2 in. x 7 1/2 in. x 8 in.) for 7/6; or less outer case 5/-.

### 3-VALVE AMPLIFIER-OSCILLATOR.

Comprises a Colpitts oscillator and 2-stage resistance capacity coupled amplifier with positive feedback. Battery operated and complete with 3 ARP12 (VP23) valves and pair of S.G. Brown Headphones. Brand new in steel case and haversack. Only 22/6 (post free). Full circuits provided.

### AERIAL TUNING UNITS.

These brand new units cover a frequency of 2.4-13 Mc/s. on 2 bands. Incorporating a 3-amp. R.F. Thermocouple meter; and a REV. COUNTER operates in conjunction with the rotating tuning coil. Overall size 5 in. x 5 in. x 9 in. Each unit is packed in its original wood transit case, 21/- (post free).

Terms: Cash with order  
**MAIL ORDER SUPPLY CO.**  
 33 Tottenham Court Road, London, W.1  
 Tele: MUSUM 6667-8-9

Economical in Time and Money!

YOURS FOR ONLY  
**6/6** MONTHLY  
£1 DEPOSIT  
SECURES  
10 monthly  
payments of 6/-



Get instant soldering heat!  
Invaluable for radio servicemen, engineers and home mechanics. Simply plug in, press the button, and in seven seconds the iron's hot! Absolutely safe, the bit cools instantly button is released and lies clear of bench when not in use. Complete with two spare bits and four yards of flex. Suitable for A.C. 200-250V, or 110-120V State model required. Limited stock. No interest charge. Send your deposit to-day for this ultra-rapid electric soldering gun. Leaflet on request.  
Cash Price £3 18s. 6d. complete.

**BURGOYNE**  
**SECOND Instant Heat**  
**SOLDERING GUN**

SEND YOUR  
DEPOSIT  
Today TO-

Trade Terms upon Request.

**The RING LAMP CO.**

81 City Road, London, E.C.1

Telephone CLerkenwell 7103

## PRATTS RADIO

1070 Harrow Road, London, N.W.10

(N. Scrubs Lane)

Tel. LADroke 1734

**AMPLIFIERS.** College general purpose Amplifiers. Model AC.10E 10 watt 4 valve unit. Neg. feedback. Separate microphone stage, separate inputs for mike and gram. Separate faders and tone control. Complete in case with chrome handles. £8/18/6 Model AC.18E 6-valve Push-Pull Amplifier with feedback over 3 stages. Separate mike stage with separate faders for mike and gram. Separate gram input. Tone control. Output 18½ watts. Complete in case with chrome handles. £13/17/6. Model UIOE 6 valve 10 watt P.P. amplifier with feedback over 3 stages for D.C./A.C. mains. Specification as AC.18E, £11/11/-. All the above have outputs to match 3.8 and 15 ohm speakers and are complete for immediate use. Guarantee with each unit. Input voltages average, on mike, less than 5 m/v, on gram less than .33 v. R.M.S. for full output. No pre-amplifier required. Model AC4C, A.C. or Model U4C, D.C./A.C. 3-valve gramophone amplifiers. Output 4 watts to 3 ohms, £4/19/6. Stamp for fuller details.

**TRANSFORMERS.** E.H.T. 2,500 v. 5 m.a. 4 v. 1½ amp., 4 v. 2 amp. C.T. for VCR. 97). Input 200-240 v. (in 10 v. steps), 27/6. 2 x 350 v. 120 m.a. 6 v. 6 a.; 5 v. 4 a., 4 v. 4 a., 3½/- (available trade). Fil. Transfr., Input 115/230 v., 6.3 v. C.T., 7/6.

**SPEAKERS.** Brand new by famous makers, 5in., 9/11; 8in., 11/9; 10in., 18/6 and 23/6; 12in. Truvox 3 ohm, 45/- Goodmans or Rola 12in. 15 ohms), £5/15/-. All P.M., less transfr.

**CONDENSERS.** Brand new fresh stock. Midget 16 x 8 mfd, 450 v., 3/9, 16 x 16 mfd, 450 v., 4/6; 8 x 8 mfd, 450 v., 3/6; 8 mfd, 350 v., 1/11; 32 mfd, 350 v., 1/11; 16 mfd, 350 v., 1/11; B.I. C'b'd' blocks 500/550 v. 3 mfd., 3/3; 8 x 8 mfd., 4/9; 16 x 8 mfd., 6/-; Ediswan Midget C'b'd's., 8 mfd, 450 v., 3/-; 16 mfd., 4/- Paper condensers, .0001 to .0005, .1, .5, .01 x 100 v. all 6d.

**VARIABLE CONDENSERS.** 2 gang .0005 mfd., 4/6; .0005 mfd. 3 gang, 6/9. Both with feet and 2½in. shaft. Solid dielectric variable. Wavemeter .0003 mfd., 3/4; .0005 mfd, 3/6. Ceramic presets, 50pF, 4d., 100pF and 0005, 1/3.

**MISCELLANEOUS.** U.S. Octal, Brit. 4.5 and 7 pin, 4d. each. Volume controls Egan, less sw., 2/9, with sw., 4/6. Jack-plugs and sockets, bakelite, 2/6. Mains droppers, .3 a. 750 or .2 a. 1,000 ohms, 4/6, with 2 sliders and ft. Chokes, 60 ma. 20 hy. 360 ohm, 6/6, 90 mA 10 hy, 13/6; 150 mA 10 hy, 14/3.

**WEARITE "P"** Coils, all types, 3/- each **DENCO** L. & M.W. Coils with reaction, A. & H.F., 6/6.

All goods are new and unused and offered on a money back guarantee basis. C.O.D. or C.W.O. Postage extra under £1. Shop hours 10-6.

You'll do better  
at

# LAWRENCES

3 good reasons why

- EXTRA SPECIAL VALUES**  
You buy at Lawrences at lowest possible prices. You get the best and most carefully selected Radio Surplus available in the country, plus substantial savings on every order.
- QUICKEST SERVICE**  
Backed by years of experience, encouraged by customers' commendation, our technical staff give express delivery, speed your order to you carefully packed against all hazards
- ABSOLUTE SATISFACTION**  
We guarantee you'll be satisfied. You play safe when you buy at Lawrences.

FREE!

**NEW COMPLETE RADIO SURPLUS BULLETIN**

Send at once for your copy of this great up-to-the-minute publication. No advertisement could keep you advised of the countless astonishing bargains available. Whether you be Amateur, Industrial Buyer, Service Engineer or Experimenter, EVERY "Wireless World" reader will find something of interest in the fully illustrated pages, packed with technical data. In addition, you get pages of hard-to-find technical information, surplus conversion data, station lists, etc., and it's all FREE.

FOR RADIO SURPLUS, A TO Z,  
YOU MUST GET A COPY NOW

**LAWRENCES RADIO, Dept OS,**  
61, BYROM ST., LIVERPOOL, ENGLAND

**PHILCO 3 VALVE TELEVISION PRE-AMPLIFIER.** A.C. Mains, 200/250 v. Slug tuned input, inter-stage and output. Size 7in. x 6in. Complete with own power supply and valves. £4, plus post and packing 2/6.

**PORTABLE CABINET,** rexine covered, leather carrying handle, size 12½in. long x 10in. high x 6½in. deep. Complete with back, aerial wound, scale and pointer, 25/- plus 1/6 postage.

**UNIVERSAL REPLACEMENT MAINS TRANSFORMER,** primary 200/250 v., secondary 230-0-280, 60 mA., 6 v. 3 amp. tapped 4 v. 5 v. 2 amp. tapped 4 v. 6 v. 0.3 amp. 10/6 plus 1/- postage.

**2½in. MOVING COIL METER,** 0-300 v. A.C. and D.C., fitted internal rectifier, 15/-.

**SUPERHET COIL KIT,** comprising long, medium and short wave coils, standard twin gang, pair 465 I.F.'s, 4 pole, 4-way switch, 6 trimmers and two trackers, complete with circuit, and 5 valve super-het chassis, I.F. and speaker cut-outs. 14/6 plus 1/- post.

**HEATER TRANSFORMER,** 230/250 input, 6.3 v. 2 amp. 6/- plus 1/- post.

**SELENIUM RECTIFIER H.T.,** half-wave 250 v. 125 mA. 4/3 plus 6d. post.

**PUSH-PULL 10 watt transformer,** 6 v. 6 matching. 3/- plus 9d. post.

**TWIN GANG,** .0005 fitted feet, trimmers and 1½in. drum : spindle tapped 6 BA. 4/6 plus 6d. post.

10in. P.M. less transformer. 14/6 plus 1/- post.

8in. P.M. less transformer. 11/9 plus 1/- post.

6in. P.M. less transformer. 8/9 plus 1/- post.

**MAINS DROPPER.** 0.2 amp. 1,000 ohms. 1/9 plus 3d. post.

**MAINS DROPPER.** 820 ohms. 0.2 amp. 1/6 plus 3d. post.

Write for lists:


## D. COHEN

Radio Engineer

67, RALEIGH AVENUE, HAYES  
MIDDLESEX
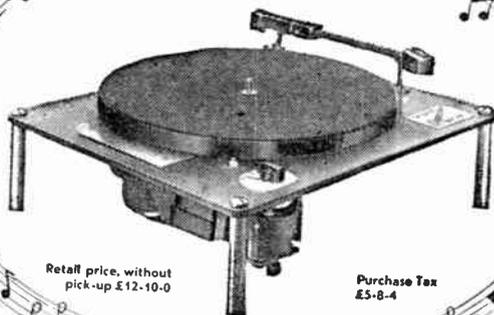
# New Two Speed-motor...

At the turn of a switch you have two speeds, 33 $\frac{1}{3}$ , or 78 r.p.m. The Turntable is a full 12" diameter; its main spindle precision ground and lapped, runs in phosphor bronze bearings. The synchronous motor is virtually vibrationless and is suitable for playing standard, transcription and microgroove recordings. Guaranteed mechanically perfect. New super light-weight pick-up available with the interchangeable heads for microgroove and standard recordings.



Retail price, without pick-up £12-10-0

Purchase Tax £5-8-4

Manufactured by

A. R. SUGDEN & CO. (ENGINEERS) LTD. WELL GREEN LANE BRIGHOUSE YORKS.




"SPIRE'S" WAY WITH YOUR

ASSEMBLY COSTS
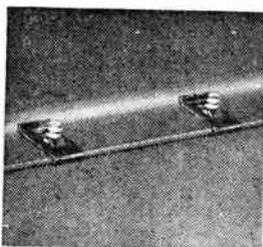
# Spire SPEED NUTS

The SNU type is self-retaining, pushed into position by thumb pressure. Expensive riveting, welding or clinching operations are eliminated. If the minute gap between assembled parts is not desirable for certain applications, the SNJ type ensures a close seal.

Spire Speed Nuts cut assembly time to a minimum; they're so easy and quick to fix, even in really difficult blind assemblies and awkward locations. They will not "clog" with paint or enamel. They eliminate a retapping operation. And once home, Spire Speed Nuts lock tight as long as they're wanted (regardless of any number of bolt removals) their unique double-spring action sees to that. If you're worrying right now over a fastening problem, why not send for more news of Spire—fastest thing in fastenings.



**THAT'S  
FIXED  
THAT**

Enquiries to: **Simmonds Aeroaccessories Ltd., Byron House, 7-8-9, St. James's Street, London, S.W.1** Head Office and Works: Treforest, Glamorgan

You are offering

\* PEAK

PERFORMANCE

with the



GRAMPHIAN  
D.P.I.

THE IDEAL MICROPHONE  
FOR P.A. WORK,  
BROADCASTING AND  
RECORDING

Here is a wide range high fidelity moving coil type Microphone which combines good sensitivity with a level response curve. Equally suitable for Auditorium or Outdoor Work, and its use can confidently be advised for Amateur as well as Professional use. Housed in modern streamlined die cast alloy case of great strength and finished in hammered metallic lacquer with chromium plated grille. Delivery from stock. List price £8.8.0

Dimensions 3" diam. 3½" back to front. Net weight 2 lb. Frequency response 60-9,000 c.p.s. Output impedance 15 ohms. Fitting 5/16" B.S.F. Connection 2-pin plug.

**GRAMPHIAN**  
P.A. EQUIPMENT

Gramphian Reproducers Ltd., Hampton Road, Hanworth, Middx.  
Phone: Feltham 2637.

**G. W. SMITH & CO., (RADIO) LTD.**

**Special Offer**

Ex R.A.F. Type 1225 Receivers. Complete with 5 E.F.50 valves, and 2 EF39 I. EB34. Suitable for conversion to Television. Limited number only at 15/6 each.

Ex-R.A.F. Type R.1124 Receivers. Complete with valves, very easily adapted for Television Sound, no modification needed, 12/6, carriage paid.

Ex-R.A.F. Type 203 Control Units. Containing 12-volt 1 amp. rectifier, 2 1000 mfd. 25 volt condensers, LT smoothing choke, High Speed relay Switches, Indicator lamps, in fact all you need is a Mains transformer and you have a complete LT supply unit. Brand new, 14/- each.

Mains Transformers. 700 volt 20 mA 4 v. 1.25 amp. Twice, Test 5,000 v. RMS, ideal for scope, primary input 230 volt 50 cycle. 17/6 each.

Filament transformers. 5 v. 3 amp., 6.3 v. 1.25 amp. Twice. 6.3 v. .5 amp. 230 volt input. 12/6 each.

Bendix 453 Receivers. complete with valves, 45/- each. Switches 1 p. 7-way, 9d. each. 1 pole 11-way, 1/3 each, both 1½ dia. Ceramic 1 pole 7-way, 2/6 each.

High Voltage Condensers. Trouble Free Oil Filled Mansbridge type .1 mfd. 3 kV, 2/9; .1 mfd. 4 kV, 3/-; .1 mfd. 5 kV, 3/3, .001 n.f.d. 5 kV mica, 1/3 each, .001 9 kV, 1/6; .001 mfd. 15 kV, 1/6 each.

OPEN ALL DAY SATURDAY

**3 LISLE STREET, LONDON, W.C.2**

Telephone: GERrard 8204



Products of  
Quality & Reliability

MAINS TRANSFORMERS  
A. F. TRANSFORMERS  
THERMAL DELAY SWITCHES  
SMOOTHING CHOKES  
POWER RESISTANCES

Made by

**OLIVER DELL CONTROL LTD**

Telephone: WOOLWICH 1422-1426  
CAMBRIDGE ROW • WOOLWICH • S.E.18

**THE Fidelity LUXURY 7-VALVE RADIOGRAM CHASSIS**

Features include variable selectivity, infinite impedance detector, electronic bass and treble controls, triode output stage; 3 wavebands 16-50, 150-550 and 1,000-2,000 metres. Audio amplifier response 30-15,000 cycles; bass, treble and volume controls operate on gramo, suitable for light weight p.u. Guaranteed 12 months Price £17.2.6

Data Sheets on request, also for Precision 5-valve chassis, £12-17-6;  
2½ Ft. eed 8-15;  
5watt amp. £14-10;  
8watt amp. £12-12

**ELECTRO-ACOUSTIC DEVELOPMENTS**  
18 BROAD RD., WILLINGDON, SX.

**WILCO ELECTRONICS**

204, LOWER ADDISCOMBE RD., CROYDON.

CR-A K'AL Feeder Cable 80 ohms. 10½d. per yard.  
METAL RECTIFIERS. 230 volt 40 mA. 1 wave, 3/- each.  
P.O. RACKS for standard 19in. panels, 5ft., 60/-; 6ft., 70/-, also a few transmitting cabinets 6ft., 6in. x 21in. x 21in. door each side, £28/10/-.  
SPEAKERS P.M. 4in. Rola in Cabinet 9 x 7½ x 4, 17/6 each.  
POWER UNIT. Including 1-SU2150A and 1-524J valve .1 mfd. 2,500 volt Condenser, Relay, etc. Bargain, 17/6 complete.  
SLOW MOTION DIALS. 200:1 Reduction or direct. 6in. diam. scaled 0-100. Front of panel mounting, 5/6. Multhead S.M., 7/6.  
CONDENSERS. Paper block type. 8 Mfd. 750 V.D.C., 10/6. 4 Mfd. 750 V.D.C., 5/-; 4 Mfd. 2,000 V.D.C., 10/6. 1.5 Mfd. 4,000 V.D.C., 10/6.  
VIBRATORS. Brand new Ex-Govt., W. & W. N8/B6, N86, No. 6. Oak V6606, 5/6 ea. TELEVISION UNIT. 2 R.F. 1 Det., 1 Video stage using EF90c and EA60. Iron cored coils. Make good sound channel. Complete with valves, 45/-. Brand new. Boxed.  
VOLTMETERS. 0-300 A.C. Moving Iron, 2½in., 5sh. 17/6; 3½in. Surface type, 23/6; 0-250 A.C. Moving Coil Rectifier, Type 3½in., 5sh. 30/-. Electrostatic 750 v. 2½in., 25/-; 2,000 v., 3½in., 35/-; 5,000 v., 3½in., 90/-.  
WEE MEGERS. In leather carrying case. Brand new, £28/10/- each.  
MICROAMMETER F.S.D. 25 microamps, scaled 0-100, 2½in., 57/6.  
SELECTOR UNIT, in metal case consisting of 2 Uniselectors, 4 pole, 25 way, 4 full wipers, internal connections to adjustable tag board. 55/-.

**RADIOMENDERS LIMITED**

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialise in

AMATEURS' WINDINGS, TRANSFORMERS  
ALL TYPES, CHOKES, PICK-UP COILS,  
INSTRUMENT COILS, Etc.

LOUD SPEAKER SERVICE

Highest workmanship

Good Delivery

**RADIOMENDERS, LTD.**

Television & Radio Apparatus, Transformer & Coilwinders.

123-5-7 Parchmore Road,

THORNTON HEATH, SURREY

LIV 2261. Trade enquiries invited. Established 16 years.


*Success through constant research - can we help you?*

# LOW LOSS CERAMICS


by

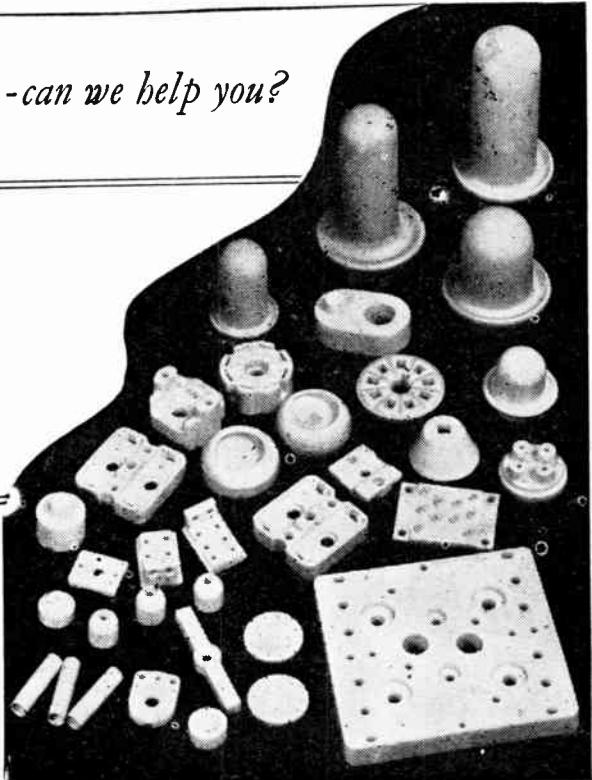**TAYLOR TUNNICLIFF**

TAYLOR TUNNICLIFF (REFRACTORIES) LTD.,  
 Albion Works, Longton, Stoke-on-Trent, Staffs.  
 London Office: 125 High Holborn, W.C.1.  
 'Phones: Stoke-on-Trent 5272 & Holborn 1951/2.



I.A.S./I.T.S

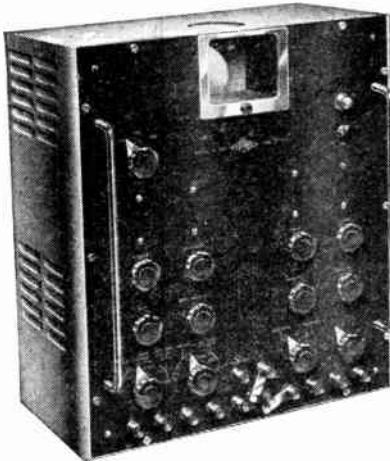

## AN ADVANCED DESIGN IN OSCILLOSCOPES



● The new Airmec Oscilloscope has been designed to incorporate features found from practical experience to be advantageous. Some characteristics are indicated briefly below. Further details are given in pamphlet No. 19 available on request. The instrument has been designed to have minimum forward dimensions and is therefore suitable for bench or rack mounting on the standard P.O. centres. Racks are available if required.


"X" trace or independent use, e.g. beam modulation.

**Frequency response:** D.C. to 5 Mc/s flat within  $\pm 2$  db.

**Time Base:** 0.5 second to 1 micro-second with provision for single stroke.

**Brilliance Control:** Manual, and automatic compensation for photography of high speed traces. 4 kV. for extra brilliance.

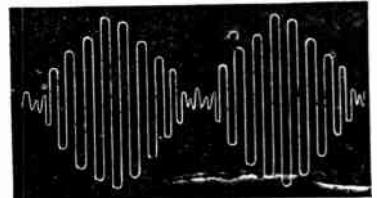**Photography:** Motor operated camera provided for mounting above oscillo-



scope. Screen visible up to instant of exposure.

**Controls:** Switches and rotary controls are provided to minimise need for manipulation of external connections.

**Tube:** 4" electrostatic type with optically flat screen and provision for direct connection to deflecting plates.

**Sensitivity:** Maximum 15 mV/cm.

**Shifts:** Instantaneous and symmetrical.

**Amplifiers:** Balanced "Y" amplifier and additional auxiliary amplifier for

## AIRMEC LABORATORIES LTD.

HIGH WYCOMBE • BUCKINGHAMSHIRE • ENGLAND • Tel. High Wycombe 2060 • Cables: Com.labs.  
 MANUFACTURERS OF ALL TYPES OF INDUSTRIAL ELECTRONIC EQUIPMENT & TEST GEAR

THE **NEW "75"**  
**SIGNAL GENERATOR Model 1**



**Frequency Range**  
110 to 50 Megacycles.  
With calibrated extension covering London, & Midland Television frequencies, at over 60 Magacycles.

**Modulation**  
400 C.p.s. sinusoidal.

**Attenuator**  
5-step ladder, with fine control.

**Output**  
Switched via single test-lead, R.F. and A.F. 1 volt Max.

**External Radiation**  
Less than 1 micro-v.

For A.C. mains operation. Complete with Standard Dummy Aerial.

**SPHERE INSTRUMENTS** LIST **12 1/2** GNS. SUBJECT.  
EXCELLENT PERFORMANCE  
ATTRACTIVE APPEARANCE  
LOW PRICE  
HIGH EFFICIENCY

**SPHERE RADIO LIMITED**  
HEATH LANE, WEST BROMWICH, ENGLAND

# LAMINATIONS

FOR

**All Radio and Electrical Uses.**

**In Silicon, Dynamo, Intermediate and Transformer Qualities.**

**Permalloy, Mumetal, Radiometal.**

**Screens for all Electrical Uses.**

**Transformer Shrouds for 35 and 74 Lams.**

**General Precision Engineers.**

**Heat Treatment.**

**Sheradising to the Trade.**

**Electrical Sound & Television Patents Ltd.**

12 Pembroke Street, London, N.1. — TERminus 4355  
2,4 Manor Way, Boreham Wood, Herts. — ELSTREE 2138

**I. F. TRANSFORMERS**  
are supplied  
**ALIGNED TO 465 KC/S**  
(and sealed)  
at **12/- pr.**  
with coloured lead-out wires  
**SIX "MM." IRON-CORED COILS**  
(High Permeability)  
at **2/3d. each**  
cover all wavebands from 10 to 2,000 metres, Aerial, H.F. and Osc. types available (465 Kc/s I.F.)

Stocked by all good dealers, or in case of difficulty write direct to:—

**LONDON TELEVISION Co., Ltd.**  
**694 LEA BRIDGE RD., LONDON, E.10**  
PHONE: LEY. 4380

## GARLAND RADIO

24 v. A.C./D.C. MOTORS: 4-pole, fitted worm reduction drive; suitable models, etc., 8/6.

MAGNETIC THROAT MIKES. 1/9 per pair.

WESTECTORS: WX6, WX12, W6, 1/- each.

WESTON MODEL 603 OIL INDICATORS. A sensitive moving coil "null-indicator" for bridges, etc., 2/6 each.

SWINGING CHOKES: 4.9H at 150 mA to 20H at no D.C., 6/- each.

3-GANG .0005 mfd. TUNING CONDENSERS: 5in. x 3 1/2in. x 1 1/2in., 3/- each.

POWER FACTOR CONDENSERS for 40 w PL Tubes; 3.25 mfd. 260 v. A.C., 5/- each.

ROTARY CONVERTERS: 23/24 v. D.C. input, 230 v. 50 cps. 75 w. output. Brush-holders/transist damaged, but electrically sound. 15/- (plus 5/- carriage).

MOTOR ALTERNATORS: 220 v. D.C. input, 80 v. 2,000 cps. 500 w. output. 40/- (plus 10/- carriage).

POTENTIOMETERS: Unused ex-Govt. 100, 200, 5K, 8K, 10K, 15K, 20K, 50KΩ w/w; 500, 25K, 50K, 100K, 150K, 200K, 250K, 300K, 1M, 2M, 3M, 3MΩ carbon, 1/9 each

**GARLAND RADIO (Dept. W.W.)**  
4 Deptford Bridge, S.E.8 Phone: TIDeway 3965

## ENGINEERS!

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES". Full details of the easiest way to pass A.M.I. Mech. E., A.M.I.E.E., A.M.I.C.E., CITY & GUILDS, MATRIC., etc. on "NO PASS—NO FEE" terms and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aeronautics, Radio, etc., Building, etc. If you're earning less than £10a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE!

**R.I.E.T.**  
377, Shaftesbury Hse., 17-19, Stratford Place, London, W.1.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

### MUMETAL and RADIOMETAL TRANSFORMERS and CHOKES

As Specialists with many years of experience we can design and supply practically any type of transformer or choke with a nickel-iron core for use on a band within the frequency range

**1 c/s to 150 kc/s**

Available for rapid delivery—Microphone Transformers, Input Transformers, Line Transformers, Pickup Transformers, Output Transformers, Rectifier Transformers, Vibrator Transformers, High Fidelity Transformers, Recorder Transformers, Midgap Transformers, High Q Chokes, High Inductance Chokes, etc., with or without Mumetal Shields.

MAINS COMPONENTS ARE ALSO STOCKED.

**SOWTER TRANSFORMERS**  
E. A. SOWTER, 1-B HEAD STREET, COLCHESTER.  
Phone COLCHESTER 545J.

We are preparing a waiting list for the first 1950 batch of Voigt Senior P.M. Units.

Work has started, but there is delay while details of the inter-changeable pole tips are being revised. Otherwise generally as per "W.W." review last March.

Anticipated Price £40 ex-works.

**Suitable horns from £19 10 0**

VOIGT PATENT LTD.,  
c/o BCM/Voigt,  
London, W.C.1

# TEST! - RADIO - TELEVISION EVERYTHING ELECTRICAL



Price 25/- Obtainable from your local dealer.


Not only radio but everything electrical can be tested with this world famous PIFCO Radiometer. Bell and telephone circuits, radio, television, vacuum cleaners, irons, car lighting, H.T. and L.T. milliamps, etc. Increasing supplies now available for the home market.



- **CIRCUIT TEST**  
Tests for open or faulty circuits in all radio and electrical apparatus and domestic appliances. Equally for testing car lighting and starting circuits.
- **L.T. TEST**  
0-6 volts AC or DC
- **MILLIAMPERE TEST**  
0/30 m.a. scale for testing total discharge from battery or testing single cell
- **VALVE TEST**  
Made by inserting valve in socket on front of meter.
- **H.T. TEST** — 0-240 volts. May be used direct on any mains, AC or DC
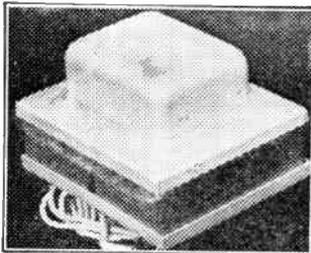
## PIFCO ALL-IN-ONE RADIOMETER

PIFCO LTD., PIFCO HOUSE, WATLING STREET, MANCHESTER, 4  
and at PIFCO HOUSE, GT. EASTERN STREET, LONDON, E.C.2




### MAINS TRANSFORMERS 16/6 POST PAID

Couophone Mains Transformers are made to the highest electrical standards and are fully guaranteed. We supply them to the Ministry of Supply Atomic Research Stations, so they will no doubt meet your requirements. Special quotations for quantities and types to order.

Standard Replacement Types. Drop-through chassis type with top shroud. Impregnated and interleaved. Screened Primaries tapped to 200/230/250 volts.

(a) 250-0-250 v. 60 mA. 6.3 v. 3 A., 5 v. 2 A.	16 6
(b) 250-0-250 v. 60 mA. 4 v. 4 A., 4 v. 2 A.	16 6
(c) 250-0-250 v. 80 mA. 0/4/6.3 v. 4 A. C.T., 0/4/5 v. 2 A.	19 0
(d) 300-0-300 v. 80 mA. 0/4/6.3 v. 4 A. C.T., 0/4/5 v. 2 A.	19 0
(e) 350-0-350 v. 80 mA. 0/4/6.3 v. 4 A. C.T., 0/4/5 v. 2 A.	19 0
(f) 250-0-250 v. 100 mA. 0/4/6.3 v. 4 A. C.T., 0/4/5 v. 2 A.	22 0
(g) 300-0-300 v. 100 mA. 0/4/6.3 v. 4 A. C.T., 0/4/5 v. 2 A.	22 0
(h) 350-0-350 v. 100 mA. 0/4/6.3 v. 4 A. C.T., 0/4/5 v. 2 A.	22 0
(i) 350-0-350 v. 150 mA. 0/4/6.3 v. 6 A. C.T., 0/4/5 v. 3 A.	39 0
(j) 425-0-425 v. 180 mA. 6.3 v. 4 A. C.T., 6.3 v. 4 A. C.T., 5 v. 3 A.	44 6
(k) 425-0-425 v. 180 mA. 4 v. 8 A. C.T., 4 v. 4 A. C.T., 4 v. 4 A.	44 6
(l) 425-0-425 v. 180 mA. 6.3 v. 4 A. C.T., 4 v. 2 A. C.T., 4 v. 2 A., 5 v. 3 v. 2 A.	47 0

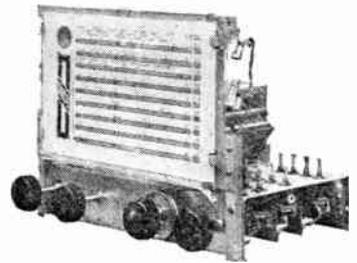Types (a) (b) (c) (d) (e) (f) (g) (h) (i) (j) (k) illustrated on left. Type (l) upright shrouded type



### FEEDER UNITS

**MODEL B DE LUXE** (illustrated above). High gain R.F. stage operative on all nine wavebands. 45/145 M., 190/550 M., 900/2000 M. Plus six ranges of Bandspread. 13.5-14.8, 16-17.4, 19-20.5, 24.2-26, 30-32, 41-43.5 metres. Large colour printed glass dial, 10in. x 6in. aperture. Horizontal drive. Wave-range indicator and needle eye. Switched pick-up sockets. Volume and Tone Controls. Completely aligned ready for connection to audio amplifier. Price less valves £18 7/6. Price for set of five valves, £31 1/5.

**MODEL A.** A first class feeder unit with R.F. stage operative on all wavebands, 16.50, 190/550, 900/2000 metres. Switched pick-up sockets. Volume control. Glass dial 5in. x 8in. in colour. Completely aligned ready for connection to audio amplifier. Price less valves, £10/8/6. Valves required, 6K7G, 6K8G, 6K70, 6Q7G. Price for set of four valves, £2/11/3. **A.F. AMPLIFIER POWER UNIT.** Specially designed for use with above units. Employs 6V6G output (4 watts) and 5Z1G rectifier. Price less valves £4/10/-. Two valves if required, £1/13/10.

**UNDRILLED 16 S.W.G. ALUMINIUM CHASSIS.** 9in. x 3in. x 2 1/2in., 10in. x 6in. x 3in., 10in. x 8in. x 3in., 8/6 ea., 12in. x 9in. x 3in., 10/6; 14in. x 9in. x 3in., 11/8; 16in. x 8in. x 3in., 11/8; 20in. x 8in. x 3in., 12/6.

**SMOOTHING CHOKES.** 40 mA., 5/-; 60 mA., 6/6; 90 mA., 7/-; 100 mA., 12/6; 200 mA., 21/-.

**EDDYSTONE COMPONENTS.** Full range stocked. Eddystone illustrated catalogue 6d.

**B.V.A. VALVES.** Large stocks. Valves sent C.O.D.

**S.T.C. BALL MICROPHONES.** High fidelity. Makers' list price approx. £22. Special Order, £4/19/6.

**MINE DETECTOR AMPLIFIERS.** Containing three 1T4 valves and ceramic valveholders. £12/6.

**GOODMANS T2/1205 12in. P.M. Speakers.** £6/15.

**GOODMANS AXIOM 12in. P.M. Speakers.** £8/6.

**ROLA 4in. P.M. Speakers.** 18/6.

**INSTRUMENT WIRES.** Comprehensive range in enamel, cotton and silk covered copper wires.

**SEND NOW.** 5d. in stamps or LATEST CATALOGUE.

Terms: C.W.O. or C.O.D.

### WILLIAMSON OUTPUT TRANSFORMER

Super job exactly to author's specification. Upright mounting £3/12/6.

## COULPHONE RADIO 53 BURSCOUGH ST. ORMSKIRK, LANCs.

'The Return of Post Mail Order Service'

Tel.: Ormskirk 987

# THE NEW B.P.L. SUPER RANGER

20,000 OHMS PER VOLT.



- D.C. VOLTS : 100 mV to 5kV
- D.C. CURRENT : 1  $\mu$ A to 1 Amp.
- A.C. VOLTS : 0.5V to 5kV.
- A.C. CURRENT : 10 mA to 10 Amps
- RESISTANCE : 1 ohm to 2 meg-ohms
- OUTPUT : 0 to 62 db
- METER : 5-inch Long arc, fitted with knife-edge pointer and mirror scale.
- LIST PRICE : £ 21 - 10 - 0.

**BRITISH PHYSICAL LABORATORIES**  
HOUSEBOAT WORKS, RADLETT, HERTS.


Tel: Radlett 5674-5-6

## Technical Excellence

combines with beauty and soundness of DESIGN in the

## OXLEY

DIFFERENTIAL AIR DIELECTRIC TRIMMER

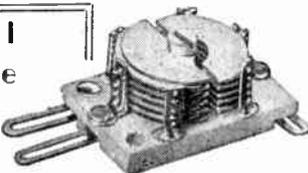

- ★ Width: 16.5 mm Length: 25 mm
- Height: 1.5 to 20 pF—8 mm
- 1.5 to 20 pF—20 mm
- 2 to 26 pF—11.5 mm
- 2 to 26 pF—12.5 mm
- Low: Straight line capacitor
- Power Factor: Less than .001
- In-ulation: Over 2,000 megohm-Volts/cm D.I.

**OXLEY DEVELOPMENTS CO., LTD.,**  
ULVERSTON, N. LANCS. TEL. ULVERSTON 3306

## TELEVISION COMPONENTS

NOW IN STOCK FOR

*The View Master*  
*Televisor!*

Complete Assembly Instructions and 8 full size Drawings 5/-

Send for latest list—6d. post paid

**COVENTRY RADIO**  
DUNSTABLE ROAD, LUTON, BEDS.

## THE BEST TUNER UNITS for THE BEST AMPLIFIERS

Model SH6: Superhet, 3 waveband. 4 miniature valves. RF stages. Flywheel tuning.

£12. 10. 0 plus £3.2.6 tax.

Model PBS: 4 stat on preset TRF. Pushbutton control. All miniature valves.

£8. 15. 0 plus £1.18.6 tax.

Prices include multiway connectors.

**FELICITY GRAMOPHONE CO.**  
87a Upper Richmond Rd., London, S.W.15  
PUFney 1665

## A HAPPY EVENT

We are pleased to announce a brand new addition to our range of high fidelity amplifiers:

## "THE BABY"

At present available in kit form only. It features high-grade components, including Partridge transformers and chokes throughout, together with performance figures altogether better than would be suggested by its low price.

Push-pull EL33s provide 6-8 watts output, heavy NFB being applied to reduce distortion. Phase shift is minimized by the use of direct coupling. The input is suitable for the majority of lightweight pick-ups.

Complete kit of parts including wiring diagram, circuit, drilled chassis and all valves. £8.10.0.

A leaflet describing the "Baby" (Model RD5) in detail will gladly be forwarded on request.

A demonstration model of the amplifier may be seen and heard at our Hampstead premises.

THE NEW WILLIAMSON P.F.E. AMPLIFIER, as described in Wireless World, NOV. 1949, is now being demonstrated.

**ROGERS DEVELOPMENTS Co.,**  
106, Heath Street, Hampstead, London, N.W.3.  
HAMPSTEAD 6901.

## KERSHAW'S KORNER KALLING

**SPECIAL!!!**  
M.O.S. LINES

TELESONIC RECEIVERS, brand new, complete with four 1.5 v. Hivac Midget valves ideal for making your own personal portable 32/6 each. Post paid.

H.T. and L.T. BATTERIES, combined for above tele-sonic receivers. 8/6 each. Post paid.

INERT 1.5 v. CELL BATTERIES, long life, fill with plain water and have continuous use. Ideal for every purpose. 3 for 2/6. Post paid.

MAKE YOUR OWN CRYSTAL SET, with polished terminal box complete with volume control, resistance, etc. 1/6 each. Post paid.

**S. KERSHAW**

93 95 PERSHORE STREET, BIRMINGHAM, 5.



Multiple Contact Relay L.F.

## RELAYS

for A.C. and D.C.

VA Coil consumption from 2 to 500 volts and tested to 2,000 volts, Aerial Change-over Relays, Mercury Relays, Mesurin; Relays and Time Delay Relays.

Ask for leaflets REJWW

## LONDEX LTD.

Manufacturers of Relays

07 Anerley Rd., London, S.E.20. S.T.D. nham 6258

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 6 words. Box Numbers, 2 words plus 1/-. Trade discount details available on application. Press Day: Annual, 1950 issue, 1st Post Mon 27, December 14th. No responsibility accepted for errors.

**WARNING**

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civil use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

**NEW RECEIVERS AND AMPLIFIERS**  
NEXT to nothing clearance sale.

18-valve receivers, containing practically all the valves and components you will need for a TV set, EF40s, EA50s, Pen46, VU39s, SP61, P61, J50 rect. trans. former is H.F. but will give 2½v at about 4a from 250v a.c. 50cs, 5 I.F. trans., 13 to 16 mc/s, and hundreds of res. and cons. choices, a good name price £22/6, plus 5/- each R1124 6-valve receivers, with 6 brand new universal valves, enough gear, with a few oddments from the junk box to make a couple of midset sets, 12/6 each, plus 2/6 curr., fl. trans. to suit these for 200-250v A.C. to 12v L.T., 6v-, 2-watt 0.0003 condensers, 1.9 each, 3-gang, 0.0001, 1.9 toggle switches, shoe-approval, SPDT, or one on and one off, 1/- each.  
RECEIVER R1225 with 5XEF50, 2XVR53 and VR54. 13 mc/s, I.F.s. for valves and spares, 17/6 each, curr. 2/6.  
R.F. units 2d 6/6, 2d mod. 27 8/6, 25 12/6, 27 22/6, all with valves and good cond. ton. Double transformers, LR 2/6, bal. arm for crystal sets, etc., 5/6, moving coil, 5/6, with mike 8/6, Mallory Vibrapacks, 12v, 150v, 75ma, unsmoothed, with vib., 6/6 each, including with 97, etc., 7 types, from 55/- to 95/-; RCA TE314/- crystal wavefilters, new and unused, but need slight repair, £3 10 each, s.a.e. for lists.  
H ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex. [4543]

MASON'S, Wivenhoe, nr. Colchester. [4543]

ILLUSTRATED catalogue, price 9d. full details of Denco and Eddystone range, tuning kits, television kits and surplus radio bargains. [4578]  
UNIVERSAL ELECTRONIC PRODUCTS, 36 Marye-Jones High St., London, W.1. Tel. Wehrk 4058.

SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 4-100 watts for domestic or industrial purposes. Our U.E.5 (6 watts) and U.E.7 (12 watts) series amplifiers are designed especially for the consumer who requires the finest possible reproduction from recorded music. Our amplifiers have a linear response over 30-20,000 cycles with a damping factor of 12, and incorporate pre-amplifier stage, together with independent control of bass and treble. Our policy is to produce an instrument which represents the highest standards in workmanship, performance and cost. A new addition to our range is the type U.E.3 (4watts) at £11 10. We also supply a range of tuning units, both t.r.f. and superhet. for use in conjunction with either our or other makes of amplifiers. We should be pleased to quote you for the design and construction of a unit or replacement chassis to your exact requirements. Full details of our products will be forwarded on request, and we would welcome the opportunity to demonstrate our equipment at any time to suit your convenience. [4552]

TELETYPE dual diversity receivers, complete with power units and loudspeakers, few only available.

MCLEROY ADAMS MFG. GROUP Ltd. (Hallcrafters), 46, Greyhound Rd., London, W.9.

R converted models from £9 10, send for lists.—Broadcast & Acoustic Equipment Co. Ltd., Tom and Norwich. [2906]

EDDYSTONE S640 with speaker and moving coil headphones, cost £39 in perfect condition, very little used, accept £17, no offers.—E. G. H. 101, 51, Tuffrey Avenue, Gloucester.

AMPLIFIERS, new, 60 watt heavy duty PA models, suit for continuous use, rating and rack mounting: £30, lists.—Broadcast & Acoustic Equipment Co. Ltd., Tom and Norwich.



NORTHREN ELECTRONIC LTD. STRIES Ltd., Windsor Works, Manchester St., Oldham, Lancs., have now in production a portable electronic gramophone designed for a.c. reproduction of gramophone records in schools, hotels, clubs, small halls and similar installations. Immediate delivery, send for illustrated results giving further details, prices, etc. [4191]

3.6 For this model, send us supply you with full constructional details for building our latest 10-watt quality amplifier with variable negative feedback; these constructional sheets are limited so that the most interested persons may build their own apparatus. Complete Home Constructor's Handbook with circuit of h.a.d.m.a. (two set), 1 extra.—Supacolls, Mail Order Office, 98, Greenway Ave., London, E.17. [0053]



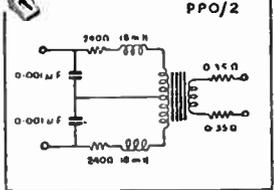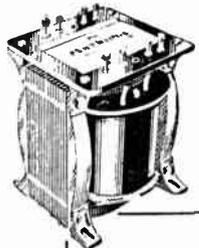**Partridge Hews**

A new standard in **PUSH-PULL** OUTPUT PERFORMANCE



THE new "PPO" output transformers permit the reproduction of a full A.F. range with minimum distortion. Rating is 12w. for 0.5% harmonic distortion at 50 cycles. Six standard models are available, for accurate matching anode to anode loads of 4,000 ohms to 12,000 ohms. The secondary in each case is brought out in two sections for series or parallel connection to match a 15 ohm or 3.7 ohm load. These standard models are available from stock, other specifications can be found to special order.

Full details are given in Technical Data Sheet No. 1, a copy of which will gladly be sent on request.

**PARTRIDGE TRANSFORMERS LTD**

ROEBUCK ROAD, KINGSTON-BY-SEA; LILLWORTH SURREY  
Telephone: ELMbridge 6737-a

**NEW RECEIVERS AND AMPLIFIERS**

THE world's finest communications receiver, Hammarlund Super Pro SPX300, power pack, matched speaker, in maker's custom new and perfect, offers considered.—The Radio Centre, 33, Tottenham Court Rd., W.1. 14497

12 watt high quality amplifiers complete, embody latest development precision output; £12 15/- sent on 7 days approval, send for lists.—Broadcast & Acoustic Equipment Co., Ltd., Tom and Norwich. [2907]

DC mains? This new Swatt all miniature valve amplifier has been designed to give you high fidelity reproduction from DC mains supply, matched for moving coil pickup, output 2.5-15 ohms, bass and treble controls, complete £21 10/- with mic. stage. £21.

FELICITY GRAMOPHONE Co., 87a, Upper Richmond Rd., S.W.15, Putney 1665. [0041]

C.T.R. ELECTRICAL AND ELECTRONIC DEVELOPMENT Ltd., Hubert St., Birmingham, 6 Aston Cross, 2430, the Midlands specially manufacturers of high fidelity equipment for the W.W. Williamson and other quality amplifiers, also tone control stages loud-speaker crossover units, distortionless contrast expanders and radio feeders, see our illustrated advert in alternate issues of this publication; send for full details and prices. [4503]

ELRAD ELECTRONICS 70, Church Rd., Upper Notwood, London, S.E.19, designers and manufacturers of Terad quality amplifiers for commercial and domestic use, these unique amplifiers with exceptional quality, gained instant popularity when first introduced at recent exhibition, built to suit the discriminating ear, bass and treble independent controls providing widest possible variation to suit all recordings and varying acoustic properties of one room with another, £18, complete, full details on request.—Write, call or phone Livingstone 1477. [4019]

MIDCO amplifiers for the enthusiast, 199 AA 5, Swatt fidelity model on enamelled chassis with tone and vol. controls, £5 10 complete, AA 10 10-watt push pull model with two-stage drive, twin inputs, tone control, complete, £10, PA 12 high fidelity model, 12-watt, record reproducer with bass and treble tone controls, twin inputs, £14 complete, PA 12M very high gain mic version, one high one low impedance inputs with full mix built complete, £14 10; PA 12 amplifiers are built in steel cases in cellulose enamels with chrome fittings, catalogue available, trade inquiries invited, Midland Radio Co. Products, 19, Newcomen Rd., Wellington. [4582]

CONNOISSEURS receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-13.5kc/sec. wide-range on medium sensitive 10-valve receiver, comparable with 12-valve and communication set, or by change of switch, maximum fidelity reception of local stations on non-superhet receiver with high quality 2-PX4 push-out amplifier incorporating all refinements, bass and treble tone controls, 10 to cut whistle filter and grain input etc. Basis rebuilt R155, write for details or call for demonstration, FEEDER units as above for use with external high-quality amplifiers. R155 specialists, receivers repaired and re-aligned also included as add-on to your requirements. R155 circuit and values 2/- post free. R.T.M.C. Ltd, 5 Gladstone Rd., Wincoburn S.W.19, Tel. Lib 3303.

THE R.T.M.C. version of the Williamson amplifier is now by general opinion recognised as the finest reproduced in this country. To speak of the R.T.M.C. version you immediately know that only the finest components are used and that the ultimate product is the finest you can buy irrespective of price. We will go so far as to say that products charged at three or four times the price will not excel the R.T.M.C. quality in reproduction or parts employed in the building of this superb amplifier. Original 7-valve version, £25 (ex cover) or new 9-valve version with built-in pre-amplifier £30 (ex cover), new type tuner 3-way-band, with large dial, £10 10/- gram motors and record changers supplied, all products specially hand built and mass produced, buy the best and be satisfied.—Details from R.T.M.C. (Ealing) Ltd., Laurel House, 141 Little Ealing Lane, W.5, Ealing 6982. [4574]

OFFICERS AMPLIFIERS SECOND HAND CR100 communication receiver, 11-valve, 6mc bandwidth, 9-13.5kc/sec. £566. [4553]

RC319, built-in 230 a.c. maker's speaker; £11. Royal Oak Home, Ringwood Hants.

NATIONAL H.R.O. Senior, 50 kc/s to 30 mc/s, 9 cnvs with power pack, good condition; 12-watt Williamson amp. in Imhoff case, £45 18

15 valve windings, Osmar valves, with high gain stage output meter, thermo-switch, plugs and sockets as new, unused, suit youth club, etc.; £23 17. Revolver Rd., S.E.16, Ber. 3629.

A R89D R.C.A. communications receiver, £60; 0-2.4kc/sec. ver. mod. fed and converted, £16, het frequency, meter type, CR74028, crystal controlled mains adapted, £8.—Apply Redman Bushlands, Hamble, Southampton.

A 123 Murphy 8-band receiver as new, with 12 tubes, 5 watt tuning on all S.W. bands; ideal set for combined B.C. and S.W. listening; T 91 Bush TV console, sensitivity 65 microvolts, peak white sound and vision interference limiters, recently checked by makers; two TV pre-amplifiers (A.F.); one R.155 receiver (bandwidth 2mc/s); other otherwise (as new), reasonable offers for part or whole of above, to Box 496.



**RADIOLYMPIA AND AFTER**

Advertising copy in a monthly journal can never be "news" as it has to be written long before publication. But as our copy seeks to be informative and accurate rather than "selling," this is our first chance to report on what happened to us during the radio show period and immediately after.

A very large number of musical enthusiasts called to see us and hear our equipment, especially the 215 speaker. We gave them absolutely unfaked demonstrations using gramophone records. The equipment was all openly visible, and nobody was twiddling knobs behind the scenes. We never have faked demonstrations nor ever will because it seems to us to be of the highest importance to let the potential customer hear exactly what he can hear in his own home. To give only one reason—it saves future arguments.

We were told that it seems uncanny that one single ordinary-looking speaker unit should be able to give such an impression of three-dimensional reproduction. We were told that the bass response of our speaker is quite phenomenal, and many were mystified by the performance of a nine-inch speaker at the lower limit of audibility. Over and over again surprise was expressed that an unpretentious 18-inch cubical box, the Boffle, should apparently impart no sort of coloration whatever to the acknowledged fine response of the 215 speaker.

But what pleased us more than anything else was the constantly reiterated statement that, judged purely on listening to the reproduction, no effective challenge to Hartley-Turner has yet been heard, and the price we ask makes the speaker and Boffle the best buy without any shadow of doubt. Here, as in the U.S.A., people are finding out that price alone does not determine the quality of the final result.

If you have not yet read "New Notes in Radio" send 2/6 today for your copy of the little book which has been called the most honestly written treatise on high-fidelity that has so far appeared, and if you would like a regular service of technical data sheets, send an extra half-crown. Descriptive literature free. HARTLEY-TURNER 215 SPEAKER £9. Output transformer £3. The BOFFLE, 18" cube. Kit of parts £6/15/0. Assembled £8/10/0.

**H. A. HARTLEY CO. LTD**  
152, HAMMERSMITH ROAD  
LONDON, W.6. Riverside 7387

**RECEIVERS, AMPLIFIERS—SECOND-HAND**

FERRANTI T.136 T.V. console, London model, 9in flat tube, £50 with pre-amp. filter. Dudley, 228, Long Shot, Nunenton. 14565  
TELEVISION receiver, oak cabinet, 12in tube, newly constructed for high reliability; may be seen working Wembley; £65; ditto, less cabinet and tube, £40; with 9in used tube, £44.—Box 492.  
TELEVISION Console, 12-inch G.E.C. BT3121. £15, new spare CRT 12-inch electrostatic G.E.C.4603. £12; power unit, type 3, for R1132A, £3/5.—Banham, West Mersea, Colchester, Essex. 14558

A88D and L.P. receivers for sale; R1124 receivers with six valves, 2/6; miniature G.E.C. split-field motors, 2/9 each; motor generators, 24 volts, 5/6 each, etc., etc.—J. Rae, 39 Penn Rd., W. Weyhampton. 14592

RECEIVERS type 76, 3 valves, ARTH2. VR53. VR92, IF output, 500 kc/s, 22 6; modulator unit type 76 (IF and output unit for the above), 2 stages of IF, detector, a.v.c. and output, also 4 valve push-pull amplifier, 9 valves, 2KT33C, 2EF36, 3EF39, 1EB33, 1EF50, 49 6 two 5/- carriage; the two units for 70 -; both brand new. Condensers: Sprague, .01, 1,000 3/4 doz; 25, 50, 5 6 doz; 25, 1,000, 6/6 doz; 4mid 425 Micropack, 10 6 doz; OS 2 52v, OS 3 52v, 1/- each; transformers: 200-250v DRI-RCA, 2,000v at 800ma, 90/-; 500-0-500 at 120ma, 3 and 4v 10v, 25 6; 350-0-350 at 200ma, 5 and 6.3v, 30/-; 500ma chokes, 20h, 15 9; many other items; s.a.e. list.—Cross Skerries, Cross Lane, Grange West Kirby, Ches. 14573

**NEW LOUDSPEAKERS**  
STILL the best for the barker, the Tridem 12D corner cabinet, supplied with or without speaker unit.

FELICITY GRAMOPHONE CO., 87a, Upper Richmond Rd., S.W.15. 10040

2in cabinet extension speaker, in handsome brown or cream plastic cabinet, fitted with volume control and lead; 29/6, post free. 9in cabinet model, with multi-ratio trans., vol. control, etc., 47 6, post free.

RADIO, UNLIMITED, Elm Rd., London, E.17.  
L. WOKER'S Flexicore Conversions will immensely improve reproduction of your present speaker, write or free descriptive leaflet.—Loozer's "Quality" Radio, 106 Davidson Rd., East Croydon. 14458

**LOUDSPEAKERS, SECOND-HAND**  
HARTLEY TURNER 215, perfect, £6/10.—15, Glover Rd., Pinner. (Pin. 931.) 14551

SOUND Sales DX1 feeder unit, as new; £12/10.—Ferrous Castings, Ltd., Warrington. 14548

GOODMANS infinite baffle, Partridge transformer, £10.—Marshall, 5, Isis Court, Chiswick, W.4. 14510

UNUSED manufacturers' surplus, P.M. speakers, 3 1/2in, 5in, 8in, 10in, 12in, 8 6, 10 6, 12 6, 18 6, 35/-.—Radio, Unlimited, Elm Rd., London, E.17. Key, 4913. 14555

HARTLEY-TURNER 215 speaker, £6; 21in cube baffle (new), £6; new boxed p.c.kups, Connaisseur, £2; Lexington senior, sapphire, £3/10.—170, Baxington Rd., Croydon. 14493

**DYNAMOS, MOTORS, ETC.**  
ROTARY converter for sale d.c. 220v input, a.c. 230v single phase 50 cycles output, 2C0w; ex-naval, as new, £15 or near offer.—Apply Preston, Home Farm, Laverstoke, Whitechurch, Hants. 14489

BATTERY chargers, 4 models 2-6-12v, 1-2-4 at 2p D.C. mains voltage; also large types special transformers, chokes, test gear, interior car heaters etc.—The Banner Electric Co. Ltd., Hoddesdon Herts. 12212

ALL types of rotating electrical machinery up to 20kw available, including rotary converters, motors, rotary transformers, petrol and diesel-engined generators, alternators and d.c. generators; we are also in a position to quote for power transformers; as actual manufacturers, we will be glad to quote for any quantity for home or export.

REVOLVING armature alternators, with separate exciter generators, 4-pole, ball bearing, 1,500rpm output 230v 50 cycles, 3kva excitation at 24/30v; new, price £28 nett ex works.

J.A.P., type 2a single-cylinder air-cooled petrol engines, 1.2bhp at 2,600rpm; price £14 ex-works.

ROTARY transformers, input 11.5v d.c., output 600v at 250ma, price £3; ditto, input 20v d.c. and dual outputs of 6.5v d.c. and 300v d.c., price 25/-.

CHAS. F. WARD, Lordseroft Works, Haverhill, Suffolk. Tel. Haverhill 253. 10039

MOTORS, 230v a.c. approx. 1/6th hp, converted rotary generators, new method, constant speed, for intermittent use, 18/6, 12 and 24w bulbs, S.B.C. hal reflector car head lamp size, dozen 9/6; transparent glass lacque, red, green, amber, 2 dram, 7d; transformers, 250v to 24v 2amps, cased, leads, 18/6; transformers, 15v at 80amps, £4.—Maiden Transformer Suppliers 200-202 Cambridge Rd., Norbiton, Surrey.

PETROL and T.V.O. charging and lighting plants, 12 and 24volt, no A.C. plants; engines, Douglas 349cc twin air-cooled, new, £20 plus carr.; J.A.P. 1-2hp air-cooled, No 2a, not ex-M.O.S., new, £14 delivered, 14-32v 290watt generators with or without control box, new, 6 and 12v; 85amp hour batteries; all engines and dynamos tested on load before dispatch; enquirers please state exact voltage and size of plant, or engine required; large 3-phase chargers still available; please see advertisement on page 79 for S.T.C. rectifiers and terms of business.—Pearce, 66, Gt. Percy St., London, W.C.1. 10014

**AMC TELEVISION**

Manufactured to "Electronic Engineering" Televisor Specification.

MIDLAND T.V. Sound and Vision Panels fitted with formers and dust cores now available.

**LINE OUTPUT TRANSFORMERS**

NEW Improved SET OF GANTRIES COMPLETE

**FOCUS COILS**

**LINE AND FRAME SCANNING COIL ASSEMBLIES**

All Steel CADMIUM PLATED POWER AND TIME BASE CHASSIS valve-holders, 3 point and 1 single socket and all necessary cut-outs.


SOUND PANEL CHASSIS ASSEMBLY, fitted with screens, valve-holders formers and dust cores.

VISION PANEL CHASSIS ASSEMBLY, fitted with screens, valve-holders, formers and dust cores.

9" C.R. TUBE SUPPORT for mounting on top of Gantry Assembly.

9" CREAM MASKS.

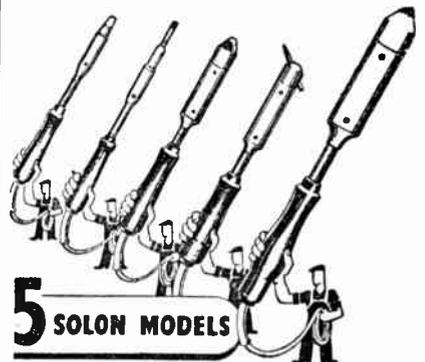5, SHAKESPEARE RD., FINCHLEY, N.3  
Phone FINchey 2188



**5 SOLON MODELS**

SOLON electric soldering irons have proved their capacity for continuous service under the most exacting conditions. 5 models; 240 watt oval tapered bit; 125 watt oval tapered and round pencil bits and 65 watt oval tapered and round pencil bits. Each model complete with 6 feet of Henley 3-core flexible. Now available from stock. Write for folder Y.ro.



W.T. HENLEY'S TELEGRAPH WORKS CO. LTD.  
61-63 Hatton Garden, London, E.C.1

**DYNAMOS, MOTORS, ETC.**

**BATTERY** chargers, 2-6-12volts, 1-amp. enclosed steel case with ammeter, a.c. mains operated; 42/6.—Thames Valley Products (W.) 28, Camden Ave., Feltham. [4264]

**NEW** rotary converters with special smoothing equipment for television, radiograms, etc., 300 watts output £23, 500 watts £30; other converters various voltages, from £2.10; also new electric motors, a.c. and d.c., B.T.H., Metrowick, etc., at low prices; trade supplies list available.

**JOHNSON ENGINEERING**, 319, Kennington Rd., Lond. N. S.E.11. Re. lance 1412-3. [4156]

**97.6**, charging switchboards, 12v-32v, 500 and 1,260 watts, volts, amps, cut-outs, fuses, resistances, etc., 4 take-offs, superb unit, in case, or send £5 carriage paid; 75/- dynamo, 24 volts, 1,000 watts, 9in x 7in, 3/4in spindle, or send 60/- carriage paid; 75/-, 230v/150, 1/2hp electric motors, incorporating 1,260 cycle converter, or send 80/- carriage paid; 58/-, mains transformer switchboards, 230v a.c. to 12v, 5 separate take-offs, complete distribution panel, all switches, fuses, amps, etc., brand new or send 60/- carriage paid; 55/-, electric motors, 12v and 24 v, 1/4hp, 4in x 4in, with 1/2in spindle for drive, beautiful job, or send 60/- carriage paid; 45/-, dynamo units, containing 12v, 24v, 130v and 300v d.c. dynamo or suitable as 6v, 12v or 24v motor approx. 1/2hp, 1 1/2 x 5in, with spindle to take small grinds, mop, etc., also contain adjustable 24v cut-out automatic voltage control, smoothing condenser, resistances, and many other extremely useful fittings, beautifully made or send 50/- carriage paid; 38/-, radio wavemeters, adjustment dial, 350-370 Mc/s, beautiful instrument in case, £12.10, or send 40/- carriage paid; host other valuable equipment; lists free.—Benmotors, Summerley St., Earlsfield, S.W.18, Wim. 3833. (100 yds S. Ry. Electric Line; 10 minutes Waterloo).

**TEST EQUIPMENT**

**AVO** electronic test meter with stand and multiplier, perfect; £27/10.—Box 593.

**O.1** Doukias coil winding machine, as new; s.a.e.—89, Manor Rd., Icthen, Southampton. [4539]

**TAYLOR** circuit analyzer 20A, new condition, price 10gns.—Gridley 52 Adelaide Grove, W.12.

**WIDE** range universal test meters, metric scale, 1,000 OPV with cap. range and a.c. d.c. 38 range; brand new ex manufacturer, £10 net.

**UNCLE TOM'S RADIO CABIN**, 5, Seven Stars Court, Manchester, 4. [3210]

**MARCONI** TP 144G standard S generator, 85kc to 25mc, as new; many other instruments in stock, s.a.e. details and lists.—Edwards 254, Cardo, Green Lane, E. Ley, E. 966.

**OSCILLOSCOPE** and wave analyzer complete £20 T.B. c/s 10 to 350 000 c/s X and Y pair amplifiers, easy to handle, has outstanding performance, fully guaranteed, immediate delivery with set of leads and booklet. Oscilloscope Technique—further details from the manufacturers.—Erskine Laboratories, Ltd., 50, St. John's Scarborough. [13456]

**SIGNAL** Generators range 100kc/s-100mc/s directly calibrated scale 4 1/2in diameter hair line cursor incorporates designed attenuator unmodulated modulated 400cps and separate AF etc., new instruments built to a standard not to price, operation AC 100.25 to 100.00% included crystal £15 17/6.—See below.

**BEAT** frequency oscillators range 30-15,000cps direct, y calibrated 5 1/2in diameter scale amplified variable and meter measured output matched 600 ohms incorporated constant accuracy check low harmonic content new precision instruments, £12.19/6.—See below.

**HP** oscillator units, covering range 100kc/s-100mc/s ready wired and tested for immediate use, less 6/5 valve, 596 direct, y calibrated scale, 9x5.5in matched to unit, 9/6, a 50 attenuator construction signal generator circuits, 2/- for illustrative data send stamp.—See below.

**MODIFICATION**, we can undertake rebuilding modification old type signal generators to cover range 100kc/s-100mc/s direct, y guaranteed 1/2% fitted new panels, etc., accuracy guaranteed 1/2% send instrument or write quotation.

**ELECTRONIC EQUIPMENT Co.**, Connaught House, West Malling, Kent. [15444]

**METERS**.—150v 2in, m/c, 10/-; 2,000v, 2 1/2in, m/c, electro-static 14/6; 3,500v, 3 1/2in, m/c, 20/-; 6,000v, 3 1/2in, m/c, 5/6; 15,600v, 2in, m/c, double reading, 8/-; 100ma 2in, m/c, 7/6; 40/120ma, 2in, m/c, double reading, 8/-; 3.5amp, 2in T.C. 5/-; 4amp 2 1/2in T.C. in case with switch, 7/6; 20amp, 2 1/2in, m/l, 9/6. Meter movements, 2in size with magnet and case (500-microamp), 2/6; Units containing two movements, 5/-; All meters post extra. Ex-R.A.F. 2-valve (2volt) microphone amplifiers, as used in plane intercom., in self-contained metal case, can be used to make up a deaf-aid outfit, intercommunication system, or with crystal set, complete with valves, 20/-, post 1/6, wooden box to hold amplifier, 1/6; crystal sets, with permanent detector, 9/6, in oak case, 18/6; headphones, 5 6, 7/6, 10/- and 12/6 pair; permanent detectors, 2/6, soldering irons, streamline, 50w, 9/-, standard 60w, 9/6; heavy duty, 150w, 12/6, all post extra; letters only; new illustrated list sent on request with 1d stamp and s.a.e.

**HIGHSTONE UTILITIES**, 58, New Weststead, London, E.11. [15440]

**ELECTRADIX**

for Best British Bargains

**MOTORS**, A.C. 50 cycle single phase 1/2 h.p. 230 volts, 1,425 r.p.m., new, £5/10/-, 1/2 h.p. 230 volts, capacitor start, 1,425 r.p.m., new, £9/10/-, Reconditioned A.C. Motors, 730 volts 50 cycles single phase G.E.C. 1/2 h.p., 1,425 r.p.m., £4/10/-, Crompton Parkinson, £4/10/-, A.C. 50 cycles 3-phase motors, 1/2 h.p., 1,425 r.p.m., 230 volts, new, £7/10/-.

**FANS**, Keith Blackman 400/440 volt 3-phase 50-cy. A.C., with 10in. blade, £4. 24 volt D.C. Wall or Table Fans, G.E.C., with 6in. blade and guard, £2/5/-, 220 volt D.C. Sterilizer Fans, for ceiling fitting, 10in. blade in copper Oxy. bowl and fixing chains, £3. 220 volt A.C. Table Fans, 10in. blade and guard, 45/-.

**DYNAMOS**, D.C. 12 volt 10 amp, totally enclosed car type, 1,400 r.p.m., 40/-, 12 volt 5 amp, 2,500 r.p.m., 25/-, 30 volt 5 amp, 1,500 r.p.m., 35/-, 24 volt 20 amp, 1,200 r.p.m., £12/10/-, Carriage on any dynamo, 5/- extra.

**FREQUENCY METERS**, 230 volt, 6in. Ironclad Switchboard Meters, 40/60 cycles, £4/10/-.

**A.C. METERS**, 5in, dia. Switchboard mounting, 0-300 volts 50 cy., 35/-, 0-50 cy, to match, 35/-, G.E.C. Meters, A.C., 50 cy., 0-40 amps. Ironclad Switchboard mounting, 35/-, Voltmeter to match, 0-60 volts, 35/-.

**PORTABLE A.C. METERS**, 6 1/2in. x 6 1/2in. x 4in., luminated dial mirror scale, 0-50 amps. and 0-75 volts, 40/- each.

**RADIO SUPPRESSORS**, Choke and condenser type, in iron box, 2-way, 5/- each; 3-way, 7/6 each.

**IRONCLAD SWITCHGEAR**, We have a large stock of Ironclad Fuses and Switch Fuses by leading Makers, 15-30 and 60 amps. Write for special leaflet "W.W."

**ROTARY SWITCHES**, 10 amp, D.P. on-off, on porcelain base with bakelite cover and knob, 3/6, 10 amp, S.P. Fuses, 2/- each.

**VARIABLE RESISTANCES**, Wire wound, 10 ohms 3 amp., 12/6, 1.5 ohms 15 amp., 7/6, 5 ohms 6 amp, 17/6. Small radio type, 10 ohms 1 amp., 2/6.

**DIMMER RESISTANCES**, 100 ohms 1/2 amp., 2/-; 50 ohms 1/2 amp., 2/-, postage 6d.

**GAUGES**, Bourdon air gauges, plus 8 lbs. per sq. inch to minus 7 lb. per sq. inch luminous dial, for testing blowers, vacuums, etc., 5/-.

**G.P.O. MAGNETO BELL** in polished box, 5/-, G.P.O. Candlestick Mike, with cord and switchhook, 7/6, postage 1/6 extra.

**SPARK COILS**, 6-12 volt D.C. input to give 1/2in. spark, with trembler and contacts, 5/-; the coil as above, fitted spark gap, 6/-, postage and packing, 1/6.

**MAGNETS**, Swift Levick S.L.S.36 instrument type, circular horseshoe 1 1/2in. dia. 1/2in. thick, 1/2in. polar gap drilled poles, weight 2 ozs., lift 3 lbs., 2/6 each, or 12/6 for six. The Alni disc magnet, the wonder midget magnet, 1/2in. dia., 1/2in. thick, 3/16in. hole in pot with keeper, 3/6, D.C. Electro Magnets, weight 10 ozs., lift on 2 volts 1 1/2 lbs., 4 volts 3 lbs., 6 volts 4 lbs., 5/-, Permanent flat bar magnets, 2 1/2in. x 1in. x 1/2in., drilled two holes each end, 2/- pair. Large stock of Horseshoe Magnets. Send for special leaflet, "W.W."

**LIGHTING PLANTS**, Villiers 550 watt sets, 2 h.p. engine direct coupled to 18 volt 30.5 amp. dynamo with switchboard in steel cabinet, £22/10/-.

**Pelaphone** 500 watt water cooled 1 h.p. engine, coupled to 50/70 volt 10 amp. dynamo, £35.

**Chore Horse** 300 watt single cylinder 4 stroke engine direct coupled to 12 volt dynamo with switchboard, £17.

**PARCELS**, 10 lb. useful oddments for the junk box. All clean, dismantled from Government and other surplus apparatus, 7/6 post free. (For home buyers only.)

Please include postage for mail orders.

**ELECTRADIX RADIOS**

214 Queenstown Road, London, S.W.3

Telephone: MACoulay 2159

**TEST EQUIPMENT**

**TAYLOR** 85a 95 ranges, 20,000amp. P. volt. with leads and booklet, as new, £14.—Jordan, 14 Carr St., Lincoln. [4571]

**OSCILLOGRAPH** Mullard E805, £45; signal generator Advance B3 mode, C £17; both in new condition; London area.—Box 497.

**STROMBERG-CARLSON** trigger oscilloscopes, U.S.A. make, brand new with 5in CRT and 13 valves—X6S7, 2X6H6, 2X6I7, 2XVR 150 30, 6AC7, 5Y4 and 2X2. Controls for signal intensity; TB frequency; velocity; TB shift; intensity; focus; sensitivity and pulse sync. Mains input 115/230v 50c/s; case 2 1/2in x 1 1/2in x 10 1/2in. Complete with circuit diagram and instructions for 15 minute modification to self running time base. Price £12/10. carriage paid.

**FRITH RADIOCRAFT**, Ltd., 69-71 Church Gate, Leicester. [10025]

**TRANSMITTING EQUIPMENT**

**WALTON'S** WIRELESS STORES, 203, Staveley Rd., Wolverhampton.

**STILL** another amazing bargain offer in partly stripped transmitter units; if you were unsuccessful in obtaining a unit before, now is your chance; just released by The Ministry of Supply, approx. 1,500 Type 1154 transmitter chassis, to conform with regulations these have been partly dismantled by the Ministry and are sold by us for the parts therein and not as transmitters; our special price, including carriage, 12.6; also a small number of the popular 1196 transmitter at 5/6; another useful item is the mounting rack for the complete 1196 installation, which includes Jones sockets for the power unit, T.X. R. X, a 24v impulse motor, a light duty relay P.O. type, and a heavy duty relay terminals, etc., our price, complete, 10.6; send s.a.e. to-day for our clearance list, a colossal stock must be cleared and in this instance the prices are of secondary importance.

**STOP PRESS!** Special offer in very sensitive headphones, ex-Army double headphones, complete with lead and jack plug, low resistance, balanced armature type, ideal for use with all types of sets or make super microphones, no batteries required, simply plug into the pick-up terminals of any domestic receiver or talker. These phones are very cheap at 30/- per pair; our price, 5/6 per pair or 2 pairs in their original box for only 10/- carriage paid.

**ALL** Mail Orders to 203, Staveley Rd., Wolverhampton. Callers only, 48, Stafford St., Wolverhampton.

**HALLICRAFTER** transmitters Type H14c (BC610), complete to makers' latest specification, covering all frequencies from 1mc to 30mc, complete with speech amplifier, connecting cables, etc.; limited quantities only now available.

**PANORAMIC** adaptor, Type MCA44, British-made, suitable fitment to any good-class communication receiver, in addition to all Hallicrafter models, immediate delivery.

**BRITISH MADE** under Hallicrafter licence, SX42 receiver, now available for export only.

**MCLEROY-ADAMS MFG. GROUP, LTD.**, 46, Greyhound Rd., London, W.6. Tel. Fulham 1802 Cables Hallicraft London [4114]

**GRAMOPHONE AND SOUND EQUIPMENT** FRITH RADIOCRAFT, Ltd., offer:—

**LATEST** radiogram units from stock include Collaro rim-drive, magnetic PU £3/2; Garrard ditto model S, £5/10/6; Plessey 10010 button start, magnetic PU, £6/18/3; Collaro auto-change lightweight PU, £10/15; Marconi AC100 auto-change lightweight PU, £10.8/8; all in ex-P.Tax post free.

**FRITH RADIOCRAFT, Ltd.**, 69-71, Church Gate, Leicester. Phone 58927.

**PLESSEY** autograph record player, perfect, hardly used; £14, best offer.—Box 597.

**R.C.A.** ribbon mic, and S.T.C. ball mic., £5 each.—Dudley, 228, Long St., Nunston.

**NEW** Hartley Turner output transformer, £2; complete; 8/9; particulars.—Abbott, Rufforth, York.

**NEW** Lexington Senior pick-up trans, Mu screen, sapphire; cost £9; sell, exchange Axton 12 or 22.—Tugby, 56, Park Ave., Potters Bar, Middlesex. [4479]

**INFINITE** baffle corner deflectors, scientifically designed acoustic chambers for 8 to 15 n speakers; lists.—Broadcast & Acoustic Equipment Co. Ltd., Tomband, Norwich. [2904]

**MAGNETIC** 1/4in TAPE recording heads, standard model record-playback with split winding for bias at 5 or 15% audio, 30/- each, erasing heads 30/- each.

**Hi-FIDELITY** 1/4in tape heads, circular Mu-metal laminations stacked 1/4in, fully screened, single unit (record-play), £4/10; twin unit with tape lifting (record-play and erase), £9; full assembly (record, play, erase, with tape lifting), £14; impedance 8 or 15% to order, bias winding for 75T osc. sec. coil; 1/4in Emittape, 3,000ft, £4/10; osc. coils, 15/-; circuits supplied free. Trade enquiries invited.—Morecambe Sound Service, 4-6, Green St., Morecambe, Tel. 1161. [4464]


**MAGNETIC** sound recording wire, steel, 5in steel, temporary wooden spools approx. 1 1/2 hours' running time at 2ft per sec.; 14/- per spool.—A. Smart, 40, Grange Rd., Halesowen.

**FOR** sale heavy duty recording machine and separate motor recording amplifier, Prestage and crystal mic, line amplifier, Burley Hill, Ryeley Road, Brierfield, Burnley, Lancs. Tel. 379 Nelson. [4523]

-towards perfection-

LOWTHER P.M.2

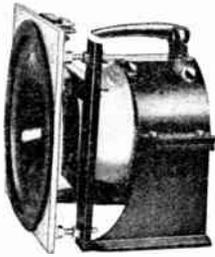is one of the most efficient loud-speaker drive units in existence.



Specification

Flux Density : 19,500 gauss average over gap area.  
 Magnet Gap. 1.6 mm. x 6 mm.  
 Diaphragm, incorporating Messrs. Voigt Patents Ltd. re-matched light coil twin diaphragm, 6in diameter, all minimum wire speech coil.  
 Weight : 19 lb. average.  
 Dimensions. 8 1/2 in. high, 8 in. wide, 7 1/2 in. deep, over plug.  
 Dynamic Impedance. 15 ohms.  
 Sound Power Output estimated 2 x 10<sup>6</sup> ergs/sec. for normal speech and music with approx. 6 watts R.M.S. per speaker current.  
 Connections : Moulded 2-pin socket and plug at rear of unit. (Pat. Nos. 618,802, 628,432 and Pending.)

Used in conjunction with Corn's Horn type P.W.I. or Volt Reflector type horn is the most outstanding combination for natural reproduction and therefore a perfect complement to your electro-acoustic equipment.

NEVER LET YOUR VALUABLE

THE LOWTHER MANUFACTURING CO.

(The Laboratory Production Unit.)

Lowther House, St. Mark's Road, Bromley, Kent RAV. 5225

THESE ARE IN STOCK

- Elements of Sound Recording. By J. G. Frayne and H. Wolfe. 51s. Postage 1s.
- Cathode Ray Tube Traces. By Hilary Moss. 10s. Postage 6d.
- Wireless Simply Explained. By R. W. Hallows. 10s. 6d. Postage 6d.
- Technique of Radio Design. By E. E. Zepler. 25s. Postage 9d.
- Basic Mathematics for Radio Students. By F. M. Colebrook. 10s. 6d. Postage 4d.
- Television Servicing Manual. By E. N. Bradley. 4s. 6d. Postage 3d.
- Radio Valve Data. Compiled by "Wireless World." 3s. 6d. Postage 3d.
- Radio Amateur's Handbook. By A. R. R. L. 15s. 6d. Postage 9d.
- Brimar Radio Valve and Teletube Manual. 4s. Postage 3d.
- Superheterodyne Television Unit. London and Birmingham Areas. 2s. 6d. Postage 2d.
- Radio Receiver Servicing and Maintenance. By E. J. G. Lewis. 8s. 6d. Postage 5d.
- Vade-Mecum 1948 Edition. Two volumes. By P. H. Brans. 19s. the set. Postage 9d.

THE MODERN BOOK CO.

(Dept. W. 12)

19-23 FRAED STREET LONDON, W.2

GRAMOPHONE AND SOUND EQUIPMENT

30 watt amp, stand mike, twin 10in spars., 2 playing desk, twin 12in turn tables and p.u.s., complete £75 or offer—39, Grammers Ave., Preston Rd., Wembley, A. and 7532, 14542  
**LATEST** American wire recorder which includes radio transmitter and crystal record player; hi-fidelity reproduction; 60 min spool; portable, 12v-250v; £95.—Parsons, 37, Woodland Way, Mitcham. 14521

**WEBSTER** wire recorder, Continental suitcase model, made for 110-240 volts 50 c/c.s. modulation level indicator, crystal mixer and three spools wire, new September and hardly used; highest offer over £30 secure.—Box 565, NE B.B.C. recorder, disc, rack, less cutting head and traverse gear, and 6J55; offers over £30, or would consider exchange for wire or tape recorder, or purchase of gear as above, or what have you?—Surplus Supplies, Northbrook St., Newbury. 14506

**TAPE** recording, an entirely new, simple and efficient method of recording is now becoming generally available; we are now publishing a booklet describing the system in simple terms and we can supply recording heads and other essential components for the construction of suitable equipment; private and trade enquiries invited.

**AUD. GRAPH, Ltd.**, 7, St. Peter's Place, Birmingham, 1. 14509

**BRITISH SOUND RECORDING ASSOCIATION**—Membership is open to all professional and amateur recording engineers and high quality reproduction enthusiasts. The official Journal, "Sound Recording," Vol. 3, Nos. 1-2-5 available at 2/3 post free. B.S.R.A. Diary for 1950 at 4/6 with eight pages of data on recording and reproducing topics, brochure and application forms from Membership Secretary, Harle J. King, 48, Mount View Rd., N. Chiswick, London, E.4. 2119

COMPONENTS—SECOND-HAND, SURPLUS

**WIRELESS** World televisions. For approved components all enquiries should be addressed to the makers. Harle J. King, 226-228, Merton Rd., Wimbledon, S.W.19. 10033

TRANSFORMERS to exact specification.

**LINE O/P** trans., for W.W. television 45/-; O/P trans., for Williamson amplifier, 75/-; mains trans., for Williamson pre-amp and radio feeder unit, 60ma O.P. 28/6; television filament trans., 6.3v 8amp and 2.4, 6.3v 2amp, 23/6; tap panels fitted as specified, trans., for amplifiers, televisions, valve testers, test gear, chargers, etc. to any published specification, or to your own design.

**E.P.D. TRANSFORMER PRODUCTS**, 31, Queenstown Rd., Battersea, S.W.8. Tel. Mar. 4130. 14579

SOUTHERN RADIO'S Wireless Bargains.

**BENDIX** command receivers, B.C.454 (40-100 metres), B.C.455 (33-49 metres), complete with 6 valves, new 35/-, plus 1/6; B.C.455 (28-41 meg for television sound), 50/-; control boxes for Command receivers, 13/6; 14ft control cables, 9/6; knob and adaptor for same, 2/9; T.R.1196 6-valve superhet receiver, with circuit, 22/6; capacitor time switches by Smith or Venner, 11/4; crystal detectors, 2/6; throat microphones with lead and plug, 3/6; universal Avon minor cases with carrying strap, leather, 10/-; Marconi lightweight headphones, 4/-; Thermal delay switches, 5/-; bomb-sight computers, 60/-; inspection lamps with lead and plug, 2/6; Westco's WX6 and W112 6.4 per dozen, special line, limited quantity only, type 58 Mk I transmitter receivers, complete with vibrator pack and batteries, complete brand new in sealed cartons, £19; Teleonic receivers, new, complete with 4-HiVac valves, 32/6; 14bra hole cutters, 5/-; most lines previously advertised still available; full range of radio books in stock; please send 2/6d for complete publication list.

**SOUTHERN RADIO SUPPLY Ltd.**, 46, Lisle St., London W.C. Gerrard 6653. 10016

**THE** simplest shot pack type M.L. M.L. waves 22/6, thousands in use.

**CRYSTAL** COIL Co. Brinklow Nr. Rugby. 10014

**CRYSTAL** microphone inserts (Coy.) and Mic-6), guaranteed brand new; 15/6 post free.

**RADIO-AID, Ltd.**, 29, Market St., Watford, Herts. Watford 5998. 10036

**HAVE** you seen our new component catalogue? Many bargains. May we send you a copy?

**M. WATTS & Co.**, Baker St., Weybridge, Surrey. 14538

**7G** valveholders and screens, 1/6.—Seven Oaks London Rd., Davenham, Northwiltshire. 14076

**LITTLEWOODS**, North London's best selection of radio and television components; pay us a visit or post or phone your enquiries, no lists.

**LITTLEWOOD & GRENER Ltd.**, 27, Bedford Lane, Finchley, N.3, En. 5060. 10055

**WILLESDEN** high quality transformers available.

**W**ave ex-stock for the D.T.N. Williamson Amplifier, Electronic Eng. Television, and all well-known circuits.

**WILKINSON TRANSFORMER Co., Ltd.**, 23, Bedford Rd., N.W.2, Tel. No. 2166. 10056

**CONDENSERS**, resistances, T.V. inductances; E.H.T. transformers, chokes, indicator units, control units, etc., etc.; send for latest lists of genuine bargains.—Black, 66, Tudor Rd., Leicester. 14568

OPPORTUNITIES IN RADIO



Get this FREE Book! "ENGINEERING OPPORTUNITIES" reveals how you can become technically-qualified at home for a highly-paid key-appointment. In the vast Radio and Television Industry. In 176 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of TELEVISION and RADIO, A.M. Brit. I.R.E., A.M.I.E.E., City & Guilds, Special Television, Servicing, Sound Film Projection Short Wave, High Frequency, and General Wireless Courses. We definitely guarantee "NO PASS—NO FEE"

If you're earning less than £10 a week, this enlightening book is for you. Write for your copy today. It will be sent FREE and without obligation.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY BIET**  
 388b SHAKEESPEARE HOUSE  
 17/19 STRATFORD PLACE, LONDON, W.1

TELEVISION

CONSTRUCTORS

Build the television receiver which proved to be successful and popular at Radiolympia!

Suitable for use with 9in., 10in., or 12in C.R. Tubes.

**INSTRUCTION BOOK 5/-** post free.

Containing all the information required for building the set, including point to point wiring diagrams. (Please state London or Midlands).

**CAN BE BUILT FOR £16.** C.R. TUBE extra.

Write for leaflet giving further details.

- Standard Range of Components :**
- Deflection coils, type DC1, per set £1 2 6
  - Line Output Transformers LTI, each £1 2 6
  - Focus Coils, type FC1 (High Resistance) each ..... 17 6
  - Focus Coils, type FC2 (Low Resistance) each ..... 17 6
  - Pre-amplifier, with self contained power pack ..... £7 10 0
- London or Midlands.

HOUGHTON & OSBORNE  
 ELECTRON WORKS, THAME, OXON

Phone : THAME 182



# RADIO DEALERS AND SERVICE ENGINEERS

should write and ask for our November Monthly bulletin price 1d. Dozens of clearance bargains, and comprehensive lists of TUNGSRAM valves, T.C.C. condensers, EGEN volume controls, B.A. screws and nuts, etc., etc., FROM STOCK QUICKLY.

**A.W.F. RADIO PRODUCTS LTD.,**  
Borough Mills, Bradford, Yorks.

**COMPONENTS—SECOND-HAND, SURPLUS**  
REMOTE control units, containing LF choke, 200 mfd. 12v condenser, 2-1 transformer, 12v re-ay, 22 ohm res.ste., panel ind.cator, bulb and 5-point rubber plug and socket, 4/- each, 2 of 7/-, post paid.—R. S. Powell, 109, Corville Rd., Quinton Broad, [4490]

**ASSORTED TUNING**, silver mica, ceramic, etc., from 4pf to 1mf, d.n.w. and guaranteed 30 for 5/6; 50 for 8/-, post paid, f.a.r. sect on s.w.n.; other bargains include oak 4p4 switch, 1/4; standard 000mfid twin gaugs ceramic ins 3/3, etc.—List from L. B. Howall & Co., 29 McWilliam Rd., Brighton 7, [4500]

**A BARGAIN**—new portable volt-ohm-meters in plastic case, size 3 1/2" x 5 1/2" x 2 1/2" with 50mg carrier; s.a.e. U-1, 0-1, 0-3v, 0-60ma 0-500ohms, 0-5,000ohms, range easily extendable, instructions on each; 12/9 each, post paid; fully tested and guaranteed.—R. S. Powell, 109, Corville Rd., Quinton Broad, [4490]

**MANUFACTURERS**—enamelled, copper wires, all gauges, laminations, all types, huge stocks radio components, s/m, m/m, p/t an. block condensers, close tolerance and high stability resistors to 1%, all goods guaranteed.—W. B. Simmons, Ltd., c/o Brydon Rd., Harrow, Middx. Telephones, Harrow 2524 and 0315.

**SYNCHRONOUS** c.c.c. units, self-starting, 200-250v a.c. 50 cyc., fitted camo motors consumption 2-watts, size 2 1/2" in dia., 2 1/2" deep geared 1 rev 60 m.n. fr.c.t.on reset; ideal movements for managing electric clocks, time switches, etc., n.c.s.e. plated finish, compete with 12 to 24 d.a.l. train and 5 n hands, price 22/6, post paid. Camo as above, f.f.a. speed, one rev. per min. less d.a.l. train, id.a. for air-room process t.m.c. etc. price 20/- each, post paid.

**CLOCK** work timers, new, suitable for processors, dark-room timing, etc., variable timing, 1 to 60 seconds, relay to operate 11 6v battery capable of handling 100watts supplied with camo movement, price with relay, 35/- each, post paid, each movement is fully tested before dispatch.

**CONDENSERS** Electrolytic, 1,000mfd. 25v d.c., W.K.G., 4/6 each, post paid, 45/- per doz. RECTIFIER units, a.c. to d.c., input 200/250v a.c., 50 cycles 1-phase, output 160/200v d.c., 1 amp; price 41/- each, post paid.

**SIEMENS** high speed relays, 2,000ohms, ideal for mode. contr.; 6/6 each, 72/- per doz. INDICATOR units type 134A, fitted 3in and 6in cathode ray tubes type ACR10 and VCR 517B and 17 valves, viz., 6 VR92, 5 VR91, 3 VR54, 3 VR65, metal rectifiers, chokes, transformers, potentiometers, condensers, etc. £3/10 each, carriage 10/-

**A.C. mains** wavemeters 250v 50cy, range 22 to 30mc/s, complete with valves and fitted in carrying case, £3 each, carriage paid.

**BATTERY** wavemeter type 105, wave range 1.540-1.220mc/s and 3.410 to 2,000mc/s; fitted microammeter 0 to 500, in n.c.e. carrying case, complete with valve, price 40/- each, carriage 3/-

**TYPE 24 R.F. units**; new in maker's cartons these make excellent S.W. converters complete with valves 30 to 40mc/s, price 15/6 each, post paid.

**MAINS** transformers, 250v a.c. outputs 250v 90ma, 2.7v 8amps, 5v 2amps, price 17/6 each, post paid.

**CONDENSERS**, 25mfd 400v d.c. working, 4/- each or 40/- per doz, post paid.

**PERFORMANCE** meters type No. 2, fitted standard mains 250v a.c., 50 cycle power pack, 2 VR91, 1 VR137, 1 5Z4G, 1 CV51, 1 VR92 and other useful components, £2.5 each, carriage 5/6.

**3 C. mains** 250v 50 cycles power pack; with variable output, 300v d.c. at 10ma, to 200v d.c. 25ma housed in nicely finished metal cabinet; size 11in x 6 1/2in x 6in complete with 5Z4G rectifier, also gives 18v a.c. 1/2amp, £2.10 each, post paid.

**CONDENSERS** electrolytic, 1,000mfd 25v d.c. w.g., 4/6 each, post paid 45/- per doz.

**A LARGE** quantity of similar items which we do not list, which are available to callers; also assortment of various ex-W.D. radar and radio equipment, relays, power packs, oscillograph units, gears, photographic apparatus, s.a.e. for lists.

**H FRANKS** 59, New Oxford St., London, W.C.1. One minute from Tottenham Court Rd. Station. Tel. MARYLEBON 9534. 10057

**TELEVISION**—P.M. focus rings, self supporting, triode of tetrode tubes, 9 or 12in. chrome plated, boxed and with instructions, 35/-; coils "E.E." London, 15/-; "E.E." B'ham, 18/6; ditto less chokes, 16/6; "W.W." s'het, London or B'ham, 20 coils, 52/6; chassis "W.W." 1P, RF and sound; units with 17 wound coils and two punched chassis; £3; copper screening boxes, 2/6 ea; your retailer, factor, or

**PEL SOUND PRODUCTS** Co., Marlborough Yard, Archway, London, N.19. Tel. North 1025.

**EXCEPTIONAL** bargain.—A fortunate purchaser chase enable us to offer a complete kit of parts, including all valves, back cradle case, and circuit, etc., suitable for constructing the McMurdo 20 watt high fidelity A.C./D.C. amplifier; the kit features high-grade components throughout, including Partridge transformers; output stage—four CL33s in parallel push-pull; normal price for complete amplifier, 40gns; our price for complete kit, £12; trade enquires invited.

**ROGERS DEVELOPMENTS** Co., 106, Heath St., Hampstead, N.W.3. Hampstead 6901. [4574]

## SOUTHERN RADIO'S WIRELESS BARGAINS

**T.R. 1193 SUPER-HET RECEIVER**, complete with six valves and fr. unit, Brand new 22/6.

**CRYSTAL MONITOR** Type 2, complete in case less crystals 6/6. With two Brand new crystals, 16/6.

**CRYSTALS**, brand new American and British 2-pin from 2040 kc. to 38 mcs., 6/- each. Twelve assorted frequencies, 60/-

**SECTIONAL AERIALS**, fit, interior-king, 3/6.

**BENDIX COMMAND RECEIVERS**, B.C. 454 (49/100 metres), B.C. 455 (38/49 metres), complete New with Six Valves, 35/- plus 1/6. A few converted to 28/41 metres for television sound, 50/-

**CONTROL BOXES** for B.C. 454/4/5 with slow motion dial, volume controls, etc., 13/6.

**DRIVE ADAPTOR** for BC454/4/5 with knob, 2/9.

**R.A.F. BOMB SIGHT COMPUTERS**, complete with Motors, Gyro, Gyro Gears, Blowers, etc., etc., 55/- Plus 5/-. The best component value ever offered.

**INDICATOR UNITS**, BC454. Complete with 7 valves, CR tube 7HP1, etc. Complete in Metal case. Ideal for Oscilloscope conversion, 44/- plus 5/-

**CONTACTOR TIME SWITCHES** by SMITH or VERNER. 10-hour movement with thermostatic control. Complete in sound-proof case. Ideal for photographic and other use, 10/- plus 1/4.

**RADIO COMPASS INDICATORS** with Selwyn Motors, 30in dial 360 deg., 13/6.

**ALDIS LAMP**, 6in. lens, complete in transit case, spare bulbs, cable, etc., 40/-

**FLASHER MOTORS**, 24 volts with smoothing and starting in case, 11/6.

**DELCO HAND GENERATORS**, 6 volt at 4 amps., 17/6.

**RECEIVERS R28 ARCS**, ideal for 2 metre conversion 100 156 Meg. V.I.P. 10-valves and Tuning Motor. Brand new in cartons and circuit, 50/-

**SLEEVING**, 1 mm. to 2 mm. aluminium quantity, 12 gross yards, 6/-

**LUBRA HOLE CUTTERS**, adjustable from 1in. to 3in. For use on wood, metal, plastic, etc., 6/6.

**CRYSTAL DETECTORS**, 2/6.


**OIL FILLED CONDENSERS**, 0.1 mfd. and 0.5 mfd. 5 kV 3/- plus 9d.

**THERMIST MICROPHONES**, complete with lead and plug boxes, 3/6.

**WEITE T.O.S.**, W+6 and W112, 6/4 per dozen. Please send 2d. for full publication list.

**Southern Radio Supply Limited**  
46, LISLE STREET, LONDON, W.C.  
Gerard 6653

### CABINETS AND COMPONENTS

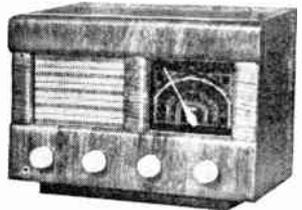

Receiver cabinets as illustrated. Beautiful walnut veneer. Size 12 1/2" x 8 1/2" x 7 1/2" deep, 35/-. We can construct any type of cabinet to your requirements.

All components to construct a T.R.F. or Superhet Receiver in above cabinet are available.



4 1/2 Watt A.C. Amplifier with negative feedback. From £5.4.7d. 5 Watt Universal similar to above from £3.16.2d. 12 Watt Universal from £8.5.0d. Full details on request.

T.R.F.—Superhet—and Personal Portable Blueprints available at 2/6d. each.


**LEWIS RADIO CO.** (Dept. W.2.)  
322, High Road, Wood Green,  
LONDON, N.22.  
Phone: BOWes Park 5997.

## Thinking of building a Television Set?



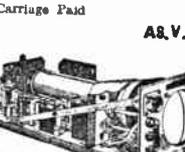**10 VALVE 1 1/2 METER SUPER-HET**

Idea for converts on into television receivers. I.F. 12 mcs. Band with 4 mega. Co-axial input and output sockets. 10 Mazda Main type 1 R05 (SP1) valves, 6-3 volt filament.



**A.V. INDICATOR UNITS Type 6 H.**

Containing seven valves and one 6 in. Cathode Ray Tube type VCR 6 Brand new and unused. In sealed wooden transit case.



**12 VALVE RADAR UNITS**

Now and unused. Contains 10 type VR 91 (E8 30) Valves, 2 type V4 54 valves, 45 Vario-a condensers, 76 various resistances, 2 Transformer, 1 Relay.



**£2.15.0**

each Carr. paid. Offered at a fraction of price of valves alone.

**Dept W WIRELESS INSTRUMENTS (Leeds) Ltd,**  
54-56 The Headrow, Leeds. Tel. 22262.

COMPONENTS—SECOND-HAND, SURPLUS

SPLIT stator T.X. type condensers, accurately calibrated 300 and 37 p.f. O.K. for standard. 6/9; 3-bague condensers, 0.1 x 350v, 0.02 x 750, 0.01 x 1kv, 3/- doz.; Micamold, 0.1 x 350, 2/6 doz.; 32 uF x 350v, 1/9; 8 uF x 500v, 1/-; Selenium recs., 12v 2a, 24v 1a, 3/6; 160v 40ma, 1/10; 275v 80ma, 3/11; post free over 10/-, under, 1/- p. case.

HATFIELD RADIO, 78, Stroud Green Rd., N.4. Arc 1593.

LINE detector units, containing 3 ITH valves 207/-; Bendix 433G compass receivers 200 1.750cc/s, 15 valves, 6K7, 6r6, 504, 6N7, etc.; control panel, drive case, hand-cook, etc.; computer homostig unit a.c./d.c. motor, etc. 25/-; BC306 antenna units, 7/6; telescope 30ft antenna masts, 85/-; aircraft 6 in c.mpasses, 20/-; 12v, 14a accumulators, 30/-; 20+90v ayer type h.t. batteries 77/-; heavy duty 230v transformers 350-0-350 175ma, 6.3v 6/8a, 5v 3a, 20/-; all items new and car. p. case.

R. HIGGINS & HAD, 12, Gower Rd., Brinnington, Stockport, Cheshire. [4343]

TELEVISION kit, including 21 valves, for £16 complete, for 9in black and white picture instructional booklet, 5/- post free, contains full details and point-to-point wiring diagrams, etc.; individual units supplied separately, sound and vision kit, £5, carr. 2/6; time base unit kit, £5 (including deflection coils and line output trans.), carr. 2/6; power pack kit, £6/10 (including mains and EHT trans.), carr. 12/6, 10/- ret. in p. case; C.R.T. control kit, £1 (including focus coil), carr. 2/6; c.w.o.—G. M. 3, Raleigh Rd., Hornsey, London, N.8. [4541]

TELEBOOSTERS for long-range television reception. R.F.2L., 40/48 mc/s variable tuned for maximum sound or vision, 3 stages. 2 V.R.91 valves EQ to E.F.50, sluz; tuned interstage and output, coaxial pipes and sockets, driving leads for 6.5v heaters, 200 h.t., 10 to 15, into receiver high gain, fully screened, price £3/12/6. R.F.1.L., 40/48 mc/s 2 s.w.ug tuned stages single valve, £2/12/6; for Birmingham R.F.2B., 55/65 mc/s twin and R.F.1.B. single as above; power supply for boosters, 230v, input 160v, d.c. and 6.5v output, 24. S.a.e. for particulars and trade test report.

BOSCOMBE RADIO ELECTRIC, 595, Christchurch Rd., Boscombe, Tel. 1704. [4032]

ALLEN & GOULD, for components, air spaced tuning condenser: .3015mfd A/g, 2/3; .3035mfd s/g, 2/6; .3055mfd s/g, 2/9; mica capacitor, .3035mfd s/g, 2/9; .465k/10, 465k/10; electrolytics: 2/200 microcap, 1/6; 2/350, 1/9; 4/200, 1/-; 4/350, 2/-; 8/450 cardboard tubular, 2/6; 8/450 canned, 3/6; 16/450 cardboard tubular, 2/9; 16/450 can, 3/6; 16/450 can, 2/6; 8/450, 4/-; 8/16/450, 4/6; 16/16/450, 5/12; 16/8/450 plus 2/6; inert coils, 1.5v, 12/6 for 50, 21/6 per hundred, metres, 0-500 m.h.iamp d.c. 3/6; 0-8a RF, 3/-; If chokes, 5h 200 MA, 7/6; 10h 50ma, 6/-; Varley double chokes, each section, 30h/20h 150ma, 12/6. Ferranti push-pull driver transformers, 11/6, PX4 push-pull output transformers, 7/6; 5 way paralleling, 6d; SP 3w 9d; SP 3w, 1/-; SP 10w, 1/9, valves over 2000 B.O.T., and transmitting valves; ask for list V7.

ALLEN & GOULD, 5, Obelisk Parade, Lewisham, S.E.13 (opposite Gaumont Cinema). Telephone Lee Green 4058.

BATTERY charger kits, Selenium h.t. and r.f. transformers, new goods with full guarantee and instructions; add postage 6d up to 12s, 1/4 above; sent carefully packed; standard charger kit, for pro. t. simple to make. S.T.C. 12v 3 amp rectifier with 60 watt transformer and barretter for 2v, 6v, 12v charger, 45/- ditto, but with 20 watt transformer for 2v, 6v, 12v, 3/6; for 6v only, 33/-; 1 amp kit for 2v, 6v, 12v, 31/-; cases for above specially manufactured with all small hardware, 17/6, med um duty kit, 12v 4amp S.T.C. rectifier with 75 watt transformer and barretter for 2v, 6v, 12v charger, 55/- case, etc., 17/6; 6v 2 amp, 12v 1 amp charger, 45/-, or ready for use 50/-; heavy duty kit, 12v 6 amp rectifier with 120 watt trans., slider resistance and ammeter for 6v, 12v charger, £4/15, ditto, but 4 amp, £3/15; Automat self regulating chargers for 6v, 12v, at 2 amp, as tested by motor weight 91b, 57/6; car charger, £2/29; 5 amp 27/6; 24v 6 amp, £3/2; 24v 3 amp 38/-, many other types with or without trans., state needs; also heavy 12v 5 amp 25/-, 6v 10 amp c. tap, 25/-; H.T. rectifiers, small space c.mact. coil running, 250v 60ma 7/-, 110 60ma 6/6, 120v 30ma elim type 6/6, or with trans., triode rectifier, 2x8mids, 2/6; E.T.2 charger for 5 amp 27/6; small chokes 2/10 extra, 350-0-350 80ma c.t. rectifiers, 9/-; 250v 100ma bridge 12/6 postage 7d; M.B.3 instrument rect., 3/6; Arrow 2mf/1.000v oil filled cond., 3/-; Luthraon mica mikes, 55/- on fly; new Rowa 8 in P.M. sp'rs, 10m, 12m, 11/-; transformer, 250v, sec. 16v, at 5 amp, tapped 10v, 23v/- also 110v auto trans., 500 watt, 11/-.

CHAMPION PRODUCTS, 43, Upland Way, London, N.21. Lab. 4457.

# GALPINS

## ELECTRICAL STORES

408, HIGH ST., LEWISHAM, LONDON, S.E.13

Telephone Lee Green 0309, Near Lewisham Hospital

ELECTRIC LIGHT CHECK METERS (watt hour type), all for 200/250 volt A.C. 50 cycles, all electrically guaranteed: 2 1/2 amp. load, 15/- each; 5 amp. load, 18/6 each; 10 amp., 21/-; 20 amp., 25/-; 30 amp., 30/-; 40 amp., 35/-; 50 amp., 42/6; 100 amp., 50/- Carriage on all types 2/- extra.

SWITCHBOARD PANELS containing 3 VARIAC Transformers 100/120 wats 0 to 110 volts, also (1) Synchronous Motor operating Relay contacts approx. 40th h.p., also numerous large type mains toggle switches, a few only to clear, 75/- each. Please note that the wire on one only of the Variacs is damaged, please allow 5/- carriage.

EX-NAVAL TELEPHONE HANDSETS, BAKELITE PATTERN (self-energized), no battery required, complete with wall bracket (new), 15/- per pair, post 1/6. Ditto, complete with Buzzer ringing mounted in weatherproof box, 24 volt required for energizing Buzzer only, complete with Hand set, 15/- each, or 25/- per pair.

LARGE TYPE RECTIFIERS. Output 50 volts 1 amp. D.C. input 70/75 volts A.C. Half wave type, 8/6 each, post 1/6. TANNOY P.M. SPEAKERS (Small Hailers), 4 ohm speech coil, complete in wooden case with output transformer, 15/- each, carriage 2/6.

EX-W.D. ROTARY CONVERTORS by well known makers, 24 v. D.C. input, 50 v. 50 cycles, 1 phase 500 watt output, £6/10/- each.

MAINS TRANSFORMERS. 230 v. input, 300 v 150 mA, C.T. 6.3 v. 8 amp. 8 v. 2 amp., 15/- each.

MOTOR ALTERNATORS, ex-R.A.F., as new, 230 v. A.C., 50 cys. 1 ph. input. Output, 250 v. 625 cys. 1 ph. at 24 amps., 75/- each. Ditto, 1.725 cys. output, 85/- Please note both these machines require a 24 v. D.C. excitation at 4 amps.

EX-NAVAL CATHODE RAY INDICATOR POWER UNITS (new). Sold for component parts only, consisting of approx. 150 Resistances and Condensers of various values, H.V. Condensers, Chokes, all mounted on solid brass chassis, weight 90 lb., to clear 25/- each, carriage forward.

EX-R.A.F. CRYSTAL MONITORS, type 2, complete in wooden carrying case, the frequency depending on crystal used, 5/- each. Short Wave Aerial Coupling Units (Wavemeters), 5/- each. PRE-PAYMENT 1/10- SLT ELECTRIC LIGHT CHECK METERS, 200/250 volts, 50 cys. 1 ph., 2 1/2 amp. load, 30/- each, carriage 3/6; 5 amp. load, 35/-, carriage 3/6. 10 amp. load, 42/6 each, carriage 3/6.

EX-R.A.F. MICROPHONE TESTERS (new). These consist of a Ferranti 0 to 450 mA, 2 1/2 in. scale meter shunted to 1 mA, incorporated Westinghouse Rectifier, the whole enclosed in polished teak case, calibrated at present 0 to 10 v., 25/- each. MAINS TRANSFORMERS, all 200/250 v. 50 cys., 1 phase input, output 700/0/700 v. 70 mA., 4 v. 2 1/2 a., 12 v. 1 a., 30/- each. Another 525/525 v., 150 mA., 6.3 v. 5 a., 5 v. 3 a., 37/- each. Another 2,350 v. at 500 mA., 85/- each. Mains Smoothing Chokes, 10 Hy. 100 mA., 6/-; 150 mA., 8/6; 350 mA., 25/-; 5 Hy. 250 mA., 17/6.

MAINS TRANSFORMERS, input 200-250 v., 50 cycles, in steps of 10 v. Output 450/0/450 v., 250 mA., 4 v. 4 a., 5 v. 4 a., 6.3 v. 8 a., 6.3 v. 8 a., 62/6. Ditto 450/0/450 v., 250 mA., 6.3 v. 4 a., 5 v. 4 a., 4 v. 8 a., 4 v. 8 a., 69/-, Another 500/350/0/350 500 v. 250 mA., 6.3 v. 8 a., 0, 4, 5 v. 4 a., twice, 6.3 v. tapped at 2 v., 2 a., 67/6. Another 350/0/350 v., 300 mA., 4 v. 8 a., 4 v. 4 a., 6.3 v. 4 a., 6.3 v. tapped 2 v. 2 a., 57/6. Another 500/1,500 v., 300 mA., 6.3 v. 8 a., 6.3 v. 8 a., 6.3 v. 4 a., 4.4 a., 5 v. 4 a., 67/6.

MAINS TRANSFORMERS (Auto Wound). Voltage Changers tapped 10, 20, 25, 90, 130, 150, 190, 210 and 230 v., all at 1,000 watts, a combination of 24 voltages can be obtained from this transformer, new ex-Government Stock, £5/13/- each, carriage 5/-. Mains Booster Transformer, tapped 0, 6, 10, 19, 175, 200, 220, 225, 240 and 250 v. at 1,500 watts (new, ex-Government), £5/5/- each, carriage 5/-. Another Auto Wound, tapped 0, 110, 150, 190, 210 and 230 v. at 1,500 watts, £6/10/- each, carriage 5/-. Ditto, 2,000 watts, £7/5/- each, carriage 5/-.

COMPONENTS—SECOND-HAND, SURPLUS

CONDENSER bargains: Oil-filled types, 4uf/3,000v 2/8; 4uf/2,000v, 5/6; 0.05+0.1, 3,000v 5/-; 2uf/500v, 6d; 0.25uf/4kv (2 1/2 in x 1 1/4 in x 7 in), 3/6; silver mica, standard m.c.a., ceramics numerous values 2pf to 0.01uf, 2/3 doz.; Mu.rhead 0.0005/20kv type AF51 in four cases, size 2.0 x 4.0 x 4.0 in, including terminals, 10/-; tubular types, waxed, 0.1/300ac, 0.15/400v, 0.01/3,000, 3/- doz.; 0.1/1,000, 3/6 doz.; mica-cased tubulars, 0.01/750-1,000v, 3/3 doz.; 0.5/350v m.c.a.molders, 4/0 doz.; 0.002 mica.mites, 3/- doz.; Duoliers, 0.01/2,000, 10 pated cases, 5/- doz.; base, coil transformers, fibred and threaded, 2/ft 1 in x 3/4 in, ditto wound 1 1/2, 2/- doz.; ceramic stand offs, 5 in x 1/4 in, 1/6 doz or 2/6 carton of 20; 2w 4w 40w double contact wafers switches, 2/-; meters, 0.5a RF, 3/6; electro.ytic condensers, 50u/20v, ad or 1/6 doz; 100u/50v (a.c. case) with terminals, 1/3 or 12/6 doz.; 16u/3,000 square metal case, 2/- or 20/- doz.; a.l first-class cean goods; please add sufficient postage, excess refunded.

J. E. L. POSTAL SUPPLIES, 133, St. James Rd., Blackburn. [4567]

NEW! £22 transmitter chassis with 122 valve bases, coils, transformers and tuning condensers, etc., 5/6 each; new 6v Vibrator power pack H.T. 250v, 80ma, 32/6 each; new oiled colapsible wire mesh reflector aerials, 5/6 each; 184A indicator units complete with 4 VR91, 4 VR91, 6 VR92, VCR, 517B, etc., etc., 80/- each; 14ft Telescope whip aerials with base 5/- each, K.24 aerial camera, new boxed 2.5 lens £9/5 each, rotary converters, new rewinds, and unused 200-240v d.c. input, 200v-230v a.c., 1 phase 50 cycle, 150 watts output, £7/10 each; a.c./d.c. 1 ph. 200p, 200v-250v a.c./d.c. ideal for sewing machines, etc., these motors are as new, fully guaranteed, and are not converted rotary transformers 40/- each. Heater transformers, 200-230v a.c. input, 6v/3m 22/6 each, L.T. transformers, most from stock, 12v, 16v, 20v, 24v, 1-10amps, 20p, 22/6 each, spec. 12v, 10amp, 20p, notice, type H.176 H.T. rectifiers 5/6 each; J.50 3/6 each; new 5mtd 3,500v wkg. condensers 3/6 each; .02, 8,000v working 4/6 each; large stocks of all types of condensers at competitive prices. Send for your enquiries, we can help you with receiving and transmitting valves, 100 v.c./d.c. motors, these are ideal for models, new 7/6 each; Aldis signal lamps 27/6 each; new hand-bearing compass with prism and provision for battery in handle for illumination 45/- each; American telephone repeater and amplifier equipment in stock; New rack mounted accessories, complete with power pack less valve, 0.25amp 2 1/2 in 15/- each; 0-1ma 12/6 each; ultra-meters, micro-amp meters, etc.; send us your enquiries, postage extra on all goods.

SERVICE RADIO SPARES, 4, Lisle Street, W.C.2. Ger. 1734.

SUPREME RADIO, 746b, Romford Rd., Manor Park, London, E.12. Tel. 11f. 1260. Est. 15 yrs. Buy now at these bargain prices; line trans., 21/- each; fly-back type line trans., with provision for EY51 valve, 22/- each; line and frame scanning coils, 25/6 ea.; P.M. focus units from £1; H.T. trans., 350-0-350v, 6.3v 6 amp, 4v 8amp, 4v 3amp, 0.2v 6.3v 2amp, 250ma with screen, 70/- ea.; 5hy. 250m a choke, 15/9 ea.; 10hy 80ma choke, 7/9 ea.; ceramic E.F.50 valve holders, 6d ea.; 5/6 doz.; retaining rings for 6d, 8d ea.; bakelite plug valve-holders, 6d ea.; co-axial plug and socket, 1/-, complete; all parts in stock for London or Birmingham; E.E. television, 1/2 watt resistances, from 100 to 10 meg 1/9 doz., 18/6 gross on;y; 1/2 watt resistances, 100 to 2 meg 1/2 doz., or 21/- gross on;y; 1/2 watt resistances, 2700, 470, 100, 100, 5.3 kn, 8.2 kn, 18 kn, 33 kn, 56 kn, 75 kn, 68 kn, 1 mf and 2 meg, 4/- doz, or 45/- gross on;y; or assorted gross; 2 watt resistances, 2 kn, 13 kn, and 1 meg 1/5 6 doz., or assorted; noise suppressor units consisting of 2.01 mfd cond. and iron-cored choke, 6d ea., 5/- doz.; 5 meg vol. controls, 7sd ea.; 1 mfd and 5 kn vol. control, 1/- ea.; 4 mfd 350v screw base metal cond., small type 6d, 5/- doz.; 12 mfd 50v screw base metal cond., 6v, 5/- doz.; 50 mfd 50v, 50 mfd 12v, 10 mfd 25v and 25 mfd 25v 1/- ea., 11/- doz., or ass. doz. on;y; tubular wire end cond., 0.01 mfd 1 kv, 0.02 mfd 750v, 0.05 mfd 500v and 0.1 mfd 500v 6d ea., 5/6 doz., or ass. doz. on;y; 0.01 mfd 500v, 6 doz.; m.d.g.t. mica cond., 0.001 mfd, 0.0005 mfd, 6d ea., 5/6 doz., or ass.; metalite cond., 0.01 mfd 350v and 0.002 mfd 500v, 9d ea., 8/- doz.; can-type cond., 0.01 mfd 450v, 2/6 ea.; 16-32 mfd 350v, 3/6 ea.; 16-8 mfd 450v, 3/6 ea.; 32-32 mfd 350v, 6/6 ea.; 32 mfd 500v drylite cardboard case output cover, wire ends, 5/- ea.; 16 mfd 350v dry lite can-type cond., 1/9 ea.; 4 mfd screw base 550v mica tubular cond., 1/- ea., 11/- doz; 2 mfd 350v cardboard wire end electric cond., 3/6 ea., 11/- doz.; we are Denco stockists, Denco catalogues 9d ea.; 5 ma meter rectifiers, 4/- ea.; 4 pole 3 way, 4 pole 2 way and 3 pole 2 way rotary switches, med. 2 ind e, 1.6 ea.; fixed mica cond., 200 pf, 300 pf, 400 pf, 500 pf, 600 pf, 650 pf, 1800 pf, 305 pf, 307 pf, 00 pf, 530 pf, 570 pf, 590 pf, 700 pf, 4550 pf, all at 2/6 doz., or ass. 23/- gross on;y; 8 mfd 600v PK 700v mica can screw base condensers, 2/6 ea.; 0.01 mfd 3 kv and 0.005 mfd mica tag end cond 3/- doz.; selenium metal rectifiers, 120 v.c.m.s., 120 m.a., c.a., 0.1 mfd 2.5 kv can type cond., 2/- ea.; many other bargain lines in stock; terms, c.w.o., no c.o.d.; send 6d extra for postage orders under £5; 2 1/2 s.a.e. all enquiries and lists. [4021]

# THE CANDLER SYSTEM will train you for your MORSE CODE TEST

Read the following extracts from unsolicited letters sent us by Candler students:—

Ref. No. 3793. (First five lessons.) "I recently passed my G.P.O. Amateurs' Morse Examination after your first five lessons." (Junior Course.)

Ref. No. 2245. (Olad to announce.) "I am glad to announce that I recently passed the P.M.G. Special Exam., and as you will see on my report, my speeds are now far above the id of the speeds needed in the examination. I therefore walked through the telegraphy part." (Junior Course.)

Ref. 2573. (A really wonderful course.) "I feel it my duty to express my appreciation for a really wonderful course. Before taking the course my 'mail' receiving speed was about 16 to 18 w.p.m., this I copied letter by letter—and was I nervous. To-day I can copy 25 to 26 w.p.m. at one word behind. I can read 30 to 35 w.p.m. as easily as reading a book. Frankly I think that all the 'profit' I have gained from the Candler System cannot be represented by—say—many words per minute; but, rather as a lifetime experience gained in a few weeks. It has been said 'you have to pay to learn'—true, but with Candler you pay so little and learn so much." (Advanced Course.)

There are Candler Courses for the absolute Beginner and for Operators desiring to increase their accuracy and speed in the Receiving and Sending of the Morse Code.

Full details of Candler Courses are given in the "BOOK OF FACTS" Sent free on request.

Courses on Cash or Monthly Payment terms.  
**THE CANDLER SYSTEM CO.**  
(55V), 121 Kingsway, London, W.C.2  
Candler System Co., Denver, Colorado, U.S.A.

**COMPONENTS SECOND-HAND, SURPLUS  
RADIO CLEARANCE.** Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9133.  
I.V. power packs, oil chassis, a.l. 15x6 1/2 in. chassis with H.I. trans. 5.v 5ma. 4v 1a H.T. trans. 360-0-360v. 220ma. 4v 8a C.T., 4v 5a 6.3v 3.5a w/red with cho.e. 5x2+8mf 450v 2 octa. w/certs for output, mains (210 2.0v 30-3v) input socket, voltage divider, variable for rect. (U8), now unused, £4 2/6 carr. paid. these units were made for well-known I.V. set using 12n C.R.T.: 360-0-360v 220ma. 4v 8a C.T., 4v 5a, 6.3v 3.5a. trans. input 210 250v 30v/s. available separately, brand new. 32 6 carr. paid. T.V. line transformer, she old in a/can. with T.C. lead (used with PBN46). 11/6; chassis (steel), 5x5 1/4 x 1 1/4 in. drilled 4 outon base holes 1/9; 5x9 1/4 x 1 1/4 in. drilled 7 button base holes, 2/3; all 17x19 1/4 x 2 1/2 in. drilled 7 int. oct. and square open-ends; 3/3; E.H.T. trans. 4.2v 1ma. 65-86Mc/s. 10 va. vps. 25/3; rec. R. 1481 covers 6n SM dial. circuit diagram, etc., brand new, in transit case, £4/4, carr. paid. personal receivers B.C.728c, 7 valve rec. using 1.4v va.ves. with 4 push buttons covering 2-6Mc/s. built in L.S. supplied and new complete with valves (1T4, 1B5, etc.) 2 and 12v VIB. 2v acc., telescopic A.E., instruction book, etc., £8 19/6; main trans., all PRI 200/250v 30c/s. Sec. 460v. 200mA. 210v 15mA. 6.3v 5A. 14/6. auto trans. 200/250v-11.v. 60W. rating enclosed 18/6. special line auto. 230v. 250-110v. 100W. 9/6. sm-wiring choices 5H 120mA. 140/1 3/3; 5H 200mA 100/1 1/1; 6H 200mA. 100/1 5/6; 5H. 250mA. 90/1 7/6; 20H 300nA. 150/1 (7x5x5.5n) 13/6. e.c.trolytics. 8mf. 150v 1/3; 8 170v 1/3; 8/350 card 1/6. can 1/11. 3/4/450v 2/3; 16/350v can 2/6; 16+R 450v large can or d/ended; 8 170v 450v can 4/6; 16+24/28 450v can 5/6; 32 450v arke can 2/9; 32/450v we 3/6; 16+8 350v can 3/9; 60+100 350v 3/6; 32/350v card 2/3; 100 mf 3v 5d; 100mf 1v 6d; 25 25v 1/3; 100/25v 1/6; 25 50v 1/3; 16/550v card 1/9; 24/350v can 2/9; 9-24 350v can 2/6; P.M. loudspeakers 5n less trans. 9/11; with trans. 4500/1 1/6; 6watt less trans. 10/11; 10in with trans. 21/6; R.F. units type 24 8/6; with valves, used in good cond' or post 1 6 extra please; output trans. 2000/20. 2500/2. 2750/1. 3000/2. 3/6; 4500/2 (7000/4) 3/6; 3 radio 7000 3500 (1750) 4/6; heavy duty 7000/2) 3/6. I.F. trans. 465 Kc/s. 0005 size, iron cored 7.6 pr.; 2 gang conds. 0005 ceramic ins., 1 in standard sp ndle 1/6; ceramic switches 2p., 5w. 1B 2/6; 3p., 5w. 1B 2/6. switches small size, 2p., 6w 3p., 4w. 5w. bank. 24/6. standard 2p., 4w. 3w. (add'ional) w/alter with shorting plate 2/6; 4p., 3w. 2B 2/6; 2p., 4w 3B 2/6; 1p., 10w. 2B 2/6; all have 3 in sp ndles; resistors 100 assorted 47 va.ues ranging 180/1 1w-100K 3w. standard sizes, best makes 10 5 post. ad.; ceramic trimmers 3 50p/3 3 on a bar 1/3; 15p/2 standard; 3 30p/air spaced cond' centric 6d; 3 25p/ V.I.C. type 3d; air spaced variable 1/4 n sp ndles 25p/ 50p/ straight, 50p/ diff ceramic bases 1/6; 35p/ butterfly 1/6; "Eddystone" 60p/ double ended 1/6. car radio vibrator packs with 12v 3 pin VIB. and OZ4 valve on chassis 5v 3x3 1/4 in. output 250v. 65mA. output brought out on 8ft screened lead 17/6; meters moving coil, metal cased. 2in circular 0/500 microA 7/6; 0 15-600v req. ext. res. 6/6; 0/20 or 0 40A with shunt 5/6; Bakelite cased 2in square 0/1m 7/6; 0/5mA 6/6; 0/50mA 7/6; 0/150mA 8/6; 0/500v series res. supplied 7/6; 3/4" white cased 2 1/4 in circular 0/500-ere 16/6; 0/30mA 7/6; 0/50mA 8/6; 0/100mA 8/6; 0 200mA 9/6; 0/15v 7/6; 100-0-100v. 1mA. F.S.D 7/6; 1mA desk type 15/6; visual indicators type 1 crossover needle, with 2 separate 60microA movement 5/6; type 3 with 2 300microA movement; and 2 low voltage neon 3/6; S.M. 200's as in R.F. 23 etc., 3/11; ex-Admiralty pat. 1257 1v in engraved 0-100 fast/slow (50-11) pin mounting, 10 1/4 in sp n. 2/6; rotary power units type 10 12v D.C. input outputs 250v 60mA 6.3v 2.5A P.M. rotary mounted on above but with supp 6 11; type 87 outputs as above but 24v input 5 11; 10 va.ve receivers, R29/ARC5 cov'r 100-150 Mc/s. brand new with va.ves (no 4-717 A.C., 42/6; modular and mixer units W5724 with 7 va.ves (1-50177 2.615 2-P61 1-VR55 1-VR54) 3 chassis 10 1/4 x 1 1/4 in. 50 5H 200mA cho.e. large trans. (500 c/s), pty. res. conds., etc. in metal case with covers 10 1/4 x 1 1/4 x 6 1/4 in 21/6 carr. paid; Wilcox Gav V.F.O. covers 2-10 Mc/s. with 0-10 mA meter, supplied brand new in original carton, with 100 accessories (picks, leads etc.) and instruction book £5 carr. paid; Wilcox Gav X'a' multipliers 2-7 Mc/s. brand new, with 907 tubes, leads, instruction book etc., in original cartons 40/6; carr. paid; superhet coils 1/4 x 1 1/4 in formers M.W. H.P. A.E. osc., L.W. H.P. A.E. osc., 1/6 per coil; I.F. trans iron cored 65 Kc/s 1/9 set of 6 coils and trans 9/6; 7 or 10 2 tubes and sockets with keyway 1/6 pr.; 3 way Jony plug and sockets with cover 1/6 pr.; V.C. carbon with sw. 2 1/4 x 3/4 in 25K. 50K. 100K 250K 500K. 4/6; 3 watt wire-wound no sw 200/1. 500/1. 1.5K. 2K. 5K. 20K. 25K. 2/6; twin w/w 2.5K/2.5K 2/6; 500/500/1 2/6; 50K/30K 3/6; twin carbon 1m. 1m 2/6; all telescopic a.e.r.s. 15n closed 7it 6n extended 3/6; receive t.p. 76. 150/503 Kc/s 3 valves ARIH2. VR53 VR32. I.F. output 560 Kc/s. brand new. in transit case, 22/6. carr. paid.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. (0015

GOVT. SURPLUS UNUSED

# CONDENSERS of all types . . .


We can offer, FOR IMMEDIATE DELIVERY from very generous stocks, a wide range of ultra-high quality fixed paper Condensers, from .001 μF to 8 μF. Also STOCKS of small, genuine MICA Condensers from .00001 (10 pf) to .01 μF (10,000 pf). Prices are exceedingly moderate.

Enquiries are invited for manufacturers' requirements, wholesale and export only for bulk quantities, and for scheduled deliveries over a period as required. Most condensers are now available for immediate delivery.

Please request our 4 page bulletin CONSEVEN 01114

**CLAUDE LYONS LTD.**  
180 Tottenham Court Rd., London, W.1  
and 76, Oldhall St., Liverpool 3, Lancs.

# ALLEN COMPONENTS LTD.

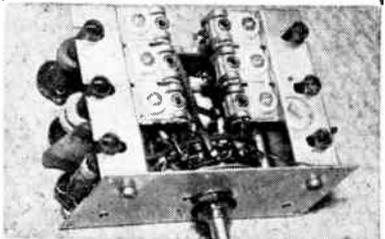

Type 300 3-wave band coil unit.

A reasonably priced assembly of exceptional performance consisting of switch, complete set of aerial and oscillator coils with all associated trimming and padding condensers. Improved aerial coupling system gives high sensitivity with exceptional discrimination against unwanted signals. A four position switch gives facilities for gramophone pickup connection and RF muting. Suitable for use with any of the standard frequency changer valves and an IF frequency of 455Kc. Calibrated glass scale available.

Ranges : 16-50, 190-550, 800-2100 metres.  
Type 300B : 11.0-26.0, 30-90, 190-550 metres.  
Television : Scanning yokes, Focus coils, Line output transformers and EHT transformers approved for Electronic Engineering televisor.

**ALLEN COMPONENTS LTD.**  
Tower Road, Willesden, N.W.10  
Telephone: Willesden 3675.

# Pennine RADIO



## AUDIO SIGNAL GENERATOR

- HIGH STABILITY
- WIDE RANGE 40-16030 C.P.S.
- LOW PRICE
- 3 WATTS OUTPUT

LIST PRICE **£9-9-0**

Write for Particulars

**PENNINE AMPLIFIERS**  
SOUTHGATE, ELLAND, Y.C.R.A.S. ENG.  
Tel.: Elland 2107

# GEE BROS. RADIO LTD

FOR

## QUALITY COMPONENTS

- 12V. 4 amp. METAL RECTIFIERS, 18/6 each.
- 24V. 4 amp. METAL RECTIFIERS, 30/- each.
- 230V. A.C. MAINS BELL, 3in. circular, Ex. Govt. (by GenCo), 3/6 each.
- ENGINE RIDGEM ALTERNATORS, type R, 1,300-4,600 cycles, 300 watts, 24v. D.C. field, 30/- each.
- 1 mfd 1,500V. CONDENSERS, 3/- each.
- 100k TOTALY SCREENED (CV25) 15 watts, potentiometers, new and boxed, 12/6 each.
- 10in. P.M. SPEAKERS, 3 ohms (by Plessey), 19/6 each.
- MIDGET 465 KC. IFT'S, 16/- pair.
- 2-GANG MIDGET CONDENSERS, with trimmers and fixing bracket, 0.000375, 7/6 each.
- MIDGET POTS, 1 meg. or 1 meg., 2/6 each.

- The above 3 items all by famous battery person receiver manufacturer.
- THE OSMOR MIDGET COIL PACK, L.M.S. with diagram, 33/-.
- H.P. STAGE for same with diagram, 15/-.
- OSMOR MIDGET BATTERY COIL PACK with frame aerial and diagram for L.M.S., 37/6.
- PULSE TRANSFORMERS (ex. radar), Ref. No. 10KB/6034, Cat. No. C7827, 30/- each.
- CRYSTAL MIXER HOLDERS for klystron connector type 10A13/342, 5/- each.
- ALL WAVE R.P. CHOKES (Eddystone) type, 1/6 each.
- 5-CORE RUBBER INSULATED CIRCULAR 1/4in. DIAMETER CABLE, 9.012, 6 colours, per 100 yards, 40/-.
- CARBON MICROPHONE INSERTS (Telephone type) P.O. No. 13 Mx. IV, 3/- each.
- ELECTRIC LIGHT CHECK METERS, 200-250v. used but in good condition, 5 amp load, 17/6 each.
- 10-20 AMP., 20/- each.
- 25-50 AMP., 30/- each.
- 100-300 AMP., 35/- each.

- SINGLE SCREENED FLEXIBLE CABLE 3/16in. diameter suitable for pickups, etc., 9d. yd., dozen yards, 7/6.
- 31N.C.R.T.(VCR138)MULLARD E.C.R.35. Complete with Mu metal screen and holder, 25/-.
- HOLDERS SEPARATELY, also fits VCR97 tube, 2/6 each.
- GYRO HORIZON INDICATOR (8sperry, U.S.A.) Type AN67361, in good order, 10/- each.
- THE R3170 RECEIVER COMPLETE, suitable for television conversion 67/6 each.
- CERAMIC VALVE HOLDERS B7G (for IT3, etc.), international octal English octal 5-pin UX, American, 7-pin UX American, 7-pin English, all at 1/- each.
- VALVE RETAINERS, all sizes 6d. each, 4/6 dozen.

- CATALOGUES AVAILABLE FOR 21d. STAMP. TRANS. C.W.O. OR C.O.D. ORDER UNDER 20/- 1/- EXTRA.

**GEE BROS. RADIO LTD.**  
15, Little Newport St.  
LONDON, W.C.2

GER 6794

### COMPONENTS—SECOND-HAND, SURPLUS

EX-G.10 impulse clock units, 1 min. 14w, 1/6 each, complete from 2/6 pair; rotary trans., 7/6 each; only communications receiver, complete with all coils (plug-in), £22/10; 1 Graham paper Morse recorder, 230 and 110v, £25; ex-A.N. 1224B battery sets, 1/10 m/v, 120v H.T. 2x-OUT ACCU. unused, 89/6 each; WEE Beegers, £6/10 each; AVO mirrors, 2/6; 100v meters, 6in dial, 30/-; Surplus Supplies, Northbrook St., Newbury, Berks. (4505)

486 only for the famous Model 30 tun:ix unit, consisting of 3-waveband Model: 30 superhet coil pack, pair 1F transformers, 2-gang condenser and attractive dial; 18x6in; each component individually selected pre-aligned, sealed and the whole matched together as a unit; the superhet you build with this unit needs no further adjustment! Full details of this and our other high quality products (coils, IFTs, mains transformers, etc.), together with many circuits and constructional tips, contained in the "Home Constructor Handbook," price 1/-; Mail order office.

SUPACOILS, 98, Greenway Ave., London, E.17.

L.A.M.O.S. waveform generators type 26 with valves—5 VR65 3 VR56 2 VR54 1 each VR116 VR55 60 resistances, 40 condensers, relays, trans., etc., 25/-; receiver in aum. case, approx 30mic/s, 2 valves VR100s type R1125B, 8/-; 2in square micro-ammeters (radiator) scaled 40-140 F.S.D 200 micro amps, 3/6; chassis 6x3 1/2 x 2 contains 1 25mfd 50v 2 other cond: octal valveholder, 3 resistances, 36v 50ma rectifier, 2 small xformers, neg. vol control, long spindle 3/9; special offer: 10 28v coloured MBC bulbs 9 yds flex, 10 coloured 'nisu' atoms makes fairy lights of any mains for Xmas, only need solder:ix 8/6; 20,000ohm: pots screwdriver control 1 1/2in diam, 6d; 5m instrument rectifiers, 2/6, 21-d stamp brings list PASSINGHAM, 95, North St., Kelghiey, 1002

JACK PORTER, Ltd (Radio), for new Sprague oil condensers, 15mfd, 750v (tapped 3, 4, 4 3mfd, with clips, 7/6; Sprague cap 2 000mfd, 15v, 2/6; Wuden push-pull p tied out transformers, 20watts load, 10 000ohm: plate to plate, speech 15ohms, weight 2 1/4lb boxed, 23/6; Dubilier 500v, .01mfd mica condensers, wire ends, 2/6 dozen; variable 30watt 3000hm slider resistances 1/-; 3watt 1000hm variable pots, 1/6; R.A. sub-standard 100Kcrystals, 10 immersion water heaters 200v, 750watts, U.S.A. make, 7/6; 20watt A.A.E., Ltd., driver transformers, 4/-; Eddystone 1000f split-stator variable condensers 1/6; Bendix RC435 flexible control drives 3/9; 1/6; extra under £21—Jack Porter, Ltd "Radio" 30 31 Colgate St., Worcester, 14410

MAINS TRANSFORMERS, fully interleaved and impregnated; primaries 200-250v 50 p.p.s., screened; drop through type 250-0-250v 60 70ma 6.3v 3a, 5v 2a, 12/11; 350-0-350v 80ma 6.3v 3a 5v 2a 15/9; midget upright type, 2 1/2-3-2 1/2in, 250-0-250v 50ma 6.3v 1.5a, 5v 2a 14/9; also full range of mains and output trans., at bargain prices; Williamson output trans., as specified by author, 57/6; selenium rectifiers 250v 65ma miniature 3/6, 250v 90ma 4/11, 120-0-120v 100ma 1/9, 120-0-120v 40ma 1/3, 60v 100ma (Bridge) 1/9, 60v 40ma (Bridge) 1/3, 12v 1 1/2 H.W. C.T. 1/3 ea., 12/- doz; receiver chassis, 16 ewg, drilled aluminium, 10.5-2in, 3/3, 11-2in, 2 1/2in 3/9, 12-R-2 1/2in 4/6, 16-R-2 1/2in 5/6, 20-R-2 1/2in 6/11; special offer, amplifier chassis 16 1/4-10 1/2-3 1/2in drilled aluminium with black crackle finish, 5/6; electrolytics, can 8-R-8mfd 40v 2 1/1, 16-16mfd 450v 3/9, 8-16mfd 450v 3/3; tubular wire ends, 1d; before you order elsewhere it will pay you to send for our full component and valve list of bargains; special list for trade; all brand new guaranteed goods; c.w.o. or c.o.d over £1, postage extra under £2.—Radio Supply Co., 15, Queen Square, Leeds, 2.

NEW S.T.C. selenium rectifiers largest 1 1/2in range from stock in Great Britain; a makers' latest products; not surplus; H4/100 E.H.T. for VR97, 18/6; H4/200 for "W.W." Televisor 29/- p.f.; H.W. rects., 16v 3/4 6/8, 1a 8/-, 2a 9/6, 3a 16/6, all p. 6d, 4a 18/-, 6a 22/6, 7a 2d, 30v 1a 12/-, 2a 16/-, 4a 21/-, 6a 36/6, 48v 2a 21/-, 4a 35/-, 6a 51/-, 100v 2a 34/6, 4a 65/-, all p. 1/-; H.D. H.W. 7 1/2in sq. cooling fins, 16v 5a 21/6, 10a 24/6, 30v 5a 35/-, 8a 38/6, 48v 2a 26/-, 5a 48/-, 8a 54/-, all p. 1/-; Full: ware bridge conn. rects., 17v 1.5a 12/1, 2a 15/6, 2.5a 20/6, 3a 21/6, 4a 25/-, 5a 27/-, 6a 29/6, 33v 3/4 18/6, 1a 21/3, 1.5a 28/6, 2a 29/6, 3a 35/-, 4a 42/-, 5a 43/6, all p. 10d, 54v 1.5a 39/-, 2a 47/6, 4a 65/-, 100v 1.5a 72/-, all p. 1/-; H.D. type with 7 1/2in cooling fins, 17v 6a 27/-, 10a 43/8, 12a 72/-, 20a 80/-, 33v 6a 64/-, 10a 71/-, 12a 124/6, 20a 140/-, 54v 6a 90/-, 10a 100/-, 72v 10a 130/-, 100v 10a 190/-, all p. 1/4; industrial type funnel cooled, 17v 12a 76/-, 20a 87/-, 30a 122/-, 50a 188/-, 33v 6a 69/-, 30v 10a 80/-, 33v 12a 124/-, 20a 144/-, 54v 6a 92/-, 10a 108/-, 72v 6a 114/-, 10a 136/-, 100v 6a 160/-, 10a 192/-, all p. 1/6; S.T.C. rectifiers for wave type chargers, fitted in 5 mins, no alterations to wiring; complete w rking chargers 2-12v 4a with H.D. trans., sliding res., fuse and ammeter and mains lead, in b.k. crackle finish, louvered steel case, wt., 25lb £5/10, del. free; also 2a, 4a 5a 6a kits; terms, c.w.o. or proforma invoice; c.o.d. over £1 on post goods only; wholesale and retail.

T. W. PEARCE, 66, Gt. Percy St., London, W.C.1, on Pentonville Rd., between Kings Cross and Angel, Sat 17 yards. (1018)

### MAINS TRANSFORMERS, FULLY INTERLEAVED, SCREENED AND IMPREGNATED ALL PRIMARIES ARE 200/250 v.

Half Shrouded

HS63. Output 250/0/250v. 60 m/a. 6.3v. at 3 amps. 5v. at 2 amps.....	15/6
HS40. Windings as above. 4v. at 4 amps. 4v. at 2 amps.....	15/6
Output	
HS2. 250/0/250v. 80 m/a.....	17/6
HS30. 300/0/300v. 80 m/a.....	17/6
HS3. 350/0/350v. 80 m/a.....	17/6
HS2X. 250/0/250v. 100 m/a.....	19/6
HS30X. 300/0/300v. 100 m/a.....	19/6
HS3X. 350/0/350v. 100 m/a.....	19/6

Fully Shrouded

Output	
FS2. 250/0/250v. 80 m/a.....	19/6
FS30. 300/0/300 v. 80 m/a.....	19/6
FS3. 350/0/350v. 80 m/a.....	19/6
FS2X. 250/0/250v. 100 m/a.....	21/6
FS30X. 300/0/300v. 100 m/a.....	21/6
FS3X. 350/0/350v. 100 m/a.....	21/6
All the above have 6.3-4-0v. at 4 amps. 5-4-0v. at 2 amps.	
FS43. Output, 425/0/425v. 200 m/a. 6.3v. 4 amps. C.T. 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded.....	42/6
FS50. Output, 450/0/450v. 250 m/a. 6.3v. 2 amps. C.T., 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded.....	62/6
F30X. Output, 300/0/300v. 80 m/a. 6.3v. 7 amps. 5v. 2 amps. Framed, Flying leads.....	26/6
F35X. Output, 350/0/350v. 250 m/a. 6.3v. 6 amps, 4v. 3 amps, 0-2-6.3v. 2 amps. Fully shrouded.....	59/6

### FILAMENT TRANSFORMERS

F4. Output, 4v. 2 amps.....	7/6
F6. Output, 6.3v. 2 amp.....	7/6
F12. Output, 12.6v. tapped 6.3 v. at 3 amps.....	15/6
F24. Output 24v. tapped 12v. at 3 amps. F12 and F24 framed with Flying Lead:	21/6
FU6. Output, 0-2-4-5-6.3v. at 2 amp.	9/-
F29. Output, 0-2-4-5-6.3v. at 4 amps.	15/-
FU6 and F29 clamped with Flying Leads	
FU5. Output, 6.3v. at 10 amps. 5v. at 10 amps, 12.6v. at 5 amps., 10v. at 5 amps.....	31/6
F6/4. Output, Four at 6.3v. tapped at 5v. at 5 amps. per winding, giving by suitable series and parallel connections 24v at 5 amp.; 20v. at 5 amp.; 18v. at 5 amp.; 15v. at 5 amp.; 12.6v. at 10 amp.; 10v. at 10 amp.; 6.3v. at 20 amp. 5v. at 20 amp. ...	47/6
F5 and F6/4 framed with Flying Leads	

### OUTPUT TRANSFORMERS

MOPI. Ratios 26, 46, 56, 66, 90, 120-1 50 m/a. max. current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel and clamped, each.....	5/-
OPI. Midget Power Pentode, ratios 30, 60, 90-1.40 m/a. Secondary 2/3 ohms. each.....	3/2
OP2. Midget Pentode, ratios 45-1, Secondary 2/3 ohms, 40 m/a. per doz.	33/-
OPI10. 10/15 watts output, 20 ratios on Full and Half primary.....	16/3
OP30. 30 watts output 20 ratios on Full and Half primary.....	23/9
Williamson's O.P. Transformer to Author's specification.....	£3/12/6
HS6. Output 250/3/250v. 80 m/a. 6.3v. 6 amps. C.T. 5v. 3 amps. For receiver R1355 Half shrouded.....	24/6
HS150. Output 350/0/350v. 150 m/a. 6.3v. 3 amps. C.T., 5v. 3 amps. Half shrouded.....	25/9
FS6. Output 250/0/250v. 100 m/a., 6.3v. 6 amps. C.T., 5v. 3 amps. Half shrouded.....	25/9
FS120. Output 350/0/350v. 120 m/a. 6.3v. 2 amps. C.T., 6.3v. 2 amps. C.T. 5v. 3 amp. Fully shrouded.....	27/6
The above have inputs of 200/250v. C.W.O. (add 1/- in £ for carriage), all order over £2 carriage paid.	

**H. ASHWORTH (Det.) W.W.)**  
673 GT. HORTON RD., BRADFORD, YORKS

# HAPPY XMAS

If you use any of the following

## AMPLIFIERS

- Leak "Point One," £25/15/-.
- Sound Sales "Tonemaster," £17/10/-.
- Vortexion "Stereophonic," 36½ Gns
- Williamson "New Version," £25/10/-.

## SPEAKERS

- Tannoy "Dual Concentric."
- Barker 148a.
- Goodmans 12 and 22.
- Also Matched pairs with crossover unit covering 25-16,000 cycles, £14/17/6.

## PICK-UPS

- Leak Dynamic, Acos GP20, RNW, Decca, Connoisseur, Brierley, Wilkins & Wright Coil.
- Also Radio Feeder Units, Tone Control Units and Speaker Cabinets.

Call and hear them at :-

**HOLLEY'S RADIO STORES**  
285, CAMBERWELL RD., S.E.5

'Phone : RODney 4988

# CHASSIS!

Build radios the easy way and save money! Our range of completely prefabricated chassis are punched for all components. These—and our unique Construction Sheets and Tuning Units—enable anyone to build a variety of domestic receivers with the sure knowledge that failure is impossible!

- Examples :
- 5 v. prefabricated chassis, size 12in. x 9in. x 2½in. .... 10/6
  - "Easy-as-A.B.C." Construction Sheets, per set .... 3/6
  - No. 1 Tuning Unit (comprising model 30 3 waveband superhet, coil pack, pr. "MM" I.F.T.'s, 8in. x 6in. dial and 2-gang condenser—the whole aligned and sealed) .... 48/6 inc.

leaving only valves and small components to complete a factory designed receiver.

- 6 v. prefabricated chassis, size 12in. x 9in. x 2½in. .... 10/6
- Construction Sheets .... 3/6
- No. 2 Tuning Unit (comprising model 40 3-waveband superhet, coil pack with R.F. stage, pair of "MM" I.F.T.'s, 8in. x 6in. dial and 3-gang condenser—the whole aligned and sealed) .... 76/9 inc.

leaving only valves and small components to complete a factory designed receiver, whose performance has been acclaimed second to none.

Send 1/- for your copy of the "Home Constructor's Handbook" for all the "gen" on how to construct these, and many other, receivers and amplifiers, etc. All standard radio lines in stock at current prices. So send us your enquiry or order for special attention.

**RODING LABORATORIES,**  
(Mail Order Dept.)  
70 LORD AVENUE, ILFORD, ESSEX

## COMPONENTS—SECOND-HAND, SURPLUS

ARMOUR and U.S. Navy w.de frequency range wire recorders. Details s.a.e.: 1,000 kc/s xials, boxed, brand new, 50/-; TR9 battery receivers, coverage 6-9 mc/s, complete with 6 2-volt valves, 15/-; m.vinc coil headphones 3/6 m/c microphones 2/6; type 18 amp fier unit, complete with 2 EP36, 2 EB33, 2 EL32, transformers, etc., 17/3; brand new blower motors, input 12-24 volts, 8/5; 19 set varometers, containing westcoaters resistors, condensers, coils, etc., 2/4; 6-volt vibrators, 4-p.n. 3/6; 12-volt 2/6; 1,000 mid 25-volt working electrolytics, U.S. manufacture, 4/6.—Haynsons, 14, St. Mary's, Bedford, W.1. 5668. (0012

## WANTED, EXCHANGE, ETC.

TAYLOR 75A or any accurate universal test meter.—Box 564. (4547

FINE wires in large quantities only, must be new and perfect material

L. E. SIMMONDS, Ltd., 8a, Byron Rd., Harrow, Tel. Harrow 2524 and 0135. (3661

VO winding machines.—S.T.S., Ltd., 29/299, High St., Croydon, Tel. 4670. (3111

WANTED, surplus reays and push-button units, any condition, large or small quantities; highest prices paid.—Box 8485. (3532

WE buy top prices for used test equipment, all types.—University Radio, Ltd., 22, Lisie St., London, W.C.2. Tel. Ger. 4447 and Ger 1582. (19592

AMERICAN radio and aircraft equipment of all types wanted.—Write for details or send list of Wilflo Products, Ltd., 222, Gorbals St., Glasgow. (14562

WANTED, all kinds of laboratory test equipment, standard signal generators, bridges, oscilloscopes, "Q" meters, etc; send price and details to:—

HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779. (10037

WESTINGHOUSE rectifiers, 1ma, W.1, J.50 and other types, large or small quantities bought for cash.—Ivali, 37, Furnival Ave., Slough, Bucks. (4513

STRATTON & Co. Ltd., West Heath, Birmingham 31, wish to acquire an Eddystone two-wave short wave receiver with mass panel manufactured in 1925/27; they also invite offers of other early Eddystone receivers for museum purposes. (14503

WE buy for cash, new, used, radio, electrical equipment all types; specially wanted radios, radograms, test equipment, motors, charts, recording gear, etc.—If you want to sell at the maximum price, call, write or phone to University Radio, Ltd., 22, Lisie St., Leicester So., W.C.2. Ger. 4447. (14503

## REPAIRS AND SERVICE

MAINS transformers rewind new transformers to any specification.

MOTOR rewinds and complete overhauls; first-class workmanship; fully guaranteed.

F.M. ELECTRIC Co. Ltd., Pottery Bldgs Warser Gate Nottingham, Est. 1917. Tel. 3855

REWINDS and conversions to mains and output trans., p.c.-ups, fields, etc., from 4.6 N.L. Rewinds, 4, Brecknock Rd., N.7. (45993

LOUDSPEAKER repairs, British, American, any make, moderate prices.—Singer Speakers, 12, Pembroke St., London, N.1. Terminus 4355. (13307

MAIN and output transformers rewind to any pattern or specification, return post service.—H. Pughe, Radio Rewind Service, Brithdir, Nr. Dolgellau, N. Wales. (3243

MAINS transformers rewind or constructed to any specification; prompt delivery.—Bede Transformer Co., Ltd., Bedesway Bede Trading Estate, Jarrow. (3117

MAINS transformers rewind or constructed to any specification, prompt deliveries.—Avon Transformer Co., 20, Heath Terrace, Leamington Spa, Warwick. (4643

REPAIRS to moving coil speakers, cone coils fitted, field rewind or altered; speaker transformers, clock coils rewind; guaranteed satisfaction; prompt service.

L.S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting London, S.W.17, Balham 2359. (4523

ALL types of ammeters, voltmeters, Avcs, etc., repaired; quick, efficient service, estimates free.—Donvin Instrument Co., 91, Princes' Rd., London, W.11, Tel. Park 4469. (4323

ALL types of receivers and programs repaired; difficult sets a speciality; liberal discount to the small trader.—E. W. Shack's, High St., Harlington, Haves M'ddx. (14137

REWIND service which duplicates or modifies as required; transformers, loudspeakers, etc.; prompt returns.—Raidel Services, 49, Lr. Addiscombe Rd., Croydon, Cro. 6537. (4523

ELECTRICAL measuring instruments of every make repaired and standardised.—The Electrical Instrument Repair Service, 329 Kiburn Lane, London, W.9, Tel. Lad. 4165. (3715

REPAIRS, E.H.T., mains and O.P. transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification; all work fully guaranteed.

WILLEDEN TRANSFORMER Co., Ltd., 29, Balmoral Rd., N.W.2, Tel. No. Willeden 2476. "SERVICE" with a smile.—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cord.—F.R.I., Ltd., 22, Howland St., W.1, Museum 5675. (1575

RADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs; armatures, F.H.P. motors, vac. units, portable tools, etc., good deliveries.—139, Goldhurst Terrace, N.W.6, Mal 6133. (19925

# LABORATORY Test Equipment.

MARCONI INSTRUMENTS equipment, reconditioned a new.

## SIGNAL GENERATORS

- Type 144G ..... £80 0
- Type 144F ..... £65 0
- Type 390F ..... £45 0
- Type 517E ..... £42 0

## VALVE VOLTMETER Type

- TF.428A ..... £40 0

## OUTPUT METER Type TF.340

- ..... £31 0

## MISCELLANEOUS EQUIPMENT

COSSOR Oscilloscope Type 339, New ..... £45 0

COSSOR Ganging Oscilloscope Type 343, New ..... £19 0

WEE MEGARAS, 500 volt. Evershed & Vignoles, complete with leather case and instruction book. New ..... £6 17

VARIACS, 2 kVA, 0-270 v., Type 103R ..... £14 0

VARIACS, 2 kVA, 0-130 v., Type 100Q ..... £14 0

VARIACS, 500 VA, 0-270 v., Type 200CMH ..... £5 10

VARIACS, 500 VA., 0-130 v., Type 200C ..... £5 10

WAVEMETERS by RCA, Type TE.149, Frequency range 200 Kc. to 30 Mc/s. by harmonics. Directly calibrated dial from 2.5 to 5 Mc/s. Scale length 9 feet. Absolute accuracy 0.02%. Crystal accuracy 0.005%. Supplied with instruction book, spare valves, components, etc., in fitted transit case. New... £9 0

ALSO in stock, we have other wave-meters up to 10.0 Mc/s. Constant voltage transformers. Precision attenuators, etc. Send for lists.

## HATFIELD INSTRUMENTS

175, UXBRIDGE ROAD, HANWELL, LONDON, W.7 Telephone : EALing 0779.

# WE DON'T

supply anything Ex-Government

ALL BRAND NEW GOODS

— fully guaranteed —

## GARRARD

- R.C.65, AC/DC AUTO-CHANGER. Mixed records ..... £20 15 0
- R.C.65, A.C. AUTO-CHANGER. Mixed records ..... £15 13 6
- U5, AC/DC Motor with turntable, pick up and auto stop ..... £12 9 2
- All the above are fitted with Magnetic head. With Decca Hi-Fi head extra ..... £2 2 0
- With Connoisseur head and transformer extra ..... £2 13 8

## COLLARO

- R.C.49, A.C. AUTO-CHANGER. Mixed records, Crystal head ..... £14 6 8
- R.C.500, A.C. AUTO-CHANGER, non-mixer, Crystal head ..... £10 15 0
- MOTOR AND TURNTABLE with Magnetic pick-up and auto stop, A.C. .... £9 13 6
- AC/DC ..... £12 18 10
- MOTOR AND TURNTABLE only, A.C. .... £5 18 4
- AC/DC ..... £9 5 6

## E.M.I./MARCONI

A.C. AUTO-CHANGER non-mix, Hi-Fi head complete with transformer £10 10 8

## TAYLOR TEST GEAR

The entire range by this famous maker is now available on Hire Purchase. S.A.E. for catalogue and terms.

## AVO TEST GEAR

AVO 7 Leather cases ..... £2 2 6

Are the largest actual stockists of Avo meters in England. S.A.E. for catalogue and price list.

All items can be supplied C.O.D. up to 15lbs. in weight. Otherwise Cash with order please.

Special attention to Overseas orders which are free of purchase tax.

## MODERN ELECTRICS LTD.

164, Charing Cross Road, London, W.C.2. Telephone : Temple Bar 7587.

# NEWS

from

## A. C. BARKER

The back room has been very active during past months preparing a further step towards our objective **NATURAL REPRODUCTION.**

We believe 148a is justly placed first amongst existing speakers for its qualities of brilliant clear-cut wide range sound, and at its price of 15 gns. offers the most economical high quality reproducer obtainable.

Now, for the connoisseur who owns first-class equipment and like ourselves, ever seeks the absolute standard, we introduce the



MODEL 150

This new unit retains our standard 12 $\frac{1}{2}$ in. frame and patented coil construction, consisting of an aluminium former over which is wound a thin layer of special pure latex and a 15-ohm aluminium coil.

The cone is of linen moulded to shape with one continuous spiral corrugation of increasing amplitude from apex to rim—a fresh extension of our original basic patent which gives a markedly flatter, smoother output.

Work with many impregnants has led to the adoption of a recent ICI product, which is now also used for the 148a.

Finally there is a new magnet system giving over 17,500  $\lambda$  lines, a 25 per cent. advance on the 148a.

**THE RESULT?** Well, according to our friends and critics who have heard it, the 150 stands ahead of contemporary achievement by a margin which makes its price of 18 gns. seem absurdly modest.

The 148a is, of course, still the best speaker for most people.

**BCM/AADU,**  
LONDON, W.C.1.

### REPAIRS AND SERVICE

**LOUDSPEAKERS** and transformers rewound cones replaced, prompt service.—Dodds, Radio Service, 131a Hurst St., Oxford. 13550  
**"STURDY"** rewinds, mains transformers, chokes, and fields, first-class work, prompt, delivers and satisfaction guaranteed.—Sturdy Electric Co., Ltd., D.pton, Newcastle-on-Tyne. 12450

**A** **SECOND**-to-none rewind service, reliable neat, return of post service, your television requirements promptly executed, EHT, LHT and heater transformers; stamp for quotations.—R. E. F., 137a, Ashton Rd., Oldham. 3519

**24**-HOUR service, 6 months guarantee, any transformer rewind, mains outputs and i.f.s., etc.; all types of new transf., etc. supplied to specification; business heading or service card for trade prices.—Majestic Windng Co., 180 Windham Rd., Bournemouth.

**L.T.P.** rewind service, all rewinds are layer wound, vacuum impregnated, pressure tested at 2,000volts and guaranteed for three months, 48 hours notice.—Enquiries London Transformer Products, Ltd., L.T.P. Works Cobhold Estate N.W.10, Tel. Willesden 6486

**METROPOLITAN RADIO SERVICE** for re-winds mains and e.h.t. transformers, re-chokes and field coils; delivery 3-5 days; new transformers designed and manufactured singly or in quantities.—Metropolitan Radio Service Company, 1021, Finchley Rd., London, N.W.11. Tel. Speedwell 300.

**REWINDS.**—Send your "burn outs" to be rewound; no technical data wanted; post transformer, etc., labelled with your name, address, and marked "rewind"; our windings are double wound, interleaved and impregnated.—Southern Trade Services, Ltd., 297-299, High St., Croydon, Tel. 4870. 3110

**NATIONAL RADIO SERVICE & TELEVISION** Co., radio and television development engineers; high quality receivers and amplifiers built to specification and modernised, repairs to all makes of receivers, transformers, coils, armatures rewound, loudspeaker cones renewed, television aerial installations, conversion, etc.—63, High St., St. John's Wood, N.W.8. Primrose 6725. 12671

### WORK WANTED

**WE** make wireless and radiogram cabinets for home and export, immediate delivery.—Radiac, Ltd., 88/90, Caledonian Rd., London, N.1. Tel. Terminus 7447. 18025

**D**RAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications, sub-contracting work of this nature undertaken.

**DRAWING & TRACING**, Ltd., 456a, Ewell Rd., T. Worthy, Surbiton, Tel. Elmbridge 7406. 16183

**FIRST-CLASS** transformers and chokes manufactured, stock lines available; also special manufacturers' components made to specifications; armatures and fields wound and motors assembled.—Avis & Baggs, Ltd., 140-141, Friar St., Reading, Berks. 12715

### MISCELLANEOUS

**"W.W."** Jan. 1945 to date; offers.—BM/CKH, London, W.C.1. 14546

**WIRELESS WORLD**, 1951 to 1944, offers.—Phone Wallington 3528 after 6 p.m. 14501

**90** Wireless Worlds covering 1940/47 for sale. Offers to 14, Old Slade Lane, Iver. 14531

**"Q.S.L.s"** and "G.P.O." approved low books. samples free.—Atkinson Bros., printers. 3082

**E**LLAND **C**ABINET for E.E. Telesvisor, mahogany console, £5/10.—Manor Cottage, Manor Road, Reigate. 14570

**E**LECTRONIC voltage stabilizers; process timers; 100 microampere power relays, etc.; enquiries invited.

**BRITISH ELECTRONIC INDUSTRIES**, 303-305, Burdett Road, London, E.14. 10031

**WIRELESS WORLD**, January, 1937 to December, 1947, four missing; good condition, offers.—Wilson, 26, Kings Park Ave., Glasgow.

**NEON** indicator lamps and holders, low voltage, 4 3 for 4/9; 15/6 doz; selenium barrier light cells from 6/6.—Lucas, 22, Hengrove Rd., Bristol. 14532

**E**XPOSURE meter components, light cell 6/6, meter movement 8/-, moulded case 9/-, assembly instructions and conversion scale reproductions 3/6.—P. R. Products, 78, Repton Rd., Bristol, 4. 14054

**T**ELEVISION mast sections, heavy steel tubular, 8ft 9in long, 3in dia 9in sockets; reach any height you require; 11/9 each plus carr.; sample 16/- carr. paid.—Foundation Oil Co., Ltd., 8, Queen Hill, Norwich. 14462

**S**PECIAL receivers, test gear, electronic apparatus, experimental and design work.—If you have a problem which needs expert handling, write in first instance to J. Mort, B.Sc., A.M.I.E.E., BCM/HIFIDEL, London, W.C.1.

**M**INE detector units with 114 valves, etc., 17/6; brown bakelite cabinets, 13in x 7in x 5 $\frac{1}{2}$ in, 15/-; 75w 230/110v autos, 10/6; all guaranteed; many other bargains; postage and lists free.—Electrad Radio, 64, Gt. Victoria St., Belfast. 14558

**E**X-GOVERNMENT steel instrument cases, copper plated and finished battleship grey, size 23in long, 10in high and 8in deep, excellent condition, 12/6 with carrying handles, 10/- less carrying handles, plus 2/6 packing and carriage Envaland and Wales.—Weatherheads, Bletchley, Bucks. 14297



### THE "FLUXITE QUINS" AT WORK

"What's on the tele to-night?"

Let's hope it'll be something bright.

Well, what d'you know

Just ooh! In a row!

Get cracking! We're needing FLUXITE!

See that FLUXITE is always by you — in the house — garage — workshop — wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all Iron-mongers—in tins, 10d., 1/6 & 3/-.

**TO CYCLISTS!** Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 2/6, or filled, 3/6



ALL MECHANICS WILL HAVE

# FLUXITE

IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT" SOLDERING and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d. each.

**FLUXITE LTD.**

(Dept. W.W.), Barmendsey Street, S.E.1

# M. WATTS & Co.

8, BAKER STREET,  
WEYBRIDGE : SURREY

Telephone—Weybridge 2542.

## TELEVISION COMPONENTS.

The following components were made by a famous manufacturer especially for Television. They are not ex-Government transformers made for another purpose.

### Blocking Oscillator Transformers.

Line. Ratio 2.2 to 1.

Frame. Ratio 3 to 1.

Price 6/- each. 11/- a pair.

Line Output Transformers. Ratio 6 to 1.

Price 8/6 each.

## MAINS TRANSFORMERS.

Large transformers. Ideal for T.V. or amplifiers. Both types have normal 50 cycle primaries tapped for 200 to 250 volts.

Type A. 400-0-400 volts 300 mA., 6.3 v. 4a., 5 v. 3 a., 4 v. 3 a., 2 v. 1 a., 2 v. 1 a. Wire ends. Price £2.

Type B. 280-0-280 volts. 180 mA., 6.3 v. 9 a., 5 v. 3 a. Tag board. Service rating. Price £2.

## PAPER CONDENSERS.

Brand new. By famous maker. 8 mfd., 500 volt working at 140 deg. F. Price 4/- each.

For details of many other lines send for our full list.

## BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE.  
3,000 STANDARD STOCK SIZES

No Quantity too Small List on application

London: H. R. LLET & Co., Ltd. Liverpool: 3 Chesham Place S.W.1. Kirkby Estate, SLOane 3463 SIMONSWOOD 3271/3

# HILL & CHURCHILL LTD.

BOOKSELLERS

## SWANAGE, DORSET

Available from stock

Schelkorf—“Electromagnetic Waves”	42/-
Fink—“Principles of Television Engineering”	33/-
C. J. Smith—“Intermediate Physics”	28/-
Starr—“Electric Circuits and Wave Filters”	25/-
Hudson—“An Introduction to Electronics”	15/-
A. R. R. L.—“The Radio Amateur’s Handbook”	16/6
Williams—“Thermionic Valve Circuits”	12/6
Cann—“Wireless Coils, Chokes and Transformers”	6/-
S. T. C.—“Reference Data for Radio Engineer”	5/-

Postage Extra

CATALOGUE ON APPLICATION

## MISCELLANEOUS

WALNUT radiogram and television cabinets, units, for few only; stamp details.

—Walters, 5C1, Hale End Rd., E.4. 14442  
DESIGNATION and valve-type waterslide transfers, black and silver, linX<sup>1</sup>/<sub>2</sub> in. 44 different titles, 66 transfers in all; most useful for those special jobs. —Send P.O. 2/6 an s.a.e. to Walter Co. Parrish, Surrey. 16154

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A. G. Engraving 19a, Windmill Rd., London, S.W.18. Brass, bronze, erinoid, perspex, dials; one knob or repetition equally entertained. (10034

FLUORESCENT lighting. 20w 5ft white enamel-ened curved trough reflector fitting, with complete ballast unit, tested 210-240v a.c. and 5ft tube. £4 only ex-works, or despatched less tube, 67/6. —Malden Transformer Supplies, 200-202, Cambridge Rd., Norbiton, Surrey.

COPPER wires enamelled, tinned Litz, cotton silk covered, all sizes; B screws, nuts washers, soldering tins, eyelets; ebonite and laminated baizeite panels, tubes, coil formers. Tinned rod; headphones, flexes etc.; latest radio publications; full range available; list s.a.e. trade supplies. Post Radio Supplies, 35, Bourne Gardens, London, E.4. 11354

HANOVA Senior sun lamp as new, 200-250v, £17/10. Avometer d.c. model good condition. £8/10; grinder, polisher, Runbaken, a.c./d.c., high speed for tools, etc. (cost £7/10). £4/5; signal lamp, powerful beam or automatic selectable morse symbols A to Z, very compact, 27/6; compass 7in de luxe, boxed, 57/6. —East Reading Radio, 1, Rupert St., Reading, Tel 61635

core cable rubber insulated, 9/012 colour coded rubber covered, 35 - 100 yards; 7-core ditto, but cellulose covered, 45/- 10 yards; stamp samples; Beiling Lee type 5-pin plugs and sockets, 80 - per 100; 7-pin ditto, 100/- per 100; high grade panel lights, frosted domed red glass crystal, pated bezel, M.B.C., 80/- per 100, £14 for 400; Ceramic EF, 50 holders, 25/- per 100; VCR, 97 holders, 18/- per dozen; throat mikes, 15/- per dozen. —J McMillan, 5, Oakhill Rd., Bristol, 8. 14372

## SITUATIONS VACANT

Vacancies advertised are restricted to persons or employments excepted from the provisions of the Control of Emigration Order, 1941

## GOVERNMENT OF IRAQ.

FIRST assistant radio engineer required by Basrah Port Directorate for one year in first instance. Salary I.D.60 rising to I.D.80 a month. High cost of living allowance of between I.D.8 and I.D.12 a month, according to dependants, is payable on salary of I.D.80 a month (Iraqi Dinar; 1 equals £1). Provident fund. Free passage. Candidates must possess P.M.G. 1st class certificate in wireless telegraphy and be A.M. (Brit.) I.R.E., or hold City and Guilds Final Certificate in radio communication. They must have had practical experience of commercial wireless transmitters and receivers and electrical equipment and preferably some experience at a large civil airport. Apply at once by letter, stating age, whether married or single and full particulars of qualifications and experience and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M/N/25005 (3B) on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. 14535

## CROWN Agents for the Colonies.

WIRELESS station superintendent required by the Gov. Coast Government post and telegraphs department for one tour of 18 to 24 months in first instance; commencing salary (including overseas pay) according to qualifications and experience in scale £660 rising to £800 a year on agreement with prospect of permanency, or alternatively on temporary contract terms in scale £720, rising to £860 a year, with gratuity of £25 for each completed period of three months' service; outfit allowance £60, free passages; candidature, under 40, must have had practical experience of modern radio transmitters and receivers and be capable of taking charge (under an engineer) of the installation and maintenance of H.F. and V.H.F. stations and the training of African staff; knowledge of teleprinter maintenance or light diesel generating sets an advantage. —Apply at once by letter, stating age, whether married or single, and full particulars of qualifications and experience, and mentioning this paper, to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M/N/25006 (3B) on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. 14536

## BUSH RADIO, Ltd.—Applications are invited from engineers and assistants for positions in the following branches:

- (a) COMMUNICATIONS and Domestic radio development.
  - (b) TELEVISION Development.
  - (c) TEST Gear Development.
- APPLY in writing giving age, qualifications, details of experience, salary required, etc., to The Personnel Manager, Bush Radio, Ltd., Power Rd Chiswick, W.4. 14388

TELEVISION engineer required for factory, production and test, south of London, write, stating age, experience and salary expected to Box 646. 14588

# RADIO CONSTRUCTORS' MECCA

The new, super COLLARO RC48 A.C. MIXED AUTO-GRAVE in black and chrome with hi-0 crystal pick-up, repeat mesh. Immediate despatch, price £14/8/8, carr. paid.

The COLLARO AC47 centre-drive GRAM. MOTOR and 12in. non-magnetic turntable, ideal for moving-coil pickups, etc., variable speed. Immediate despatch, price £5/18/4, carr. paid.

COLLARO AC504 GRAMOPHONE UNIT—Motor, Pick-up (latest magnetic type) and Autotop, fixed speed, 10in. turntable. Immediate despatch, price £5/3/2, carr. paid.

COLLARO AC506 GRAMOPHONE UNIT—no 504, but centre-drive, variable speed and crystal pick-up. Immediate despatch, price £8, carr. paid.

The new MARCONI AC100 AUTOCHANGER, plays 10 records (8 of 12in. (not mixed), fitted high fidelity lightweight pick-up. Price, complete with pick-up transformer and pocket of "Columbia 99" needles, £10/15/-. Immediate despatch.

4-watt QUALITY AMPLIFIER, single 6V6 output with special neg. feedback circuit giving equivalent to push-pull results. Pick-up and Tuner inputs, 3 ohm. output (other output to order). Price £5/19/6. Complete Kit, £5/10/-. Black crackle case 15/- extra. Immediate delivery.

12-watt QUALITY AMPLIFIER, push-pull 6V6 output, special neg. feedback circuit, gram., mike and tuner inputs; 3, 7.5 and 15 ohm. output. Price 10/6/2. Complete Kit, £9. Available in black crackle cabinet £2 extra. Immediate delivery.

No. 1 HIGH-QUALITY TUNER. T.R.F. circuit, infinite impedance detector, M. & L. waves, excellent reports from "Williamson" and "Look 1" users. Price £5. Immediate delivery. Complete Kit £4/10/-. No. 2. SUPERHET TUNER, L., M. & S. waves, special "quality" hand-wrought elaborate full-vision dial assembly. Price £8/10/-. Immediate delivery. Complete Kit, £7/10/-.

TERMS: C.W.O. or C.O.D. any amount. "W.W." BARGAIN LIST 2½d.

**Northern Radio Services,**  
102 PARKHILL ROAD, LONDON, N.W.3

# TRANSFORMERS & COILS TO SPECIFICATION.

MANUFACTURED OR REWOUND  
Filter Coils + 1% a Speciality.

**JOHN FACTOR LTD.**  
9-11 EAST STREET, TORQUAY, DEVON.  
Phone: Torquay 2162

# LOCKWOOD

makers of  
**Fine Cabinets**

and woodwork of every description for the Radio and allied trades  
**LOCKWOOD & COMPANY**  
Oswan's Road, Harrow, Middlesex. Byron 3704

## B. & H. RADIO East Street, Darlington

Loud Speaker Bass & Treble Separator  
Complete kit of parts and instructions. Enables speakers of different impedance to be used for bass and treble and also gives control of amount of treble relative to bass. Cross over 1000 c.p.s. £1 9 6

Scratch Filter ..... 15 0  
Gives a very marked reduction of scratch level without serious effect on treble response.

Variable Selectivity I.F. Transformer  
465 Kc/s. Gives three degrees of selectivity. Circuit diagram of high fidelity receiver included.  
Per pair ..... £1 0 0

Aerial Circuit I.F. Filter 465 Kc/s ..... 3 9



100 kcs.  
QUARTZ  
CRYSTAL  
UNIT -  
Type  
Q5/100



for Secondary Frequency Standards

- ★ Accuracy better than 0.01%.
- ★ Temperature coefficient 2 parts in a million per degree Centigrade temperature change.
- ★ Gold electrodes applied by cathodic sputtering direct to the faces of the crystal, giving permanence of calibration.
- ★ Simple single valve circuit gives strong harmonics at 100 kcs. intervals up to 20 Mcs.
- ★ Octal based mount o compact dimensions.

Full details of the Q5/100 including circuit are contained in our leaflet Q1. Send stamp to-day for your copy.

THE QUARTZ CRYSTAL Co., Ltd.

63-71 Kingdon Road,  
New Malden, Surrey  
Telephone: MALden 0334

TELEVISION CONSTRUCTORS!

E.E. Televisor Demonstrated Daily  
MIDLAND CONSTRUCTORS ETC.  
ARE INVITED TO SEND FOR OUR COMPLETE  
COMPONENT LIST AND TAKE ADVANTAGE  
OF OUR

PROMPT POSTAL SERVICE

J. T. FILMER

MAYPOLE ESTATE,  
SEXLEY, KENT.  
Tel. Bexleyheath 7257



TYPE G (BTG BASE)

ENQUIRIES FOR ALL TYPES INVITED

BROOKES CRYSTALS LTD.

10 STOCKWELL STREET,  
GREENWICH, LONDON. S.E.10.  
PHONE GRE. 1828. CABLE. XTALS LONDON.

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark.



Designed for Wireless Assembly  
and Maintenance.

- Working temperature reached in 1 1/2 mins., consumption 25 watts weight 2 1/2 ozs.
- Supplied in voltage ranges from 6.7v to 230/250v
- 3/8" diam Copper B.c. (standard model) 22/6
- 1/2" diam. Cooper B.c. 25/-
- Replacement Unir B.c. Elements available
- British and Foreign patents

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED  
Alliance House, Caxton Street, London, S.W.1  
Write or Phone: WHI. 0030.

SITUATIONS VACANT  
HIS Majesty's Colonial Service. Gold Coast.

VACANCIES exist for wireless engineers in the posts and telegraphs department, to install and maintain police wireless network and to train police staff; the appointments are on probation for permanent and pensionable employment, or in the case of candidates over 40 years of age on contract/gratuity terms; the salary scale is £660-£1,300 per annum, including expatriation pay; point of entry depending on war service, qualifications and experience; a temporary non-pensionable cost of living allowance is payable on basic salaries below £640 per annum. CANDIDATES must be Associate Members of the Institution of Electrical Engineers or ho.d. equivalent qualifications giving exemption from Sections A and B of the associateship examination and have had at least two years' experience with an industrial concern engaged in the manufacture of electronic or radio equipment; experience of planning, installation and operation in either (a) H.F. radio-telephone and radio-teletype circuits, or (b) V.H.F. radio links. H.F. and V.H.F. direction finding.

PARTLY furnished Government quarters will be provided, if available, at a rent of £60, £75 or £90 per annum, according to salary; free first-class passages are provided for the officer and wife on first appointment and on leave; income tax is at local rates which are very much lower than those in the United Kingdom; the tour of service is from 12-24 months; leave on full salary is granted at the rate of 7 days per month after normal tours of 18 months.

INTENDING candidates should write forthwith for form of application and further particulars to the Director of Recruitment, Colonial Office, Sanctuary Buildings, Great Smith St., S.W.1, quoting Reference No. 27323/5 and giving brief details of age, qualifications and experience.

MINISTRY OF SUPPLY invites applications for an established post as principal scientific officer at the Royal Aircraft Establishment, Farnborough, Hants.

CANDIDATES should be at least 31, and should possess a good honours degree in physics with good mathematical knowledge and research experience on radar display digital and analogue computers, pulse and pulse-coded communications.

SALARY assessed on age, qualifications and experience, within the range £910 to £1,177 (men) or £790 to £1,016 (women), plus F.S.S.U. benefits.

WRITE, quoting A264/49/EW, to Technical and Scientific Register, 10 York House, Kingsway, London, W.C.2, for application form, which should be returned completed by 20th December 1949.

IN any grade or capacity there is usually a need for the right man at Sound Sales Limited; applicants should state age, details of experience, salary or wage required, by letter; testimonials should not be forwarded with inquiry.

THE Managing Director, Sound Sales Ltd., West Farmham, Surrey. (10054)

SERVICE mechanic required for leading hearing aid firm, West End; must be fully qualified and experienced in miniature L.F. amplifiers; state age, experience, and salary required to—Box A2936, Haddons, Salisbury Square, Fleet Street, E.C.4. (4512)

REQUIRED for electronic laboratory development work, young engineer with laboratory experiences, to assist in the development of equipment associated with magnetic recording; commercial experience an asset but not essential; apply in first instance by letter to:

THERMIONIC PRODUCTS, Ltd., Development Laboratories 7, Pratt Walk, London, S.E.11.

TELEVISION service engineers required by manufacturers to carry out servicing, instruct in service technique and take charge of servicing workshops; previous experience essential; must be able to drive; location Birmingham only quoting Ref. 711 to Box 8391 (4506)

YOUNG man with B.Sc. or Higher National Certificate in electrical engineering required, preferably with some knowledge of measurements to carry out electrical and magnetic measurements on all kinds of special alloys and the application thereof.—Full particulars to Box 537. (4540)

WORKS manager required for small electronics works in west London engaged in the design and construction of individual indicator and signalling systems; knowledge of stock control and buying desirable.—Box No. B.R. 2/0 Brockle, Has'am & Co., 231, Strand, London W.C.2. (4501)

RADIO engineers required for positions in the development laboratory of large manufacturer in East London area; applicants need not have academic qualifications but must have not less than three years' experience in radio receiver development laboratory; state full details to—Box 490. (4594)

TOLL pant superintendent (Brazil)—The advertiser wishes to thank those applicants who answered the advertisement for this position under Box W W 407 at 191 Gresham House, F.C.2, and would state that those applicants whose qualifications were considered suitable have now been advised. (4523)

SOFTL INDUSTRIES Ltd., have a few vacancies in the main industrial areas for first-class service engineers operating from their own homes; there are responsible and well-paid posts with transport provided by the company—Applications, with full details, to Service Manager, Langley Park, Slough, Bucks. (4516)

SUPACOILS

OFFER

Model 30 Coil Pack.—The 3-waveband superhet pack with adjustable iron cored coils and trimmers for absolute accuracy in padding and tracking. This pack is gaining more and more favour among experienced engineers and amateurs for its sound design, high quality workmanship and high sensitivity and selectivity..... 21/- or 24/- fully aligned.

Model 40 Coil Pack.—Similar to the Model 30 but with RF stage..... 42/- or 47/- fully aligned.

Model 30 Tuning Unit.—This is now one of the most popular units for easy and efficient superhet construction. It consists of a Model 30 coil pack, pair "MM" I.F. transformers, 2-gang condenser and attractive dial. Components are 48/6 aligned together as a unit in an actual receiver, and sealed. No further alignment is required.

Model 40 Tuning Unit.—Similar to above with provision for R.F. stage 76/9 FREE. A Free Copy of the enormously successful HOME CONSTRUCTOR'S HANDBOOK will be given to every purchaser. Or a copy can be obtained for 1/- from

SUPACOILS (Mail Order Office)  
98, Greenway Avenue, London, E.17

MIDCO AMPLIFIERS  
5 WATTS £5 10'  
COMPLETE WITH VALVES  
OTHER MODELS FROM £4.00 ON  
THREE GUARANTEES INVOLVED  
NEWCOMEN R  
WELLINGBOROUGH

YOUR METER DAMAGED ?

Leading Electrical Instrument Repairers to the Industry.

Repairs by skilled craftsmen to all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Test meters Electrical Thermometers, boards; Instruments, synchronous Clocks, etc. Quick deliveries—for use by ultimate and directly—Instrument by registered post to

L. GLASER  
SCIENTIFIC & ELECTRICAL INSTRUMENT REPAIRERS  
341 CITY ROAD, E.C.1  
Tel. Terminus 2489

HIGH-CLASS DESIGN.  
VACUUM-IMPREGNATED  
TRANSFORMERS BY  
MILLETT & HOLDEN LTD.,  
BIRCHAM WORKS, BIRCHAM ROAD,  
SOUTHEND-ON-SEA, Essex.  
Southend 68409



**DE LUXE INSTRUMENT CASE**




12in. x 8in. x 5in. in 18G. Steel with Radiused Top Corners, Louvred Back and fitted with Chromium Plated 4in. Handle and four P.V.C. feet. Finished in Black, Grey or Brown Wrinkle Enamel. 18G. steel front panel..... £1 1 0  
 With front panel in 16G Aluminium £1 2 0  
 Small steel chassis with angle brackets to fit. Black..... 4 6  
 Ditto, in 16G. Aluminium, self-colour 6 0  
 Postage and Packing 1/6.  
 Carriage Paid on Orders over £2.  
 Illustrated Lists on request.  
 Trade Terms on application.  
**REOSOUND ENGINEERING & ELECTRICAL COMPANY, "Reosound Works," Colleshill Road, Sutton Coldfield.**  
 Grams: Reosound, Sutton Coldfield.  
 Tel.: SUT. 4085.

**MASTER CONTACTOR WINDING CLOCK MOVEMENT**

**10/6**

Post Free

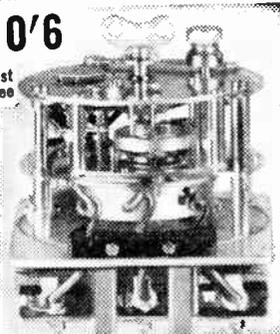

**SIGNALLING LAMPS**

**5/6 POST FREE S.B.C.**

**FITTING.** With Hinged Hardwood Case.

Send stamps for descriptive leaflets of other Bargains.

**UNIVERSAL BAZAARS (M/c) Ltd.,**

81, Brown Street, Manchester 2. DEA 5079

**SITUATIONS VACANT**

**TELEVISION**/Radio service engineer, fully experienced, permanent position with excellent opportunities; full particulars and salary required to—W. J. Elliott, Ltd., Howardsgate, Welwyn Garden City, Herts. 14513  
**R**ADIO Service engineer, age 25-35 preferred, fully qualified, smart appearance and accustomed to carrying out installation in the home; full knowledge of all H.M.V. and Marconiphone instruments essential.—Apply, stating experience and salary required, to Manager, His Master's Voice, 363 Oxford Street, W.1. 14563

**SENIOR** technical sales representative with experience of communications systems utilizing VHF, HF, or microwave equipments; technical qualifications not essential but sales experience and knowledge of operating and installing communications equipments required; state full details including age and salary required to—Box 491. 14496

**R**ADIO service engineer required for provincial firm of high standing, must be of first-class technical standard, and have considerable practical experience, knowledge of television an advantage; wage according to ability and confirmed after one month's probation.—Apply Messrs. Barnes & Avis, Ltd., 140 141, Friar St., Reading, Pers. 14492

**D**EVELOPMENT engineers with industrial design experience in light engineering required to work near Esher, Surrey; good salaries and excellent working conditions are offered to qualified men; the work is of an important and interesting character with ample opportunities for advancement in a new organization.—Please reply to Box 494. 14514

**A**PPLICATIONS invited from college-trained engineers with radar experience covering centimetre aerials, wave guides and receivers; circuit and general electronic experience also essential; salary offered will be from £550 upwards according to qualifications and experience.—Write giving full particulars, quoting Ref. 733, to Box 499. 14529

**E**LECTRONIC engineer aged 25/30 required for work in inspection department, qualifications: Higher National Certificate standard with production experience of radio engineering, knowledge of A.I.D. work in this branch would be an advantage.—Please write giving full details to Personnel Dept., E.M.I. Engineering Development Ltd., 87th Rd., Hayes, Middx. 14483

**E**LECTRONIC research and development engineers required; first class honours degree or equivalent preferred; vacancies for senior engineers with industrial experience and for juniors; interesting new projects; pension scheme; apply stating age, qualifications, experience and salary required to: Personnel Manager, Fairey Aviation Company, Ltd., Hayes, Middx. 14350

**SENIOR** and junior development engineers and draughtsmen for radio, radar, electronics, speakers, etc.; service engineers radio, television, radar, P.A. equipment; wiremen (skilled and semi-skilled) radio, instrument, radio; H.F. repairs, testers, inspectors, radio, television, radar; other positions vacant, consult.—Technical Employment Agency, 179, Clapham Rd., S.W.9 (London 3497). 14443

**E**XPERIENCED estimators are required by a large manufacturer of radio and allied equipment situated in East London area; applicants should be practically trained men with estimating experience either, of radio components and intricate mass-produced mechanisms, or of telephone and telecommunications equipment; state full details including age and salary required to—Box 499. 14493

**LEADING** component manufacturers situated in Southern Scotland, require chief inspector possessing drive and initiative; applicants must be sound technicians with qualifications at least equivalent to inter-B.Sc., and with experience of modern testing technique; duties would include dealing with government inspection departments; initial training period in London; write stating experience and salary required to—Box 493. 14511

**BRITISH INSULATED CABLES** Ltd. require a physicist for the development of sound recording media; candidates should be experienced in physical, electromagnetic and electroacoustic measurements and be capable of carrying out development work on own initiative; permanent position; salary according to age and qualifications.—Apply writing to Staff Officer, B.I.C.C., Ltd., Prescot, Lancs. 14494

**E. K. COLE** Ltd., (Electronics Division) Malmesbury, Wilts, invite applications for the post of assembly shop charge hand (male), used to Government contract material and equipment and with a knowledge of training female labour, good disciplinarian; this post qualifies for entry into the pension scheme after a period of service.—Forms of application obtainable from Personnel Manager, Ekco Works, Malmesbury Wilts. 14494

**A**PPLICATIONS are invited by leading manufacturers of radio equipment for the following vacancies: (a) Test and inspection of radio, television and wireless equipment; (b) maintenance of equipment; (c) training of personnel with experience in the following: (i) testing and repair of radio and television sets; (ii) repair of British

**THE BRITISH NATIONAL RADIO SCHOOL**  
 ESTD. 1940

**National Recovery**  
 Our CONTRIBUTION, REDUCED FEES  
 Yours IMPROVED EFFICIENCY  
 INDIVIDUAL COACHING BY POST  
 in  
**RADIO, TELECOMMUNICATIONS, RADAR · PHYSICS · MATHS.**

All examinations C. & G., P.M.G. Brit. I.R.E.

We can arrange for most examinations to be taken anywhere, aboard ship or furthestmost outpost. Free Booklet from

**STUDIES DIRECTOR**  
**BRITISH NATIONAL RADIO SCHOOL**  
 66, ADDISCOMBE ROAD, CROYDON  
 Phone: Addiscombe 3341

**R.F. E.H.T. SUPPLIES**

Type	Price
Type SH 17/50 2-5.5kV	£3-15-0
Coil only	£1-2-6
Type SH 8/50 5-8 kV	£4-15-0
Coil only	£1-10-0
Type SH 30/50 10-12.5 kV	£10-10-0
Coil only	£3-10-0

Type SH 4/50 15-25 kV  
 50 kV unit  
 Price on application  
**TRANS-LIN**  
**ST. GERS LTD.**  
**40N. ON ROAD,**  
**SHT-BIDGE, S.W.3**

**YOU SHOULD HAVE A NEW TAYLOR**  
 \* \* \* \* \*  
 We can supply the latest Taylor Test-Equipment, and take your used Equipment in part exchange. Balance by cash or hire purchase.  
 Write, phone or send your gear along for inspection and offer.  
 \* \* \* \* \*  
**UNIVERSITY RADIO LTD.**  
 22 LISLE ST. Tel. GERRARD 4447 & 582

**TELEVISION RECEIVERS SCANNING and FOCUS COILS TIME BASE COMPONENTS and JKV EHT. RF. UNITS and TRANSFORMERS**  
  
 Publications post free  
**HAYNES RADIO LTD.**  
 Queensway, Enfield.

**INSTRUMENT WIRE ENAMELLED, D.C.C. SILK COVERED.** ETC. all sizes from 10 s.w.g. to 42 s.w.g. in stock.  
**INSULATING MATERIALS.** Empire cloth, leatheroid, paxolin, etc.  
 Send S.A.E. for list to  
**STAN. HOLT,**  
 349, HIGH ST. SMETHWICK, STAFFS  
 Telephone WOODGATE 3789

**‘Radiospares’ Quality Parts**

**THE SERVICE ENGINEER'S FIRST CHOICE**

If you've not heard our best... can't delay heard a record at its best... person... regret that the further with appointment will improve.  
**LOW & COLE**  
 2, Leazes Avenue, Leazes, Essex.  
 Tel: - Sea, Essex.  
 Don't forget our special and Rawind... ing Service—It's equal and cheaper.

**SITUATIONS VACANT**  
**GARDNERS RADIO** require qualified chief inspector for transformer test department. Applicant should be conversant with Admiralty, M.O.S. and A.I.D. procedure.—Gardners Radio, Ltd., Somerset, Christchurch, Hants. 14612

**GARDNERS RADIO** require experienced transformer assembly supervisors. Applicant is required to have had previous experience in the manufacture of all types of radio transformers.—Gardners Radio Ltd., Somerset, Christchurch, Hants. 14611

**LABORATORY** engineer required, holding City and Guilds Final or Higher National Certificate, experienced in work of general radio and television design; applicants should also be proficient at executive work.—Write, stating age, experience and salary required to box 596. 14534

**PYE, Ltd., Cambridge**, have vacancies for experienced engineers in the television and radio communications divisions of their engineering department, vacancies also exist for senior and junior draughtsmen, salaries in accordance with qualifications and experience.—Applications will close to Employment Dept., Pye, Ltd., Cambridge. 14619

**DRUGHTSMAN** required for radio technical drawing work, ability to produce first-class drawings from rough notes is essential, good prospects, permanency and superannuation benefits.—Apply stating age, qualifications, experience and salary required to the Secretary, Wireless Telegraph Co., Ltd., New St., Chelmsford. 14591

**ADVERTISING** manager wanted for the monthly technical journal, 'Electrica', engineering and electronics, must have experience of advertising, applicants having acquaintance with products of manufacturers and knowledge of electronic industry will be given preference.—Send full particulars of experience and age to: Staff Director, Morgan Brothers (Publishers), Ltd., 2d Essex St., Strand, W.C.2. 14326

**MARCONI'S WIRELESS TELEGRAPH COMPANY** require for their works at Chelmsford a senior engineer to take charge of the research and development of domestic television receivers; applicants who must have had extensive experience in this class of work and a capacity for leading a development team should write giving full particulars quoting Ref. 296 to Central Personnel Services, English Electric Co., Ltd., 24/50, Gillingham St., Westminster, S.W.1. 14502

**HIGH-CLASS** technical representative required by electronic, television and radio accessory manufacturers, must be accustomed to dealing direct with high level technical executives in commercial concerns and Government departments and capable of continuing and expanding its present volume; excellent salary, commission and expenses allowance.—Write, stating age, position held (in chronological order), technical qualifications, etc. to Box 499. 14534

**A FEW** unusual opportunities occur in the laboratories of Ferguson Radio Corporation, Ltd., for senior and junior development engineers for work on domestic radio and television receivers and electronic equipment for Government services; applicants must possess a university degree, preferably in engineering, or equivalent qualifications; designer-draughtsmen are also required for similar work; previous experience essential; excellent prospects for keen, enthusiastic men.—Write with full details to Chief Engineer, Ferguson Radio Corporation, Ltd., Great Cambridge Rd., Enfield. 14530

**PAN-AMERICAN** World Airways have immediate openings at London Airport for three radio, electrical mechanics. Applicants must have good background in electrical and radio theory, at least four years' experience in the maintenance of airborne equipment and components, be prepared to work shifts both indoors and outdoors in all seasons and all weather. Be prepared to perform electrical and related mechanical aircraft maintenance in addition to radio maintenance. Experience of American-type equipment helpful. Desired age is 21 to 27 years. Character references required. Starting salary is £8/14 per 48-hour week. All applications should be made in writing to Maintenance Dept., Pan-American World Airways, London Airport, Feltham, Middlesex. 14575

**SITUATIONS WANTED**  
**EXPERIENCED** radio engineer, A.M.I.E.E. (134) eight yrs. with Admiralty, requires post in West of England, Devon or Somerset.—Box 438. 14492

**DEVELOPMENT** engineer, 11 years present post, seeks chance, commercial and M.O.S. VHF FM communication receiver development components.—Box 497. 14477

**REPAIRING**  
 Course, theory, rate...

**“CHRISTMAS CRACKERS”**  
 Presented by  
**RADIO UNLIMITED**  
 Elm Road, London E.17  
 Telephone: KcY 4813  
 Universal Main Microgram Amplifier, 6 watt, push pull output. Separate Vol. and Tone controls for Mic. and Gram. Tapset output 2, 3, 15 Ohms. Housed in black crackle case with Chrome handle. 9 Gas. Carriage paid.  
 A.C. Mains Amplifier Chassis, 4 valve, 41 watts output. Vol. and Tone controls, etc. Complete with valves and P.M. speaker. £5 10/6. Carriage paid.  
 Really first-class unit. 35/-, Post Free.  
 Superbet Chassis 5 valve, 3 valves and 8/6bed speaker. Very limited supplies at £9 18/6, inc. tax.  
 Folding Microphone Stand. Heavy Chrome. Less than half list price. 29/6. Post Free.

Our 1950 fully illustrated Catalogue is now Available  
 3/- Post Free  
**BERRY'S**  
 (SHORT WAVE) LTD  
 25, HIGH HOLBORN, LONDON, W.C.1

**ELECTRONICS**  
**DUPELEY**  
 LTD.  
 CRANMER AV. EALING, W.13.  
 Transformer and Coil Manufacturers to the Trade  
 Telephone EALING 568

**mathematics**  
 Our new Home-Study Course make maths really interesting and easy to learn. Write for booklet to Dept. W.  
**T. & C. RADIO COLLEGE,**  
 KING EDWARD AVE., AYLESBURY.


**“Globe-King” MARVEL**  
 (REGD) IN MINIATURE  
**SHORT-WAVE RADIO KIT**  
 Probably the smallest one valve Short-Wave Radio receiver in the world using standard parts with Bandspread tuning device.  
 “Magnificent performance”... vide testimonials British Isles and Abroad. Built and designed to precision standards, complete kit costs only 49/6—write today for descriptive catalogue.  
**JOHNSONS (RADIO) MACCLESFIELD**  
 (SPECIALISTS) CHESHIRE (ENG)

**POST RADIO SUPPLIES**  
 OFFER EX STOCK  
**COPPER INSTRUMENT WIRE.**  
 ENAMELLED, TINNED, LITZ.  
 COTTON AND SILK COVERED  
 Most gauges available.  
 B.A. SCREWS, NUTS, WASHERS  
 soldering tags eyelets and r.vets.  
 EBONITE AND BAKELITE PANELS,  
 TUFNOL ROD PAXOLIN TYPE COIL FORMER AND TUBES, ALL DIAMETERS.  
 Latest Radio Publications.  
 Send stamped, addressed envelope for comprehensive lists. Trade supplied.

**POST RADIO SUPPLIES**  
 The Gardens London E.4  
 Phone: CL:50.0 4668

# TELERADIO.

Radiogram Equipment

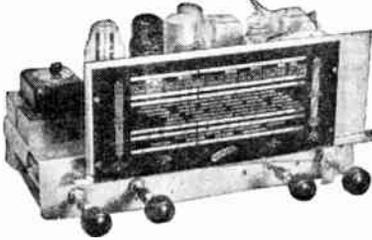

**MODEL A70.** 6 valve all-wave modern superhet chassis with tuning indicator, tone control and radiogram switch. The ideal replacement chassis. £12 12 0d. including Tax, plus valves, £3 3 0d.

**MODEL 70 TU.** As above but as 3 valve tuning unit feeding model 77 amplifier £8 0 0d. plus 34/10d. Purchase Tax.

**MODEL 77.** 4 valve push pull amplifier with 2 6V6 fed by phase inverter. Approx. 8 watts output £7 5 0d.

AVAILABLE AS KIT OF PARTS } Blueprints 4/-

Send for leaflet to:

**THE TELERADIO CO.,**  
157, Fore St., Edmonton, N.18

## SOUND-POWERED TELEPHONES



Ex-Admiralty, unused, famous British make. Require NO batteries, transformers or amplifiers. Just connect two together for instant clear speech over any length of line. Detach one earpiece and use as desk or wall mounting telephone; or leave as twin headset and breast microphone (original purpose) for outdoors, T.V. aerial installation on roof, etc., with both hands free. Countless uses in home, sick-room, office, shop, garage, farm, boat, etc. NOT a kit of oddments to assemble, but two excellent ready to use Telephones for 77/- post paid, with instructions and diagrams for bell circuits. Instant despatch.

Bulk enquiries invited

**WIRELESS SUPPLIES UNLIMITED**  
264-266 OLD CHR. ST. CHURCH RD.  
BOURNEMOUTH - HANTS.  
Telegrams: Limitrad, Bournemouth

### TUITION

**WIRELESS** officer's attendance and "Radio-certs" postal course—App'y Manager, The Wireless School Manor Gdns., London, N.7.

**WIRELESS**, land, sea and air; students, both sexes, age 14 upwards, trained for interesting appointments in all branches of radio; low fees, boarders accepted; 2d stamp for pros.—Wireless College, Colwyn Bay. [0018]

**AIR** and radio officers courses.—The 1st class P.M.G. Certificate assures early and well-paid employment; obtain it with the help of our special day-time course commencing January, 1950.

**WRITE** for full details to E.M.I. Institutes, Ltd., Dept. W.W., 43, Grove Park Rd., London, W.4 Chiswick 4417-8. [0001]

**A.M.I.Mech.E., A.M.I.E.E., City and Guilds,** etc., on "No Pass—No Fee" terms, over 95% successes; for details of exams, and courses in all branches of engineering, building, etc., write for 102-page handbook—free.—B.I.E.T. (Dept. 227B), 17, Stratford Place, London, W.1.

**TELEVISION** postal course for radio trades Examination Board's diploma, also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitter licence.—App'y British School of Telegraphy Ltd., 178, Capham Rd., London, S.W.9. (40 years' experience in radio engineering in wireless telegraphy and allied sub. etc.). [2588]

**RADIO ENGINEERING SCHOOL** Air Service Training, Hambro, Southampton, provides the best full-time training for responsible positions in industry or aviation; students coached on C & G, later, and Final Certs. in radio or tele-communications; graduation of Brit. R.E. & M.C. radio engineer licence, and for air and marine radio officers' licences; full details from the Commandant. [2260]

**TELEVISION.**—Special evening class for members of the radio trade commences 6.30 p.m. Tuesday, 15th November, dealing fully with T.V. theory and practical fault finding. Late entries accepted up to end of Nov. Class subject to complete course in six months.—For particulars, apply The Principal, The Wireless Telegraph College, 25, John Dalton St., Manchester, B.a. 7501. [4590]

**TELEVISION.**—The Gothic Television School specialises solely in training in television. It offers courses: university degrees and/or corporate membership of professional institutions and is also providing individually to postal-course students to ensure complete and thorough training. Principals, M.B.E., B.Sc., M.Brit. R.E., education committee members, etc. Courses assume no previous television knowledge and provide guaranteed training for Brit. R.E. and R.T.E.B. examinations. Numerous well-known companies have adopted the School's Basic Television Course as standard television training for their staffs. Moderate fees. Details from Gothic Television School, 13, North Avenue, London, W.13. [0051]

### TRADE MARKS

**THE** trade mark Converte registered under No. 652213 in respect of battery eliminator units was assigned on March 24, 1949 by Ampion (1932), Limited, of 230, Tottenham Court Rd., London, W.1 to London & Provincial Factors, Limited, of 230, Tottenham Court Rd., London, W.1, without the goodwill of the business in which it was then in use. [4522]

### BOOKS INSTRUCTIONS, ETC.

**FRITH RADIOCRAFT, Ltd.** offer:—

**"VIEWMASTER"** complete television assembly instructions by W. I. Fack (joint author "Electronic Engineering" Home Built Television). 8 full-size prints showing wiring in easy stages using standard parts by famous makers; large 32-page booklet giving the most complete "gen" ever offered to the home constructor. London version from stock—Midland version expected shortly. Price only 5/- + 6d. post. Early delivery of all components—price list free on request. Brimar Radio Valve & Tube Manual. The latest edition of this popular Valve Manual giving complete up-to-date list of all types manufactured by Standard Telephones & Cables together with relevant valve data, operating characteristics, etc., including metal rectifiers, Brimstors Substituted Lissis Formulae, Circuits, Fouvalents, etc., 4/- + 6d. post.

**FRITH RADIOCRAFT, Ltd.,** 69-71, Chancery Gate, Leicester. [0024]

**WEBB'S** 1948 radio map of world, new multi-colour printing, with up-to-date call signs and fresh information on heavy air power. 4/6 post 6d on linen on rollers 11/6, post 9d—Webb's Radio, 1-4 Soho St., W.1. Gerrard 2087

**"HOME Constructors' Handbook,"** the latest edition of this famous handbook containing hints and complete constructional and servicing notes and complete catalogue, is now available at only 1/6, mail order only.

**SPACOL'S,** 93 Greenway Ave., London, E.17

**"PERSONAL Portables,"** a new book by Edwin N. Bradley, is the first to describe a whole range of miniature personals, including the first-ever all wave personal set, with no theorising or padding; the book is illustrated with circuits, layouts, drilling, constructed loudspeaker-type sets, and costs 2/6 (2/8 posted) from—Dept. W., Bradbooks, Sennen, Penzance, Cornwall. [4507]

# L.R.S.

**For Prompt & Efficient Service**  
CASH OR EASY TERMS

When you purchase on L.R.S. Convenient Terms Formalities are reduced to a Minimum and you deal direct with us from beginning to end.

**—AMSTRONG ALL WAVE CHASSIS—**  
(incl. speaker and output transformer)

**Model EXP/833.** Cash price £18 17 1, or £4 12 0 with order and £2 monthly instalments of 26/-.

**Model RF1033.** Cash price £26 10 0 or £4 12 0 with order and 12 monthly payments of £2 0 0. And other models.

Also available on our Easy Terms

**Goodsell-Williamson Amplifier and Tuner Units**  
**Collaro Radio-Gram Units and Record Changers**

**The Barker Loudspeaker**  
**Goodman's Loudspeakers**  
**Hartley-Turner Loudspeakers**  
**Wharfedale Loudspeakers**

Please let us know your Radio requirements (enclosing 2d stamp) and we shall be pleased to quote.

Personal attention to all enquiries

**THE LONDON RADIO SUPPLY CO.**

Est. 1925

**BALCOMBE SUSSEX**

## "You can rely on us"

**FOR CLEAN COMPONENTS AT COMPETITIVE PRICES**  
**IMMEDIATE DISPATCH**

**MIDGET SUPERHET COIL PACKS**  
MW/LV Size 2 1/2 in. long, 1 1/2 in. deep, 1 1/2 in. high, Type "R" ..... 25/-  
MW/LV Size 2 1/2 in. long, 1 1/2 in. deep, 1 1/2 in. high, Type "S" ..... 25/-  
SW/MW LV Size 3 in. long, 1 1/2 in. deep, 1 1/2 in. high, Type "C" ..... 28/6  
Comprising, from-ringed midget coils, wavechange switch, ceramic trimmers, neatly assembled for one hole fitting. The difficult part of a superhet overcome.  
**PEAKER TRANSFORMERS**  
Super midget for "Persuella" to match D1.92, 834, etc. .... 4/3  
Pendulo output type 55:1 at bargain price for quality ..... 4/6  
Midget mains output transformer ..... 3/9  
All Brand New—Not Ex-Govt.

**LOUDSPEAKERS**  
Celebration 2 1/2 in., 25/6; 3 1/2 in., 10/6; 5 in., with dust cover, 9/9; 4 1/2 in., 12/6, with transformer, 17/6.  
8 in., 16/6, with transformer, 19/6.  
All brand new.

**COILS**  
Wearite "P" Coils 3/- each, full range stocked—Blueprint with data supplied.  
T.R.F. matched pair MW/LV First quality, pair ..... 7/6

**FILAMENT TRANSFORMERS**  
Primary 200-240 v., Secondary 6.3 v., 1.5 a.  
Black crackle finish of small dimensions, standard speaker transformer size ..... 8/6

**TUBULAR CONDENSERS**  
Up to 1 mfd., 6d. each; 5 mfd. 350 v., 1/3; 25 mfd. 25 v., 1/6; Midget 1 mfd. 1 in. x 1 in., 1/-; Metallized, .005 mfd., .001 mfd., .01 mfd., 1/8 each.  
**RESISTORS**  
1 watt, 3d. each; 1 watt, 4d. each; 1 watt, 8d. each.  
**BARGAIN OFFER**  
1 Pole 3 Way Rotary Vaxley type switch, 1/3.

**VIEWMASTER TELEVISION**  
7 notes to print circuits and booklet, 5/-. Components included.

**LIST OF OTHER LINES.**  
Write, phone, or call for:  
Price and Data folder containing Bargain List, 2/4. L.P.P.

**RADIO SERVICING Co.**

444, Wandsworth Road, London, S.W.8


Phone: M4Cauly 4155.

77, 77A, Bus 28, Tram, Wandsworth Rd. S.R. Station. Open till 6.30 p.m.

INDEX TO ADVERTISERS

Acoustical Mfg. Co., Ltd. ....	50	Frith Radiocraft, Ltd. ....	58	Premier Radio Co. ....	10, 11
Adco Products, Ltd. ....	84	Galpins ....	77	Pye, Ltd. ....	11
Aerialite, Ltd. ....	55	Garland Radio ....	68	Quartz Crystal Co., Ltd. ....	94
Airmec Laboratories, Ltd. ....	67	Gea Bros. Radio, Ltd. ....	79	radio Exchange Co. ....	59
Albert Mfg. Co. ....	72	General Electric Co., Ltd. ....	19	radio servicing Co. ....	87
Allan, Richard, Radio, Ltd. ....	26	General Lamination Products, Ltd. ....	32	Radomeques, Ltd. ....	85
Allen Components, Ltd. ....	75	Gaser, L. ....	84	radiospares, Ltd. ....	85
All-Power Transformers, Ltd. ....	50	Goodmans Industries, Ltd. ....	55	radio Unlimited ....	86
Amassador Radio ....	25	Goosier, Ltd. ....	46	Reliance Mfg. Co. (Southwark), Ltd. ....	88
Antiference, Ltd. ....	53	Grampian Reproducers, Ltd. ....	66	Resound Ltd. & Electrical Co. ....	85
Armstrong Wireless & Television Co., Ltd. ....	85	Gray, Arthur, Ltd. ....	62	Reproducers of Amplifiers, Ltd. ....	39
Ashworth, H. ....	79	Hallam, Sleigh & Cheston, Ltd. ....	54	ring Lamp Co. ....	64
Astor Bissellier & Lawrence, Ltd. ....	25	Hartley, H. A., Co., Ltd. ....	72	roving Laboratories ....	80
Automatic Coil Winder & Electrical Equip. Co., Ltd. ....	1	Hatfield Instruments ....	80	Rogers Developments Co. ....	70
A.W.F. Radio Products, Ltd. ....	76	Hazeaurst Designs, Ltd. ....	85	rouet, H., & C., Ltd. ....	82
B. & H. Radio ....	82	Heymann Electronics Laboratories ....	48	ruco Products ....	38
Bakers "Seinurst" Radio ....	46	Henley & W. T., Telegraph Works Co., Ltd. ....	72	Salford Electrical Instruments, Ltd. ....	42
Barber, A. C. ....	81	Hill & Churchill, Ltd. ....	62	Sangamo Weston, Ltd. ....	61
Belling & Lee, Ltd. ....	41	Holley's Radio Stores ....	82	Savage Transformers, Ltd. ....	34
Berrys (Short Wave) Ltd. ....	81	Hoit, Stand ....	86	Schnarr, Erwin ....	30
Biro, S. S., & Sons, Ltd. ....	26	Houkton & Osborne ....	74	Simmons Aerocoseries, Ltd. ....	65
Birmingham Sound Reproducers, Ltd. ....	36	H.P. Radio Services, Ltd. ....	58	simon sound service ....	12
Brerney, J. H. (Gramophones & Recordings), Ltd. ....	34	International Correspondence School, Ltd. ....	60	Smith, G. W. (Radio), Ltd. ....	66
Britain Chas. (Radio), Ltd. ....	50	Johnson, Matthey & Co., Ltd. ....	2	Southey Transformers ....	68
British Institute of Engineering Technology ....	68, 74	Johnsons (radio) ....	86	soel Industries, Ltd. ....	54
British Insulated Callender's Cables, Ltd. ....	11	Kershaw, S. ....	70	sound Sales, Ltd. ....	44
British National Radio School ....	85	Laskey's Radio ....	64	southern radio Supply, Ltd. ....	76
British N.S.F. Co., Ltd. ....	15	Lawrence, G., & Co. ....	64	Sphere Radio, Ltd. ....	68
British Physical Laboratories ....	75	Leak, H. J., & Co., Ltd. ....	64	Standard Radio Components, Ltd. ....	32
Brookes Crystals, Ltd. ....	84	Lewis Radio Co. ....	25	Standard Telephones & Cables, Ltd. ....	39, 47
Brown, S. G., Ltd. ....	24	Loxwood & Co. ....	76	Stearns & Foreman Products, Ltd. ....	5
Buigin, A. F., & Co., Ltd. ....	505	Londen, Ltd. ....	82	stern Radio, Ltd. ....	75
Bull, J., & Sons ....	85	London Central Radio Stores ....	70	Stratton & Co., Ltd. ....	57
Bulkers, Ltd. ....	61	London radio Supply Co. ....	35	Sugden, A. R., & Co. (Engineers), Ltd. ....	65
Candler System Co. ....	22	London Television Co., Ltd., The ....	68	Supacols ....	84
Celestion, Ltd. ....	22	Lowtner Mfg. Co. ....	74	Szymanski, S. ....	20
Charles Amplifiers, Ltd. ....	21	Ludlow & Cole ....	86	T. & C. Radio College ....	86
Chloride Electrical Storage Co., Ltd., The ....	32	Lyons, Claude, Ltd. ....	78	Taylor Electrical Instruments, Ltd. ....	44
Cinema-Television, Ltd. ....	22	Mail Order Supply Co. ....	63	Taylor, Tunncliff (Refractories), Ltd. ....	67
Clydesdale Supply Co., Ltd. ....	53	Marconi Instruments, Ltd. ....	34	Tele-Radio (1945), Ltd. ....	62
Cohen, D. ....	53	Measuring Instruments (Pullin), Ltd. ....	15	Telegraph Condenser Co., Ltd. ....	Cover III
Collaro, Ltd. ....	16	Metro Pex, Ltd. ....	18	Telegraph Construction & Maintenance Co., Ltd., The ....	32
Cosmocord, Ltd. ....	40	Metropolitan Vickers Electrical Co., Ltd. ....	84	Teleradio Co. ....	87
Cossor, A. C., Ltd. ....	6	Midco Amplifiers ....	80	Thermionic Products, Ltd. ....	7
Couphone Radio ....	69	Midland Instrument Co. ....	80	Trix Electrical Co., Ltd. ....	Edit. 501
Coventry Radio ....	70	Millet & Holden, Ltd. ....	80	Truxox Eng. Co., Ltd. ....	4
Davis, Alec., Supplies, Ltd. ....	56	Modern Boos Co. ....	84	Universal Bazaars, Ltd. ....	85
Desoutter Bros., Ltd. ....	23	Modern Electrics, Ltd. ....	87	Universal Electrical Instruments Corpn. ....	56
Duplex Electronics, Ltd. ....	86	M.R. Supplies, Ltd. ....	84	University Radio, Ltd. ....	51, 86
Edison Swan Electric Co., Ltd. ....	27	M.S.S. Recording Co., Ltd. ....	74	Valradio ....	56
Electradix Radios ....	70	Mullard Electronic Products, Ltd. ....	22	View Master ....	24
Electrical Sound & Television Patents, Ltd. ....	63	Multicore Solders, Ltd. ....	56	Vitavox, Ltd. ....	17
Electro Acoustic Developments ....	66	Murphy Radio, Ltd. ....	Cover 13	Voigt Patents, Ltd. ....	68
Electronic Instruments, Ltd. ....	58	Nagard, Ltd. ....	13	Vortexion, Ltd. ....	43
Electronic Precision Equipment ....	66	Northern Radio Services ....	12	Watts, M., & Co. ....	82
Electrosound Supplies Co. ....	49	Oliver Pell Control, Ltd. ....	62	Webb's Radio ....	14
E.M.I. Institutes, Ltd. ....	44, 45	Osmer Radio Products, Ltd. ....	82	Westinghouse Brake & Signal Co., Ltd. ....	20
E.M.I. Sales & Service, Ltd. ....	45	Oxley Developments Co., Ltd. ....	18	Weston Products (L'pool), Ltd. ....	54
Enthoven, H. J., & Sons, Ltd. ....	20	Painton & Co., Ltd. ....	70	Wharfedale Wireless Works ....	63
Erle Resistor, Ltd. ....	31	Park Radio ....	52	Whiteley Electrical Radio Co., Ltd. ....	42
Factor, J., Ltd. ....	82	Partridge Transformers, Ltd. ....	48	Wilco Electronics ....	66
Felicity Gramophone Co. ....	70	Pennine Amplifiers ....	71	Wilson Electric Co. ....	9
Ferranti, Ltd. ....	29	Pifco, Ltd. ....	48	Wimbledon Eng. Co., Ltd. ....	9
Fielden (Electronics), Ltd. ....	14	Post Radio Supplies ....	69	Wireless Instruments (Leeds), Ltd. ....	57
Filmer, J. T. ....	84	Pratts Radio ....	86	Wireless Supplies Unlimited ....	87
Fluxite, Ltd. ....	81			Woden Transformer Co., Ltd. ....	52
French, Cyril, Ltd. ....	80			Wolsey Television, Ltd. ....	88
				Wright & Weaire, Ltd. ....	37

**New! SUPER  
T.V. AERIAL BY  
WOLSEY**

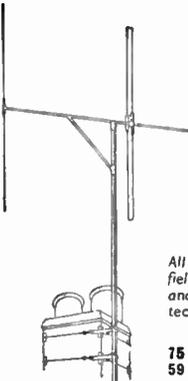


A big success at Radiolympia! An entirely new IN-LINE 3-ELEMENT FOLDED DIPOLE ARRAY giving a gain of 7.5 Dbs. The most advanced aerial for fringe areas or the reduction of severe interference.

All WOLSEY T.V. Aerials are laboratory designed and field tested. Send for Brochure illustrating all outdoor and indoor types, and giving polar diagrams and technical data.

**WOLSEY TELEVISION LTD.**  
75 Gresham Rd., London, S.W.9      BR1ton 8651/2  
59 Soho Hill, Birmingham, 13.      Northern 2762

**POTENTIOMETERS**  
by  
**RELIANCE**

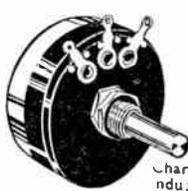

Wire-wound and Composition types. Single, Ganged, Tandem Units.


Characteristics: linear, log., semi-log, non-inductive, etc. Full details on request.

**RELIANCE MFG. CO. (SOUTHWARK), LTD.**  
Sutherland Road Higham Hill, Walthamstow, E.17.  
Telephone: Larkswood 3245

Printed in Great Britain for the Publishers, LIPFEE and SONS LTD., Dorset House, Stamford Street, London, E.C.4, by THE CORNWALL PRESS LTD., Paris Garden, Stamford Street, London, S.E.1. "Wireless World" can be obtained abroad from the following—AUSTRALIA and NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: Imperial News Co.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd.; William Dawson & Sons (S.A.), Ltd. UNITED STATES: The International News Co.
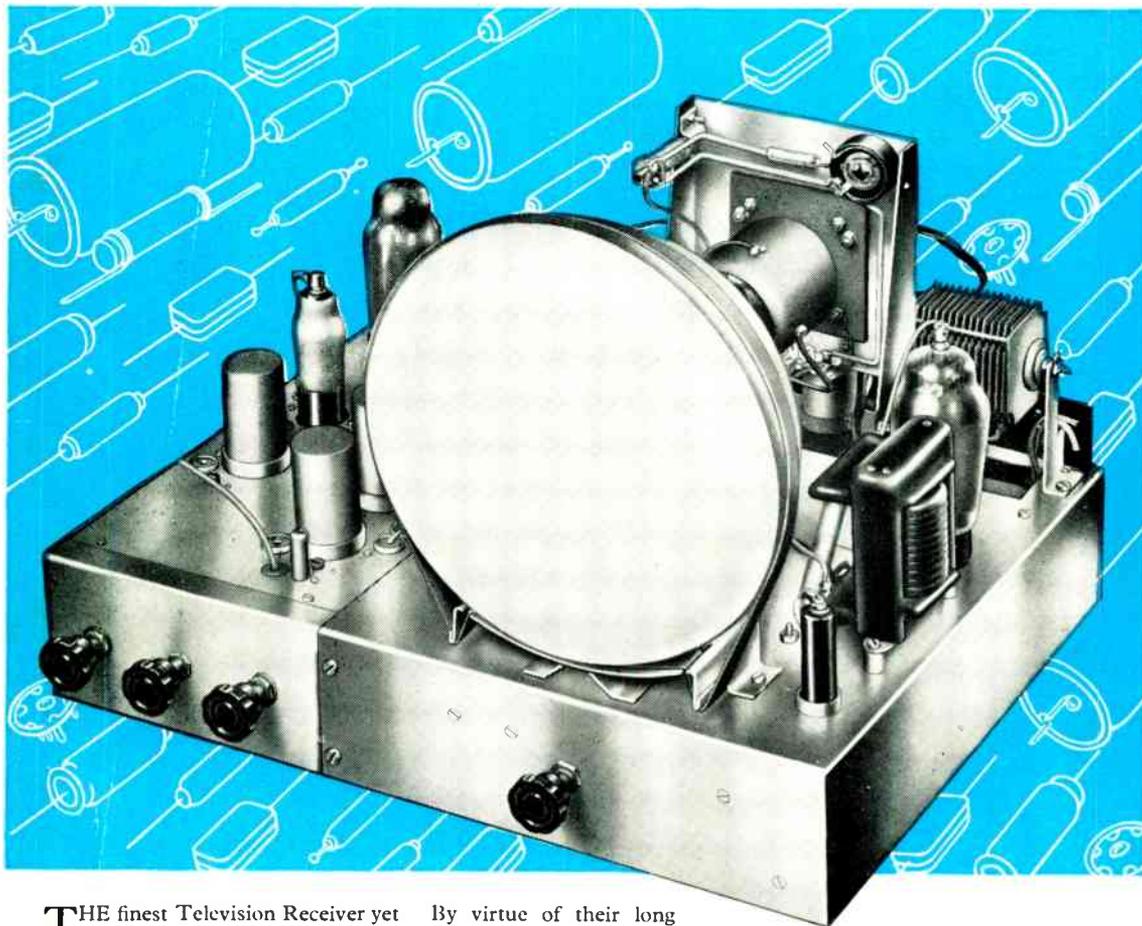
# T.C.C. CAPACITORS

exclusively specified for the "View Master"



THE finest Television Receiver yet designed for the Home Constructor\* uses T.C.C. Capacitors exclusively. The reason is obvious. In any Television circuit capacitors play a vital role. According to their function some must be extremely accurate and stable, others highly resistant to heavy voltage surges. But whatever their function they must all give trouble-free dependable service throughout the life of the Receiver.

By virtue of their long experience and outstanding research facilities T.C.C. can rightly claim to be the logical choice for all capacitor requirements—with a range of types without equal in the industry.

*\* The "View Master" is fully described in a Constructor Envelope containing 8 full size wiring and assembly drawings together with a 32 page booklet profusely illustrated giving much practical information on Television. Copies 5 - each from all Wireless Shops or Newsagents. In case of difficulty direct from us post free 5/6.*



**THE TELEGRAPH CONDENSER CO. LTD.**

RADIO DIVISION

NORTH ACTON · LONDON · W · 3

Telephone. ACORN 0061

## Made in Britain - - - acclaimed by U.S.A. Television Manufacturers

### ERSIN

# Multicore

#### TECHNICAL ADVANTAGES: MULTICORE SOLDER

- Three separate cores of flux eliminate possibility of no flux in a portion of the wire, which may occur in single cored solder. Guaranteed continuity of the flux stream prevents "dry" joints.
- Although there are three cores of flux in Multicore the total percentage of flux to solder is less than many single cored solders.
- Very rapid melting results from the multiple core construction which provides thinner walls of solder than are found in same gauge single cored solder.
- Ability to tin rapidly produces perfect joints with less solder. Greater coverage per pound.


#### ERSIN FLUX

- Ersin Flux is exclusive to Multicore and will not be found in any other solder. It is high grade rosin, homogeneously activated.
- Ersin Flux has a vigorous fluxing action and possesses the non-corrosive and protective feature of the original rosin.
- Soldered joints made with Ersin Flux do not corrode even after prolonged exposure to any degree of humidity. It has been tested under climatic conditions ranging from the Arctic to the Tropics.
- Free from objectionable odour. Non-toxic in use.

Technical information and samples for manufacturers on request


The economy and reliability of Ersin Multicore Solder are preferred by almost all British Television Manufacturers. Pys of Cambridge, have used it exclusively for 10 years.

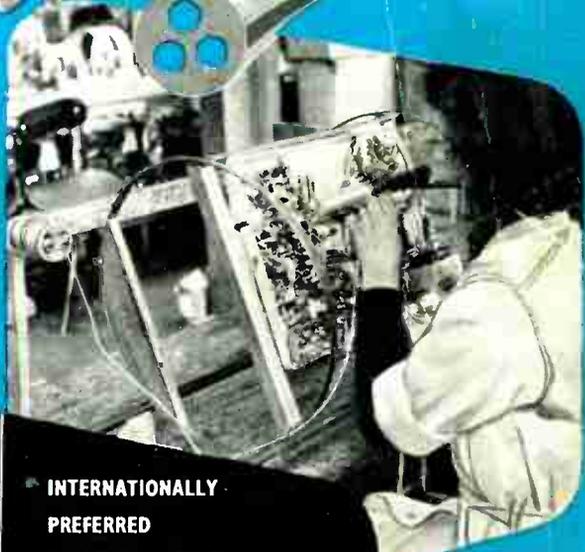One of the 30 U.S.A. Television factories where British made Ersin Multicore Solder is used—the DuMont factory at Newark, U.S.A.



INTERNATIONALLY PREFERRED BY LEADING TELEVISION MANUFACTURERS

The Finest Cored Solder in the World

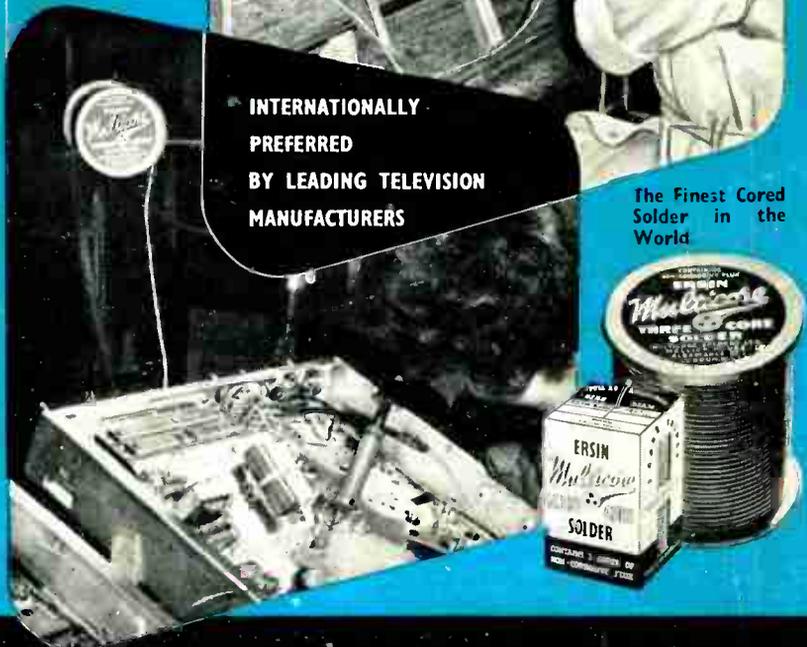

U.S.A. and Canada

### MULTICORE SALES CORP.

164 Duane Street · New York 13, N.Y.

Other territories

### MULTICORE SOLDERS LTD.

Mellier House, Albemarle Street, London, W.1, England