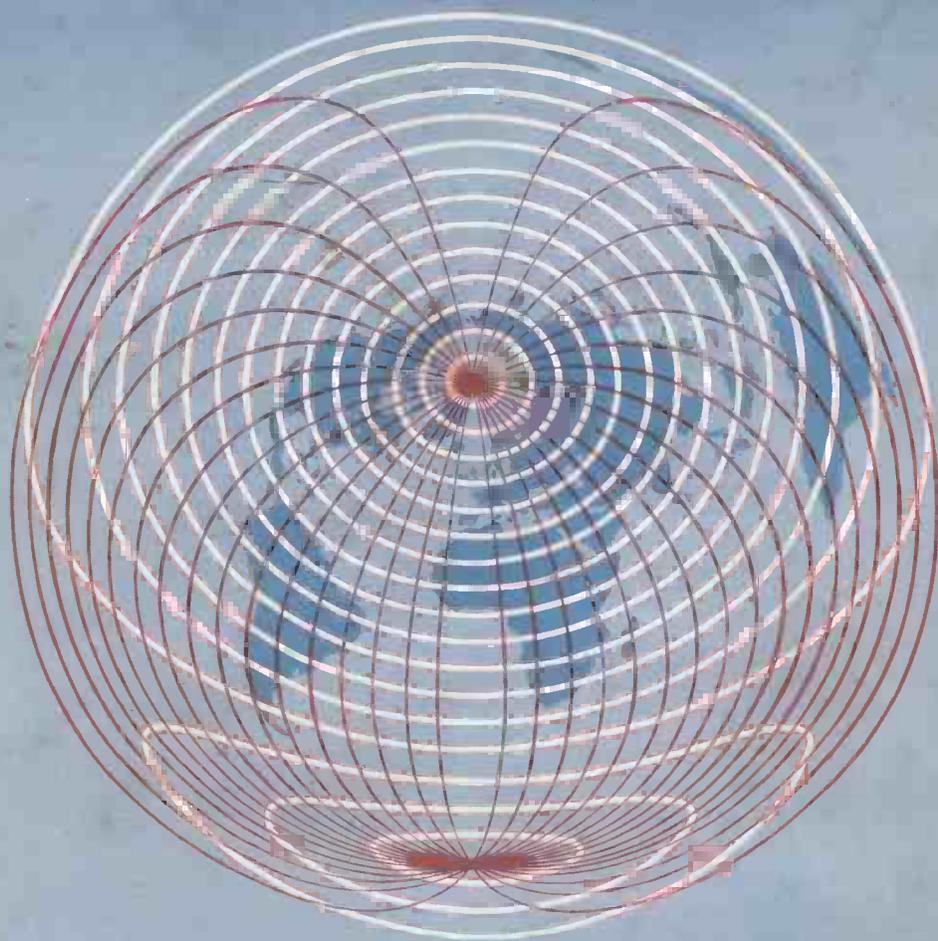


# Wireless World

RADIO AND ELECTRONICS




**Vol LVI No 1      Two Shillings      January 1950**

# RADIO ENGINEERS — *let us send you this publication*

It contains up-to-date information on BICC Radio Frequency cables which have been developed particularly for use with television receivers.

The construction of the three main types of cable is described and illustrated.

Send to-day  
for Publication 244 T

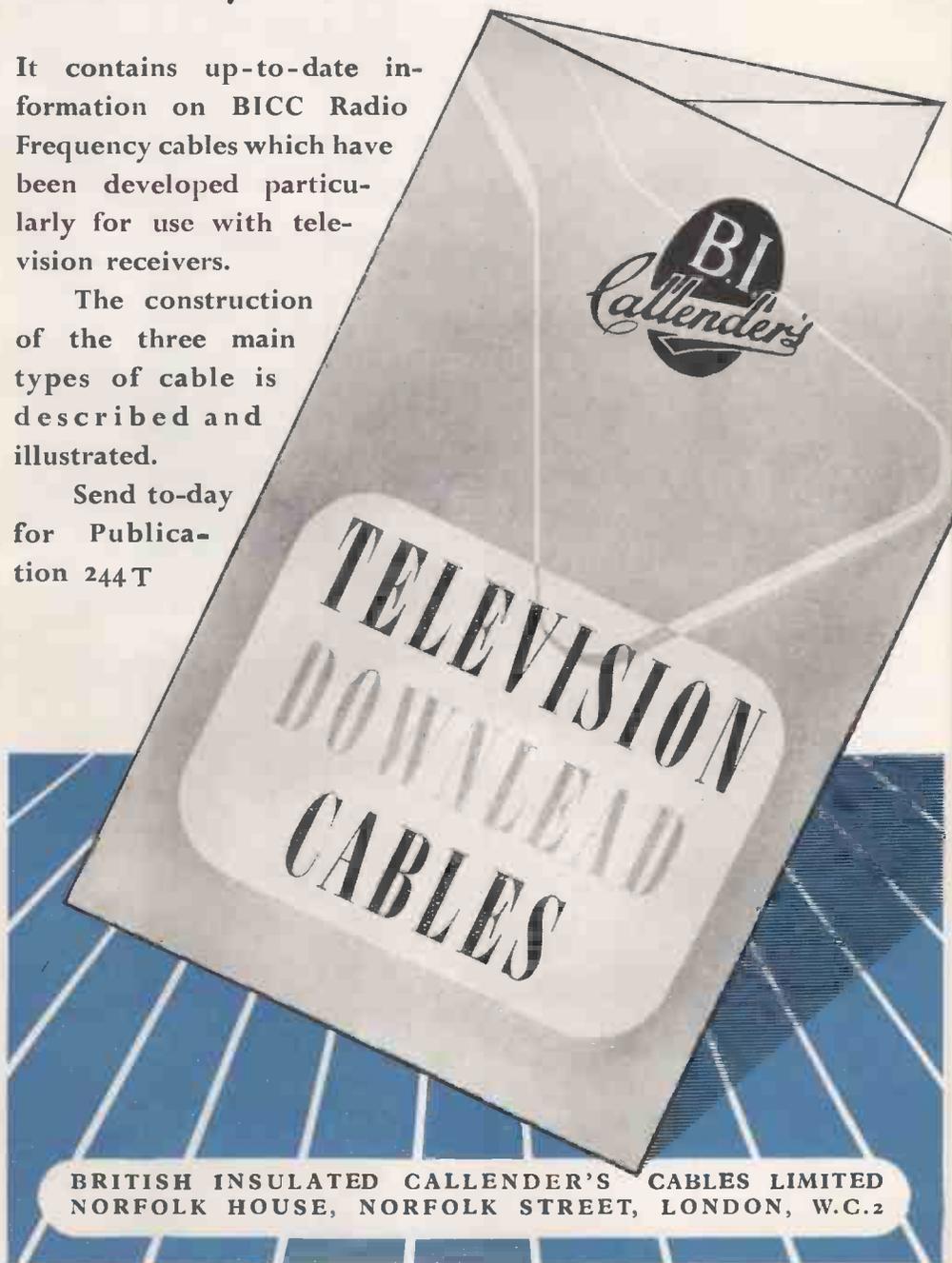

39th YEAR OF PUBLICATION


## In This Issue

Managing Editor : HUGH S. POCOCK, M.B.E.  
 Editor : H. F. SMITH

EDITORIAL COMMENT .. .. .	1
AMERICAN HEARING AIDS. By <i>A. Dinsdale</i> .. .. .	2
T-MATCH TELEVISION AERIAL. By <i>B. Mayson</i> .. .. .	6
NEW BRIDGE TECHNIQUE. By <i>T. Roddam</i> .. .. .	8
CORNER RIBBON LOUDSPEAKER .. .. .	11
AMATEUR EXHIBITION .. .. .	12
EXTENDING TELEVISION .. .. .	14
WORLD OF WIRELESS .. .. .	16
EASING IMPEDANCE CALCULATIONS. By <i>M. G. Scroggie</i> .. .. .	19
ELECTRONIC CIRCUITRY. By <i>J. McG. Sowerby</i> .. .. .	21
HIGH-QUALITY AMPLIFIER. By <i>D. T. N. Williamson</i> .. .. .	24
FILTERS. By "Cathode Ray" .. .. .	25
UNBIASED. By <i>Free Grid</i> .. .. .	30
A.C./D.C.-BATTERY POWER SUPPLIES. By <i>L. Miller</i> .. .. .	31
MANUFACTURERS' PRODUCTS .. .. .	33
LETTERS TO THE EDITOR .. .. .	35
SHORT-WAVE CONDITIONS. By <i>T. W. Bennington</i> .. .. .	37
RANDOM RADIATIONS. By "Diallist" .. .. .	38
RECENT INVENTIONS .. .. .	40

Published monthly: Price 2/- (last Thursday of preceding month) by ILIFFE & SONS LTD. Dorset House, Stamford St., London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Echaworld, Sedist, London."  
 Annual Subscription: Home and Overseas, £1 6s. 0d.; U.S.A. and Canada, \$4.50.

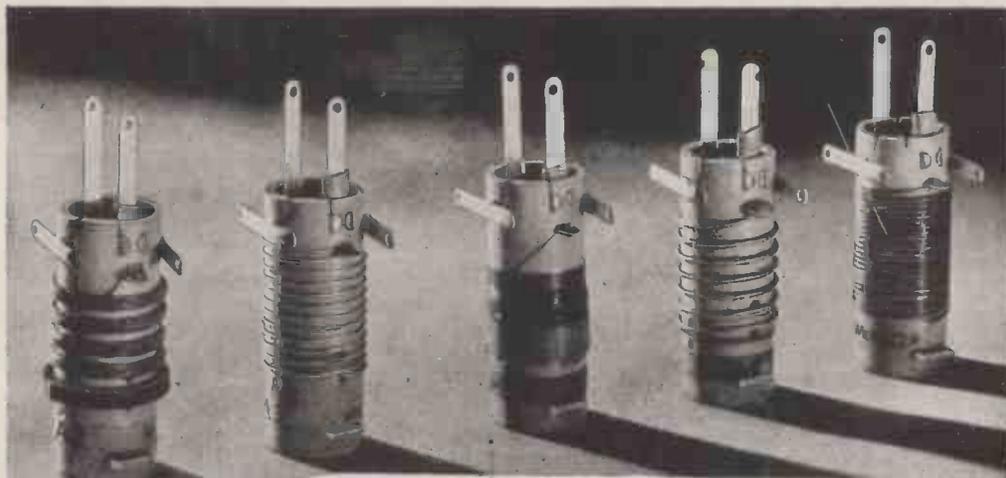BRANCH OFFICES:  
 Birmingham : King Edward House, New Street, 2.  
 Coventry : 8-10, Corporation Street.  
 Glasgow : 26B, Renfield Street, C.2.  
 Manchester : 260, Deansgate, 3



**WEARITE**


**COIL PACKS**

**"P" COILS**

... for Aerial, R.F., and Oscillator Tuning and readily available in all ranges.

**WRIGHT & WEAIRE LIMITED**  
 138 Sloane Street, London, S.W.1.

Telephone: SLOane 2214/5.  
 Factory: South Shields, Co. Durham.

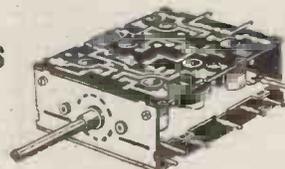

Send 6d. in stamps for the "Wearite" COILPACK Book of Technical Data and Circuits.



# Valves and their applications

## TELEVISION SYNCHRONIZING & TIME BASE CIRCUIT USING EF42, ECC34 & EL38. No. 4.

### FRAME SYNCHRONIZING PULSE SEPARATOR USING 1/2 ECC34

The problem of obtaining a good interlace is a major one in television receiver design and this article is concerned with some elements of the problem and a circuit designed to illustrate the principles involved.

The circuit in Fig. 1. is part of the complete circuit shown in the November issue of the "Wireless World". The waveforms associated with the circuit are shown in Fig. 2 and it will be seen that the chain of eight 40  $\mu$ s frame pulses is converted into one positive pulse.

The waveform E is interesting as it gives the control grid potential of the frame blocking oscillator on the same expanded time scale as the synchronizing waveforms. With the setting of the frequency control (VERTICAL HOLD) corresponding to the waveform shown, the grid potential is some 40 volts below cut-off when the synchronizing pulse arrives. The blocking oscillator then takes current for a period of about 50  $\mu$ s. Towards the end of the conducting period when the grid has ceased to take grid current an oscillation in the leakage inductance and stray capacitance of the transformer T1 occurs.

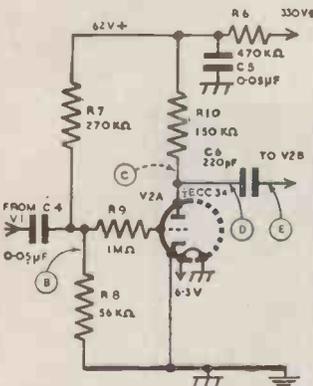


FIG. 1.—CIRCUIT OF SECOND LIMITER IN SYNCHRONIZING PULSE SEPARATOR.

It is apparent from Fig. 2 that the derived frame pulse is of different length for consecutive pulses and this difference appears in the waveform at the grid of the valve V2B. This does not produce non-interlace because the instant of firing is determined by the leading edge of the pulse. This edge is sufficiently steep to ensure that any slight difference in the potential of its base has a negligible effect on the time at which the waveform reaches a given potential. To obtain a perfect interlace the instant, relative to the chain of frame synchronizing pulses at which the blocking oscillator ceases to take current and the potential to which the "charging" capacitor has been discharged at this instant must be identical for consecutive frames. Normally this also implies that the instant at which the blocking oscillator is fired or starts to take current must have the same relationship to the frame pulses for consecutive frames. It is very misleading to assume that a correctly

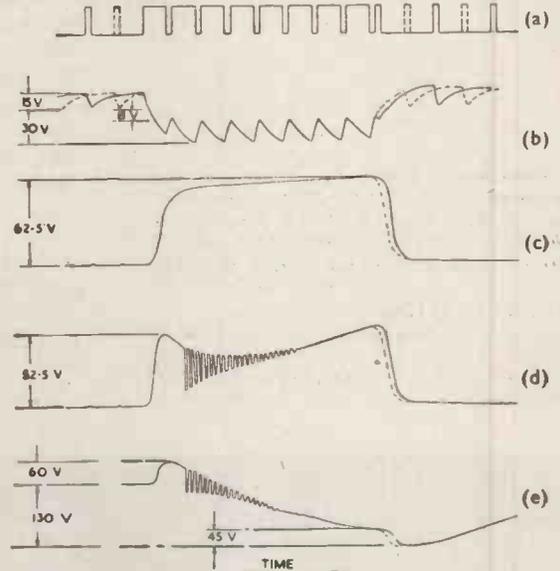


FIG. 2.—WAVEFORMS OF POTENTIAL ASSOCIATED WITH SECOND LIMITER OR FRAME SYNCHRONIZING PULSE SEPARATOR.

fired frame time base will be correctly interlaced. This fact can be readily checked by increasing the brightness and observing that the beginning of the flyback is interlaced in the majority of receivers where interlace is lacking in the picture.

The methods described above ensure that the time base is fired correctly and also the blocking oscillator is protected, during the critical period when it is taking current, by its synchronizing channel being open-circuited, i.e. the valve V2A is cut off. With a reasonable layout no pulses from the line base can find their way into the frame blocking oscillator and a good interlace is obtained.



Reprints of this report with additional circuit notes and also the other reports from the Mullard Laboratory giving full circuit and constructional details of the four valve synchronizing and time base circuit are available, free of charge, from the address below.

**MULLARD ELECTRONIC PRODUCTS LTD.,**  
**TECHNICAL PUBLICATIONS DEPARTMENT,**  
**CENTURY HOUSE, SHAFESBURY AVE., W.C.2**  
 (MVM111)

# Wireless World

VOL. LVI. No. 1.

JANUARY, 1950

## *Planning Television Extensions*

AS soon as data has been collected on the working of the new Birmingham television station the last remaining excuse will have disappeared for delay in formulating—if not for putting into execution—clear-cut plans for developing the British television service to a stage where it will provide a signal for the majority of the population. True, a plan does exist (we publish a summary of it elsewhere in this issue), but many of the details are incomplete and, in particular, there is as yet no precise information as to when the various stations will come into operation. Without this knowledge, the industry cannot, in its turn, make long-term plans for producing receivers, the demand for which is closely linked with the number of homes served by available transmissions.

Apart from these questions of delay, the basis on which coverage of the major part of the country has been planned seems in general to represent the best possible compromise between the many factors that must obviously be taken into account. Clearly, the general idea was to provide the largest possible proportion of the population with a signal, subject to certain economic and technical limitations.

The location of stations in any large-scale system of distribution is always interesting, and it is rather surprising that the details have not been more widely discussed in technical circles. In general, the distribution of the stations is very much what one would anticipate, though at first sight it would seem that the Tyneside station could have been better sited on a vantage point at the northern end of the Pennine chain. By increasing at the same time the power of the station, it would appear that one of the more obvious gaps in our national coverage could have been filled in at relatively low extra cost, as the counties on the western side of the Pennines would stand a chance of enjoying a fair signal. Admittedly, however, the additional area

that would then be served is one of low population density.

THE problems of providing for East Anglia and Wales are, as a glance at our map on page 14 will show, much less simple, though it is to be expected that the more densely populated parts of South Wales will come well within the service area of the Bristol station, presumably on the Mendip Hills. It should be stressed that part at least of the plan is tentative, and so may be revised in the light of experience gained from the Midlands.

No doubt there will be protests from sections of the country that stand to be poorly served. While sympathizing with them, we hope they will derive some comfort in the thought that our distribution system is organized on a rational and equitable basis, and they suffer merely from the accident of geography. We hope the B.B.C., in its turn, will not allow the action of energetic "pressure groups" to deflect it from sound principles. Whatever the merits and demerits of our system of broadcast distribution may be, it does at least make orderly development possible. Difficulties of the post-war years have tended to offset our initial advantage of an early start in television, but there is no real reason why we should not now make up for the ground that has been lost.

THOUGH the delays that have arisen in extending the service are to be deplored, there is nothing to make us think that British television will fail to develop in a steady and healthy manner. The public has accepted it; that view is confirmed by recent licence figures, which show for the first time that the monthly increase in the number of viewers exceeds the number of newly licensed listeners to sound broadcasting. We are more than ever convinced that our moderate-definition standards represent the best possible compromise, allowing both cheap receivers and a transmission service that can be extended at reasonable cost.

# American Hearing Aids

*Current Practice in Design and Fitting*

By A. DINSDALE



American "Acousticon" hearing aid, Model A-120.

**I**N dealing with this subject, I must of necessity confine myself to a discussion of the hearing aids with which I am most familiar; that is, American hearing aids in general, and more particularly those manufactured by Acousticon International of New York.

Essentially, a hearing aid consists of a microphone, amplifier, receiver and power supply. The overall performance of the hearing aid can be adjusted or altered by varying one or more of these essential components.

The most important consideration is that the final evaluation of a hearing aid must be based upon the total performance of the entire instrument as judged by a deaf person. It has been found that out of two or more instruments which perform identically so far as quantitative measurements are concerned, a hard-of-hearing person can frequently express a very definite preference for one instrument over the others.

Looking for pointers for research into this problem, Acousticon turned to a series of reports issued

---

Though the views expressed in this article are often at variance with conclusions arrived at in this country (see, for example, Medical Research Council Special Report No. 261, "Hearing Aids and Audiometers," published by H.M. Stationery Office) we publish it as an indication of present trends in the development of hearing aids on the other side of the Atlantic.

by the U.S. Public Health Service in 1938 on the results of a nation-wide survey of deafness, supplemented by several articles published in 1940 by Dr. Willis C. Beasley, the director of this survey. In passing, it is interesting to note that the survey uncovered the fact that 10 per cent of the population of the United States suffered from loss of hearing in some form.

Based on audiometric measurements, the survey established three stages of partial deafness.

*Stage 1.* Can understand direct conversation without difficulty, but has difficulty in hearing properly in church, theatre, and in groups.

*Stage 2.* Has difficulty in hearing ordinary conversation unless voice is raised, but can hear on the telephone.

*Stage 3.* Cannot hear direct conversation unless shouted directly into the ear, but can hear with hearing aid or amplified telephone.

The survey also revealed three general types of hearing loss:—

(1) Relatively greater loss for frequencies above 1,500 c/s in varying degrees of intensity. (Nerve deafness.)

(2) Relatively greater loss for frequencies below 1,500 c/s. (Conductive deafness.)

(3) Approximately uniform loss for all frequencies. (Mixed deafness.)

Dr. Beasley recommended various patterns of acoustic gain, in varying degree, to compensate for these various types of losses. The essential principle brought out is that all speech sounds, of whatever frequency, appear to a person with normal hearing to have equal loudness. But to a person with a hearing loss, some speech frequencies are heard normally, others faintly or not at all. A person with normal hearing has *balanced hearing*. A person with a hearing loss is most likely to have *unbalanced hearing*.

Accurately to rebalance hearing in a wide range of hearing losses, it is held that a variety of hearing aids with a wide range of characteristics should be made available, and provision must be made in the fitting procedure for an accurate diagnosis of a particular loss, and for the selection of equipment with the proper characteristic to compensate accurately for that loss and thus restore the balance. Acousticon maintain a policy of providing a wide variety of hearing-aid responses to meet the essential requirements of the hard-of-hearing public. Specifically, the current Acousticon "Constellation" models provide 36 different combinations. There are three "transmitters" (microphone-amplifier-power supply) of various powers, to which may be connected

12 receivers (earphones) of different characteristics.

The three transmitters are known as A-120, A-130 and A-140, which are designed for Stage 1, Stage 2, and Stage 3 degrees of deafness, respectively. Maximum peak acoustic outputs, as suggested by the model numbers, are 120 db, 130 db, and 140 db relative to the threshold of hearing. The first two are self-contained instruments; the A-140 requires outside batteries.

The A-120 (illustrated) measures 4 in x 2 5/8 in x 7/8 in, and weighs six ounces, complete with batteries. The "A" (l.t.) battery, a Mallory mercury cell, will give 80-90 hours of service. The service life of the 15-volt "B" (h.t.) battery depends upon the volume control setting and with a drain of 220 to 300 μA will vary between 250 and 450 hours.

The A-130 is slightly longer, to accommodate a 22 1/2-volt "B" battery. "A" battery life is the same. The "B" battery drain varies from 500 to 800 μA, giving a life of 150-300 hours.

The A-140 is a much smaller and lighter instrument, because the battery compartment has been omitted. The external 1 1/2-volt zinc-type "A" battery will give 70-75 hours' service. The 30-volt "B" battery drain ranges between 850 and 1,350 μA, giving a battery life of 150-300 hours.

As stated above, the choice of transmitter is governed by the degree of loss, and the amount of power required to make the patient hear properly. The percentage of instruments in use is as follows: A-120, 65%; A-130, 32%; A-140, 3%.

### Individual Characteristics

To compensate for the characteristics of individual hearing, there are nine air receivers and three bone conductors of various characteristics. These are listed below by type number, peak frequency response, and percentage ratio of use:—

Type	Peak Frequency (c/s)	Per Cent In Use
M4	400	2.5
M6	600	1.7
N	900	3.1
E	1100	8.7
S	1600	14.9
T	2000	19.5
L	1100-2400	12.7
P	3000	11.0
U	Uniform 400-3000	10.3

To peak these receivers at any desired frequency, the diaphragms are mechanically loaded to achieve the requisite damping. The manufacturing process is difficult and expensive, because the percentage of rejects is high. Each receiver is individually checked, and must conform closely to specifications. Thus, there is a temptation to reduce the number of receivers. But the demands of the hard of hearing, as indicated by percentage figures of use, do not permit of any reduction. Response curves obtained from six Type S receivers of each type, chosen at random and superimposed, are shown.

The three bone conductors are classified as low, medium and high and the percentages in use are 8.2, 5.2 and 2.2 respectively. It has not so far been possible to devise suitable equipment to measure the


response of a bone conductor accurately. A bone conductor is applied to the mastoid bone behind the ear, under considerable pressure supplied by a head-band. Where conductive deafness (due to middle ear disease) is indicated, the patient can often hear better with a bone conductor than with an air receiver, and in severe cases of conductive deafness, it may be the only way to make him hear.

The performance of any given "transmitter" can be varied slightly by means of a 4-position tone control. The first position provides no alteration of basic response. The second position attenuates low frequencies. The third position attenuates high frequencies. In the fourth position, uniform attenuation is introduced *before* the signal enters the second amplifier tube. This suppresses high-level background noise which would otherwise mask reception of desired speech. This feature is extremely helpful when in a noisy place, such as a restaurant, city street, or while riding in an automobile.
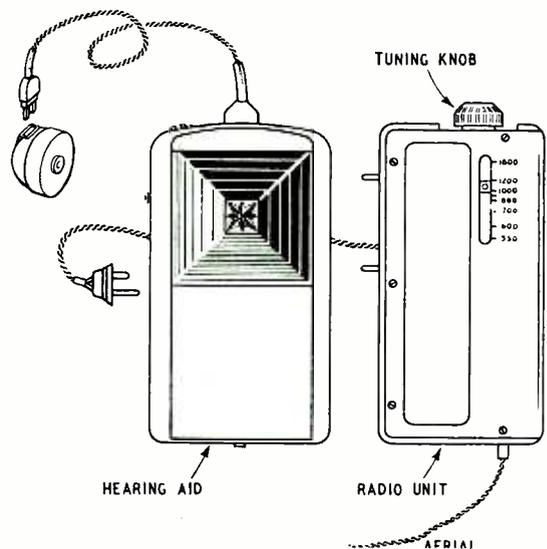
### The Analytic Speech Test

For a number of years it has been (and still is) customary in America to use an audiometer as an aid to the fitting of hearing aids. An audiometer is an excellent diagnostic tool in the hands of an ear specialist, but there is considerable doubt, even among those who use it, as to its efficacy for the purpose of fitting a hearing aid properly. After all, the ultimate criterion of an effective hearing aid is how well it will permit the wearer to hear *and understand* speech.

Acousticon therefore devoted many years of research into the problem of devising an effective method of testing with speech. The extensive experimental work done by the Bell Telephone Laboratories provided much useful information to start with. However, the various standard word tests, composed of random assortments of all speech



Showing inter-connections between hearing aid "transmitter" and auxiliary radio receiver unit.

### American Hearing Aids

sounds, failed to reveal the hearing unbalances which Acousticon sought to identify. What was needed was a test which would reveal the relative ability of a hard-of-hearing person to perceive speech sounds having predominantly low-frequency and high-frequency content.

As finally developed, the Acousticon speech test consists of two lists of monosyllabic words, one in the low-frequency range, and one in the high-frequency range. In the l.f. range there are words like *roar, war, home*; in the h.f. range, words like *patch, cease, chief*. Thus, instead of one average score, as in previous tests, the Acousticon test provides two scores, one in each frequency range.

For example, a phonetically balanced (PB) word list may provide a score of 50% at a given intensity, as shown in Fig. 1(a). The same subject, when given the Acousticon test, might come up with a score of 75% in the low-frequency range, and 25% in the high-frequency range, as shown in Fig. 1(b). This averages out at 50%, as with the PB list, but it reveals clearly the nature of the hearing loss, and the steps which must be taken to correct it and restore balanced hearing.

From the indications given in Fig. 1(a), it would appear that all that is needed is a universal type of hearing aid with enough acoustical gain to drive the score up to 100%. This is the brute-force method. When Fig. 1(b) is studied, it becomes clear that enough brute force will drive the weak h.f. score up to 100%. But what of the l.f. end? At that end of the scale, sufficient power to correct the h.f. deficiency will overpower the patient and cause acute distress.

If the patient persists in wearing a hearing aid which is misfitted in this way, he will eventually become a nervous wreck, and the strain on the nervous system, in turn, is likely to produce various more-or-less serious physical disabilities.


Further study of Fig. 1(b) will suggest that the commonsense procedure, before applying power indiscriminately, is to apply correction to the h.f. end to restore the balance. The ideal correction would raise the h.f. score to 75%. This having been accomplished, it is then safe to apply just sufficient power to overcome the *degree* of loss.

### Fitting Procedure

The Acousticon fitting procedure is designed to achieve the results described in the preceding paragraph, by enabling the examiner to determine exactly the nature and extent of the loss, and select the proper fitting (receiver) and transmitter which, in combination, will restore the patient's hearing to as nearly normal as the age and severity of his disability will permit.


The equipment employed consists of a hearing aid transmitter, a "coupler," and a pair of headphones.

The characteristic curve of the amplifier in the transmitter rises slightly from the l.f. to the h.f. end. The coupler contains a filter which flattens this curve to a uniformly flat response at all frequencies. Thus, when testing, the gain is the same at all frequencies. Also included in the coupler is a switch by means of which the operator can direct his speech into either or both of the patient's ears.

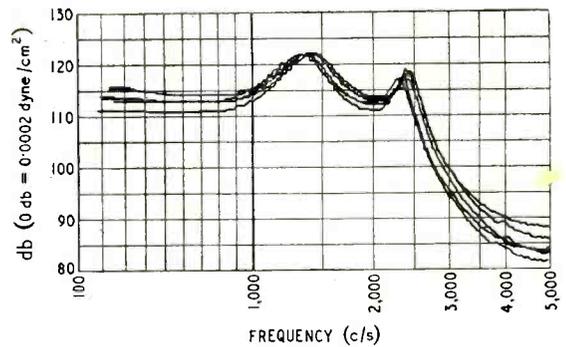

Response curves of six Type S receivers taken at random. Measured on an artificial ear of 2 c.c. volumetric capacity with a constant electrical input of 100 mV.

Fig. 1. (a) Results of normal phonetically balanced (PB) test; (b) Acousticon word test.

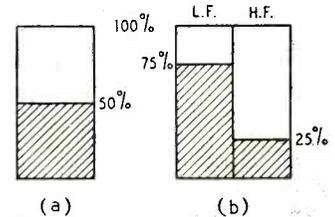

In preparation for the test, the operator talks to the patient (both ears), using adequate power to be heard easily. Then he switches first to one ear and then the other, to determine whether one ear may be totally deaf, and to measure by the volume control setting the degree of power required for each ear. The two ears are very seldom alike, either in degree or nature of loss.

Having selected one ear to start on, the operator then slowly reduces power until the patient can just barely understand him and no more. In cases of very light loss, this may involve moving several feet away from the transmitter. Then, using a silken lip mask to prevent the patient from reading his lips, the operator reads over the word lists, waiting for the patient to call back each word—if he can identify it. Each correctly repeated word is scored. The process is repeated for the other ear. Then the scores are added up and reduced to percentages.

Wherever possible, Acousticon prefers to fit the "bad" ear. The reason for trying to do so is to leave the "good" ear open to hear what it can, and thus reinforce the assisted "bad" ear, to provide better overall hearing, and some degree of directional sense. However, in extreme cases, it is not always possible to provide understanding of speech through the "bad" ear, due to irretrievable damage. In such cases, the "good" ear must be fitted.

Having studied the patient's scores and evaluated them with respect to high- and low-frequency loss, plus consideration of the degree of loss in each ear, the operator decides which ear to fit. To find the correct fitting (receiver), he transfers the score figures on to a special slide rule, which indicates the preferred fitting and an alternative. The preferred and alternative fittings are tried and the patient is asked to say which seems best to him. In cases of conductive deafness (low l.f. score), the operator will also try

a bone conductor to determine whether the patient can hear better with an air receiver or a bone conductor.

There is a weakness at this point which has caused much trouble in the past. The patient is not always a reliable witness as to how well he hears. If he has been hearing badly or not at all for some years, any sort of improvement seems wonderful to him. But his judgment as to how well he hears may be seriously impaired. Or he may be the incoherent type, who cannot express intelligently just what he hears, or how well.

So the patient's opinion is used only as a rough guide. When it seems that the best fitting has been selected, the word test is applied again, this time through the medium of the complete hearing aid and the correction thereby supplied. If the fitting is correct, the l.f. and h.f. scores will balance. If they don't balance, then another receiver is chosen, higher or lower in pitch as indicated by the score. The test is applied again, and if the operator is an expert he will usually hit it this time.

The important point is that when he has finished, the operator does not rely on the doubtful judgment of the patient as to how well he hears. As a result of his scientific check-back, he *knows* for certain. Next come sentence tests and distance tests, to prove to the patient that he is properly fitted, and demonstrate how well he can hear.

All this seems simple enough but, as with all things, there is danger in over-simplification. Many factors caused by the psychological condition of the patient enter into the picture, but this is no place to discuss such problems. Suffice it to say that the psychological problems are very real, and must be taken into consideration. They call for expert handling and sound judgment by an experienced operator.

There is one other physical factor which must be taken into consideration. When a patient begins to wear a hearing aid for the first time, using an air receiver (this does not apply with bone conduction), changes gradually take place in his hearing. Thus, after the first few weeks, the original fitting becomes unsuitable, and it must be changed for another, which a re-check with word tests reveals as now correct. If the patient will wear this instrument steadily, day after day, his hearing will usually stabilize within two or three months. During that period, one or two changes of fitting may be necessary—in extreme cases, four or five changes.

The exact cause of this change is a subject of medical controversy in the United States. But it seems apparent that the stimulation provided by the direct application of properly-corrected sound into the ear canal does produce changes of some sort in the hearing mechanism. The important fact is that *changes do take place*, and they must be compensated for. Otherwise, the hearing aid is discarded in disgust, or worn in spite of its inadequacy, to the ultimate detriment of the patient's nervous and physical health.

That is why it is Acousticon's policy to sell *and maintain* good hearing, rather than just another hearing aid. There is no charge for changing fittings during the initial period.

Various attachments and accessories are available to hearing aid users. Of interest to *Wireless World* readers is Acousticon's "Super-Radion." This is

a miniature radio which can be plugged into any of Acousticon's current models. As can be seen from the illustration, it is smaller than the smallest of the hearing aids (A-120). It consists essentially of a two-valve circuit—one stage of r.f. amplification and detector—powered by the hearing aid batteries. The output goes into the three-valve a.f. amplifier of the hearing aid itself, so that the combination is the equivalent of a five-valve set.

Two aerials are provided, both plug-in. One is a 4ft length of flexible insulated wire; the other, a 15ft length. In the average home at night, especially if the aerial wire is draped over the telephone, or an electric lamp, it is possible to pick up stations all over the United States.

The inspiration for this idea came from the miniature radios, made up to look like hearing aids, which were employed by European underground movements during the war.

Many hard-of-hearing persons complain that they cannot hear the radio properly, with or without a hearing aid. This is due, in part, to the fact that many American radio announcers and speakers tear along like a rocket, and do not always enunciate properly. In part, it is due to the losses and distortions which occur: (1) in the radio; (2) in room acoustics; and (3) losses in pick-up by the hearing aid. All these losses are eliminated by using the "Super-Radion."

The set can also serve a very valuable function in rehabilitation. Many people who have been severely deafened for many years suffer a sound-memory loss. Certain words, not heard for years, are forgotten, and by listening attentively to the radio for a certain period every day, the ability to hear and recognize words is improved.

## Future Trends

There are several new developments in the way of design or components. One of these is a new receiver just placed in the market which has a diameter no greater than a sixpence. This is smaller than anything yet produced. The advantage claimed for it is that it can be seated further into the ear and thus made less conspicuous. Receivers now available must (except with very large ears) be held outside of the ear by building up the earmould appropriately. In the new receiver, the attachment to the earmould can be offset to fit the ear, and the amount of moulded material reduced to permit snug seating of the receiver within the outer ear.

One or two American hearing-aid manufacturers have already incorporated printed circuits and/or automatic volume control, but some manufacturers with very high standards are not yet satisfied that these developments can be incorporated in their instruments to advantage.

Another development being worked on is the rechargeable "A" battery. The idea here, of course, is to reduce the cost of operation.

A leading contender in this field is a silver oxide-zinc cell, being pioneered by André and Yardeny. While two American hearing aid manufacturers have "jumped the gun" with batteries of this type, it is felt by conservative engineers that this battery has not yet reached the stage where it can safely be entrusted into the hands of the public.

# T-Match Television Aerial

Built Inexpensively with Simple Tools

By B. MAYSON (*Marconi's Wireless Telegraph Company*)

**I**N the field of v.h.f. communications the T-match type of aerial has been in use for some years, although for television purposes it appears to have been entirely neglected in favour of the split dipole. It is not clear why this should be so because the T-match type has three basic points which should make it attractive to the home constructor, if not to the manufacturer.

First, the use of a continuous rod for the receiving element, reinforced by the matching section, gives mechanical strength and electrical efficiency with ease of construction. Secondly, close aerial-feeder matching can be achieved. Thirdly, the whole metallic structure can be earthed to provide not only a lightning conductor but a drain for static charges, with a consequent reduction in receiver noise.

Having decided on the type of aerial to be made, the next step was to fix its measurements. Not an easy matter this, especially as regards the T-match, for design is influenced by many factors, some opposing others, and by differences in expert opinion. The measurements decided on are shown in Fig. 1. In general, the T dimensions were determined from data obtained experimentally.

Great care was taken in selecting materials, especially when it came to the vertical rods. One can see the sorry results of false economy in this respect all too often.

Half-inch duralumin tubing with a wall thickness of  $\frac{1}{16}$  in was chosen for the vertical rods. A lesser gauge is risky. Aluminium tubing is quite unsuitable for the purpose, not having the necessary mechanical strength, otherwise many metals and alloys will meet the requirements. Whatever material is used, the rods should be obtained each in one piece, if possible. In the writer's case 6-ft lengths only were available, necessitating a joint at the centre of each rod, which was done by getting some round duralumin rod, just oversize to the bore of the tubing, rubbing it down, and making a force fit. Care was taken during this, and subsequent operations, not to damage the tubing.

Three-quarter-inch gas tubing was used for the assembly shown in Fig. 2 (a), the threads

being cut by a local tradesman. This resulted in an extremely strong but rather heavy job. Where weight is an important consideration half-inch gas tubing would be preferable and would no doubt be quite strong enough.

In Fig. 2 (a), B is a hole drilled in the underside of the horizontal member nearest the receiving rod. It is fitted with a rubber bush. Through this hole the feeder is passed from the matching section and thence down the mast section C, which, like the horizontal part of the H, consists of three-quarter-inch gas tubing having a wall thickness of  $\frac{3}{16}$  in. A mast section length of 10ft was used, attached to a wooden pole, as described later. A similar length would be just right for a chimney mounting. Alternatively, where a lighter assembly is required, half-inch gas tubing having a similar wall thickness would do very well, with a horizontal part to match.

The receiver and reflector rods were fitted with the aid of reducing adaptors, A in Fig. 2. When purchased, of course, these adaptors had threaded bores, fortunately about  $\frac{1}{16}$  in less in diameter than the duralumin rod.

Accordingly, after being softened in a gas flame, the adaptor bores were filed to take the rods. Next, two rounded grooves were filed in each adaptor as shown in Fig. 2 (b). Then, with the adaptors screwed into the T-pieces, the duralumin rods were positioned and finally secured by means of pins driven into the adaptor grooves. Small oval nails, minus heads, were used as pins.

Fig. 3 gives details of the matching section, duralumin tubing as specified above being used for the rods. The porcelain insulator has metal end bushes, tapped 2 B.A. On to each of these ends was screwed an inch of ebonite tubing, to which the matching rods were secured by pushing them over the ebonite. The brass supporting strips C were secured to the duralumin rods by 6-B.A. screws and nuts. These strips were fixed at right-angles to the horizontal part of the H, but the positioning is in no way critical.

The 80-ohm co-axial feeder was terminated with a co-axial

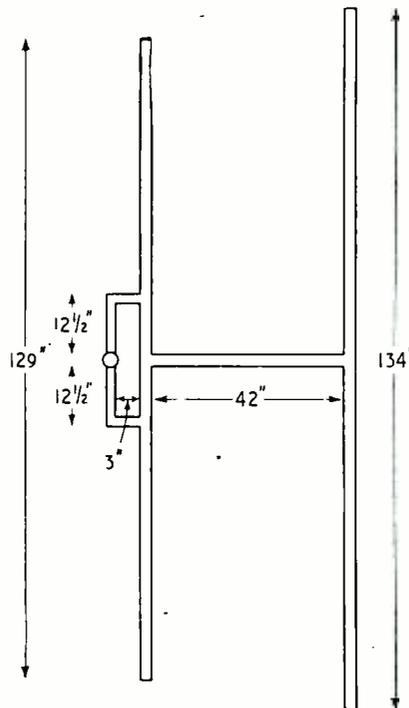


Fig. 1. General form of T-match aerial

plug, fitted into a socket. The socket (feeder inner conductor) was connected to the upper matching rod clip by means of a 16-s.w.g. Telcothene-covered wire. The plug (braid) was connected to the lower matching rod clip in a similar manner. The soldering was very carefully done; readers who are not used to working with light co-axial cables should note that it is only too easy, when soldering the outer part of the plug to the feeder braid, to run the solder through on to the inner conductor. A simple way of avoiding this fault is to slip a tube of brown paper between the insulation and braid.

Considerable attention was given to weather-proofing the completed aerial, bearing in mind that duralumin is particularly liable to corrosion and that dissimilar metals joined together are subject to electrolytic action.

To begin, all metallic parts were thoroughly prepared in the normal manner and then roughened with a wire brush to provide a good base for the paint. If the reader can get his parts sand-blasted, so much the better. All electrical connections in the matching section were well cleaned before being screwed up. Joints and connections were sealed with Bostik B Compound, which was also used for plugging the ends of the tubes. The feeder connection was wrapped in insulating tape and tied with fishing line. Finally, the assembly was given a coat of red lead followed by two coats of good aluminium paint.

### Mounting the Aerial

How the aerial is mounted will naturally depend on the reader's circumstances. The writer's choice was a 30-ft spruce pole, erected in the garden about 40ft from the house. The mast section, C in Fig. 2, was clamped to the pole by means of shaped metal bands  $\frac{1}{2}$  in thick, made with some difficulty without the aid of an anvil. A 16-s.w.g. earthing wire was run from C down the pole to a buried copper plate. Two sets of stays were fitted to the pole, three stays to a set. These were considered necessary owing to the weight of the aerial assembly, and because the pole diameter at the top was 2 in only. The stays were made of 14-s.w.g. galvanized iron-wire sections connected by egg-type insulators spaced 7ft apart. Whether insulators are really necessary in the case of a receiving aerial of this kind is a matter of opinion; the writer considers it good practice to fit them.

The measurements given in Fig. 1 were based on the London vision frequency, 45 Mc/s. Suggested measurements for Sutton Coldfield, 61.75 Mc/s, are:—

Reflector rod .....	97.5in
Receiving rod .....	93.5in
H spacing .....	31.0in
Matching rods, each .....	9.0in
T spacing .....	3.0in
Insulator spacing on stays .....	5.0ft

(Reflector rod = 0.51 wavelength. Receiving rod = 0.49 wavelength. H spacing = 0.16 wavelength. Insulator spacing on stays =  $\frac{1}{4}$  wavelength. Wavelength = vision wavelength of station required.)

As explained above, the remaining dimensions were determined from experimental data.

The aerial described was built at a cost of £3 10s.

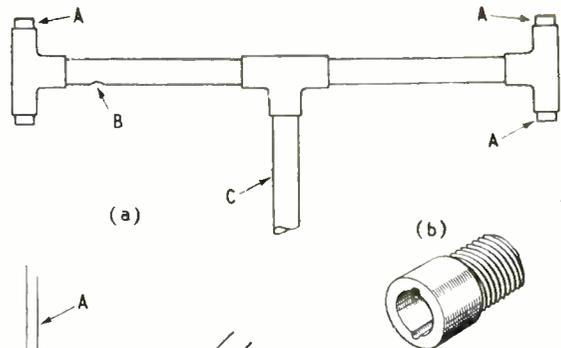


Fig. 2. The detail of the horizontal member is shown at (a) with a "close-up" sketch at (b) of one of the modified reducing adaptors.

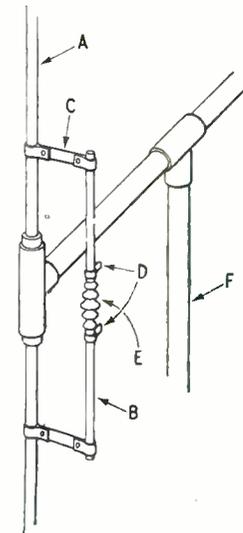


Fig. 3. Perspective sketch of the T-matching section; A = aerial rod, B = matching rods, C = brass supporting strips, D = cable-connecting clips, E = insulator, F = upper part of mast section.

including the pole and feeder. It is located on low-level ground 30 miles from the London transmitter and has been in use for some months, the performance being completely satisfactory.

In conclusion, readers who have not yet been at close quarters with a television array are reminded that the finished assembly is a very awkward thing to handle where space is limited; a little thought given to this point before construction is started may well save trouble later on.

### RADIO TAXI

Although many private-hirecars have been fitted with two-way radio, the first London taxi to be so equipped has now been approved by the Commissioner of Police. The Marconi 10-W v.h.f. transmitter-receiver (Type H16) is installed under the driver's seat and, as can be seen in the photograph, the microphone is fitted above the windscreen and the combined control unit and loudspeaker below the dashboard.



# New Bridge Technique

Square-wave Excitation Instead of Sine Waves for Measuring Complex Impedances

By THOMAS RODDAM

**A** LETTER to *Nature*\* recently described a new bridge technique which appears to be of considerable interest. Bridge circuits, as generally used, operate at a single frequency and give an answer which is valid at that frequency alone. Often this does not matter: if the impedance which is being measured is a good resistor, or a good capacitor, the value of resistance or capacitance is the same at 50 c/s as it is at 5,000 c/s. If the impedance which is being measured is not a simple one, it is necessary to know what form it has if the results of a measurement at a single frequency are to be properly interpreted.

Let us, for example, consider a circuit consisting of a resistance and capacitance in parallel. The admittance of such a circuit is  $(1/R + j\omega C)$ , so that the impedance is  $R/(1 + j\omega CR)$ . This can be written as

$$\frac{R}{1 + \omega^2 C^2 R^2} + \frac{j}{\omega} \frac{CR^2}{1 + \omega^2 C^2 R^2}$$

This is the impedance of a resistance  $\frac{R}{1 + \omega^2 C^2 R^2}$  in series with a capacitance  $\frac{1 + \omega^2 C^2 R^2}{CR^2}$ . If, therefore, we balance the unknown circuit by using a resistance and capacitance in series in the bridge arm, we shall obtain values which depend upon frequency and shall have great difficulty in discovering just what the unknown network is.

The new bridge technique gets round this difficulty very easily by demanding that the bridge should be balanced simultaneously at all frequencies.

\* *Nature*, Vol. 163, p. 132, Jan. 22nd, 1949 (Yates), and p. 571, April 9th, 1949 (Prowse and Laverick).

Fig. 1. Simple form of bridge with inductive ratio arms, showing stray capacitances  $Z_A$ ,  $Z_C$ ,  $Z_D$ .


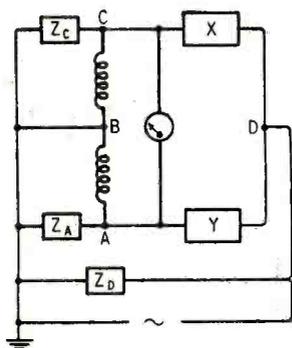


Fig. 2. Circuit with generator and detector connections interchanged.

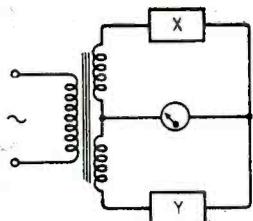

This is not as complicated as it sounds, because the frequencies are applied together in the form of a square wave. The bridge output is viewed on a cathode-ray oscilloscope, and the bridge components adjusted until the balance is obtained.

The actual bridge circuit used is one first suggested by Blumlein. It has the particular advantage that it is almost immune from earth capacitance effects. Fig. 1 shows the basic circuit, which differs somewhat from that given in *Nature* in a way to be discussed later. The bridge will be balanced if the currents entering A and C and leaving the tapped coil at B produce no voltage difference between A and C. For tightly-coupled windings of low resistance this means that the products of current and number of turns must be equal for the two windings. The flux in the core will then be zero, so that the potential difference between A, C and B will be very small, being produced by the drop in the resistance and leakage inductance only. This means that the voltage across the capacitances shown as  $Z_A$  and  $Z_C$  will be very small, so that these capacitances can have little effect on the balance of the bridge.  $Z_D$ , being across the generator, cannot affect the balance of the bridge. The bridge is therefore practically immune from the effects of capacitances to earth.

The two impedances X and Y shown in the circuit are, of course, the unknown and the measuring arm. The output from the bridge is easily determined. Suppose that a current  $2I$  is produced by the generator. If the inductance of the ratio arm system is very great, the current will divide equally at B, and the drop across the two external arms will be  $IX$  and  $IY$ , giving a voltage of  $I(X - Y)$  across the detector. If we interchange the generator and the detector, and assume that the detector has a low impedance, the current through the detector becomes  $V(I/X - I/Y)$ . It is this interchange of detector and generator which characterizes the circuit described in *Nature*. In Fig. 2 the circuit is shown in this revised form, using a third winding to inject the alternating-current input.

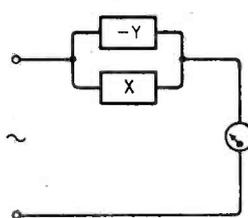


Fig. 3. Equivalent circuit of bridge shown in Fig. 2.

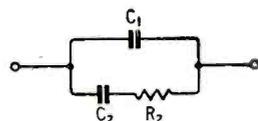



Fig. 4. Typical circuit for which the bridge is particularly well suited.

This last expression is a very interesting one. The output current is proportional to the difference of the admittances, so that the circuit is equivalent to the circuit shown in Fig. 3. In the application for which the bridge is intended, this equivalent is particularly useful. Suppose that X consists of a parallel pair of circuits, as shown in Fig. 4. By adjusting one component of Y, the capacitance  $C_1$  can be completely balanced out, leaving only the circuit consisting of  $C_2$  and R.

A special application of this is already well known. It is the crystal filter used in communication receivers. By adjusting the variable capacitance the value of capacitance in parallel with the series resonant circuit can be varied over a range which includes negative values. In this way the anti-resonant frequency of the combination, at which the filter has a high rejection peak, can be put above or below the narrow pass-band.

The bridge circuit, of course, can be used as an ordinary a.c. bridge, and a number of commercial audio- and radio-frequency bridges have been produced using the inductance ratio arms. Let us now see what happens if we put in a square wave. Consider first the circuit of Fig. 3, with Y equal to zero. If we have a resistance at X, we shall get a square wave of current through the detector, which is now, of course, the input to a cathode-ray oscilloscope amplifier. If we have a capacitance, we

Fig. 5. Circuit of crystal filter used in some communication receivers and its equivalent network.

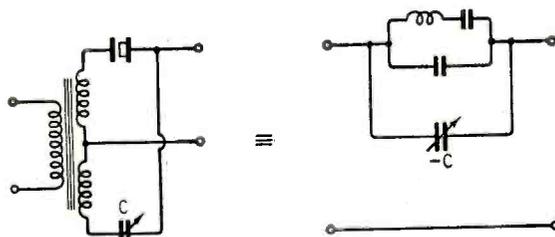

shall get a sudden peak of current, dying away as the capacitance charges up. Five typical waveforms are shown in Fig. 6. By looking at the waveform on the oscilloscope, which is, of course, synchronized with the square wave, we can make a pretty good guess at the type of impedance which we have at X. Suppose that we obtain a response like that shown in Fig. 6 (4). We can connect a capacitor at Y in the bridge circuit, and adjust its value until we get a square wave, like the one shown in Fig. 6 (1). Then we add a parallel resistance, adjusting this until we get no deflection at all on the cathode-ray oscilloscope. In Fig. 7 the various waveforms obtained are shown, and it will be seen how easily the two components can be balanced separately. When the bridge has been balanced for


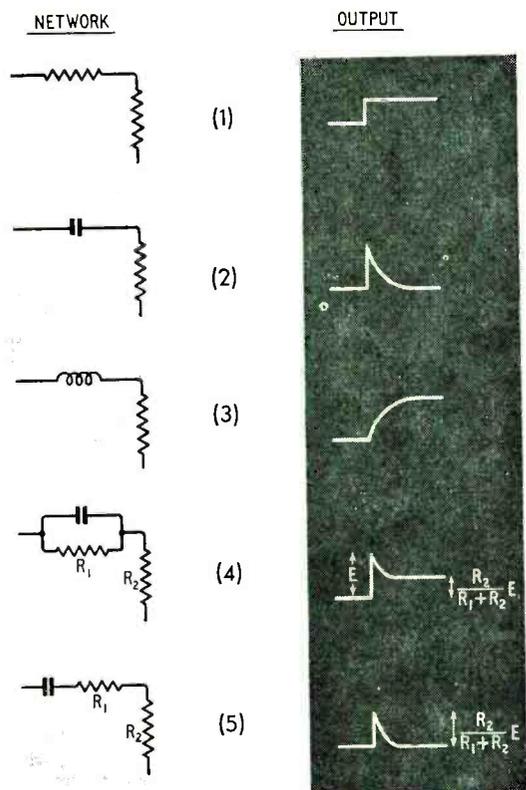


Fig. 6. Typical responses to square-wave inputs.

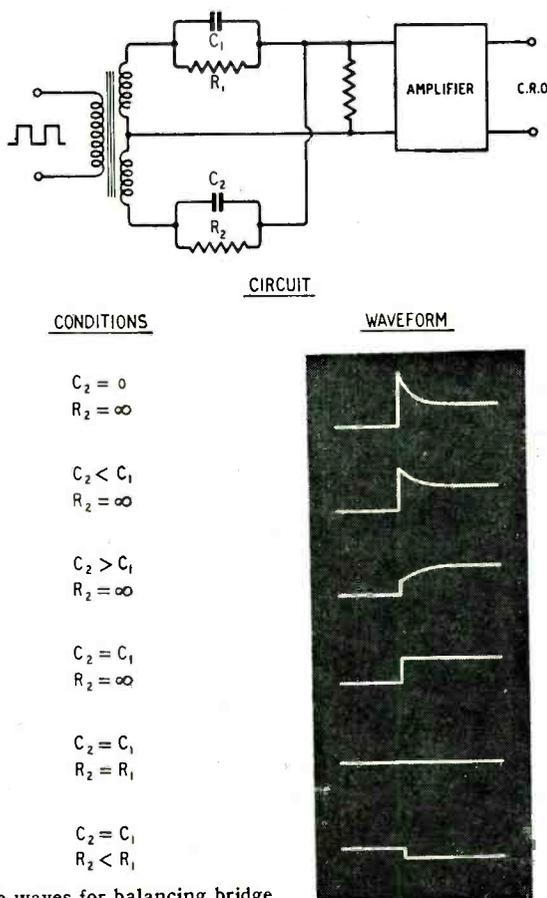(Right) Fig. 7. Typical circuit and waveform using square waves for balancing bridge.



### New Bridge Technique

square waves, the Y network is exactly equivalent to the unknown. No calculation is needed.

A special application, which is actually that for which the bridge was designed, is the study of dielectrics. An ordinary paper capacitor, the sort used for filtering in power packs and other odd jobbery, has an equivalent circuit which is shown in Fig. 8. In this circuit  $C$  is just the usual capacitance, and  $R$  the leakage: all capacitors lose their charge ultimately, and usually the product  $CR$  is of the order of some thousands of megohm-microfarads. The extra components,  $c$ ,  $r$ , represent a feature of capacitors which can be both dangerous and annoying.

If a capacitor is kept charged for some time, and then discharged, it will be found that after say 30 seconds it has apparently become recharged. This means that if you short-circuit the capacitors in the television power pack with a screwdriver before you start work on it, you may still get quite a sharp blow when you put your hand on a hot spot a couple of minutes later. That's the dangerous end. The annoying end is that in some circuits operating down to d.c. and using feedback through capacitors, and circuits of this kind are common in servo devices,

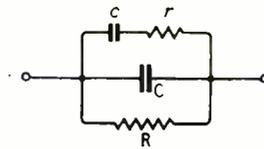


Fig. 8. Complete equivalent circuit diagram of a typical filter capacitor.

there will be a drift due to this secondary charging and discharging. This phenomenon has been called "dielectric hysteresis," though I suspect a typist was to blame: another term, which I prefer, is "soaking"; the charge soaks into the dielectric like butter into hot toast. I refuse to pursue the analogy. In circuit terms, the capacitance  $c$  is charged slowly through  $r$ , and if  $C$  is discharged, the charge on  $c$  leaks back slowly to recharge  $C$ . The way in which this effect varies with temperature is considered to provide a clue to the molecular effects in the dielectric which cause soaking. The bridge is used with  $C$  and  $R$  balanced out, so that the response is due to the  $cr$  circuit alone. Changes in this circuit then produce changes in the waveform on the cathode-ray oscilloscope which are not lost in the effects due to  $C$  and  $R$ .

## NEW BOOK

*Radio Engineering* (Volume 2). By E. K. Sandeman, Ph.D., M.I.E.E. Pp. 579+xxi, Chapman and Hall, Ltd., 37, Essex Street, London, W.C.2. Price 40s.

THIS volume completes the work of which Vol. 1 was reviewed in the April, 1948, issue. It deals mainly with interference and noise, receivers, measuring equipment, response adjustment and equalizer design, feedback, network theory, and filters.

The chapter on network theory is the longest and most fully developed. The novices, for whom, among others, the whole book is intended, would probably welcome a few numerical examples to help them through this chapter.

In the chapter on feedback, the aspects of stability and input impedance are treated exceptionally fully.

The chapter on measuring equipment is of interest chiefly for its fairly detailed descriptions of instruments used mainly in broadcasting. All else is very perfunctory except for r.f. bridges and frequency comparison by Lissajous figures. The latter method, which is made to appear far more difficult and confusing than it is in practice, is one of very few applications of the c.r.t. included. The only c.r.t. shown is a diode type; brilliance control is not mentioned. The treatment of a.f. capacity bridges includes measurement of leakage but ignores other losses. Even though this chapter apparently does not attempt more than a B.B.C.'s-eye view of the subject, one would

have expected that intermodulation would have been recognized as a form of distortion worth mentioning, if not actually measuring.

The chapter on receivers is even more disappointing, in that it is not only unbalanced but actually misleading. Obsolete practice is given prominence and a number of important considerations unmentioned. The latter part of the chapter is devoted to B.B.C. instructions on receiver measurements. They have to be read in conjunction with the specification tentatively introduced by the now extinct R.M.A. in 1936. Incidentally, the statement that an inductance of 0.5H "may be constituted conveniently by a 50-000- $\mu$ H Bulgoin H.F. choke" seems to suggest a regrettably wide manufacturing tolerance!


The chapter on interference and noise is, on the whole, a good survey of the subject. But i.f. harmonic interference should certainly have been included among those to which the superhet is subject.

Introducing the 75-page bibliography, the author admits that it is incomplete and unsystematic, and that inclusion of a reference does not guarantee that it is useful even in its own sphere. If this is so—and it obviously is—one wonders why so much space was devoted to it.


It is a pity that among the many authorities to whom the author acknowledges help in providing the material for this book—much of it very sound and hitherto unpublished—he had not included any to advise on balance and presentation.

M. G. S.

## Electronic Photo-engraver

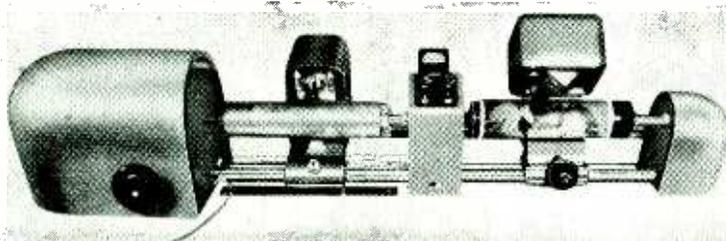


Designed for the rapid production of half-tone blocks, this machine by the American Fairchild Corp. scans the original print (right) by means of a photoelectric cell, and engraves a plastic sheet on the roller (left) with the equivalent half-tone dots through the medium of an amplifier and a current-heated stylus. Average time for the production of a column block is six minutes, and the maximum size available is 8in  $\times$  10in.

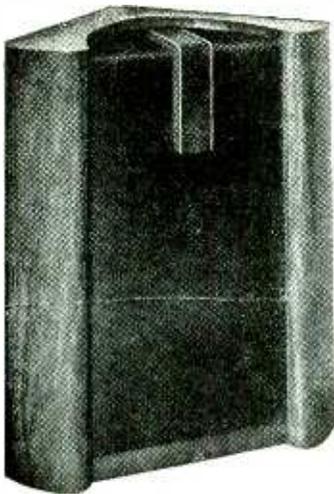

# Corner Ribbon Loudspeaker

*Realistic Sound Distribution*

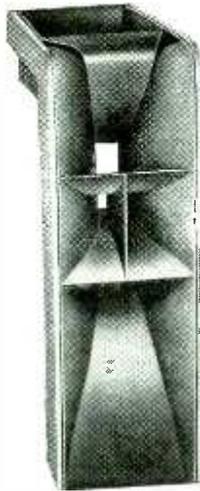

Dimensions of the Corner Ribbon loudspeaker are: height, 34in.; maximum radius, 24in. The high-frequency horn is segmented to give improved sound distribution.

**T**HE development of this high-quality reproducer, which is made by the Acoustical Manufacturing Company, of Huntingdon, has been carried out against a background of measurement and subjective listening tests involving comparison between the original and the reproduced sound. In deciding on the final design, considerations of naturalness and "presence," for which methods of measurement have not yet been evolved, were given due weight.

Essentially, the unit comprises a twin cone diaphragm loudspeaker for low frequencies and a horn-loaded ribbon diaphragm for frequencies above 2,000c/s. The back radiation from the l.f. unit is modified by a two-stage acoustic filter and emanates from a vent at the bottom of the cabinet. Two stages are used to give a smooth downward extension of the low-frequency response without introducing complications in the region of 150-200c/s.


The 0.00025in-thick aluminium ribbon diaphragm of the h.f. unit is loaded at the front by a multiple horn designed to give the optimum distribution both vertically and horizontally. The back radiation is directed towards the corner walls of the room and provides further extension of the sound source. To enhance the realism of orchestra music. On speech the residual directional properties of the main cone predominate and give the appropriate effect of a point source.

We have had an opportunity of listening to this loudspeaker on a variety of programmes, and the manner in which the apparent source adapts itself automatically to the frequency content of the original is strikingly effective. Another outstanding quality of the performance is the transient response. One does not need to wait for loud and dramatic passages in the music to demonstrate this. It is there all the time, in the bowing attack of strings in pianissimo passages and in other subtle ways that will be appreciated by those that have ears to hear. For instance, the difference in quality between a


spherical and an elliptical reproducing point on high-quality recordings is at once apparent

The bass response is smooth, and judging from some organ recordings, effective down to frequencies of the order of 20 to 30c/s. In the top register the character of surface noise is much less objectionable than usual, due no doubt to the effective damping of the ribbon and the absence of resonant coloration. The response has not been measured by the makers above 18 kc/s, but is believed to extend to 30 kc/s.

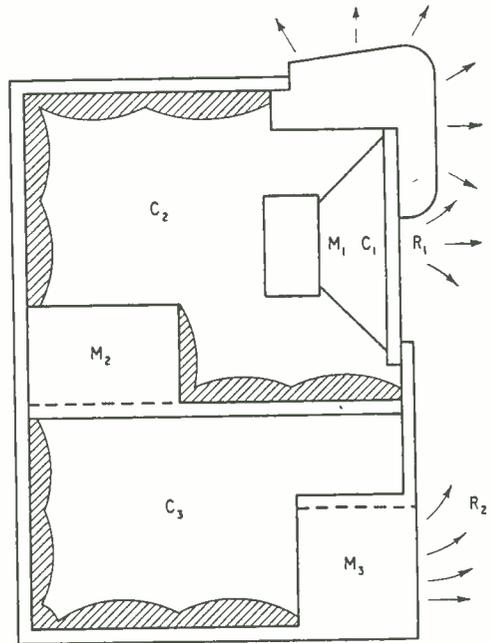A cross-over network is included and the input impedance is 15 ohms. It is important that sustained single-tone inputs to the h.f. unit should not exceed a power of 1.5 watts, but on speech and music the power input to the loudspeaker as a whole can be raised to 12 watts. Normally, the Corner Ribbon loudspeaker will be installed by the manufacturers, and the price is £83.



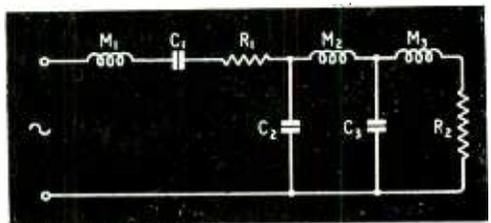Section of bass acoustic filter, with equivalent circuit.  $R_1$  and  $R_2$  represent radiation resistance of the front of the cone and the cabinet vent.



# Amateur Exhibition

*Third Annual Show Held by the R.S.G.B.*

THE visitor seeking advice on any of the products displayed at this year's amateur exhibition rarely found difficulty in obtaining the kind of information he required, as among the staffs of the various firms present could usually be found one or more wearing the familiar R.S.G.B. button hole badge of the licenced amateur.

Keen interest was taken in the latest equipment for the higher radio frequencies, especially for 460 Mc/s (70 cm). A particularly impressive and well-executed corner reflector aerial system was shown by G.S.V., which being constructed of light alloy, weighs 12 lb only and, curiously enough, gives a gain of 12 db over a half-wave dipole.

Any new valves, especially of the v.h.f. variety, were bound to attract attention. G.E.C., for example, had a miniature version of the KT61 output tetrode, the N78, with an anode dissipation of 9 watts and giving 4 watts audio output. It has several applications in small transmitters, such as for crystal oscillator and frequency doubler and tripler up to about 100 Mc/s.

A miniature L63, in the form of the L77, is new and in addition to its use as an a.f. voltage amplifier it finds many applications in transmitting circuits up to 250 Mc/s. Disc-seal triodes cater for the higher frequencies, the DET22 being one that can be used as an oscillator up to 3,000 Mc/s (10 cm). As amateur activities now extend into the 1,215 Mc/s region such valves are of definite interest.

Other new G.E.C. valves were the TT17, an equivalent to the American 820B but with a 19-volt heater, the TT16, which closely resembles the Eimac 4-125A triode. There was also a range of germanium and silicon crystals.

Some of the new miniature valves shown by Standard Telephones have dual personalities in that whilst they appear to be receiving types they can also be used in transmitting circuits. The 12AT7, which is a double triode on the B9A or "Noval" base, makes an efficient frequency changer for v.h.f. superhets,

one triode being the oscillator, the other the mixer. It can be used in this way up to 300 Mc/s.

Also on the Noval base is a miniature r.f. beam power tetrode, the 5763, having an anode dissipation of 12 watts, which finds application as frequency doubler and tripler up to 175 Mc/s and as the output valve in small transmitters.

For still higher frequencies Standard Telephones have a range of disc-seal triodes, one of which, the 3A/147J, or CV82, has already proved its worth in 460 Mc/s amateur equipments. It functions well on quite low voltages and should prove useful in low-power v.h.f. transmitters for radio control of models.

Miniature quartz crystals as used in commercial v.h.f. equipments for some time past are now becoming available to amateurs. The new type F shown by the Quartz Crystal Company has pin spacing to fit an international octal valveholder, two units being easily accommodated in one socket. These have gold plated quartz plates with the crystal suspended in the holder by its connecting wires, a form of shock-proof mounting that renders the crystal practically immune to damage by rough handling.

Examples of miniature plated crystals were shown also by Salford, one type measuring  $\frac{3}{4} \times \frac{3}{4} \times \frac{3}{4}$  in only is fitted with pins to plug into an octal valveholder.


Another method of mounting oscillator and resonant-type crystals is in small glass envelopes with base pins resembling the new miniature valves. This type were shown by Quartz Crystals, Salford and Standard.

The paucity of communications receivers was a matter of some surprise as this kind of set forms the backbone of all amateur stations. Webb's Radio had a fairly comprehensive range of Eddystone sets including the latest model 710, also described as the "All World Six," and designed primarily for overseas use as it takes all power from a 6-volt accumulator. The price is £37 10s.


Several improvements have been made in the Denco DCR19 communications receiver, this set being notable for its unusually high intermediate frequency of 1.6 Mc/s. It has an r.f. and three i.f. stages with eight tuned circuits, and additional selectivity is afforded by a crystal filter and also an audio filter, all individually switchable. The coverage is 36 Mc/s to 175 kc/s and the price is £49 10s.

Redesigned coil turrets with shortened contacts and made largely of polystyrene, some incorporating r.f. and f.c. stages, were shown by Denco, which firm had also a range of television parts, one being a combined line output transformer and e.h.t. unit. But in general components were not over plentiful although Webb's Radio had a range of Eddystone parts and Southern Radio showed examples of Labgear, Q-Max, Raymart and Wearite products.

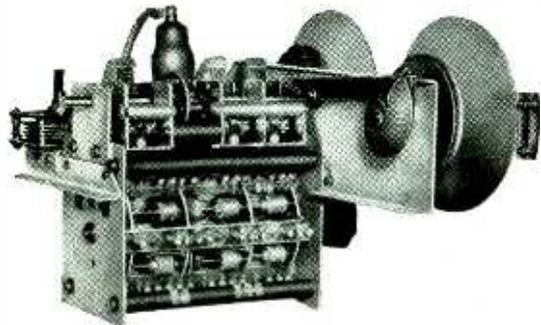The extent to which T.C.C. capacitors cater for all amateur needs was well exemplified by this firm's exhibit, and as befitted the occasion, emphasis was



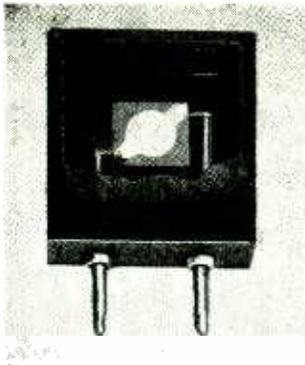
Denco rotary coil turret, Type CT4C, fitted with r.f. and f.c. valves. Mechanical bandspread is incorporated.



Shock-proof mounting of crystal plate adopted by Quartz Crystal Company.



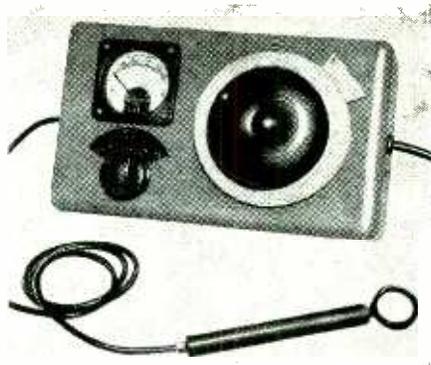Group of T.C.C. miniature capacitors including a Micadisc, Plastapack, Metalicon and various ceramic types.



E.M.I. absorption wavemeter covering 1.6 to 30 Mc/s. There is another model covering the v.h.f. range 100 to 160 Mc/s.

placed on the latest miniature ranges such as Micro-packs, Picopacks, Plastopacks (which are noted for extremely high insulation resistance) and a wide selection of small silvered ceramic capacitors employing the new "High-k" material.

Mains, audio and modulation transformers of various designs and characteristics constituted the Woden exhibit and an opportunity was offered here to examine at first hand the various transformers and chokes needed for the *Wireless World* "Williamson" amplifier.

A.F. components were a feature of the Varley exhibit and these shared space with a range of heavy-duty variable resistors and e.h.t. transformers.

A number of useful pieces of test apparatus, designed especially for amateur stations, were shown by E.M.I. There was an absorption wavemeter, with a germanium crystal and micro-ammeter as the indicator covering 1.6 to 30 Mc/s and a companion model, for the v.h.f. worker, with a range of 100 to 160 Mc/s. Others comprised a grid-dip oscillator, a spot frequency meter with a 1-Mc/s crystal giving detectable harmonics up to the 146th, and a cathode-ray tube modulation indicator.

Taylor Electrical had a comprehensive display of their various items of test gear including a new television signal generator giving a pattern and covering the London and Birmingham frequencies. There were also pointer instruments and instrument parts on this stand while AVO showed a range of Avometers extending back over 25 years for historical interest and supported this with most of their latest products in the test instrument class.

For the discriminating amateur, who likes his station neat, tidy and safe at high voltages, Imhof had a wide range of metal cabinets and associated items, such as panels, chassis and panel fittings. To select one item only, the Model 1022DR cabinet typifies a style that should prove popular, as it accommodates three chassis 17½ in x 10 in with panels 19 x 10½ and it is totally enclosed.

If non-standard cabinets are required the demand can be met by Philpotts Metal works, which firm showed a number of "tailor-made" cabinets.

It may be interesting to record that S. G. Brown's adjustable-reed headphones—much sought after even before World War I—are still made and the latest

pattern, Type "A" closely resemble the early ones in appearance, but the magnet system is greatly improved. They cost £3 17s 6d a pair.

Rola and Celestion loudspeakers, ranging in size from 2½ in to 18 in, were shown by Cyril French in company with a comprehensive selection of McMurdock valveholders, including all the newest miniatures.

Finally, mention must be made of the apparatus displayed by the General Post Office. By a neat arrangement of "trafficator" lamps, the current distribution on correctly and incorrectly terminated twin-wire and co-axial feeders was convincingly demonstrated. Another demonstration showed the latest development in aerial lenses for centimeter wavelengths.

Group of Osram valves including the TT17, L77, N78, DET20 and a Germanium crystal.



The 12AT7, 5763, 2C26A, and 3A/147J valves shown by S.T.C.




# Extending Television

## Second Link in Proposed Chain

WITH the opening of the Midland television station at Sutton Coldfield, some 10 miles north of Birmingham, on December 17th, the second link in the proposed chain of transmitters in the United Kingdom was completed. Although data giving the service area of the Midland station has not yet been completed, Sir Noel Ashbridge has stated that while the average range will be about 50 miles—as shown on the accompanying map—"it will be greater to the east than to the west, where the Welsh hills will constitute a formidable obstacle." During tests reception at two or three times the distance has been recorded.


The vision transmitter, which, together with the control equipment, has been supplied by E.M.I., is operating on 61.75 Mc/s with a power of 35 kW—more than twice the power of Alexandra Palace. The crystal drives for both the vision and sound transmitters have been provided by Marconi's, whilst the vision r.f. amplifiers came from Metrovick. The Marconi 12-kW, Class "B," amplitude-modulated sound transmitter is operating on 58.25 Mc/s.

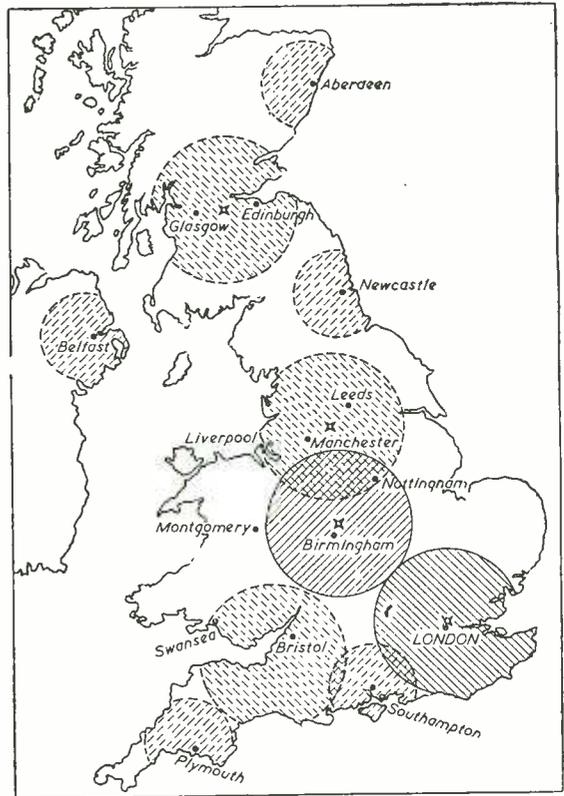
The single wide-band aerial, which will radiate both sound and vision and consists of two tiers of four vertical folded dipoles arranged in cruciform, was designed by the B.B.C. Research Department in



This map gives some idea of the anticipated coverage of the proposed chain of ten stations. Sites for the Bristol and low-power stations are not yet chosen.

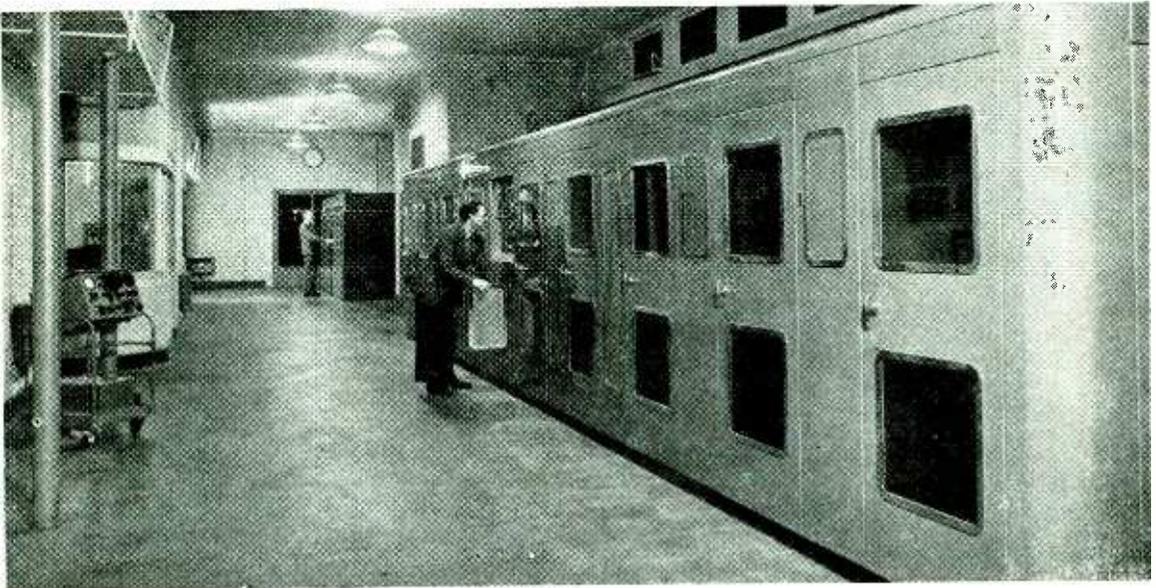The transmitter hall at Sutton Coldfield with the E.M.I. 35-kW vision transmitter in the foreground and, beyond, the Marconi 12-kW sound transmitter.



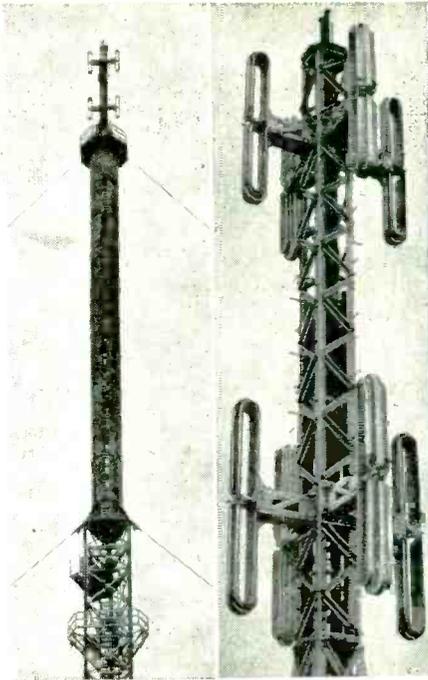

Combined sound and vision aerial array (centre) at the top of the 750-ft mast—constructed by B.J. Callender's Cables—is some 1,300 feet above sea level. The cylindrical structure below the television array (left) includes slot aeriels for the proposed e.h.f. broadcasting experiments.

Control desk for the sound and vision transmitters is shown below.




collaboration with Marconi's, the manufacturers. Sound and vision signals are fed from the respective transmitters to a Marconi "Diplexer," or combining unit, from which the combined transmission is fed to the eight dipoles. We hope later to include a technical description of the station.

The plans for extending the television service to half the population of the United Kingdom within two years and to some 80 per cent by the end of 1954, provide for ten transmitters—five high-power and five low-power. The site for the third main

transmitter has already been chosen at Holme Moss in the West Riding of Yorkshire.

The site for the Scottish station has not yet been announced, although negotiations are said to be proceeding for the purchase of ground near Harthill, Lanarkshire, which is some 10 miles south of Falkirk and equi-distant from Edinburgh and Glasgow. The fifth main station is to be in the Bristol Channel area. The service area of the five low-power stations is of course still a matter of conjecture and they are shown on the map with a 30-mile radius.

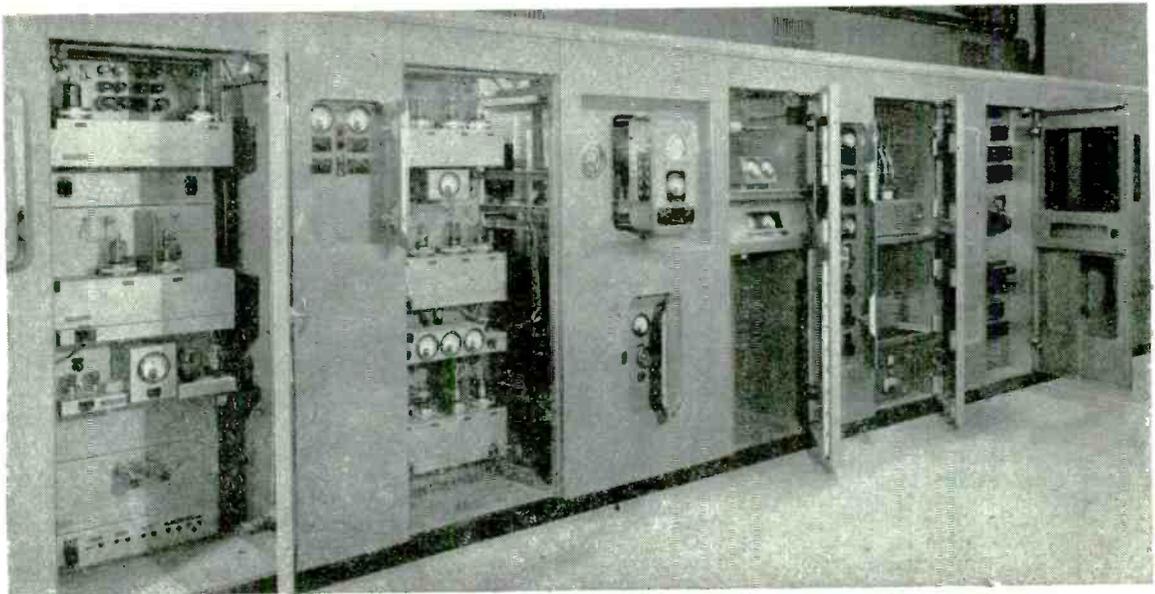Modulator stages of the Sutton Coldfield vision transmitter are on the left and the r.f. stages on the right.



# WORLD OF WIRELESS

## Television Progress ♦ Radar Film ♦ Remotely-Controlled Transmitter ♦ Receiver Production

### Receiving Licences

FOR the first time the monthly increase in television licences exceeded that of "sound" licences.

Of the 12,124,250 broadcast receiving licences current in Great Britain and Northern Ireland at the end of October, 188,350 were for television sets. Increases of 15,300 "sound" and 17,350 television licences were recorded during the month. The record television increase was almost double that in September. One wonders how much the increase in television licences is due to Radiolympia, to the extension of the television service to the Midlands, or to both.

### Ionosphere Disturbances

ADDITIONAL information on ionosphere disturbances is now being radiated by the United States Bureau of Standards transmitter WWV at Washington.

At 19 and 49 minutes past the hour the station now radiates on the standard radio frequencies one of three letters, N, W or U, in Morse, to indicate conditions of the ionosphere. N indicates normal conditions; W that disturbed conditions are present or are expected within twelve hours; and U—the additional classification—that conditions are unstable.

### Marine Radar

A DOCUMENTARY film, "In All Weathers," showing the background against which the pre-eminence of British radar for merchant ships has been achieved, was given a press preview in London recently. It has been made under the auspices of the Central Office of Information and is for showing overseas to stimulate interest in British commercial marine radar.

The film includes some interesting shots of s.s. *Manchester City* berthing at St. John, New Brunswick, at night and in thick weather. It also traces the development of the Ministry of Transport prototype marine radar from Admiralty designs and emphasizes the rigorous performance tests which commercial sets must pass before being granted a Ministry of Transport Certificate of Type-Testing.

Eight types of set made by four manufacturers—Cossor, Metrovick, Kelvin-Hughes and Marconi—have so far passed these tests which are undertaken by the Admiralty Signal and Radar Establishment on behalf of the M.o.T. British merchant ships are now being fitted with commercial radar sets at the rate of 15 a month. Some 400 U.K. ships and over 200 foreign vessels have so far been equipped with British gear.

### Multiple-unit Transmitter

A TRANSMITTER has been designed by Wayne Kerr for unattended operation at remotely controlled stations and is being used by the B.B.C. at the Brighton Third Programme station. It has duplicate low-power radio-frequency and modulator units, and ten identical modulated amplifier units, each of which comprises a r.f. amplifier, series modulator and power supply.

Each unit is provided with an automatic protection circuit which, in the event of a fault, isolates the unit from the remainder of the transmitter. Any five of the ten modulated amplifier units can fail before the transmitter shuts down. With all ten units operating in parallel, as they normally do, the

r.f. carrier power output is 1.5 kW.

The series modulator employs an unconventional circuit, in which the modulator valve acts as a cathode-follower with the modulated amplifier valve as cathode load. Thus all the advantages of a cathode follower are obtained, particularly low distortion.

### Television Sales

RECORD sales of approximately 36,500 television receivers by manufacturers to dealers in October is announced by the British Radio Equipment Manufacturers' Association. The total is a 75 per cent increase on the sales during the whole of the first three years of the television service (1936-1939) and 10,000 more than that for the whole of 1947. The previous highest monthly sales figure was 21,000 in September. Sales in October exceeded production by nearly 10,000.

According to figures issued by B.R.E.M.A. the industry has manufactured 300,000 television receivers since the war. Manufacturers' home sales of broadcast receivers during September reached 100,000—nearly twice the August figure—and radio-gramophones 8,000.

American production figures show that in October nearly 305,000 television sets were made. The total for the year ending October 31st was 1,707,600.

### Airport V.H.F. Radio

DEMONSTRATIONS showing how time and effort can be saved and the working efficiency improved by the use of mobile v.h.f. radio telephones were given recently at London Airport by Marconi.



A section of the Wayne Kerr multiple-unit transmitter is shown withdrawn from its housing on the trolley provided for maintenance.



Marconi walkie-talkie (Type H19) as used by one of the airport staff.

Although weather conditions hampered movements of aircraft and vehicles, reports and ground control instructions were rapidly passed between a temporary headquarters station, members of the staff at distant points equipped with Marconi walkie-talkies and aircraft tenders fitted with the mobile Type H18 two-watt transmitter-receiver. The headquarters station used the 10-watt equipment (Type 16A).

## PERSONALITIES

**Air Comdre. W. E. G. Mann, C.B.E., M.I.E.E., R.A.F. (Ret.)**, has been appointed Director-General of Navigational Services in the Ministry of Civil Aviation in succession to Air Comdre. W. G. P. Pretty, O.B.E., who was seconded from the R.A.F. to the M.C.A. During the war Air Comdre. Mann was Chief Signals Officer, R.A.F. Middle-East, and since joining the M.C.A. has held several administrative telecommunications posts. Since August 1948 he has been Director of Navigational Services (Telecommunications).

**R. W. J. Sullivan, B.Sc.**, who succeeds Air Comdre. Mann as Director of Navigational Services (Telecommunications) at the M.C.A., began his radio career as a student apprentice at Siemens and was subsequently in the Technical Service Department of Radio Transmission Equipment, Ltd., a subsidiary of Mullards. During the war he was at Fighter Command headquarters. He was appointed Assistant Director of Telecommunications at the M.C.A. in 1947 and Deputy Director of Telecommunications in 1948.

**Hugh Townsend, C.B.**, is retiring from the position of Director of Telecommunications, G.P.O., to take up the post of Assistant General Secretary of the International Telecommunications Union. He will commence work in Geneva in January. He has been a member of the present Government Television Advisory Committee since it was formed in 1945.

**B. J. Edwards, M.B.E.**, technical director of Pye, Ltd., is leading the team of eight technicians who are demonstrating the company's television transmitting and receiving equipment in the U.S.A. The first demonstration was in Washington on November 21st.

**Peter E. M. Sharp, B.Sc. (Eng.)**, who has been appointed Industrial Officer (electronic equipment) with the Council of Industrial Design, was, until recently, with Standard Telephones and Cables, where he was responsible for the production of technical publications. He will be responsible for liaison between manufacturers of electronic gear and the Festival of Britain, and for that part of the 1951 Stock List—from which exhibits will be selected—dealing with domestic radio and television, industrial electronics, radar and communications equipment.

**Leslie Hotine**, who, as recorded last month, was recently placed in charge of one of the two sections of the reorganized Operations and Maintenance Departments of the Engineering Division of the B.B.C., is leaving the Corporation after more than 26 years' service. He was successively engineer-in-charge of the Glasgow, Daventry and Brookman's Park stations and, since 1943, has been Senior Superintendent Engineer.

**J. P. Jeffcock, O.B.E., M.I.E.E.**, has joined Mullard Electronic Products, Ltd., as commercial manager of the Equipment Division, and has been appointed a director of Mullard Equipment, Ltd. From 1929 to 1936 he was with the Western Electric Co., engaged in the design of sound-on-film equipment. He joined the Air Ministry in 1936 and the Ministry of Aircraft Production in 1941. He was appointed a member of the Civil Aviation Radio Advisory Committee in 1942, and organized the Central Radio Bureau,



J. P. Jeffcock joins Mullards.

which has continued in peacetime to promote the exchange of information between the U.S.A. and the British Commonwealth.

## IN BRIEF

**Wrotham.**—It is understood that the Marconi f.m. transmitter which has been installed at Wrotham, Kent, for the B.B.C. has passed the initial tests and has been accepted by the Corporation. It will be recalled that this 25-kW trans-

mitter will be used initially for experimental work preparatory to the erection of a chain of some 30 e.h.f. stations to cover the whole of the country.

**F.M. Criticized.**—C. O. Stanley, director of Pye, Ltd., has criticized the B.B.C. expenditure on f.m. in an address to the members of the Brit. I.R.E. in these terms:—"At the time when every penny of capital was wanted to establish television they [the B.B.C.] started on this Wrotham station. It may be a very interesting scientific investigation. The fact that it has been investigated elsewhere in the world and most things are known about it does not seem to have had much weight with the B.B.C. . . . Today in America broadcasting time on f.m. transmission is very nearly unsaleable . . . I am sure that if the energy and money that have gone into f.m. broadcasting had been available for television we would have been much better off."

**American Praise** for the Williamson amplifier is voiced in an article in *Audio Engineering*, November 1949. The authors (David Sarser and Melvin C. Sprinkle) of "Musician's Amplifier—an adaptation of a famous English circuit" add this peroration: "To a couple of fiddlers—one who fiddles all day on a Stradivarius, the other who fiddles all day with amplifiers, this amplifier is the best we have heard."

**Amateur V.H.F. Achievement.**—What is believed to be the first amateur two-way telephony communication in this country in the 1215-1300Mc/s band (24cms) was made by stations G8DD/P and G6CW on November 17th. Conditions were far from ideal as owing to rain one transmitter-receiver was located indoors with the aerial behind a closed window, while the other operated—complete with aerial—from inside a car. Despite these adverse conditions signals were S9 in both directions over a distance of 4½ miles.

**Faraday Lecture.**—This year's Faraday lecturer is Dr. R. A. Smith, M.A., superintendent of the Research Department of the Telecommunications Research Establishment, Great Malvern. His subject is radar. The lecture was first given at Birmingham on December 5th and, as will be seen from "Meetings," is being repeated at other I.E.E. centres. The London lecture, which will be given at the Central Hall, Westminster, on January 18th at 6.30, is open to the public.

**Television Fund.**—Admiral Dorling, director of the R.I.C., is a member of the committee of the National Television Fund which has been established to "create resources from which grants may be made to provide sets in places where, for example, sick or crippled children or aged people may otherwise be without hope of enjoying the facilities of television." The fund is operating under the aegis of the British Charities Association. Donations should be sent to 12, Whitehall, London, S.W.1.

**Index to "W.E." Abstracts.**—A monthly feature of our sister journal, *Wireless Engineer* is the section devoted to abstracts from and references to articles appearing in the world's technical journals. Throughout the year

some 3,600 abstracts and references are published and an index to these is issued by our Publishers. Copies of the 1949 index, price 2s 6d plus 2d postage, should be available in February.

**Fleming Centenary.**—To mark the centenary of the birth of Sir Ambrose Fleming—November 29th—the Science Museum, South Kensington, exhibited the original "oscillation valve," which was invented in 1904, in a place of honour for two weeks.

**"Television Explained."**—A third (fully revised) edition of this popular book by W. E. Miller, Editor of our associated journal, *The Wireless Trader*, has now been issued. The television receiver circuit is split up into self-contained units and a chapter devoted to each. Aerials and the nature of the television signal are also covered, and there are some useful screen photographs showing how various faults reveal themselves. The book is distributed by our Publishers and costs 5s (by post 5s 4d).

**Distress Signals.**—An additional v.h.f. radio-telephone channel is now being used by the R.A.F. for the location of lost aircraft. This is the International Aeronautical Distress Channel of 121.5 Mc/s which is in addition to those given in our September issue.

**Electronics Exhibition.**—An exhibition of industrial electronics is being organized by the Midlands Branch of the Institution of Electronics to be held at the Exhibition Floor, Lewis's, Ltd., Bull Street, Birmingham, 4, on January 5th, 6th and 7th. Further particulars are available from Dr. W. Summer, 31 Beech Road, Bournville, Birmingham, 30.

**Canadian Television.**—Commenting on the recent announcement that American rather than British equipment will be used in the C.B.C. television stations at Toronto and Montreal, the Director of Television at the Academy of Radio Arts said "... after a great deal of study and comparison, I am fully convinced that it [British equipment] is every bit as good [as American] and that the old country product possesses many operational characteristics and innovations that are truly unique. It is perhaps not as well styled as the American counterpart, but it is a great deal more functional.

**G.E.C. in Singapore.**—The sound reproducing equipment installed in the Victoria Memorial Hall, Singapore, for the recent United Nations conferences was supplied by the G.E.C. It included 29 microphones with a separate line amplifier for each channel. The G.E.C. has also installed in the Singapore area v.h.f. radio-telephone equipment providing inter-island communication for the oil depots of the Shell Oil Co. and the Standard Vacuum Oil Co.

**Egypt.**—Two high-power short-wave broadcasting transmitters have been ordered by the Egyptian Government from Standard Telephones and Cables for installation at a new station under construction at Abu Zabal, about 12 miles from Cairo.

**Car Radio.**—The current price of the Ekco Model CR61 car radio receiver, reviewed in our December issue, is now £31 10s, inclusive of all accessories except the aerial. The home sales purchase tax is £6 16s 6d.

## NEW ADDRESSES

**Allen Components, Ltd.**, of Tower Road, London, N.W.10, manufacturers of radio and television coils and transformers, etc., have moved to 1 Shrewsbury Road, Stonebridge, London, N.W.10. (Tel.: Willesden 3675.)

**International Aeradio, Ltd.**—A typographical error appeared in the note in our last issue announcing the company's change of address. The new head office is 40 Park Street, London, W.1.—not Parker Street.

**Speaker Services, Ltd.**, have moved to new premises at Central Road, West Hoe, Plymouth, and are now able to undertake repairs to Rola Types F, 5Z, 6Z, 8Z, 10Z and pre-war G12 loudspeakers.

**Sinclair Speakers.**—The head office of Electrical Sound and Television Patents, Ltd., manufacturers of Sinclair loudspeakers, has been transferred from Pembroke Street, London, N.1, to the factory at 3 and 4, Manor Way, Boreham Wood, Herts.

**Willesden Transformer Co.** has moved from 28, Balmoral Road, London, N.W.2, to 781, Harrow Road, London, N.W.10 (Tel.: Ladbroke 2846).

**Engineering Appointments.**—The offices of the Professional Engineers' Appointments Bureau have been moved from 13 to 9, Victoria Street, London, S.W.1 (Tel.: Abbey 1737).

## MEETINGS

### Institution of Electrical Engineers

"Radar Echoes from Precipitation," by J. E. N. Hooper, B.Sc., and A. A. Kippax, B.Sc.Tech., at 5.30 on January 12th.

Faraday lecture on "Radar," by R. A. Smith, M.A., Ph.D., at 6.30 on January 18th, at the Central Hall, Westminster, London, S.W.1.

**Radio Section.**—"The Relative Merits of Presentation of Bearings by Aural-Null and Twin-Channel Cathode-Ray Direction-Finders," by S. de Walden, Dipl. Ing., and J. C. Swallow, M.A.; and "Some Experiments on the Accuracy of Bearings Taken on an Aural-Null Direction-Finder," by F. Horner, M.Sc., at 5.30 on January 11th.

"Factors Influencing the Design of a Rubber Model," by G. B. Walker, M.A.; and other demonstrations of apparatus for solving the Laplace equation by E. Colin Cherry, M.Sc. (Eng.), and E. E. Hutchings, B.Sc. (Eng.), at 5.30 on January 17th.

**Electronic Components**—Government and Industrial Relations and Co-operation; Commercial, Professional and Service Standards," discussion opened by D. H. Black, Ph.D., and N. F. S. Hecht, at 5.30 on January 23rd.

Unless otherwise stated, the above meetings will be held at the I.E.E., Savoy Place, London, W.C.2.

**Cambridge Radio Group.**—"The Application of Differential Analyzers with Electrolytic Tanks for Tracing Electron Trajectories," by K. F. Sander, M.A., at 8.15 on January 17th, at the Cavendish Laboratory.

**Mersey and N. Wales Centre.**—"Hot-Cathode Thyratons: Practical Studies of Characteristics," by H. de B. Knight, M.Sc., at 6.30 on January 2nd at the Liverpool Royal Institution, Colquitt Street, Liverpool.

**North - Western Centre.**—"Radar Echoes from Precipitation," by J. E. N. Hooper, B.Sc., and A. A. Kippax, B.Sc. Tech., at 6.15 on January 3rd at the Engineers' Club, Albert Square, Manchester.

**North - Western Radio Group.**—"Some Considerations in the Design of Negative-Feedback Amplifiers," by W. T. Duerdoh, B.Sc. (Eng.), at 6.30 on January 18th, at the Engineers' Club, Albert Square, Manchester.

**Southern Centre.**—Faraday lecture on "Radar," by R. A. Smith, M.A., Ph.D., at 6.30 on January 20th at the Guildhall, Southampton.

**Western Centre.**—"The Application of Frequency Modulation to v.h.f. Multi-channel Radiotelephony," by J. H. H. Merriman, M.Sc., and R. W. White, B.Sc., at 6.0 on January 2nd at the South Wales Institute of Engineers, Park Place, Cardiff.

Faraday lecture on "Radar," by R. A. Smith, M.A., Ph.D., at 6.30 on January 13th at the Brangwyn Hall, Swansea.

### British Institution of Radio Engineers

**London Section.**—"The Performance and Stability of Permanent Magnets," by A. J. Tyrrell, at 6.30 on January 19th at the London School of Hygiene and Tropical Medicine, Keppel Street, London, W.C.1.

**South Midlands Section.**—"Commercial Marine Radar," by M. J. Millane, B.Sc., at 7.0 on January 26th, in Room A5, The Technical College, Coventry.

**Scottish Section.**—"Ultrasonics," by B. E. Noltingk, Ph.D., at 6.45 on January 5th at the Heriot-Watt College, Edinburgh.

**West Midlands Section.**—"The Performance and Stability of Permanent Magnets," by A. J. Tyrrell at 7.0 on January 25th, at the Wolverhampton and Staffordshire Technical College, Wulfruna Street, Wolverhampton.

**North-Eastern Section.**—"Activities and Equipment of an Industrial Electronic Laboratory," by G. H. Hickling, at 6.0 on January 18th at Neville Hall, Westgate Road, Newcastle-on-Tyne.

### Television Society

**London Meeting.**—"High-Frequency Cables in Television," by R. C. Mildner (Telecon), at 7.0 on January 27th at the Cinema Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

**Constructors' Group.**—"Some Aspects of Single-Sideband Receiver Design," by W. M. Lloyd, B.Sc. (Bush Radio), at 7.0 on January 12th at the Cinema Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

**Midlands Centre.**—"Some Problems Associated with Synchronizing Signals," by C. E. Horner (Philips Electrical), at 7.0 on January 2nd at the Lecture Hall, The Crown Restaurant, Corporation Street, Birmingham.

### British Sound Recording Association

**London Meeting.**—"Magnetic Tape: Its Properties and Measurement," by G. F. Dutton, Ph.D., at 7.0 on January 27th at the Royal Society of Arts, John Adam Street, London, W.C.2.

### Radio Society of Great Britain

"The Use of v.h.f. for Radiotelephone Services," by J. Neale, B.Sc. (Eng.), (Post Office Engineering Department), at 6.30 on January 27th at the I.E.E., Savoy Place, London, W.C.2.

# Easing Impedance Calculations

By M. G. SCROGGIE, B.Sc., M.I.E.E.

## Rearranging the Expression for Continuous Slide-Rule Operation

THE fact that one is so often obliged to evaluate expressions of the form  $x = \sqrt{a^2 \pm b^2}$  is an irritating feature of a.c. calculations. Finding the value of Z, R or X (given two of them) is the commonest example of this type of work, but of course there are others, such as adding currents or voltages having 90° phase displacement or different frequencies. It can be dodged to some extent by the use of *j*, but sooner or later one is bound to want the modulus (or magnitude). To find  $a^2$  and  $b^2$  with the slide-rule necessitates two operations; pencil and paper are then usually needed to add them together before performing the final operation of taking the square root. During this sequence of four separate operations it is only too easy to go wrong with the decimal place.

By a slight rearrangement of the expression it can be evaluated in one continuous slide-rule operation in about half the time, and with less likelihood of making a slip. Assuming for the moment that the positive sign applies, as in calculating Z from R and X, and that *a* stands for the larger of the two knowns, the rearranged form is

$$x = b \sqrt{\left(\frac{a}{b}\right)^2 + 1}$$

Adopting the convention of referring to the four basic scales of a slide-rule by the letters A, B, C and D (reading from top to bottom), divide *a* by *b* in the usual way by bringing *b* on C over *a* on D.  $(a/b)^2$  is then indicated on scale A by the end of B. Next, move the slider to the right to increase this figure by 1. The end of scale C will then point to  $\sqrt{(a/b)^2 + 1}$  on scale D, while *b* on scale C points out the answer, *x*. It may, of course, be necessary to shift the slider a distance equal to the length of scale C in order to get the final reading. The whole business takes less time to do than to describe, and the saving of time and mental effort is very considerable, especially in work involving a succession of values of R and X.

As an example, suppose  $a = R = 15.4 \text{ k}\Omega$  and  $b = X = 8.75 \text{ k}\Omega$ . With the rule set to divide 15.4 by 8.75, the 100 end of the B scale marks 3.10 on A. When it is shifted up to 4.10, 8.75 on the C scale marks 17.7 on D, which is the answer, Z, in  $\text{k}\Omega$ . There is no uncertainty about the decimal place, because the answer is bound to be between *a* and  $\sqrt{2}a$ .

Provided that *a* is not more than nearly 10 times *b*, there is also no room for doubt about how much of the A scale represents 1 when performing the addition, because the scale markings, 1 to 100, hold good as they are. If *a* does exceed 10*b* there is seldom much

point in doing any calculation at all, for the error in regarding *x* as equal to *a* does not then exceed 0.5%. However, if the method is used when  $a > 10b$ , the A scale must be reckoned as running from 100 to 10,000, and of course this makes the shift of 1 look very small.

An alternative method, by which small differences between *x* and *a* can be calculated very accurately, will be described in a moment or two; but in the meantime the procedure for calculating R or X, given Z and X or R, should be noted. Since the formula is

$$R = X \sqrt{\left(\frac{Z}{X}\right)^2 - 1}$$

(or the corresponding one with R and X interchanged), the only difference is to subtract 1 instead of adding it. Try it by working the above example backward. Finding R by dividing 17.7 by 8.75, and then shifting the slider from 4.1 to 3.1 on the A scale, reading  $R = 15.4$ , calls for no comment. But if X is the unknown, dividing 17.7 by 15.4 indicates 1.32 on the A scale. Deducting 1 gives 0.32, which necessitates moving the slider to the right so that 1 on B corresponds with 32 on A. Unless one does this carefully with a large slide-rule, the answer is likely to look more like 8.70 than 8.75, because it is difficult to read scale A accurately enough to see that the original figure should be 1.322+. (Calculating the smaller of the two components of impedance is liable to result in relatively large errors whatever method is adopted.) Although examples such as the last involve a shift of decimal place on scale A, they should cause no confusion, since it is a logical consequence of following the general method.

It may be interjected here that the trick of transforming a sum or difference of two quantities into (a ratio  $\pm 1$ ) is widely useful, and often leads to a clearer picture of the situation. "Cathode Ray" has recently given some examples.\*

It is not always realized how rapidly *x* approaches *a* as *a/b* increases. The difference when *a/b* is 10 is, as already stated, only 0.5%. Figures worth noting are:

$\frac{a}{b}$	Difference between <i>x</i> and <i>a</i>
7	1%
10	0.5%
22.4	0.1%

\* "Generalized Graphs," Sept. 1949; "Smoothing Circuits," Oct. and Nov. 1949.

### Easing Impedance Calculations

If for any reason one wants to know with some accuracy how much larger  $x$  is than  $a$  when  $a$  is considerably larger than  $b$ , this can be done very simply by an alternative method. The first two terms in the binomial expansion of  $(a^2 + b^2)^{1/2}$  are  $a$  and  $b^2/2a$ . The latter is, of course, easily computed by marking the smaller quantity,  $b$ , with the cursor on scale D, giving  $b^2$  on scale A. The latter is then divided by  $2a$  by movements of scale B.

For example, suppose the reactance of a circuit is known to be  $245\Omega$  and its series resistance  $15\Omega$ . What is its impedance? Computing  $15^2/(2 \times 245)$  gives 0.46, so  $Z$  is  $245.46\Omega$ . Note that by this method the answer can (assuming sufficient accuracy of data) be given correct to more significant figures than a slide-rule is capable of when used straightforwardly. Reckoning in differences, when they are

relatively small, is another trick with a wide range of application.

The third term in the binomial expansion, representing the major part of the error here is negative. Even when  $b$  is as much as  $a/3$ , it is only  $-0.1\%$  of  $x$ , so for large values of  $a/b$  it is extremely small.

Transforming resistances and reactances in series into their parallel equivalents, or vice versa, invariably brings in  $R^2 + X^2$ . The larger of the two quantities being denoted, as before, by  $a$ , the form of expression can be altered for purposes of slide-rule calculation to  $b^2 [(a/b)^2 + 1]$ . The advantages are not quite so pronounced as in the first method described here, but are worth considering. The procedure is identical except that the answer is read on scale A instead of D. And the decimal point can usually be located without difficulty, remembering that the answer must be between  $a^2$  and  $2a^2$ .

## NEW TELEVISION RECEIVER

### *Two-Unit Design to Simplify Maintenance*

THE English Electric Co. has entered the television field with a receiver, Model 1550, having some unusual features. Designed in conjunction with Marconi's W. T. Co., an associate of English Electric, the receiver is of the console type with a 15-in. c.r. tube and in addition to television, provision is made for reception of the B.B.C. experimental f.m. transmissions.

The set is of the superheterodyne type with one r.f. stage. On the sound side there are three i.f. stages followed by a diode detector for a.m. or a discriminator and double-diode detector for f.m. A triode audio stage and a tetrode output valve with negative feedback are fitted. On vision there are four i.f. stages with single-circuit couplings and traps for sound-channel rejection, a diode detector, a diode sync separator and one v.f. stage.

The 15-in. tube is operated at 9kV which is obtained from a ringing choke circuit and rectifier; this is pulsed at line frequency through a tetrode valve. The tube has an ion trap with permanent magnets and a permanent magnet is also used for focusing. A fine adjustment of focus is obtained by varying the e.h.t. supply by a control which adjusts the screen potential of the "ringing-choke" valve.

Magnetic deflection is used with a high-inductance frame coil. The h.t. supply is taken straight from the mains through a metal rectifier and smoothing circuit and an auto-transformer is used for the heater supplies. For use in areas


subject to interference a special sync circuit can be provided. This takes the form of a transformer and additional valves which can be plugged into sockets provided and which then give a fly-wheel effect to the line-scanning circuit and enable it to run regularly upon the mutilated sync pulses which are likely in areas of poor field strength. The system is termed synchrophase, and is arranged as a plug-in unit because it is an unnecessary refinement in the normal good-reception areas.

Mechanically, the main chassis carries all parts but the power supply and is removable from the cabinet in a matter of seconds. All inter-unit connections are by plug and socket and two thumb screws hold the chassis to the cabinet. This chassis is actually in two halves—a time-base unit and the receiver proper. They can be separated without removing the tube by undoing a few screws and, again, the connections are by plug and socket.

For work on the chassis a metal frame is available which plugs into holes provided and which enables the chassis to be turned upside down for servicing without any risk of damaging the tube.

It is intended that servicing shall be carried out by means of a unit replacement scheme by which method it is hoped to put any receiver into service again in a maximum of 48 hours.

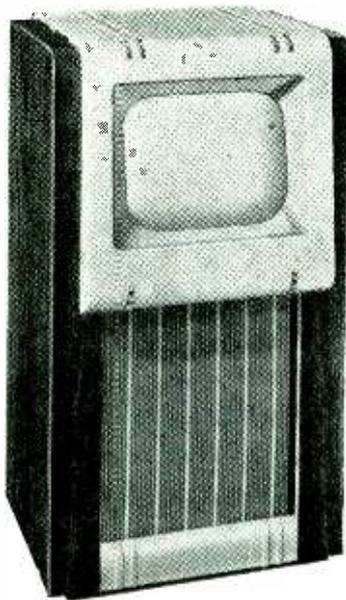The makers are English Electric Co. of Queen's House, Kingsway, London, W.C.2, and the set is priced at 90 guineas, plus purchase tax.



English Electric Model 1550 console television receiver with 15-in. tube.

# Electronic Circuitry

Selections from a Designer's Notebook

By J. McG. SOWERBY (Cinema-Television, Ltd.)


## COUPLINGS IN D.C. AMPLIFIERS

**D**IRECT coupled amplifiers are used in a variety of applications ranging from amplifiers for oscilloscopes to industrial electronic equipment of various types. The design of such amplifiers is often quite specialized, and to those unfamiliar with these devices one of the commonest sources of difficulty is the question of the coupling between successive stages.

In ordinary amplifiers for audio signals, say, the coupling presents no difficulty and the ordinary RC coupling is commonly used. Such a coupling does not transmit zero frequency however, and as soon as extension to zero frequency is required, difficulties begin to arise. The simplest coupling in d.c. amplifiers is that shown in Fig. 1, which is really not a coupling at all inasmuch as the grid of the second stage is directly connected to the anode of the first. Unfortunately the anode of  $V_1$  is positive to earth by the voltage  $V_a$  and this is equally true of the grid of  $V_2$ . For this reason the cathode of  $V_2$  must be held at a positive voltage  $V = (V_a + V_k)$ , where  $V_k$  is the bias voltage for  $V_2$ .

In practice it is inconvenient to use a battery to supply  $V$ , so that the cathode of  $V_2$  is either tapped into a bleeder network across the h.t. supply, or, better, held at the required voltage by a cathode follower as in Fig. 2. If  $V_2$  and  $V_3$  are similar valves, then if the grid of  $V_3$  is held at a positive potential equal—or nearly so—to  $V_a$ , suitable working conditions will be obtained for  $V_2$ . The standing current in  $V_2$  will be approximately  $V_a/2R_k$ , and the same will be true of  $V_3$ . It is obvious from the circuit that  $V_2$  and  $V_3$  form a cathode coupled pair with an anode load on one valve only ( $R_{a2}$  on  $V_2$ ). If  $V_2$  is a triode, then the usual Miller effect will throw a relatively large capacitance across  $R_{a1}$ . This may be avoided by short-circuiting  $R_{a2}$ , and placing an equal load ( $R_{a3}$ ) in the anode circuit of  $V_3$ , as shown dotted. The gain of the

Fig. 1. A simple anode-grid coupling in d.c. amplifiers

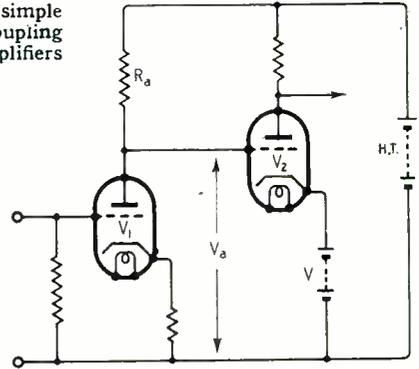

$V_2$ ,  $V_3$ , circuit from the grid of  $V_2$  to the anode of  $V_3$  is given by :

$$A_{2,3} = \frac{\mu R_{a3}}{R_{a3} + 2r_a + \frac{r_a(R_{a3} + r_a)}{(\mu + 1)R_k}} \dots \dots (1)$$

where  $\mu$  = amplification factor } of  $V_2$  and  $V_3$   
 $r_a$  = anode resistance

The disadvantage of this method of coupling is the high value of h.t. supply potential ( $V_b$ ) required. Provided the grid-cathode bias of  $V_2$  and  $V_3$  is small compared with  $V_a$ , the effective supply potential for  $V_2$  and  $V_3$  is only  $(V_b - V_a)$ , and this must be sufficient to supply the voltage drop across  $R_{a3}$  (or  $R_{a2}$ ), and the anode potentials of  $V_2$  and  $V_3$ . It would be more convenient if we could arrange to operate the cathode of  $V_2$  at earth potential; this may be done with the circuit of Fig. 3.

In Fig. 3 a negative supply of  $V_c$  volts is used. If  $V_2$  is to be operated at zero bias, it turns out that  $(V_c R_1 = V_a R_2)$  is the condition which must be satisfied. In fact the grid of  $V_2$  will nearly always be

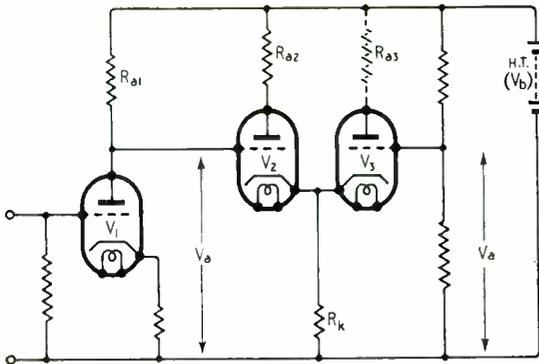


Fig. 2. Direct coupling on to cathode-coupled pair, with cathode of  $V_2$  held at required voltage by  $V_3$

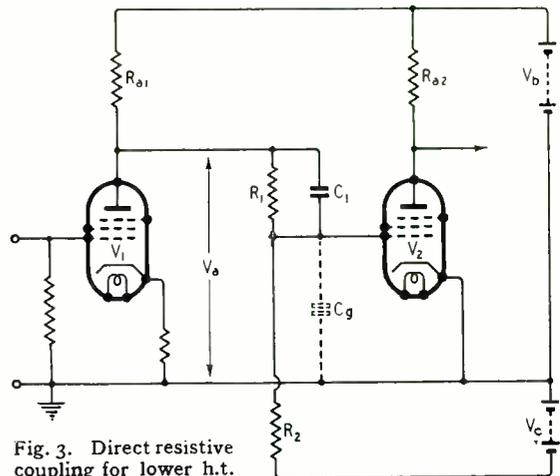


Fig. 3. Direct resistive coupling for lower h.t.

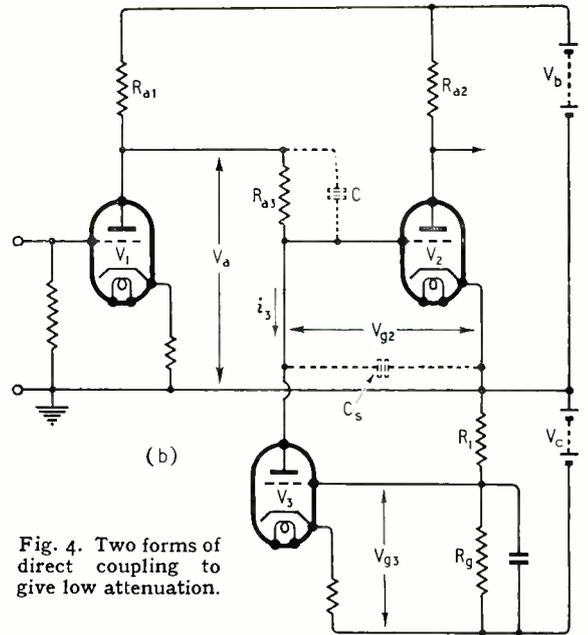
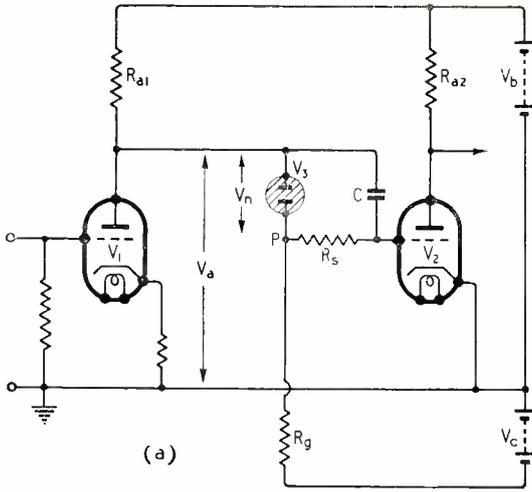


Fig. 4. Two forms of direct coupling to give low attenuation.

operated negative to earth, so that this simple expression is only an approximation. However if  $V_c$  is large compared with the grid base of  $V_2$ , the bias of  $V_2$  may be neglected in the calculation of  $V_c$ . The disadvantage of this method is obviously the fact that an attenuation of  $R_2/(R_1 + R_2)$  is inserted between the two stages, and if  $V_a = V_c$  the loss will be one half. A virtue may be made of this disadvantage if high frequencies are important, as  $R_1$  may be shunted by a condenser  $C_1$  to make the time constant  $R_1 C_1 = R_2 C_g$ , where  $C_g$  is the input capacitance of  $V_2$ . The attenuation of the  $R_1, R_2$  network is then independent of frequency, and the capacitance loading on the anode of  $V_1$  by the grid circuit of  $V_2$  is reduced from  $C_g$  to  $C_g/(1 + C_g/C_1)$ .

**Low Attenuation Couplings**

In purely low frequency applications, the loss of gain introduced by the coupling may be important and two means have been found for overcoming this disadvantage; these are shown in Fig. 4(a)<sup>1</sup> and (b)<sup>2</sup>. At (a) a gas discharge stabilizer tube has been substituted for  $R_1$  of Fig. 3. As such a tube has the property of maintaining a nearly constant potential across its terminals, it follows that any changes at the anode of  $V_1$  will be transferred without alteration in amplitude to the point P. As the point P will have to be negative to earth by the bias of  $V_2$ , a series resistor,  $R_g$ , to a negative supply,  $V_c$ , is needed to maintain sufficient current in the stabilizer to maintain the discharge. It is not difficult to see that the minimum safe value of  $V_c$  is given by:

$$V_c \text{ min} = V_s + V_g$$

where  $V_s$  is the striking voltage of  $V_3$ .

In order to maintain  $V_2$  at the required bias ( $V_g$ ) it is also not difficult to see that

$$V_n = V_a + V_g$$

where  $V_n$  is the running voltage of  $V_3$ .

The resistance  $R_s$  and the condenser  $C$  are included because stabilizer tubes often have an impedance varying with frequency.

If  $R_s$  is made large compared with the nominal

internal resistance of  $V_3$  ( $R_n = 500 \Omega$  or so) and the time constant  $CR_s$  made sufficiently long (1/10 to 1/100 second), variations of  $R_n$  with frequency become unimportant at the higher frequencies, as  $C$  progressively approximates to a short circuit as the frequency increases.

Because of these difficulties with stabilizer tubes the alternative circuit of Fig. 4(b) is sometimes used. In this arrangement the valve  $V_3$ , and its anode and cathode loads  $R_{a3}$  and  $R_k$ , form the coupling network. As readers are well aware, the use of negative current feedback introduced by a cathode resistor leads to a very high effective anode resistance,  $r_{ao}$ . In fact

$$r_{ao} = (\mu_3 + 1)R_k + r_{a3} \dots \dots \dots (2)$$

where  $r_{a3}$  = anode resistance of  $V_3$ . So that the transmission of the coupling is

$$T = \frac{(\mu_3 + 1)R_k + r_{a3}}{(\mu_3 + 1)R_k + r_{a3} + R_{a3}} \dots \dots (3)$$

If  $V_3$  is a high- $\mu$  valve this transmission is generally not far short of unity.

The circuit is easy to design if  $V_3$  is a high- $\mu$  valve, for then the current,  $i_3$ , in  $V_3$  is nearly  $V_{g3}/R_k$ , and the voltage drop across  $R_{a3}$  is  $i_3 R_{a3} = \frac{R_{a3}}{R_k} V_{g3}$ .

In practice low current high- $\mu$  valves like the 6Q7G, or 6F5G, are very suitable for the  $V_3$  position, and the coupling transmission then approaches unity. Taking a practical example let us make  $V_a = 145$  volts,  $V_{g3} = 50$  volts,  $R_k = 100 \text{ k}\Omega$ , so that  $i_3 = \frac{1}{2} \text{ mA}$  approx. If the required bias on  $V_2$  ( $V_{g2}$ ) is 5 volts,  $R_{a3}$  must drop  $145 + 5 = 150$  volts at  $\frac{1}{2} \text{ mA}$ . Thus  $R_{a3} = 300 \text{ k}\Omega$ . If  $\mu_3 = 50$  and  $r_{a3} = 70 \text{ k}\Omega$  (for a 6Q7G) the transmission turns out to be

$$T = \frac{51 \times 100 + 70}{51 \times 100 + 370} = 0.945$$

If good high frequency performance is required—when  $V_1$  and  $V_2$  will usually be pentodes— $R_{a3}$  may be shunted by a condenser  $C$  so that  $CR_{a3} = C_s r_{ao}$  and

<sup>1</sup> Miller, S., *Electronics*, Nov. 1941.  
<sup>2</sup> Valley and Wallman, "Vacuum Tube Amplifiers," p. 486.

then the value of  $T$  will become independent of frequency. In our example above  $r_{ao}$  was  $5.17M\Omega$ , and if we assume  $C_s = 20pF$ , a likely value,  $C = 5.17 \times 20/0.3 = 345pF$ . In the circuit of Fig. 4(b), the bias of  $V_2$  may be adjusted over a small range by variation of  $R_k$  or  $R_g$  with but little change in the transmission of the coupling.

One other<sup>3</sup> rather interesting coupling is very useful for wideband direct coupled amplifiers. This is a variant on the ordinary resistive coupling of Fig. 3, and is shown in Fig. 5. It is applicable only when  $V_1$  is a pentode as shown. In wideband amplifiers it is essential to use a low value of anode load, in order that the inevitable stray shunting capacitance shall produce the usual droop in the high frequency response at some conveniently high frequency. If  $R_{g1}$  in any of the previous circuits is made small, then  $V_a$  would assume a value approximating to the full h.t. potential. This involves a greater loss in the coupling than is the case with Fig. 5.

Consider now the circuit of Fig. 5 at some high frequency, but not so high that the stray capacitance has produced noticeable loss of gain. At such a frequency  $C_d$  is a virtual short-circuit, and so is  $C_1$ . Thus the load on  $V_1$  is  $R_a$ , and all the signal voltage across  $R_a$  is transmitted to the grid of  $V_2$  through  $C_1$ . Now consider the circuit at zero frequency. The total load on  $V_1$  is  $(R_a + R_{ad})$  so that  $V_a$  may be made relatively low compared with  $V_b$ . At the same time any zero frequency signal is transmitted to  $V_2$  with a loss of  $R_2/(R_1 + R_2)$ . If  $(R_a + R_{ad})$  is small compared with  $r_a$  of  $V_1$ , the gain of  $V_1$  will be proportional to the anode load. If the gain times the coupling loss can be made constant at all frequencies where loss of gain due to stray capacitance is negligible, a very advantageous result will have been secured. In the arrangement shown we may take the signal current ( $I_a$ ) in  $V_1$  to be constant with constant input ( $v$ ), and in passing we see that

$$I_a = \frac{g_{m1}v}{1 + g_{m1}R_k} \dots \dots \dots (4)$$

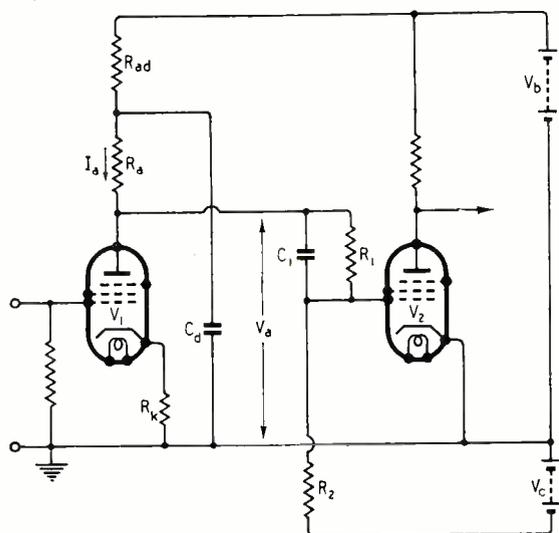


Fig. 5. A direct coupling used in wideband amplifiers.

<sup>3</sup> Edwards and Cherry, *J.I.E.E.*, Vol. 87, p. 178 (1940).

It turns out on analysis that if

$$\left. \begin{aligned} R_2 &= nR_a \text{ and} \\ R_1 &= nR_{ad} \end{aligned} \right\} \text{Where } n \text{ is any convenient numerical ratio, e.g. 20 or 50.}$$

and  $R_1C_1 = R_{ad}C_d$  the output signal voltage is simply

$$V_o = \frac{n}{n+1} I_a R_a$$

at all frequencies where stray capacitances are unimportant.

Consequently the gain of  $V_1$  from the grid of  $V_1$  to the grid of  $V_2$  is

$$A = \frac{g_{m1} R_a}{1 + g_{m1} R_k} \cdot \frac{n}{n+1} \dots \dots (5)$$

which is the usual expression for the gain of a pentode with an un-bypassed cathode bias resistor, except for the factor including  $n$  which may be made to approach unity by making  $n$  large.

The circuit of Fig. 5 is in fairly wide use now, and one of its main advantages is that  $R_{ad}$ ,  $C_d$ , form a decoupling network which reduces the injection into the h.t. supply of the higher frequency components of the signal current in  $V_1$ . This is very useful in preventing instability and undesired feedback from one stage to an earlier one via a common impedance in the h.t. supply.

At low frequencies approaching zero, decoupling networks cease to be effective, so that in multi-stage direct coupled amplifiers a very low impedance h.t. supply—preferably stabilized—has to be used. The same is true of the negative supplies shown in various coupling circuits, although here it is usually stability rather than low impedance that is the prime consideration, since the currents taken from the negative supply are usually quite small.

No mention has been made of drift in d.c. amplifiers in the foregoing, but as any changes in the anode voltage of the first valve due to changes in the valve itself with changing temperature or other electrode potentials, are transmitted more or less completely to the next stage, a steady undesired drift in the anode potential of the output stage occurs only too frequently. There are various means of combating this, which can be found in the extensive literature of the subject.

## TELEVISION RECORDING

A SYSTEM of television recording has been developed by B.B.C. engineers. It is a combination of cinematographic and television apparatus and enables programmes to be "telefilmed"—as it is called—so that they can be re-transmitted at some future time with little loss of the original picture quality. The Service of Remembrance and the Lord Mayor's Show were among the first O.B.s to be telefilmed for a second transmission in the evening programmes.

The recording system uses a continuous-motion film camera in which the movement of the film is chased by an optical image of the television screen picture reflected from a rotating mirror drum. By this means all the 405 interlaced lines of the picture are recorded on the film and the difficulties of relating the television frame frequency to the picture repetition frequency on the film are overcome.

The method was proposed by H. W. Baker, Engineer-in-Charge at Alexandra Palace, and H. G. Whiting, now Engineer-in-Charge of Sutton Coldfield, in collaboration with D. R. Campbell, a senior engineer at Alexandra Palace, and was perfected by W. D. Kemp, of the B.B.C. Planning and Installation Department.

# High - Quality Amplifier

Replies to Queries Frequently Raised by Constructors and Other Correspondents

By D. T. N. WILLIAMSON

**T**HE series of articles recently published on the High-Quality Amplifier has aroused considerable interest and given rise to correspondence. It is hoped that these notes, which deal with matters of general interest arising from the correspondence, may be of assistance to readers who have similar difficulties.

**Valves.**—There is no exact equivalent for the Osram type KT66, and its use is recommended where possible. When the equipment is to be used overseas, the KT66 may be difficult to obtain, and 6L6 glass and metal types may be regarded as direct replacements, with the proviso that the total anode and screen dissipation should be reduced from 25 W to 21.5 W by reducing the total current from 125 mA to 110 mA by adjustment of  $R_{21}$ . The use of these valves with reduced rating entails a slight reduction of the maximum output. The 807 may be used at the full rating of 25 W, with modifications to the valve connections.

Since the articles were written, a modification of the EF37 has appeared under the number EF37A. This has improved heater construction giving greater freedom from hum, and its use may be advantageous for  $V_k$  and  $V_{13}$ .

No other changes in valve types can be recommended, as their use would involve radical redesign.

**Output Transformer.**—When assembling the core of the transformer, care should be taken to ensure that the edges of the T and U laminations butt together. The magnetic properties of the core are dependent upon careful assembly and tight clamping.

**Static Balancing.**—The method of balancing the standing currents in the output valves, which was suggested in the article in the August issue, is dependent for its success on close matching of the d.c. resistances of the halves of the output transformer primary. Nominally the sections are identical, and when carefully machine-wound from the same reel of wire, the resistances should not differ materially. It is possible, however, due to variations in wire diameter and insulation thickness, for the resistances to differ by up to 5 per cent and even, in extreme cases, 10 per cent. Should this occur, a compensating resistor should be added in series with the low-resistance side in order to equalize the resistances, and the meter connected across the equalized sections.

Other more direct methods may, of course, be used to adjust the anode currents to equality, but unless

the transformer has a split primary winding they are inconvenient, and great care should be taken to ensure that the insertion of instruments does not cause oscillation which could give misleading readings.

**Construction.**—There is little to add to the constructional data on the main amplifier given in the August issue, except perhaps to explain that the purpose of the sub-chassis screen, shown in Fig. 3, is to prevent feedback from the anode connections of the output valves to the input of the amplifier. It should extend downwards to the full depth of the chassis.

The method of construction of the preamplifier and tone-compensation units will usually be adapted to individual circumstances. One suggested method of construction for the preamplifier circuit of Fig. 15 is to use a shallow chassis about 9 in  $\times$  3 in  $\times$  1 in. The valves and electrolytic capacitors are mounted in a group along the centre of this chassis, and the other components mounted vertically above the chassis on tag strips arranged on each side of the central group. The connections to the valveholders are taken through slots cut in the top of the chassis. The input transformer should be mounted on the top of the chassis at one end. With the sizes given, there is ample room for a screened component of dimensions up to 3 in  $\times$  3 in  $\times$  2 in. The whole unit should be fitted with screening covers, and mounted on the underside of the motorboard as close as possible to the pickup.

The tone compensation unit of Fig. 19 may be constructed on orthodox lines, the only essential being to provide sufficient frontal area to accommodate seven controls. Grid leads should be kept short to avoid hum pick-up. The blank valveholder terminals (pin 6) should *not* be used as anchors for the leads to the top-cap grids. The power supply components can, with advantage, be assembled on a separate chassis.

**Conclusion.**—The circuits published in the series have been evolved over a considerable period of time and are capable of giving a very high standard of performance. Requests have been received for data on modifications, but as it is rarely possible to determine the full effect of these without carrying out tests, in general, no such data can be supplied by the writer.\* It is regretted that due to the volume of correspondence received, it has not been possible to reply to all letters.

\* Or, for that matter, by *Wireless World*.—Ed.

# FILTERS

## 1. The Importance of $Z_0$ , the "Characteristic Impedance"

By "CATHODE RAY"

AS I said two months ago, I had to think, not twice, but several times before being lured on to the subject of filters. One difficulty is that a mere outline of it takes up the space of a whole book. Another is that it bristles with mathematics and especially with hyperbolics. Not that there is any difficulty in using hyperbolics—it is in fact easier than looking up a log table—but if one doesn't know what they mean they are not much help towards *understanding* filters.

Anybody who expects to master filters completely in one short easy lesson will be disappointed. But I hope to show how they are related to the ordinary familiar circuits (such as tuning circuits and smoothers), how they work and how their theory and design are tackled. In other words, the sort of introductory things that the textbooks evidently consider too obvious to explain, but which may be quite puzzling to those not in the know. And I am not going to assume any knowledge of hyperbolic functions, but will try to show why they are so often used. All this I hope may make more detailed study easier to start and to follow.

To anybody who understands reactance and how it is related to inductance and capacitance, the last two sessions (on smoothing circuits) should have been quite easy. That was because we assumed that the impedance of the output circuit or load was too high to make much difference to the results. Doing that, we could treat each section of a smoother as a simple potentiometer (Fig. 1). If the output terminals are tapped across one quarter of the whole impedance between the input terminals, then the output voltage is one quarter of the input voltage; and so on. In general terms,  $V_{IN}/V_{OUT} = Z_{OUT}/Z_{IN}$ .

If the whole thing is made up of resistance, then it can be used as a voltage reducer (or attenuator), the attenuation being the same at all frequencies. The object of filters (including smoothers), however, is to discriminate between different frequencies, so at least one arm must have reactance. (Arms are the

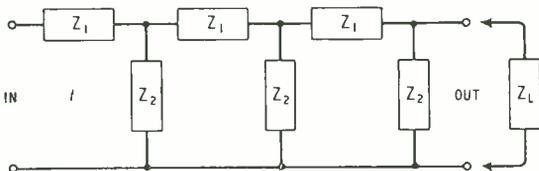


Fig. 2. Three potential-dividers (or  $\pi$  sections) in cascade. The influence of the load impedance,  $Z_L$ , complicates matters considerably.

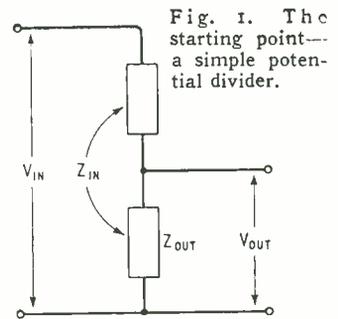


Fig. 1. The starting point—a simple potential divider.

impedances represented by oblongs in Fig. 1). If, for example, the lower arm in Fig. 1 consists of a capacitive reactance, while the upper is a resistance, the attenuation increases steadily with frequency. If the upper arm is also a reactance, it must be inductive—another capacitive arm would just give a constant attenuation at all frequencies above zero.

### Number of Sections

There is an important difference in principle between attenuators and filters that may not be so obvious. It is, of course, possible to connect two or more potentiometers in cascade—one feeding into another. But except for dodging stray reactance or for convenience in switching or some other incidental reason, there is no point in doing this. Any attenuation one likes can be obtained with the simple Fig. 1 arrangement, by tapping the output off at the right place. It is quite different with filters—but don't imagine that the fact that we spent a large part of the last two instalments in finding the best number of smoother sections has anything to do with it. The motive there was economy in components; a single

section to reduce 100 c/s hum to  $\frac{1}{100,000}$  would need, say 1000H and 250  $\mu F$ , whereas it could be done much more economically with several sections. We won't get as far as the question of economy with filters; the matter in mind now is the performance, as judged by the frequency characteristic. This matter was rather obscured when we were considering smoothers, because the requirements were comparatively simple—the only frequency to be passed was zero, and so long as all the ripple frequencies were attenuated as much as necessary it didn't matter two hoots what the smoother did with frequencies between zero and the lowest of them. But filters in the more general sense are liable to be faced with problems such as passing all frequencies completely up to, say, 1000 c/s, and heavily attenuating all those above 1200 c/s; or vice versa. Or, more tricky still, attenuating all frequencies above one frequency and below another (higher) one.

These sudden transitions from go to no-go just can't be organized by any single section, no matter what the kind and values of the components. One must be prepared to use several sections. These could simply be repetitions of the Fig. 1 potential-divider cascade, such as Fig. 2 where three are shown. We used this sort of thing quite satisfactorily as a smoother; but there we were lucky, because we found that in practice the shunting effect could be neglected, so that

## Filters

the attenuation (at any frequency) of the whole system was approximately equal to the product of the attenuations (at that frequency) of the separate sections. If each of them reduced the input voltage by 20 to 1 three would reduce it by  $20^3$  to 1. Or if the attenuations were expressed in decibels, one just added them. Even so, we noticed errors of 30% or more, but that didn't matter much with smoothers. Filter-users are not always so tolerant; and, anyway, it is rarely safe to assume that the load impedance is too high to matter, or that the input impedance of one filter section is too high for the section in front to notice it.

The moment we are forced to abandon this shunting assumption we get into difficulties. Starting at the input end of Fig. 2 and trying to calculate the voltage drop in the first section we can't do it until we know the impedance of the second section, and we can't find that until we know the impedance of the third section, and to find that we have to take into account the impedance of the load. Evidently we started at the wrong end.

### Meaning of Characteristic Impedance

Starting at the back, we can find the impedance of  $Z_2$  and  $Z_L$  in parallel, and thereby see that the attenuation of the last section is  $\frac{Z_1 + Z_2 Z_L / (Z_2 + Z_L)}{Z_2 Z_L / (Z_2 + Z_L)}$ .

Considering that the  $Z$ 's have to be worked out in detail according to what they consist of, taking account of phase, this is already beginning to look rather tiresome; but it is nothing to what emerges when we get to work on the middle section; and that in turn looks simple by the side of the full expression for the first section. Given unlimited time, paper and patience, it can be done, no doubt; but, as mathematicians say, it lacks elegance.

Yet that is a very easy case, consisting of only three sections, all identical, and containing only two different impedances besides the load. If you consider it, you will see that it is this load impedance that is the cause of most of the trouble. Suppose, for

example, that it is low compared with  $Z_2$ ; then it affects the last section considerably. But it won't affect the middle section so much, because  $Z_1$  stands between and may be quite a high impedance. The front section may be hardly affected at all. If the  $Z_1$ 's are very low, however, it will be. In general, every section will be working under different conditions, and will have a different attenuation. Obviously that makes things very complicated. If we could arrange matters so that every section were shunted to the same extent by the next section, then each would be working under the same conditions and it would be practically as easy to calculate  $n$  sections as 1. What this amounts to is finding a particular value of  $Z_L$  that makes it true. That is the most important idea in the whole subject of filters.

Imagine we had a filter consisting of an infinitely large number of identical sections. If that is too difficult, imagine we had a thousand million. The attenuation would be so great that whatever was connected to the far end would make no noticeable difference to the input end. Reckoned between the input terminals, that filter would have a certain impedance, regardless of the load impedance. Suppose for example, measurement showed it to be  $500\Omega$  resistance (Fig. 3(a)). If the first section or two, or even a dozen, were removed, the total number left would still, to a high degree of approximation, be a thousand million, so their input impedance would be  $500\Omega$ . Therefore a  $500\Omega$  resistor could be substituted for them at the output of the few front sections without making any difference at the input of those few (Fig. 3(b)). They would in every way be the same as if the nearly-a-thousand-million were still there. If, then, we make the load  $500\Omega$  resistance, the filter calculation is quite easy. Alternatively, if we are given a certain load impedance (not necessarily a pure resistance) it is advisable to design the filter so that that is its *characteristic impedance*†—i.e. the input impedance of an infinitely long chain; symbol  $Z_0$ , or (if resistive)  $R_0$ .

The beauty of the idea is that it didn't matter in

† Sometimes called *iterative impedance*.

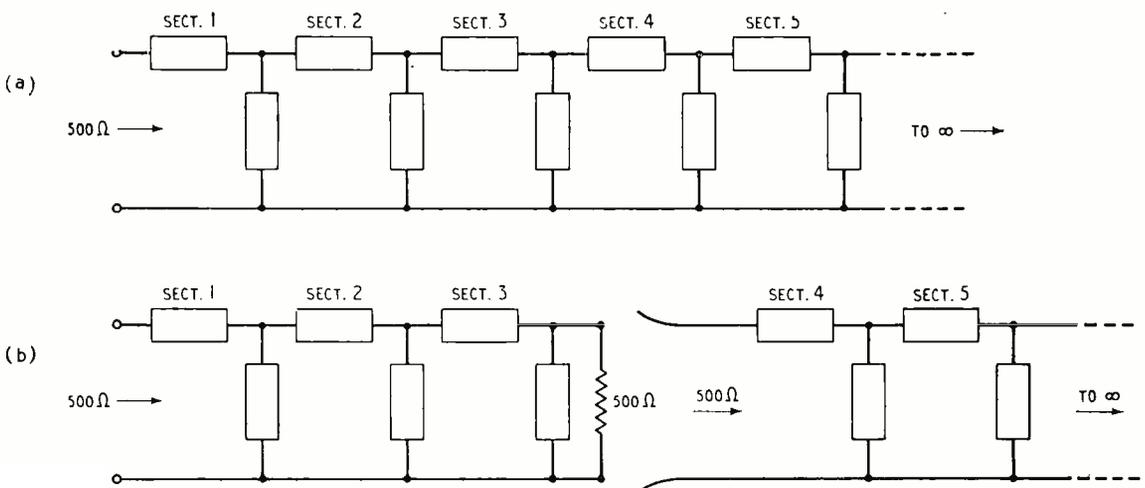


Fig. 3. If the filter chain is infinitely long, its impedance measured at the input terminals depends on itself only (a). An impedance of this value (called  $Z_0$ ) can therefore be used to simulate an infinite chain (b) and the impedance will be the same as this at the input to every section.

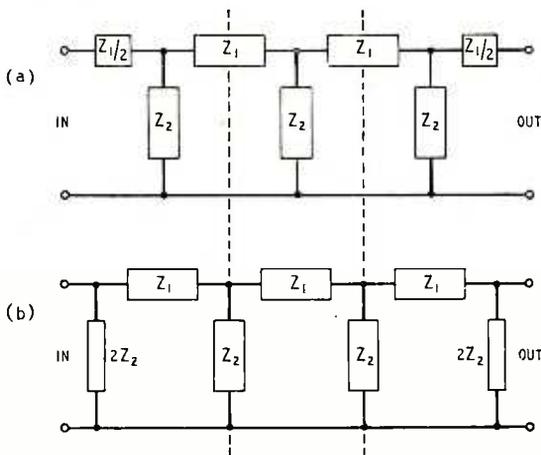


Fig. 4. By transferring half a section in Fig. 2 from one end to the other, the filter can be made to look the same from both ends. Splitting a series arm across gives T sections (a), and splitting a shunt arm lengthwise gives  $\pi$  sections (b).


Fig. 3 whether we knocked off one, two, three, four, or any practical number of sections; so long as we terminated them with  $Z_0$  the input still looked like  $Z_0$ .

The next question is, what decides  $Z_0$ ? It would be awkward and expensive to construct a filter comprising an infinitely large number of sections, or even a thousand million, in order to find out. Fortunately it isn't necessary. A single section will do. You might terminate it with a variable impedance and vary it until the impedance measured at the input to the section was the same. That is very troublesome in practice, because you have to be able to vary not only the ohms but also the phase angle from  $-90^\circ$  to  $+90^\circ$  at any frequency. There is a more convenient way, by making two input measurements, one with the output shorted and the other with it open. It is an important method theoretically as well as practically, and the books discuss it fully.

It is also quite an easy exercise in quadratic equations to work out  $Z_0$  on paper, either for the general case of a filter section consisting of two or more impedances,  $Z_1, Z_2$ , etc., or for particular cases (e.g.,  $Z_1 = \omega L$ ;  $Z_2 = 1/\omega C$ ; etc., or even particular numerical values in ohms resistive and reactive). The result depends on the form of the filter; i.e. how the arms are arranged in each section. So far we have been thinking exclusively in terms of the inverted-L form. It has the great merit of simplicity, requiring only two arms, and it can be made to have any desired  $Z_0$  at its input terminals; but the more critical kinds of filter users turn it down because it doesn't look the same from both ends. They insist that not only shall the impedance at the input be  $Z_0$  when a load equal to  $Z_0$  is connected at the back, but also that its impedance measured from the back, when a generator with an impedance  $Z_0$  is connected to the input, shall also be  $Z_0$ . The point is this: inserting the filter between a generator and a load must not upset the matching conditions.

Sometimes—as with a rectifier power unit—impedance matching doesn't come into it, and there is no reason for not using the simple  $\pi$  type. But in

Fig. 5. How to calculate  $Z_0$  for one (or any number of) T sections.

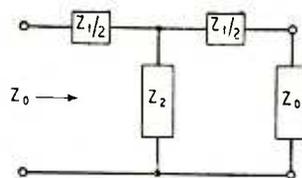

the general calculation of filters it would add considerably to the difficulties if one were faced from the start with all possible varieties of load mismatching. So it is actually easier to take a rather more complicated form of filter that is capable of matching  $Z_0$  in both directions; then, when the principles of that have been fully grasped, one can start finding out what happens when there is a mismatch due to the load not being equal to  $Z_0$ . Before expending effort on calculating  $Z_0$  for the unsymmetrical  $\pi$ -type, then, we had better see what forms are more generally useful.

To make the 3-section  $\pi$  filter of Fig. 2 symmetrical, all we need do is chop the first  $Z_1$  in half and stick it on at the back, as shown in Fig. 4(a). To divide this filter up again into three identical sections, the cuts have now to be made midway along the original  $Z_1$  arms, as shown by the dotted lines. So each section of this type of filter (known for obvious reasons as the T) consists of one shunt arm, impedance usually denoted by  $Z_2$ , and two series arms, each  $Z_1/2$ .

An alternative method of dealing with Fig. 2 is as it were, to split the last  $Z_2$  lengthwise, into two parallel impedances each equal to  $2Z_2$ . One of these is then moved to the front (Fig. 4(b)). When this filter has been divided into its sections, each consists of one series arm  $Z_1$  and two parallel arms each  $2Z_2$ . We have to go to the Greeks for a letter— $\pi$ —appropriate to this type.

Now we can start finding how  $Z_0$  is related to  $Z_1$  and  $Z_2$ . Taking one T section terminated with  $Z_0$ , as in Fig. 5, we can write down an equation connecting them, thus:  $Z_0$  equals  $Z_1/2$  plus  $Z_2$  and  $Z_1/2 + Z_0$  in parallel. One way of writing the solution to this (when you have solved it) is

$$Z_0 = \sqrt{Z_1 Z_0} \cdot \sqrt{1 + \frac{Z_1}{4Z_2}} \dots \dots \dots (1)$$

That is not quite the tidiest form, but the reason for preferring it will appear soon.

The solution for a  $\pi$  section is the same except that the first factor ( $\sqrt{Z_1 Z_0}$ ) is divided by the second. These are two really important formulae.

### How $Z_0$ Varies with Frequency

Next, it is time to open the sealed Z boxes and reveal the contents. They vary according to what the filters are for. The one bit in the whole filter story that never gives anybody any trouble is the classification of the main types, so I just show these as Fig. 6 and leave it at that. There are of course plenty of other types, but these are the ones everybody is expected to know about.

Seeing that the Editor is obliged to leave some room for other writers, I won't be able to go into detail about all these. I propose to concentrate (as an example) mainly on the low-pass T type.

**Filters**

Unless one is much too bright to be reading this, one begins by assuming that the arms are perfectly free from resistance. They never can be in practice, of course, but the results deduced comparatively simply on this basis are a good guide to the general behaviour of reasonably low-loss filters; and, moreover, the effects of unavoidable resistance (like those of mismatching) can best be studied at a later stage when the main outline is clear.

Getting down to our low-pass T, shown on a larger scale in Fig. 7, we have  $Z_1 = j\omega L$  and  $Z_2 = 1/j\omega C$ . Before substituting these in equation (1) you should take note of a custom that is no doubt all for the best but is apt to trip up beginners. Because each of the series arms is half  $Z_1$ , the inductance of each is half  $L$ . That is quite reasonable when you remember how we derived the T from the  $\Gamma$ , but it is easy to forget when working out values. In the same way the two shunt arms in a  $\pi$  section are each twice  $Z_2$ , so if they are capacitive they consist of—and here is another catch—half  $C$ .

Substituting in equation (1):

$$Z_0 = \sqrt{\frac{L}{C}} \sqrt{1 - \frac{\omega^2 LC}{4}} \dots \dots \dots (2)$$

By meditating on this result it is possible to learn a lot about low-pass T sections, in spite of the fact that we seem to be no nearer discovering what their frequency-attenuation curve is than when we started. But let us see.

It consists of two factors, the first of which is

$\sqrt{L/C}$ . Anybody who knows the first thing about transmission lines will recognize this at once as the characteristic impedance—a remarkable coincidence! If  $\omega^2 LC$  is equal to zero—which of course it is at zero frequency—the second factor becomes equal to 1, so the first interesting discovery is that at zero frequency the characteristic impedance is  $\sqrt{L/C}$ , the same as that of a loss-free transmission line. If  $L$  and  $C$  are both made very small indeed,  $\omega^2 LC/4$  may be much smaller than 1 (and  $Z_0$  therefore is approximately equal to  $\sqrt{L/C}$ ) even at fairly high frequencies. A transmission line can be considered as a low-pass filter with an infinitely large number of sections in each of which  $L$  and  $C$  are infinitesimally small, so that  $\omega^2 LC/4$  never amounts to anything significant at any finite frequency, and  $Z_0 = \sqrt{L/C}$  over the whole range.

So here, incidentally, we have a link with something that might have been considered quite a different subject.  $Z_0$  begins as  $\sqrt{L/C}$  at zero frequency, and gets less as the frequency is raised; but the smaller  $L$  and  $C$  are, the higher the frequency before the lessening is substantial, until, when  $L$  and  $C$  are infinitesimal, as in a uniform line,  $Z_0$  remains constant at all frequencies.

The next thing to do is to find out more exactly how  $Z_0$  varies with frequency, and the most helpful method is to draw a graph. If the principle of generalized graphs (see September issue) appeals to you, you will take as the unit of  $Z_0$  the quantity  $\sqrt{L/C}$ . And when you expand the term  $\omega^2 LC/4$  to bring out  $f$ , the frequency, you get.

$$\frac{\omega^2 LC}{4} = \frac{(2\pi f)^2 LC}{4} = (\pi \sqrt{LC} f)^2$$

So on the same principle you will choose  $\pi \sqrt{LC}$  as the unit of frequency, and plot  $Z_0^* = \sqrt{1 - f^{*2}}$

where  $Z_0^*$  is  $Z_0$  in units of  $\sqrt{L/C}$  and  $f^*$  is  $f$  in units of  $\pi \sqrt{LC}$ . If you find generalized graphs confusing, you will have to fill in some values for  $L$  and  $C$  and plot the graph in the ordinary way, but of course the actual figures will apply only to a filter section with those particular values of  $L$  and  $C$ . Still, the shape will be the same, and that is the main thing.

It is obvious that as  $f$  increases from zero (where  $Z = \sqrt{L/C}$ ),  $Z_0$  decreases; and the decrease gets faster until  $f^* = 1$  (or  $f = 1/\pi \sqrt{LC}$ ), when  $Z_0$  becomes zero (Fig. 8(a)). (The nimbler mathematicians may have noticed that the relationship between  $Z_0^*$  and  $f^*$  is the same as


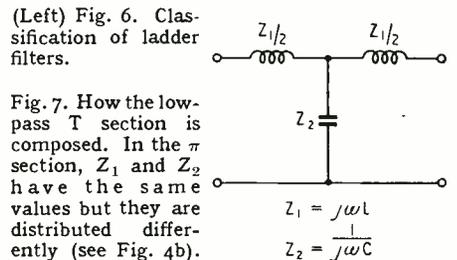


Fig. 7. How the low-pass T section is composed. In the  $\pi$  section,  $Z_1$  and  $Z_2$  have the same values but they are distributed differently (see Fig. 4b).

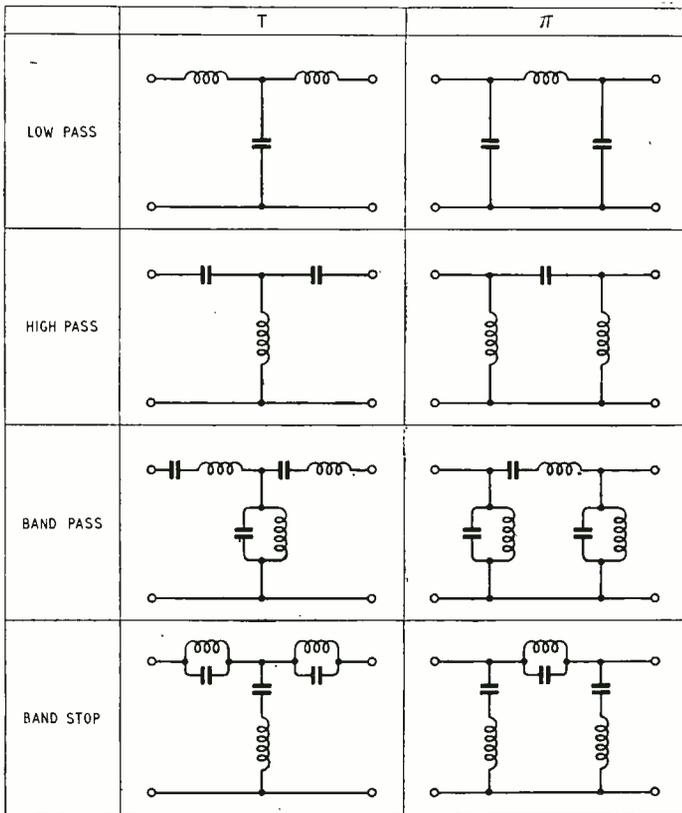

(Left) Fig. 6. Classification of ladder filters.

that between the sin and cos of an angle, so it may be no surprise to them that this part of the curve is a quadrant).

Up to this point,  $j$  has been entirely absent, so we conclude that  $Z_0$  is a pure resistance. But when  $f^*$  exceeds 1, we are faced with the square root of a negative number, and have to bring in  $j$ . Multiplying outside the root sign by  $j$  and inside by  $j^2 (= -1)$ , we have

$$Z_0^* = j\sqrt{j^2 - 1}$$

and so continue plotting the curve. This part of it, being covered by  $j$ , must represent a pure reactance.

So we find that if the load impedance is going to meet the requirements at all frequencies it must be a pretty versatile sort of fellow—a pure resistance varying in a quarter-circle from  $\sqrt{L/C}$  ohms at zero frequency to zero at  $1/\pi\sqrt{LC}$  cycles per second, and then suddenly changing into a pure inductive reactance, increasing steadily without limit. The advantages of meeting this involved requirement, let us remember, are both theoretical and practical—theoretical because it enables any number of sections to be used without complicating the calculations; and practical, because it avoids mismatching and consequent divergence from scheduled performance.

We do know a simple circuit that has a critical frequency and an increasing inductive reactance above that frequency—a simple series resonance circuit. But below the critical frequency it is a capacitive reactance, not a resistance. So that won't fit. Actually, nothing will. Thus the low-pass T filter is awkward at the start; its  $Z_0$ , without which both theory and practice are unsatisfactory, is impracticable. In spite of this, it is quite a commonly used type of filter. What, then, about the  $Z_0$  difficulty?

If you remember that the  $Z_0$  formula for the  $\pi$  section is the same as for the T except that the second factor is a divisor instead of a multiplier, you will see that it is the reciprocal of the  $Z_0$  for the T. So instead of coming down to zero at the critical frequency it soars up to the sky (Fig. 8(b)). And the reciprocal of an inductive reactance is a capacitive reactance. The high-pass filters are similar, but turned left to right (i.e., reciprocal as regards frequency). And the band filters have two critical frequencies. But all of them have the first factor in common, namely,  $\sqrt{L/C}$ . The normal practice is to regard  $\sqrt{L/C}$  as the impedance of the load (and generator), unless there is any special reason for not doing so. The filter will then be correctly matched only at one frequency (zero in Fig. 8), but it will be nearly right over what might be an important range of frequency. Even though it is hopelessly out near the critical frequency, the assumption that  $R_L = \sqrt{L/C}$  is at least a definite condition, for which it is possible (though not very easy) to calculate the departures from simple ideal theory.

It is time to end, and we still haven't found what the attenuation is doing, but we have laid a good foundation on which we can build next month. In the meantime I strongly recommend you to consolidate that foundation by working out for yourself the  $Z_0$

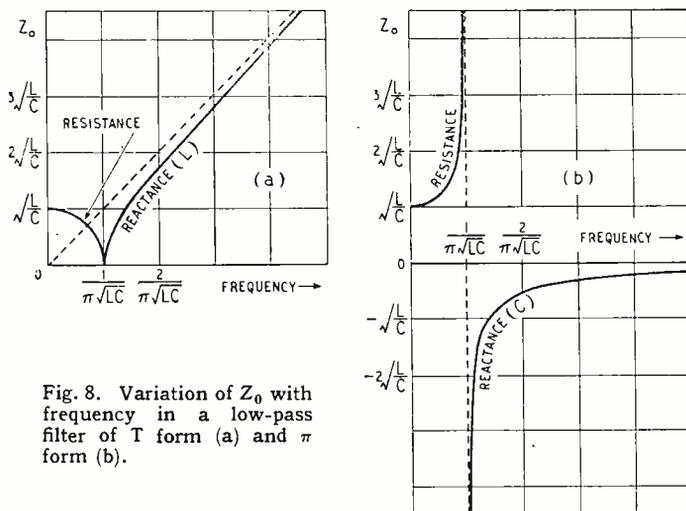


Fig. 8. Variation of  $Z_0$  with frequency in a low-pass filter of T form (a) and  $\pi$  form (b).

curves for various values of  $L$  and  $C$ —try some of last November's smoother sections, for instance. You might also see how nearly the shapes of the curves fit what you would expect from the various sections by looking at them. (In Fig. 7, for example, if the input frequency were enormously high  $Z_2$  would be practically a short circuit and the impedance would consist almost entirely of  $Z_1/2$ , which would be a high inductive reactance.) But especially consider the critical frequency, and what it signifies, and whether it has any connection with any other sort of critical frequency you know of, and why. A whole lot of very instructive and interesting thought can be generated by these innocent-looking little circuits. Some of the answers will come next month.

## LOUDSPEAKER CABINET DESIGN

AT a meeting of the British Sound Recording Association on November 25th last, G. A. Briggs gave a lecture on "Some Aspects of L.F. Performance of Loudspeakers" in which he emphasized the importance of the loudspeaker mounting. After demonstrating the modification of the speaking voice by talking into a number of "megaphones" of various shapes—including a conventional extension loudspeaker cabinet—he went on to discuss the baffle systems available for preventing short-circuiting of front and back radiation from the loudspeaker cone at low frequencies.

Comparative tests were then made with an open-backed cabinet, vented cabinets with and without matching to the loudspeaker resonance, a tapered pipe with variable point of entry for the loudspeaker aperture, and a heavily-built "reflex" corner chamber of brick and concrete. Both on speech and music, and with random noise input having a continuous frequency spectrum from 15c/s to 20kc/s, the differences in coloration were clearly demonstrated.

Mr. Briggs stressed the point that coloration in some degree was inevitable, but expressed no preference for any one method of mounting. The choice of the individual would be governed by psychological as well as objective factors and would depend as much upon what was listened for as upon what was being listened to.

# UNBIASED

By FREE GRID

## Houyhnhnms and Yahoos

WHELKS and wireless have not much in common but having recently seen the proprietor of a Southend whelk stall lunching in one of the most Lucullan of West End restaurants and apparently enjoying it by the gusto with which, mouth-organ fashion, he was attacking a leg of chicken, I wondered whether manufacturers of radio receivers consumed their own products or preferred those of their rivals.

Accordingly I visited the house of one of them who is no mean musician. I found him enjoying himself with a mixture of radio and records, assisted by the very latest thing in quality amplifiers made by a rival firm, complete with bass boost, treble turn-up and all the other what-nots which one finds on these instruments. As his own firm makes both radio sets and radiograms, I naturally asked him for an explanation.

He excused himself on the ground that results from such an instrument as he was using could only be appreciated by a handful of musical Houyhnhnms like himself. He felt that it would be a wicked waste of materials and skilled technical labour to cast super-quality amplifiers before Yahoos—in which class he evidently included the majority of listeners who, as he explained, only demanded of a wireless set that it be capable of producing a reasonable row.

Undoubtedly there is a certain amount of truth in what he said and I don't suppose that the general public would be prepared to pay for extra valves solely for juggling with bass and treble balance. In any case they would make a hopeless hash of the juggling and then blame the instrument. But I do think that it is time the manufacturers of what

I will call "ordinary" sets, to distinguish them from the super-quality push-pull jobs, provided an outlet to which those of us who think ourselves musical highbrows could couple our own or somebody else's version of a quality amplifier.

It is true that most manufacturers of quality amplifiers sell excellent r.f. units to go with them, but the few that I have seen, while they would look thoroughly at home in a ship's wireless room, just wouldn't blend with a Louis Quinze drawing-room, and they can't be shoved under the sofa like an a.f. amplifier. No woman would permit them to be installed permanently in a reception room, and as such refusal forms no valid ground for divorce, most of us are compelled to temper the joys of the ear with those of the eye. I hope, therefore, to see quality output sockets on all "ordinary" sets at the next Radio-lympia, and shall take their absence on any set as a tacit admission on the part of its manufacturer that quality is too mangled in the pre-a.f. section for there to be any hope of its resuscitation.

## A Ticklish Question

A KINDLY reader writing to me from the watery wastes of Westmorland draws my attention to some investigations he has been making into a peculiar form of interference occurring about 11 p.m. and lasting only a couple of seconds. Eventually he found the trouble to be caused by the bedtime removal of what he, with an appropriate sense of delicacy, calls "certain feminine undergarments." While publicly thanking my correspondent for the report on his research work, I must inform him that it is by no means original, as I carried out some researches into this matter nigh on twenty years ago and published my findings in these columns in 1931.

In those far-off days I was merely a voice crying in the wilderness, but things are vastly different nowadays, as I have the full weight of the law behind me in my endeavour to stop this interference; at least I have in theory, but so far the Post Office authorities have been singularly loath to investigate this source of interference. As for the manufacturers of anti-interference devices, they do not, so far as I am aware, make a single suppressor for dealing with this particular form of man-made, or rather woman-made, interference at the source. I firmly

believe that their laboratories haven't done any practical research work in the matter whatever, due, I suppose, to the dearth of properly qualified women engineers.

It is, however, high time that something was done about it, and I hope that before long one of the more go-ahead firms will market



Silk-stocking Static.

suppressors together with the necessary instructions for connecting them up and that they will at the same time not be afraid to submit a specimen to the Editor for a test report.

If anybody doubts the seriousness of this kind of interference, let him do what I have been doing recently—attempting to receive television at a spot by the silvery sea hard by one of our most famous girls' public schools. So far the only thing I have learned as a result of my investigations is the girls' bedtime, which produces a most appalling snowstorm on the screen. Very much later in the evening a snowstorm of less intensity appears, due, I presume, to the retirement of the mistresses. This additional snowstorm is, however, sufficiently heavy to make it obvious that the mistresses are no bluestockings.

If it is found that a suitable suppressor unit cannot be designed I trust that the Editor will not hesitate to attack those at the head of the women's underclothing trade and smite them hip and thigh with a stern demand for a return to the days of flannelette and wool on which foundations England's greatness was built. It is not too much to say that had radio been in existence in Queen Victoria's time the force of public opinion would have rendered underwear suppressors unnecessary, as the offending kind of underwear would itself have been suppressed.



Push-pull in Action.

# A.C./D.C.-Battery Power Supplies

Design Considerations for Maximum Economy

By L. MILLER

THE design of a combined a.c., d.c. and dry-battery operated receiver calls for departure from the orthodox only in so far as the power supply is concerned. It should be apparent that the power supply for a "three-way" receiver will be called upon to give a smoothed d.c. supply for the valve filaments as well as the normal h.t., as, of course, directly-heated valves will be used for the receiver in order to keep down the heater watts when the set is to be run on the self-contained dry batteries. The obvious choice will be the "all-dry" 0.05-A valves.

Next comes the question of series or parallel wiring of the filaments. Parallel operation for both mains and battery supplies is ruled out by the high losses which would be incurred in the voltage-dropping resistor, and the extra space which would be needed to provide adequate ventilation. Series-parallel switching is one method of overcoming this difficulty, but a really reliable switch is necessary and when this is found will inevitably add to the cost of the set.

We will therefore assume that series operation is to be used on all supplies. In the usual four-valve superheterodyne circuit, three 1.5-V and one 3.0-V valves will require a filament current of 50 mA at 7.5 V.

## Choice of Rectifier

If the same output valve is to be used on a.c., d.c. and batteries, then the metal rectifier will almost certainly be chosen, as it takes up no more room than a valve rectifier and requires no heater current. Some commercial three-way receivers incorporate an auxiliary mains-type output valve which is automatically switched in circuit when mains

operation is used. With this type of set it is quite a practical proposition to use a valve rectifier, as its heater will be wired in series with the mains output valve heater and will only be consuming current which normally would be wasted.

As 90 V is the maximum voltage that will be required, it may appear obvious at first thought to drop the surplus 100 or so volts before rectification, and indeed in almost all of the American-made sets this procedure is adopted, but only for the reason that 110 V is the standard pressure in the U.S.A. and the extra pre-rectification dropping resistor has been added to enable the receiver to be operated on mains in the region of 200-230 volts.

In England 100 V mains are comparatively rare, and unless the designer contemplates ever being located in a 100-V district there is nothing gained in dropping the surplus volts before rectification except, perhaps, that a slightly smaller rectifier could be employed.

One economical method of "losing" the extra volts is to dispense with the reservoir condenser. As half-wave rectification will be employed, the d.c. output from the rectifier will be very nearly half the input, which will give a value closely approximating to that which we require.

This also has the very important advantage of providing good voltage regulation, since the average voltage appearing across a reservoir condenser is dependent upon the current being

drawn from it during the non-conducting half-cycle, and is liable to vary appreciably with quite small changes in load.

With no reservoir condenser the only factor affecting voltage output is the resistance of the rectifier itself, and as this factor is also present with both systems, and we do not need the extra volts which a reservoir condenser will supply, it is obvious to our advantage to dispense with it, as voltage regulation is a very important point when dealing with the filament supply, which needs 7.5 V—not just "about 7.5 V."

## Smoothing

In order to keep the filament regulation good, it may be considered advantageous to split the smoothing into two sections, as shown in Fig. 1. Assuming that a mains supply of 200 V is the minimum we are likely to encounter, and that a small dropping resistor is used before rectification for mains adjustment as shown, the d.c. output from the rectifier will be 100 V less the drop across the rectifier. This voltage drop due to the rectifier will have to be determined by experiment unless the resistance of the rectifier under working conditions is known. Probably the best plan would be to construct the entire power pack using a small 300-ohm

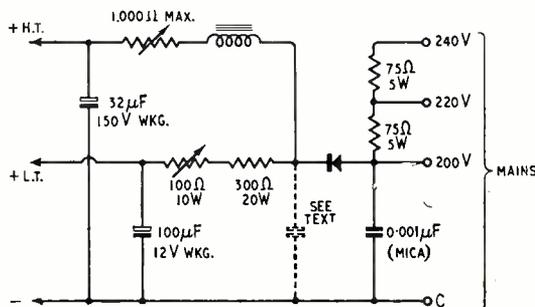


Fig. 1. Supply circuit using metal rectifier.

### A.C./D.C. Battery Power Supplies

smoothing choke for the h.t. section and place loads across the two outputs equivalent to the h.t. and l.t. requirements. If the h.t. is too high an extra small value of resistor may be placed in series with the choke, while if the h.t. is too low a *small* value of reservoir condenser should be placed across the output from the rectifier. Usually a 0.25 or 0.5  $\mu\text{F}$  will be sufficient to compensate for the drop lost across the rectifier, and such a small value will not materially affect the regulation of the supply.


On the l.t. side we have to drop the 90 or so volts to the required 7.5 V, and the resistor needed can also conveniently serve for smoothing purposes. A really large filter condenser can be employed, as the voltage will never rise above the 7.5 V, and a very low working voltage, bias-type condenser, say 100 or even 200  $\mu\text{F}$ , can be used.

### Voltage Adjustment

For really accurate adjustment it is a good plan to make up the l.t. dropping resistor with one fixed and one variable, as shown in Fig. 1 and connect a temporary resistor of 150 ohms (one-watt type will suffice) across the l.t. output, and one 8,000- to 9,000-ohm across the h.t. output, then make the h.t. and l.t. adjustments as described.

Upon removing these temporary

Fig. 2. A valve rectifier can conveniently be used when separate output valves are provided for battery and mains operation.

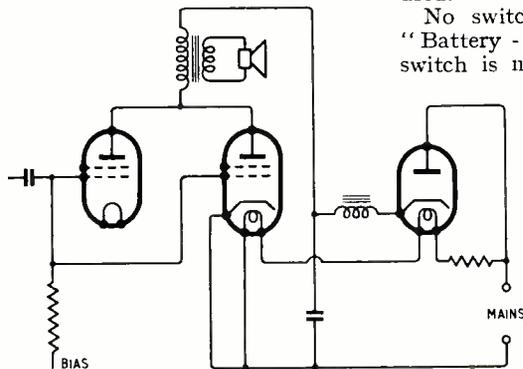

resistors the power pack is ready for operation and should require no further adjustment. Any change of h.t. current, say between 5-10 mA, will have a negligible effect on the l.t. output, as the only resistance common to both l.t. and h.t. circuits is that of the rectifier itself, which is normally quite low; should it tend to increase the l.t. voltage the filaments will consume more current, which will to a large extent offset the increase, but in any case the deviation from 7.5 V will be very slight.

It was mentioned earlier in this article that some commercial firms incorporate an auxiliary mains output valve for use on a.c. and d.c. mains. Obviously the ideal lying behind this is to get "mains

quality" and better volume when current economy is of no importance and, if this refinement is required, a valve rectifier can be used.

No switching other than the "Battery - Mains" changeover switch is necessary, both valves being connected in parallel as shown in Fig. 2. as the "Battery - Mains" switch ensures that h.t. is applied only to one of the output valves.

An interesting point arises here. The 50L6 is very suitable as an output valve for this type of receiver when using the mains supply, as the heater current is only 0.15 A. It consumes 53 mA of h.t. with a supply voltage of 110 V and requires 7.5 V grid bias.

### Cathode-current Heating

It is a comparatively simple matter to adjust the anode voltage of the 50L6 so that exactly 50 mA flows, and to wire our four battery valves between cathode and earth, as shown in Fig. 3. As the 50 mA will obviously be flowing through the valve filaments and as we know that when 50 mA is flowing through the valve filaments the combine voltage across them will be exactly 7.5 V, which is the bias required by the 50L6, it will at once be realized that we have here a very convenient means of heating our battery valve filaments without taking any additional current from the rectifier. The 50L6 acts as the smoothing and voltage-dropping "resistor," and the 100  $\mu\text{F}$  capacitor serves the dual purpose of filter and bias condenser for the valve.

If this method is adopted it will be necessary to add a further two-way switch (which should be ganged to the "Battery - Mains" switch) as shown, to cut the h.t. supply off the battery output valve when the mains output valve is used.

The writer claims no originality for this type of circuit which is believed to be used by many commercial manufacturers in the U.S.A.

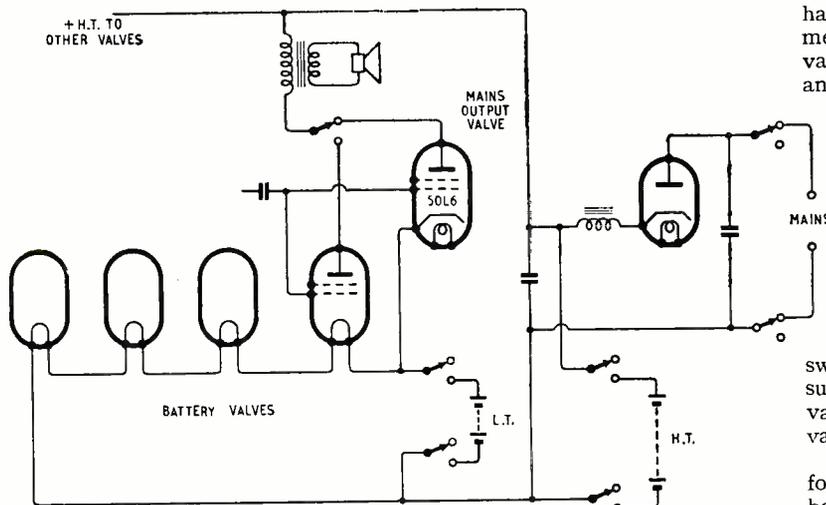


Fig. 3. Filament heating of early valves by anode current of "mains" output valve. All switch elements are, of course, ganged together.

# Manufacturers' Products

## New Equipment and Accessories for Radio and Electronics


### Miniature Standard Cell

A STANDARD Weston cell (1.01859V abs. at 20°C) has been developed by Muirhead, Elmers End, Beckenham, Kent, and is contained in a square-section vertical moulded case measuring only  $\frac{7}{8} \times \frac{7}{8} \times 3\frac{1}{2}$  in. A single tube has been adopted in place of the conventional H construction and the electrodes, which lie side by side, are separated by a glass web. One advantage of this form of construction is that there is less risk of temperature differences arising between the mercury and cadmium amalgam half-cells.
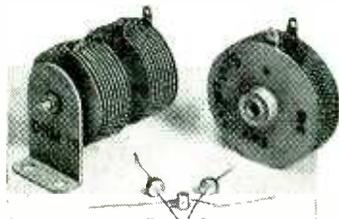
### Miniature Rectifiers

FOLLOWING the general trend of miniaturization, Standard Telephones and Cables, Connaught House, Aldwych, London, W.C.2, have introduced some miniature "Centercel" rectifiers for h.t. and r.f. use. They are the selenium type, the h.t. models being known as the RM1, RM2 and RM3, their d.c. outputs being 60, 100 and 120 mA respectively. The maximum r.m.s. input to a single rectifier is 125 volts, but two or more can be joined in series for higher voltages. Likewise they can be employed as voltage doublers or triplers, or bridge-connected for full-wave rectification. Their small size (the RM1 measures  $1\frac{1}{8}$  in in diameter and  $\frac{1}{2}$  in thick), enables combinations of this kind to be accommodated in a small space.

A miniature r.f. rectifier for use up to 5 Mc/s is also included. Its size is  $\frac{1}{2}$  in  $\times$   $\frac{1}{2}$  in  $\times$   $\frac{1}{2}$  in and it is so light it can be suspended in the wiring; it weighs 0.0150z only. Among its many applications are those of second detector in superhets, a.g.c. rectifier, noise limiter



Some of the new S.T.C. miniature rectifiers for h.t. and r.f. use. The dual assembly consists of two RM1 rectifiers. Type M1 shown in front.

and d.c. restorer. It is the type M1.

Its principal characteristics are: Self-capacitance, 20 pF; forward resistance, 12 k $\Omega$ ; reverse resistance, 20 M $\Omega$ ; and maximum peak inverse voltage, 50. For satisfactory rectification a minimum voltage of 0.5 is needed.

### Big-tube Television

A PICTURE size of 12 $\frac{1}{2}$   $\times$  10 in on a 15-in aluminized tube is provided in the new V176C Murphy television receiver. The superhet circuit, which is available for either the London or Birmingham transmissions, includes interference suppression on both sound and vision. Focusing is effected by a combination of permanent and electro-magnets and is stabilized against mains fluctuations. The makers are Murphy Radio, Welwyn Garden City, Herts, and the price, including tax, is £176.

### Precision-drawn Waveguide Tubing


WAVEGUIDE tubing in long lengths (10ft), having close dimensional tolerances, small radii of internal corners and a very high internal finish, is now being made by Johnson, Matthey and Co., 73-83, Hatton Garden, London, E.C.1.

This guide is available not only in brass and copper but also in silver-lined brass or copper, silver-copper alloy and aluminium. A range of sizes is available from 2.0  $\times$  0.667 in, including the normal service requirements, down to 0.180  $\times$  0.09 in internal dimensions.

A technical service has been made available to assist in establishing satisfactory service to the consumer both in choice of guide and subsequent processing, and tubes having non-standard dimensions can be manufactured to specification providing the quantities involved justify the production of special tools.
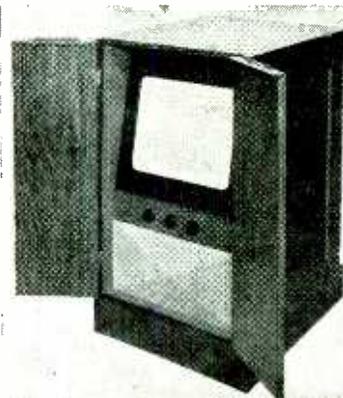
### Portable Recorder

A SELF-CONTAINED recording machine has just been introduced by ElectroSound Supplies, 99, Belgrave Road, London, S.W.1. It makes use of the "Technifon" Type TG2 traverse gear which is a development of the Type TGI described in the July, 1947 issue of



Murphy television receiver, type V176C, with aluminized screen.



"Technifon" portable disc recorder.

this journal; it has a moving-iron type cutter head with a response of 50 to 6,000 c/s. The lead screw is friction-driven from the centre of the record and the traverse gear as a whole is hinged and can be lifted clear of the record.

The turntable is an aluminium alloy casting running in oil-retaining bearings and is belt-driven by a motor developing a torque of 400 gm/cm.

A three-stage amplifier with an output of 5 watts is built on the underside of the motor board, and a monitoring loudspeaker is fitted in the lid of the carrying case. A high-grade moving coil microphone is included.

The light-alloy carrying case, which is finished in durable enamel,

## Manufacturers' Products

measures  $1\frac{1}{4}\text{in} \times 1\frac{1}{2}\text{in} \times 10\frac{1}{2}\text{in}$ . The cost of the complete equipment is £85.

## Moving-iron Meters

**R**EPULSION-TYPE movements giving a substantially linear scale from 20 per cent to full-scale deflection are a feature of a new range of moving-iron panel-mounting meters recently introduced by Taylor Electrical Instruments, 419-424, Montrose Avenue, Slough, Bucks.

The Series 400 and Series 500 with  $4\text{in}$  and  $5\text{in}$  scale lengths in rectangular cases are already available and a circular type with  $3\frac{1}{2}\text{in}$  scale is in course of development.

## New R.F. Cables

**T**HE following new types have been added to the range of "Co-Ax" air-spaced articulated cables made by Transradio, Ltd., 138A, Cromwell Road, London, S.W.7: Type C34, low-capacitance cables; outside diameter  $0.85\text{in}$ , capacitance  $4.8\ \mu\text{F}/\text{ft}$ ; impedance 231 ohms. Type C344, very-low-capacitance cable; o.d.  $0.85\text{in}$ , capacitance  $4.3\ \mu\text{F}/\text{ft}$ ; impedance 259 ohms. Type A34, highly flexible medium-power transmission line; o.d.  $0.85\text{in}$ , impedance 73 ohms. At 100 Mc/s attenuation  $0.65\text{ db}/100\text{ft}$  and loading  $1.5\text{ kW}$ . Bending radius  $3\text{in}$ . Type A344, flexible  $51.5\text{-ohm}$  medium-power transmission line; o.d.  $0.85\text{in}$ , nominal impedance  $51.5\ \text{ohms}$ , bending radius  $4\text{in}$ . Loading  $2.3\text{ kW}$  and attenuation  $0.78\text{ db}$  at  $100\text{ Mc/s}$ .

## Photo-Electronic Relay

**T**HE Model 71 photo-electronic relay made by Electronic Instruments, Paradise Road, Richmond, Surrey, is sensitive to changes of input of the order of  $2\ \mu\text{A}$  over a range from zero to 2 amps.

The input is backed off by a

potentiometer which can be graduated directly in the units to be measured (e.g., temperature, pH), and applied to a conventional moving-coil meter which is normally operated at zero. A small lamp below the dial illuminates a vacuum photo-cell through a narrow slot which is obscured when the pointer of the meter is deflected. The current from the photo-cell passes through a d.c. amplifier to operate a mechanical relay with on-off, change-over contacts rated at 3A, 250 V a.c. or d.c.

The operating point is continuously variable and the backing-off potential is derived from a neon-stabilized source. By reversing the input connections the relay can be made to function on either a rise or fall of input.

## Miniature Hearing Aid

**W**EIGHING only 5 oz with batteries, and contained in an engraved gold-finished case, this hearing aid employs a three-valve circuit drawing only  $0.4\text{ mA}$  from a 15-V sub-miniature h.t. battery. The h.t. life is approximately 350 hours, and the l.t. 8 hours from a standard "pen" cell, or 30-35 hours if a Kalium U7 cell is employed.

The crystal microphone is concealed behind the coronet motif on the front of the case, and either a magnetic or crystal insert earpiece is supplied. In addition to the volume control, two stages of tone control for top or bass cut are provided. The circuit incorporates automatic volume limitation.


Plug-in type valves are used and the chassis is removable after withdrawing two screws.

Made by Bonochord, Ltd., 48, Wigmore Street, London, W.1, the "Micropak" hearing aid costs 27 guineas.



Bonochord "Micropak" miniature hearing aid.

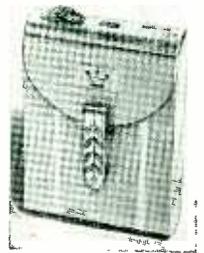(Left) Model 71, photo-electric relay made by Electronic Instruments.



## Record Changer

**U**P to sixteen 10in or 12in records can be accommodated in the "K.F." record changer sold by Brooks and Bohm, 90, Victoria Street, London, S.W.1. Only one record at a time is on the turntable, and after playing the record is removed to a hopper at the side. Records can be added to or removed from the stack while playing, so that a continuous programme can be arranged. The change cycle occupies less than  $2\frac{1}{2}$  seconds.

The trigger mechanism which operates when the pickup enters the run-off groove has a light action and will function with needle pressures down to  $\frac{1}{4}\text{oz}$ . A ruby stylus is fitted to the pickup and the needle pressure is adjustable.

The single-knob control includes a "delay" position which raises the pickup and returns it to the record at the same point. This feature is useful for interjecting announcements, and for musical games.

A constant-speed rim drive motor for a.c. supply is fitted and the weight of the complete instrument is 12 lb. The price, including tax, is £16 5s.


## New Hearing Aid Valves

**M**ULLARD ELECTRONIC PRODUCTS, LTD., have announced two flat-type sub-miniature valves of extremely small size. The DF66, a voltage amplifier pentode, is  $1.1\text{in}$  long, and the DL66, an output pentode, is  $1.38\text{in}$  long; both are  $0.33\text{in}$  wide and  $0.2\text{in}$  thick.

An important feature is economy in filament battery drain. The DF66 filament is rated at  $0.625\text{ V}$  and the DL66 at  $1.25\text{ V}$ , but each consumes only  $15\text{ mA}$ , as compared with  $25\text{ mA}$  for previous Mullard valves and  $30$  and  $45\text{ mA}$  for similar American types. Using a  $22.5\text{ V}$  h.t. battery, the DF66 will give a voltage gain of  $30\text{ db}$  per stage whilst the DL66 will give a power output of  $2.5\text{ mW}$  at less than 10 per cent distortion.



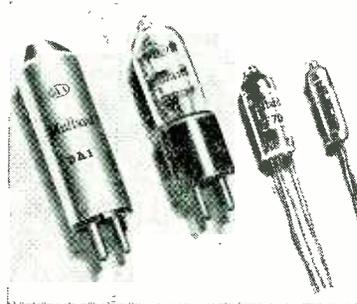"K.F." automatic record changer for sixteen 10in or 12in discs.



The DF66 (extreme right) with earlier Mullard sub-miniatures.

## LETTERS TO THE EDITOR

### Academic Qualifications

ALTHOUGH sympathizing with your correspondent, "Unemployed A.M.Brit.I.R.E.," I feel that he, like many others, fails to appreciate the proper interpretation of academical and professional qualifications.

The Higher School Certificate should be regarded as proof that the holder has the power to assimilate the theory of certain basic sciences. It is no proof that he is capable of putting those theories into practice. The same could be said of C. & G. Telecommunications, except that it is almost impossible to obtain the full certificate without the aid of considerable practical experience.

On the other hand, professional qualifications such as Corporate Membership of the Brit.I.R.E. are proof of sound theoretical knowledge combined with at least five years of practical experience in a responsible position.

An intelligent employer appreciates these facts, and should he require staff which he intends to train and mould to suit his own particular specialized class of work, he accepts those who have the Higher School Certificate.

However, should he desire staff who can take over a job of work almost immediately with the minimum of guidance or supervision, he looks for those with technical and professional qualifications.

From my knowledge of the Royal Aircraft Establishment, Farnborough, with its departmental groups and specialized divisions of labour, the advertisement referred to by your correspondent is not as anomalous as he would have us believe, nor would any applicant be turned down simply because he had C. & G. Radio-Comm. plus Tech. Elec. II, or A.M.Brit.I.R.E. instead of Higher National Certificate.

I am not conversant with the inner workings of the Technical and Scientific Register, nevertheless I would advise him to take heart rather than umbrage, and not to take such advertisements too literally. H. WILLAN CRITCHLEY.  
Scarborough.

MAY I as a regular reader of *The Wireless World* encroach upon your space to support the views of "Unemployed, A.M.Brit.I.R.E." in the November issue?

I, also, have City and Guilds Radio-Communication I, II and III and Technical Electricity II and am employed by the Admiralty as an Assistant Scientific Officer on radar. I find that my colleagues who ob-

tain Higher National Certificates are usually rewarded with promotion to A.E.O. (two grades higher) but City and Guilds certificates receive no recognition at all, although the latter are much more closely related to our daily work.

I feel it is time that Government departments assessed the value of other qualifications and gave the holders due recognition.

"BUNNY."

London, S.E.1.

### Valve Types

THE valve position in this country has always been notable for its confusion and we all had hopes that with the benefit of octal based valves we should have a standard which would serve for the majority of purposes.

It appears that new sets are being made in which rectifiers and output valves are of the all-glass type. It is generally agreed that this construction makes for much better tubes at v.h.f., but has it any advantages at audio and power frequencies?

It has three disadvantages:—

1. The pins generally do not make such good contact with the holder.
2. The bases are liable to crack round the pins.
3. The price is usually considerably higher.

If there is a good reason for the change I should like to know it; otherwise I hope that, in the majority of cases when replacements fall due, someone will change the valve holders for octal type.

H. O. BRADSHAW.

Birmingham, 31.

### Beacon Interference


I AM very glad that the matter of these medium-wave beacons has been raised again. I feel, though, that "Mikerobe" (your November issue) is either considerably less critical or more long-suffering than I am.

My letter to my M.P. on this subject produced a reply from the Assistant P.M.G., dated 20th October, 1947, to which I called your attention at the time.

In particular, we have a very fine local phenomenon, in the shape of a 2nd harmonic from Crowdon Airport beacon on 400kc/s, though this has never bothered me, as it appears to be crystal controlled, unlike the others, and keeps off the B.B.C.

I hope that it will not be neces-

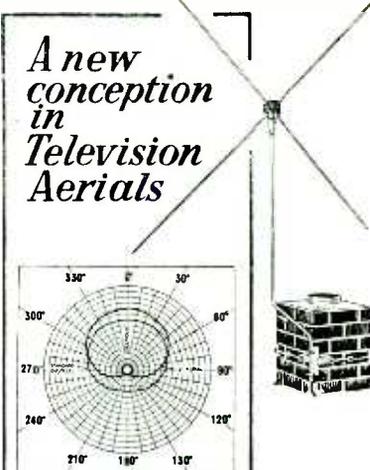**A new conception in Television Aerials**



**Horizontal Polar diagram at 45 Mc/s**  
The Forward Gain of the "Antex" Aerial is 2db better than a standard "H" array.

**THE "ANTEX" (REGD.)**  
**Greater Signal Strength**  
**Greater Noise Cut**  
**Less weight - Less Cost**

Antiference research and engineering knowledge once more lead the way with this revolutionary new "ANTEX" (Regd.) Aerial. With front-to-back ratio of 22.0 db and a forward gain of 2 db when compared with the standard 'H' aerial, it brings a new level of quality to television reception.

The electrical and mechanical design of this aerial is protected by Prov. Pat. Nos. 35957/46 and 12178/49 and Regd. Design No. 859630.

**FRONT/BACK RATIO**

Standard Dipole and Reflector ('H' array)— 7.5 db, "ANTEX" AERIAL ('X' array) — 22.0 db

**MODEL XL for London ; XL/B for Birmingham,** including 7-ft mast and chimney lashing equipment as illustrated. - - - **£3-15-0**

**MODEL XW for London ; XW/B for Birmingham,** including 7-ft mast and - - - **£3-0-0**  
wall mounting bracket - - -

**ANTIFERENCE**  
LIMITED  
67 BRYANSTON ST., LONDON, W.1.

## Letters to the Editor

sary for the Post Office to take action against these offenders, and that they will quietly disappear.

South Croydon. J. B. ROSCOE.

## Photomicrography

**Y**OUR report on C. E. Watt's address to the B.S.R.A. (December, 1949 issue) on his valuable work in the photographic examination of record grooves, styli, etc., refers throughout to this technique as "microphotography."

This is incorrect, as this term relates to the production of miniature transparencies or prints from normal negatives or objects of ordinary dimensions, e.g., letters, documents. The proper description for the preparation of these greatly enlarged negatives or prints of objects of microscopic dimensions is "photomicrography," which word was used in the title of the lecture.

In the same issue another term that interests me is in the opening paragraph of E. W. Berth-Jones's article on measuring turntable speed fluctuations, where erratic non-cyclic speed changes are said to be frequently called "watering"; surely this is a misprint for "waver-ing"? DONALD W. ALDOUS.

Torquay, Devon.

[No, this was not a misprint. We understand the term "watering" is widely used, particularly in film recording.—ED.]

## "Pick-up Design"

**I** READ with horror the last paragraph of the article by T. S. Marshall in the November issue. His suggestion that a jewelled point be used on old and valuable records will surely be ridiculed by the serious collector, because in the olden days there was little consistency in any one make of record, let alone different makes. The tip-radius would depend on the make of record, the factory it came from, the year it was made, and the amount of wear it has already had; indeed, it would become difficult to single out the correct tip to use.

Imagine the plight of an old disc after having (*n-1*) ill-fitting hard tips ploughing their way along its inconsistent groove and ruining once and for all its already poor and equally inconsistent surface, in an effort to find the best size. One need glimpse only once the bushy mass of swarf around the tip of a decent sapphire after playing even a modern record under as nearly ideal conditions as possible.

Any enthusiast knows that the only way to play an old record with a minimum of surface noise and wear is to use a soft point. Now

let me make it perfectly clear that I am not advocating a triangular needle in a sound-box which one can hardly lift (these gave easily the best results of their day, and I have yet to see a record appreciably worn under these conditions), because even we "Soft-Point-Men" have advanced a little.

I, like many others, use a miniature thorn in a light-weight pickup of reputable make. If thorn needles are used intelligently (which includes keeping them dry and crisp) one sharpening will last enough sides for all but the idealist. Furthermore, they do not pick up dust to chew up the groove, at least, not as far as my eye can see with the aid of a biological microscope. As proof of this, I have a collection of over 500 selected recordings which, though very much played, are all in that immaculate fibred condition which high-class dealers demand.

But back to Mr. Marshall's theme of noise reduction by large tip-radius. A thorn soon wears to the optimum size and stays there, however old the record, hence the correct top-cut is quite automatically brought into operation.

I fully appreciate the age of this controversy, which has gone on since the gramophone needle was invented, and most emphatically I do not wish to restart it. All I ask is that collectors of old records pick one that does not matter if they wish to use a sapphire—or any other hard point—since these are all we possess to remind us of the lost artistry of olden days.

JAMES A. MacHARG.

Gosforth.

**R**EFERRING to the first point in Mr. Lowden's letter in your December issue, I introduced the term "pinch effect" because I thought it would convey very clearly to readers the conception of the included angle of the groove walls not being constant but varying continuously throughout the modulation cycle. What I did, and still do, intend to state is the fact that where the groove is too large for the stylus it will, in the course of the cycle, penetrate the groove so deeply as to come in contact with the bottom thereof and be compelled to lose contact with one of the groove walls. No amount of theoretical argument as to what groove dimensions records are supposed to be cut, will get over the fact that *in practice* a large number of commercial pressings will not play with a 0.0025in stylus, and that one has to go up to a 0.0035in stylus, and sometimes even beyond, before a satisfactory signal-noise ratio can be achieved.

Second, the groove depicted in Fig. 3 was found by shadow-graph-

ing the unmodulated groove on a well known standard frequency record. Whether or not it has the dimensions intended by the makers, I do not know, but I think it can be assumed to be fairly typical of pre-war pressings. As to fitting the groove, the fit is to be regarded from the engineering viewpoint, and was never intended to be taken as satisfactory from the reproducing standpoint.

It must be remembered that in developing this new pick-up we were not concerned solely with providing one that would do full justice to the latest recordings but also one that would give acceptable results with recordings that are normally regarded as unplayable on modern equipment. I have had the pleasure of personally helping several very disheartened record collectors in this respect, and it was primarily for such folk that the article was written.

T. S. MARSHALL.

London, E.18.

## CLUB NEWS

**Basingstoke.**—At the next meeting of the Basingstoke-District Amateur Radio Society on January 6th at 7.45 at the British Workmen's Restaurant, Basingstoke, the design and construction of communication receivers will be discussed. Sec.: L. S. Adams, 16, Bramblvs Drive, Basingstoke, Hants.

**Cleckheaton.**—L. Butterworth, of R. N. Fitton (Ambassador) will deal with radiogramophones at the meeting of the Spen Valley Radio and Television Society at 7.30 on January 18th at the Temperance Hall, Cleckheaton. Sec.: N. Pride, 100, Raikes Lane, Birstall, Nr. Leeds, Yorks.

**Croydon.**—Members of the British Television Viewers' Society will be addressed by D. F. Wolfe-Murray (B.B.C. Television Liaison Officer) and Harold Cox (B.B.C. Newsreel Manager) at their next monthly meeting on January 16th at 8.0 at Kennard's Restaurant, Croydon. Sec.: F. E. Gearing, 58, Woodland Way, Mitcham, Surrey.

**Manchester.**—Monthly meetings of the Manchester Area Group of the Radio Controlled Models Society are held alternately on Saturdays and Sundays. The next meeting will be on January 15th. Sec.: L. Witcombe, 12, The Crescent, Prestwich, near Manchester, Lancs.

**Sunderland.**—A series of lectures on valve manufacture by members of the staff of the Edison Swan Electric Co. has been arranged for the Sunderland Radio Society (G3CSR). The third of the series — on "Grids," by R. Matthews — will be given on January 18th. At the meeting on January 11th A. E. Coghlan will talk on "Design of R.F. Components for Superhets." Meetings are held at 8.0 at the Club Room, Prospect House, Prospect Row, Sunderland. Sec.: C. A. Chester, 38, Westfield Grove, High Barnes, Sunderland, Co. Durham.

# SHORT-WAVE CONDITIONS

## November in Retrospect : Forecast for January

By T. W. BENNINGTON (*Engineering Division, B.B.C.*)

**D**URING November the average maximum usable frequencies for these latitudes increased considerably during the daytime, and decreased considerably by night. This was in accordance with the normal seasonal trend. Daytime working frequencies were, in fact, rather higher than had been expected. 28Mc/s, for example, was regularly usable over most circuits from this country at the appropriate time of day, and American police signals on 42Mc/s were often receivable here. The London television signals were received in South Africa on very many occasions during the month. At night the highest regularly usable frequencies were about 6 or 7 Mc/s.

Sunspot activity during the month was, on the average, only slightly lower than during the previous month, and now stands at a value much higher than was expected a year ago. This high solar activity accounts, no doubt, for the particularly high values of the daytime working frequencies.

Ionospheric storms occurred during the periods 1st-5th, 11th-12th, 19th-22nd and 29th-30th, and on 6 nights during the month,

within each of these periods, the storms were accompanied by displays of the Aurora Borealis visible in this country. Dellinger fadeouts were reported as occurring at 1158 on 5th, 0940 and 1133 on 17th and 1030 on 19th.


**Forecast.**—There should be little change in either day-time or night-time m.u.f.s. between December and January, the former remaining relatively high (though not so high as in November) and the latter being, on the average, near the lowest values for the present winter season.

Long-distance working frequencies should thus be high by day and low by night. The period during which the higher frequencies should be usable will, of course, be relatively short, and that for the lower frequencies relatively long. Frequencies as high as 28Mc/s should be frequently usable over most circuits at the appropriate time of day (regularly usable to the eastern part of North America), whilst at night those as low as 7 or 6Mc/s will be really necessary over most paths.

Ionospheric storms are likely to be troublesome after dark in January, although this is not usually a bad month. Long-term prediction here

is, of necessity, effected at present solely on the basis of the 27-day recurrence tendency in ionospheric and magnetic disturbances. As a rule this gives good results at certain periods in the sunspot cycle, but has not been doing so lately. Until either the 27-day recurrence tendency begins to give better prediction results, or other data becomes available on which to base long-term predictions, we shall not, therefore, in this column, attempt to specify the days on which ionospheric storms may occur.

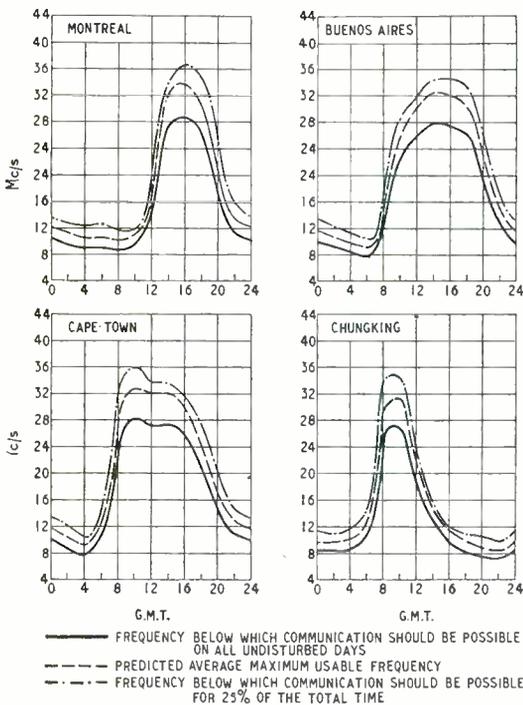The curves indicate the highest frequencies likely to be usable over four long-distance circuits from this country during January.



# New TRIX Quality SOUND EQUIPMENT



MODEL T.101

12 Watt

## High Fidelity AMPLIFIER

This latest Trix model is a versatile high fidelity amplifier suitable for numerous applications. It incorporates special twin channel tone compensation circuits with controls for bass and treble boost, and push-pull output stage with inverse feedback, thus providing exceptional quality of reproduction.

Separate input sockets are fitted for gramophone pick-up, microphone and radio inputs with appropriate selector switch on the front panel.

A socket is also incorporated for H.T. and L.T. supply to feed an external mixer or radio feeder unit.

The output is high impedance, allowing several external speakers to be connected, on long lines without loss of power.

Full details of this amplifier and other models in the large Trix range of Sound Equipment available on request. Send for latest catalogues and price lists.

**THE TRIX ELECTRICAL CO. LTD.**  
1-5 Maple Place, Tottenham Court Road,  
London, W.1. Phone: MUSeum 5817  
Grams & Cables: "Trixradio, Wesdo, London."

AMPLIFIERS · MICROPHONES · LOUDSPEAKERS

# RANDOM RADIATIONS

By "DIALLIST"

## Take Off the Brakes!

AS THE DAYS GO BY, I read of television development programmes in other countries and become, by turns, more depressed and more wrathful over the slow *tempo* and the general inadequacy of what is being done here. That's one reason why I make no apology for returning to the subject. We were first in the field of television. We have adopted a system which makes good reception possible with domestic apparatus priced considerably lower than that manufactured in other countries. The interest shown by our people in television is enormous. Home sales of television receivers could be many times what they are if we had a scheme for completing a country-wide transmitting system within, say, two years from now. Nor can there be any doubt that we should have a fine chance of building up important overseas markets for transmitting and receiving gear. The B.B.C.'s plans for a country-wide system are cut and dried, so that something like a complete service could be in operation within a couple of years. Nothing is needed but permission to go ahead from the "Powers that Be." Let's hope that they'll have vision enough to realize the importance of the matter and to take off the brakes.

## Interfering Fluorescent Lamps

A LETTER FROM a Netherlands reader has raised a very interesting point. Briefly, he told me that though the firm with which he is associated uses fluorescent lamps in its workshops, it has had to return to lamps of the incandescent type in rooms where wireless apparatus is demonstrated to customers, on account of the interference which fluorescents were found to cause. Could I, he asked, tell him of any successful suppressor for these lamps? I knew from experience that some tubes (though only a small percentage) cause interference with short-wave radio and with television. My own practice has long been, like that of my Dutch friend, to change over from fluorescent to

incandescent lighting when any sort of s.w. or u.s.w. reception is in progress. When I recalled that at Radiolympia there had been hundreds of fluorescent lamps without any apparent interference with television reception, I realized that something must have been done about it.

## Oscillation Problem

Drawing a bow not so much at a venture as with a fair feeling of certainty that my arrow was aimed at the right direction, I sent a line to E. M. Lee of the firm which makes the prevention of interference one of its special studies. His reply told me several things about fluorescent tubes that I didn't know, and I am sure that some of them will be news to most readers. About 6 per cent of new tubes give rise to interference, which, as a rule, does not start until about a quarter of an hour after they have been switched on. At the end of this time an interference-producing tube suddenly starts to oscillate. Some tubes, however, which are blameless when new, develop interference-producing properties with age. An oscillating (and therefore interfering) tube can often be stabilized by tapping the glass; but it falls back into oscillation in a matter of minutes. So

far, tube manufacturers know of no means of controlling or preventing this oscillation, or of predicting whether or not a given tube will be liable to it.

## Heater "Poisoning"

Next time you find that a fluorescent tube is causing interference take a look at the heater at either end through the clear glass near the caps. On one of them you will see a noticeably bright spot. Tap the glass and it disappears at once; so does the interference. But both return simultaneously within from three to 15 minutes. The trouble is believed to be due to a form of "poisoning" of the heater coating. Belling and Lee have produced a neat little suppressor, easily fitted to any existing fluorescent tube mounting. How effective it is was proved by conditions at Olympia. The Radio Industry Council laid down that every fluorescent tube in the building should be fitted with this suppressor. This was duly carried out—but on the opening day there was some interference with television. The source was found to be a particular stand on which one or two tubes were oscillating. Suppressors had been provided, but the electricians who fitted them had connected them incorrectly. The connections having been put right, there was no more interference.

## Television and Broadcasting

FORECASTS BY WRITERS on the other side of the Atlantic that "sound" broadcasting will soon be ousted by television have been



## Books Published for "Wireless World"

	Net Price	By post
RADIO VALVE DATA. Characteristics of 1,600 Receiving Valves	3/6	3/9
RADIO DATA CHARTS, by R. T. Beatty, M.A., B.E., D.Sc., Fifth Edition—revised by J. McG. Sowerby, B.A., A.M.I.E.E.	7/6	7/11
GUIDE TO BROADCASTING STATIONS. Fifth Edition	1/6	1/7
BASIC MATHEMATICS FOR RADIO STUDENTS, by F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. Second Edition	10/6	10/10
RADIO LABORATORY HANDBOOK. Fourth Edition, by M. G. Scroggie, B.Sc., M.I.E.E.	12/6	12/11
WIRELESS SERVICING MANUAL, by W. T. Cocking, M.I.E.E., Seventh Edition	10/6	10/10
TELEVISION RECEIVER CONSTRUCTION. A reprint from "Wireless World" (London area only)	2/6	2/9
SUPERHETERODYNE TELEVISION UNIT. A reprint from "Wireless World"	2/6	2/9
WIRELESS DIRECTION FINDING. By R. Keen, M.B.E., B.Eng.(Hons.), Fourth Edition	45/-	45/9

A complete list of books is available on application

Obtainable from all leading booksellers or from  
ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1.

echoed by some writers in this country. Nothing of the sort is likely to happen for a great many years—if it ever does happen! Gloomy predictions of that kind are made about most new things; they are going to kill this or that. Such prophecies come true only when a new system offers a better and cheaper way of doing something that was previously costly and inefficient. The steamship was bound to render the merchant sailing ship obsolete because it could run to a time-table and was less dependent on weather; but it will be a very long time—if it ever does come about—before the steamship is ousted by the 'plane as the most economical way of conveying passengers and goods over the sea. Like radio and television, steamship and 'plane are complementary; each does something that the other can't. Unless basic changes come about in television methods, there can be no near vision equivalent of the three-valve radio set, and certainly not of the crystal set. Vision programmes, again, are far more costly to provide than those for "sound" broadcasting, and that is reason enough for feeling pretty sure that television is likely to remain for a long time a provider of entertainment for only a few hours each day.

**MANUFACTURERS' LITERATURE**

CATALOGUE of receiving aerials and accessories, from Aerialite, Ltd., Castle Works, Stalybridge, Cheshire.

The following new leaflets have been received from the Baldwin Instrument Co., Brooklands Works, Dartford, Kent:—No. 113, Decade Resistance Boxes; No. 114, Visual Null Indicator; No. 116, Farmer Electrometer-Voltmeter; No. 120, Gamma Radiation Detector (Type PP); No. 1001, Scientific and Industrial Measuring Instruments; No. 1002, Scientific Measuring Instruments for X-rays and other Ionizing Radiations; No. 1003, Scientific Measuring Instruments for Photometry.

List of r.f. coils and transformers, from the British Distributing Co., 66, High Street, London, N.8.

Supplement No. 1 to literature describing the Type NMT industrial noise measuring equipment made by A. E. Cawkell, 7, Victory Arcade, The Broadway, Southall, Middlesex.


Illustrated leaflets describing amplifying and intercomm. equipment made

*Quality* **ELECTRONIC COMPONENTS**

**FAMOUS ALL OVER THE WORLD**

THE EXPERIENCE OF 25 YEARS BEHIND EVERY COMPONENT

**SWITCHES**

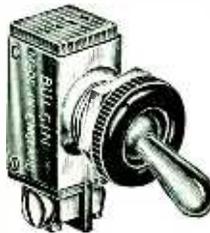

List No. S.472.P.D.




heavy duty lever switch, 1-pole 2-way or Change-Over. For 10A. at 6V., to 4A. at 250V. max. working. Cr.-plated steel frame with highest grade insulation. Guaranteed for 25,000 operations.

List No. S.325

—new version of the long-popular 1-pole M.-B. switch, showing two of the many variations obtainable on all models; pear dolly, and insulated front ring. For all 0-250V., 5A. max. circuits. Laminated-by-Edite construction, for long life.

**SIGNAL-LAMP FITTINGS**

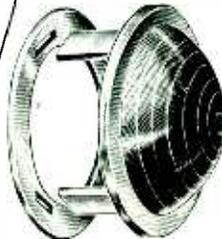

List No. D.600



List No. D.380



List No. D.270



List No. D.300



List No. D.150


Bulgin Signal-lamp fittings and 'Lens' Bushes—are found on all types of electronic and domestic apparatus. Made to take lamps by all well-known makers. For low and main voltages, with metal bezels or moulded bezels in many brilliant colours. Made in all sizes from .343 in. dia. to 1 1/2 in. dia. Chrome, Nickel, Bronze, metal finishes available.

**DISTINCTIVE MOULDINGS**

—twin fuseholder with cover, taking standard BS.646B 1 1/2 x 1/4 in. dia. fuses; 6 B.A. terminals. For 250V., 5A. max. Complete with 1 Amp. Fuses unless specified.



List No. F.10

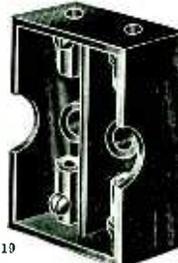

List No. P.443

—moulded Internat. Octal plug or adaptor has silver-plated pins, removable cover, and wide range of uses. Precisely made to standard valve-base dimensions. Takes up to 1A. per pole.

EVERY COMPONENT GUARANTEED

SEND FOR NEW ILLUSTRATED CATALOGUE 1/- post free

**BULGIN**

A. F. BULGIN & CO. LTD.  
BYE-PASS ROAD, BARKING  
Telephone: RlPpleway 3474 (5 lines)

## MANUFACTURERS' LITERATURE

by Easco Electrical, Brighton Terrace, London, S.W.9.

Descriptive leaflet of "Kling" protective cellulose lacquers, from the East Anglia Lacquer Co., Street One, Aycliffe, Darlington.

Abridged leaflet listing rotary converters for radio, television and p.a. equipment, from the Electro Dynamic Construction Co., St. Mary Cray, Kent.

Illustrated list (EST<sub>2</sub>) of miniaturized hermetically sealed transformers, from Ferranti, Ltd., Hollinwood, Lancashire.

Illustrated catalogue of standard electronic instrument cases, including

a new range of enclosed racks, from Alfred Imhof, 112-116, New Oxford Street, London, W.C.1.

Catalogue "Special Valves and Electronic Devices for Industry and Research," including the new type 57CV photometric cell, from Mullard Electronic Products, Century House, Shaftesbury Avenue, London, W.C.2.

Reference card of useful data and tables for radio technicians, and a new leaflet, "Hints on Soldering," from Multicore Solders, Mellier House, Albemarle Street, London, W.1.

Brochure "Methyl Bromide Extinguishers for Electrical Fire Risks" (including applications to radio transmitters), from the National Fire Pro-

tection Co., Argosy Works, Kingston Road, Leatherhead, Surrey.

Illustrated leaflet dealing with synthetic sapphire inserted gramophone needles, from Salford Electrical Instruments, Silk Street, Salford, 3, Lancashire.

Bulletin F/SRT5 (Edition 2), "Low Current Tubular Rectifiers," and Bulletin F/SRT6 (Edition 3), "Single Phase Medium Current Rectifiers," from Standard Telephones and Cables, Rectifier Division, Warwick Road, Boreham Wood, Herts.

Illustrated leaflet describing "Triette" portable electric gramophones and record players, from Phonodisc, Ltd., 1-5, Maple Place, London, W.1.

# RECENT INVENTIONS

## A Selection of the More Interesting Radio Developments

### Magnetic Recording

THIS relates to the use of a magnetizable grooved disc record instead of the conventional type.

Sound recording and reproducing heads which are essentially similar but may differ in detail, comprise an elongated spool *a* lined with a thin tube *b* of Permalloy or like material. The end of the bore is tapered and the bore accommodates a similarly shaped needle *c* of material of high electrical resistance and low coercive force (e.g., 6 per cent silicon alloy). The needle is held in place by set screw *d* through

resilient washer *e*. The whole is surrounded by a magnetizable frame *f*. The reproducing head may have a magnetic shield *g*, while a recording head may have a separate d.c. winding to give a unidirectional magnetic bias.

The British Thomson-Houston Co., Ltd. Convention date (U.S.A.) January 9, 1945. No. 625,563.

### T-R Aerial System

COMMON T-R aerial systems have various advantages for duplex working from the point of view of space, ease of alignment and so on. A system of this character relying on cross

polarization of the waves operating in the two directions and utilizing a waveguide system is shown on the sketch; this comprises a radially positioned transmitting probe *a* and an axially placed receiving probe *b*, the two being spaced by a block *c* of polystyrene of semicircular section which may be grooved to receive the receiving probe *b*. This block is of such length that an  $H_{11}$  mode wave which is vertically polarized will be transformed into an  $E_0$  mode wave and *vice versa* but will have no effect on a horizontally polarized  $H_{11}$  mode wave. With the probes arranged as shown, the transmitting probe will not excite the receiving probe. The aerial system of the other station will, of course, have the transmitting probe vertically arranged with the flat face of the block parallel thereto so that duplex working is possible. Local oscillator signals of the receiver may set up an E mode wave in the guide which will be transformed by the block *c* into a vertically polarized  $H_{11}$  mode wave which, however, is not receivable by the remote aerial system and thus cannot interfere with reception.


E. Coop. Application date, November 21st, 1946. No. 623,770.

### Crystal Mountings


PIEZO crystals of rectangular or disc form, cut to oscillate in a thickness shear mode, many tend to vibrate only at their centre, hence they are clamped at their corners or around their periphery.

The mounting described is relatively simple and cheap and permits a small frequency adjustment. Three or more silver "spots" are deposited towards the edges of the crystal, which are then lapped down so that when mounted between plates, which function as energizing electrodes, but are not in physical contact with the crystal.

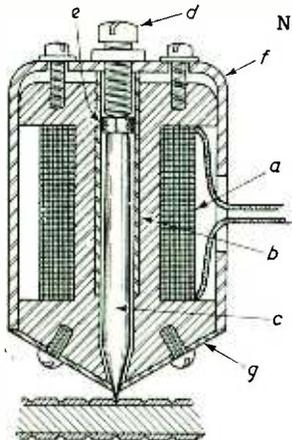The General Electric Co., Ltd., G. M. Wells and L. Rollin. Application date, March 3rd, 1947. No. 625,180.



Needle-type magnetic recording head.

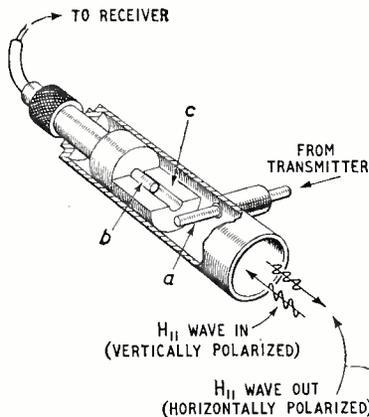

Junction for duplex working on a common T-R aerial system.

The British Abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 2/- each.



PRICE  
**£35**

This instrument, which is an up-to-date example of current instrument practice, has been developed to meet the growing demand for an instrument of laboratory sensitivity built in a robust and portable form, for use in conjunction with electronic and other apparatus where it is imperative that the instrument should present a negligible loading factor upon the circuit under test.

The instrument consists basically of a balanced bridge voltmeter. It incorporates many unique features and a wide set of ranges so that in operation it is as simple to use as a normal multi-range testmeter.

The instrument gives 49 ranges of readings as follows:—


- D.C. VOLTS: 2.5mV. to 10,000V.  
(Input Resistance 111.1 megohms).
- D.C. CURRENT: 0.25 $\mu$ A. to 1 Amp.  
(150mV. drop on all ranges)-
- A.C. VOLTS: 0.1V. to 2,500 V. R.M.S. up to 1 Mc/s. With external diode probe 0.1V. to 250 V. up to 200 Mc/s.
- A.C. OUTPUT POWER: 5mW. to 5 watts in 6 different load resistances from 5 to 5,000 ohms.
- DECIBELS: -10db. to +20db.
- CAPACITANCE: .0001 $\mu$ F. to 50 $\mu$ F.
- RESISTANCE: 0.2 ohms to 10 megohms.
- INSULATION: 0.1 megohm to 1,000 megohms.

The thermionic circuit gives delicate galvanometer sensitivity to a robust moving coil movement. It is almost impossible to damage by overload. The instrument is quickly set up for any of the various tests to be undertaken, a single circuit selector switch automatically removing from the circuit any voltages and controls which are not required for the test in question.

Fully descriptive pamphlet available on application.

Sole Proprietors and Manufacturers:

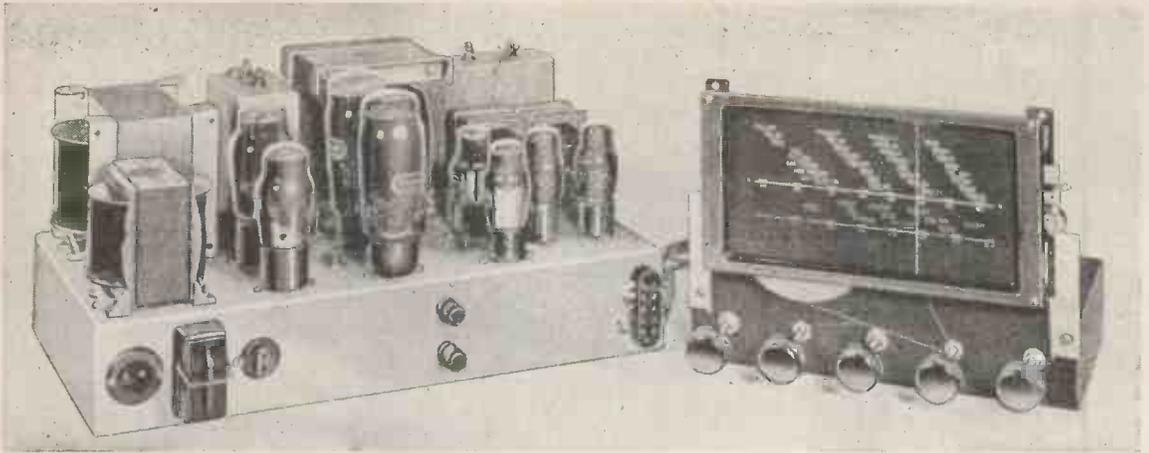**The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.**  
WINDER HOUSE • DOUGLAS STREET • LONDON • S.W.1 Telephone: VICTORIA 3404/9



# GOODSELL

15-WATT HI-FIDELITY AMPLIFIERS ARE UNSURPASSED IN PERFORMANCE

AS DESCRIBED BY T. D. N. WILLIAMSON IN "Wireless World" AUG, 1949.

The fidelity of reproduction given by the Williamson Amplifier is now an accepted standard throughout the world. This high standard is made possible by the following important features.

- Specially designed output transformer.
- Low phase shift.
- Heavy feedback, which includes the output transformer and all the valves.

These features make possible :

- Low linear distortion, with less than 0.1 per cent. harmonic content.
- Low intermodulation distortion.

Our amplifiers are built to strict specification and incorporate only the finest components. After assembly and adjustment by experts they are severely tested to ensure the highest possible standard of performance.

## PRICES:

Amplifiers ..... from £19 19 0 } No  
 Pre-Amplifiers ..... from £8 0 0 } tax

Three types of Radio Feeder Units available for varying listening conditions.

- Local Distance TRF.
- Two RF stage, four station pretuned, with AVC.
- Super-het with RF and one IF stage, quality detector, also embodying an additional switch position whereby the set becomes a local distance quality receiver with single RF and infinite impedance detector.

All the above available with built-in tone control stage, as per our amplifier booklet.

Full details in illustrated leaflet.

Send for free illustrated brochure.

Manufactured by **GOODSELL LTD, 40 GARDNER ST., BRIGHTON, SUSSEX** Telephone: 6735

Easy Terms from **LONDON RADIO SUPPLY CO., Balcombe, Sussex.**

# Virginia Mayo

Starring in the Samuel Goldwyn  
Technicolour Production  
"A Song is Born"



**USING  
HER**



*Made in England. Protected  
by British & Foreign Patents  
and Patents Pending.*

*Full details from the Manufacturers, or Demonstrations by  
Appointment.*

**THERMIONIC PRODUCTS LTD.**  
**MORRIS HOUSE, JERMYN STREET,**  
**HAYMARKET, LONDON, S.W.1**  
Telephone: WHItchall 6422 (5 lines)

The tremendous advantages offered by the Soundmirror Magnetic Recorder have been seized upon not only by screen and stage stars, but by eminent lecturers and educationalists, leading men in the professions and musicians and music lovers.

The Soundmirror is a high-fidelity Instrument which records and reproduces on reels of inexpensive magnetic tape, speech, music and sound of every kind. Each reel gives a full half-hour's recording. Short recordings can be cut and joined together. Playback is immediate, and recordings are permanent, or if desired, can be automatically erased as new items are recorded.

Simple to operate, the Soundmirror has a single finger-tip control for Play, Record, Fast Re-wind or Fast Forward requirements. Built-in jacks enable you to use the Soundmirror in conjunction with radio or public address equipment.

# PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.



**PREMIER MIDGET RADIO KIT.** Due to greatly increased production we are now able to offer this Kit at a greatly reduced price. Including an attractive Bakelite case, 12in. long x 6in. wide x 6in. high. The valve line up is 6K7, 6J7, 6V6 and a Selenium Rectifier in the A.C. model; and 6K7, 6J7, 25A6 and Selenium Rectifier in the A.O./D.C. model. Both are for use on 200 to 250 volt mains. The dial is illuminated, and the receiver presents a very attractive appearance. Coverage is for the medium and long wavebands. Complete kits of parts with cabinet and diagrams, £4/19/6, Inc. Purchase Tax.

**PREMIER MIDGET SUPERHET KIT.** This powerful Midget Superhet Receiver is designed to cover the short-wave bands between 10 and 50 metres and the medium wavebands between 200 and 657 metres. Two models are produced, one for 200-250 volt A.C. mains, and the other for 200-250 volts A.C. or D.C. mains. Both are supplied with the same plastic cabinet as the TRF Receiver. The A.C. valve line-up is 6K8, 6K7, 6Q7, 6V6 and a selenium rectifier. The A.O./D.C. line-up is the same, with the exception of the output valve which is a 25A6. The dial is illuminated, making a very attractive receiver. Complete kit of parts with cabinet and diagrams, £6/19/6, Inc. Purchase Tax.

**PLASTIC CABINETS,** as illustrated above. In Brown, 17/6. In Ivory, 22/6.

**COLLARO AUTOMATIC RECORD CHANGERS.**

Type RC600 Rim-drive. Plays nine 10in. or 12in. records. A.C. 100/250 v., with High Fidelity Magnetic or Crystal Pick-up, £10/15/-. With Sapphire Stylus, £11/8/4.

**COLLARO GRAMOPHONE UNITS.**

High grade Rim-drive Motors, complete with Pick-up and Automatic Stop-Start. A.C. 100/250. With Magnetic Pick-up, £5 3/2. With Crystal Pick-up, £5 17/7.

**COLLARO GRAMOPHONE UNITS AT NEARLY HALF PRICE.** Motor, Tone arm and Pick-up in one unit. Auto Stop-Start, variable speed, 12in. turntable. Induction Motor for 100/250 v., 50 cycles. with Magnetic Pick-up, £6/6/-. With Crystal Pick-up, £7/4/8.

**CONRAD GRAMOPHONE MOTORS.**

A reliable Rim-drive Motor for A.C. 100/250 v. operation, £2/17/6.

**SECTIONAL WHIP AERIAL.** Seven sections which plug into each other making an aerial 14ft. long. Thinnest section 1in. diam., thickest section 1in. diam. Weather proof enamel. 3/6 each complete.

**INSULATED BASE** for above, 2/6 each.

**METER KIT.**

A FERRANTI 500 MICROAMP MC METER, with separate High Stability, High Accuracy, Resistors to measure, 15, 60, 150 and 600 volts D.C. Scale length 1 1/2in., diameter 2 1/2in. 10/- the complete kit.

5 KV. ELECTROSTATIC VOLT METER. Scale length 3 1/2in., flush mounting, 4 1/2in. diameter, £2/10/-.

**METERS.**

Full Scale Deflection	Scale Marking	Scale Length	Scale Movement	Price
1 mA.	0-100	2 1/2in.	M/C D.C.	15/11
1 mA.	0-1	2 1/2in.	M/C D.C.	7/6
5 mA.	0-5	2 1/2in.	M/C D.C.	5/-
30 mA.	0-30	2 1/2in.	M/C D.C.	10/8
50 mA.	0-50	2 1/2in.	M/C D.C.	8/6
150 mA.	0-150	2 1/2in.	M/C D.C.	6/-
200 mA.	0-200	2 1/2in.	M/C D.C.	8/6
2.5 Amp.	0-2.5	2 1/2in.	Thermo	5/-
3 Amp.	0-3	1 1/2in.	Thermo	5/-
3.5 Amp.	0-3.5	1 1/2in.	Thermo	5/-
20 Amp.	0-20	2 1/2in.	M/C D.C.	7/6
25 Amp.	0-25	2 1/2in.	M/D.C.	2/11
40 Amp.	0-40	2 1/2in.	M/C D.C.	7/6
20 v.	0-20	2 1/2in.	M/C D.C.	5/9
40 v.	0-40	2 1/2in.	M/C D.C.	5/9
300 v.	0-300	1 1/2in.	M/C D.C.	10/-
5,000 v.	0-5,000	3 1/2in.	Elect.	50/-
500 u.a.	0-15 or 0-600	2 1/2in.	M/C D.C.	5/-
500 u.a.	0-500	2 1/2in.	M/C D.C.	7/6
500 u.a.	0-500	2 1/2in.	M/C D.C.	19/6

V.C.R.97. C.R. Tubes. New and tested to give full-size picture, 35/- each.

The following C.R. Tubes for callers only:—

VCR516A	40/-	VCR522	15/-
VCR517E	30/-	VCR511B	60/-
VCR140	50/-	VCR138	5/-
Mullard MW.22-3	9in. Magnetic Tubes at	£3/15/-	
<b>TRANSMITTING AND SPECIAL PURPOSE VALVES</b>			
705A	10/-	RL18 (CV1197)	5/-
401	2/10	803	25/-
432	10/-	HY114B (CV3505)	15/-
YS168 (CV1068)	6/8	MR300/E (CV3558)	15/-
EL266 (CV15)	40/-	1616	5/-
805	17/6	8012	10/-
KB/S (CV180)	60/-	843	5/-
EI191 (CV12)	60/-	1625	5/-
BHTT (CV19)	60/-	U19 (CV187)	6/6

**ELECTRON MULTIPLIER PHOTO CELL TUBES.** Type 931A. Brand new. Guaranteed, 30/-.

**T.V. WHITE RUBBER MASKS.**

We can now supply a specially designed White Rubber Mask for 6in. C.R. Tubes at 7/6 each.

12in. White Masks 15/9

**SUPER QUALITY TELEVISION MAGNIFYING LENS** to suit 6in., 6in. or 7in. Tubes. Increase picture size considerably, 25/- each.

**FRAME AND LINE COIL ASSEMBLY.** Suitable for all standard Magnetic Tubes, 12/6 each.

**PERMANENT MAGNET FOCUS POTS.** Available for all Tubes, 15/- Please state Tube used.

**THE NEW PREMIER 1950 CATALOGUE**

contains all the newest TV Kits, Components, Aerials, Tubes, etc., in addition to thousands of Radio Bargains.

Now ready — 3d.

**NEW 2-VALVE ALL WAVE KIT.** 16 to 2,000 metres. Switched Coil Pack retd. wired and tested. 2 Mazda HL23 Valves, 'Phones, H.T. and L.T. Batteries, Condensers, resistors, diagrams and steel case, all ready to assemble, £3/10/- including Purchase Tax.

**SUPER MOVING COIL MIKE AND STAND.** We have purchased the entire stock of a famous Manufacturer of P.A. Equipment at a very low price, and are offering a £5/5/- Super Moving Coil Mike, with a chromium plated folding stand to match. The list price of the stand was £3/3/-.

**WE OFFER THE PAIR AT 79/6. LESS THAN HALF THE USUAL PRICE.**

**THE NEW PREMIER TABLEGRAM.**



A modern Tablegram, incorporating many new features. Covers Medium and Long Wavebands. Operates on 200-250 v. A.C. Mains. A high-fidelity pick-up and the latest Collaro electric gram. motor ensure excellent record reproduction, £19/19/- including Purchase Tax.

**A LARGE NEW PURCHASE ENABLES US TO OFFER AT A LOWER PRICE THAN EVER R107. ONE OF THE ARMY'S FINEST COMMUNICATIONS RECEIVERS.** (See 'W.W.' August, 1945.)



9 valves, R.F. amp. osc. Frequency Changer, 2 I.F.s. (465 kc.), 2nd Detector, A.V.C. Af. amp. B.F.O. A.C. mains, 100-250 v. or 12 v. accum. Frequency range 17.5 to 7 Mc/s, 7.5 Mc/s to 2.9 Mc/s, 3.0 to 1.2 Mc/s. Monitor L.S. built in. Complete. Write for full details Price £12/12/-, plus 2/- carriage and packing.

**BATTERY CHARGERS.** Input 100/250 v. A.C. Output 15 volts at 16 amps. Continuously variable metered output. Usual price £24. Our price £10/10/- each, plus 10/- carriage.

**BATTERY CHARGER KITS.**

All Incorporate Metal Rectifiers. Transformers are suitable for 200-250 v. A.C. 50 cycles.

Cat. No.	Description	Price.
2002.	Charges 6-volt Accumulator at 1 amp. Resistance supplied to charge 2 v. Accumulator.	£12/6
2003.	Charges 12-volt Accumulator 1 amp.	£17/6
2004.	Output 15 v. 4 a. Variable Resistance and Meter	£3/15/-
2005.	Output 15 v. 6 a. Variable Resistance and Meter	£5/-
2007.	Output 30 v. 5 a. Variable Resistance and Meter	£6/-
2009.	Output 24 v. 3 a. Variable Resistance and Meter	£4/5/-

**ALUMINIUM CHASSIS.** 16 S.W.G. Substantially made of bright aluminium with four sides.

Size	Price.
7 x 3 1/2 x 2 1/2in.	3/3
9 1/2 x 4 1/2 x 2 1/2in.	4/-
10 x 8 x 2 1/2in.	5/6
12 x 9 x 2 1/2in.	6/8
14 x 9 x 2 1/2in.	6/11
16 x 8 x 2 1/2in.	7/3
20 x 8 x 2 1/2in.	7/11
22 x 10 x 2 1/2in.	10/-
10 x 9 x 3 1/2in.	6/3
12 x 10 x 3 1/2in.	6/10
14 x 10 x 3 1/2in.	7/11
16 x 10 x 3 1/2in.	8/6
20 x 10 x 3 1/2in.	10/-

**GOVERNMENT SURPLUS MAINS TRANSFORMERS.**

All are for use on 230 volt 50 cycle Mains.

Type	Price.
42 800-0-500 v. 170 mA. 4 v. 4 a.	25/-
44 10 v. 5 a., 10 v. 5 a., 10 v. 5 a.	35/-
53 250-0-250 v. 60 mA., 5 v. 2 a., 6.3 v. 2.3 a.	15/-
64 275-0-275 v. 60 mA., 5 v. 2 a., 6.3 v. 2.3 a.	15/-
55 250-0-250 v. 100 mA., 5 v. 2 a., 6.3 v. 3.5 a.	17/6

**OIL FILLED MANSBRIDGE CONDENSERS.** 1 mF. 600 v. working, 13 each; 12/- doz. 2 mF., 600/800 v. working, 13 each; 17/- doz. 4 mF., 1,000 v. working, 7/6 each.

mF. Working	Price	mF. Working	Price
8+8 350 v. . . . . 3/6	32+32 350 v. . . . . 4/11		
8+8 450 v. . . . . 3/9	32+32 500 v. . . . . 6/-		
12+12 350 v. . . . . 3/11	4 350 v. . . . . 1/9		
16+8 450 v. . . . . 4/11	8 350 v. . . . . 2/-		
16+16 400 v. . . . . 3/9	16 350 v. . . . . 2/6		
16+32 350 v. . . . . 3/9	50 50 v. . . . . 2/-		

**PORTABLE LOUDSPEAKER CABINETS.**

16 1/2in. x 13 1/2in. x 5 1/2in. Inside. To take 10in. Speaker. Suitable for Portable Amplifier. Price 21/8; or with 10in. Robt Speaker, 39/6.

**POWER SUPPLY UNIT WITH OUTPUT STAGE** for the R155 RECEIVER, in steel case, 10in. x 8in. x 6in., £3/10/-.

**CARBON HAND MICROPHONES,** with switch in handle includes cord, 2/11 each, 24/- doz. Transformers, 2/6 each.

**207, EDGWARE ROAD, W.2**

Phone : AMBassador 4033

**BRANCHES AND AT —**

All POST ORDERS to 167, LOWER CLAPTON ROAD, LONDON, E.5.

Phone: AMHerst 4723

Terms of Business: Cash with order or C.O.D. over £1. Send 2d. stamp for list.

**EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS**

# PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

You can build a commercial looking and working

## TELEVISOR WITH PREMIER KITS FOR

— £17.17.0 —

This Receiver consists of 4 units:

The Sound Receiver, Vision Receiver, Time Base and Power Pack. As is usual in all Premier Kits, every single item down to the last bolt and nut is supplied. All chassis are punched and layout diagrams and theoretical circuits are included.

The cost of the Kits of Parts is as follows :

- VISION RECEIVER with valves, £3/13/6.  
Carriage 2/6.
- SOUND RECEIVER with valves, £2/14/6.  
Carriage 2/6.
- TIME BASE with valves, £2/7/6.  
Carriage 2/6.
- POWER SUPPLY UNIT with valves, £6/3/-.  
Carriage 5/-.

### THE TUBE ASSEMBLY UNIT.

Which contains the VCR97 Cathode Ray Tube and Socket. 6in. P.M. M.C. Loudspeaker with closed field for televisions. Tube Mountings, etc. £2/18/6. Carriage and packing 2/6.



A well-made pedestal cabinet in walnut is available at £5/10/- plus 7/6 packing and carriage.

The Instruction Book costs 2/6, but is credited if a Kit for the Complete Televisor is Purchased.

Any of these Kits may be purchased separately ; in fact any single part can be supplied. A complete priced list of all parts will be found in the Instruction Book.

20 valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver is a screwdriver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

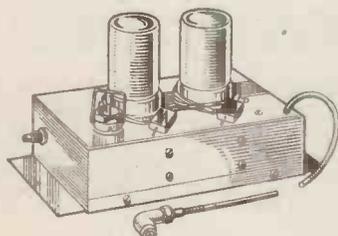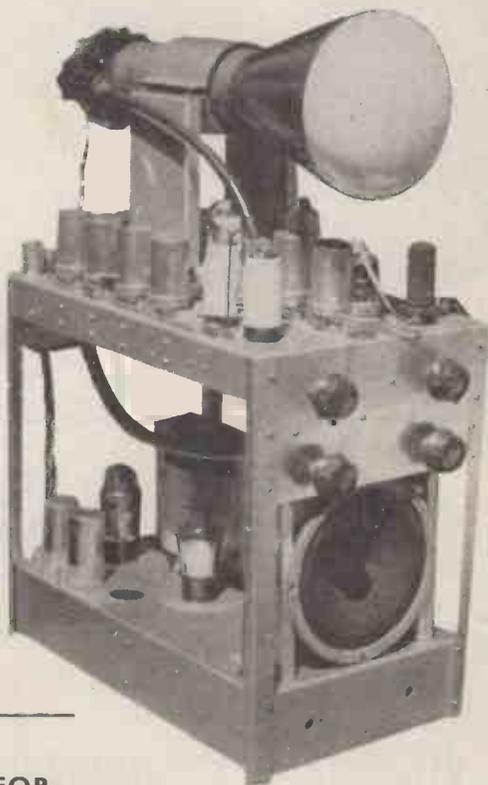Those wishing to build the MIDLAND version of this Televisor can obtain the complete kit with the exception of the coils and rejectors from stock. These will be available a few days after the commencement of full power transmission. The Coils and Rejectors are included in the price of £17/17/-.



### PRE-AMPLIFIER FOR FRINGE RECEPTION AREAS

We can supply the complete kit of parts to make this wide band width Pre-Amplifier, using 2 EF54 Pentodes. Powered by the TV Kit, it is completely screened. With all parts, valves, chassis, diagrams, etc., 27/6. All parts available separately.

WORKING MODELS CAN BE SEEN DURING TRANSMITTING HOURS AT OUR FLEET ST. & EDGWARE RD. BRANCHES

AT **-152-153, FLEET STREET, E.C.4** Phone: CENTral 2833

All POST ORDERS to 167, LOWER CLAPTON ROAD, LONDON, E.5. Phone: AMHerst 4723

Terms of Business: Cash with order or C.O.D. ovs: £1. Send 2' stamp for list.

**EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAY;**

*if*

SEEING IS BELIEVING  
**AMBASSADOR**  
 TELEVISION IS YOUR CHOICE



MODEL TV.2  
**£69.10.0**  
 TAX PAID  
 A.C. only  
 Registered Design  
 No. 859761



MODEL TV.1  
**£105**  
 TAX PAID  
 A.C. only

*Write for illustrated leaflets.*



BRIGHOUSE, YORKSHIRE

# MYCALEX

(REGD. TRADE MARK)

## THE INSULATOR

*May solve your Insulation Problems*  
 with the following

### UNIQUE COMBINATION OF PROPERTIES

- HIGH DIELECTRIC STRENGTH
- LOW-LOSS FACTOR
- HEAT RESISTING
- MANUFACTURED TO CLOSE TOLERANCES
- NON-TRACKING
- RESISTANT TO FUNGUS GROWTH
- WILL NOT SHRINK OR WARP
- LOW EXPANSION CO-EFFICIENT

MACHINED TO CUSTOMER'S REQUIREMENTS OR AVAILABLE  
 IN SHEETS, RODS AND MOULDINGS

Also makers of INGRAM MYCALEX Capacitors utilising MYCALEX  
 as a dielectric with plates moulded in, to form a sealed unit

'Phone: CIRENCESTER 400 or send enquiries to

**MYCALEX COMPANY LTD · ASHCROFT ROAD · CIRENCESTER GLOS**

# 45!


## Right for Every pocket

# TRUVOX

Truvox speakers can be obtained from all good dealers. Full technical data and price lists of the complete Truvox range will be gladly forwarded upon request.

# 12"

# C.P.M.

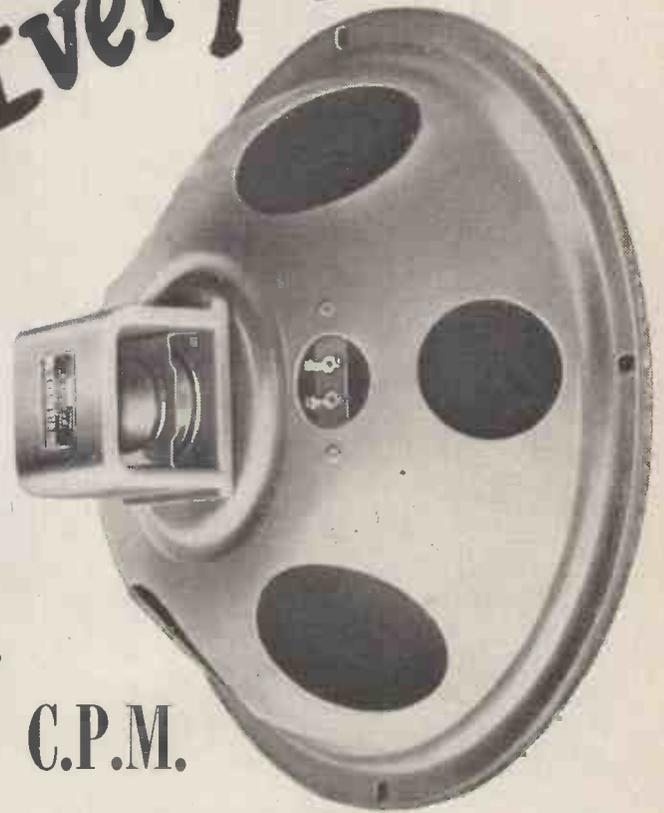

Frequency range 60-8,000 c.p.s. bass resonance 65 c.p.s.; flux density 10,000 gauss; power handling capacity 10 watt (peak). Voice coil D.C. Resistance 2.6 ohms. The specification speaks for itself. The TRUVOX 12 inch C.P.M. speaker Model BX11, marks something of an economic revolution in the high quality reproduction of sound.

**TRUVOX ENGINEERING CO. LTD., EXHIBITION GROUNDS, WEMBLEY, MIDDX.**

*"UNO" and "OCO" floor polishing machines are also manufactured by TRUVOX—send for details.*

The  
**MAGNAVISTA**  
TELEVISION LENS

HOW DO  
YOU VIEW?

The connoisseur uses a "MAGNAVISTA" Television Lens because he knows it gives high magnification, absolute clarity, a wide angle of view, and is optically correct, being constructed in accordance with specifications arrived at in consultation with eminent independent authorities on lens computation.

PRICES

Type	£	s.	d.
A.7, 6in.....	3	3	0
A.1, 2, 4, 5, 8 and 9, 9in. ....	4	14	6
D.1, C.1, 10in. and 12in.....	5	5	0
D.1, 15in. ....	5	15	6
A.3 (Universal), 9in. ....	6	16	6
B.2 (Universal), 10in. ....	7	7	0

**MAGNAVISTA Magnification**  
*is Television Perfection*

**METRO PEX LTD**

Head Office:  
38, Gt. Portland St., London, W.1  
(\*Phone: Museum 9024-5)

Midlands Depot:  
Kings Heath Stn., Birmingham, 14  
(\*Phone: Highbury 2765)



AN EXAMPLE from the Furzehill range of fine instruments is this high-grade oscilloscope for industrial, radio and television applications. Both axes have identical d.c. coupled high sensitivity amplifiers with symmetrical inputs and a level frequency characteristic from zero to 3 M/cs. Particularly valuable features are the instantaneous action of the shift controls, expansion of the time base scan from  $\frac{1}{2}$  to 5 screen diameters, negligible phase shift in the amplifiers and automatic amplitude-limited synchronisation.

For full details of this, and other instruments in the Furzehill range, write for our new illustrated catalogue.



**FURZEHILL LABORATORIES LIMITED**  
BOREHAM WOOD HERTS Tel. ELStree 1137

# Three uses for the Osram KT66

- 1. In Audio-Frequency Power Amplifier Circuits**
- 2. In Radio Frequency Circuits**
- 3. In Voltage Stabilisers**

The Osram Valve Type KT66 is a versatile power tetrode with a number of useful applications. The valve is designed as a beam tetrode with aligned grids which reduce losses in the screen and make for the highest possible power conversion efficiency. The KT66 may be used in the output stage of an audio-frequency power amplifier, either tetrode-connected for maximum sensitivity and power output, or triode-connected for Quality Amplifiers.

**NOTE** — *the characteristics of KT66 and 6L6G are not identical*

THAT THE DEMAND FOR THE OSRAM KT66 IS INCREASING, IS INDISPUTABLE EVIDENCE OF BETTER PERFORMANCE.



**DATA FOR OSRAM KT66**


Heater rating	- -	6.3 volts	1.27 amps.
Anode voltage	- - -	500 max. volts	
Anode dissipation	- - -	25 max. watts	
Screen voltage	- - -	400 max. volts	
Screen dissipation	- - -	3.5 max. watts	

Mutual conductance { as Tetrode 6.3 mA/volt  
as Triode 5.5 mA/volt

PRICE 15/- P.T. 3/3 extra

# Osram

VALVES

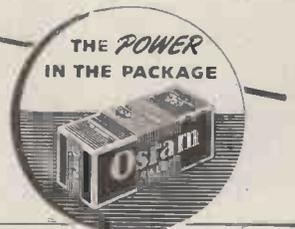

# New Two Speed-motor....

At the turn of a switch you have two speeds, 33 $\frac{1}{3}$  or 78 r.p.m. The Turntable is a full 12" diameter; its main spindle precision ground and lapped, runs in phosphor bronze bearings. The synchronous motor is virtually vibrationless and is suitable for playing standard, transcription and microgroove recordings. Guaranteed mechanically perfect. New super lightweight pick-up available with the interchangeable heads for microgroove and standard recordings.



Retail price, without pick-up £12-10-0

Purchase Tax £5-8-4

A **Connoisseur** PRODUCT

Manufactured by,

A. R. SUGDEN & CO. (ENGINEERS) LTD. WELL GREEN LANE BRIGHOUSE YORKS.

# TEST! - RADIO - TELEVISION EVERYTHING ELECTRICAL



Price 25/- Obtainable from your local dealer.

Not only radio but everything electrical can be tested with this world famous PIFCO Radiometer. Bell and telephone circuits, radio, television, vacuum cleaners, irons, car lighting, H.T. and L.T. milliamps, etc. Increasing supplies now available for the home market.




- **CIRCUIT TEST**  
Tests for open or faulty circuits in all radio and electrical apparatus and domestic appliances. Equally for testing car lighting and starting circuits.
- **L.T. TEST**  
0-6 volts AC or DC
- **MILLIAMPERE TEST**  
0/30 m.a. scale for testing total discharge from battery or testing single cell
- **VALVE TEST**  
Made by inserting valve in socket on front of meter.
- **H.T. TEST** — 0-240 volts. May be used direct on any mains, AC or DC

**PIFCO**  
ALL-IN-ONE  
**RADIOMETER**

**PIFCO LTD., PIFCO HOUSE, WATLING STREET, MANCHESTER, 4**  
and at PIFCO HOUSE, GT. EASTERN STREET, LONDON, E.C.2
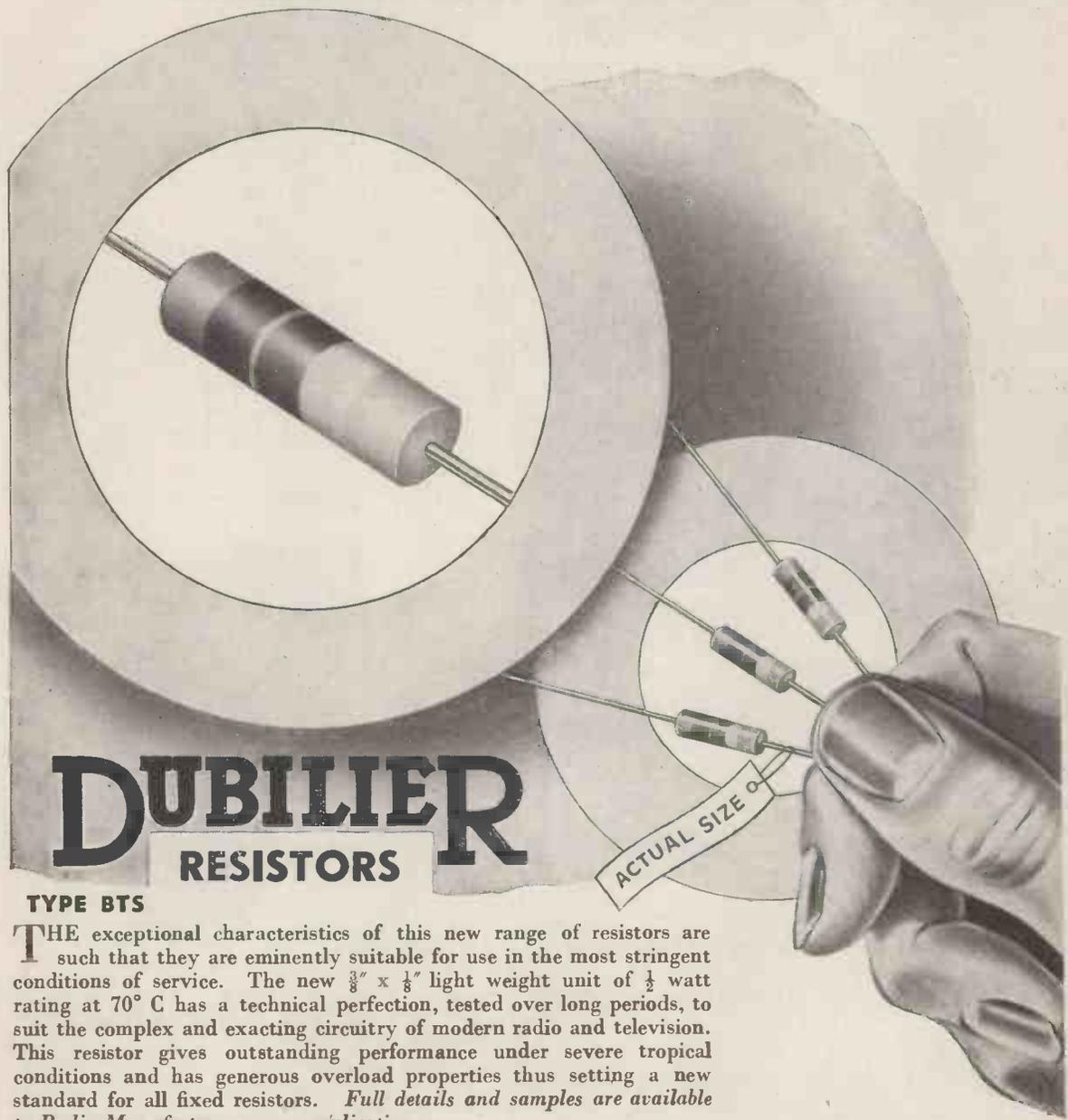
# The Latest Technical and Engineering Achievement in Resistors



## DUBILIER RESISTORS

### TYPE BTS

**T**HE exceptional characteristics of this new range of resistors are such that they are eminently suitable for use in the most stringent conditions of service. The new  $\frac{3}{8}$ " x  $\frac{1}{8}$ " light weight unit of  $\frac{1}{2}$  watt rating at 70° C has a technical perfection, tested over long periods, to suit the complex and exacting circuitry of modern radio and television. This resistor gives outstanding performance under severe tropical conditions and has generous overload properties thus setting a new standard for all fixed resistors. *Full details and samples are available to Radio Manufacturers upon application.*

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, N. ACTON, LONDON, W.3

'Phone : Acorn 2241 (5 lines)

'Grams : Hivoltcon, Wesphone, London

Cables : Hivoltcon, London.

Marconi International Code



# B.C.C.

communications  
equipment

**Speaking with confidence**

*this Officer carries the B.C.C. Hand Portable.*

*The Complete range of B.C.C. v.h.f. communications equipment consists of:-*

- FIXED STATIONS . . . MODELS L.III & H.III
- MOBILES . . . . . MODELS L.67 & H.67
- PACKSET . . . . . MODEL L.45V
- HAND PORTABLE . . . MODEL L.45 AV

*For further Particulars and full technical data write to:-*

**BRITISH COMMUNICATIONS CORPORATION LTD.**  
GORDON AVENUE, STANMORE, MIDDLESEX. Tel. GRIMSDYKE 1455



FDX.21G

The best  
**HIGH**  
and  
**LOW**



**Exide AND Drydex**

LOW TENSION ACCUMULATORS

HIGH TENSION BATTERIES

for better battery radio reception

ISSUED BY THE CHLORIDE ELECTRICAL  
STORAGE COMPANY LIMITED

**designed . . . .**

**with  
your  
specific  
needs  
in  
mind**



MODEL 1035

The Cossor general purpose Oscillograph is designed and built by electronic engineers who are themselves familiar with the every-day problems which technicians have to face. The instrument consists of a Double Beam Tube operated at 2kV., a Time Base, Y Deflection Amplifiers and Internal Power Supplies. The 90 mm. screen is flat, and traces

are presented over the full area. Signals are normally fed through the Amplifiers, and the calibrated Y-Shift controls provide a measurement of the applied voltages. The Time Base operates repetitively, or by external trigger (for single stroke operation), or at trigger pulse repetition frequency for continuous scanning. A calibrated X-Shift Control is provided for the measurement of Time.



**Model 1428  
CAMERA**

Specially developed for use with Cossor Oscillographs, it provides the simplest means of recording stationary or non-recurrent waveforms and slow transients by the moving film method on standard perforated 35 mm. film or paper. Of robust construction, it has provision for power drive by the Cossor Three-Speed Motor Attachment, Model 1429.

# COSSOR

**Double Beam**

## OSCILLOGRAPH

Further details obtainable on application to:—

**A. C. COSSOR LTD., INSTRUMENT DIVISION, Highbury, London, N.5**

CI11

# VOLTAGE REGULATED POWER SUPPLY




TYPE SRS. 150

WIDE BAND AMPLIFIERS  
VIDEO OSCILLATORS  
PULSE GENERATORS  
DISPLAY UNITS  
VALVE VOLTMETERS  
ATTENUATORS  
IGNITION DELAY METERS  
TACHOME ERS  
OCTAVE FILTERS  
LOGARITHMIC AMPLIFIERS

- D.C. OUTPUT : 0 - 500 volts at 100 m.a.
- RIPPLE VOLTAGE : 3 millivolts.
- INTERNAL RESISTANCE : 3 ohms.
- THREE VARIABLE NEGATIVE LINES :  
0 to -9v./-9v. to -100v./-85v. to -170v. stabilised.
- METER : Indicates volts and load current.
- A.C. OUTPUT : 6.3 volts at 6 amps. unregulated.

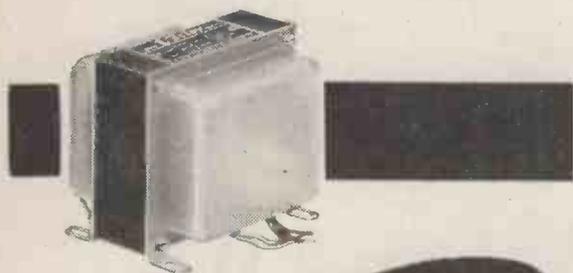**SOLARTRON LABORATORY INSTRUMENTS LTD.**  
22 HIGH STREET, KINGSTON-ON-THAMES Kingston 1787



## MAINS TRANSFORMERS & CHOKES



All "Varley" products are manufactured from the highest quality materials.

Transformers etc., are individually wound and have interleaved windings with ample insulation, ensuring freedom from breakdown.

The comprehensive range of Shielded and Open type Transformers available meets the requirements of every circuit. Write for list etc.

MADE BY

**OLIVER PELL CONTROL LTD**  
CAMBRIDGE ROW · WOOLWICH · S·E·18  
Telephone: WOOLWICH 1422



## HOME STUDY

**backs radio experience with  
sound technical knowledge**

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television include the following:

Complete Radio Engineering Radio Service Engineers  
Radio Service and Sales Advanced Short-Wave Radio  
Elementary Electronics, Radar and Radio  
Television Technology


And the following Radio Examinations:

British Institution of Radio Engineers  
P.M.G. Certificates for Wireless Operators  
City and Guilds Telecommunications  
Wireless Operators and Wireless Mechanics, R.A.F.

Write today for our FREE "Radio" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need of and the means of instruction.

*International*  
**CORRESPONDENCE SCHOOLS**

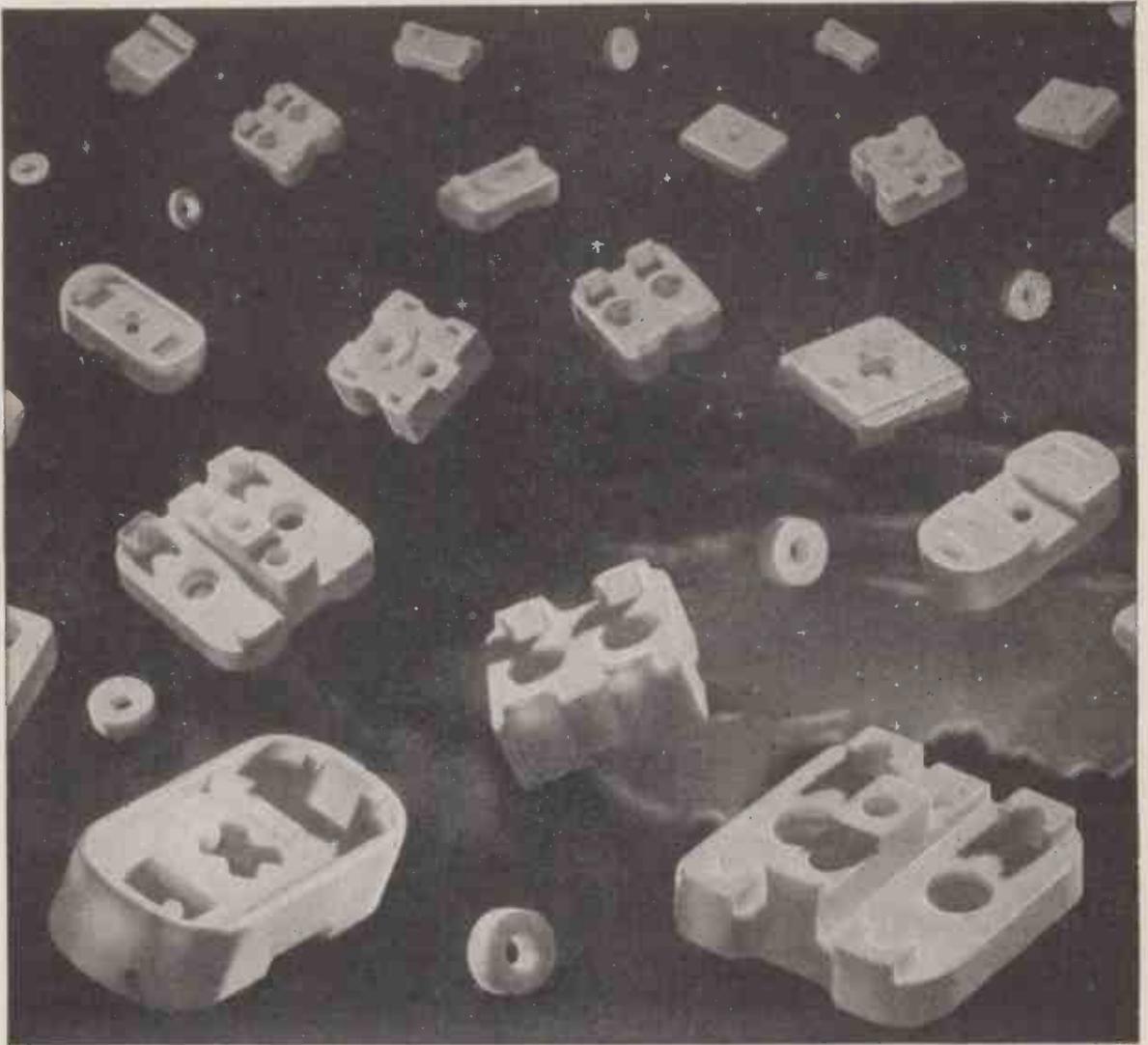Dept. W.L.6, International Buildings, Kingsway, London, W.C.2



# CERAMICS

FOR TRIMMER CONDENSERS  
and all radio components  
FREQUENTITE-FARADEx-TEMPRADEx


**STEATITE & PORCELAIN PRODUCTS LTD.**

Stourport on Severn, Worcester.

Telephone: Stourport 111.

Télegrams: Steatint, Stourport



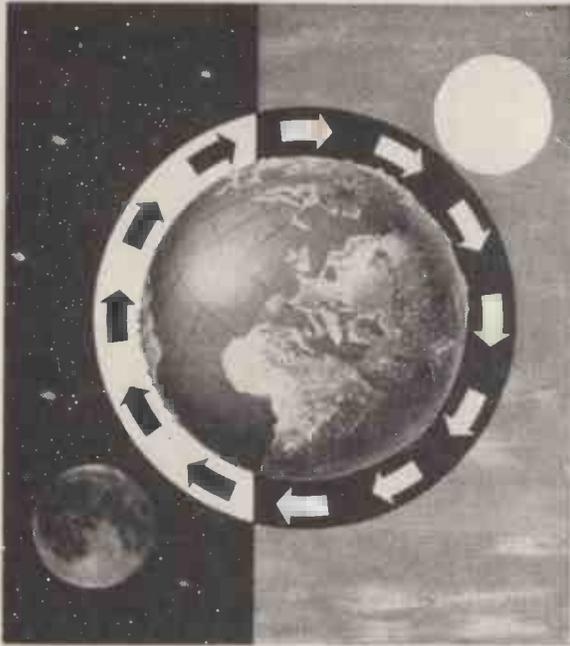

## Continuously in Service, Day and Night

Noon over Nanking. Dawn over the Atlantic. Blackness over the Andes. In all parts of the world, at all times of the day and night, Marconi built stations are in operation, broadcasting or sending telegraph messages and giving unrivalled service. Wherever ships and aircraft are plying, you will find Marconi apparatus guiding them, every hour of the day, every day of the week. Pioneers in Wireless Communication fifty years ago, Marconi's still maintain their leadership. Behind every new development there will be Marconi's accumulated experience. Behind every new piece of Marconi equipment there will be the honoured name as an assurance of maximum efficiency.

# Marconi



the greatest name in wireless

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD.,

MARCONI HOUSE, CHELMSFORD, ESSEX.

## IMPROVED D.C.-A.C. CONVERTER

BY VALRADIO

MODEL 230/110/A D.C.-A.C. CONVERTER offers a number of improvements both in design and performance. These are detailed briefly below. Full details of the whole Valradio programme gladly sent on request. Please state whether you are interested in Converters, D.C. Voltage Changers or Heavy-Duty Rectifiers.

### SPECIAL FEATURES

- Input. 180 to 270 v. D.C. Output 200-250 v. A.C. at 110 watts.
- 50 or 60 cycle models available.
- Plug-in vibrator easily replaceable.
- H.F. and L.F. smoothing.
- More compact in size.
- More easily inspected and serviced.


### VALRADIO SPECIALISE IN POWER CONVERSION

★ Valradio D.C. Voltage Changers are proving most successful. Available for operation from 6, 12, 24 or 32 v. They will deliver up to 2,000 v. D.C. and 150 watts. Details on request.

VALRADIO LTD., 57 FORTRESS ROAD, N.W.5  
GULLIVER 5165
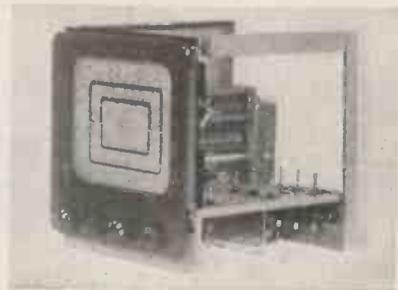
## ANOTHER WINNER BY RUCO'S

A 6-POSITION VARIABLE SELECTIVITY  
3-WAVE BAND FEEDER UNIT. R.F. STAGE.  
INFINITE IMPEDANCE DETECTION.



**DON'T DELAY!**  
*Write now for details*  
**RUCO PRODUCTS**  
**197 Lower Richmond Road**  
**RICHMOND, SURREY**

'Phone PRO. 7463.

**To the electrical and radio service engineer . . .**

**An oscilloscope in miniature . . .**

The criterion of usefulness of a cathode-ray tube as an oscilloscope is the ratio of the screen diameter to the diameter of the spot but there is a practical limit to the extent to which the screen diameter can be reduced, even though the spot size is reduced in proportion. One outstanding feature of this oscilloscope is the comparatively large screen for an instrument of such small dimensions. Although the overall dimensions of the case are  $11\frac{1}{2}$  in.  $\times$   $5\frac{3}{4}$  in.  $\times$   $4\frac{1}{4}$  in., the tube has a  $2\frac{3}{4}$  in. screen.

**The  
Miniature  
Cathode-ray  
Oscilloscope  
Type 244**



**METROPOLITAN-VICKERS ELECTRICAL CO. LTD.**  
MANCHESTER 17, ENGLAND

synonymous with  
**PLUGS & SOCKETS**

**PAINTON & CO LTD KINGSTHORPE NORTHAMPTON**

## M.R. SUPPLIES Ltd

We only offer material, whether Government surplus or commercial, in brand new and perfect condition. Our careful buying is your guarantee of satisfaction. All prices nett. Immediate delivery.

**SENSITIVE MOVING COIL RELAYS** (Elliott type H/DC) Coil resistance 1,000 ohms, operating current 238 micro-amps.—each with test report. In windowed housing 6 1/2 in. x 3 1/2 in. x 2 1/2 in. on base 9 in. x 4 1/2 in. with 2 coil and 3 switch terminals, switching 1-pole C.O. Very fine instruments, 37/6 (despatch 2/-). **MINIATURE RELAYS** (U.S.A. type No. 1604). Size approx. 1 1/2 x 1 1/2 in. Res. 60 ohms, 2-pole change-over with heavy contacts switching up to 4 amps, 7/6 each, special quote for quantities **LONDEX RELAYS**, 230 v. A.C. (or 6 volt D.C.) Coil, with 10 amp. mercury switch (either normally closed or open) mounted and housed in 6 in. x 4 1/2 in. x 2 1/2 in. cover 49/6 (despatch 1/-).

**HIGH DUTY RECTIFIER UNITS.** Operation on 200/250v., 50 cycles, D.C. output at 122 deg. F., 36 volts 56 amps. Metal rectified, fitted switch and fuses, contained in steel housing 36 in. by 20 in. by 20 in. (weight approx. 2 cwt.). These cost approx.

£75. We have 22 only at £22/10/0 each. (They must be collected and, owing to possible prior sale we suggest enquiry be made before sending). **HIGH DUTY SELENIUM RECTIFIERS** (S.T.C.). Funnel cooled, size overall 13 1/2 x 12 1/2 x 3 1/2 in. D.C. delivery 24 volts, 50 amps. (max. A.C. input 36v.). Should be used in pair for above delivery at full-wave rectification. Brand new in original cartons, 72/6 each (despatch 2/-). The list price of these is about £9 each. **HIGH DUTY H.T. SELENIUM RECTIFIERS** (S.T.C.). D.C. delivery up to 360 v. 1.2 amp. A pair in bridge will provide A.C. mains voltage conversion to D.C. at 1.2 amps, full-wave—

very useful for lab. work, 22/6 each, 39/6 pair. **RECTIFIER UNITS.** For E.H.T., H.T. and L.T. (D.C.) supply. Unit 'A' (E.H.T.) input 200/250 v. (10v. taps), 50 cycles, output fully choke/capacity smoothed, 1,200 volts D.C. 200 m/a. at 50 deg. C. ambient. In ventilated steel housing 19 x 18 x 9 in., approx weight 60 lb, £7/10/0. Unit 'B' (H.T. and L.T.). Input as above, outputs 6.3v. D.C., 13 amps, and 220 v. D.C. 110 m/a. both choke/capacity smoothed. In ventilated steel housing 19 x 18 x 12 in., approx. wt. 50 lb, £8/10/0, or the pair for £15. These are new, housing slightly soiled in perfect electrical order. Prices as ex this address.

**E.H.T. TRANSFORMERS.** Primary: 100/250v. 50 cycles (10v. taps). Secondary: 2,000-2,000 v. (4,600v. C.T.), 400 m/a. (at 50 deg. C), size 16 in. cube, enclosed with top terminal panel. Weight approx. 50 lb. £4/10/0 (despatch 7/6). **VOLTAGE CHANGING TRANSFORMERS** (Portable) 100, 110v./200v., 220v., 240v. (and vice versa) auto-wound, loading 1.25 kva., in steel cabinet 9 in. x 8 in. x 6 in., with carrying handle. Just right for mobile cine work. First class make, £4/15/0 (despatch 5/-).

**ROTARY CONVERTERS**, input 110v. D.C., output 230v. 50 cycles, 1 ph., 100 watts. New machines at under half list price, £5/17/6 (despatch 5/-).

**STAGE LIGHTING DIMMERS.** Full-bright to blackout at stated load at 220/240v. Sliding type, 100-watt 32/6, 200-watt 37/6, 500-watt 50/- (despatch 2/-). Screw motion, with handwheel, 1,000-watt £6/3/0, 1,500-watt £7/18/0, 2,500-watt £9/5/0 (despatch 5/-). All enclosed.

**F.H.P. MOTORS**, 200/250v. A.C. Brand new shaded pole type, suitable for stirrers, tape recorders, cine projectors, cooling fan extractors, fans, grammo-motors (when suitably geared), etc. 1,200 r.p.m., running torque 400 gram./cms., frame 3 1/2 x 3 1/2 in., ventilated enclosed, 28/6 (despatch 1/-).

**ELECTRIC PUMPS.** The reliable Stuart range from stock. 220/250v. A.C., direct coupled motor to centrifugal pump. No. 10 (120 g.p.h.), £5/15/0 (despatch 1/6). No. 12 (900 g.p.h.) £8/10/0 (despatch 3/6). Larger models, and piston pumps from stock. Details on request. **HIGH DUTY BRONZE PUMPS** (new, ex Admiralty), power required, 1 h.p. Vane impeller, approx. 3,000 g.p.h., £8/15/0 (despatch 4/0). Despatch cost apply to mainland only. Double for water-note areas.

**M. R. SUPPLIES Ltd., 68, New Oxford Street, London W.C.1**

Telephone MUSeum 2958

## SERVICE ENGINEERS!

Do YOU know that the  
**Guild of Radio Service Engineers**

is the accepted Organisation representing Radio and Television Service Technicians?

It is recognised by the employers' and other Trade Organisations, and by the appropriate Government Departments, as the representative body for the Service side of the Trade.

Write for full particulars to:

**THE ASSISTANT GENERAL SECRETARY**  
**88, MADEIRA ROAD**  
**HOLLAND-ON-SEA, ESSEX**



DESIGNED BY  
**SPECIALISTS**  
FOR THE  
**SPECIALIST**



**EM49A MIXER UNIT**

A very efficient four channel electronic mixer employing the latest type low noise valves. Three microphone channels and one pick-up or radio channel, each with independent fader, are provided.

*Inputs 1/2/3:* 20Ω at 70 microvolts.

*Input 4:* 50 kΩ at 300 millivolts.


*Output:* 1 volt. Imp: 5.5 kΩ.

*Noise Level:* -60 db approx. at full output.

*Response:* ±1 db 50 c/s to 20 k/c.

*Dimensions:* 5" × 14" × 9½".

*Weight:* 10 lbs.

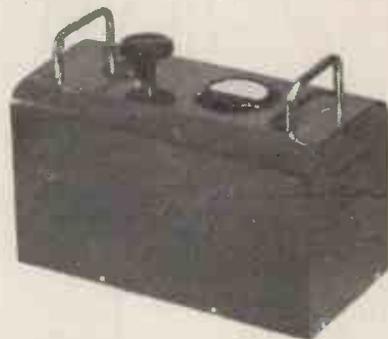

**VC12 CONVERTER**

A compact vibratory converter for battery operation of recording equipment and all applications where frequency stability is required. Housed in steel case finished in blue stove enamel and fitted with chrome carrying handles. Equipped with voltmeter and output frequency control.

*Input:* 12 volts D.C.

*Output:* 230 volts, 50 cycles.

*Rating:* 150 watts.

*Dimensions:* 13" × 6½" × 8".

*Weight:* 26 lbs.

**DR49A DISK RECORDER**

A professional disk recorder of advanced design for use with existing amplifying equipment or as a companion unit to our self-contained recorder CDR49A.

The carrying case is finished in dark blue leatherette and equipped with locks, carrying handles and detachable lid.

*Capacity and Speed:* 5" to 13" disks at 78 r.p.m.

*Drive:* 1/50 h.p. fully synchronous motor.

*Cutting Head:* Improved design 15Ω magnetic head. Response level ±2 db up to 12 k/c. Requires 4 volts input (1.05 watts) for full modulation at 1 k/c.

*Other Features:* Variable groove pitch (80/120 g.p.i.), depth of cut and stylus angle. Inside or outside start. Scrolling control with automatic closure of final groove.

*Dimensions:* 20" × 14" × 13½".

*Weight:* 40 lbs.



**SIMON SOUND SERVICE**

Recorder House, 48/50, George Street, Portman Square, London, W.1, England

Telephone: Welbeck 2371 (4 lines)

Telegrams: Simsale, Wesdo, London


Cables: Simsale, Londqn


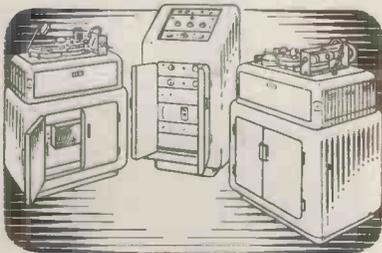
## DIRECT RECORDING ON DISK

**T**HE year 1930 marked a vital point in sound recording progress. It was then that Mr. C. E. Watts, founder of the M.S.S. Recording Co. Ltd., produced the first cellulose lacquer-coated disk—an achievement which paved the way to—indeed made possible—to-day's high-fidelity sound reproduction. That same pioneering spirit, consistently prompting every endeavour of the M.S.S. organisation, has produced a range of sound recording equipment which is acknowledged supreme wherever there is an appreciation of true fidelity in sound reproduction. Apart from its "quality" performance, every item of M.S.S. equipment—whether a complete recording channel or a cutter head—is built to a standard of technical excellence which assures long-maintained efficiency under the most exacting operating conditions. In this connection it is interesting to mention that the first disk recorder used by the B.B.C. for broadcast programmes and supplied by M.S.S. in 1933, is still in use in their training school.

*Illustrated below is a typical M.S.S. Studio Recording equipment, but the M.S.S. range includes Portable Studio Recording equipment, Portable Recorders for the professional and also home recording equipment. Full details will gladly be sent on request.*



**M.S.S. RECORDING CO., LIMITED**  
POYLE CLOSE, COLNBROOK, BUCKS  
Telephone: COLNBROOK 115

# LONDON

OR

# BIRMINGHAM!

Here is an opportunity worth grasping,  
build your own Television Receiver at  
a price you can afford.

- Designed around common types of valves.
- No unusual types to obtain.
- Will suit 9", 10" or 12" Tubes.
- The most competitive price on the market.

**CAN BE BUILT FOR £16 (C.R. Tube Extra)**

Instruction books PRICE 5/- post free.

Write today for further details.

COMPLETE RANGE OF COMPONENTS AVAILABLE

Focus Coils High Res. 17/6	Deflection Coils..... 22/6
" " Low " 17/6	Line Output Trans. 22/6
Perm. Magnet Focussing Assemblies from 21/-	
Pre-Amplifiers for London or Birmingham £7 10s.	

## HOUGHTON & OSBORNE

Electron Works, Thame, Oxon.

Telephone: Thame 182.

## HIGH FIDELITY EQUIPMENT

Available from stock

### Loudspeakers :

Wharfedale SUPER 8 C/S .....	£3 15 0
Wharfedale " Golden " .....	£3 15 0
Wharfedale " Golden " CSB .....	£4 5 0
Wharfedale W12 C/S .....	£7 5 0
Wharfedale W15 C/S .....	£11 10 0
Goodmans " Axiom 12 " .....	£8 8 0
Goodmans " Axiom 22 " .....	£12 13 0
Goodmans Bass Reflex Cabinet, MODEL G2/8 .....	£16 16 0
Barker Model 148A .....	£15 15 0
Barker Model 150 .....	£18 18 0
Barker Bass Reflex Cabinet, MODEL B/8 .....	£16 16 0
Truvox SS10A .....	£6 17 6

### Pick-ups :

Lowther moving coil, with tungsten carbide reproducing point .....	£12 19 10
Transformer for above, Type 20T .....	£1 17 6
Decca Model " D," with 8in. arm .....	£3 15 4
Decca Model " D " or " C," with 12in. arm .....	£4 6 1
Acos Model GP20 .....	£3 11 5
Connoisseur Super-Lightweight .....	£5 14 8
Connoisseur Single-Speed Motor .....	£18 19 0

Detailed component price list for the new Williamson Pre-Amplifier ("W.W.," Nov. '49) available on request.

**ROGERS DEVELOPMENTS Co.,**  
106, Heath Street, HAMPSTEAD, London, N.W.3.

HAMPstead 6901




# Important to designers of MOBILE V.H.F. TRANSMITTERS

## SWITCHED FILAMENT for BATTERY SAVING

The new Mullard directly-heated Double Tetrode, QQZ04-15, makes possible the design of compact mobile transmitters which will operate efficiently up to frequencies of 186 Mc/s. The main features of this valve are as follows:—

- No filament drain on "Stand-by"
- Small size (100 x 32 mm)
- Transmitters using QQZ04-15's in each stage give full output within 3 seconds of switching to "transmit"
- No neutralizing required.
- Good frequency multiplier.
- Sections may be used in cascade.

OPERATING CONDITIONS (INTERMITTENT USE)	
$V_f$	6.3 V
$I_f$	0.68 A
$f$	186 Mc/s
$V_a$	400 V
$I_a$	2x40 mA
* $P_{load}$	16.5 W
* For circuit efficiency = 85%	

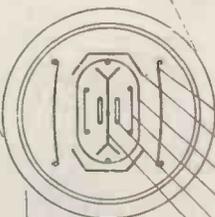

- 1 Planar Anodes
- 2 Beaming Plates
- 3 Common Screen Grid
- 4 Planar Control Grids
- 5 Filament Loop Centre Tapped
- 6 Section Separator Plate

### Mullard

#### NEWS LETTER

If you are not already on the mailing list for this service of advance information on new valves, please write to us for full particulars on your business letterheading.



# Mullard

## THERMIONIC VALVES & ELECTRON TUBES

Industrial Power Valves · Thyratrons · Industrial Rectifiers · Photocells · Flash Tubes · Accelerometers  
Cathode Ray Tubes · Stabilisers and Reference Level Tubes · Cold Cathode Tubes · Electrometers, Etc.  
Mullard Electronic Products Ltd., Century House, Shaftesbury Avenue, London, W.C.2

## A NEW INSTRUMENT FOR THE AUDIO FREQUENCY ENGINEER

For taking the response curves of amplifiers, speakers, transformers, filters and microphones, or measuring the acoustic properties of rooms, studios and radio cabinets, etc., we introduce the:

**MODEL 1900 A.F. RESPONSE CURVE TRACER.**

### FEATURES :

- Entirely electronic in operation.
- Log. frequency scale.
- Frequency range 25 cps. to 20 kcs. in two ranges.
- Accurate frequency calibration based on passive circuit elements.
- Repetition or single stroke frequency sweep.
- Remote single stroke sweep initiation.
- Sweep speed proportional to frequency.
- Approximately constant writing speed.
- Simple recording facilities.
- Built-in stabilised power supply.
- Portability.
- A practical price.

Write for specifications. Early delivery now available.

In preparation : Model 1950 Visual A.F. Wave Analyser.

# INDUSTRIAL ELECTRONICS,

## 99 Gray's Inn Road, London, W.C.1

Telephone : Holborn 9873/4

## DIRECT CURRENT TO RADIO FREQUENCY

The only oscilloscope combining

- Linear Response from Zero Frequency (DC) to Radio Frequency (0-100 k/c.).
- High Deflection Sensitivity on both axes (70 mV. cm.).
- Complete freedom from amplifier drift under D.C. conditions.
- Absolute independence of controls.
- Perfect synchronising at all Frequencies.
- True portability (weight only 18 lbs.).
- Price £32.
- Six months' guarantee.

Model 1400B Visual Alignment Signal Generator shows the shape and characteristics of a tuned circuit response curve on the oscilloscope screen. Perfect alignment of I.F. or R.F. circuits is easily accomplished without an additional signal generator. Price £8 10s.



Stop worrying about that metal work problem—there's always Ritherdon's!

This old established firm make Instrument Cases, Amplifier Racks, Fuse Boxes, Busbar Chambers, etc. to customers' specifications.

Experience has taught them that it costs no more to work to individual requirements than to produce standard lines. Bring that problem to Ritherdon's, all enquiries are welcome and will receive prompt attention.

## RITHERDON & CO LTD

LORNE STREET, DARWEN, LANCs. Phone: Darwen 1028

Specialists in fine sheet metal work since 1895.

## DRAYTON MOTOR UNITS



### R. Q. G. GEARLESS MOTOR UNIT

A miniature capacitor induction type motor running at 2,700 r.p.m. Normally supplied with built-in fan, condenser mounted on fan cover. Motor can be supplied totally enclosed, condenser separately mounted. For continuous or intermittent running in either direction or continuously reversed. Torque: 1.75" oz.

### R. Q. R. GEARED MOTOR UNIT

The R.Q.R. is a compact, self-contained component, consisting of the R.Q.G. motor geared to a final shaft. Supplied for continuous or intermittent running in either direction, with or without self-switching. An additional two-way switch is fitted, actuated by the final shaft, for operating auxiliary gear. Final shaft speed: 27m.p.r. to 600r.p.m. Torque 60" lbs. to 1/4" lbs. according to speed.



Supplied for Voltages 100/120 or 200/250 A.C. 50 cycles.

Send for List No. N 302-1

R. Q. B

DRAYTON REGULATOR & INSTRUMENT CO. LTD.,  
WEST DRAYTON • MIDDLESEX. West Drayton 2611

# LONDON CENTRAL RADIO STORES

Government Surplus - Immediate Delivery from Stock


## PHILIPS 6-VALVE COMMUNICATIONS RECEIVER



16-50, 200-500 and 800-2,500 metres. R/F, F/C, 2 I.F.s. D.D.T. Pentode Output. Spin-wheel tuning. In black metal case with built-in speaker. Complete with power pack, AC 200-250 v. Can also be supplied with 12 v. D.C. power pack if required. BRAND NEW—EX-GOVT. **£17.10.0**
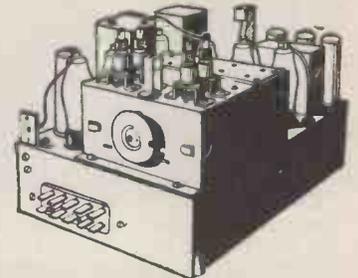
## R.A.F. 6-VALVE SUPERHET RECEIVER UNIT No. 25


All valves guaranteed. This unit is easily adapted to Short-wave reception for home use. In addition to two EF36, two EF39, one EK32 and one EBC33 valves, it contains 1 pr. 400 Kc/s iron dust I.F. Transformers, Mic. and phone output transformers, a number of resistances and fixed condensers of useful values, two 1 mfd. 500 v. wkg. and four .1 tubular condensers, pot/meters, Int. Octal Valve holders, Tuning Coil, etc., mounted on steel chassis 8½ x 6½ x 2½ in. FREE circuit diagram 9 in. x 19 in. showing all components, supplied with each set.



In new condition.


**22/6**

## EX-R.A.F. TUNING UNIT TYPE 207A

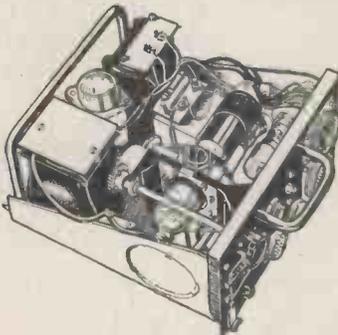

BRAND NEW. Includes Clystron valve, 3 Neon tubes CV71, 1 6Z4G and other useful components. As illustrated, plus metal cover. **21/6**


## G.E.C. ELECTRIC TORCH

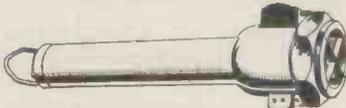

Aluminium body 10½" long. Powerful beam. Adjustable for spot or flood. Takes three U2 cells. Complete with 3.5 volt bulb, but less batteries. **25/-**

4 MFD. CONDENSERS 2,000 v. D.C. .... 4/6

NEW MILNE'S H.T. UNITS (Everlasting)

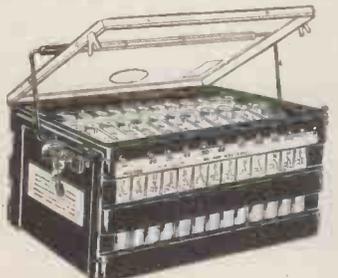

120 v. 600 mA. Will charge from 6 v. accumulator. Callers only ..... **67/6**

HEADPHONES. Low resistance with headbands, new, 4/6 pair. New American midget Reel type, 90 ohms, no headbands, 3/9 pair. American lightweight. Suitable for deaf aid, 7/6 pair.

BLOWER MOTORS. 12-24 v. 17/6, 80 v. 15/-.

2-VOLT VIBRATORS. 50/- rectifying. Output 200 v. at 80 mA., 7/6.

VIBRATOR PACK. Admiralty pattern, 12 v. D.C., 300 v., 100 mA. output, 30/-.

POWER UNIT, Type 280. Contains four VU133, one 5U4, one VR65 valves, 22/6.

VISION UNIT, Type 182. Complete with 6in. 517 OR. Tube, 2in. 139 C.H. Tube, one 807, three VR65, one 6J3 valves. 0.5 millimeter, condensers, etc. Suitable for Television, 55/-.

1/30th H.P. MOTORS. Constant speed. Double-ended spindles. 220-250 v. These motors are new, not surplus conversions and are suitable for 16 mm. projectors and many other purposes. AC/DC, with feet, 42/6. AC, without feet, 35/-.

MOVING COIL HAND MICROPHONE. Complete, 5/6.

INSERTS, as above, 2/6.

7-VALVE V.H.F. RECEIVER, Type B1147A. Range approx. 200 megacycles (with 4 Acorn valves). A Real Opportunity. Beautifully constructed and fitted with micro-condenser drive. Valve types: two EF36, one EBC33, three 954 one 955. In black metal case, 8 x 7 x 6in. Set complete with valves, 30/-.

EX-ARMY TEST SET NEW, Type Demolition Mk. 1. For circuit continuity and general testing. In hardwood carrying case, 42/-.

FIVE-WAY RUBBER COVERED CABLE. Suitable for lighting and other purposes. Per doz. yds., 8/-.

EX-GOVT. 100ft. COPPER AERIALS, ebonite chain Insulators, 30ft. guy rope, 4/3.


EX-R.A.F. CAMERA MOTORS. Dimensions 3in. x 2in. x 1½in. 24 v. AC/DC. 8/8.

NEW LATEST PLASTIC COVERED WIRE. Red or Black, by Armaduct. 100 yard coil, 6/6.

20-VALVE RECEIVER Type No. 3515. Includes 13 Mc. strip suitable for Television sound or vision when used in conjunction with R.F. unit Type 25. Contains the following valves: 10 SP61, 5 EF36, 3 EBC33, 1 EB34, 1 Mazda A832, relays, condensers, resistances, etc. Brand new in metal case and supplied in wood transit case, 55/-.

## WESTERN BALL MICROPHONE

Manufactured by Standard Electric.

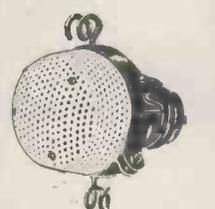

Suitable for broadcasting and recording. Moving Coil (Dynamic). Omnidirectional.

No energising necessary. High Fidelity. Coil impedance 15 ohm. and will work very well in conjunction with an ordinary speaker transformer.


Is of the type used by many leading bodies, such as the B.B.C. and G.P.O. for high fidelity **£4.17.6** reproduction.

PHOTO-ELECTRIC CELLS. Type G516. These cells are the gas-filled type with caesium Cathode. Made by Cintel. Minimum sensitivity 100µA/lumen, working volts 100 D.C. or peak A.C. Projected cathode area 16 sq. cm. Suitable for 16 mm. Home Cinema Talkie equipment, Safety Devices, Colour and Photo Matching, Burglar Alarms, Automatic Counting, Door Opening, etc. Brand new in original cartons. 42/6.

## PLEASE NOTE

● All carriage paid unless otherwise stated. ● Carriage charges relate to British Isles only. ● We do not issue lists or catalogues. ● We have hundreds of items in stock too numerous to list, including Special Admiralty Transmitters, Receivers, etc., so when in Town pay us a visit.

## TYPE 73A VISUAL UNITS.

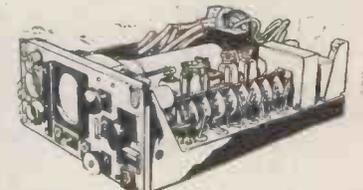

With 4in. Cathode Ray Tube, VCR138A, 4 SP61, 1 EB34 valves, potentiometers, etc. Complete on chassis, 16 x 12 x 5½ in. **35/-**

12in. C.R. TUBES VCR140. Blue Screen, 90/-.

NEW VCR97 CATHODE RAY TUBES, 37/6.

R.C.A. CINEMA SPEAKERS. 110 v. Complete with wood horns. 2ft flare. For CALLERS ONLY. **£5.10.0**

EX-R.A.F. TUBULAR CONDENSERS. .02 mfd. 8 Kv. D.C. working, 6½ in., 4/-.

## FRACTIONAL H.P. A.C. MOTORS

Converted from ex-Govt. Generators



Brush type 220-250 v. 50 cycles approx. 5,000 r.p.m. Overall diam. 10 x 4in. ½ in. spindle extends 1in. both ends. **21/-**

## EX-R.A.F. TEST SET TYPE 202.

7 EF50, 2 VR116, 1 5Z4G, 2 VR54 valves, electrolytic condensers, transformer, potentiometers, resistances and condensers. **60/-**

## TELEPHONE LINE OR UNI-SELECTOR SWITCHES

As new, 6-bank ..... **37/6**



BRAND NEW ACCUMULATORS. 6 v., 85 a. Size 12 x 9 x 7in. Weight 45 lbs. British made. **£3.10.0**

# LONDON CENTRAL RADIO STORES, 23, LISLE ST. (GERrard 2969) LONDON, W.C.2.

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.



# NEW STANDARDS IN STABILISED POWER




Ripple: <math>< 1\text{mV}</math> Peak  
 Reg : 0.04%  
 Imp. DC : 0.15Ω  
 Weekly : 0.2V  
 200 - 360 V } A  
 150 mA }  
 200 - 360 V } B  
 75 mA }  
 150 V. Neg.  
 6.3 V. 8 Amp  
 4.0 V. 8 Amp

Two separate Regulated Power Supplies provide easy testing of multiple units without Decoupling. All D.C. Points metered Current and Voltage
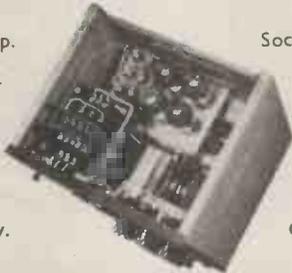
## WITH SUPERB

Sliding Top.  
 Sliding Bottom.  
 Easy access  
 to Check  
 Points. Tag  
 Strip Assembly.



Socket and Spade  
 outputs. HS  
 Resistors.  
 WW Resis-  
 tors. Oil filled  
 Condensers.

## MECHANICAL CONSTRUCTION

AVAILABLE IN FOUR DIFFERENT RATINGS

Rating	Reg. %	Ripple PEAK	D.C. Imp. Ω	Stab. Week.
A	0.75	3.0mV	4.0	± 1V.
B	0.20	1.0mV	0.8	0.25V
C	0.04	0.5mV	0.15	0.2V
D	0.003	0.4mV	0.15	0.1V

Neon Stabilized

### Type 120

200-360V. 150mA. Reg.  
 Neg. 150V. 2mA. Reg.  
 450V 150mA not Reg.  
 6.3V. 6A.  
 4.0V. 6A.




100 Volts to 5,000 Volts. Write for Details

## EX-STOCK OR DESIGNED ESPECIALLY



7 CHILTERN STREET, W.1. Tels. Welbeck 6029, 5809

# A Pre-Fab Cabinet Widney

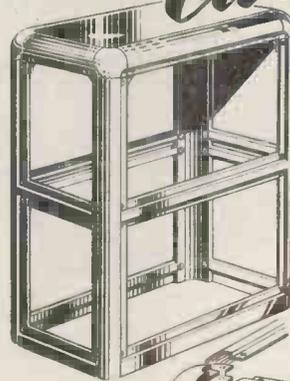

- **DORLEC**  
REGD

## CABINET SYSTEM

providing an easily constructed cabinet for manufacturers and laboratories. The range of extruded sections, corners and brackets now available enables a housing for individual designs to be easily erected.

Technical & Sales Agent

**G. H. DAVIS**  
59, BROMPTON RD.  
LONDON, S.W.3

Write for illustrated leaflet.



MANUFACTURERS

HALLAM, SLEIGH & CHESTON LTD  
WIDNEY WORKS • BIRMINGHAM • 4

ESTABLISHED 1898

Phone: Alton Cross 0914 (4 lines) • Grams: Superfine, Birmingham 4

# WEYRAD

Components for all users. If you are interested in these or any other items please write for further details.

**BANDSPREAD UNITS**—Ranges to suit all requirements—9 Wavebands—with or without R.F. stage.

**TUNING SCALES NOW AVAILABLE.** Size 9in. x 9in.

**COIL PACKS**—3 and 4 Waveband with R.F. stage. 3-Wave packs—Special versions for battery operation.

**COILS**—12.5 to 2,000 Metres. Air cored, Iron cored midget and Screened types available.

**I.F. TRANSFORMERS**—Minlature, Midget and Standard types, all of high performance.



**FILTERS, CHOKES AND SPECIAL COILS** to order. We are coil winding and assembly Contractors to well known manufacturers at home and overseas. Your enquiries, large or small, are invited.

**WEYMOUTH RADIO MANUFACTURING CO., LTD.,**

**CRESCENT STREET, WEYMOUTH**

**VALVES FOR TELEVISION RECEIVERS**

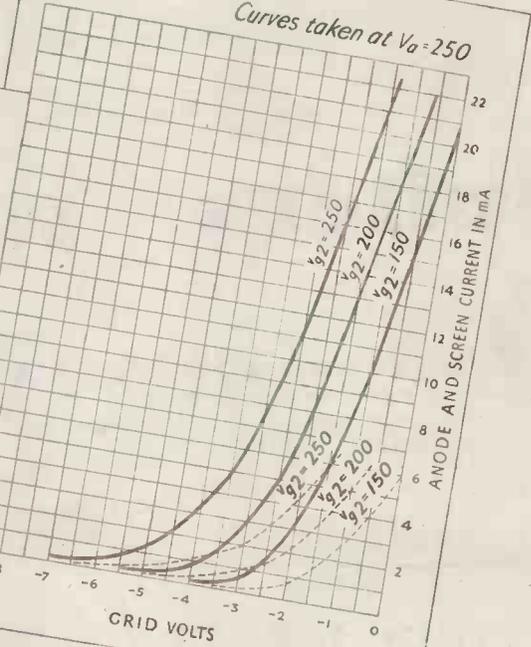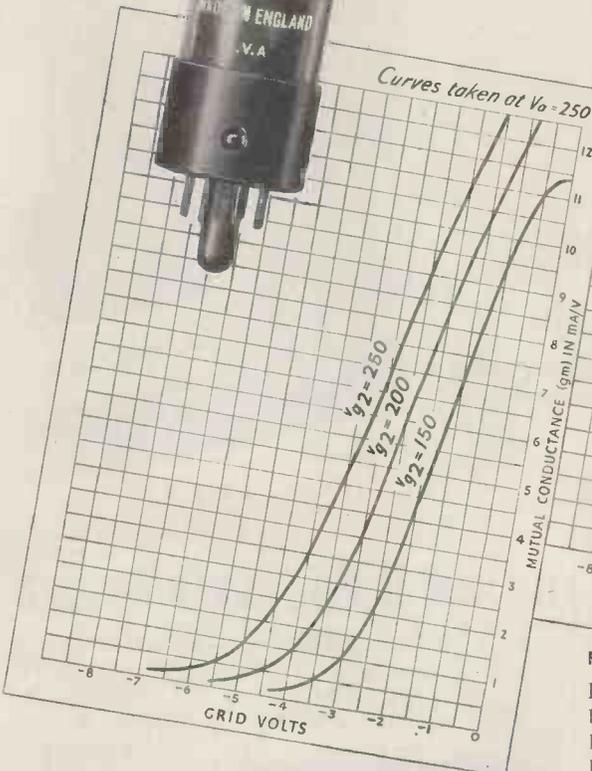**6F13 HIGH SLOPE SCREENED R.F. PENTODE**



The Mazda 6F13 is a High Slope Screened R.F. Pentode suitable for use in R.F., I.F., and Video stages of a Television Receiver. It may also be used as a Mixer in a two-valve Frequency Changer Circuit.

**LIST PRICE 15/6**

**RATING**

Heater Voltage (volts)	$V_h$	6.3
Heater Current (amps)	$I_h$	0.35
Maximum Anode Voltage (volts)	$V_a$	250
Maximum Screen Voltage (volts)	$V_{g2}$	250
Mutual Conductance (mA V)	$g_m$	*9.0
Maximum Anode Dissipation (Watts)	$P_a$	† 3.5
Maximum Screen Dissipation (Watts)	$P_{g2}$	† 1.0
Maximum Potential Heater/Cathode (volts DC)	$V_{h-k(max)}$	150

\*Taken at  $V_a = V_{g2} = 200v$ ;  $V_{g1} = -1.8v$ .  
 †With grid cathode resistance not exceeding 10,000 ohms.

Further details will be supplied on application to the Radio Division.

**EDISWAN  
MAZDA**

**RADIO VALVES AND TELEVISION TUBES**

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2

*The better they are made  
the more outstanding the results*

**MADE IN THREE PRINCIPAL MATERIALS.**

**FREQUELEX.** An insulating material of low Dielectric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

**PERMALEX.** A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

**TEMPLEX.** A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.


# Bullers



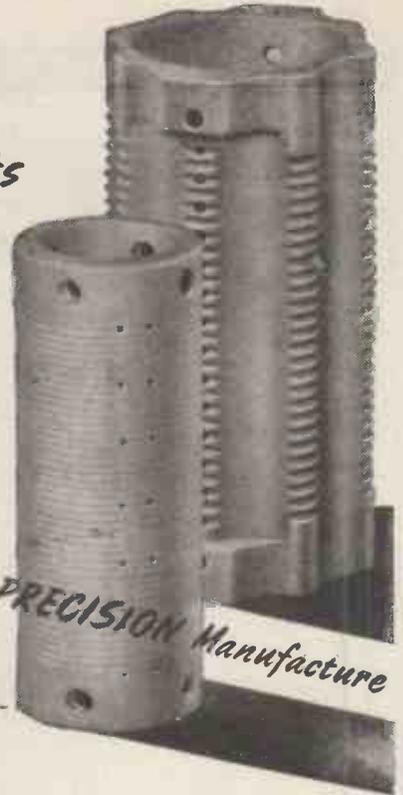**BULLERS LOW LOSS CERAMICS**

*Specialize in PRECISION Manufacture*

BULLERS LTD., 6, Laurence Pountney Hill, London, E.C.4. Phone: Mansion House 9971 (3 lines)  
Telegrams: "Bullers, Cannon, London."



## THE "VIEW MASTER"

Easy to build television receiver.

All specified components can be supplied from stock including:—

**Chassis drilled,  
Cathode Ray Tubes,  
Cabinet,  
Valves,  
Permanent Magnet focusing unit,  
Scanning coils,  
Line Output transformers,  
Resistors, condenser, etc.**

Complete book of instructions with seven easy to follow diagrams of wiring point to point and component layout, together with chassis drilling template.

Complete including postage, 5/6.

Approximate total cost of everything including Cabinet and Cathode Ray tube, £46 15s. 0d.

Send for complete component price list.

Shop hours: Monday-Saturday, 9-6 p.m. Thursday, 9-1 p.m.

## TELE-RADIO (1943) LTD.

177, EDGWARE RD., LONDON, W.2

Phone: AMB 5393. PAD 6116. PAD 5606.

## THE NEW B.P.L. SUPER RANGER

20,000 OHMS PER VOLT.



**D.C. VOLTS :**  
100 mV to 5 kV

**D.C. CURRENT :**  
1  $\mu$ A to 1 Amp.

**A.C. VOLTS :**  
0.5V to 5 kV.

**A.C. CURRENT :**  
10 mA to 10 Amps

**RESISTANCE :**  
1 ohm to 2 meg-ohms

**OUTPUT :**  
0 to 62 db

**METER :**  
5-inch Long arc, fitted with knife-edge pointer and mirror scale.

**LIST PRICE :**  
£ 21 - 10 - 0.

**BRITISH PHYSICAL LABORATORIES**

HOUSEBOAT WORKS, RADLETT, HERTS.

Tel: Radlett 5674-5-6



# The longest Journey...

## begins with one step

'CINTEL' guarantees a step in the right direction where electronics are concerned. We illustrate three typical 'CINTEL' instruments from our wide range for the modern laboratory. Please write for further particulars.



'CINTEL' MICROSECOND COUNTER CHRONOMETER



'CINTEL' R.C. OSCILLATOR & AUTOMATIC FREQUENCY MONITOR



'CINTEL' MUTUAL & SELF INDUCTANCE BRIDGE

## CINEMA - TELEVISION LIMITED

FOREMOST IN THE MANUFACTURE OF

- Counters & Chronometers ● Metal Detectors ● Oscilloscopes ● Photo-Electric Cells
- Cathode Ray Tubes ● Geiger-Muller Tubes ● Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S-E.26

Telephone: Hither Green 4600

Northern Agents:  
F. C. ROBINSON & PARTNERS LIMITED  
308 Deansgate, Manchester 3

Scottish Agents:  
ATKINS, ROBERTSON & WHITEFORD LIMITED  
100 Torrisdale Street, Glasgow, S.2



REGISTERED TRADE MARK

# Measurement by Mullard



Mullard Oscillograph type E.800, 1

The name of Mullard has for long been connected with cathode ray oscillographs, and their experience in this field is unequalled. Mullard cathode ray tubes, Mullard valves and Mullard circuitry have been combined to produce the accepted standard oscillograph.

## Type E.800/1

Time base frequency 0.25—16,000 c/s.  
 Amplifier response (2 dB loss) 0.1—40,000 c/s.  
 Amplifier sensitivity (Max. Gain) 1 mV.rms/cm.  
 Delivery—Ex stock.

## Type E.805

Time base frequency 5 c/s—150 Kc/s.  
 Amplifier response (3 dB loss) 2 c/s—2 Mc/s.  
 Amplifier sensitivity (Max. Gain) 5 mV. rms/cm.  
 Delivery—Ex stock.



# Mullard

## Electronic Products Ltd.

Electronic Equipment Division

ABOYNE WORKS, ABOYNE ROAD, LONDON, S.W.17.

(MI.276)

# Stars for Sale!

## TELEVISION COMPONENTS FROM STOCK

"VIEWMASTER" Whiteley chassis kit and brackets, 50/-. Plesey frame transformer, 18/6. line do., 21/3. Width control, 8/9. Focus magnet, 19/6. Scan coils, 25/6. Boost choke, 5/-. CRT supports, 14/-. Whiteley heater transformer, 35/-. Choke, 12/6. Stentorian speaker, 27/6. Westinghouse rectifier kit, 62/6. Bulgin kit of tags, etc., 12/6. G.E.C. neon lamp, 2/9. Billing Lee mains connector, 7/6. Set of Wearite coils and RFC, 22/-. Colvern control kit, 19/3. Morgan resistors "T" 20%, 41d.; "T" 10%, 6d.; "R" 20%, 6d.; "R" 10%, 9d.; "Q" pots 100K or 250K, 4/6. Full range of TCC "Metal-milts." ceramics, electrolytics, etc., at list prices or the complete kit at £6/15/-. Instruction book and wiring diagrams, 5/-.  
 "WIRELESS WORLD" B.T.H. crystal diodes CG1/C, 11/3. S.T.C. H4/200 H.V. rectifiers, 28/-. Reliance T.W. pots, 1k, 2k, 10k, 5/7. Do. 50 pots, 150k, 2 mec., 6/10. Publier mica's .001/5 kV, 5/-, .002/5 kV, 6/-. B.I. 32/500 v. electrolytics, 7/6. Coils, London or Birmingham, 52/8 set. Line OPT, 70/-. Mounted focus and scan assembly, 126/-. Blocking Osc. transformer, 15/-. Edystone 23-25 pF. condenser, 7/6. T.O.C. mica .001 CM20, 1/9. .01/500 v. tubular 543, 11d.

18 9. Time base chassis with v/holders, 17/6. Power pack chassis with v/holders and sockets, 25/-. Set of gantries, 9/-. Varley EHT transformer 4 kV., 67/6. do. 5 kV., 72/6. Woden potted mains trans. PTM31, 98/6. Varley chokes 5 H 250 mA., 18/6. 10 H 80 mA., 17/-. Also full range of resistors and condensers. Handbook (London), 2/6. wiring diagram, 2/6. Midland Handbook, complete with diagram, 4/6.

"DENCO" Scanning coil assembly, 30/-. Screened line OPT, 27/-. Combined line OPT and EHT unit with 2 EY51 valves and smoothing, 79/6 + P.T. 6/6. Focus coils, 5,000 or 130 ohms, 25/-. Television kits:—R.F. chassis kit with all parts, valves and 9in. C.R.T., £18/11/7. Time base and E.H.T. chassis kit with all parts and valves, £16/4/3. Power unit kit for above, 310 v. 220 mA., 6.3 v. 6.5 a., £6/10/9. All above parts are standard and interchangeable with current DENCO T.V. receivers. Completely wired 9-in. or 12-in. receivers can be supplied for building into your own cabinet. Constructional data, 5/-. Limited supplies of console T.V. cabinets are available for callers only, but please write first.



# "STEWART"

## HIGH GRADE TRANSFORMERS

Types Available for Delivery ex Stock

ANY OTHER SPECIFICATION TO ORDER

Primaries tapped 210-230-250v.

Type No.	Secondaries	Price
X2	260-0-260v 65 m/a 6.3v 2a 5v 2a	27/6d.
A6	350-0-350v 75 m/a 6.3v 3a 5v 2a	28/6d.
A4	or 4v 4a 4v 2a	
B6	350-0-350v 100 m/a 6.3v 3a 5v 2a	34/6d.
B4	or 4v 5a 4v 2a	
C6	350-0-350v 150 m/a 6.3v 4a 5v 3a	46/6d.
C4	or 4v 6a 4v 2.5a	
S/28/1**	425-0-425v 200 m/a 6.3v 4a 5v 3a 6.3v 2a	70/-d.
S/28/2*	350-0-350v 250 m/a 6.3v 6a 0-4-5v 3a 0-2-6.3v 2a 4.0v 8a	90/-d.
S/28/3	350-0-350v 250 m/a 6.3v 7a 0-2-6.3v 2a 5.0v 2a	82/6d.
S/24/1	1000v 10 m/a	40/-d.
S/24/2	1750v 10 m/a	
S/24/3	2500v 10 m/a	
S/24/4*	4000v 5 m/a	63/-d.
S/24/5*	5000v 5 m/a	
		75/-d.


\* For "Electronic Eng." Telesvisor.  
 \*\* For The "Williamson" Amplifier.

## STEWART TRANSFORMERS Ltd.

1021 FINCHLEY RD., LONDON, N.W.11

Tel.: SPeedwell 3000 and 3533

# Neostron COLD CATHODE TETRODES

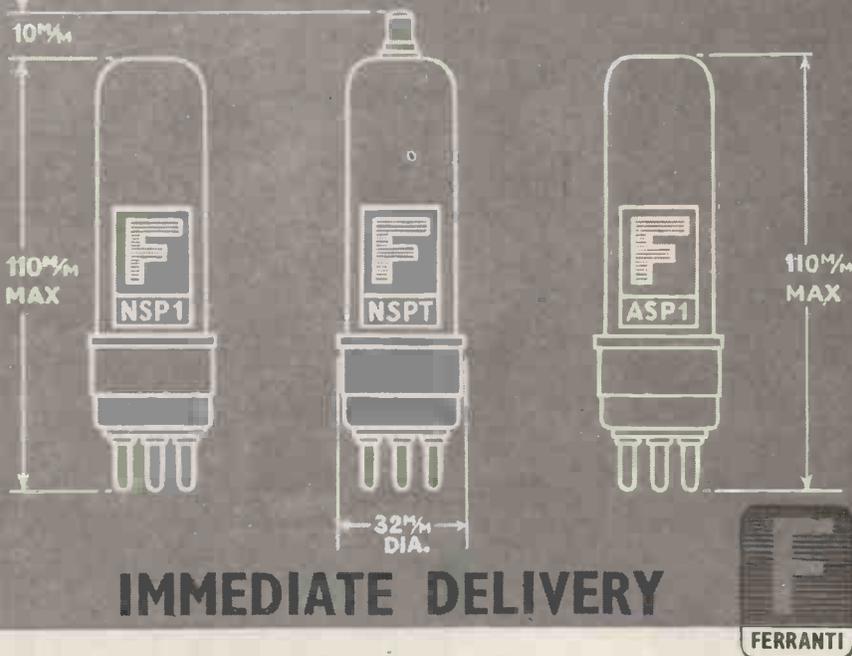

**IMMEDIATE DELIVERY**

**FERRANTI**

The Ferranti Neostron is a cold cathode tetrode filled with neon, designed for use as a stroboscopic light source, a flashing indicator, or an electronic relay.


The discharge in the anode is started by initiating a glow discharge between the screen and grid electrodes, the screen being at a fixed positive bias, a negative impulse being applied to the grid.

Operating Characteristics	NSP1	NSPT	ASP1
Max. Anode Voltage	400	650	400
Normal Anode Voltage	300	600	300
Mean Anode Current	40-100* mA	40-100* mA	40-100* mA
Peak Anode Current	250 Amps.	250 Amps.	250 Amps.
Max. Operating Frequency	250 c.p.s.	250 c.p.s.	300 c.p.s.
Anode Connection	in base	Top cap	in base
Gas Filling	Neon	Neon	Argon

\*Dependent upon frequency of operation

All types can be supplied with English 4 pin or American 4 pin bases.

**FERRANTI LTD** ELECTRONICS DEPT. MOSTON MANCHESTER 10

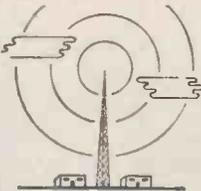★ *The Basis of*  *World Standards*


# TELCON R.F. CABLES

Technical excellence supported by constant research and an unrivalled knowledge and experience of Radio Frequency Cable applications, ensures the continuance of the lead established by TELCON in this field.

Even before the introduction of Telcothene\* as a cable dielectric, an application pioneered by TELCON, a range of Radio Frequency cables with unique capacity and attenuation characteristics was produced, using Telconax.

Today, developments are still going on and the solution of any problems involving the application of Radio Frequency cables will be found in the wide range manufactured by TELCON.

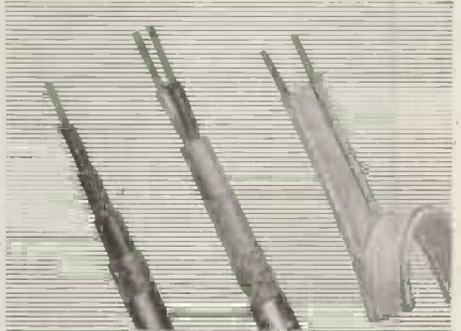★ *Telcothene (Regd.)—Polythene processed by Telcon to provide specific characteristics*



Ask also for details of  
**TELCON METALS**

**THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD**   
Head Office : 22, Old Broad Street, London, E.C.2. Tel : LONdon Wall 3141  
Enquiries to : Telcon Works, Greenwich, S.E.10. Tel : GREenwich 3291

FOR QUICK DELIVERY  
AT  
REASONABLE PRICES  
OF  
RADIO & ELECTRONIC PRODUCTS  
(Wholesale Only)

Write or phone:—

*S. Szymanski*  
(pronounced SHE-MAN-SKEE)

ELECTRONIC ENGINEER & STOCKIST  
95 STRODES CRESCENT  
STAINES, MIDDLESEX

Staines 3971

VALVES are our speciality—Probably the  
Largest Actual Stockist in England

EXPORT ENQUIRIES WELCOMED

The Revolutionary  
**GOLDRING**  
*Headmaster*  
HYPERFIDELITY  
**PICK-UP**



With an interchangeable Pick-Up Head for every type of record.

Supplied In attractive Display Carton complete with Goldring Tonaliser and Transformer

★

Goldring Products include:  
PICK-UPS, PICK-UP HEADS,  
SAPPHIRE JEWEL POINT  
NEEDLES, AND RADIOGRAM  
ACCESSORIES.

Write for full Descriptive Lists and Technical Information

**ERWIN SCHARF**  
49-51a DE BEAUVIOR ROAD, LONDON, N.1  
Telephone: CLISSOLD 3434



## Video Oscillator

Type. O.221 7 Kc/s - 8 Mc/s

Amplitude range of adjustment +10db to -55db on 1 volt peak to peak, adjustable -0.5db steps. Amplitude constant to  $\pm 0.5$ db at any frequency setting. Harmonic content better than 40 db below fundamental - output impedance 75 ohms  $\pm 5\%$ .

The instrument is built to meet a specification of the Design Department of the B.B.C. It can be mounted to a standard G.P.O. 19" rack or alternatively is supplied with a light transportable case as illustrated.

Wayne Kerr



THE WAYNE KERR LABORATORIES LIMITED  
NEW MALDEN, SURREY, PHONE: MALDEN 2202

*You simply must make a*

# WIRE OR TAPE RECORDER!

With very simple mechanism and your own amplifier you can record and playback speeches, radio programmes and family gatherings, or copy your friends' best records. Play them back time and time again, and then finally obliterate them and make a new recording using the same wire or tape.

We can supply all the necessary parts (including amplifier parts) from stock. The recorder need not cost more than about £16 with amplifier, or £20 for a super job using precision parts. Plenty of wire and tape in stock.

Send 5/- now for the complete Constructional Data, including price list of the necessary components.

**PARK RADIO of MANOR PARK**

(A division of Judge Industries)

676/8 ROMFORD ROAD, E.12

**NEW**

**SERIES 800 ELLIPTICAL**

(Type 874)

CAN 4=8? Of course it can't. And a 4" speaker can no more equal the performance of an 8" than a quart can come out of a pint pot. BUT that is no reason why a 4" speaker cannot be a really good 4" speaker. Precision in machining, exactness of assembly and, of course, CO-AXIAL ALIGNMENT of all component parts is just as important as in any other of our speakers.

Dimensions and Data  
 Horizontal 7.1" (18 cm.)  
 Vertical 4.1" (10.3 cm.)  
 Axial 2.4" (6 cm.)  
 Flux Density 8,000 or 9,000 Gauss

We are really pleased with our 4" x 7" Elliptical. So will you be when you hear it.

**REPRODUCERS AND AMPLIFIERS LIMITED**  
**FREDERICK STREET WOLVERHAMPTON ENGLAND**

Telephone : Wolverhampton 2241  
 Telegrams : "Audio, Wolverhampton."



**ETA TOOL CO**

MANUFACTURERS OF

**COIL WINDING MACHINES FOR LAYER & WEAVE WOUND COILS**

**MACHINES & EQUIPMENT TO CUSTOMERS' SPECIFICATIONS**

Machines supplied complete with cabinet stand etc.

**SOLE AGENTS ABROAD**

K. G. Khosla & Co., 22, School Lane, New Delhi, India.

Etabils Octavo Houart, 14, Quai de L'Industrie, Sclessin-lez-Liege.

J. P. Fielding Co. (Canada), 2, Gould Street, Toronto, 2, Ontario.

Hefye & Frogg, Oslo, Norway, Storgaten, 15.

**ETA TOOL CO (LEICESTER) LTD**  
**29a WELFORD ROAD, LEICESTER**  
 PHONE 5386

*Size counts!*



**THE SMALLEST SILVERED MICA CAPACITOR**



Our type 10B capacitors are now extensively used as a standard component for low capacitance values. Their small size offers the advantage of low stray capacitance and also allows a better spacing from coil assemblies where a high Q value must be maintained.


**STABILITY RADIO COMPONENTS LTD**

**14, NORMAN'S BUILDINGS CENTRAL STREET, LONDON, E.C.1.**


Telephone : CLErkenwell 5977,8



## SO SMALL— IT DOES A BIG JOB

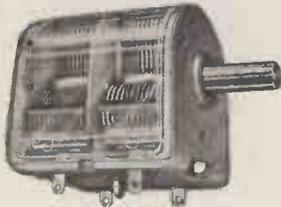

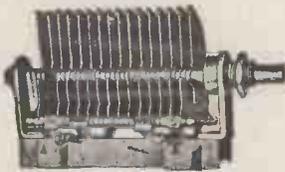Miniature in size, but big in performance. The *M.M. 2 Gang Condenser* has frame dimensions of only  $1\frac{1}{8}'' \times 1\frac{3}{8}'' \times 1\frac{1}{8}''$ . Complete with dust cover. Cat. No. 4702. PRICE 10/6



**TYPE 604** (illustrated) is a low-loss shortwave condenser suitable for Chassis or one-hole fixing. Brass vanes are soldered to supports and electroplated.

**TYPE 603** is a split stator condenser of similar construction. The S.1 series in both types are particularly suitable for low power transmitters.

PRICES: Type 604 15/3—17/0  
Type 603 16/0—17/6

PRECISION COMPONENTS BY

# JACKSON

BROS (LONDON) LIMITED  
KINGSWAY · WADDON · SURREY  
Tel: Croydon 2754-5 Grams: Walfilco, Souphone, London

## A NEW

# FIELDEN TECHNIQUE

*in micro - measurement  
and control*

FOR ANY INDUSTRIAL OR RESEARCH  
PROBLEM RESOLVABLE INTO MINUTE  
ELECTRICAL CAPACITANCE CHANGE


*ACTUATION BY PROXIMITY of solid or  
liquid conductors or insulators to an electrode  
terminating a co-axial cable.*



**THE FIELDEN PROXIMITY METER—SENSITIVITY 0.01 mmf—** indicates minute capacitance changes, whether caused by very small mechanical displacement or dielectric change. It measures, for instance, strains in structures, it gauges components to less than 0.00001 in., monitors sheet,

foil and wire sizes, measures liquid and other levels precisely, monitors dimensions and compositions, compares dielectric properties of non-conducting liquids etc. It does what is impossible mechanically and, in many fields, surpasses all other micro-measurement methods.

### THE FIELDEN TEKTOR—SENSITIVITY

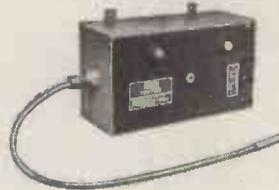

**0.25 mmf —** is a unique, stable, high-speed capacity relay which solves many problems of counting, temperature control, level control of liquids and solids, and so on where simple direct-switching is impossible.

Please send for specification FE/4 to the SPECIALISTS  
IN INDUSTRIAL ELECTRONIC EQUIPMENT

*Fielden*

**(ELECTRONICS) LIMITED**

HOLT TOWN

MANCHESTER

Telephone: ARDwick 2619

**MODEL 90A FORTY RANGE  
TAYLORMETER**

1000 ohms per volt

**RANGES**

**Voltage.** Up to 1000 V. A.C. and D.C.  
**Current.** Up to 1 amp. A.C. and D.C.  
**Output.** Up to 250 V. Six decibel ranges.  
**Resistance.** From 1 ohm to 1 megohm self contained. Buzzer fitted for quick continuity tests. Meter overload protection fitted.



**LIST PRICE £15 . 15 . 0**

All Windsor and Taylor test equipment is available on H.P. at Trade Price. Send for details and catalogues.

**DELIVERY EX STOCK.**

**TAYLOR ELECTRICAL INSTRUMENTS LTD.**  
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND  
Telephone: Slough 21381 (4 lines) • Grams & Cables: Taylins, Slough

Other Products Include: Multirange A.C. D.C. Test Meters • Signal Generators • Valve Testers • A.C. Bridges • Circuit Analysers Cathode Ray Oscillographs • High and Low Range Ohmmeters • Output Meters • Insulation Testers • Moving Coil Instruments



**Microarmature Pickup.**

**Type JB/P/A/1**

The Microarmature Pickup which has an output of 1/15v., a working point pressure of 1/4 oz. and a special tungsten carbide point that wears 80 times as long as sapphire has the additional advantage that it is reasonably robust. In the event of accidental damage caused by mishandling, repairs are easily carried out and therefore relatively inexpensive.

Full information will be sent on request.

"Reproduction of Records." The first edition was sold out immediately and a further edition is now coming to hand.

**J. H. BRIERLEY (GRAMOPHONES & RECORDINGS) LTD.**  
46, TITHEBARN STREET, LIVERPOOL. 2.


**HI VAC**  
THE SCIENTIFIC VALVE  
BRITISH MADE

*Pioneers & Specialists in Small Valves*

LONDON, H.V.C. P.M. NOV 1948 BRITAIN

Messrs. Hi vac Ltd  
Greenhill Crescent,  
Harrow-on-the-Hill, Middx.

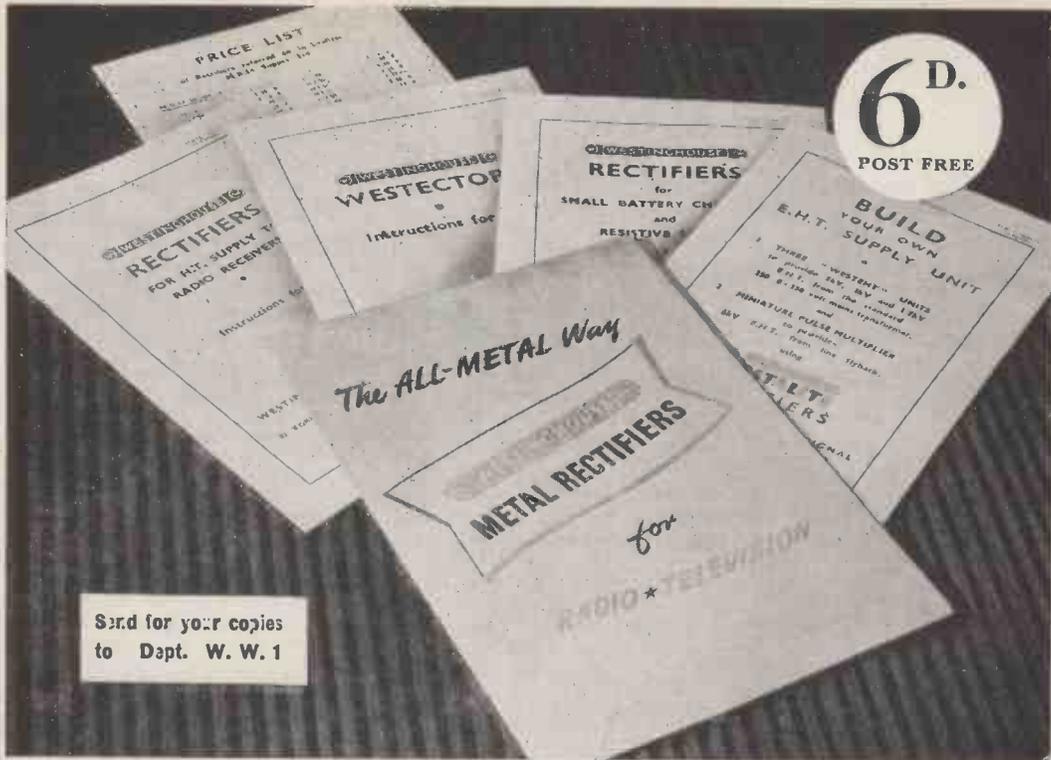**THE address for:—**  
*Subminiatures - Midgets - Miniatures  
and Cold Cathode Tubes*




Send for your copies to Dept. W. W. 1

WESTINGHOUSE BRAKE & SIGNAL CO., LTD., 82, YORK WAY, KING'S CROSS, LONDON, N.1

# Wharfedale OUTPUT TRANSFORMERS

O.P. 3

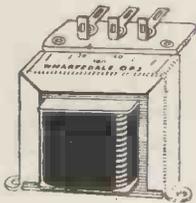

The new W.15 output transformer is illustrated on the right. The inductance is 70 H. with a leakage inductance of only 0.1 H., thus ensuring satisfactory results in wide response circuits with negative feedback. Maximum input 20 watts.



W.15.

**LIST PRICES**

O.P. 3, 3 ratios .. .. .	6/9	De Luxe, 6 ratios with C.T. .. .. .	22/6
Type P, 4 ratios with C.T. .. .. .	8/-	W.12, 3 ratios with C.T. .. .. .	21/-
G.P. 8, 8 ratios with C.T. .. .. .	11/6	W.12.—Any ratio to order .. .. .	25/-
Universal, 6 ratios with C.T. .. .. .	13/6	W.15.—Any ratio to order .. .. .	60/-

## WHARFEDALE WIRELESS WORKS

BRADFORD ROAD, IDLE, BRADFORD

Telephone : IDLE 461.

Telegrams : Wharfedel, Idle, Bradford

# AERIALITE

makers of the world's best  
**AERIALS & EQUIPMENT**

Introduce their **NEW-**



**AERIALITE ...**  
the most advertised  
aerials made!

According to statistics supplied by "The Statistical Review," Aerialite Aerials are easily the most extensively advertised aerials made. Our present campaign includes advertising in the "Radio Times," "Daily Express," "Daily Mail," "News Chronicle," "News of the World," "The People," "Sunday Express," "London Evening News," "The Star," "London Evening Standard," and the leading Midlands papers. The public are asking for "AERIALITE," —The Best!

**AERIALITE Ltd.**  
STALYBRIDGE, CHESHIRE

## AERIAL Fitting SERVICE

Are you missing sales through the inability to fit an aerial? If so, cash in now on the **AERIALITE AERIAL FITTING SERVICE**. This new service by the World's Largest Makers of Aerials applies to the wide range of **AERIALITE TELEVISION and MASTATIC AERIALS**. We shall also be pleased to receive applications to join our organisation from dealers who have experience in aerial fitting. **EXAMPLE:** Fitting of our new Popular D.P.O. MODEL 52. You can supply this low-priced Television Aerial complete and erected for £8.0.0 only. D.P.O. MODEL 52. Complete with 10ft. steel mast and Chimney Lashing Brackets, etc., £4.10.0. Complete Erection Costs, £3.10.0—Total Cost £8.0.0. Write today for full details.

*Make sure you can meet the demand!*

DESIGNERS —  
MANUFACTURERS —  
AMATEURS —

For EFFICIENCY &  
RELIABILITY  
INSIST on —

**Cyldon**  
VARIABLE  
CAPACITORS

All standard laws,  
capacity ranges,  
& voltages up to 15kV.

- AIR-SPACED TRIMMERS
- MICA DIELECTRIC COMPRESSION TRIMMERS
- VARIABLE TRANSMITTING CAPACITORS

Manufacturers:  
**SYDNEY S. BIRD & Sons, Ltd.**  
Cambridge Arterial Rd., Enfield, Middx.  
Phone: Enfield 2071-2

*"You're CERTAIN to get it at ARTHURS!"*

★ **VALVES**: We have probably the largest stock of valves in the country. Send your enquiries. We will reply by return.

**AVO METERS IN STOCK**

Avo Model 7	£19 10 0
Avo Model 7, high resistance	£19 10 0
Avo Model 40	£17 10 0
Valve Tester	£16 10 0
Test bridge	£11 0 0
Avo Minor, AC/DC model	£8 10 0
Electronic Test Meter	£35 0 0
Signal Generator	£25 0 0


**LATEST VALVE MANUALS**  
Mazda - 1/- ea.  
Mullard - 5/- ea.  
Brimar - 2/6 ea.  
Brimar Telostube Annual - 4/-  
Post 4d. extra

**ELECTRIC LAMPS**, all types.  
**TAYLORS METERS**. List on request.  
**DECCA PICK-UPS** ..... £3 15 5  
**DECCA HEAD** (o. Garrard) £2 19 2  
Adaptors ..... 3 8

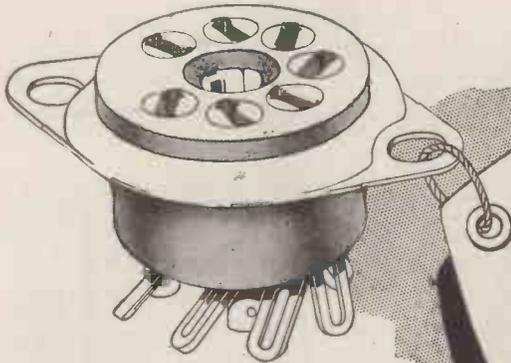**LONDON'S OLDEST LEADING RADIO DEALERS**

**Arthur's** EST. 1919  
PROPS: ARTHUR GRAY, LTD. Terms C.O.D. or cash with order

Our Only Address: Gray House, 150/152 Charing Cross Rd., London, W.C.2 TEMple Bar 5833/4 and 4735  
**ELECTRICAL, TELEVISION & RADIO ENGINEERS.**



**B.7.C.**  
 Ref. No. F.M.7/U  
 Moulded in **P.T.F.E.**  
 ★  
 Ref. No. B.M.7/U  
 Moulded in **Phenol-Formaldehyde**

The McMURDO INSTRUMENT COMPANY LTD., VICTORIA WORKS, ASHTEAD, SURREY

Ashtead 3401

**INTRODUCING THE R22/12, 20-WATT, 12" P.M. LOUDSPEAKER**




**MORE POWER—STILL  
 GREATER EFFICIENCY—**  
 the ultimate development of the famous T2.  
 Available with two types of Cones:—  
**CONE TYPE "1205"**  
 Fundamental Resonance 75 c.p.s.  
 (Designed for PUBLIC ADDRESS)  
**CONE TYPE "1206"**  
 Fundamental Resonance 55 c.p.s.  
 (Designed for BASS REPRODUCTION)  
 Write for descriptive leaflet D10.



**GOODMANS**  
**R22** 20-WATT 12" P.M.  
 17,500 GAUSS  
*Loudspeaker*

FULLY DUSTPROOF

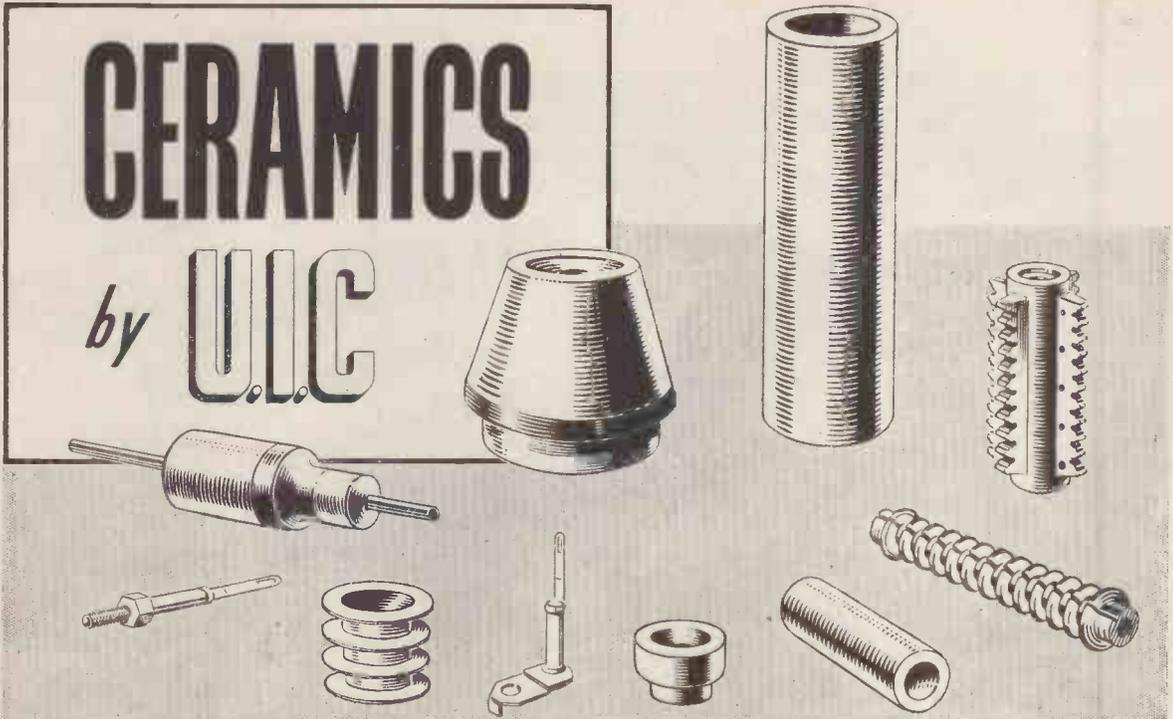**GOODMANS INDUSTRIES LTD.** Lancelot Rd., Wembley, Middx.  
 Telephone: WEMbley 1200 (8 lines)      Telegrams: Goodaxiom, Wembley



# CERAMICS

by **U.I.C.**

**UNITED INSULATOR COMPANY LTD.**

Cables : Calanel, Surbiton.

**TOLWORTH**

**SURBITON**

**SURREY**

**ENGLAND**

Telephone : Elmbridge 5241

*All your switching Problems solved!*



As specified for conversion of the TR 1196

## OSMOR

### 'Q' COILPACKS

Just 5 connections (1-hole fixing) and all your coil and switching difficulties are over! The midget Osmor "Q" Coilpack saves you hours of wasted time and gives

you a really first-class job at very little cost. Pre-aligned with full instructions and complete circuit diagrams included.

★ Portable battery model now available.

Send stamp for FREE circuits and our new lists of coils, Coilpacks and matched radio components, also latest Bargain-Bulletin.

**OSMOR RADIO PRODUCTS LTD. (Dept. W.2.)**  
 Bridge View Works, Borough Hill, Croydon, Surrey

Telephone: Croydon 1220.

**Economical in Time and Money!**

**YOURS FOR ONLY 6 MONTHLY**

**6/6** £1 DEPOSIT SECURES 10 monthly payments of 6/6



Get instant soldering heat. Invaluable for radio servicemen, engineers and home mechanics. Simply plug in, press the button, and in seven seconds the iron's hot! Absolutely safe, the bit cools instantly button is released and lies clear of bench when not in use. Complete with two spare bits and four yards of flex. Suitable for A.C. 200-250V. or 100-150V State model required. Limited stock. No interest charge. Send your deposit to-day for this ultra-rapid electric soldering gun. Leaflet on request. Cash Price £3 19s. 6d. complete

## BURGOYNE SECOND Instant Heat SOLDERING GUN


SEND YOUR DEPOSIT Today TO-

Trade Terms upon Request.

**The RING LAMP CO.**

**81 City Road, London, E.C.1**

Telephone CLERkenwell 7103

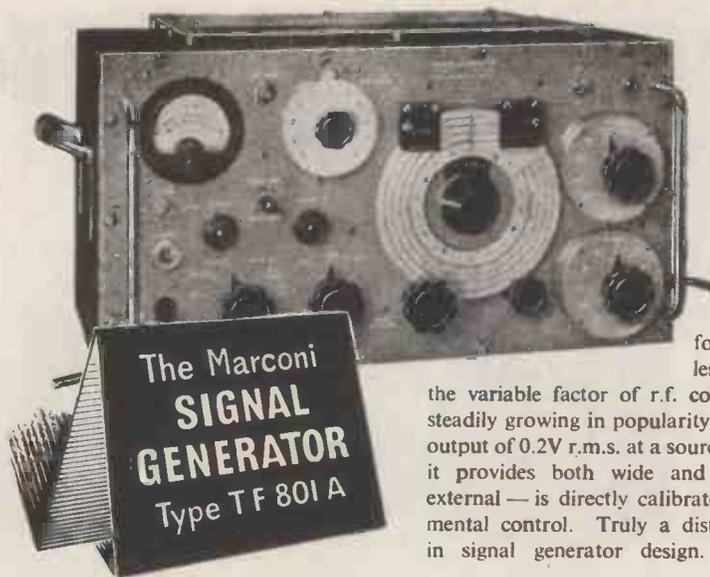

The Marconi  
**SIGNAL  
GENERATOR**  
Type TF 801A

## Equipment without Equivalent

MARCONI TEST EQUIPMENT is without equivalent. Signal Generator TF 801A, for instance, has the unique feature of contactless waveband selection thereby eliminating the variable factor of r.f. contact resistance. The instrument, which is steadily growing in popularity, has a range of 10-300 Mc/s and a maximum output of 0.2V r.m.s. at a source impedance of 75Ω. A.C. mains operated, it provides both wide and narrow band modulation—internal and external—is directly calibrated in frequency and is fitted with an incremental control. Truly a distinguished example of Marconi ascendancy in signal generator design. Full specification available on request.

Please ask for folder  
"SUMMARY OF  
COMMUNICATIONS TEST GEAR"

### MARCONI INSTRUMENTS LIMITED

ST. ALBANS, HERTFORDSHIRE · Telephone: St. Albans 6161/5

Northern Office: 30 Albion Street, Hull · Western Office: 76 Portview Road, Avonmouth · Midland Office: 19 The Parade, Leamington Spa · Southern Office & Showrooms: 109 Eaton Square, London, S.W.1

# Call the tune....

Visit your dealer's showroom today—ask to SEE and HEAR the Collaro Automatic Microgram play your favourite records—and judge this wonderful instrument yourself.

The Auto-Microgram is fitted with the Collaro R.C.500 Record Changer—incorporates spring suspension, eliminating acoustic feed back—and it's portable! Price £18-18-0 plus P.T.



...with the **COLLARO**  
AUTOMATIC  
**Microgram**  
*Portable Electric Gramophone*

\* If you prefer—write without obligation to Collaro Ltd. for illustrated literature describing the Automatic Microgram and "De Luxe" Microgram—the world's finest portable electric gramophone.

Trade enquiries to:—


COLLARO LTD., RIPPLE WORKS, BY-PASS ROAD, BARKING, ESSEX

Telephone: RIPPLEWAY 3333.


Telegrams: "KORLLARO, BARKING."



# Leaders in their field

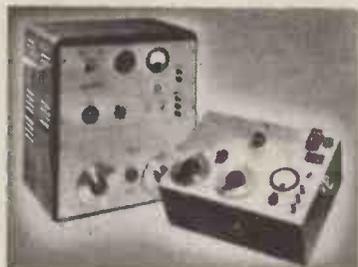

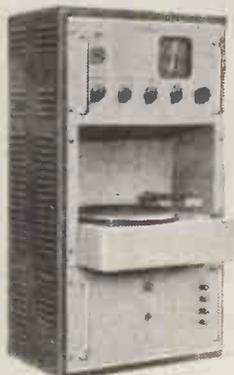BEAT FREQUENCY OSCILLATORS & LABORATORY INSTRUMENTS



INDUSTRIAL SOUND INSTALLATIONS



PORTABLE AND MOBILE AMPLIFIERS




DIRECT DISC RECORDERS FOR HIGH FIDELITY DISC RECORDING



TELEMASTER INTER-OFFICE COMMUNICATION EQUIPMENT



G.U.2 GRAMOPHONE UNIT

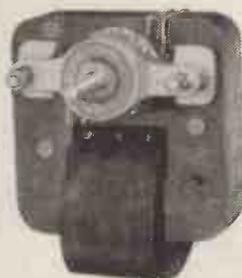

SHADED POLE MOTORS



T.U.2 TURNTABLE UNIT

## BIRMINGHAM SOUND REPRODUCERS LTD.

Telephone:  
Cradley Heath 6212/3

CLAREMONT WORKS, OLD HILL, STAFFS.

'Grams: 'ELECTRONIC'  
Old Hill, Cradley Heath

39th YEAR OF PUBLICATION


## In This Issue

Managing Editor : HUGH S. POCOCK, M.B.E.  
 Editor : H. F. SMITH

EDITORIAL COMMENT .. .. .	1
AMERICAN HEARING AIDS. By <i>A. Dinsdale</i> .. .. .	2
T-MATCH TELEVISION AERIAL. By <i>B. Mayson</i> .. .. .	6
NEW BRIDGE TECHNIQUE. By <i>T. Roddam</i> .. .. .	8
CORNER RIBBON LOUDSPEAKER .. .. .	11
AMATEUR EXHIBITION .. .. .	12
EXTENDING TELEVISION .. .. .	14
WORLD OF WIRELESS .. .. .	16
EASING IMPEDANCE CALCULATIONS. By <i>M. G. Scroggie</i> .. .. .	19
ELECTRONIC CIRCUITRY. By <i>J. McG. Sowerby</i> .. .. .	21
HIGH-QUALITY AMPLIFIER. By <i>D. T. N. Williamson</i> .. .. .	24
FILTERS. By "Cathode Ray" .. .. .	25
UNBIASED. By <i>Free Grid</i> .. .. .	30
A.C./D.C.-BATTERY POWER SUPPLIES. By <i>L. Miller</i> .. .. .	31
MANUFACTURERS' PRODUCTS .. .. .	33
LETTERS TO THE EDITOR .. .. .	35
SHORT-WAVE CONDITIONS. By <i>T. W. Bennington</i> .. .. .	37
RANDOM RADIATIONS. By "Diallist" .. .. .	38
RECENT INVENTIONS .. .. .	40

Published monthly: Price 2/- (last Thursday of preceding month) by ILIFFE & SONS LTD. Dorset House, Stamford St., London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Echaworld, Sedist, London."  
 Annual Subscription: Home and Overseas, £1 6s. 0d.; U.S.A. and Canada, \$4.50.

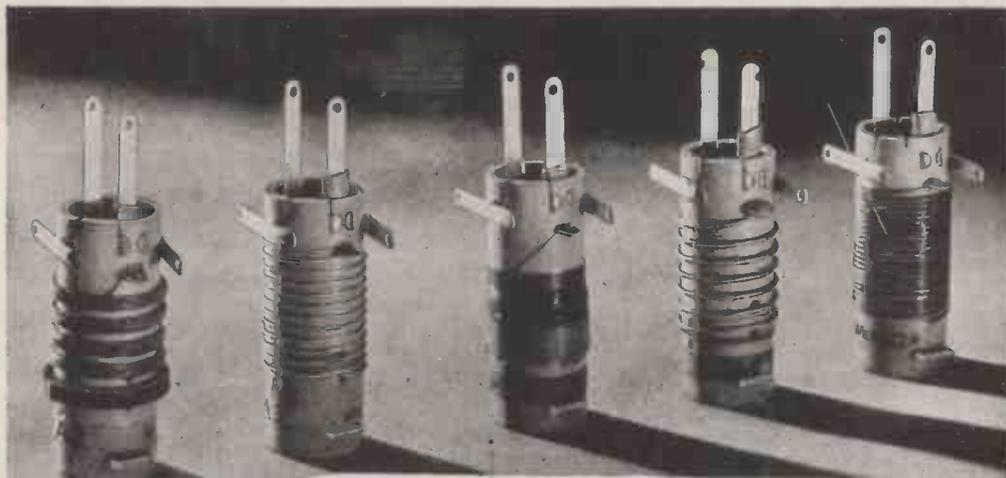BRANCH OFFICES:  
 Birmingham : King Edward House, New Street, 2.  
 Coventry : 8-10, Corporation Street.  
 Glasgow : 26B, Renfield Street, C.2.  
 Manchester : 260, Deansgate, 3



**WEARITE**


**COIL PACKS**

**"P" COILS**

... for Aerial, R.F., and Oscillator Tuning and readily available in all ranges.

**WRIGHT & WEAIRE LIMITED**  
 138 Sloane Street, London, S.W.1.

Telephone: SLOane 2214/5.  
 Factory: South Shields, Co. Durham.

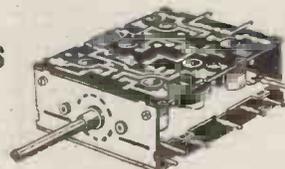

Send 6d. in stamps for the "Wearite" COILPACK Book of Technical Data and Circuits.



# Valves and their applications

## TELEVISION SYNCHRONIZING & TIME BASE CIRCUIT USING EF42, ECC34 & EL38. No. 4.

### FRAME SYNCHRONIZING PULSE SEPARATOR USING 1/2 ECC34

The problem of obtaining a good interlace is a major one in television receiver design and this article is concerned with some elements of the problem and a circuit designed to illustrate the principles involved.

The circuit in Fig. 1. is part of the complete circuit shown in the November issue of the "Wireless World". The waveforms associated with the circuit are shown in Fig. 2 and it will be seen that the chain of eight 40  $\mu$ s frame pulses is converted into one positive pulse.

The waveform E is interesting as it gives the control grid potential of the frame blocking oscillator on the same expanded time scale as the synchronizing waveforms. With the setting of the frequency control (VERTICAL HOLD) corresponding to the waveform shown, the grid potential is some 40 volts below cut-off when the synchronizing pulse arrives. The blocking oscillator then takes current for a period of about 50  $\mu$ s. Towards the end of the conducting period when the grid has ceased to take grid current an oscillation in the leakage inductance and stray capacitance of the transformer T1 occurs.

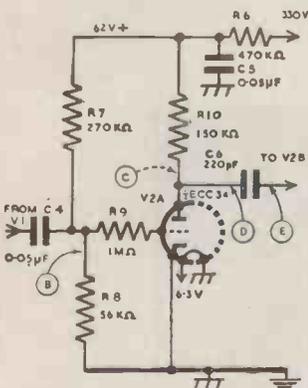


FIG. 1.—CIRCUIT OF SECOND LIMITER IN SYNCHRONIZING PULSE SEPARATOR.

It is apparent from Fig. 2 that the derived frame pulse is of different length for consecutive pulses and this difference appears in the waveform at the grid of the valve V2B. This does not produce non-interlace because the instant of firing is determined by the leading edge of the pulse. This edge is sufficiently steep to ensure that any slight difference in the potential of its base has a negligible effect on the time at which the waveform reaches a given potential. To obtain a perfect interlace the instant, relative to the chain of frame synchronizing pulses at which the blocking oscillator ceases to take current and the potential to which the "charging" capacitor has been discharged at this instant must be identical for consecutive frames. Normally this also implies that the instant at which the blocking oscillator is fired or starts to take current must have the same relationship to the frame pulses for consecutive frames. It is very misleading to assume that a correctly

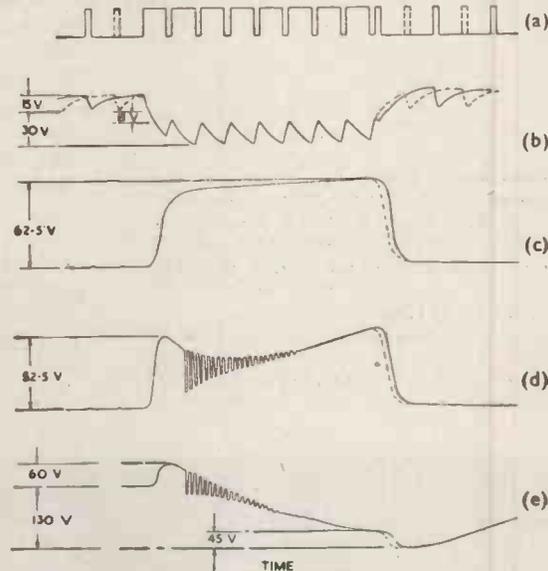


FIG. 2.—WAVEFORMS OF POTENTIAL ASSOCIATED WITH SECOND LIMITER OR FRAME SYNCHRONIZING PULSE SEPARATOR.

fired frame time base will be correctly interlaced. This fact can be readily checked by increasing the brightness and observing that the beginning of the flyback is interlaced in the majority of receivers where interlace is lacking in the picture.


The methods described above ensure that the time base is fired correctly and also the blocking oscillator is protected, during the critical period when it is taking current, by its synchronizing channel being open-circuited, i.e. the valve V2A is cut off. With a reasonable layout no pulses from the line base can find their way into the frame blocking oscillator and a good interlace is obtained.



Reprints of this report with additional circuit notes and also the other reports from the Mullard Laboratory giving full circuit and constructional details of the four valve synchronizing and time base circuit are available, free of charge, from the address below.

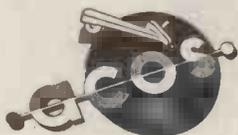**MULLARD ELECTRONIC PRODUCTS LTD.,**  
**TECHNICAL PUBLICATIONS DEPARTMENT,**  
**CENTURY HOUSE, SHAFESBURY AVE., W.C.2**  
 (MVM111)





## A new approach to "High Fidelity" ... and the coming of "New-True Fidelity"

PERHAPS no phrase in sound reproduction has been more loosely used in the past than "high fidelity." What some people would term high-fidelity reproduction caused others to shake their head. Obviously, ideas and ideals of fidelity were measured by differing standards. What, then, is "true fidelity"? Fortunately, this can accurately be measured and graphically expressed, but we have to seek the assistance of a very critical science—that of acoustics—which provides objective rather than subjective answers.

Here we are concerned more particularly with the reproduction of sound via an electrical pick-up. The authority of acoustic science has laid down a performance which it regards as ideal, but naturally, one that is unconcerned with the practical limitations which beset the manufacturer. For matters of cost and usage are no concern of the theorist. Indeed, the manufacturer could produce a pick-up with the approved ideal response, but such an instrument might cost, say, twenty-five guineas; and again it is conceivable that it would be so fragile as to preclude its use in the home. Further, even given a pick-up with the ideal response, and built on the most robust lines, its actual reproduction is still limited by the characteristics of commercial recordings. A practical pick-up must be capable of being used with a wide range of equipment, each item of which has its own idiosyncrasies. So the manufacturer's problems multiply, and a compromise of some kind is necessary.

### The Quest . . .

A year ago, however, after long experience in the design and mass production of pick-ups, Cosmocord Limited were convinced that an entirely new approach was essential. The easy way might have been to set a new, good, practical standard and say "This is high fidelity, and you ought to like it." But the honest approach starts

the other way round, viewing everything from the user's point of view and the while, stimulating research at every step. That was the Cosmocord way.

### And the Conclusions . . .

The most important conclusions were:

- (1) That the average user does not want to spend time and money finding suitable equalising networks, etc. The pick-up must be a success from the word "go."
- (2) he wants his records to last—the pick-up must, therefore, cause the minimum possible wear.
- (3) he wants the pick-up to be robust enough to withstand even the most careless of handling.
- (4) and lastly, he wants the pick-up at a price he can afford.

Moreover, defects such as high tone-arm resonance, high needle-tip impedance and high tracking weight, excessive needle talk, reproduction of motor rumble and tracing distortion in the upper register, all these must be eliminated. So with these considerations in mind *acos* research set about developing the ideal pick-up—and the result is the GP.20.

### Stage by Stage Achievement

First the stiffness of the assembly was reduced until the pick-up satisfactorily tracked commercial records at seven grams. Then, because warped records or badly aligned turntables and badly sprung motors might cause the pick-up to jump grooves, the tracking weight was deliberately increased to 13-14 grams. This extremely low needle pressure, coupled with the use of a flexible, sprung permanent sapphire stylus, reduces record wear to an absolute minimum, thus ensuring vastly longer life to records. Further, this flexibility of the assembly makes the unit virtually damage-proof.

Needle talk, tracing distortion and distortion due to "pinch

effect," were greatly reduced by increasing the vertical compliance of the assembly until it was little less than the lateral compliance. The outstandingly good frequency-response was achieved by making the crystal assembly appear as a terminated mechanical transmission line, and arranging that the terminating section would give pre-emphasis of approximately 6 db per octave above 1,000 cps. This resulted in the working pick-up characteristic from commercial recordings (turn over at 250 cps) being substantially flat from 20 to 250 cps, dropping approximately 6 dbs between 250 and 1,000 cps, and flat beyond that frequency up to 9 Kcs, the response falling above this frequency.

The pre-emphasis between 250 and 1,000 cps provides an automatic bass boost, eliminating equalising circuits of any kind. The frequency response was set flat to 9,000 cps, as being completely adequate to give the best reproduction from commercial records.

The output of the GP.20 is more than half a volt at 1,000 cps, and sufficient to load fully any domestic set or amplifier. The GP.20 is free from peaks in the upper register, the response being smooth over the whole range.

The tone-arm design is unique in that it is supported on a single needle point, thereby reducing lateral and vertical friction to the barest possible minimum. Torsional arm resonance is eliminated.

### Finally—the Cost . . .

Last, but not least, is the cost. The list price of the GP.20 in Great Britain is 50s. plus 21s. 5d. purchase tax. So *acos* research and *acos* mass production techniques, utilising the most efficient piezo-electric assembly, have produced an instrument comparable in price with ordinary pick-ups, but with a laboratory performance. Indeed a justification of the new approach to "high fidelity" reproduction, since it produced the GP.20 and achieved what we like to term "New-true Fidelity"—for that, assuredly, it provides.

COSMOCORD LIMITED • ENFIELD • MIDDLESEX

# THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

## Ghosts that come in the night (and go). Seriously!

We have had one or two cases of double images (commonly called "ghosts"), in television reception when using an aerial apparently correctly sited for the particular receiver.

Now readers will know that the phenomenon of "ghosts" is due to a reflected signal arriving by a longer path than the direct signal. Gasholders are common sources of such reflections, and there are several within a few miles of Alexandra Palace.



Until the advent of a particular complaint, we considered a gasholder a permanent feature of a landscape, but the erratic behaviour of the television receiver installation caused us to devote further attention to the matter. The "ghost" was not there when our engineers carried out their investigation. It took us longer than it should have done, to realise that the gasholder was down during the afternoon, and rose to its effective height by the time the evening transmissions were on the air. It was necessary, in this case, to change from a dipole to a "Viewrod,"\*1 "H" type.

### 1/4 λ versus 1/7 λ spaced "H"

In the case described above, the site for the "Viewrod" was within a few miles of Alexandra Palace. Normally an indoor aerial would have been satisfactory, but as it was in a closely built up and semi-industrial area with a lot of interference, an outside dipole was erected. When the gasholder made itself troublesome, its position, relative to the transmitter, called for an "H" type "Viewrod," but, as the aerial was being used to reduce a form of interference, in a region of strong signal, it was not necessary to fit one of the senior range of "H" type aerials. We fitted an L.700/L which employs elements


spaced 0.15 wave. This choice showed a saving to the customer of 21/-.

In such a locality, if either model had been used with the dipole between the transmitter and the reflector, the signal would have been far too strong, the picture too white and it would have been necessary to fit attenuators. Unfortunately this sort of thing is far too common and just gets the industry a bad name.
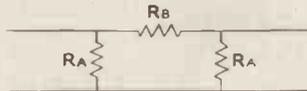
### Attenuation.

When it is necessary to fit an aerial that provides too much signal, i.e., where an "H" type or "Multirod"\*2 is used to provide a better signal-to-interference ratio, although a single dipole would provide adequate signal pick-up, it is necessary to fit attenuators in the receiver or feeder cable.


A suitable arrangement for an unbalanced 80 ohm feeder is shown below.



Suggested values for various degrees of attenuation are as follows:—

Attenuation	RA	RB
6 db	240 ohms	62 ohms
12 db	130 ohms	150 ohms
18 db	100 ohms	330 ohms
24 db	91 ohms	620 ohms

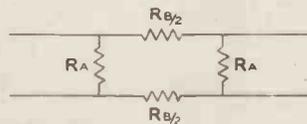For a balanced 80 ohm feeder the arrangement shown in Figure 3 should be used. There is a series resistor in each line, of half the value of the single series resistor RB in Figure 2.



### Interference.

The most prevalent form of interference with television is that from the ignition systems of motor cars, appearing as a snowstorm effect on the Television screen. This can be cured by arranging that the television aerial be erected outside the field of such interference. If it wasn't for this particular form of annoyance, there would be tens of thousands more indoor television aerials. Many

thousands of motorists are helping to remove the trouble by fitting a single suppressor in the lead from the coil to the distributor. It actually screws into the distributor and costs 1s. 6d. Many viewers have given these to neighbours whose cars are troublesome, and to tradesmen regularly passing. But, of course, these tactics are useless if the viewer is on a busy main road.

If the direction of the television transmitter is up or down the road in question, and the distance less than fifteen miles, great relief may be obtained by the use of a "Belling-Lee" inverted "V" dipole erected as high as possible and parallel with the road.

This aerial picks up very little signal at right angles to the direction in which it lies. If the aerial is between the road and the dipole an "H" type "Viewrod" will help, with reflector between the road and the transmitter. If the road is between the aerial and the transmitter use an "H" type, and get as far from the road as practicable, and keep high, except in the few cases where relief is obtained by using the house to screen the aerial from the road. This sometimes helps without unduly attenuating the wanted signal. The last case is the most difficult.

\*1 "VIEWROD" (Regd.) "H" type television aerials:

Senior range 1/4 λ spaced.

London L648, Midland L652, from £3 2s. 6d.

Lightweight range 0.15λ spaced. London L700, Midland L701, from £2 10s. 0d.

\*2 "MULTIROD" (Reg'n applied for):

Dipole and reflector and two directors (for fringe areas):


London L698, Midland L699, price £13 18s. 0d., complete with 14 foot light alloy mast.

**BELLING & LEE LTD**  
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND

# ESSENTIALS

FOR THE BEST PRODUCTION!

## THE PHASE INVERTER SPEAKER

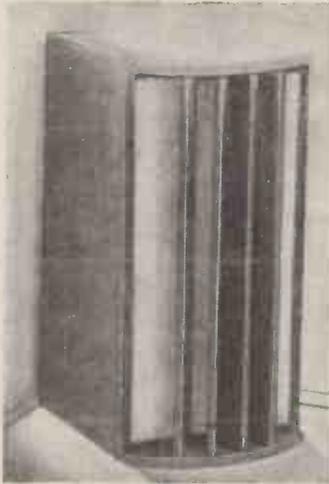

Beloved by its numerous users and flattered by imitation. Measuring only 29" high x 14" square, this instrument provides the music lovers' perfect answer to the "Baffling" problem. Response 25 to 13,000 cps; fitted with the famous Sound Sales dual suspension auditorium unit. Input impedance 6 ohms.

Price £12 10 0

### HEAVY DUTY OUTPUT TRANSFORMER TYPE 036,


characteristic  $\pm$  1db,  
from 20-20,000 cps.

Price £2 6 8

**WEBB'S RADIO, 14, Soho St., London, W.1**

supply all SOUND SALES products on Deferred Terms

## ALLOY CORED SCRATCH FILTER CHOKE

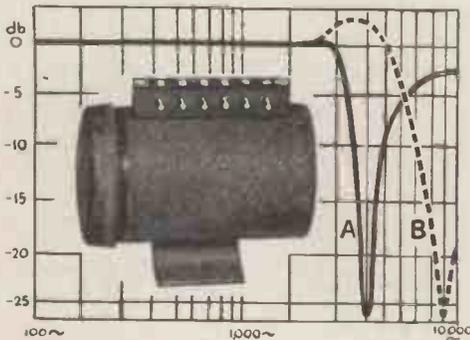

### TYPICAL RESPONSE CURVES

A Tuned for maximum rejection at 4,000 cycles  
B Tuned for maximum rejection at 9,000 cycles

WHERE SURFACE NOISE IS THE LIMITING FACTOR TO SUPREME QUALITY OF REPRODUCTION, fit a Sound Sales alloy cored steep trough tuneable filter. We know the problem of removing Surface Noise or Heterodyne whistle is not easy to solve, but the steep trough filter has so far produced the most encouraging results we have encountered when using a compact component which can be incorporated in existing apparatus.

CHOKE TYPE: C/SF, Dia. 2½", length 3¼" PRICE £1.8.9 each  
Obtainable directly from Sound Sales Ltd., appointed Agents, and the best Retailers


**SOUND SALES LIMITED**  
MANUFACTURERS OF ELECTRONIC PRODUCTS SINCE 1931

Showrooms & Offices—

125, OXFORD STREET, LONDON, W.1

GERrad 8782

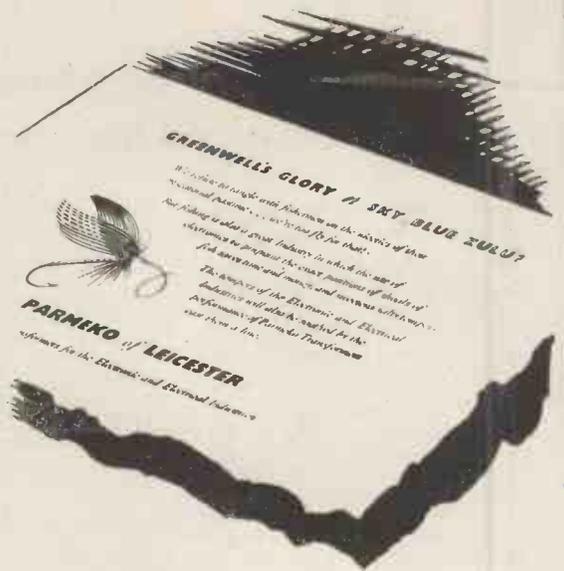Works : West Street, Farnham, Surrey. Tel : Farnham 6461/2/3  
Contractors to the Admiralty, Air Ministry, Ministry of Supply  
G.P.O., B.B.C., etc. On A.I.D. List.



"I LIKE THE LOOK  
OF THESE PEOPLE . . ."

. . . and the Managing Director presented another balance sheet in a most excellent black . . . the shareholders think the world of him!

This Parmeko advertisement, torn out and passed to the Design Department, resulted in a new type of Transformer designed specially for this Company's use: result - better performance, greater savings! A Transformer designed by people devoted solely to that task; produced on single-purpose plant by an organisation with 25 years experience of supplying Britain's largest manufacturers with Parmeko Transformers for most Electronic or Electrical circuits.

## PARMEKO of LEICESTER

Makers of Transformers for the Electronic and Electrical Industries.



# HIGH QUALITY REPRODUCTION

"FIFTY and THIRTY WATT" CINEMA AMPLIFIERS as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required. PRICES range from **34½ gns.** to **42½ gns.**



### TYPE C.P. 20A AMPLIFIER

For AC Mains and 12 volt working giving 15 watts output, has switch change-over from AC to DC and "Stand-by" positions. Consumes only 5½ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.

PRICE **£28 . 0 . 0.**

### FOUR-WAY ELECTRONIC MIXER

This unit has 4 built-in balanced and screened microphone transformers, normally of 50-30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less, and any impedance can be supplied to order. PRICE **£24 . 0 . 0.**



### OTHER MODELS IN OUR RANGE OF AMPLIFIERS

- "SUPER-FIFTY WATT" - - - - - PRICE **36½ gns.**
- "THIRTY WATT" - - - - - " **30½ gns.**
- "10-15 WATT RECORD REPRODUCER" " **25½ gns.**

These are fitted in well ventilated steel cases with recessed controls, as illustrated.

*Full details upon request.*

**EXPORT ENQUIRIES INVITED.**

**VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19**  
 Telephones: LIB 2814 and 6242-3  
 Telegrams: "Vortexion Wimble, London."



# Stentorian

## CONCENTRIC DUPLEX

A new quality speaker for the enthusiast

This twin "quality" reproducer, incorporating two independent speakers, is the latest application of the now well-known 'Series gap' magnet system, originated by W.B. engineers.

The centre pole is hollow, and forms the beginning of the pressure horn which loads the convex high-frequency diaphragm at the rear. In front this pole piece is surrounded by a separate gap, in which the low-frequency speech coil operates. The speaker should not be confused with the double-cone type.

There is no cross modulation, and the range very evenly covered (especially if a crossover network is used) is from 50 to 14,000 c.p.s.

Although suitable for outputs up to 6 watts only, this small speaker is nevertheless a high-fidelity reproducer in the best sense of the word. You should try it.

PRICE **£6-6-0**

complete with matching transformer and filter condenser.

Mounted in de luxe table cabinet - - - - £11-3-0  
 Corner console twin speaker, less transformer - - £12-12-0

WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS



### SPECIFICATION

Series Gap Magnet of Alcomax 3.  
 Cone: 10" diameter.  
 Flux in L.F. gap, 12,000 gauss on 1" pole.  
 Flux in H.F. gap, 13,000 gauss on 1" pole.  
 Power handling capacity (both component speakers) 6 watts.  
 Chassis material pressure die-cast from Mazak 3, non-magnetic and non-resonant alloy.



## PLAN YOUR CAREER

RADIO · TELEVISION and other INDUSTRIAL ELECTRONIC subjects

ELEMENTARY & ADVANCED COURSES

### DAYTIME

- Principles and Practice of Radio—1 year.
- Telecommunication Engineering—2 years.
- Electronic Engineering—3 years (including one year's practical training in E.M.I. Factories)—leading to C & G full Technological Certificate. (Next courses begin April 1950)
- Marine and Air Radio Officers' Course (for P.M.G. Licence).

### also HOME STUDY

- Basic Radio ● Basic Television ● Intermediate Maths. ● Higher Maths. ● Industrial Electronics

Write for FREE BOOKLET to Dept: 16a

# E.M.I. INSTITUTES

10 PEMBRIDGE SQUARE, NOTTING HILL GATE, W.2

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.

B.166

from the range of  instruments

## Model 44 SUBSTANDARD MULTI-RANGE METER

A self-contained precision instrument for general laboratory use and for calibrating first grade single and multi-range meters. The accuracy on the 44 ranges is Substandard on d.c. and within  $\pm 0.5\%$  on a.c. These meters are made with the greatest care and have been supplied for a number of years to the leading laboratories at home and abroad.



ELECTRONIC INSTRUMENTS LTD  
 17 PARADISE ROAD · RICHMOND · SURREY



# The New WESTON S75 Multi-Range Test Set



## 53 Ranges with Rotary Switch Selection

This uniquely comprehensive Test Set has 53 ranges for measuring AC and DC current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500 V. Selection is carried out by two 20-position switches. A fully protective safety device is fitted and is operative for forward or reverse overload. The 150-division 6" scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89 covering first-grade instruments. Full details of the ranges covered and of the complete specification will gladly be supplied on request.

# SANGAMO WESTON LIMITED

ENFIELD · MIDDX · Tel: Enfield 3434 (6 lines) and 1242 (4 lines)

201 St. Vincent Street,  
Glasgow  
Tel.: Central 6208

Milburn House,  
Newcastle-on-Tyne  
Tel.: Newcastle 26867

22 Booth Street,  
Manchester  
Tel.: Central 7904

33 Princess Street,  
Wolverhampton  
Tel.: Wolverhampton 21912



For the "Electronic Engineering"  
**HOME-BUILT TELEVISOR  
 AND  
 FREQUENCY MODULATED RECEIVER**

We are proud to announce that the designers of these two famous receivers used "Sommerford" Transformers and Chokes in their Prototype models. Chosen for their accuracy and reliability "Sommerford" components contribute in no small measure to the success of these outstanding designs. The constructor can be assured of obtaining the very high standard of reliability of which these sets are capable only by using the specified components—"Sommerford" is your safeguard. Full details and specifications may be had upon request.

THESE ARE THE SPECIFIED TYPES

For the TELEVISOR

R.135A. C.247  
 C.268 HV.357

For the RECEIVER

R.110B C232B  
 OP. 748B

**GARDNERS RADIO** Ltd  
 SOMERFORD CHRISTCHURCH HANTS  
 Telephone: CHRISTCHURCH 1025

**Mr. Dealer & SON**

The many technical difficulties of all types in modern Radio and Television DEMAND that you should give your son every opportunity of mastering them. Our 1-YEAR DAY COURSE is designed for precisely this purpose. We have other attendance as well as postal courses.

Write today for our

**FREE BOOKLET** to Dept. 16

**E.M.I. INSTITUTES**

10, PEMBRIDGE SQUARE, NOTTING HILL GATE, W.2

Associated with  
 "H.M.V."  
 MARCONIPHONE  
 COLUMBIA  
 ETC.

B.164

**ACRU**

*neon  
 indicator  
 lamps*



**ONE-HOLE  
 FIXING**

In handsome Black Bakelite holder complete with series resistance and leads, to show Pink, Red, Amber or Green, on 230v or 400v AC or DC. Specially designed for easy assembly in 1/2-inch mounting hole.

Send now for full details, prices and terms.

For  
 SWITCHBOARDS,  
 INDICATOR PANELS,  
 MACHINE CONTROLS,  
 HEATING APPLIANCES,  
 ETC.

**THE ACRU ELECTRIC TOOL MFG. CO. LTD.**  
 123, Hyde Road, Manchester, 12.

Ardwick 4284.

N.L.

# BRITAIN'S BEST AUDIO AMPLIFIER

The amplifier whose PERFORMANCE FIGURES have been CHECKED and SUBSTANTIATED by the

## NATIONAL PHYSICAL LABORATORY

### TESTS OF TL/12 12 WATT AMPLIFIER

	H. J. LEAK & CO. LTD. REPORT	N.P.L. REPORT
<b>TEST CONDITIONS.</b>	The following are the "pass" figures on final test of amplifiers carried out in our own laboratory. They are the performance figures advertised in preceding issues of the "Wireless World."	In all cases the input was applied to a 50,000Ω resistor connected to the amplifier by 3 feet of screened cable. The output load was in all cases a resistor of 18Ω and the output transformer secondary windings were connected for the "15Ω-20Ω" condition.
<b>HARMONIC DISTORTION.</b>	0.1% for 10 watts output at 1,000 c/s. 0.19% for 10 watts output at 60 c/s.	0.03% for 10 watts output at 1,000 c/s. 0.1% for 10 watts output at 60 c/s.
<b>HUM AND NOISE.</b>	- 80 db. referred to 10 watts.	- 80 db. referred to 10 watts.
<b>SENSITIVITY.</b> Input required for 12 watts output at 1,000 c/s.	160 mV.r.m.s.	148 mV.r.m.s.
<b>LOAD DAMPING FACTOR.</b> (Load impedance/output impedance.) For 10 watts output at 1,000 c/s.	20.	42.
<b>FREQUENCY RESPONSE.</b> Gain relative to that at 1,000 c/s. measured at 7.5 watts.	c/s. 20-20,000 db. ± 0.1	c/s. 20 60-1,000 5,000 10,000 15,000 20,000 db. + 0.1 0 - 0.1 - 0.3 - 0.4 - 0.7
NOTE the N.P.L. figures for frequency response include the losses introduced at the higher frequencies by the capacitance of the input cable shunting the input resistance of 50,000Ω.		

TL/12 12 WATT AMPLIFIER Price £25.15.0

RC/PA REMOTE CONTROL PRE-AMPLIFIER Price £6.15.0

Used with the RC/PA pre-amplifier and the best complementary equipment the TL/12 power amplifier gives to the music-lover a quality of reproduction unsurpassed by any equipment at any price. It is designed in a form so that the power amplifier can be housed in the base of a cabinet and the small pre-amplifier mounted in a position best suited to the user.



If you are interested in high-fidelity reproduction or recording you are certain to find our 16-page illustrated booklet of considerable value. It is presented in a form acceptable both to the professional communications engineer and to the amateur enthusiast seeking the highest possible quality of reproduction.



WRITE FOR BOOKLET W/TL/12

# H. J. LEAK & CO. LTD. (Est. 1934)

BRUNEL ROAD · WESTWAY FACTORY ESTATE · ACTON, W.3

Phone : SHEpherds Bush 5626.

Telegrams : Sinuscidal, Ealux, London.

Foreign : Sinusoidal, London.



## 18 TOTTENHAM COURT ROAD, LONDON, W.1

Tel: MUScum 2453

Tel: MUScum 4539

Shop hours: Monday-Friday 9—5.30. Saturday 9—1

**FULL MAIL ORDER FACILITIES Please add postage**

### "ELECTRONIC ENGINEERING" TELEVISOR

Home Built Televisor booklet—Sutton Coldfield reception. Complete with wiring diagram (Postage 2d.) 4/6.

Home Built Televisor booklet—London area reception (Postage 2d.) 2/6.

Wiring diagram for London area booklet. (Postage 2d.) 2/6.

### "VIEWMASTER"

Complete assembly instructions for building the "VIEW MASTER"—the Television set you can build at home from standard parts. London area only. (Postage 3d.) 5/-.

### "WIRELESS WORLD"

"Television Receiver Construction." A reprint of ten articles in "Wireless World" covering the construction of a TRF Televisor, "Superheterodyne Television Unit." A reprint of two articles describing a long range receiver for use with the "Wireless World" Televisor. (Postage 2d.) 2/6.

### T.C.C.

.001 mfd 6KV. d.c. wkg. Visconol CP56QO, 4/6

.01 mfd. 5KV d.c. wkg. Visconol CP56QO, 7/6.

.1 mfd 2KV d.c. wkg. Visconol CP56X, 7/6.

.1 mfd 7KV d.c. wkg. Visconol CP38QO, 15/-.

1 mfd 350 v. d.c. wkg. Picopack CE30N, 2/6.

2 mfd 150 v. d.c. wkg. Picopack CE30G, 2/6.

20 mfd. 12v. d.c. wkg. Picopack CE30B, 2/6.

Complete set of TCC Condensers for "View Master" 26/15/-.

### SCANNING EQUIPMENT

Scanco scanning coils for 9in. or 12in. CRT. (Postage 9d.) 25/6.

Scanco line output transformer ratios 4:1, Max d.c. 75 mA. (Postage 9d.) 25/6

Scanco focus coil for 9in. or 12in. CRT Max d.c. 40 mA. (Postage 9d.) 30/-.

Scanco special focus coil for 12in. CRT. 25,000 turns. (Postage 1/-) 35/-.

Bel Ticonal Focus Ring. A permanent magnet focusing to suit any type of standard 9in. or 12in. CRT. (Demonstration model always on view). (Postage 1/6.) 37/6.

Complete set of Plessey equipment for "View Master" (Postage 1/6) 25/12 2.

### COILS

Wearite iron-cored coils for "View Master" (Postage 6d.) 21.

Bel Sound Television coils all marked and boxed (Postage 6d.):

"Electronic Engineering" Televisor (London) 15/-.

"Electronic Engineering" Television (Birmingham) 18/6.

"Wireless World" TRF (London) 48/6.

"Wireless World" Superbet (London or Birmingham) 52/6.

### MISCELLANEOUS

Set of Westinghouse rectifiers for "View Master" (Postage 6d.) 23/2/6.

Set of Bulgin components for "View Master" (Postage 6d.) 12/6.

Set of Belling-Lee components for "View Master" (Postage 6d.) 7/6.

Set of Whiteley components for "View Master" (Postage 1/6) 26/5/-.

Set of Morganite resistors for "View Master" (Postage 6d.) 21/6 0.

Set of Olivern Wire Wound pots for "View Master" (Postage 6d.) 19/3.

### VALVES AND C.R.T.'s

Mazda 6P28	21/4	Mullard EF30	21/4	Cossor 451U	18/3
.. 6P25	15/11	.. EB91	12/10	.. 8130	7/6
.. T41	12/10	.. EBC33	11/7	Ostram KT61	12/10
.. Pen45	12/10	.. EL33	12/10	.. DH63	11/7
.. Pen46	18/3	.. EL38	24/4	GRC 6501	211/6/10
.. CRM121	215/2/5	Mullard MW22-14C	211/6/10		

# EVEN THE EXPERTS SAID IT WAS IMPOSSIBLE!

THE problem was to produce a portable Pattern Generator which would simulate the B.B.C. wave form without employing hundreds of valves and involving circuiting. And the experts shook their heads and said it just couldn't be done!

Well, it has been done—by Murphy, of course, who have accomplished the seemingly impossible in their TPGII, using only a handful of valves yet giving a test pattern with all the correct timing pulses, etc., enabling a television receiver to be tested and fully adjusted when the B.B.C. is not transmitting! Checking for interlace, picture size linearity and other awkward problems are possible with the amazing TPGII.

## INVITATION

I do not expect you to believe this—no one does until he has seen it, so make an appointment for an actual demonstration.

Write: 65 Barnsbury St., London, N.1  
or get in personal touch with F. Livingston Hogg by telephone (TUDor 5277)

## F. LIVINGSTON HOGG

65 BARNSBURY STREET, LONDON, N.1

and at WRITTLE, ESSEX

# CLYDESDALE

Bargains in Ex-Services Electric Equipment

**BRAND NEW IN MAKER'S CARTON.**

**WIRELESS SET NO. 48 (MARK I). TRANSMITTER/RECEIVER.** American version of the No. 18 Set, modified to U.S. requirements. Transmits C.W. or Fone, frequency coverage of 6-9 mc/s (33.3 M to 50 m.) for use with dry batteries or a hand driven generator, which is supplied with the kit. Transmitter has variable freq. osc., I.A.5, and PA 2/1299's modulated by a 1LD5. A 1,000 kc/s crystal standard is built into the Tx. (1LD5) a further 1LD5 is the diode R.F. Rect. Receiver is a 6 valve superhet employing 1LN5 R.F., 1LA6 Mixer, 1LN5 1st I.F., 1LD5 2nd I.F. and B.F.O., 1LD5 1st L.F. and AVC and a 1A5 output—I.F. freq. 455 kc/s with 17 kc/s at 10 db down. The aerial consists of 10ft. rod (11 sections) range 5 miles on R/T, 10 miles on C.W. greater ranges can be obtained with a normal aerial. All circuits are metered with a 500 microammeter. Power requirements, 162 volts 60 m/a. 3.1 volts .3 amp.

The generator supplies all power requirements (plus 12 volts bias when switched for 18 set). Dimensions of Set and Battery container: 11½ x 10½ x 17½ in.

**CLYDESDALE'S PRICE ONLY. £14/10/- CARRIAGE PAID.**

**Brand New, in Maker's Carton. REMOTE CONTACTOR No. 4.** Relay (24V) with Ratchet drive mechanism, switch, etc., used for remote switching. Unit size: dia., 3½ in. flange dia. 4 in. depth, 2½ in. **CLYDESDALE'S PRICE ONLY. 2/8 each POST PAID 27/6 per doz.**

**Brand New, in Maker's Cartons. A UNIVERSAL MOTOR.** By simple external wiring, full data supplied. For 220-250 volts, A.C. or D.C. mains. New method gives better than 1/6 h.p. Ideal for light bench work, and unit has a lining spindle which becomes available for driving when the fan is removed. **Ex. R.A.F.** Motor Generator Type 29. Size 11 x 5½ x 5½ in. Input 24 v. 16 a, output 1,200 v. 200 m/a. **CLYDESDALE'S PRICE ONLY. 25/- CARRIAGE PAID**

**JUMPER LEAD ASS. (for WS-19) BRAND NEW.** 60ft. of 5 core flex fitted each end with a 5-way rubber plug, ZA2994. **CLYDESDALE'S PRICE ONLY. 7/6 POST PAID**

**CONNECTOR 12 PT (for WS-19) BRAND NEW.** 12ft. 2in. of 12-way rubber covered cable fitted each end with a 12-way metal clad socket ZA/US 10624. **CLYDESDALE'S PRICE ONLY. 5/6 POST PAID**

**CONNECTOR 4 PT (FOR WS-19) BRAND NEW.** 4ft. lin. of 6-way braided screened rubber covered cable fitted one end with a 6-way socket ZA/US 10631, a chassis union fitted to the other end, the lead left flying with 4 solder-tags. **CLYDESDALE'S PRICE ONLY. 3/6 POST PAID**

**CO-AXIAL CONNECTOR (for WS-19) BRAND NEW.** 4ft. length of tuned co-ax. feeder, fitted with a Pye angle socket at one end, and a direct entry socket at the other. **CLYDESDALE'S PRICE ONLY. 2/6 POST PAID**

**CONNECTOR 12 PT (for WS-19) BRAND NEW.** 6ft. Bin. 12-way braided cable rubber covered, fitted each end with a 12-way socket—ZA/US 10625. **CLYDESDALE'S PRICE ONLY. 3/6 POST PAID**

**SPECIAL CABLE BARGAIN OFFER.** 6 lengths Cables as above, 2/H151, 1 each, H152, H153, H154, H155, all Brand New. **CLYDESDALE'S PRICE ONLY. 19/6 POST PAID**

**MOVING COIL MIC./HEADPHONE ASSY. BRAND NEW.** With a moving coil microphone (Hand No. 7) attached 3ft. lead with rubber 5 point socket. Imp. per insert 60 ohm. approx. **CLYDESDALE'S PRICE ONLY. 12/6 POST PAID**

**AERIAL BASE (for WS-19) BRAND NEW.** This base is of enforced moulded rubber with a metal centre to which is fitted a 1½ in. threaded bush with lock-nut, the centre of which retains a co-axial feed through with ceramic insulation. 6-2BA retaining heads are mounted into the rubber. **CLYDESDALE'S PRICE ONLY. 3/- POST PAID**

**Brand New in Maker's Carton. INSTALLATION KIT FOR WS. No. 19. U.S.A. made by R.C.A.** Complete Kit comprises, Con. 12 pt. 12ft. 2in. cable with 12W. Skt. each end, Ditto 6ft. Bin., Con. 4 pr. with 4ft. lin. 6 wq. cable and 6W. skt. one end, co-ax. con., 2 Jumper leads, 2/Satchels, 3 sets M.C. Mic/H/Phone Assy., Aerial Base, Beam Ant. mtg. Control Unit No. 2, with O.P. leads, Control Unit No. 1, with 6W leads, Junction Box No. 3 with D.P. leads and 6W lead., mtgs., etc., etc. screws, nuts, washers, plus installation and wiring diagrams. **CLYDESDALE'S PRICE ONLY. 42/6 each CARRIAGE PAID**

**BEAM, ANTENNA MOUNTING (for WS-19).** Substantially constructed sleeve and fixing flange. **CLYDESDALE'S PRICE ONLY. 2/6 POST PAID**

**STILL AVAILABLE.** Units of SCR-522 B.C.624 Receiver, Chassis, with valves etc., plus FREE GIFT B.C.625 Transmitter Chassis (partly stripped by B.O.T.) At 37/6

R1481 V.H.F. Receiver Unit at ..... 99 6  
A.C. Power Unit type 3 at ..... 79 6  
Or Both above items at ..... £8 8 0

Master Oscillator type MI-19467-A at ..... 79 6  
Crystal Multiplier type MI-19468, at R-28/ARC-5 100-150 mc. Receiver Unit at ..... 37 6  
BC-733-D Receiver Unit at ..... 30 0  
Bridge Megger 100 meg. at 1,000 v. at ..... £35 0 0  
Wee Megger 20 meg. at 250 v. at ..... £5 19 6  
Power Unit 247 at ..... 59 6  
Battery Amplifier A.1368 at ..... 11 6  
SCR-720 Blower, with shunt motor at ..... 17 6  
Reflector Aerial (MX-137/A) at ..... 5 6  
As previously advertised, price includes carr.

**NOW READY.** New Illustrated List No. 6 (152 pages). New applicants please send 6d. to cover distribution cost. Please print name and address

**AN/ARC-5 SCR-274-N "COMMAND" RECEIVERS.**  
R-23/ARC-5.....BC-453.....550-190 kcs.  
or  
R-26/ARC-5.....BC-454.....3.0-6.0 mcs.  
or  
R-26/ARC-5.....BC-455.....6.0-9.0 mcs.  
Brand New in maker's carton or Unused, good condition. **CLYDESDALE'S PRICE ONLY. 50/- each. POST PAID**

Or Used, with case dented at 37/6 each post paid.  
Set of Circuits for SCR-274-N at 4/6 or BC-453 or BC-454 or BC-455 Circuits 13/- each, post paid.

**MEDIUM WAVE CONVERSION COIL ASSEMBLIES.**  
Cat. H67 for BC-453 or H68 for BC-454 or H69 for BC-455. **CLYDESDALE'S PRICE ONLY. 10/- each POST PAID**

**Brand New, Ex-U.S. Navy. CONTROL BOX CCT-23155.** Equal to U.S. Army. BC-496-A. For Two Command Receivers, with dual tuning and volume controls, switches, inlet and Outlet points, Black crackle finish box, dimension: 6½ x 4 x 1½ in. **CLYDESDALE'S PRICE ONLY. 10/6 each POST PAID**

**SACHEL, AMERICAN PRODUCT (for WS-19) BRAND NEW.**

A beautifully finished close knit material, lined sachel with shoulder strap and buckled flap. Dim.: Lg. 10in., Wd. 4in., Ht. Bin.

**CLYDESDALE'S PRICE ONLY. 2/6 POST PAID**

**WIRELESS CONTROL UNIT No. 2 (for WS-19) BRAND NEW.**

Containing: 3 wafer 4-pole 2-way and 3 wafer 3 pole 3-way, switches with terminal knobs, red pilot lamp holder, 4-way terminal board, 2/12 way plug receptacles, 2ft. Bin. 5-way cable with 5 point plug. 5½ x 4 x 2½ in. Grey.

**CLYDESDALE'S PRICE ONLY. 4/6 POST PAID**

**CONTROL UNIT No. 1 (for WS-19) BRAND NEW.**

Containing: 2 wafer, 3-pole 3-way, 3/4-way terminal boards, cartridge fuse and holder, 1/12-way plug receptacle, 7ft. 6in. 6-way braided screen rubber covered cable, with flying leads tagged. 2 2ft. 6in. lengths of 5-way flex with 5 point plugs fitted.

**CLYDESDALE'S PRICE ONLY. 3/6 POST PAID**

**JUNCTION DISTN. No. 3 (for WS-19) BRAND NEW.**


Contains: 4/4-way terminal st., and press button 2 2ft. 6in. lengths of 5-way flex with 5 point plugs. 10ft. 9in. 6-way braid screen rubber covered cable with flying leads and tags.

**CLYDESDALE'S PRICE ONLY. 3/6 POST PAID**

**Brand New in Original Packing. Adm Patt. 3685. MAGNETIC KEY.**

2 contacts, 2 way, Heavy duty, on metal base 9½ x 5½ in. packed in a wood case, 11½ x 2½ x 6½ in. Weight, 13½ lbs.

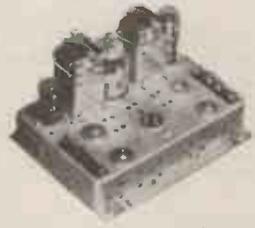**CLYDESDALE'S PRICE ONLY. 7/6 POST PAID**



**Brand New, in Maker's Cartons. BC-456 SPEECH MODULATOR.**

A unit of the SCR-274-N (Command) Equip't. Employing screen modulation, complete with valves 1625, 12J5, and stabilizer VR105/30. Transformer, chokes, etc., (less dynamotor). in metal case 10½ x 7½ x 4½ in.

**CLYDESDALE'S PRICE ONLY. 19/6 each POST PAID**

Order direct from:—  
**CLYDESDALE SUPPLY 2 BRIDGE STREET CO. LTD. GLASGOW - G.5**  
VISIT OUR BRANCHES IN SCOTLAND, ENGLAND AND NORTHERN IRELAND.  
Phone: South 2706/9.



## New Year's Specials

**6 VOLT VIBRATOR PACKS. NEW AND UNUSED.** (Cancelled export order). Output 300 volts 80/100 m/a. With minimum of conversion this unit will operate any normal A/C mains radio from a 6 volt source. Supplied complete with 6 volt vibrator and 6 x 5 rectifier. In black metal case, size: 6in. x 4in. x 5in. **BRITISH MANUFACTURE.**

LASKY'S PRICE 25/-. Postage 1/6 extra.

**PHOTO-ELECTRIC CELLS. TYPE VA28.** Requires 100 volts D.C., or peak A.C. LASKY'S PRICE 12/6. Postage 1/6 extra.

**BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL CARTONS. PACKARD-BELL PRE-AMPLIFIER.**

Supplied complete with circuit. Contains 2 valves: 6SL7 twin triode and 28D7 twin pentode. Also input and output transformers and many other components. Enclosed in lightweight metal case. Size: 4in. x 5in. x 4in. Weight 3 1/2 lbs. LASKY'S PRICE 12/6. Post free.

Supplied with two spare valves. LASKY'S PRICE 19/6.

**THE VIEWMASTER. ALL PARTS AND KITS NOW IN STOCK.**

Envelope with full instructions, 32 page booklet and wiring diagrams for building a full size television receiver. PRICE 5/-. Post free.

A few samples of the kits now in stock:

T.C.C. condenser kit, £8/15/-; Westinghouse rectifier kit, £3/2/6; Bulgin kit 12/6; Plessey kit, 2/6; Whiteley kit, £6/5/-; Belling-Lee kit, 7/6; West: coil kit, £1; 9in. and 12in. CATHODE RAY TUBES. By Mazda, Mullard, G.E.C., Brimar, Ferranti. Prices: 9in., £11/18/10, inc. tax; 12in., £15 2/5, inc. tax.

**ANTENNA REELS. TYPE 1142A. BRAND NEW IN MAKER'S ORIGINAL CARTONS.** Complete with 1/13th h.p. motor, 28 volt input, detachable pulley reel, reduction gearbox, 2 micro-switches. Perfect condition.

LASKY'S PRICE 22/6. Post 1/6 extra.

**MOVING COIL METERS.**

0-500 micro-amps, 2in. round. With fixing ring. LASKY'S PRICE 7/11.

0-1 amp., 2in. round. LASKY'S PRICE 5/-. 0-20 amps., 2in. round. LASKY'S PRICE 5/-. Postage 1/6 extra per meter.

**THE IDEAL UNIT FOR A MINIATURE OSCILLOSCOPE. INDICATOR UNIT TYPE S/LC. No. 5.**

Consists of a chassis, size: 1 1/2in. long, 6 1/2in. wide, 3 1/2in. high, complete with a mounting bracket and holder for a 3in. cathode ray tube (VCR139), also 5 pot/meters and 3 valves: 2 5P61 and 1 P63.

Assorted resistances, condensers, etc., including a block condenser 24 mfd., 650 v. working.

The unit is completely enclosed by a detachable metal cover, with a hinged front glass viewing window for the cathode ray tube. Overall dimensions, with the cover on: 12in. long, 6 1/2in. wide, 9in. high.

LASKY'S PRICE (less the c.r. tube) 7/6. Plus 1/6 postage.

LASKY'S PRICE (less the c.r. tube and valves) 5/-. Plus 1/6 postage.

**SPEAKER SPECIALS.**

6in. Rola m/e. 700 ohms field less o/trans., 9/-; 8in. R. & A.P.M. 3 ohms, 12/-; 8in. R. & A.P.M. with o/trans., 13/6; 10in. Plessey P.M. with o/trans., 21/-.

Postage extra.

**T/V FEEDER CABLE.**

Co-axial, 1/4in. diam. Price 8d. per yard, 7/6 doz. Co-axial, 1/2in. diam. Price 9d. per yard, 8/6 doz. Twin balanced feeder cable. Price 5d. per yard, 4/6 doz.

**FILAMENT TRANSFORMERS.** Primary 200-240 volts 50 c.p.a. tapped. Secondary 4 v. and 6.3 v. at 4 amps. Fully shrouded, vacuum impregnated. Size: 3in. x 2 1/2in. x 2 1/2in. **FULLY GUARANTEED.**

LASKY'S PRICE 15/-. Post 9d. extra.

**MAINS TRANSFORMERS.** 200-250 volts tapped primary.

Type 8B7/1. 330-0-330 volts, 80 m/a; 6.3 v. 3 a; 5 v. 2 a. Price 15/-. post 1/6.

Semi-shrouded, black finish.

Type 8B7/2. 350-0-350 volts 80 m/a; 6.3 v. 3 a; 5 v. 2 a. Price 18/-. post 1/6.

Semi-shrouded, silver finish, mains tapping board.

Other types in stock.

**INDICATOR UNIT TYPE 102.**

Contains 2 cathode ray tubes, 1 6 1/2in. VCR517 and 1 2 1/2in. VCR139. Also the following valves: 1 807; 2 5P61; 4 EA50; 1 6J5; 1 0V67. A 24 volt motor, 0-1 m/a meter.

Dozens of resistances, condensers etc. Size: 12in. x 9in. x 19in.

LASKY'S PRICE 42/-. Carriage 7/6 extra.

**CATHODE RAY TUBES TYPE VCR97. NEW EX-GOVERNMENT. FULLY GUARANTEED. SUPPLIED IN SPRUNG WOOD TRANSIT CASE.**

Characteristics: Heater 4 volts 1 amp. H.T., 2.5 Kv., maximum.

LASKY'S PRICE 35/-. Carriage free.

**VCR97 SCREEN ENLARGER. LATEST TYPE PLASTIC OIL FILLED LENS. TOP QUALITY. LASKY'S PRICE 25/-. Post 1/6 extra.**

**E.H.T. TRANSFORMER FOR THE VCR97 CATHODE RAY TUBE.**

200-250 volts primary. Secondary 2.5 Kv., 4 m/a; 4 v. 1.1 a; 4 v. 1.4 a OT.

LASKY'S PRICE 35/-. Post free.

**E.H.T. SMOOTHING CONDENSERS. 1 mfd. 2.5 Kv. working. LASKY'S PRICE 2/6.**

Post free.

Send a 2d. stamp with your name and address (in block letters please) for a copy of our current stock list of Ex-Government equipment, The Lasky's Radio Bulletin.

## LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(opposite Paddington Hospital)

Telephone: CUNningham 1979

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. half day

## THE FAMOUS 1155 COMMUNICATIONS RECEIVER



Aerial tested. Perfect condition. 10 valve: one 6L63, three ECH35, three KT62, two MHL, one Y63. Five wavebands, 18 to 7.5 mcs, 7.5 to 3 mcs, 1,500-600 kcs, 500-200 kcs, 200-75 kcs. Magic Eye Tuning Indicator. Black crackle cabinet. Easily operated from A.C. mains. Outstanding value. Conversion details, 6d. Price £10/17/6, carriage paid.

**WAVEMETER TYPE W1191A.** Frequency Calibrated Tuning Dial. Micrometer control. 8 Ranges. Crystal check, 1,000 kc. Crystal. Trans/Receiver/CW switch. Output control. On/off switch. Output attenuator. Indicator light. Telephone socket. Accuracy 1 per cent. Operation from 2 v. L.T. and 60 v. H.T. Air Force grey enamelled cabinet with flap lid enclosing full set of calibration charts and instructions. Battery compartment. Measurements, L. 12in., W. 10 1/2in., D. 1 1/2in., weight 30 lbs. Frequency Ranges: 1. 100-220 kcs. 2. 200-400 kcs. 3. 400-800 kcs. 4. .8-1.667 mcs. 5. 1.667-3 mcs. 6. 3-6 mcs. 7. 5-10 mcs. 8. 10-20 mcs. 30 only. In Guaranteed, Brand New Condition £5-19-6 carriage paid.

### BC.306

**Antenna Units. Size 16in. x 8in. x 8in. Black Crackle Cabinet.** Aerial Loading Variometer 3 pole 5 way Ceramic Switch. 4 porcelain lead-through Insulators. Precision slow motion dial. 3 6000 v. 80 mmf. block condensers. Brand New. 10/- each. Carr. 2/6.



**Receiver Type 26/ARCS.** 3-6 mc/s. 6 valves. 28 v. dynamotor fitted. Brand New in Original Sealed Cartons. Price 59/6 each. Carr. 1/4.



**Antenna Reels. Type R1142A.** Motorised 1/13 h.p. Motor. 28 v. 5 amps. 6in. Detachable Pulley. Elaborate Reduction Gearing. Instantaneous positive stop. Brand New in Sealed Cartons, each 30/-. Carr. 1/4.

**PROMPT DELIVERY AND SATISFACTION GUARANTEED AS ALWAYS**

2 1/2d. stamped envelope must accompany all enquiries.

LISTS AVAILABLE

**H.P. RADIO SERVICES LTD.**

Britain's Leading Radio Mail Order House

Estd. 1935

**55 COUNTY ROAD, WALTON, LIVERPOOL, 4**

Tel.: Aintree 1445

Staff Call Signs, G3DGL, G3DLV

EXPORT  
ORDERS  
INVITED

# CHARLES BRITAIN (RADIO) LTD.

11 UPPER SAINT MARTIN'S LANE, LONDON, W.C.2


(Three minutes from Leicester Square Tube Station. Up Cranbourne Street.)

Shop hours 9-6 p.m. daily (9-1 p.m. Thursday). Open all day Saturday.

TEMPle Bar 0545

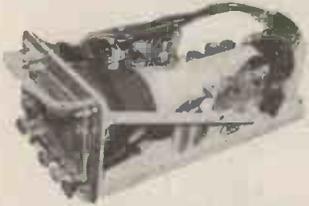**Some New Year Advice — Best Buy at Britain's**

**INDICATOR UNIT 116H.** Brand new and in impeccable condition. Packed in manufacturer's original wooden crates. Actually a more up to date version of the famous 6A. The contents include a VCR97 tube, 4 EF50, 3 EB34 and hosts of useful components associated with a



superb unit of this type. This is the ideal Indicator Unit for TV use, and we unhesitatingly recommend it for this purpose. **ONLY £4/10/-**, plus 7/6 carriage and packing. A limited number now available.

**AMERICAN IFF UNIT.** Supplied complete with 10 International Octal based valves and motor generator, which is easily converted to a motor running from either A.C. or D.C. 230 v. mains. In new condition. **ONLY 27/6** each, carriage paid, while they last.

**SYNCHRONIZER UNIT TYPE BC993.** Brand new American equipment. This outstanding unit is housed in a handsome black crackle finished cabinet and contains the following valves: 2 6SL7, 1 735, 3 6AC7, 1 2X2, 1 6N7, 2 6SN7 and 5 713, together with a 3in. type 3EPI C.R. Tube. Ideal for making a small 'scope. Chassis dimensions: 20 x 10½ x 7½ins. **ONLY 59/6**, carriage paid. A unique opportunity.

**CONTROL UNIT 409.** Perfectly suitable for quick conversion to an audio-amplifier, pulse generator, small transmitter, etc. Includes a Mains Transformer 230 v. 50 cycle input: 300-0-300 at 40 mA.; 6.3 v. at 2 amp., 5 v. at 2 amp. These are service ratings and may be safely exceeded. Valve line-up: 1 5Z4, 1 807, 1 EF50, complete with all smoothing condensers and choke. **ONLY 35/-**, plus 5/- carriage and packing. Super value.

**RECEIVER R1155.** Most renowned and popular of communication receivers. We have available now a limited stock of type 1155B—the model with super slow-motion drive! Complete with all valves and air tested before despatch. In brand new condition... **ONLY £11/19/6**, carriage paid. A New Year Bargain. Submit your order early.

**R.C.A. LOUDSPEAKER, 8in.** Mounted in a handsome metal case, size 1½ x 10½ x 6ins., with sparkling chrome grilles. Brand new and boxed. Offered at a fraction of the original cost. **ONLY 50/-**, post paid.


**CLASS D WAVEMETERS, No. 1 MARK 2.** These instruments are universally known and need no introduction to "Wireless World" readers. Suffice to point out that they are always in demand and enjoy great popularity among "Hams" everywhere. Complete in transit cases with valve, vibrator, spare valve and vibrator. crystal and instruction manual. In brand new condition. **ONLY £3/19/6**, plus 3/6 carriage and packing. Hurry, hurry...

**ADMIRALTY RECEIVER TYPE B36.** A super communications receiver made by Marconi Wireless Telegraph Company. Valve line-up: 2 RF's, freq. changer, 3 IF's, double diode triode, BFO, and output pentode. Freq. Coverage 1-20 Mcs. (15-300 metres) in 4 bands unbroken via turret coil change. Tuning and valve check meter incorporated. Sensitivity for 10 db's signal to noise ratio—better than 1 microvolt! Filament transformer for 230 v. A.C. operation is included, but the H.T. supply is required. Valves required are: International Octal types two KTW61, two X65, three KTW63, one DH63, one KT63. Supplied complete with circuit diagram. NEW and IN UNUSED CONDITION. A chance to buy a £100 receiver for **ONLY £12/10/-** plus 10/- carr. and packing.

**ADMIRALTY TRANSFORMER.** 500-0-500 at 170 mA., 4 v. at 4 a., 230 v. primary 50 cycles. New, boxed and guaranteed. **ONLY 22/6**, carr. paid.

**VCR97 C.R. TUBES.** Brand new. Rigorously tested as to suitability for TV use. **ONLY 35/-**, carriage paid.

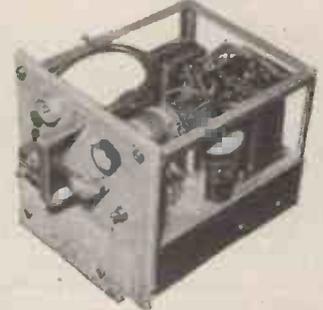**PERFORMANCE METER No. 2.** For A.C. Mains 230 v. operation, and complete with the following valves: 2 EF50, 1 EC52, 1 5Z4G, 1 EA50, and a Y63 (Magic Eye). Brand new condition. Housed in a robust grey steel case, size



9 x 10 x 8ins. Constitutes a most desirable basis for an Amplifier, Measuring Bridge, etc. One of our most popular items to-day. **ONLY £2/5/-**, carriage paid.

**RECEIVER R1355.** The now famous receiver unit specified in the "Inexpensive Television" booklet. Valve line-up: eight 5P61, one VR92, one VU120 and a 5Z4. In new and unused condition but slightly store soiled. Offered at only 59/6 carriage paid. First come first served! Order early.

**A LIMITED NUMBER OF HRO'S ARE AVAILABLE FOR CALLERS.**

## AMERICAN TRANSCIEVERS TYPE 48

Frequency coverage 6-9 Mcs. We are offering the complete station which is all brand new and packed in 6 cartons, comprising the following items: 1 Transmitter/Receiver Type 48 complete in case, and complete with 10 valves and 1 one mega-cycle crystal; 2 satchels; 1 ground aerial, spare valve case complete with 10 spare valves, 1 key assembly, 1 hand microphone, 2 headset, 1 hand generator together with mounting tripod, 2 battery boxes and all necessary interconnecting cables. **£13.19.6** carr paid. (Instruction Manual included.)

**RECEPTION SET BP413.** Made by Philco. 4-valve battery superhet. Valve line-up: freq. changer, IF amplifier, double diode triode and output pentode. Complete with all valves and 5in. P.M. speaker. Provision for phone output incorporated. Cabinet size 10½ x 7½ x 7½in. Controls are volume, on/off switch, and tuning. Freq. coverage: 1.4 to 4 Mcs., 75-222 metres (Trawler, 80 and 160 metres Amateur bands). **ONLY £3/19/6** plus 5/- carriage and packing, 2 v. accumulator and 90 v. H.T. supply required. **SPECIAL CONDENSER OFFER.** .1 mfd. 3 kV. 2/6 each post free.

## TELEVISION WITHOUT TEARS

**OUR KIT OF PARTS** (down to the last nut and bolt) is proving doubly popular because (a) the price of £16/19/6 is amazingly low and (b) the explicit nature of our instructions and easy to follow point-to-point wiring diagrams ensures success for all. Its most convincing feature, however, is that the conversion of ex-government units is **NOT** involved.

The Televisor is built from standard radio components and assembled on two chassis, one for the Vision Receiver, Sound Receiver and Time Base, the other for the Power Supplies. It operates on A.C. Mains 200-250 volts.

If price is the primary consideration we can supply the complete Kit for only £15. In this case the valves and CRT are slightly used but guaranteed perfect. The carriage charge on either Kit is 10/-. Price of the comprehensive point-to-point wiring diagrams and 17 pages of data is 5/- post free. May we urge you to send for these initially. If a Kit is subsequently purchased the 5/- will, of course, be credited.

**PLEASE SPECIFY LONDON OR SUTTON COLDFIELD WHEN ORDERING THIS DATA.**

### NOTE THESE ★ FEATURES.

- ★ NO knowledge of television technique essential.
- ★ ALL parts complete, brand new and of the finest quality.
- ★ ALL parts may be purchased separately.
- ★ ROCK-STEADY picture assured because six EF50 valves are used in the Time Base, and Synch. Separator.
- ★ UNIQUE "AFTER-SALES" SERVICE. Testing and alignment of receivers after completion of assembly undertaken for a nominal sum. **WE GUARANTEE RESULTS.**

Our Televisor is equal to many commercial models. Why not come along and see a demonstration during viewing hours?


## "VIEWMASTER" TELEVISION KIT

ALL SPECIFIED KITS OF COMPONENTS ARE NOW IN STOCK. ENVELOPES WITH FULL CONSTRUCTIONAL DATA 5/- POST FREE. EVERY TECHNICAL ASSISTANCE, INCLUDING ALIGNMENT, ETC., WILL BE GIVEN TO CONSTRUCTORS WHO PURCHASE THEIR KITS FROM US.

## Greetings

HEARTIEST SEASONAL GREETINGS ARE EXTENDED TO OUR MANY FRIENDS EVERYWHERE. SINCERE THANKS FOR YOUR PAST SUPPORT. WE LOOK FORWARD WITH PLEASURE TO FURTHER CO-OPERATION AND A CONTINUANCE INTO THE NEW YEAR OF THE AMICABLE RELATIONS WHICH HAVE PREVAILED IN THE PAST.

# RADIO EXCHANGE CO.

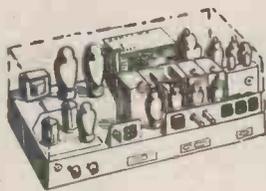

J. C. BRETT-JONES, of Bedford, presents the **WORLD'S CHEAPEST TELEVISION!** The S.L.C. receiver, with two E.F.s, four I.F.s, and all ancillary circuits, PLUS additional stages which will convert for Time Base, is the ideal foundation unit, and with the addition of a mains transformer, VCR97, four condensers, three pots, one resistor and two J50s, can be converted into a self-contained vision receiver, for approximately £6. The receiver only, 30/- carriage paid. Conversion data, 3/- per copy. J50 rectifiers, 2/6 each.

**NOISE LIMITER KITS.** A complete sub-assembly, with all small parts ready to fit in your chassis. The instruction booklet, referring to a U.S.A.A.F. receiver, is sufficiently comprehensive to enable the unit to be fitted in ANY superhet. Price 3/6.

**RECEIVER TYPE 21.** The ex-Army receivers, with six VP23s and three HL33DDs, function as a superhet from 4.2-7.5 mcs. and as a double superhet from 18-31 mcs. They require 120/150v. H.T. and 6v. L.T. Removal of filament dropping resistors will enable the set to be used with a 2v. accumulator. Complete with circuit, 35/-.

**RF25s.** The frequency changer stages of the 1355... they may be used as a very efficient converter for receiving T.V. sound through your domestic all-wave receiver. **ONLY 15/-.**

**WESTERN ELECTRIC** high fidelity wire recorders, with four stage amplifier, detachable head, which contains automatic switches, 40/45 mins. wire, and uses machine-cut gears throughout, are still available. For further details send stamp for leaflet "WR."



**TELEPHONES D MK. V.** Self-contained telephones, with bell, buzzer, and standard P.O. type handset; ideal for intercom purposes, 27/6 each.


**I.F.F. TRANS-RECEIVERS.** One of the best known surplus units... can be converted for 144 mcs or will provide a goldmine of parts. Complete with 13 mains operated (6.3v.) valves, and a 9v. motor generator which can be converted into a mains motor. **OUR PRICE,** with mains into a mains motor, £2/6.

**INDICATOR UNIT 198.** A 9in. short persistence C.R.T., 48F81s, 3EA30s and dozens of pots, resistors, condensers, switches, etc., make this the ideal oscilloscope unit. Brand new, in sealed maker's cartons, £2.

**VELOCITY TYPE SPEAKERS,** really robustly constructed speaker units, which when correctly loaded with a horn, are capable of handling up to 50 watts at high quality. **OUR PRICE,** £1 each.

**AMPLIFIERS 185.** A small chassis with five mains operated valves comprising two audio amplifiers, one EBC33 driven by EF36, two push-pull EL32s driven by EF36. The two units may be "seriesed" to provide a four stage amplifier. Complete with circuit, 17/6.

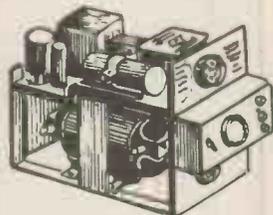**POWER UNIT TYPE 19.** Used with the famous W/S19, this unit consists of a motor generator delivering 540v. at 40 mA., and 275v. at 110 mA., PLUS a vibrator pack (OZ4 rectifier) delivering 275v. Input is 12 or 2 1/2 v., and outputs are fully smoothed. **TO CLEAR, 12/6.**



**RADIO EXCHANGE CO., (W),**

**9 CAULDWELL STREET, BEDFORD.** phone 5569

All goods sold as used unless otherwise stated.

*For Perfect Playing*

## S. G. BROWN Precision SAPPHIRE NEEDLES

The ideal reproducing medium for gramophone records. They give high fidelity reproduction with the minimum wear on the record.

Steel needle after one playing.

There are five types available and they are designed and manufactured to suit all types of pick-ups.

**TYPE NO. 5.** "Miniature Solid Sapphire" Needle for use with light-weight pick-ups.

This S. G. Brown needle gives a definite improvement in fidelity of reproduction due to its homogeneous nature.

**PRICES.** Nos. 1-4 10/1 ea. No. 5 13/4 ea.

Your local dealer can supply. In cases of difficulty, apply direct.

★ ★ ★ ★ ★

The enlarged photographs were taken after laboratory tests using a standard light-weight pick-up with a pressure at needle point of one and one third ounces.

### A "TIP" WORTH TAKING

An interesting and instructive Brochure giving technical details, valuable information and advice on the choice of an S. G. Brown Sapphire Needle or suit your pick-up, will be sent on request. Write Dept. "W".




Sapphire needle after two thousand playings.

Telephone : Watford 7241.

**S.G. Brown, Ltd.**

**SHAKESPEARE STREET, WATFORD, HERTS.**

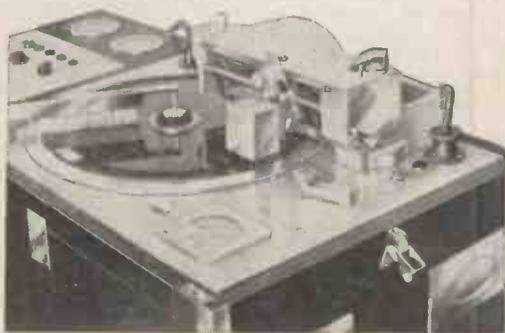

13" PROFESSIONAL

# Brown-E.R.D.

High Fidelity Sound on Disc  
Recorders for every Purpose

Particulars from:—

**S. G. BROWN LTD.**  
SHAKESPEARE STREET,  
WATFORD, HERTS, ENGLAND

Telephone : WATFORD 7241

# RADIO SPARES

## MAINS TRANSFORMER

Half-shrouded drop-through type, 300-0-300 at 80 m.A., 6.3v. at 4 amp, 5v. at 3 amp., primary tapped for 200-240, fitted primary screen and impregnated, 6/6.

## MAINS TRANSFORMER

260-0-260 at 60/70 m.A., 6.3v. at 3 amp, 5v. at 2 amp., otherwise as above, 13/9.

## TUNING CONDENSERS

2-gang .0005 long spindle, 3/6  
2-gang midget .00035 with dust cover and trimmers, 6/6.

## ELECTROLYTIC CONDENSERS

8 mfd. 350v. ....	1/6
16 mfd. 350v. ....	1/11
25 x 25 mfd. 200v. ....	3/11
8 mfd. 150v. ....	1/3
25 mfd. 25v. ....	1/-
25 mfd. 50v. ....	1/6
50 mfd. 12v. ....	10d.
10 mfd. 25v. ....	10d.
2 mfd. 450v. ....	1/-
4 mfd. 450v. ....	1/3
8 mfd. 450v. ....	1/11
16 mfd. 450v. ....	2/8
8 x 8 mfd. 450v. ....	3/4
8 x 16 mfd. 450v. ....	3/4
16 x 16 mfd. 450v. ....	3/9
16 x 8 x 24 mfd. ....	4/2
8 mfd. 500v. BR. 850 ...	2/6
16 mfd. 500v. BR. 1650 ...	3/6

## P.M. SPEAKERS

Size	with trans.	less trans.
2 1/2 in.	—	10/6
3 1/2 in.	—	8/6
5 1/2 in.	12/3	10/6
6 1/2 in.	12/6	10/6
8 in.	14/6	12/6
10 in.	21/6	17/6
12 in.	—	39/6

When ordering speakers add 1/- each extra for insurance.

## MOVING COIL METERS

0-1 mA., 2 1/2 in., 12/6 2 in., 8/6.  
5-0-5 mA., 2 1/2 in., 10/6 0-500 mA.  
2 1/2 in., 15/-.

## FILAMENT TRANSFORMERS

6.3v. 1 1/2 amp., 6/-.

## I.F. TRANSFORMERS

465 kc/s, iron cored, 6/9 pair.

## OUTPUT TRANSFORMERS

Standard pentode matching midget, 3/6 small, 3/- standard 3/3. Push-pull matching, 4/-.  
Multi-ratio, 4/6.

## 6 1/2 in. ENERGISED SPEAKER

700 ohm field with output transformer, "ROLA," 11/6.

## IMPORTANT

Postage must be included orders up to 10/-, 1/-, over 10/-, 1/6. £3 and over post free unless otherwise stated.

# PARTS FOR MAGNETIC T.V.



## FRAME AND LINE COIL ASSEMBLY.

Perfectly made by a very famous maker, for standard type magnetic tubes, 9in., 10in., 12in. or 15in., we have a limited number only, the price is 16/6, and cannot be repeated once these are cleared, so please act quickly.

**PERMANENT MAGNETIC FOCUSING UNITS.** No current drain—for all makes of tubes—patented method of adjusting the gap, giving really clean pictures and even focus of whole of the tube free. Price 16/6 each.

**P.M. FOCUSING for clear pictures**

**R.F. E.H.T. Non-Lethal**

R.F. E.H.T. We were so pleased with the quality of this unit that we have taken up the entire output of the manufacturer, the voltage can be adjusted to make it suitable for working 9in., 12in. or 15in. tubes, the unique design and vacuum impregnation combine to give a trouble-free unit which will give years of satisfactory service, and, of course, the big point about the R.F. E.H.T. is that it is not lethal, the size is only 4 1/2 x 3 1/2 x 4 in., price, complete ready to operate, 65/-.


**£16 FOR A MAGNETIC TELEVISOR** (and H.P. terms if you wish), this we think you will agree a remarkable low price, even though the tube is not included, but the quality of the picture has not suffered, this was demonstrated to thousands of people at Radiolympia. We will demonstrate to you if you call. Full constructional data for novice or expert, 5/-.  
Explanatory leaflet free.



## MISCELLANEOUS ITEMS


Blocking Osc. Transformer, 6/6. 9ft. dural. tube for aerial, 4/6.  
.1 mfd. 2.5 kV., 2/6. .1 mfd. 5 kV., 4/9. .02 8 kV., 3/9. .1 7 kV., 13/6. Vision Receiver strip (type 194), 45/-.  
Varley E.H.T. Transformer, 4 kV., 67/6. 2.5 kV., 27/6. B7G Valve Holder, 1/3. EF50 Valve Holder, 6d. Chokes, 200 mA. 10 henry, 10/-.  
200 mA. 3 henry, 6/-.  
80 mA. 10 henry, 4/6. 80 ohm feeder, thin, 10d. per yd.; thick, 8d. per yd. Plastic 8 kV. Sleeveing, 3/- doz. yds.

## OSCILLOSCOPE PARTS

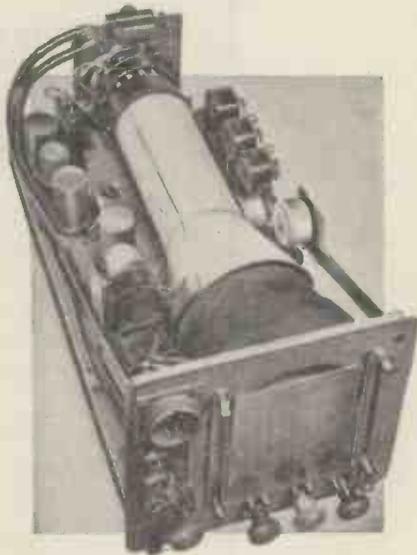

**TYPE 6 INDICATOR.** As specified for the "Wireless World" oscilloscope (reprint of data 9d.). Also for the "Inexpensive Television" (booklet 1/6), and the Mark I Televisor (constructors envelope, 2/6). These indicators are brand new, packed and sealed in manufacturer's original crates, they contain VCR97 Cathode Ray Tube, 4 EF50 valves, 3 other valves, and hundreds of useful components, including wire wound pots. Price is only £4/10/-, plus carriage and packing, 7/6.

# SPECIALS

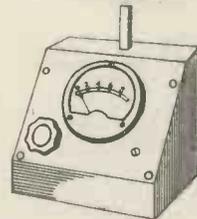

## SHORTED TURNS COIL TESTER

You know that it is almost an impossibility to test for shorted turns in I.F. Transformers, Coils, L.T. Transformers, etc., with an ordinary ohmmeter. Our mains operated shorted turns coil tester will reveal these faults in a second. For one month only we are offering these to you at the remarkably low price of £5/10/- each.

## THE "SPEE-DEE" SIGNAL TRACER

A small metal case a few inches square, a flex terminating in a probe, a twin lead for connecting to either A.C. or D.C. mains, no switching, no tuning controls, and there you have the "SPEE-DEE" Signal Tracer. H.F., I.F., or L.F. checks—makes no difference: note frequency change is automatic. The fault is in the no-note stage. Yes it's as simple as that. Price, with directions, £4. leaflet free.

## ELECTRIC HEATERS



Heavy cast framework totally encloses the elements, so these are 100% safe even in confined spaces,

just right for your radio den, garage, office, shop, etc. 900 watt (general) model, 19/6, plus 5/6d. carriage. Other models available are: 750 watt, 500 watt, 250 watt, all these are 23/6 each, plus 4/6 each carriage. The 250 watt model used as a foot-warmer keeps legs and body warm for less than a farthing per hour.



## HOUSE TELEPHONES

Suitable for intercommunication between offices, workshops, stores, garages, big houses, kitchens, etc. Each station consists of normal size Bakelite handsets and desk or wall mounting cabinet with built-in selector switch, buzzer and push. All stations can communicate with one another independently. Each installation is absolutely complete and internally wired. 3-station installation complete with 50 yards 5-core cable £6/10/-.  
4-station installation, complete with 50 yards 6-core cable, £8/10/-.  
2-station installation, complete with 25 yards 4-core cable, £3/17/6.



**PRECISION EQUIPMENT** (2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDLESEX

# LAWRENCES

## NEW RADAR EQUIPMENT

### MODEL VG RADAR INDICATING EQUIPMENT, TYPE CG-55AEB.

Designed and produced by the General Electric Co., U.S.A., for installation in ships or shore stations. This Projection Type Plan Position Repeater performs a duty similar to the conventional P.P.I., except that the pattern is optically projected on to a large flat horizontal surface, instead of being observed directly on a cathode ray tube face. The complete unit is approximately the size of a desk, 35in. high, with the viewing screen occupying half of the top surface, and is operated as a plotting table, on which the actual map-in-motion is portrayed. Navigational calculations are made directly on the paper viewing screen, which can be replaced at will from the built-in 30 yard roll supply.

The full screen may be employed to map an area of 4, 10, 20, 80, or 200 mile radius, the choice of range being made by a range selector switch. Electronically generated range marks divide the screen into concentric rings for ranging purposes. In addition, two bearing scales are projected on to the screen, one being fixed to present true or relative bearing, the other rotating to present heading. The radar pattern is therefore far more significant, because it can be observed simultaneously with the pattern of actual bearing.

The equipment is designed for operation with any radar system, of repetition rates of from 60 to 1,000 per second, and only very limited arrangements are necessary to provide the video, trigger and synchro inputs.

#### BRIEF TECHNICAL SPECIFICATION

**Power requirements:** 115 v. A.C. Single phase, or 230 v. with auxiliary transformer. Total consumption 1765 watts.

**Input requirements:** Trigger voltage 5-40 volts peak. Video voltage 3 volts peak max.

**Ambient Temperature Limits of Operation:** 0°C to +50°C.

**Screen Diameter:** 25½in.

**Picture Diameter:** 24in.

**Image Visibility:** Image on Projection Screen may be observed in the presence of approx. 1 foot candle of indirect lighting.

**Optical System:** Highest grade components by Bausch & Lomb.

**Range Accuracy:** ±1% of total designated range.

**Bearing Accuracy:** Within .75 degrees.

**Overall Dimensions:** 59in. x 34in. x 35in.

**Weight unpacked:** 1,000 lb.

The exceptional quality of construction, together with the numerous operational advantages, are several of many features which make this advanced equipment of outstanding interest in the field of Radar Engineering.

**MODEL VE RADAR INDICATING EQUIPMENT, TYPE CAY-55ADV.** Manufactured by The Westinghouse Mfg. Co., U.S.A., for installation in ships or shore stations. A Plan Position Indicator Repeater of conventional type, employing a seven inch electro-magnetic cathode ray tube. Instrument is fully enclosed in console type housing.

#### BRIEF TECHNICAL SPECIFICATION.

**Power requirements:** 115 v. A.C. Single phase, or 230 v. with auxiliary transformer.

**Range Calibrations:** Electronic, with switched selection of ranges 4, 20, 80, 200 miles radius.

**Overall Dimensions:** 13in. x 24in. x 26in.

Full technical details of the above equipments available on request from:

**LAWRENCES, 61 BYROM ST., LIVERPOOL.3**


Phone: CENTral 4430

# CONSISTENTLY

## Accurate

# PULLIN

## INDUSTRIAL SWITCHBOARD INSTRUMENTS

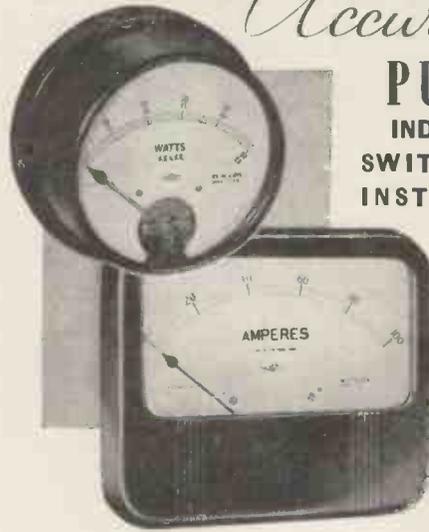

PULLIN Type S Industrial Switchboard Instruments are completely new in design. The 4" and 6" Round Projecting Type case is of pressed steel, has a full open dial, and can be converted easily to flush type by using a separate fitting. The 6" dial rectangular pattern has a clear open scale. All

types are available in Moving Iron, Moving Coil or Dynamometer Pattern.



We can give early deliveries—write for details

Address all enquiries to

### MEASURING INSTRUMENTS (PULLIN) LTD

Dept. J, Electr. Works, Winchester Street, London, W.3

Telephone: ACOrn 46513 and 4995.

## RECORD

## PLAYERS

by

### Richard Allan



C.D.M. With variable speed regulator, automatic start and stop, 12" cloth covered turntable. Price £15 : 1 : 0  
Tax Paid

R.D.M. (illus.) This powerful rim driven model is fitted with fool-proof start and stop mechanism beneath the unit plate. Price £12 : 0 : 8  
Tax Paid

C.D.U.M. Universal model operating on A.C. or D.C. Current. Price £20 : 15 : 8  
Tax Paid

FROM ALL  
GOOD DEALERS

*There is a most comprehensive range from  
which to choose*

## RICHARD ALLAN RADIO LTD.

BAFFLETTE HOUSE · BATLEY · YORKS

Makers of the famous BAFFLETTE Extension Speakers

# UNIVERSITY RADIO, LIMITED

## Offer Guaranteed Used Equipment at Attractive Prices

Decca Deccaloon, three only, in perfect condition and working order. As new..... £23 10 0

Collaro Record-Player Unit, centre drive, as new, each..... £6 5 0

M.S.S. Disc Recorder Unit, 1948 model, complete less amplifier. As new. Unused. Two only..... £35 0 0

B.S.R. Ampligram, model AG4, as new..... £22 0 0

Eddystone 640, with speaker. As new..... £22 10 0

Hambander, as new..... £13 0 0

BC348, converted for A.C. 200-250 volts. Perfect..... £15 0 0

MCR-1, complete with power-pack, phones, coils, etc. As new..... £8 0 0

Taylor Model 20A, circuit analyser. As new..... £11 0 0

Labgear Electronic Fault-Tracer, 1948 model. As new..... £18 0 0

Taylor 65B Signal Generator. As new..... £11 0 0

Hallcrafters Panoramic Adaptor, model SP44, 110 volts A.C. As new..... £22 10 0

Marconi 1949 Model Television cost £86/0/0, model No. VT50A. As new. Our price... £50 10 0

Rotary Converter, 12 volt D.C. to 230 volts A.C., 50 cycles, one phase, 100 watts. One only..... £5 0 0

Technifon Recording Unit, complete less amplifier, as new..... £22 0 0

Lustraphone Moving Coil Microphones, three only left. Each..... £3 10 0

S.T.C. Ball Mikes, the best m/c. mikes made. Six only left. New, ex-W.D..... £5 5 0

Two Only S.T.C. Ball and Biscuit Mikes, each..... £8 0 0

Connoisseur Pick-up, with transformer, as new..... £2 5 0

Decca FFRR Pick-up, high impedance. As new..... £2 10 0

Record Minor Meggers, 500 volt, in new condition, each... £7 10 0

Portogram Junior 8 watt A.C./D.C. Record-Player, with built-in amplifier and speaker. As new, in portable case..... £18 0 0

Sangamo Weston 20000 O.P.V., A.C./D.C. Test Meter, as new..... £16 10 0

M.S.S. Cutting-Heads, perfect, as new..... £8 10 0

Garrard RC60 Mixer-Changer, in perfect condition and Working order..... £12 10 0

Spring Drive Recording Motor, perfect, in portable case..... £4 10 0

Morrisflex Unit, with accessories, cost £36/0/0, in perfect condition. Our price..... £22 0 0

Vitavox H-F Unit, 6 cell, complete with 10 watt unit..... £9 0 0

Marconi Signal Generator, type 51YE, in perfect condition £25 0 0

Pye Output Power Meter, 50-5,000 milliwatts, as new..... £7 15 0

Taylor Model 30 'Scope, as new..... £18 10 0

Minniphone Intercommunication (Office) Unit, combined with four extensions, radio set, and car radio adaptor, as new, unused. One only..... £24 0 0

### WE NEED GOOD USED EQUIPMENT URGENTLY. PLEASE SEND, BRING OR PHONE FOR OFFER

B.I. A.C. Check-Meters, 230-240 volts A.C., one phase, 50 cycles, 12 only. In perfect condition. Each..... 17 6

Cambridge Unipivot Galvanometer, latest model, pattern L, 0-120 millivolts, in wood case..... £8 0 0

Portable Chrome Mike-Stands, brand new, 12 only left, each... £1 11 10

B.P.L. Signal Generator, as new. Cost £21/0/0. Two only. Each..... £1 10 0

1154 Transmitter, complete with valves..... £9 0 0

Evershed's 500 volt Megger, in aluminium case. Perfect working order..... £9 10 0

Radio and Transformer Services Audio Oscillator, complete in perfect condition, almost new. A.C. 200-250 volts..... £13 10 0

Vortexion 15 watt Amplifier Chassis, complete with all valves. Perfect..... £10 10 0

AR88 LF, in perfect working order, and perfect condition, complete with all valves..... £37 10 0

AR88-F, Rack model. In exceptionally good condition, complete with all valves..... £40 0 0

Evershed's 500 Volt Wee Megger, in leather case. As new..... £9 0 0

Valradio D.C.-A.C. Vibrator Converter, 200 watts. In new condition and perfect working order..... £9 0 0

M.S.S. (1946) Recording Unit, with play-back pick-up. Less amplifier. Perfect. In portable case..... £25 0 0

Sound Sales Amplifier Chassis, complete with bass and treble controls, mike and 'gram inputs and valves. Perfect..... £14 0 0

Taylor, Model 313C, Capacity and Inductance Adaptor, as new..... £2 17 6

Service Co. Capacity and Resistance Bridge, as new... £5 10 0

Taylor Model 45A Valve Tester, as new..... £12 10 0

Evershed's Bridge Megger, 500 volt. As new, in leather case... £20 0 0

Rotary Converter E.D.C. with filter unit, 24 volts D.C. to 230 volts A.C., 300 watts..... £12 10 0

¼ (One Quarter) h.p. Motors, single phase, 1248 R.P.M., 220-250 volts A.C., various first-class makes. New. Each..... £4 10 0

Evershed's Bridge Megger, 500 volts, with built-in resistance box. Perfect condition..... £15 10 0

Another, as new..... £20 0 0

Goodmans 12in. P.M. Speaker. As new..... £4 10 0

Goodmans Axiom 12, as new £5 17 6

Goodmans Axiom 22, as new £9 10 0

Vitavox 12in. P.M. Speaker. As new..... £4 0 0

Sound Sales Cabinet Speaker, 1949 model. Perfect condition £9 0 0

Sound Sales Tuner Unit, perfect, complete with valves. 1949 model..... £11 0 0

Phillip's PCR-1 Communication Receiver, with valves and power pack. Perfect..... £14 10 0

Two only No. 19 Sets, Trans. Rec. Complete with power-pack, etc. Perfect. Each..... £19 10 0

R.C.A. Oscilloscope, two only, as new..... £22 0 0

Sphere Signal Generator, type 75, model I. As new..... £9 0 0

Avo 1948 Model Signal Generator. As new..... £10 10 0

Avo Valve-Testers (1948), with roller panel. As new..... £11 10 0

Avo Capacity and Resistance Bridge, as new..... £7 0 0

Thrush Capacity and Resistance Bridge. As new..... £7 15 0

E.D.C. Rotary Convertors, 220-240 volts D.C. to 230 volts A.C., 50 cycles, single phase, 120 watts, with radio filter unit..... £10 10 0

As above, 180 watts..... £12 10 0

As above, 250 watts..... £15 0 0

M.S.S. Play-back Pick-up, with transformer. Perfect. As new £3 10 0

Charles Amplifiers, used, but perfect, with valves. Selling at half price. Complete with valves.....

WE SUPPLY THE LEADING FIRMS IN THE INDUSTRY WITH EQUIPMENT. ANY TIME YOU ARE IN THE DISTRICT PLEASE PAY US A VISIT. WE MAY HAVE JUST THE EQUIPMENT YOU ARE LOOKING FOR.

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE PAID.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

'Phone GERrard 4447 and 8592.

Hours 9 to 6.

Thursdays 9 to 1.



Maximum sensitivity with uniform frequency response from a more compact speaker, appreciably reduced in weight—that is what Rola technicians have achieved with the new G.12. Special features include dust-proof suspension completely protecting coil and magnet gap and the powerful Alcomax II magnet. Write for details and also for particulars of Rola 3" and 4" P.M. models, dust-proofed and equipped with Alcomax II magnets.

**best  
of the  
BIG  
speakers**

BRITISH ROLA LTD. · FERRY WORKS · SUMMER ROAD · THAMES DITTON · SURREY  
Telephone : EMBERBROOK 3402 (5 lines)

## COIL PACKS

Improved performance at lower price with the new F. P. series. 3 and 5 waveband models with or without R. F. stage.

## VALVE TESTER

Type 218 for the Laboratory and Service Engineer

Full particulars from:—

**H. C. ATKINS  
LABORATORIES**

32 CUMBERLAND RD., KEW GARDENS.  
Telephone—RICHmond 2950.

## G2AK **IMPORTANT** G2AK ANNOUNCEMENT

We have made a successful purchase of the extensive stocks of Messrs. Radiomart, and have taken over the Central retail premises at 110 Dale End. We intend to offer these stocks at really competitive prices and to give a service to our mail order customers that is *second to none*.

*From the date of this announcement*

ALL CALLERS TO: 110 DALE END, BIRMINGHAM  
MAIL ORDERS TO:  
102 HOLLOWAY HEAD, BIRMINGHAM  
Telephone: Midland 3254

## *This Month's Bargains*

**RCA SPEECH AMPLIFIERS** Complete with 7 valves (4-6J7, 2-6L6, 1-5U4G) 15 watts output. 15 and 500 OHMS output. Standard 230 V. input. Brand New.  
£15 Plus 10/- Packing and carriage.

**SPECIAL FOR AR88 USERS.** AR88 Cabinets finished in Black crackle. In strict rotation £3-17-6 carr. paid.

**AR88 MATCHING SPEAKERS** 2.5 OHMS. Black crackle case £3-15-0 carr. paid.

**AR88 SPARE CRYSTALS** For D Model only 455 KC  
15/- each.

Carriage paid on all orders over £1 except where stated.  
Please include carriage on orders under £1.

**CHAS. H. YOUNG, G2AK**  
102 HOLLOWAY HEAD, BIRMINGHAM

# MINIATURE VITREOUS ENAMELLED RESISTOR

TYPE M.V.1

**RATING** 3 watts for 250°C rise.

**RESISTANCE RANGE** 1-4700 ohms.

Full rated watts over the whole resistance range

**DIMENSIONS** - 15/32" × 13/64"

Agents in Belgium: Monsieur Paul Groeninckx, 43 Avenue Jean Stabbaerts, Bruxelles.



Actual size of resistor

TYPE APPROVED



KINGSTHORPE, NORTHAMPTON.

## The R. H. QUALTAPE MAGNETIC RECORDER KIT OF PARTS

**EASY TO ASSEMBLE**

**EASY TO OPERATE**



- ★ LOW COST
- ★ EASY TO PLAY
- ★ COMPACT
- ★ PRECISION MADE
- ★ CAPSTAN DRIVE

The ideal Tape Recorder for ham use. For home — office — schools — hospitals — Board Meetings, etc. Use it to improve musical and vocal talent — provide synchronised speech and music for home cine — all these and many more with the Qualtape.

TOP QUALITY PLASTIC TAPE (not included in kit) 25/- for 1200 ft. reels

Complete Kit of Parts  
£12.10.0.

**R. H. ELECTRONIC SERVICE** 93 BUTTON LANE SHEFFIELD Tel: 21690

# Henry's

RADIO COMPONENTS  
ELECTRONIC  
& TELEPHONE  
EQUIPMENT

**A SIGNAL TRACE** at minimum cost. An easy-to-build unit that can be used for R.F., I.F. and Audio signal tracing, without any switching or tuning. Highly sensitive, easy-to-build, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain, 3-stage resistance-coupled audio frequency amplifier, with a 6-inch speaker in the Output of the Power Amplifier stage. We shall be pleased to supply a complete kit for the construction of the above, right down to the last nut and bolt, for the low price of **£3/19/6**. Concise instructions and circuits are supplied. If preferred, circuit and instructions only can be supplied for 1/6 post free. All items may be purchased separately. This is a highly efficient instrument, and a **MUST** for every radio man.

**P.M. SPEAKERS.** All are by leading manufacturers. Less Transformer—3in. 15/-; 3in. 9/-; 5in. 10/-; 6in. 12/6; 8in. 15/-; 10in. 23/6; 12in. 37/6. With Transformer: 5in. 12/6; 6in. 15/-; 8in. 17/6; 10in. 25/6.

**BARGAIN PARCEL FOR MIDGET CONSTRUCTORS.** Comprising IT4, IS5, IS6 and IS4, 1.4 v. battery valves. Four ceramic valve-holders for same. One pair midget "Wearite" I.F. Transformers, Type M400B. One 3in. P.M. Speaker. One midget two-gang .000375 mfd. with trimmers, vanes covered with perspex. All items absolutely brand new. The whole 57/6 only.

**E.H.T. TRANSFORMERS.** Output 2,500 v. 5 m.a., 4 v. 1.1 amps. 2-0-2 v. 2 a. (for VOR97), 35/- only. Output 3,250 v. 5 m.a., 6.3 v. 1 a., 2-0-2 v. 2a. (for 6CPI) 39/6. Output 4,000 v. 10 m.a., 2-0-2 v. 2 a., 48/- only. Output 5,000 v. 10 m.a. 2-0-2 v., only 60/- only. All input 200/250 v. and fully guaranteed.

**R.1355 MAINS TRANSFORMER.** 200/250 v. input. Outputs 250-0-250, at 80 m/a., 6.3 v. at 3 a. Fully shrouded top chassis mounting and guaranteed 100%. Only 28/6.

**MINIATURE MAINS TRANSFORMER.** 250-0-250, 60 m/a., 6 v. 3 a., 5 v. 2 a., fully shrouded, well finished, size 3in. x 3in. x 2in. Price 21/-.

**MAINS TRANSFORMER.** A special purchase from a leading manufacturer enables us to offer the following:—250-0-250, 70 m/a., 6 v. 2 a., 5 v. 2a., half-shrouded, drop-through type, with voltage adjuster panel. Absolutely brand new and guaranteed, 15/- only, plus 9d. post.

**BCA 931A PHOTO-ELECTRIC CELL AND MULTIPLIER.** For facsimile transmission, flying spot telecine transmission and research involving low light-levels 9-stage multiplier. Brand new and guaranteed. Only 30/-. Included free is a data sheet, plus details of the resistor network. Valve-holder for this cell can now be supplied at 4/6.

**TX VALVES.** Westinghouse 813 at 50/-. 832 at 20/-. 866A at 15/-. Klystron 723A/B at 82/6. 3E29 (829B) at 59/6. All brand new and boxed.

**"SEGIC" INSTANTANEOUS ELECTRIC SOLDERING GUN.** Light weight, balanced grip, smooth trigger. Low voltage bit, insulated from the earthed casing, shock proof. Saves time and money in any workshop. Weight, 30 oz. Consumption, 100 watts (intermittent), 220/250 v. A.C. only. Price (including 6 bits), 63/-. Fully guaranteed for 12 months.

**RELAY ASSEMBLY.** Comprising 28 v. 1,000 ohm S.P.C.O. miniature relay and 8 mfd. 450 v. tubular condenser. 2/10 post free.

**OSMOR MIDGET "Q" COIL PACKS.** Size 3in. x 2 1/2 in. x 1 1/2 in. Amazing performance. Polystyrene formers with adjustable iron cores. One-hic fixing, only five connections. Factory aligned complete with full receiver circuits and instructions. 8'het for 465 kc/s, 33/- only. L.M.S. also for TRF operation M. and L. W., 30/-. We can now offer the latest "Q" pack for 8'het battery operation. Complete with circuits incorporating either 1A7 or IT4 series. Valves. This pack is supplied with ready-wound main aerial. Price 37/6.

Please note that separate E.P. Stage, for addition to the above Mains Superhet Coil Pack, can now be supplied at 15/- only. Complete with all necessary easy-to-follow instructions.

**TRIMMER KIT, "Quadrad."** An essential to every radio man. This famous kit can be supplied by us at 30/- only (list price 45/-). Comprising: 1, 2, 4, 5, 6, 8 BA box-spanners, 5 screwdriver trimmers (vertical and horizontal), 4 spanners, vane-setter, and thickness gauge. Attractively finished in white ivory. All neatly laid out in black crackle box. An absolute bargain!

**VIEW-MASTER.** This now well-known T.V. kit can be supplied by us at list prices as under. Constructor's Envelope, containing eight full-size assembly and wiring diagrams, and 32-page illustrated booklet packed with technical information. All required components are standard. Envelope price, 5/-, post free. Component kits are available as under: W.B. Chassis and Speaker kit, including choke and transformer, etc., 28 5s. 0d. T.C.G. Complete Condenser Kit, £8 15s. 0d. Westinghouse Rectifier Kit, 23 2s. 6d. Morganite Resistor Kit, £1 6s. 9d. Plessey Focus, Scanning Coils, etc., etc., Kit, £5 12s. 6d. Colvern W/W Potentiometer Kit, 19/3. Bulgin panel and switch Kit, 12/6. Wearite Coils and Choke Kit, £1 2s. 0d.

All required valves are in stock, and can be supplied. Cabinets will shortly be made available. Either 9in. or 12in. Tubes can be used, and all suggested types are in stock. All orders executed in strict rotation.

Send stamp for current Component List. Probably the most comprehensive in the trade.

**5, HARROW ROAD, LONDON, W.2**  
**PADDINGTON 1008/9**

## MIDLAND INSTRUMENT CO.

FOR GOVT. SURPLUS STOCK, ETC.

**HOOVER INDUCTION MOTORS, TYPE S.P.201,** shaded pole, 200/250 v. 50 cycle, A.C. mains only, approx. 4,000 watts, 1,800 r.p.m., fitted 1in. long 1in. dia. shaft, motor size 3 1/2 in. long, 2 1/2 in. dia., has 101 uses, brand new boxed, 20/-, post 9d. **MASTER CONTACTORS,** a high grade clockwork movement, provides 2 impulses per sec. In smart wood or bakelite cases, brand new, 10/-, post 1/-. **REMOTE CONTACTORS** (for use with above), requires 120 impulses for 1 rev. of pointer setting device and switch, brand new, 5/-, post 9d. **BATTERIES,** sealed and unused, guaranteed by us, first grade 1948 manufacture, 150 v. H.T., plus 3 v. L.T., size 6 1/2 in. x 5 1/2 in. x 2 1/2 in., 6/-, post 1/-. **24 v. H.T.,** plus 1.5 v. L.T., size 6 1/2 in. x 5 1/2 in. x 2 1/2 in., 5/-, post 9d. **SELECTOR SWITCHES,** 12 or 24 v. D.C., will motor and stop at any of 4 Yakley switch positions, new, boxed, 3/6, post 9d. **MAINS MOTORS,** one end fitted fan blower, the other fitted reduction gear-box with 3 final drives of approx. 5, 25 and 125 r.p.m., fan blower can be removed to expose initial drive of approx. 3,000 r.p.m., exceptional bargain, new, 35/-, post 1/4. **ACCUM ULTRATOR CUT-OUTS, TYPE D,** 5c/1615 12 v. 60 amp., also 5c/1616 24 v. 60 amp., new, unused, 7/6 each, post 9d. **ELECTRIC MOTORS,** easily one of the finest of ex-Govt. motors, 24 v. D.C. 1/10th h.p., speed 3,000 r.p.m., fitted 5/16in. shaft, motor size 6 1/2 in. long 3 1/2 in. dia., standard base mg., easily worth 60/-, our price 20/-, post 1/4. **U.S.A. FLEXIBLE DRIVES,** for light power transmission or remote control, outer spiral casing 1/2 in. dia., end caps for screw fitting, 4 sizes, 3ft. 2/6, 6ft. 3/6, 8ft. 4/6, 12ft. 5/6 all brand new, post 9d. **CAMERA CONTROLS, TYPE 35 12 VOLT,** includes motor geared to escapement, dial setting 1 to 50 sec. timing device, exposure counter 1 to 125 indicator lamps, etc., in smart metal cases, and wood transit case, an exceptionally fine instrument, brand new, 20/-, post 1/4. **OBSERVERS REPEATER COMPASSES,** contains a repeater motor with reduction gearing, will operate from 30 v. A.C., requires 8/10 mfd. condens. to self-start, new, 3/6, post 9d. **EK-U.S.A. UNITS,** contains 12 valves, 6SH7 (3), 6E6 (3), 7193 (3), also 3 relays, various coils, chokes, v-control and over 80 resistors and cond., chassis mounted with lowered cover, size 12 1/2 in. x 8 in. x 6 in., new condition, 15/-, post 1/4. **MAGNETIC COMPASSES, TYPE P-8,** alcohol fluxgate, cardinal points and cross wires luminous, 5 1/2 in. dia., 3in. deep, brand new in wood carrying cases, 10/-, post 1/-. **MOVING COIL HEADPHONES,** with moving coil microphone fitted with, brand new, boxed, 10/-, post 9d. **SERIES WOUND MOTORS,** 12 v. 20 amp. D.C., 1/2 h.p., 4-brush type, fitted 1/2 in. dia. shaft, motor size 7in. long, 4in. dia., weight 9 lbs., an ideal motor for an electrically propelled vehicle, superior job, new, unused, 15/-, post 1/4. **INTERPHONE AMPLIFIERS, TYPE BC-21-D,** complete with 2 6C5 valves, input and output transformers, switch, etc., operates from 6 or 12 v. L.T., 220, 290 or 350 v. H.T., in smart metal cases, 3in. x 4 1/2 in. x 2 1/2 in., with circuit, brand new, boxed, 12/6, post 9d. **ROLLS PEARCE COMPRESSORS,** piston type, develops 450 lb. sq. in., at 1,200 r.p.m., strokes 1in. and 3/4 in. bore 1 in. and 1 1/4 in., splined shaft fitting, superior manufacture, brand new, boxed, 25/-, post 1/4. **ENGINE DRIVEN GENERATORS (dynamos),** tandem type, generates 24 v. 500 watts, D.C. and 500 watts A.C. at 1,300/2,600 cycles, fitted 1in. splined shaft, new in wood cases, bargain, 20/-, carriage 7/6. **TELEPHONE STANDS,** consists of handset rest, hand generator, A.C. bell, induction coil and condens., length of 6-way cord and junction box, new, unused, 5/-, post 1/4; brand new telephone handsets, fitted 4-way cord to fit these stands, 10/-, post 9d. **VARIABLE RESISTORS,** wire wound on vitreous steel, carbon brush helical control traverse, 5.7 ohm 8 amp., superior make, new, unused, 12/6, post 1/4. **BOOKS BY MODERN UNIVERSITY PRESS:** "An Introduction to Frequency Modulation," 1/-, "Basic Radar," 1/-, "Fundamentals of Electricity," 1/-, "Servicing the Modern Radio Receiver," 1/-, "Electrical Wiring Installation," 1/-, All post 3d.; the 5 books sent for 4/-, post 6d. Also hundreds of other items; send 2d. and s.a.e. for current lists. Our C.O.D. service is cancelled for the time being.

**MOORPOOL CIRCLE, BIRMINGHAM, 17**

Tel. HARBorne 1308 or 1664

## G. W. SMITH & CO. (RADIO) LTD.

### Special Offer

**Combined Television E.H.T. Power Packs.** Ex-W.D. Type 285, A.C. input 230 volt 50 cycles. Output 2,500 volt, 10 m/a. 500 x 500 volt, 250 m/a. 6.3 volt, 15 amp. Limited number only. Complete with all valves. **£5/19/6.**

**Trouble Free Oil Filled Mansbridge Type Television E.H.T. Condensers.** .1, 3,000 volt, 2/- each. .1, 4,000 volt, 3/- each. .1, 5,000 volt, 3/3 each.

**Television Coil Formers.** Slugged with cores, 1/2 x 1 single hole fixing in "Polystyrene." 4/9 per dozen.

**Special offer Electrolytic Condensers.** Brand New 16 x 16 MFD, 350 volt working, 1/6 EACH. Callers only.

OPEN ALL DAY SATURDAY.

**3 LISLE STREET, LONDON, W.C.2**

Telephone: GERrard 8204

# A CAPACITOR . . .



Actual photograph

for the  
tightest  
of  
**TIGHT  
CORNERS**

## TYPE W99 MOULDED METALLISED PAPER

(HUNT'S PATENT)

### STANDARD DIMENSIONS

3/16" dia. x 7/16" long

RANGES 150v D.C. : 0.004uF to 0.01uF

350v D.C. : 50 pF to 3000 pF

(Additional capacitances at higher working voltages will be available shortly).

TEMP. RANGE: -15° C to + 71° C.

I.R. Better than 20,000 megohms.

SELF-HEALING

**TRULY MINIATURE.** There are more than two hundred Type W99 Capacitors piled on this standard match box! Another new development by Hunts to meet the increasing needs of designers and manufacturers for a quality capacitor for use in light weight, compact equipment employing miniature valves and for T.V. equipment.


**SPECIAL NOTE.** Now available in the W99 range and in the same standard dimensions—1000 pF 250 v. A.C. wkg. at 71° C. As a decoupling capacitor, this is suitable for a frequency range of 50 c.p.s. to 100 mc's

*Full details of all Hunts types, samples and advice on any capacitor application, gladly supplied on request.*



DRY ELECTROLYTICS • FOIL AND PAPER • METALLISED PAPER • STACKED AND SILVERED MICAS • TRIMMERS • PADDERS • ETC.  
A. H. HUNT LTD., WANDSWORTH, LONDON, S.W.18 TELEPHONE: BATTERSEA 3131 ESTD. 1901

## Not a test to destruction . . .

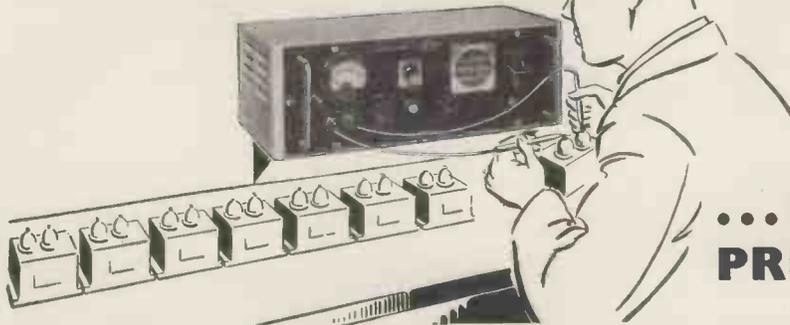

## ... but a test to PRESERVATION

Normal testing of capacitors by the application of a voltage greatly in excess of their working voltage as a safety precaution is unnecessarily ruthless. Some components apparently withstanding the test may be damaged by it and subsequently fail in service, whilst others break down immediately under the increased stress, to which they would never be subjected in normal service, and are destroyed. The AIRMEC non-destructive Ionisation Voltage

Tester will give immediate aural and visual indication of incipient breakdown and is completely infallible as a test of insulation even in the hands of unskilled personnel. Moreover it indicates condition — showing weaknesses which may be remedied — and thereby safeguards quality and prestige.

The instrument is self-contained, portable and low in first and operational costs. Test voltages up to 5 kV are available.

## AIRMEC LABORATORIES LTD.

HIGH WYCOMBE • BUCKINGHAMSHIRE • ENGLAND  
Telephone: High Wycombe 2060. Cables: Commlabs

MANUFACTURERS OF ALL TYPES OF INDUSTRIAL ELECTRONIC EQUIPMENT & TEST GEAR

## A RADIOGRAM FOR UNDER £5?

Convert your radio receiver to a radiogram by adding this superb radiogram unit offered at *exactly half* manufacturer's list price!

**INDUCTION MOTOR** with magnetic pick-up (Type AC47) in manufacturer's cartons. Brand new and guaranteed.

List price £9.13.0  
Our price  
(carr. & pkg. 3/6)  
Limited quantity only.

# £4.16.6

### REPEAT OFFER

Our November offer of *Mine Detectors* is renewed, as we have just secured a further small quantity of these metal locating equipments, brand new and unused.

**BARGAIN PRICE OF 79/6**

(Set of batteries, 22/6 extra.)

Full circuits available separately, 2/6 per manual. Equipment: 3-valve battery-operated amplifier in steel case, a shoulder haversack, two search coils with poles, junction boxes, headphones, 2 spare valves, circuit diagrams, log book, connecting cables and sensitivity measuring stick, operating instructions. Ready for use as soon as batteries are connected. Packed in robust transit case.

In view of the huge demand expected no correspondence can be exchanged concerning this offer.

### DUAL LOUDSPEAKERS

A Parmeko 10-watt speaker as used by the Admiralty on all types of craft. Two 8in. dia. P.M. Speakers mounted back to back and complete with volume control. Housed in black moulded frame and fitted with base fixing plate. Ideal for all purposes. **£2.10.0**

To callers.

Add 10/- for carriage and packing by rail.

### BURGOYNE SOLDER GUN

Indispensable to all who solder! Now available on extended payment terms. £2 down and 5/- per month. Cash price **£3.19.6** Post free.

VCR97 CRT'S Brand new 35/- (Post and pkg. 3/6).

EHT Transformer for above (completely shrouded), 32/6 (post and pkg. 1/-).

EHT Transformer for 'Inexpensive Television' receiver, 27/6 (post and pkg. 1/-).

Universal filament transformer (for all heaters), 17/6 (post and pkg. 1/-).

VCR97 Magnifying lens, 25/- (post and pkg. 1/-).

VCR97 Bases, 2/6 (post 6d.).

ARE YOU A REGULAR SUBSCRIBER TO THE FAMOUS M.O.S. NEWSLETTER? If not send 1/- for current copy, and subscription form.

### THERMO-COUPLE METERS

.5 amp. R.F. zin. Square Flush Mounting Type. Clearance Sale, 6 for 15/- (post and packing 1/6).

### WHILE THEY LAST

Brand new R.F. 24 Converters in sealed cartons complete with 3 valves. Frequency coverage 20-30 Mc/s, tunes to 5 spot frequencies. CALL IF YOU CAN. **10/6** (carr. and pkg. 3/6). ONLY

### NATIONAL 1.10A

The new improved version of the popular 1-10 super regenerative receiver. Frequency coverage 1-11 metres, complete with external speaker, 4 valves and mains power supply. BRAND NEW. Only one left. Best offer secures.

### CARBON HAND MICROPHONES

Brand new, and complete with lead and jack-plug. For this month only **2 for 3/6** (post 9d.).

To the Discriminating Listener we offer THE "CRYSTAL TONE" BRUSH PIEZO CRYSTAL PICK UP.

Outstanding features are:—

- (i) High Fidelity Tone Reproduction.
- (ii) Full recorded frequency range covered.
- (iii) Light weight of pick up on record practically eliminates wear and surface hiss.
- (iv) Robust construction and modern design.
- (v) Convenient to handle for easy needle change. ONLY **37/6** (2/6 post and packing.)

### R.1355 I.F. TRANSFORMER UNITS

Replacement for 6 Mc/s I.F. Units for the famous R1355. Four for 5/-, post free.

### BALLAST RESISTORS

British made equivalents to U.S.A. types C9266, K52H, K55B or K55H. All at **7/6** each, plus 9d. postage.

### W.B. EXTENSION UNITS

In handsome cream cabinet, comprising 5in. P.M. speaker with multi ratio output transformer and volume control. Brand new **36/-** (post and packing 2/-).

Full H.P. facilities on all Taylor instruments.

Terms: Cash with Order

# M.O.S.

MAIL ORDER SUPPLY CO.

33 Tottenham Court Road, London, W.1  
Tele: MU5um 6667-8-9

**PHILCO 3 VALVE TELEVISION PRE-AMPLIFIER.** A.C. Mains. 200/250 v. Slug tuned input, inter-stage and output. Size 7in. x 6in. Complete with own power supply and valves. £4, plus post and packing 2/6.

**PORTABLE CABINET,** rexine covered, leather carrying handle, size 12½in. long x 10in. high x 6½in. deep. Complete with back, aerial wound, scale and pointer, 25/-, plus 1/6 postage.

**UNIVERSAL REPLACEMENT MAINS TRANSFORMER,** primary 200/250 v., secondary 280.0-280, 60 mA., 6 v, 3 amp. tapped 4 v. 5 v. 2 amp. tapped 4 v. 6 v. 0.3 amp. 10/6, plus 1/- postage.

**MOVING COIL METER,** 0-300 v. A.C. and D.C., fitted internal rectifier, 15/-.

**SUPERHET COIL KIT,** comprising long, medium and short wave coils, standard twin gang, pair 465 I.F.'s, 4 pole, 4-way switch, 6 trimmers and two trackers, complete with circuit, and 5 valve super-het chassis, I.F. and speaker cut-outs. 14/6 plus 1/- post.

**SELENIUM RECTIFIER H.T.,** half-wave 250 v. 125 mA. 4/3 plus 6d. post.

**TWIN GANG.** .0005 fitted feet, trimmers and 1½in. drum: spindle tapped 6 BA. 4/6, plus 6d. post.

12in. P.M. less transformer. 29/6, plus 1/- post.

10in. P.M. less transformer. 14/6, plus 1/- post.

8in. P.M. less transformer. 11/9, plus 1/- post.

6in. P.M. less transformer. 8/9, plus 1/- post.

**MAINS DROPPER.** 0.2 amp. 1,000 ohms. 1/9, plus 3d. post.

**MAINS DROPPER.** 820 ohms, 0.2 amp. 1/6, plus 3d. post.

**MINIATURE CHASSIS,** size 8½in. long, 3½in. wide, 1½in. deep, miniature twin gang, miniature 465 kc. I.F.'s type 400B, four B7G valve holders, frame aerial and medium wave oscillator coil. Complete £19/6, plus 1/6 post.

**HEATER TRANSFORMER,** 6 volt, 1½ amp. 6/-, plus 9d. post.

**COMPLETE A.C. MAINS 200/250 volt 5-VALVE CHASSIS,** complete with 8in. speaker and valves, L.M. & S. and gram on press-button. P. tax paid, £8/19/6.

**MINIATURE 465 kc. IRON CORED I.F.'s,** type 400B. 12/6 per pair, plus 6d. post.

Write for lists:

**D. COHEN**

Radio Engineer

67 RALEIGH AVENUE, HAYES, MIDDLESEX

## POTENTIOMETERS



Wire-wound and Composition types. Single, Ganged, Tandem Units.

Characteristics: linear, log., semi-log., non-inductive, etc. Full details on request.

**RELIANCE MFG. CO. (SOUTHWARK), LTD.,**

Sutherland Road, Higham Hill, Walthamstow, E.17.

Telephone: Larkwood 3245

TRANSFORMERS  
**SAVAGE OF DEVIZES**  
LIMITED

INTRICATE TRANSFORMER CONSTRUCTION

SAVAGE TRANSFORMERS LIMITED

NURSTEED ROAD • DEVIZES • WILTS

TELEPHONE DEVIZES 534

# TELEVISION PATTERN GENERATOR



## MODEL 240 A SPECIFICATION

**FREQUENCY RANGE**  
40-70 Mc/s, directly calibrated.

**OUTPUT VOLTAGES**  
Approx. 50 mV., 5 mV. and 500 mV., at end of a 75 ohm co-axial cable.

**MODULATION**  
Horizontal bars, vertical bars, unmodulated.

**POWER SUPPLY**  
100-125 and 200-250 volts  
40/100 c/s.


**LIST PRICE £14.0.0**  
**EARLY DELIVERY**

other products include:

- Multirange A.C. D.C. Test Meters
- Signal Generators
- Valve Testers
- A.C. Bridges
- Circuit Analysers
- Cathode Ray Oscillographs
- High and Low Range Ohmmeters
- Output Meters
- Insulation Testers
- Moving Coil Instruments

ALL WINDSOR & TAYLOR TEST EQUIPMENT IS AVAILABLE ON H.P. AT TRADE PRICES. SEND FOR DETAILS AND CATALOGUES  
**TAYLOR ELECTRICAL INSTRUMENTS LTD**  
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND  
Tel. SLOUGH 21381 (4 lines) • Grams & Cables TAYLINS, SLOUGH

## LISTEN-IT'S A GOOD SOUND JOB

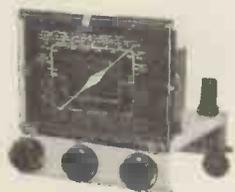


### R.A. TUNING UNIT

A really fine design with lasting high performance. R.F. stage on all wave-bands. High fidelity super-het or T.R.F. performance. Suitable for any amplifier.  
Price 10 gns., plus £2.6.8 tax.  
(2 years guarantee)


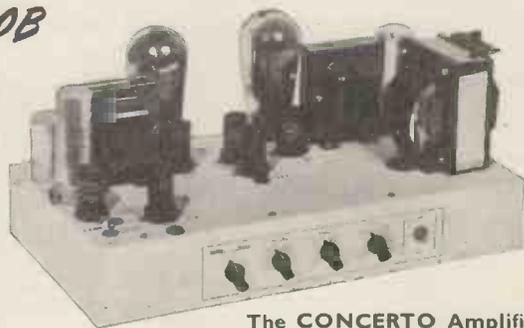
### THE K.I. AMPLIFIER

A seven-valve amplifier especially designed for the light-weight high-fidelity type pick-up. Independent bass and treble controls. Price complete 17 gns., or in kit form, 13 gns.  
Blueprint available separately 2/6



### The CONCERTO Amplifier

... acclaimed by music lovers for its exceptionally high fidelity, this magnificent amplifier covers all normal requirements for home or concert hall. Distortion level below 0.5 per cent. Two channels of bass boost ensure unusually smooth balance and depth. Designed for any type of pick-up. Radio input socket provided. Two-year guarantee. Price £27.10.0. Heavy perforated steel cover with bottom plate and rubber feet, 45s. extra. Delivery by passenger train. Carriage Paid. 10s. deposit (returnable) for crate.

DEFERRED TERMS AVAILABLE ON ALL MODELS

Our equipment can also be seen at  
**Webb's Radio, Soho St., W.1.**  
**University Recording Co.,**  
16 Burleigh Place, Cambridge  
**Ernest Buchan,**  
28 Belmont Street, Aberdeen.  
**Farmer & Co., 83 George St.,**  
Luton.



### THE TRICORNE SPEAKER CHAMBER

For optimum acoustic performance with any good 12-in. speaker. Labyrinth construction, walnut veneered and cross-braced.

Price 11 gns. plus 20/- deposit (returnable) for crate.


Phone :  
WESTern  
3350

*Charles*  
**AMPLIFIERS**  
(SALES LTD)

181 KENSINGTON HIGH STREET · LONDON · W.8

FOR THE UTMOST REALISM FROM RECORDS & RADIO

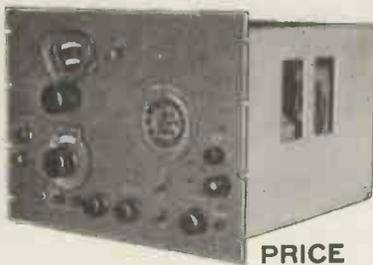**SPECIAL  
OFFER  
TO THE  
Enthusiast**



**PRICE**

**£23.10**

Famous U.S.A. Radio Communications Receiver, Type BC1147A. This Receiver was one of the last types to be sent into this country for use with the Armed Forces and is a 13-Valve Superheterodyne of high efficiency covering from 1.5 to 30 m/cs in four bands, with 5 per cent. frequency overlap between bands. Band division is 1.5 to 3.1 m/cs, 3.1 to 6.6 m/cs, 6.6 to 14.0 m/cs and 14.0 to 30.0 m/cs. Frequency calibration is accurate to within 1 per cent. of indicated value. The set has a built-in power pack for operation from 115 volts A.C. 50/60 cycles and we supply a suitable Auto Transformer to operate from standard 230-volt A.C. mains for use with each set. The Receiver employs two stages of B.F. Amplification with 455 KC's IF's which have an externally controlled broad and sharp response switch. Valve Line Up: 1 6SH7, 4 6SK7, 1 6SA7, 1 6J5, 1 6BE, 1 6S47, 1 6SQ7, 1 6K6 or 6V6, 1 VR150 and 1 5U4G. The Handsome Front Panel is complete with Aerial Matching Control, Wave-band Switch, Tuning Control, AF Gain Control, 1F Selectivity Control, BFO Control, Sensitivity Control, Power On/Off Switch, BFO On/Off Switch, AVO and Manual Control, Built-in Loudspeaker and Indicator Light Control. Size 19in. wide, 14in. high and 19in. deep. Price includes suitable Auto Transformer, Packing in Wooden Case, and Carriage Paid to your door.

**NO CARRIAGE OR PACKING CHARGES**

Carriage paid on all orders in U.K. For Fire and Export additional charges must be added or we will quote.

N.B.—The price of £28/10/0 quoted in the December, 1949, issue was a misprint due to a typing error.

**WESTON PRODUCTS**

(LIVERPOOL) LTD. • TEL: ROYAL 5754/5.

71-GT. GEORGE STREET-LIVERPOOL-1

## PRATTS RADIO

**1070 Harrow Road, London, N.W.10**

(Nr. Scrubbs Lane) Tel. LADbroke 1734.

**AMPLIFIERS.** College general purpose Amplifiers. Model AC.10E 10 watt 4 valve unit. Neg. feedback. Separate microphone stage, separate inputs for mike and gram. Separate faders and tone control. Complete in case with chrome handles. £8/18/6. Model AC.18E 6-valve Push-Pull Amplifier with feedback over 3 stages. Separate mike stage with separate faders for mike and gram. Separate gram input. Tone control. Output 18½ watts. Complete in case with chrome handles. £13/19/6. Model UIOE 6 valve 10 watt P.P. amplifier with feedback over 3 stages for D.C./A.C. mains. Specification as AC.18E, £11/11/-. All the above have outputs to match 3.8 and 15 ohm speakers and are complete for immediate use. Guarantee with each unit. Input voltages average, on mike, less than 5 m/v, on gram less than 33 v. R.M.S. for full output. No pre-amplifier required. Model AC4C, A.C. or Model U4C, D.C./A.C. 3-valve gramophone amplifiers. Output 4 watts to 3 ohms, £4/19/6. Stamp for fuller details. Why not come along for a demonstration?

**TRANSFORMERS.** E.H.T. 2,500 v. 5 ma. 4 v. 1½ amp., 4 v. 2 amp. C.T. (for VCR. 97). Input 200-240 v. (in 10 v. steps), 27/6. 2 x 350 v. 120 m.a. 6 v. 6 a.; 5 v. 4 a., 4 v. 4 a., 35/- (available trade). Fil. Transfr., Input 115/230 v., 6.3 v. C.T., 7/6. 30 watt 10 ratio O/trans., 23/9.

**SPEAKERS.** Brand new by famous makers, Sin., 9/11; 8in., 11/9; 10in., 18/6 and 28/6; 12in. Truvox 3 ohm, 45/-. Goodmans or Rola 12in. (15 ohms), £6/15/-. All P.M., less transfr., 6½in. mains energised, 10/-.

**CONDENSERS.** Brand new fresh stock. Midget 16 x 8 mfd. 450 v., 3/9; 16 x 16 mfd. 450 v., 4/6; 8 x 8 mfd. 450 v., 3/6; 8 mfd. 350 v., 1/11; 32 mfd. 350 v., 1/11; 16 mfd. 350 v., 1/11; B.I. C'b'd blocks 500/500 v., 8 mfd., 3/3; 8 x 8 mfd., 4/9; 16 x 8 mfd., 6/-; Ediswan Midget C'b'd's., 8 mfd. 450 v., 3/-; 16 mfd., 4/-; Paper condensers, .0001 to .0005, 1, 1.5, .01 x 1,000 v., all 6d.

**VARIABLE CONDENSERS.** 2 gang .0005 mfd., 4/6; .0005 mfd. 3 gang, 6/9; Both with feet and 2½in. shaft. Solid dielectric variables. Wavemaster .0003 mfd., 3/4; .0005 mfd., 3/6. Ceramic presets, 50pF, 4d., 100 pF and .0005, 1/3.

**MISCELLANEOUS.** U.S. Octal, Brit. 4.5 and 7 pin, 4d. each. Volume controls Egan, less sw., 2/9, with sw., 4/6. Jack-plugs and sockets, bakelite, 2/6. Mains droppers, 3 a. 750 or 2 a. 1,000 ohms, 4/6, with 2 sliders and ft. Chokes, 60 ma. 20 hy. 360 ohm, 6/6, 90 ma. 10 hy., 10/6; 150 ma. 10 hy., 14/3. 80 ma. 8 hy., 75 ohm, 3/9.

**WEARITE "P" Coils,** all types, 3/- each. **DENCO L. & M.W.** Coils with reaction, A. & H.F., 6/6.

**"VIEWMASTER" TELEVISOR.** All parts available. All goods are new and unused and offered on a money back guarantee basis. C.O.D. or C.W.O. Postage extra under £1. Shop hours 10-6.

"INEXPENSIVE TELEVISION" is the title of a booklet describing how to make a Televisor for the London or Birmingham frequencies using ex-Govt. Radar Material. Send only 1/9 to cover cost and postage for a copy, and also price list of material required.

**RECEIVERS R.1355.** As specified for above Televisor. Complete with all valves and a copy of the booklet. ONLY 45/- (Carriage 7/6).

**INDICATOR UNITS TYPE 6.** The Indicator unit specified for above, this being complete with the Cathode Ray Tube VCR97 and all valves. BRAND NEW IN MAKERS' CRATES. ONLY 90/- (Carriage 7/6).

**TRANSFORMERS** for the above TV have been specially made as follows: Time Bases and Vision Transformer, 350-0-350 v. 160 mA, 5 v. 3 a., 6.3 v. 6 a., 6.3 v. 3 a., ONLY 34/- Sound Receiver Transformer, 250-0-250 v. 100 mA, 5 v. 3 a., 6.3 v. 6 a. ONLY 27/6. EHT Transformer for VCR 97 Tube 2500 v. 5 mA., 4 v. 1.1 a., 2-0-2 v. 2 a., ONLY 27/6. Postage etc. 1/6 per transformer.

**MAGNIFYING LENS** for 6in. C.R. Tube. Brings up the picture size to approximately that given by a 9in. tube. A new contract enables us to price them at ONLY 25/- (Postage etc. 1/6).

**RECEIVERS R.3585.** An ideal unit for conversion to TV in the London Service Area, as it contains a "PYE" 45 mcs. I.F. Strip, and valves as follows: 7 of EF50, 4 of SP61, 8 of EF36, 1 of EB34, 1 of EF39. BRAND NEW. ONLY 90/- (Carriage etc. 7/6).

**BATTERY SUPERSEDERS.** Replace that H.T. Battery with a low consumption Vibrator Power Unit which operates from 2 v. accumulators. Originally made for the Canadian Forces by Electronic Laboratories of America, this fine little unit is easily adaptable for normal use, and comes to you complete with a copy of the original instruction book which gives circuit details of the whole equipment in which it was used. Consumption is approximately ½ of an amp, and it delivers 90 v. and 180 v. H.T., and 1.4 v. L.T. ONLY 60/- (postage 2/-).

**TELESCOPIC AERIALS** as used on Canadian Walkie Talkie. 15in. in length extending to 103in. Completely enclosed in metal case with dust cap. ONLY 12/6 (Postage etc. 1/-). C.W.O. Please. S.A.E. for lists.

**U.E.I. CORP., The Radio Corner**  
138 GRAY'S INN ROAD, LONDON, W.C.1

(Phone: TERminus 7937)

Open until 1 p.m. Saturdays, we are 2 minutes from High Holborn (Chancery Lane Station), and 5 minutes by bus from King's Cross.

## NEW INDOOR T.V. AERIAL

FOR LONDON AND BIRMINGHAM



The WOLSEY "All Flex" Braided Indoor Aerial is perfectly efficient within close limits of London and Birmingham transmissions where there is no fear of reflections or interference. Readily installed anywhere. When extended vertically its performance equals that of a normal single dipole in same position. Price, complete, only **16'6**

There are WOLSEY Aerials for every purpose and place, from the above simple indoor model to the Super folded 3 Element array for fringe areas. Brochure on request.

**WOLSEY TELEVISION LTD.**  
75 Gresham Rd., London, S.W.9. BRIXton 6651/2  
59 Soho Hill, Birmingham, 19. Northern 2762

## GARLAND RADIO

**VIEWMASTER TELEVISION KITS** now available. Whiteley, 125/-; Plessey, 118/6; R.C.C., 135/-; Westinghouse, 82/6; Bulgin, 12/6; Bellini-Lee, 7/6; Colvern, 18/3; Morganite, 35/11; Wright & Westre, 22/0; G.E.C. Neon, 2/9. Carriage free.

Viewmaster Booklet and Blueprints, 5/4.

**INDICATORS** 95 and 157, containing VCR97 C.R. Tube, 16 of SP61, 2 of EB34, 2 of EA50, Crystal, etc. For callers only, 65/-.

**WAVEMETER TYPE 4 (10T/534)**, containing waveguide, CV61, VE92, VU39, SP61, etc., 25/- each.

**BATTERY AMPLIFIER** No. A127, with 220B valve, brand new, 5/6.

**TELESCOPIC AERIALS**, extending to 7ft., 3/- each.

**VCR97 BASES**, 1/9 each.

**PLUGS AND SOCKETS**, complete. Jones 4, 1/-; Jones 6, 2/-; Jones 8, 2/6; Jones 12, 3/-; Pye straight, 1/6; Pye angle, 1/6.

The above and many other new and surplus items may be seen at our new and larger premises.

**GRESHAM HOUSE, DEPTFORD BROADWAY, S.E.8**

Phones: TIDeway 4412/3.

# Wireless World Classified Advertisements

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1/- Trade discount details available on application. Press Day: February 1950 issue, first post Monday, January 2nd. No responsibility accepted for errors.

## WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

## NEW RECEIVERS AND AMPLIFIERS

**MASON'S**, Wivenhoe, nr. Colchester.  
**ILLUSTRATED** catalogue, price 9d, full details of Denco and Eddystone range; tuning units, television kits and surplus radio bargains. [4578]  
**UNIVERSAL ELECTRONIC PRODUCTS**, 26, Marylebone High St., London, W.1. Tel. Welbeck 4058.  
**SPECIALISTS** in the design and manufacture of high fidelity reproducing equipment from 4-100 watts for domestic or industrial purposes. Our U.E.5 (6 watts) and U.E.7 (12watts) series amplifiers are designed especially for the connoisseur who requires the finest possible reproduction from recorded music; both amplifiers have a linear response over 30-20,000 cycles with a damping factor of 12, and incorporate pre-amplifier stage, together with independent control of bass and treble. Our policy is to produce an instrument which represents the highest standards in workmanship and performance and no expense has been spared to achieve this object. A new addition to our range is the type U.E.3 (4watts) at £11/10. We also supply a range of tuning units, both t.r.f. and superhet, for use in conjunction with either our own or other makes of amplifiers. We should be pleased to quote you for the design and construction of a unit or replacement chassis to your exact requirements. Full details of our products will be forwarded on request, and we would welcome the opportunity to demonstrate our equipment at any time to suit your convenience. [3352]

**HALLICRAFTERS** dual diversity receivers, speakers; few only available.  
**MCLEROY ADAMS MFG. GROUP, Ltd.** (Hallcrafters), 46, Greyhound Rd., London, W.6.

**AMPLIFIERS**, new, 60 watt heavy duty P.A. models, built for continuous rating and rack mounting; £40; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tomland, Norwich

**DC** mains? This new 5watt all miniature valve amplifier has been designed to give you high fidelity reproduction from DC mains supply, matched for moving coil pickup, output 2.5-15 ohms, bass and treble controls, complete £21/10, or with mic. stage, £24.  
**FELICITY GRAMOPHONE Co.**, 87a, Upper Richmond Rd., W.12, Wey 1665. [0041]

**12** watt high-quality amplifiers, precision built instrument, bass and treble boost, high gain, complete with power pack, £12/10, less power pack, £8/15; send for descriptive literature and approval terms.—Broadcast & Acoustic Equipment Co., Ltd., Tomland, Norwich

**BUY** direct from the manufacturers. Our 5-valve all-wave superhet radiogram chassis is now available. The price suits the pocket too, only £12 complete with valves and 8in. P.M. speaker. Give yourselves a treat. Fit our A/C55 in place of that old chassis and make a new radiogram of it. S.a.e. for illustrated leaflets. Trade enquiries invited.—Bayly Bros., 46, Pavilion Drive, Leigh-on-Sea, Essex. [4595]



**MIDCO** amplifiers for the enthusiast, type AA/5, 5watt fidelity model on enamelled chassis with tone and vol. controls, £5/10 complete; AA/10 10-watt unit with tone and vol. controls, £11/10; PA/12 high fidelity models, 12-watt record reproducer with bass and treble tone controls, twin inputs. £14 complete; PA/12M very high gain mic version, one high one low impedance inputs with full mix/fade complete, £14/10; PA/12 amplifiers are built in steel cases in cellulose enamels with chrome fittings; catalogues available; trade inquiries invited.—Midland Radio Coil Products, 19, Newcomen Rd., Wellington, Wellingborough. [4552]

**THE** pioneers of the new world topus Williamson amplifier offer T.R.F. mixed tuner with monitor speaker built on lines suggested in current "W.W." by Mr. Williamson. This tuner in conjunction with our W.W. amplifier constitutes the connoisseur's final choice. Distortion as low as point nought five per cent. Tuner £12; 7-valve amplifier (with improvements), £25/10; 9-valve model with built-in pre-amplifier and tone control, £30/10; covers extra; PX4 model, £17/10; 3 waveband tuner, £10; complete equipment, amplifier, tuner, speaker and record changer on H.P. terms from £7. Details from pioneer and world's finest producers of quality reproducers, R.T.M.C. (Ealing), Ltd., Laurel House, 141, Little Ealing Lane, W.5. Ealing 6962. [3674]


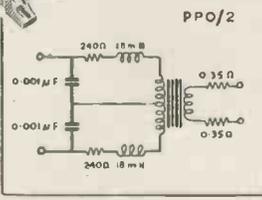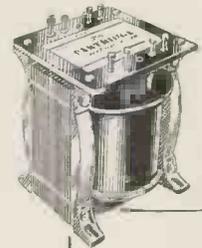
## Partridge News

A new standard in PUSH-PULL OUTPUT PERFORMANCE



**THE** new "PPO" output transformers permit the reproduction of a full A.F. range with minimum distortion. Rating is 12w. for 0.5% harmonic distortion at 50 cycles. Six standard models are available, for accurate matching anode to anode loads of 4,000 ohms to 12,000 ohms. The secondary in each case is brought out in two sections for series or parallel connection to match a 15 ohm or 3.7 ohm load. These standard models are available from stock, other specifications can be wound to special order.

Full details are given in Technical Data Sheet No. 1, a copy of which will gladly be sent on request.

**PARTRIDGE TRANSFORMERS LTD**  
 ROEBUCK ROAD, KINGSTON-BY-PASS  
 TOLWORTH SURREY  
 Telephone: ELMbridge 6737-8

## NEW RECEIVERS AND AMPLIFIERS

**TELRAD ELECTRONICS** 70, Church Rd., Upper Norwood, London, S.E.19, designers and manufacturers of Telrad quality amplifiers for commercial and domestic use; these unique amplifiers, with exceptional quality, gained instant popularity when first introduced at recent exhibition; built to satisfy the discriminating ear, bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; £15 complete; full details on request.—Write, call or phone Livingstone 4879. [0019]

**CONNOISSEUR'S** receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-1.500-metre, world-wide results on highly sensitive 10-valve receiver, comparable with any good communication set, or by change of switch, on maximum fidelity reception of local stations on non-superhet receiver with high quality 2-PX4 push-pull amplifier incorporating all refinements, bass and treble tone control (boost to cut), whistle filter and gram input, etc.; basis rebuilt R155; write for details or call for literature. **FEEDER** units as above, for use with external high-quality amplifiers; R155 specialists, receivers repaired and re-aligned, also modified as above, or to your requirements; R155 circuit and values 2/- post free.—R.S. Ltd., 5, Gladstone Rd., Wimbledon, S.W.19. Tel. Lida 335.

**QUALITY** radio feeder units and amplifiers; R155 Tuner T.R.F. L. & M. wave, infinite impedance detector, 6.5v valves, excellent reports from "Williamson" and "Leak 1" amplifier users, £5; complete kit, £4/10. No. 2 Tuner, 3-waveband superhet, special bandwidth, elaborate dial assembly, £8/10; complete kit, £7/10. No. 3 audio amplifier, 4-watt undistorted, 6V6 output, special neg. feedback circuit, 30hms impedance (or to order), gram, and tuner inputs, £5/19/6; complete kit, £5/10; super crackle cabinet if required, 15/- extra. No. 2 amplifier, 12-watt push-pull 6V6 output (5, 7 & 15ohms), neg. feedback, gram, mike and tuner input, price 10gms; complete kit, £9; super crackle cabinet if req'd., £2 extra; terms, c.w.o. or c.o.d.: W.W. bargain list 2/4d.—Northern Radio Services, 16, King's College Rd., Swiss Cottage, London, N.W.5. Primrose 8314. [0005]

**R.T.M.C. (EALING, Ltd.)**. Ask yourself a question. An amplifier (details published in "Wireless World") and sponsored by E.G. must obviously be a "quality product." Our version of this now famous amplifier is such that it is without doubt the finest reproducer in the world. We say this without fear of contradiction. The R.T.M.C. "Williamson" is now known the world over as the best that money can buy and no other amplifier can approach it for quality of parts used or results. Also price, you do not want to waste money. At £25/10 (ex cover) we are lower than any other quality product. Our 9-valve model incorporates pre-amplifier and costs only £30/10 (ex cover). We have experimented considerably with this amplifier and our models incorporate many refinements making it the world's best, on price and quality and performance figures. We also supply tuners at £10/10, speakers and record players.—Full details from R.T.M.C. (Ealing), Ltd., Laurel House, 141, Little Ealing Lane, W.5. Ealing 6962. [3674]

## RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

- R1155** (mod) power pack, new extn. speaker, £15 or offer.—Box 1001.—[4599]
- MCR1**, complete, as new, bargain; £7/- 6s. Gainsford Rd., Southampton. [4668]
- L**OWTHER amplifier, 15 watts output, 1948, perfect order; offers over £30.—Box 1072. [4730]
- HALLICRAFTERS** 536 F.M./A.M. v.h.f. revr, 27-145 m/cs. Just overhauled and realigned; £35.—Box 1140. [4764]
- BARGAIN** AE 88D, in first-class condition, with speaker; best offer over £15.—7, Sherwood Rd., S.W.19. [4762]
- EDDYSTONE** S640 with speaker, 9 valve 32-1.7 m/cs., almost unused, illness, must sell; best offer; London.—Box 1005. [4613]
- PHILCO** de luxe combined all-wave radio, 12in tube television and auto-change gramophone; £200 or nearest.—Ealing 0521. [4684]
- R.M. H.R.D.**, complete with power pack, 9 coils, headphones, spare valve set; £40, bargain.—46, Purbrook Ave., Watford. [4682]
- 1155** ex-R.A.F. communications receivers, in first class condition; £6/10, carriage paid.—T. Tysler, 63, Gellatly St., Dundee, Angus. [4765]
- TELEVISION**, Marconi VT50A; (London); little used; 2v, pre-amp. H-type aerial; £50 the lot; cost nearly £100.—1350 Stratford Rd, Birmingham, 28. [4693]
- VOIGT** 1/c twin 1/s, p/pack, 2xPX25 n/t amplifier, £23; Baird 12in console t.v. and radio, £50; Murphy A40 15v, £35.—10 Cowper Rd., Hanwell, W.7. [4752]
- 8-VALVE** AC/DC superhet R.G. chassis, 5 w.b. 12w. P.F. output, P.S. 15; 7-w. A.C. 3 w.b. feeder unit and amplifier in cabinet, £20; output, £17/10; Ever Ready Personal, £9/10; Valradio 200/250 D.C. to A.C. converter, £9; Masteradio car vibrator unit with valve rectifier, £5/10.—Box 1011. [4630]



## A New Year Message

For all the courtesies shown by our customers and correspondents during the past year—our very best thanks. It is a constant pleasure to us to find that our desire to do business in the good old-fashioned way in a world that is becoming increasingly synthetic and shoddy is appreciated so much by men who have no use for synthetic and shoddy sound reproduction.

Our business methods are old-fashioned in that we do not expect payment for work badly done, but our technical methods are such that new customers frequently express surprise that such a comparatively small firm as ours should have such a big reputation. That reputation was not gained by trying to build up a reputation; it was the inevitable outcome of doing a specialist job truly and well, and not trying to do anything else.

In the new year we shall announce still further advances in technique, which, we suppose, will enhance the Hartley-Turner reputation a little further. What is much more important to you is that the means will be provided for still better music reproduction at a price which will not make you look and feel wistful.

A happy new year to you all

**H. A. HARTLEY CO. LTD**  
152, HAMMERSMITH ROAD  
LONDON, W.6. RIVERSIDE 7387

**NEW S.T.C. SELENIUM RECTIFIERS.**  
Largest L.T. range from stock in Gt. Britain. ALL makers' current products. NOT SURPLUS. H4/200 E.H.T. for "W.W." Televisor, 28/-; H4/100 E.H.T. for VR97, 18/6, post free.

### HALF WAVE RECTIFIERS.

16v. 2a. 6/8; 1a. 8/-; 2a. 9/6; 3a. 16/6; all post 6d. 4a. 18/-; 6a. 22/6; post 10d. 30v. 1a. 12/-; 2a. 14/-; 4a. 24/6; 6a. 36/6; 48v. 2a. 21/-; 4a. 35/-; 6a. 51/-; 100v. 2a. 34/6; 4a. 65/-; all post 1/-.

### HALF WAVE HEAVY DUTY. 7½in. S.Q. COOLING FINS.

16v. 5a. 21/6; 10a. 24/6; 30v. 5a. 35/-; 8a. 38/6; 48v. 2.5a. 26/-; 5a. 48/-; 8a. 54/-.

### BRIDGE CONNECTED FULL WAVE.

17v. 1.5a. 12/1; 2a. 15/6; 2.5a. 20/6; 3a. 21/6; 4a. 25/-; 5a. 27/-; all post free. 33v. 2a. 18/6; 1a. 21/3; 1.5a. 28/6; 2a. 29/6; 3a. 35/-; 4a. 42/-; 5a. 43/6; all post 10d. 54v. 1.5a. 39/-; 2a. 47/6; 4a. 65/-; 100v. 1.5a. 72/-; all post 1/-.

### HEAVY DUTY BRIDGE. 7½in. S.Q. COOLING FINS.

17v. 6a. 34/1; 10a. 43/8; 12a. 72/-; 20a. 80/-; 33v. 6a. 64/-; 10a. 71/-; 12a. 124/-; 20a. 140/-; 54v. 6a. 90/-; 10a. 100/-; 72v. 10a. 130/-; 100v. 10a. 190/-; all post 1/4.

### INDUSTRIAL TYPE FUNNEL COOLED BRIDGE.

17v. 12a. 76/-; 20a. 87/-; 30a. 122/-; 50a. 188/-; 33v. 6a. 69/-; 30v. 10a. 80/-; 33v. 12a. 124/-; 20a. 144/-; 54v. 6a. 92/-; 10a. 108/-; 72v. 6a. 114/-; 10a. 136/-; 100v. 6a. 160/-; 10a. 192/-; all post 1/6.

### VALVE CHARGER REPLACEMENTS.

Philips & Tungsar. No wiring alterations.

Wholesale and Retail.

**T. W. PEARCE** (Est. 18 yrs.)

66, GREAT PERCY STREET, LONDON, W.C.1  
Off Pentonville Rd. Between King's Cross and Angel

## RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

TF1445. Marconi standard sig. ren. with attachments, instr. book. £59; TF340 output power meter. £22/10; both ex. cond. AMATEUR'S Den, 181, Lake Rd., Portsmouth. [4761]

CHARLES quality amplifier. £13; 1155 and C power pack. £10; EC348 9-valve receiver. £16; all 240v and carriage paid.—Blackwell, 41, Meadway, London, N.14. [4600]

R.A.F. model 1155, new, complete with valves, converted models from £8/10; send for lists.—Broadcast & Acoustic Equipment Co., Ltd., Tomland, Norwich. [0066]

R.1155 B receivers, new surplus, perfect condition, but cases slightly scratched. £7 incl. case and carriage.—Champion Products, 43, Uplands Way, London, N.21. [4759]

R.1155 mod. for a.c., 6V6 o.p., fitted grey enam. front panel, etc., laboratory aligned and tested; full test data available; seen London area; £14 or offer.—Box 1122. [4755]

£8, RAF 1155, perfect, in original transit case; £11 converted with output valve and smoothed mains power pack.—Jakubskind, 69, Church Rd., Moseley, Birmingham. [4771]

W.W. Qual. amp., gram. feeder by Sound Sales, Rola 12in speaker, local station unit, complete with valves, perfect; £20.—Deadman, 6, Abingdon Rd., Kensington, London, W.8. [4741]

A R77E Rk-mtg 10v comm. Rx, 500kc-30Mc, good cond., £19; a.c./d.c. 3-wvd. s/het chassis, 4v+R., £5; S.T.C. ball mike, £2/5; 550v 200ma 6.5v 5v trsf., £2; many components for disposal.—Box 1035. [4708]

15 w feedback amplifier and mains unit, 2 input chnns., Partridge Xformers, 6J7, 6Y, 6V6 PP, 5V4, complete at £18 or nearest.—R. Jackson, 11, Amherst Rd., Fallowfield, Manchester. Tel. Rus. 5111. [4624]

HARTLEY-TURNER radiogram chassis and power unit, type 215 speaker, all in polished wood cabinet, turntable and connoisseur P.U. as separate unit, excellent tone, high fidelity reproduction, 1948 model, owner going abroad.—Box 1012. [4640]

15 valve double superhet, 3 chassis, 10-6,000 metre continuous, current and signal meters, variable calibrated B.F.O., noise limiter, T.F. regeneration, 1.5, complete at £18 or nearest.—R. Jackson, 11, Amherst Rd., Fallowfield, Manchester. Tel. Rus. 5111. [4624]

Tensler, stabilised H.T. and 6.3v, 3 valves, metal case, new, ideal for oscillator, etc., 32/6; power unit APA/17, 5R4, transformers, chokes, condensers, relays, fuses, etc., ideal for amplifier, new, 50/-; modulators 5-K744, 2-U17 or VE111—M14, etc., 25/- (two 45/-); power units, 100-250v, a.c. in, 15v atamps and 300v 40amps, d.c. out, 32/6; 1355, 37/6; carriage paid.—G. R. Adcock, 113, Norwich Rd., Walton, Norfolk. [4632]

STOCKTAKING offer! Brand new R.C.A. amplifiers in manufacturer's sealed cartons, representing the cream of American production, complete with beautifully finished R.C.A. high fidelity moving coil microphone to match; valve line-up 4 6J7's followed by 2 1622s in push-pull (5U4G rect.) with neg. feedback giving approx. 20 watts output; 200-250v a.c. operation; price complete with valves, £18, less valves, £15 only; Garrard electric gram motors, 250v a.c. auto-stop, £4; electrolytics, 25mfd, 12v, 9d each, 7/6 doz.; 2½d stamp brings full detailed list of other miscellaneous bargains.—B. G. Jelley, Radio Specialist, London Rd., Larkfield, nr. Maidstone, Kent. Tel. Aylesford 7372. [4706]

H.R.O.s senior model with valves, S meter & crystal, less coils, in excellent condition. £12/10 ea.; £27, less valves and S meter needs clean up and slight attention. £10; another minus front panel and knobs, £8; Canadian 52, 13 valves, crystal cal. 3 bands, 1.75-16 Mc/s, built-in speaker, less pack. £12/10; AR88d excellent, £40; indicator units with VCR97, brand new in cartons. £4 ea.; 7 other types from 55/-; power units 332, 230v A.C., 50c/s, 700v smoothed output, rated 70ma but gives effortless 120ma, brand new with valves, £2/19 ea.; Mallory 12v vibrapacks, 150v 60ma, new, tested, with synchronous vibrator, 7/6 ea.; Tannoy 20 watt pressure units, 50hm coil, new, £2; telephone sets with G.F.O. type dual handset, mag. bell, etc., 25/- ea. or 45/- pr.; ditto with buzzer and morse key, 22/6 or £2 pr.; all Bakelite type with bell, mag & buzzer £2 ea. or £3/15 pr.; ditto with amplifier, £6 pr.; RF units, type 24, 3/8; 24 mod 27, 8/6; 27 or 22/6; volt-meters, 0-40, 4/6; ammeters, 20-0-20 or 50-0-50 @4/6; 0-5ma 7/6; others in stock, R.C.A., TE/149 crystal wavemeters, new £6/15 ea.; ditto, need slight attention, £3/10 ea.; suppressors, small, 3/6, medium 8/6, large 30/- & £2; G60 wavemeter, new, less valves, with 10mc crystal, 180-250 Mc/s, £3 ea.; E107, sound condition, untested, £8/10; technical manual ANTPX/3, 15/-; SCR269G, prelim, 5/-; maintenance 10/-; SCR609a & 610a 5/-; if you are interested in projectors, telescopes, binoculars, rifle sights, episcopes, enlargers, microscopes, etc., it will pay you to get our new booklet "How to use ex-Govt. Lenses & Prisms" price 2/6 ea. instructions sheets for a 2¼x2¼ vertical enlarger for which we can supply all parts, 5/6 ea.; optical and radio list free on receipt of your s.a.e. H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex. [4760]

## CABOT RADIO

R.C.A. H.T. TRANSFORMER. Input 190/260 v. (10 v. steps), 50 cps. sec. 2300, 1750, o. 1750, 2300 v. (for nominal outputs 2000 v. or 1500 v. D.C. at 800 m/a). Wt. 97lbs. net. Size 9in.x9in.x 7½in. New in cases. £4 plus 7/6 carr.

R.C.A. MODULATION TRANSFORMER. Primary 10,000 ohms CT. Sec. 4000 ohms approx. (Push-pull 810's, 805's, TZ40's, etc., to any P.A. up to 1kW.) Wt. 67lb. net. Size 9in.x 9in.x 7½in. New in cases. £3 plus 5/- carr.

SPECIAL OFFER. Both the above transformers together in one case. £6 10 0, plus 10/- carr.

SMOOTHING CHOKE. British made for 1131 tx. 15/20 H. 500 m/a, 80 ohms. Wt. 20lb. 25/-, plus 2/6 carr.

CONDENSERS. 4 + 4 mfd. 3KV wkg. 25/-, 4 mfd. 2KV wkg., 15/-, 4 mfd. 1,500 v. wkg., 10/-. All Carr. Paid.

TRANSMITTER. 1196 Phone and MCW 4.3-6.7 Mc/s. Easily modified for other frequencies. Complete with valves (EF50, OSC, TT11 PA, and EL32 Modulator) and circuit diagram. 27/6 plus 2/6 carr.

RECEIVER 1196, 6-valve Superhet, complete with valves (EF39RF, EK32FC, EF39IF, EF36AVC Amp, EBC33 Det, EF36AF Amp). 25/-, plus 2/6 carr. Also with circuit diagram.

CRYSTAL DIODES. CV101/111, suitable Xtal sets, F.S. meters, etc., 2/9 each, 8 for £1. Post free.

SOIL HEATING AND DEFROSTING TRANSFORMERS. (1) Primary 230 v. 50 cps. Secondary 11-13.5 v. (adj. Prim. tap). Service rated at 70 amps but O.K. for 150 amps. £4 10 0, carr. paid. New in Box.

(2) Primary 230 v. 50 cps. sec. 6.75 + 6.75 v. 20A but O.K. for 40A. New. 50/-. Carr. Paid.

**CABOT RADIO COMPANY LIMITED**  
28, BEDMINSTER PARADE, BRISTOL, 3.

Phone: 64314

**PENNINE RADIO**



**AUDIO SIGNAL GENERATOR**

- HIGH STABILITY
- WIDE RANGE 40-16000 C.P.S.
- LOW PRICE
- 3 WATTS OUTPUT

LIST PRICE **£9-9-0**

Write for Particulars  
**PENNINE AMPLIFIERS**  
SOUTHGATE, ELLAND, YORKS, ENGL.  
Tel.: Elland 2107

**NEW LOUDSPEAKERS**

**S**TILL the best for the barkers, the Tridem 12D corner cabinet, supplied with or without speaker unit.  
**FELICITY** GRAMOPHONE CO., 87a, Upper Richmond Rd., S.W.15. [0040]  
**H**IGH fidelity reproducer cabinets to Goodmans and Barker spec. from £7/5/- new 12in speakers, 45/-; comp. lists from Cabinetware, Summit Works, Heyes St., Blackburn. [4206]  
**S**PECIALIST distributors for the high fidelity S Wharfedale speakers: Standard 8in, 28/6; bronze 8in, 35/-; super 8in, 65/-; super 8in C.S. (cloth surround), 75/-; golden 10in, 75/-; golden C.S. 10in, 85/-; W.12 12in, 135/-; W.12 C.S. 12in, 145/-; stat. s/c imped. (3 or 15ohms); c.w.o. or c.o.d.; lists 2/4d.—Northern Radio Services, 16, King's College Rd., Swiss Cottage, London, N.W.3. Primrose 8314. [0006]

**LOUDSPEAKERS—SURPLUS AND SECONDHAND**

**L**AATEST Barker 148A, perfect makers' carton; £10/10.—113, Hazel Rd., Long View, Liverpool. [4294]  
**H**ARTLEY-TURNER 2.15 in cube baffle polished cabinet 39in high, as new; £10/10.—84, Beaumont Rd., Nuneaton. [4758]  
**C**RESCENDO infinite baffle corner deflector. 12in unit, 15 watts capacity.—Blackshaw, 38, Northfield Grove, Merry Hill, Wolverhampton.  
**V**OIGT twin unit, 200v field, Edibel horn, £15; 2 others, 6v without diaphragms, £9/10 each.—67, Hammersmith Grove, W.6. Riv. 6942. [4751]  
**H**ARTLEY Turner 215 in 24in mahogany baffle, £10; two No. 14 C.M.T. pick-ups with transformers, 30/- each.—Cratt, Exton, Gt. Osham, Devon. [4759]  
**H**ARTLEY Turner speaker with O/P transformer on H.M.V., 3ft 6in square, polished baffle on wheels: £15.—Spencer, Cross House, Millborne Port, Somerset. [4657]  
**H**ARTLEY-TURNER 21in cube baffle (new), £6; Goodman Axion 12 speaker, £6/10; Wilkins Wright coil pick-up (new), £6; Axion Axion 22.—170, Bakinton Rd., Coventry. [4750]  
**L**OUNDSPEAKERS in stock for immediate delivery; brand new by famous makers at knock-out prices: PM 5in, 10/-; 6 1/2in with trans, 15/-; 8in, 16/6; 10in, 22/-; mains energized, 1250 ohm field 8in, 5/-; 10in, with trans, 22/- (add 9d post).—Roding Labs., 70, Lord Avenue, Ilford. [4733]

**NEW DYNAMOS, MOTORS, ETC.**

**B**BATTERY chargers, 4 models 2-6-12v. 1-2-4 amp D.C.; any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddlegate, Herts. [2212]  
**A**LL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators, and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.  
**R**EVOLVING armature alternators, with separate exciter generators, 4-pole, ball bearing, 1,500 rpm, output 230v, 50 cycles, 3kva, excitation at 24-30v, price £29; ditto, 2-pole, ball bearing, 3,000rpm with 4.5kva output, £29.  
**R**OTARY transformers, input 20v d.c., outputs 6.5v d.c. and 300v d.c., permanent magnet field, 20/-; ditto, input 28v d.c. and 1,200v, 70ma d.c. output, energised field, 35/-; ditto, input 12v d.c., output 500v, 90ma d.c., energised fields, 35/-.  
**P**ETROL electric generator plants, comprising a J.A.P. No. 2a single-cyl engine coupled by vee rope drive to an alternator, giving an output of 230v, 50 cycles, 400 v.a., with screened iron cabinet and filtering condenser, engine suitable for operating television and radio on farms, etc., price £40; such plants can be supplied with various outputs a.c. or d.c., for other applications.  
**C**HAS F. WARD, Lordcroft Works, Haverhill, Suffolk. Tel. 253. [0039]

**DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND**

**2** Rotary converters, 24 d.c., to 230 a.c. 250 watts, new and unused; £15 each, or nearest offer.—Box 1070. [4726]  
**9**7/6, charging switchboards, 12v-32v, 500 and 1,260 watts, volts, amps, cut-outs, fuses, resistances, etc., 4 take-offs, superb unit, in case, or send £5 carriage paid; 75/-, dynamo, 24 volts, 1,000 watts, 8in x 7in, 3 1/2in spindle, or send 80/- carriage paid; 75/-, 230v/150, 1/2hp electric motors, incorporating 1,260 cycle converter, or send 80/- carriage paid; 59/-, mains transformer switchboards, 230v a.c. to 12v, 5 separate take-offs, complete distribution panel, all switches, fuses, amps, etc., brand new, or send 60/- carriage paid; 55/-, electric motors, 12v and 24 v, 1/2hp, 4in x 4in, with 1/2in spindle for drive, beautiful job, or send 60/- carriage paid; 45/-, dynamo units, containing 12v, 24v, 130v and 300v d.c. dynamo or suitable as 6v, 12v or 24v motor, approx. 1/2hp, 1 1/2in x 5in, with spindle to take small grindstone, mop, etc., also contain adjustable 24v cut-out automatic voltage control, smoothing condenser, resistances, and many other extremely useful fittings, beautifully made, or send 50/- carriage paid; 35/-, radio avometers, adjustment dial, 350-370 Mc/s, beautiful instrument in case, or send 40/- carriage paid; best other valuable equipment; lists free.—Benmotors, Summerley St., Earsfield, S.W.18. Wim. 3833. (100 yds S. Rly. Electric Line; 10 minutes Waterloo).

**ELECTRADIX**

for Best British Bargains

**TRANSFORMERS.** Foster 100 watt 230 volts 50 cy. input, 50volts, 2amp output, double wound insulated terminal block 4-hole fixing, 15/-, B.T.H. 200/230/250 volts 50 cy. input, 2 volts 20 amps. 75 volts 6 amp output with 15 taps, 45/-.

**COMPASSES.** Binnacle Boat Compasses, Liquid Model, in housing with glass windows 40/-.

**AUTO TRANSFORMERS** 230/110 volts 85 watts, 25/-, 150 watts, 35/-, 1 kw., £7/10/0.

**TRANSFORMERS** for rewind, ex G.P.O., with laminations and wire, 500 watt size, 17/6.

**LIGHTING PLANTS.** Villiers 550 watt sets, 2 h.p. engine direct coupled to 18 volt 30.5 amp. dynamo with switchboard in steel cabinet, £22/10/-.

Pelophone 500 watt water cooled 1 h.p. engine, coupled to 50/70 volt 10 amp. dynamo, £35.

Chore Horse 300 watt single cylinder 4 stroke engine direct coupled to 12 volt dynamo with switchboard, £17.

**MOTORS.** A.C. 50 cycle single phase 1/2 h.p. 230 volts, 1,425 r.p.m., new, £5/10/-, 1/4 h.p. 230 volts, capacitor start, 1,425 r.p.m., new, £9/10/-, 50 cycles single phase G.E.C. 1/2 h.p., 1,425 r.p.m., £4/10/-, Crompton Parkinson, £4/10/-, A.C. 50 cycles 3-phase motors, 1/2 h.p., 1,425 r.p.m., 230 volts, new, £7/10/-.

**FANS.** Keith Blackman 400/440 volt 3-phase 50-cy. A.C., with 10in. blade, £4. 24 volt D.C. Wall or Table fans, G.E.C., with 6in. blade and guard, £2/5/-, 220 volt D.C. Sterilizair Fans, for ceiling fitting, 10in. blade in copperoxy bowl and fixing chains, £3. 220 volt A.C. Table Fans, 10in. blade and guard, 45/-.

**DYNAMOS.** D.C. 12 volt 10 amp., totally enclosed car type, 1,400 r.p.m., 40/-, 12 volt 30 amp., 2,500 r.p.m., 25/-, 30 volt 5 amp., 1,500 r.p.m., 35/-, 24 volt 20 amp., 1,200 r.p.m., £12/10/-, Carriage on any dynamo, 5/- extra.

**FREQUENCY METERS.** 230 volt, 6in. Ironclad Switchboard Meters, 40/60 cycles, £4/10/-.

**A.C. METERS.** 5in. dia. Switchboard mounting, 0-300 volts 50 cy., 35/-, 0-50 amp. to match, 35/-, G.E.C. Meters, A.C., 50 cy., 0-40 amps Ironclad Switchboard mounting, 35/-. Voltmeter to match, 0-60 volts, 35/-.

**PORTABLE A.C. METERS.** 6 1/2in. x 6 1/2in. x 4in. luminated dial mirror scale, 0-50 amps and 0-75 volts, 40/- each.

**RADIO SUPPRESSORS.** Choke and condenser type, in iron box, 2-way, 5/- each; 3-way, 7/6 each.

**IRONCLAD SWITCHGEAR.** We have a large stock of Ironclad Fuses and Switch Fuses by leading Makers, 15-30 and 60 amps. Write for special leaflet "W.W."

**ROTARY SWITCHES.** 10 amp. D.P. on-off on porcelain base with bakelite cover and knob 3/6.

**VARIABLE RESISTANCES.** Wire wound, 10 ohms, 3 amp., 12/6. 1.5 ohms 15 amp., 7/6. 6 ohms 6 amp., 17/6. Small radio type, 10 ohms 1 amp., 2/6.

**MAGNETS.** Swift Levick S.L.36 instrument type, circular horseshoe 1 1/2in. dia. 1/2in. thick, 1/2in. polar gap drilled poles, weight 2 ozs., lift 3 lbs., 2/6 each, or 12/6 for six. The Alni disc magnet, the wonder midget magnet, 1/2in. dia., 1/2in. thick, 3/16in. hole in pot with keeper, 3/6. D.C. Electro Magnets, weight 10 ozs., lift on 2 volts 1 1/2 lbs., 4 volts 3 lbs., 6 volts 4 lbs., 5/-, Permanent flat bar magnets, 2 1/2in. x 1in. x 1/2in., drilled two holes each end, 2/- pair. Large stock of Horseshoe Magnets. Send for special leaflet, "W.W."

**PARCELS.** 10 lb. useful oddments for the junk box. All clean, dismantled from Government and other surplus apparatus, 7/6 post free. (For home buyers only).

Please include postage for mail orders.

**ELECTRADIX RADIOS**

214 Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

**DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND**

**B**BATTERY chargers, 2-6-12volts, 1-amp. enclosed steel case with ammeter, a.c. mains operated; 42/6.—Thames Valley Products (W), 28, Camden Ave., Feltham. [4264]

**P**PETROL and T.V.O. charging and lighting sets, 12volt; no a.c. plants at moment; new Douglas 349cc ohv engines, air-cooled, complete on stand, £20 and carr.; J.A.P. engine, No. 2a, 1.2hp, air-cooled, new, £14, delivered; 14-32v 230watt, with or without control box; 6v 5amp-hour batteries, unused, £3/10 delivered; inquirers kindly state exactly what you are interested in; see displayed advertisement on page 68 for S.T.O. rectifiers. Please note: Closed for stocktaking 2nd-7th Jan., 1950.  
 PEARCE, 66, Gt. Percy St., London, W.C.1 [0014]

**NEW TEST EQUIPMENT**

**D**ID you see the new Amplion test-meter at Radiolympia? A.C., D.C. and ohms, 1,800 o.p.v., 10 ranges, handy pocket size, for 67/6 (post 1/-), 5,000v test prod., 9/6 extra; this is a high-class, accurate moving-coil instrument.—Westmead Radio, 117, Westmead Rd., Sutton, Surrey. [4615]

**O**SCILLOSCOPE and Wobbulator complete. £20; T.B. c/s 10 to 350,000 c/s X and Y plate amplifiers, easy to handle, with immediate performance, fully guaranteed, immediate delivery with set of leads and booklet. "Oscilloscope Technique"; further details from the manufacturers.—Erskine Laboratories, Ltd., Scalby, Scarborough. [3456]

**TEST EQUIPMENT—SURPLUS AND SECONDHAND**

**E** & V bridge megger, in leather case, as new; £20.—Ealing 0521. [4683]

**5**ma. instrument rectifier, 2/6.—A.C., Stansfield, 230, Park Lane, Kighley, Yorks. [4756]

**T**AYLOR model 30A oscilloscope, in new condition, £18 or offers.—Box 1118. [4758]  
 VO oscillator, 95kc/s to 80mc/s, a.c. mains. A perfect, £6.—1350 Stratford Rd., Birmingham, 28. [4694]

**T**AYLORMETER 70A, 50 range, 1,000 o.p.v.; also Junior 120A, both unused; offers.—34, Coleridge Ave., Sutton, Surrey. [4616]

**W**ESTON Analyser model E772, 1,000 ohms per volt, in portable case, as new, £10; carriage paid.—76, Burlidge Rd., Chell, Stoke-on-Trent. [4644]

**C**OSSOR d.b. scope model 339, in good order, with 2 spare c.r. tubes, £27/10; Avo electronic test meter, as new, £25.—Coffin, High St., Selsey, Sx. [4740]

**C**OSSOR oscilloscopes, d.b., £27/10; s.b. with X and Y amplifiers, £37/10; output meter, Bulgain, 40 ranges, £5 Avomitors, a.c. d.c., £5; d.c. in case, £2/10; Taylor 65B, £12/10; all in new condition.—7, Wallis Ave., Lincoln. [4746]

**W**ESTON 20,000 o.p.v. selective analyzer, £20; Triplett 20,000 o.p.v. multi-meter, D.C./A.C., £10; Avo valveter with 1.4v attachment, £10; Avo capacity/resistance bridge, £8; Hunts CRB capacity/resistance bridge, £9; Taylor 30A oscilloscope, £20; Eta "A" motor driven coil winder, double end drive for potentiometer strips, re-set counter, complete, £19; all in perfect order.  
 WANTED, late model H.E.O.'s with or without coils and power packs.—Cosmic Radio, Ltd., 129, Oxtord Rd., Birkenhead. [4635]

**S**TROMBERG-CARLSON trigger oscilloscopes. S. U.S.A. make, brand new with 5in CRT and 3 valves—4X6S7, 2X6X6, 2X6X7, 2X6X7R, 150-30, 6AC7, 5Y4 and 2X2. Controls for signal intensity; TB frequency; velocity; TB shift; intensity; focus; sensitivity and pulse sync. Mains input 115/230v 50c/s; case 2 1/2in X 1 1/2in X 1 1/2in. Complete with circuit diagram and instructions for 15 minute modification to self running time base. Price £12/10, carriage paid.  
 FRITH RADIOGRAPH, Ltd., 69-71, Church Gate, Leicester. [0025]

**TRANSMITTING EQUIPMENT**

**H**ALLICRAFTER transmitters, Type HT4E (BC610), complete to makers' latest specification, covering all frequencies from 1mc to 30mc, complete with speech amplifier, connecting cables, etc.; limited quantities only now available.

**P**ANORAMIC adaptor, Type MCA44. British-made, suitable fitment to any good-class communication receiver, in addition to all Hallicrafter models, immediate delivery.

**H**IGH-FADE under Hallicrafter licence, SX42 receiver, now available for export only.  
 McELROY-ADAMS MFG. GROUP, LTD., 46, Greyhound Rd., London, W.6. Tel. Fulham 1802. Cables, Hallicraft, London. [4114]

**NEW GRAMOPHONE AND SOUND EQUIPMENT**

**M**AGNETIC 1/4in TAPE recording heads, standard model record-playback with split winding for bias and 5 or 15c1 audio, 30/- each, erasing heads, 30/- each.  
 HI-FIDELITY 1/4in tape heads, circular Mu-metal laminations stacked 1/4in, fully screened, single unit (record-play), £4/10; twin unit with tape lifting (record-play and erase), £9; full assembly (record, play, erase) with tape lifting £14; impedance 1/2 or 15c1 to order, bias winding, for 75T osc. sec. coll.; 1/4in Emitape, 3,000ft., £4/10; osc. coils, 15/-; circuits supplied free. Trade enquiries invited.—Morecambe Sound Service, 4-6, Green St., Morecambe. Tel. 1161. [4464]

**ALLEN COMPONENTS LTD.**



**Type 300 3-wave band coil unit.**

A reasonably priced assembly of exceptional performance consisting of switch, complete set of aerial and oscillator coils with all associated trimming and padding condensers. Improved aerial coupling system gives high sensitivity with exceptional discrimination against unwanted signals. A four position switch gives facilities for gramophone pick-up connection and RF muting. Suitable for use with any of the standard frequency changer valves and an IF frequency of 455Kc. Calibrated glass scale available.

Ranges : 16-50, 190-550, 800-2100 metres. Type 300B : 11.0-26.0, 30-90, 190-550 metres.

Television: Scanning yokes, Focus coils, Line output transformers and EHT transformers approved for Electronic Engineering television.

**ALLEN COMPONENTS LTD.**

Tower Road, Willesden, N.W.10

Telephone: Willesden 3875.

**NEW GRAMOPHONE AND SOUND EQUIPMENT**

**I**NFINITE baffle corner deflectors, scientifically designed acoustic chambers for 8 to 15in speakers; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tomland, Norwich. [2904

**T**APE recording; an entirely new, simple and efficient method of recording is now becoming generally available; we are now publishing a booklet describing the system in simple terms and we can supply recording heads and other essential components for the construction of suitable equipment; private and trade enquiries invited.

**A**DDIGRAPH, Ltd., 7, St. Peter's Place, Birmingham, 1. [4509

**N**EW super Collaro RC49 a.c. mixed auto-changer, in black and chrome, with hi-fi crystal pick-up, repeat, reject mech., price £14/6/8, carr. paid; the Collaro AC47 centre-drive gram. motor, non-magnetic turntable, ideal for moving-coil pick-ups; etc., variable speed, £5/18/4, carr. paid; Collaro AC504 gramophone unit, motor, pick-up (latest magnetic type), and autostop, fixed speed (78 r.p.m.), 10in turntable, £5/3/2, carr. paid; the Marconi AC100 auto-changer, plays 10 records, 10 or 12in (not mixed), fitted high fidelity lightweight pick-up, price complete with pick-up transformer, £10/10/8, carr. paid; N.R.S. de luxe microgram, comprising Collaro AC504 unit, 4-watt amplifier and twin speakers, in rexine covered portable table cabinet, 17in X 15in X 9in, £15/10, carr. paid, cabinet only, £2, terms c.w.o. or c.o.d.; W.W. list 244d—Northern Radio Services, 16, King's College Rd., Swiss Cottage, London, N.W.3. Primrose 8314. [0004

**GRAMOPHONE AND SOUND EQUIPMENT —SURPLUS AND SECONDHAND**

**P**LESSEY record changer, a.c., 10in and 12in mixed, as new; £9/10.—Box 1028. [4696

**S**T.C. m/c. ball milkes, unused; £4; list £16.—32, Chester Ave., Twickenham, Middx. [4748

**B**RIERLEY armature pick-up, JB/P/A, and transformer, unused; £6.—10, Calder Ave., Walsall. [4748

**H**ARTLEY TURNER P.U. unused; 75/-.—McRoble, 18, Firshaw Rd., Hoylake, Cheshire. [4602

**F**OR sale, 2 B.S.R. DR35 recorders, perfect; may be seen London; nearest offer £90 each.—Box 106. [4618

**C**OLLARO mixed auto changer, £11; Lexington Senr. lead and arm, £2; both as new.—Tucker, Ham. 5264. [4700

**R**UCO model A tuning unit less valves, £6; Plessey record player, inner-tip control, £4; both as new.—Box 1065. [4718

**N**EW wire recorder for sale, type A model by Bosey and Hawks with Bosey spool, foot and hand attachments, earphones, etc.; what offers?—Write Box 1026. [4687

**R**ECORDING equipment (studio), twin turntables (13in), amplifiers, speakers, mike, etc.; view London by appointment.—Box S.O., c/o Bartlett's, 31, Museum St., W.C.1. [4678

**M**AGNETIC sound recording wire, stainless steel, temporary wooden spools approx. 1½ hours' running time at 2½ per sec.; 14/- per spool.—A. Smart, 40, Grange Rd., Halesowen. [4669

**R**ADIOGRAM, rebuilt with 40 watt output, autochange light-weight pickup, suitable restaurant or small dance hall, will feed large external speaker, beautiful pre-war cabinet; £150.—Box 1068. [4724

**M**.S.S. recording unit, B.S.R. P.A. amplifier. R.V.A. ribbon microphone and stand, 2 10in speakers, guaranteed perfect condition; £85 or nearest offer.—Hart & Churchill, Ltd., 24, Wellington Place, Belfast, N.I. [4669

**R**ECORDING amplifier, 25 watt 5-channel input, all mixed, built-in monitor amplifier, pre-amp heaters, d.c. fed, many special refinements; £50 or near offer.—Goddards Sound Studios, 686, Fulham Rd., S.W.6. Pat. 3242. [4653

**A**MPLIFIER, Williamson circuit with gram pre-amp, £10; 2 RF pre-tuned feeder, £5; Sound Sales phase inverter, L.S., £7; Barker 148in corner cabinet to maker's specification (cost £32), £20; all in perfect condition.—Box (London) 1016. [4649

**T**RIX T.633 B radio, gramophone, amplifier; recently completely overhauled and new in 1947, all in good condition; also Goodman's 12in 20watt speaker in temporary cabinet, nearly new; what offers?—Wade, The Mill, Doccumbe, near Moreton Hampstead, Devon. [4776

**P**UBLIC address system, all equipment for sale comprising twin 50-watt amplifiers and H.M.V. turntables, 8 speakers, 2 m.c. microphones with stands, 3 Lucas 12v batteries, 25-0 watt Ward Rotary converter, 500 records, cost over £375; accept £145 for quick sale.—Wilson, 45, Earls St., Thetford, Norfolk. [4699

**NEW COMPONENTS**

**T**RANSFORMERS to exact specification.

**L**INE O/P trans., for W.W. television, 45/-; O/P trans., for Williamson amplifier, 75/-; mains trans. for Williamson pre-amp and radio feeder unit, 60ma O/P, 28/6; television filament trans., 6.3v 8amp and 2, 4, 6.3v 2amp, 28/6; tag panels fitted as specified, trans., for amplifiers, television valve testers, test gear, chargers, etc., to any published specification, or to your own design.

**E.P.D. TRANSFORMER PRODUCTS, 31, Queenstown Rd., Battersea, S.W.8. Tel. Mac. 4180. [4579**



**CHARGERS CHARGER KITS RECTIFIERS**

**L.T. AND H.T. NEW GOODS WITH FULL GUARANTEE**

**CHARGERS, CHARGER KITS, RECTIFIERS L.T. AND H.T.** New goods with full guarantee, sent carefully packed, please add postage.

**FOOLPROOF CHARGER KITS** with full instructions. Standard Kit, 12 v. 3 amp. S.T.C. selenium rectifier, 80 watt high grade transformer, ballast barettor for 2 v., 6 v., 12 v. charger, 46/6 post 1/4. Ditto but 2 amp rectifier and 46 watt trans., 36/8. Ditto, but 2 v., 6 v. only 35/-. Minor kit for 6 v. 2 amp and 12 v. 1 amp. 33/-; or with handsome black crackled case and small parts 42/-. Charger Kit as No. 1 but 6 v. 4 amp. also charges 12 v. at 2 amp, 48/6. Medium Duty Kit 12 v. 4 amp. rectifier 78 watt trans and ballast barettor for 2 v. 6 v., 12 v. charger, 52/6. Specially manufactured steel cases ready drilled with screw terminals etc. for 3 amp, 4 amp above 17/6 for 2 amp. 15/-

**TRICKLE CHARGER TRANSFORMER AND RECTIFIER.** 2 v. 0.5 amp. 12/6, post 6d. Heavy duty charger kit. 12 v. 4 amp. rectifier, 100 watt transformer slider resistance, high grade anmeter for 6 v., 12 v., only 75/-, post 2/-. Or ditto, but 6 amp. max. with giant finned rectifier, 95/-. For radio cells, kit of transformer rectifier ballast bulb for 1 to 20 cells at 1.3 amps., 24/18/-. For continuous running, **CHARGERS.** Slider type as illus., 6 v., 12 v. 4 amp. max. weight, 22lb., £5 17/6. Plus 7/6 crate, 5/- carr. "Automat" Heavy Duty home charger for 6 v. or 12 v. output 2 amp. vt. 8½lb., 65/-. Or minor 6 v. 2 amp/12 v. 1 amp. 50/-, or 12 v. 1.5 amp. 55/-. All with 12 months guarantee. "Automat" 5 amp charger for 6 v. or 12 v. 27/5/-, weight 23lb.

**ELIMINATOR KIT,** for 120 v. 40 mA. eliminator, trans., h.t. rect., 2 v. trickle rect., 2 x 8 mfd. condensers, 35/-, case 7/6. **SLIDER RESISTANCES,** 1 ohm, 10amp. 16/-; 0.5 ohm, 20 amp. 12/6; 10 ohm, 3 amp. 27/6; High grade 0-6 amp ammeters, 12/6 post 6d.

**RECTIFIERS.** S.T.O. 12/16 v. 3 amp., 17/6; 4 amp. 21/-; 5 amp. 26/6; Giant finned type 6 amp. 29/8; 10 amp. ditto, 42/-; also 6 v. 4 amp 16/8; 6 v. 10 amp. 25/-; trickle types 12 v. 1 amp., 8/6;

**CHAMPION PRODUCTS**

43 Upland Way, London, N.21 Phone: LAB 4457

**AMERICAN MALLORY "VIBRAPACKS"**

**Special offer of Model G366A. Input 12 Volts. Output 110-120 Volts D.C.**

Besides the usual applications, have you thought of carrying your domestic 110-volt AC/DC midget radio in the car? If you don't make it a fixture you don't need a separate licence! Useful also for dry shaving in car or boat.

Fully screened, very compact, only 5½ in. long, 2½ in. wide, 5 in. high. Incorporates Power Transformer, plug-in synchronous Vibrator, buffer and bypass Condensers, RF Choke, etc. Limited quantity available at this clearance price of 12/9 each, post paid. Despatched immediately on receipt of order and remittance, subject to being unsold.

**WIRELESS SUPPLIES UNLIMITED**

264-266, Old Christchurch Road, Bournemouth, Hants.

**-towards perfection-**

**LOWTHER Diamond, Moving-Coil PICK-UP**  
(Licd., Pat. No. 538058)



Equalled only in precision by the cutting head which creates the recording. Enjoy the finesse of modern reproduction with a Lowther Pick-up. £18 with Diamond styli plus P.T. Selected t/carbide styli £9 plus P.T. Equaliser Unit 20.T.C. £2 10 0. Transformer Unit 20.T.C. £1 17 6.

Full descriptive leaflet, write:—

**THE LOWTHER MANUFACTURING CO.**  
(The Laboratory Production Unit.)  
Lowther House, St. Mark's Road, Bromley, Kent RAV. 5225

**NEW COMPONENTS**  
WIRELESS World televisors

FOR approved components all enquiries should be addressed to the makers. "Handyparts," 226-228, Merton Rd., Wimbledon, S.W.19. Lib. 7461. S.a.e. for replies. 10033

THE simplest s'het pack, type M1, M.L. waves. 22/6; thousands in use.

DOUGLAS COIL Co., Brinklow, Nr. Rugby. CRYSTAL microphones inserts (cosmo cord MIC-6), guaranteed brand new, 15/6 post free.

RADIO AID, 29, Market St., Watford. Tel. 5988. 10036

WILLESDEN high quality transformers available ex-stock for the D.T.N. Williamson Amplifier, Electronic Eng. Televisor, and all well-known circuits.

WILLESDEN TRANSFORMER Co., Ltd., 781, Harrow Rd., N.W.10. Tel. No. Ladbroke 2846.

THE brain of any good radio is an Osomor Q coilpack, used with our matched components you can build a radio really worth boasting about, write to-day for the circuits and our latest lists, including the Bargain Bulletin.

OSMOR RADIO PRODUCTS, Ltd., Bridge View Works, Borough Hill, Croydon. (Cro. 1220.)

WIRELESS WORLD televisor, deflector coil assembly, 22/-; focus coil, 25/-; block. OSC trans., 7/6; Bel superhet coils, London or Birmingham, 22/6; V.R.11 valve slug, chassis kits, E6; rectifier H4/200, 28/-; R. F. Shilton, 19, Clarendon Rd., Salisbury, Wilt. 14608

TWO-VALVE s/h.t. receiver, a two-valve a.c., two-wave, superhet receiver with the performance of a normal 4 or 5-valve set, complete kit of parts with fullest instructions for assembly, complete to last nut and bolt, speaker and valves included, less only cabinet; 8s. From

RADIO COMPONENTS, East St., Darlington. 14766

TELEBOOSTERS for long range television reception, super high gain single-stage pre-amplifier, 2-stage, V.R.11 valve slug, tuned London or Birmingham, co-axial plugs and sockets flying leads for high and low tension, fully screened, low noise, price £2/12/6; power units for above, £3/10; s.a.e. for trade test report.

BOSCOMBE RADIO & ELECTRIC, 595, Christchurch Rd., Boscombe, Bournemouth. Tel. 36522. 10032

4/8 only for the famous Model 30 tuning 50 unit, consisting of 3-waveband Model 50 superhet coil pack, pair I.F. transformers, 2-gang condenser and attractive dial (8in x 6in); each component individually selected pre-aligned, sealed and the whole matched together as a unit; the superhet you build with this unit needs no further adjustment! Full details of this unit, including wiring diagrams (coils, I.F.T.s, mains transformers, etc.), together with many circuits and constructional tips, contained in the "Home Constructor Handbook," price 1/-. Mail order office.

SUPACOILS, 98, Greenway Ave., London, E.17.

TELEVISION.-Bel p.m. focus rings, self-supporting, micrometer adjustment. Ticonal magnet, chrom. finish, all tubes 9 or 12in, with instructions, 35/-; Coils: EE Birmingham, 18/6; ditto less chokes, 16/6; EE London, 15/-; Wireless World s'het, 1 or b., 20 coils, 52/6; set of 10 coils for the newest televisor, 16/-; booster choke, 4/6; chrome, 1/6; valve kits, with v/h and grommets, 57/6; as foregoing but with our own mod. for Mid and freq., whole set, 29/6; W.W. s'het chassis kits, copper and aluminium, semi-drilled, including 2 r.f., 2 timebase, 1 v.f. chassis, 11 screening boxes, 66/- alternatively, 2 r.f. chassis only with 17 associated coils, £3 plus 2/6 per screening box; W.W. deflector coils, exactly to spec., 35/-; r.f. e.h.t. osc. coils, £1, c.c.t. supplied; Williamson r.f. feeder unit, 7/- set of 2 coils.

BEL SOUND PRODUCTS Co., Marlborough Yard, Archway, N.19. North 1025. 14745

**COMPONENTS-SURPLUS AND SECONDHAND**

SOUTHERN RADIO'S wireless bargains:

PERISCOPIES ex-U.S.A. type M8 complete brand new with telescope, 17/6; crystal detectors, 2/6; telephone line units complete in polished wooden case with relays, rectifiers, etc., 5/-.

RECEIVERS R28/ARCS complete with 10 valves 100/156 meg. brand new and cartoned with circuit, 50/-; moving coil headsets, headphones and microphone attached, 7/6; transformers 1:1 ratio, 2/6; microphone transformers 50:1, 3/6; Lucas inspection lamps with lead and plug, 2/6; carbon microphone inserts, 2/-.

T.R.1196 Receivers, complete with 6 valves, with circuit, 22/6.

DINGHY transmitters T1333, complete in transit cases, 55/-; thousands of other lines for callers, please see display advertisement; full publication list, 2/6d.

SOUTHERN RADIO SUPPLY, Ltd., 46, Lisle St., London, W.C. Gerrard 6653. 10016

FRAME aerials, M.L. chassis mounting, 94in x 54in, 7/6; manufacturers' surplus midket L.F. chokes, 2/6.

HILLFIELDS MAIL RADIO, 8, Burnham Rd., Whitley, Coventry. 10022

TELEVISION, all parts in stock for EE televisor. Haynes scan and focus coils; line trans. model on view.-H.G. Radio, 1350, Stratford Rd., Birmingham, 28. 147418

WAGNET cabinets, 20/-; steel chassis, 12x6, 2/6; octal valves, 3/- doz.; resistors, 50 4/6; condensers, 2/6 doz.-Sparrow, 28, Lancaster Gdns., Clacton-on-Sea. 14638

# GALPINS

## ELECTRICAL STORES

408 HIGH STREET, LEWISHAM, LONDON, S.E.13

Telephone: Lee Green 0309. Near Lewisham Hospital.

TERMS: CASH WITH ORDER. NO C.O.D.

THURSDAY EARLY CLOSING

**ELECTRIC LIGHT CHECK METERS** (watt hour type), all for 200/250 volt A.C. 50 cycles, all electrically guaranteed: 2 1/2 amp. load, 15/- each; 5 amp. load, 18/6 each; 10 amp., 21/-; 20 amp., 25/-; 30 amp., 30/-; 40 amp., 35/-; 50 amp., 42/6; 100 amp., 50/-. Carriage on all types 2/- extra.

**SWITCHBOARD PANELS** containing 3 VARIAC Transformers 100/120 watts 0 to 110 volts, also (1) Synchronous Motor operating Relay contacts approx. 40th h.p., also numerous large type mains toggle switches, a few only to clear, 75/- each. Please note that the wire on one only of the Variacs is damaged, please allow 5/- carriage.

**EX-NAVAL TELEPHONE HANDSETS, BAKELITE PATTERN** (self-energized) no battery required, complete with wall bracket (new), 15/- per pair, post 1/6. Ditto, complete with Buzzer ringing mounted in weatherproof box, 24 volt required for energizing Buzzer only, complete with Hand-set, 15/- each, or 25/- per pair.

**LARGE TYPE RECTIFIERS.** Output 50 volts 1 amp. D.C. input 70/75 volts A.C. Half wave type, 8/6 each, post 1/6. TANNON P.M. SPEAKERS (Small Hailers), 4 ohms speech coil, complete in wooden case with output transformer, 15/- each, carriage, 2/6.

**EX-W.D. ROTARY CONVERTERS** by well-known makers, 24 v. D.C. input, 50 v. 50 cycles, 1 phase 500 watt output, £6/10/- each.

**MAINS TRANSFORMERS.** 230 v. input, 300 v. 150 mA. C.T. 6.3 v. 8 amp. 5 v. 2 amp., 15/- each.

**EX-NAVAL CATHODE RAY INDICATOR POWER UNITS** (new). Sold for component parts only, consisting of approx. 150 Resistances and Condensers of various values, H.V. Condensers, Chokes, all mounted on solid brass chassis, weight 90 lb., to clear, 25/- each, carriage forward.

**PRE-PAYMENT 1/- SLOT ELECTRIC LIGHT CHECK METERS.** 200/250 volts, 50 cys. 1 ph., 2 1/2 amp. load, 30/- each, carriage 3/6; 5 amp. load, 35/-; carriage 3/6. 10 amp. load, 42/6 each, carriage 3/6.

**EX-R.A.F. ELECTRIC TESTERS** (new). These consist of a Ferranti 0 to 450 mA. 2 1/2in. scale meter shunted to 1 mA., incorporated Westinghouse Rectifier, the whole encased in polished teak case, calibrated at present 0 to 10 v., 25/- each.

**MAINS TRANSFORMERS,** all 200/250 v. 50 cys., 1 phase input, output 700/0700 v. 70 mA., 4 v. 2 1/2 a., 12 v. 1 a., 30/- each. Another 525/525 v., 150 mA., 6.3 v. 5 a., 5 v. 3 a., 37/- each. Another 2,350 v. at 500 mA., 85/- each. Mains Smoothing Chokes, 10 Hy. 100 mA., 6/-; 150 mA., 8/6; 350 mA. 25/-; 5 Hy. 250 mA., 17/6.

**MAINS TRANSFORMERS,** input 200-250 v., 50 cycles, in steps of 10 v. Output 450/0/450 v. 250 mA., 4 v. 4 a., 5 v. 4 a., 6.3 v. 8 a., 6.3 v. 8 a., 62/6. Ditto 450/0/450 v., 250 mA., 6.3 v. 4 a., 5 v. 4 a., 4 v. 8 a., 4 v. 8 a., 60/- . Another 500/350/0/350 500 v. 250 mA., 6.3 v. 8 a., 0, 4, 5 v. 4 a. twice, 6.3 v. tapped at 2 v. 2 a., 67/6. Another 350/0/350 v., 300 mA., 4 v. 8 a., 4 v. 4 a., 6.3 v. 4 a., 6.3 v. tapped 2 v. 2 a., 57/6. Another 500/0/500 v., 300 mA., 6.3 v. 8 a., 6.3 v. 8 a., 6.3 v. 4 a., 4 a., 5 v. 4 a., 67/6.

**MAINS TRANSFORMERS** (Auto Wound). Voltage Changers tapped 10, 20, 25, 90, 130, 150, 190, 210 and 230 v., all at 1,000 watts, a combination of 24 voltages can be obtained from this transformer, new ex-Government Stock, £5/10/- each, carriage 5/-. Mains Booster Transformer, tapped 0, 6, 10, 19, 175, 200, 220, 225, 240 and 250 v. at 1,500 watts (new ex-Government), £5/5/- each, carriage 5/-. Another Auto Wound, tapped 0, 110, 150, 190, 210 and 230 v. at 1,500 watts, £6/10/- each, carriage 5/-. Ditto, 2,000 watts, £7/5/- each, carriage 5/-.

**MOTOR ALTERNATORS.** Ex-Government, as new, 230 v. A.C. 50 Cycle 1 ph. input, output 250 v., 1,725 cys., 1 phase at 0.4 amps. output separately energised from 24 v. at .04 amps D.C., price 75/- each, carriage paid.

**MAINS TRANSFORMERS.** 230 v. input 50/1 outputs 3 x 4 volt windings at 4/5 amps, 15/- each, post 1/-. Another 230 v. input with 2 x 6.5 volt windings at 5 amps, 15/- each. Another 230 v. input 12 v. at 12 amps. output, 30/- each.

**D.C. MOTORS** 110/220 v. rated at 1/12th h.p. with laminated fields suitable when fields re-wound for A.C. Mains, 22/6 each. Another 110 v. approx. 1/2 h.p. D.C. only shunt wound, 10/- each. A.C. Motors name plate reads 230 v. 50 cys. 1 ph. 180 r.p.m. 5 output leads connections not known. Sold as rewinds, 50/- each.

**EX-R.A.F. NO. 6 AMPLIFIERS** for use with 2 P x 4 valves output, these units contain both input and output Transformers, output Meter 0 to 150 mA. wired already for use less Valves and Power Pack, 32/6 each.

**PETROL DRIVEN HOUSE** lighting plants 1,260 watts at 36 v., complete with Switchboard containing 5 Meters v./amps. and Variable Resistances may need slight attention, £22/10/- each (3 only to clear special price quoted taking the lot).

**POWER TRANSFORMERS.** Auto Wound Voltage changer tapped 0, 110, 150, 190, 230 v. to carry 1,600 watts, £5/5/-. Ditto, 2,000 watts, £6/5/-. Another of a 1,000-watt rating with a range of 32 varofous tappings from 5 to 230 v. including 110 v. All tappings at a 1,000-watt rating, £5/15/- each. Another 115 to 230 v. or vice versa at 1,000 watts, £4/15/-. Another, double wound, 4,000 watts, 130 to 250 v. or vice versa, weight 100lb., £10 each, carriage paid.

**EX-U.S.A. HAND DRIVEN GENERATORS,** complete with all smoothing output 450 v. 110 mA., also two L.T. tappings, as new, 25/- each. Ditto, 160 v. at 60 mA., Output 1 l.t., tapping, 20/- each D.C.

**STUD SWITCH-ARM** type Dimmer Resistances 2,700 Ohms, to carry 1/2 amp. protected, 17/6 each. Ditto, unprotected 50 Ohms to carry 1.4 to 9 amps., 35/-. Another 10 ohms to carry 9 to 14 amps., 32/6 each.

**EX-R.A.F. CRYSTAL MONITERS,** less crystal and valves. These units contain many useful parts, Transformers, Condensers, Resistances, etc., the basis of a Midget receiver all contained carrying case (new), to clear, 5/- each, carriage paid.

**ISENTHAL MAINS VARIABLE DIMMER RESISTANCES.** W.W. control 60 ohms, max. 2 1/2 amps. as new, 27/6 each. Ditto Zenith slider variable resistances, protected type, 1,500 ohms to carry 0.45 amps., 32/6 each.


**SWITCHBOARD AMPMETERS,** 4 1/2in. 0-14 amps. AC/DC, 25/- each.

**EX-G.P.O. GALVANOMETERS,** vertical type reading 30.0-30, 8/6 each.

**EX-R.A.F. ROTARY CONVERTERS,** 100 volts D.C. input, 50 or 100 volts, 500 cycles, 1 phase at 300 watts output, 82/6 each, carriage paid.

**MAINS TRANSFORMERS,** input 200/250 volts in steps of 10 volts, output 425/0/425, 150 mA., 6.3 volts 3 amp. twice, 5 volt 3 amp. (Williamson amplifier), 39/6 each. Another (Electronic Engineering) output 350/0/350 volts 300 mA., 4 volt 8 amp., 4 volt 4 amp., 6.3 volt 6 amp., 6.3 tapped 2 volt at 2 amps., 57/6 each. Another, 350/0/350 volts 180 mA., 5 volt 3 amps., 6.3 volts 4 amp., 4 volts 4 amp., 37/6 each. Another, 500/0/500 volts 150 mA., 4 volt 4 amp., 5 volt 3 amp., 6.3 volt 4 amp., 42/6 each.

# OPPORTUNITIES IN RADIO

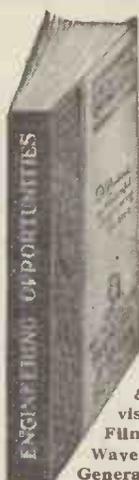

Get this FREE Book! "ENGINEERING OPPORTUNITIES" reveals how you can become technically-qualified at home for a highly-paid key-appointment in the vast Radio and Television Industry. In 176 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of TELEVISION and RADIO, A.M. Brit. I.R.E., A.M.I.E.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.

We definitely Guarantee "NO PASS—NO FEE"

If you're earning less than £10 a week, this enlightening book is for you. Write for your copy today. It will be sent FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

388b SHAKESPEARE HOUSE 17/19 STRATFORD PLACE, LONDON, W.1



# SOUTHERN RADIO'S WIRELESS BARGAINS

T.R. 1196. Six valve Super-het Receivers. Complete with Circuit, 22/6.  
 CRYSTAL MONITORS. Complete in case, less Crystals, 6/-. With two crystals, 16/6.  
 CRYSTALS. American and British 2-pin types from 2040 kc/s to 38 mc/s, 8/- each. Twelve assorted frequencies, 60/-  
 SECTIONAL AERIALS. 8ft. interlocking, 3/6. Base for same, 2/6.  
 BENDIX COMMAND RECEIVERS. B.C. 454 (49-100 metres). B.C. 455 (33-49 metres). Complete with six valves, 35/-, plus 1/6 postage. A few only converted to 28-41 metres for television sound, 50/-  
 CONTROL BOXES, for B.C. 454/4/5. Complete with slow motion dials, Volume Controls etc., 13/6.  
 TRANSMITTER-RECEIVERS. Type 58, Mark I. Complete in original cartons with Vibrator Pack, Batteries etc., 21/6.  
 R.A.F. BOMB-SIGHT COMPUTERS. Complete with Motors, Gyro, Gears, Blowers etc., etc., 55/-, plus 5/- carriage. The best component value ever offered.  
 INDICATOR UNITS. 280a. Complete with 7 valves C.B. Tube, 3BP1 and all components in metal case. Ideal for Oculiscope conversion, 44/-, plus 5/- carriage.  
 CONTACTOR TIME SWITCHES, by Smith or Venner 10-hour movement with thermo-static control. Complete in sound proof case, 10/-, plus 1/4.  
 RADIO COMPASS INDICATORS, with Selsyn motor, 3in. dial, 360 degrees, 13/6.  
 ROTOTHERM METERS. Chromium finish, 6/-  
 BRAZING LAMPS. 5-pint size with extension hose and nozzle, 40/-  
 ALDIS LAMPS. 6in. lens. Complete in transit case with spare bulbs, cable etc., 40/-, smaller size for signalling. Complete in metal case with taper etc., 16/-  
 DELCO HAND GENERATORS. 6 volts at 4 amps complete ready for use, 17/6.  
 LUCAS GENERATORS. 12 volt input to 480 volts D.C., 10/-  
 SLEEPING. 1 mm. and 2 mm., 6/- gross yards. Minimum quantity one gross.  
 LUBERA HOLE CUTTERS. Adjustable from 3in. to 3 1/2in. For use on wood, metal, plastic etc., 5/6.  
 WESTOTHERM Wax and W112, 6/4 per dozen.  
 Thousands of bargain lines for Callers. All goods unconditional guaranteed. Please send 2/4 for full publication list.

Southern Radio Supply Limited  
 46, LISLE STREET, LONDON, W.C.  
 GERARD 6653

## COMPONENTS—SURPLUS AND SECONDHAND

TELEVISION. HANNEY OF BATH Offers:—  
 POLYSTYRENE and Paxolin formers for the "Wireless World" superhet receiver. All other components are available ex-stock; condensers, resistors, Reliance potentiometers, aerials, etc.  
 MULLARD Mw31/14c c.r.t.s. limited number, £15/2/5.  
 MULLARD Mw22/14c c.r.t.s. now available for immediate delivery, £11/6/10 each, pd.  
 CHASSIS in 16 s.w.g. all, 4 sides, 9 sizes; 2, 4 and 6 B.A. nuts, bolts and washers; enamelled copper wire in 1/4, 1/2, 1 or 7/8 reels, 16 to 40 s.w.g.  
 COMPLETE set of parts for the Williamson amplifier, 118ns (less valves), or wired and tested, £25/10 (with valves), guaranteed 2 years. ALL high stability resistors and matched condensers in stock for the new Williamson pre-amp and tone system.  
 B.S.R. gram motors, £3/4/3 inc. tax and the new E.M.I. auto-changer at £9/10/10 inc. tax.  
 WE CARRY comprehensive stocks by all makers of repute; Eddystone, Raymart, Denco, Wearite, T.C.C., B.I., Hunts, Dubilier, Morganite, Reliance, Elstone, Gardner, Goodmans, Avo. Taylor, Fridge, etc., etc., etc.  
 SEND NOW for (a) T.V. list; (b) amplifier list; (c) S.W. list. 2/4 stamp please, for a host of useful literature.  
 L. F. HANNEY, 77, Lower Bristol Rd., Bath., 14535

INTRODUCING the radio constructor's accessory kit.  
 IT'S here! The kit you've been waiting for, no matter how difficult the sound or television receiver you contemplate building, this kit will definitely assist you and give your set a professional finish, here is a list of the contents of every kit:  
 BOX of screws, containing approx. 3lb; box of approx. 1 gross insulating washers; box of resin-cored solder; 12 tag strips and small bakelite panels; box of assorted solder tags; approx. 2 dozen assorted metal angle brackets; an assortment of mounting strips, terminal strips, etc.; several coils of Sleeving and Systonox; various sizes of wire, etc.; only 10/6, carriage paid; send s.a.e. today for details of our special clearance parcels, £20 worth of goods for 21/-.  
 WALTON'S WIRELESS STORES, 203, Staveley Rd., Wolverhampton. [0061]

K. W. LOGAN, Radio, Electrical, Television, 1, West Alley, High Street, Hitchin.  
 CARBON mike, 2/-; headphones, 2/6 pair; throat mike, 2/-; pair; headphones and mike combined, 4/-; new headphones and throat mike, 4/6; Morse key, 1/3; small condensers, 2/- doz assorted; assorted resistors, 6/6 a 100; assorted SW coils, 8/6 doz; 8 ufd condensers, 8/- doz; 4 nfd condensers, 5/- doz; 2 ufd condensers, 3/- doz; 1 ufd, 2/6 doz; 1mm sleeving, 5/- 10yds; 2mm, 4/-; twin braided screened PVC, 6d yd; 7/044 twin trs power cable, 1/6 yd; Selenium rectifiers, 230v 75 m/a, and 140v 150 m/a, 2/- each; 378v 1.2a, 22/6 each; will work dc radio from ac; Coax plug and socket, 9d; 3-wave multi-colour scale, 1/-; octal v-holder, 4d; 12v vibrator, 2/6; control unit No. 16 contains 1 Yaxley-type switch 7w 4b, 1 Yaxley-type switch 5w 4b, indicator m.e.s. holder, knobs, plugs and sockets, etc., 2/6; SLC No. 3 receiver, 20 valves 7 x VR65 6 x VR92 2 x VU39 2 x VR136 2 x VR66 1 x VR127 and 1 J50 rectifier plus dozens of condensers, resistors, IF transformers, etc., all for 30/- or less valves, 7/-; power unit type 297 24v input 12v 200v output 5 smoothing chokes, relay, 5-pin v. holder panel fuse holder 3k ohm v. f resistor 9 output socket 4 x 0l condensers, 4/6 and 2 ufd condensers and stabiliser valve all for 5/6; F107 British Army communication receiver 9 valves 4 x EB33 4 x EP39 1 x 6X5G BFO 3 wavebands, 1.2-3 mc/s 2.9-7.25 mc/s 7-18 mc/s 100-250 volts ac 50cps or 12 volt dc, £10 each.  
 LOGAN, West Alley, Hitchin, Herts. [4692]

LITTLEWOODS, North London's best selection of radio and television components; pay us a visit or post or phone your enquiries; no lists.  
 LITTLEWOOD & GRUNER, Ltd., 27, Ballards Lane, Finchley N.3. Fin. 3060. [10055]  
 VACUUM relays, thermal type 6v 35ma (approx.) will switch 230v 10amps, length 5 1/2in. diam. 1in. fitted with standard 4-pin valve base; 6/6 ea.  
 VELODYNES, Magislp and Selsyns, many types in stock, send for list, technical advisory service available.  
 HOPTON RADIO, 1, Hopton Parade, Streatham High Rd., London, S.W.16. Streatham 6165.

218 MODULATORS, 4 VU111, 1 VU508, 1 CV73, 1 EF55, 1 EF50, 2 EA50, 1 CV125, 1 CV189, 7kv 0.5uf condenser, 4 relays, pots, etc.; new, 57/6.—E and S, 115, Manor Park, London, S.E.13. [4648]

YOU'LL probably get it at Smith's, Edgware Rd. Everything for the constructor, from a 1/10watt resistor to a radiogram cabinet, lowest prices, biggest variety.—Near Metropolitan Music Hall. Pad. 5891. [8005]

0-01, 1000v, 0.1 350v condensers, 3/6 doz; TRF coils with reaction, boxed with circuit, 4/9 pair; 100PF ceramic, 2/6 doz; 50PF + 50PF ceramic trimmers, 5d each, etc.; list from—T. Howell & Co., 29, McWilliam Rd., Brighton, 7. [4721]

16-16 uF, 350v, 2/9; 16-16 uF, 450v, 3/-; 25 uF x 25v 10d, 25 uF x 50v 1/-; mains droppers, 0.2amp, 7170, tapped 1000, 1/-; 0.1 uF, 2/6 doz; electrolytic, 2/-; post free over 10/-.—Hatfield Radio, 78, Stroud Green Rd., N.4. [14763]

# R.A.F. COMPUTER UNIT



A WEALTH OF USEFUL PARTS FOR THE EXPERIMENTER AND MODEL BUILDER including GYROSCOPE, 2 x 27 VOLT MOTORS, 2 REV. COUNTERS, 25 GEAR WHEELS, WORM GEARS, RACK GEARS, etc., etc. 50/-  
 Carriage 5/- Extra.



4 - LIGHT FITTINGS Adaptable for BED WARMERS, FLOOD LIGHTING, etc. 6/-  
 Post Free

Send 1d. Stamp for Descriptive Leaflets of this and Other Bargains. Large Range of Technical Books.

UNIVERSAL BAZAARS (M/c) Ltd. 9/10, Brown Street, Manchester 2. DEA 5009

# BARGAINS

In slightly used Hi Fidelity sound Equipment.

## AMPLIFIERS

Charles "Concerto", 14 gns. Sound Sales 14 watt with T/C unit, 16 gns. Vortexion 15 watt in Rexine carrying case fitted two 10-inch Speakers, 27 gns. Also several other 5-15 watt amplifiers needing slight attention, from 15s.

## SPEAKERS

Barker 148a, £11/10/0. Axiom 12, £5/7/6. Goodmans 12 inch P.M., £4/10/0. Hartley Turner 215, £4/15/0. Sound Sales "Auditorium", £5/0/0. Other offers include, 12in. 1/5. cabinets from 39/6, several light weight pick-ups from 30/- each, Ward Rotary Converter 250 D.C.-250 A.C. with filters, £20/0/0, Radio Feeder Units from £7/10/0.

# HOLLEY'S RADIO STORES

285, CAMBERWELL RD., S.E.5  
 Phone: RODney 4988



**THESE ARE IN STOCK**

**Fundamentals of Radio-Valve Technique.** By J. Deketh. 35s. Postage 1s.  
**Amateur Radio Receivers.** By S. K. Lewer. 3s. 6d. Postage 2d.  
**Basic Television.** By Bernard Grob. 55s. 6d. Postage 1s.  
**Television Servicing Manual.** By E. N. Bradley. 4s. 6d. Postage 3d.  
**The Technique of Radio Design.** By E. E. Zepfer. 25s. Postage 9d.  
**Practical Wireless Circuits.** By F. C. Camm. 6s. Postage 4d.  
**Wire Recorder Manual.** By G. R. Judge. 2s. 6d. Postage 2d.  
**Radio Valve Data.** Compiled by "Wireless World." 3s. 6d. Postage 3d.  
**Principles of Radar.** By M. I. T. 35s. Postage 9d.  
**Fundamentals of Vacuum Tubes.** By A. V. Eastman. 47s. Postage 1s.  
**Radio Engineering, Volume 2.** By E. K. Sandeman. 40s. Postage 9d.  
**The Electronic Musical Instrument Manual.** By Alan Douglas. 18s. Postage 6d.  
**Sound Reproduction.** By G. A. Briggs. 7s. 6d. Postage 6d.  
**The Radio Amateur's Handbook.** By A. R. R. L. 15s. 6d. Postage 9d.  
 We have the finest selection of British and American radio books. Complete lists on application.

**THE MODERN BOOK CO.**

(Dept. W. 1)  
**19-23 PRÆD STREET**  
**LONDON, W.2**

**COMPONENTS—SURPLUS AND SECONDHAND**

**SYNCHRONOUS** clock units, self-starting, 200-250v ac 50 cycle, fitted Sangamo motors, consumption 2½ watts, size 2¼in dia. 2in deep geared 1 rev 60 min. friction reset; ideal movements for making electric clocks, time switches, etc., nickel plated finish, complete with 12 to 1 dial train and 5in sands, price 22/6, post paid; Sangamo as above, final speed, one rev. per min. less dial train, ideal for dark-room process time, etc., price 20/- each, post paid.  
**SANGAMO** motors with gear train, final speed 1 rev 12 mins approx; 16/- each; ditto, final speed 1 rev 1½mins approx; 15/6 each, post paid.  
**TRANSFORMERS:** input 200-230 volts, outputs 350-0-350 80ma, 2-0-2 volts 2.5 amps, 2-0-2 volts 5 amps; 16/6 each, post paid.  
**CLOCK** work; timers, new surplus, suitable for process work; dark-room timing, etc., variable timing 1 to 60 seconds, relay to operate off 6v battery capable of handling 100 watts supplied with each movement; price with relay, 36/- each, post paid; each movement is fully tested before dispatch.  
**CONDENSERS** Electrolytic, 1,000mfd, 25v dc W.K.G.; 4/6 each, post paid; 45/- per doz.  
**RECTIFIER** units, ac to dc, input 200-250v ac, 50 cycles 1-phase, output 160-200v dc, ¼amp; price 41/- each, post paid.  
**SIEMENS** high speed relays, 2,000 ohms, ideal for model control; 6/6 each, 72/- per doz.  
**TYPE 24 R.F. units;** new surplus, in maker's cartons, these make excellent S.W. converters, complete with valves 30 to 40 mc/s, price 15/6 each, post paid.  
**CRATER** rotary switches, 250v 10 amps ac single pole 3-way series; parallel, ideal for photo floods, etc.; price 4/- each or 40/- per doz, post paid.  
**PERFORMANCE** meters type No. 2 fitted standard mains 230v ac, 50 cycle power pack, VR91, 1 VR37, 1 SZ4G, 1 CV51, 1 VR22 and other useful components; £2/5 each, carriage 3/6.  
**AC** mains 230v 50 cycles power packs with variable output, 300v dc at 10ma, to 200v dc 25ma, housed in nicely finished metal cabinet size 11in x 6¼in x 6in complete with SZ4G rectifier, also gives 18v ac ½amp; £2/10 each, post paid.  
**A LARGE** quantity of single items which we do not list, which are available to callers; also assortment of various ex-W.D. radar and radio equipment, relays, power packs, oscillograph units, gears, photographic apparatus; s.a.e. for lists.  
**H. FRANKS, 58, New Oxford St., London, W.C.1.** One minute from Tottenham Court Rd. Station. Tel. Museum 9594. [0057]

**POWER** packs, super quality units, used to drive T1154 and R1155 from 200-250v 50c mains, unit 1, 7x e.h.t. 1,200v 200ma, fully smoothed at 50° C., in compact ventilated steel case 19x18x9½in with handles. £5, carr. 15/-; Unit 2, smoothed d.c. l.t. 6v 13a (ex. heavy charger if smoothing removed), also R.X. h.t., 220v 110ma, smoothed, similar case 19x18x12in. £6, carr. 15/-; selenium rects. through hole Rugged construction, conservative ratings, new, slightly soiled, guaranteed, special offer! Pair £9/19, carr. £1.  
**THE AMATEUR'S DEN, 181, Lake Rd., Ports-mouth.** [4762]

**BRAND** new guaranteed goods, mains transformers, fully interleaved and impregnated, primaries screened 200-250v, 50 c.p.s., drop through taps 200-0-250v 65ma, 6.3v 5a, 5v 2a, 12/11, 350-0-350v 80ma 6.3v 3a, 5v 2a, 15/9; midge type upright mounting 3-2½-3in 250-0-250v 60ma 6.3v 1.5a, 5v-4v 2a, 16/11, fully shrouded upright mounting 350-0-350v 100ma 6.3v 4a, 5v 2a, 27/6, 250-0-250v 80ma 6.3v 6a, 5v 3a (for 1355 conversion), 22/9, 425-0-425v 200ma, 6.3v-4v 4a c.t., 6.3v-4v 4a c.t. 5v-4v 3a, 41/6; Williamson output transformers, exactly to authors' specification, 59/6; electrolytics can 8-8mfd 50v 3/9; Vibrators Ok band 12v 4-pin 4/6; smoothing chokes 80ma 350ohm 12-15 5/6; 100ma 300ohm 10h 5/11; selenium rectifiers 250v 65ma h.w. (midset) 3/9, 250v 90ma h.w. 4/11, 120-0-120v 100ma f.w. 1/9 ea., 16/- doz., 120-0-120v 49ma f.w. 1/6 ea., 14/- doz., 12v 1¼a. h.w. c.t. 1/3 ea., 12/6 doz; send 2½d stamp for full list of bargains; special list for trade; c.w.o. or c.o.d. over £1; postage extra.  
**RADIO SUPPLY CO., 15, Queen Sq., Leeds. 2.** [0003]

**RADIO UNLIMITED, Elm Rd., London, E.17.** Tel. Key. 4813, offer the following spotless, guaranteed, surplus bargains; fresh stock condensers, 8mfd, 450v, 3/-; 8X8, 450v, 3/3; 8X8X8, 450v, 3/6; 8X16, 450, 4/6; 0.1, 500v, 3/- doz.; 2.2 meg pots, 1/-; p/pull hand mic w/switch, 5/6; mic trans 2/6; m/coil hand type m/w/switch, 3/6; alum dilled chassis with valves 6V6, 6K7, 6K8, 6Q7, 5Z4, 37/6; A1134 battery amplifier, with valves, soiled but O.K., 9/6; twin meter test panel, 12/6; m/iron 0-25 ammeter, 2/11; 0-40 m/coil ammeter, 4/6; 0-50volt 4/6; Morse training units with wire, battery and microphone, 8/6; amplifier cabinet, black crackle finish, 15/6; toggle switches 1/3; bal/arm headphones with lead and plug, 4/6; m/coil phone & mic sets, 5/6; 5in P.M. speaker with trans, 11/6; clockwork flasher device 10/-, carrying case battle cabinet for 10in speaker, 21/-; throat mics 2/3; A.C./D.C. 3 plus rec. amplifier, 105/-; headphone matching unit, high to low impedance, 3/6; multi-ratio output trans. 6/6; EF50 holders 6d; chrom pltd mic stand (folding), 29/-; high-grade m/coil mic, listed at 5ms, offered at 42/-; hundreds other lines; stamp list; mention W.W. [0062]

**We can supply your requirements for Television construction**

**ELECTRONIC ENGINEERING COMPONENTS**

**POWER CHASSIS.** P1/C. Steel chassis cadmium plated, fitted with valve-holders, sockets. £16/-.  
**TIME BASE CHASSIS.** Cadmium plated, fitted with six valve-holders, TB1/C, 18/6.  
**VISION CHASSIS.** Fitted valve-holders, screens, coil-formers V1/M, 23/6.  
**SOUND CHASSIS.** S1/M. Fitted valve-holders screens, etc., 20/-.  
 When ordering the above parts please state whether for Midland or London transmission.  
**FOCUS COIL.** Complete assembly. 33/6.  
**DEFLECTOR COILS.** Complete yoke. 38/6.  
**TUBE CARRIERS.** For 6in. tubes. 18/6.  
**GANTRY BRACKETS AND FRONT STRAPS.** Complete set, 10/-.  
**LINE OUTPUT TRANSFORMER.** 33/6.  
**COILS C.O.** London. Complete set of permeability tuned coils and chokes, sound and vision. CCM as above but for Midland, 19/3 per set.  
**COIL FORMERS,** with cores. Standard for London, 11/- doz., 11d. each. Midget for Midland, 8/- doz., 8d. ea.  
**TRANSFORMERS.** 5K6EH 5,000 v. A.C. with 204 v'appings, £3/10/-, 4K5EG 4,000 v. A.C. with 2-4-6 v'appings, £3/4/-, 9K3EH 1,750 v. with 2-4 v'appings, £2/6/-, PT/1 Power Transformer, 350-0-350 v. 280 ma., 6.3 v. 6 a., 4 v. 8 a., 0.2-6 v. 2 a., 4 v. 3 a., £4/10/-, plus carriage and packing.  
**HANDBOOKS.** "Electronic Engineering." London, 2/6. Wiring Diagram, 3/9. Midland complete with wiring diagram, 4/6. All plus 3d. postage.  
**ALL GOODS ARE POST FREE EXCEPT WHERE OTHERWISE STATED.**  
 Goods can be sent C.W.O. or C.O.D.

**VALLANCE'S**

VALLANCE & DAVISON LTD., W.W. Dept.  
**144, Briggate, Leeds, 1**  
 'Phone 29428-9

**AMC TELEVISION**

Manufactured to "Electronic Engineering" Teleserv Specification.

**MIDLAND T.V. Sound and Vision** Panels fitted with formers and dust cores now available.

**LINE OUTPUT TRANSFORMERS**

**NEW Improved SET OF GANTRIES COMPLETE**

**FOCUS COILS**

**LINE AND FRAME SCANNING COIL ASSEMBLIES**

All Steel **CADMIUM PLATED POWER AND TIME BASE CHASSIS** valve-holders, 3 point and single socket and all necessary cut-outs.

**SOUND PANEL CHASSIS ASSEMBLY,** fitted with screens, valve-holders, formers and dust cores.

**VISION PANEL CHASSIS ASSEMBLY,** fitted with screens, valve-holders, formers and dust cores.

**9" G.R. TUBE SUPPORT** for mounting on top of Gantry Assembly.

**9" CREAM MASKS.**

**5, SHAKESPEARE RD., FINCHLEY, N.3**  
 'Phone: FINchley 2188

**"You can rely on us"**

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES IMMEDIATE DISPATCH

**MIDGET SUPERHET COIL PACKS**  
 MW/LW Size 2½in. long, 1½in. deep, 1½in. high, Type "R" ..... 25/-  
 MW/SW Size 2½in. long, 1½in. deep, 1½in. high, Type "S" ..... 25/-  
 SW/MW/LW Size 3in. long, 1½in. deep, 1½in. high, Type "C" ..... 28/6  
 Comprising, iron-core magnet coils, wavechange switch, ceramic trimmers, neatly assembled for one hole fixing. The difficult part of a superhet overcome.  
**SPEAKER TRANSFORMERS**  
 Super midget for "Personals" to match DL92, 384, etc. .... 4/3  
 Pentode output type 85: 1 at bargain price for quality ..... 4/6  
 Midget mains output transformer ..... 3/9  
**LOUDSPEAKERS**  
 Celestion 2½in., 25/6; 3½in., 10/6; 5in. with dust cover 9/9; 6½in., 12/6; with transformer, 17/6; 8in., 18/6; with transformer, 19/6; 10in., 21/-; 12in., 39/6; special lightweight 6in. small magnet, 10/6.  
**COILS**  
 Weartie "P" Coils, 3/- each, full range stocked. Blue print with data supplied.  
 T.R.F. Matched pair, first quality, pair... 7/6  
 MW iron core with reaction ..... 3/8  
**FILAMENT TRANSFORMERS**  
 Primary 200/240 v. Secondary 6.3 v. 1.5a. Black crackle, small dimensions ..... 9/6  
 Secondary 4 v. 3 a. .... 12/6  
**RESISTORS**  
 ¼ watt, 3d.; 1 watt, 4d.; 1 watt, 8d. Large stock.  
**BARGAIN OFFER**  
 Choke 70 ma 150 ohms, super quality. Boxed ..... 5/-  
**VIEWMASTER TELEVISION**  
 7 point to point circuits and booklet. Post free ..... 5/6  
 Components stocked.

**HOT OF OTHER LINES.** Write, phone, or call for: Price and Data folder containing Bargain List, 2½d. Stamp.  
**RADIO SERVICING CO.**  
 444, Wandsworth Road, London, S.W.8  
 'Phone: MAgazley 4155.  
 77, 77A, Bus 28, Tram, Wandsworth Rd. S.R. Station. Open till 6.30 p.m.



GOVT. SURPLUS, UNUSED

# CONDENSERS

of all types . . .

We can offer, FOR IMMEDIATE DELIVERY from very generous stocks, a wide range of ultra-high quality fixed paper Condensers, from .001  $\mu$ F to 8  $\mu$ F. Also STOCKS of small, genuine MICA Condensers from .00001 (10 pf) to .01  $\mu$ F (10,000 pf). Prices are exceedingly moderate.

Enquiries are invited for manufacturers' requirements, wholesale and export only for bulk quantities, and for scheduled deliveries over a period, as required. Most condensers are now available for immediate delivery.

Please request our 4 page bulletin CONSEVEN 0114

## CLAUDE LYONS LTD.

180 Tottenham Court Rd., London, W.1 and 76, Oldhall St., Liverpool 3, Lancs.

### LABORATORY Test Equipment

HIGH GRADE laboratory test equipment reconditioned as new and GUARANTEED EQUAL in every way to the maker's specifications.

MARCONI INSTRUMENTS equipment. SIGNAL GENERATORS  
 Type TF.144G. 85 kc. to 25 Mc/s. £80 0  
 Type TF.144F. 85 kc. to 25 Mc/s. £65 0  
 Type TF.390G. 10 Mc/s. to 150 Mc/s. £45 0  
 In type TF.390 other frequency ranges to order.  
 Valve Voltmeter type TF.428A... £40 0  
 Output Meter type TF.340... £31 0

MISCELLANEOUS EQUIPMENT  
 Wavemeters by R.C.A. Type TE.149. Frequency range 200 kc. to 30 Mc/s. by harmonics. Directly calibrated dial from 2.5 to 5 Mc/s. Scale length 9 feet. Absolute accuracy 0.02 per cent. Crystal accuracy 0.005 per cent. Supplied with instruction book, spare valves, components, etc., in fitted transit case. NEW £9 0

PRECISION TEMPERATURE CONTROLLED OVENS  
 Suitable for Quartz Crystals. Will give a stability with suitable crystals of better than two parts in a million. The ovens are fitted with a precision thermostat and thermometer. Oven temperature adjustable between 40-60 per cent Weight 15 lbs. Dimensions 6 1/2 x 6 1/2 x 10 in. deep. £5 0

COSSOR Signal generator and ganging oscillator type 343, complete with instruction book and sealed in maker's packing case. NEW £19 0

ALSO in stock we have wavemeters up to 1,000 Mc/s., VARIACS, Constant voltage transformers, Precision attenuators. Send for lists. Telephone: B.A.Ling 0779


HATFIELD INSTRUMENTS 175, Uxbridge Road, Hanwell, London, W.7

### COMPONENTS—SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. 20watt high fidelity amplifier kits for constructing the McMurdo, 8-valve, AG/DC amplifier, low impedance input (suitable for moving coil mikes, etc.), by triple shielded trans to E.F.37. R.O. coupled to triode strapped stage (EF37), with switched bass and top cut provided, trans coupled to output stage using four GL53's in parallel push pull, large O.P.T. matches to 10 or 15 $\Omega$  rectifiers two UR5C's parallel, alternative high impedance input to second stage, for Xtal pick-ups, tuner units, etc., required inputs for full output, high imp. 0.5v r.m.s., low imp. 1millivolt, V.C. operates on both inputs, chassis isolated from mains, complete kit of first-class components (including Partridge trans), all valves, black crackle chassis (ready drilled), black crackle and chromium case (15 1/2 in x 6 1/2 in x 8 in), circuit diagram etc., everything required for the construction of a fine job, £15/13, carr. paid.


PERSONAL receivers 5-valve T.R.F. receivers using I.T.4's, contained in handsome Bakelite case, with lift up lid, size 7 in x 6 1/4 in x 5 in with lid closed, plastic carrying handle, frame aerial in lid, these receivers cover the medium wave-band and operate on 100, 200, 400, 800, 1600, 3200 kc. dry batteries, types B.101 and U2, output to a pair of lightweight high resistance 'phones, 2 gang conds with s.m.d., opening the lid switches on; supplied brand new in maker's carton, with valves, 'phones and batteries, an ideal set for children, invalids, and many other purposes, these receivers are not Govt. surplus, and are offered ready to play, £3/19/6 carr. paid; 360-0-360v 220ma, 4v 8a C.T., 4v 3a, 6.3v 3.5a. trans., input 210/250v 50c/s, new, 32/6 carr. paid; T.V. line transformers, shielded in all can with T.C. lead (used with FE46), 11/6; chassis (steel) 5 x 5 1/4 x 1 1/4 in. drilled 4 button base holes. 1/9; 5 x 9 1/2 x 1 1/4 in. drilled 7 button base holes. 2/3; all 17 x 19 1/2 x 2 1/2 in. drilled 7 int. oct. and square open-ends. 5/3; E.H.T. trans. 4kv 1ma. 2v 2a. Pri. 250v 50c/s; 29/6; rec. R. 1431 covers 65-86Mc/s. 10 valves (6.3v), tuning meter. 6in SM dial. circuit diagram, etc., brand new, in transit case, £4/4, carr. paid; personal receivers B.C.728c, 7 valve rec. using 1.4v valves, with 4 push buttons covering 2-8Mc/s, built in case, supplied brand new, complete with valves (IT4 IR5, etc.) 2 and 12v VIB, 2v acc., telescopic A.E., instruction book, etc., £8/19/6; mains trans., all PRI 200/250v 50c/s; Sec. 460v, 200ma, 210v 15ma, 6.3v 5A, 14/6; auto. trans., 200-250v-11v, 60W rating enclosed 18/-; medical line auto. 250/110v, 100W, 9/6; smoothing chokes 5H 120ma, 140 $\Omega$  3/3; 5H 200ma 100 $\Omega$  4/11; 6H 200ma, 100 $\Omega$  5/6; 5H 250ma, 90 $\Omega$  7/6; electrolytics, 8mf, 150v 1/3; 8/170v 1/3; 8/450v 2/3; 16/550v can 2/3; 3-+3 450v large can or d/ended 3/6; 8+32 450v can 4/-; 6+24 450v can 5/-; 32 450 large. can 2/9; 32/450v w/e 3/6; 16+8 350v can 3/-; 60+100 350v 3/-; 32/350v card 2/3; X100mf 3v 3d; 100mf 6v 6d; 25/25v 1/3; 100/25v 1/6; 25/50v 1/3; 16/350 card 1/3; 24/350 can 1/2; 8+24 3/6; P.M. loudspeakers 5in less trans. 9/11; with trans. 4500 $\Omega$  11/6; 6in less trans. 10/11; 10in with trans. 21/-; R.F. units type 24 8/6; with valves, used in good condition, post 1/6 extra please, output trans. 2000/20, 2500/20, 2750/20, 3000/20, 3/-; 4500/20 7000/20, 3/6; 3 ratio 7000/3500/1750/400, 4/-; heavy duty 7000/20 3/6; I.F. trans. 465 Kc/s small size, iron cored 7/6 pr.; 2 gang conds. .0005 ceramic ins., 1in standard spindle 4/6; ceramic switches 2p., 3w. 1B, 2/-; 5p., 5w. 1B 3/6; switches, standard size 2p., 4w. 1B (additional water with shorting plate) 2/6; 4p., 3w. 2B 2/6; 2p., 4w 3B 2/6; 1p., 10w. 2B 2/6; all have 3in spindles; resistors 100 assorted, 47 values ranging 180 $\Omega$  4w-100K 3w. standard sizes, best makes 10/6, post 6d; ceramic trimmers 3/500 $\Omega$  1/2 on a bar 1/3; 1/15pf single 4d; 3/30pf air spaced concentric 6d; 3/25pf U.I.C. type 3d; air spaced variables 1/4in spindles 25pf, 50pf, straight, 50pf diff. ceramic bases 1/-; 35pf butterfly 1/-; car radio vibrator pks with 1.5, 2.5, 3.5, 999.5, 1000.5

### CABINETS AND COMPONENTS

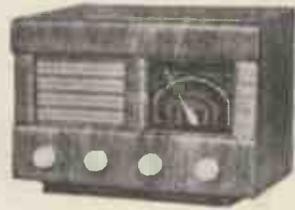


Receiver cabinets as illustrated. Beautiful walnut veneer. Size 12 1/2" x 8 1/2" x 7 1/2" deep. 35/-. We can construct any type or quantity of cabinets to specification. Send full details.

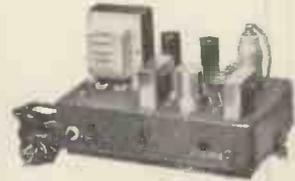All components to construct a T.R.F. or Superhet Receiver in above cabinet are available. Lists on request.



4 1/2 Watt A.C. Quality Amplifier with negative feedback. From £5.47d. 5 Watt Universal similar to above from £3.16.2d. 12 Watt Universal from £8.5.0d. Full details on request.

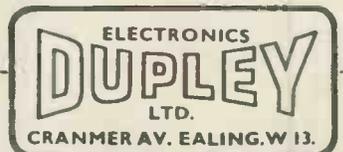LEWIS RADIO CO. (Dept. W.3.)  
 322, High Road, Wood Green, LONDON, N.22.  
 'Phone: BOWes Park 5997.



Transformer and Coil Manufacturers to the Trade  
 Telephone: E.A.Ling 5888

### AN APOLOGUE THE SOUND MAGNET

We apologise to all those who have placed orders with us for the Sound Magnet Tape Recorders, that we have been able to meet only a very small percentage of their requirements before Christmas.

Production is steadily increasing, and with other assembly lines coming into operation in the New-Year, a steady output will be maintained.

Our sincere thanks and appreciation to all those patiently awaiting a Sound Magnet.

### GENERAL LAMINATION PRODUCTS LIMITED

294 Broadway, Bexleyheath, Kent

'Phone Bexleyheath 3021

(Continued on page 77)

**MAINS TRANSFORMERS, FULLY INTERLEAVED, SCREENED AND IMPREGNATED. ALL PRIMARIES ARE 200/250 v.**

**Half Shrouded**

HS63. Output 250/0/250v. 60 m/a. 6.3v. at 3 amps. 5v. at 2 amps	15/6
HS40. Windings as above. 4v. at 4 amps. 4v. at 2 amps.	15/6
<b>Output</b>	
HS2. 250/0/250v. 80 m/a.	17/6
HS30. 300/0/300v. 80 m/a.	17/6
HS3. 350/0/350v. 80 m/a.	17/6
HS2X. 250/0/250v. 100 m/a.	19/6
HS30X. 300/0/300v. 100 m/a.	19/6
HS3X. 350/0/350v. 100 m/a.	19/6

**Fully Shrouded**

<b>Output</b>	
FS2. 250/0/250v. 80 m/a.	19/6
FS30. 300/0/300v. 80 m/a.	19/6
FS3. 350/0/350v. 80 m/a.	19/6
FS2X. 250/0/250v. 100 m/a.	21/6
FS30X. 300/0/300v. 100 m/a.	21/6
FS3X. 350/0/350v. 100 m/a.	21/6
All the above have 6.3-4-0v. at 4 amps. 5-4-0v. at 2 amps.	
FS43. Output, 425/0/425v. 200 m/a. 6.3v. 4 amps. C.T. 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded.	42/6
FS50. Output, 450/0/450v. 250 m/a. 6.3 v. 2 amps. C.T., 6.3v. 4 amps. C.T. 5v. 3 amps. Fully shrouded.	62/6
F30X. Output, 300/0/300v. 80 m/a. 6.3 v. 7 amps. 5v. 2 amps. Framed. Flying leads.	26/6
F35X. Output, 350/0/350v. 250 m/a. 6.3v. 7 amps., 4v. 8 amps., 4v. 3 amps., 0-2-6.3v. 2-amps. Fully shrouded.	59/6

**FILAMENT TRANSFORMERS**

F4. Output, 4v. 2 amps.	7/6
F6. Output, 6.3v. 2 amps.	7/6
F12. Output, 12.6v. tapped 6.3v. at 3 amps	15/6
F24. Output 24v. tapped 12v. at 3 amps.	21/6
F12 and F24 framed with Flying Leads	
FU6. Output, 0-2-4-5-6.3v. at 2 amps.	9/-
F29. Output, 0-2-4-5-6.3 v. at 4 amps.	15/-
FU6 and F29 clamped with Flying Leads	
F5. Output, 6-3v. at 10 amps., 5v. at 10 amps., 12.6v. at 5 amps., 10v. at 5 amps.	31/6
F6/4. Output, four at 6.3v. tapped at 5v. at 5 amps. per winding, giving by suitable series and parallel connections 24v. at 5 amp.; 20v. at 5 amp.; 18v. at 5 amp.; 15v. at 5 amp.; 12.6v. at 10 amp.; 10v. at 10 amp.; 6.3v. at 20 amp.; 5v. at 20 amp.	47/6
F5 and F6/4 framed with Flying Leads	

**OUTPUT TRANSFORMERS**

MOPI. Ratios 26,46, 56, 66, 90, 120-1, 50 m/a. max current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel and clamped, each.	5/-
OPI. Midret Power Pentode, ratios 30, 60, 90-1, 40 m/a., Secondary 2/3 ohms. each	3/2
OP2. Midret Pentode, ratios 45-1, Secondary 2/3 ohms, 40 m/a. per doz.	33/-
OPI0. 10/15 watts output. 20 ratios on Full and Half primary	16/3
OP30. 30 watts output, 20 ratios on Full and Half primary	23/9
Williamson's O.P. Transformer to Author's specification	£3/12/6
<b>The following framed with Flying Leads :</b>	
EHTU. Tapped EHT. 1,500v.-2,000v.-2,500v.-3,000v. up to 5 m/a., 2-0-2v. at 1.5 amps., 4v. at 1.5 amps.	42/6
EHT.1. 1,000v. 5 m/a. 2-0-2v. 2 amps., 4v. 1.1 amps.	32/6
EHT.2. 2,000v. 5 m/a. 2-0-2v. 2 amps., 4v. 1.1 amps.	35/-
EHT.25. 2,500v. 5 m/a. 2-0-2v. 2 amps., 4v. 1.1 amps.	36/6
C.W.O. (add 1/- in £ for carriage), all orders over £2 carriage paid.	

**H. ASHWORTH**  
(Dept. W.W.)  
876 GT. HORTON RD., BRADFORD, YORKS

**COMPONENTS—SURPLUS AND SECONDHAND**

(Continued from page 76)  
50K 3/-; twin carbon 1m/1m 2/6; all telescopic aerials, 15in closed 7ft 6in extended 3/6; receivers type 76, 150/505 Kc/s 5 valves ARTH2, VR53, VR92, I.P. output 560 Kc/s, brand new, in transit case, 22/6, carr. paid.  
RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. [0015

**WANTED, EXCHANGE, ETC.**  
WANTED, new Williamson amplifier; details and price.—Box 1121. [4753

FINE wires in large quantities only, must be new and perfect material  
L. E. SIMMONDS, Ltd., 8a, Byron Rd., Harrow, Tel. Harrow 2524 and 0135. [3661

CASH offered for service sheets; any quantity if all different.—Box 1021. [4662

WANTED, ORM 91 tube, sensible price; also soft or burnt-out ditto.—Box 1022. [4663

WANTED, "W.W." July, 1948, good cond.—Cook, 10, Charlesburg Ave., Gosport. [4754

WANTED, Magnetophone tons. B with spares (amplifier not required).—Box 1069. [4725

VOIGT corner reflector horn, light twin; reasonable; Southern area.—Box 1029. [4698

SMALL 12 or 24v perm-mag motors.—Bartrum, 230, Pettits Lane, North Romford. [4728

WANTED, "Wireless World," May, 1940, and August, 1940.—Steffensen, Ehlersvej 8, Hellerup, Denmark. [4715

WANTED, Lexington Sapphire Styli tip, rad. 0.0025in.—Smallwood, 34, Clarence Rd., Birmingham, 15. [4768

WANTED, hire, loan, purchase service manual or sheets, H.M.V. 1200.—McMenemy, 31, Golspie St., Glasgow, S.W.1. [4712

WANTED, buy or loan, copy "W.W." Sept., 1942.—Lihou, "Homesla," Baissieres Rd., St. Peter Port, Guernsey, G.I. [4695

WANTED, service manual for V.F. telegraph S+DX (Mark 1 or 2).—Pankhurst, Northamptonshire Newspapers, Kettering. [4645

WANTED, surplus relays and push-button units, any condition, large or small quantities; highest prices paid.—Box 8485. [3532

GARRARD 2-speed gram. motor (78x33%). No. 201B, also Hallicrafter HT-9 transmitter.—Wade, 46, Cottage Rd., Leeds, 6. [4717

WE pay top prices for used test equipment, all types.—University Radio, Ltd., 22, Lisle St., London, W.C.2. Tel. Ger. 4447 and Ger. 8582. [9992

WANTED, all kinds of laboratory test equipment, standard signal generators, bridges, oscilloscopes, "Q" meters, etc.; send price and details to—  
HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779. [0037

WE buy for cash, new, used, radio, electrical equipment, all types: specially wanted, radios, radiograms, test equipment, motors, chargers, recording gear, etc.—If you want to sell at the maximum price call, write or phone to University Radio Ltd., 22, Lisle St., Leicester Sq., W.C.2. Ger. 4447. [9992

**REPAIRS AND SERVICE**

MAINS transformers rewound, new transformers to any specification.  
MOTOR rewinds and complete overhauls; first-class workmanship, fully guaranteed.  
F.M. ELECTRIC Co., Ltd., Pottery Bldgs., Warser Gate, Nottingham, Est. 1917. Tel. 3855.

REWINDS and conversions to mains and output trans., pick-ups, fields, etc. from 4/6  
N. L. Rewinds, Brecknock Rd., N.7. [4593

RADIOS and televisions repaired, trade discount; assistance to home builders.—E. W. Shackle, High St., Harlington, Hayes, Middx. [4711

TRANSFORMER and choke rewinds, duplicate and to specification; prompt service.—F. Hadfield, Musard Place, Staveley, Chesterfield. [4617

LOUDSPEAKER repairs, British, American, any make, moderate prices.—Sinclair Speakers 12, Pembroke St., London, N.1. Terminus 4355. [3508

MAINS transformers rewound or constructed to any specification; prompt delivery.—Bede Transformer Co., Ltd., Bedesway, Bede Trading Estate, Jarrow. [3198

MAINS transformers rewound or constructed to any specification, prompt deliveries.—Avon Transformer Co., 20, Heath Terrace, Leamington Spa, Warwick. [4498

REPAIRS to moving coil speakers, cones, coils fitted, field rewound or altered; speaker transformers, clock coils rewound; guaranteed satisfaction, prompt service.  
L.S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting, London, S.W.17. Balham 2359.

ALL types of ammeters, voltmeters, Avos, etc., repaired; quick, efficient service, estimates free.—Dorwin Instrument Co., 91, Princesale Rd., London, W.11. Tel. Park 4469. [0059


REWIND service which duplicates or modifies as required; transformers, loudspeakers, etc.; prompt returns.—Raidel Services, 49, Lr. Addiscombe Rd., Croydon, Cro. 6537.

ELECTRICAL measuring instruments of every make repaired and standardised.—The Electrical Instrument Repair Service, 329 Kilburn Lane, London, W.3. Tel. Lad. 4168. [3715

**VIEWS ON**

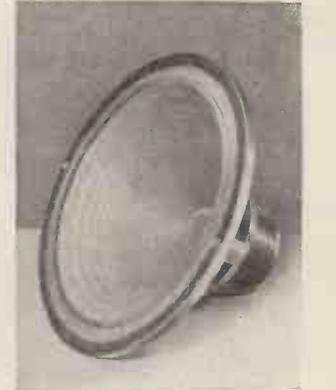**BARKER SPEAKERS**

We do not usually quote comments from our correspondents, but a letter which arrived from U.S.A. last week is so interesting that it deserves note. It says: I have done quite a bit of listening on FM, and must say results are astonishingly fine. Live FM broadcasts supply the most thrilling demonstration of what your speaker is capable of. As you may know, FM transmitters broadcast to 15 Kcs., with wider dynamic range and virtually no noise of any sort. It is a practically perfect input which gives a good idea of the capabilities of reproducing equipment.



It is a pity that here we possess so limited a choice within so limited an area of VHF broadcasts. Those who are fortunate enough to live in the service area of our one experimental station will certainly find a 150 or 148a a most rewarding investment, and possessors of a good quality receiver for television, able to divert their sound output from the second detector to a good amplifier, will also find satisfying hours.

As a home correspondent has said: I can't help repeating that the performance of the Barker is positively uncanny; this is the first time I have felt limited by the input rather than the speaker.

Let us hope that matters will be improved during 1950.

Now a word on deliveries. We have had to keep some friends waiting for their speakers, and it looks as if this will continue for a while. The 148a is unlikely to exceed 10 days, but the 150 may run to two or three weeks. So the wise will act promptly.

**BCM/AADU, LONDON, W.C.1.**

# WE DON'T

supply anything **EX-GOVERNMENT**.  
ALL BRAND NEW GOODS—fully guaranteed.  
All items advertised in recent issues still available.

This month's special offer:—  
**CELESTION 3½in. SPEAKERS**, P.M., brand new, boxed and guaranteed; few only, 14/9.

Unrepeatable bargain: **AVO UNIMINOR**, listed at 5 gns.; while stocks last these instruments are being offered at the old price of 4 gns. New boxed and guaranteed.

**LEATHER CASES** for the Avo 7 and similar instruments £2 2 0

**PIFCO RADIOMETERS**: 0-6 v., 0-240 v., A.C. or D.C., 0-30 mA. £1 5 0

**GARRARD A.C./D.C. GRAM UNIT TYPE U.5 MOTOR AND PICK-UP**, with auto stop and 12in. plate. Few only offered at £12 9 2

**TAYLOR TEST INSTRUMENTS** now available on our Hire Purchase scheme. Please send S.A.E. for catalogue and terms.

**STROBOSCOPES**, 78 r.p.m., 50 cycles, 6d. each, 8½d. post free.

All orders can be sent C.O.D. if under 15 lb. in weight.

Special attention to overseas orders, which are free of purchase tax.

**MODERN ELECTRICS LTD.**  
164, Charing Cross Road, London, W.C.2  
Phone: TEMple Bar 7587

## REPAIRS AND SERVICE

**R**epairs.—E.H.T., mains and O.P. transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification; all work fully guaranteed.  
**WILLEDSEN TRANSFORMER CO., Ltd.**, 781, Harrow Rd., N.W.10. Tel. No. Ladbroke 2846.

**"SERVICE with a smile."**—Repairers of all types of British and American receivers; coil rewinds; American valves, spare line cord.—**F.R.I., Ltd.**, 22, Howland St. W.1. Museum 5675. [1575]

**R**ADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs; armatures; F.H.P. motors, vac. units, portable tools, etc.; good deliveries.—139, Goldhurst Terrace, N.W.6. Mai. 6133. [9925]

**"STURDY"** rewinds, mains transformers, chokes, and fields, first-class work, prompt deliveries and satisfaction guaranteed.—**Sturdy Electric Co., Ltd.**, Dipton, Newcastle-on-Tyne. [2430]

**F**IRST grade quality transformers, Williamson output (both types), £4/4; Williamson power, £2/7/6; Williamson chokes (the pair), £2/2/6.—**A. Orman**, 3, Leslie Pl., Edinburgh Scotland. [4605]

**24-HOUR** service, 6 months' guarantee, any transformer rewind, mains outputs and i.f.s., etc.; all types of new transf., etc., supplied to specification; business heading of service card for trade only.—**Majestic Winding Co.**, 180, Windham Rd., Bournemouth.

**L**T.P. rewind service, all rewinds are layer wound, vacuum impregnated, pressure tested at 2,000volts and guaranteed for three months, 48-hour service.—**Enquiries London Transformer Products, Ltd.**, L.T.P. Works, Cobhold Estate, N.W.10. Tel. Willesden 6488.

**M**ETROPOLITAN RADIO SERVICE for re-winding, mains and e.h.t. transformers, chokes and field coils; delivery 3-5 days; new transformers designed and manufactured singly or in quantities.—**Metropolitan Radio Service Company**, 1021, Finchley Rd., London, N.W.11. Tel. Speedwell 300.

**R**EWINDS.—Send your "burn outs" to be rewound; no technical data wanted; post transformer etc., labelled with your name, address, and marked "for rewind"; our windings are double wound, interleaved and impregnated.—**Southern Trade Services, Ltd.**, 297-299, High St., Croydon. Tel. 4870. [3110]

**N**ATIONAL RADIO SERVICE & TELEVISION Co., radio and television development engineers; high quality receivers and amplifiers built to specification and modernised; repairs to all makes of receivers, transformers, coils, armatures rewound, loudspeaker cones renewed, television aerial installations, conversion, etc.—82, High St., St. John's Wood, N.W.8. Primrose 6725. [2671]

## WORK WANTED

**D**RAWING and tracing work undertaken promptly to customers' requirements. Box 1015. [4693]

**C**ONSULTANT and development work undertaken by qualified University graduates with industrial experience.—Box 1117. [4736]

**W**E make wireless and radiogram cabinets for home and export, immediate delivery.—**Radiac, Ltd.**, 88/90, Caledonian Rd., London, N.1. Tel. Terminus 7447. [8025]

**S**PECIAL receivers, test gear, electronic apparatus, experimental and design work.—If you have a problem which needs expert handling, write to **Mr. J. J. Mort, B.Sc., A.M.I.E.E.**, BCM/HIFIDEL, London, W.C.1.

**D**RAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications, sub-contracting work of this nature undertaken.

**DRAWING & TRACING, Ltd.**, 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 7406. [4183]

**F**IRST-CLASS transformers and chokes manufactured, stock lines available; also special manufacturers' components made to specifications; armatures and fields wound and motors assembled.—**Avis & Baggs, Ltd.**, 140-141, Friar St., Reading, Berks. [2715]

## MISCELLANEOUS

**E**LECTRONIC voltage stabilizers; process timers; 100 microampere power relays, etc.; enquiries invited.

**BRITISH ELECTRONIC INDUSTRIES**, 303-305, Burdett Road, London, E.14. [0031]

**J.I.E.E.**, all parts, 1946-47; Ghirardi's "Radio Physics Course," perfect; offers.—**BM/Plymouthian, W.C.1.** [4757]

**W**ALNUT radiogram and television cabinets, manf. samples, few only; stamp details.—**Walters, SCI, Hale End Rd., E.4.** [4442]

**W**ALNUT radiogram cabinets, £18; new 12in speakers, 45/-; stamp details.—**Cabinetware, Summit Works, Heyes St., Blackburn.** [4807]

**N**EOON indicator lamps and holders, low voltage, 3 for 4/9; 15/6 doz; selenium barrier light cells from 6/6.—**Lucas, 22, Hengrove Rd., Bristol, 4.** [4532]

**"A**MERICAN Electronics," October 1946—Sept., 1949, inc.us.ve, good condition.—Offers to **Webb, 10, St. Barnabas St., London, S.W.1.** [4596]

**L**ATEST Masseurle printing press, bought late 1943, very little used, with several platens, some type, foil and cabinets; bargain.—**Harwood Press (Advertising), Ltd.**, 47, West St., Harrow, Middx. Byron 3545. [4586]

# MORSE CODE TRAINING

YOU CAN do what these students have done:

Ref. 5529 says:—"I feel sure you will be interested to learn that yesterday I took the G.P.O. test in Morse for an Amateur Transmitting Licence, and passed very comfortably. I sent a faultless 18 w.p.m. without effort and received at 14 w.p.m. with no errors; my numerals were also well on the right side, sending 12 and receiving 14 in the allotted one and a half minutes. I am now full of confidence as a result of this success and delighted with the progress I have made."

Ref. 6160.—Many thanks for your letter regarding my son. I will pass your letter on to him, and ask him to reply to you. He told me quite definitely that he had derived great help from your course. You will be pleased to know that he was successful in passing his First Class P.M.G. He had to leave home at short notice to take up a position under Marconi Co., and is now at sea."

Ref. 2245.—"I am glad to announce that I recently passed the P.M.G. Special Exam, and as you will see on my report, my speeds are now far ahead of the speeds needed in the examination. I therefore walked through the telegraphy part."

The Original letters can be inspected at London Office.

## MORSE CODE COURSES For Beginners and Operators

Just send for the Candler "BOOK OF FACTS" It places you under no obligation

**THE CANDLER SYSTEM CO.**  
(55 W.), 121 KINGSWAY, LONDON W.C.2  
Candler System Co., Denver, Colorado, U.S.A.

**B. & H. RADIO**  
EAST STREET, DARLINGTON

**BASS & TREBLE SEPARATOR**  
kit of parts £1 9 6

**SCRATCH FILTER**  
Gives a marked reduction of scratch level without serious effect on treble response. 15 0

**VARIABLE SELECTIVITY I.F. TRANS.**  
465 kc. Gives 3 degrees of selectivity..... per pair £1 0 0

**TONE CONTROL UNIT**  
To connect to any equipment and gives independent control of bass and treble. £4 10 0

**POST RADIO SUPPLIES**  
OFFER EX STOCK

**COPPER INSTRUMENT WIRE.**  
ENAMELLED, TINNED, LITZ.  
COTTON AND SILK COVERED.  
Most gauges available.

**B.A. SCREWS, NUTS, WASHERS,**  
soldering tags, eyelets and rivets.

**EBONITE AND BAKELITE PANELS,**  
TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.  
Latest Radio Publications.

Send stamped addressed envelope for comprehensive lists. Trade supplied.

**POST RADIO SUPPLIES**  
33, Bourne Gardens, London, E.4.  
Phone: CLIssold 4688

**MUMETAL and RADIOMETAL TRANSFORMERS and CHOKES**

As Specialists with many years of experience we can design and supply practically any type of transformer or choke with a nickeliron core for use on a band within the frequency range.

1 c/s to 150 kc/s

Available for rapid delivery—Microphone Transformers, Input Transformers, Line Transformers, Pickup Transformers, Output Transformers, Rectifier Transformers, Vibrator Transformers, High Fidelity Transformers, Recorder Transformers, Midget Transformers, High Q Chokes, High Inductance Chokes, etc., with or without Mumetal Shields.

**MAINS COMPONENTS ARE ALSO STOCKED.**

**SOWTER TRANSFORMERS**  
E. A. SOWTER, 1-B HEAD STREET, COLCHESTER.  
Phone: COLCHESTER 5450.

6½in. Sangamo Weston Movement, new condition, boxed ...	£3 0 0
3½in. Weston Thermal, 120 v....	15 0
3½in. Weston Thermal, 12 v. ...	15 0
G.E.C.P.M. Horn Driver Units, with Trans. ....	£1 10 0
Res. and Condenser Boards (large) .....	2 6
H.T. Rectifiers .....	2 6
4 M.F.D. Condensers, 350 v. ...	1 0
1 M.F.D. Mansbridge, 250 v. working .....	per doz. 2 0
Relays, many types, .....	from 1 6
Res. and small condensers, send for type required, lowest prices.	

Many other Manufacturers' surplus lines, send requirements.

**Radiomart Sound Service**  
71, Cricklade Street, Cirencester, Glos.

**JUST OUT!!**

**THE NEW**

**8th EDITION**

(23rd printing)

OF

**P. H. BRANS'**

**RADIO VALVE**

**VADE  
MECUM  
1950**

**THE VALVE BOOK,  
WHICH CUSTOMERS IN  
73 COUNTRIES ARE  
AWAITING.**

The most complete and outstanding encyclopædia of the World's electronic tubes.

Characteristics of well over 15,000 valves, as supplied by 247 Valve-Manufacturers from all over the world. Among the newest additions: radiation counter tubes, nonodes, transducers, accelerometers phasitrons, projection tubes and all crystal-diodes and -triodes.

**Published by P.H.Brans, Ltd.  
28, Prince Leopold Street,  
ANTWERP (Belgium)**

530 pp.  
12" x 8" From all Booksellers:

**Price: 20/-** (plus 1/- postage)

Single copy service:

UNIVERSAL SERVICES

16, Lyndhurst Avenue, London, N.12

**MISCELLANEOUS**

"W.W." Vols. 19-25, 29-40 (Inclusive), bound and indexed: £1 each.—Stevenson, Pendley Manor, Tring, Herts. [4707]

RADIO and television cabinets made to individual requirements.—Sketch and details to Burman's, 64, Reighton Rd., London, E.5. [4755]

6 B.A. X 1/4 in. ch. hd. brass screws, 10/- per 1,000; 8 B.A. hex. nuts 7/6 per 1,000; 4 B.A. X 1/4 in C.S. hd., 8/- per 1,000; 10 B.A. X 3/32 in. ch. hd., nickelled, 5/- per 1,000; 8 B.A. X 1/4 in ditto. 6/- per 1,000.  
E. NORMINGTON, 7, Collin Rd., Paignton [4679]

ENGRAVING, amateurs and trade could take full advantage of the opportunity of etching problems in the future by getting in touch with A. G. Engraving 19a, Windmill Rd., London, S.W.18. Brass, bronze, erinoid, perspex, dials; one knob or repetition equally entertained. [0054]

FLUORESCENT lighting, 80watt control ballast unit, fully wired and tested on 210-240v A.C., fitted with two tube holders, ready for immediate use, but without 5ft. tube, 45/3 only; buy tube locally.—Malden Transformer Supplies, 200-202, Cambridge Rd., Norbiton, Surrey. [0038]

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges; BA screws, nuts, washers, soldering tags, eyelets; ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod; headphones, flexes, etc.; latest radio publications, full range available; list & s.a. trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4. [1454]

"HOW green was my Telly," and how very small! Now it's a View-Master, beats them all. Constructor's envelopes (5/-, post 3d) & London parts in stock, Birmingham model when released, early Jan. Easiest yet to build, 9in or 12in tube without alteration. Complete 12in model costs less than any 12in commercial receiver.—Westmead Radio, 117, Westmead Rd., Sutton, Surrey. [1614a]

3/6.—For this modest sum we supply you with full constructional details for building our latest 10watt quality amplifier with variable negative feed-back; these constructional sheets are simplified so that the most inexperienced person may build and obtain first-class results. Complete Home Constructor's Handbook with circuit of this and many other sets, 1/- extra.—Supacoils, Mail Order Office, 98, Greenway Ave., London, E.17. [0055]

5-core cable, rubber insulated 9/012 colour ccced rubber covered, 35/- 100 yards; 7-core ditto, but cellulose covered, 45/- 10 yards, stamp samples; Belling Lee type 5-pin plugs and sockets, 30/- per 100; 7-pin ditto, 100/- per 100; high grade panel lights, frosted domed red glass crystal, plated bezel, M.B.C., 80/- per 100, £14 for 400; Ceramic EF. 50 holders, 25/- per 100; VCR. 97 holders, 18/- per dozen; throat mikes, 15/- per dozen.—J. McMillan, 5, Oakfield Rd., Bristol, 8. [4372]

BRITISH SOUND RECORDING ASSOCIATION.—Membership is open to all professional and amateur recording engineers and high-quality reproduction enthusiasts. The official Journal, "Sound Recording," Vol. 3, Nos. 1-2-5 available at 2/8 post free. B.S.R.A. Diary for 1950 at 4/6 with eight pages of data on recording and reproduction, plus, forms, and application forms from Membership Secretary, Harrie J. King, 48, Mount View Rd., N. Chingford, London, E.4. [2119]

SITUATIONS VACANT  
Vacancies advertised are restricted to persons or employments excepted from the provisions of the Control of Engagements Order, 1947.

HIS MAJESTY'S COLONIAL SERVICE  
VACANCIES exist for Engineers, Posts and Telegraphs Department, Gold Coast. Salary £660 to £1,300 per annum, plus cost-of-living allowance of 15% of basic salary, point of entry according to age, war service, qualifications and experience.

CANDIDATES must be competent engineers and be Associate Members of the Institute of Electrical Engineers or hold an equivalent qualification exempting them from Part A and B of the examinations. They should have had a thorough training in telegraph and telephone engineering with experience in the engineering department of a Post and Telegraphs Administration. They should also have undergone an apprenticeship with subsequent practical experience of power generation and distribution. The post is permanent and pensionable. The officer appointed will be provided with free first-class passages for himself and wife on first appointment and on leave, partly furnished quarters are provided at low rentals; free medical attention; leave is granted at the rate of seven days for each month of residential service after each tour of 18 months; income tax is at Colonial rates.

CANDIDATES should write at once for further particulars and form of application to the Director of Recruitment (Colonial Service), Colonial Office, Sanctuary Buildings, Great Smith St., S.W.1, quoting reference No. 27323/3 [4701]

TESTERS, inspectors and faultfinders required; 5-day week, good prospects.  
ACE RADIO, Ltd., Tower Works, Tower Rd., N.W.10, Willesden 3904/5. [4774]

RADIO-television service engineer required, experienced, good salary for efficient man, permanency.—Killbourn, Abingdon, Berks. [4747]

**THIS  
RACK  
SAVES  
YOU  
MONEY**



- ★ Initial cost keenly competitive.
- ★ A standard article, available from stock, immediate delivery.
- ★ No design or tool charges.
- ★ Desk unit, gram. unit, mobile base, telescopic chassis runners, panels and chassis available as stock accessories.
- ★ Unique design cuts instrument assembly and maintenance time to a minimum.
- ★ Only extra rack bodies required for multiple units.

Write for catalogue giving complete range of standard instrument cases, racks, handles, etc. and details of our metal cabinet design and production service.

**IMHOF'S**

112-116 NEW OXFORD ST., LONDON, W.C.1  
TELEPHONE MUS. 7878 (20 lines)

## THE BRITISH NATIONAL RADIO SCHOOL

ESTD. 1940

### OUR CLAIM


NOT the BIGGEST, NOT the  
CHEAPEST, but simply the  
WORLD'S  
**MOST RESPECTED**  
Correspondence School

Write today for our free  
booklet "RADIO Offers You  
a Career" and our Pamphlet  
"TRUTH in ADVERTISING".

BRIT. I. R. E., City and Guilds,  
P.M.G. (THEORY ONLY) Exam-  
ination courses also the finest  
RADAR Course ever written!
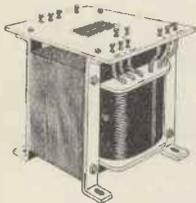
### STUDIES DIRECTOR

BRITISH NATIONAL RADIO SCHOOL  
66, ADDISCOMBE ROAD, CROYDON  
Phone: Addiscombe 3341



### HIGH- CLASS DESIGN.

### VACUUM- IMPREGNATED

TRANSFORMERS BY  
**MILLETT & HOLDEN LTD.,**  
BIRCHAM WORKS, BIRCHAM ROAD,  
SOUTHEND-on-SEA, Essex.  
Southend 68409

## LUDLOW & COLE

for  
TRANSFORMERS

CHOKES—FILTERS  
TAG PANELS

HIGH FIDELITY  
SOUND EQUIPMENT

Trade Enquiries Invited

PICKETTS AVENUE,  
LEIGH-ON-SEA, ESSEX.  
Telephone: SOUTHEND 76589

### SITUATIONS VACANT

**F**OR South Sussex coast town. domestic radio, television mechanic; must have first-class experience and references; accommodation not offered.—Box 485. [4475]

**E**XPERIENCED salesman for amateur and surplus gear required for high-class West End showroom.—M.O.S. 33, Tottenham Court Rd., London, W.1. [4689]

**Q**UALIFIED television service engineers required; only those with experience of commercial sets need apply.—J. & F. Stone, Ltd., 351 Mare St., Hackney, E.8. [4610]

**S**ERVICE engineer required for hearing aid manufacturing company. Must be of good appearance and have knowledge of H.F. amplifiers.—Apply Box 1013. [4641]

**T**ELEVISION/RADIO engineer required for indoor and outdoor work by old-established West End firm; good references essential; must be able to drive van.—Apply Box 1014. [4642]

**A**MALGAMATED WIRELESS (AUSTRALASIA), Ltd., invite applications for positions in its research laboratories and works, Sydney, Australia, in the following categories:—

(1) SENIOR engineers and physicists with about seven years' personal experience in research development or design work in telecommunications followed by experience in the supervision of a small group engaged in such work; men with University degree in electrical engineering or science or Corporate Membership of I.E.E. preferred.

(2) ENGINEERS or physicists with about three years' personal experience in research development or design work in telecommunications; men with University degree in electrical engineering or science or Corporate Membership of I.E.E. preferred.

(3) RADIO engineers, City and Guilds standard or equivalent with about five years' experience in the development and preparation of prototype models for the production of electronic equipment. APPLICATIONS giving particulars of training should be addressed to Box 1176. [4779]

**T**ROUBLE Shooter—Service Engineer for radio and television work in central service department located in Bedford; top rates of day and output bonus.—Apply with full details, Box 1066. [4719]

**T**ESTERS required by amplifier manufacturers in the London area. Applicants with actual experience in this field should state details of a.c. qualifications and salary required; 5-day week.—Box 95. [4439]

**R**ADIO and television service engineer, must be conversant with television; write stating experience and salary required; permanent job for right man.—Hammants, Bell St., Henley-on-Thames. Tel. 220. [4697]

**C**APACITOR manufacturers require experienced process engineer to assist in production and development of electrolytic capacitors.—Apply to Chief Chemist, A. H. Hunt, Bendon Valley, S.W.18. [4690]

**T**ELEVISION engineers required by East London firm with all leading agencies; salary £9/10 p.w., perm. position; only first-class men need apply.—Leytonia Radio, 828, High Rd., Leyton, E.10. Tel. Ley. 1396. [4655]

**D**YNATRON RADIO require service manager; good technical experience and education with ability to answer correspondence essential.—Apply Personnel Manager, Dynatron Radio, Ltd., Ray Lea Rd., Maidenhead, Berks. [4672]

**I**NSPECTOR wanted, qualified in both mechanical and electrical branches, able to take charge of inspection in factory S.W. London manufacturing radio and electronic apparatus.—Apply Managing Director, Box 1020. [4660]

**L**OUDSPEAKERS, experienced senior executive with knowledge of loudspeaker production, including cones, required for managerial position, apply in strict confidence with full details of qualifications and experience to Box 1175. [4777]

**L**ARGE industrial organisation having opened 10 laboratories in mid-Surrey on work involving electronic and electro-mechanical development and design in a new and interesting technical field, have immediate vacancies for:—**D**RUGHTSMEN with apprenticeship or a minimum of 4 years' shop experience.

**D**EVELOPMENT engineer with degree or equivalent standard. GOOD salaries and first-class working conditions, with staff canteen facilities. The positions are progressive and permanent. Applicants must be of British nationality and should submit full details of education, experience and salary required to Box 1027. [4688]

**D**YNATRON RADIO require highly experienced radio and television service engineer; first-class applicant with pleasing personality and a good driver only need apply.—Personnel Manager, Dynatron Radio, Ltd., Ray Lea Rd., Maidenhead, Berks. [4673]

**E**LECTRICAL engineers required for progressive positions as design and development engineers; qualifications: Degree or equivalent in electrical engineering or physics with actual design experience in one of the following or allied fields:—

(a) HOUSEHOLD appliances. (b) Small electric motors. (c) Power supply unit for airborne radio equipment. (d) Recording equipment (disc, film or tape). (e) Radio components and transformers. (f) UHF oscillator and aerial design. (g) Radar and television equipment.

APPLICANTS should write giving full details to Personnel Dept., E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. [4661]

# ATOM BOMBS AND ELECTIONS


may have you worried, but you can forget them if you possess a copy of the new, revised "HOME CONSTRUCTOR'S HANDBOOK" (now in its sixth edition!). This justly famous book is crammed full of many good things for ALL radio beginners, servicemen, dealers, experimenters, etc.

- Eight tested and guaranteed circuits, with full descriptions and parts lists.
- Feeder Units, Tuning Units and Superhets.
- Quality Amplifiers.
- Servicing and Constructional Hints and Tips.
- Resistance Colour Code, Charts, etc.
- Simple Formulae, etc.
- And many other interesting items.

We are proud to make the special offer once again of this useful book to "W.W." readers for 1/- ONLY. Send NOW for your copy of the new issue and catalogue. Letters of praise continue to reach us daily regarding the improved model 40 coil pack with CERAMIC switching for improved performance. These letters confirm our opinion that this unit has no equal anywhere even at double the price. P.S.H. of H.M.S. "Harrier" states: "I must add that your coil pack and IF's do everything you claim them to do."

The price is still unchanged at 42/- inclusive, or 47/- aligned and sealed for 465 kcs. I.F.

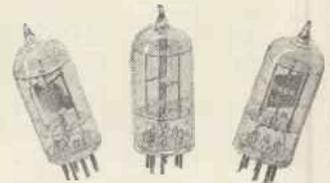**RODING LABORATORIES,**  
70 LORD AVENUE, ILFORD, ESSEX



TYPE G (BYG BASE)

ENQUIRIES FOR ALL TYPES INVITED

**BROOKES CRYSTALS LTD.**

10 STOCKWELL STREET,  
GREENWICH, LONDON, S.E.10.

PHONE GRE. 1828. CABLE. XTALS LONDON.

## SURPLUS 450v. MIDGET CANS

8 mfd. .... 2/3 16 mfd. .... 3/-  
8 - 16 mfd. .... 4/- 8-8 mfd. .... 3/6  
32 mfd. .... 4/3d, 16 - 16 mfd. .... 4/3

All recent manufacture — cash with order  
Subject to being unsold.

### ALSO 500v. Wire Ends.

Cardboard Tube 8 mfd. 2/8 (B.R. 850)  
Cardboard Tube 16 mfd. 3/9 (B.R. 1650)

Send postcard for complete list detailing  
many radio component bargains.

**FEDERAL RADIO CO.**  
734, HIGH ROAD, LONDON, N.17.

# When Quality Counts . . .



. . . the **HOMELAB** Signal Generator is a wise choice. But there is a snag—we cannot give immediate delivery. The fact is that the large demand for this instrument has, until recently, exceeded our manufacturing capacity. Some of our customers have had to wait longer than was anticipated, but we have now obtained additional premises for the production of the **HOMELAB** and are able to make lots more of them. During the next few weeks we will be able to get right up to date with orders. We offer our apologies to those who have patiently awaited delivery—but we gather from the letters we receive that the **HOMELAB** is well worth waiting for. May we remind you that the **HOMELAB** Signal Generator has the following features:

- 100KCS. to 130 MCS.
- 30 per cent. MODULATION AT 400~ or
- UNMODULATED CARRIER
- PROVISION FOR EXTERNAL MODULATION
- OUTPUT IMPEDANCE 10Ω
- LOW EXTERNAL FIELD
- BUFFER STAGE
- VARIABLE 400~ OUTPUT
- ACCURACY OF CALIBRATION ±1 per cent.
- A.C. MAINS OPERATION ONLY.

**PRICE £6:11:0** plus 5/- for packing, etc.

Please send S.A.E. for full technical details and enclose P.O. for 2/6 if circuit diagram required. The **HOMELAB** Signal Generator can be seen at our new showrooms—the address is **HOMELAB INSTRUMENTS**, 374, High Road, London, E.11—but orders can only be accepted by post and these, together with all enquiries should be addressed to:—

**HELY-MANN**  
**ELECTRONICS LABORATORIES**  
116, GROVE RD., LONDON, E.17.

### SITUATIONS VACANT

**PILOT RADIO**, Ltd., requires immediately fault finders and testers for radio and television alignment; experienced in factory production five-days a week with good rates of pay. APPLY or write to Park Royal Rd., London, N.W.10 [4517]

**RADIO** and television testers required in Cambridge; also vacancies for electronic wiremen and testers on transmission and specialised equipment.—Write, giving full details to the Works Manager, Pvc. Ltd. St. Andrew's Rd., Cambridge. [4720]

**RADIO** draughtsman required; excellent opportunity occurs for the radio technician with a flare for drawing; must also be able to develop circuits and produce technical literature; Acton area.—Write, stating age and salary required, to Box 1071. [4727]

**TECHNICAL** representative required by manufacturers of high-class electronic and industrial measuring instruments in West London area; applicants must have initiative, experience and some technical knowledge; good future for right man.—Box 1009. [4626]

**TEST** foreman for radio and radar production; must have sound technical knowledge and experience in control of male and female staff, London district.—Write, stating qualifications and salary, to Box Y5101, A.K. Adv., 212a, Shaftesbury Av., W.O.2. [4656]

**P.A.** engineer required, fully qualified and of smart appearance; experience in installation and maintenance work; write stating age, experience and salary required to British Relay Wireless, Ltd., Public Address Department, 343/5, Walworth Rd., London, S.E.17. [4778]

**ENGINEERS** required for servicing radar equipment; technical qualifications: Higher National certificate or degree; previous experience on electronics work; desirable; commencing remuneration up to £400 per annum, depending on experience or qualifications. APPLY Construction Department, The British Thomson-Houston Co., Ltd., Rugby. [4652]

**IN** any grade or capacity there is usually a job for the right man at South Essex Limited; applicants should state, in full, details of experience, salary or wage required, by letter; testimonials should not be forwarded with inquiry. THE Managing Director, Sound Sales, Ltd., West St., Farnham, Surrey. [40054]

**TELEVISION** and radio trouble shooters required by large company in East London area for increase in television production; applicants should have previous factory experience and adequate technical knowledge.—Kindly state full details to Box 1141. [4767]

**LOUDSPEAKERS**, production superintendent required, fully experienced on tooling and production of all sizes of loudspeakers for radio and television; state, in full, details of experience, salary or wage required, by letter; testimonials should not be forwarded with inquiry. APPLY Construction Department, The British Thomson-Houston Co., Ltd., Rugby. [4652]

**LOUDSPEAKERS**, fully experienced designer and servicing of industrial electronic apparatus, maintenance of mechanical transducers, etc.; West London area; forward full details of education, experience and salary required to—Box A.C.761, c/o Central News, 17, Moorgate, London, E.C.2. [4680]

**RADIO** factory in Bombay requires chief of test; must have held responsible position in test department Britain or U.S.A.; good technical background and some domestic receiver design experience desirable.—Send full particulars, including date of birth and salary required, to Box 1017. [4656]

**TO** first-class radio engineers.—We have vacancies in all parts of the country for skilled television engineers and, if you are proficient in radio theory we will train you in television. Lucrative positions offered to those passing the course.—Write for full particulars to Box 1034. [4709]

**CHIEF** engineer required to take charge of small laboratory at radio manufacturers in N.E. London; must have good technical ability in design of R.F. test equipment and radio components.—Write, giving full particulars of qualifications and experience, stating age and salary required, Box 1010. [4627]

**TELEVISION** Service Engineers required in all parts of the country by large company; these men will be required for service in the field and must be capable drivers; permanent position, with good prospects, for conscientious men.—Give full particulars and commencing salary required to Box 1030. [4702]

**ASSISTANT** required for Works Laboratories of important engineering factory in West London district, conversant with modern methods of metallurgical analysis, and electroplating solutions; age 20-25 years; commencing salary £300-£350.—Apply stating age, full details of education and experience to Box 1035 [4710]

# 'VIEW TV MASTER'


the Television set anyone can build at home from standard parts.

9in. or 12in. Screen ● 12 valves only ● Magnetic focusing ● Automatic interference Suppression ● Easily aligned without Instruments ● Constructor envelops containing 8 full-size stage-by-stage assembly drawings with full instructions and a 32 pp. book on construction, aerial systems, lining up, faults and correction, simple non-technical explanation of how T.V. works.

**5/-**  
6d. post.

We have also the necessary components, and are listing a few only:—

T.C.C., complete kit of condensers, £6/15/0. STENTORIAN V.B. Television speaker, with transformer, £1/7/6. BELLING-LEE T.V. Aerials, from 17/6. WESTINGHOUSE Rectifiers, complete kit of 5, £3/2/6. MORGANITE Potentiometers, 100 k., 250 k., each 4/6. EDISWAN, Line E.H.T. Transformer, £1/3; frame TRANS., 18/6; width control, 8/9; scanning coil, 25/6; focus coil, 19/6; Video, comp. choke, 5/-; metal chassis parts for tube mounting, 14/-. BULGIN kit of tag strips, etc., 12/6. VALVES, all available in reliable makes.

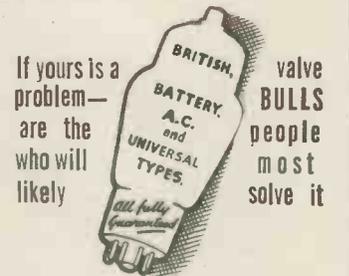

For instance, BRIMARIZED Replacements: 6B5, 6F5, 6N8, 6P8, 6U5/6C5, 12A7, 12F5, 12Z3, 15D1, 25A7, 32L7, 36, 39/44, 41, 45, 47, 50L6, 70L7, 84/6Z4, 117Z6, and more Equivalents, in fact the whole range of B.V.A. types at B.O.T. prices and many rare valves.

HIVAC, X9G, XV, XH, XD, XL, XLO, XP, XY and holders. Please enquire for any valve. We are fully stocked and well assorted. Lists sent. Equivalent books, 2/8.

SERVICE SHEETS again available! One of your own choice (even some out of print) is included FREE in a dozen of sheets at 10/6.

EASY TERMS again on all TAYLOR meters. Please ask for illustrated catalogue and application form.

BOOKS on every aspect of Radio in stock. We shall be pleased to send special list. Valve Equivalent charts with quick reference index, 2/8, post free.

RADIO, TELEVISION AND ELECTRICAL REPAIRS. Illustrated. Edited by Roy O. Norris, 448 Pages. Over 400 Illustrations. This new, comprehensive book is of universal importance to all interested in the servicing and maintenance and repair of radio, television and general electrical appliances. 10/6, post 9d.

EK-W.D. CHASSIS, with valves in brand new condition as follows: 1B5, 1T4, 1B5, 1B4, 27B.

MORSE BUZZER, training set, Silver point fitted tapper, twin coil buzzer, adjustable for high and low pitch, with diagram on back, 5/-. PIFCO. All-in-one Radiometers, A.C./D.C., 25/-.

AVO Instruments—full range available. Catalogue sent. CELESTION, 2 1/2in. Speakers, 25/6; 3in. Speakers, 12/6. Cabinets, 6/-. CONDENSERS: 4 mfd., 450 v., 2/-; 25 mfd., 25 v., 1/6; 0.5 mfd. 350 v., 1/-; Variable .0005 2-gang W. Trimmers, perspex covered, 7/6.

POTENTIOMETERS, 10,000 ohms, 2/-. TEST PRODS, superior job, 3/8.

### STOP PRESS

AMERICAN Service Manuals—A Bargain, greatly reduced from 12/6 each to 12/6 for three different volumes. Not many left.

AERIALITE Coaxial feeder, 60 foot Coil, 25/-. CELESTION all-purpose test meter, 10 ranges, A.C./D.C., moving coil, New Bargain, £3/7/6.

ENCYCLOPEDIA. Complete International Radio standard work, covering over 14,500 tubes on 496 pages. Full cloth bound, 42/- plus 9d. post.

Please mark envelope W.W.

Happy New Year to All Our Friends



**MAINS TRANSFORMERS.** Primary 230 volts 50 c. Secondary, 620-550-375-0-375-550-620 volts. The 620 or 550 volt winding is for 200 mA. and the 375 volt winding for 250 mA. Two 5-volt 3-amp windings are also provided. Both the 200 mA. and 250 mA. supplies may be used simultaneously and this transformer is ideal for supplying both exciter and P.A. of a 100-watt transmitter or for supplying driver and output stages of modulators and large amplifiers. Fully shrouded and weighing 24lb. Tested and guaranteed perfect. Price 52/6, carr. paid.

**AUTO TRANSFORMERS.** 0-69-115-161-184-207-230 volts all at 12 amps. Size: 9in. x 9in. x 9in. Price £3 0 0, carriage paid.

**INDICATOR TYPE R78A/APS15A.** Containing 43 valves amongst which are the following: 7 type 6L6G; 8 type 6SN7; 11 type 6AC7; 2 type 6AG7; 2 type 884; 3 type 5U4G; etc. 1 type 5FP7 and 1 type 2AP1 cathode ray tubes. Hundreds of resistors and condensers. 115 volt 400 c. input. All for £7/15/-, carriage paid.

**DOUBLE WOUND CHOKES.** 10H, 150 mA. each section, 20H., total 15/-, carriage paid.

**A. FANTHORPE**  
6-8 HEPWORTH'S ARCADE, HULL  
Phone: 35694

### TELEVISION CONSTRUCTORS!

E.E. Telesvisor Demonstrated Daily  
**MIDLAND CONSTRUCTORS ETC.**  
ARE INVITED TO SEND FOR OUR COMPLETE COMPONENT LIST AND TAKE ADVANTAGE OF OUR  
**PROMPT POSTAL SERVICE**

**J. T. FILMER** MAYPOLE ESTATE,  
BEXLEY, KENT.  
Tel. Bexleyheath 7257

### mathematics

Our new Home-Study Courses  
make maths really interesting  
and easy to learn. Write for  
booklet to Dept. W.

**T. & C. RADIO COLLEGE,**  
KING EDWARD AVE., AYLESBURY.

### SPOTLESS SURPLUS BARGAINS

Offered by

**RADIO UNLIMITED**  
Elm Road, London, E.17.

**TWIN METER TEST PANEL,** containing M/coil 0-5 m/amp. meter and 0-20 Voltmeter, 3 Potentiometers, Variable resistance, Switches, etc., 12/6.

**HEADPHONES.** Bal/alm phones. (BA5.) Complete with lead and plug, 4/6 pair. Complete with Throat Microphone, 6/6. M/coil type, complete with hand Mic., 5/6 set.

**P.M. SPEAKERS.** New and Boxed. Covered by our guarantee of satisfaction. 5in. 10/-, 6in. 12/6, 10in. 16/6, 12in. 35/-.

**M/COIL SUSPENSION TYPE MICROPHONE.** 30 ohms. New/Boxed and Guaranteed. 35/- post free.

### SITUATIONS VACANT

**COIL designer.**—Experienced engineer required for design of low-frequency coils and small power transformers, by laboratory in Esher area. Must be able to see designs through to production stage. This is a progressive and permanent appointment offering excellent working conditions in pleasant surroundings.—State full details to Box 1004. [4609]

**ADVERTISING Manager** required by firm supplying materials to radio manufacturers; knowledge of layouts and type; ability to write good English; excellent opportunity for advancement for ambitious man in London West End offices; commencing salary according to experience, at least £500 p.a.—Write stating age and history.—Box 1064. [4714]

**RADIO and television service engineer;** expansion provides opportunity for additional service engineer in business in which vacancies seldom occur; good pay and conditions for a good man who wants to stop in a good job.—Write for interview and further details. Arthur Chattell, Murphy and H.M.V. dealer, 40, High Street North, Dunstable. Tel. 340. [4665]

**JUNIOR engineers** for development work on a wide range of electronic work, excluding television and radio; applicants should have a good grasp of basic principles of electronic circuitry and some experience of similar work.—Write, stating age, experience and salary required, to Cinema-Television, Ltd., Worsley Bridge Rd., Lower Sydenham, S.E.26. [4722]

**ELECTRONIC research and development engineers** required, first class honours degree or equivalent, preferred; vacancies for senior engineers with industrial experience and for juniors; interesting new projects; pension scheme; apply stating age, qualifications, experience and salary required to Personnel Manager, Fairey Aviation Company, Ltd., Hayes, Middx. [4350]

**ELECTRONIC engineer,** aged 25-30, required for work in inspection department; qualifications: Higher National Certificate standard with production experience of radio engineering, knowledge of A.I.D. work in this branch would be an advantage.—Please write, giving full details, to Personnel Dept., E. M. I. Engineering Development, Ltd., Blyth Rd., Hayes, Middlesex. [4769]

**TECHNICAL assistant** required in patent department of company engaged in the manufacture of precision instruments, radar, etc.—knowledge and experience of electronics and UHF technique required and experience of patent work; salary according to qualifications and experience. Write stating age, experience, etc., to Personnel Manager, Sperry Gyroscope Co., Ltd., Great West Rd., Brentford, Middlesex. [4677]

**ACOUSTIC physicist** required by established London company for technical sales development with medical profession on science of hearing, extremely interesting and satisfying work; qualifications are extensive knowledge acoustics and electronic theory, some practical experience; good appearance and personality, business ability, energy; age 25-35 and capable of earning a salary of £750 p.a. minimum.—Write Box 1073. [4731]

**SENIOR electronic research engineers** required for development of (a) communication equipment up to 400 mc/s. (b) h.f. signal generators. (c) aerial systems. (d) industrial electronic equipment. (e) development of components; London area; salary and status commensurate with qualifications and experience.—Write in confidence, stating age, full details of qualifications and experience, to Chief Engineer, c/o Box 1007. [4621]

**AN assembly shop superintendent** is required by a well-known firm of loudspeaker manufacturers. He will be required to control all assembly processes from enamelling to packing and must have some years' experience in the mass production of loudspeakers. The position, which is a permanent one, has become available owing to ill-health; applicants should write, giving their age, experience and salary required, to Box 1008. [4625]

**SENIOR Engineer** required by South London Telecommunications Company to specialize in enlargement of range of polarized relays. Sound fundamental knowledge and familiarity with laboratory technique essential; experience in relay design problems an advantage; minimum commencing salary £700-£725 p.a., maximum salary according to merit.—Write Box Y5276, A.K. Adv., 212a, Shaftesbury Avenue, London, W.C.2. [4703]

**SENIOR engineer** to take charge of laboratory engaged upon design, development and application of R.F. heating equipment; applicants must have an Honours Degree in engineering and previous experience in R.F. heating; age from 28-45 years; salary to be paid in accordance with qualifications and experience; applications should be addressed to the Personnel Manager, Airmec Laboratories, Ltd., Cressex, High Wycombe, giving full details. [4780]

**SPECIALITY radio-telephone salesman,** salary, comm., expenses; senior and junior development engineers and draughtsmen for radio, radar, electronics, etc.; service engineers, radio, television, radar, electronics; wiremen (skilled and semi-skilled); radar, radio, etc. R.F. repairers, testers, inspectors, radio, television, radar; numerous other positions vacant.—Technical Employment Agency, 179, Clapham Rd., S.W.9. (Brixton 3487). [4742]

## SOLONS FOR YOUR SOLDERING JOBS!

Types available—65 watt oval tapered bit,  
65 watt round pencil bit,  
125 watt oval tapered bit,  
125 watt round pencil bit,  
240 watt oval tapered bit.



These five models will satisfy practically every soldering demand whether for the occasional household job or continuous soldering under workshop or factory conditions. With the Solon the heat is in the bit itself... continuously... hour after hour; all connections housed at end of handle away from heat. Each model complete with 6 feet Henley 3-core flexible. Now available from stock. Write for folder Y.10.

**W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.**  
51-53 Hatton Garden, London, E.C.1

### Autofeed SOLDERING IRON

Simple self-feed speeds up soldering. Better work. Saves solder. Write for leaflet 30.J.



### RUNBAKEN · MANCHESTER 1

### ELECTRONIC & ELECTRO-MECHANICAL EQUIPMENT

developed for industrial applications. Reasonable charges.

**SPENCER-WEST**  
QUAY WORKS, Gt. YARMOUTH

### TELEBOOSTERS

for long range Television reception. Super high gain single-stage pre-amplifier. 2 stage, 1 VR91 valve, slug tuned, London or Birmingham. Co-axial plugs and sockets, flying leads for High and Low tension, fully screened, low noise. Price £2/12/6. Power units for above £3/10/0.

S.A.E. for trade test report.

**BOSCOMBE RADIO & ELECTRIC,**  
595, Christchurch Road, Boscombe,  
Bournemouth. Phone: 36522

**Up-to-date and first-rate Radio Frequency Heating Equipment**

By L. L. Langton, A.M.I.E.E. The author has been intimately connected with the development of this modern industrial process, and his book is of first-rate importance to engineers and others interested in the equipment which has been evolved. Illustrated 17/6 net.

"Rather more than the usual type of technical handbook... ten highly-informative chapters."—TIMBER AND PLYWOOD.

**Pitman**  
Parker Street,  
Kingsway, London, W.C.2

**DUKE & CO.,**  
219 ILFORD LANE,  
ILFORD, ESSEX. ILF. 0295

This Month's Bargains

**SPEAKERS.** TRUVOX Elliptical, very latest, 19/8; 3 1/2 in. 9/6; Standard 5 in., 10/-; 5 in. with transformer, 13/8; 6 in. Truvox, 11/3; 8 in. Plesey, 11/9; 10 in., 19/8; 12 in., 35/6. All guaranteed new goods.

**CONDENSERS.** 32 mfd. 350 v. D.C., 3/6; 8-16 mfd. 450 v. D.C., 2/6; 16-16 mfd. 350 v. D.C., 3/6; 16 mfd. 350 v. D.C., 3/-; 16 mfd. 450 v. D.C., 3/6; 8 mfd. 500 v. D.C., 2/6; 8-8 mfd. 450 v. D.C., 3/6; .005, 0.1, .01 and .25 mfd. 500 v. D.C., all at 6d. each. New guaranteed standard sizes and fittings.

**TRANSFORMERS.** O/P transformers, 45:1, 2/6; multi-ratio, 4: ratio, 4/6; 5 ratio, 6/6. I.P. transformer, 450 Kva., slug tuned, 8/8 pair. Dual range T.R.F. coils, aerial and H.F., 6/6 matched pair with drawings.

**TUNING CONDENSERS.** .0005 single, 2/2; .0005 two-gang, 4/6; 2-gang, 2/6.

**DOMESTIC RADIO RECEIVER KITS.** A 3-valve T.R.F. 2-wave band receiver, with new and improved circuits, giving quite surprising results, all parts included; condensers, resistors, coils, speaker, chassis, valves and a smart walnut, bakelite cabinet. Complete kit, 24 18s. 6d. Ivory cabinet available. 6/- extra.

**HEADPHONES.** New condition, low resistance, 2/6; high resistance, 4/6.

**CRYSTAL SETS.** Reception guaranteed. A neat job in bakelite cabinet, 8/6.

**SPECIAL OFFER.** Electrolytics, first quality, 50 mfd. 25 v. D.C., and 4 mfd. 200 v. D.C. Cardboards, wire ends; 3 of each for 3/- plus 9d. post. Trimmers, air spaced, new ex-W.D., 9d. each.

**METERS.** One 1.5 m/a, full scale and one 40-40 voltmeter, 4/-, post 1/- 8-pin International Octal Anphonal holder, 1d. each in dozens, plus 4d. post. 9in. TELEVISION white plastic escutcheons, 2/6, post 9d.

**INDUCTION MOTORS,** 200/250 v. A.C. for milk shakes, complete with long spindle, runs smooth and silent, small, 17/6, plus post 1/-.

**SMOOTHING CHOKES,** 40-60 m/a, new, good make, 1/-, plus post 3d.  
**E.H.T. TRANSFORMERS,** 2,000 v., 19/6. Ideal for V.C.R. 97.

**REMEMBER.** We carry the largest valve stocks in E. London and at only B.O.T. prices. New valves post free. When remitting C.W.O. please, an 1/- allow sufficient for postage.

Send stamps ONLY for detailed lists. TRADE enquiries invited.

**SITUATIONS VACANT**

**SENIOR** television development engineer required by large manufacturer in the London area; applicants must have several years experience of television development and adequate technical education; a permanent position with a salary of £300 per annum is available to the selected applicant; kindy state full particulars including age to—Box 1119. [4743]

**MARCONI'S WIRELESS TELEGRAPH Co.,** require for their research laboratories at Chelmsford, senior and junior research and development engineers for domestic television receivers; applicants, who must have had extensive experience in television receivers, should write giving full particulars quoting reference 265 to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [4651]

**MARCONI'S WIRELESS TELEGRAPH Co.,** Ltd., Chelmsford, require a machine shop superintendent to take charge of a light machine shop employing 160 operatives; applicants must have adequate experience covering this class of work and be conversant with ratelising, planning and progress techniques.—Write giving full particulars quoting ref. 319 to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., Westminster, S.W.1. [4666]

**MARCONI'S WIRELESS TELEGRAPH Co.,** Ltd., Chelmsford, require an assembly shop superintendent, experienced in modern assembly methods covering light switchgear, control gear or light and heavy duty wireless equipment; applicants with a comprehensive knowledge of ratelising, planning and progress work should write giving full particulars, quoting ref. 318, to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., Westminster, S.W.1. [4667]

**TECHNICAL** assistant required by Alrmec Laboratories, Ltd., Cressex, High Wycombe, for their mechanical engineering laboratory. Applicants should have had previous experience in light engineering and electric-mechanical engineering and have technical qualifications to the Higher National Certificate standard in mechanical engineering.—Applications should be addressed to the Personnel Manager, stating age, qualifications, experience and salary required. [4634]

**TECHNICAL** representative, aged 25-35, required by the Morgan Crucible Co., Ltd., for the sale of radio components; working knowledge of electronics essential and some experience in sales field desirable. The successful applicant must be resident in London area of energetic personality and ambitious to be successful in this sphere.—Write, giving details of age, experience, qualifications and salary required, to the Staff Manager, Battersea Church, S.W.11. [4622]

**A GRADUATE** engineer or equivalent, with experience in the operation, installation and maintenance of broadcasting or television equipment required by Marconi's Wireless Telegraph Company; applicants with similar Service experience will be considered, it is desirable that candidates should also have a knowledge of sales and contracts work.—Write giving full details quoting ref. 264 to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., Westminster, S.W.1. [4671]

**VACANCIES** exist at the Nelson Research Laboratories, English Electric Co., Ltd., Stafford, for draughtsmen. Applicants must have had experience of electronic circuit or similar work and preference will be given to those interested in electronic circuit development; salary in accordance with age, qualifications and experience.—Write giving full particulars, quoting reference 109, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., Westminster, S.W.1. [4654]

**ENGINEER** for a laboratory engaged upon design and development of R.F. communication equipment; applicants must have technical qualifications up to a degree standard in engineering or physics; previous experience must preferably have been in radio or light engineering industry; the age range is from 24-35 years; salary will be paid in accordance with qualifications and experience; application should be made in writing to the Personnel Manager, Alrmec Laboratories, Ltd., Cressex, High Wycombe. [4781]

**ELECTRONICS** Engineer.—Applications are invited for the position of Instrument Engineer (Electronics) in a large iron and steel works plant in this country. Candidates will be required to undertake the original design and development of electronic apparatus and its application to works problems. Previous steelworks experience is not essential but initiative and technical ability are considered of first importance. A substantial salary will be paid to the suitable applicant.—Replies giving details of experience to Box 1032. [4705]

**A VACANCY** exists with Marconi's Wireless Telegraph Company for a resourceful and tactful young man to take charge of a small mobile television demonstration unit; the successful candidate must have wide practical experience in the operation and maintenance of this type of equipment or Service equivalent; applicants, who must be of at least H.N.C. standard and who are prepared to travel at short notice to any part of the world should apply in writing, quoting ref. 303, to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., Westminster, S.W.1. [4670]

**MAINS TRANSFORMERS**

As supplied to the Ministry of Supply, B.B.C., Education Authorities, etc. Interleaved and impregnated. Screened primaries tapped 200/250 v.

**DROP THROUGH TYPE. TOP SHROUD.**

- (a) 250-0-250 v. 60 mA., 6.3 v. 3 a., 5 v. 2 a. 15/6
- (b) 250-0-250 v. 60 mA., 4 v. 4 a., 4 v. 2 a. 15/6
- Following types have Universal L.T. windings.
- 6.3-4-0 v. 4 a. C.T., 5-4-0 v. 2 a.
- (c) 250-0-250 v. 80 mA. 17/6
- (d) 300-0-300 v. 80 mA. 17/6
- (e) 350-0-350 v. 80 mA. 19/8
- (f) 250-0-250 v. 100 mA. 19/8
- (g) 300-0-300 v. 100 mA. 19/8
- (h) 350-0-350 v. 100 mA. 19/6

**FULLY SHROUDED UPRIGHT TYPES.**

- (i) 350-0-350 v. 150 mA., 6.3 4-0 v. 6 a. C.T., 5-4-0 v. 3 a. 39/-
  - (j) 425-0-425 v. 180 mA., 6.3 v. 4 a. C.T., 6.3 v. 4 a. C.T., 5 v. 3 a. 42/6
  - (k) 425-0-425 v. 180 mA., 4 v. R a. C.T., 4 v. 4 a. C.T., 4 v. 4 a. 42/6
  - (l) 425-0-425 v. 180 mA., 6.3 v. 4 a. C.T., 4 v. 2 a. C.T., 4 v. 2 a. C.T., 5 v. 3 a. 47/-
- Note.—Model (j) above is suitable for Williamson Amplifier.

**WILLIAMSON OUTPUT TRANSFORMER.**

Built to Author's specification, 1.75 secondaries £3 12 6

**SMOOTHING CHOKES.**

40 ma., 5/-; 60 mA., 6/6; 90 mA., 7/-; 100 mA., 12/6; 200 mA., 21/-; 250 mA., 25/-.

**FEEDER UNITS.**

High-class radio feeder units with R.F. stage. Switched pick-up sockets. Glass shades. Completely aligned.

**MODEL A.** Covers 16/50, 190/500 and 900/2,000 metres. Price, including P. Tax. £10 8 6  
Set of 4 valves £2 11 3

**MODEL B DE LUXE.** Covers 45/145, 190/550, 900/2,000 metres and six ranges of band spread. Price, incl. P. Tax. £18 7 8  
Set of 5 valves £3 2 3

Note.—Both feeder units illustrated in our catalogue

**"VIEW MASTER" TELEVISION RECEIVER.**

Designed in conjunction with prominent British Radio Manufacturers using new components—not surplus. **CONSTRUCTOR'S ENVELOPE**, containing full instructions, layouts, diagrams, etc., 5/4, post free.

W.B. Chassis and Speaker, etc. £8 5 0  
T.C.C. Condensers £8 15 0  
Westinghouse Rectifiers £3 2 6  
Morganite Resistor Kit £1 6 9  
Plessey Transformers, Focus Coils, etc. £5 12 6  
Govern Wire Wound Potometers £19 3 6  
Bulbin Panels and Switches £19 3 6  
Wearite Coils and Choke £1 2 0

**B.V.A. AND TUNGSRAM VALVES.**

Over 350 different types in stock, including difficult obsolete types. B.O.T. prices. Send for the valve you urgently require. C.O.D.

**POLISHED ALUMINIUM CHASSIS, 16 S.W.G., 4 SIDES, 3 in. DEEP.**

10in. x 6in., 10in. x 8in., 8/6; 12in. x 9in., 10/6; 14in. x 9in., 16in. x 9in., 11/6; 20in. x 8in., 12/6.

**EDDYSTONE SHORT-WAVE COMPONENTS.**

Full range stocked. Eddystone illustrated catalogue, 6d.

**HIGH FIDELITY LOUDSPEAKERS.**

Goodmans T2/1205, 12in. P.M. £6 15 0  
Goodmans Axion, 12in. P.M., Twin Cone £8 8 0

**INSTRUMENT WIRES.**

Comprehensive range in enamelled, cotton and silk covered-copper wires from 16 S.W.G. to 40 S.W.G.

**EX-GOVT. SURPLUS.**

A good range of equipment at bargain prices. S.T.C. Ball Microphones. List approx. £22 £4 15 0  
Mine Detector Amplifiers. Containing three 11A valves in ceramic base, condensers, resistors, etc. £1 2 6

SEND NOW 5d. in stamps for LATEST CATALOGUE.

Terms C.W.O. or C.O.D.

**COULPHONE RADIO**  
"The Return of Post Mail Order Service"  
**53, BURSCOUGH STREET,**  
**ORMSKIRK, LANCs.**

Phone 987

# frequency calibration service

## 5/-

The frequency of any type or make of Quartz Crystal Unit will be measured, and a calibration certificate issued. Crystal Units are returned to the customer within 48 hours. For further particulars write for leaflet QC. 4812 to:—

SALFORD ELECTRICAL INSTRUMENTS LTD., Pee Works, Silk Street, Salford, 3.

## BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE.

3,000 STANDARD STOCK SIZES

No Quantity too Small List on application

London: H. ROLLET & Co., Ltd. Liverpool: 6, Chesham Place, S.W.1. Kirkby Estate. SLOane 3463 SIMONSWOOD 3271/3

## INSTRUMENT WIRE

ENAMELLED, D.C.C. SILK COVERED, ETC., all sizes from 10 s.w.g. to 42 s.w.g. in stock. INSULATING MATERIALS, Empire cloth, leatheroid, paxolin, sleeving etc.

Send S.A.E. for list to

STAN. HOLT,  
349, HIGH ST. SMETHWICK, STAFFS  
Telephone: WOODGATE 3789

## SUPACOILS

### OFFER

**Model 30 Coil Pack.**—The 3-waveband superhet pack with adjustable iron cored coils and trimmers for absolute accuracy in padding and tracking. This pack is gaining more and more favour among experienced engineers and amateurs for its sound design, high quality workmanship and high sensitivity and selectivity ..... 21/- or 24/- fully aligned.

**Model 40 Coil Pack.**—Similar to the Model 30 but with RF stage ..... 42/- or 47/- fully aligned.

**Model 30 Tuning Unit.**—This is now one of the most popular units for easy and efficient superhet construction. It consists of a Model 30 coil pack, pair "MM" I.F. transformers, 2-gang condenser and attractive dial. Components are 48/6 aligned together as a unit in an actual receiver, and sealed. No further alignment is required.

**Model 40 Tuning Unit.**—Similar to above with provision for R.F. stage 76/9 FREE. A Free Copy of the enormously successful HOME CONSTRUCTOR'S HANDBOOK will be given to every purchaser. Or a copy can be obtained for 1/- from

**SUPACOILS (Mail Order Office)**  
98, Greenway Avenue, London, E.17

### SITUATIONS VACANT

**ENGLISH ELECTRIC** require a senior circuit engineer (electronics) for their Nelson Research Laboratories at Stafford. Applicants must hold a university degree or Associate Membership of the Institution of Electrical Engineers, have had two or three years' industrial experience, and be interested in the development of electronic circuits. The work will involve design of special circuits.—Write, giving full particulars, quoting reference 313, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., Westminster, S.W.1. [4650]

**BRITISH** engineering firm in Bangkok, Thailand (Siam), require the services of a qualified radio engineer with experience in the sale and servicing of domestic radio receivers, sound amplifying equipment and, if possible, theatre sound equipment; principals hold representation in Thailand for well-known American manufacturers, and applicants, who should preferably be unmarried and not be more than 30 years of age, must be capable of handling and organising a trained local staff of salesmen and service engineers.—Write in first instance to Box "R.R.R." c/o 95, Bishopsgate, London, E.C.2. [4685]

**SENIOR** inspector required by the component division of the Plessey company; applicants must have predominantly electrical training, comprehensive knowledge of radio components and allied electrical equipment, and must have adequate technical knowledge. To be between the age of 30 and 45 years, having the above experience and having controlled a large inspection staff, the company offers a senior and permanent position with excellent prospects.—Written applications only, stating full details including a trained local staff of salesmen and service engineers.—Write in first instance to the Personnel Manager, The Plessey Co., Ltd., Ilford, Essex. [4647]

**UNIVERSITY COLLEGE LONDON** has a vacancy for a technician in the Department of Phonetics for work mainly concerned with acoustics and hearing; age between 20 and 35; applicants should hold National or Higher National Certificates in Communications or Electrical Engineering or have had equivalent experience; initiative and adaptability more essential than previous experience of audio-frequency work; salary according to qualifications and experience; family allowance and pension schemes; write in the first instance for application form to the Secretary, University College London, Gower St., W.C.1. quoting Phonetic/1. [4770]

### SITUATIONS WANTED

**R**EPRESENT or agency, sales or tech., in Preston area by technician, part-time, own car.—Box 1003. [4603]

**I**NSSTALLATION engineer, City & Guilds, aged 33, experienced in control equipment, marine, etc., seeks post demanding initiative in South Coast area; full time or part.—Box 1067. [4723]

**P**OSITION as technical representative required by man with over 10 years' executive experience on design and development of radio and television; good appearance and address; own car.—Box 1002. [4601]

**Y**OUNG man, educated in England to matriculation, at present with Canadian Defence Research Board, Ottawa, 10 years' radio experience, understanding of Canadian requirements, sales methods, wishes to represent British firm in Eastern Canada.—Reply D. Adams, 584, MacLaren St., Ottawa, Canada. [4631]

**A**DVERTISER, 20 years experience, television, radar, aviation and navigation radio, technical and sales, also technical editorial experience England and N. America, at present with large manufacturer, seeks sales promotion or press or appointment; willing to go abroad; R.A.F. and Army service.—Box 1025. [4576]

### AGENCIES

**O**LD-ESTABLISHED export merchants, with excellent overseas connections, desire representation of small radio-makers anxious to increase export turnover.—Box 1031. [4704]

### FINANCIAL PARTNERSHIP

**D**IRECTORSHIP offered keen man with knowledge of quality amplifiers; must be first-class man with good technical knowledge; knowledge of television, Canadian requirements; accommodation, flat with 4 rooms could possibly be arranged; capital required, about £1,500/£2,000.—Full details to Box 1018. [4658]

### BUSINESSES FOR SALE AND WANTED

**F**ACTORY possessing machine tools to the value of £1,000,000 is desirous of selling entire plant, either in bulk lots or as individual items, machines of all types offered; quick sale is essential for accommodation reasons; only enquiries for specific machines replied to.—Box 1174. [4775]

**W**EST London.—Small manufacturing business making well known quality product for sale as going concern, very valuable lease of fine corner premises and valuable goodwill; price including lease, stock (about £2,000) all at £3,500; ample scope for enterprising person.—Write Box 1023. [4674]

**P**ROMINENT position, main road, West London, shop, service room, and flat of 4 rooms, for sale as going concern, Murphy dealership doing good business; price all at, including lease, goodwill, stock and H.P. accounts, £4,500; ample scope for purchaser to add cycles, etc.—Apply Box 1024. [4675]

## Lyons Radio

Accumulators. Brand New. Unused Govt. Surplus American made.

12 v. 34 amp. hour at 5 hr. rate. Case size 10 1/2 x 10 x 5 1/2 in. approx. with terminal cover projecting on one side 3 1/2 in. Price 75/-  
24 v. 11 amp hour at 5 hr. rate. Case size 8 x 7 1/2 in. sq. approx. Term. cov. prjts. 3 1/2 in. Price 52/6. Carriage either type 10/6. (5/- returnable on packing crate).

**Receivers Type R1132.** High-grade 11-valve superhet. Frequency range 100 to 125 Mc/s. Fitted with precision slow-motion drive, tuning meter, R.F. & L.F. gain controls, etc. As new and unused and supplied with circuit diagram in Maker's original packing cases. Price £4/19/6. Carriage free.

**Power Unit Type 3.** Operation from 200 to 250 v. A.C. mains with outputs of 220 v. D.C. at 70 mA and 6.3 v. A.C. at 4A. Designed for use with the R1132 and 1481 receivers but suitable for most other communications receivers. Size 19 x 7 x 1 1/2 in. Two section filter gives high degree of smoothing. Fitted with 0/300 voltmeter and 0/150 milli-ammeter. In perfect working. PRICE £4/4/0. Carriage free.

**Special Offer.** Receiver R1132 and Power Unit together, £8/8/-. Carriage free.

3 GOLDHAWK ROAD (Dept. M.W.)  
SHEPHERDS BUSH, LONDON, W.12  
Telephone: Shepherds Bush 1729

## TELEVISION RECEIVERS SCANNING and FOCUS COILS TIME BASE COMPONENTS 7KV. EHT. RF. UNITS and TRANSFORMERS



Publications post free

**HAYNES RADIO LTD.**  
Queensway, Enfield.

Our 1950 fully Illustrated  
Catalogue is now Available  
3? Post Free

# BERRY'S

(SHORT WAVE) LTD.

25, HIGH HOLBORN, LONDON, W.C.1

## re THOMAS BERTRAM WIMBUSH Deceased

PURSUANT to the Trustee Act 1925, Section 27 NOTICE TO CREDITORS.

NOTICE IS HEREBY GIVEN THAT ALL PERSONS having claims against the Estate of THOMAS BERTRAM WIMBUSH late of 27/29 Canning Street Burnley in the County of Lancaster who died at Regent Street Haslingden in the said County on the 20th day of March 1949 and Administration of whose estate was granted on the 23rd day of September 1949 by the Principal Probate Registry to Audrey Winifred Wimbush and Clara Wimbush must send PARTICULARS of such claims to the undersigned Solicitors on or before the 31st day of January 1950 after which day this Deceased's assets will be distributed having regard only to the claims of which Notice shall have then been received AND all persons indebted to the said Estate are asked to pay their respective debts at once.

DATED this 4th day of November 1949.

(signed) Robt. Kidd, Whitaker & Pratt,  
1 Queen Street,  
Accrington,  
Lancs.

## Thinking of building a Television Set?




### 10 VALVE 1 1/2 METRE SUPER-HET

Ideal for conversion into Television Receivers. I.F. 12 Megs. Band width 4 megs. Co-axial input and output sockets. 10 Mazda Main type VR65 (8P6) valves, 6-3 volt filaments.

4 gns.  
Carriage Paid


### AS.V. INDICATOR UNITS Type 6 H.

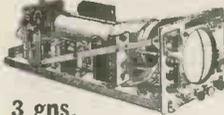

Containing seven valves and one 6 in. Cathode Ray Tube type VOR 37. Brand new and unused. In sealed wooden transit case

3 gns.  
plus 5/- Carriage

### 12 VALVE RADAR UNITS

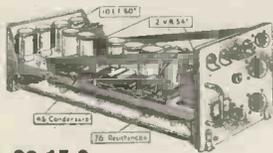


New and unused. Contain 10 type VR 91 (EF 50) Valves, 2 type VR 54 valves, 45 various condensers, 76 various resistances, 2 Transformers, 1 Relay.

£2.15.0  
each  
Carr. paid.

Offered at a fraction of price of valves alone.

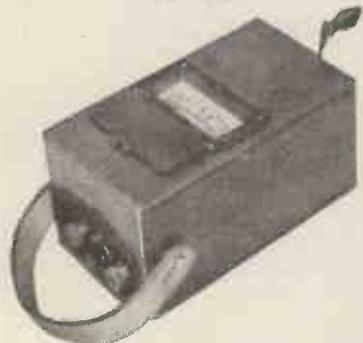Dept. W WIRELESS INSTRUMENTS (Leeds) Ltd  
54-56 The Headrow, Leeds. Tel. 22262.



## THE "MAJOR" INSULATION TESTER

Compact and light in weight, this latest addition to the Record family has a Constant Pressure generator of patent design. Ranges up to 500 volts 50 megohms with or without Continuity range of 0/30 ohms are available. Send for leaflet D/b.

THE RECORD ELECTRICAL CO. LTD.  
BROADHEATH, ALTRINCHAM, CHESHIRE  
Phone: Altrincham 9221/3 'Grams: "Infusion" Altrincham.  
London Office: 23 Victoria St., S.W.1. 'Phone: Abbey 5148

**BUSINESSES FOR SALE AND WANTED**  
RADIO, television and electrical appliances, fittings and accessories, established in main shopping centre S.W. district; moderate rent with living accommodation; good stock with fully equipped workshop; lease, stock, fittings and equipment, £1,500 or near offer, owner going abroad.—Box 1019. [4659]

**TECHNICAL TRAINING**  
ADVANCED Radio Servicing Course, thoroughly reviews receiver design theory and practice; introduces faster, more accurate servicing methods.—Details, BCM/Circuit, London, W.C.1. [4569]

**TUITION**  
RADIO training.—P.M.G. exams and I.E.E. Diploma; prospectus free.—Technical College Hull. [1061]

WIRELESS officer's attendance and "Radio-certs" postal course.—Apply Manager, The Wireless School, Manor Gdns., London, N.7.

"MARINE and Air Radio Officers Course."—The first-class P.M.G. certificate assures early and well-paid employment; obtain it with the help of our day-time course commencing January 1950.

WRITE for full details to E.M.I. Institutes, Ltd., Dept. W.W., 43, Grove Park Rd., London, W.4. Chiswick 4417-8. [10001]

WIRELESS, land, sea and air; students, both sexes, age 14 upwards, trained for interesting appointments in all branches of radio; low fees, boarders accepted; stamp for prospectus.—Wireless College, Colwyn Bay. [10018]

A.M.I.E.E., City and Guilds, etc., on "no pass, no fee" terms; over 95% successes. For full details of modern courses in all branches of electrical technology, send for our 176-page handbook—free and post free.—B.I.E.T. (Dept. 385A), 17, Stratford Place, London, W.1. [12570]

A.M.I. Mech.E., A.M.I.E.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 176-page handbook—free.—B.I.E.T. (Dept. 387B), 17, Stratford Place, London, W.1. [13777]

TELEVISION postal course for radio trades Examination Board's diploma, also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting Licence.—Apply British School of Telegraphy Ltd., 179, Clapham Rd., London, S.W.9. (40 years' experience in coaching students in wireless telegraphy and allied subjects.)

SEE the world in a well-paid and interesting job, enrol now for one of our marine and air radio officers' courses of instruction; constant personal supervision and attention by our expert instructors with recent operational experience; apply for free literature giving full particulars.—E.M.I. Institutes, Dept. W.W., 11, Pembroke Square, Notting Hill Gate, London, W.2. [10001]

TELEVISION.—The Gothic Television School specialises solely in training in television. All tutors possess university degrees and/or corporate membership of professional institutions and are appointed individually to postal course students to ensure complete and thorough training. Principals, M.B.E., B.Sc., M.Brit. I.R.E., education committee members, etc. Courses assume no previous television knowledge and provide guaranteed training for Brit. I.R.E. and R.T.E.B. examinations. Numerous well-known companies have adopted the School's Basic Television Course as standard television training for their staffs. Moderate fees. Details from Gothic Television School, 13, North Avenue, London, W.13. [10051]

**BOOKS, INSTRUCTIONS, ETC.**  
VIEWMASTER TV construction, 8 full-size, stage-by-stage, assembly drawings with 32-page booklet, 5/-+6d post.  
"EE" home-built televisor for Sutton Coldfield, 77-page book with wiring diagram, 4/6+4d post.  
Bernards high definition TV manual, 54-page book with details for a unit-built receiver, 3/8+3d post.  
Brimar radio valve and tube manual, latest edition, 191 pages of valve data, including all the latest midget types, formulae and circuits, 4/-+6d post.  
Eddystone 145 Mc/s guide, 1/6+3d post.

LOUDSPEAKERS, The Why & How of Good Reproduction, 87-page book by G. A. BRIGGS of Wharfedale Speakers, 5/-+4d post.  
Sound reproduction, companion volume to Loudspeakers, 143 pages by the same author, 7/6+6d post.  
International Radio Tube Encyclopaedia, 410 pages, giving details and pin connections of 15,000 valves of every known type in the world, made by 97 different makers, CV types are included, technical data is in 14 languages, 42/-post free.

FRITH RADIOCRAFT, Ltd., Churchgate, Leicester. [10028]

"PERSONAL Portables," the new book by E. N. BERRY, describes a whole range of tested loudspeaker-type personal sets. Build yours now for the holiday season, the circuits, layouts, drilling, constructional and wiring diagrams make it easy and interesting; 2/8 post free from Bradbooks, Sennen, Penzance, Cornwall. [4681]

"RADIO Valve Data: Characteristics of 1,600 Receiving Valves." Compiled by the staff of "Wireless World." Gives the main electrical characteristics for normal operating conditions, arranged in tabular form, and diagrams showing base connections. Index enables any valve to be found by type designation, size 10in wide x 7in 80ps x 3/8 net, from all book-sellers, or 3/9 by post from The Publishing Dept., Dorset House, Stamford St., S.E.1. [PS]



## PROMPT & EFFICIENT SERVICE CASH OR EASY TERMS

When you purchase on L.R.S. Convenient Terms. Formalities are reduced to a Minimum and you deal direct with us from beginning to end.

## ARMSTRONG ALL WAVE CHASSIS (incl. speaker and output transformer)

Model EXP/83/3. Cash price £18 17 1, or £4 12 0 with order and 12 monthly instalments of 26/-.  
Model RF103/3. Cash price £26 10 0 or £4 12 0 with order and 12 monthly payments of £2 0 0.  
All other Armstrong Chassis are available on similar terms.

Also available on Easy Terms  
**GOODSELL-WILLIAMSON**  
AMPLIFIER and TUNER UNITS  
COLLARO RADIOGRAM UNITS  
and RECORD CHANGERS

LEAK TUNERS and AMPLIFIERS  
GRAMPHON SOUND EQUIPMENT  
SOUND SALES AMPLIFIERS  
and TUNERS

A.G. BARKER'S LOUDSPEAKERS  
GOODMAN'S LOUDSPEAKERS  
Axiom 12 and 22 also 12" Standard Unit

HARTLEY-TURNER LOUDSPEAKERS  
WHARFEDALE LOUDSPEAKERS  
ATLAS BATTERY CHARGERS

and most of the other High-Grade Equipment advertised in "Wireless World".

## also REMINGTON FOURSOME ELECTRIC SHAVERS

Please let us know your Radio requirements (enclosing 2½d. stamp) and we shall be pleased to quote.

Personal attention to all enquiries  
**THE LONDON RADIO SUPPLY CO.**  
Estd. 1925  
**BALCOMBE, SUSSEX**

We are preparing a waiting list for the first 1950 batch of Voigt Senior P.M. Units with the new re-matched diaphragm.

There is delay while details of the pole tips are being revised, otherwise generally as per "W.W." review last March p.103. Anticipated price including B.B.C. corrector £40 ex-works. Suitable horns (in the white) at £19.10.0 and £47.10.0 ex-works. For details of the new diaphragm see "W.W." Sept. p.33 adverts.



VOIGT PATENT LTD.,  
c/o BCM/Voigt,  
London, W.C.1.

P.S. Mr. Voigt has not yet recovered fully.

**HILL & CHURCHILL LTD.**  
BOOKSELLERS

**SWANAGE, DORSET**

Available from stock

Fink—"Principles of Television Engineering"	33/-
Chaffee—"Theory of Thermionic Vacuum Tubes"	39/-
Reich—"Theory and Applications of Electron Tubes"	33/-
Schelkunoff—"Electro-Magnetic Waves"	42/-
Terman—"Measurements in Radio Engineering"	27/-
Zworykin & Morton—"Television"	42/-
Cooke & Orleans—"Mathematics Essential to Electricity & Radio"	21/-
Hudson—"An Introduction to Electronics"	15/-

Postage Extra

CATALOGUE ON APPLICATION

**★ "Globe-King" MARVEL (REGD) IN MINIATURE SHORT-WAVE RADIO KIT**

Probably the smallest one valve Short-Wave Radio receiver in the world using standard parts with Bandspread tuning device. "Magnificent performance" . . . vide testimonials British Isles and Abroad. Built and designed to precision standards, complete kit costs only 49/6—write today for descriptive catalogue.

**JOHNSONS (RADIO) MACCLESFIELD (SPECIALISTS) CHESHIRE (ENG)**

**TESTSCOPE Mains Tester**

For high & low voltage testing—:

1/30 & 100/850 volts A.C. or D.C. New popular model for 60/400 volts A.C. or D.C. — 2/6. Write for interesting booklet 50P.

**RUNBAKEN - MANCHESTER 1**

100 kcs. QUARTZ CRYSTAL UNIT

Type Q5/100



for Secondary Frequency Standards

★ Accuracy better than 0.01%. ★ Temperature coefficient 2 parts in a million per degree Centigrade temperature change. ★ Gold electrodes applied by cathodic sputtering direct to the faces of the crystal, giving permanence of calibration. ★ Simple single valve circuit gives strong harmonics at 100 kcs. intervals up to 20 Mcs. ★ Octal based mount of compact dimensions. PRICE 45/- Post Free

Full details of the Q5/100 including circuit are contained in our leaflet Q1. Send stamp to-day for your copy.

**THE QUARTZ CRYSTAL Co., Ltd.**  
63-71 Kingston Road,  
NEW MALDEN, SURREY  
Telephone: MALden Q334

**BOOKS, INSTRUCTIONS, ETC.**  
"HOME Constructors' Handbook," the latest edition of this famous handbook containing circuits, radio constructional and servicing hints and complete catalogue, is now available at on y 1/-; mail order on y.  
SUFAGOILS, 93, Greenway Ave., London, E.17.

**WEBB'S 1948** radio map of world, new multi-colour printing, with up-to-date call signs and fresh information on heavy art paper 4/6. post. 6d. on linen on rollers 1/1/6. post. 9d.—Webb's Radio, 1-4, Soho St., W.1. Gerrard 2089.

"TELEVISION Superheterodyne Unit." A reprint of articles from "Wireless World" giving constructional details for a long-range receiver for reception of Alexandra Palace transmissions, with a map showing the service area of A.P. Size 9 1/2 in X 7 1/4 in. Price 2/6 net from all booksellers, by post from The Publishing Dept., Dorset House, Stamford St., S.E.1.

"TELEVISION Receiver Construction." Reprinted from articles in "Wireless World," this book contains a full description of constructional details, including special components, of a modern television receiver for the London area. Size 7 1/4 in wide X 9 1/4 in. 43pp. with 58 diagrams and illus. 2/6 net, from all Booksellers, or 2/9 by post from The Publishing Dept., Dorset House, S.E.1. [P4]

"WIRELESS Servicing Manual," 7th Edition. By W. T. Cocking, M.I.E.E. A reliable guide to which the professional can turn for reference. Essential testing apparatus and logical testing methods are described and the process of deducing and remedying defects explained. Size 7 1/4 X 4 1/4 in. 328pp. Price 10/6 net, from all booksellers, or 10/10 by post from The Publishing Dept., Dorset House, Stamford St., S.E.1. [P1]

"RADIO Circuits: Step-by-Step Survey of Superhet Receivers," 2nd Edition. By W. E. Miller, M.A. (Cantab.), M.Brit.I.R.E.; Editor of "The Wireless and Electrical Trader." Although this book deals mainly with the superhet receiver it is equally applicable to the straight set. The circuit of the superhet is dealt with section by section up to the complete receiver. Size 8 1/2 in X 5 1/4 in. 62pp. 3/6 net from all booksellers, or 3/9 from The Publishing Dept., Dorset House, Stamford St., S.E.1. [P3]

"BASIC Mathematics for Radio Students," 2nd Edition. By F. M. Colebrook, B.Sc. D.I.C., A.C.G.I. Presents the whole subject in an easily understandable and interesting form. The author deals first in a general manner with the fundamental mathematical processes that are the foundation of all applied science, and then discusses the application of mathematical ideas to radio problems. Size 7 1/4 X 4 1/4 in. 298pp. 77 diagrams. Price 10/6 net from all booksellers, or 10/10 by post from The Publishing Dept., Dorset House, Stamford St., S.E.1.

**ENGINEERS!**

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES". Full details of the easiest way to pass A.M.I. Mech. E., A.M.I.E.E., A.M.I.C.E., CITY & GUILDS, MATRIS, etc. on "NO PASS—NO FEE" terms and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. If you're earning less than £10 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE!

**B.I.E.T.**  
397, Shakespeare Hse., 17-18, Stratford Place, London, W.1.  
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

**YOU SHOULD HAVE A NEW TAYLOR**

\*\*\*\*\*

We can supply the latest Taylor Test-Equipment, and take your used Equipment in part exchange. Balance by cash or hire purchase.

Write, phone or send your gear along for inspection and offer.

\*\*\*\*\*

**UNIVERSITY RADIO LTD.**  
22 LISLE ST. Tel. GERRARD 4447 & 8682

**—WILCO ELECTRONICS—**

**RACKS P.O.** Standard 19in., with heavy angle iron base, 4ft. 9in. high, £3 each, lighter type, £2/10/-.

**POWER UNITS.** 19in. Rack Mounting, panel 19in. x 10 1/2 in., input 200-250 v., 50 cys., output 280-0-280 v. at 150 mA., 6.3 v. at 9A., 5 v. at 2A. Complete with choke, condensers, D.P. mains switch, indicator lamp, Bulgin connector, 5U4G Rect. and Cover, £3/17/6.

**TRANSMITTER POWER PACKS.** Input 200-240 v. A.C. 50 cys., Output 1.3 to 1.5 kV with separate heater trans for 2-U.15 Rects., 400 mA. Complete with smoothing relays, etc., in ventilated metal case less valves, £6. CO-AX CABLE. 60-70 ohm, 10yd. per yard.

**SPEAKERS P.M.** 8in. Tannoy with Trans., 21/- 4in. Rola less Trans., in case, 17/6.

**CONDENSERS.** Paper 8 m.f.d., 750 v. D.C. working, 10/6 each. 4 m.f.d. 750 v. D.C. working, 4/6 each.

**Vibrators.** Non Synch., 6 v. types, 5/6 each.

**INTERNATIONAL RADIO TUBE ENCYCLOPAEDIA,** 42/- each.

**204 LOWER ADDISCOMBE RD., GROYDON ADD. 2027**

**TRANSFORMERS & COILWINDERS**  
NEW AND REWINDS

All transformers interleaved & impregnated Tested for (1) Shorted turns. (2) Insulation at 2 K.V. minimum. E.H.T. A SPECIALITY. "E.E." MIDLAND SOUND & VISION COILS 1 1/2 SET. £W.O.

**J. E. THORNER & SONS**  
3 DEAN AVE · MANCHESTER 16  
C/O 3849 EST. 1925

**LOCKWOOD**  
makers of  
**Fine Cabinets**  
and woodwork of every description for the Radio and allied trades

**LOCKWOOD & COMPANY**  
Lowland's Road, Harrow, Middlesex. Byron 3704

**MUSIC LOVERS**

The famous LTC push-pull Quality Amplifier with variable negative feedback (ensuring flat response at all frequencies) is NOW available in kit form for the remarkable price of £10 7s. 6d. including ready punched chassis, ALL components, valves, output transformer, etc. Every kit is supplied with a copy of the Home Constructor's Handbook and UNIQUE Construction Sheets, which are designed to ensure that ANYONE can get the "tops in Quality" at the "bottom price".

**LONDON TELEVISION CO. LTD.**  
694 LEA BRIDGE ROAD,  
LEYTON, E.10.

## AMPLIFIERS Quality KIT for HOME CONSTRUCTORS

A complete set of components to construct a 10 watt amplifier including Woden potted mains transformer, 5 valves, 10 in. speaker with transformer. Components of the highest quality. No Govt. surplus. Three switched inputs, negative feed back, push-pull output, tone control, steel chassis. Suitable home or small hall.

*Price Complete to the last screw*

**CASH WITH ORDER £7 10 0**

**BEETHOVEN LTD**  
ELECTRIC EQUIPMENT  
Chapel Lane, Sands, High Wycombe Tel: 1152/3

## THE BEST TUNER UNITS for THE BEST AMPLIFIERS

Model SH6: Superhet, 3 waveband. 4 miniature valves. RF stages. Flywheel tuning.

**£12. 10. 0** plus £3.2.6 tax.

Model PB5: 4 station preset TRF. Pushbutton control. All miniature valves.

**£8. 15. 0** plus £1.18.6 tax.

Prices include multiway connectors.

## FELICITY GRAMOPHONE CO.

87a Upper Richmond Rd., London, S.W.15  
PUTney 1665

## "ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark.



Designed for Wireless Assembly and Maintenance.

Working temperature reached in 1½ mins., consumption 25 watts, weight 2½ ozs. Supplied in voltage ranges from 6/7v. to 230/250v ¼" diam. Copper Bit (standard model) 22/6.

½" diam. Copper Bit 25/-.

Replacement Unit Bit Elements available. British and Foreign patents

Sole Manufacturers:

**ADCOLA PRODUCTS LIMITED**  
Alliance House, Caxton Street, London, S.W.1  
Write or Phone: WHI. 0030.

## COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925

- 2 gang .0005 mfd. Condensers 6s. 6d.
- 2 " with trimmers " " 8s. 6d.
- 3 Wave-band Superhet Coil Packs..... 29s. 6d.
- 465 Kc. I.F. Transformers, Screened ..... pair 12s. 0d.

ALL COMPONENTS IN STOCK FOR THE VIEWMASTER TELEVISOR.

Send for latest Catalogue 6d. post paid.

**COVENTRY RADIO**  
DUNSTABLE RD., LUTON, BEDS.

★

## 'Radiospares' Quality Parts

The Service Engineer's First Choice



## YOUR METER DAMAGED ?



Leading Electrical Instrument Repairers to the Industry.

Repairs by skilled craftsmen to all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Test meters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to:



**L. GLASER**

SCIENTIFIC & ELECTRICAL INSTRUMENT REPAIRERS

341 CITY ROAD, E.C.1.

Tel. Terminus 2489

## RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

*We specialise in*

AMATEURS' WINDINGS, TRANSFORMERS ALL TYPES, CHOKES, PICK-UP COILS, INSTRUMENT COILS, Etc.

Highest workmanship

Good Delivery



### RADIOMENDERS, LTD.

Television & Radio Apparatus, Transformer & Coilwinders.

123-5-7 Parchmore Road,

THORNTON HEATH, SURREY

LIV 2261. Trade enquiries invited. Established 16 years.

ELECTRICAL & ELECTRONIC DEVELOPMENT LTD



PRESENTING... THE FAMOUS WILLIAMSON AMPLIFIER

Precision built by experts to instrument-standards. Special models available for conversion of existing equipment (as illustrated), and for recording and cinema work.

Full particulars of this and other productions on application.

HUBERT STREET, ASTON, BIRMINGHAM, 6  
Telephone: Aston Cross 2440

## KERSHAW'S KORNER KALLING SPECIAL!! SPECIAL!!!

BRAND NEW HOOVER MOTORS (Not Government Surplus)

Type S.P. 201 Shaded - Pole (Brushless) Fractional H.P. 200-250 volts, 50 cycles, A.C.— Speed 500 r.p.m. approx. With long ¼" shaft.

IDEAL AS GRAMOPHONE MOTORS — BUFFING MACHINES AND MIXERS, ETC.

STUPENDOUS VALUE **30/-** EACH POST PAID

**S. KERSHAW**  
93/95 PERSHORE STREET, BIRMINGHAM, 5

## THE IDEAL MICROPHONE FOR TELE-COMMUNICATION

MODEL **C 51**

MOVING-COIL MICROPHONE BY

Designed and developed essentially for G.P.O. hand-sets, with mobile tele-communication and P.A. work in view, LUSTRAPHONE Model C.51 is fast establishing itself wherever a good microphone is called for. It provides maximum intelligibility at extreme range and under adverse conditions, and is used extensively by Broadcast Engineers and others needing quality and dependability. Available as insert unit, or complete hand instrument. Data sheet on request.

**LUSTRAPHONE** LUSTRAPHONE LTD. 84, BELSIZE LANE, N.W.3.

# INDEX TO ADVERTISERS

	PAGE		PAGE		PAGE
Aaru Electric Tool Mfg. Co., Ltd.	50	Furzehill Laboratories, Ltd.	8	Fennine Amplifiers	68
Adcola Products, Ltd.	87			Pico, Ltd.	10
Aerialite, Ltd.	36	Galpins	71	Pitman, Sir Isaac, & Sons, Ltd.	63
Airtec Laboratories, Ltd.	65	Gardners Radio, Ltd.	50	Post Radio Supplies	78
Albert Mfg. Co.	74	Garland Radio	66	Pratts Radio	66
Allan, Richard, Radio, Ltd.	58	General Electric Co., Ltd.	66	Premier Radio Co.	4, 5
Allen Components, Ltd.	70	General Lamination Products, Ltd.	76	Quartz Crystal Co., Ltd.	86
Ambassador Radio	6	Glaser, L.	87	Radio Exchange Co.	56
Antiference, Ltd.	35	Goodmans, Industries, Ltd.	37	Radiomart Sound Service	78
Armstrong Wireless & Television Co., Ltd.	75	Goodsell, Ltd.	2	Maqomenders, Ltd.	87
Ashworth H.	77	Gray, A., Ltd.	36	Radio Servicing Co.	74
Atkins, H. C. Laboratories	60	Guild of Radio Service Engineers	18	Radiospares, Ltd.	87
Automatic Coil Winder & Electrical Equipmt. Co., Ltd.	1	Hallam, Sleigh & Cheston, Ltd.	24	Radio Unlimited	82
B. & H. Radio	78	Hartley, H. A., Co., Ltd.	68	Record Electrical Co., Ltd.	80
Barker, A. C.	77	Hatfield Instruments	76	Reliance Mfg. Co. (Southwark), Ltd.	64
Beethoven, Ltd.	32	Haynes Radio, Ltd.	84	Reproducers & Amplifiers, Ltd.	32
Belling & Lee, Ltd.	45	Hely-Mann Electronics Laboratories	81	R.H. Electronic Service	61
Berrys (Short Wave), Ltd.	84	Henry's W. T. Telegraph Works Co., Ltd.	62	Ring Lamp Co.	38
Bird, S. S., & Sons, Ltd.	36	Hill & Churchill, Ltd.	86	Ritherdon & Co., Ltd.	22
Birmingham Sound Reproducers, Ltd.	40	Hivac, Ltd.	34	Roding Laboratories	20
Boscombe Radio & Electric	32	Hogg, P. Livingston	52	Rogers Developments Co.	80
Brans, P. H., Ltd.	79	Holley's Radio Stores	84	Rollett, H., & Co., Ltd.	84
Brierley, J. H. (Gramophones & Recordings), Ltd.	34	Holt, Stan	20	Ruco Products	16
Britain, Chas. (Radio), Ltd.	55	Houghton & Osborne	20	Runbakken Electrical Products	82, 86
British Communications Corp'n. Ltd.	12	H. P. Radio Services, Ltd.	54	Salford Electrical Instruments, Ltd.	84
British Institute of Engineering Technology	72, 86	Hunt, A. H., Ltd.	65	Sangamo Weston, Ltd.	49
British Insulated Callender's Cables, Ltd.	Cover 11	Imhof, A., Ltd.	79	Sanvay Transformers, Ltd.	64
British National Radio School	80	Industrial Electronics	22	Scharf, Erwin	30
British Physical Laboratories	26	Inter Electron Industries	24	Simon Sound Service	19
British Role, Ltd.	60	International Correspondence School, Ltd.	14	Smith, G. W. (Radio), Ltd.	62
Brookes Crystals, Ltd.	80	Jackson Bros. (London), Ltd.	33	Solartan Laboratory Instruments, Ltd.	14
Brown, S. G., Ltd.	56	Johnsons (Radio)	86	Sound Sales, Ltd.	46
Bulgin, A. F., & Co., Ltd.	Edit. 39	Kershaw, S.	87	Southern Radio Supply, Ltd.	72
Bull, J., & Sons	81	Kidd, Robt., Whitaker & Pratt	84	Sower Transformers	78
Bullers, Ltd.	26	Lasky's Radio	54	Stability Radio Components, Ltd.	32
Cabot Radio Co., Ltd.	68	Lawrence, G., & Co.	58	Standard Telephones & Cables, Ltd.	43
Candler System Co.	78	Leak, H. J., & Co., Ltd.	51	Stearlite & Porcelain Products, Ltd.	15
Champion Products	70	Lewis Radio Co.	76	Stern Radio, Ltd.	23
Charles Amplifiers, Ltd.	85	Lockwood & Co.	86	Stewart Transformers, Ltd.	78
Chloride Electrical Storage Co., Ltd.	12	London Central Radio Stores	23	Sugden, A. R., & Co. (Engineers), Ltd.	10
C. J. R. Elec. and Electronic Development, Ltd.	87	London Radio Supply Co.	85	Supacolis	84
Cinema-Television, Ltd.	27	London Television Co., Ltd., The	86	Szymanski, S.	30
Clydesdale Supply Co., Ltd.	53	Lowther Mfg. Co.	70	T. & C. Radio College	82
Cohen, D.	84	Ludlow & Co.	87	Taylor Electrical Instruments, Ltd.	34, 65
Collaro, Ltd.	39	Lustraphone, Ltd.	80	Telegraph Condenser Co., Ltd.	Cover 111
Cosmocord, Ltd.	44	Lyons, Claude, Ltd.	76	Telegraph Construction & Maintenance Co., Ltd.	30
Cossor, A. C., Ltd.	13	Lyons Radio	84	Tele-Radio (1943), Ltd.	26
Coulphone Radio	85	Mall Order Supply Co.	64	Thermionic Products, Ltd.	3
Coventry Radio	87	Marconi Instruments, Ltd.	39	Thorner, J. E., & Sons	86
David Alec, Supplies, Ltd.	52	Marconi's Wireless Telegraph Co., Ltd.	16	Trix Electrical, Co., Ltd.	Edit. 37
Drayton Regulator & Instrument Co., Ltd.	52	McMurdo Instruments (Pullin), Ltd.	37	Truvox Engineering Co., Ltd.	7
Dublier Condenser Co. (1925), Ltd.	83	Measuring Instruments (Pullin), Ltd.	58	United Insulator Co., Ltd.	38
Duke & Co.	76	Metro Pex, Ltd.	8	Universal Bazaars, Ltd.	72
Duple Electronics, Ltd.	83	Metropolitan-Vickers Electrical Co., Ltd.	17	Universal Electrical Instruments Corp'n.	66
Edison Swan Electric Co., Ltd.	25	Midland Instrument Co.	62	University Radio, Ltd.	59, 86
Electradix Radios	69	Millett & Holden, Ltd.	80	Vallance & Davison, Ltd.	74
Electro Acoustic Developments	88	Modern Book Co.	74	Valradio	16
Electronic Instruments, Ltd.	48	Modern Electrics, Ltd.	78	Voigt Patents, Ltd.	85
Electronic Precision Equipment	57	M.R. Supplies, Ltd.	18	Vortexion, Ltd.	47
E.M.I. Institutes	48, 52	M.S.S. Recording Co., Ltd.	20	Wayne Kerr Labs., Ltd., The	31
Eta Tool Co. (Leicester), Ltd.	32	Mullard Electronic Products, Ltd.	21, 28, 42	Westinghouse Brake & Signal Co., Ltd.	35
Fanthorpe, A.	82	Multicore Solders, Ltd.	Cover 1v	West, Spencer	82
Federal Radio Co.	80	Mycalex, Ltd.	6	Weston Products (L'pool), Ltd.	66
Felicity Gramophone, Co.	87	Oliver Pell Control, Ltd.	14	Weymouth Radio Mfg. Co., Ltd., The	24
Ferranti, Ltd.	39	Osmor Radio Products, Ltd.	38	Wharfedale Wireless Works	35
Fielden (Electronics), Ltd.	32	Oxley Development Co., Ltd.	88	Whiteley Electrical Radio Co., Ltd.	48
Filmer, J.	82	Painton & Co., Ltd.	18, 61	Wilco Electronics	86
Fluxite, Ltd.	75	Park Radio	51	Wireless Instruments (Leeds), Ltd.	85
Frith Radiocraft, Ltd.	28	Parmerco, Ltd.	46	Wireless Supplies, Unlimited	70
		Partridge Transformers, Ltd.	67	Wisey Television, Ltd.	66
		Pearce, T. W.	68	Wright & Wearle, Ltd.	41
				Young, C. H.	60



**THE *Fidelia***  
LUXURY 3-VALVE  
RADIOGRAM CHASSIS

Features include variable selectivity, infinite impedance detector, electronic bass and treble controls, push-pull triode output stage: 3 wavebands 16-60, 190-550 and 1,000-2,000 metres. Audio amplifier response 30-18,000 cycles; bass, treble and volume controls operate on grammo, suitable for light weight p.u. Guaranteed 12 months. Price £21/5/-

Data Sheets on request, also for 'Fricton' 5-valve chassis, £12/17/8; 2R.F. feeder, 8 gns. 6 watt amp, £12/12


**ELECTRO Acoustic DEVELOPMENTS**

18 BROAD ROAD, WILLINGDON, SUSSEX.



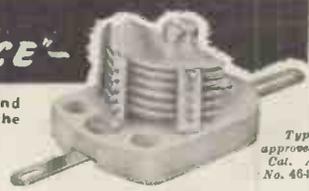**TECHNICAL EXCELLENCE**

—combines with beauty and soundness of DESIGN in the



**OXLEY**

AIR DIELECTRIC TRIMMER

Width: 16.5 mm. Length: 22 mm. Height: 1.5 to 6pF—7.5 mm. 1.5 to 20pF—10 mm. 2 to 26pF—11 mm. 2 to 32pF—12 mm. Lvs: Straight line capacity. Power Factor: Less than .001. Insulation: Over 2,000 megohms. Voltage: 500 D.C.

**OXLEY DEVELOPMENTS CO. LTD.**  
ULVERSTON, NORTH LANCs. TEL: ULVERSTON 3306

Type approved Cat. A No. 464.

Where voltages are **HIGH**

... choose  
**'VISCONOL'**  
 Cathodray  
 Condensers

**LOW POWER  
 FACTOR**

**COMPLETE  
 DIELECTRIC  
 STABILITY**

**RESISTANT TO  
 VOLTAGE SURGES**

**AMPLE RATING  
 AT HIGHER  
 TEMPERATURES**

**PROOF AGAINST  
 BREAKDOWN OR  
 FLASH OVER**



The 'Visconol' Process — exclusive to T.C.C. — means greater dependability and a longer useful life than ever before. It is the answer by T.C.C. research engineers to the insistent demand for condensers which will stand up to higher and still higher voltages. A selection from the range is given below: full details on request.



CAPACITY in Mfds.	MAX. WORKING VOLTS (at 60°C.)	DIMENSIONS IN INCHES		TYPE NUMBER	LIST PRICE each
		Overall Length	Overall Diameter		
.0005	25000	5 1/8	1 1/8	CP57H00	13/6
.001	6000	2 1/2	1 1/8	CP55Q0	4/6
.001	12500	3	1 1/8	CP56V0	7/6
.002	18000	5 1/8	1 1/8	CP57X0	13/6
.0025	3000	2 1/2	1 1/8	CP55H0	4/6
.005	6000	3	1 1/8	CP56Q0	7/6
.01	6000	3	1 1/8	CP56Q0	7/6
.05	6000	5 1/8	1 1/8	CP57Q0	13/6
.1	7000	6 1/2	2	CP58Q0	15/-
.25	1000	3	1 1/8	CP56V	7/6
.5	3000	6 1/2	2 1/8	CP59H0	23/-
1.0	750	5 1/8	1 1/8	CP57T	13/6

T.C.C. Condensers are exclusively specified in the View Master — the Television Set you build at home from standard parts. Constructor Envelope, (London Area), with 8 full-size assembly drawings and 32 page booklet, 5/- from all Wireless Shops. In case of difficulty, direct from us, post free 5/6.

**THE TELEGRAPH CONDENSER CO. LTD**

RADIO DIVISION: NORTH ACTON · LONDON · W.3. Telephone: ACORN 0061