
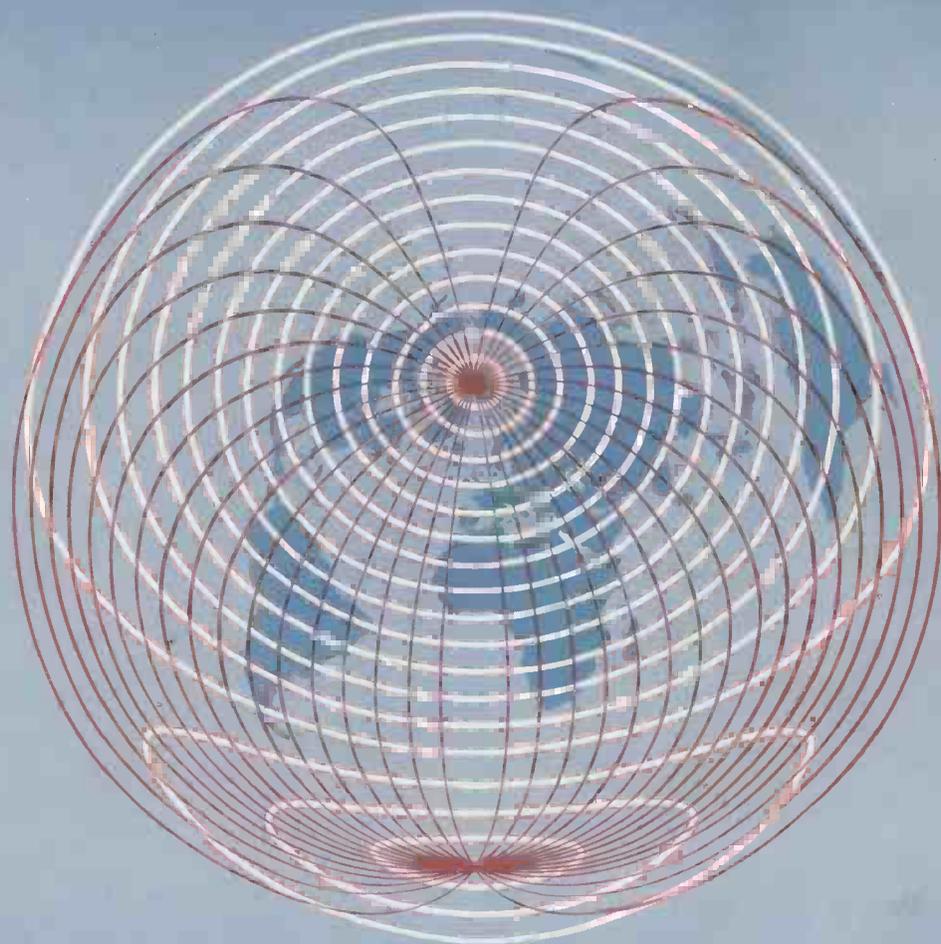


Wireless World

RADIO AND ELECTRONICS

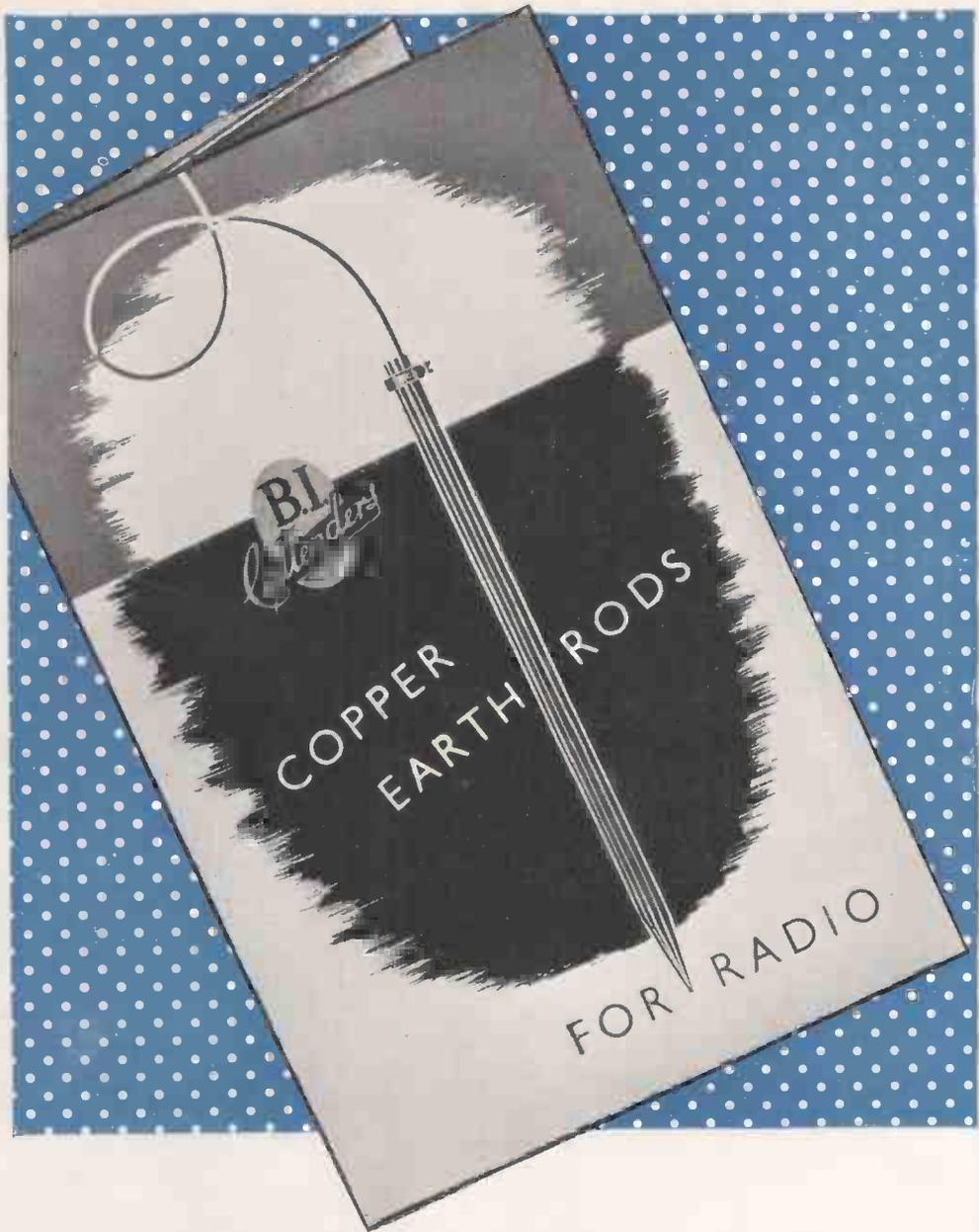

Vol LVI No 2 Two Shillings February 1950



Made from solid-drawn high-conductivity copper, BICC earthing rods are specially designed for use with radio and television receivers. Further information, including sizes and construction, is contained in this Publication (No. 243 T). Send for a copy to-day.

**BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2**

Wireless World

RADIO AND ELECTRONICS

February 1950

39th YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK M.I.E.E.

Editor: H. F. SMITH

PUBLISHED MONTHLY: Price 2/- (last Thursday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Ethaworld, Sedist, London."


ANNUAL SUBSCRIPTION: Home and Overseas, £1 6s. 0d.; U.S.A. and Canada, \$4.50.

BRANCH OFFICES:

Birmingham: King Edward House, New Street, 2.
 Coventry: 8-10, Corporation Street.
 Glasgow: 26B, Renfield Street, C.2.
 Manchester: 260, Deansgate, 3

In This Issue

EDITORIAL COMMENT	41
MIDLANDS TELEVISION STATION	42
NEW SUB-MINIATURE VALVES. By C. C. Gee	46
OUTPUT IMPEDANCE CONTROL. By Thomas Roddam	48
TEST REPORT: DENCO DCR19	50
IONOSPHERE REVIEW. By T. W. Bennington	53
SHORT-WAVE CONDITIONS	56
WORLD OF WIRELESS	57
FILTERS—2. By "Cathode Ray"	61
UNBIASED. By "Free Grid"	66
AIR-SEA RESCUE UP-TO-DATE. By Basil R. Clarke	67
MIDGET 3-VALVE A.C. MAINS RECEIVER. By S. W. Amos	68
NEW BOOKS	70
PREFERRED-VALUE ATTENUATORS. By E. W. Berth-Jones	71
MARINE COMMUNAL AERIALS	73
CONCENTRIC DUPLEX LOUDSPEAKER	74
LETTERS TO THE EDITOR	75
RANDOM RADIATIONS. By "Diallist"	78
MANUFACTURERS' PRODUCTS	80

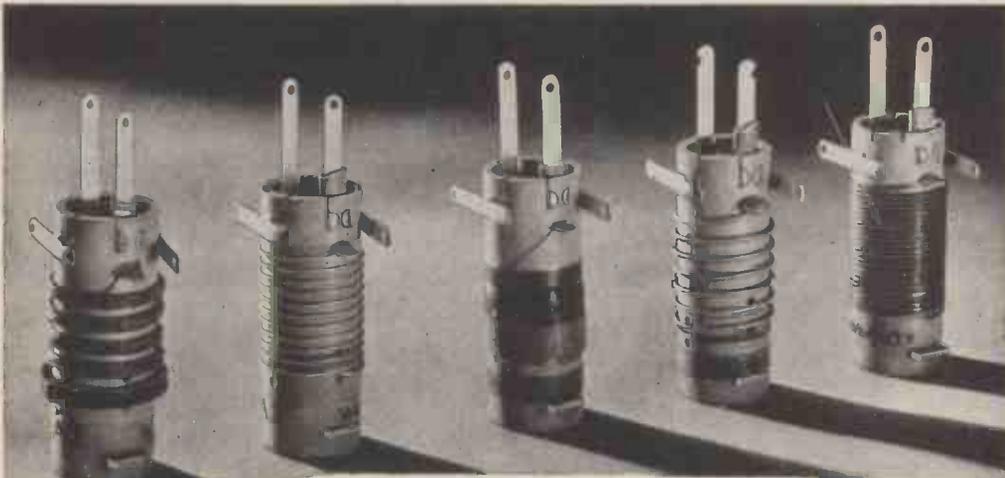


WEARITE COIL PACKS

"P" COILS

... for Aerial, R.F., and Oscillator Tuning and readily available in all ranges.

WRIGHT & WEAIRE LIMITED
 138 Sloane Street, London, S.W.1.

Telephone: SLOane 2214 5.
 Factory: South Shields, Co. Durham

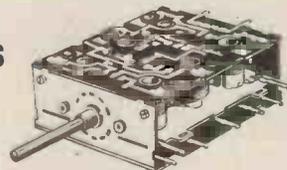


Send 6d. in stamps for the "Wearite" COILPACK Book of Technical Data and Circuits.



Valves and their applications

USE OF EF37A TO MEASURE HIGH RESISTANCE

The measurement of resistances of many millions of megohms generally involves the use of a special valve such as an electrometer triode. When the resistance to be measured is somewhat lower, say below one million megohms, a much simpler arrangement is possible and a conventional valve may be used provided its input impedance is sufficiently high. A suitable circuit for this purpose is shown below :

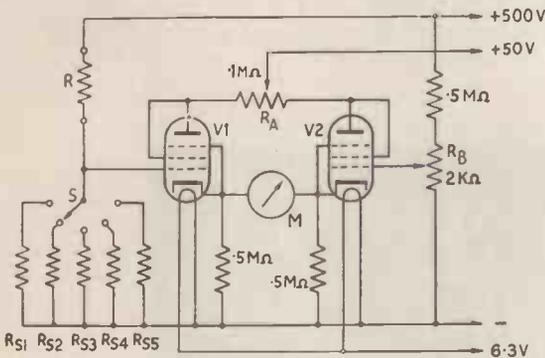

The circuit is essentially a bridge. The reference resistors R_{S1} , R_{S2} , R_{S3} . . . may for convenience be made equal to 1,000, 10,000, 100,000 . . . 10^9 ohms; they are selected by means of a high-grade switch S, preferably ceramic-insulated. Both valve grids are initially earthed by means of a further bank on switch S (not shown) and the potentiometer R_A is adjusted to give zero current in the microammeter M. Switch S is then set so that the grid-to-ground resistance R_S of V_1 is of the order of one-thousandth of the resistance R to be measured. By this means a voltage of between 0.15 and 1.5 volts is applied to the grid of V_1 and by setting R_B to the appropriate value a balance will again be obtained. If the potentiometer R_B is suitably calibrated it will then be possible to read off the value of R as the product of the reading of R_B and the value of R_S .

The simplicity of the arrangement will be apparent. Its usefulness is, however, restricted by the fact that for large values of R_S grid current flowing in V_1 may disturb the calibration. In order to minimise this effect it is convenient

to use a valve such as the EF37A whose grid-current is low and to select suitable operating conditions. Using EF37A's in the circuit shown, this grid-current is a negative current (electrons flowing from grid to cathode within the valve) and is made up of

- (1) ionisation current
- (2) grid emission
- (3) leakage currents

Ionisation current increases with anode current and also with the velocity of the electrons constituting the anode current, i.e. with anode voltage. It is therefore desirable for V_1 (and also V_2) to operate at low anode current and voltage. Grid emission results largely from the fact that the grid is warmed by the neighbouring cathode, and is dependent on cathode temperature, proximity of control grid, etc. Leakage currents may occur either inside or outside the glass envelope; from the standpoint of internal leakage it is again desirable to work at low voltages while insofar as external effects are concerned it is important to ensure that the surface of the glass is kept clean and dry.

The requirements outlined in the last paragraph are largely satisfied by the circuit shown. Furthermore, a special version of the type EF37A is available which operates at low heater voltage and, consequently, low cathode temperature. Using this valve under the above conditions the grid current is less than ten micro-microamps. This valve is known as type ME 1400.

A D.C. amplifier may be used between the bridge circuit and the meter. This gives increased accuracy and permits the use of a robust and inexpensive meter. With such a circuit measurements can be made up to one million megohms with somewhat lower accuracy.



Reprints of this report together with additional circuit notes are available, free of charge, from the address below.

MULLARD ELECTRONIC PRODUCTS LTD.,
TECHNICAL PUBLICATIONS DEPARTMENT,
CENTURY HOUSE, SHAFESBURY AVE., W.C2
 (MVM 119)

Wireless World

VOL. LVI. No. 2.

FEBRUARY, 1950

Growth of Television

THE new B.B.C. television transmitter at Sutton Coldfield may now fairly be hailed as a success, and everyone concerned with its design and construction is to be congratulated. The initial breakdowns may, it is fair to assume, be attributed largely to the initial difficulties that might reasonably be expected to arise from the high power of the transmitter—the highest power yet used for television and, indeed, exceptionally high power for any form of e.h.f. transmitter on comparable frequencies. Range has proved to be considerably greater than early official estimates would suggest and, over the densely populated area immediately surrounding the station, signal strength is so tremendous that good pictures are receivable on the simplest and cheapest installations. The method of feeding picture modulation to the transmitter by means of a radio link has proved entirely successful, and viewers in the Midlands are under no disadvantage as compared with those around London: there is certainly no detectable deterioration as a result of relaying.

On the broader issue, much encouragement can be taken from this first step in spreading television over the whole country. The basic standards chosen for our system, the method of distributing a single programme and the relatively austere nature of our projected national service all fit in well with the present economic position. Receivers for our medium-definition system can be manufactured at a price which brings them into the mass market—an essential for the growth of television—while the radio-frequency bandwidths required are of reasonable width, thus simplifying at least some of the problems of distribution.

There has been some dissatisfaction at the tardiness of putting into effect this first step in serving the provinces with television. Now that the ice has been broken, we hope development will proceed in a rapid and orderly manner—just as fast as sets for would-be viewers can be made and ancillary requirements—such as the training of technicians for installation and maintenance—can be met.

Vicissitudes of "Electronics"


A CONTROVERSY has arisen in the U.S.A. on the origin of the word "electronics" and also of its adjective, "electronic," and it is suggested there that the former word was used in England long before 1929, which is the critical date for the American discussion.

This is an argument to which we find it difficult to contribute anything helpful to the participants. There is no doubt that Johnstone Stoney in the last century coined the word "electron" to describe an elementary electrical particle; it seems safe enough to guess that "electronic" appeared soon afterwards as the adjectival form. It is rather less safe to guess, though it is possibly true, that at about the same time the word "electronics" was used to describe the science of electricity according to the electron theory.

But all this does not get us much further, as we cannot trace in this country any early use of the

word "electronics" in the restricted sense rather arbitrarily later ascribed to it somewhere. The official American definition nowadays is "that branch of science and technology which relates to the conduction of electricity through gases or *in vacuo*."

We are interested to see that the Americans confine their controversy to the origin of the word; happier than us, they seem to be in no doubt as to what it means. Here, we regret to observe, it tends to become rather meaningless, and, unless we are careful, will become just another catchword like "streamlined." Perhaps the most popular definition of "electronics" at the moment is "radio techniques as applied to non-communication uses," but there are plenty of others. Perhaps that is why wise practitioners in the art now tend to be shy of the word, restricting its use to contexts where they feel the meaning will be clear.

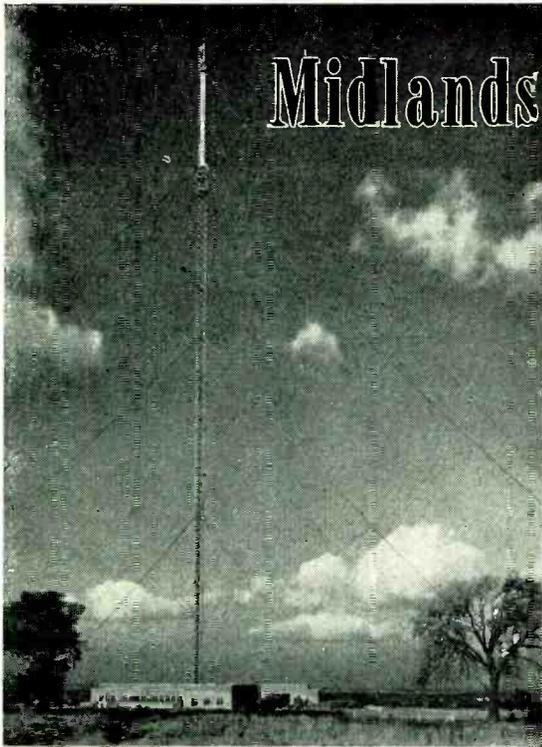

The 750-ft mast of the Sutton Coldfield station carries eight dipoles at the extreme top which radiate both sound and vision. The lower tubular section, between the dipoles and the lattice structure is a "slot" radiator intended for future v.h.f. broadcasting.

Midlands Television Station

Details of the New Transmitter

THE Sutton Coldfield television transmitter, which was officially opened on 17th December, has a peak power of 35 kW and is claimed to be the largest in the world. Situated about eight miles north of Birmingham the station is some 500 ft above sea level and is provided with a 750-ft mast to bring the aerial system 1,250 ft above sea level.

The mast is of triangular section with 9-ft sides for the first 610 ft. Above this it is circular for another 100 ft and this part contains a slot aerial system intended for future v.h.f. broadcasting. The television aerials are higher still and comprise eight folded dipoles arranged in two tiers of four each. All dipoles are common to both sound and vision channels.

A lift is provided in the mast up to 610-ft level. In order to permit angular movement in wind the mast rests on a steel ball and is supported by four sets of stays. It was designed and constructed by British Insulated Callender's Construction Co., and the topmast and aerials were made by Marconi's W. T. Company.


The separate transmitters for sound and vision together with their ancillary equipment are contained in a single-storey building. The sound transmitter, by Marconi's W.T. Company, is of 12-kW average carrier power output at 58.25 Mc/s with class B anode modulation of the output stage. The drive unit is followed by three push-pull amplifier stages. The final stage is a single BR128 valve in an earthed-grid coaxial-type circuit, the output being fed through a concentric feeder to the aerials. Air cooling is used for the valves.

The vision transmitter provides up to 35 kW peak power with a carrier frequency of 61.75 Mc/s. It was constructed jointly by E.M.I. and Metropolitan-Vickers, the latter firm being the sub-contractors for the major part of the radio-frequency equipment. On the r.f. side the transmitter starts with an r.f. drive unit, supplied by Marconi's W.T. Company, similar to that used for the sound channel; it contains a crystal oscillator and two stages of frequency multiplication. This is followed by a three-stage low-power amplifier beginning with a single-valve pentode followed by a push-pull tetrode stage and ending with a pair of triodes in push-pull in the earthed-grid connection.

The driver stage, following this, has two ACT26 triodes operating as a class C neutralized push-pull amplifier. The final stage uses CAT21 triodes in an earthed-grid circuit with parallel-line circuit elements and it feeds the output coaxial-line feeder. This stage is grid modulated



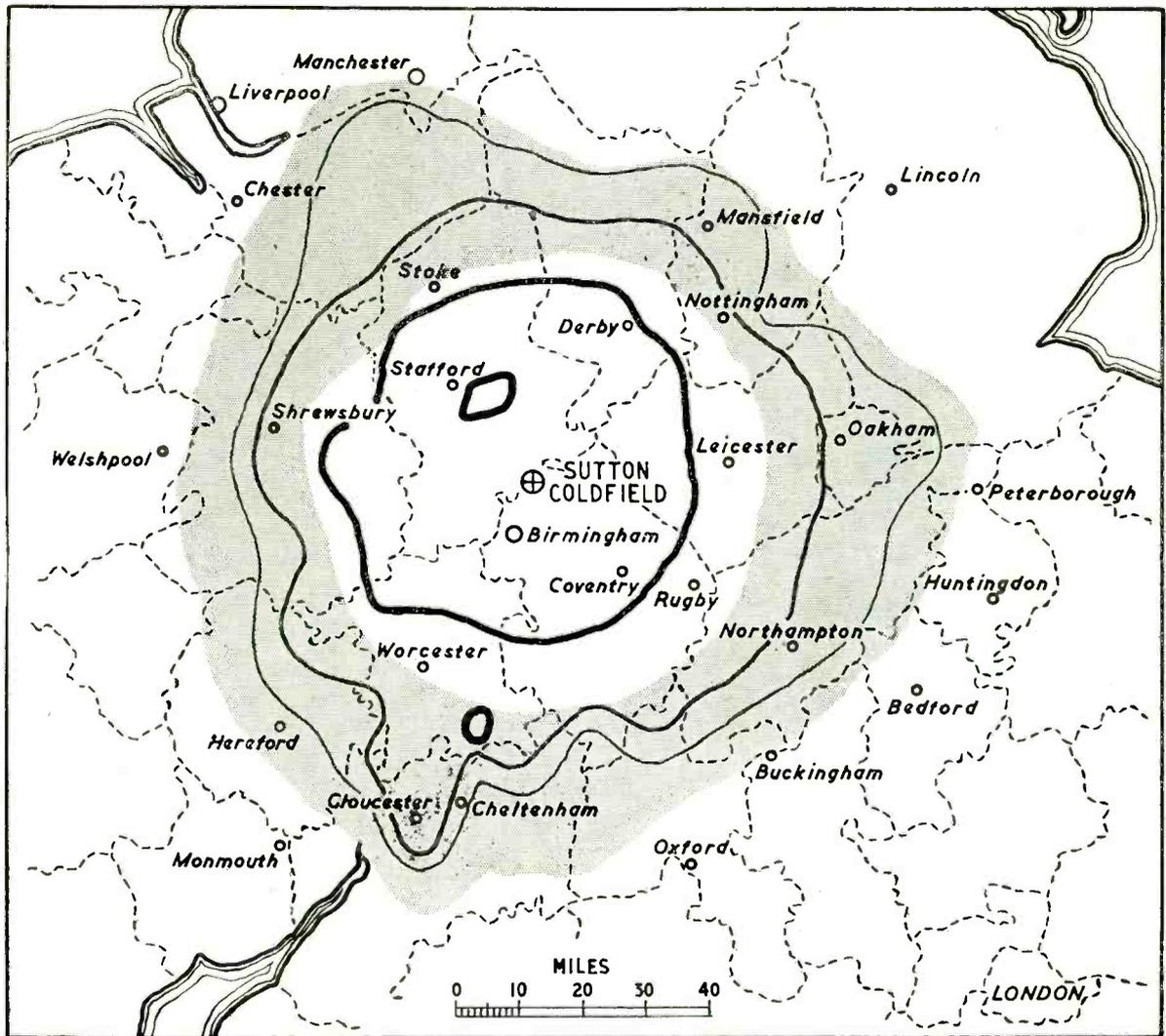This photograph shows the r.f. side of the vision transmitter with the waveform monitor in the foreground. The power supply is in a room immediately behind the transmitter.



This map of the service area of the Sutton Coldfield transmitter is based on calculation and indicates the strength of signal to be expected on theoretical grounds. The heavy contours are for field strengths of 5 mV/m, the medium 500 μ V/m, and the light 100 μ V/m; the figures are for peak-white transmission and a receiving aerial 30 ft above ground. In the shaded zone satisfactory reception will be subject to favourable local conditions and some fading may be experienced at times; beyond the shaded zone consistent reception cannot be expected. The service area which will actually be obtained cannot be known until the station has been in operation for some months, but the preliminary reports during the first weeks indicate that it is likely to be much greater than this map depicts.

by the vision signal. This final stage is water cooled, but the others are all air cooled.


The vision signal enters the station through a cable link by which it is conveyed from the terminal station (in Birmingham) of the London-Birmingham radio link. The signal has an amplitude of about 1 V and is applied to a pre-amplifier which is arranged to have an adjustable curvature of its input/output characteristic. This amplifier also enables the relative amplitudes of the picture signal and the sync pulses to be controlled.

Further amplifiers are designated the sub-sub-modulator and the sub-modulator, a black-level clamp being provided between the two. The modulator is a cathode follower using four valves in parallel. It gives no voltage amplification, but has a

sufficient power output at very low impedance to supply the 3.5-A grid current of the final r.f. stage as well as the large capacitive current which it demands. ACM₃ valves are used throughout the modulators and are air-cooled.

The transmitter output is taken through a coaxial line to the vestigial-sideband filter. It is of the constant-resistance type and includes a high-pass and a low-pass section constructed of coaxial line. The output of the l.p. section is taken through a coaxial line to the aerial, this line forming the termination of the filter. The high-pass section, however, is terminated by a water load in which the power of the unwanted sidebands is absorbed.

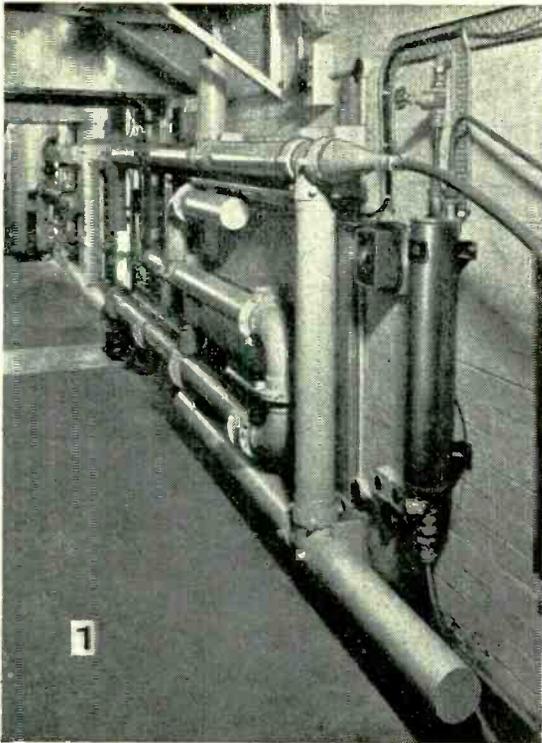The filter transmits the lower-frequency sidebands to the aerial but increasingly attenuates the upper



(1) The vertical-sideband filter is of the constant-resistance type with high- and low-pass sections. It is constructed of coaxial lines and the power from the unwanted sidebands is absorbed in a "water load."

sidebands for vision frequencies above 0.75 Mc/s. At 63.25 Mc/s, the sound channel of an adjacent future television station, the attenuation is 12 db.

The r.f. outputs from the two transmitters are taken up the mast in separate coaxial feeders. They are of 5-in outside diameter and 51- Ω impedance. They are made in 12-ft sections and expansion joints are fitted every 150 ft to allow for temperature changes. Dry air is blown continuously through them to prevent condensation. In order to facilitate adjustment and testing, the vision transmitter output can be switched to a water load in which the power is then dissipated and measured.


Towards the top of the mast the feeders terminate in a diplexer. This is a device which combines the sound and vision signals and at the same time prevents power from one feeder from being fed down the other. It is the equivalent of the hybrid transformer so widely used in a.f. lines technique.

The combined signals in the output of the diplexer are taken through feeders to a pair of unbalance-to-balance transformers and thence by two pairs of coaxial feeders to the aerials. One pair feeds the north-south dipoles in each tier and the other the east-west dipoles.

The Aerials

Phase shifts are introduced into the dipole feeds and in the opposite sense for the sound and vision signals. Clockwise from north the vision signal in both tiers is phased 0°, 90°, 180°, 270°, while the sound is phased 0°, 270°, 180°, 90°. The aerial gain in a horizontal plane is 4 db. The dipoles themselves are made from 10-in galvanized steel strip; 7.5-kW heaters are fitted to prevent ice formation.

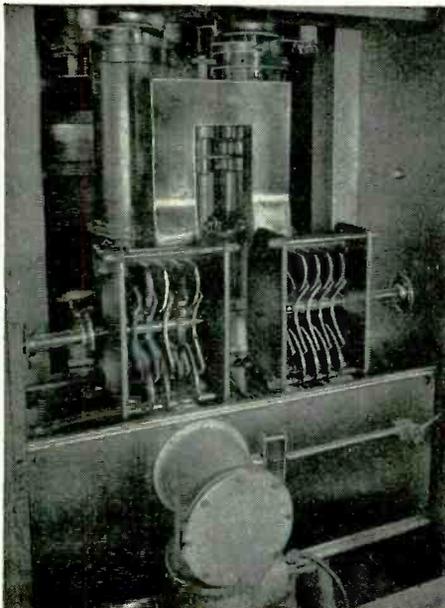(2) The photo on the left shows the interior of the final stage of the vision transmitter. The vertical tubes form the anode tuning inductances and are mounted below the CAT21 valves. The output circuit tuning capacitors are visible in the front above the output feeder. The photo on the right shows the control desk for the sound and vision transmitters; it includes a c.r. wave-form monitor tube. Picture-monitor tubes are provided and the control room has windows looking into the transmitter hall.



The transmitting equipment is rack-mounted and the racks are assembled in line against one wall of the transmitter hall. On the other side of this wall the power-supply apparatus is fitted, the connections passing through the wall and being consequently quite short. Hot-cathode mercury-vapour rectifiers are used for the vision transmitter and the supply at 415-V 3-phase is stabilized and phase-balanced by three moving-coil voltage regulators. The smoothing circuit for the final stage is built out to a low constant resistance and the high-voltage anode supplies for the other stages have valve stabilizers.

Voltage Control

A.C. heating is used for the valve filaments except in the modulated stage, where a d.c. supply from a motor generator is used. An electronic regulator is employed to keep the voltage within 0.1 per cent of its nominal value. The power is derived from the grid system at 11 kV and transformed to the 415-V used in the building. An emergency lighting system at 240 V from batteries is provided.

The equipment for cooling is located between the two power-supply rooms for the sound and vision transmitters. The heated air can be switched into the main building for space heating in winter.


Looking into the transmitter hall is the control room in which a control desk enables one man to operate both transmitters. In addition to meters, a c.r. tube is provided as a waveform monitor and there are picture monitor tubes to show both the incoming signal and the radiated signal. A diagram with 200 miniature lamps provides a tell-tale; the lamps light in turn as the supplies to each stage are established.

The station contains no studio since it is intended to be fed normally by a picture originating in London. When local programmes are required the standard outside-broadcast equipment is to be used. A film-scanner is provided, however, and its purpose is mainly to provide a source of programme in the event of a breakdown in the link to London.

ITALIAN TELEVISION TESTS


WE learn from our Italian contemporary *Elettronica and Televisione* that tests have recently been concluded in Italy with both French and American television equipment preparatory to starting a service. The transmitters were erected by the Italian broadcasting authority on a 700-metre hill in the vicinity of Turin and receivers were installed in public buildings in a number of towns.

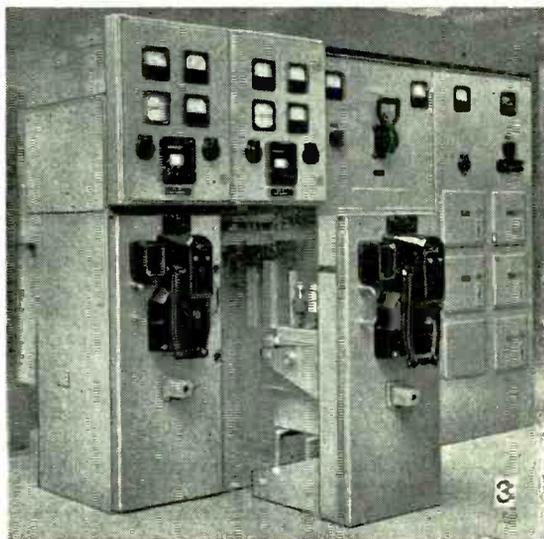The American equipment, which operated on 83.25 Mc/s (vision) and 87.75 Mc/s (sound), was built to U.S. standards—with negative modulation and the lower sideband suppressed—except that the scanning rate was 625 lines with 25 frames instead of 525 with 30 frames. Sound was frequency modulated. The French transmitter employed the new 819-line standards of the projected French system.



(3) Power switchgear for the transmitters supplied by Brush Electrical Engineering.

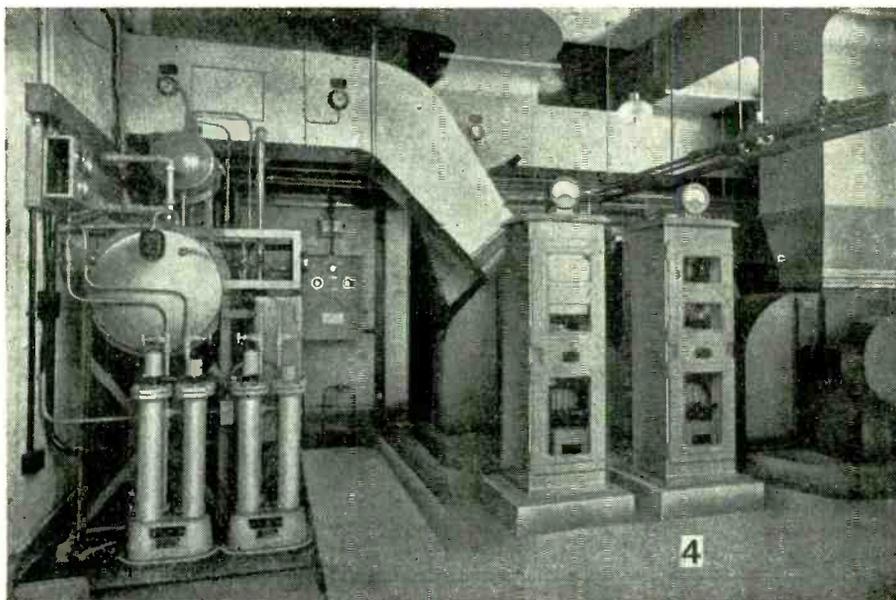(4) The cooling plant is shown in this photo. On the left is part of the water-cooling equipment for the final stage of the vision transmitter. The other valves are air-cooled and the heated air can be utilized, if required, for heating the building.



New Sub-miniature Valves

"Flat" Types with Filaments Drawing Only 15mA

By C. C. GEE (Mullard Electronic Products)

IN the March, 1948, issue of *Wireless World* an account was given of a series of 10-mm sub-miniature valves which were specially developed by Mullard for use in the National Health Hearing Aid, "Medresco." These valves, which had 25-mA filaments, compared favourably in performance with corresponding valves of American manufacture, and fully met the requirements of the specification laid down by the Post Office Research Station. However, from the very onset of the development of these valves there was a pressing demand for still smaller types, of flat construction, having even lower filament currents.


The new series of flat sub-miniatures, represented by the Mullard voltage-amplifying pentode DF66, and the output pentode DL66, meet this demand, and mark a notable advance in valves specifically designed for hearing aids. As a result of this development, it will be possible to reduce still further the size and weight of these instruments, and at the same time extend the life of the batteries. It is claimed that the new valves will not only satisfy the requirements of manufacturers of hearing aids in this country, but will also be able to compete on very favourable terms with American types in the world market.

Some idea of the rapid progress that has been made in the development of hearing aid valves during the past thirteen years may be gathered from Table I. From the table it will be seen that the volume of the new voltage-amplifying sub-miniature DF66 is

TABLE I

	DA1 Voltage-amplifying triode	DC51 Voltage-amplifying triode	DF70 Voltage-amplifying triode	DF66 Voltage-amplifying triode
Year introduced ...	1936	1939	1947	1949
Overall length (mm) (in)	60 2.36	62 2.44	29.5 1.16	27 1.06
Overall dia. or (mm) cross-section (in)	19 0.74	17 0.66	10 0.39	8.3 × 6.1 0.32 × 0.24
Volume ... (mm ³) (in ³)	17,000 1.04	14,100 0.87	2,320 0.141	1,400 0.085
Cross-sectional area. (mm ²) (in ²)	280 0.43	225 0.34	78 0.12	52 0.08
Filament current (mA) ...	50	67	25	15

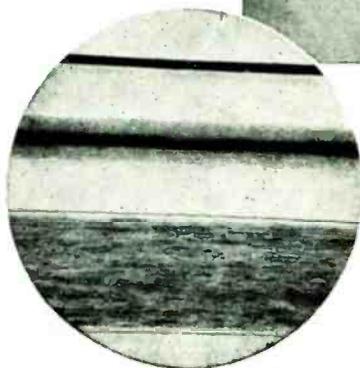The Mullard type DF66 valve fitted into a standard sub-miniature holder.




Uncoated and coated filament of the Mullard DF66 flat sub-miniature valves compared with a human hair.

less than one-twelfth that of the Mullard DA1, introduced in 1936; moreover, the filament current has been reduced from 50mA to 15mA. Comparing the DF66 with its equivalent 10-mm type, DF70, it will also be noted that not only has the volume been reduced but, as a result of the flat type of construction, there has been a marked reduction in the cross-sectional area. The importance of this in the design of extremely compact hearing aids may be judged from the fact that the total cross-sectional area enclosed by three of the new valves is only 156 sq mm (0.24 sq in) as against 234 sq mm (0.36 sq in) for three of the 10-mm type sub-miniatures. This results in approximately a two-thirds saving in space. Three of the latest flat-type American valves similarly placed enclose a cross-sectional area of 213 sq mm (0.33 sq in). This means that the space saved by using the new British valves in place of equivalent American types amounts to over a quarter.

Filament Diameter

The low filament current of the new valves has been obtained through the use of highly emissive, oxide-coated filaments, having a tungsten core of no more than 7.8 microns (3/10,000th in) diameter. The remarkable precision of the tungsten wire and the uniformity of the oxide coating is apparent from the photograph, which shows the coated and uncoated filaments scaled against a human hair. From this it is estimated that the tungsten wire is less than

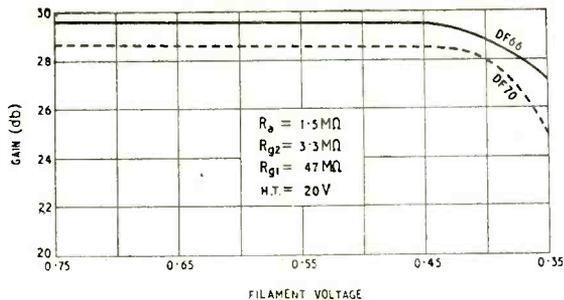

Typical curves showing gain in relation to filament voltage for the DF70 and DF66 type valves.

1/10th as thick as the hair, whilst the coated filament is less than 1/3rd as thick.

In spite of the extreme fineness of the filament wire, it has been found possible to produce the filaments on a mass-production basis on conventional filament-making machines. During all stages of manufacture, every precaution is taken to ensure the highest possible standards of purity and surface smoothness of the wire. Extreme care is also taken in the coating of the wire, in order to ensure stable emission.

Sealing Technique

The special sealing technique employed in the production of these valves is such that the heat is directed away from the electrode assembly during the sealing process. In this way the problem of electrode poisoning and distortion is largely overcome. It is this sealing technique which makes possible the use of extremely fine filaments. Since in this method the envelopes are sealed directly to the glass bases, it has also been possible to reduce the length of the valves.

Another important feature is freedom from microphony. This has been achieved by reducing the length of the electrode system and improving the methods of springing. As a result of this the fundamental frequency of the filament of the DF66 has been raised to about 6,000 c/s. This is far above the upper frequency limit of 4,000 c/s specified for most hearing aids at present in use.

The lead-out wires in these valves may be either soldered directly to the circuit components, or may be cut back to about 1/4 in, and fitted into standard sub-miniature sockets as shown in the photograph.

It would normally be expected that the reduction in filament current from 25 mA to 15 mA, which has been achieved in these new valves, would result in a considerable reduction in the gain. This, however, has been offset by a marked improvement in the design of the grids. By using fine wire and by taking extreme care in the symmetry of the electrode assembly, it has, in fact, been possible to improve the gain of the DF66 voltage amplifier by one or two db compared with the 10-mm type DF70. Moreover, as shown by the gain curves, the fall of the gain with decreases in the filament voltage is not quite so rapid in the DF66. This means that even when the voltage of the l.t. battery is reduced from its normal 1.25 V to 0.8 V the response of the hearing aid circuit can be maintained at a reasonably high level.

On account of their small size and low filament current, these new valves should prove of particular value in the design of hearing aids in which both the l.t. and h.t. batteries are housed in the case of the instrument. It is estimated that instruments of this kind having a nominal output of about 2.5 mW should meet the requirements of over 70 per cent of those suffering from defective hearing. Using two DF66 voltage-amplifying pentodes in series, feeding into a single DL66 output pentode, it should be possible to produce hearing aids weighing less than 5 ounces. These could be easily concealed about the person of the wearer, so as to be almost undetectable. By using l.t. cells of the mercury type, it is probable that such instruments would give over 50 hours of useful service before it is necessary to replace the l.t. battery. A similar instrument embodying one of the ordinary leclanché-type cells should give over 12 hours of continuous use.

With the introduction of these new flat sub-miniatures it appears that the reduction in size of valves of this class has almost reached its limit. Future developments will possibly be in the direction of even lower filament currents and higher gains. As a result of these improvements it should be possible to extend still further the life of hearing aid batteries, or, conversely, reduce their size for a given life period. It will be realized that this is the most practical way of designing smaller lightweight hearing aids when it is considered that, in such instruments, it is the batteries which account for a large percentage of the size and weight.

It is interesting to note that, parallel with this development, Mullard are bringing out a complete range of both battery and mains 10-mm sub-miniatures for use in miniature communication equipments, and other compact, lightweight electronic units.

TABLE II

Principal Characteristics Compared

	10-mm Sub-miniatures		Flat Sub-miniatures	
	DF70 Voltage-amplifying pentode	DL71 Output pentode	DF66 Voltage-amplifying pentode	DL66 Output pentode
V_f (V)	0.625	1.25	0.625	1.25
I_f (mA)	25	25	15	15
V_a (V)	30	45	22.5	22.5
V_{g2} (V)	30	45	22.5	22.5
V_{g1} (V)	0	-1.25	-1.05	-1.4
I_a (mA)	0.375	0.6	0.05	0.3
I_{g2} (mA)	0.125	0.15	0.015	0.075
g_m mA/V	0.22	0.55	0.1	0.35
$P_{out}(10\% \text{ distortion})$ (mW)	—	6	—	2.5

Output Impedance Control

Variable Loudspeaker Damping Without Alteration of Output Level

By THOMAS RODDAM

WHENEVER the Editor feels rather lonely in his eyrie overlooking the South Bank, and wants readers to write to him, he publishes an article on the loudspeaker damping problem. As the best "damping factor" depends on the loudspeaker design, letters pour in, and he feels that it must be Christmas again. Although no one seems to have used this simile, the choice of a damping factor is very much like the adjustment of a swing door: with too little damping the door swings to and fro several times after it is released; with too much damping it shuts very slowly, leaving a most unfriendly draught blowing for some seconds after each person comes in. The loudspeaker cone behaves in the same way: too little damping and it oscillates on its own whenever it receives a shock; too much, and transients are lost completely. At this point the usual thing is to jump in and quote a magic figure for damping factor, which will solve all problems. I don't propose to do this, because I'm pretty certain that all types of loudspeaker require different answers. Some, I suggest, are like galvanometers I have encountered, and need negative resistance to provide critical damping.

The obvious thing to do is to change the damping factor until it sounds right. There are rather more complicated ways of checking the damping factor, but if you can't hear the difference, why worry; your friends won't be impressed. In this article I shall show how an amplifier can be constructed with a variable output impedance, with the rather important feature that as you vary the impedance the output stays the same. You can alter the impedance with a signal on and listen to the effect, without any disturbing level changes or distortion: the distortion actually varies slightly, but it is low enough to be disregarded anyway. The impedance can be brought right down to zero, or even made negative, but of course if the negative output impedance is bigger than the load the amplifier becomes an oscillator:

this effect is easily detected by the pragmatic test: you can hear it!

I shall assume that the reader has a file of back numbers of *Wireless World* and that before he goes any further he will read "Cathode Ray's" article in the February 1946 issue. In this, the effect of negative feedback on the output impedance of the amplifier is explained. Summarizing, negative voltage feedback reduces the output impedance, while negative current feedback increases it. By applying the reasoning which leads to these results it is easy to show that positive current feedback will reduce the output impedance. We therefore have two ways of reducing the impedance, one of which, negative feedback, is very commonly used. Within certain limits we could use only negative feedback, but the disadvantage for our present purpose is that as we alter the feedback we alter the overall gain of the amplifier. This does no harm if we are adjusting the circuit once for all, but if we are studying the way different damping factors sound, it is not desirable to have to adjust the level each time we change the impedance. In addition, we are restricted in the range over which the impedance can be adjusted.

Writing A for the voltage amplification without negative feedback, and B for the fraction of the output voltage fed back, the gain of the amplifier is $A/(1 + AB)$ with feedback. So long as A is large we can take $(1 + AB) \approx AB$, and the gain as just $1/B$. This is a good approximation in most practical cases: for example, in a two-stage amplifier we may have $A = 1,000$ and $B = 1/100$, giving $AB = 10$. The voltage amplification is then exactly 90.1 , or approximately 100 , a difference of only 0.9 db. If A increases to $4,000$, the gain increases to 97.7 times, or by 0.7 db. Thus by using enough feedback to reduce the gain 20 db we keep the gain constant within $\pm \frac{1}{2}$ db however we increase A .

We can make use of this by applying negative


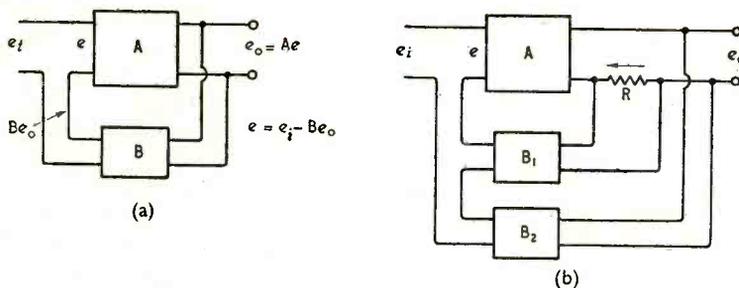


Fig. 1. (a) Normal connections in a negative voltage feedback amplifier. (b) Mixed voltage and current feedback. Fig. 2. (right) Basic positive feedback circuit.

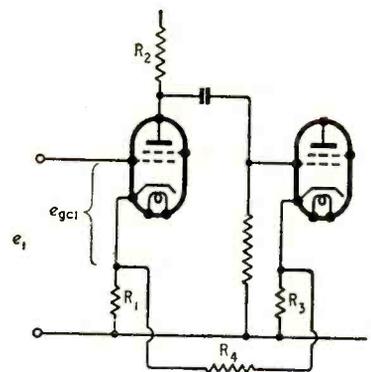

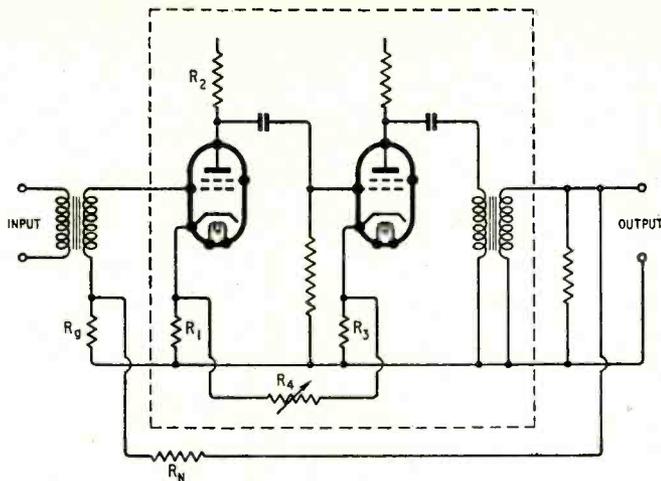


Fig. 3. Combined feedback circuit of amplifier with variable output impedance. R_4 is the control; suitable values are suggested in the text.

feedback round the whole amplifier, and at the same time putting positive current feedback round an inner loop. Fig. 1 shows a normal negative voltage feedback amplifier and an amplifier having two feedback paths, B_1 for current feedback and B_2 for voltage feedback. For this amplifier the input voltage e will be $e_i + B_1 i R - B_2 e_o$, where B_1 is the positive current feedback path and B_2 the negative voltage feedback path. I shall not develop the equations, because this particular arrangement is easily seen to be inconvenient as soon as earths are to be applied to the circuit. Instead, let us consider the circuits of Fig. 2.

Design Relationships

In this two-stage pentode amplifier, the first valve has a mutual conductance g_1 , and the second g_2 . The current in the anode load of the first valve will be $g_1 e_{gc1}$, producing a voltage at the grid of the second valve equal to $-g_1 e_{gc1} R_2$. For this valve, we have

$$e_{gc2} = -g_1 e_{gc1} R_2 - g_2 e_{gc2} R_3 \text{ giving}$$

$$e_{gc2} = -\frac{g_1 e_{gc1} R_2}{1 + g_2 R_3}$$

Across the cathode load R_3 we have a voltage $g_2 e_{gc2} R_3$, of which a fraction $R_1/(R_1 + R_4)$ appears across the cathode resistance of the first valve, so long as R_4 is much larger than R_2 . The input voltage e_1 required to produce the grid-cathode voltage e_{gc1} is therefore

$$e_1 = e_{gc1} + e_{gc1} g_1 R_1 - \frac{R_1}{R_1 + R_4} \cdot \frac{g_1 e_{gc1} R_2}{1 + g_2 R_3}$$

We can have a finite value of e_{gc1} for $e_1 = 0$ by making

$$1 + g_1 R_1 = \frac{R_1}{R_1 + R_4} \cdot \frac{g_1 R_2}{1 + g_2 R_3}$$

This means that we have infinite gain, which is the condition for zero impedance to appear at the anode of V_2 . To simplify this expression, let us take $g_1 = g_2$, $R_1 = R_3$ and $g_1 R_1 = g_2 R_3 = 1$, with $g_1 R_2 = 100$.

Then

$$\frac{R_4}{R_1} + 1 = \frac{1}{2} \cdot \frac{100}{2} = 25$$

or $R_4 = 24 R_1$

Now let us look at Fig. 3. If this is compared with the top diagram in Fig. 1 it will be seen that the circuit inside the dotted box is simply an amplifier A, and the B circuit is now R_g and R_N , with a value of $B = R_g/(R_g + R_N)$ or $\approx R_g/R_N$. As we saw, we can increase the gain A inside the box as much as we like without affecting the overall gain, which stays very close to $R_N/R_g = 1/B$. (The gain due to the input transformer is neglected at the moment). We are therefore free to alter R_4 , which alters the output impedance, without altering the overall level, unless, of course, we make the circuit unstable. If we fix a minimum value of R_4 at about 20 times R_1 we can

persuade the output impedance to go just negative, and by increasing R_4 we can produce a range of output impedances up to a maximum of $[\gamma_a/(1 + AB)] \sqrt{n}$ where γ_a is the anode impedance of the valve and n is the output transformer ratio.

At this point I feel a certain diffidence. My landlord occupies the flat above me, and the temptation to build one of those nice 100-watt audio amplifiers has always been sternly repressed. In fact, as I write the loudspeaker is operating at a pleasant 50 mW. My work on this variable-impedance amplifier has been based on a 1-watt output level, using a single-sided amplifier. The valves used were a 6J7 and a 6L6, because the foreign customer to whom the equipment is to be sold refuses to be committed to valves from one particular maker. He hasn't any dollars, but by using American types he can get a much wider choice of suppliers than if he has valves on the British Spring 1949 base which will go out of fashion sooner than did the New Look. With these valves, R_2 in Fig. 3 was 33 k Ω , R_1 620 Ω , R_3 220 Ω , and R_4 a 100-k Ω variable resistor. No trouble was experienced due to small bias changes caused by the d.c. which flows through R_4 . With this circuit an output impedance of less than one-tenth of the load impedance was easily obtained.


There is another use for this circuit. If you like having the same programme in all the rooms in your house, if you have a house and can't make one speaker heard all through it, this low impedance amplifier is very useful. By feeding a line from a very low-impedance amplifier, additional loudspeakers can be added without altering the level at those already connected. Obviously the amplifier must have sufficient power available to drive the maximum number of loudspeakers, but if this is so the amplifier adjusts itself to deliver constant voltage irrespective of the load.

Examination of the Williamson amplifier circuit (Aug. 1949 issue) suggests that it should be possible to apply positive feedback from V_5 to V_3 and from V_6 to V_4 . This involves splitting R_{10} into two 780-ohm resistors, and R_{22} into two 300-ohm resistors. Equal amounts of feedback must be provided, but readers who have constructed this amplifier may find the experiment of interest.

TEST REPORT

Denco Model DCR19

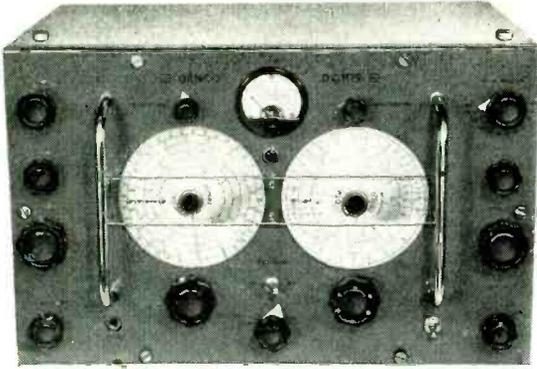Communications Receiver Embodying a Coil Turret and Crystal Calibrator



General view of the DCR19 receiver showing layout of the front panel. The left-hand scale is for bandspread, the right-hand one carries the six main scales.

ONE of the distinctive features of the Denco DCR19 communications receiver is the use of a rotary coil turret which removes all the idle coils from the circuit and short circuits any that might act as absorbers for those in use. The turret is particularly well made and all coils are wound on polystyrene formers and have air-spaced trimmers.

Embodied in the coil unit is a mechanical bandspread tuning system which enables a small part of any of the six wavebands to be expanded for ease of tuning, it also enables very accurate measurement of the received stations' frequency to be made. For this purpose a 500-kc/s crystal calibrating oscillator is used.

The six wavebands provided by this receiver have respective coverages of the following frequencies:—

- 175 to 525 kc/s
- 515 to 1,545 kc/s
- 1.65 to 5.0 Mc/s
- 4.8 to 9.6 Mc/s
- 9.4 to 18.8 Mc/s
- 18.0 to 36.0 Mc/s

The parts selected for bandspreading are the five amateur wavebands as follows:—

- 3.5 to 3.8 Mc/s
- 7.0 to 7.4 Mc/s
- 14.0 to 14.8 Mc/s
- 21.0 to 21.8 Mc/s
- 28.0 to 29.8 Mc/s


Inclusion of the 21-Mc/s band is in anticipation of its release as it is not yet allotted for amateur use in this country. These bandspread selections would indicate that the receiver is largely intended for the amateur market both here and overseas. The inclusion

of a power outlet socket at the back of the set for operating a converter, presumably of the v.h.f. variety, also lends weight to this assumption. In any case, it is a useful feature as it gives access to a 6-volt a.c. supply and to the h.t. on-off switch connections so that a relay could be fitted externally to the set and operated from a remote point if needed.

An examination of the specification reveals that the unusually high intermediate frequency of 1.6 Mc/s is used. This choice undoubtedly assists image signal rejection and enables one r.f. stage to suffice for all bands. For this an EF91 valve is used, and in view of the high efficiency of the wave-change system and of the coils quite a high gain is given by this single stage.


High intermediate frequencies have their disadvantages as well as advantages, but the only one of any consequence is the need to employ a few more tuned circuits in order to obtain adequate adjacent channel selectivity. In the DCR19 there are eight circuits distributed between three i.f. amplifying stages using 9D6 valves. Together they give a maximum bandwidth of 8 kc/s.

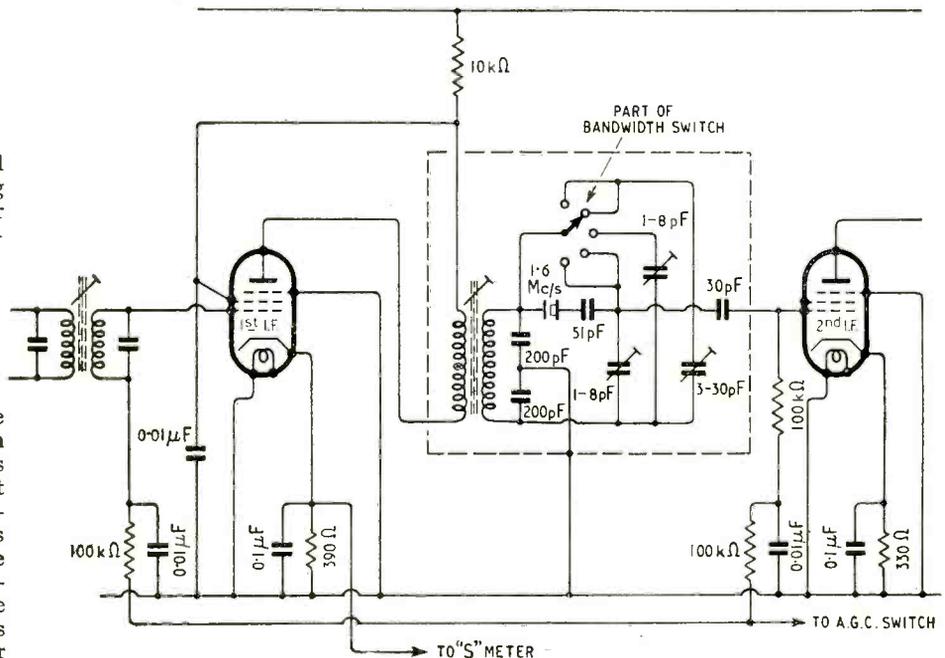There are, all told, five different bandwidths available; the 8-kc/s one already mentioned, 8 kc/s plus



Circuit details of the inter-stage coupling following the first i.f. valve showing crystal filter and part of the bandwidth switching which includes also switches for the audio filter and i.f. gain.

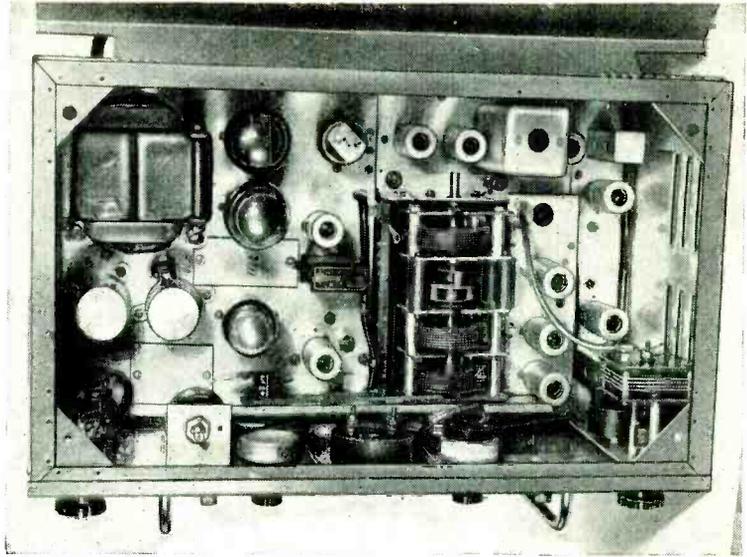This view of the inside of the receiver shows the gang capacitors, the crystal calibrator in the centre and the aerial matching capacitor on the right.




an audio filter, 1.5 kc/s, 0.5 kc/s and 0.5 kc/s plus an audio filter. A quartz crystal gate is used for the last three and the audio filter mentioned, which is used mainly for c.w. reception, has a mid-point frequency of 950 c/s and, with the crystal, gives an effective bandwidth of about 100 c/s.


Although the frequency changer is an EHC35 triode-hexode valve it has a separate oscillator (EF91), but this combination is not uncommon in communications receivers.

It is followed by the three i.f. stages already mentioned, then by an EB91 double diode combining the functions of second detector and a.g.c. with another EB91 for the noise limiter. There is also a beat oscillator (EF91) for c.w. reception, the 500-kc/s crystal calibrator (EF91), a penultimate a.f. amplifier, and finally a pentode output stage giving about 4 watts of audio for an external 3-ohm

loudspeaker. Provision is made for headphones. The crystal calibrator is not exclusively a refinement, but it plays a large part in the bandspread system. Without it there would be some uncertainty in setting the main tuning dial to the exact beginning of the band-spread portion. With it all uncertainty is removed and the frequency calibrations of the band-spread dial then have a real meaning. Opinions may differ regarding the value of an "S" meter, but no communications set appears to be without one. They can be of considerable help if the receiver's gain is kept reasonably constant, not only over the individual ranges but over the waveband as a whole. In the DCR19 a serious effort has been made to achieve this by adjusting the gain of the i.f. amplifiers when switching from one bandwidth to another and in the r.f. amplifier by suitable design of the interstage couplings. From the frequency changer to the second detector the gain of the set is controlled normally by a.g.c. voltages

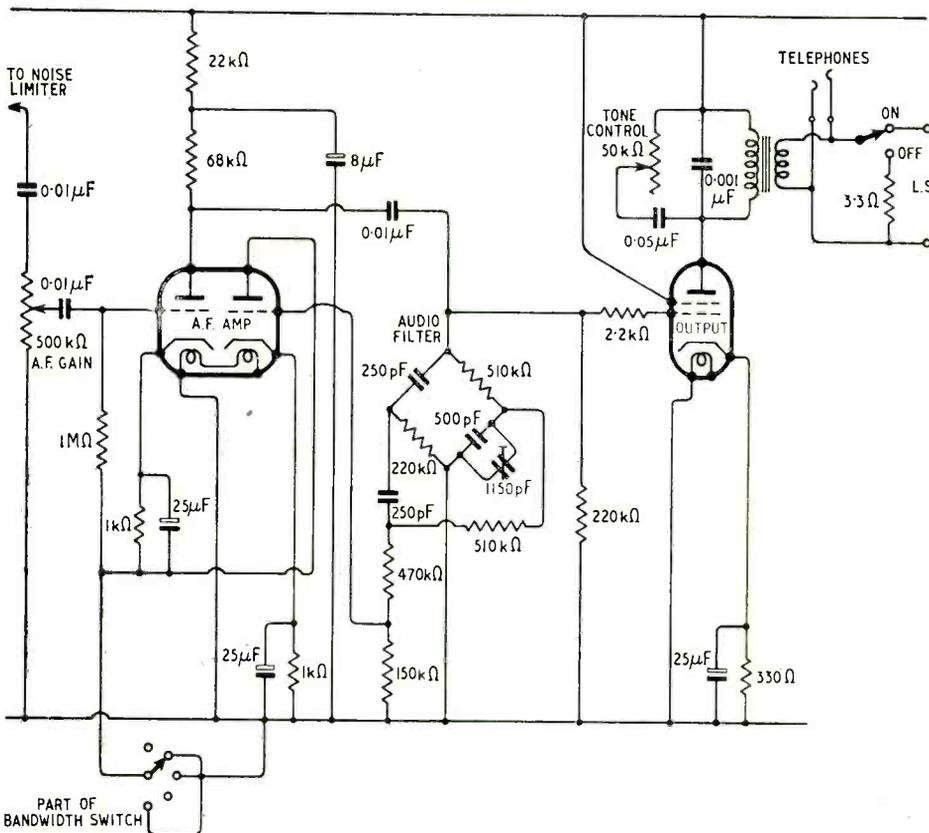

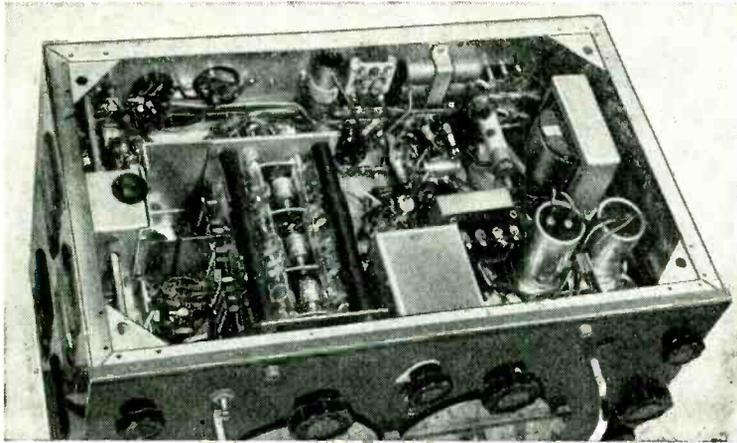Incorporated in the first audio amplifier is a negative feedback circuit which behaves as an audio filter. The negative feedback becomes operative only when the bandwidth switch brings the audio filter into use. A dummy load is incorporated for use with telephones.



Removing the bottom plate of the cabinet reveals the coil turret, boxed-in b.f.o. (in centre) and gives access to all the under-deck wiring.

developed by the signal. The r.f. stage is not controlled in this way, but there is a manual gain control having a limited effect, as this valve is not one of the variable- μ kind. This control must be set to maximum gain position for the "S" meter readings to have any meaning.

Manual control of the i.f. gain is provided as an alternative to, but not in conjunction with, a.g.c., and this is effected by applying a variable negative bias, derived from a resistor joined between h.t. negative and chassis, to the first two i.f. stages. A potentiometer is connected across this resistor. All stages have cathode resistors for providing minimum bias.

The receiver is a.c. mains operated and incorporates a power transformer, valve rectifier and all smoothing circuits, a VR150/30 voltage stabilizer giving a perfectly steady d.c. voltage for the local oscillator, mixer screen, beat oscillator and for "bucking" the "S" meter.

Though not difficult to operate, this Denco set calls for a few hours of handling fully to appreciate its merits. Sensitivity is high, which is not surprising with three i.f. amplifiers, and it is well maintained throughout the entire waveband. Exceptionally good results were obtained on the highest frequency range in daylight.

The lack of a bandwidth intermediate between 1.5 and 8 kc/s was occasionally felt as the first is rather narrow for telephony while the second is rather broad for some parts of the short-wave ranges, when a 3.5 kc/s bandwidth is generally the most useful. This does not mean to say that speech is by any means unintelligible with a 1.5 kc/s bandwidth; it is not, but the receiver must be very accurately tuned, and this is where the "S" meter comes in very useful. Slight mistuning under these conditions can produce quite noticeable distortion and, with very strong signals, to overloading of the i.f. stages which normally depend solely upon a.g.c. to control the gain. Of course, it is always possible to turn to manual control, but the a.g.c. behaves so well on telephony (and m.c.w.) and c.w. telegraphy that one is reluctant to dispense with its aid.

For c.w. reception the time constant of the a.g.c. system can be lengthened considerably by switching to the "c.w." position, and under these conditions there is no rise in sensitivity (and in background) during the brief intervals between morse characters.

When the proper procedure is followed the band-

spread calibration becomes surprisingly accurate. On the 80-metre amateur (3.5 Mc/s) band it is easily possible to read a station's frequency to within 2 kc/s on the dial, and as the calibration of each of these ranges is checked initially against the 500-kc/s crystal oscillator, a very high order of accuracy is possible. On the 10-metre (28 Mc/s) band the reading accuracy is to within about 5 kc/s.

Checks of the calibration made throughout the waveband, and using the 500-kc/s oscillator, showed that the frequencies marked on the scale are, in the main, to be relied on. In a few cases small discrepancies were noticed but in the majority of cases they amounted to little more than the thickness of the line on the cursor.

Six coloured spots are marked on the cursor for range identification, and they tally with like coloured spots on the waveband change knob which operates the coil turret.

No other indication of range, or position, appears on the turret control so that in a poor light, or if the operator is a little uncertain of his colours (the blue and the green were not very distinct on our receiver), confusion might arise. Figures or letters to supplement the coloured spots would be desirable.

To sum up, the DCR19 possesses about as much sensitivity as can be used in any ordinary location. Some experience is necessary before the best can be extracted from it, but this qualification is not exclusive to radio sets. In the main, the set gives an extremely good account of itself and performs the functions one expects of a communications receiver. Some emphasis has been laid on the qualities for amateur use, and in view of its general form and price it should have a wide appeal in this sphere.

The receiver is housed in a well-ventilated metal cabinet with a hinged lid that folds right back and the finish is grey enamel.

The overall size of the set is $16\frac{1}{2} \times 10\frac{1}{2} \times 11\frac{1}{2}$ in, the weight 30 lb and the price £49. The makers are Denco (Clacton), Ltd., Old Road, Clacton-on-Sea, Essex.

Scaled Valve Containers

A NEW method of packing electronic valves for dispatch overseas has been introduced by the General Electric Company. Cylindrical flanged containers are formed by impact extrusion from an aluminium slug and fitted with lids which are hermetically sealed by the cold pressure welding process recently evolved by the G.E.C. Research Laboratories.

"K.F." Record Changer

We are asked to state that the "K.F." automatic record changer described on page 34 of the January issue is made by Kingsbury Fitch and Company, Sidcup, Kent. Brooks and Bohm are one of the main distributors of this product.

Ionosphere Review: 1949

Sunspot Cycle and Short-wave Propagation Survey, with Forecast for 1950

By T. W. BENNINGTON (Engineering Division, B.B.C.)

ALL doubts as to the time of occurrence of maximum activity in the present sunspot cycle were set at rest with the publication from Zurich, about the middle of 1949, of the final sunspot numbers for 1948. These showed that during no month of 1948 did the mean level of the sunspot number reach so high a value as that which was recorded for May, 1947, and, furthermore, that the twelve-month average value for the sunspot number was also at its peak about that time, namely, at the epoch May/June, 1947. We may therefore assume that that was the epoch of maximum activity in the present cycle.

Since the maximum some rather peculiar variations in sunspot activity have taken place; peculiar, however, only when viewed in relation to the relatively smooth variations which occurred during several years prior to 1947. In short, sunspot activity has not, since the maximum, decreased in anything like a smooth manner, but has undergone some large and erratic up-and-down variations. The activity during 1949 was, on the average, only very slightly lower than that during 1948, a fact which may seem somewhat surprising with the maximum so long past. However, smooth variations—even in the twelve-month running average values—cannot legitimately be expected with confidence, for, if the sunspot cycles of the past 200 years are examined, it is seen that similar up-and-down variations to those which are now taking place are really quite a common occurrence.

Wireless World has, at the end of the past several years, published a review of sunspot and ionospheric conditions, in order to indicate how the conditions for short-wave propagation have varied, and how they may vary in the immediate future. The present review, therefore, will deal with these points as revealed by past measurements of sunspot activity and of ionospheric critical frequency, with particular reference to the changes which occurred during 1949, and to those which may occur during 1950.

Course of the Sunspot Cycle.—In order to show the general course of the present sunspot cycle and the degree of sunspot activity prevailing at present the curve of Fig. 1 is given. In this are plotted the mean annual values of the sunspot relative numbers for a period covering the whole of the last and present sunspot cycles. The maximum in the present cycle is seen to have been considerably higher than that in the last—which was itself a relatively high one—and was, in fact, one of the highest maxima on record since 1749, when continuous records of the sunspot numbers first began. Since 1947—the year of maximum activity—the sunspot activity has decreased only slightly and, during 1949, was very little lower than during the preceding year. Thus the smooth cyclic variations of the preceding years were somewhat upset during 1949. The main point

to note is that the decrease since the maximum has been very slow, so that at the end of 1949 we find ourselves experiencing considerably higher sunspot activity than would have been expected on the basis of the past years' relatively smooth variations.

It will be noted also that, since the sunspot activity is still considerably higher at the end of 1949 than it was at the last sunspot maximum, quasi-maximum conditions still prevail. As will be later shown, ionospheric and short-wave conditions since the maximum have followed the sunspot activity very closely, so that the above remark applies to these as well as to the sunspot numbers. The ionospheric critical frequencies in northern latitudes were, in fact, somewhat higher in the autumn of 1949 than in that of 1948 and only slightly lower than those for the maximum year of 1947. The frequencies usable for short-wave communication are still very high.

Ionospheric Variations.—The top (full line) curve in Fig. 2 gives the monthly mean values of the sunspot relative numbers for each month during the present sunspot cycle, while the two bottom (dashed) curves give the monthly means of the F_2 -layer critical frequencies for noon and midnight respectively. The latter data are those obtained at the Slough station of the D.S.I.R.

Despite erratic month-by-month variations sunspot activity showed a generally increasing tendency from the minimum of 1944 to the maximum in May, 1947. Since that time the variations have often been of greater amplitude, and after decreasing considerably for several months the sunspot number has then several times returned to a value almost as great as that of the maximum. So far as 1949 is concerned it cannot be said that any decided tendency to decrease has become apparent.

The critical frequency curves, which have large seasonal variations in them, both show a gradual

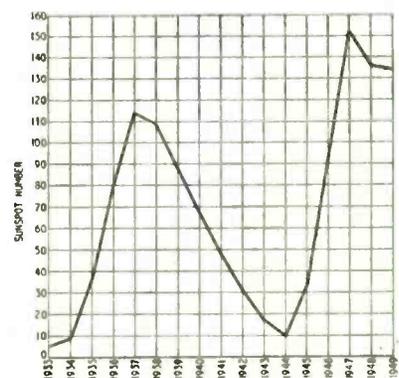


Fig. 1. Mean annual values of sunspot relative numbers.

upward sweep towards the maximum, but since then only a slight tendency to decrease. As has been said the noon value for November, 1949, was greater than that for the same month of the previous year, indicating that higher daytime working frequencies could have been used for short-wave communication. Short-wave working frequencies during this, the third winter season after the maximum, were still of the very high order generally associated with the sunspot maximum itself.

The seasonal variations in the critical frequency curves are very interesting in themselves. So far as the noon values are concerned it is seen that the lowest occur in summer and the highest towards the winter, and that there is a far greater difference between summer and winter values when the sunspot activity is high than when it is low. This means that the magnitude of the critical frequency increase due to the effects of the solar cycle is far greater in winter than in summer.

It is very interesting to note the small subsidiary decrease in critical frequency which occurs in the noon curves at the extreme mid-winter period, resulting in the peak seasonal values occurring at about November and February. It will be observed that this decrease has occurred during every winter of the present cycle, though during the 1947/48 winter alone there was no subsequent recovery after the decrease, resulting in the curve for that winter being a single-peaked one, whereas all the others are double-peaked. It will be noted that during January and February, 1948, there was a sharp decrease in the sunspot number, and there can be little doubt that this lowered solar activity, which occurred at a time when the critical frequency usually increases, was the responsible factor.


Such an occurrence as this well illustrates the difficulties with which forecasters of ionospheric conditions have to contend when making predictions for short-wave propagation some months ahead.

The midnight critical frequency curves show (as is always the case) seasonal variations of a character opposite to those for noon, the highest values occurring in mid-summer and the lowest in mid-winter. It is due to the earlier onset of darkness in winter than in summer, during which ionization by the sun ceases and only recombination takes place.

Correlation between Sunspot and Ionospheric Measurements.—In Fig. 3 are given (full line curve) the twelve-month running average values of the sunspot number during the present cycle, and (dashed line curves) the twelve-month running averages of the noon and midnight F_2 -layer critical frequencies over the same period, taken from the measurements made at Slough. By taking twelve-month running averages of these quantities the month-by-month variations in the sunspot number and the seasonal variations in the critical frequencies are smoothed out, so that the long-period effects in both quantities are made more apparent. The twelve-month average for the epoch at the centre of any month is the average of the twelve monthly means having that month as the centre.

These curves show that both noon and midnight critical frequencies responded to the changing sunspot activity very faithfully, though towards the maximum the sunspot number appeared to increase more rapidly than the critical frequency. Generally speaking, the correlation between the curves—sunspot and critical frequency—is very good, and it may be mentioned that the same good agreement between the sunspot curve and those for critical fre-

Fig. 2. Relationship between solar activity changes and propagation conditions: monthly mean values of sunspot numbers and of noon and midnight F_2 -layer critical frequencies during the present sunspot cycle.

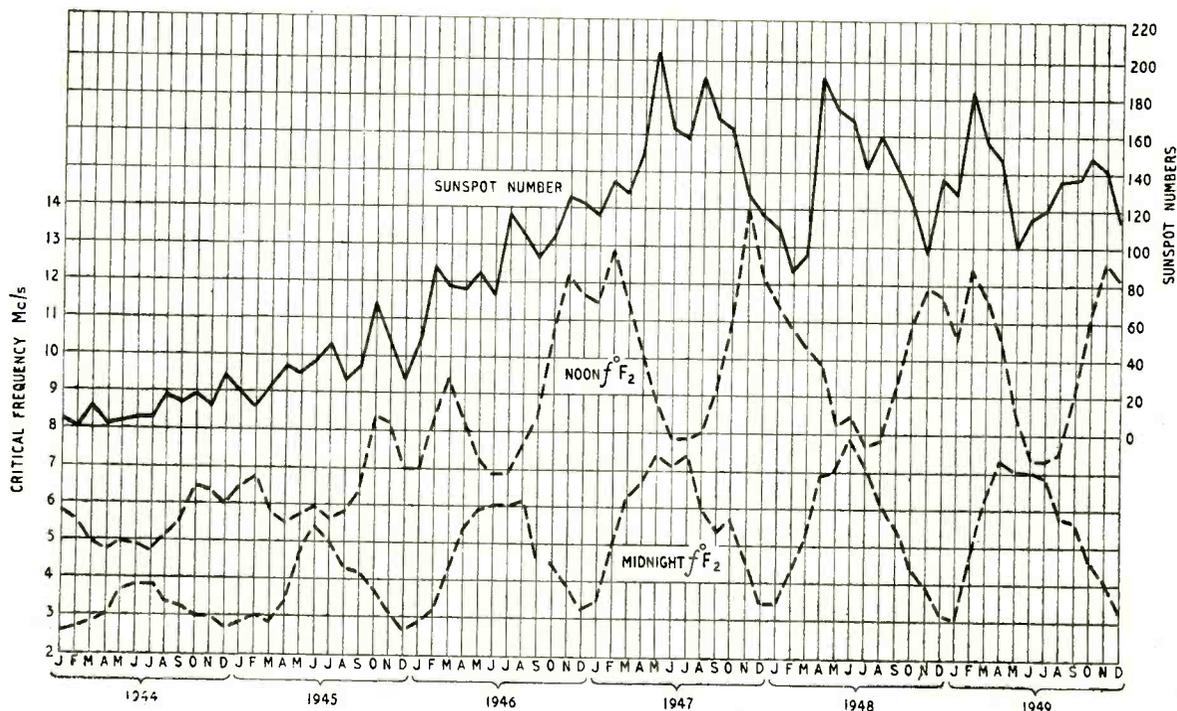

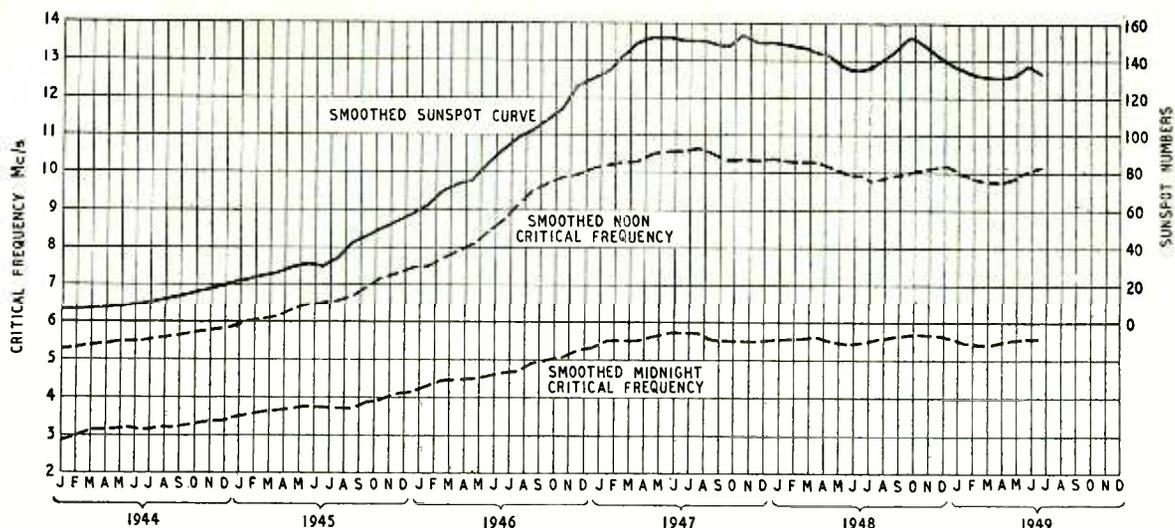


Fig. 3. Twelve-month running averages of sunspot numbers and of noon and midnight F-layer critical frequencies.

quency can be had for other times of day, and for other ionospheric layers, though the magnitude of the variation is different for different times of day, and for different layers. All this shows that the critical frequencies, and thus the m.u.f.s, for short-wave communication, are, at least to a first approximation, directly proportional to the sunspot number.

Having noted that the maximum in the sunspot curve occurred at the epoch May/June, 1947, we become particularly interested in what has happened to both curves since that time, and more particularly during the last 12 months. It will be noted that in a twelve-month running average curve it is only possible to plot up to an epoch six months back from the date of the latest data available. The smoothed sunspot curve—indicating the general degree of solar activity—is seen to have undergone but a slight measure of decline since the maximum, and there has been one very considerable increase to nearly maxima values. Each trough and peak in the sunspot curve is seen to be reflected in those for the noon and midnight critical frequencies, though the latter show these effects somewhat later. For example, the maximum in both critical frequency curves appears to have occurred one month later than that in the sunspot curve, while the trough of May/June, 1948, and the peak of September/October, 1948, are followed by similar troughs and peaks in both critical frequency curves about two months later. All this, when one considers the rather arbitrary nature of the sunspot number, is rather remarkable.

The year 1949 can be regarded as one of particularly good short-wave conditions, for the following reasons. When the ionization of the F₂-layer is exceptionally high, as it was during 1949, the high limiting frequency for short-wave communication is at its greatest value. Under the same conditions of high sunspot activity the ionization of the D-layer—the principal absorbing region—is also raised, but only to a moderate extent as compared with that of the F₂-layer. The absorption determines the low limiting frequency, and as this is not unduly increased, it means that the band of useful frequencies is exceptionally wide. Such wide band conditions

will not prevail when sunspot activity becomes appreciably lower and the restriction of useful bandwidth will become particularly acute at night.

Practical Results.—That the highest frequencies actually propagated during 1949 were of the same order as during 1948 is confirmed by the records of reception conditions in this country during 1949. The critical frequency curves of Fig. 2 imply that, in the ionosphere immediately above Slough the mean m.u.f. for February was of the order of 41 Mc/s, that in June it had fallen to about 24 Mc/s, and in November had risen again to the order of 42 Mc/s, a value slightly greater than that of November, 1948. Of course, the m.u.f. is much modified by conditions over the whole transmission path, which generally tend to reduce it from the value prevailing at either end, on the other hand it frequently is higher than the mean value for a particular month. Nevertheless, these figures give some idea of the order of things to be expected.

The records show that during January, February and March, American police and other signals were frequently received in this country on frequencies of 36 to 42 Mc/s, whilst the London television service on 45 and 41.5 Mc/s was received in South Africa on many occasions. In March there were also one or two reports of amateur reception on 50 Mc/s in this country from South Africa. In late April the amateur frequency of 28 Mc/s began to show signs of failing in certain directions, in May this effect became accentuated, whilst in June and July it was very seldom usable. In April the London television station was received in South Africa frequently, in May on a few occasions only, and in June and July not at all. By September 28 Mc/s was becoming much more frequently usable in many directions from this country, while by October it was in regular use over most circuits. During September television was received in South Africa on seven days, whilst in October such reception again became frequent. In November and December American police and f.m. signals on frequencies up to 43 Mc/s were again received here frequently, and television was almost regularly received in South Africa.

These results exemplify the high order of fre-

quencies the ionosphere is at present capable of propagating, and closely agree with those indicated by the ionospheric measurements.

Forecast for 1950.—It is impossible to say, from a study of the top curve of Fig. 3 how the sunspot activity may vary during 1949. As is seen, the activity of late has shown no very definite trend. All things considered, however, it is likely to decrease and even to do so at a somewhat greater rate than has been apparent since the maximum. If the cycle is compared with the more recent of the past ones this would appear to be the most likely thing to happen, and from this comparison we should estimate that the running average sunspot number for the epoch at the middle of 1950 might be about 106. If this were so it is probable that the running average noon critical frequency will fall to about 9.5 Mc/s, and that for midnight to about 4.8 Mc/s.

We cannot here venture to predict what the m.u.f.s. for each month of 1950 are likely to be, but if the sunspot variation is of the order indicated above the m.u.f. for longest distance working in these latitudes should, by November, 1950, have fallen to about 36 Mc/s, as compared with 42 Mc/s in November,

1949. The "optimum working frequency" should then be about 30.6 Mc/s. The detailed specification of o.w.f.s. for every direction from this country is, of course, very complicated, and cannot be attempted here.

Predictions for certain circuits will be given month by month in "Short Wave Conditions." So far as the frequencies now generally in use for long-distance communication are concerned it does not appear likely that any great changes will take place in 1950, for not until sunspot activity has decreased considerably do the ionospheric changes begin to make themselves felt and the regularly used frequency bands become unworkable. It is unlikely, however, that the amateur 50-Mc/s band will be workable for long-distance communication at any time during the year, or that the 28-Mc/s band will be usable from about April to October.

Summing up the prospects for 1950, we may use exactly the same words as concluded this review last year, by stating that during 1950 "good radio conditions should in general prevail, and conditions tend to favour the high, but not the exceptionally high, short-wave frequencies."

SHORT-WAVE CONDITIONS

December in Retrospect: Forecast for February

THE average maximum usable frequencies for these latitudes decreased both by day and night during December, which was in accordance with the usual mid-winter trend. Day-time working frequencies were, however, still relatively high, and American police and other transmissions on about 40 Mc/s were often received in this country during the first half of the month. Reception of the London television service in South Africa was not so frequent as during November. The 28-Mc/s band was usable on undisturbed days at the appropriate times over most circuits. Night-time working frequencies above 7 Mc/s were not *regularly* usable.

Sunspot activity was, on the average, considerably lower than during November, and lower, in fact, than in any month since June.

December was an exceptionally quiet month and no severe ionospheric storms occurred. Storms of minor intensity took place on 4th, 7th-8th, 10th-12th, 17th-19th. A severe Dellinger fadeout occurred at 1256 on 12th, but only one other, of minor intensity, was reported during the month.


Long-range tropospheric propagation apparently occurred on several occasions during the month, and was particularly noticeable on the evening of 7th.

Forecast.—During February day-time m.u.f.s. in these latitudes should be considerably higher than during the past two months, whilst night-time m.u.f.s. should also increase.

Long-distance working frequencies should therefore be exceptionally high by day, and frequencies as high as 28 Mc/s should be *regularly* usable over most circuits at the appropriate time of day, whilst those up to about 40 Mc/s may become workable on occasional days during the month. At night, frequencies of the order of 7 or 8 Mc/s are likely to be the highest *regularly* usable over most circuits.

As a rule ionospheric storms are not particularly frequent during February, but those which do occur are often very troublesome during the dark hours.

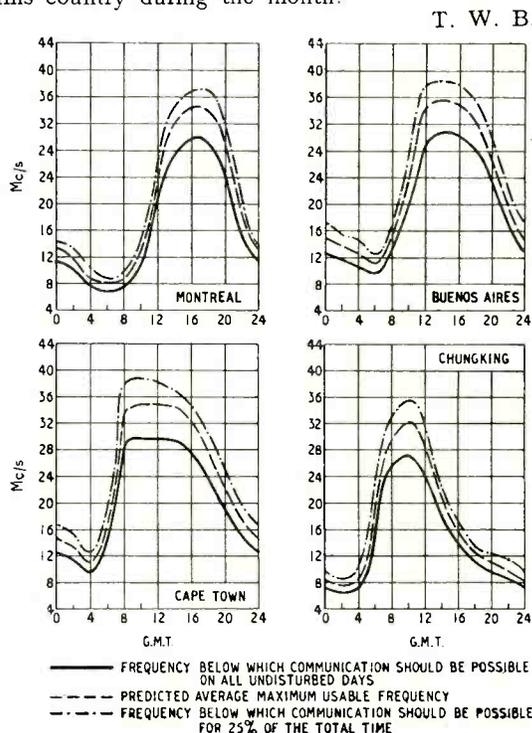The curves indicate the highest frequencies likely to be usable over four long-distance circuits from this country during the month.



WORLD OF WIRELESS

New International Organization? Television Standards for Europe ♦ "H" Aerial Controversy ♦ Servicemen's Wages

European Broadcasting

WHEN the Copenhagen Convention and wavelength plan for European stations was drawn up it included the provision that "an international expert organization" should be appointed to supervise the introduction of the Plan—due on March 15th.

It will be recalled that for the past two years or more there have been two European broadcasting organizations—the International Broadcasting Union (U.I.R.), which has been operating for many years, and the International Broadcasting Organization (O.I.R.), which was formed in 1946.

Great Britain is not a member of either organization, having withdrawn its support from the U.I.R. some years ago. It is perhaps understandable therefore that the B.B.C. has been asked to convene a conference of the broadcasting organizations of countries in the European zone which are members of the International Telecommunication Union. The object of the conference, which is arranged to open on February 6th, is to form a new European broadcasting organization. As the president of the U.I.R. was present at the meeting in Paris, at which this decision was taken, it is presumed that the U.I.R. will be superseded by the new organization.

This decision follows quickly upon the announcement that eleven member countries have withdrawn their support of the O.I.R. on the grounds of the domination of the Eastern European bloc.

International Television

WITH a view to the cultural unification of television in Great Britain, France, Belgium, the Netherlands and Luxembourg, representatives of each of the countries met in London on January 10th.

It will be recalled that at a recent meeting in Zurich, representatives of France agreed to change her present 455-line transmissions to conform with the British 405-line standard. France further stated that she would continue to develop her 819-line system. It was an-

nounced by the British representatives that when a change was made in this country to a higher definition it would be to 800 lines or more.

The Netherlands has rejected both standards in preference for 625 lines which, when the difference in mains periodicity is taken into account, is comparable with the American 525-line system.

The outcome of the meeting is awaited with interest.

Television Aerials

CONSIDERABLE interest centres around the television aerial—especially the "H" variety—at the present time. Whilst it cannot be claimed that these aspirate excrescences are things of beauty, they are essential in areas of low field strength. It is only in places where the signal is strong that a loft aerial is adequate. It is therefore with some misgivings that we read of the decisions of a number of borough and district councils prohibiting their use.

There have been a tremendous number of references to this matter in the lay Press, especially since the opening of the Midland station. Whilst some councils have banned the erection of television aerials on their property, others require a deposit of as much as £5 from tenants before they are allowed to erect an aerial—part of this is returnable

when the installation has been approved by the borough surveyor.

In one housing estate, only indoor aerials are permitted, except in the case of bungalows where a single dipole is allowed. Many boroughs have stipulated that aerials must be fitted by an approved dealer.

Midland Exhibition

THE Radio Industry Council is planning to hold an exhibition at Castle Bromwich, Birmingham, in September, with television as the main feature. As already announced there will not be a national radio exhibition at Olympia this year.

Service Technicians' Wages

A NEW scale of wages for certified service technicians has been announced by the Joint Standing Committee for the Radio Service Trade. Technicians on the Register of the Joint Standing Committee (previously known as the Radio Service Trade Register), will now receive the following minimum weekly rates according to the class of certificate held (the previous rate was in each case 7s 6d less):—

Holders of certificate "A," which is issued to persons admitted to the register by virtue of their having passed the R.T.E.B. examination, £6 12s 6d per week.


Holders of certificate "B," which is issued to radio service technicians admitted to the register on the basis of having served an approved apprenticeship or having had five years' experience in an approved employment, £6 7s 6d per week.

Holders of the television certificate, which is issued to holders of "A" or "B" who have also satisfactorily finished the television course of a manufacturer, £6 17s 6d a week.

The minimum wage for servicemen over 21 who are not on the Register is £5 5s.

Servicing Certificate Exam

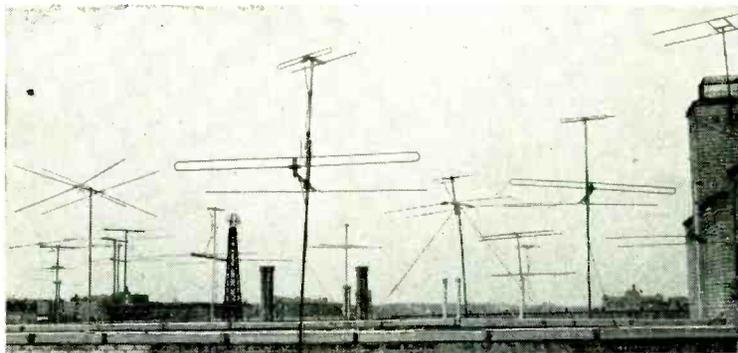THE Radio Trades Examination Board announces that the closing date for entries for the next Radio Servicing Certificate examina-



NEW YORK SKY-LINE. This photograph of the variety of television and f.m. aerials on a block of flats in New York is pertinent in view of the television aerial controversy in this country. There are, of course, 7 television stations in New York, all working on different frequencies.

ation, which is held jointly by the R.T.E.B. and the City and Guilds, is February 1st.

The written examination will be held on May 2nd and 4th at centres throughout the country, and the practical examination on May 20th at only five centres—London, Birmingham, Manchester, Glasgow and Bristol.

Further details are obtainable from the R.T.E.B., 9, Bedford Square, London, W.C.1.

B.B.C. Governors

THE KING has approved the appointment of three new Governors of the B.B.C. in place of Sir Richard Peck, Miss Barbara Ward and Geoffrey Lloyd, who retired at the end of the year. The new Governors, who will serve for two years, are Lord Tedder, Lord Clydesmuir and Prof. Barbara Wootton.

The seven members of the Board of Governors control the policy of the B.B.C. and it is to them that the Director-General—Sir William Haley—is directly responsible for the efficient working of the Corporation. The chairman of the Governors is Lord Simon and the other members, the Marchioness of Reading, Dr. Ernest Whitfield and John Adamson.

Standard Frequencies

AN experimental standard frequency transmitting station is being operated by the U.S. National Bureau of Standards on the Island of Maui, Hawaii. This station, which uses the call WVVH and operates on 5, 10 and 15 Mc/s with a power of 3 kW, is being used in addition to WWV, Washington.

The station has been installed to investigate problems relating to the simultaneous operation of more than one transmitter on the frequencies allocated at Atlantic City for standard frequency broadcasts. Details of the station were given in the September issue of our New York contemporary, *Communications*.

HONOURS

John V. Foll, managing director of Muirhead & Co. has been made an Officer of the Order of the British Empire (O.B.E.).

Among the recipients of the M.B.E. are:

Thomas M. Brennan, who is a radio officer of Flight Refuelling, Ltd., for services in the Berlin Airlift;

Henry G. M. Castell who is attached to the Diplomatic Wireless Service in the Foreign Office;

Ernest Hoyle, chief draughtsman at the Ministry of Supply's Telecommunications Research Establishment, Malvern;

Kenneth B. Ling, superintendent of Standard Telephones and Cables' factory at Treforest, Glamorganshire;

James B. Stevenson, a director of E.M.J. Factories, Ltd.; and

Geoffrey W. Warren, a physicist in the G.E.C. Research Laboratories, Wembley.

The British Empire Medal has been awarded to James D. Sweetnam who is assembly superintendent at E. K. Cole's Malmesbury, Wilts, factory.

PERSONALITIES

Air Cmdr. L. Dalton-Morris, C.B.E., has been appointed chief signals officer at the Middle East R.A.F. Headquarters at Ismailia, Egypt. For two years he has been commandant of the R.A.F. Central Signals Establishment at Watton, Norfolk, prior to which he was Director of Signals at the Air Ministry. During the war he was associated with the development of radio and radar counter-measures.

Dr. Harry F. Olson, director of the R.C.A. Acoustical Research Laboratory, Princeton, N.J., has been awarded the first John H. Potts Memorial Medal by the Audio Engineering Society of America "for outstanding accomplishments in the field of audio engineering." The medal is named after the late Editor of our New York contemporary, *Audio Engineering*.

A. John Gale, who was appointed television manager of the Scophony-Baird factory at Wembley a year ago has gone to the United States to investigate the marketing of Baird television receivers in North America.

A. C. Gale has been appointed manager of the Liverpool district office of the Edison Swan Electric Company.

J. S. Mitchell, who for many years was commercial manager at Cossor's, has joined Sobell Industries in an executive capacity.

R. Petch has been appointed by E. K. Cole as Outside Television Service Engineer covering the London area.

C. Clark Ramsay, who has been Press Relations Officer with E. K. Cole for four years, is returning to the publishing world. He is rejoining George Newnes, Ltd.



M. J. PULLING, M.A., who was recently appointed B.B.C. Senior Superintendent Engineer (Television), is vice-president of the British Sound Recording Association.

IN BRIEF

Receiving Licences.—Although there were 17,350 fewer broadcast receiving licences in force at the end of November than a month earlier, 18,350 new television licences were issued during the month. The total number of licences at the end of November was 12,106,900, including 206,700 for television. A notice bearing the words "Warning! Is Your Wireless Set Licensed?" is being posted in all Post Offices reminding owners of broadcast and television sets of the necessity of obtaining a licence.

Radio Control.—The First International Radio-Controlled Model Boats Contest to be held in this country, has been arranged for Easter Sunday and Monday, April 9th and 10th. Details of the contest, which will be held at Fleetwood, Lancs, are obtainable from J. Heathcote, General Secretary, Radio-Controlled Models Society, 8 Henniker Street, Swinton, nr. Manchester. The society is exhibiting at the second Northern Models Exhibition which is being held in Manchester from March 24th to 26th.

Standard Solder.—A revision of the war emergency edition of the British Standard BS219, which restricted the number of grades of solder to five, has now been issued. It includes the composition of five antimonial and five non-antimonial solders. Appendices give the melting characteristics and typical uses of the solders listed and information on solders intended for use at temperatures higher than those for which normal alloys covered by the Standard are suitable. BS219:1949 is obtainable from the British Standards Institution, 24 Victoria Street, London, S.W.1, price 2s post free.

Ship-to-Shore Stations.—The British Post Office short-range ship-to-shore coastal radio stations at Malin Head, Donegal, and Valentia, Co. Kerry, which since the establishment of the Irish Free State have been operated by the Irish Post Office on behalf of the British Post Office, have now been transferred to the Irish Government.

S.B.A.—Television Interference.—Owing to the interference caused by the Alexandra Palace television transmitter with the reception of S.B.A. (Standard Beam Approach) in aircraft flying in the London area, one of the marker beacons (Type R1125D) has to be modified. The selectivity of the receiver has been found insufficient when a horizontal wire aerial, capacitively coupled to the grid circuit of the first valve, is used. Details of the modifications are given in the Ministry of Civil Aviation's circular 141/1949.

G.R.S.E.—At the fifth annual general meeting of the Guild of Radio Service Engineers, the following officers were elected;— president, M. Majury; chairman, T. F. Winning; vice-chairman, W. T. G. Wanden. The recently appointed assistant secretary is J. A. Monk and the registered office of the Guild is now 88 Madeira Road, Holland-on-Sea, Essex. (Tel.: Holland-on-Sea 3101.)

Television Explained.—Some 750 teen-agers attended the I.E.E. Christmas Lecture for Older School Children on "Television," delivered by H. L. Kirke, head of the B.B.C. Research Department, on January 3rd and 4th.

The lecture, which was illustrated by lantern slides, included mechanical and electronic demonstrations of the principle of scanning.

French Scientific Instruments.—A number of research organizations in France have combined to present in this country an exhibition of French scientific instruments—including some for radio research. The exhibition, during which a number of lectures will be given, is to be held at the Science Museum, South Kensington, London, S.W.7, from February 9th to 26th.

New Transmitter.—The B.B.C. has recently brought into service a new 2-kW transmitter in Bellahouston Park, Glasgow, to radiate the Third Programme. It replaces the 1-kW transmitter installed in Broadcasting House, Glasgow, as an emergency measure in 1940.

C. & G. Report.—The recently issued report of the Department of Technology of the City and Guilds of London Institute for 1948 shows that there was a net increase in the number of entries for the subjects grouped under "Telecommunication Engineering" of 2,208. Of the 20,962 examinees, 8,034 failed. Some 28 per cent of the 213 who sat for the Radio Service Work Examination failed to qualify.

B.S.R.A. Exhibition.—Plans are being made by the British Sound Recording Association to hold an exhibition of sound recording, reproducing and allied equipment for the weekend of May 20th and 21st, 1950, at the Waldorf Hotel, London, W.C.2. Lectures and demonstrations will be included in the programme.

Imports.—Among the range of goods from which import licensing restrictions were removed on January 5th are "parts of gramophones and radio-gramophones." Certain countries, mainly those in the "dollar area" and Eastern Europe, are excluded from this relaxation.

Channel Islands Telephony.—The temporary single-channel radio-telephone link between Alderney and Guernsey has been replaced by a permanent six-channel link.

Elementary Radio Classes, including Morse instruction, are being held on Wednesdays and Thursdays at 7.45 at the Deptford Men's Institute, Childeric Road School, New Cross, London, S.E.14.

World Broadcasting.—The 1949 edition of the "World-Radio Handbook for Listeners," published in English by O. Lund Johansen, Copenhagen, Denmark, is now available from Surridge Dawson and Co., 101 Southwark Street, London, S.E.1, price 6s 6d. It gives a wealth of information on the world's broadcasting stations and the organizations operating them.

Amateur Radio.—"The Transmitting Licence—or how to become a radio amateur," published by the Incorporated Radio Society of Great Britain, New Ruskin House, Little Russell Street, London, W.C.1, is now available in its third edition. Its purpose is well explained in the following opening passage taken from the introduction—"... to present in a convenient form the essential information required by those who wish to obtain an Amateur Transmitting Licence." The price is 9d (1s by post).

Philips sound reproducing equipment being installed in Exeter Cathedral includes twelve microphones and 32 loudspeakers. The speakers will be incorporated in the lighting pendants.

Industrial R.F. Heating.—A special course of four lectures on "High-Frequency Heating in Industry" has been arranged by the Polytechnic, Regent Street, London, W.1. The lecturers are J. A. L. Wharton, R. E. Bazin, P. M. Paine, and E. S. Wilson, who are members of the research and design staff of Redifon, Ltd. Enrolment forms for the course, which will be given on Fridays at 6.30 commencing on February 24th, are obtainable from the Head of the Electrical Engineering Department. The fee for the course is 10s.

Student Exchange.—The second annual report of the International Association for the Exchange of Students for Technical Experience (I.A.E.S.T.E.), which was founded in 1948, shows that the number of students taking advantage of industrial experience overseas increased from 920 to 1,236. Great Britain sent 285 overseas and received 314. The next highest among the ten countries participating was Sweden. Ten radio manufacturers in this country received foreign students.

Professional Engineers.—Two additional branches of the Engineers' Guild—an association of professional electrical, mechanical and civil engineers—have recently been formed—the North-Western and the Southern.

Courses in Radiotechnology have been started at Allan Glen's School, Glasgow, as part of the Glasgow Corporation's Further Education Scheme.

A Joint Conference is being organized by the Institutions of Electrical, Mechanical and Civil Engineers to be held in London to coincide with the Festival of Britain, 1951. The proposed dates are June 4th to 15th.

Television Costs.—It was recently stated by the Postmaster-General that the annual rent of the London-to-Birmingham television link, whether the cable or the radio link was used, would be of the order of £50,000. This will, of course, have to be paid by the B.B.C. to the Post Office.

Scientific Film Census is being undertaken by the Scientific Film Association to bring up to date its records of documentary, instructional, educational and scientific films. Further particulars of the details required are obtainable from the association, 4, Great Russell Street, London, W.C.1.

Servicemen are not covered by the Government Order which specifies statutory wages for retail shop assistants. The Order (No. 2276/49), which came into force on January 23rd, includes, however, shop assistants in the radio and television retail trade.

Apprenticeships.—A brochure has been issued by the English Electric Co. outlining the apprenticeships available in the English Electric group of companies, which includes Marconi's and Marconi Instruments. It is available from the company's head office, Queen's House, Kingsway, London, W.C.2.

Marconi marine radio and radar gear has been installed in the New Zealand Shipping Co.'s latest vessel, *Rangitane*. The first *Rangitane*, which was sunk

during the war, was equipped by Marconi's in 1929.

Ideal Home Exhibition, organized annually by the *Daily Mail*, will be held at Olympia, London, from March 7th to April 1st.

E.M.I. Institutes have acquired new premises at 10 Pembroke Square, London, W.2, for the college. (Tel.: Bayswater 5131/2).

Mullard Equipment, Ltd., is the new name given to the Mullard subsidiary which was previously known as Electronic Transmission Equipment, Ltd. The subsidiary was formed in 1947 for the development and manufacture of communications apparatus. The company's products are marketed by the Communications Division of Mullard Electronic Products, Ltd.

Electronic Tubes, Ltd.—It was announced at the annual general meeting of E.M.I. that all the ordinary shares in Electronic Tubes, Ltd., had been purchased by E.M.I. It will be recalled that Electronic Tubes, manufacturers of c.r.t.s and valves with a factory at High Wycombe, Bucks, were, until recently, a subsidiary of Cosson's.

F. C. Robinson & Partners, Ltd., of Dalton House, Hargate Drive, Hale, Cheshire, have been appointed sole northern agents for Baldwin Instruments and Mullard Electronic Products.

FROM ABROAD

Switzerland.—We have received a copy of the 18th annual report (1948) of the Swiss broadcasting organization. The sections dealing with each of the three main transmitters are printed in the language radiated—Sottens in French, Monte Ceneri in Italian, and Beromünster in German. The material regarding the general organization of Swiss broadcasting—both internal and international—is in French. The statistics show that 84 per cent of the families in Switzerland own broadcast receivers. The total number of licensed sets at the end of 1948 was 969,606.

Anglo-American Exchange of radio engineers is suggested by our New York contemporary, *Tele-Tech*. "The stimulus of an interchange of engineering thought in the field of radio and television should benefit both countries. For the British; U.S. methods of production would be an eye-opener... and some U.S. manufacturers could learn from the solid built-to-last construction of their British counterparts."

A pictorial list of the tuning signals of 77 American television stations is included in the January issue of our New York contemporary *Radio-Electronics*. It is interesting to see that about 50% are purely pictorial and are in no way intended as test patterns to facilitate receiver adjustment.

Indian Licences.—A 50 per cent increase in the broadcast receiving licence fees has been introduced in India. The new licence fee for domestic valve sets is Rs15 and that for sets in business premises Rs50. The fee for community receivers is Rs10 whilst a fee of Rs3 is payable by schools and institutions. The latter fee is also charged for crystal sets.

Indian Peoples' Set.—The design of a cheap medium-wave receiver for local reception is being undertaken by the

Research Division of All India Radio. The prototype two-valve a.c./d.c. set, which is expected to sell at between Rs25 and Rs30, has a cabinet said to cost only 4 annas. The valves used are the 6SJ7 and the 3ZL7GT.

Colour Television Tests.—It is understood from Washington that as a result of the recent investigation to formulate plans for the re-allocation of television frequencies in the U.S., the F.C.C. has called for public tests of colour television. Manufacturers of colour television equipment have been asked to transmit regular daily programmes for a specified period and to provide domestic receivers for the tests.

819-line Television.—The power of the French high-definition television transmitter, which has been in use experimentally since November 15th with a power of only 0.7kW, has now been increased to 3kW. The aerial is erected on the Eiffel Tower, Paris.

International Television.—The Swiss Television Committee has issued a statement following a recent meeting in which it is pointed out that 625 lines is becoming a world standard. The optimum bandwidth for this standard has yet to be agreed internationally. The two possibilities are 4.25 and 5Mc/s.

NEW ADDRESSES

British Relay Wireless, Ltd.—The head office of B.R.W. and its associated companies, is now at Giltspur House, 6 Giltspur Street, London, E.C.1. (Tel.: City 3280.)

E.M.I. Sales & Service is opening a Midland television service depot at City Chambers, 111-117 John Bright Street, Birmingham.

Mullard has opened a valve and cathode-ray service depot at 108, Dale End, Birmingham, 4. The service is restricted to callers.

Telephone number of the London office and showrooms of E. K. Cole at 5 Vigo Street, W.1., is now Regent 7030/9.

MEETINGS

Institution of Electrical Engineers

Radio Section.—"Ground-Wave Propagation Over an Inhomogeneous Smooth Earth," by G. Millington, M.A., B.Sc., and G. A. Isted, on February 15th.

Informal Meeting.—Discussion on "Interference Suppression," opened by E. M. Lee, B.Sc., on February 13th.

Both meetings will be held at 5.30 at the I.E.E., Savoy Place, London, W.C.2.

Cambridge Radio Group.—"Some Considerations in the Design of Negative-Feedback Amplifiers," by W. T. Duerdoth, B.Sc. (Eng.), at 8.15 on February 7th at the Cavendish Laboratory (Joint meeting with the Cambridge University Wireless Society).

North-Eastern Radio Group.—Discussion on "Control and Measuring Equipment; Electronic versus Non-electronic Apparatus" on February 6th. "Theory and Design of Magnetic Amplifiers," by H. M. Gale, B.Sc. (Eng.) and P. D. Atkinson, M.A., on February 20th.

Both N.E. Radio Group meetings will be held at 6.15 at King's College, Newcastle-on-Tyne.

North-Western Radio Group.—"Printed Circuits, including Miniature Components and Sub-miniature Valves," by J. E. Rhys-Jones, M.B.E., and G. W. A. Dummer, M.B.E., at 6.30 on February 22nd, at the Engineers' Club, Albert Square, Manchester.

South Midland Centre.—"Television Radio Relay Links," by A. H. Mumford, O.B.E., B.Sc. (Eng.), and C. F. Booth, O.B.E., at 6.0 on February 6th, at the James Watt Memorial Institute, Great Charles Street, Birmingham. (Joint meeting with the Institution of Post Office Electrical Engineers.)

Western Centre.—"Magnetic Amplifiers," by A. G. Milnes, M.Sc. (Eng.), at 6.0 on February 6th, at Electricity House, Colston Avenue, Bristol.

Faraday lecture on "Radar," by R. A. Smith, M.A., Ph.D., at 6.30 on February 13th, at the Guildhall, Swansea.

London Students' Section.—"Blind Landing," by T. E. Schilizzi, B.A., on February 1st.

Address by the President, Prof. E. B. Moullin, M.A., Sc.D., on February 20th.

Both Student meetings will be held at 7.0 at the I.E.E., Savoy Place, London, W.C.2.

British Institution of Radio Engineers

London Section.—"Travelling-Wave Tubes," by R. L. Kompfner, at 6.30 on February 23rd, at the London School of Hygiene and Tropical Medicine, Keppel Street, W.C.1.

West Midlands Section.—"Electronics and the Brain," by H. W. Ship-ton at 7.0 on February 22nd, at the Wolverhampton and Staffordshire Technical College, Wulfruna Street, Wolverhampton.

Scottish Section.—"The Performance and Stability of Permanent Magnets," by A. J. Tyrrell, at 6.45 on February 2nd, at the Institution of Engineers and Shipbuilders, Glasgow.

Mercyside Section.—"The Measurement of Small Currents," by D. R. Hardy, M.Sc. (Eng.), at 7.0 on February 1st, at the Accountants' Hall, Derby Square, Liverpool.

North-Eastern Section.—"Single-Sideband Systems Applied to Long-Range Wireless," by Major S. R. Rickman, at 6.0 on February 15th, at Neville Hall, Westgate Road, Newcastle-on-Tyne.

Television Society

London Meeting.—Demonstration and discussion on television aids—polaroid lenses, filters, aerials and interference suppressors at 7.0 on February 24th, at the Cinema Exhibitors' Association, 164 Shaftesbury Avenue, London, W.C.2.

Constructors' Group.—"Mullard Projection Receiver," by Emlyn Jones (Mullard), at 7.0 on February 9th, at the C.E.A., 164 Shaftesbury Avenue, London, W.C.2.

Midlands Centre.—"The V.H.F. Link," by A. H. Mumford (Post Office, Radio Branch), at 7.0 on February 6th, in the Lecture Hall, The Crown Restaurant, Corporation Street, Birmingham.

Bristol and S.W. Centre.—"The Electronic Engineering Televisor," by W. I. Flack, at 7.30 on February 7th, at the Royal Hotel, Bristol.

British Sound Recording Association

"High Quality Reproduction—How to Achieve It," by H. J. Leak, at 7.0 on February 24th, at the Royal Society of Arts, John Adam Street, London, W.C.2.

Radio Society of Great Britain

"Panoramic Reception," by B. H. Briggs, M.A. (G2FJD), at 6.30 on February 24th, at the I.E.E., Savoy Place, London, W.C.2.

Institute of Navigation

A symposium of papers on air traffic control at 4.0 on February 17th, at the Royal Geographical Society, 1, Kensington Gore, London, S.W.1.

Guild of Radio Service Engineers

Edinburgh Branch.—"Valves and the Service Engineer," by D. N. S. Toms (Standard Telephones & Cables), at 7.30 on January 26th.

Lecture by F. Henderson of the Osram Valve Department at 7.30 on February 23rd.


Both meetings will be held at Unity House, 4 Hillside Crescent, Edinburgh.

"A.C./D.C.-Battery Power Supplies"

An Important Correction

IN Fig. 1 of the article on page 31 of the January issue it is regretted that incorrect values were given for some resistors in the l.t. and mains voltage adjustment circuits. The corrected circuit is reproduced herewith.

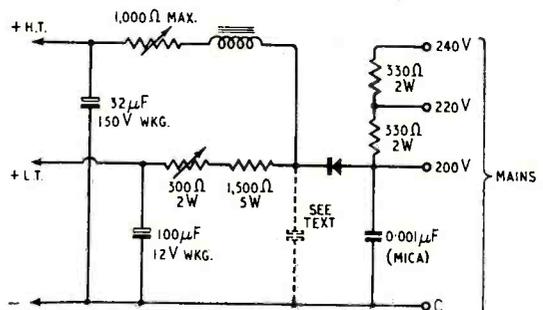It should also be emphasized that the method of "losing" surplus mains voltage, involving the omission of the rectifier reservoir capacitor, applies only to a.c. mains and this particular circuit should not be used on a d.c. supply.



FILTERS

By "CATHODE RAY"

2. Debunking the Cosh—and Other Mathematical Weapons

FOR the sake of those who haven't read Part 1 (and perhaps of some who did) I will start by recapitulating. We found that unless the calculation of filters is to be unbearably tedious or mathematically advanced it is necessary for the load impedance to be related to the impedances of the filter components in a special way. The main result of this relationship is that the impedance measured at the input of every section of the filter is the same, and equal to the load impedance. This particular value of impedance is called the characteristic or iterative impedance and denoted by Z_0 . Directly the form of the filter (T, π , etc.) has been settled, one can write down an equation connecting Z_0 with the impedances of its "arms." For a T section, for example, it is

$$Z_0 = \sqrt{Z_1 Z_2} \sqrt{1 + \frac{Z_1}{4Z_2}} \dots \dots \dots (1)$$

where Z_1 and Z_2 are respectively the total series and shunt impedances of the filter section. In a simple low-pass section, as shown in Fig. 1, $Z_1 = j\omega L$ and $Z_2 = 1/j\omega C$, and when these are substituted in (1) we get

$$Z_0 = \sqrt{\frac{L}{C}} \sqrt{1 - \frac{\omega^2 LC}{4}} \dots \dots \dots (2)$$

We noted that the first factor, $\sqrt{L/C}$, is a constant depending on the filter components, and is multiplied by a second factor which depends on frequency (since $\omega = 2\pi f$). If the frequency is zero, Z_0 is just $\sqrt{L/C}$, a resistance. As the frequency rises, this resistance drops to zero at a certain critical frequency $1/\pi\sqrt{LC}$ (because it makes $\omega^2 LC/4 = 1$). Above that it is a pure inductive reactance, increasing steadily. All this can best be seen by drawing the graph, Fig. 2.

We had taken note of the awkward fact that no practical load behaves in exactly this way, and what most people do is just to use a resistance of $\sqrt{L/C}$ ohms, which is correct at very low frequencies but causes a mismatch at other frequencies. (Usually of course, the procedure is vice versa; you are given a load of, say, 1000 ohms, and you choose filter components such that $\sqrt{L/C} = 1000$.) The results of a mismatch remained to be revealed, and so did the all-important question of how the attenuation of a filter varies with frequency.

Non-Mathematicians Read on!

It is at this crucial stage in the argument that the less mathematically advanced students tantalizingly lose consciousness as a result of a well-aimed blow with a cosh; in other words, the writer resorts to hyperbolic functions. As I said before, coshes and other hyperbolic functions are no more difficult to look up in tables than sines and coses, but the reason for bringing them in at all is not always transparently

clear. It is possible to dodge this issue a little longer, however, and at the same time see something of the answer.

Considering first of all the part of the curve in Fig. 2 up to where the frequency is $1/\pi\sqrt{LC}$, we see that Z_0 is a pure resistance. Therefore all the power put into the filter must be dissipated somewhere. The filter itself has no resistance, so the only place where the power can be dissipated is the load, which (being equal to Z_0) is of course a resistance. If all the power goes right through the filter without loss, there can be no attenuation. So up to a certain frequency—which, you may note, you can make what you like by a suitable choice of component values, because it is $1/\pi\sqrt{LC}$ —the filter doesn't attenuate at all. That is one remarkable fact that can be arrived at simply from the most elementary principles. (But remember the load resistance has to vary with frequency according to the curve in Fig. 2.)

You can see at once from Fig. 1 that there should be no attenuation at zero frequency; the impedance of the series arms is nil and the shunt arm infinity. It is not nearly so easy to see why it should be so at other frequencies. A.c. flowing through the coils is bound to cause a voltage drop, and, with the load resistance falling, the current will tend to increase and cause the drop to be greater. So how can the insertion of the filter have no effect? The explanation is that this increasing voltage drop across Z_1 is exactly

Fig. 1. The type of filter section being considered—a low-pass T—terminated by its characteristic impedance Z_0 (see Fig. 2).

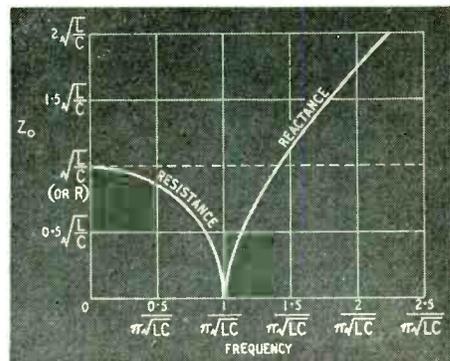
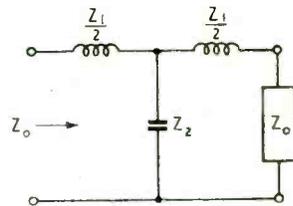


Fig. 2. How the characteristic impedance of the Fig. 1 type of section varies with frequency.

offset by a tendency to resonate with Z_2 . As you know, in a resonant circuit the voltages across the reactances can each be much larger than the input voltage. And the effect of the load resistance is to keep the input current exactly in phase with the voltage at all pass frequencies. It is a fascinating thing to ponder over.

Next, what is the significance of the critical frequency where Z_0 drops to zero (or soars to infinity in the π type)? Its formula, $1/\pi\sqrt{LC}$ will almost certainly have rung a bell by now—or perhaps half rung it? It is so very like $1/2\pi\sqrt{LC}$, the formula for the frequency at which a series circuit made up of L and C resonates. The coincidence is too remarkable to mean nothing; but why should the 2 be missing? In other words, why should the filter's critical frequency be double the resonant frequency?

Looking at Fig. 1 and drawing in the load and generator resistances, which at this frequency must both be zero, we find that the two series arms, each made up of $L/2$ come in parallel with one another and with C. The total inductance in parallel with C is therefore $L/4$, and if you substitute $L/4$ for L in the resonance formula you find the resonant frequency comes out as $1/\pi\sqrt{LC}$. So this mysterious critical frequency is where the filter resonates!

The same conclusion can be arrived at by considering a π section, Fig. 3. At the critical frequency its Z_0 rises to infinity, so it can be regarded as being open-circuited, just as shown. The two capacitance arms are in series with one another, and as their separate capacitances are $C/2$ (to make $2Z_2$) the capacitance in parallel with the coil is $C/4$ and the resonant frequency $1/\pi\sqrt{LC}$, as before.


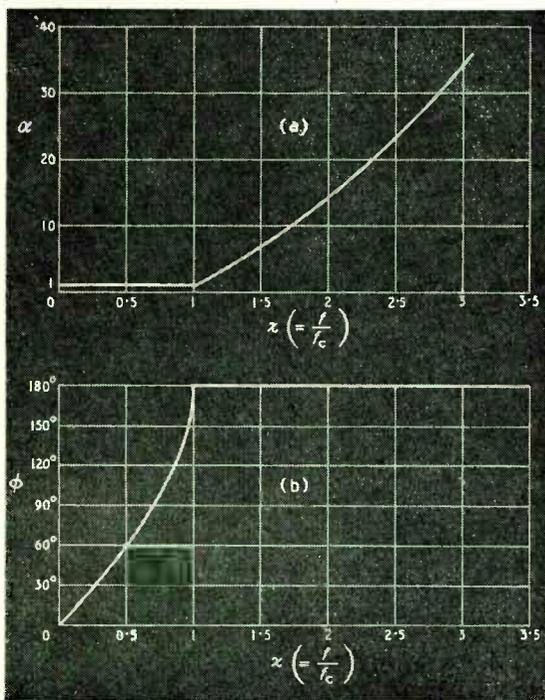


Fig. 4. Attenuation (a) and phase angle (b) curves against frequency for a low-pass ladder filter terminated by Z_0 . Note the abrupt changes at the cut-off frequency (where $f/f_c = 1$).

Fig. 3. Low-pass π section.

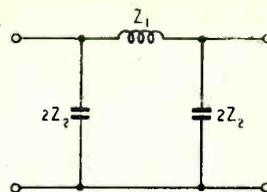

At all higher frequencies, the filter (and its load) looks to the generator like a pure reactance, which means that no power is accepted. From a power point of view, therefore, it attenuates completely. That does not mean, of course, that no current or voltage can reach the output. And, let us remember, it is based on the rather unpractical assumption that the load suddenly becomes a reactance, whereas in practice it is likely to remain a resistance. Still, if you consider the situation carefully, you may reach the conclusion that above the critical frequency the filter attenuates. Whether you do or not (and don't be worried if it isn't obvious!) it does in fact; so what we have been calling the critical frequency is known as the cut-off frequency, usually denoted by f_c (sometimes f_0).

Algebraical Detour

And now we can really no longer evade what in days gone by would have been called (not very politely) a *pons asinorum*. This is where, as I said, most writers make good their escape by resorting to the cosh. Actually the thing can be done by perfectly straightforward algebra, greatly aided by j (which we saw in the Feb. 1948 issue was not really a difficult trick to acquire). Most things in so-called higher mathematics can be done by straightforward algebra, but they are apt to be so intolerably tedious that way that they never would be done unless neater and shorter methods had been devised. Unfortunately these short cuts look so dangerous to those who have never gone by them before that they prefer to toil around the long but more familiar routes.

I haven't sufficient space to show in full every step of the way in finding the attenuation of a filter, say as in Fig. 1, but here is a sketch plan:

What you want—the attenuation—can be expressed as the ratio of the input and output currents. The input current (I_i) divides between Z_2 and the second $Z_1/2$ (and Z_0) in Fig. 1. The latter part is the output current (I_0). So what goes through Z_2 must be $I_i - I_0$. Now because $Z_1/2 + Z_0$ and Z_2 are in parallel with one another, the voltages across them are obviously the same. The voltage across Z_2 is $Z_2(I_i - I_0)$ and the voltage across $Z_1/2 + Z_0$ is $I_0(Z_1/2 + Z_0)$. As these two are equal, you have a simple equation connecting I_i , I_0 , Z_1 , Z_2 and Z_0 . Z_0 can be expressed in terms of Z_1 and Z_2 (equations (1) or (2)), and the result can be put into a form showing the attenuation (I_i/I_0 or α) in terms of Z_1 and Z_2 . So when you have chosen Z_1 and Z_2 you can find the attenuation. Because Z_1 and Z_2 depend on frequency you can turn the equation into one connecting α with f , and draw a graph of it. And since the section is terminated by Z_0 , you can use any number of sections and each will have the same attenuation. For two sections the whole attenuation will be α^2 ; for three, α^3 ; and so on. The only tricky part of this algebra is keeping account of the phase. It could be done without j , but j makes it very much easier. A further simplification is to

generalize the whole thing by putting it in terms of f/f_c instead of f . It makes it neater to denote f/f_c by some single letter, say x . Then $\omega\sqrt{LC}/2$ can be written simply as x . Another dodge is to denote $\sqrt{L/C}$, the zero-frequency Z_0 , as R . Then $Z_{1/2} = j\omega L/2 = jRx$, and $Z_2 = 1/j\omega C = R/j2x$.

The final result of all this manipulation should come out as

$$\alpha = 1 - 2x^2 + j2x\sqrt{1-x^2} \quad \dots \quad (3)$$

If you dislike j , the alternative is

$$\alpha = \sqrt{(1-2x^2)^2 + (2x\sqrt{1-x^2})^2} \quad \dots \quad (4)$$

It looks reasonably simple to substitute various numbers for x and draw up a table connecting x and α , from which to draw a graph of attenuation against frequency (relative to cut-off frequency as 1), but there are one or two things.

Starting off with values of x less than 1 (i.e. in what we have reason to believe is the no-attenuation or pass region in a low-pass filter), α calculated by (4) turns out to equal 1 every time. (Remember, (4) gives the magnitude only without regard for phase.) That means that $I_0 = I_i$; so there is no attenuation (Fig. 4(a)).

It is interesting to calculate the phase angle. $1 - 2x^2$ is the in-phase component, and $2x\sqrt{1-x^2}$ the 90° component, so $2x\sqrt{1-x^2}/(1-2x^2)$ is the tangent of the phase angle. Having calculated this, we can find the angle from a table of tangents. The result of this investigation shows that the output current starts off in phase at zero-frequency ($x = 0$), and increases steadily to 180° at the cut-off frequency ($x = 1$), as in Fig. 4(b). (Incidentally, the shape of this part of the curve is a quarter of a sine wave stood up on end.)

So in the pass region the filter doesn't attenuate but it does shift the phase.

Directly we start putting $x =$ more than 1 in (3) or (4) we encounter the square root of a negative quantity. This brings the j -less users of (4) to a complete standstill, but the j men carry on merrily with (3) by substituting $-2x\sqrt{x^2-1}$ for $j2x\sqrt{1-x^2}$; and the whole equation now appears as


$$\alpha = -(2x^2 - 1 + 2x\sqrt{x^2-1}) \quad \dots \quad (3a)$$

The minus sign signifies what we already know for $x = 1$, namely, that the output current is 180° out of phase with the input. And as j is absent for all values of $x > 1$ we see that the phase remains constant at this, as shown by the flat top in Fig. 4(b). The magnitude of α can be calculated straightforwardly now, and rises in a curve as shown in Fig. 4(a).

So now we have full details of the performance of one or any number of low-pass filter sections terminated by Z_0 ; and can easily adapt the method to apply to high-pass filters, and (a little less easily) to band filters. And all without a trace of a cosh or a e^{ix} or any such-like fearsome apparition! Are these things merely to frighten possible intruders away from the filter experts' "closed shop"?

The answer lies in the amount of time and effort you have expended in working out the data for Fig. 4 from equation (3) and (3a)—supposing you have been painstaking enough to have done it. The hyperbolic man just takes a good look at the equation and says "Catch me doing all that work! Why; can't you see? $\cosh \log_e \alpha = 2x^2 - 1$!" And so he looks up his table of coshes, and then finds α from his log_e table or, if he is that sort of man, he will probably not

Fig. 5. Attenuation curves for a filter terminated (a) correctly by the theoretical Z_0 —this is the same as Fig. 4(a) but to a decibel scale this time—and (b) by the practical load resistance $R (= \sqrt{L/C})$.

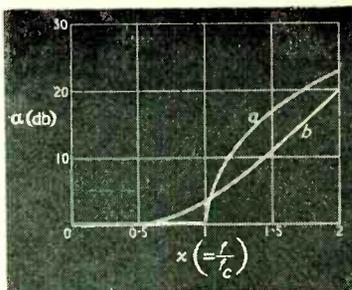

bother, but just call the $\log_e \alpha$ figures the attenuation in "nepers"—units each equal to 8.686 decibels).

The practical value of the cosh, then, lies in the fact that it enables one to dodge most of the work by looking up tables. For instance, when $x = 2$, $2x^2 - 1 = 7$, and the thing that 7 is the cosh of is (from the table) 2.632. Multiplying this by 8.686 gives the attenuation in decibels—22.8, which is 13.9 in α ratio. Anybody can do that without knowing anything about the theory of hyperbolic functions.

If 22.8 db at twice the cut-off frequency is not enough, then just add more sections. Two will give 45.6; three, 68.4, and so on. To design a filter to given requirements one would know f_c , the desired cut-off frequency, and also R , the nominal characteristic impedance (at zero-frequency in a low-pass filter). The information we already have gives $L = R/\pi f_c$ and $C = 1/\pi R f_c$ —the component values.

Conditions Near Cut-off

All this is most interesting, but unfortunately it relates to a load impedance that exists only in imagination. It would be much more practical to know what happens when the load is not the fantastically varying Z_0 but the solid constant R . Fig. 2 shows that everything would go according to plan at zero frequency (much use that is!) and probably nearly so at all frequencies much lower than f_c . But near f_c there is bound to be violent mismatching, and in any case all our beautiful calculations based on Z_0 fall down.

That is not to say that they have been a waste of time. As I suggested earlier, the policy is to use this comparatively simple but purely theoretical case as a main framework, and then find out how it is modified by practical conditions such as a constant resistive load and losses in the filter components. Fortunately, the modifications are much less drastic than one might expect. The losses in well-designed filters usually cause a little rounding off near f_c and some reduction in α at the highly-attenuated frequencies. Fig. 5 shows what happens near f_c when $R (= \sqrt{L/C})$ is substituted for Z_0 as the load following a single section. For comparison the Z_0 curve from Fig. 4(a) is repeated, but both curves in Fig. 5 are plotted to a decibel scale. If the load impedance is very different from R —especially if it is much greater—the departures from the Z_0 curve really are drastic; but it is generally not difficult to use R .

When several sections are used the curve becomes rather more complicated, with a noticeable waviness; but it never departs very far from the Z_0 curve.

The methods of arriving at the corrected curves are too much to go into here. But we have found what I hope is an intelligible theoretical route, as well as a good short cut, to a performance curve for

the theoretical Z_0 -terminated filter; and when the sharp corner has been smoothed off slightly it makes a good enough design curve for an R-terminated filter.

If you are more interested in high-pass filters, all you have to do in Figs. 4 and 5 is to substitute $1/x$ for x .

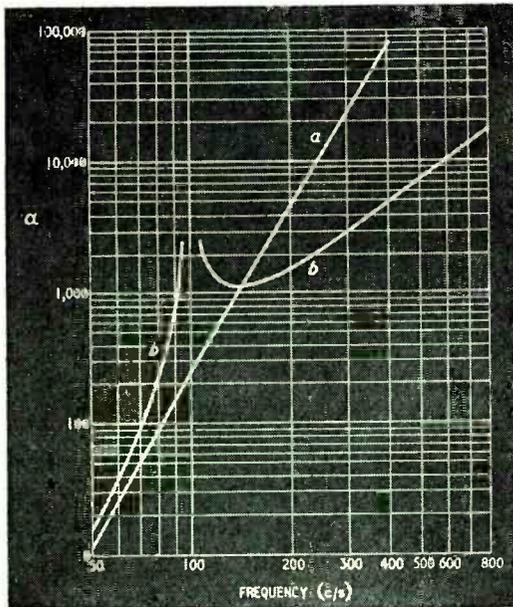


Fig. 6. The attenuation curves we had (Nov. 1949) for a typical smoothing system (b) with and (a) without choke tuning. This technique is elaborated in m-derived filters.

Fig. 7. One form of m-derived section corresponding to the simple low-pass T. An alternative is to put inductance in series with the vertical arm, to form an acceptor.

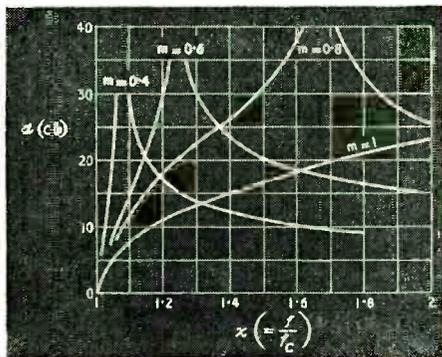
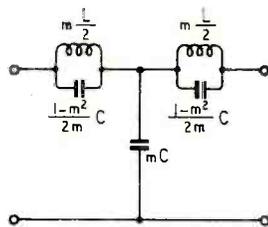


Fig. 8. How the attenuation curves of m-derived sections compare with that of the original "constant-k" (for which $m=1$). The cut-off is greatly sharpened at little extra cost.

There are any number of other types of filters (T. H. Turney defines a filter as *any* set of coils and condensers connected up anyhow, with input and output terminals). One of the most important is called the lattice, though it is exactly the same circuit as the Wheatstone bridge, drawn in such a way as to make it difficult to recognize. The only other one I have room to say anything about is a modification of the T and π types (collectively termed "ladder" filters). The basic types we have been concentrating on are sometimes called "constant-k" filters. That follows from a practice of denoting $\sqrt{Z_1 Z_2}$ in equation (1) by the letter k; as we have seen, in the case we considered, it is a constant for all frequencies, amounting to $\sqrt{L/C}$. It is, in fact, what we have been calling R. The same applies to the corresponding high-pass filters and also to band filters in which the series and shunt L's and C's are equal.

m-Derived Filters

There are two objections to constant-k filters. One is that their Z_0 varies so much over the pass band (Fig. 2). The other is that if you don't like the attenuation curve (Fig. 5) you have to lump it. Although you can multiply the α scale by using more sections, no adjustment of component values will make the cut-off per section sharper. So if you want to eliminate a frequency quite close to the cut-off with a constant-k filter you have to use an un-economically large number of sections, which may give far more attenuation at the remoter frequencies than you need. You may remember that three months ago we took note of a useful dodge for getting over this difficulty in the case of smoothing circuits using perhaps as few as two sections, by tuning one of them to reject the undesirable frequency. This dodge converted a rather gradual attenuation curve, (a in Fig. 6), into a really sharp cut-off with a peak at the frequency to be rejected (b). The fact that the attenuation at remote frequencies is less enormous doesn't usually matter.

In our smoother we just added capacitance across one of the chokes, sufficient to tune it to the offending frequency; and that was almost all there was to it. In filter books they dignify this simple modification with the title "m-derived filter" and devote a whole chapter to it, with several new lots of formulae. What is "m," and why? And what is all the fuss about?

Again, it is not really evidence of a "closed-shop" mentality. With the smoother, we didn't have to bother about what happened between the rejected frequency and zero. And (mainly for that reason) there was no question of matching impedances. But the sort of filter we are talking about now has to refrain from attenuating at all over a predetermined band of frequencies, and then cut off rapidly. To make it do this—and also to be able to predict the results with reasonable accuracy, and avoid mismatching—it is necessary to keep as close as possible to the ideal of working into and out of the characteristic impedance, Z_0 . It has been found that if, when the constant-k type of section is being modified into the tuned type, the L and C values are altered according to a set plan, it is possible to keep its cut-off frequency and its initial or nominal Z_0 (R) unaltered, so that the modified section will match the same load and also other modified or unmodified sections. No

only so, but its Z_0 can be made more nearly equal to R over the pass band, so going some way to meeting the other objection to the constant- k type.

The key to the plan is m , where m is the fraction by which the original arm impedances are multiplied or divided. The smaller m is, the closer the resonant frequency is to the cut-off frequency. When $m = 1$, there is no modification. I am not going into details, because anybody who is interested can look them up, and the rules are very easy to follow. Just as an example of the kind of thing, Fig. 7 shows how the original T section is modified into a "shunt-derived" T section, Fig. 8 shows how the value of m affects the position of the rejected frequency (f_r) relative to the cut-off frequency (f_c) (the formula is $m = \sqrt{(1 - f_c^2/f_r^2)}$), and Fig. 9 shows how m affects Z_0 . One can see from Fig. 9 that for keeping Z_0 as nearly constant as possible the best m is somewhere between 0.6 and 0.7, making f_c/f_r between 0.8 and 0.7, which may or may not be convenient.

Fig. 7 shows that the capacitance and inductances have been reduced to the fraction m of what they were, and two new capacitances have been introduced to tune the coils. This is not the simplest m -derived section to choose; my only reason is that it is derived from the type we have been considering most, so that (for example) Fig. 9 can be directly compared with Fig. 2. For simplicity one would choose the "shunt-derived π " (with only one tuned arm) or the "series-derived T" (with an acceptor circuit in the vertical arm). Another possibility is to use half a Fig. 7 section tacked on to a π (Fig. 3). If there are several different frequencies to be rejected, several derived sections can be used, each with a different value of m .

A good way of getting a grip of this introduction to filters is to work out the component values to meet

any requirements you may care to name. If you have the facilities for constructing filters from the resulting designs and testing them, that of course is the best way of all.

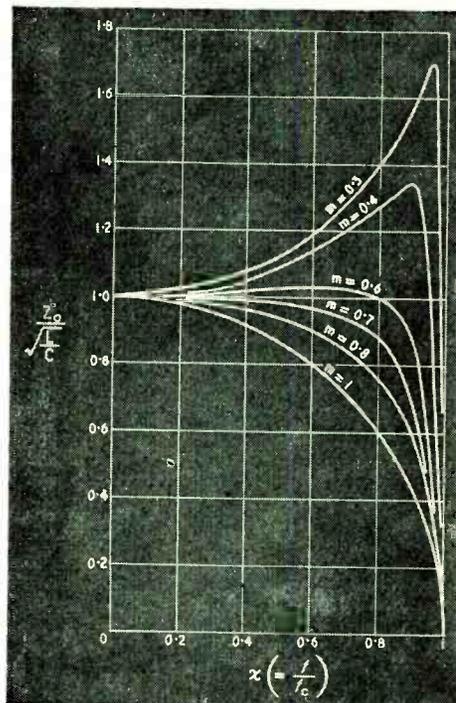


Fig. 9. Characteristic-impedance curves plotted for various values of "m" in Fig. 7.

Published Reports

Preferred Valves

Welcome example in limiting the bewildering number of valves at present in use has been set by the Scientific Instrument Manufacturers' Association, in publishing a list of preferred types for electronic instruments. The valves in each category have been chosen to give marked differences of characteristics, and whenever possible to have alternatives in this country or America; whilst in limiting base types, the aim has been to concentrate on International Octal for standard-sized valves and on B7G for miniatures. Characteristics and base connections are given in this booklet, which can be obtained from S.I.M.A., Ltd., 17, Princes Gate, London, S.W.7, price 2s 6d by post.

Tilts in the Ionosphere

Errors in direction finding at h.f. may be caused by lateral deviations from the great circle path of waves reflected from the F_2 layer. Radio Research Special Report No. 19, from the Department of Scientific and Industrial Research, ascribes this effect to random tilting of the layer at the point of reflection, and gives details of observations made with spaced-loop direction-finders on various h.f. broadcasting stations during 1938-1947. The report is published by H.M. Stationery Office, price 10d by post.

Marine Interference Suppression

A standard of interference suppression for ships is provided by a recently published British Standard (1597:1949), covering frequencies up to 30 Mc/s. It specifies the permissible limits of interference in terms of aerial terminal voltages, lays down conditions for the construction of wireless rooms and gives requirements to be satisfied by the ship's electrical machinery and wiring installation. There are also notes on the components used for suppression. B.S. 1597:1949 is available in booklet form from the British Standards Institution, 24-28, Victoria Street, London, S.W.1, price 4s by post.

Educational Film

"High Frequency" Heating, produced by Merton Park Studios, Ltd., for the British Electrical Development Association, is one of seven films which explain the fundamental principles of familiar electrical effects, and is designed for the age group 13 upwards. It runs for nine minutes and deals with both induction and dielectric heating, showing diagrammatically the process by which heat is generated in each case, and giving practical applications such as case-hardening drills and cooking a loaf of bread. The film, in 16mm. or 35mm., with teaching notes, is available on loan from the Association at 2, Savoy Hill, London, W.C.2.

UNBIASED

By FREE GRID

Radio-Rocket Racket

IT is now more than half a century since wireless was first used in warfare—field sets were taken by the Army to the Boer war in 1899. Range and reliability were—to use the jungle English of Whitehall—both in short supply and it is not surprising, therefore, that wireless played a very minor rôle in the campaign. It was, in fact, so minor that, as Mr. Churchill tells us, news of the customary early British disasters in warfare was signalled to his incoming ship by more reliable methods. It can be said without fear of contradiction that wireless had no influence whatever on the outcome of the Boer war, whereas on that of the next one it will be decisive.

I am not thinking so much of the radio-guided block-busters, which we may expect from Strelsau should we find ourselves in conflict with Ruritania, but of what I feel sure the popular Press will call "mercy missiles" in the shape of radio-controlled rockets containing food and all the other supplies which in the last two wars had to come to us over the submarine-infested seas.

In using these radio ration rockets for the dispatch of the meat, wheat and wool which we may expect from them, our friends in the Antipodes will, if, in the interests of fuel economy they choose a Great Circle route, obviously have to be careful to select the correct one of the alternatives available to them. If you will give Mercator a miss and plot on a *W.W.* Great Circle map the routes between us and the Antipodes you will see why. I speak with some feeling in this matter, for the last time I was "south of sixty" I found that some of the natives were



"South of Sixty."

no more friendly to this country than Commander Campbell's Patagonians and they might attempt, therefore, to deal with the rockets as the Ancient Mariner did with the albatross in these latitudes except, of course, that they would use micro-wave guns instead of a cross-bow.

I am laying some stress on the viewpoint that the beneficent rôle of radio rockets will far outweigh any "maleficence" (what a word!), because I think that the other point of view is, and always has been, over-emphasized in the Press and elsewhere; so much so that it is justifiable to call it a radio-rocket racket. As long ago as 1911 there was a display at Earls Court of model radio-controlled aircraft dropping radio-released bombs, and even this venerable journal, in its report of the matter, did not see fit to point out that the bombs might just as well have been sacks of ground-nuts or barrels of dehydrated beer. I would point out, too, that the radio-controlled rockets, which bring the much-needed manna, could, if necessary, be used on their return journey to evacuate the women and children.


I trust, therefore, that people will more and more realize that no matter whether we find ourselves in conflict with Ruritania or Erewhon, or at peace with all men, "radio is on our side" as it has always been.

Looking Ahead

WE are now well into 1950, but not in the second half of the 20th century, as so many people seem to think. It is perhaps scarcely surprising that they think so when the editor of one of our most widely circulated national "dailies" thinks so too, and has produced special editions to celebrate his error. I do not, of course, intend any reflection on his integrity, for editors are, above all, men of honour and wield the blue pencil mercilessly on anything they believe to be lacking in accuracy. Some of them, however, are a little weak in their arithmetic and, in the case of editors of specialist journals, also somewhat lacking in knowledge of matters outside their immediate ken, so that they accept without question statements made by their contributors.

A remarkable instance of this in the realm of radio occurred shortly before the opening of the Sutton Coldfield television station. Several

The opening ceremony in 1952.

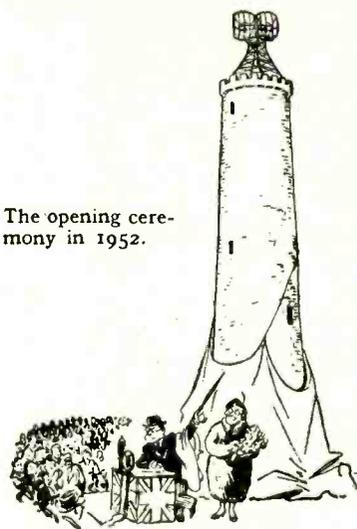

Midland newspapers, the editors of which had obviously never heard of d.c. television receivers, made the wild statement that residents in certain areas in the neighbourhood of the station would be denied television because of their lack of a.c. It is true that they were repeating words attributed to the chairman of the local Electricity Board, but surely editors know that the utterances of administrators on technical matters are often no more to be trusted than those of Mr Bevan on the treatment of chilblains.

Not only do some lay editors get their radio facts wrong, but they omit to bring to public attention things which cry out aloud for it. I refer more particularly to the fact that, so far as I am aware, not one single newspaper or periodical—including, I am sorry to say, *Wireless World*—has demanded the building of super-television studios on the south bank of the Thames after the shouting and the tumult of the 1951 Festival of Britain has died and its temporary pavilions are one with Nineveh and Tyre. A permanent concert hall is now being erected and a national theatre is planned, but these will take up only a small part of the space available. Surely, with such easy access to the West End, the site is ideal, in contrast to the proposed studios in the remote White City—also a relic of a bygone exhibition.

In addition, the famous Shot Tower is ideally situated for the necessary 30-centimetre link to be erected on top of it. Now is the time to demand this site before other interests stake their claim. In conclusion, I would stake my own claim to be invited to perform the opening ceremony in 1952; in this I have the full support of Mrs. Free Grid, who is, as a matter of fact, already trying to decide what she shall wear on the occasion.

Air-Sea Rescue Up-to-Date

Radio's Rôle in an International Organization

By BASIL R. CLARKE



Radar scanner on one of the Ocean Weather Ships.

ONE of the more successful international achievements, in which radio plays a leading rôle, is the combined Air Sea Rescue system now operating in many parts of the world. The International Civil Aviation Organization is the coordinating body responsible for the general planning. The U.K.'s field of operation is the North Atlantic and the waters surrounding our coasts.

A search and rescue operation in which the writer took part was the first, other than rehearsals, under the international scheme and the comparative smoothness with which it ran is a great tribute to the designers of the system.

Rolling gently in the North Atlantic at 61° N. 130° W. the U.K. Ocean Weather Ship *Weather Observer* was carrying out her normal duties as well as standing by for a flight of U.S.A.F. jet aircraft from Iceland to Stornoway. The weather, hitherto good, was deteriorating when at 1600 hrs. a relayed S.O.S. reached her from Prestwick—the control station for that area—giving the estimated position of the *Erik Boye*, a 400-ton Danish steamer in distress, with a shifted cargo and a flooded engine room. The original message from the *Erik Boye*, which was fitted with R.T. only, had been relayed by a Farøes trawler to Thorshavn Radio, which had in turn passed it to Prestwick. The only fault in the system appeared to be the delay between the first distress call and the time that Prestwick was called.

The *Weather Observer* was ordered to proceed to the position, about 200 miles west of the Farøes, and to carry out a visual and radar search. Also in the


search were two trawlers and a Danish radar-equipped passenger ship, R.A.F. aircraft from Scotland and U.S.A.F. lifeboat-carrying aircraft from Iceland. Under orders from Prestwick, the *Weather Observer* laid down a plan for a "box" search (see diagram) by the radar-fitted aircraft and ships, thus eliminating any danger of duplication in some areas while leaving others unsearched.

The Ocean Weather Ship was the focal point for all control messages and also provided a positive navigational datum point, her Loran providing a continuous position check for herself, and her Naval radar (Type 277) for the searching aircraft.

At 1000 hrs. the next morning a U.S.A.F. aircraft found the *Erik Boye*, and, having informed the other searchers, settled down to fly in small circles over her, with a radio beacon operating. All the ships immediately began to converge and, as soon as the *Weather Observer* had sighted the distressed ship the aircraft set course for her base. Some 22 hours after the search began four ships were standing by the *Erik Boye*, whose true position was found to be many miles from that originally given.

Radar, a medium-frequency beacon, Loran, m.f. and v.h.f. direction finding, m.f., h.f. and v.h.f. telephony, and long-range high-frequency c.w., all played their part in a rescue in which a Danish ship was sought by British, Danish and Farøes ships, British aircraft from Scotland and American aircraft operating from an Icelandic base.

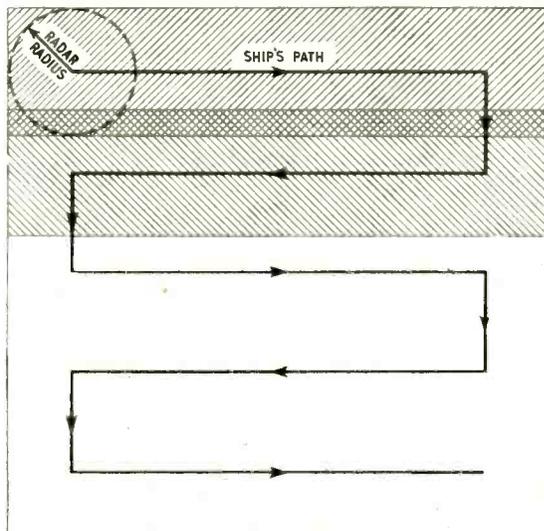General principle of the "box" search system. The same method is employed by aircraft using A.S.V. or visual methods.



Midget Three-Valve A.C. Mains Receiver

Adding Long Waves and a

Stage of Tuned R.F. Amplification to the Original Two-Valve Receiver

By S. W. AMOS, B.Sc. (Hons.), Grad.I.E.E. (Engineering Training Department, British Broadcasting Corporation)

THE article in the March, 1949, issue on a midget 2-valve a.c. mains receiver aroused much interest and the author has received many requests from readers for guidance in adding an r.f. stage, a long-wave band or both to the receiver. These requirements are met in the t.r.f. model described in this article; it is a 2-band receiver using EF50's in r.f., detector and output stages. The sensitivity is markedly superior to that of the 2-valve receiver and is such that worthwhile results can be obtained on signals of less than $100 \mu\text{V}$ amplitude; it should be adequate for reception of B.B.C. programmes in most parts of the country whereas the original 2-valve receiver was intended for use only near high-powered transmitters. The new receiver, illustrated in the accompanying photographs, is constructed on a chassis measuring $9\text{in} \times 5\text{in} \times 2\frac{1}{2}\text{in}$, the overall height being $6\frac{1}{2}\text{in}$. The 5-in diameter loudspeaker used with the new model is larger than on the original receiver and gives better quality. The total cost of the components for the new receiver is about £4 5s.

The circuit is given in Fig. 1; it has much in common with that of the 2-valve receiver and comparatively few additional components are necessary to modify the original set to the t.r.f. circuit. Tuning is by a 2-gang variable capacitor and the tuning inductors have standard values, commercial dual-

range coils (Denco type C) being used in aerial and intervalve circuits. To give high selectivity and to minimize the effects of different aerial constants on the first tuned circuit, shunt-capacitance aerial coupling is used, the low voltage gain of this form of coupling being largely offset by the high g_m of the r.f. valve. The primary windings of the aerial r.f. transformer are not used. The 470-ohm resistor R_1 is necessary to preserve d.c. continuity in the grid circuit of V_1 , and also to make the receiver input impedance low at 50 c/s; with a high value of R_1 , weak signals tend to be modulated at 50 c/s.

EF50 valves are cheap and plentiful and because of their low heater consumption they are used in all stages of the receiver. The use of this valve as r.f. amplifier introduces a problem in controlling gain, because the EF50 is not a variable-mu valve, and whatever form of gain control is used must prevent overloading of the leaky-grid detector. The method finally adopted is shown in Fig. 1; a 50-k Ω potentiometer is connected in the primary circuit of the intervalve r.f. transformer and the slider is taken to the anode of V_1 , this particular circuit being chosen to keep the damping of the detector tuned circuit constant, in spite of variations in gain setting. The gain control gives no protection against overloading of the r.f. amplifier but, of course, this receiver is


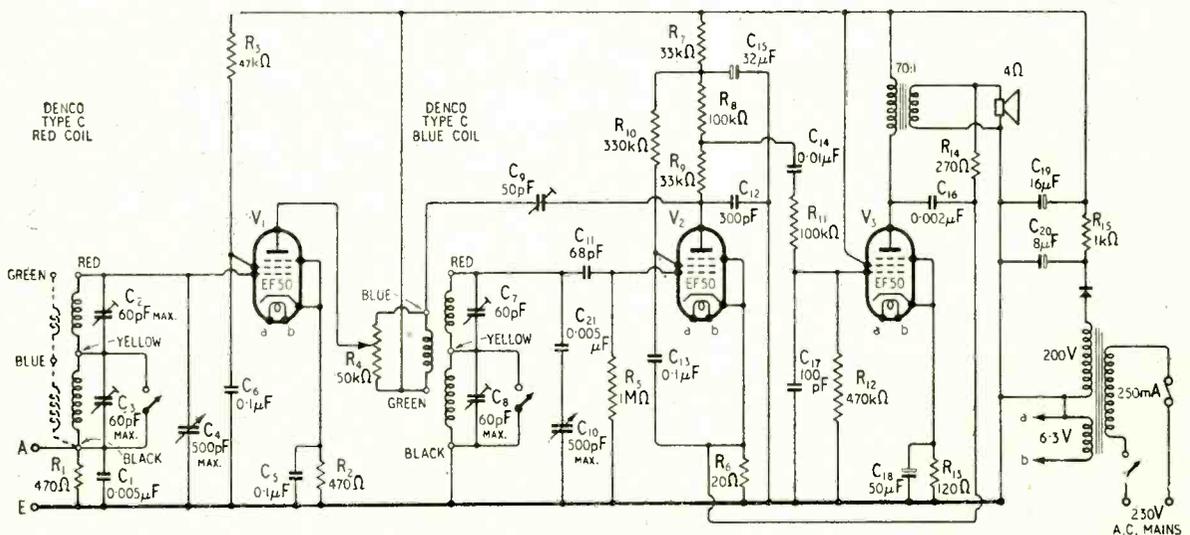


Fig. 1. Complete circuit diagram with component values. All resistors can be of $\frac{1}{2}$ -watt rating.

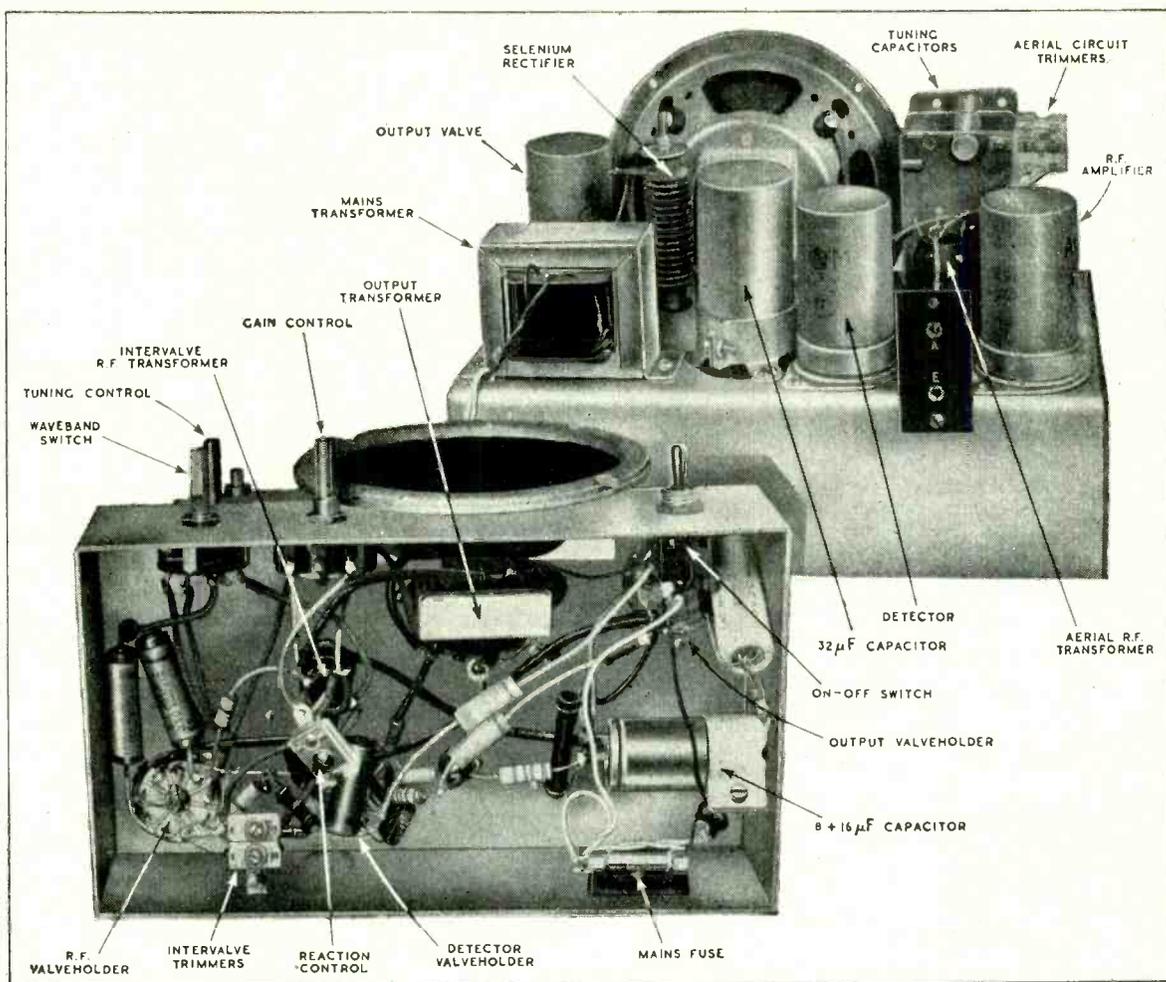

Two views showing the general layout of the receiver. To ensure r.f. stability the components in the grid circuit of the r.f. amplifier are mounted above the chassis and those in the detector grid circuit are located on the underside.

primarily intended for use in areas of comparatively low field strength. Nevertheless, the low voltage gain and high selectivity of the aerial circuit give good protection against overloading of V_1 and no symptoms of cross-modulation have been noted using the receiver within a few miles of a high-power transmitter.

Reaction is applied by a small pre-set capacitor; this should be adjusted well below the point of oscillation, but even so gives a useful improvement in gain and selectivity.

The $0.005 \mu\text{F}$ capacitor C_{21} is included to simulate the aerial-coupling capacitor C_1 and makes the effective tuning capacitance in the intervalve and aerial tuning circuits approximately equal, thus ensuring good ganging at the low-frequency ends of the wavebands.

When an r.f. valve is used in the output stage, particular attention must be paid to post-detector r.f. filtering, for even a small r.f. signal in the a.f. amplifier can mar reproduction. Three measures are used to suppress r.f. signals in this receiver: C_{12} shunts the anode load of V_2 and reduces the r.f. amplitude there; further attenuation is provided by

R_{11} and C_{17} ; finally C_{16} connected between the anode of V_3 and the cathode of V_2 gives considerable negative feedback at radio frequencies without affecting the performance at audio frequencies.

As the gain control operates in the r.f. section of the receiver, a fixed amount of voltage negative feedback can be used in the a.f. amplifier and is provided by R_6 and R_{14} . Fixed feedback is an advantage because it means that less h.t. smoothing is necessary for a given amount of hum; thus it has been found possible to reduce the value of the first smoothing resistor R_{15} from $5 \text{ k}\Omega$ in the 2-valve model to $1 \text{ k}\Omega$ in the 3-valve model, yet the hum of the new receiver is less than that of the original. By reducing the value of R_{15} the h.t. voltage is kept reasonably high (170 volts) in spite of the additional drain of the r.f. stage.

Apart from the alteration in the value of R_{15} the mains rectifying and smoothing components are identical with those used in the original receiver.

To align the receiver the trimmers C_2 and C_7 should first be set to their minimum capacitance and then advanced until a frequency of approximately 1,500 kc/s (200 meters) is received with the tuning capaci-

tors at minimum and the waveband switch set to medium waves. Finally, the trimmers should be accurately adjusted to give maximum output from the receiver on a signal near the high-frequency end of the medium-wave band such as the third programme on 1,474 kc/s. Trimmers C_3 and C_6 should be adjusted in a similar manner near the high-frequency end of the long-wave band, but on this band the trimmers should first be set at their maximum capacitance otherwise it may prove impossible to receive the low-frequency end of the band. The coil manufacturers (Denco, 355-9, Old Road,

Clacton-on-Sea) recommend a trimming capacitance of 70 pF for this band.

With many receivers the addition of an earth lead makes comparatively little improvement in reception, but with this receiver (and with the original 2-valve model) the addition of the earth lead makes a considerable difference, and it is recommended that a good earth connection be used whenever possible. Needless to say, a good aerial should also be used and it is perhaps worth stressing that the calibration and selectivity of this receiver are practically unaffected by the constants of the aerial used.

NEW BOOKS

Radio Aerials. By E. B. Moullin, M.A., Sc.D. Pp. 514+x1; figs. 243. Geoffrey Cumberlege, Oxford University Press, Amen House, Warwick Square, London, E.C.4. Price 50s.

THIS is the second volume in a new series of monographs describing recent advances in the scientific field. It deals only with a limited class of radio aerials, but does so in great detail.

The first section of the book is theoretical. The Lorentz vector and scalar retarded potential functions are first established and then applied to specific problems. These include the fields due to filaments, the effect of flat sheet and V-shaped reflectors, and problems relating to cylinders immersed in electromagnetic fields.

Some hypothetical problems are solved rigorously, usually in terms of Bessel functions, and practical problems are considered as approximations—usually very close ones—to the hypothetical cases. The power gain of typical arrays with various current distributions is calculated, and methods of suppressing the side-lobes discussed. A short section is devoted to the isolated aerial.

The remaining one-third of the book describes experimental procedure, and the results of measurements made on some of the aerials described in the first section. Results for V aerials are given in great detail, and include the radiation patterns for various V angles and sizes of sheet.

The reader who is interested in the practical applications of the aerials described, but does not wish to plod through the mathematics, will find plenty of interest in this section, and indeed throughout the book. From time to time the author draws attention to many practical design considerations—how far it is worth while increasing the size of sheet reflectors in order to improve the aerial performance, the permissible tolerance on the shape of the reflector, the use of netting and rods instead of continuous sheet, and similar problems of great importance to the aerial designer. The many examples of measured aerial performance will also be of interest—too little information has in the past been available, both in technical journals and in text books, on this subject.

The treatment is mainly mathematical, however, and the reader will require a reasonable knowledge of mathematics if he is to derive full benefit from this book. It will therefore appeal more to the aerial specialist or post-graduate student. A valuable feature of the book is that the author gives physical interpretations and justifications of his methods, which helps the reader to get the feel of the mathematics.

To sum up, this will be found valuable not only as a book of reference on the types of aerial covered, but also for the clear and logical development of the general theory.

H. P.

Industrial High Frequency Electric Power by E. May, B.Sc., A.C.G.I., M.I.E.E. Pp. 355+x1; figs. 208. Chapman & Hall, 37, Essex St., London, W.C.2. Price 32s.

MOST radio engineers look upon low-frequency alternators as a relatively unimportant part of their power supply equipment. This book leads them all the way from these low-frequency alternators up to the high-frequency oscillators which they are more at home with, and helps to present the whole subject as a single problem and, to give a new way of looking at it. It is interesting, for instance, to read of resonance as seen from the eyes of someone who has been brought up to believe it to be an evil thing, which an engineer can by his skill sometimes turn to his advantage.

The examples of equipment and applications in the lower frequency part of this field are well selected and authoritatively presented, and (once one has got over the shock of seeing a 400-cycle alternator called a "high-frequency alternator") can afford a valuable introduction to a subject which has been inadequately covered.

Readers of *Wireless World* will no doubt be more interested in the radio-frequency sections of this book. It must be regretfully said that in these the author is out of his depth. Is it true, for instance, that push-pull oscillators are more frequency-stable than single-sided oscillators? Is not there a risk that they will be more liable to parasitic oscillations? Has Mr. May never heard of parasitic oscillations? Does he really think that one of the reasons for coupled output circuits in high-frequency oscillators is to save d.c. drop in the tank circuit? Do arc oscillators produce damped waves? Spluttery and bubbly, perhaps, but are they damped? Is it necessary to spend a lot of time on idealized graphical solutions of oscillator performance including the usual simplified and quite erroneous load-line treatment only to reach conclusions which are either wrong or irrelevant (such, for instance, as the statement that the anode current is independent of grid drive as long as the grid bias remains constant)?

It is all a great pity; either as a text-book or a reference book about the lower-frequency end of the high-frequency heating problem this work is attractive and one would like to be able to recommend it to radio-frequency engineers as being complementary to their own store of knowledge. But the author has written a book which has one good and one bad half, and the bad half will discredit the good half in the eyes of so many people to whom it would have been useful.


A. H. C.

Book Received

Accumulator Charging. By W. S. Ibbetson, B.Sc., A.M.I.E.E. (Tenth Edition). Detailed treatment of the processes of charging, maintenance and repair. Pp. 190+xvii; Figs. 41. Sir Isaac Pitman & Sons, Parker Street, London, W.C.2.

Preferred-Value Attenuators

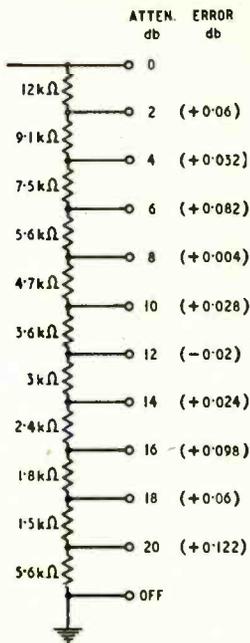Choosing Suitable Resistors from a Limited Range



By
E. W. BERTH-JONES,
 B.Sc.

Fig. 1. Potentiometer giving attenuation of 1 db per stud, with maximum errors of -0.032 db and $+0.054$ db. Total grid-earth resistance is 47.3 k Ω .

IN audio engineering the demand often arises for a stepped attenuator in the form of a grid potentiometer, the steps giving equal increments of attenuation of one or more decibels. For many applications the accuracy, and hence the cost, of a commercially obtainable precision attenuator is not justified.

It is perhaps not generally realized that a very useful range of potentiometers can be constructed, using preferred-value carbon resistors and ordinary wafer type switches. The maximum possible error introduced by the preferred values can, for the purposes of computation, be broken down into two components: (a) a maximum standing error of about $+0.1$ db, representing the difference between the ideal calculated resistance and the nominal value of the nearest preferred resistor; and (b) an error representing the greatest deviation from the mean error of all the resistors used. To make (b) a little clearer, we will take an example. Supposing that we decide to use resistors of ± 5 per cent tolerance, we may find in practice that all the samples chosen fall between $+2$ per cent and $+4$ per cent of their nominal value. The mean error of the resistors is then $+3$ per cent, and the greatest deviation from this is ± 1 per cent, representing 0.09 db. So for this particular example we see that the maximum possible error in the attenuator, (a) plus (b), will be 0.1 db $+ 0.09$ db = 0.19 db, say 0.2 db. This assumes the worst case, of course, when both the components (a) and (b) are additive on the same resistor, and in general the actual errors encountered will probably be considerably less than this value.

With the figures quoted in the above example, the overall resistance of the potentiometer will be about 3 per cent above the designed value, due to the mean error in the resistors, but this fact is usually of no consequence. The first example is a potentiometer having a nominal resistance of 50 k Ω , suitable for working into a triode grid. Attenuation is provided in ten steps of 1 db, together with an "off" position.

The appropriate resistance values are as shown in Fig. 1, and it will be noticed that all the figures quoted appear in the list of preferred values. The total resistance works out at 47.3 k Ω , which is sufficiently near the nominal total of 50 k Ω for most practical applications. The resistors are assembled on a single-pole 12-way make-before-break wafer switch, which provides the click action usually desirable with step type attenuators. Obviously this selection of values is equally applicable in any decade, say, for a 500 - Ω or 500 -k Ω nominal potentiometer, but the values must not be transposed to give other totals.

Higher Values of Attenuation

Another example sometimes useful is a potentiometer giving attenuation of 10 db per step. Here each two steps give 20 db loss, a resistance ratio of 10:1, so that we require only two values, repeated as often as required in successive decades. Suitable figures are 68 and 22, with 10 between the lowest stud and earth, and a 100-k Ω potentiometer based on these numbers is shown in Fig. 2. The range of attenuation has been limited to 60 db because it is not practicable to exceed this value for normal applications, on account of the peak-signal/noise ratio of the following valve.

In this example it would be permissible to add an extra resistance of 220 k Ω at the upper end to give the potentiometer shown in Fig. 3, which has a total resistance of 320 k Ω . Note that the resistances at the lower end are not changed. Owing to Miller capacity

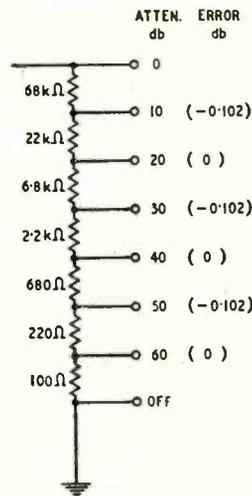


Fig. 2. Potentiometer giving attenuation of 10 db per stud, with a maximum error of -0.102 db. The total resistance is 100 k Ω .


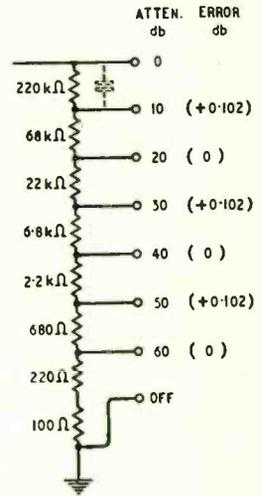


Fig. 3. Potentiometer giving attenuation of 10 db per stud, with a maximum error of $+0.102$ db. The total resistance is 320 k Ω .

Fig. 4 (below). Potentiometer giving attenuation of 2 db per stud, with maximum errors of -0.02 db and $+0.122$ db. Total resistance here is 56.8 k Ω .

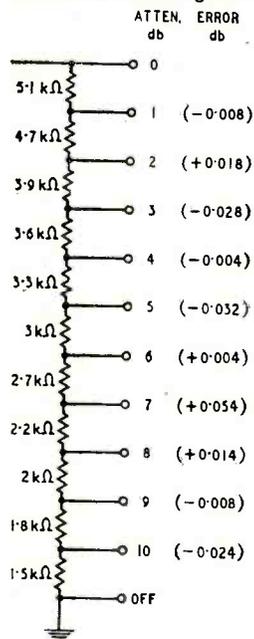

of the following valve, in combination with such a high value of grid potentiometer, some loss of high frequencies would probably be noticed on the stud giving 10db attenuation, and a small condenser might be advisable between this stud and the top of the potentiometer, as shown dotted.

Another good example is the potentiometer giving 2 db per stud shown in Fig. 4, which has a total

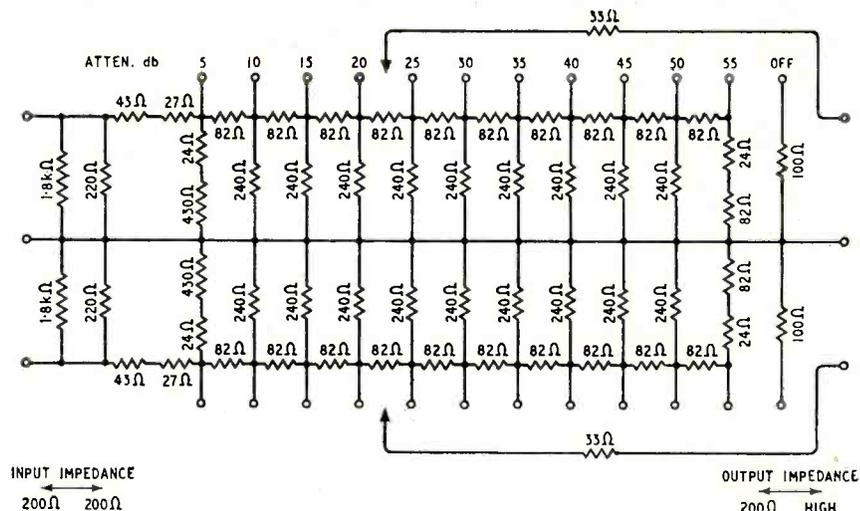


Fig. 5. (Above) Balanced- π attenuator. The resistors have been selected so that the positive and negative errors will alternate.

resistance of 56.8 k Ω . This has the useful property that, if extra studs are available, it may be extended either upwards or downwards as required, repeating the resistance values in the next decade, provided due attention is paid to the resistance between the lowest stud and earth.

The examples shown by no means exhaust the possibilities. They may, however, encourage the rather fascinating mental exercise of trying to produce others. As a final illustration, Fig. 5 shows a balanced- π attenuator having an insertion loss of 5 db and attenuation of 5 db per step, with terminations to match a $200\text{-}\Omega$ source and present 200Ω to the load. A 12-way double-bank switch is used, again with make-before-break contacts. With such a network, resistances of positive and negative error should alternate, in order to prevent the error becoming cumulative.

Choice of Radio Materials

THE high standard of reliability demanded of radio apparatus in its many and varied applications to-day and the consequent necessity for using exactly the right material for each particular job is the reason for the recent publication by the Radio Industry Council of Specification RIC/1000/A. This specification is described as a guide to manufacturers in the choice of materials for radio and electronic equipment and for components used in that equipment. It is intended to provide the industry with help in settling its own materials problems along lines comparable with those on which the Inter-Service Specification RCS/1000 helps the Services to deal with their distinct but similar problems. It is hoped that eventually the relevant sections of both these specifications may be linked together in one national standard to be published by B.S.I.

Specification RIC/1000/A deals with the following subjects: Ferrous metals; aluminium and aluminium alloys; copper and copper alloys; solders; zinc and zinc alloys; plastics (thermo-setting and thermo-plastic); elastomers; inorganic insulating materials; insulating, filling and sealing compounds; textile materials and paper; timber; lubricants; wire and sleeving; miscellaneous materials, including adhesives and fluxes.

The needs of manufacturers of equipment for export

are borne in mind, and in many sections of the specification the suitability or otherwise of materials for tropical climates is touched upon.

The specification has been prepared jointly by the Technical Specification Committee of the R.I.C. and the Materials and Finishes Sub-Committee of the R.I.C. in consultation with the British Radio Equipment Manufacturers' Association, the Radio Communication and Electronic Engineering Association and the Radio and Electronic Component Manufacturers' Federation. It has been approved for publication by the Technical Directive Board of the R.I.C. on which all the constituent associations of the R.I.C. are represented.


Copies of the specification are obtainable from the Radio Industry Council, 59, Russell Square, London, W.C.1, for 3s 6d each, post free.

A further guide dealing with "Finishes" is being prepared by the R.I.C. but it is not expected to be completed until well into 1950.

The R.I.C., in conjunction with the Radio Communication and Electronic Engineering Association, have also recently published Specification No. RIC/271/A—Pin Connectors of Piezo-Electric Quartz Crystals mounted in B7G Valve-type Envelopes. A limited number of copies is available from the R.I.C., price 1s.

Marine Communal Aerials

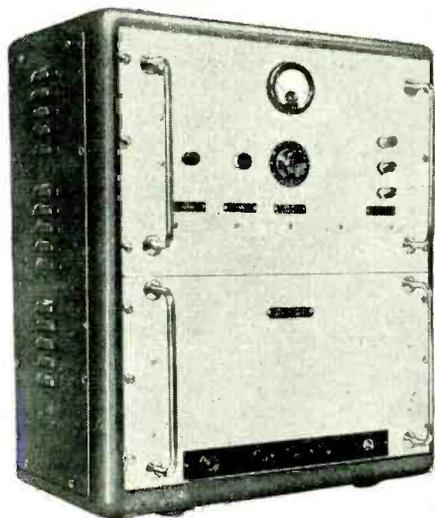Ship's Distribution Systems Providing Interference-free Reception with Private Receivers



Communal aerial amplifier for the Redifon distribution system which is capable of feeding 300 private receivers from a single ship's aerial.

THE indiscriminate erection of aerials on board a ship by passengers and crew so that they can use their own wireless receivers at sea is frowned upon by the ship's officers, as, apart from being very unsightly, a host of small aerials can prove a serious source of error in the ship's direction-finding equipment.

A communal aerial is the only satisfactory alternative, but to be really efficient the system must be properly engineered. If an attempt is made to use a large number of receivers on a single aerial without certain precautions being taken many peculiar effects may be encountered. These can take the form of varying signal strength as receivers elsewhere are tuned over the broadcast bands; heterodyne whistles due to leakage of local oscillators into the distribution system; cross modulation; and, in the case of a ship, complete wipe out of all signals whenever the ship's transmitters come into operation. Some, if not all, of these troubles can also be experienced when separate aerials are used.

Several of the principal firms in the United Kingdom engaged in installing radio in ships have given this matter their attention and at

least two communal aerial systems, which allow trouble-free reception with private sets, have been installed in some of the larger vessels launched recently.


The system evolved by the Marconi International Marine Communication Co. consists of a main unit having three basic output circuits and this is augmented by supplementary units throughout the ship, which vary in number according to the size of the installation.

As it is possible to operate up to three receivers from each of the basic output circuits the main unit alone would serve a total of nine receivers. When more are needed, supplementary units are brought into use and, as each of these has six output circuits each capable of operating up to three receivers, a supplementary unit

will cater for eighteen sets. As the supplementary units provide amplification as well as circuit isolation there is no limit to the number of such units that can be employed.

The main unit, to which the aerial is connected, contains the necessary filter and rejector circuits to rid the broadcast signals of interference from the ship's transmitters. After these come a channel splitting stage then a three-channel amplifier. Each channel has a voltage amplifying stage and an output stage and is completely isolated from other channels.

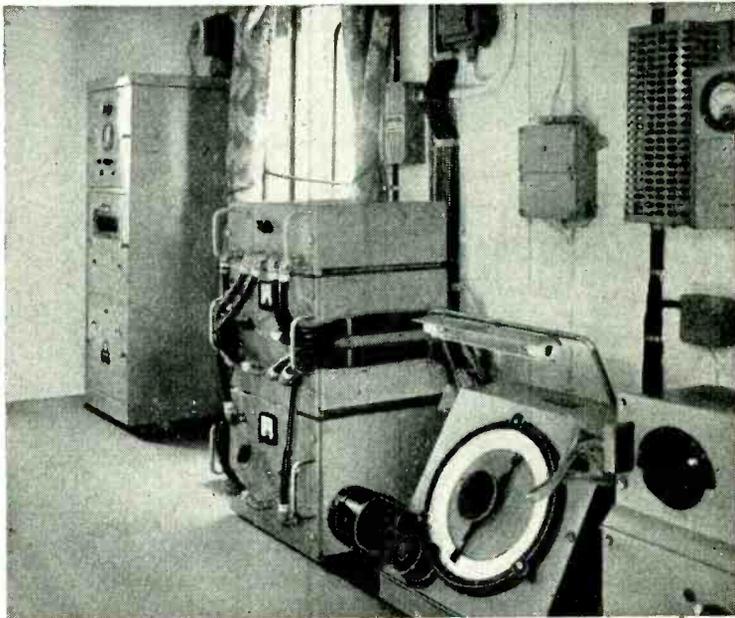A stage of amplification is used in the supplementary units and this feeds six separate output valves giving an adequate signal in all receivers over the 180- to 550-metre and 12- to 67-metre bands with small gaps as required to prevent interference from the ship's transmitters. There are no



The Marconi communal aerial unit installed between the direction finder and the auto-alarm in the wireless cabin of the cable ship *Edward Wilshaw*.

filters in the supplementary units and all the rejection is effected in the main unit.

All units have self-contained power supplies and are available for either 110V or 220V d.c., or 230V a.c. The power consumption of each unit is between 60W and 110W according to the nature of the supply.

The system designed by Redifon provides optimum working conditions for about 300 receivers in the ship. Incoming signals from the aerial are fed via a cathode follower to two wideband amplifiers, one covering the medium- and long-wave bands, and the other the short-wave broadcast bands. The output from each chain is fed to a mix-

ing circuit and thence to three power stages each connected as cathode followers and feeding into separate output lines of from 70 to 150 ohms impedance. The receiving bands provided are 200 to 2,000 metres and 13 to 60 metres, with small gaps where necessary to reject frequency bands required for the ship's transmitters. This equipment is known as the Type Ar33.

At appropriate points in the system special junction boxes are fitted and in each cabin, or receiving point, is an outlet unit—for matching the receiver input circuit to the line—and the aerial and earth sockets. Isolating capacitors are included in these units so that under no conditions

can mains voltages get into the distribution system.

In the Redifon system all amplifiers, filters and rejectors are contained in a single unit which gives about 25 times overall amplification from the aerial to each of the output sockets. An a.c. power pack is also incorporated in the unit and the only external equipment needed, apart from the line apparatus, is a rotary converter to provide the necessary power when an a.c. supply is not available. The whole is housed in a sturdy metal case, measuring approximately 2ft 1½in × 1ft 3in × 1ft 9in, and weighing 115 lb, and fitted with shock-absorbing bushes for bulkhead or desk mounting.

CONCENTRIC DUPLEX LOUDSPEAKER

A Compact Reproducer with a Wide Frequency Range

BASED on a design originally developed in 1935 by the Whiteley Electrical Radio Company, Victoria Street, Mansfield, Notts., the W/B Concentric Duplex loudspeaker is a small high-quality unit consisting of two moving coils working in separate gaps at either end of a powerful Alcomax III permanent magnet. One coil drives a horn-loaded "spherical" metal diaphragm and the other a 10-inch graduated-fibre cone diaphragm. The "tweeter" horn passes through the centre pole of the magnet and terminates in a non-resonant moulded bakelite flare.

Both coil drives have a pole diameter of 1 inch and the flux densities are 13,000 gauss in the tweeter and 12,000 gauss in the cone drive.


A multi-ratio transformer is fitted, and various combinations of high- and low-frequency matching are possible, since the low-frequency coil impedance is 3 ohms and the high-frequency, 30 ohms. To limit the excursion of the high-frequency diaphragm a 2-μF condenser is in series with the h.f. coil and transformer secondary.

We have heard this loudspeaker in operation and there can be little doubt that the makers' claim of a frequency range of 50 to 14,000 c/s can be substantiated. On the equipment used in the test there seemed to be an excess of medium-high frequencies, but this

could no doubt be adjusted by experiment with the matching arrangements. Indeed, it is the accessibility of the connections to the two units and the possibility of experiment with various matching alternatives, or the introduction of more elaborate cross-over filters, which will provide one of the chief attractions for the quality enthusiast.

On a plane baffle the Concentric Duplex gives a clean and full-bodied bass response of surprisingly good quality for a 10-in diaphragm. The diaphragm suspension is also of a type well-suited for use in conjunction with a cabinet of the "bass reflex" type if this is preferred.

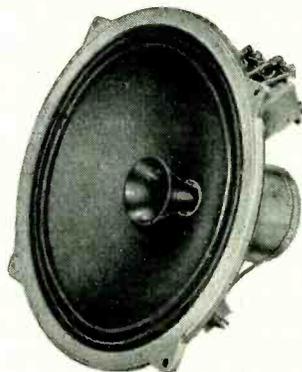The price is £6 6s complete with output transformer and condenser.



A non-resonant and non-magnetic die-cast frame is used to support the low-frequency cone in the W/B Concentric Duplex loudspeaker.

Responder Beacon

A 200-Mc/s beacon has been designed by Flight Refuelling Ltd., to assist their "tanker" aircraft to locate and intercept "customer" aircraft requiring fuel. It is carried by the "customer" and consists, basically, of a receiver and a pulse transmitter, arranged so that upon reception of an interrogating radar pulse from a Rebecca set in the "tanker," the receiver triggers the pulse transmitter, which radiates a reply pulse.

A notable feature is its long range, which is claimed to be 150 miles air-to-air; this is achieved with a

transmitter peak output power of 500 watts and pulses of 5- or 7-μsec duration. If required, the beacon will respond to interrogations from anything up to 25 aircraft.

An automatic coding unit is provided for identification purposes, and can be conveniently pre-set to give any combination of any three Morse characters. Either gap coding (keying the circuit) or pulse-width coding can be selected.

The power unit will operate on the ground from 110-240V mains, or from an 80-115V 1000-c/s aircraft supply.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents.

Radio Exports

I WAS very interested in the report given by the Commercial Secretariat of the British Embassy here in Tehran (p. 388, your October 1949 issue). So far as the published report goes it is correct but I should like to amplify it.

This country does not seem to be very important in the minds of British exporters of radio equipment, for they do not appear to have studied conditions sufficiently. It is in the interests of Britain that they should pay more attention, for Iran obtains its dollars from sterling; in fact the country can be considered as a "leakage" of Britain's dollars reserve. This "leakage" can be stopped by making British goods more attractive and less expensive than those obtainable from the American market.

How can this be done?

First by ensuring that importers are backed by a good sales and service organization. It is no use handing out agencies without first investigating whether the importer has the ability to sell and service the equipment. I can assure you that here in Tehran agencies seem to have been handed out indiscriminately.

It is realized that a great deal of responsibility must be placed in an agent's hands. The cost of providing a British representative for each firm would in most cases be uneconomical. Why not appoint representatives of the British Radio Equipment Manufacturers' Association to those countries which, as far as radio is concerned, are considered undeveloped? They could advise agents on the most up-to-date methods of demonstration, window display, advertizing, etc., and give lectures on servicing. In fact their job would be to provide a "welfare" organization for British radio equipment in each country.

My second suggestion is that exporters should undertake market research. In most eastern countries the populations can be separated into two sections, i.e., rich and poor. The poor outnumber the rich by ten to one; but who buys the present high-priced receivers? I leave you to answer. Now, what about the poor? All they want to listen to is their own station; no other station interests them. What they want is a small two-valve battery receiver, one waveband and, most important of all, low priced. I say battery,

because mains electricity is too expensive to install.

Surely a large manufacturing concern could turn out hundreds of this type of set cheaply, for, this problem not only concerns Iran but all other non-manufacturing countries where a large section of the population is poor.

Battery prices must also come down. A 120-V battery here in Tehran costs between three and four hundred rials (bank rate at present ninety to the pound). Something wrong somewhere!

As regards communication equipment, Iran has recently ordered a considerable quantity of American apparatus for airport installations. British equipment was far too expensive and even since the fall of the pound the prices are not equal. Of this I am assured by the radio engineer at the Tehran airport. Why can't British manufacturers get together and, instead of showing equipment at displays in England, go out and display it in the "wilds." On-the-spot demonstrations, even in miniature, with good advice thrown in, do more good than all the "at home" displays.

A. J. LIKEMAN,

(Radio Technician to
Imperial Iranian Air Force)

Tehran, Iran.

"Watering"

THE terminology of any branch of technology is important and so I would appreciate an opportunity to comment on your footnote reply to the query in my letter (January, 1950, issue) on the term "watering."

Three authorities on aspects of sound recording/reproduction, consulted independently, say that they have not heard of the term and it is certainly *not* widely used in film recording.

Apart from the accepted term "flutter," the colloquial and onomatopoeic term "wow" is certainly well known in the field, and the following terms are employed occasionally to describe various types of speed fluctuation: "wow-wows," "whine," "whiskers," "waver," "wobble," "gargle" and "drift."


The Sound Committee of the Society of Motion Picture Engineers in 1947 made an extensive study in an effort to reach standardization of flutter and wow terminology and measuring techniques, subsequently

TRIX

Quality

SOUND EQUIPMENT

BATTERY OPERATED EQUIPMENTS

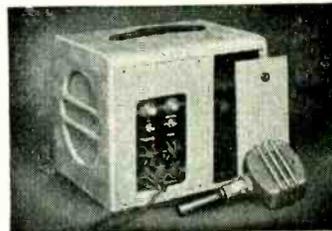


PORTABLE MODEL — B65
A completely self-contained low-power P.A. system.

This exceptionally compact equipment incorporates the amplifier complete with loudspeaker, rotary transformer, 6-volt unspillable accumulator, and microphone with cable, all self-contained in an easily portable case, and provides an output of approximately 5 watts.

The equipment forms a most useful outfit for political meetings, religious gatherings, auctioneers, etc., and numerous other applications where no electric supply mains are available.

Price Complete - - - £29 10 0

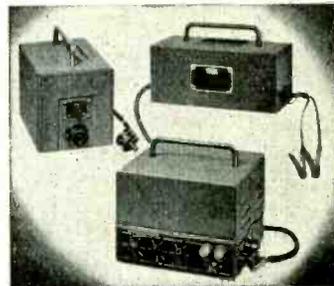

BATTERY — MAINS
Combined equipment Model B619

This model is designed for 12-volt battery operation and can also be used on AC mains by means of a separate plug-in adaptor unit. It operates with our standard moving coil microphones and various types of speakers are available for indoor or outdoor use. Power output when used on mains or batteries, approximately 16 watts.

Full details of these models and others in the large Trix range of equipment available on request.

Send for latest catalogues and price list.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place, Tottenham Court Road,
London, W.1. Phone: Museum 5817
Grams & Cables: "Trixadlo, Wesdo London."

AMPLIFIERS MICROPHONES LOUDSPEAKERS

publishing a long report on its findings (*Journal of the Society of Motion Picture Engineers*, Vol. 49, pp. 147-149, August 1947), but nowhere is the description "watering" mentioned.

Therefore, the derivation and any literature references containing this term that Mr. Berth-Jones can supply would be of great interest to me personally and, I am sure, to the B.S.I. Committee now working on sound recording terminology.

DONALD W. ALDOUS.

Torquay, Devon.

"American Hearing Aids"

I HAVE read with interest the article in your January issue and would like to correct the impression given concerning the newest miniature André-Yardeny type accumulator.

The writer of the article thinks this type of battery has not yet reached the stage where it can be safely entrusted to the public; this view is not shared by my company, who, having subjected these small accumulators to extensive tests over a period of some months, are satisfied that they can provide a reliable and economical low-tension supply for a hearing aid.

The Belclere Monomite P.3 instrument is now available with an accumulator for the l.t. supply, and a charger for the convenience of the user is provided. The accumulator, which costs 9s 6d, should, with ordinary care when recharging, give anything up to two years' service in the instrument.

O. C. LEADBITTER.

John Bell and Croyden, Oxford.

Academic Qualifications

I HAVE experienced some trouble in the past over this matter, and the following may be of interest to your readers.

I am a Graduate of the British Institution of Radio Engineers and hold the Full Technological Certificate of the City and Guilds. I applied some time ago to be placed on the Technical and Scientific Register, but was told that this was for persons with degrees and some professional qualifications, the I.E.E. being included but not the Brit.I.R.E. or the Full Tech. Cert. of the C. and G. I wrote to the Brit.I.R.E., who have been looking into the matter with the appropriate Ministry.

Your correspondent "Bunny" (January issue) may like to know that I obtained employment with the Ministry of Supply as an Assistant Experimental Officer. The rules regarding establishment specify "... B.Sc. ... or the five-year course of the C. and G. ..."

I am struck by the confusion that exists in the industry and the ministries regarding these various qualifications. I found it necessary when applying for posts to carry a copy of the various syllabuses about with me.

The confusion appears to arise concerning the following qualifications:—(1) Grad. Brit.I.R.E. (2) the old C. and G. exams, viz., Radio Comm. and Tech. Elec. 2. (3) The new C. and G. exams, viz., the Final Cert. and the Full Tech. Cert. The latter may include, for instance, Radio 1, 2, 3, 4, Telecomm. Principles 1, 2, 3, 4, 5 and Maths 1, 2, 3, 4, 5.


It appears to me that a real service could be done to young engineers about to start in the industry if the Brit.I.R.E. and the C. and G. could get together and circularize the various Ministries and private firms with a full statement of the position, giving exact details of the syllabuses etc., especially in view of the recent revision of the C. and G. course and their action in calling one of their group certificates "Final" when it is, in fact, followed by the Full Tech. Cert.

H. C. BERTOYA.

London, E.17.

"Easing Impedance Calculations"

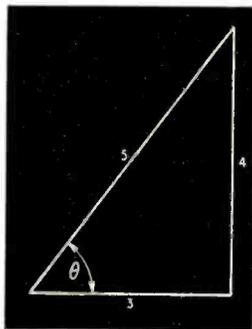I HAVE read with interest the article by M. G. Scroggie in your January issue on how impedance calculations can rapidly be made by



means of the slide-rule and a rearrangement of the original expression. You may be interested to know that for some years I have used a method of slide-rule operation which is almost the same as Mr. Scroggie's, but which may be slightly more simple in practice. This method is derived from the same source, namely, the well-known expression $1 + \tan^2\theta = \sec^2\theta$.

To calculate an impedance value, take the smaller value of either resistance or reactance and set it on the "C" scale to the left-hand index of the slide-rule. Slide the cursor

along to the larger value on the "C" scale. Read off on the "A" scale and add 1, sliding the cursor to this value. The resultant impedance is then indicated on the "C" scale.

The method may be proved by referring to my diagram of the familiar 3,4,5 right-angled triangle. If 3 on the "C" scale is set to the left-hand index and the cursor is moved along to 4, we get $4/3 = 1.33$, which is $\tan\theta$ on the D scale, and $\tan^2\theta = 1.778$ on the "A" scale. To this value 1 is added to give $\sec^2\theta = 2.778$ on "A" and $\sec\theta = 1.667$ on "D." Without further movement of the slide or cursor, $\sec\theta$ is automatically multiplied by 3, which gives the resultant impedance $3 \times 1.667 = 5$ under the hair line on the "C" scale.

ROBERT POLLARD.

London, S.E.26.

Pickup Design

I AM loth to take up more space, but James A. MacHarg's letter (your January issue) and wild statements cannot be allowed to go unchallenged. If he will re-read the article he will find that most of his letter need never have been penned.

I should point out, though, that if a pickup damages or distorts the record surface or groove in any way at all, it will be audible in the reproduction. Therefore a high-fidelity pickup that damages a record cannot be a high-fidelity pickup. Also many readers will know the Danse Macabre recording by Decca that is very popular as a demonstration record. A customer of ours, whose electrical and musical knowledge are beyond question, reports that during eight months' use of the pickup under discussion with a very good amplifier and loudspeaker system, he has played this record, among many others, over forty times without any signs of distortion. This, mark you, on the original sapphire.

T. S. MARSHALL.

London, N.1.

Pickup Damage

IN your December issue J. E. Ellis drew attention to the damage that can be caused to new records during auditions in the shop. Surely the solution is to buy, by post if need be, only from shops which use modern equipment properly.

It is still my view that minimum record wear is achieved with a good lightweight pickup using—dare I say it—miniature thorn needles. If such needles are carefully pointed they seem to be capable of giving reproduction aurally indistinguishable from a new sapphire, and at the same time will play a number of sides of 12-inch records without noticeable deterioration. The Decca "frrr"

gliding tone test record, for example, is quite reproducible at 13-14kc/s with these needles.

The thorn point is best used appreciably "sharper" than the normal sapphire point radius. Although this appears theoretically to involve an undesirable lack of "fit" in the groove, in practice no disadvantage appears to ensue. Mr. C. E. Watts' interesting report on the microscopic examination of records, also in your December issue, mentions that during a test, high-quality reproduction of gramophone records was found not to depend on continuous contact between the sides of the groove and the stylus point.

The reputed defects of thorn needles, namely, comparative pliability and rapid wear, seem much less significant when lightweight, lightly damped pickups with moving parts of low inertia are used.

As the above remarks are based on aural tests, I should perhaps say that my reproducer is a simple moving-coil pickup of my own design, amplified by a *W. W.* Quality Amplifier, feeding a high grade speaker in a reflex cabinet. I realize that such a.f. equipment is not up to the best modern "distortionless" standards, but the differences between the qual-

ity of current recordings seem to be incomparably greater than those between different types of good reproducers, and in my experience completely swamp them. These very wide variations in recording quality, even between the products of the same maker, are very puzzling.

A. M. POLLOCK.

Hatch End, Middlesex.

"Universal" Receivers

In your January issue L. Miller suggests series running of 1.4-volt 0.05-amp valves.

It is widely agreed that this practice is generally unsatisfactory, as filament breakdown becomes a frequent occurrence. This is due to the wide tolerance limits of 1.4-volt filaments which vary very greatly from valve to valve.

I have in mind one particular valve (type DAC32) used in a well-known a.c./d.c.-battery portable: it is not unusual to find 2 volts or more across its filament pins with a consequent drop across the filament pins of the remaining valves in the series chain. Very frequent replacement is found to be necessary.

W. G. EVERSLED.

Gomshall, Surrey.

CLUB NEWS

Birmingham.—At the meeting of the Slade Radio Society on February 17th, M. Moston, of the Winter Trading Co., will speak on "Television Components for the Home Constructor." On the 18th members will be visiting the Birmingham Police Radio Headquarters. Meetings are held on alternate Fridays at 7.45 in the Parochial Hall, Broomfield Road, Erdington. Sec.: C. N. Smart, 110, Woolmore Road, Erdington, Birmingham, 23.

Birmingham.—At a recent meeting of the Radio-Controlled Models Society the Birmingham Area Group was formed. Details of forthcoming meetings are obtainable from the secretary, G. F. Golding, 32, Beechfield Road, Smethwick, Staffs.

Cleckheaton.—At the meeting of the Spen Valley Radio and Television Society on February 1st, H. Clegg (G3FX) will deal with "Unusual Aerials." Meetings are held fortnightly at 7.30 at the Temperance Hall, Cleckheaton. Sec.: N. Pride, 100, Raikes Lane, Birstall, Nr. Leeds.

Enfield.—Meetings of the Enfield Radio Society are now held in St. James' Hall, Durants Road, Ponders End, at 7.0 on Mondays. Sec.: F. A. Ticknell, 10, Cowdrey Close, Enfield.

London.—The next meeting of the London Area Group of the Radio-Controlled Models Society will be held on February 12th at 2.0 at the St. Ermin's Hotel, Victoria, London, S.W.1. Sec.: Lt. G. C. Chapman, Pine Corner, Heathfield, Sussex.

Southall.—A lecture on "Multi-vibrators" will be given by H. K. Winwood to members of the West

Middlesex Amateur Radio Club on February 8th. Meetings are held on the second and fourth Wednesdays of the month at 7.30 at the Labour Hall, Uxbridge Road, Southall. Sec.: H. C. Bostock, 1, Grange Road, Hayes.

Southend.—Exhibits for the Pocock cup which is awarded annually to members of the Southend and District Radio Society for home-constructed equipment will be judged on February 24th. Sec.: J. H. Barrance, M.B.E. (G3BUJ), 49, Swanage Road, Southend-on-Sea, Essex.

Speke.—The recently formed Speke Radio and Television Society now meets on Fridays in the Stockton Wood Road School. Sec.: H. Timms, 101, Western Avenue, Speke, Lincs.

Sunderland.—The chairman of the Sunderland Radio Society, R. V. Duesbury (G3CTE), will address members on "Sensitive Relays" at the meeting on February 8th at 8.0 at Prospect House, Prospect Row, Sunderland. Sec.: C. A. Chester, 38, Westfield Grove, High Barnes, Sunderland.


Whittington.—The recently formed Whittington Radio Club meets each Wednesday at 7.0 in the Angel Inn Club Room, South Street, New Whittington. Sec.: W. Watson, 44, Handley Road, New Whittington, Chesterfield, Derbyshire.

British Amateur Television Club.—The purpose of this club is to encourage activity by amateurs in television. Particulars of the club, which issues a duplicated magazine called "CQ-TV," are obtainable from M. Barlow (G3CVO), Cheyne Cottage, Dukes Wood Drive, Gerrards Cross, Bucks.


ANTIFERRENCE 'Fourway'

The
VERSATILE

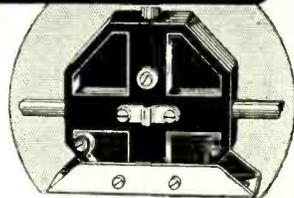
TV AERIAL for
STRONG SIGNAL AREAS
FOR INDOOR USE



ONE TYPE FOUR WAY

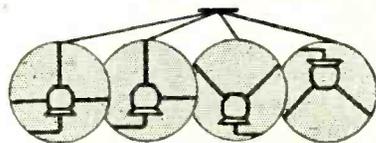

FOR OUTDOOR USE

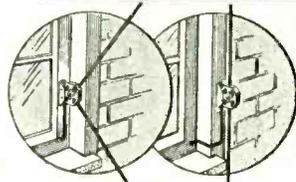

WHEREVER signal strength permits the use of an indoor aerial, the "FOURWAY" has proved itself by fulfilling every demand of the most critical. Its adaptability to widely varying structural requirements enables the "Fourway" to be mounted in the loft or unobtrusively in any part of the house. Although originally designed for indoor mounting, the "Fourway" gives even better performance when mounted outdoors (as illustrated) and is the ideal aerial for flat dwellers and those who find that an indoor aerial provides insufficient signal strength. Suitable for use with every type of television receiver and feeder cable.

LIST PRICE { London Transmission—Model 4-way/L
Midland Transmission—Model 4-way/B

25/-

ANTIFERRENCE
LIMITED

67 BRYANSTON ST · LONDON W.1

RANDOM RADIATIONS

By "DIALLIST"

The Clash of Symbols

AN EMINENT READER of *W.W.* sheds light on the reason why in some French publications batteries appear in circuit diagrams with short, fat positives and long, thin negatives. This arrangement, he tells me, was widespread on the Continent until a certain international conference was held. The British delegates stuck out for the "thin plus"; but one or two European parties refused to play unless they received something in exchange for their acquiescence. After much thought, our people agreed to make the British symbol for a slow-to-operate relay conform to Continental practice, and honour was satisfied! The position now is that, officially, all European countries have adopted the familiar long, thin line for positive and short, thick line for negative. Some publications, however, prefer to assert their individuality by using fat pluses and thin negatives. Another eminent correspondent mentions that books produced in this country are not wholly guiltless of befogging their readers by misusing the battery symbols. In one fairly recent work all the circuit diagrams show h.t. and l.t. batteries apparently connected the wrong way round! Seems a pity, doesn't it, that we can't achieve unanimity on even so

simple a point as this. My sympathies are all with the sorely tried beginner who, having mastered the symbols used in his first book, finds that in the next one he tackles they have just the opposite meanings.

Useful Tip

One of the readers mentioned in the preceding paragraph sends me a convenient way of remembering the polarity of a rectifier as represented in a circuit diagram by its conventional symbol. By "polarity" is meant that of the battery which could be substituted in a power circuit for the rectifier. Here's the tip: Draw the symbol for a single cell, with thin positive and fat negative poles. Whilst thickening-in the negative, permit yourself to indulge in a little mild doodling and shape it into a triangle. The cell now becomes a rectifier with the polarity correctly shown. There's not, of course, any real need to do the doodling. All you have to remember is that in the symbols for cell and rectifier the thin element is the positive and the fat one the negative. That is, naturally, so long as either symbol is correctly used.

Sutton Coldfield

ONE OF THE STRONGEST impressions left by a walk round the

Sutton Coldfield transmitting station is of the neatness of its layout and design. There's no wasted space and no overcrowding. The outside of the building can't be described as beautiful, for it is distinctly severe in style. Nevertheless, it is pleasing to look at because its design is functional. A great deal of thought, clearly, went into making the interior of the world's biggest television station as labour-saving as possible from both the engineers' and the cleaners' points of view.

Teething Troubles

An emergency occurred at Sutton Coldfield at a moment which Fate, in one of her most pernicky moods, must have selected specially to bring home to mortal man that he still can't say with certainty, "At such and such a time I shall do this or that." A second or two before the station was due to make its much-heralded opening transmission there was an arc-over in one of the CAT₂₁ triodes of the output stage of the transmitter. The valve didn't "blow up," as was suggested by some lay publications. It was back in service within ten minutes and, so far as I know, it is still doing its stuff. There have been other breakdowns since—in fact Sutton Coldfield has had more than its share of bad luck in this way—but all have been speedily dealt with.

Stand-by Apparatus

One could, of course, guard against the consequences of almost any kind of breakdown by duplicating every stage of the transmitter and by providing automatic switching arrangements to bring stand-by apparatus instantly into use when this part or that of the normal gear went "phut." When I expressed a certain wonder that duplication hadn't been carried further at Sutton Coldfield, it was pointed out that other parts of the country would take a rather poor view of the B.B.C. television development policy if it installed as stand-by apparatus at Sutton Coldfield bits and pieces that should be part and parcel of the main transmitters in other regions. I hadn't quite realized that, whatever its purchasing power, the B.B.C. must take its allotted place in the long queue of those seeking to acquire equipment. That being so, Sutton Coldfield "Paul" could not be equipped with complete stand-by gear without robbing of their birthright the unborn "Peters" in eagerly awaited new



"WIRELESS WORLD" PUBLICATIONS

	Net Price	By post
RADIO VALVE DATA. Characteristics of 1,600 Receiving Valves	3/6	3/9
RADIO DATA CHARTS, by R. T. Beatty, M.A., B.E., D.Sc., Fifth Edition—revised by J. McG. Sowerby, B.A., A.M.I.E.E.	7/6	7/11
GUIDE TO BROADCASTING STATIONS. Fifth Edition	1/6	1/7
BASIC MATHEMATICS FOR RADIO STUDENTS, by F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. Second Edition	10/6	10/10
RADIO LABORATORY HANDBOOK. Fourth Edition, by M. G. Scroggie, B.Sc., M.I.E.E.	12/6	12/11
TELEVISION RECEIVER CONSTRUCTION. A reprint from "Wireless World" (London area only)	2/6	2/9
SUPERHETERODYNE TELEVISION UNIT. A reprint from "Wireless World"	2/6	2/9
WIRELESS DIRECTION FINDING. By R. Keen, M.B.E., B.Eng.(Hons.), Fourth Edition	45/-	45/9

A complete list of books is available on application

Obtainable from all leading booksellers or from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1.

television service areas. And even as a child one learnt to appreciate what happened when birthrights were bartered away. I could at this point perpetrate a joke about Esau and 'E didn't see—but I refrain.

Signs of the Times?

THE OTHER EVENING I had a telephone call from a friend who lives nearby. Rather diffidently, he asked whether there had been anything in the six o'clock news about something or other—what, exactly, it was I don't remember, though it was, no doubt, very important at the time. "Your wireless set misbehaving?" I asked, when I'd given the desired information. "As a matter of fact," he said, "we haven't a wireless set now." He told me, rather sheepishly, that they'd found just before Christmas that the old wireless set was on its last legs. To recondition it would have cost more than it was worth. They had decided to have a new receiver when their eldest young hopeful pointed out—and kept on pointing out—that it wouldn't cost all that much more to have a television set. Having at length given way to his entreaties, they were now discovering with no small chagrin that the television can supplement the wireless set, but certainly cannot replace it. I'm hoping that the epidemic won't spread to others of my friends, for I get quite enough telephone calls as it is. And am I acting strictly within the terms of my receiving licence if I "publish" the gist of broadcast programmes over the telephone to inquirers?

SOLDERING ALUMINIUM

ONE of the reasons for the difficulty of soldering aluminium is its affinity for oxygen and the fact that in air a thin transparent film of oxide forms on the surface immediately after cleaning.

To disrupt this film continuously and thus expose the pure metal to the action of the solder, Mullard Electronic Products, Century House, Shaftesbury Avenue, London, W.C.2, have developed soldering iron (Type E7587), in which the bit is maintained in ultrasonic vibration by means of a magnetostriction transducer powered from a valve oscillator unit. The bit is heated by a conventional resistance winding and of the normal copper type.

Solders with a tin-zinc base are recommended and no flux is required. Ordinary tin-lead solders can be used, but may give rise to subsequent electrolytic corrosion.

Quality ELECTRONIC COMPONENTS

FAMOUS ALL OVER THE WORLD

THE EXPERIENCE OF 25 YEARS
BEHIND EVERY COMPONENT

NEW PRODUCTS OF INTEREST



List No. P.440



List No. F.155



List No. C.R.21

List No. P.440—New valve-top connector of modern appearance and design. Moulded in RED or BLACK. "Standard" base.
List No. P.441—"Octal" base version.

List No. F.155—New moulded panel-mounting 1-pole fuseholder for Bulgin "PAK" and all 1/4" dia. x 1 1/2" cartridge fuses, which select with bayonet-engaging vibration-proof front knob.

List No. C.R.21—New croc. clip for gripping fine wire without damaging it. Shown open to demonstrate special jaws. Nickel-plated.
List No. C.R.23—Brass, self-finish version.

NEW SWITCHES

List No. S.450—Small rotary button-knob switch in polished plastic. Offers continuous "On-Off" Right-hand rotary action.

List No. S.451—New moulded type for all 24v. max. circuits. Snaps ON, and OFF, with a click. Silver-plated contacts.

List No. S.264—Popular 1-pole C-O switch, for all 0-250v., 2A max. circuits. Guaranteed—like all BULGIN switches—for at least 25,000 operations.


List No. S.220—Push-pull 1-pole M-B action; pull for OFF. For 6A at 0v., 4A. at 110v., and 3A. at 250v. circuits. Polished plastic knob unacrews for mounting.




List No. S.451



List No. S.450

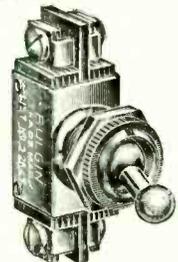

List No. S.264

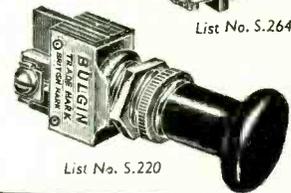

List No. S.220

DISTINCTIVE MOULDINGS

These famous BULGIN knobs are of distinctive design and greatly enhance the appearance of all apparatus. Those shown are but a few of the many models illustrated in the BULGIN CATALOGUE. All are designed for firm grip and accurate adjustment, and are fitted with a hardened and well-sunk 4 B.A. grub screw for standard 1/4" dia. shafts. Normally finished in highly-polished BLACK, with white-filled "hair-line". This range includes some of the most popular BULGIN components.



List No. K.58



List No. K.324



List No. K.111



List No. K.18



List No. K.6

EVERY COMPONENT GUARANTEED

SEND FOR NEW ILLUSTRATED CATALOGUE 1/- post free

BULGIN

A. F. BULGIN & CO. LTD.
BYE-PASS ROAD, BARKING
Telephone: R1Ppleway 3474 (5 lines)

Manufacturers' Products

New Equipment and Accessories for Radio and Electronics

Checking Mobile Equipment

TWO useful pieces of v.h.f. test apparatus for tuning and checking mobile radio installations have been introduced by Mullard Electronic Products, Century House, Shaftesbury Avenue, London, W.C.2. One is a radiation monitor (Type GME₅₀₁/X) consisting of a current transformer and crystal rectifier housed in an insulated case with a centre hole attached to a long handle, which, when slipped over the whip aerial used on vehicles and "Walkie-Talkies," gives a measurement of aerial radiation.

The actual indicator is a separate 0-500 micro-ammeter, which is used also with the other item, an r.f. tuning indicator (Type GFE-506/X). Basically it consists of a short length of concentric line, which is inserted in the aerial feeder at the transmitter end. The line incorporates an r.f. probe and rectifier and measures the voltage on the inner conductor without disturbing the impedance of the line.

This unit is housed in a metal box and is fitted with co-axial sockets for the feeder and plain

sockets for the meter connections.

Both indicators can be used with transmitters up to 20 watts output and for frequencies of from 65 to 200 Mc/s.

The aerial monitor costs £3 19 6 and the tuning indicator £2 17 6. The price of the micro-ammeter is £6 13 6.

Television Pattern Generator

MANUFACTURED by Murphy Radio, this television pattern generator, Type TPG11, provides an r.f. output modulated with a test pattern and sync pulses conforming to the B.B.C. waveform. It therefore enables a receiver to be adjusted in the absence of any transmission so that subsequently it needs nothing beyond the proper setting of the contrast control for proper reception. It should thus be of great value to dealers who can install and adjust sets with its aid outside the hours of television transmission.

On the r.f. side, the generator consists of an oscillator covering 40-70 Mc/s and an amplifier which is suppressor-grid modulated by the required waveform. The output is taken through a 10-db-step ladder attenuator and a continuous control to a coaxial cable. The r.f. output is of the order of 40 mV maximum and up to 65-db attenuation is provided.

The output can be unmodulated, modulated with a 250-c/s square wave or modulated with sync pulses and a pattern. These waveforms are generated by a series of multivibrators and flip-flops which start with a 20,250 c/s multivibrator. Correct frequency is ensured by locking to the mains frequency.

The pattern produced consists of

four equally spaced horizontal black bars and one broad vertical black bar. In addition, there are some 26 very narrow vertical grey bars.

Because the sync waveform is correct, a receiver can be adjusted for proper interlace and aspect ratio, while linearity can be adjusted by setting the controls for equal spacing of the pattern bars. By setting the r.f. output at the value corresponding to the field strength in the area, even the contrast control can be set approximately.

The test pattern waveform and the sync pulses are available for video testing and test sockets are provided in case adjustments to the instrument are needed. The generator weighs 30 lb and the power unit, which is separate, 20 lb. The approximate overall dimensions are 18½ in tall by 12½ in by 12 in for the generator and 12 in by 7 in by 7½ in for the power unit. It costs £140 and is sold by F. Livingstone Hogg, 65, Barnsbury St., Islington, London, N.1.

MANUFACTURERS' LITERATURE

CATALOGUE (No. 180) of radio components from A. F. Bulgin & Co., Bye Pass Road, Barking, Essex.

Synopsis of "Cintel" electronic instruments for research and industry from Cinema-Television, Ltd., Worsley Bridge Road, Lower Sydenham, London, S.E.26.


Catalogue of H.M.V. television receivers for the Midland transmitter frequencies, and an illustrated leaflet describing the Model 2103 automatic record player, from the Gramophone Company, Hayes, Middlesex.

Folder giving list of "Somersetford" transformers and chokes, including components specified in the Williamson High Quality Amplifier, and a brochure of audio output transformers, from Gardners Radio, Somersetford, Christchurch, Hants.

Data sheet of Marconi receiving valves from the Marconiphone Company, Hayes, Middlesex.


"Industrial Photocells"—a 20-page booklet of data on vacuum and gas-filled types, with circuit recommendations—from Mullard Electronic Products, Century House, Shaftesbury Avenue, London, W.C.2.

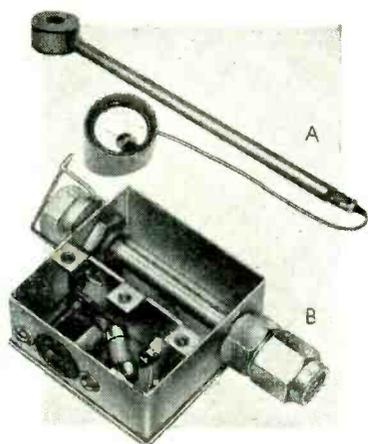Illustrated leaflets describing the Type D-365-A; Duddell oscillograph; Type A-18r-A inductance bridge; Type D-101-A frequency bridge and a universal unit conductivity bridge, from Muirhead & Co., Beckenham, Kent.



The Mullard radiation monitor with micro-ammeter is shown above at A, while B depicts the tuning indicator with its cover removed.

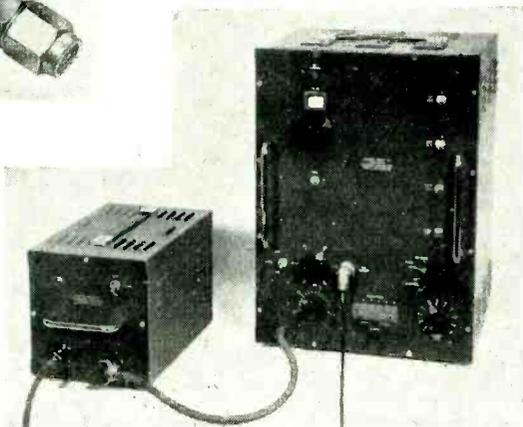Murphy Radio television pattern generator with its power unit.



Another worthy addition

TO THE RANGE OF

'AVO' Test Instruments

A Signal Generator of wide range and accuracy of performance, designed for use in the laboratory or by the service engineer. Turret coil switching provides six frequency bands covering 50 Kc/s to 80 Mc/s.

50 Kc/s—150 Kc/s	1.5 Mc/s—5.5 Mc/s
150 Kc/s—500 Kc/s	5.5 Mc/s—20 Mc/s
500 Kc/s—1.5 Mc/s	20 Mc/s—80 Mc/s

Note these Attractive Features:

Stray field less than $1\mu\text{V}$ per metre at a distance of 1 metre from instrument. General level of harmonic content of order of 1 per cent.

Direct calibration upon fundamental frequencies throughout range, accuracy being better than 1 per cent. of scale reading.

45in. of directly calibrated frequency scales with unique illuminated band selection giving particularly good discrimination when tuning television "staggered" circuits.

Of pleasing external appearance with robust internal mechanical construction using cast aluminium screening, careful attention having been devoted to layout of components with subsidiary screening to reduce the minimum signal negligible level even at 80 Mc/s.

Four continuously attenuated ranges using well designed double attenuator system.

Force output 0.5 volts.

Internal modulation at 400 c/s., modulation depth 30 per cent., with variable L.F. signal available for external use.

Mains input 100-250 volts A.C., 40-60 c/s.

Battery Model available having same general specification and covering 50 Kc/s—70 Mc/s., powered by easily obtainable batteries.

Fully descriptive pamphlet available on application

Sole Proprietors and Manufacturers:

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON • S.W.1 Telephone: VICTORIA 340419



Mains Mode

£25

Battery Model

£24



WILCOX ...First Choice for Transatlantic Airline Communication

The whirling propellers of the international airlines make daily mockery of the vast space of the Atlantic Ocean. Intercontinental passengers and cargo come and go hourly at New York, Miami, Gander, Shannon, Ireland, and Lisbon, Portugal. These European and American airports are equipped with modern long-range, multichannel WILCOX Transmitters.

Oslo, Norway, and Stockholm, Sweden, use WILCOX Transmitters as basic communications

equipment, and radio beacon service is provided at Reykjavik, Iceland, by WILCOX Type 96-200 Transmitters.

Thus, the giant airliners of the world's major airways are protected in flight and guided safely to the runways of Europe's and America's principal ports of entry.

WRITE TODAY...for complete information on air-borne, ground station, point-to-point, or shore-to-ship communications equipment.



WILCOX ELECTRIC COMPANY
KANSAS CITY MISSOURI



Heralding the
latest advancement
in electronic
equipment



SQUARE WAVE GENERATOR

This instrument provides a square wave of amplitudes from 5mV to 50v peak to peak calibrated, at a repetition frequency of from 5c/s to 150Kc/s. The mark/space ratio is 1:1 and the wave is flat to within less than $\pm 1\%$ top and bottom. Alternative positive and negative pulses of 0.05, 0.1, 0.2, or 0.3 μ Secs can also be obtained with amplitudes of from 5mV to 5v peak to peak.

For further particulars—please write to:—

CINEMA - TELEVISION LIMITED

FOREMOST IN THE MANUFACTURE OF


- Counters & Chronometers • Metal Detectors • Oscilloscopes • Photo-Electric Cells
- Cathode Ray Tubes • Geiger-Muller Tubes • Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S·E·26

Telephone: HITHer Green 4600

Northern Agents:
F. C. ROBINSON & PARTNERS LIMITED
308 Deansgate, Manchester 3

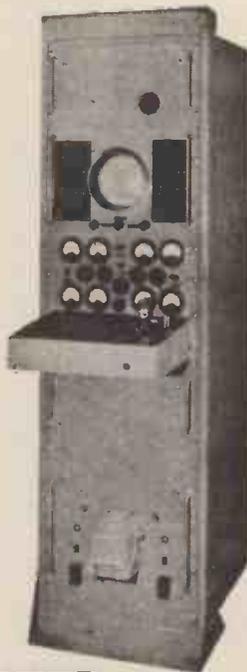Scottish Agents:
ATKINS, ROBERTSON & WHITEFORD LIMITED
100 Torrissdale Street, Glasgow, S.2



**UNIVERSAL
VALVE
TESTER**

This instrument will display on a cathode ray tube the Anode volt/Anode current curves for any receiving type valve. Curves for eleven different grid voltages are shown simultaneously and a calibration pattern is displayed enabling the voltage and current characteristics to be checked.



REGISTERED TRADE MARK

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.



PREMIER MIDGET RADIO KIT. Due to greatly increased production we are now able to offer this kit at a greatly reduced price. Including an attractive Bakelite case, 12in. long x 5in. wide x 6in. high. The valve line up is 6K7, 6J7, 6V6 and a Selenium Rectifier in the A.C. model; and 6K7, 6J7, 25A6 and a Selenium Rectifier in the A.C./D.C. model. Both are for use on 200 to 250 volt mains. The dial is illuminated, and the receiver presents a very attractive appearance. Coverage is for the medium and long wavebands. Complete kit of parts with brown or Ivory cabinet and diagrams, **£4/19/6**, inc. Purchase Tax.

PREMIER MIDGET SUPERHET KIT. This powerful Midget Superhet Receiver is designed to cover the short-wave bands between 15 and 50 metres and the medium wavebands between 200 and 557 metres. Two models are produced, one for 200-250 volt A.C. mains, and the other for 200-250 volts A.C. or D.C. mains. Both are supplied with the same plastic cabinet as the TRF Receiver. The A.C. valve line-up is 6K8, 6K7, 6Q7, 6V6 and a selenium rectifier. The A.C./D.C. line-up is the same, with the exception of the output valve which is a 25A6. The dial is illuminated, making a very attractive receiver. Complete kit of parts with brown or Ivory cabinet and diagrams **£6/19/6**, inc. Purchase Tax.

PLASTIC CABINETS. as illustrated above. In Brown or Ivory 17/6.

COLLARO AUTOMATIC RECORD CHANGERS. Type RQ500 Rim-drive. Plays nine 10in. or 12in. records. A.C. 100/250 v., with High Fidelity Magnetic or Crystal Pick-up, **£10/15/-**. With Sapphire Stylus, **£11/8/4**.

COLLARO GRAMOPHONE UNITS. High grade Rim-drive Motors, complete with Pick-up and Automatic Stop-Start. A.C. 100/250. With Magnetic Pick-up, **£5/3/2**. With Crystal Pick-up, **£5/17/7**.

COLLARO GRAMOPHONE UNITS AT NEARLY HALF PRICE. Motor, Tone arm and Pick-up in one unit. Auto Stop-Start, variable speed, 12in. turntable. Induction Motor for 100/250 v., 60 cycles, with Magnetic Pick-up, **£6/6/-**. With Crystal Pick-up, **£7/4/8**.

CONRAD GRAMOPHONE MOTORS. A reliable Rim-drive Motor for A.C. 100/250 v. operation, **£2/17/6**.

GOVERNMENT SURPLUS MAINS TRANSFORMERS. All are for use on 230 volt 50 cycle Mains.
 Type Price.
 42 500-0-500 v. 170 mA. 4 v. 4 a. 25/-
 44 10 v. 5 a., 10 v. 5 a., 10 v. 5 a. 35/-
 53 250-0-250 v. 60 mA., 5 v. 2 a., 6.3 v. 2-3 a. 15/-
 54 275-0-275 v. 60 mA., 5 v. 2 a., 6.3 v. 2-3 a. 15/-
 55 250-0-250 v. 100 mA., 5 v. 2 a., 6.3 v. 3-5 a. 17/6

WILLIAMSON AMPLIFIER KIT. We can supply the Kit of Parts for the latest version of this famous amplifier complete in every detail for **£10/10/-**.

WILLIAMSON AMPLIFIER OUTPUT TRANSFORMERS to specification, **63/-**. Mains Transformers, **45/-**.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. All parts to construct an eliminator to give an output of 120 volts at 20 mA. and 2 volts to charge an accumulator. Uses metal rectifier. **35/-**.

TELEVISION AERIALS. The K.A. Loft Aerial for those close to the transmitter. London or Birmingham frequency, **20/-**.

WALL FIXING DIPOLE, 32 6.

WALL FIXING DIPOLE with reflector, **60/-**.

See our new catalogue for complete range.

V.C.R.97. O.R. Tubes. New and tested to give full-size picture, 35/- each.
 The following O.R. Tubes for callers only:—
 VOR516A 40/- VOR522 15/-
 VOR517E 30/- VCR511B 60/-
 VCR140 50/-

TRANSMITTING AND SPECIAL PURPOSE VALVES.
 705A 10/- RL18 (OV1197) 5/-
 861 10 808 25/-
 832 10/- HY114B (OV3505) 15/-
 V868 (OV1068) 6/6 MR300E (OV3568) 15/-
 EL266 (CV15) 40/- 1816 5/-
 805 17/6 8012 10/-
 KB/8 (CV160) 60/- 845 5/-
 E1191 (CV12) 60/- 1625 5/-
 EHTT (CV19) 60/- U19 (OV187) 6/6
 VT30 (CV1080) 7/6 956 (CV649) 3/6
 U17 (OV1118) 5/- N82 (OV1199) 5/-
 E1232 (CV32) 20/- CV97 (Kivstrom) 5/-
 PT25H (CV1046) 5/- O150 (OV1072) 7/6
 VU133A (CV54) 6/6 1826 (CV1755) 3/6

ELECTRON MULTIPLIER PHOTO CELL TUBES.
 Type 931A. Brand new. Guaranteed, 30/-.

T.V. WHITE RUBBER MASKS. We can now supply a specially designed White Rubber Mask for 6in. O.R. Tubes at 7/6 each.
 9in. White Masks, 9/6. 12in. White Masks, 15/9.

SUPER QUALITY TELEVISION MAGNIFYING LENS. To suit 5in., 6in. or 7in. Tubes. Increase picture size considerably, 25/- each.

FRAME AND LINE COIL ASSEMBLY. Suitable for all standard Magnetic Tubes, 12/6 each.

PERMANENT MAGNET FOCUS POTS. Available for all Tubes, 15/- Please state Tube used.

THE NEW PREMIER 1950 CATALOGUE
 contains all the newest TV Kits, Components, Aerials, Tubes, etc., in addition to thousands of Radio Bargains.
Now ready—3d.

SUPER MOVING COIL MIKE AND STAND. We have purchased the entire stock of a famous Manufacturer of P.A. Equipment at a very low price, and are offering a £15/- Super Moving Coil Mike, with a chromium plated finishing stand to match. The list price of the stand was **£3/3/-**.


WE OFFER THE PAIR AT 79/6. LESS THAN HALF THE USUAL PRICE.

THE NEW PREMIER TABLEGRAM.



A modern Tablegram, incorporating many new features. Covers Medium and Long Wavebands. Operates on 200-250 v. A.C. Mains. A high-fidelity pick-up and the latest Collaro electric gram. motor ensure excellent record reproduction, **£19/19/-**, including Purchase Tax.

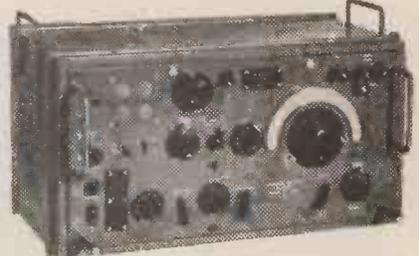A LARGE NEW PURCHASE ENABLES US TO OFFER AT A LOWER PRICE THAN EVER £107. ONE OF THE ARMY'S FINEST COMMUNICATIONS RECEIVERS. (See "W.W." August, 1945.)



9 valves, R.F. amp. osc. Frequency Changer, 2 I.F.s. (465 kc.), 2nd Detector, A.V.C. Al. amp. B.F.O. A.C. mains, 100-250 v. or 12 v. accum. Frequency range 17.5 to 7 Mc/s. 7.35 Mc/s to 2.9 Mc/s. 2.0 to 1.2 Mc/s. Monitor L.S. built in. Complete. Write for full details. Price **£12/12/-**, plus 21/- carriage and packing.

BATTERY CHARGERS. All incorporate Metal Rectifiers. Transformers are suitable for 200-250 v. A.C. 50 cycles.
 Cat. No. Price.
 2002. Charges 6-volt Accumulator at 1 amp. Resistance supplied to charge 2 v. Accumulator **£12/6**
 2003. Charges 12-volt Accumulator 1 amp. **£17/6**
 2004. Output 15 v. 4 a. Variable Resistance and Meter **£3/15/-**
 2005. Output 15 v. 6 a. Variable Resistance and Meter **£5/-**
 2007. Output 30 v. 5 a. Variable Resistance and Meter **£6/-**
 2009. Output 24 v. 3 a. Variable Resistance and Meter **£4/5/-**

BATTERY CHARGER KITS. All incorporate Metal Rectifiers. Transformers are suitable for 200-250 v. A.C. 50 cycles.
 Cat. No. Price.
 2002. Charges 6-volt Accumulator at 1 amp. Resistance supplied to charge 2 v. Accumulator **£12/6**
 2003. Charges 12-volt Accumulator 1 amp. **£17/6**
 2004. Output 15 v. 4 a. Variable Resistance and Meter **£3/15/-**
 2005. Output 15 v. 6 a. Variable Resistance and Meter **£5/-**
 2007. Output 30 v. 5 a. Variable Resistance and Meter **£6/-**
 2009. Output 24 v. 3 a. Variable Resistance and Meter **£4/5/-**

ALUMINIUM CHASSIS. 16 S.W.G. Substantially made of bright aluminium with four sides.

	Price
7 x 3 1/2 x 2 1/2 in.	3/3
9 1/2 x 4 1/2 x 2 1/2 in.	4/-
10 x 8 x 2 1/2 in.	5/6
12 x 9 x 2 1/2 in.	6/8
14 x 9 x 2 1/2 in.	7/3
16 x 8 x 2 1/2 in.	7/6
20 x 8 x 2 1/2 in.	7/11
22 x 10 x 2 1/2 in.	10/-
10 x 9 x 3 in.	6/3
12 x 10 x 3 in.	6/10
14 x 10 x 3 in.	7/11
16 x 10 x 3 in.	8/8
20 x 10 x 3 in.	10/-

MAINS NOISE ELIMINATOR KIT. Two specially designed chokes with three smoothing condensers with circuit diagram. Cuts out all mains noise. Can be assembled inside existing receiver. 6/- complete.

CO-AXIAL CABLE. Super quality cable, consisting of a centre copper core, a polyvinylresin type insulator, a flexible screen, a weather-proof P.V.C. outer cover. Just the thing for Television lead-in, super mike cable, etc., 80 ohms impedance. Cat. No. G.755, 3d. per foot.

GRAMOPHONE AMPLIFIER KIT. Consists of Complete Kit of Parts for a 2 1/2 watt. Mains-operated 2-stage Amplifier for use with any type of pick-up. Volume and tone controls are incorporated. Output impedance is 3 ohms. Cat. No. AMP147. Price complete, 65/- For 200-250 v. mains with valves and diagrams.

SECTIONAL WHIP AERIAL. Seven sections which plug into each other making an aerial 14ft. long. Thinnest section 1/4 in. diam. thickest section 1/2 in. diam. Weather-proof enamel. 3/6 each complete. INSULATED BASE for above, 2/6 each.

METER KIT. A FERRANTI 500 MICROAMP M/G METER, with separate High Stability, High Accuracy. Resistors to measure, 15, 60, 150 and 600 volts D.O. Scale length 1 1/2 in. diameter 2 1/2 in. 10/- the complete kit.

5 KV. ELECTROSTATIC VOLTMETER. Scale length 3 1/2 in., flush mounting, 1/2 in. diameter, **£2/10/-**.

207, EDGWARE ROAD, W.2 Phone : AMBassador 4033 AND AT —

All POST ORDERS to 167, LOWER CLAPTON ROAD, LONDON, E.5. 'Phone : AMHerst 4723

Terms of Business : Cash with order or C.O.D. over £1. Send 2d. stamp for list.

EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS

BRANCHES

PREMIER RADIO COMPANY

MORRIS & CO. (RADIO) LTD.

THE BIRMINGHAM VERSION OF THE "PREMIER" TELEVISOR KIT

is now ready. The price is the same as the London Model

—£17 - 17 - 0—

As is usual in all Premier Kits every single item down to the last Bolt and Nut is supplied. All chassis are punched and layout diagrams and theoretical circuits are included.

Five Easy to Assemble Kits are supplied :—

VISION RECEIVER with valves, carriage 2/6.....	£3 13 6
SOUND RECEIVER with valves, carriage 2/6	£2 14 6
TIME BASE with valves, carriage 2/6.....	£2 7 6
POWER SUPPLY UNIT with valves, carriage 5/-.....	£6 3 0
TUBE ASSEMBLY , carriage and packing 2/6.....	£2 18 6

This unit includes the VCR97 Tube, Tube Fittings and Socket and a 6in. P.M. Moving Coil Speaker with closed field for Television. The Instruction Book costs 2/6, but is credited if a Kit for the complete Televisor is purchased.

Any of these Kits may be purchased separately ; in fact, any single part can be supplied. A complete priced list of all parts will be found in the Instruction Book.



20 Valves are used, the coils are all wound and every part is tested. All you need to build a complete Television Receiver is a screw-driver, a pair of pliers, a soldering iron and the ability to read a theoretical diagram.

A well-made walnut finish

PEDESTAL CABINET

is available at £5/10/0 plus 7/6 carriage and packing.

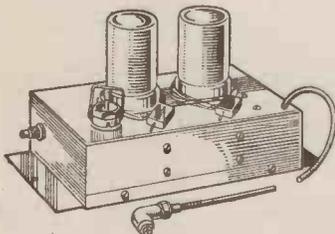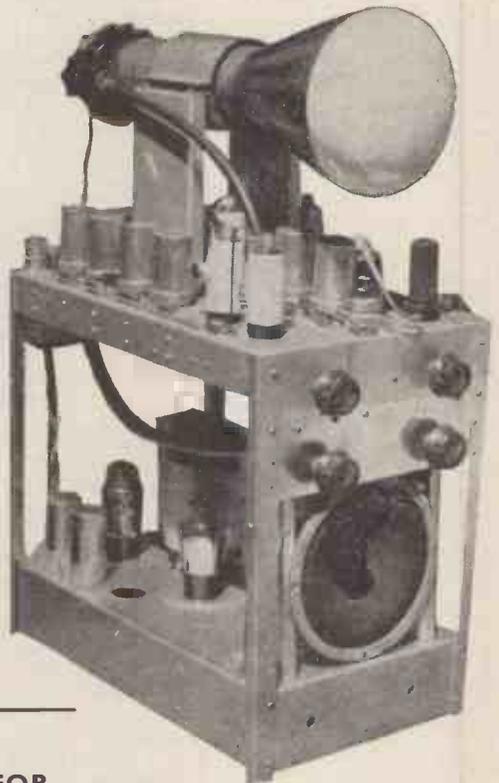Working Models can be seen during transmitting hours at our Fleet Street and Edgware Road Branches.



PRE-AMPLIFIER FOR FRINGE RECEPTION AREAS

We can supply the complete kit of parts to make this wide band width Pre-Amplifier, using 2 EF54 Pentodes. Powered by the TV Kit, it is completely screened. With all parts, valves, chassis, diagrams, etc., 27/6. All parts available separately.

PLEASE STATE IF THE LONDON OR BIRMINGHAM MODEL IS REQUIRED.

AT
-152-153, FLEET STREET, E.C.4 Phone : CENTral 2833
 All POST ORDERS to 167, LOWER CLAPTON ROAD, LONDON, E.5. 'Phone : AMHerst 4723
 Terms of Business : Cash with order or C.O.D. over £1. Send 2d. stamp for list.
207, EDGWARE ROAD IS OPEN UNTIL 6 p.m. ON SATURDAYS

MAINS TRANSFORMERS

Ordinary—E.H.T.—Special.
All transformers are suitable for 200-250 v. 50 cycle mains, are fitted with primary screens, fully impregnated and complete with all necessary clamps, etc.

260-0-260 at 80 mA. 6.3 v. at 4 amp. 5 v. at 3 amp. Half shrouded drop through, 15/-.

260-0-260 at 60 mA. 6.3 v. at 3 amp. 5 v. at 2 amps. Half shrouded drop through. Price 13/9.

350-0-350 at 80 mA., 4 v. at 6 amps. 4 v. at 3 amps., drop through or upright mounting, primary having an additional tapping for 110 v. mains. Obviously a useful replacement type for old type receivers. 16/6.

350-0-350 at 100 mA., 6.3 v. at 5 amps., 5 v. at 2 amps. Fully shrouded upright mounting, 19/6.

260-0-260 at 60 mA. 4 v. at 4 amps. 4 v. at 3 amps. Half shrouded drop through. Price 13/9.

235-0-235 at 60 mA. 6.3 v. at 3 amp., 5 v. at 2 amps. Fully shrouded upright mounting, 15/- Primary has an additional tap for 110 v.

Filament Transformer, 6.3v. 1 1/2 amps, upright, 6/-.

350-0-350 at 160 mA., 5 v. at 3 amps., 6.3 v. at 6 amps., 6.3 v. at 3 amps. Fully shrouded upright mounting, 36/-. Note this transformer and next two below are the correct specification for the "Inexpensive Televisor."

250-0-250 at 100 mA., 5 v. at 3 amps., 6.3 v. at 6 amps., 27/6.

2,500 v. at 5 mA., 4 v. at 1.5 amp., 202 v. at 2 amp., 27/6.

4 KV. at 5 mA., 2 v. at 2 amp., potted with insulators, 67/6.

Special combined transformer designed to be suitable for Televisor or oscilloscope using a 6in. tube VCR97, etc.

400-0-400 at 150 mA., 2.5 KV. at 5 mA., 6.3 v. at 6 amps., 6.3 v. at 6 amp., 6.3 v. at 2 amp., 4 v. at 1 amp., 4 v. at 2 amps., 5 v. at 3 amp., 70/-.

IMPORTANT

Postage must be included, orders up to 10/-, 1/-, over 10/-, 1/6. £3 and over post free unless otherwise stated.

PARTS FOR TELEVISORS



FRAME AND LINE COIL ASSEMBLY.

Perfectly made by a very famous maker, for standard type magnetic tubes, 9in., 10in., 12in. or 15in., we have a limited number only, the price is 16/6, and cannot be repeated once these are cleared, so please act quickly.

PERMANENT MAGNETIC FOCUSING UNITS. No current drain—for all makes of tubes—patented method of adjusting the gap, giving really clean pictures and even focus of whole of the tube free. Price 16/6 each.

P.M. FOCUSING
for
clear pictures

R. F. E. H. T.
Non-Lethal

R.F. E.H.T. We were so pleased with the quality of this unit that we have taken up the entire output of the manufacturer, the voltage can be adjusted to make it suitable for working 9in., 12in. or 15in. tubes, the unique design and vacuum impregnation combine to give a trouble-free unit which will give years of satisfactory service, and, of course, the big point about the R.F. E.H.T. is that it is not lethal, the size is only 4 1/2 x 3 1/4 x 4in., price complete ready to operate, 65/-.

£16 FOR A MAGNETIC TELEVISOR (and H.P. terms if you wish). This Televisor is suitable for use with 9, 10, or 12in. magnetic tube (not included in the £16). No Ex-Government units are used, you start off with all basic components, brand new and guaranteed, except for the valves which are Government Surplus though again guaranteed. This Televisor was demonstrated at Radiolympia, and we will demonstrate to you if you can call during transmitting time. All parts available separately for those already having some of them. Detailed point-to-point wiring and instructions for novice or expert, 5/-. Explanatory leaflet free. When ordering booklet please state whether for Birmingham or London.



£15/5- FOR A COMPLETE TELEVISOR, this is our famous Mark II which is doing good service all over the country. Two Ex-R.A.F. Units are used, and these save you a good deal of work. These and all the other parts including the loudspeaker needed to make the working televisor are included in the £15/5-. Technical knowledge is necessary because you have to work from theory diagrams. 24 pages of data are included free if you buy the Kit, or alternatively will be supplied at 7/6 per copy.

"50 PITFALLS FOR TELEVISION CONSTRUCTORS." If you are having difficulty in getting a perfect picture, then this publication may solve your problem. The price is only 2/6 post free.

WHITE PLASTIC MASK. Designed to fit a 6in. electrostatic tube, VCR.97, etc. This will give a professional look to your home-built Televisor. If yours is a bigger than usual picture, the size of the opening can be enlarged to suit your own needs. The price is 7/6 post free.

MAGNIFYING LENS. De Luxe type. The lens which is really designed to give optical perfection. First-class quality and workmanship throughout. Guaranteed against any discoloration of the special oil content. Price 39/6, postage, packing and insurance 5/-.

AERIALS. Indoor type—for fitting in loft. Very simple in installation. Full instructions and fixing clips, etc., supplied with every one. Order "SNAPPY AERIAL KIT," price 15/-.

VCR.97 CATHODE RAY TUBES. Brand-new in original cartons. Price 35/-, carriage and insurance paid. Buy a spare now while they are still available at this silly price.

PRE-AMPLIFIER FOR TELEVISION. Complete conversion details using RF27 (ex-R.A.F. Unit). Unit with details 22/6, nothing else needed, suitable for sound or vision. Details separately, 2/3 post free.

CO-AXIAL CABLE. 80 ohm thin, 10d. per yard, 80 ohm Government surplus thick, 8d. per yard. Twin balanced feeder, 4d. per yard.

E.H.T. CONDENSERS. .1 mfd. 2.5 K.V., 2/6. .1 mfd. 5 K.V., 4/9. .1 mfd. 7 K.V., 13/6. .02 mfd. 8 K.V., 3/9.

DECOUPLING CONDENSERS. Very small bakelite moulded mica insulation, .001 mfd. or .0005 mfd., 6/- per dozen.

SPARES

ELECTROLYTIC CONDENSERS

8 mfd. 350 v.	1/6
16 mfd. 350 v.	1/11
25 x 25 mfd. 200 v.	3/11
8 mfd. 150 v.	1/3
25 mfd. 25 v.	1/6
25 mfd. 50 v.	1/-
50 mfd. 12 v.	10d.
50 mfd. 50 v.	1/9
10 mfd. 25 v.	10d.
2 mfd. 450 v.	1/-
4 mfd. 450 v.	1/3
8 mfd. 450 v.	1/11
16 mfd. 450 v.	2/8
8 x 8 mfd. 450 v.	3/4
8 x 16 mfd. 450 v.	3/4
16 x 16 mfd. 450 v.	3/9
16 x 8 x 24 mfd.	4/2
8 mfd. 500 v. BR.850	2/6
16 mfd. 500 v. BR.1650 ...	3/6

P.M. SPEAKERS.

	with less	
Size	trans.	trans.
2 1/2 in.	—	10/6
3 in.	—	8/6
3 1/2 in.	12/3	10/6
6 1/2 in.	12/6	10/6
8 in.	14/6	12/6
10 in.	18/6	16/6
12 in.	—	39/6

ENERGISED SPEAKERS

Size 6 1/2 in. with 700 ohm field and output transformer (Rola), 11/6. Less trans., 9/6.

Size 8 in. 2,000 ohm with output transformer, 15/6.

I.F. TRANSFORMERS

465 kc/s, iron dust cored standard size can, 6/9 pair.

465 kc/s, iron dust core, midjet size can, 12/6 pair.

465 kc/s, air cored small size can, 5/9 pair.

OUTPUT TRANSFORMERS

Standard pentode matching to 3-4 ohm speech coil. Standard size, 3/3, small size 3/-, midjet size 3/6.

Multi-ratio, standard size 4/6.

TUNING CONDENSERS

Small size
2 gang .0005
with long
spindle, 4/6.
Ditto, with
trimmers, 6/6.
Midjet size 2

gang .00035 with dust cover and trimmers, 7/6.

4 gang .0005 with built-in trimmers, fitted into screening compartment, but easily removable, 3/9.

IRON CORED CHOKES.

200 mA. 10 henry	10/-
200 mA. 5 henry	6/-
200 mA. 3 henry	5/-
80 mA. 10 henry	4/6
80 mA. 5 henry	4/-

MISCELLANEOUS ITEMS

8 kv. sleeving, 3/- doz. yds.
B7G ceramic valve holder, 1/3.
Ditto, EF50, 9d. Pax EF50, 6d.
Int. Oct. Valve holder Amphenol, 6d. Pax, 3d. Miniature look pots., 1/6.



(2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDXX.

SPANNER KIT

For servicing all types of British and American gear. You have needed these spanners in the past and you will continually need them in future. Total of 50 precision tools:—

- 5 Whitworth ring spanners 1/4 to 3/4
- 5 American ring spanners, 1/4 to 3/4
- 6 Double-ended Whitworth 1/4 to 3/4
- 6 Double-ended American 1/4 to 3/4
- 3 Whitworth obstruction wrenches, 1/4 to 3/4
- 3 American obstruction wrenches, 1/4 to 3/4
- 6 B.A. Ignition spanners 1 to 6 B.A.
- 6 American Ignition spanners.
- 4 Small B.A. Fitters' spanners.
- 3 Small American Fitters' spanners.
- 3 Small Whitworth Fitters spanners.

This complete kit, £5/17/6.

B.A. SOCKET SPANNERS.



Covering sizes 0-6 B.A. and with double ended wrench as illustrated. A really good set which will help you with those nuts in awkward corners, price 5/6 complete.


POLISHED B.A. SPANNERS.

Covering sizes 1 to 6 B.A., these are so made to have a straight and a right angle end for each B.A. size. 6/- set.

QUADRANT-TYPE SCRIBERS.

For marking out chassis these are the ideal tool, normal price 7/6, our price while they last, 3/9.

PUSH-BUTTON SWITCH UNIT.

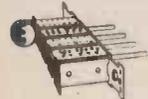

For three waveband and mains on/off complete with knobs. 1/6.

EGG INSULATORS.

For all sorts of aerials including T.V. 1 1/2" long x 1" x 1". 4d. each. 3/6 doz.

TELEPHONE JACK PLUGS



As illustrated 7d. each, sockets to suit, 10d. each.

METAL RECTIFIERS.

Selenium 250 v. 100 ma., 4/3.

5-WAY PORCELAIN CONNECTOR BLOCKS

Hundreds of useful applications, 1/3.

33 R.P.M. GRAM MOTORS
Ex-Government but in good condition only a few left, £3 each.

IMPORTANT

Postage must be included orders up to 10/-, 1/-, over 10/-, 1/6. £3 and over post free unless otherwise stated.

HALF LIST PRICE

Radiogram unit by a very famous maker, comprising centre drive induction motor, type AC47 with speed regulator, auto-stop and magnetic pick-up all mounted on full size unitplate. Brand-new in manufacturer's cartons. Limited quantity, £4/16/6, plus 3/6 carriage and insurance.

SELECTED SURPLUS (Ex-Govt.)

10 K.V.A. ALTERNATOR SETS. Ideal for country house or if you are setting up a workshop or laboratory in a remote place, then these are an ideal unit because in addition to the main output of 10 K.V.A. 230 v. 50 cycles 3 phase there is also 1.5 K.V.A. 230 v. 400 cycles. These alternator sets are complete with exciter, voltage regulators, switch board, frequency meters, amp. meters, and iron-clad switch fuses for output. They are mounted on stout angle-iron stand and are complete with "Vee" belt pulley, the alternator is designed to run at 1,500 r.p.m., but being belt driven they can, of course, be driven by an engine of almost any speed, as the difference can be adjusted by the size of the pulley on the engine. Unused but storage soiled. Price is £85 each, ex works.

TYPE 6 INDICATOR. As specified for the "Wireless World" oscilloscope (reprint of data 9d.). Also for the "Inexpensive Telesvisor" (booklet 1/6), and the Mark I Telesvisor (Constructors envelope 2/6). These indicators are brand-new, packed and sealed in manufacturer's original crates, they contain VCR.97 Cathode Ray Tube, 4 EF50 valves, 3 other valves, and hundreds of useful components, including wire-wound pots. Price is only £4/10/-, plus carriage and packing 7/6.

10 VALVE 1 1/2 METRE SUPERHET. Ideal for conversion into a Midlands or London region Telesvisor. These contain 6 valves type SP61, and 1 each RL7, RL16, and EA50. 6 I.F. Transformers of 12 mc/s, 4 mc/s band width, and hundreds of other useful components. Complete with three 11 mm. formers, price 59/6, plus carriage and packing 5/-. These receivers are unused, being in original wrappings.

RADAR RECEIVER TYPE 3084A. These require only the smallest of modification to make them into a sound and vision telesvisor. Main contents are valves: 7 EF50, 2 VR136, 1 VR137, 1 HVR2, 1 R3, 1 V507, 1 EA50, wire-wound variable resistors, small 80 v. A.C. motor, and dozens of useful components, resistors, condensers, etc. Brand-new, in original manufacturer's packing and transit case, price 59/6, carriage 5/-.

RECEIVER R.3585. An ideal unit for conversion to T.V. in the London Service Area, as it contains a "PYE" 45 mc/s I.F. Strip, and valves as follows: 7 EF50, 4 SP61, 8 EF36, 1 EB34, 1 EF39, brand-new—only 90/- carriage, etc., 7/6.

RECEPTION SET BP413. Made by Philco. 4 valve battery superhet. Valve line-up, frequency changer, I.F. amplifier, double diode triode and output pentode. Complete with all valves and 5in. P.M. speaker. Provision for phone output incorporated. Cabinet size 10 1/2 in. x 7 1/2 in. x 7 1/2 in. Controls are volume, ON/OFF switch, and tuning. Frequency coverage 1.4 to 4 mc/s, 75-222 metres (Trawler, 80 and 160 metres Amateur bands). Only £3/19/6, plus 5/- carriage and packing.

TRANSMITTING AND SPECIAL VALVES

ALL BRAND-NEW IN ORIGINAL CARTONS, MOSTLY AMERICAN MAKE.

813	47/6	866A	10/6	807.....	7/6
6L6	10/6	6A3	12/6	2A3	9/-
TZ40	27/6	CV57	30/-	8011	18/6
5Z3	13/6	6N7	6/6	832.....	16/6
GU21 (CV5)		VS68 (STV280/40)		PT15 (VT104)	
VT25 (DET25)		VU508 (CV1508)			

Many other types available including Magnetrons, Klystrons, Thyratrons, etc., etc. Send us your enquiries.


HOUSE TELEPHONES

Suitable for intercommunication between offices, workshops, stores, garages, big houses, kitchens, etc. Each station consists of normal size Bakelite handsets and desk or wall-mounting cabinet with built-in selector switch, buzzer and push. All stations can communicate with one another independently. Each installation is absolutely complete and internally wired. 3-station installation complete with 50 yards 5-core cable £6/10/-. 4-station installation, complete with 50 yards 6-core cable, £8/10/-. 2-station installation, complete with 25 yards 4-core cable, £3/17/6.




ELECTRIC HEATERS

Heavy cast iron work totally encloses the elements, so these are 100% safe even in confined spaces, just right for your radio den, garage, office, shop, etc. 900 watt (heavy) model, 19/6, plus 5/6d. carriage. Other models available are: 750 watt, 500 watt, 250 watt, all these are 23/6 each, plus 4/6 each carriage. The 250 watt model used as a foot-warmer keeps legs and body warm for less than a farthing per hour.

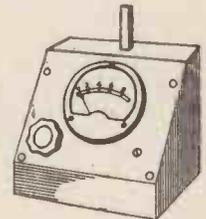

SHORT TURNS COIL TESTER

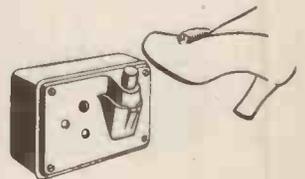You know that it is almost an impossibility to test for shorted turns in I.F. Transformers, Coils, L.T. Transformers, etc., with an ordinary ohmmeter. Our mains operated shorted turns coil tester will reveal these faults in a second. An essential instrument in all coil-winding shops as it will test for continuity at the same speed. £6/10/-.



15 amp. shuttered switch plug, bakelite moulded surface mounting type, made by very famous maker, made to B.S.S. 6/- each.




PRECISION EQUIPMENT (2) ELECTRON HOUSE, Windmill Hill, RUISLIP MANOR, MIDDX.



DIRECT RECORDING ON DISK

THE year 1930 marked a vital point in sound recording progress. It was then that Mr. C. E. Watts, founder of the M.S.S. Recording Co. Ltd., produced the first cellulose lacquer-coated disk—an achievement which paved the way to—indeed made possible—to-day's high-fidelity sound reproduction. That same pioneering spirit, consistently prompting every endeavour of the M.S.S. organisation, has produced a range of sound recording equipment which is acknowledged supreme wherever there is an appreciation of true fidelity in sound reproduction. Apart from its "quality" performance, every item of M.S.S. equipment—whether a complete recording channel or a cutter head—is built to a standard of technical excellence which assures long-maintained efficiency under the most exacting operating conditions. In this connection it is interesting to mention that the first disk recorder used by the B.B.C. for broadcast programmes and supplied by M.S.S. in 1933, is still in use in their training school.

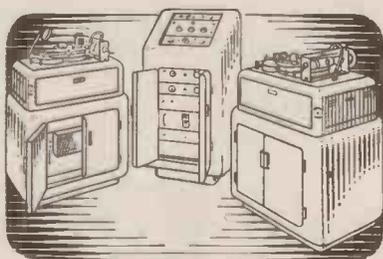Illustrated below is a typical M.S.S. Studio Recording equipment, but the M.S.S. range includes Portable Studio Recording equipment, Portable Recorders for the professional and also home recording equipment. Full details will gladly be sent on request.



M.S.S. RECORDING CO., LIMITED
POYLE CLOSE, COLNBROOK, BUCKS
Telephone: COLNBROOK 115


A NEW

FIELDEN TECHNIQUE

*in micro - measurement
and control*

FOR ANY INDUSTRIAL OR RESEARCH
PROBLEM RESOLVABLE INTO MINUTE
ELECTRICAL CAPACITANCE CHANGE

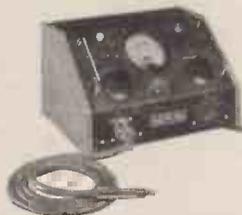*ACTUATION BY PROXIMITY of solid or
liquid conductors or insulators to an electrode
terminating a co-axial cable.*



**THE FIELDEN PROX-
IMITY METER—SEN-
SITIVITY 0.01 mmf—**indicates minute capacitance changes, whether caused by very small mechanical displacement or dielectric change it measures, for instance, strains in structures, it gauges components to less than 0.00001in., monitors sheet,

foil and wire sizes, measures liquid and other levels precisely, monitors dimensions and compositions, compares dielectric properties of non-conducting, liquids etc. It does what is impossible mechanically and, in many fields, surpasses all other micro-measurement methods.

THE FIELDEN TEKTOR—SENSITIVITY



0.25 mmf — is a unique stable, high-speed capacity relay which solves many problems of counting, temperature control, level control of liquids and solids, and so on where simple direct-switching is impossible.

Please send for specification FE/4 to the SPECIALISTS
IN INDUSTRIAL ELECTRONIC EQUIPMENT

Fielden

(ELECTRONICS) LIMITED


HOLT TOWN

MANCHESTER

Telephone: ARDwick 2619.

INSIDE INFORMATION

*about the
switch that
is superior*

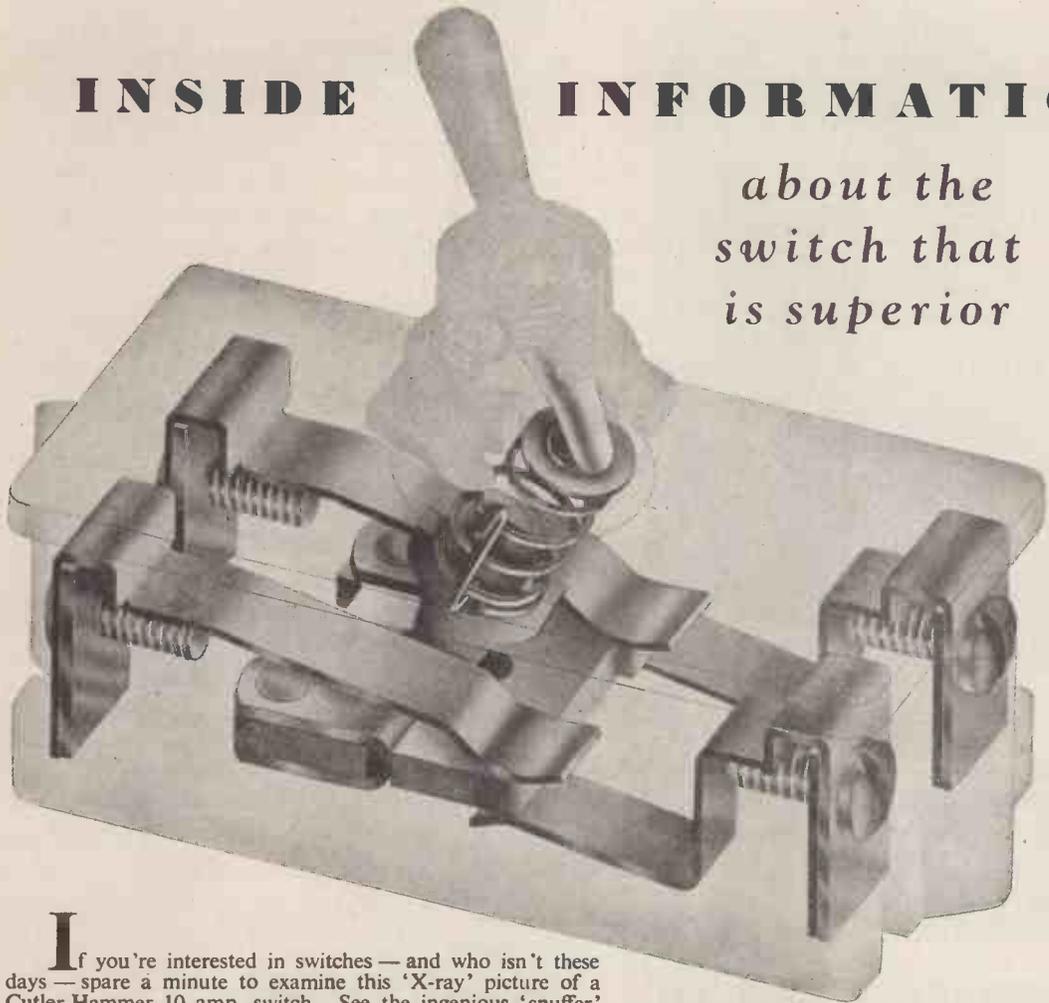

If you're interested in switches — and who isn't these days — spare a minute to examine this 'X-ray' picture of a Cutler-Hammer 10 amp. switch. See the ingenious 'snuffer' action — an original C-H feature — which eliminates pitting and arcing when breaking heavy loads. Note also that the silver alloy moving contact is self-aligning and self-cleaning. And finally observe the substantial area of the spring-leaf fixed contacts to ensure cool working.

Now if you're looking for a robust switch for a real job of work, here's the fellow to do it. May we submit samples and details of the wide range of operating mechanisms available?

NOTE THESE C-H. FEATURES

- Famous Cutler-Hammer "Snuffer" action
- Spring leaf fixed contacts ● Silver alloy Bridging contact ● Long helical actuating spring ● One piece moulded case ● Insulated toggle lever ● Large headed terminal screws ● Quick make and break mechanism.

Nominal ratings 6 or 10 amps. 250 volts — suitable for A.C. and D.C. service. Available in a wide range of single and double pole types operated by lever, plunger, slider or trigger, with screw terminals. Enquiries invited.



Other British N.S.F. products include: 'Oak' Rotary, Push-button and Slider switches; Carbon and wire-wound potentiometers for Television and Radio applications; Paper tubular capacitors; Wire-wound resistors.



BRITISH N·S·F CO. LTD.

KEIGHLEY · YORKS

Phone: Keighley 4221/5. Grams: ENESEF, Keighley

LONDON OFFICE: 9 Stratford Place, W.1. Phone: Mayfair 4234

Licensees of Igranic Electric Co. Ltd. for the above products of Cutler-Hammer Inc. Milwaukee, U.S.A.



... more about THE CORNER RIBBON



Price £83 0 0 ex-works.
Full details available on request.

★ Research . . .

Subjective group listening tests carried out in direct comparison with live instruments under carefully controlled conditions.
Investigation covering 22 different directional characteristics with single and multiple point sources, with and without reverberation.
Investigation of various cabinet enclosures including the effects of such enclosures on middle as well as bass frequencies.
An investigation between large area plane wave sources and spherical wave point sources for the reproduction of various types of programme material.
Investigation into the subjective importance of phase shift in two unit systems.
The relative importance of damping, in particular with relation to twin unit systems with crossover.
The optimum apparent distance of sound source for various types of programme material.

★ Development . . .

High frequencies radiated and reflected from above and behind to provide large area source on reverberant programmes yet retaining point source radiation from "dead" studio programmes.
The development of a high frequency ribbon unit giving aperiodic response from 2 k/cs to supersonic frequencies.
An extended bass response without deleterious effects at middle frequencies.
A directional characteristic which is effectively uniform yet retaining slight forward sense for realism in speech reproduction.

★ Result . . .

A loudspeaker which is arousing tremendous enthusiasm among musicians and technicians alike and which we believe provides reproduction of the highest quality yet achieved.



18 TOTTENHAM COURT ROAD, LONDON, W.1

Tel: MUSEum 2453

Tel: MUSEum 4539

Shop hours: Monday-Friday 9—5.30. Saturday 9—1

FULL MAIL ORDER FACILITIES Please add postage

"VIEWMASTER" (post free)

Complete booklet on "Viewmaster" including constructional details and blueprints. 5/-.

Complete set of T. C. O. Condensers as specified, £8/15 0.

Complete set of Whiteley components including L/S, £8/5 0.

Complete set of Plessey components as specified, £5/12/6.

Complete set of Westinghouse components as specified, £3/2/6.

Complete set of Weirite coils and choke as specified, £1 2/0.

Complete set of Morganite fixed resistors as specified, £1/6 9.

Complete set of Carbon Potentiometers type Q as specified, 9/-.

Complete set of Bulgin components as specified, 12/6.

Complete set of Belling & Lee components including fuses, 8/6.

G.E.C. Neon Lamp type G, 2 9.

9in. Cathode Ray Tube Mullard MW22/14C, Mazda ORM92, or G.E.C. 8504 (carton extra), £11/6/10.

Mullard EF50, 21/4.

Mullard EBC33, 11/7.

Mazda 6K25, 12/10.

Oeram KT61, 12/10.

Mullard EB91, 12/10.

Mullard EL33, 12/10.

Mazda 6P28, 21/4.

QUALITY COMPONENTS A.D.S. QUALITY AMPLIFIER

Full constructional details of our 4½ watt inexpensive quality amplifier are now available including circuit diagram layout pictures. Post free, 10d.

Complete set of components for above amplifier including drilled chassis, cabinet, knobs, etc. Carriage free, £8/10/0.

Complete amplifier constructed and tested. Carriage free, £9/9/0.

LOUDSPEAKERS

Wharfedale super 8 C/S speech coil impedance 2/3 ohms or 12/15 ohms. Suitable for refined quality up to 4 watts (post 1/3), 75/-.

Wharfedale Golden Unit. Peak input 8 watts, cone dia. 10in. The most popular of the better quality reproducers (post 1/6), 75/-.

As above with cloth surround (post 1/6), 85/-.

Wharfedale W10/C8. The well known 10in. speaker with the cloth suspension. Power handling capacity 5/8 watt dependent on mounting (post 1/6), 27.

Goodmans 12in. 15 watt P.M. dust proof speaker. Ideal for small halls, etc. (carriage 2/6), £6/15/0.

Goodmans Axiom 12, 12in. Twin cone high fidelity speaker (carriage 2/6), £8/8/0.

Goodmans Axiom 22. The latest 20 watt High Fidelity 12in. Loudspeaker (carriage 2/6), £12/13/0.

PICKUPS

Connoisseur Pick-up, a high impedance pick-up giving approx. .5 volts at the secondary of the special coupling transformer. Level frequency response from 50 to 1,000 cps. Below 50 cps a rising frequency response gives a bass resonance near 25 cps. Above 1,000 cps the output falls steadily giving a loss of approx. 5 db at 3,500 cps and 9 db at 12,000 cps. Price complete with transformer incl. P.T., £4/10/5.

Wilkins & Wright Pick-up. A light weight moving coil pick-up with an overall response of 5 cps to 15,000 cps flat within 3 db from 30 cps to 9,000 cps. Coil impedance 5 ohms. Output impedance from special transformer 100,000 ohms. Approx. needle pressure 1 oz. adjustable within ½ oz. to 1 oz. Price complete with transformer, £7/10/7.

NEEDLES (all prices include P.T.)

Connoisseur miniature needles 20 per pkt., 2/10.

Columbia Chrome (normal size), 10 per pkt., 1/9.

Columbia 99 Miniature needles, 10 per pkt., 3/7.

Where excellent quality reproduction is essential . .

. . the Metrovick


AUDIO AMPLIFIER

is the instrument to use

This instrument is designed to give excellent quality reproduction with the added advantages of being a self-contained unit, portable and attractive in appearance. Thus it will prove ideal for Public Address work, educational authorities and similar organisations.

SPECIFICATION.

- Supply :** 200/250V 50 c/s single-phase ; consumption approximately 170 VA for full output.
- Input :** Gramophone 0.2V for full output. Microphone 0.02V for full output. The two circuits can be mixed as required.
- Impedance :** 7 ohms, 15 ohms and 45 ohms.
- Output :** 20 watts with negligible distortion.
- Tone Control :** Continuously variable.
- Response :** ± 1 db from 30 to 15000 c/s at zero position of tone control.
- Controls :** These are recessed to avoid damage and are illuminated when in operation.
- Dimensions :** $18\frac{1}{2}'' \times 8\frac{1}{2}'' \times 10\frac{1}{4}''$.
- Finish :** The instrument is housed in an attractive steel case, stove enamelled in cream or blue as desired. A leather carrying handle is fitted.

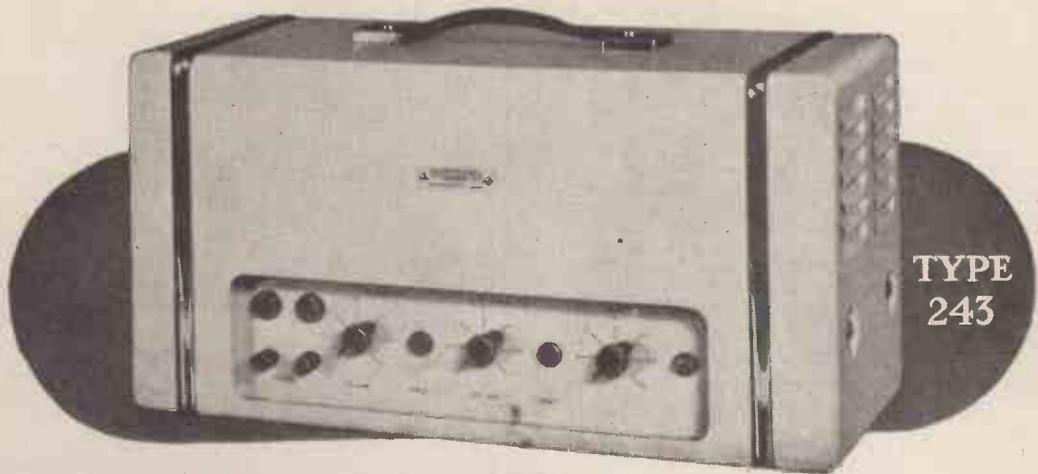

METROPOLITAN-VICKERS ELECTRICAL CO. LTD.

TRAFFORD PARK, MANCHESTER 17

**10 to
310
mcs.**

Light Weight
36 lbs.

Negligible
Stray Field.

Frequency
Calibration 1%

Modulation
30% sine wave
1,000 and
pulsed 50/50
square wave
at 1,000

Attenuation
Max. error at
300mcs. ± 2dB

Precision
Slow-Motion
Dial.

Wide Range.
10-310 mcs.

Compact
12½ in. x 13½ in.
x 7½ in.

Dual-Power
Supply
200-250v., 40-100
80-v., 40-2,000



**“Advance”
Signal Generator
type D.1.**

This “ADVANCE” Signal Generator is of entirely new design and embodies many novel constructional features. It is compact in size, light in weight, and can be operated either from A.C. Power Supply or low-voltage high-frequency supplies.

An RL18 valve is employed as a colpitts oscillator, which may be Plate modulated by a 1,000-cycle sine wave oscillator, or grid modulated by a 50/50 square wave. Both types of modulation are internal, and selected by a switch. The oscillator section is triple shielded and external stray magnetic and electrostatic fields are negligible. Six coils are used to cover the range, and they are mounted in a coil turret of special design. The output from the R.F. oscillator is fed to an inductive slide wire, where it is monitored by an EA50 diode. The slide wire feeds a 75-ohm 5-step decade attenuator of new design. The output voltage is taken from the end of a 75-ohm matched transmission line.

The instrument is totally enclosed in a grey enamelled steel case with a detachable hinged lid for use during transport.

Price £80

Prompt Delivery.

Write for descriptive Leaflet.

ADVANCE COMPONENTS, LTD.
BACK ROAD, SHERNHALL STREET,
WALTHAMSTOW, LONDON, E.17

Telephone: Larkwood 4366-7-8

The
MAGNAVISTA
TELEVISION LENS

**IT IS QUALITY
THAT COUNTS**

Viewing quality is the essence of television enjoyment and viewing quality is ensured by MAGNAVISTA which, in lens manufacture, means angle of view, minimum distortion, clarity of picture as well as maximum enlargement. This is why the MAGNAVISTA viewer always says MAGNAVISTA magnification is television perfection.

PRICES

Type	Tube	£	s.	d.
A.7	6"	3	3	0
A.1, A.2, A.4, A.5, A.8, A.9 A.9a, A.10, A.11 and A.12	9"	4	14	6
B.1, C.1	10" & 12"	5	5	0
D.1	15"	5	15	6
A.3 (Universal)	9"	6	16	6
B.2 (Universal)	10"	7	7	0
C.1x	12"	7	7	0

Subject to Trade Discount

METRO PEX LTD

Head Office:
38, Gt. Portland St., London, W.1
(*Phone: Museum 9024-5)

Midlands Depot:
Kings Heath Stn., Birmingham, 14
(*Phone: Highbury 2765)

Danny Kaye

Starring in the Samuel
Goldwyn Technicolor
Production,
"A Song Is Born"



USING HIS

Soundmirror

MAGNETIC TAPE RECORDER

*Made in England. Protected
by British & Foreign Patents
and Patents Pending.*

Full details from the Manufacturers, or Demonstrations by
Appointment.

THERMIONIC PRODUCTS LTD.
MORRIS HOUSE, JERMYN STREET,
HAYMARKET, LONDON, S.W.1


Telephone: WHItchall 6422 (5 lines)

With this one compact and reasonably priced Instrument you are completely equipped for all Sound Recording and Reproducing.

The Soundmirror is a high-fidelity Instrument which records and reproduces on reels of inexpensive magnetic tape Speech, Music, and every other sound audible to the human ear. Each reel gives a half-hour's uninterrupted playing. Short recordings can be cut and joined together. Playback is immediate. Recordings are permanent or if desired, can be automatically erased as new items are recorded.

The Soundmirror is simple to operate—Single finger-tip control for Play, Record, Fast Re-wind or Fast Forward requirements.

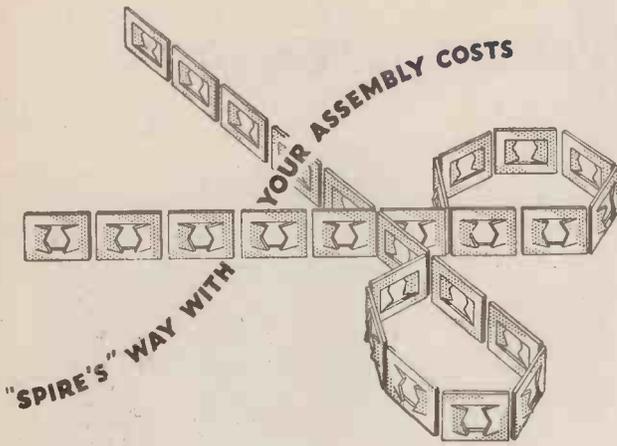Built-in jacks enable the Soundmirror to be used in conjunction with radio or public address equipment.




Assembly costs come down when you employ Spire Speed Nuts. They're so much easier and quicker to put on; such a saving in time, trouble and money. Spire hold tighter—it's the unique double-spring locking action that does it. Their large bearing surfaces are ideal for vitreous enamelled assemblies, glass, plastic, etc., to say nothing of just plain sheet metal. Engineers with assembly problems are invited to write for more information about Spire Speed Nuts—fastest thing in fastenings.

Spire

Regd.

SPEED NUTS

THAT'S
FIXED
THAT

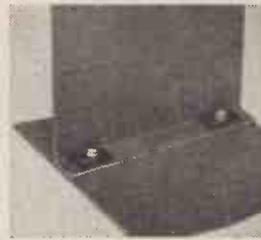

The SNP type replaces machined nut and lock washer. No spanner is necessary to hold these streamlined nuts designed for use with machine screws and sheet metal screws.

Enquiries to: Simmonds Aerocessories Ltd., Byron House, 7-8-9 St. James's St., London, S.W.1. Head Office & Works: Treforest, Glamorgan

15

RECORD PLAYERS

by

Richard Allan



C.D.M. With variable speed regulator, automatic start and stop, 12" cloth covered turntable. Price £15 : 1 : 0
Tax Paid

R.D.M. (illus.) This powerful rim driven model is fitted with fool-proof start and stop mechanism beneath the unit plate. Price £12 : 0 : 8
Tax Paid

C.D.U.M. Universal model operating on A.C. or D.C. Current. Price £20 : 15 : 8
Tax Paid

FROM ALL
GOOD DEALERS

There is a most comprehensive range from which to choose

RICHARD ALLAN RADIO LTD.

BAFFLETTE HOUSE · BATLEY · YORKS

Makers of the famous BAFFLETTE Extension Speakers

THE NEW "75" SIGNAL GENERATOR Model 1



Frequency Range
110 to 50 Megacycles.
With calibrated extension covering London, & Midland Television frequencies, at over 60 Megacycles.

Modulation
400 C.p.s. sinusoidal.

Attenuator
5-step ladder, with fine control.

Output
Switched via single test-lead, RF. and AF. 1 volt Max.

External Radiation
Less than 1 micro-v.

For A.C. mains operation. Complete with Standard Dummy Aerial.




LIST **12 1/2** GNS. SUBJECT.

EXCELLENT PERFORMANCE
ATTRACTIVE APPEARANCE
LOW PRICE
HIGH EFFICIENCY


INQUIRIES INVITED

SPHERE RADIO LIMITED
HEATH LANE, WEST BROMWICH, ENGLAND

DISC-SEAL TRIODES for Ultra High Frequencies

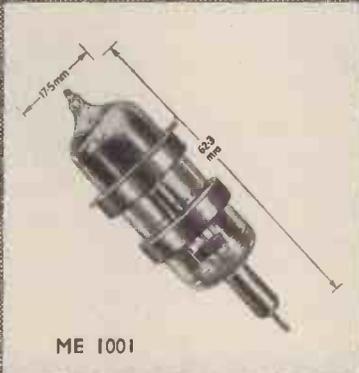

ME 1001

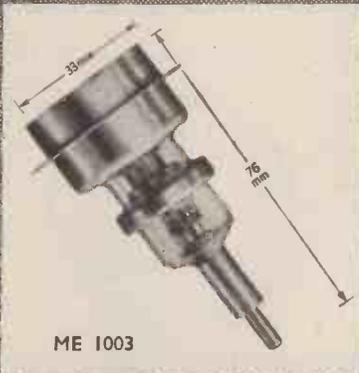

ME 1003

Mullard NEWS LETTER

If you are not already on the mailing list for this service of advance information on new valves, please write to us for full particulars on your business letterheading.



INDUSTRIAL POWER VALVES · THYRATRONS · INDUSTRIAL RECTIFIERS · PHOTOCELLS
FLASH TUBES · ACCELEROMETERS · CATHODE RAY TUBES · STABILISERS AND
REFERENCE LEVEL TUBES · COLD CATHODE TUBES · ELECTROMETERS, ETC.

For U.H.F. links, local oscillators, and wide band applications such as multi-channel communication systems and radar altimeters, frequencies up to 1500 Mc/s or even 3000 Mc/s are often required. The Mullard Disc-Seal Triodes have been designed specifically for such purposes.

In the ME1001, adequate cooling and low inductance are combined in the design of the anode and grid discs to give an anode dissipation of 10 watts and an upper frequency limit (as an oscillator) of 3750-3500 Mc/s (8-8.5 cm).

The ME1003 is basically similar in design to the ME1001, but the larger electrodes permit an anode dissipation of 25 watts. However, the larger clearances necessary to obtain this value, limit the upper frequency to 2500 Mc/s.

PRINCIPAL CHARACTERISTICS

	ME 1001	ME 1003
Heater Voltage (V)	6.3	6.3
Heater Current (A)	0.4	1.0
Max. Anode Voltage (V)	350	500
Max. Anode Dissipation (W)	10	25
Max. Anode Current (mA)	50	200
Max. Peak Anode Current (mA)	150	500
Power Output (W)	0.5 (at 3000 Mc/s) 3.5 (at 500 Mc/s)	6 (at 1500 Mc/s) 20 (at 430 Mc/s)
Mutual Conductance (mA/V)	6	20
Amplification Factor	30	30

Mullard

THERMIONIC VALVES & ELECTRON TUBES

Webb's RADIO

NEWS about FOUR EDDYSTONE RECEIVERS

EDDYSTONE '680' Communications Receiver

Uses fifteen modern valves in advanced circuitry. Designed primarily for professional communications requirements and critical amateur use. Coverage 30 Mc/s to 480 Kc/s (10 to 620 metres) continuous. Export orders take priority **BUT WEBB'S HAVE A FEW '680' RECEIVERS IMMEDIATELY AVAILABLE FOR THE HOME MARKET.** Fully informative brochure free on request.

EDDYSTONE '680' RECEIVER—Price £89.5.0
(No Purchase Tax)

EDDYSTONE '750' Communications Receiver

An amateur and professional receiver offering a new approach to selective reception in congested frequency bands. Uses eleven valves in a double superheterodyne circuit with variable selectivity. Covers 32 to 1.7 Mc/s and 1465 Kc/s to 480 Kc/s. **SUPPLIES OF THE '750' EXPECTED VERY SHORTLY,** please ask Webb's for full technical details.

EDDYSTONE '750'—Price.....£49.10.0
(No Purchase Tax)

EDDYSTONE '670' Marine Receiver

Designed primarily for ship's cabin listening, working from A.C. or D.C. 110-200-230 volts. (Incidentally good results are still obtained when mains are down to 90 volts). **DEPENDENT ON EXPORT ALLOCATIONS A SMALL NUMBER OF '670' RECEIVERS ARE AVAILABLE FOR THE HOME MARKET.** The home listener requiring an efficient and reliable A.C.-D.C. receiver is invited to enquire from WEBB'S as to availability. Our sea-going friends know WEBB'S make a speciality of supplying to the London Docks at short notice.

EDDYSTONE '670' — Price£39.7.6
Plus Purchase Tax£8.19.2

EDDYSTONE '710' All World Six Receiver

An overseas receiver, six valves, including R.F. Stage and push-pull output. For operation from a 6 volt accumulator, a feature being the low current drain of 2.5 amperes. **AVAILABLE EX STOCK AT WEBB'S FOR OVERSEAS ORDERS, ALSO LIMITED ALLOCATION FOR HOME SALES.**

EDDYSTONE '710' — Price£39.7.6
Plus Purchase Tax£8.19.2
(Purchase Tax is not applicable if exported).

Webb's Radio, 14, Soho St., Oxford St., London, W.1.

Phone: GERrard 2089. Shop Hours: 9 a.m.—5.30 p.m. Sats. 9 a.m.—1 p.m.

ACRU

neon
indicator
lamps



ONE-HOLE
FIXING

In handsome Black Bakelite holder complete with series resistance and leads, to show Pink, Red, Amber or Green, on 230v or 400v AC or DC. Specially designed for easy assembly in ½-inch mounting hole.

Send now for full details, prices and terms.

- For SWITCHBOARDS,
- INDICATOR PANELS,
- MACHINE CONTROLS,
- HEATING APPLIANCES, ETC.

THE ACRU ELECTRIC TOOL MFG. CO. LTD.
123, Hyde Road, Manchester, 12.

Ardwick 4284.

N.L.

You are offering

*** PEAK PERFORMANCE**

with the



**GRAMPHIAN
D.P.I.**

THE IDEAL MICROPHONE FOR P.A. WORK, BROADCASTING AND RECORDING

Here is a wide range high fidelity moving coil type Microphone which combines good sensitivity with a level response curve. Equally suitable for Auditorium or Outdoor Work, and its use can confidently be advised for Amateur as well as Professional use. Housed in modern streamlined die cast alloy case of great strength and finished in hammered metallic lacquer with chromium plated grille. Delivery from stock. List price £8.8.0

Dimensions 3" diam. 3½" back to front, Net weight 2 lb. Frequency response 60-9,000 c.p.s. Output impedance 15 ohms. Fitting 5/16" B.S.F. Connection 2-pin plug.


GRAMPHIAN

P.A. EQUIPMENT

Gramphian Reproducers Ltd., Hampton Road, Hanworth, Middx.
Phone: Feltham 2657.

Television

AERIAL FEEDERS

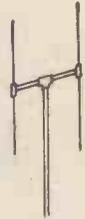

Scientifically designed cables for efficient service in all areas

Retain this page as your guide to improved picture quality



CHARACTERISTICS & NOMINAL DIMENSIONS

CHARACTERISTIC IMPEDANCE ohms	50 Ω Coaxial		75 Ω Coaxial			80 Ω Twin		
SERVICE AREA	Local	Fringe	Local	Local	Fringe	Local	Local	Fringe
CODE NUMBER	K16M	AS93M	PTIM	K19M	AS60M	K20	K12SM	BA24PSM
DESCRIPTION	Solid	Air Spaced	Solid	Solid	Air Spaced	Unscreened	Screened	Screened
CAPACITY μF/Foot	29	22.5	21.5	21.5	17	19.5	19	22
Attenuation db/100ft. 1 Mc/s ..	0.7	0.24	0.4	0.65	0.2	0.3	1.2	0.5
" 45 "	4.8	1.7	2.6	3.7	1.5	2.1	5.9	2.5
" 100 "	7.1	2.6	4.2	5.7	2.4	3.2	7.5	3.6
Diameter in inches :—								
Over Copper Conductor ..	7/0.0076	7/0.022	0.022	7/0.0076	0.048	0.036	0.029	0.048
" TELCOTHENE	0.085	0.180	0.128	0.128	0.200	—	0.070	0.088
" Twin Cores	—	—	—	—	—	0.19×0.1	0.140	0.200
" Wire Braid	0.109	0.210	0.152	0.152	0.230	—	0.180	0.237
" TELCOVIN Sheath	0.159	0.275	0.202	0.202	0.300	—	0.232	0.297

Dielectric is TELCOTHENE* and Sheath is TELCOVIN (P.V.C.)

*Polythene processed by Telcon to provide specific characteristics.

Prices and samples may be had on application to the sole manufacturers.

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD


Founded 1864

Head Office: 22 OLD BROAD STREET, LONDON, E.C.2

Enquiries to: TELCON WORKS, GREENWICH, S.E.10

Telephone: LONDON Wall 3141

Telephone: GREenwich 2291

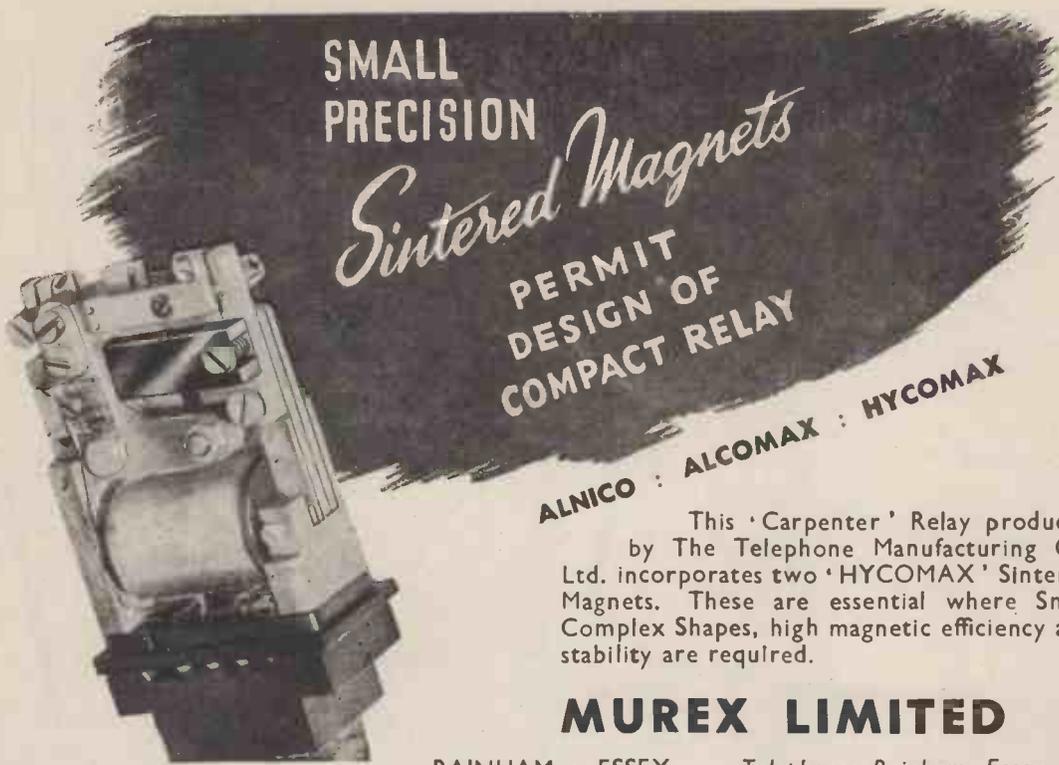

**SMALL
PRECISION
Sintered Magnets
PERMIT
DESIGN OF
COMPACT RELAY**

ALNICO : ALCOMAX : HYCOMAX

This 'Carpenter' Relay produced by The Telephone Manufacturing Co. Ltd. incorporates two 'HYCOMAX' Sintered Magnets. These are essential where Small Complex Shapes, high magnetic efficiency and stability are required.

MUREX LIMITED

RAINHAM · ESSEX Telephone: Rainham, Essex 240

S.G. BROWN

*Precision
Sapphire Needle*
For high Fidelity of Reproduction
with minimum of wear on the record



FIVE TYPES TO CHOOSE FROM

The above are designed and manufactured to suit all types of pick-ups.

Each S. G. Brown Sapphire Needle gives

2,000 PERFECT PLAYINGS

and the cost is less than one sixteenth of one penny per playing for perfect reproduction.

PRICES: — Nos. 1-4, 10/1 each. No. 5, 13/4 each.

Your local dealer can supply.
In cases of difficulty, apply direct.

A "TIP" WORTH TAKING

An interesting and instructive Brochure giving technical details, valuable information and advice on the choice of a S. G. Brown precision Sapphire Needle to suit your pick-up, will be sent on request. Write Department "W"

Telephone:
Watford,
7241.

S.G. Brown, Ltd.

SHAKESPEARE STREET, WATFORD, HERTS.



13" PROFESSIONAL

Brown-E.R.D.


*High Fidelity Sound on Disc
Recorders for every Purpose*

Particulars from:—

S. G. BROWN LTD.
SHAKESPEARE STREET,
WATFORD, HERTS, ENGLAND

Telephone: WATFORD 7241

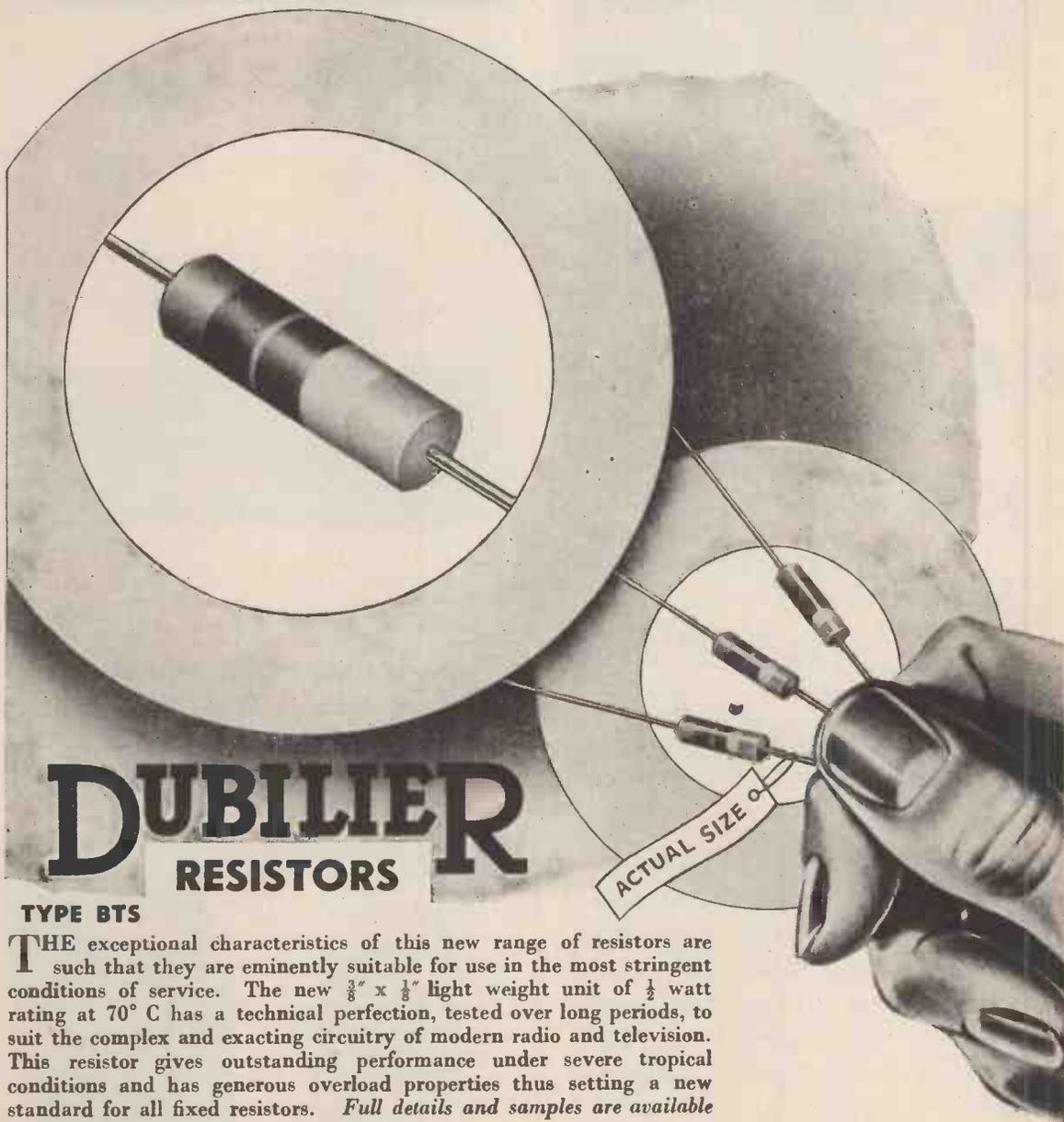The Latest Technical and Engineering Achievement in Resistors



DUBILIER RESISTORS

TYPE BTS

THE exceptional characteristics of this new range of resistors are such that they are eminently suitable for use in the most stringent conditions of service. The new $\frac{3}{8}'' \times \frac{1}{8}''$ light weight unit of $\frac{1}{2}$ watt rating at 70°C has a technical perfection, tested over long periods, to suit the complex and exacting circuitry of modern radio and television. This resistor gives outstanding performance under severe tropical conditions and has generous overload properties thus setting a new standard for all fixed resistors. *Full details and samples are available to Radio Manufacturers upon application.*

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, N. ACTON, LONDON, W.3


'Phone: Acorn 2241 (5 lines)

'Grams: Hivoltcon, Wesphone, London

Cables: H.voltcon, London.

Marconi International Code

D36A

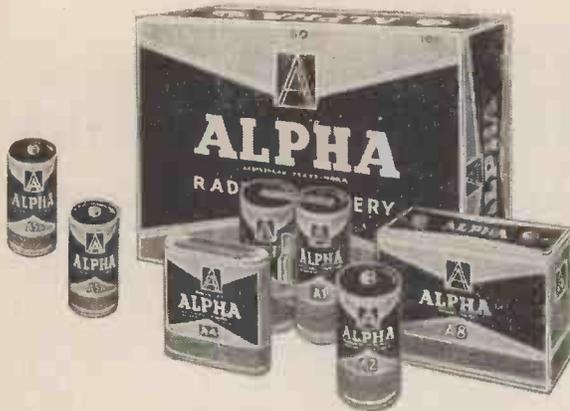

ALPHA BATTERIES

- ★ *First for quality*
- ★ *First for performance*
- ★ *First for reliability*
- ★ *First for long-life*

Alpha offer a range of batteries for radio and lighting second to none in high quality performance. Remember, too, that amongst the Alpha range of batteries for lighting, is the unique Leak-proof battery which will operate or store in any climate.

ALPHA ACCESSORIES LTD.
SALES OFFICE, GRAMOPHONE BUILDINGS
BLYTHE ROAD, HAYES, MIDDLESEX
Telephone: Southall 2468, Ex. 793

"Cyldon" VARIABLE Capacitors



Type No. 19 $1\frac{1}{2}$ " long.
 $1\frac{1}{2}$ " wide.
 $\frac{1}{2}$ " high.



Type No. 1 P $\frac{7}{8}$ " long.
 $\frac{3}{4}$ " wide.
 $\frac{3}{16}$ " high.



Type No. 16G.
4 to 40pF. 1 to 6 way. $1\frac{1}{2}$ "
between trimming plate
centres. $\frac{3}{8}$ " between fixing
screws. $\frac{1}{2}$ " high.

MICA TRIMMERS to AIR DIELECTRIC
HIGH-VOLTAGE *Transmitting Capacitors*

SYDNEY S. BIRD & SONS, LTD.
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX.
Phone: Enfield 2071-2. Grams: Capacity, Enfield.

from the range of  instruments

Model 26 LABORATORY VALVE VOLTMETER

This instrument sets an entirely new standard of performance in mains operated valve voltmeters. It measures d.c. and a.c. voltages from 0.2 to 250v. and has an upper frequency limit of 200 M/cs. Four resistance ranges extending up to 500 megohms and a decibel range are included. The meter is a six inch movement with a mirror scale.



★ The accuracy on all voltage ranges conforms to B.S.89:1937 for First Grade moving coil meters—a performance which has not hitherto been claimed for a valve voltmeter.

ELECTRONIC INSTRUMENTS LTD
17 PARADISE ROAD · RICHMOND · SURREY



NEW high efficiency



Actual size illustration

E.H.T. rectifier for Television Tubes **Osram** U37

RATINGS

Filament Voltage.....	1.4 volts
Filament Current.....	0.14 amp
Peak Inverse Voltage.....	15 max. kV★
D.C. Output Current.....	2 max. mA
Peak Anode Current.....	12 max. mA
Surge Anode Current.....	40 max. mA

★ For circuits where anode and filament voltages rise at approximately the same rate, e.g., as in fly-back and R.F. oscillator circuits. Where used on power input circuits with full A.C. anode voltage applied on switching, the maximum P.I.V. is 10 kV.

MINIATURE BULB

The Osram Type U.37, because of its low heater rating, greatly improves circuit efficiency. This miniature directly-heated half-wave rectifier has been primarily designed to provide E.H.T. for cathode ray tubes from an R.F. source or by rectification of the fly-back voltage. It is a soldered-in type valve, 48 m.m. overall, excluding connections.

Osram

VALVES



THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, W.C.2

Call the tune....

Visit your dealer's showroom today—ask to SEE and HEAR the Collaro Automatic Microgram play your favourite records—and judge this wonderful instrument yourself.

The Auto-Microgram is fitted with the Collaro R.C.500 Record Changer—incorporates *spring suspension*, eliminating acoustic feed back—and it's portable! Price £18-18-0 plus P.T.



...with the **COLLARO**
AUTOMATIC
Microgram
Portable Electric Gramophone

* If you prefer—write without obligation to Collaro Ltd., for illustrated Literature describing the Automatic Microgram and "De Luxe" Microgram—the world's finest portable electric gramophone.

Trade enquiries to:—

COLLARO LTD., RIPPLE WORKS, BY-PASS ROAD, BARKING, ESSEX

Telephone: RIPPLEWAY 3333.

Telegrams: "KORLLARO, BARKING."

Size counts!



THE SMALLEST
SILVERED MICA CAPACITOR

SRC

Our type 10B capacitors are now extensively used as a standard component for low capacitance values. Their small size offers the advantage of low stray capacitance and also allows a better spacing from coil assemblies where a high Q value must be maintained.

STABILITY RADIO COMPONENTS LTD

14, NORMAN'S BUILDINGS
CENTRAL STREET, LONDON, E.C.1.

Telephone: CLERKENWELL 15977/8

Stars for Sale!

TELEVISION COMPONENTS FROM STOCK

"VIEWMASTER." Whiteley chassis kit and brackets, 50/-; Plesey frame transformer, 18/6; line do., 21/3; Width control, 9/9; Focus magnet, 19/6; Scan coils, 25/6; Boost choke, 5/-; CRT supports, 14/-; Whiteley heater transformer, 35/-; Choke, 12/6; Stentorian speaker, 27/6; Westinghouse rectifier kit, 62/6; Bulgin kit of tags, etc., 12/6; G.E.C. neon lamp, 2/9; Belling Lee mains connector, 7/6; Set of Wearite coils and RFO, 22/-; Colveru control kit, 19/3; Morgan resistors "T" 20%, 4d.; "T" 10%, 6d.; "R" 20%, 6d.; "R" 10%, 9d.; "Q" pots 100K or 250K, 4/6; Full range of TOC "Metalmites," ceramics, electrolytics, etc., at list prices or the complete kit at 26/15/-; Instruction book and wiring diagram, 5/-.


"WIRELESS WORLD." B.T.H. crystal diodes C010, 11/3; S.P.C. H4200 H.V. rectifiers, 23/-; Reliance T.W. pots, 1k, 2k, 10k, 5/7; Do. S.G. pots, 100k, 2 meg., 8/10; Dubilier mica .001/5 kV., 5/-; .002/5 kV., 6/-; B.I. 32/500 v. electrolytics, 7/6; Coils, London or Birmingham, 52/8 set; Line OPT, 70/-; Mounted focus and scan assembly, 129/-; Blocking Osc. transformer, 15/-; Eddystone 25 + 25 pF. condenser, 7/6; T.G.C. mica .001 CM20, 1/9; .01/500 v. tubular B43, 11d.

"ELECTRONIC ENGINEERING." Vision chassis L or B with v/holders and coil formers, 22/6. Ditto sound.

18/8. Time base chassis with v/holders, 17/6; Power pack chassis with v/holders and sockets, 25/-; Set of gantries, 9/-; Varley EHT transformer 4 kV., 67/6; do. 5 kV., 72/6; Woden potted mains trans. PTM31, 98/6; Varley chokes 5 H 250 mA., 18/6; 10 H 80 mA., 17/-; Also full range of resistors and condensers; Handbook (London), 2/6; wiring diagram, 3/6; Midland Handbook, complete with diagram, 4/6.

"DENCO." Scanning coil assembly, 30/-; Screened line OPT, 27/-; Combined line OPT and EHT unit with 2 EHT valves and smoothing, 79/6 + P.T. 6/6; Focus coils, 5,000 or 130 ohms, 25/-; Television kits:—R.F. chassis kit with all parts, valves and 9in. C.R.T., £18/11/7; Time base and E.H.T. chassis kit with all parts and valves, £16/4/9; Power unit kit for above, 3/10; 229 mA., 8.3 v. 5.5 a., 23/10/9. All above parts are standard and interchangeable with current DENCO T.V. receivers. Completely wired 9-in. or 12-in. receivers can be supplied for building into your own cabinet. Constructional data, 5/-; Limited supplies of console T.V. cabinets are available for callers only, but please write first.

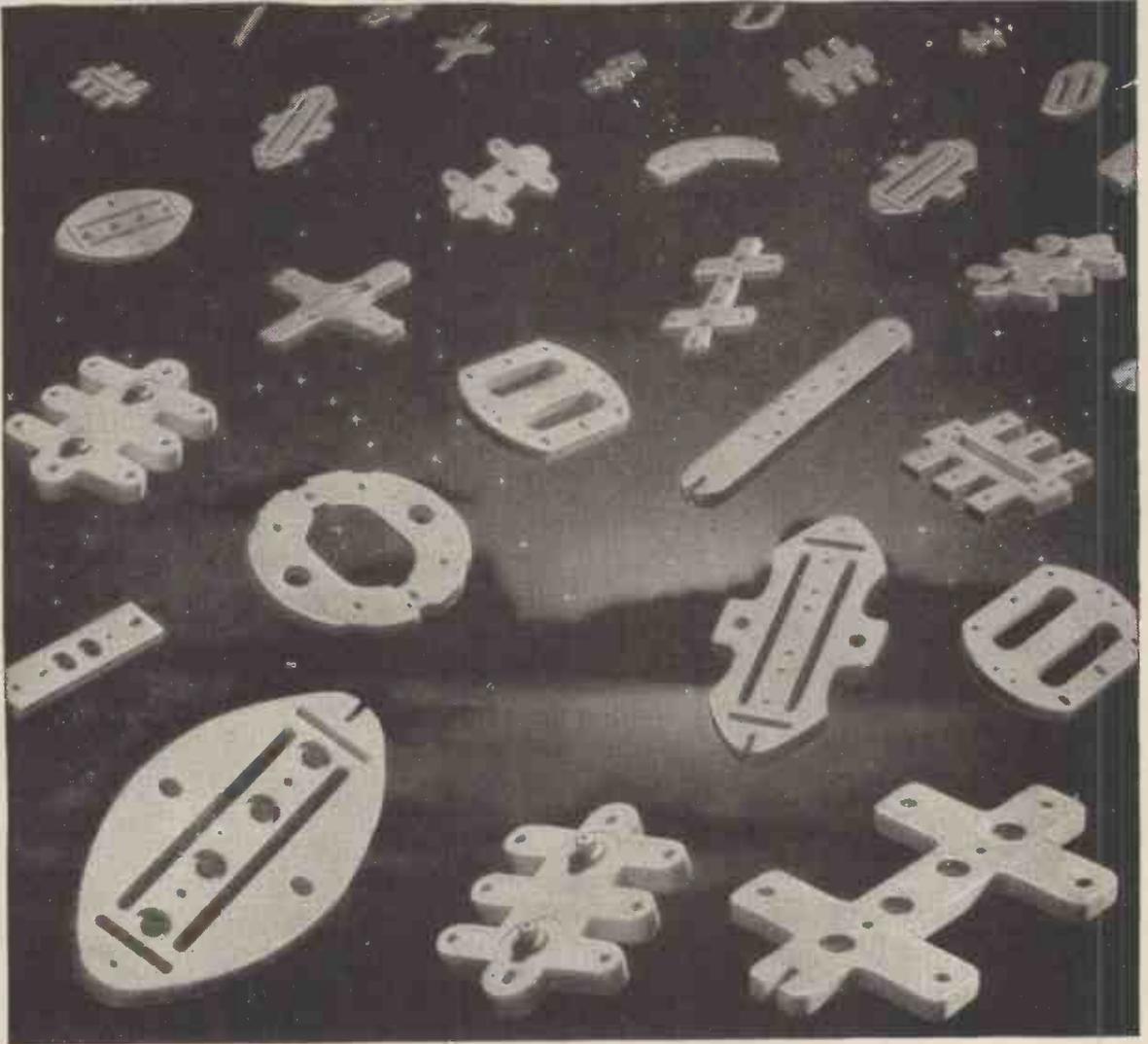**Frith
RADIOCRAFT Ltd.**
60-71 CHURCH GATE LEICESTER
PHONE 58921
G104 G301 G2R1



CERAMICS

FOR ELECTRODE SUPPORTS
and all radio components
FREQUENTITE – FARADIX – TEMPRADIX

STEATITE & PORCELAIN PRODUCTS LTD.

Stourport on Severn, Worcester

Telephone: Stourport 111

Telegrams: Steatoin, Stourport





THIS SET

will satisfy your expert judgment

When you criticise a radio, you must in fairness, ask yourself: is this set as good as it could be for the price? When you examine a Sobell set, any Sobell set, we feel confident that you will agree that it gives superb value for the money.

Look at Model 610, for instance. It is a typical model from the large Sobell range—a 6 valve, all-wave superhet with easily removable scale for new wavelengths, 10" speaker, and 6 watts push-pull output, A.C. mains, 200/250 volts. We invite you to check every component—circuits, signal rectification, tuning controls, the I.F. selectivity, the radio sensitivity. We know that you'll find them even better than you expected.

WITH

2 years

FREE ALL-IN-SERVICE
IN THE HOME

★ Valves and Cathode
Ray Tubes are subject
to the standard B.V.A.
guarantee.

Because you know much more about radio than the average man-in-the-street, we needn't stress the fact that we just couldn't afford to operate the Sobell 2 years free maintenance plan* if our sets were not the good sets they are.

The Sobell dealer in your district will be glad to arrange a demonstration of any of the new models—one of which will suit your pocket, and give you the technical efficiency you so rightly demand—a set you will be proud to own.

SOBELL

RADIO AND TELEVISION

SOBELL INDUSTRIES LTD., Langley Park, Slough, Bucks.

Tel.: Slough 22201/5

Dependable Di-electrics

OKERIN waxes

and DI-JELLS

—for insulating, filling, impregnating, waterproofing, sealing and finishing radio and electrical components, cables, etc.

ALL GRADES ARE DESIGNED TO MEET DEFINITE CHEMICAL, PHYSICAL AND ELECTRICAL STANDARDS.

For technical advice and samples, phone
TEMPLE BAR 5927.

Sales Department

ASTOR BOISSELIER & LAWRENCE LTD
NORFOLK HOUSE, NORFOLK STREET, STRAND, W.C.2

Works and Laboratories: West Drayton, Middlesex.

M.R. SUPPLIES Ltd.

offer the following new and perfect material for immediate delivery. We only handle goods which are sure to satisfy. Prices nett.

TELEPHONE SETS ("L" Mk. 1 star). Each compactly housed in steel case, 10" x 6 1/2" x 4 1/2" with hinged lid, and detachable carrying sling. First-class combine handset is accommodated within the case for transit. Magneto ringing—suitable for long and short distance use in factory, office, home, farm, smallholding, hotel, club, etc. Unused and unsealed, in makers' wrapping. Supplied ready for use (less 3-volt battery) at 29/6 each set (despatch 1/6 per set). 25 the pair, carr. paid.

HIGH DUTY SELENIUM RECTIFIERS (S.T.C.). Funnel cooled, size overall 13 1/2" x 12 1/2" x 4 1/2". D.C. delivery up to 32 v. 50 amps. (A.C. input 38 v.). Should be used in pair, for above delivery up to full-wave rectification. Brand new, in original cartons 72/6 each (des. 2/-). The current price list of these is about 25, and this is an exceptional opportunity for a very limited supply. H.T. SELENIUM RECTIFIERS (S.T.C.). D.C. delivery up to 360 v. 1.2 amp. A pair in bridge will provide A.C. mains voltage conversion to D.C. at 1.2 amps., full-wave—very useful in laboratories, etc., 22/8 each, 39/6 pair (des. 2/-).

BATTERY CHARGERS (ex-A.M.). For use on 200/250 v. A.C. mains. Charging 2 to 15 volt batteries up to 5 amps. Metal rectified, fitted sliding resistance, ammeter, fuses, etc., in steel housing 15" x 13" x 7", with wall-mount lugs, ready for use, 23/18/6 (des. 3/6).

HYDROMETERS (Battery Testing). "Breaknot," superior U.S.A. model, fitted thermometer calibrated 0/120 F. for compensation against non-tilt float, which is calibrated 1150/1300. Indispensable to all accumulator users. In good plush-lined case, 9/6 (des. 1/-).

AMMETERS. First-grade moving coil with 5" square flange. Deflection 0/80 amps., with external shunt. Ideal for use with above high duty rectifiers. Clear even scale with 2-amp. divisions, 42/6. Also 0/80 M/coil Voltmeters in same style and make, 39/6. Also MINIATURE MICRO-AMMETERS, 0/500 micro-amps., 1 1/2" dia., single-hole mount, back terminals, new, boxed, 10/6.

VOLTAGE CHANGING TRANSFORMERS (portable), 100/110 v.—200/240 v. (10 v. taps) and vice versa, auto-wound, loading 1.25 kva., in steel cabinet 9 1/2" x 8" x 6", with carrying handle. Just right for mobile cine work. Exceptional offer, 24/15/- (des. 5/-).

ANODE CONVERTERS (Rotary Transformers). We are again able to offer this most useful machine. Input 12 v. D.C., output 250 v. D.C. 125 m.a., brand new in cartons ex original cases of eight. A limited supply at 25/6 each (des. 1/6). These cost 2/10 each.

ROBAY CONVERTERS. New machines under half list price. Input 110 v. D.C., output 230 v. 50 c. 1 ph. 100 watt, 25/17/6 (des. 5/-). Also same machine mounted on all-wave radio filter, 29 (des. 5/-).

SENSITIVE MOVING COIL RELAYS (Elliott type H/DC) Coil res. 1,000 ohms, operating current 238 microamps—each with test report. In windowed housing 6 1/2" x 3 1/2" x 2 1/2", on base 5" x 1 1/2" with 2 coil and 3 switch terminals, switching 1 pole 0.0., 37/6 (des. 2/-).

MINIATURE RELAYS, size 1 1/2" x 1" x 1". Res. 60 ohms, 2-pole 0.0., with heavy contacts switching up to 4 amps., 7/6 each. Special quote for quantities.

STAGE LIGHTING DIMMERS. Full bright to blackout at 220/240 v. Sliding type, 100-watt, 32/6; 200-watt, 37/6; 500-watt, 50/- (des. 2/-). Screw motion, with handwheel, 1,000-watt, 28 3/0; 2,500-watt, 29/5/0 (des. 5/-). All fully enclosed.

P.A. PROJECTOR SPEAKERS. Exceptional opportunity for brand new G.E.C. 1860 10-watt Pressure Units, 15 ohms coil, with built-in multi-line transformer, in weatherproof cowling, 24 model for only 65/- (des. 1/6). 30" all-metal square section Dispersive Horns to suit, 45/- (des. 3/6). Or the complete speaker for 25/12/6, carr. paid U.K.

STEEL TRIPODS to suit all P.A. speakers, extending up to 12ft., strong and rigid, 55/- (des. England 5/-, Scotland and Ireland 8/6).

M. R. SUPPLIES Ltd., 68, New Oxford Street, London, W.C.1

Telephone: MUSeum 2958

TRUVOX

the balanced speaker

fidelity of response speaks for itself to the discriminating ear. Precision manufacture is no less eloquent to the trained engineer. These qualities make TRUVOX speakers famous.

C.P.M. 12" SPEAKER. The outcome of intensive development by specialist engineers, the method of construction employed in the Truvox "C.P.M." series offers a notable economy in size, weight and cost. Ranging from "midgets" to auditorium speakers, each model in the TRUVOX "C.P.M." series is precision-designed to combine maximum flux density with the widest frequency coverage for its size.

Model BX11



12" HEAVY DUTY. Rigid die-cast chassis; square casting for the magnet seating, secured with large hexagon head bolts; centre pole and bottom plate all in one forging; ring-clamped cone; die-cast centring ring; practical construction matched by excellent response and high sensitivity—all made for HEAVY DUTY.

Response 55-11,000 C.P.S; flux density 13,000 Gauss; powerhandling capacity 10 watts (A.C.)

Model SS10A

6½" WAFER. Wherever the requirements call for minimum space, minimum weight, robustness and normal sensitivity and response, Truvox "Wafer" speakers are the answer. Designed by specialists with twenty years' pioneering experience in loudspeaker manufacture, they are the outcome of a completely fresh approach to the problems of speaker weight and size in relation to efficiency.

Designers and manufacturers of personal and television receivers, car radio, and intercommunication equipment, and all other users needing real compactness, will find the "Wafer" speaker range of superlative interest.



Model BS1650

MONOBOLT. Unshakably rigid in transit and extended use, the unique construction of Truvox "Monobolt" loudspeakers gives unequalled reliability and consequent freedom from service troubles. The use of a one-inch pole-piece allows large power handling capacity free from distortion.

Model BX82 8"

Model BX102 10"




Full technical details of all Truvox Speakers available on request.

Your local dealer can supply you with Truvox.

TRUVOX ENGINEERING CO. LTD., EXHIBITION GROUNDS, WEMBLEY, MIDDX.

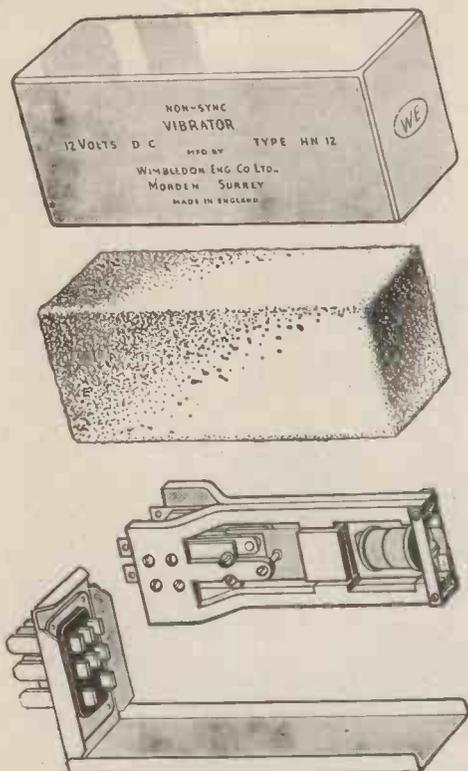"JUNO" and "OCO" floor polishing machines are also manufactured by TRUVOX. Send for details.



NEW!

Heavy Duty VIBRATOR



Introducing, after a lengthy period of research, a "big brother" to the popular standard WIMBLETON Vibrators. It has all their desirable qualities, but is produced specially for heavy work. Note these advantages.—

1. Carefully designed and tested.
2. Made throughout from selected high grade materials.
3. Will give satisfactory service over a long period.
4. Reliable in operation under rated conditions of use.

Available in both SYNCHRONOUS and NON-SYNCHRONOUS Types; POWER UNITS to suit.

Write for illustrated leaflet to

WIMBLETON


ENGINEERING COMPANY LIMITED

GARTH ROAD · LOWER MORDEN · SURREY · TEL.: DERWENT 4814-5010

CRC 4

ANOTHER WINNER BY RUCO'S

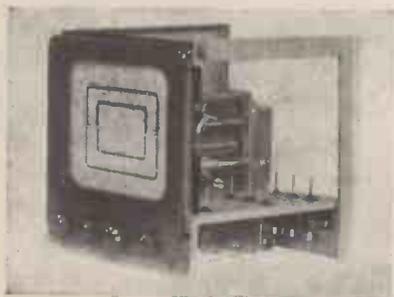A 6-POSITION VARIABLE SELECTIVITY
3-WAVE BAND FEEDER UNIT. R.F. STAGE.
INFINITE IMPEDANCE DETECTION.



DON'T DELAY!
Write now for details
RUCO PRODUCTS
197 Lower Richmond Road
RICHMOND, SURREY

Phone PRO. 7463.

James Booth

for COPPER and BRASS

Seamless and brazed tubes
(round and shaped)
Extruded rods and sections
Phosphor-bronze tubes for pressure gauges
Condenser tubes in brass,
aluminium-brass and cupro-nickel
Copper stay bars (solid and hollow)
Large forgings in brass
and other copper alloys
Formed strip sections
Drawn strip and wire
Rolled sheet and strip



JAMES BOOTH & CO. LTD., ARGYLE ST. WORKS, BIRMINGHAM 7

WESTERN BALL MICROPHONE

Manufactured by . . .
STANDARD ELECTRIC
 All in perfect condition


Suitable for broadcasting and recording. Moving Coil (Dynamic). Omni-directional. No energising necessary. High Fidelity. Coil Impedance 15 ohm. and will work very well in conjunction with an ordinary speaker transformer.

Is of the type used by many leading bodies, such as the B.B.C. and G.P.O. for high fidelity reproduction. **£4.17.6**



PHILIPS 6-VALVE COMMUNICATIONS RECEIVER

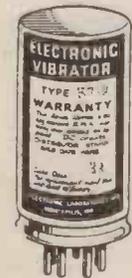
16-50, 200-550 and 800-2,500 metres. R/F, F/C, 2 I.F.s, D.D.T. Pentode Output. Spin-wheel tuning. In black metal case with built-in speaker. Complete with power pack, AC 200-250 v. Can also be supplied with 12 v. DC. power pack if required. **BRAND NEW £17.10.0**
 EX-GOVT.



2-VOLT VIBRATORS

Type R76C
 These 7-pin self-rectifying vibrators have an output of 200 v. at 60 mA. Made by Electronic Laboratories Inc. **7/6**

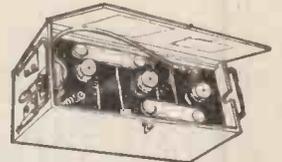GOVERNMENT SURPLUS IMMEDIATE DELIVERY FROM STOCK



BRAND NEW ACCUMULATORS

As illustrated. 6 v., 85 a. Size 12 x 9 x 7 in. Weight 45 lb. British made. **£3.10.0**



G.E.C. ELECTRIC TORCH

Aluminium body 10 1/2 in. long. Powerful beam. Adjustable for spot or flood. Takes three U2 cells. Complete with 3.5 volt bulb, but less batteries. **25/-**

NEW MILNES H.T. UNITS (everlasting) 120 v. 600 mA. Will charge from 6 v. accumulator. Callers only. 67/6.

1/30th H.P. MOTORS. Constant speed. Double-ended spindles. 220-250 v. These motors are new, not surplus conversions and are suitable for 10 mm. projectors and many other purposes. AC/DC, with feet, 42/6. AC, without feet, 35/-.

HEADPHONES. Low resistance with headbands, new, 4/6 pair. New American midget Reed type, 90 ohms, no headbands, 3/9 pair. American lightweight. Suitable for deaf aid, 7/6 pair.

BLOWER MOTORS. 12-24 v., and 80 v., 15/- each.

VISION UNIT. Type 182. Complete with 6in. 517 OR. Tube, 2in. 139 O.R. Tube, one 807, three VR65, one 6J5 valves. 0.5 milliammeter, condensers, etc. Suitable for Television, 55/-.

PHOTO-ELECTRIC CELLS. Type GS16. These cells are the gas-filled type with caesium Cathode. Made by Cintel. Minimum sensitivity 100mA/lumen, working volts 100 D.C. or peak A.C. Projected cathode area 16 sq. cm. Suitable for 16 mm. Home Cinema Talkie equipment, Safety Devices, Colour and Photo Matching, Burglar Alarms Automatic Counting, Door Opening, etc. Brand new in original cartons. 42/6.

MOVING COIL HAND MICROPHONE. Complete, 5/6. INSERTS, as above, 2/9.

7-VALVE U.H.F. RECEIVER. Type R1147A. Range approx. 200 megacycles (with 4 Acorn valves). A Real Opportunity. Beautifully constructed and fitted with micro-condenser drive. Valve types: two EF36, one ERC33, three 954, one 955. In black metal case, 8 x 7 x 6 1/2 in. Set complete with valves, 30/-.

PLEASE NOTE.—All carriage paid unless otherwise stated. ● Carriage charges relate to British Isles only. ● We do not issue lists or catalogues. See last issue for other Bargains.

CATHODE RAY TUBES
 12in. VCR140 Blue Screen 90/-
 New VCR97 37/6

LONDON CENTRAL RADIO STORES

23 LISLE ST.

LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.

Tel: GERrard 2969

New Two Speed-motor....

At the turn of a switch you have two speeds, 33 $\frac{1}{3}$ or 78 r.p.m. The Turntable is a full 12" diameter; its main spindle precision ground and lapped, runs in phosphor bronze bearings. The synchronous motor is virtually vibrationless and is suitable for playing standard, transcription and microgroove recordings. Guaranteed mechanically perfect. New super light-weight pick-up available with the interchangeable heads for microgroove and standard recordings.



Retail price, without pick-up £12-10-0

Purchase Tax £5-8-4

A Connoisseur PRODUCT

Manufactured by

A. R. SUGDEN & CO. (ENGINEERS) LTD. WELL GREEN LANE BRIGHOUSE YORKS.

CELESTION

The Foremost Name in Sound Reproduction



MODEL P44.

- Overall Diameter 12 $\frac{3}{16}$ "
- Voice Coil Impedance ohms 3.0
- Magnet Pole Diameter 1 $\frac{1}{2}$ "
- Flux Density (Gauss) 10,000
- Total Gap Flux (Maxwells) 60,000
- Peak Power Capacity 10W

The General Public should please order through their Local Dealers.

Manufacturers are invited to write for details of the full range of Celestion speakers.

CELESTION LTD. SUMMER ROAD, THAMES DITTON, SURREY

Telephone: EMBERBROOK 3402-5

Why you should use...



- 1 Maximum "Wetting" Capacity.
- 2 Accelerated Fluidity.
- 3 Moderate soldering bit temperatures.
- 4 Mechanical bonding and perfect Electrical conductivity ensured.
- 5 Minimum amount of solder used per joint.
- 6 Residue sets hard, is non-corrosive, and of high dielectric strength.
- 7 No harmful fume deposits.
- 8 Continuous, unvarying core.
- 9 Even distribution of activator in core.
- 10 Approved by Air Ministry and General Post Office.

Supplied in a wide range of Gauges and Alloys on 1 lb and 7 lb reels, works coils, or as required. Prices on application.

Sole Manufacturers:

H. J. Enthoven & Sons, Ltd.
 89, UPPER THAMES STREET, LONDON, E.C.4.
 Phone: Mansion House 4533. Works: Rotherhithe, Croydon, Derbyshire.

designed

**with
your
specific
needs
in
mind**



MODEL 1035

The Cossor general purpose Oscillograph is designed and built by electronic engineers who are themselves familiar with the everyday problems which technicians have to face. The instrument consists of a Double Beam Tube operated at 2kV., a Time Base, Y Deflection Amplifiers and Internal Power Supplies. The 90mm. screen is flat, and traces

are presented over the full area. Signals are normally fed through the Amplifiers, and the calibrated Y-Shift controls provide a measurement of the applied voltages. The Time Base operates repetitively, or by external trigger (for single stroke operation), or at trigger pulse repetition frequency for continuous scanning. A calibrated X-Shift Control is provided for the measurement of Time.



**Model 1428
CAMERA**

Specially developed for use with Cossor Oscillographs, it provides the simplest means of recording stationary or non-recurrent waveforms and slow transients by the moving film method on standard perforated 35 mm. film or paper. Of robust construction, it has provision for power drive by the Cossor Three-Speed Motor Attachment, Model 1429.

COSSOR


**Double Beam
OSCILLOGRAPH**

Further details obtainable on application to:—

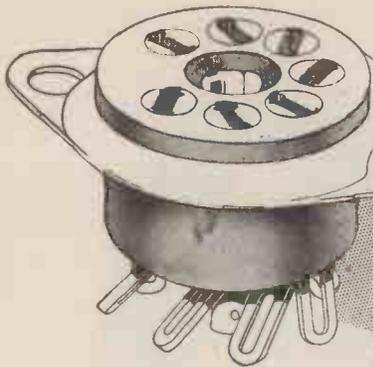A. C. COSSOR LTD., INSTRUMENT DIVISION, Highbury, London, N.5

CU11

Recognised as the Most Reliable Valveholders



B7G



Ref. No. **BM7/U** moulded in Phenol-Formaldehyde

Ref. No. **FM7/U** moulded in PTFE



THE McMURDO INSTRUMENT COMPANY LTD., VICTORIA WORKS, ASHTEAD, SURREY · ASHTEAD 3401

ICS

HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following:

Complete Radio Engineering Radio Service Engineers
Radio Service and Sales Advanced Short-Wave Radio
Elementary Electronics, Radar and Radio
Television Technology

And the following Radio Examinations:

British Institution of Radio Engineers
P.M.G. Certificates for Wireless Operators
City and Guilds Telecommunications
Wireless Operators and Wireless Mechanics, R.A.F.

Write today for our FREE "Radio" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need of and the means of instruction.

International
CORRESPONDENCE SCHOOLS

Dept. W.L.7, International Buildings, Kingsway, London, W.C.2

A NEW CONVERTER by VALRADIO

Specially designed for operating radio-gramophones, and radio receivers from Direct Current Mains, this new Valradio Converter supplies steady and dependable A.C., and incorporates many new and improved features which greatly extend its usefulness. Standard models have 50 cycle output. 60 c.p.s. models available to order. **£10 · 15 · 0**

SPECIAL FEATURES

- Input 180 to 270 v. D.C. Output 200-250 v. A.C. at 110 watts.
- Available also for D.C. inputs of 12, 24, 32, 50, or 110 volts at the same price.
- Plug-in vibrator easily replaceable.
- H.F. and L.F. suppression.
- More compact in size.
- More easily inspected and serviced.


VALRADIO SPECIALISE IN POWER CONVERSION

★ Valradia D.C. Voltage Changers are proving most successful. Available for operation from 6, 16, 24 or 32 v. D.C., they will deliver up to 2,000 v. D.C. and 150 watts. Details on request.

VALRADIO LTD., 57 FORTRESS ROAD, N.W.5
GULLIVER 5165

VITAVOX

*can solve
your sound
problems*

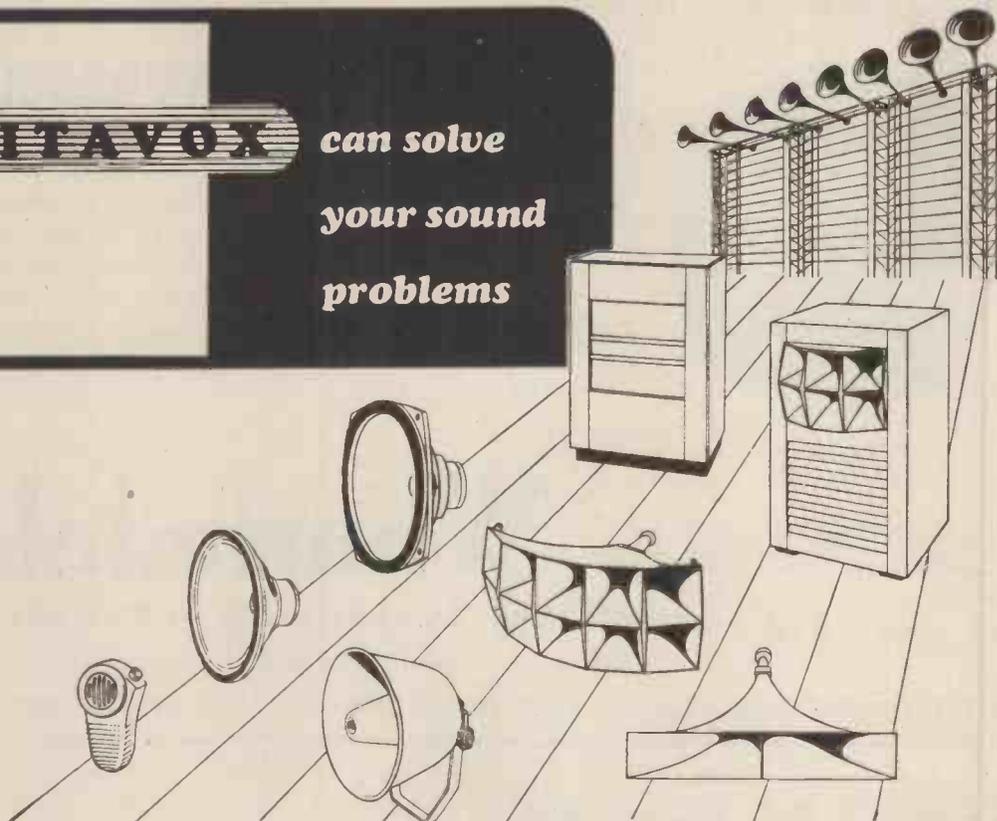

If you have a problem of sound reproduction and distribution, you will find the solution with one or a combination of the quality units in the VITAVOX range. From a 12" cone type loudspeaker to a huge industrial, theatre or stadium sound system, VITAVOX can supply your individual need. Each unit has been specially designed to solve a specific sound problem. Thousands of VITAVOX loudspeakers, microphones, units and horns are now in use in the motion picture, public address and radio industries. Remember—if your problems are sound—VITAVOX have the answer. Illustrated above are:

- A typical installation of Vitavox 75" Circular Horns.
- Console Reproducer. Model KC.10.
- Bitone Reproducer. Model 6201.
- 15" Cone Loudspeaker. Model K15/40.
- Multicell Horns: Type 220. In 3, 6, 10 and 15 cell units.
- G.P.1 Pressure Unit.
- 12" Cone Loudspeaker: Models K12/10 K12/20.
- Beam Projector Loudspeakers Model B.P.28.
- Microphone. Type B50. (Hand held model).


Write for full details of any or all the Vitavox range.

VITAVOX LIMITED

WESTMORLAND ROAD · LONDON · N.W.9 · ENGLAND · TELEPHONE: COLINDALE 8671/3
TELEGRAMS: VITAVOX · HYDE · LONDON · CABLEGRAMS: VITAVOX · LONDON

Expressly designed for . . .

PERFECT BASS REPRODUCTION

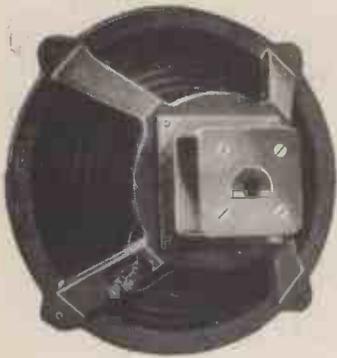

MODEL W.15/CS

Alcomax Magnet

Flux Density 13,500 lines/cm². 2" centre pole. Total Flux 180,000 lines. Speech Coil 6 or 15 ohms. Peak Input 15 watts. Chassis diameter 14½ inches. Weight 17 lbs.

PRICE (less transformer)

£12 : 0 : 0

THE W.15/CS Loudspeaker is a recent Wharfedale model, with cloth suspension, for low resonance and rich tonal quality. It has been specially designed to give clean bass without frequency doubling down to 25 cycles, with reasonable air loading—and is the perfect L.F. Unit for crossover networks. Open baffle resonance—34 cycles.

Wharfedale

CLOTH SUSPENSION LOUDSPEAKERS

for Low Resonance and Clean Quality of Tone

WHARFEDALE WIRELESS WORKS · BRADFORD RD · IDLE · BRADFORD · YORKS

THE NEW B.P.L. SUPER RANGER

20,000 OHMS PER VOLT.



D.C. VOLTS :
100 mV to 5 kV

D.C. CURRENT :
1 μA to 1 Amp.

A.C. VOLTS :
0.5V to 5 kV.

A.C. CURRENT :
10 mA to 10 Amps

RESISTANCE :
1 ohm to 2 meg-ohms

OUTPUT :
0 to 62 db

METER :
5-inch Long arc, fitted with knife-edge pointer and mirror scale.

LIST PRICE :
£ 21 - 10 - 0.

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS, RADLETT, HERTS.

Tel: Radlett 5674-5-6

LONDON

OR

BIRMINGHAM!

Here is an opportunity worth grasping, build your own Television Receiver at a price you can afford.

- Designed around common types of valves.
- No unusual types to obtain.
- Will suit 9", 10" or 12" Tubes.
- The most competitive price on the market.

CAN BE BUILT FOR £20 (C.R. Tube Extra)

Instruction books PRICE 5/- post free.

Write today for further details.

COMPLETE RANGE OF COMPONENTS AVAILABLE

Focus Coils High Res. 17/6 Deflection Coils..... 22/6
 " " Low " 17/6 Line Output Trans. 22/6
 Perm. Magnet Focussing Assemblies from 21/-
 Pre-Amplifiers for London or Birmingham £7 10s.

HOUGHTON & OSBORNE

Electron Works, Thame, Oxon.

Telephone: Thame 182.

if

SEEING IS BELIEVING

AMBASSADOR

TELEVISION IS YOUR CHOICE



MODEL TV.2
£69.10.0
 TAX PAID
 A.C. only
 Registered Design
 No. 859761



MODEL TV.1
£105
 TAX PAID
 A.C. only

Write for illustrated leaflets.



BRIGHOUSE, YORKSHIRE



DESIGNED BY
SPECIALISTS
 FOR THE
SPECIALIST

A very efficient four channel electronic mixer employing the latest type low noise valves. Three microphone channels and one pick-up or radio channel, each with independent fader, are provided.



EM49A MIXER UNIT

Inputs 1/2/3: 20Ω at 70 microvolts.
 Input 4: 50 kΩ at 300 millivolts.
 Output: 1 volt. Imp.: 5.5 kΩ.
 Noise Level: -60 db approx.
 Response: ±1 db 50 c/s to 20 k/c.s.
 Dimensions: 5" × 14" × 9½".
 Weight: 10 lbs.

SIMON SOUND SERVICE


Recorder House, 48/50, George Street, Portman Square, London, W.1, England

Telephone: Welbeck 2371 (4 lines)

Telegrams: Simsale, Wesdo, London

Cables: Simsale, London

TELEVISION PATTERN GENERATOR

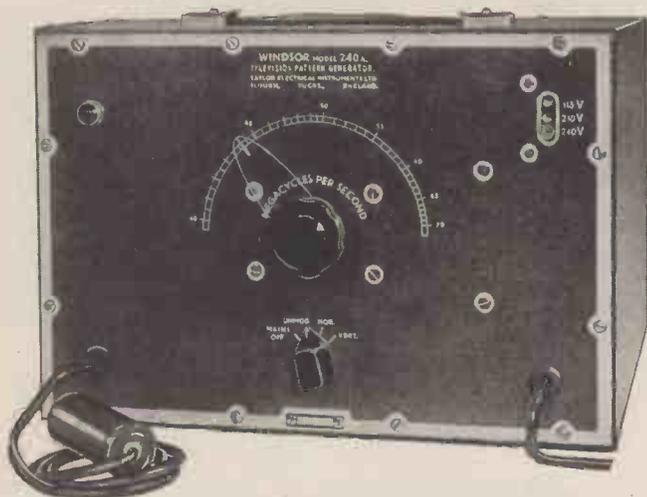

MODEL 240A SPECIFICATION

FREQUENCY RANGE
40-70 Mc/s, directly calibrated.

OUTPUT VOLTAGES
Approx. 50 mV., 5 mV. and 500 mV., at end of a 75 ohm co-axial cable.

MODULATION
Horizontal bars, vertical bars, unmodulated.

POWER SUPPLY
100-125 and 200-250 volts
40/100 c/s.

LIST PRICE £14.0.0
EARLY DELIVERY


other products include:

- Multirange A.C. D.C. Test Meters
- Signal Generators
- Valve Testers
- A.C. Bridges
- Circuit Analysers
- Cathode Ray Oscillographs
- High and Low Range Ohmmeters
- Output Meters
- Insulation Testers
- Moving Coil Instruments

ALL WINDSOR & TAYLOR TEST EQUIPMENT IS AVAILABLE ON H.P. TERMS. SEND FOR DETAILS AND CATALOGUES

TAYLOR ELECTRICAL INSTRUMENTS LTD
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND
Tel. SLOUGH 21381 (4 lines) Grams & Cables TAYLINS, SLOUGH

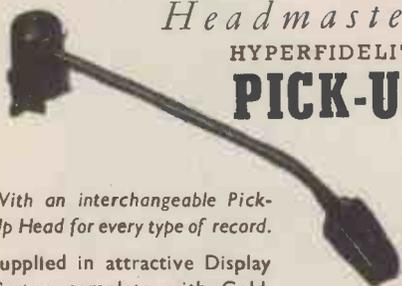The Revolutionary **GOLDRING** *Headmaster* HYPERFIDELITY **PICK-UP**



With an interchangeable Pick-Up Head for every type of record.
Supplied in attractive Display Carton complete with Goldring Tonaliser and Transformer




Goldring Products include:
PICK-UPS, PICK-UP HEADS, SAPPHIRE JEWEL POINT NEEDLES, AND RADIOGRAM ACCESSORIES.

Write for full Descriptive Lists and Technical Information

ERWIN SCHARF
49-51a DE BEAUVIOR ROAD, LONDON, N.1
Telephone: CLISSOLD 3434

A Pre-Fab Cabinet *Widney*

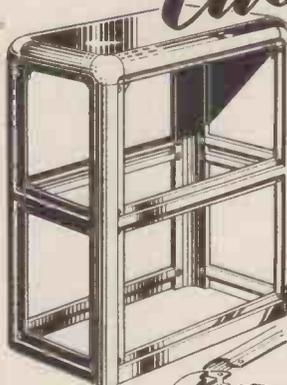

Widney - **DORLEC** REGD **CABINET SYSTEM**

providing an easily constructed cabinet for manufacturers and laboratories. The range of extruded sections, corners and brackets now available enables a housing for individual designs to be easily erected.

Technical & Sales Agent
C. H. DAVIS
59, BROMPTON RD.
LONDON, S.W.3

Write for Illustrated leaflet.



ESTABLISHED 1898

MANUFACTURERS

HALLAM, SLEIGH & CHESTON LTY
WIDNEY WORKS - BIRMINGHAM - 4

Phone: Aston Cross 0714 (4 lines) Grams: Superfine, Birmingham, 4



The NEW EDDYSTONE '680' COMMUNICATIONS RECEIVER

A high-grade instrument with wide frequency coverage for PROFESSIONAL COMMUNICATION REQUIREMENTS

The '680' is a fifteen valve superheterodyne receiver embodying advanced technique. Among its special features are included: continuous coverage from 30 Mc/s to 480 K/c/s, two R.F. stages, two I.F. stages, crystal filter, B.F.O., push-pull output stage, variable selectivity, "S" meter, noise limiter, standby switch, stabilised H.T. voltage to oscillator, provision for relay operation of transmitter, high signal-to-noise ratio and sensitivity, highly attenuated image response, very effective A.V.C., provision for twin feeder and single aerial, modern miniature all-glass valves, mechanical bandspread logging device. Available for rack mounting.

The complete frequency range is covered by five switched coil assemblies with an overlap between each. The gear-driven, flywheel controlled mechanism is positive, free from backlash and very smooth in action. The mechanical bandspread device takes the form of an auxiliary dial and gives a scale length equal to ninety inches per range. The dial can be read to one degree. I.F. transformers are permeability tuned to 450 K/c/s. Operates from A.C. mains 110 and 200/240 volts, 40/60 cycles. The front panel and tuner unit chassis are aluminium, and the remaining units of stout brass, heavily nickel-plated. Lift up lid. The cabinet and front panel are finished a handsome ripple black, set off by plated handles. The finger plate is black and silver. 16 $\frac{1}{2}$ in. x 13 $\frac{3}{4}$ in. x 8 $\frac{1}{2}$ in. high. Weight 41 lbs.

LIST PRICE IN U.K. £89.5.0 (No Purchase Tax)

Manufacturers:

STRATTON & Co. Ltd., West Heath, Birmingham 31 Cables: STRATNOID, BIRMINGHAM

YOUR EQUIPMENT CAN HAVE THE PROFESSIONAL LOOK



BY USING WODEN POTTED COMPONENTS

Woden Potted Transformers and Chokes ensure a clean layout with uniform smart appearance. They are used by many leading Radio and Television Manufacturers and this is sufficient testimony to the high standard of efficiency which characterize these components. Available for "Wireless World" Williamson Amplifier, "Electronic Engineering" Home Built Telesvisor and other popular circuits.


THE EQUIPMENT SHOWN IS THE TOP BAND CABINET TRANSMITTER AS DESCRIBED IN THE "SHORT WAVE MAGAZINE".



MOXLEY ROAD BILSTON STAFFS

PHONE: BILSTON 41959

LISTEN-IT'S A GOOD SOUND JOB

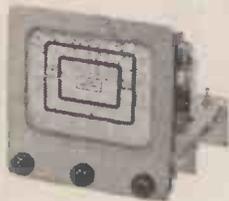

R.A. TUNING UNIT

A really fine design with lasting high performance. R.F. stage on all wave-bands. High fidelity super-het or T.R.F. performance. Suitable for any amplifier. Price 10 gns., plus £2.6.8 tax. With escutcheon plate as shown 5/- extra. (2 years' guarantee)



THE K.I. AMPLIFIER

A seven-valve amplifier especially designed for the light-weight high-fidelity type pick-up. Independent bass and treble controls. Price complete 17 gns., or in kit form, 13 gns. Blueprint available separately 2/6



The CONCERTO Amplifier

... acclaimed by music lovers for its exceptionally high fidelity, this magnificent amplifier covers all normal requirements for home or concert hall. Distortion level below 0.5 per cent. Two channels of bass boost ensure unusually smooth balance and depth. Designed for any type of pick-up. Radio input socket provided. Two-year guarantee. Price £27.10.0. Heavy perforated steel

with bottom plate and rubber feet, 45s. extra. Delivery by passenger train. Carriage Paid. 10s. deposit (returnable) for crate.

DEFERRED TERMS AVAILABLE ON ALL MODELS

Our equipment can also be seen at Webb's Radio, Soho St., W.1. University Recording Co., 16 Burleigh Place, Cambridge. Ernest Buchan, 28 Belmont Street, Aberdeen. Farmer & Co., 83 George St., Luton.

Write for your copy of our fully illustrated catalogue today.



THE TRICORNE SPEAKER CHAMBER

For optimum acoustic performance with any good 12-in. speaker. Labyrinth construction, walnut veneered and cross-braced.

Price 11 gns. plus 20/- deposit (returnable) for crate.

Phone : WESTern 3350

Charles
AMPLIFIERS
(SALES) LTD

181 KENSINGTON HIGH STREET LONDON W.8

FOR THE UTMOST REALISM FROM RECORDS & RADIO

• CONSTANT VOLTAGE • POWER SUPPLY UNITS

MODEL 101-C

Output: 250/400v. 0.250mA max.
Stability: Better than 0.1%.
Output Impedance: Less than 1 ohm.
Output Ripple: Less than 2mV. R.M.S.
Mains Supply: 200/250v. 45-60c/s.
Regulation down to zero load.



DETAILS ON REQUEST.

ALL-POWER TRANSFORMERS LTD.
CHERTSEY ROAD, BYFLEET, SURREY
Tel : Byfleet 3224/5.

★ GOOD NEWS

for Gramophone Enthusiasts!

GREAT REDUCTION IN PRICES OF ROTHERMEL CRYSTAL PICK-UPS

As and from January 1st, 1950, the prices of the famous Rothermel Crystal Pick-ups are greatly reduced. The cost of even the more expensive models is now within the price limit of the most slender purse, and the superb performance of these high-class instruments can now be enjoyed by all. The demand is bound to be heavy, so make your choice and secure now.

	Old Price	New Price
SENIOR MODEL	45/-	28/-
S.8 MODEL - -	42/-	26/-
S.12 MODEL - -	42/-	26/-
U.48 MODEL - -	25/-	19/6

Purchase Tax extra

If you have any difficulty in obtaining supplies from your retailer, write direct to:-

R.A. ROTHERMEL LTD.

ROTHERMEL HOUSE,
CANTERBURY ROAD, KILBURN, LONDON, N.W.6

Telephone : MAIDA VALE 6066 (3 lines)

PULSE GENERATOR

WITH VARIABLE DELAY

TYPE OPS. 100



WIDE BAND AMPLIFIERS
 REGULATED POWER SUPPLIES
 VIDEO OSCILLATORS
 IGNITION DELAY METERS
 OCTAVE FILTERS
 LOGARITHMIC AMPLIFIERS
 DISPLAY UNITS
 ATTENUATORS
 INSTRUMENTS CONSTRUCTED
 TO SPECIFICATION

- PULSE WIDTH : 1 – 40 micro-seconds.
- OUTPUT AMPLITUDE : 0 – 75 volts.
- REPETITION RATE : Up to 100 Kc/s.
- DELAY INTERVAL : 2 – 3,400 micro-seconds.
- SYNC. OUTPUT PULSE : Width 2 micro-seconds.
 AMPLITUDE : 20 volts.
- RISE TIME : Less than .1 micro-seconds.

SOLARTRON LABORATORY INSTRUMENTS LTD.
 22 HIGH STREET, KINGSTON-ON-THAMES Kingston 1787

Difficult Problems?



Made in Three Principal Materials

FREQUELEX

An insulating material of Low Di-electric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX

A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

TEMPLEX

A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.



Bullers

BULLERS LOW LOSS CERAMICS


BULLERS LTD., 6, LAURENCE POUNTNEY HILL, LONDON, E.C.4

Telephone : Mansion House 9971 (3 lines)

Telegrams : "Bullers, Cannon, London"



Leaders in their field

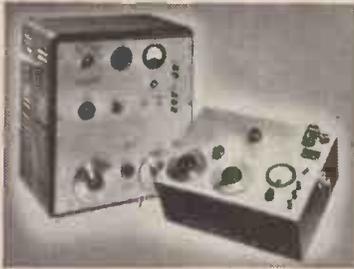

BEAT FREQUENCY OSCILLATORS & LABORATORY INSTRUMENTS



INDUSTRIAL SOUND INSTALLATIONS




PORTABLE AND MOBILE AMPLIFIERS




DIRECT DISC RECORDERS FOR HIGH FIDELITY DISC RECORDING



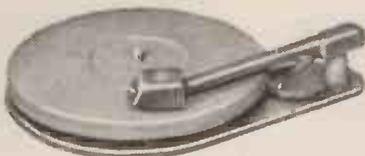TELEMASTER INTER-OFFICE COMMUNICATION EQUIPMENT



G.U.2 GRAMOPHONE UNIT

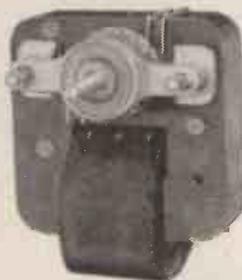

SHADED POLE MOTORS



T.U.2 TURNTABLE UNIT

BIRMINGHAM SOUND REPRODUCERS LTD.

Telephone: Cradley Heath 6212/3

CLAREMONT WORKS, OLD HILL, STAFFS.

'Grams: 'ELECTRONIC Old Hill, Cradley Heath

Wireless World

RADIO AND ELECTRONICS

February 1950

39th YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK M.I.E.E.

Editor: H. F. SMITH

PUBLISHED MONTHLY: Price 2/- (last Thursday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Echaworld, Sedist, London."


ANNUAL SUBSCRIPTION: Home and Overseas, £1 6s. 0d.; U.S.A. and Canada, \$4.50.

BRANCH OFFICES:

Birmingham: King Edward House, New Street, 2.
 Coventry: 8-10, Corporation Street.
 Glasgow: 26B, Renfield Street, C.2.
 Manchester: 260, Deansgate, 3

In This Issue

EDITORIAL COMMENT	41
MIDLANDS TELEVISION STATION	42
NEW SUB-MINIATURE VALVES. By C. C. Gee	46
OUTPUT IMPEDANCE CONTROL. By Thomas Roddam	48
TEST REPORT: DENCO DCR19	50
IONOSPHERE REVIEW. By T. W. Bennington	53
SHORT-WAVE CONDITIONS	56
WORLD OF WIRELESS	57
FILTERS—2. By "Cathode Ray"	61
UNBIASED. By "Free Grid"	66
AIR-SEA RESCUE UP-TO-DATE. By Basil R. Clarke	67
MIDGET 3-VALVE A.C. MAINS RECEIVER. By S. W. Amos	68
NEW BOOKS	70
PREFERRED-VALUE ATTENUATORS. By E. W. Berth-Jones	71
MARINE COMMUNAL AERIALS	73
CONCENTRIC DUPLEX LOUDSPEAKER	74
LETTERS TO THE EDITOR	75
RANDOM RADIATIONS. By "Diallist"	78
MANUFACTURERS' PRODUCTS	80

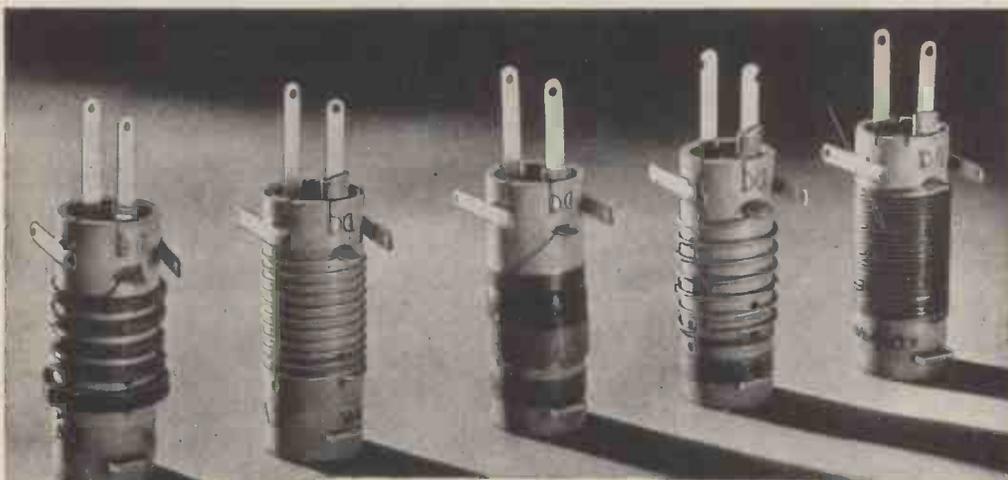


WEARITE COIL PACKS

"P" COILS

... for Aerial, R.F., and Oscillator Tuning and readily available in all ranges.

WRIGHT & WEARE LIMITED
 138 Sloane Street, London, S.W.1.

Telephone: SLOane 2214 S.
 Factory: South Shields, Co. Durham

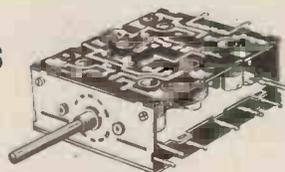


Send 6d. in stamps for the "Wearite" COILPACK Book of Technical Data and Circuits.



Valves and their applications

USE OF EF37A TO MEASURE HIGH RESISTANCE

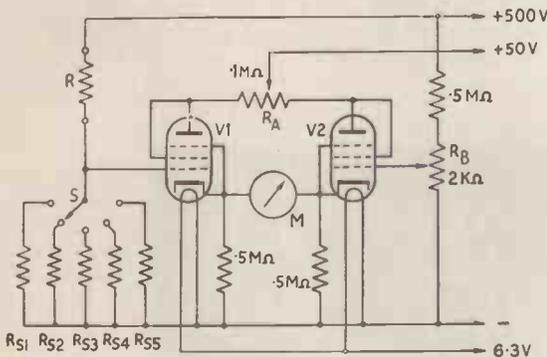The measurement of resistances of many millions of megohms generally involves the use of a special valve such as an electrometer triode. When the resistance to be measured is somewhat lower, say below one million megohms, a much simpler arrangement is possible and a conventional valve may be used provided its input impedance is sufficiently high. A suitable circuit for this purpose is shown below:



The circuit is essentially a bridge. The reference resistors R_{S1} , R_{S2} , R_{S3} . . . may for convenience be made equal to 1,000, 10,000, 100,000 . . . 10^9 ohms; they are selected by means of a high-grade switch S, preferably ceramic-insulated. Both valve grids are initially earthed by means of a further bank on switch S (not shown) and the potentiometer R_A is adjusted to give zero current in the microammeter M. Switch S is then set so that the grid-to-ground resistance R_S of V_1 is of the order of one-thousandth of the resistance R to be measured. By this means a voltage of between 0.15 and 1.5 volts is applied to the grid of V_1 and by setting R_B to the appropriate value a balance will again be obtained. If the potentiometer R_B is suitably calibrated it will then be possible to read off the value of R as the product of the reading of R_B and the value of R_S .

The simplicity of the arrangement will be apparent. Its usefulness is, however, restricted by the fact that for large values of R_S grid current flowing in V_1 may disturb the calibration. In order to minimise this effect it is convenient

to use a valve such as the EF37A whose grid-current is low and to select suitable operating conditions. Using EF37A's in the circuit shown, this grid-current is a negative current (electrons flowing from grid to cathode within the valve) and is made up of

- (1) ionisation current
- (2) grid emission
- (3) leakage currents

Ionisation current increases with anode current and also with the velocity of the electrons constituting the anode current, i.e. with anode voltage. It is therefore desirable for V_1 (and also V_2) to operate at low anode current and voltage. Grid emission results largely from the fact that the grid is warmed by the neighbouring cathode, and is dependent on cathode temperature, proximity of control grid, etc. Leakage currents may occur either inside or outside the glass envelope; from the standpoint of internal leakage it is again desirable to work at low voltages while insofar as external effects are concerned it is important to ensure that the surface of the glass is kept clean and dry.

The requirements outlined in the last paragraph are largely satisfied by the circuit shown. Furthermore, a special version of the type EF37A is available which operates at low heater voltage and, consequently, low cathode temperature. Using this valve under the above conditions the grid current is less than ten micro-microamps. This valve is known as type ME 1400.

A D.C. amplifier may be used between the bridge circuit and the meter. This gives increased accuracy and permits the use of a robust and inexpensive meter. With such a circuit measurements can be made up to one million megohms with somewhat lower accuracy.



Reprints of this report together with additional circuit notes are available, free of charge, from the address below.

MULLARD ELECTRONIC PRODUCTS LTD.,
TECHNICAL PUBLICATIONS DEPARTMENT,
CENTURY HOUSE, SHAFESBURY AVE., W.C.2
(MVM 119)

These Valves make News!

RELEASE OF B9A (Noval) Types

A complete new range of double triodes especially designed for television and industrial applications. Each type features separate cathode connections and centre tapped heaters for operation on AC or AC/DC supplies.



Bulb diameter $\frac{7}{8}$ in. max.
Seated height, $1\frac{1}{2}$ in. max.

TYPE 12AT7

Heater Voltage	6.3	} or {	12.6 volts.
Heater Current	0.3		0.15 amp.
Anode Voltage	300 volts max.		
Anode Dissipation	2.5 watts max. per section.		
Mutual Conductance	6.6 mA/Volt.		
Amp. Factor	62		

Application :—As Oscillator up to 600 Mc/s. Frequency changer up to 450 Mc/s.

TYPE 12AU7

Heater Voltage	6.3	} or {	12.6 volts.
Heater Current	0.3		0.15 amp.
Anode Voltage	300 volts max.		
Anode Dissipation	2.75 watts max. per section.		
Cathode Current	20 mA. max. per section.		
Mutual Conductance	3.1 mA/V.		
Amp. Factor	19		

Application :—Oscillator, phase inverter and A.F. amplifier.



Bulb diameter, $\frac{7}{8}$ in. max.
Seated height, $1\frac{1}{2}$ in. max.



Bulb diameter, $\frac{7}{8}$ in. max.
Seated height, $1\frac{1}{2}$ in. max.

TYPE 12AX7

Heater Voltage	6.3	} {	12.6 volts.
Heater Current	0.3		0.15 amp.
Anode Voltage	300 volts max.		
Anode Dissipation	1.0 watt max. per section.		
Mutual Conductance	1.6 mA/V.		
Amp. Factor	100		

Application :—A.F. Amplifier and phase inverter in high gain circuits.

BRIMAR

TECHNICAL ADVICE SERVICE

WRITE NOW TO DEPT. 4530 for data sheets on the above valves.

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.

RECORD NEWS...

for MUSIC LOVERS &
those seeking faithful reproduction

A revelation awaits every serious gramophone user and connoisseur of true fidelity who has not yet heard his records reproduced via the **acos G.P.20 NEW-TRUE Fidelity Pick-up**. Revolutionary in design—and in appearance too—the G.P.20 assures a tonal quality and a brilliance hitherto associated only with laboratory instruments. Moreover, this outstanding performance is attained WITHOUT RECOURSE TO EQUALISERS or other extra components—just connect it to your radiogram or amplifier. Ask your dealer for a demonstration.

With these unique revolutionary features:

Output $\frac{1}{2}$ v. at 1,000 c.p.s.
—5 to 20 times greater
than comparable
magnetic types.



Automatic bass-boost
—can be fitted to any
domestic radio without
additional equalisers.



Needle talk and motor
rumble negligible.



Low needle pressure—
13 grms. — virtually
eliminates record wear.



Unbreakable and non-
hygroscopic crystal
element.



Permanent sapphire
stylus eliminates needle
change.

acos

**GP20 NEW TRUE
FIDELITY PICK-UP**



PRICE **£2 · 10** Plus 21/5
Purchase Tax

Heavy export commitments have severely curtailed supplies to the home market—a position which is rapidly being remedied by increased production, but in the meantime we ask your indulgence.


COSMOCORD LIMITED · ENFIELD · MIDDX

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

The "Belling-Lee" Mobile Research Unit

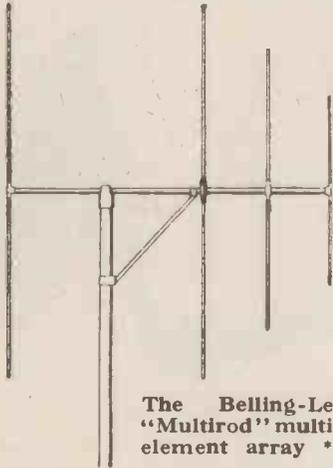For many months we have had this unit in commission, touring the country taking field strength measurements, polar diagrams of aerials etc. It is fully equipped for work of this kind, and has been examined by numbers of technically interested people in locations as far apart as Stoke-on-Trent and Bristol. Early in the New Year this research unit



The Belling-Lee "Multirod" multi-element array *1

will start out on a planned tour of the fringe areas of Sutton Coldfield with a view to obtaining authoritative information as to reception conditions in various localities. The same aerial system will be used for all tests at a constant height (30ft.) from the ground to ensure uniformity of conditions. Field strength measurements will be taken and reception received on two standard communal receivers having respective peak white sensitivities of 50 and 150 microvolts. From the results we will be able to state, with considerable assurance, the general reception potentialities of the district taking into consideration high and low topographical locations.

This survey should give a fair indication of the most likely types of aerials which should be stocked by dealers in order to cope with local variations of signal strength.

This information will be made available to everyone as soon as it comes to hand.

"H" Type or Simple Dipole.

We are constantly reading provincial and other press notices where writers deprecate the selling of "H" type aerials within, say, twenty miles from a television transmitter. We agree most heartily, but we feel it quite wrong to make such a statement without qualification. A simple dipole, outdoor or indoor, is useless where interference is strong, regardless of the distance from the transmitter. We know of many cases within a few miles of Alexandra Palace, where an "H" type


is essential to combat interference, and we all know there is a lot of interference. We also know of indoor aerials giving every satisfaction in residential parts of Southend, thirty miles away. In our opinion quite as much harm can be done by the erection of a single dipole in the wrong place, resulting in a bad picture, as by erecting an "H" type which would give a clear picture. When we have to recommend an "H" type relatively close to a transmitter, and to combat interference, we suggest our lightweight range with 0.15 wave-spacing*2. It is quite unnecessary to instal a senior quarter-wave spaced "H" for the reduction of interference in localities of strong signal.

Strong Signal on "Doorod"

Reports have come in of too strong signal on "Doorods" *3. It should be quite unnecessary to fit attenuators to such aerials. If the flexible element is fixed at right angles to the vertical element, i.e. horizontal, the "Doorod" will only have half the pick-up. The flexible element may be folded, or brought still closer to the vertical element



FLEXIBLE MEMBER

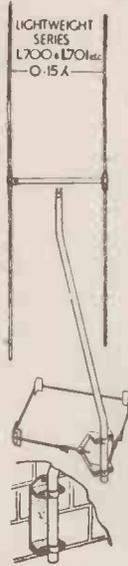


LIGHTWEIGHT SERIES L700 & L701 etc. 0.15λ

to cut down the efficiency still further. To quote an extreme case, if used as an inverted "V" and orientated at right angles to the transmitter, little or no signal should be received.

"Coronette"

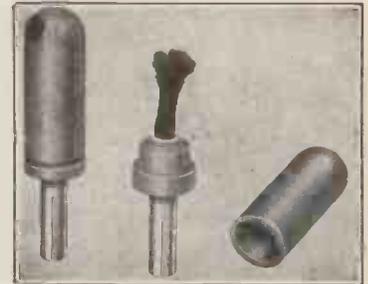This silent aerial discharger is gaining in popularity. We heard that in the Bristol area a good vertical aerial installation was always a source of potential trouble from rain static until the "Coronette" *4 made its appearance. In this area our informant told us



The Coronette silent aerial discharger

that they were a hundred per cent effective. From the report we would judge that the intensity of rain static is not so severe in this area as in some other districts. The "Coronette" reduces the trouble by some 40 db's. If the interference is very severe, the residue may still be troublesome.

*1 "MULTIROD" multi-element array for fringe areas with 14ft. x 2in. dia. light alloy mast.

London L698, Midland L699, £13 18s. 0d.

*2 "VIEWROD" 0.15 spaced "H" type aerials.

London L700, Midland L701. With suffixes below.

-/C for own mast, 50s.

/W Mast, wall fixing, 75s.

/L Mast, 1 lashing, 87s. 6d.

*3 "DOOROD" full sized half-wave television aerial for use indoors.

London L645, Midland L678. With suffixes below.

/1 with coaxial feeder, 30s.

/2 with balanced twin, 26s. 6d.

*4 "CORONETTE" silent aerial discharger.

L643, 4s. 9d.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND


EDISWAN
SPECIAL PURPOSE
VALVES



Smaller Vacuum Thermal Delay Switches

These two new delay switches are recommended for use wherever a switching delay of 30-180 secs. is required. They have been developed for use in applications similar to those of the EDISWAN DLS10 but, in line with modern equipment design — which makes the physical size of the switches of prime importance — the dimensions have been reduced to the minimum compatible with reliability and ruggedness.

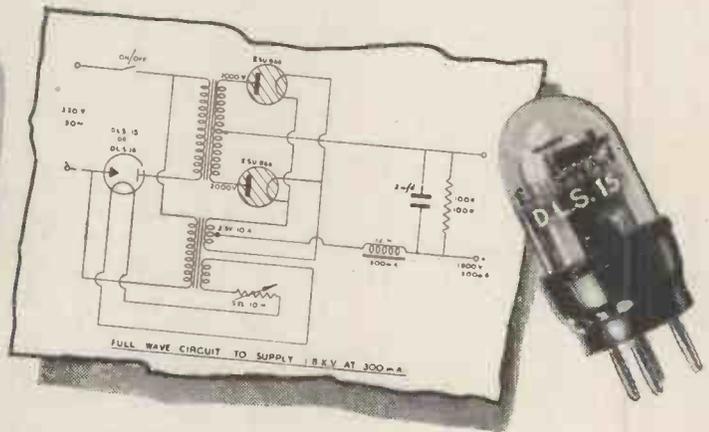The DLS15 is intended as a plug-in replacement for the DLS10 while the DLS16 fulfils the demand for a delay switch with a 6.3v heater and an International Octal base.



DLS15 Rating.

Filament Voltage (volts)	4
Filament Current (amps)	0.75*
Delay time at 4 volts (secs.)	Min. 30 ;	Max. 90	
<i>(Delay time may be increased to 180 secs. by variation of filament voltage)</i>				
Maximum Peak Current (low voltage rating)				5 amps at 240v.
Maximum Peak Current (high voltage rating)				100mA at 1 kv.
Maximum overall length (not including pins)	60 mm.			

*at approximately 4 volts

DLS16 Rating.

Filament Voltage (volts)	6.3
Filament Current (amps)	0.48*
Delay time at 6.3 volts (secs.)	Min. 30 ;	Max. 90	
<i>(Delay time may be increased to 180 secs. by variation of filament voltage)</i>				
Maximum Peak Current (low voltage rating)				5 amps at 240v.
Maximum Peak Current (high voltage rating)				100mA at 240v.
Maximum overall length (not including pins)	65 mm.			


*at approximately 6.3 volts

EDISWAN



HIGH QUALITY REPRODUCTION

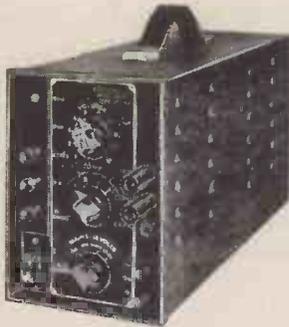"FIFTY and THIRTY WATT" CINEMA AMPLIFIERS as illustrated for single or double P.E.C. input with separate adjustable bias. Full range of tone controls to suit all needs with built-in Exciter Supply if required. PRICES range from **34½ gns.** to **42½ gns.**



TYPE C.P. 20A AMPLIFIER

For AC Mains and 12 volt working giving 15 watts output, has switch change-over from AC to DC and "Stand-by" positions. Consumes only 5½ amperes from 12 volt battery. Fitted with mu-metal shielded microphone transformer for 15 ohm microphone, provision for crystal or moving iron pick-up with tone control for bass and top. Outputs for 7.5 and 15 ohms. Complete in steel case with valves.

PRICE **£28 . 0 . 0.**

FOUR-WAY ELECTRONIC MIXER

This unit has 4 built-in balanced and screened microphone transformers, normally of 50-30 ohms impedance. It has 5 valves and selenium rectifier supplied by its own built-in screened power pack consumption 20 watts. Suitable for recording and dubbing, or large P.A. Installations since it will drive up to six of our 50 watts amplifiers whose base dimensions it matches. The standard model has an output impedance of 20,000 ohms or less, and any impedance can be supplied to order. PRICE **£24 . 0 . 0.**



OTHER MODELS IN OUR RANGE OF AMPLIFIERS

- "SUPER-FIFTY WATT" - - - - - PRICE **36½ gns.**
- "THIRTY WATT" - - - - - " **30½ gns.**
- "10-15 WATT RECORD REPRODUCER" " **25½ gns.**

These are fitted in well ventilated steel cases with recessed controls, as illustrated.

*Full details upon request,
EXPORT ENQUIRIES INVITED.*

VORTEXION LIMITED, 257-261 THE BROADWAY, WIMBLEDON, LONDON, S.W.19

Telephones : LIB 2814 and 6242-3

Telegrams : "Vortexion Wimble, London."

"YANKS ROLL IN LIKE LOCALS"

WHEN YOU HAVE A "D.X. PLUS TWO FEEDER UNIT" working in conjunction with the "TONEMASTER AMPLIFIER."

Every feature to ensure good listening is incorporated in this equipment, including Tone Controls, and Master Volume Controls brought out to a separate panel to facilitate mounting.

THE "D.X. PLUS TWO FEEDER UNIT" covers from 5 to 2,000 metres in five overlapping steps, plus infinitely variable selectivity, tuning indicator, etc.

THE "TONEMASTER" AMPLIFIER incorporates push-pull output, negative feedback and separate electronic tone control circuits.

OVERALL COST £44.10.0 plus purchase tax.



SOUND SALES' PRODUCTS are backed by 12 MONTHS' GUARANTEE, plus 20 years' experience in the manufacture of electronic equipment.


Sound Sales Limited

London Office, Demonstrations—LLOYDS BANK CHAMBERS, 125, OXFORD STREET, LONDON, W.1.

Telephone: Gerrard 8782.

Head Office and Works—WEST STREET, FARNHAM, SURREY. Farnham 6461/2/3.

CO-AX AIR-SPACED ARTICULATED R.F. CABLES

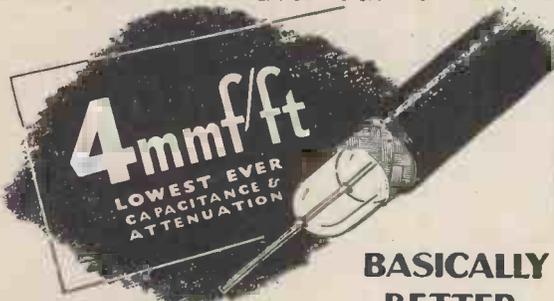

IMMEDIATE DELIVERIES FOR HOME & EXPORT

HIGH POWER FLEXIBLE

LOW ATTN. TYPES	IMPED. OHMS	ATTEN. db/100 ft. at 100 Mc.	LOADING $\frac{Kw}{100 Mc.}$	O. D.
A.1	74	1.7	0.11	0.36
A.2	74	1.3	0.24	0.44
A.34	73	0.6	1.5	0.85

FOR RADIO FREQUENCIES

PHOTOCELL CABLE

LOW CAPAC. TYPES	CAPAC. mm/ft.	IMPED. OHMS	ATTEN. db/100 ft. 100 Mc.	O. D.
C.1	7.3	150	2.5	0.36
P.C.1	10.2	132	3.1	0.36
C.11	6.3	173	3.2	0.36
C.2	6.3	171	2.15	0.44
C.22	5.5	184	2.8	0.44
C.3	5.4	197	1.9	0.64
C.33	4.8	220	2.4	0.64
C.44	4.1	252	2.1	1.03

FOR VIDEO and SPECIAL APPLICATIONS

VERY LOW CAPACITANCE CABLES

Write for data sheets to the originators of air-spaced R.F. Cables.

TRANSRADIO LTD.
CONTRACTORS TO H.M. GOVERNMENT.

138A CROMWELL ROAD
LONDON, S.W.7.



PLAN YOUR CAREER

RADIO - TELEVISION and other INDUSTRIAL ELECTRONIC subjects
ELEMENTARY & ADVANCED COURSES

DAYTIME

- Principles and Practice of Radio—1 year.
- Telecommunication Engineering—2 years.
- Electronic Engineering—3 years (including one year's practical training in E.M.I. Factories)—leading to C & G full Technological Certificate. (Next courses begin April 1950)
- Marine and Air Radio Officers' Course (for P.M.G. Licence).

also HOME STUDY

- Basic Radio • Basic Television • Industrial Electronics • Maths. • Physics.

Write for FREE BOOKLET to Dept: 16a

E.M.I. INSTITUTES

10 PEMBROKE SQUARE, NOTTING HILL GATE, LONDON, W.2
Telephone: BAYswater 5131/2.

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC.



**The
WESTON
S.75
Multi-Range
Test Set**

53 Ranges with Rotary Switch Selection

This uniquely comprehensive Test Set has 53 ranges for measuring AC and DC current and voltage, resistance and insulation. It is completely self-contained, with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500 v. Selection is carried out by two 20-position switches. A fully protective safety device is fitted and is operative for forward or reverse overload. The 150 division 6" scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89 covering first grade instruments. Full details of this, and other Weston electrical measuring instruments will gladly be supplied on request.


**SANGAMO WESTON LIMITED
ENFIELD, MIDDLESEX**

TELEPHONE: ENFIELD 3434 (6 LINES) AND 1242 (4 LINES)

AREA DEPOTS:

- 201 St. Vincent Street, Glasgow.
- Milburn House, Newcastle-on-Tyne.
- 22 Booth Street, Manchester.
- 33 Princess Street, Wolverhampton.

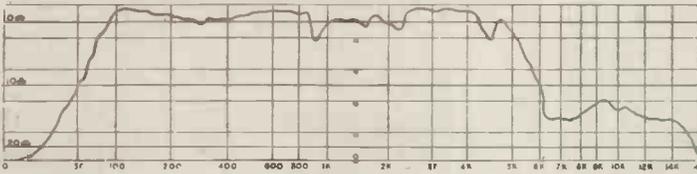
- Central 6208
- Newcastle 26867
- Central 7904
- Wolverhampton 21912



The above curve will show you at once why this new twin-reproducer, incorporating two independent loudspeakers, has been so enthusiastically welcomed by quality fans.

Never before has so wide a range been covered so evenly by a small domestic instrument. Although moderately priced, this is a high-fidelity speaker in the best sense of the word. Leaflet on application, with pleasure.

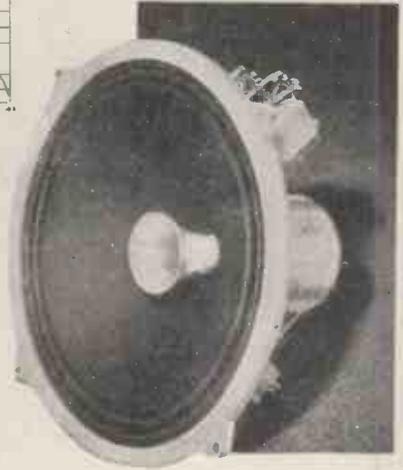SPECIFICATION: Series Gap magnet of Alcomax 3.
 Flux in LF gap 12,000 gauss on 1" pole
 " " HF " 13,000 gauss " " "
 Power handling capacity, 6 watts. Frequency range 50-14,000 c.p.s. Fundamental bass resonance, 65 c.p.s.



PRICE £6-6-0

Complete with matching transformer and filter condenser.

De Luxe table cabinet model £11.30

Corner console model, less transformer - - - £12.12.0



Stentorian Concentric Duplex

HIGH FIDELITY REPRODUCER

WHITELEY ELECTRICAL RADIO CO. LTD · MANSFIELD · NOTTS · ENGLAND

TELEVISION MINDED?

**Improved Postal Course at
Greatly Reduced Price**

In view of the rapidly increasing interest in Television and our large number of enrolments, we have reduced the price of our **BASIC TELEVISION POSTAL COURSE** by 25%. At the same time the scope of the course has been increased by including comprehensive material dealing with the latest television receiver techniques.

The course covers the examination for the Television Service Engineer's Diploma set jointly by the Radio Trades Examination Board and the City & Guilds Institute.

Where desired, selected lessons are available at an appropriately reduced price. Many other courses in **RADIO, MATHEMATICS, INDUSTRIAL ELECTRONICS**, etc. are available.

Write for **FREE BOOKLET** to Dept. 16,

E.M.I. INSTITUTES

10, PEMBRIDGE SQ., NOTTING HILL GATE, W.2
 Tel. - BA Yearwater 5131/2

Associated with
 "H.M.V."
**MARCONIPHONE
 COLUMBIA
 ETC.**

BI38

MODERN PRACTICAL RADIO AND TELEVISION

This work covers every phase of Radio and Television Engineering from many viewpoints and meets a great demand. The author, C. A. Quarrington, A.M. Brit., I.R.E., with a long and wide experience of Radio Engineering, has been responsible for training a large proportion of the Radio and Television Service Engineers in this country, and is also well known as a lecturer on Radio and Cathode-ray subjects to Universities, Radio Societies, Trade Associations and other interested bodies throughout the country.

It is impossible to detail even briefly in this small space the exhaustive ground covered by this comprehensive work, but the pamphlet we can send you will show you that these few remarks are no exaggeration.

THE ILLUSTRATIONS

"Modern Practical Radio and Television" is profusely illustrated. It contains 16 full-page plates, over 400 diagrams in the text and 7 large folding insets. Each illustration has been specially selected for its practical utility.

SEND FOR FREE PAMPHLET

To THE CAXTON PUBLISHING CO., LTD., 42, Clun House, Surrey Street, London, W.C.2.

Please send me, free of charge, Pamphlet describing "Modern Practical Radio and Television."

Name.....
 (Send this form in unsealed envelope) (1d. stamp)

Address

N.2

NATIONAL PHYSICAL LABORATORY REPORT

On tests of 12 watt amplifier
marked: "POINT ONE", TL/12, H. J. LEAK & CO. LTD.

Ref. E.388.150. Aug. 30th., 1949

Test Conditions. In all cases the input was applied to a $50,000\Omega$ resistor connected to the amplifier by 3 feet of screened cable. The output load was in all cases a resistor of 18Ω and the output transformer secondary windings were connected for the " $15\Omega - 20\Omega$ " condition.

HARMONIC DISTORTION.

0.03% for 10 watts output at 1,000 c/s.
0.1% for 10 watts output at 60 c/s.
2nd and 3rd harmonics predominated, and were approximately equal in magnitude.

HUM AND NOISE.

-80 db. referred to 10 watts.

SENSITIVITY.

148 mV.r.m.s. input gave 12 watts output at 1000 c/s.

LOAD DAMPING FACTOR. (Load impedance/output impedance).

42 for 10 watts output at 1,000 c/s. (Output impedance 0.43Ω).
45 for 2.5 watts output at 1,000 c/s. (Output impedance 0.40Ω).
The output impedance was found to be substantially resistive.


FREQUENCY RESPONSE.

Gain relative to that at 1,000 c/s. measured at 7.5 watts output, including the losses introduced at the higher frequencies by the capacitance of the input cable shunting the input resistance of $50,000\Omega$.

c/s.	db.
20	+0.1
60-1,000	0
5,000	-0.1
10,000	-0.3
15,000	-0.4
20,000	-0.7

WRITE FOR BOOKLET W/TL/12 which explains how these results are achieved.

THE LEAK DYNAMIC PICK-UP

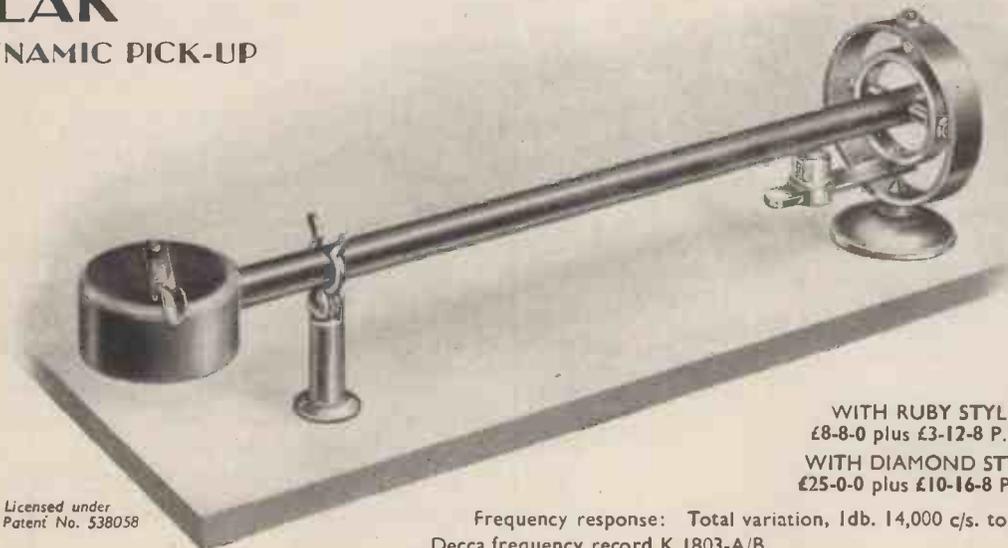

Licensed under
Patent No. 538058

WITH RUBY STYLUS
£8-8-0 plus £3-12-8 P. TAX
WITH DIAMOND STYLUS
£25-0-0 plus £10-16-8 P. TAX

Frequency response: Total variation, 1db. 14,000 c/s. to 40 c/s. from Decca frequency record K.1803-A/B.

In mechanical detail and electrical performance the LEAK DYNAMIC PICK-UP is as far ahead of other pick-ups as the LEAK "POINT ONE" TL/12 AMPLIFIER is ahead of other amplifiers.


WRITE FOR LEAFLET W/P.

BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3

Phone: SHEpherds Bush 5626.

Telegrams: Sinusoidal, Ealux, London.

Foreign: Sinusoidal, London

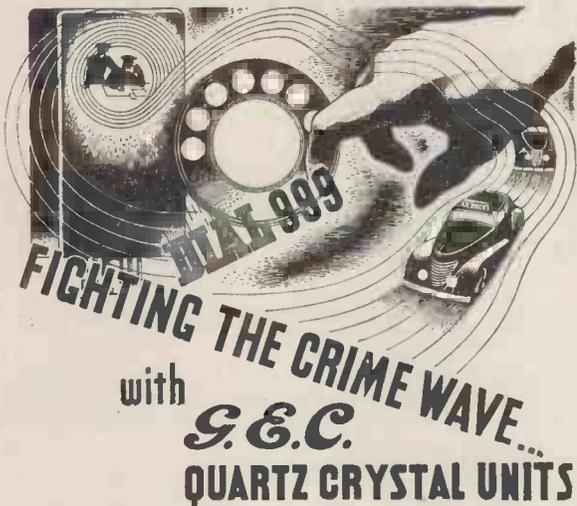

The Police "999" emergency call system depends for its successful operation on instantaneous radio communication between Police headquarters and the fleet of patrol cars. Radio equipment in the patrol cars is used under the most arduous conditions but it must be available for instant use 24 hours in the day.

No wonder then that more and more Police authorities throughout the country are using G.E.C. quartz crystals in their radio equipment.

Pioneering research and experience in making over a million units, ensure a product of the highest quality. For all your quartz crystal requirements be sure to specify G.E.C.

Quick delivery service for urgent requirements for experimental or replacement purposes.

Write for our leaflet QC.4904.



SALFORD ELECTRICAL INSTRUMENTS LTD
PEEL WORKS, SILK STREET, SALFORD 3, LANCs.

A Subsidiary of

THE GENERAL ELECTRIC CO. LTD., OF ENGLAND

LAWRENCES

NEW RADAR EQUIPMENT

MODEL VG RADAR INDICATING EQUIPMENT, TYPE CG-55AEB.

Designed and produced by the General Electric Co., U.S.A., for installation in ships or shore stations. This Projection Type Plan Position Repeater performs a duty similar to the conventional P.P.I., except that the pattern is optically projected on to a large flat horizontal surface, instead of being observed directly on a cathode ray tube face. The complete unit is approximately the size of a desk, 35in. high, with the viewing screen occupying half of the top surface, and is operated as a plotting table, on which the actual map-in-motion is portrayed. Navigational calculations are made directly on the paper viewing screen, which can be replaced at will from the built-in 30 yard roll supply.

The full screen may be employed to map an area of 4, 10, 20, 80, or 200 mile radius, the choice of range being made by a range selector switch. Electronically generated range marks divide the screen into concentric rings for ranging purposes. In addition, two bearing scales are projected on to the screen, one being fixed to present true or relative bearing, the other rotating to present heading. The radar pattern is therefore far more significant, because it can be observed simultaneously with the pattern of actual bearing.

The equipment is designed for operation with any radar system, of repetition rates of from 60 to 1,000 per second, and only very limited arrangements are necessary to provide the video, trigger and synchro inputs.

BRIEF TECHNICAL SPECIFICATION

Power requirements: 115 v. A.C. Single phase, or 230 v. with auxiliary transformer. Total consumption 1765 watts.

Input requirements: Trigger voltage 5-40 volts peak. Video voltage 3 volts peak max.

Ambient Temperature Limits of Operation: 0°C to +50°C.

Screen Diameter: 25½ in.

Picture Diameter: 24 in.

Image Visibility: Image on Projection Screen may be observed in the presence of approx. 1 foot candle of Indirect lighting.

Optical System: Highest grade components by Bausch & Lomb.

Range Accuracy: ±1% of total designated range.

Bearing Accuracy: Within .75 degrees.

Overall Dimensions: 59 in. x 34 in. x 35 in.

Weight unpacked: 1,000 lb.

The exceptional quality of construction, together with the numerous operational advantages, are several of many features which make this advanced equipment of outstanding interest in the field of Radar Engineering.

MODEL VE RADAR INDICATING EQUIPMENT, TYPE CAY-55ADV. Manufactured by The Westinghouse Mfg. Co., U.S.A., for installation in ships or shore stations. A Plan Position Indicator Repeater of conventional type, employing a seven inch electro-magnetic cathode ray tube. Instrument is fully enclosed in console type housing.

BRIEF TECHNICAL SPECIFICATION.

Power requirements: 115 v. A.C. Single phase, or 230 v. with auxiliary transformer.

Range Calibrations: Electronic, with switched selection of ranges 4, 20, 80, 200 miles radius.

Overall Dimensions: 13 in. x 24 in. x 26 in.

Full technical details of the above equipments available on request from :

LAWRENCES, 61 BYROM ST., LIVERPOOL 3

Phone: CENTral 4430

UNIVERSITY RADIO, LIMITED

Offer Guaranteed Used Equipment at Attractive Prices

AR88-LF in perfect condition, complete with all valves. A.C. 110-230 v. £37 10 0

AR88-LF Chassis, with all valves, in perfect condition. No cabinet £25 0 0

R.M.E.69, with Pre-selector and Speaker, perfect, and complete with all valves, etc. £25 0 0

2 only R208's. Complete with all valves. Perfecteach £12 0 0

BC348, unconverted, perfect with all valves £15 0 0

As above, converted to A.C. mains 200-250 v. £15 0 0

BC342, converted to A.C. mains, 200-250 v. £15 0 0

Ex-W.D. U.S.A. SCR625 Mine Detectors, complete less batteries. A few only each £9 0 0

Avo 1948 Model Battery All-wave Signal Generator, as new, with batteries £10 10 0

As above, case scratched, but good condition and working order £8 0 0

Avo Signal Generator, as new. A.C. mains, 200-250 volts £11 0 0

Taylor Circuit Analyser, Model 20A, as new £11 0 0

R.C.A. 'Scope, in new condition. 110 volts, A.C. £20 0 0

Taylor A.C.-D.C. Test Meter Model 70A, as new £7 10 0

Taylor A.C.-D.C. Test Meter, Model 90A, as new £10 0 0

Taylor A.C.-D.C. Valve Tester, Model 45A, as new £14 0 0

Taylor A.C.-D.C. Valve Tester, Model 47AP, as new £18 10 0

Avo 7's, in perfect working order. As new £13 0 0 (Leather cases £2 extra).

Hunt's Capacity and Resistance Bridge, model CRB. As new ... £11 0 0

1948/9 Model Charles Amplifier in perfect condition. Complete with all valves £10 0 0

Plessey Record-Change, listed £14/10/-. Our Price £9 10 0

Roger's Development Co. Junior Amplifier, cost £19/19/-. complete with all valves, Also Radio Feeder Unit, which cost £9/10/-. Both items as new. Our price for the pair £17 10 0

Collaro Bsr Type Mixer-changers, As new £12 0 0

Vitavox Pressure Unit, 20 watt type G.P.I. As new £6 0 0

E.D.C. & Ward Rotary Converter, 200-250 volt D.C. 230 A.C., 50 cycle, in cabinet with Filter Unit. 120 watts £10 10 0

As above, 250 watts £14 0 0

As above, 300 watts £15 0 0

Auto-transformers,, Ex-W.D. U.S.A. 115 to 230, 50 cycle 2.2 kVa Transformer 200-250 volts A.C. 6/9/12 volt, 90 amp. A first class job £4 10 0

GB-L516 16 mm. Silent or Sound on Film Projector, A.C./D.C. 110 volt. Less speaker and step down resistance. Almost new £75 0 0

Another GB-L516, complete and perfect in every detail, with 8ft. 6in. screen. Absolutely ready to use. £89 10 0

S.T.C. Ball Mikes. Type 4021C. High quality Recording mikes. Used by all the leading recording studios. As new, each £5 5 0

WE NEED GOOD USED EQUIPMENT URGENTLY. PLEASE SEND, BRING OR PHONE FOR OFFER

Taylor 65B Signal Generator, as new £11 10 0

1948 B.P.L. All-wave Signal Generator. As new £10 10 0

Advance E-I Signal Generator, as new £15 0 0

Ex-W.D. Marconi U.H.F. Signal Generator, type TF517E, with Power-pack. In perfect condition and working-order £25 0 0

Ex-W.D. U.S.A. Bendix U.H.F. Signal Generator, type 1/130/A As new with all leads, etc. £18 10 0

WE HAVE OTHER TYPES ARRIVING DAILY FROM £6.

Evershed's 500 volt Wee Meggers in leather cases. As new £8 10 0

Others, less cases (500 volt) £6 10 0

250 volt Wee Meggers £4 10 0

Evershed's 100 volt Wee Megger and Megger Ohm-meter, in leather case. As new £7 10 0

Evershed's 500 volt Bridge Megger in leather case. Cost £48. Our price, in new condition £20 0 0

As above, in perfect working order, but case slightly soiled £15 0 0

Evershed's 500 volt Meggers, in aluminium case £11 0 0

Record Wee Meggers, 500 volt, in leather cases. In perfect condition, each £7 10 0

Brand new Deschophone inter-comm. set. Master Unit with four extensions. Cost £27/10/-. Complete with all valves, etc., A.C. and D.C., 200-250 volts. ... £13 10 0

Taylor 313C Capacity and Inductance Adaptor, as new £3 0 0

Taylor Capacity and Resistance Bridge, model 110A, as new ... £8 0 0

Taylor 85AP Test Meter, as new £14 10 0

Taylor 'Scope, model 30, in perfect condition and working-order £16 10 0

Pam 25 watt Amplifier, complete with 2 Pam Speakers and Pam Gramo' Player unit. In perfect working order. The lot £31 0 0

H.M.V. 10 watt 'gram Amplifier in metal case, one only, in perfect working order. A.C. 200-250 volts. A real bargain £10 10 0

Pullin Series 100 A.C./D.C. Test Meter, 10,000 (Ten Thousand) O.P.V. As new £7 10 0

12 to 15 Watt Parmeko Mobile Amplifier, Ex-W.D. in grey metal cases. Complete with all valves and mike (hand). Each £11 0 0

Webb's Pre-selector, as new. With coils, valves, etc. Complete with 5-10 meter Adaptor, and separate Power pack for both ... £15 0 0

Supreme (U.S.A.) Valve-Tester and A.C./D.C. Test-Meter, combined in portable case with valve charts. 200 250 volts A.C. As new £17 0 0

Triplet as above, 110 volts A.C. £12 10 0

Vitavox 10 Watt Pressure Unit type B. Perfect £3 10 0

Vitavox Pressure Unit, 20 watt, type N, Perfect £5 0 0

Vitavox K-12-20 Speaker. As new £6 0 0

Vitavox K-12-10. As new £4 0 0

Goodman's 12in. P.M. 15 ohm. As new £4 0 0

Goodman's Axiom 12, as new ... £5 17 6

Pye 6 volt Car Radio 14 guinea model. Perfect and complete ... £9 10 0

Supreme (U.S.A.) Diagnosticscope, Model 555, a complete Tester incorporating 'Scope, All Wave Signal Generator and Audio Sig. Gen. A.C. 200-250, 50 cycles. Perfect and complete in streamlined metal case, with all data sheets £25 0 0

B.P.L. latest model "Super Ranger" Test-Meter, 1000 O.P.V. As new. AC/DC £14 0 0

2 only, B.T.H. new 1/2 (one quarter) h.p. motors, 1,245 r.p.m. 400-440 volt A.C., 3 phase, each £4 0 0

Cintel (Cinema and Television) Power Pack, 20 25 kV., 5 mA. Complete in metal case, as new ... £12 0 0

Crypton Battery Charger, Model A31F5A513, 200-250 volts A.C., 36 cells at 1 amp. In new condition £13 0 0

1 only twin Turntable Cabinet. Beautifully finished in oak. With motor-board. Brand new £4 10 0

1 only Decca Decaloon, in perfect condition and working order. Complete. (Not record changer.) Cost £35 £21 0 0

Sound Sales Cabinet and Speaker, in perfect condition... £8 10 0

Weston E772, 20,000 O.P.V. A.C./D.C. Test Meter in portable case. As new £15 10 0

As above, 1,000 O.P.V. £12 0 0

C.D.P. Recording Units, less Amplifier. As new £23 0 0

Collaro AC/DC 'Gram Unit, motor and turntable. As new ... £6 10 0

3 only Garrard Mixer-changers. Model RC65/U-16C. Brand new. Tax paid £22 10 6

Avo 7's, as new £13 0 0

Cossor Ganging Oscillator, model 3343 with Data Book. In perfect condition £10 0 0

A SPECIAL BARGAIN !! Bell & Howell (U.S.A.) 16 mm. Sound on Film Projectors, complete and portable, with all parts, valves, speaker, cables, lens, etc., less step-down transformer. Believed in working order, but we cannot guarantee them so. We are prepared to exchange any faulty part. We consider these a genuine bargain. £57 10s. 0d. each.


CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE PAID.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

'Phone GERRard 4447 and 8582.

Hours 9 to 6.

Thursdays 9 to 1.

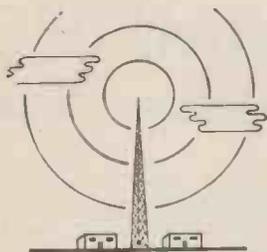


TELCON METALS

are used extensively for

RADIO & TELEVISION COMPONENTS

The value of MUMETAL for magnetic screening is well appreciated and shields for cathode ray tubes, transformers and other devices susceptible to stray magnetic fields are made in large quantities. Apart from producing a range of MUMETAL SCREENS for all normal applications, we undertake the manufacture of special screens, either in the form of DEEP DRAWN CANS for large quantity production, or hand fabricated assemblies for the shielding of apparatus of complicated shape. Whether the screening reduction is to be 10 dB, or 100dB, we can offer a solution, and the services of our technicians are always available. A list of standard sizes of screens will be sent on request. We also manufacture RADIOMETAL, RHOMETAL, H.C.R. ALLOY, TELCON BIMETAL, TELCON BRONZE (Beryllium - Copper), TELCUMAN and TELCOSEAL GLASS SEALING ALLOYS.

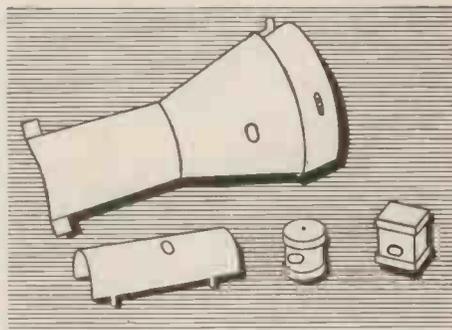

Ask also for details of
TELCON
R. F. CABLES


THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD

Head Office: 22 OLD BROAD ST., LONDON, E.C.2. Tel.: LONDON Wall 3141

Enquiries to: TELCON WORKS, GREENWICH, S.E.10. Tel.: GREENWICH 3291



RADIO EXCHANGE CO.

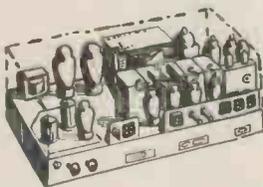

J. G. BRETT-JONES, of Bedford, presents the **WORLD'S CHEAPEST TELEVISION!** The S.L.C. receiver, with two R.F.s, four I.F.s, and all ancillary circuits, PLUS additional stages which will convert for Time Bases, is the ideal foundation unit, and with the addition of a mains transformer, VCR97, four condensers, three pots, one resistor and two J50s, can be converted into a self-contained vision receiver for approximately £8. The receiver only, 30/-, carriage paid. Conversion data, 3/- per copy.

RECEIVER TYPE 21. The ex-Army receivers, with six VP23s and three HL23DDs, function as a superhet from 4.2-7.5 m/cs. and as a double superhet from 18-31 m/cs. They require 120/150 v. H.T. and 6 v. L.T. Removal of filament dropping resistors will enable the set to be used with a 2 v. accumulator. Complete with circuit, 35/-.

W/S21 POWER UNIT. A small vibrator pack, designed for use with the Wireless Set 21, and operating from a 6 v. input. The 6 v. filament circuit of the receiver enables a small, complete unit to be fitted into one cabinet. . . . ONLY 18/6.

RF25s. The frequency changer stages of the 1355 . . . they may be used as a very efficient converter for receiving T.V. sound through your domestic all-wave receiver. ONLY 15/-.

MOVING COIL UNITS . . . separate moving coil headphone units, complete in bakelite cases, which may be used as midset speakers, microphones, etc., 45 ohms impedance, and made by various famous makers. TO CLEAR 2/- each. Balanced armature headphones, approx. 100 ohms, complete with headbands, 2/6 pair.



TELEPHONES D MK. V. Self-contained telephones with bell, buzzer and standard P.O. type handset. Ideal for intercom. purposes, 27/6 each.


I.F.F. TRANS-RECEIVERS. One of the best known surplus units . . . can be converted for 144 m/cs or will provide a goldmine of parts. Complete with 13 mains operated (6.3 v.) valves, and a 9 v. motor generator which can be converted into a mains motor. OUR PRICE, with mains motor conversion data, 22/6.

INDUATOR UNIT 188. A 3in. short persistence G.R.T. 48P61s, 3EA50s and dozens of pots, resistors, condensers, switches, etc., make this the ideal oscilloscope unit. Brand new, in sealed maker's cartons, £2.

VELOCITY TYPE SPEAKERS, really robustly constructed speaker units which, when correctly loaded with a horn, are capable of handling up to 50 watt, at high quality. OUB PRICE, £1 each.

NOISE LIMITER KITS. A complete sub-assembly, with all small parts ready to fit in your chassis. The instruction booklet, referring to a U.S.A.A.F. receiver, is sufficiently comprehensive to enable the unit to be fitted in ANY superhet. Price 3/6.

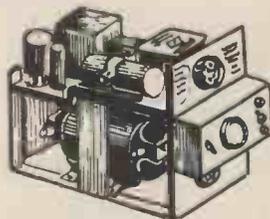POWER UNIT TYPE 19. Used with the famous W/S19, this unit consists of a motor generator delivering 840 v. at 40 mA., and 275 v. at 110 mA., PLUS a vibrator pack (OZ4 rectifier) delivering 275 v. Input is 12 or 24 v., and outputs are fully smoothed. TO CLEAR, 12/6.




RADIO EXCHANGE CO., (W),

9 CAULDWELL STREET,
BEDFORD. phone 5569

All goods sold as used
unless otherwise stated.


CLYDESDALE

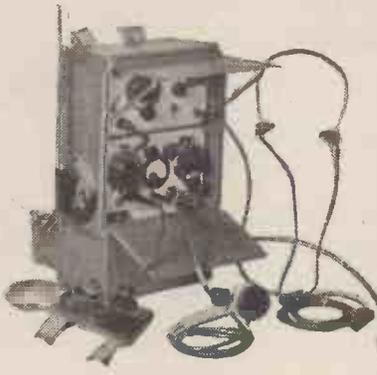Bargains in Ex-Services Radio and Electronic Equipment



HAND DRIVEN GENERATOR, supplying H.T. and L.T. plus 12v. bias (when switches for WS18) with operators seat, etc.
AERIAL, 10ft. Rod type (11 sections) range 5 miles R/T. 10 miles C.W. greater ranges can be obtained with a normal aerial. Plus, cables and **INSTRUCTION BOOK**. This equipment can also be used with dry batteries (not supplied) as a **PORTABLE WALKIE-TALKIE**.
 Power requirements H.T. 162v. 60 m/a. L.T. 3-1V. 0-3A.
 Dimensions : Set and battery container : 11½ x 10½ x 17½ in.
CLYDESDALE'S PRICE ONLY £14/10/0 CARRIAGE PAID

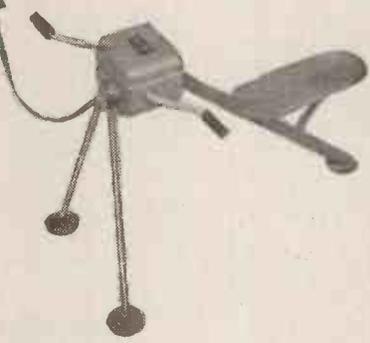In Maker's Original Packing.
WIRELESS SET No. 48 MK. I. Transmitter/Receiver
 American version of the No. 18 Set, modified to U.S. Army requirements.
 Frequency coverage, 6 to 9 mc/s—33.3 to 50 metres.
 Complete equipment for "Phone" and C.W. comprising :—
TRANSMITTER, with 1000 kc. Xtal, 5 valves, 1A5, 2/1299s, 2/1LD5s, etc.
RECEIVER, with 6 valves, 4/1LD5s, W1L6, 1A5, etc., etc.



LABORATORY RESISTOR ASSEMBLY R369.
 H.175, 330,000 ohm resistors, 5 watt to withstand 5,000 volts. 2in. dia. Can be mounted with ceramic ins., price 10/6, post paid.
VALVE RETAINING CLAMP.
 H.71, snap action, price 1/-, post paid.
STRIP RESISTORS, H.174.
 10 ohm 35 watts. 8in. long, ¾in. wide, with fixing flange. Price 1/-, post paid.

BENDIX MI-4A AMPLIFIER.
 Two valve, two stage audio amplifier with built-in 24 volt vibrapack, 12S17, 25L6, fully smoothed, complete with transformers, etc., in metal case 13 x 8½ x 3½ in.
CLYDESDALE'S PRICE ONLY 35/- each. POST PAID

Units of the SCR-522 (TR5043) for experiments on 3 meters T.V. and Radio Telephone wavebands.
BC-624-A Receiver Unit Chassis.
 Frequency 100-156mc/s with 11 valves, complete chassis (less Xtals) with I.F.T.s Relay, etc. Power requirements (external) H.T. 300v. D.C., 75 m/a. L.T. 24v. D.C. 3A. Dimensions : 15½ x 7½ x 6 in.
 Circuit supplied.
PLUS, Free Gift BC-625-A Transmitter Unit Chassis, partly stripped, but containing many useful parts. R.F. section in good order, no valves, modulation trans. or Xtal switch. Dimensions as receiver.
CLYDESDALE'S PRICE ONLY 37/6 CARRIAGE PAID
 Circuits for Ex-Services Equipment available, full list on application.

CO-AXIAL CABLE, ANY LENGTH SUPPLIED.
 12 mm. 52 ohms solid core at 6d. per yard. Minimum 20 yards, 10/-, post paid.
 12 mm. 80 ohms Airspaced core at 9d. per yard. minimum 20 yards 15/-, post paid.
 12 mm. 90 ohms Airspaced core at 7d. per yard. Minimum 20 yards 11/8, post paid.
 10 mm. 110 ohms Airspaced core at 7d. per yard. Minimum 20 yards 11/8, post paid.

H.V. INSULATED VALVE TOP CONNECTOR.
 E.156 moulded in red bakelite with side entry for 4 mm. cable, to suit standard valve top 9 mm.
CLYDESDALE'S PRICE ONLY 9d. each. POST PAID

SUPPLY UNIT RECTIFIER FOR CANADIAN ARMY No. 43 TRANSMITTER.
 This unit is a complete power unit for use with 110v. A.C. 50 cycle input. The outputs are various.
 Components include : Transformers H.T. 2100-0-2100, tapped 500-0-500. L.T. 2.5 C.T. twice for 866s 450-0-450, 12v. C.T. volts, 6.3v. C.T. volts, 6.3 volts, 5 volts, Thermal starter 6.3 volts. Chokes 2/15H. 375 m/a. 120 ohm 15H 450 m/a. 66 ohm 20H 162 m/a. 160 ohm 2/15H 110 m/a, 260 ohm H.V. Condensers. Valves : 4/866A/866, 5Z3, LV Starter, VR150/30, 6SJ7, 2/6A3. Regulator circuit. Dimensions : 2ft 6in. x 1ft. 6in. x 1ft. with shock absorbing feed. Weight 420 lb. In metal case, finished in drab olive crackle, with O.P. and L.P. sockets, switches.

CLYDESDALE'S PRICE ONLY £16 each CARRIAGE PAID

In Maker's Original Packing.
R.F. UNIT TYPE 24.
 For 30-20 mc/s, 10-15 metres.
 Switched tuning 5 pre-tuned spot freq. 3/VR65 (SP61) output approx. 7-8 mc/s in metal case 9½ x 7½ x 4½ in.
CLYDESDALE'S PRICE ONLY 19/6 each. POST PAID
 Used, good condition at 12/6, post paid.

NOW READY.
 New Illustrated List No. 6 (152 pages), send 6d. to cover distribution cost. Please print name and address.

MAINS TRANSFORMERS.
 E.542, ideal for R1355 receiver.
 Pri., 0-250v. Tapped 200, 220, 240v.
 Sec., 350-0-350 volts, 100 m/a.
 Capable of delivering up to 150 m/a. with slight temperature rise.
 6.3v. 6A. 5v. 2.5A.
 Size : 4½ x 4½ x 4 in. Weight 12 lb.
CLYDESDALE'S PRICE ONLY 30/- CARRIAGE PAID

EHT TRANSFORMER, E.531.
 Ideal for VCR-97.
 Pri., 0-250v. Tapped 200, 220, 240v.
 Sec., 2,000 volts, 5 m/a.
 4v. 1.1 amps.
 2-0-2v. 1 amp.
 Upright mtg. Dimensions : 3½ x 3½ x 3 in.
CLYDESDALE'S PRICE ONLY 29/6 POST PAID

Brand New. E.536 MODULATION TRANSFORMER.
 Thermador potted type (U.S.A. made) with ceramic stand of terminals. Pri., 6,700 ohms C.T. Sec., 4,500, 5,000 and 5,500 ohms max. op. 470 freq.—10db. 400-4,000 c/s. Test 5,000v. suits TZ40, T35, 813, etc. Size : 7 x 6½ x 5½ in. Weight 22 lb.
CLYDESDALE'S PRICE ONLY 42/6 each CARRIAGE PAID

R.C.A. DRIVER TRANSFORMER (110K/117) XT. 3202.
 E.562 C.T. Primary : Inductance 3.4 henries. 2 Secondaries : Inductance 14 henries each. Ratio : whole pri. to one sec. 1 : 2 approx. Dimensions : Ht. 4½ x 3½ x 3½ in. Weight 6½ lb. 4-hole fixing.
CLYDESDALE'S PRICE ONLY 15/- each. POST PAID

Brand New. HIGH VOLTAGE ROTARY TRANSFORMER (by Hoover).
 Type HT32. Input 11.5 volts D.C. Output 490 volts, 65 m/a.
 Dimensions : 5½ in. long x 3in. dia. cylindrical.
CLYDESDALE'S PRICE ONLY 25/- each. POST PAID

STILL AVAILABLE.
 RI481 V.H.F. Receiver Unit at..... 99 6
 A.C. Power Unit type 3 at..... 79 6
 Or both above items at..... £8 8 0
 Master Oscillator type MI-19467-A at..... 79 6
 Crystal Multiplier type MI-19468 at..... 39 6
 R-28/ARC-5 100-150 m/c. Receiver Unit at..... 37 6
 BC-733-D Receiver Unit at..... 30 0
 Bridge Megger 100 megs. at 1,000v. at..... £35 0 0
 Vee Megger 20 megs. at 250v. at £5 19 6
 Battery Unit 247 at..... 59 6
 Power Amplifier A.1368 at..... 11 6
 SCR-720 Blower, with shunt motor at..... 17 6
 Reflector Aerial (MX-137A) at..... 5 6
 As previously advertised, price includes carriage.

MOVING-COIL MIC/HEADPHONE ASSEMBLY



Comprising moving coil microphone (Hand No. 7) with pair of M.C. Headphones and 3ft. lead with rubber 5 point socket. Imp. approx. 60 ohms per insent.
CLYDESDALE'S PRICE ONLY 12/6 POST PAID

Order direct from :—
CLYDESDALE SUPPLY 2 BRIDGE STREET GLASGOW - C.5
 Phone: South 2708/9. Visit our Branches in Scotland, England and Northern Ireland.

Announcing the £15 T/V for the Midlands

Constructors in the Midland TV Area will be pleased to learn that the Data for our Mk. II Televisor for operation on the Sutton Coldfield Frequencies is now available. All constructors of this Televisor who have not yet received the information should write in quoting date of purchase and invoice number, when the full details will be supplied gratis.

This Televisor, many hundreds of which are in service, is designed round two Radar Units which cost only £6 the pair. One unit is an Indicator containing a VCR97 C.R. Tube, and the majority of the valves and components, and the other unit is a ready made Vision Receiver which only requires modification for the TV Frequencies. Use of this latter item, which was made regardless of cost to a planned layout, eliminates many of the headaches experienced by those who have attempted the construction of a Vision Receiver from scratch. The Constructional Data is most detailed, with photographs, parts lists, circuit diagrams, etc., and costs only 7/6, or is supplied gratis with the two Radar Units. Alternatively, it may be purchased, and the cost will be credited against the subsequent purchase of the Radar Units within 14 days. A fully detailed price list shows that the total cost is £15/4/9. Please note that orders for the Radar Units should include an additional 12/6 carriage costs, plus 10/- deposit on packing case.

For Constructors embarking on other circuits we can supply a wide range of component parts, many of which are listed below:—

RECEIVERS R1355. As specified for "Inexpensive Television." Complete with all valves, and a copy of the booklet (which can be supplied for 1/9). ONLY 45/- (carriage, etc., 7/6).

RF UNITS TYPE 25 specified for London Area Station, 17/6 (postage 1/6), OR R1355 RECEIVER AND RF UNIT 25, 62/6 (carriage 7/6).

RF UNITS TYPE 26, specified for the Birmingham Station are now all sold, but we can supply the RF Unit 27 with full details of modification to cover the TV Frequencies, simply by retrimming. ONLY 35/- (postage 1/6), OR R1355 RECEIVER AND RF UNIT 27 FOR 75/- (car. 7/6).

INDICATOR UNITS TYPE 6. The indicator unit specified for "Inexpensive Television," this being complete with the VCR97 Tube and valves. BRAND NEW IN MAKERS CRATES. ONLY 90/- (carriage 7/6).

TRANSFORMERS for above TV have been specially made as follows: Time Bases and Vision Transformer, 350.0-350v. 160 m/a, 5v. 3a., 6.3v. 6a., 6.3v. 3., ONLY 36/- Sound Receiver Transformer, 250.0-250v. 100m/a, 5v. 3a., 6.3v. 6a., ONLY 27/6. EHT Transformer for VCR97 Tube, 2.0-2v. 1.1a., 2.0-2v. 2a., EHT at 5m/a.

MAGNIFYING LENS for 6in. C.R. Tube. Brings up the picture size to approximately that given by a 9in. tube. ONLY 25/- (postage 1/6).

SMOOTHING CHOKES. 10H. 80 m/a., 8/6, 3H. 200 m/a., 6/- (postage on each 9d.).

EHT CONDENSERS. 2,500v. .1 mfd oil filled tubulars, 2/6 (post 3d.), 3,000v. .1 mfd block paper size 3½ x 2½ x 3¾in (inc. terminals), 4/6 (post 9d.).

CO-AXIAL CABLE, 75-80 ohms, 1/3 per yard.

PYE CO-AXIAL plug and socket, 1/- pair or 6d. each.

SPEAKERS. 10in. Truvox PM less transformer, 17/6 (postage, etc., 2/6).

CONDENSERS. 2 pf to .1 mfd, mica, silver mica, or paper 6d. each.

RESISTORS. ¼w. 4d., ½w. 5d., 1w. 6d., 2w. 9d.

CWO please. Add postage where not stated on orders under £2.

U.E.I. CORP., The Radio Corner
138 GRAY'S INN ROAD, LONDON, W.C.1

(Phone: TERminus 7937)

Open until 1 p.m. Saturdays, we are 2 minutes from High Holborn and 5 minutes from King's Cross.

TELEVISION WITHOUT TEARS

OUR Kit of Parts (down to the last nut and bolt) is proving doubly popular because (a) the price of £16 19s. 6d. is amazingly low, and (b) the explicit nature of our instructions and easy to follow point-to-point wiring diagrams ensures success for all. Its most convincing feature, however, is that the conversion of ex-government equipment is NOT involved.

The Televisor is built from standard radio components and assembled on two chassis, one for the Vision Receiver, Sound Receiver and Time Base, the other for the Power Supplies. It operates on A.C. Mains 200-250 volts.

If price is the cardinal consideration we can supply the Complete Kit for only £15. The valves and C.R.T. are slightly used but guaranteed perfect in this case. The carriage charge on either Kit is 10s.

Price of the comprehensive point-to-point wiring diagrams and 17 pages of data is 5s. post free. May we urge you to send for these initially. If a Kit is subsequently purchased the 5s. will, of course, be credited. PLEASE SPECIFY LONDON OR SUTTON COLDFIELD WHEN ORDERING THIS DATA.

NOTE THESE ★ FEATURES

- ★ NO knowledge of television technique essential.
- ★ ALL parts complete, brand new, and of the finest quality.
- ★ ALL parts may be purchased separately.
- ★ ROCK-STEADY picture assured because six EF50 valves are used in the Time Base and Synch. Separator.
- ★ UNIQUE "After-Sales" Service. Testing and alignment of receivers after completion of assembly undertaken for a nominal sum. WE GUARANTEE RESULTS.

Our Televisor is equal to many commercial models. Why not come along and see a demonstration during viewing hours?

AN UNIQUE OFFER

AMERICAN TRANSCEIVERS TYPE 48, frequency coverage 6-9 Mcs. We proudly offer the complete station which is all brand new and packed in 6 cartons, comprising the following items: 1 Transmitter/Receiver type 48 ("walkie-talkie") complete in case and complete with 10 valves and one 1 megacycle crystal; 2 satchels 1 ground aerial, spare valve case complete with 10 spare valves, 1 key assembly, 1 hand microphone, 2 headsets, 1 hand generator, together with mounting tripod, 2 battery boxes and all necessary interconnecting cables, and a comprehensive Instruction Manual. Only £13 19s. 6d. carriage paid, while they last.

Indicating Unit Type 230. This unit works from A.C. Mains 110 or 230 v. 50 cycles. Contains a mains transformer giving 350.0-350 80 m/a, two 6.3 windings, one 5 v. 2 amp. and the following valves: 1 5Z4, 1 Y63, 1 EA50, 4 EF50. Housed in metal case and in good condition. Made by G.E.C. Only 39s. 6d., plus 3s. 6d. carriage and packing.

Receiver Unit 25/73. Good news. Another large purchase enables us to offer these exceptionally popular units at 22s. 6d. post free. Valve line-up: 2 EF39, 1 EK32, 1 EBC33 and 2 EF36; and one pair of 460 Kcs IF Transformers, resistors, condensers, etc. Easily and rapidly converted to an ordinary superhet receiver. Circuits and conversion data supplied. Order early.

Indicator Unit, Type 182A. Includes VCR517 tube and 8 valves as follows: 3 EF50, 1 5U4, 4 SP61; and 2 pot./meters, numerous condensers and resistors. Dimensions of case 18 x 8 x 7in. ONLY 45s., plus 7s. 6d. carriage and packing. The C.R. Tube stringently tested prior to despatch and the whole unit is in excellent condition. **Receiver R1155A.** BRAND NEW, UNUSED and IN TRANSIT CASES. First come first served! The R1155A is justifiably the most renowned and popular of communication receivers. Our price of £11 19s. 6d. carriage paid to your door brings this superlative receiver to you at a modest price. We repeat: absolutely brand new and in magnificent condition.

Receiver, Type 21. The receiver section of the Wireless Set 21. Operates as a superhet from 4.2-7.5 Mcs. and as a double superhet from 18-31 Mcs. Complete with nine 2 v. valves. Designed for 6 v. L.T. input but can be modified for 2 v. L.T. in a matter of minutes! Crash limiter and B.F.O. incorporated. Circuit diagram provided. ONLY 35s., post free.

Mullard Resistance Capacity Bridge. BRAND NEW. Measures 10 pf to 10 mfd, and 0.1 ohms to 10 megohms. A.C. mains operation. ONLY £8 19s. 6d. carriage paid. Our stock is now limited.

DURING FEBRUARY WE ARE DISPOSING OF MANY USEFUL ARTICLES OF WHICH WE HAVE TOO FEW TO ADVERTISE. THESE ARE BEING SOLD AT "GIVE-AWAY" PRICES. MAKE A POINT OF CALLING AND SECURING YOUR BARGAIN.

Best Buy at Britain's



CHARLES BRITAIN (Radio) Ltd.

11, UPPER SAINT MARTIN'S LANE,
LONDON, W.C.2 TEM 0545

3 minutes from Leicester Square Station (up Cranbourne Street)

Shop Hours: 9-6 p.m. (9-1 p.m. Thursday).

Open all day Saturday

M.O.S. STILL THE LEADERS!

COSSOR BANDSPREAD SHORT WAVE 5 VALVE SUPERHET RECEIVERS

An 'export only' model released to the home market in limited quantities.


These superb receivers incorporate the most up-to-date and successful Band Spread Tuning system for Short Waves. Each of the five short-wave bands is furnished with a tuning scale several inches long and instead of being crowded on a small section, the individual stations are spread apart so that many can be separately calibrated by name and thus readily identified. The consequent much greater ease in tuning lends an entirely new programme value to short-wave stations. Another notable feature is the Spin-flywheel tuning by which the dial pointer is traversed with smooth rapidity. The extremely attractive cabinets are polished walnut and sycamore, a large fabric-covered speaker panel balancing the clear-view illuminated dial. Size of cabinet 17½ x 11 x 9 in.

WAVEBANDS COVERED

Medium: 1550 to 526 Kc/s (193 to 570 metres).
Medium-short: 7.54 to 2.42 Mc/s (41 to 124 metres).

BAND-SPREAD TUNING

31 metre band (9.90 to 9.40 Mc/s).
25 metre band (12.18 to 11.60 Mc/s).
19 metre band (15.72 to 14.93 Mc/s).
16 metre band (18.35 to 17.38 Mc/s).
13 metre band (22.30 to 21.10 Mc/s).

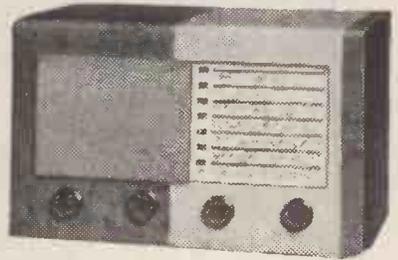

MODEL 472.UX FOR D.C.-A.C. MAINS

6½ in. P.M. Speaker, 5 Cossor Valves, Delayed A.V.C., Four-position Tone Control. For use on D.C. or A.C. Mains 100-120 and 190-250 volts (adjustable). A.C. 40-100 cycles. Approx. consumption 50 watts. 3 watts undistorted output.

FULL MAKERS SERVICE GUARANTEE!! (Tax REDUCED TO £17. 17. 0. paid).

OR £3 12s. od. CASH with 12 monthly payments of 26s. 3d. (carriage and packing 10s.).

AGAIN!
Brand new R1155A Receivers in transit cases
£11. 19. 6.
(Carr. & Pkg., 10/-)

£10,000 WAS SPENT to give YOU PERFECT SOLDERING!



For a limited period we are offering the already famous **BURGOYNE INSTANT HEAT SOLDERING GUN** (advertised and sold by the makers at 79/6) FOR **52/6 ONLY**

We are setting a standard for value which you will find hard to beat. This offer has been possible only by an ACCIDENT—a blocked export shipment that missed the last boat to South Africa!

SAVE TIME ON SOLDERING!

Just press the button, count seven, and solder and the bit will remain at soldering heat until you release the pressure, when it cools off instantly.

No waiting to warm up or cool down—no element to burn out—no mica to crack or splinter—no risk of shock.

Few tools possess so many advantages as the "Seven-Second" Solder Gun; and certainly no engineer can consider himself up to date without one. For A.C. mains, 200-250v.

THE SPEDA UNIVERSAL PUNCH

Designed and produced to fill a long felt want for a multiple cutting tool for light alloys. PRICE, 26/- POST FREE. Delivery from stock.

2 VOLT VIBRATOR PACKS: ONLY 35/-

We can now supply the famous U.S.A. made 2 volt Vibrator Power Supply as used on the Canadian Type 58 Walkie-Talkie. BRAND NEW and complete with Vibrator. Add carr. and pkg. 2/6.

Specification:—2v. input, 90v. or 180v. 35 m/a, 1.5 v. L.T. outputs.

Size 8 x 3½ x 4 in. Charging circuit for Accumulators supplied. Also available complete with two 2v. Accumulators in case for 50/-. Carr. and pkg. 5/-.

COMPARE OUR PRICES!


MARCONI SHORT WAVE RECEIVERS

A brand new full size 5 valve superhet made for the export market (110v. A.C.). The Receiver is housed in a handsome light walnut cabinet with built-in speaker. Frequency coverage 13-46, 46-150, 190-560 metres. The Receiver is fully tropicalised and most of them are in wooden transit cases.

Full maker's service guarantee. An unrepeatable offer for only **£15** including tax. (Carr. and pkg. 10/-.)

We give away with each of these fine Receivers an Auto Transformer to convert the mains voltage input for use on all A.C. mains (voltages 110-250). **ONLY A LIMITED QUANTITY AVAILABLE.**

IMPEDANCE MATCHING UNITS

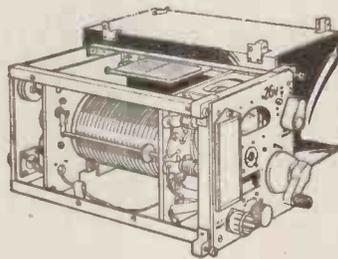


Provide correct impedance matching for your Receiver or Transmitter for any length of aerial. This BRAND NEW tuning unit will give you greatly increased signal strength over a frequency coverage of 2.4 to 13 m/cs. The unit is a compact assembly comprising rotating coil assembly with pulley arrangement to operate the revolution counter. An 0-3 ammeter is mounted on the front panel together with the tuning handle for the coil. This handle may be locked in any desired position. Size of the unit 5 x 5 x 9 in. Each one fitted in original wooden transit case. PRICE **13/11** (Post and packing 1/1).

M.O.S. NEWSLETTER

A lively journal packed with good ideas circuits, etc., and news of the best in "surplus." Send 1/- for specimen copy or 5/- for a year's subscription.

D.C. 'STEP-UP' GENERATOR

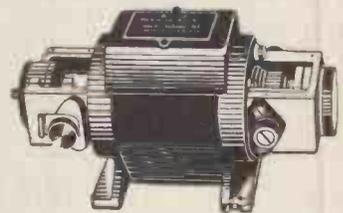

A universal Purpose Motor Generator fully guaranteed, brand new and in original maker's cartons.

This unit can be driven from D.C. voltages from 2v. to 14v. and will give varying outputs according to the input voltage. For example: At 6v. D.C. input an output of about 230v. 30 m/a will be obtained.

At 4v. D.C. input, 180v. 25 m/a will be obtained.
At 12 v. D.C. input, 480v. 40 m/a will be obtained.

The motor will also provide sufficient power for use as a grinder, polisher, etc., as a spindle protrudes in. from the casting of sufficient length for mounting these. Approximate R.P.M. at 12v. D.C. input, is 2,000 (varying according to the applied voltage.)

The cost of manufacturing these useful equipments was approximately £8 to £9. **OUR PRICE 8/11** (Post and pkg. 1/1). **REMEMBER EACH ONE CARRIES FULL GUARANTEE.**

M.O.S. RADIO ALARM KIT

A simple radio time switch in kit form which can be made in a few hours by anyone possessing the normal household tools.

Awaken to the strains of early morning music. Full wiring diagram and instructions included. **the KIT. 12/6**

"SNIP" COMPONENT OFFER
½ Meg. Volume Controls with Double Pole Switch Spindle in. **3 for 12/6**
Small overall diameter 1 ½ in.

Terms: Cash with order

MAIL ORDER SUPPLY CO., THE RADIO CENTRE, 33 Tottenham Court Rd., W.1 (Museum 6667-8-9)

NEW

SERIES 800 ELLIPTICAL

(Type 874)

CAN 4=8? Of course it can't. And a 4" speaker can no more equal the performance of an 8" than a quart can come out of a pint pot.

BUT that is no reason why a 4" speaker cannot be a really good 4" speaker. Precision in machining, exactness of assembly and, of course, CO-AXIAL ALIGNMENT of all component parts is just as important as in any other of our speakers.

We are really pleased with our 4" x 7" Elliptical.

Dimensions and Data
 Horizontal 7.1" (18 cm.)
 Vertical 4.1" (10.3 cm.)
 Axial 2.4" (6 cm.)
 Flux Density 8,000 or 9,000 Gauss

REPRODUCERS AND AMPLIFIERS LIMITED
 ENGLAND
 WOLVERHAMPTON
 Telephone: "Audio, Wolverhampton."
 Telegrams: "Wolverhampton 22241"



"You're CERTAIN to get it at ARTHURS!"

★ **VALVES**: We have probably the largest stock of valves in the country. Send your enquiries. We will reply by return.

AVO METERS IN STOCK

Avo Model 7	£19 10 0
Avo Model 7, high resistance	£19 10 0
Avo Model 40	£17 10 0
Valve Tester	£16 10 0
Test bridge	£11 0 0
Avo Minor, AC/DC model	£8 10 0
Electronic Test Meter	£35 0 0
Signal Generator	£25 0 0
Valve characteristic meter	£40 0 0

DENCO COILS & COMPONENTS in stock

TAYLORS METERS. List on request.

DECCA PICK-UPS	£6 14 6
DECCA HEAD for Garrard	£4 11 0
Adaptor	3 8
COSSOR DOUBLE BEAM OSCILLOSCOPE	£85 10 0

LONDON'S OLDEST LEADING RADIO DEALERS

ALL KITS FOR VIEWMASTER TELEVISION IN STOCK

LATEST VALVE MANUALS

Mazda - 7/- ea.
 Brimar - 2/6 ea.
 Brimar - eletube & Radio - 4/-
 Post 4d. each extra

Arthur's

EST. 1919
 PROPS: ARTHUR GRAY, LTD. Terms C.O.D. or cash with order

Our Only Address: Gray House, 150/152 Charing Cross Rd. London, W.C.2
 TEMple Bar 5833/4 and 4755
ELECTRICAL, TELEVISION & RADIO ENGINEERS.

Economical in Time and Money!



YOURS FOR ONLY 6/11
 MONTHLY
 £1 DEPOSIT SECURES
 10 monthly payments of 6/11

Get instant soldering heat. Invaluable for radio servicemen, engineers and home mechanics. Simply plug in, press the button, and in seven seconds the iron's hot! Absolutely safe, the bit cools instantly when released and lies clear of bench when not in use. Complete with two spare bits and four yards of flex. Suitable for A.C. 200-250V, or 100-130V State model required. Limited stock. No interest charge. Send your deposit to-day for this ultra-rapid electric soldering gun. Leaflet on request.
 Cash Price £3 19s. 6d. complete

BURGOYNE
SECOND Instant Heat SOLDERING GUN

SEND YOUR DEPOSIT Today TO -

Trade Terms upon Request.
The RING LAMP CO.

81 City Road, London, E.C.1
 Telephone CLerkenwell 7103

CONSISTENTLY *Accurate*

PULLIN A.C. DYNAMOMETER MULTI RANGE TEST SET TYPE P.D.440 with the well known Pullin iron-free dynamometer movement combines the functions of a Precision Indicating Ammeter, Voltmeter and Wattmeter. Covers an extremely wide range to fine limits of accuracy :-

5 Voltage—Ranges from 25 to 500 Volts A.C. or D.C. Accuracy plus or minus 0.5%.

6 Ampere—Ranges from 0.5 to 25 (A.C. only). Accuracy plus or minus 0.5%.

30 Watt—Ranges from 12.5 to 12,500 (A.C. only). Accuracy plus or minus 1%.

Entirely self-contained in polished hardwood case with carrying handle and removable lid, as shown.

Weight 17 lbs. Size 10½ in. x 13½ in. x 7¼ in.



Get full details without delay from:

MEASURING INSTRUMENTS (PULLIN) LTD.

Electrin Works, Winchester St., Acton, London, W.3.

Telegrams: MIPULLCO EALUX LONDON.

Tel.: AGO 4651/3 & 4955.

SPECIAL ALUMINIUM

TUBING FOR AERIALS

BUY FROM THE MAN WITH EXPERIENCE—
THE TUBE MANUFACTURER



SUPPLY FULL

TECHNICAL DATA

WITH THEIR SPECIAL
ALUMINIUM TUBING FOR
AERIALS (NO EXTRA COST)

SIZE OF DIPOLE AND REFLECTOR	SIZE OF CROSSARM	MOMENT OF INERTIA I ins. ⁴	SECTION MODULUS Z ins. ³	STRESS (σ) IN 7 M.P.H. WIND	STRESS (σ) IN 40 M.P.H. WIND	REFLECTION OF DIPOLE IN 40 M.P.H. WIND

TO
TELEVISION
AERIAL
MANUFACTURERS

Southern Forge LTD

IN ASSOCIATION WITH
ASSOCIATED
ALMIS LIMITED
1941-1942 (INCORPORATED)
FARNHAM ROYAL-BUCKS

MEADFIELD ROAD · LANGLEY · BUCKS · Tel: LANGLEY 301

D. COHEN

Radio and Television Components

CONSTRUCTOR'S PARCEL comprising miniature chassis, size 8½in. x 3½in. x 1½in., miniature twin gang .00037, pair of miniature Wearite IFs Type M400B, 4 B7G valve holders, frame aerial and medium wave osc. coil. £1/9/6. Post and packing 1/6.

CONSTRUCTOR'S PARCEL comprising chassis 10½in. x 5½in. x 2in., with speaker and V.H. cut-outs, Rola 5in. P.M. with trans. twin gang with trimmers, pair of T.R.F. coils, 4 valve holders, 17/6, plus 1/6 Post and Packing.

P.M. SPEAKERS. All by leading manufacturers. Less transformer. 6in. 8/9, 8in. 11/9, 10in. 14/6, 12in. 29/6. With transformer 5,000 ohm impedance. 5in. 11/-, 6in. 11/-, 8in. 14/-, 12in. 31/9. All plus 1/- P. & P.

ELECTROLYTIC CONDENSERS. All by good manufacturers. 2 mfd. 350 9d., 16 x 24 mfd. 350 2/11, 16 x 16 mfd. 450 3/6, 8 x 8 mfd. 450 3/6, 8 x 16 mfd. 450 3/6, 8 mfd. 450 1/11, 12 x 12 mfd. 450 2/9, 32 x 32 mfd. 450 5/6, 24 x 24 mfd. 200 work 1/3, 500 mfd. 6 v. 1/3, 250 mfd. 12 v. 1/3, 50 mfd. 50 v. 1/9, 50 mfd. 12 v. 1/-, 25 mfd. 25 v. 1/-.

VOLUME CONTROLS, with switch, long spindle, ½ meg. 3/10 1 meg. 3/6, .35 meg. 2/9, 25 k. 3/-, 50 k. 3/-.

VOLUME CONTROLS, less switch, long spindle, 1 meg. miniature 1/6, 5 k. 1/9, 50 k. 1/6, 20 ohm wire wound miniature 2/6.

METAL RECTIFIER. 250 v. 125 mA., 4/3. Post 6d.

METAL RECTIFIER. 250 v. 60 mA., 2/6. Post 6d.

METAL RECTIFIER. 24 v. 4 amp., 18/6. Post 1/-.

MAINS DROPPER. .2 amp. 1,000 ohms, tapped 900. 1/9. Post 3d.

MAINS DROPPER. .2 amp. 717 ohms, tapped 100. 1/6. Post 3d.

UNIVERSAL REPLACEMENT MAINS TRANSFORMER. Input 200/250 v. Sec. 280/0/280 v., 60 mA., 6 v. tapped 4 v. 3 amp. 5 v. tapped 4 v. 2 amp. 6 v. 0.3 amp., 10/6. Post 1/-.

MAINS TRANSFORMER. Input 200/250. Sec. 350/0/350 v. 130 mA. 6 v. 5 amp. 5 v. 3 amp., 19/6. Post and Packing 1/-.

STANDARD OUTPUT TRANSFORMER. 5,000 ohm impedance, 3/3. Post 6d.

MIDGET OUTPUT TRANSFORMER. 5,000 ohm impedance, 2/9. Post 6d.

SMOOTHING CHOKE. 10 hy. 80 mA., 3/9. Post 6d.

SMOOTHING CHOKE. Midget 40 mA., 1/11. Post 3d.

WAVE CHANGE SWITCHES. 6 pole 3 way 1/2, 6 pole 2 way 1/2, 5 pole 3 way 1/2, 3 pole 2 way 1/2. Miniature 2 pole 2 way 1/6.

.0005 TWIN GANG, 3/6. Post 6d.

.0005 TWIN GANG, with feet, 4/-, Post 6d.

0005 TWIN GANG, fitted feet, trimmers and drum, 4/6. Post 6d.

MINIATURE TWO GANG, .00037, 6/-.

MINIATURE TWO GANG, fitted trimmers and Perspex dust cover, 6/6.

TWIN TRACKERS. 100 and 500 pf. 9d., 100 and 200 pf. 9d., 300 and 300 9d.

WHITE OR BLACK PLASTIC LOUVRE. Size 6½in. x 12½in., 4/6. Post 6d.

TRIPLEX TELEVISION GLASS, for 9in. or 12in. tube, 4/6. Post 6d.

COMPLETE A/C MAINS. 200/250 v. 5-VALVE CHASSIS. 8in. energised speaker. L.M.S. and gram. on press buttons. Made by a good manufacturer. Tax paid. £8/18/6.

SUPERHET COIL KIT, comprising long, medium and short wave coils, twin gang, pair of 465 IFs, 4 pole 4 way switch, 6 trimmers, 2 trackers, 5-valve superhet chassis, IF and speaker cut-out and circuit, 14/6, plus 1/- P. & P.

Send stamp for current list.

POST ORDERS ONLY

67, RALEIGH AVENUE,
HAYES, MIDDX.

HIGH FIDELITY PLUS

We are now demonstrating the latest BARKER loud-speaker, the MODEL 150, mounted in an improved version of the "RD Corner Cabinet."

The performance of this combination is extremely satisfying, the reproduction of solo instruments, speech, and orchestral music is uncannily natural. In particular the reproduction of massed strings is smooth and realistic, with no loss of detail.

Two amplifiers are being used for demonstration, the "Williamson," and the "RD Junior."

The latter is proving increasingly popular with enthusiasts who appreciate high performance at a reasonable price.

For record reproduction the DECCA Model "C" Pick-up with 12in. arm is used.

Barker Model 150 Loudspeaker	£18 18 0
Barker Model 148A	£15 15 0
RD De Luxe Corner Cabinet	£32 10 0
Williamson Amplifier, Model "A"	£27 10 0
Williamson Amplifier, Model "B"	£29 10 0
Pre-amplifier, Model RD3	£10 10 0
Pre-amplifier, Model RD4	£6 10 0
RD Junior Amplifier	£19 10 0
Decca, Model "C" Pick-up with 12in. arm	£3 0 0
Purchase Tax	£1 6 1

Demonstration Times: 10.30 a.m.-12.30 p.m. 1.30 p.m.-5.30 p.m. DAILY. Thursdays: 10.30 a.m.-12.30 p.m. Nearest Underground Station—Hampstead—Northern Line.

ROGERS DEVELOPMENTS Co.,
106, Heath Street, HAMPSTEAD, London, N.W.3.
HAMPstead 6901



THREE PICKUPS ARE NOW BEING PRODUCED

RIBBON MOVING COIL
AND MICROARMATURE

ALL HAVE THEIR SPECIAL APPLICATION AND FULL DETAILS WILL BE SENT ON REQUEST.


Anyone who has applied for information during the last 12 months will automatically receive a copy and is requested not to make another application immediately.

J. H. BRIERLEY (GRAMOPHONES & RECORDINGS) LTD.
46, TITHEBARN STREET, LIVERPOOL, 2.

AERIALITE

**makers of the world's best
AERIALS & EQUIPMENT**

Introduce their **NEW**

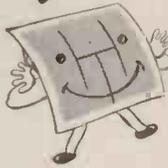

**AERIALITE ...
the most advertised
aerials made!**

According to statistics supplied by "The Statistical Review," Aerialite Aerials are easily the most extensively advertised aerials made. Our present campaign includes advertising in the "Radio Times," "Daily Express," "Daily Mail," "News Chronicle," "News of the World," "The People," "Sunday Express," "London Evening News," "The Star," "London Evening Standard," and the leading Midlands papers. The public are asking for "AERIALITE," —The Best!

AERIAL Fitting SERVICE

- Are you missing sales through the inability to fit an aerial? If so, cash in now on the AERIALITE AERIAL FITTING SERVICE. This new service by the World's Largest Makers of Aerials applies to the wide range of AERIALITE TELEVISION and MASTATIC AERIALS.
- We shall also be pleased to receive applications to join our organisation from dealers who have experience in aerial fitting.
- EXAMPLE: Fitting of our new Popular D.P.O. MODEL 52. You can supply this low-priced Television Aerial complete and erected for £8.0.0 only. D.P.O. MODEL 52. Complete with 10ft. steel mast and Chimney Lashing Brackets, etc., £4.10.0. Complete Erection Costs, £3.10.0—Total Cost £8.0.0. Write today for full details.

**AERIALITE Ltd.
STALYBRIDGE, CHESHIRE**

Make sure you can meet the demand!



**A RADIO-TELEPHONE
you can
TUCK-UNDER
THE DASH**

**NOTE THESE
FEATURES**

Size T/R. 11½ in. x 8 in. x 4 in. (30 cm. x 21 cm. x 10 cm.)
Power Pack 8 in. x 5½ in. x 3½ in. (21 cm. x 14 cm. x 8 cm.)
Weight T/R. 15½ lbs. (7 kg.), Power Pack 9½ lbs. (4.2 kg.)

The Transceiver is easily installed below the instrument panel with the small power pack in any convenient place. The remarkably low battery drain permits connection of the set to the car batteries, obviating the cost and weight of auxiliary accumulators or larger dynamo.

B.C.C. v.h.f.

Radio Telephone Equipment

The B.C.C. Mobile Radio-Telephone illustrated here will give two-way communication with the Fixed Station up to a distance of 25 miles or with the portable Pack-set up to 5 miles.

This B.C.C. equipment sets a new standard in V.H.F. Communications Technique and has been approved by the G.P.O. and Home Office. The complete range consists of:

- FIXED STATION Model L111
- MOBILES Models L67 & H67
- PACK SET Model L 45V
- HAND PORTABLE ... Model L 45AV

This equipment can be supplied to cover any spot frequency in the 75-100 Mc/s or 156-185 Mc/s bands.

Write now for full details and outstanding features of this remarkable equipment.



BC.306

Antenna Units. Size 16in. x 8in. x 8in. Black Crackle Cabinet. Aerial Loading Variometer 3 pole 5 way Ceramic Switch. 4 porcelain lead-through insulators. Precision slow motion dial. 3 6000 v. 80 mmf. block condensers. Brand New. 10/- each. Carr. 2/6.



Receiver Type 26/ARCS. 3.6 mc/s. 6 valves. 28 v. dynamotor fitted. Brand New in Original Sealed Cartons. Price 59/6 each. Carr. 1/4.



Antenna Reels. Type R1142A. Motorised 1/13 h.p. Motor. 28 v. 5 amps. 6in. Detachable Pulley. Elaborate Reduction Gearing. Instantaneous positive stop. Brand New in Sealed Cartons, each 30/-, Carr. 1/4.

MICROPHONES. Hand pattern. Moving Coil. With screened connecting lead. 12/6 each, post paid.

MORSE KEYS. All brass. Ex-Govt. Brand new. Lovely job. With connecting lead and jack plug, 12/6, post paid.

MAINS FILTER UNITS. Ex-Govt. Brand new, size 4 1/2 in. x 4 in. x 2 in. Contain elaborate smoothing for noisy mains. 10/- each, postage 1/-.

CONDENSERS. Large purchases enable us to offer at unequalled prices. .1 1,000 v. wkg. .25 500 v. wkg. .02 750 v. wkg. In minimum lots of one dozen which may be assorted. 6/- dozen, post free. .01 5,000 v. Can type ex-Govt. In pairs mounted on insulated base. 2/6 per pair, post 9d. 2 mfd. 500 v. Mansbridge type ex-Govt.. 4/- doz., post paid. Three-gang tuning condensers for Receiver R1155, 7/6, post 9d. .0003 Brass vanes variable condensers. Wide spacing. Ideal for transmitters, 1/- each, post 6d.

VALVE HOLDERS for EF50. Brand new, 3/- doz., post 6d.
DUAL RANGE PLUG IN COIL UNITS, type C380. Aluminium casing coverage. 201-398 kcs. and 4150-7700 kcs. Brand new, 5/-, post 6d.

MEDIUM WAVE CONVERSION COILS for BC453/4/5B receivers, 10/-, post paid. State set number. Tuning spindle and knob, 2/6.

TERMINAL PANELS. Small. Suitable for A and E, LS, PU, etc., 6d. each.

TAG BOARDS to mount 12 small components, 1/-, post 6d.

SWITCH BOARDS. 17in. long, 10in. wide, 4in. deep. Has 12 on/off switches and outlets. Organise the switching in the shack with one of these fine ex-Govt. units. 10/- each, post 1/4.

JACK BOXES. BC365. Has 2-pole 5-way switch, rheostat, two jacks and very neat grey enamelled case 3 1/2 in. x 4 1/2 in. x 2 1/4 in. Brand new in sealed cartons, 3/6, post 6d.

BRAND NEW R1426 RECEIVERS for the Inexpensive Television Receiver (in original crates). 63/-, plus 5/- carriage.

TUNING UNITS. TUSB. Well known for its easy conversion to a stable VFO. Frequency range 1500-3000 kcs. Complete with outer case in new condition, 22/6, carr. paid.

TU6B 300-4500 kcs., in new condition, less outer case, 10/-, carr. 1/4.
TU8B 6200-7700 kcs., in new condition less outer case, 10/-, carr. 1/4.

PROMPT DELIVERY AND SATISFACTION GUARANTEED AS ALWAYS

2 1/2 d. stamped envelope must accompany all enquiries

LISTS AVAILABLE

H.P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House

Estd. 1935

55 COUNTY ROAD, WALTON, LIVERPOOL, 4

Tel.: Aintree 1445

Staff Call Signs, G3DGL, G3DLV

HIVAC
THE SCIENTIFIC

BRITISH VALVE MADE


Pioneers & Specialists in Small Valves

Messrs. Hivac Ltd
Greenhill Crescent,
Harros-on-the-Hill,
Middx.

*THE address for:—
Subminiatures - Midgets - Miniatures
and Cold Cathode Tubes*

Switch

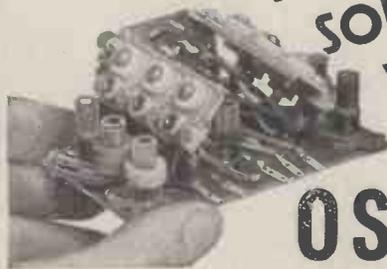**PROBLEMS TO
THE RIGHT
SOLUTION
WITH...**



**OSMOR
'Q' COILPACKS**

As specified for conversion of the Type 25 unit of the TR. 1196

A simple answer to all your coil and switching problems—is an Osmor 'Q' Midget Coilpack. With only 5 connections and 1-hole fixing, the job is done in double quick time, yet efficiently and cheaply. Full circuit diagrams and instructions are supplied with each prealigned coilpack.


A Portable Superhet Battery model is also available. Send stamp for FREE circuits and our new lists of coils, Coilpacks and matched radio components, also "Bargain Bulletin."

Trade and Export enquiries invited.

OSMOR RADIO PRODUCTS LTD. (Dept. W.3.)
BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON SURREY
Telephax: Croydon 1220.

CONTROL

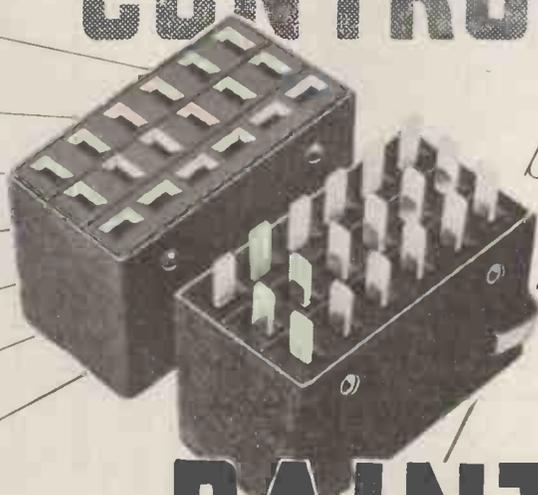- TYPE APPROVED COMPONENT.
- AVAILABLE IN TYPES FROM 2 TO 33 WAYS.
- CADMIUM PLATED BRACKETS AND CABLE CLAMPS.
- BERYLLIUM COPPER (SILVER PLATED) CONTACTS.
- PAPER LAMINATED RESIN BONDED INSULATORS.
- HIGH QUALITY DURABLE CRACKLE FINISH.
- SOLID DRAWN BRASS CASES.



PAINTON

PAINTON & CO LTD · KINGSTHORPE · NORTHAMPTON · PHONE 2820



Opus 923 for the Television Band

TF 923, the Marconi TELEVISION SWEEP GENERATOR is designed for the visual checking and alignment of television or f.m. receivers, aerials and feeders, and is used in conjunction with a suitable c.r.o. The main radio frequency carrier output embraces the five television bands allocated to the B.B.C. in the range 40 to 70 Mc/s. Intermediate bands are 5 to 15 Mc/s and 20 to 30 Mc/s; video frequency coverage 0 to 10 Mc/s. Sweeping of continuously variable width is obtained by a vibrating capacitor driven by a moving coil system. The generator, which is a.c. mains operated, is a timely addition to the Marconi range of television measuring instruments. Detailed specification on request.



TELEVISION SWEEP GENERATOR Type TF 923

Please ask for folder: SUMMARY OF COMMUNICATIONS TEST GEAR

Marconi Instruments Limited

ST. ALBANS, HERTFORDSHIRE Telephone: St. Albans 6161/5.

Northern Office: 30 Albion Street, Hull Western Office: 76 Portview Road, Avonmouth Southern Office & Showrooms: 109 Eaton Square, London, S.W.1 Midland Office: 19 The Parade, Leamington Spa.



Henry's
RADIO
COMPONENTS
& TELEPHONE
ELECTRONIC
EQUIPMENT

A SIGNAL TRACER at minimum cost. An easy-to-build unit that can be used for R.F., I.F., and Audio signal tracing, without any switching or tuning. Highly sensitive, easy-to-build, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain, 3-stage resistance-coupled audio frequency amplifier, with a 5-inch speaker in the Output of the Power Amplifier stage.

We shall be pleased to supply a complete kit for the construction of the above, right down to the last nut and bolt, for the low price of £3/18/6. Concise instructions and circuits are supplied. If preferred, circuit and instructions only can be supplied for 1/6 post free. All items may be purchased separately. This is a highly efficient instrument, and a MUST for every radio man.

TX VALVES. Westinghouse 813 at 50/-; 832 at 20/-; 866A at 15/-; Klystron 723A/B at 82/6. 3E29 (829B) at 59/6. All brand new and boxed.

R1355 MAINS TRANSFORMER. 200/250 v. input. Outputs 250-0-250, at 80 m/a., 6.3 v. at 6 a., 5 v. at 3 a. Fully shrouded top chassis mounting and guaranteed 100 per cent. Only 28/6.

MINIATURE MAINS TRANSFORMER. 250-0-250, 60 m/a., 6 v. 3 a., 5 v. 2 a., fully shrouded, well finished, size 3 1/2 in. x 3 in. x 2 1/2 in. Price 21/-.

RECEIVER TYPE 25. The receiver portion of the T/R 1196. Covers 4.3-6.7 Mc/s, and makes an ideal basis for an all-wave receiver, as per "Practical Wireless," August issue. Complete with valves types EF36(2), EF39(2), EK32 and EBC33. Supplied complete with necessary conversion data for home use. Only 22/6. Chassis only, 8/6.

OSMOR MIDGET "Q" COIL PACKS. Size 3 1/2 in. x 2 1/2 in. x 1 1/2 in. Amazing performance. Polystyrene formers with adjustable iron cores. One-hole fixing, only five connections. Factory aligned complete with full receiver circuits, and instructions. S'her for 465 kc/s, 33/- only. L.M.S. also for TRF operation M. and L., W., 30/-.

We can now offer the latest "Q" pack for S'her battery operation. Complete with circuits incorporating either IA7 or IT4 series. Valves. This pack is supplied with ready-wound frame aerial. Price 37/6.

Please note that separate H.F. Stage, for addition to the above Mains Superhet Coil Pack, can now be supplied at 15/- only. Complete with all necessary easy-to-follow instructions.

"VIEW-MASTER"

This now well-known T/V kit can be supplied by us at list prices as under. Constructor's Envelope, containing eight full-size assembly and wiring diagrams, and 32-page illustrated booklet packed with technical information. All required components are standard. Envelope price 5/-, post free. State London or Midlands.

Component kits are available as under:—
W.B. Chassis and Speaker kit including choke and transformer, etc., £6 5s. T.C.C. Complete Condenser Kit, £6 15s. Westinghouse Rectifier Kit, £3 2s. 6d. Morganite Resistor Kit, £1 6s. 9d. Scanning Coils, etc., Kit, £5 12s. 6d. Govern W./W. Potentiometer Kit, 19/3. Bulgin panel and switch Kit, 12/6. Wearite Coils and Choke Kit, £1 2s.

All required valves are in stock, and can be supplied. Cabinets will shortly be made available. Either 9in. or 12in. Tubes can be used, and all suggested types are in stock.

All orders executed in strict rotation.

PICK-UP BOBBIN. Standard replacement, for all types, 2000 ohms. 5/-.

METER DISTRIBUTION BOARDS. Comprising 0-300 v. M.I. Meter, 3 1/2 in. AC/DC Input Plug and Socket, 3 Output Sockets, 2 porcelain fuses. Total size 12in. x 6in. Brand new and individually boxed 17/6 complete.

POCKET VOLTMETER. Ex-Govt. Two range 0-15 v., 0-250 v., D.C. Brand new and complete in Web carrying case, only 10/6.

MILLIAMMETERS. 0-1 m/a., 2in. scale, square, moving coil, panel mounting, only 10/- each.

0-1 m/a., 2 1/2 in. scale, moving coil, panel-mounting, 15/- each.

0-5 m/a., 2 1/2 in. scale, moving coil, two mounted on panel, 12/6 pair.

MICROAMMETER. 0-500 micro/a., 2in. scale, moving coil, panel-mounting, 7/6 each.

VCR. 139A C/R TUBES. Electrostatic 2 1/2 in., tested and guaranteed O.K. Only 15/- each, plus 2/6 post and packing. Bases can be supplied at 2/- each.

Please include postage on all orders under £1.

Send stamp for current Component List. Probably the most comprehensive in the trade.

5, HARROW ROAD, LONDON, W.2
PADdington 1008/9

G2AK This Month's Bargains G2AK

American Telescopic Plywood Masts

These excellent 30ft. masts can be erected by two people in half an hour on tripod support and will carry a really heavy beam antenna, their hollow construction lends itself to this application, together with the fact that they are non-metallic and the telescopic feature allows tune up at a height of only 10ft. 5in. dia. at base, 3in. dia. at top, tripods 8ft. long, 4in. dia.

OUR PRICE
only
£4. 10. 0
each

Packing and Carriage 10/-.

Please write for photographs of above.

R.C.A. Speech Amplifiers, complete with all Valves. Line up, 4 type 6J7, 2 type 6L6, 1 type 5U4. Input 200-250 v. 50-60 c/s. Input for 30 ohms M.C. Microphone. Output 15 watts high quality phone. Output impedances, 500 ohms and 15 ohms.

ONLY
Complete in handsome grey cabinet 17in. long, 9in. high, 11in. deep. These are brand new **£15. 0. 0.** in original cartons and are unbeatable value at Plus 10/- carr.

300 ohm Twin Ribbon Feeder, 5d. per yard. Any length. Plus Postage 1/6.

Transmitting Valves. 250TH, 45/-; 100TH, 35/-; 813, 55/-; 807, 7/6; 15E, 10/-; 316A, 17/6; 8012, 17/6; 805, 30/-; 836, 17/6; 811, 20/-; 866A, 22/6; 723A/B, 60/-; 872A, 35/-; 832, 16/6; TZ40, 30/-; 35T, 25/-.

Power Trans. 320/320v 130 ma., 6.3 v. 5A ct., 5 v. 3 A. Primary 200/220/250 v. 50 c. Drop through type with loose leads. Our price, 18/6, Post and Packing 1/6.

CHAS. H. YOUNG, G2AK

Mail Orders to:

102 HOLLOWAY HEAD, BIRMINGHAM

Callers only to:

110, DALE END, BIRMINGHAM.

Phone: - Midland 3254

The Most Successful Aerial FOR FRINGE AREAS

of London and Birmingham transmissions

The **WOLSEY** Triple Reflector Array TR/MI is widely used and has proved remarkably efficient in numerous areas on the extreme fringe of the London transmission. Equally satisfactory reports are being received concerning the model TR/MI B for the Birmingham area. Both models have been laboratory designed to give a high gain and wide bandwidth. List Price **£6**

Brackets and Pole extra

Also recommended to overcome severe interference within all limits. Brochure illustrating all types of **WOLSEY** T.V. Aerials with polar diagrams free on request

WOLSEY TELEVISION LTD.

Established 1934

LONDON: 75 Gresham Rd., S.W.9. BRiXton 6651/2
BIRMINGHAM: 59, Soho Hill, 19. Northern 2762



KERSHAW'S KORNER KALLING SPECIAL!! SPECIAL!!! BRAND NEW HOOVER MOTORS

(Not Government Surplus)


Type S.P. 201 Shaded - Pole (Brushless) Fractional H.P. 200-250 volts, 50 cycles, A.C.— Speed 500 r.p.m. approx. With long 1/2" shaft.

IDEAL AS GRAMOPHONE MOTORS — BUFFING MACHINES AND MIXERS, ETC.

STUPENDOUS VALUE **30/-** EACH POST PAID

S. KERSHAW

93/95 PERSHORE STREET, BIRMINGHAM, 5

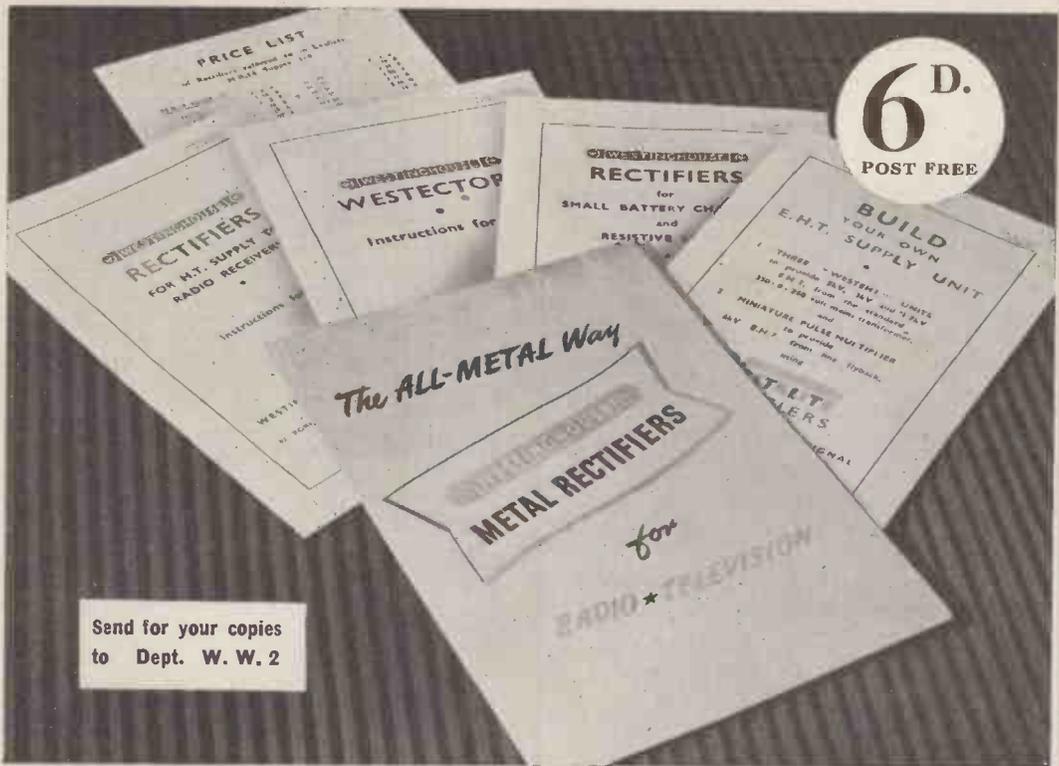


WESTINGHOUSE BRAKE & SIGNAL CO., LTD., 82, YORK WAY, KING'S CROSS, LONDON, N.1

Serving the Four  Corners of the World

The need for reliable Radio communication is being met throughout the world by Redifon equipment for many civil, commercial, marine and aeronautical services. The G.41, illustrated, is a typical example of a 5-7½ KW Transmitter for world wide, high speed Telegraphy, Teleprinter, Telephony and Broadcast purposes.

COMMUNICATIONS
Redifon
Radio

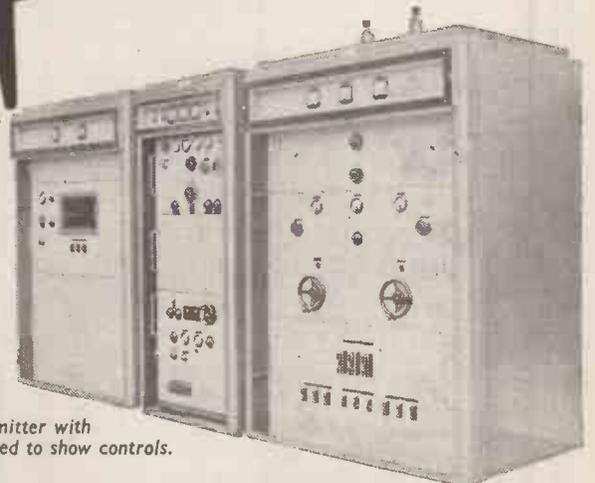

G.41 Transmitter with doors removed to show controls.

Radio Communications Division

REDIFON LIMITED, BROOMHILL ROAD, WANDSWORTH, S.W.18
DESIGNERS & MANUFACTURERS OF RADIO COMMUNICATION & INDUSTRIAL ELECTRONIC EQUIPMENT. Phone: VANdyke 5691



EVERYTHING FOR THE TELEVISION CONSTRUCTOR

A 9in. or 12in. picture at a minimum cost. "THE VIEWMASTER." As exhibited at Radiolympia. A 32-page booklet packed with information and other necessary data is supplied, together with 8 full-size working drawings and stage by stage wiring instructions.

This receiver incorporates a brilliant black and white picture with all the latest developments, and can be built from standard components. 7 DAYS' APPROVAL. MONEY REFUNDED IF DISSATISFIED. DATA FOR ALEXANDRA PALACE AND/OR SUTTON COLDFIELD NOW AVAILABLE. PRICE 5/- POST FREE.

- VALVES: EB91 @ 12/10; 6K25 @ 12/10; 6P28 @ 21/4.
- BULGIN KIT. Complete, including switch, 12/6.
- WESTINGHOUSE METAL RECTIFIER KIT. Price £3 2s. 8d.
- COMPLETE SET OF WIRE WOUND POT/METERS. 5 Colvern, 2 Morganite. Price 25/6.
- COLVERN POT/METER. CLR 901 @ 2/9. CLR 4089/22 @ 5/6 each, all values.
- MORGANITE VARIABLE RESISTANCES. Type Q, 4/6 each, 9/- the pair.
- COMPLETE KIT OF CONDENSERS BY T.C.C., comprises 55 condensers and 5 fixing clips. Price £6 15s. 0d. in kit. T.C.C. MICAD1829, 500 pf., price 1/6 each.
- WEARITE COILS. COMPLETE SET IRON CORED. 20/- the set.
- WEARITE R.F. CHOKE, 230 microhenries, price 2/-.
- PLESSEY EQUIPMENT. Boost choke L10, 72000. 5/-; frame transformer 72001, 18/6; front and rear c.r. tube supports 72007, 14/-; scanning coil 72003, 25/8; focus ring 72004/5, 19/6; wide h control 72002, 8/9; ERT transformer 72000, 21/3; COMPLETE KIT OF PLESSEY COMPONENTS 72000-7. Price £5 12s. 6d.
- G.E.C. Neon Lamp, type G, 2/9.
- W/B EQUIPMENT. Video chassis with 8 valve holders and rubber grommets, 22/6. Video chassis supports, 5/-; Time base chassis with 4 valve holders, 22/6.
- HEATER TRANSFORMER. 200-240 volts tapped input. Output 6.3 v. 7 a.; 6.3 v. 2 a. (tapped at 2 v.), price 35/-. SMOOTHING CHOKE, price 12/6. 6in. Loud-speaker with transformer (special type), 27/6.
- COMPLETE SET OF W/B PARTS (order VM/WB). Items 1-6, 28 5s. 0d. the set.
- COMPLETE RESISTANCE KIT BY MORGANITE (Order VM/40A), 26/9.
- BELLING-LEE MAINS CONNECTOR UNIT. With fuses, type L707, price 7/6.
- CATHODE RAY TUBES. By Mullard, Mazda, G.E.C., Ferranti, etc. Price: 9in., £11 6s. 10d., inc. tax; 12in., £15 2s. 5d., inc. tax.
- The above tubes are for callers only. We regret that owing to the great risk of breakage these cannot be sent by carrier.
- RUBBER MASKS (WHITE) for 9in. CATHODE RAY TUBES. Price 7/6 and 11/6.
- RUBBER MASKS (WHITE) for 12in. CATHODE RAY TUBES. Price 22/-. New 12" black rubber masks. Price 17/6.
- A few 12in. masks, slightly soiled, black rubber. Price 12/6.
- TELEVISION AERIALS. All types in stock. Indoor from 15/-. Outdoor from 37/6.
- POST FREE ON ALL ORDERS OF £4 or OVER.

EX-A.M. RECEIVER. Type 71. Contains 8 valves: 4 EF50, 1 EL32, 2 EF39, 1 EB93. Also many components, resistances, condensers, coils, etc. Frequency covers 124 Mc/s. Superhet unit with an R.F. stage and three I.F. stages. Overall dimensions, 10 1/2 x 7 1/2 in. x 6 in. The breaking up value is well over £3. LASKY'S PRICE 19/-. Carriage 3/6 extra.

EX-A.M. RECEIVER. Type R1155. BRAND NEW IN MAKER'S ORIGINAL WOOD TRANSIT CASE. A ten-valve communication receiver covering amateur and broadcast bands. Supplied complete with all valves, circuit, full modification data and power pack diagram. LASKY'S PRICE £12 10s. 0d. Carriage 7/6 extra.

BRAND NEW AND UNUSED POWER UNITS, Type CP/11. Primary, 200-250 volts, 50 C.P.S. Tapped. Contains 2 heavy duty transformers, 2 of U50 rectifiers, 3 chokes, condensers, etc. Output 250 volts, 6 volts and 5 volts. Can be supplied with one 5Z4 and one KT61 in lieu of the two U50 rectifiers at no extra cost. LASKY'S PRICE, 65/-. Carriage 7/6 extra.

BRAND NEW IN MAKER'S CARTON. PACKARD-BELL PRE-AMPLIFIER. Supplied complete with circuit. Contains 2 valves, 6SL7 twin triode and 28D7 twin pentode. Also input and output transformers and many other components. Enclosed in lightweight metal case, size 4 1/2 in. x 5 in. x 4 in. Weight 3 1/2 lbs. LASKY'S PRICE 12/6. POST FREE.

EX-A.M. POWER UNIT, Type 567C/WV. BRAND NEW AND UNUSED. IN MAKER'S ORIGINAL CARTON. Containing 11 new valves: 2 5Z4, 2 5U4G, 1 VU120, 1 6X5GT, 1 EF50, 1 EF55, 1 6V6G, 2 V870 (voltage stabilisers). Dozens of various components, including high voltage condensers, chokes, pot/meters, resistances, condensers (8 mfd. 500v.w.), etc. Totally enclosed in metal case. Size, 12in. x 11 1/2 in. x 8in. Weight 40 lbs. LASKY'S PRICE 49/6. Carriage 5/- extra.

VALVE HOLDERS. Ceramic (EF50) B9G, 6d. each, paxolin 5d. each. Ceramic (EB91) B7G, 10 1/2 d. each, paxolin 6d. each. International octal paxolin 6d., amphenol 6d.

TOGGLE SWITCHES. 1/- each. TERMINAL STRIPS: 3-way 3d., 5-way 6d., 7-way 9d. GROUP BOARDS: 5-way 4 1/2 d., 8-way 6d.

EX-SERVICE POT/METERS. Wire wound. 500, 1,000, 5,000, 10,000, 25,000 ohms. The above are priced at 2/- each.

EX-SERVICE VARIABLE RESISTANCES. 1/2 meg., 1 meg., 1 meg., 5K, 10K, 50K, 100K ohms. Price 2/6 each.

ALL TYPES OF CONDENSERS IN STOCK. LET US KNOW YOUR REQUIREMENTS.

BEL COILS. Set of 10 iron cored, 16/-; BEL 250 mA R.F., Choke 1/8.

6in. TRUVOX speaker, 13/6; 8in. R. & A. speaker with transformer, 17/6.

All values of resistances: 1/2 w., 3d. each, 2/6 doz.; 1 w., 4 1/2 d. each, 3/6 doz.; 1 w., 6d. each, 5/- doz.; 2 w., 9d. each, 7/6 doz.

Send a 2d. stamp with your name and address for a copy of our current list of Ex-Government bargains. The Lasky's Radio Bulletin.

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(opposite Paddington Hospital)

Telephone: CUNningham 1979


Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. half day

PRATTS RADIO

1070 Harrow Road, London, N.W.10

(Nr. Scrubbs Lane)

Tel. LADbroke 1734.

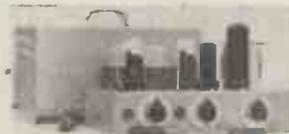

MODEL AC10E £8 18 6

AMPLIFIERS. College general purpose units. Model AC10E 10 watt 4 valve unit. Neg. feedback. Separate Mike stage, separate inputs for mike and gram with twin faders. Tone control. Complete in case with chrome handle, £8/18/6. Model AC18E 6 valve unit with push-pull output and feedback over 3 stages. Inputs, etc., as AC10E. Twin faders and cone control. Output 18 1/2 watts. Complete with case and chrome handles, £13/19/6. Model UI0E 6-valve unit with push-pull output and feedback over 3 stages for D.C./A.C. Mains. Output 10 watts. Specification as AC18E, £11/11/-.

All above have outputs to match 3, 8 or 15 ohm speakers and are ready for immediate use. Input voltages average less than 003 v. mike and 3 v. gram. No pre-amplifier required. Model AC4C, A.C. or U4C, A.C. D.C. 3-valve Gramophone amplifiers. Output 4 watts to 3 ohms, £4/19/6. Stamp for fuller details.

TRANSFORMERS. E.H.T. 2,500 v. 5 mA 4 v. 1 1/2 A, 4 v. 2 A C.T. (for VCR97), Input 200-240 v. (in 10 v. steps), 27/6. 2 x 350 v. 120 mA, 6 v., 6 A; 5 v. 4 A; 4 v. 4 A, 35/-.

Heavy Duty Output Transformers, 30 watt 10 ratio. 20-1 to 140-1 C.T., 23/9. Ultra Midget for 154, 354, etc., 3/11. (All new manufacture.)

SPEAKERS. Truvox 2 1/2 in., 17/6; 8 in., 14/6; 12 in., 37/6. Rola 5 in., 13/-; 12 in., 130/-; Plessey 8 in., 11/9; 10 in., 18/6; Rola M-Energised 6 in., 700 ohm, 10/-.

CONDENSERS. B.1 500 550 v. C'b'd. blocks, 8 mfd., 3/3; 8 + 8, 4/9; 8 + 16, 6/-; Midget 450 v. Can Type, 16 + 8, 3/9; 8 + 8, 3/6; 16 + 16, 4/-; 25 mfd. 25 v., 10d. 2 mfd. 350 v., 1/-; Philips type 32 mfd. 350 v., 5/9.

VARIABLE CONDENSERS. 2 gang .0005, 4/3, 3 gang, 6/9. With feet and long shaft. Presets. 50 pf. 4d. 100 and 500pf, 1/3.

MISCELLANEOUS. Ceramic U.S. Octal Base, 5d. Paxolin EF50, 7 1/2 d., B7G, 7 1/2 d. Volume Controls with switch, 4/6, less switch, 2/9. Chokes, 60 mA, 20 Hy 400 ohm, 6/6; 90 mA 10 Hy, 10/6; 150 mA 10Hy, 14/3. Bulgin Jack sockets, 1/6; Plugs, 9d.; Wearite 'P' Coils, 3/- each.

All Goods New and Unused. C.O.D. or C.W.O. Post Free over £1.

Technical Excellence

combines with beauty and soundness of DESIGN in the



OXLEY DIFFERENTIAL AIR DIELECTRIC TRIMMER

- ★ Width: 16.5 mm Length: 25 mm
- Height: 1.5 to 8pf-8 mm
- 1.8 to 20pf-12.5 mm
- 2 to 26pf-11.5 mm
- 2 to 32pf-12.5 mm
- Law: Straight line capacity
- Power Factor: Less than .001
- Insulation: Over 2,000 megohms
- Voltage: 500 D.C.

OXLEY DEVELOPMENTS CO., LTD., ULVERSTON, N. LANCS. TEL. ULVERSTON 3306

RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialise in

AMATEURS' WINDINGS, TRANSFORMERS ALL TYPES, CHOKES, PICK-UP COILS, INSTRUMENT COILS, Etc.

Highest workmanship

Good Delivery

RADIOMENDERS, LTD.

Television & Radio Apparatus, Transformer & Coilwinders.

123-5-7 Parchmore Road,

THORNTON HEATH, SURREY

LIV 2261. Trade enquiries invited. Established 16 years.




Another **GOODMANS** *Axiom*

HIGH (FIDELITY + POWER) ^{Regd.}


With an exceptionally high electro-acoustic efficiency, this new version of the well-known "Axiom Twelve" has been developed to satisfy the great demand for High Fidelity power reproduction.

Send for illustrated folder D20

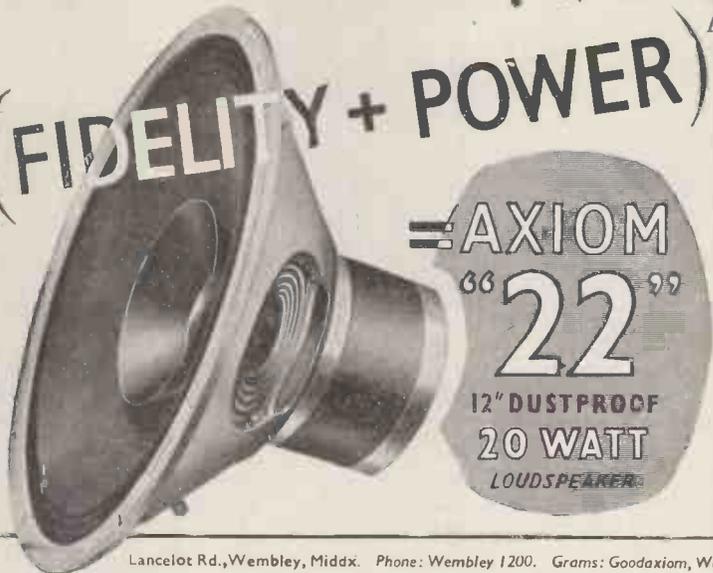

GOODMANS INDUSTRIES LTD.,

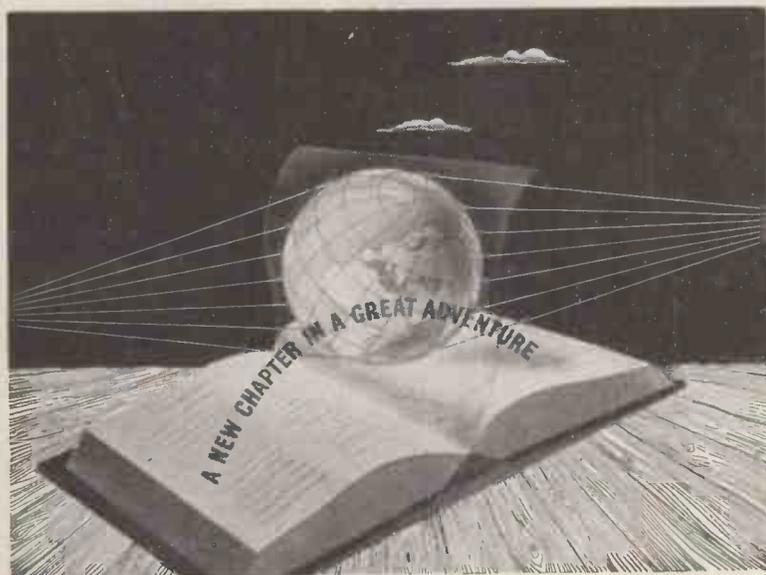Lancelot Rd., Wembley, Middx. Phone: Wembley 1200. Grams: Goodaxiom, Wembley




From the first great adventure of wireless communication half a century ago, the story of Marconi has been one of successive achievement. Wireless telegraphy, wireless telephony, broadcasting, television, radar, wireless navigational aids at sea, on land, and in the air — Marconi's have played a pioneer part in their development. With a vast accumulation of knowledge and experience behind them, Marconi's are now engaged on new developments which will more than maintain their shining reputation.

Marconi

THE GREATEST NAME IN WIRELESS



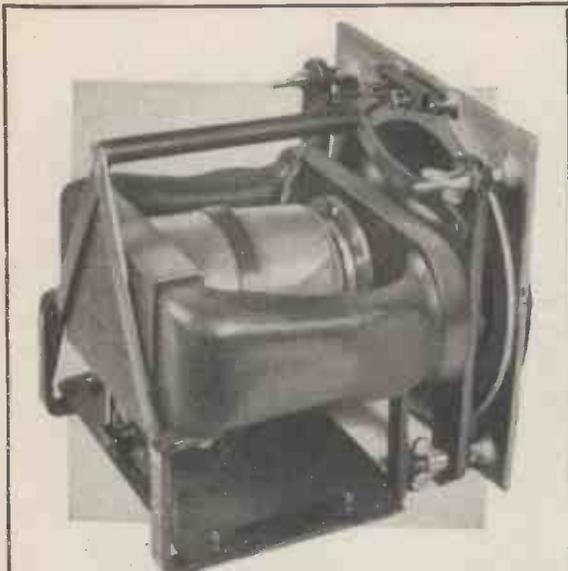MARCONI'S WIRELESS TELEGRAPH COMPANY LIMITED, MARCONI HOUSE, CHELMSFORD, ESSEX



The VOIGT P.M. Unit

for use with horn loading.

(As reviewed "W.W." March 1949, Page 103).

Work done since last spring, and reports from experimenters who have tested a delicate variety of the REMATCHED diaphragm requiring a gap of 1 mm. only, indicate that this should be sufficiently stable for practical use. Two directions for progress become possible from this modesty in demand for gap width.

(1) The **REALISTIC**: to use a smaller magnet, such as the best mass production types, but adapted to suit the diaphragm and provide a flux density comfortably into the saturation region, the combination producing a result rather better than our pre-war best, and eminently suited to average present day conditions or export. Anticipated price under £25. Prototype now being tested. Please await further announcement.

(2) The **IDEALISTIC**: to drive the gap flux density well into the super saturation region between 20,000 and 24,000 lines, thus producing a Laboratory speaker years ahead of its time, suitable for home use when an undistorted input is available. Our first 1950 batch will be of this form. External appearance as above. Anticipated price including B.B.C. corrector and revised experimental pole tips £40 ex Works.



CORNER HORNS (in the white) £47 : 10 : 0 and £19 : 10 : 0 ex works.

Send your order to :

VOIGT PATENTS LTD.
c/o BCM/VOIGT, London, W.C.1

MIDLAND INSTRUMENT CO.

FOR GOVT. SURPLUS STOCK, ETC.

MAGNET MOTORS, 3in. transmitter MK-9, two of these motors can be wired in series for 100v., or in parallel for 50v. A.C. single phase, in this way, when the shaft of one motor is turned, the other will follow in perfect step, clockwise or anti-clockwise, ideal where a perfectly synchronised remote control is required. Motors are approx. 5in. long, 3 1/2in. dia., weight 4 lb., fitted 1in. long 5/16in. shaft, unused condition. Two motors (worth £10) supplied with wiring instructions for 15v., post and packing 1/6 extra. Four or five motors can be used across 200/250v. A.C. mains, any one motor controlling the other three. **CHOBERT RIVETERS** TYPE "R," an automatic hand tool for repetition placing of tubular rivets (blind); takes approx. 90 rivets in magazine, complete with two of each, 3-size mandrels, also other spares. Instructional Booklet, unused in good cases, size 23 x 6 x 5in., worth £15, our price 37/-, post 1/4. **TYPE 21 RECEIVERS**, 2-band, 4.2 to 7.5, and 19 to 31 Mc/s, contain 11 valves, AR12/VE23 (7), AR5/HL23DD (4), also Mallory type 650 6v. vibrator, slow-motion drive and dial engraved in Mc/s, with other controls, chassis mounted with side protection frame, size 9 1/2 x 8 1/2 x 9 1/2in., designed for 6v. operation, complete with data for converting to 2v. L.T. supply operation, unused condition, 37/6, post and packing 2/6 extra. **TRANSFORMERS**, input 230v. 50 cycles, outputs 650v. at 20 mA., three 4v. windings at 1.25 amp., also 6.3v. at 1 amp., all terminations engraved, 4 1/2in. high, 3 1/2in. square, weight 4 1/2 lb., new boxed, worth 50/-, our price 15/-, post 1/-. **CHOKES**, 100 H. at 10 mA., 5,000v. R.M.S., weight 1 1/2 lb., brand new boxed, 5/-, post 9d. **TELEPHONE CABLE** D8, twin twisted rubber covered and braided yellow/black, 880ft. wound on wood drums, new unused, 25/-, carriage 5/-. **MAINS TRANSFORMERS**, input 230v. 50 cycles, single phase, output 50v. 11 amp., or with little alteration 100v. at 5 1/2 amp.; unused 25/-, carriage 5/-. **FLEXIBLE DRIVES**, approx. 1/2in. outer spiral metal casing, with ends for screw fitting, suitable for light power transmission, speedometers, remote control, etc.; 5 different sizes, 1 1/4, 1 1/8, 3/4, 2/8, 1/4, 3/8, 1/2, 5/8, 3/4, 1 1/8, 1 1/4, 1 1/2, 1 3/4, 2, 2 1/4, 2 1/2, 3, 3 1/2, 4, 4 1/2, 5, 762 1/2, 763, 763 1/2, 76

MEGOHMMETER

MODEL · RM 175-L

★



This instrument measures the insulation resistance at continuously variable test pressure up to 1,000 volts D.C., and is direct reading up to 10 million megohms. An automatic pre-charging device is incorporated. The apparatus is arranged for the connection of 3 terminal electrodes for the measurement of surface or volume resistivity.

★

For particulars of this and our full range of measuring instruments, write to:—

**BRITISH PHYSICAL
LABORATORIES
HOUSEBOAT WORKS,
RADLETT, HERTS. Tel.: RADLETT 5674-5-6**

★

WHAT CAN I DO THIS WINTER?

Well, if you know something about radio and are reasonably good with your hands, you can make yourself a Magnetic Recorder. This fascinating hobby is within your reach; using Park Radio's plans and parts you can make the recorder, including super-quality amplifier, for £20.

Recordings are made on wire or tape; they can be played time and time again without deteriorating, and when no longer required can be erased completely. In this way the wire or tape can be used over and over again.


Send 5/- now for complete Constructional Data, working drawings, and a price list of all parts.

PARK RADIO of MANOR PARK

676/8 ROMFORD ROAD, LONDON, E.12

(A division of Judge Industries)

SPECIAL OFFER TO THE Enthusiast!

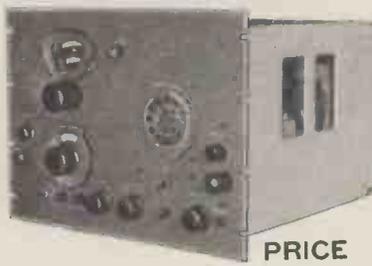

PRICE £23.10

Famous U.S.A. Radio Communications Receiver, Type BC1147A. This Receiver was one of the last types to be sent into this country for use with the Armed Forces and is a 13-Valve Superheterodyne of high efficiency covering from 1.5 to 30 m/c/s in four bands, with 5 per cent. frequency overlap between bands. Band division is 1.5 to 3.1 m/c/s, 3.1 to 6.6 m/c/s, 6.6 to 14.0 m/c/s and 14.0 to 30.0 m/c/s. Frequency calibration is accurate to within 1 per cent. of indicated value. The set has a built-in power pack for operation from 115 volts A.C. 50/60 cycles and we supply a suitable Auto Transformer to operate from standard 230-volt A.C. mains for use with each set. The Receiver employs two stages of R.F. Amplification with 455 KC/s IF's which have an externally controlled broad and sharp response switch. Valve Line Up: 1 6SH7, 4 6SK7, 1 6SA7, 1 6A5, 1 6H6, 1 6SJ7, 1 6SQ7, 1 6K6 or 6V6, 1 VR150 and 1 5U4G. The Handsome Front Panel is complete with Aerial Matching Control, Wave-band Switch, Tuning Control, AF Gain Control, IF Selectivity Control, BFO Control, Sensitivity Control, Power On/Off Switch, BFO On/Off Switch, AVO and Manual Control, Built-in Loudspeaker and Indicator Light Control. Size 19in. wide, 14in. high and 19in. deep. Price includes suitable Auto Transformer, Packing in Wooden Crate, and Carriage Paid to your door.

NO CARRIAGE OR PACKING CHARGES

Carriage paid on all orders in U.K. For Air and Export additional charges must be added or we will quote.

N.B.—The price of £28/10/0 quoted in the December, 1949, issue was a misprint due to a typing error.

WESTON PRODUCTS

(LIVERPOOL) LTD. • TEL: ROYal 5754/5.
71-GT-GEORGE STREET-LIVERPOOL-1

NEW COMPONENTS FROM STOCK

PM Focus Unit (Bel. Universal)	£1 15 0
PM Focus Unit (Bel. Tetrode CRT).....	£1 12 6
PM Focus Unit (A.M.C. for all Mullard tubes 9 and 12in.)	£1 1 0
PM Focus Unit (A.M.C. for all tubes 9 and 12in. other than Mullard).....	£1 2 6
Haynes Line Output Trans. TW6/126 4-1...	£1 16 0
Haynes Scanning Coil S914.....	£1 18 3
Haynes Focus Coil F912H.....	£1 16 0
Haynes EHT (RF) Unit, 5 to 8 Kv.	£5 8 0
Hazlehurst 2 to 5.5 Kv. EHT Unit (RF)...	£3 15 0
Hazlehurst 5 to 8 Kv. EHT Unit (RF).....	£4 15 0
Hazlehurst 2 to 5 Kv. coil only.....	£1 2 6
Hazlehurst 5 to 8 Kv. coil only.....	£1 10 0
Cathode Ray Tubes, G.E.C. 6504 9in. flat face	£11 6 9
Cathode Ray Tubes, Mullard MW22-14C 9in.	£11 6 9
Cathode Ray Tubes, Mazda CRM92 9in.....	£11 6 9
Cathode Ray Tubes, Mullard MW31-14C 12in.	£15 2 5
Cathode Ray Tubes, Mazda CRM121 12in....	£15 2 5
Cathode Ray Tubes, Ferranti flat faced 12in.	£15 2 5

Send for television components lists.

When ordering, please include sufficient for postage and packing.

Shop hours: 9-6 p.m. Monday-Saturday, 9-1 p.m. Thursday

TELE-RADIO (1943) LTD.

177, EDGWARE RD., LONDON, W.2
Phone: PAD 6116. PAD 5606.

SUPACOILS OFFER

Model 30 Coil Pack.—The 3-waveband superhet pack with adjustable iron cored coils and trimmers for absolute accuracy in padding and tracking. This pack is gaining more and more favour among experienced engineers and amateurs for its sound design, high quality workmanship, high sensitivity and selectivity 21/- or 24/- fully aligned.

Model 40 Coil Pack.—Similar to the Model 30 but with RF stage 42/- or 47/- fully aligned.

Model 30 Tuning Unit.—This is now one of the most popular units for easy and efficient superhet construction. It consists of a Model 30 coil pack, pair "MM" I.F. transformers, 2-gang condenser and attractive dial. Components are 48/6 aligned together as a unit in an actual receiver and sealed. No further alignment is required.

Model 40 Tuning Unit.—Similar to above with provision for R.F. stage 76/9
FREE. A Free Copy of the enormously successful HOME CONSTRUCTOR'S HANDBOOK will be given to every purchaser. Or a copy can be obtained for 1/- from

SUPACOILS (Mail Order Office)
98, Greenway Avenue, London, E. 17

THE Fidelia
LUXURY 8-VALVE
RADIOGRAM CHASSIS

Features include variable selectivity, infinite impedance detector, electronic bass and treble controls, push-pull triode output stage: 3 wavebands 16-50, 190-550 and 1,000-2,000 metres. Audio amplifier response 30-18,000 cycles; bass, treble and volume controls operate on gramo, suitable for light weight p.u. Guaranteed 12 months. Price 291/6/-.

ELECTRO Acoustic DEVELOPMENTS

18 BROAD ROAD, WILLINGDON, SUSSEX.

COVENTRY RADIO

Component Specialists since 1925

10,000

Radio Valves in stock, all types. Immediate delivery at current list prices. Full range of 1st Grade makes of components—Note we do NOT stock surplus, only new goods. New list available shortly.

COVENTRY RADIO

189, Dunstable Road, Luton

THIS — Does these

ACCURATELY and QUICKLY

Chassis, Brackets, Shrouds
Condensers and Transformer
Clips, in Steel or Aluminium.
(Five sizes—12" to 36")
Trepanner available

NEW! "SNAP" Cutting Attachment. Cuts corners, shears and notches.

Details with pleasure

Please Quote File No. or Serial No. of your tool if possible.

YES! We are still in business. We have been trying to overtake our order book. We can now accept new business for reasonable delivery.

A. A. TOOLS (W), 197a Whiteacre Road ASHTON-U-LYNE

★

LUDLOW & COLE

PICKETTS AVENUE
LEIGH-ON-SEA
ESSEX

Tel.: Southend 76589

●

Specialists in
Transformers

★

MODEL 90A FORTY RANGE TAYLORMETER

1000 ohms per volt

RANGES

Voltage. Up to 1000 V. A.C. and D.C.
Current. Up to 1 amp. A.C. and D.C.
Output. Up to 250 V. Six decibel ranges.
Resistance. From 1 ohm to 1 megohm self contained. Buzzer fitted for quick continuity tests. Meter overload protection fitted.

LIST PRICE £15 . 15 . 0


All Windsor and Taylor test equipment is available on H.P. Terms. Send for details and catalogues.

DELIVERY EX STOCK.

TAYLOR ELECTRICAL INSTRUMENTS LTD.
 419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND
 Telephone: Slough 21381 (4 lines) • Grams & Cables: Taylins, Slough



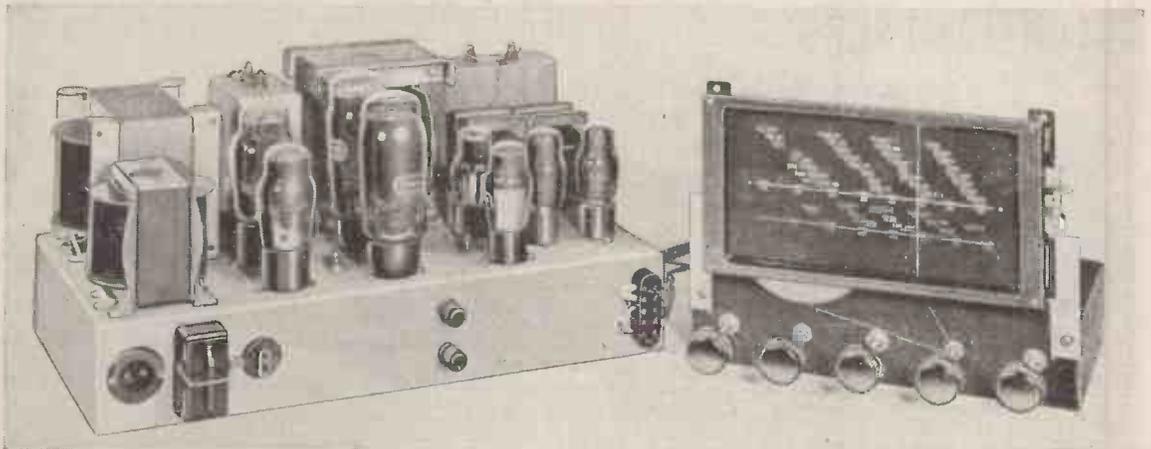Other Products Include: Multirange A.C. D.C. Test Meters • Signal Generators • Valve Testers • A.C. Bridges • Circuit Analysers Cathode Ray Oscillographs • High and Low Range Ohmmeters • Output Meters • Insulation Testers • Moving Coil Instruments



GOODSELL

HI-FIDELITY AMPLIFIERS

As described by T. N. Williamson in "Wireless World," Aug., 1949

ALSO HI-FIDELITY TUNERS & PRE-AMPLIFIERS

PRICES

Amplifiers	from £19 19 0	} No Tax
Pre-Amplifiers	from £8 0 0	
Tuners with Pre-Amplifiers	£10 10 0	} Plus Tax

Send for free illustrated brochure.

N.B. We regret that owing to unprecedented demand there is a slight delay in delivery. All orders will however, be executed in strict rotation.

Manufactured by **GOODSELL LTD., 40, GARDNER ST., BRIGHTON, SUSSEX** 'Phone : 6735

Easy terms from LONDON RADIO SUPPLY CO. BALCOMBE, SUSSEX

G. W. SMITH & CO., (RADIO) LTD.

TELEVISION. Ex-R.A.F. type 208 Amplifier units, complete with 2 E.F.50 valves. Ideal as Pre-Amplifier for both Vision and Sound, with full conversion instructions for sound and vision, 25/- each.

Transmitter Units, type T.U.B. Nos. 5, 6, 7, 8, 9, 10 and 26 complete with cabinet, 15/- each.

B.C. 455 Receivers, complete with valves, 22/6 each. **B.C. 454 ditto,** 25/- **B.C. 453, 39/6.**

Television High Voltage type Mansbridge Condensers, "TROUBLE FREE" .1 3000 v. 2/-; .1 4000 v. 3/-; .1 5000 v. 3/3 each

Transformers, Adm. Patr., 230 volt 50 cycle, Primary, Secondary, 700 volt 20 M/a. Filaments Tested at 5000 volt, 2 of 4 volt 1.25 amp., ideal transformer for 'scope unit. 17/6 each. Brand New and Boxed.

Filament Transformers, Ex-W.D. 230 volt primary 6.3 volt C.T. 3-5 amp. 10/6 each.

Filament Transformers, Ex-W.D. 230 volt primary 5 v. 3 amp., 6.3 v. 1.25 amp. twice, 6.3 v. .6 amp. 12/6 each.

Television Condensers, 1000 pf. 500 pf. midget moulded mica, 4d. each. .001 mfd. 5000 v. mica 1/3 each. .001 mfd. 9000 v. 1/3 each. .001 mfd. 15000 v. 1/6 each.

Open All Day Saturday.

3 LISLE STREET, LONDON, W.C.2

Phone : GERRARD 8204

FOR QUICK DELIVERY
AT
REASONABLE PRICES
OF
RADIO & ELECTRONIC PRODUCTS

(Wholesale Only)

Write or phone:—

S. Szymanski
(pronounced SHE-MAN-SKEE)


ELECTRONIC ENGINEER & STOCKIST
95 STRODES CRESCENT
STAINES, MIDDLESEX

Staines 3971

VALVES are our speciality—Probably the
Largest Actual Stockist in England

EXPORT ENQUIRIES WELCOMED

POTENTIOMETERS

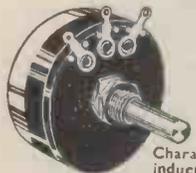

by
RELIANCE

Wire-wound and Composition types.
Single, Ganged, Tandem Units.

Characteristics: linear, log., semi-log., non-inductive, etc. Full details on request.

RELIANCE MFG. CO. (SOUTHWARK), LTD.,
Sutherland Road, Higham Hill, Walthamstow, E.17.

Telephone: Larkwood 3245

FT.300 TRANSMITTERS Manufactured by Federal Telephone & Radio Corp. U.S.A. Four RF units operating on C.W. simultaneously at 3 kW output each. 2 Mc to 20 Mc.

RCA TRANSMITTERS. Type E.T. 4332B, 2 Mc to 20 Mc, 350 W. c.w., 250-w. rft, two 813's output. Separate speech amplifier. Two 805 modulators. Rectifier—four 866's.

HALLCRAFTERS. BC610 with speech amplifiers, aerial tuning units, tuning boxes and coils.

HIGH SPEED TELEGRAPH equipment, "Boehme" (U.S.A.). Up to 400 words per minute on line or wireless. New. Working demonstration on request.

AR.88.D's. SX 28's. HRO's with 5 or 9 coils, power packs.

METAL RECTIFIERS type 7B. Max. D.C. output at 36 v. 56 amp. Supply voltage. 200/250 v. Brand new.

All above items in excellent working conditions with new valves. Large stock of transmitting condensers, valves and other components. Alignment and repair of communication receivers and all other amateur equipment.

P.C.A. RADIO

THE ARCHES CAMBRIDGE GROVE, LONDON W.6. Phone RIV. 3279

Branch, 170, Goldhawk Road.

MUMETAL and RADIOMETAL TRANSFORMERS and CHOKES

As Specialists with many years of experience we can design and supply practically any type of transformer or choke with a nickel-iron core for use on a band within the frequency range.

1 c/s to 150 kc/s

Available for rapid delivery—Microphone Transformers, Input Transformers, Line Transformers, Pickup Transformers, Output Transformers, Rectifier Transformers, Vibrator Transformers, High Fidelity Transformers, Recorder Transformers, Midget Transformers, High Q Chokes, High Inductance Chokes, etc., with or without Mumetal Shields.

MAINS COMPONENTS ARE ALSO STOCKED.

SOWTER TRANSFORMERS

E. A. SOWTER, I.B. HEAD STREET,
COLCHESTER.

Phone : COLCHESTER 5459.

You can master MATHEMATICS

If you wish to understand radio really thoroughly you must know Mathematics. Our new Home-Study Courses make them really interesting and easy to learn.

T. & C. RADIO COLLEGE

Specialists in Home-Study Tuition
in Mathematics, Radio & Television.

Write for free booklet "W" to:—

R. Heath Bradley, T. C. R. C.,

50, Harland Road,

SOUTHBOURNE, BOURNEMOUTH.

AMPLIFIERS' Quality KIT for HOME CONSTRUCTORS

A complete set of components to construct a 10 watt amplifier including Woden potted mains transformer. 5 valves, 10 in. speaker with transformer. Components of the highest quality. No Govt. surplus. Three switched inputs, negative feed back, push-pull output, tone control, steel chassis. Suitable home or small hall. Price Complete to the last screw

CASH WITH ORDER **£7 10 0**

BEETHOVEN LTD ELECTRIC EQUIPMENT LTD

Chapel Lane, Sands, High Wycombe Telt 1152/3

Wireless World Classified Advertisements

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 6 words. Box Numbers, 2 words plus 1/- Trade discount details available on application. Press Day: March 1950 issue, first Post Monday, January 30th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee: Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

MASON'S, Wivenhoe, nr. Colchester.
ILLUSTRATED catalogue, price 9d, full details of high fidelity reproduction equipment, from 4-100 watts for domestic or industrial purposes. Our U.E.5 (6 watts) and U.E.7 (12watts) series amplifiers are designed especially for the connoisseur who requires the finest possible reproduction from recorded music, both amplifiers have a linear response over 30-20,000 cycles with a damping factor of 12, and incorporate pre-amplifier stage, together with independent control of bass and treble. Our policy is to produce an instrument which represents the highest standards in workmanship and performance and no expense has been spared to achieve this object. A new addition to our range is the type U.E.3 (4watts) at £11/10. We also supply a range of tuning units, both t.r.f. and superhet, for use in conjunction with either our own or other makes of amplifiers. We should be pleased to quote you for the design and construction of a unit or replacement chassis to your exact requirements. Full details of our products will be forwarded on request, and we would welcome the opportunity to demonstrate our equipment at any time to suit your convenience. [3352]

UNIVERSAL ELECTRONIC PRODUCTS, 36, Marylebone High St., London, W.1. Tel. Wetbeck 4058.
SPECIALISTS in the design and manufacture of high fidelity reproduction equipment, from 4-100 watts for domestic or industrial purposes. Our U.E.5 (6 watts) and U.E.7 (12watts) series amplifiers are designed especially for the connoisseur who requires the finest possible reproduction from recorded music, both amplifiers have a linear response over 30-20,000 cycles with a damping factor of 12, and incorporate pre-amplifier stage, together with independent control of bass and treble. Our policy is to produce an instrument which represents the highest standards in workmanship and performance and no expense has been spared to achieve this object. A new addition to our range is the type U.E.3 (4watts) at £11/10. We also supply a range of tuning units, both t.r.f. and superhet, for use in conjunction with either our own or other makes of amplifiers. We should be pleased to quote you for the design and construction of a unit or replacement chassis to your exact requirements. Full details of our products will be forwarded on request, and we would welcome the opportunity to demonstrate our equipment at any time to suit your convenience. [3352]

AMPLIFIERS, new, 60 watt heavy duty P.A. models, built for continuous rating and rack mounting; £40; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich.

DC mains? This new 8watt all miniature valve amplifier has been designed to give you high fidelity reproduction from DC mains supply, matched for moving coil pickup, output 2.5-15 ohms, bass and treble controls, complete £21/10, or with m/c. stage, £24.

FELICITY GRAMOPHONE Co., 87a, Upper Richmond Rd., S.W.15. Futurist. [3341]

12 watt, high-quality amplifiers, precision built instrument, bass and treble boost, high gain, complete with power pack, £12/10, less power pack, £8/15; send for descriptive literature and approval terms.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0067]

BUY direct from the manufacturers. Our 5-valve all-wave superhet radiogram chassis is now available. The price suits the pocket too, only £12 complete with valves and 6in P.M. speaker. Give courses for fitting out A/C55 in place of that old chassis and make a new radiogram of it. S.a.e. for illustrated leaflets. Trade enquiries invited.—Bayly Bros., 46, Pavillon Drive, Letch-on-Sea, Essex. [4595]

C. J. R. ELECTRICAL AND ELECTRONIC DEVELOPMENT, Ltd, Hubert St, Birmingham, 6 (Aston Cross 2440). the Midlands specialist manufacturers of high fidelity equipment for the "W.W. Williamson" and other quality amplifiers; also tone control stages, loud-speaker crossover units, distortionless contrast expanders and radio feeders; see our illustrated advert, in alternate issues of this publication; send for full details and prices. [3503]

CONNOISSEUR'S receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-1,500-metre, world-wide results on highly sensitive 10-valve receiver, comparable with any good communication set, or by change of switch, maximum fidelity reception of local stations on non-superhet basis with high quality 2-PX4 push-pull amplifier incorporating all refinements, bass and treble tone control (boost to cut), whistle filter and gram input, etc.; basis rebuilt R1155; write for details or call for demonstration. FEEDER units as above, for use with external high-quality amplifiers; R1155 specialist receivers repaired and re-aligned, also modified as above, or to your requirements; R1155 circuit and values 2/- post free.—R.T.S., Ltd., 5, Gladstone Rd., Wimbleton, S.W.19. Tel. Lib. 5303.

TELRAD ELECTRONICS, 70, Church Rd., Upper New Wood, London, S.E.19. Designers and manufacturers of Telrad quality amplifiers for commercial and domestic use; unique amplifiers, with exceptional quality; built to satisfy the discriminating ear, bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; £18, complete; full details on request.—Write, call or phone Livingstone 4879. [0019]



Partridge Mews

Now-hermetically sealed

IN OIL!



Illustrated is a typical Partridge Transformer (Type DN) in its Mumetal Screening Box. It is merely to remind you that all Partridge Precision Components (standard or "to specification" types) are now available as hermetically sealed units.



Then there's the 'PPO' range, designed to meet more fully the particular demands of push-pull output transformers where wide A.F. range with low distortion are vital.

FULL DATA ON REQUEST

PARTRIDGE TRANSFORMERS LTD

ROEBUCK ROAD, KINGSTON-BY-PASS
TOLWORTH SURREY
Telephone: ELMbridge 6737-8

NEW RECEIVERS AND AMPLIFIERS

HALLICRAFTERS dual diversity receivers, complete with power units and loudspeakers; few only available.

McELROY ADAMS MFG. GROUP, Ltd. (Hallicrafters), 46, Greyhound Rd., London, W.6.

QUANTITY radio feeder units and amplifiers: No. 1 Tuner T.R.F., L. & M. wave, infinite impedance detector, 6.3v valves, excellent reports from "Williamson" and "Leak 1" amplifier users; £5; complete kit, £4/10. No. 2 Tuner, 3-waveband superhet, special bandwidth, elaborate dial assembly; £5/10; complete kit, £7/10. No. 1 audio amplifier, 4-watt undistorted, 16 output, special neg. feedback circuit, 30ohms impedance (or to order), gram. and tuner inputs, £5/19/6; complete kit, £5/10; super crackle cabinet if reqd., £2 extra; terms, c.w.o. or c.o.d.: W.W. bargain list 24d.—Northern Radio Services, 16, King's College Rd., Swiss Cottage, London, N.W.3. Primrose 8314. [3005]

MIDCO amplifiers: AA/5 5-watt model with tone and vol. controls, £5/10; AA/10 10-watts P-P, with twin mix/fade inputs and tone control, £10; PA/12T record reproducer bass and treble tone controls twin mix/fade inputs, £14; PA/12M high gain m/c. model, one high one low "Z" inputs, £14/10; PA/12s are built in steel cases with indicator lamps, chrome handles, new model P/E1 amplifier and power pack chassis 8-10 watts fidelity reproduction, from 6V6 with two NFB loops, with approx. 2v drive, this unit is designed for use with separate radio feeder or gram pre amp. with tone and volume controls, £15/10; suitable feeder units available or built to specification; supplies for preamp 6V 2A, 300v 50mA available; enquiries for specials, further details and trade terms invited; competitive quotations for radio and amplifiers to specification; catalogue available.

MIDLAND RADIO COIL PRODUCTS, 19, Newcomen Rd., Wellingborough. [4871]

THERE is an amplifier which excels in quality of reproduction and that is the R.T.M.C. version of the now world-famous Williamson Amplifier, "exports all over the world and leading articles in the American Press prove that the R.T.M.C. version of a quality amplifier is the best so far produced in England or any other country. We invite you to compare performance figures with any other advertised quality amplifier. We produce also a PX4 version which, whilst much cheaper, is still in the "super-quality class"; we invite you to send for full details describing this wonderful amplifier; our files are filled with testimonials which can be sent any time; original 7-valve version (with improvements), £25/10; 9-valve version with built-in pre-amplifier, £30/10; separate pre-amp £6; PX4 version £17/10; tuners from £10/10; latest T.R.F. tuner with monitor speaker £12/10, as per latest Williamson circuit; write to the pioneers of this famous amplifier and be sure you get the best reproducer there is.

R.T.M.C. (Ealing), Ltd., Laurel House, 141, Little Ealing Lane, W.5, Ealing 6962. [3674]

RECEIVERS, AMPLIFIERS—SURPLUS

AND SECOND HAND

R88D and AR6LF receivers for sale.—J. Rae, 39, Penn Rd., Wolverhampton, Staffs. [4872]
R.A.F. model 1155, new, complete with valves, converted models from £8/10; send for lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0066]

HALLICRAFTERS Super Skyriver SX16, 7-valve model with loudspeaker, in superb walnut case; £30.—Levy, 6, Amberden Av., Finchley, N.3, Finchley 2440. [4849]

R. RAF 1155, perfect, in original transit case; £11 converted with output valve and smoothed mains power pack.—Jakubskind, 69, Church Rd., Moseley, Birmingham. [4771]

TELEVISION console, 12in tube, perfect order, £50; ditto less cabinet and tube, £25; vision units with valves, £4; seen working N.W. London; write to the suppliers; 10/-.—Box 1500. [4869]

R.F. units, 24 and 24 mod., 27 at 8/6, post 1/3, 25 at 12/6, 27 at 22/6; receiver type 1225 with 5XEF50, 2XVR53 and VR54, £1 ea.; wave-meter G60, 180-230m/c, complete with 1Cn/5 crystal less valves, £4; duo Marconi, Ekco, CLT No. 3, 50-90m/c, a.c. mains with valves and microphone, £6/10; selector switches, 12w 6/4, 9w 1b 1/6; S.T.C. metal recs., 230v 1 1/4, HW, new, 21/- ea., 4 for £3/10, 4 in bridge give 175v 5a from 230v direct; 10 assorted medium and short wave coils, mainly with dust cores and trimmers, 6/-; 100 assorted res. and caps mainly on tag boards, 8/6; 100 assorted tubulars, mainly 1,000Ω, 10/-; hand generators for high or low vts., 12/6 ea.; No. 19 power units tested OK, 17/6; rotaries only 12v 500w 50ma, 175v 110ma, 12/6; liquid compasses for ariel setting, electrically illuminated with prismatic sighting; 55, Cosmor DB scope, £20; H.R.O. Senior, £12/10; power units type 392, £3; LR phones, 3/6; balanced arm, 5/-; MC, 8/6; MC with m/c, 10/6; R1124 receivers with 6 new 18v universal valves, 12/6, plus 2/6 carr.; Goodmans 4in speakers with grill, 10/6; Rola 6in, 12/6; if you are interested in optical equipment, our new booklet "How to Use ex-Gov. Lens and Prisms," price 2/6 ea., will interest you.

H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex. [4868]

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

HALLICRAFTER SX24, perfect condition: £28.—Blackwood, Maplecroft, Bath Rd., Bradford-on-Avon. [4790]
R.1155 just overhauled and realigned by R.E.T.S., Ltd., power pack and original case; £16.—near—4, Limes Ave., N.W.7. Mil. 3822.
VORTEXION Super 50-watt amplifier, for sale, 1947 model, without case, very little used, silent school holidays.—Offers, enquiries, Alden, Bradford College, nr. Reading. [4832]

NEW LOUSPEAKERS

STILL the best for the barker, the Tridem 12D corner cabinet, supplied with or without speaker unit.
FELICITY GRAMOPHONE CO., 87a, Upper Richmond Rd., S.W.15. [0040]

MINIATURE 3 1/2 in low impedance extension speakers, walnut veneered cabinet, volume control, flex lead; absolute bargain, 19/6, plus post.—Whitex Co., Farnham. [4812]

HIGH fidelity reproducer cabinets to Goodman and Barker spec. from £9, new 12 in speakers, 45/-; comp. lists from Cabinetware, Summit Works, Heyes St., Blackburn. [4812]

THE finest speaker on the market at the price; the "Phase-in" twin reproducer; separate treble and bass Wharfedale units (W10/CSB and W12/CS), with 1,000 c.p.s. crossover; heavy (inch wood throughout) hand French polished oak or 74830 veneered, special high frequency diffusion; price 29/6 complete; other models from 13/6; send s.a.e. to

"PHASE-IN" SPEAKERS, 99, Ashbank, Bucknall, Stoke-on-Trent. [4815]

SPECIALIST Reproducers for the high fidelity Wharfedale speakers: Standard 8in, 28/6; Bronze 8in, 35/-; super 8in, 65/-; super 8in C.S. (cloth surround), 75/-; golden 10in, 75/-; golden C.S. 10in, 85/-; W.12 12in, 135/-; W.12 C.S. 12in, 145/-; state etc impedance (3 or 15 ohms) c.w.o. or c.o.d.; lists 2/4.—Northern Radio Services, 16, King's College Rd., Swiss Cottage, London, N.W.3. Primrose 8314. [0006]

LOUDSPEAKERS—SURPLUS AND SECONDHAND

VOIGT H.C. horn, bass chamber, less unit, passed make-over.—Box 402, [4877]

BARKER 148A loudspeaker, mint condition, £11; Voigt twin cone unit, new surround, £14; Magnavox duode, new surround, 2,500a field, £5.—White, 90, Fairbank Rd., Bradford 42812. [4830]

LOUDSPEAKERS in stock for immediate delivery; brand new by famous makers at knock-out prices; FM 5in, 10/-; 6 1/2 in with trans, 15/-; 8in, 16/6; 10in, 22/-; mains energised 1250 ohm Field 8in, 15/-; 10in with trans, 22/- (add 9d post).—Roding Labs., 70, Lord Ave, 4753 Ilford. [4733]

NEW DYNAMOS, MOTORS, ETC.

BATTERY chargers, 4 models 2-6-12V, 1-2-4 amp D.C.; any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co. Ltd., Hoddesdon, Herts. [4212]

ALL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators, and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.

REVOLVING armature alternators, with separate exciter generators, 4-pole ball bearing, 1,500 rpm, output 230v, 50 cycles, 2.25kva, excitation at 24-30v, price £29; 2-pole, ball bearing, 3,000rpm with 4kva output, £29.

ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 300v d.c., permanent magnet field, 20/-; ditto, input 28v d.c. and 1,200v, 0.5ma d.c. output, energised field, 35/-; ditto, input 12v d.c., output 500v, 0.5ma d.c., energised fields, 35/-.

PETROL electric generator plants comprising a J.A.P. No. 2a single-cyl engine coupled by vee rope drive to an alternator giving an output of 230v, 50 cye, 400 w., with screened ignition and filtering on generator, eminently suitable for operating television and radio on farms, etc., price £40; such plants can be supplied with various outputs a.c. or d.c., for other applications.

CHAS F. WARD, Lordcroft Works, Haverhill, Suffolk, Tel. 253. [10039]

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

9 7/6, charging switchboards, 12v-32v, 500 out, fuses, resistances, etc., 4 take-offs, superb unit, in case, or send £5 carriage paid; 3 1/2- dynamo, 24 volts, 1,000 watts, 9 1/2 x 7 1/2 in spindle, or send 80/- carriage paid; 7 1/2- 230v/150, 1/2hp electric motors, incorporating 1.260 cycle converter, or send 80/- carriage paid; 5 1/2- mains transformer switchboards, 230v a.c. to 12v, 5 separate take-offs, complete distribution panel, all switches, fuses, amps, etc., brand new, or send 60/- carriage paid; 5 1/2- electric motors, 12v and 24 v, 1/2hp, 4 1/2 x 4 1/2 in spindle for drive, beautiful job, or send 60/- carriage paid; 4 1/2- dynamo motor units, containing 12v, 24v, 130v and 300v d.c. dynamo, or suitable as 6v, 12v or 24v motor, approx. 1/2hp, 1 1/2 x 5 1/2 in, with spindle to take small grindstone, mop, etc., also contain adjustable 24v cut-out automatic voltage control, smoothing condenser, resistances, and many other extremely useful fittings, beautiful job, or send 50/- carriage paid; 3 1/2- radio wavemeters, adjustment dial, 350-370 Mc/s, beautiful instrument in case, or send 40/- carriage paid; host other valuable equipment; lists free.—Benmotors, Summerley St., Earsfield, S.W.18. Wm. 3835. (100 yds S. Rly. Electric Line; 10 minutes Waterloo).



Are You Crossing Over?

Until we introduced the 215 Speaker to American high-fidelity enthusiasts it was thought that multiple-unit speakers were essential for the best results. The argument seemed so obvious, but the practical outcome was that the quest for more cycles involved the unfortunate customer in an outlay of many more dollars. The price of "high-fidelity" speakers advanced from around \$30 to over \$500. And still there were some who thought that mere width of frequency response did not produce results which were acceptable to music-lovers. In Britain this trend is reflected in current design. Yet we, who introduced the first twin-speaker system to the world as a commercial proposition, do not make them now, but pin our faith to a highly specialised single unit, and the total cost to you is only £9. Our speaker sells for \$40 in the U.S.A., and the people who have bought it say it gives better results than others costing hundreds of dollars. They say that—not us. So in this country you may find on investigation that mere spending of more money is not enough to secure the best results.

Write for free literature to-day.

H. A. HARTLEY CO. LTD
152, HAMMERSMITH ROAD
LONDON, W.6. RIVerside 7387


Thinking of building a Television Set?



4 gns. Carriage Paid

10 VALVE 1 1/2 METRE SUPER-HET

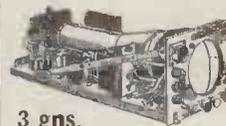
Ideal for television Receivers, I.F. 12 Megs, Band width 4 megs. Co-axial input and output-sockets. 10 Mazda Main valves, 6-3 volt filaments.



3 gns. plus 5/- Carriage

A.S.V. INDICATOR UNITS Type 6 H.

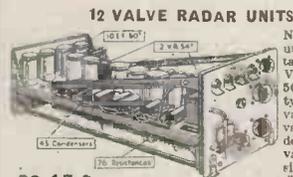Containing seven valves and one 6 in. Cathode Ray Tube type VOR 97. Brand new and unused. In sealed wooden transit case



£2.15.0 each Carr. paid.

Offered at a fraction of price of valves alone.

Dept. WIRELESS INSTRUMENTS (Leeds) Ltd
54-56 The Headrow, Leeds. Tel. 22262.

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

WARD rotary converter, special smoothing filter equipment, soundproof box absolutely as new, 110volt d.c. input, 220 a.c. output 300watts: £23.

NICHOLLS, Dolven, Llandewy, Llandrindod Wells, Radnorshire. [4819]

PETROL and T.V.O. charging and lighting sets, 12volt; no a.c. plants at moment; new Douglas 349cc ohv engines, air-cooled, complete on stand, £20, new carr.; J.A.P. engine, No. 2a, 1 1/2hp, air-cooled, new, £14, delivered; 14-32v 230watts with or without control box; 6v 35amp-hour batteries, unused, £3/10, delivered; inquirers kindly state exactly what you are interested in; see advt. under Components for S.T.C. rectifiers.

PEARCE, 66, Gt. Percy St., London, W.C.1. [0014]

NEW TEST EQUIPMENT

BATTERY chargers, 2-6-12volts, 1-amp. enclosed steel case with ammeter, a.c. mains operated; 42/6.—Thames Valley Products (W) 28, Camden Ave., Feltham. [4264]

DO you see the new Ampleon test-meter at Radiolympia? A.C., D.C. and ohms, 1,300 o.p.v., 10 ranges, handy pocket size, for 67/6 (post 1/-), 5,000v test prod., 9/6 extra; this is a high-class, accurate moving-coil instrument.—Westmead Radio, 117, Westmead Rd., Sutton, Surrey. [4615]

17 range a.c./d.c. multimeter, small size, movement 200ua m.c. ranges, a.c./d.c. volts 10, 50, 100, 500, 1,000v at 4,500ohm per volt, d.c. current 1.0, 10, 100, 500ua resistance 0-5k1, 0-500k1, 0-5meg, all self-contained, fully guaranteed; £5/10, complete with leads and test leads; send for literature at least. C. & W. ELECTRONICS, 13, Oswald Rd., Oswestry, Salop. [4878]

OSCILLOSCOPE and Wobbulator complete, £20; T.B. c/s 10 to 350,000 c/s X and Y plate amplifiers, easy to handle, has outstanding performance, fully guaranteed, immediate delivery with set of leads and booklet, "Oscilloscope Technique"; further details from the manufacturers.—Erskine Laboratories, Ltd., Scalby, Scarborough. [3456]

TEST EQUIPMENT—SURPLUS AND SECONDHAND

BPL RS 600 Signal generator, very good condition; Taylor 75A multi-range meter, one rd. also; also unused Avo valve Tester available.—Apply Box 1464. [4843]

VARIACS, type 100L, input 230v, 1-ph, 50cps, output 0 to 230v, 8amps, £12 each; type 100L-5G, input 400v, 3-ph, 50cps, output 0 to 400v, 3-ph, 6kva, £36 each; all as new and perfect.

P. B. CRAWSHAY, 166, Pixmore Ave, Letchworth, Herts. [4888]

A VOMINor in case, £3/17/6; Avo valve tester, £5/10; Avo sig. gen., a.c., £10; Acos auto sw. Xtra, pick-up, 30/-; Roth sen. Xtra, p.u., £2.—J. Law, A.M.I.R.E., 21, Linton Ave., Penn. Wolverhampton. [4874]

MARCONI Sig. Gens., TF 144G, TF 390, TF 517s, output meters TF 340, Taylor ditto, 140A, Cossor kankin oscillator £43, BC 221, a/s as new; enquiries invited; also large quantities components, etc.; send stamp for lists.—R. E. 1. Service, 254, Grove Green Rd., London, E.11, Lev. 4986. [0056]

TRANSMITTING EQUIPMENT

TR9 transmitter-receivers; these were formerly sold at £6 each, the remaining 30 are cleared at 25/- carriage paid.

THE STAMFORD RADIO Co., 199, Stamford St., Ashton-under-Lyme, Lancs. [4795]

HALLICRAFTER transmitters, Type HT4E (BC610), complete to makers' latest specification, covering all frequencies from 1mc to 30mc, complete with speech amplifier, connecting cables, etc.; limited quantities only now available.

PANORAMIC adaptor, Type MCA44, British-made, suitable fitment to any good-class communication receiver, in addition to all Halli-crafter models, immediate delivery.

BRITISH-MADE under Halli-crafter licence, SX42 receiver, now available for export only.

MCELROY-ADAMS MFG. GROUP, LTD., 46, Greyhound Rd., London, W.6. Tel. Fulham 1802. Cables, Halli-crafter, London. [4114]

NEW GRAMOPHONE AND SOUND EQUIPMENT

VOIGT twin unit, £12; rectifier, 50/-; 2ft horn, 30/-; 4ft horn, 80/-.—Vernon, Cinema, Tarporley, Cheshire. [4818]

MAGNETIC 1/4 in TAPE recording heads, standard model record-playback with split winding for bias and 5 or 15Q audio, 30/- each, erasing heads 30/- each. HI-FIDELITY 1/4 in tape heads, circular Mu-metal laminations stacked 1/4 in, fully screened, single unit (record-play), £4/10; twin unit with tape lifting (record-play and erase) £9; full assembly (record, play, erase) with tape lifting, £14; impedance 5 or 15Q to order, bias winding, for 75T osc. sec. coil; 1/4 in Emtape, 300ft, £4/10; osc. coils, 15/-; circuits supplied free. Trade enquiries invited.—Morecambe Sound Service, 4-6, Green St., Morecambe, Lanc. [0078]

INFINITE baffle corner deflectors, scientifically designed acoustic chambers for 8 to 15in speakers; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0064]

WARITE tape recording decks, £25; M.S.S. recording machines, blank discs, etc., processing your own masters, 32/6 per side; microphones, magnetic tape, amplifiers, etc. full trade terms; immediate delivery.—Sound Discs (Supplies), Ltd., 178, Bispham Rd., Southport, Lancs. [4801]

NEW GRAMOPHONE AND SOUND EQUIPMENT

WEBSTER wire recorder, model 80, modified by maker to 11x250.5 c/m, modulation level indicator, crystal mike, new Sept. and hardly used; offers or £85.—Box 1463. (4842)

TAPE recording/wire recording, for the finest components, service and satisfaction, record heads, coils, tape or motors, at prices that satisfy.—E. & M. Developments, 9, Troy Grove, Wyche Ave., Kings Heath, B'ham, 14. (4884)

NEW super Collaro RC49 a.c. mixed auto-changer, in black and chrome, with hi-fi crystal pick-up, repeat, reject mech., price £14/6/8, carr. paid; the Collaro AC47 centre-drive gram. motor, non-magnetic turntable, ideal for moving-coil pick-ups, etc., variable speed, £5/18/4, carr. paid; Collaro AC504 gramophone unit, motor, pick-up (latest magnetic type), and autostop, fixed speed (78 r.p.m.), 10in turntable, £5/3/2, carr. paid; the Marconi AC100 auto-changer, plays 10 records, 10 or 12in (not mixed), fitted high fidelity lightweight pick-up, price complete with pick-up transformer, £10/10/8, carr. paid; N.R.S. de luxe microgram, comprising Collaro AC504 unit, 4-watt amplifier and twin speakers, in rexine covered portable table cabinet, 17in x 15in x 5in, £15/10, carr. paid; cabinet only, £2; terms, c.w.o. or c.a.; W.W.W. list 214d.—Northern Radio Services, 16, King's College Rd., Swiss Cottage, London, N.W.3. Primrose 8314. (10004)

GRAMOPHONE AND SOUND EQUIPMENT—SURPLUS AND SECONDHAND

WIRE recorder, new condition, from U.S.A., with amplifier and speaker, any examination invited, £37/10, c.a. or c.w.o. T.G. & Co., Wyche Ave., Kings Heath, Birmingham. (4885)

MAGNETIC sound recording wire, stainless steel, temporary wooden spools, approx. 1½ hours' running time at 2ft per sec.; 14/- per spool. A. Smart, 40, Grande Rd., Halesowen.

NEW COMPONENTS

WIRELESS World televisors

FOR approved components all enquiries should be addressed to the makers, "Handyparts," 226-228, Merton Rd., Wimbledon, S.W.19. Lib. 7461. S.a.e. for replies. (10033)

TRANSFORMERS to exact specification.

LINE O/P trans. for W.W. televisor, 45/-; O/P trans., for Williamson amplifier, 75/-; mains trans., for Williamson pre-amp and radio feeder unit, 60ma O/P, 28/6; television filament trans., 6.3v 8amp and 2, 4, 6.3v 2amp, 28/6; tag panels fitted as specified, trans., for amplifiers, televisors, valve testers, test gear, chargers, etc., to any published specification, or to your own design.

E.P.D. TRANSFORMER PRODUCTS, 31, Queenstown Rd., Battersea, S.W.8. Tel. Mac. 4180. (14579)

TELEVISION. HANNEY OF BATH offers:—

POLYSTYRENE and Paxolin formers for the "Wireless World" superhet receiver. All other components are available ex-stock; condensers, resistors, Reliance potentiometers, aerials, etc. **COMPLETE** sets, round exactly to specification, with copper and brass slugs, London or B'ham, 45/-.

S.T. & C. H.2400 rectifiers, 28/-; Eddystone 583 split stator, 7/6; Reliance pots, type TW, 5/8; Reliance pas, type SG, 6/10. H. 1/2. G. 1/2. W.W.W.'s receiver we have it to the last nut and bolt.

MULLARD Mw31/14c c.r.t.s. limited number, £15/2/5.

MULLARD Mw22/14c c.r.t.s. now available for immediate delivery, £11/10, carr. pd.

COMPLETE set for parts for the Williamson amplifier, 11gms (less valves), or wired and tested £25/10 (with valves), guaranteed 2 years.

ALL high stability resistors and matched condensers in stock for the new Williamson pre-amp and tone system.

ALL ERIE and MORGANITE resistors in stock from 10 ohms to 10 meg. in 1/5, 1 1/2 and 2 watt.

WE CARRY comprehensive stocks by all makers of repute; Eddystone, Raymart, Denco, Wearite, T.C.C., B.I. Hunts, Dubliner, Morganite, Reliance, Elstone, Gardner, Goodmans, Avo, Taylor, Partridge, etc., etc.—new goods only. SEND NOW for (a) E.V. list, (b) Williamson list, (c) S.W. list, 214d stamp please.

L. F. HANNEY, 77, Lower Bristol Rd., Bath. The simplest 'het' pack, type M.L. M.L. valves. £2/6; thousands in use.

DORGLAS Co. Ltd., B'klow Nr. Rugby

U20 Transformers, 500 watt, weight 22lb. £230/10v, new but sold; £2/2 incl. carr.—Champton Products, 43, Uplands Way, N.21 Lab. 4457. (14997)

WILLESDEN high quality transformers available ex-stock for the D.T. Williamson Amplifier, Electronic Eng. Televisor, and all well-known circuits.

WILLESDEN TRANSFORMER CO. Ltd., 781, Harrow Rd., N.W.10. Tel. No. Ladbrooke 2846.

THE brain of any good radio is an Osmor Q coilpack, used with our matched components you can build a radio really worth boasting about write to-day for free circuits and our latest lists. Including the Bargain Bulletin.

OSMOR RADIO PRODUCTS, Ltd., Bridge View Works, Borough Hill, Croydon. (Cro. 1220.)

TELEBOOSTERS for long range television reception, super high gain single-stage pre-amplifier, 2-stage, 1 VR91 valve slug tuned London or Birmingham, co-axial plugs and sockets flying leads for high and low tension fully screened, low noise, price £2/12/6; power units for above, £3/10; s.a.e. for trade test report.

BOSCOMBE RADIO & ELECTRIC, 595, Christchurch Rd., Boscombe, Bournemouth, Tel. 36522.

It Pays to Purchase ELECTRADIX BARGAINS

LABORATORY GEAR. Sullivan Marine Galvo suspended Moving Coil, on solid base with adjusting feet, in lacquered brass case, £10. Sullivan Testing Keys, Reversing, £4. Weston Moving Coil Relay 380 ohms resistance 50 micro amps, £3/10/-. Sullivan Moving coil Relay, £3. G.P.O. Polarised Relays in brass case with glass top, plat. contacts, 25/-; G.P.O. Sounders, 25/-; Pickin Lab. Resistances 50 ohms 2 amps. mounted in polished wood base with glass front and heavy ebonite control knob, 40/-; few with damaged glass. 25/-; Avo-All Wave Oscillator 95 Kc to 40 megacycles in 6 ranges, brand new, £20 each. Bridge Megger 500 volts 40 meg. with decade Resistance box in wood cases, £25. 250 volts 20 meg., £20.

RESISTANCES. Variable wire wound lab. type laminated brush gear 1.2 ohms 15 amp., 7/6; 6 ohm, 6 amp., 15/-; 300 ohm, 1/2 amp., 15/-; 290 ohm .45 amp., 15/-; lenthal Geared Resistances, 60 ohm, 2.8 amp., 15/-.

TRANSFORMERS. Foster 50 ohm, 2 amp. double wound, 15/-; B.T.H. 200/230/250 volts to 75 volts 6 amp. and 2 volts 20 amp., 45/-; Auto Booster Transformers 900 watt size 200/250 volts in 10-volt steps, useful in power cuts, £5. Auto Transformers 230/110 volts, 85 watt, 25/-; 150 watt, 35/-; 1 kW, £7/10/-. Ex-W.D. Transformers 220 volts, 50 cycles, input 53 volts, 15 amp., 0.30, 0.60 volts 1 amp. and 6 volts 5 amp., £5.

IRONCLAD SWITCHGEAR. We have a large stock of Ironclad Switches and Switchfuses by leading makers, write for special list "W."

DYNAMOS. For battery charging on boats, etc., for use ashore or afloat, 24 volt 30 amp, 4-pole 1,000/1,200 revs. shunt, fan cooled, £20 each. 24 volt 18 amps., shunt fan cooled, £17. 24 volt 18 amp., 1,200 revs. vent. enclosed, £12/10. 12 volt 25 amp. 800/1,000 revs. fan cooled, £15 with control box. Carriage extra on all Dynamos.

D.C. DYNAMOS. 12 volt 10 amp. C.A.V. 1,400 r.p.m., £2. 24 volt 100 amp. 4,000/6,000 revs., £5/10/-; 30 volt 5 amp. 1500 revs., 35/-; carriage on any Dynamo, 5/-.

A.C. MOTORS. Small sewing machine motors, 230 volts A.C., square construction, with pulley belt and bracket, £4/10/-; foot control, 55/- extra.

LIGHTING PLANTS. A.C. Onan Plants, 2½ kVA 110 volt 3.7 h.p. 2 cy. 4-stroke aircooled 1,800 r.p.m. Generator 110 volt 21.7 amp., S.P. new Government surplus, £60 each. 3kV 3-phase plant, 5 h.p. 1-cy. 2-stroke air cooled, Gen. 380 volt, £50.

D.C. LIGHTING PLANTS. Villiers 500 watt 2 h.p. engine direct coupled to 18 volt 30 amp. D.C. Gen. for battery charging, with Switchboard and fuel tank, £22/10/-; Pelapone 500-watt water cooled Plants, 1 h.p. engine direct coupled to 50/70 volt 10 amp. Dynamo, £35.

FREQUENCY METERS. 230 volt 6in, Ironclad, 40/60 cycles; Switchboard type, £4/10/-.

TELEPHONES. Ex-G.P.O. wall-type set of Constructors parts for office or garage use, comprising Bracket Mike, Mag, Bell, Transformer and condenser, Switch-Hook and Receiver, connection strip in polished box 8in. x 6in. x 3½in. Hand Mag, Generator and wiring diagram, 35/-; carriage 5/- extra.

A.C. MOTORS. 1/2 h.p. 230 volt 1,425 r.p.m., new, £5/10/-; 1/2 h.p. capacitor start 230 volt 50 cy. s.p. 1,425 r.p.m., £8/10/-.

D.C. MOTORS. 1/2 h.p., 110 volt A.E.G., 30/-.

PUMPS. Rotary Suds Pumps 8ft. lift, 35ft. head, 60 g.p.h., with pulley, £4/10/-.

MOTOR PUMPS. Suds type 1/2 h.p. 200 or 400 volt 3-phase 50 cy., 1,425 r.p.m., 10ft. head, 600 g.p.h., £8/10/-.

MAGNETS. Swift Levick S.L.36 instrument type, circular horseshoe 1½in. dia. jin. thick, jin. polar gap drilled poles, weight 2 ozs., lift 3 lb., 2/6 each, or 12/6 for six. The Alni disc magnet, the wonder midget magnet, jin. dia., jin. thick, 3/16in. hole in pot with keeper, 3/6. D.C. Electro Magnets, weight 10 oz., lift on 2 volt 1½ lb., 4 volt 3 lb., 6 volt 4 lb., 5/-. Permanent flat bar magnets, 2½in. x lin. x jin., drilled two holes each end, 2/- pair. Large stock of Horseshoe Magnets. Send for special leaflet, "W.W."

COMPASSES. Binnacle Boat Compasses. Liquid Model, in housing with glass windows, 40/-.

PARCELS. 10 lb. useful oddments for the junk box. All clean, dismantled from Government and other surplus apparatus, 7/6 post free. (For home buyers only).

Please include postage for mail orders.

ELECTRADIX RADIOS

214 Queenstown Road, London, S.W.8

Telephone: MACaulay 2159

NEW COMPONENTS

TELRAID ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19, television components for "View Master," Belling & Lee Bulgin, Colvern, Morganite, Piessey T.C.C., Wearite, Westinghouse, Whiteley; complete parts as specified in stock; also E.E. chassis, mains transformers, etc.—Write, call or 'phone your order Livingston 4879. (10020)

SYNCHRONOUS clock units, self-starting, 200-cyc. ac 50 cycle fitted Sanaemo motors, consumption 2½ watts, size 2½in. dia. 2in. deep geared 1 rev 60 min. friction reset; ideal movements for making electric clocks, time switches etc., nickel plated finish, complete with 12 to dial train and 5in hands, price 22/6, post paid; Sanaemo as above, final speed, 22 rev. per min., less dial train, ideal for dark-room process time, etc., price 20/- each, post paid.

SANGAMO motors with gear train final speed 1 rev 12 mins approx. 16/- each; ditto, final speed 1 rev 1½ mins approx. 13/6 each, post paid.

INDICATOR UNITS TYPE 184A—Fitted 3in and 6in cathode ray tubes type ACR.10 and V.C.R. 517B, and 17 valves, viz. 6 V.R.92: 5 V.R.91: 3 V.R.54: 3 V.R.65; metal rectifiers, chokes, transformers, potentiometers, resistances, condensers, etc.; £10/10 each, carriage 10/-.

BATTERY WAVEMETER TYPE 1095.—Wave-ranges 1540-1220 k/cs and 3417 to 2000 k/cs; fitted microammeter 0 to 500 in nice carrying case; complete with valve; price 40/- each, carriage 10/-.

MODULATOR TYPE 67.—Fitted standard mains 230 V.A.C. 50 cycle power pack, giving 345 V.D.C. 125mA.; 6.3 volts 5 mps; 6.3 volts, 25 amps; 12 valves, viz. 5 V.R.65; 2 V.R.54: 2 V.R.116; 1 5Z4G, and various useful components; £4 each, carriage 7/6 each.

CLOCK work; timers, new surplus, suitable for process work, dark-room timing etc., variable timing 1 to 60 seconds relay to operate off 6v battery capable of handling 100 watts supplied with each movement; price with relay, 36/- each, post paid; each movement is fully tested before dispatch.

CONDENSERS Electrolytic 1,000mf. 25v dc W.K.G.; 4/6 each, post paid; 25/- per doz.

RECTIFIER units, ac to dc, input 200-250v ac, 50 cycle 1-phase, output 160-200v dc, 15amp; price 4/- each, post paid.

SIEMENS high-speed relays, 2,000 ohms, ideal for model control; 6/6 each, 72/- per doz.

CRATER rotary switches 250v 10amps ac single phase 3-way series; parallel ideal for photo floods, etc.; price 4/- each or 40/- per doz, post paid.

PERFORMANCE meters type No. 2 fitted standard mains 230v ac 50 cycle power pack 2 VR91, 1 VR137, 1 5Z4G, 1 CV51 1 VR92 and other useful components; £2/5 each, carriage 3/6.

AC mains 230v 50 cycles power packs with variable output, 300v dc at 10ma, to 200v dc 25ma, housed in nicely finished metal cabinet size 11in x 6½in x 6in complete with 5Z4G rectifier, also gives 15v ac 15amp; £2/10 each, post paid.

A LARGE quantity of single items which we do not list, which are available to callers: also assortment of various ex-W.D. radar and radio equipment, relays, power packs, oscillograph units, gears photographic apparatus; s.a.e. for lists.

H. FRANKS, 58, New Oxford St., London, W.C.1 One minute from Tottenham Court Rd. Station. Tel. Museum 9594. (10057)

£8/6 only for the famous Model 30 tuning coil, consisting of 3-waveband Model 30 superhet coil pack, pair 1.2. Transformers, 2-gang condenser and attractive dial (8in x 6in); each component individually selected pre-aligned, sealed and the whole matched together as a unit; the superhet you build with this kit needs no further adjustments. For details of this and other high quality products (coils, IFTs, mains transformers, etc.), together with many circuits and constructional tips, contained in the "Home Constructor Handbook," price 1/-, Mail order office.

SUPACOILS, 98, Greenway Ave., London, E.17.

NEW S.T.C. selenium rectifiers, largest l.t. range from stock in Great Britain; all makers' latest products; not surplus; H4/100 E.H.T. for VR97, 15/6; H4/200 for W.W. Televisor 28/-; p.f. H.W. rects., 16v 5/6 6/8 1/10 8/-, 2a 9/6, 3a 16/6, all p. 6d, 4a 18/9-, 6a 22/6, p. 10d, 30v 1a 12/-, 2a 14/-, 4a 24/9-, 6a 36/6, 48v 2a 21/-, 4a 35/-, 6a 51/-, 100v 2a 34/6, 4a 65/-, all p. 1/-. H.D. H.W. 7½in sq. cooling fins, 6a 21/6, 10a 24/6, 30a 35/-, 8a 35/6, 48v 2.5a 26/-, 5a 48/-, 8a 54/-, all p. 1/-. Full-wave bridge conn. rects., 17v 1.5a 12/1, 2a 15/6, 2.5a 20/6, 3a 21/6, 4a 25/-, 5a 27/-, all p.f. 33v 1/4a 18/6, 1a 21/3, 1.5a 28/6, 2a 29/6, 3a 35/-, 4a 42/-, 5a 43/6, all p. 10d, 54v 1.5a 39/-, 5a 47/6, 4a 65/-, 10v 1.5a 72/-, all p. 1/-. H.D. type with 7½in cooling fins, 17v 6a 27/-, 10a 43/8, 12a 72/-, 20a 80/-, 33v 6a 64/-, 10a 71/-, 12a 124/-, 20a 140/-, 54v 6a 90/-, 10a 100/-, 72v 10a 130/-, 100v 10a 190/-, all p. 1/4, industrial type tunnel cooled, 17v 12a 76/-, 20a 87/-, 30a 124/-, 50a 188/-, 33v 6a 69/-, 30v 10a 80/-, 33v 12a 124/-, 20a 144/-, 54v 6a 92/-, 10a 108/-, 72v 6a 114/-, 10a 136/-, 100v 6a 160/-, 10a 192/-, all p. 1/6; S.T.C. replacements for valve type chargers, fitted in 5 mins, no alterations to wiring; complete working chargers 2½v 4a with H.D. trans., sliding reed fuse and ammeter and mains lead, in blk. crackle finish, louvered steel case, wt., 25lb £5/10, del. free; also 2a, 4a 5a, 6a kits, terms, c.w.o. or proforma invoice; c.o.d. over £1 on post goods only; wholesale and retail.

T. W. PERCE, 66, Gt. Percy St., London, W.C.1, off Pentonville Rd., between King's Cross and Angel. Est. 17 years. (10013)

"High Fidelity"
EQUIPMENT DEMONSTRATED
DAILY

AMPLIFIERS
LEAK "Point one"
SOUND SALES "Tonemaster"
WILLIAMSON
VORTEXION
ACOUSTICAL


SPEAKERS
TANNOY
BARKER
WHARFEDALE
GOODMANS
SOUND SALES

PICK-UPS
Brierley, Decca, Wilkins and
Wright, ACOS, Connoisseur,
RNW and Marconi.

FEEDER UNITS by leading
makers.

ARMSTRONG ALL WAVE
CHASSIS from £18 17s. 1d.
Gram motors and Autochangers.

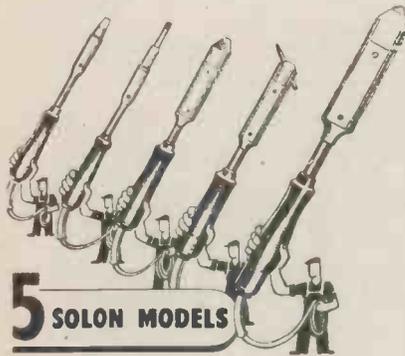HOLLEY'S RADIO STORES,
285, Camberwell Road, S.E.5
Phone: RODney 4988



5 SOLON MODELS

SOLON electric soldering irons have proved their capacity for continuous service under the most exacting conditions. 5 models; 240 watt oval tapered bit; 125 watt oval tapered and round pencil bits and 65 watt oval tapered and round pencil bits. Each model complete with 6 feet of Henley 3-core flexible. Now available from stock. Write for folder Y.10.

**HENLEY
SOLON**
ELECTRIC
SOLDERING IRONS

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
61-63 Hatton Garden, London, E.C.1

NEW COMPONENTS

ALLWAVE a.c. kits, 5 valves, including rectifier, panel and chassis ready drilled, supplied with medium wave coil; carriage paid £5/10; extra coils 4/6 each.
RADIO-AID, Ltd., Retail Section, 29 Market St., Watford, Herts. 10036

MIDGET volume control of the future, diameter the size of a halfpenny, 3in spindle from 50,000 ohms to 2 meg, with switch 6/-; d.p. switch, 7/6; less switch, 4/-; post free; trade enquiries invited.—D. Diamond, 15, Saxon Av., Manchester, 8. 14787

TELEVISION.—Bel P.M. Focus Rings approved "Electronic Engineering," self-supporting, micrometer adjustment, 15ohm magnet, chrome finish, all tubes 9 12in. with instructions, 35/-; Coils: EE Birmingham 18/6; ditto less chokes, 16/6; EE London, 15/-; Wireless World s'het L. or B., 20 coils, 52/6; set of 10 coils for the newest televisor, 16/-; booster choke, 4/6; video choke, 1/6; chassis kits, with v/h and trimmets, 57/6, as foreorder but with our own mod. for Midland freq. whole set, 29/6; W.W. s'het chassis kits, copper and aluminium, semi-drilled, including 2 r.f., 2 timebase, 1 v.f. chassis, 11 screening boxes, 26; alternatively, 2 r.f. chassis only with 17 associated coils, 23, plus 2/6 per screening box; W.W. deflector coils, exactly to specn., 35/-; R.F., E.H.T. osc. coils, 6kv. £1, c.c.t. supplied; Williamson r.f. feeder unit, 7/-; set of 2 coils, or set of 4x £1; Attenuators as described by "Wireless Trader," per set, 24/-; sets of 10 preference resistors, 12/6; BEL SOUND PRODUCTS Co., Marlborough Yard, Archway, N.19, North. 1025. 14896

COMPONENTS—SURPLUS AND SECONDHAND

BRAND-NEW guaranteed goods.

MAINS transformers, fully interleaved and impregnated; primaries 200-230-250v 50 c.p.s., screened, drop in chokes, types 250, 250v 60ma, 6.3v 3a, 5v 2a 13/11, 350-0-350v 80ma, 6.3v 3a, 5v 2a 16/9; midget type upright mounting, 250-0-250v 60ma, 6.3v 1.5a, 5v 2a, size 3-2 1/2-3in., 17/9; fully shrouded upright mounting types, 350-0-350v 100ma, 6.3v-4v C.T., 3a, 5v-4v 2a 21/-, 350-0-350v 120ma, 6.3v 4a, 5v 2a 25/-, 350-0-350v 150ma, 6.3v 4a, 5v 3a 27/9, 250-0-250v, 6.3v 6a, 5v 3a for 1355 conversion 25/9, 425-0-425v 200ma, 6.3v-4v 4a C.T., 6.3v-4v 4a C.T., 5v-4v 3a 41/6; vibrator transformers, 6v input 300-0-300v 60ma output, 8/9; Rola 6 1/2in mains energised speakers, 2-3 ohms, field 750 ohms) 9/6; Ceramic double trimmers 45 plus 45mmfd; 4/9 doz; co-axial plugs and sockets, 6/9 doz; electrolytics, metal tubular, 8mf 275v, 12/-; doz; Can 32mf 350v, 1/9 ea; volume controls, standard length spindle, 0.5 meg, with switch, 1/3 ea, 34/-; doz; fully punched 5-valve superhet chassis, cadmium plated steel, 14-6-2 1/2in, 2/6 ea; full list of component bargains 2 1/2d; special list trade; c.w.o. or c.o.d. over £1; postage extra under £3.

E. POWELL, 3, Rockingham St., Leeds, 2. 10003
Callers, 15, Queen Square, Leeds, 2. 10003

SOUTHERN RADIO'S wireless bargains:

PERISCOPIES ex-U.S.A. type M8 complete brand new with telescope, 17/6; crystal detectors, 2/6; telephone line units complete in polished wooden case with relays, rectifiers, etc., 5/-; RECEIVERS R28/ARCS complete with 10 valves 100/150 mex. brand new and complete with circuit, 50/-; moving coil headsets, headphones and microphone attached, 7/6; transformers 1-1 ratio, 2/6; microphone transformers 50/1, 3/6; Lucas inspection lamps with lead and plug, 2/6; carbon microphone inserts, 2/-; T.R.1196 Receivers, complete with 6 valves, with circuit, 22/6.

DINGHY transmitters T1333, complete in transit cases, 55/-; brand new, 140/-; callers, please see display advertisement; full publication list, 2 1/2d.

SOUTHERN RADIO SUPPLY Ltd., 46, Lisle St., London, E.C. Gerrard 6653. 10016

FRAME aeriols, M.L. chassis mounting, 9 1/4in X5 1/4in, 7/6; manufacturers' surplus midget L.F. chokes, 2/6.

HILLFIELDS MAIL RADIO, 8, Burnham Rd., Whitley, Coventry. 10022

1/16hp motors, 230v, a.c., 50cps, squirrel cage, totally enclosed, ball bearings, precision made by G.E.C. brand new; 15/6; K. LOGAN, Westaley, Hitchin, Herts. 14886
3 w.b. glass dials, 8in X5in, 3/3; 3 w.b. gold metal dials, 5in X4in, 2/6; Weymouth dials, 2/-; w.b. dials, 1/6; v.c. w/sw 1/2meg, 1meg, 3/5; ball sw. 4v 3v, 4p sw. 2/3; tubular conds., 0.001 to 0.1mf, 5d; 25x25 conds., 9d; 5in p.m.l.s., 8/6; 8in p.m.l.s., 15/-; sil. mica conds., 100pf, 3/-; smoothing chokes, 60ma, 4/9; v/hs, all types, 4d.; resistors, all values, 1/4w 2d., 1/4w 4d., 1w 6d.; sleeving, 1d. yd; m.c. meters, 0-1ma., 7/6; h.t. and osc. coils, Polystyrene formers, 2/3; electronic conds., 24x24ms 200v, 5/-; 8+16, 16+16, 450v 5/6; clock time switch, 10/-; J. Law, A.M.I.R.E., 21, Linton Ave., Penn, Wolverhampton. 14880

LITTLEWOODS, North London's best selection of radio and television components; pay us a visit or post or phone your enquiries; no lists, LITTLEWOOD & GREENING, Ltd., 27, Balmain Lane, Finchley, N.3, Fin. 3060. 10055

CHASSIS, alum. 16g folded 4 sides punched, 5/6, valve superhet 12in x 9in x 2 1/2in, 10/6; resistors asstd., popular values, 1/4w-5w, 10/- per 100; 465kcs IFT's, 10/- pr. Pots, 10k 25k 1/4M, 2/- ea.; Selenium rects., 50 ma 230v, 2/3, 60 ma, 4/3; P coils, 3 ea., 1/4 C (col) 2/3 ea.; 3 way s'het 1/2 coil packs, 21/-; Intervalve trans., 1/6 ea.; thousands of other items; stamp for lists.—Rodding Labs., 70, Lord Avenue, Ilford.

GOVT. SURPLUS, UNUSED

CONDENSERS

of all types . . .

We can offer, FOR IMMEDIATE DELIVERY from very generous stocks, a wide range of ultra-high quality fixed paper Condensers, from .001 μ F to 8 μ F. Also STOCKS of small, genuine MICA Condensers from .00001 (10 pf) to .01 μ F (10,000 pf). Prices are exceedingly moderate.

Enquiries are invited for manufacturers' requirements, wholesale and export only for bulk quantities, and for scheduled deliveries over a period, as required.

Most condensers are now available for immediate delivery.

Please request our 4 page bulletin CONSEVEN 01114

CLAUDE LYONS LTD.

180 Tottenham Court Rd., London, W.1
an 76, Oldhall St., Liverpool 3, Lancs.

GEE RADIO LTD

FOR

QUALITY COMPONENTS & SATISFACTION

ROTARY CONVERTERS. 12v. D.C. Input to 230v. 50 cycles A.C. output, approx. 800 watts, in perfect condition, complete with A.C. output volt meter and adjustable regulator mounted in original case with input and output connections, £8/10/0, carriage 10/-.

24v. D.C. to 230v. 50 CYCLES A.C. ROTARY CONVERTERS. 100 watts output, mounted in original casing, with lid, in perfect condition, also input and output connections, £3/15/0, carriage 5/-.

813 CERAMIC VALVE HOLDERS, 10/6 each.

87G CERAMIC VALVE HOLDERS, complete with skirt and screening can, 1/6 complete.

MULTI-RATIO 8 WATTS SPEAKER TRANSFORMERS to match almost any output from 3-15 ohms, new and guaranteed. Probably the finest job obtainable. Only 25/-.

0-100 MICRO-AMP METERS (scale) as 0-1,500 yds., 2 1/2in. dial circular flush mounting in perfect order, 20/- each.

C.R.T. 3in. TYPE 3BP1, in perfect condition. A few only available. 21/- only.

6v. C.T. AT 20 AMPS. TRANSFORMER. Input 110-180-230v. Size 4 x 2 1/2 x 3 1/2in. 25/- each.

18v. D.C. 2 AMP. METAL RECTIFIERS, 7/6 each.

WE CAN NOW SUPPLY FROM STOCK ALL COMPONENTS AS REQUIRED FOR THE HOME BUILT VIEWMASTER TELEVISOR. AS FOLLOWS:—

THE PLESSEY KIT, complete, £5/12/6.

THE WESTINGHOUSE KIT, complete, £3/2/6.

THE MORGAN RESISTOR KIT, £1/6/9.

THE COLVER POTENTIOMETER KIT, 10/3, etc., Also C.R.T. MAZDA, MULLARD, etc., 8in £11/6/5; 12in. £15 2/5.

C.W.O. or C.O.D. Orders under £10/0/1 1/- extra.

GEE BROS. RADIO LTD.

15, Little Newport St.

LONDON, W.C.2

GER 6794

COMPONENTS—SURPLUS AND SECONDHAND

NEW condition, Partridge combined E.H.T. h.t. and l.t. oscilloscope transformer; half set. 31/6.—Box 1504. 14823
SUPREME RADIO, 746B, Romford Rd., Manor Park, London E.12. Tel. Hf. 1260. Est. 15 years. 1950 bargains.
PLY-BACK type line trans. with provision for EY51 valve, 22/6 ea.; line and frame scanning coils, 25/6 ea.; P.M. focus units from 21/- ea.; H.T. trans., 350-0-350V 6.3V 6 amp, 4V 3 amp, 4V 2 amp, 0.2V 8.3V 2 amp, 250 mA, with screen 70/- ea.; 5 hy 250 m/a choke, 15/9 ea.; 10hy 80 m/a choke, 8/3 ea.; all parts in stock for London or Birmingham E.E. television, ceramic E.P.50 valve holders, 6d ea., 5/6 doz.; retaining rings for same, 8d ea.; bakelite E.A.50 valve holders, 6d ea.; 1/2-watt resistors, 10d, 22d, 27d, 47d, 82d, 120d, 180d, 250d, 330d, 390d, 820d, 1k, 3.3k, 10k, 47k, 100k, and 10M, 1/9 doz, or assorted doz, 18/6 gross only; 1/2-watt resistors, 2.2k, 6.8k, 16k, 18k, 33k, 100k, 150k, 220k, 2.2k doz, or assorted doz, 21/- gross only; 1-watt resistors, 270d, 470d, 1k, 3.3k, 8.2k, 18k, 33k, 56k, 68k, 100k, 1M and 2M, 4/- doz, or assorted, 45/- gross only; 2-watt resistances, 2k, 18k, 100k, 5/6 doz only, or assorted; noise suppressor units, consisting of 2, 0.1mfd cond. and iron cored chokes, 6d ea., 3/- doz; 3 meg. vol. controls, 7 1/2d ea.; 1M carbon and 5K W.W. vol. controls, 1/- ea.; 4mfd 350V screw base metal can, small, 6d ea.; 4mfd 550V screw base cond., metal, 1/- ea.; 11/- doz; 12mfd 50V screw base cond., 6d ea.; 5/- doz only; 50mfd 50V, 50mfd 12V, 25mfd 25V and 10 mfd 25V, metal tag end type, 1/- ea.; 11/- doz, or assorted doz only; tubular wire end cond., 0.01 mfd 1 k/v, 0.02mfd 750V, 0.05 mfd 500V and 0.1mfd 350V, 6d ea., 5/6 doz only, or ass. doz only; 50mfd mica cond., 0.001mfd, 0.0005mfd, 0.0003 mfd, 6d ea.; 1/2-watt cond., 1/9 ea.; Metallized cond., 0.01mfd 350V, and 0.002mfd 500V, 3d ea.; 8/- doz, or ass. can type cond., 8mfd 450V, 2/6 ea.; 16+32mfd 350V, 3/6 ea.; 16+8mfd 500V, 3/6 ea.; 32mfd 500V Drylytic cardboard outer case, with ends cond., 5d ea.; 16mfd 350V Drylytic metal case, small type cond., 1/9 ea.; Metallized switches med. spindle, 1/6 ea., fully shrouded; mains trans., 350-0-350V 80m/a, 6.3V 3a, 5V 2amp, primary tapped for 200-250V, fully shrouded, 15/6 ea.; also 250-0-250V 80m/a 6.3V 3amp, 5V 2amp, primary tapped for 200-250V, fully shrouded, 12/6 ea.; fixed mica can ppt type, 40 ppt, 50 ppt, 60 ppt, 65 ppt, 180 ppt, 305 ppt, 307 ppt, 500 ppt, 530 ppt, 570 ppt, 590 ppt, 700 ppt, 1,800 ppt, and 4,500 ppt, all at 2/6 doz only, or ass. 0.01mfd 3 k/v and 0.005mfd mica can type cond., 3/- doz; 0.1mfd 2.5 k/v/w mica can type cond., 2/- doz; 2 other bargains in stock; terms, c.w.o.; no c.o.d.; send extra for postage orders under £5; 2 1/2d s.a.e. all enquiries and list [0021
VACUUM relays, thermal type 6V 35ma 5 1/2in. diam., 1/2 inch switch 230V 10amps, length 5 1/2in. diam., 1/2 in. fitted with standard 4-pin valve base; 6/6 ea.
VELODYNES, Mag slip and Selsyns, many types in stock, send for list, technical advisory service available.
HOPKON RADIO, 1, Hopton Parade, Streatham High Rd., London, S.W.16, Streatham, 6185.
CONSTANT voltage transformers, 1.6kva, by Foster, input 180-260V, 1ph., 50cps, output 230V, plus/minus 1%, 7amps, oil filled, new, unused; £18 each 1 o.r.
P. E. CRAWSHAY, 166, Pixmore Way, Letchworth, Herts. 14887
TELEVISION, all parts in stock for EE television, Haynes scan and focus coils; line trans. model on view.—H.G. Radio, 1350, Stratford Rd., Birmingham, 28 [1418
80% COO silver m.c. condensers, 350 p.p.f. plus or minus 20% miniature type, for sale in one lot or smaller quantities.—Best offers to Radio Centre, 33, Tottenham Court Rd., London, W.1. [14841
YOU'LL probably get it at Smith's, Edgeware Rd., W.1. Everything for the constructor, from a 1/10watt resistor to a radiogram cabinet, lowest prices, biggest variety.—Near Metropolitan Music Hall, Pad. 5891. [18005
REDUCTION drives, 9d; 0.01, 0.001, 0.0001, 350V, 3.6 doz; 70-400p/170-900p padders, 1/3; 100p/ceramics, 2/6 doz; 2-bank 50p trimmers, 5d.—List from T. Howell & Co., 29, McWilliam Rd., Brighton, 7. 14898
HIGAIN coil packs, wired, tested, complete padders, trimmers, covering long, medium and short bands, 19/11; matched non-cored I.F.s, 465kc, 9/11 pair; circuit or 5-valve superhet free with order; chassis, gangs, scales, condensers, etc.
CENTRAL RADIO PREMISES, The Square, West Malling, Kent. 14851
HIGH quality output transformers, Williamson type, £2/12/6; standard drilled and tapped racks for 19in panels, 5ft 6in angle iron, £1 each; 6ft 3in channel, new, £3/15; VT104 trans. valves, 1/6 each; 100p/ceramic; 8 Acoustic Equipment Co., Ltd., Tombland, Norwich. [0069
MANUFACTURERS.—Enamel, copper wires, all gauges, laminations, all types, huge stocks radio components, s/m, m/m, p/t and block condensers, coils, resistors and high stability resistors to 1%; all goods guaranteed.—L. E. Simmonds, Ltd., 8a, Byron Rd., Harrow, Middx. Telephones, Harrow 2524 and 0315.
CO-AXIAL double end plugs 10H/628, 3/- dozen; rheostats 15ohms 1.5amp, 12ohms 2amp, 15ohms 1.5amp, 15ohms 1amp, 15ohms 1amp, 7500 volts 1/6; insulating tape, 1in, 1/4in, 1/2; Westcoats W.L. 1/-; hot wire ammeters, 4 1/2in dial 0-2amp, 5/6; M.I.L. 5amp 2-pin socket (sulfate) and fused plug, 2/-; small auto-trans 230/110, 8/6.
PASSINGHAM, 95, North St., Kelghley. [0002



You're SURE to get it at STERN'S ESTABLISHED 25 YEARS
Denco T.R.F. Matched pair Medium and Long Waves, 6/6 pair. Weymouth T.R.F. Matched pair M. and L. Waves 9/6 pair. Superhet Matched pair S.M. and L. Waves, 8/9 or 11/6 pair. All types Wearite "P" Coils, 3/- each, in stock. Weymouth Midget 1 1/4 in. x 3/4 in. Iron Core, Aerial H.F. or O.C., 3/6 each.
Electrolytic Condensers, B.E.C. Midget Can Tubular, 8 mfd. 450 v. (1 1/4 in. x 1 in. dia.), 2/6; 8-8mfd. 450 v. (1 1/4 in. x 1 in. dia.), 4/-; 16-8 mfd. 450 v. (1 1/4 in. x 1 in. dia.), 4/6; 32 mfd. 350 v. 2/6 (450 v., 5/-); 16-16 mfd. 450 v. (1 1/4 in. x 1 in. dia.), 5/-; Dubilier "Dritio" Card Tubular, 4 mfd. 500 v., 3/6; 8 mfd. 500 v., 4/-; 16 mfd. 500 v., 4/6; R.I. Can, standard size, 8 mfd. 500 v., 3/6; 8-8 mfd. 500 v., 5/-; 16 mfd. 500 v., 4/3; 16-16 mfd. 500 v., 5/3; 32 mfd. 500 v., 5/-; All New Stock.
Denco I.F. Liner for accurately tuning-up 465 k/c or 1.6 m/c. I.F. channels. Pre-tuned circuits, battery operated and completely self-contained. Price 39/6 (incl. bty.).
Omar Midget Coil Pack, Size 3 1/2 in. x 2 1/2 in. x 1 1/2 in. covering S. M. and L. waves. Coils wound on Polystyrene Formers with adjustable Iron Core, ensures efficient performance. Factory wired and aligned. Price, including full circuit for Superhet 465 k/c. Unit, 33/6. For T.R.F. circuit covering M. and L. Waves, 30/-. The Battery Portable Superhet Pack including ready wound aerial is now available at 37/6.
Output Transformer.—Stern's, Midget 1 1/4 in. x 1 in., ratio 60-1, 4/6 (or ratio 90-1, 4/6). Elstone Multi-ratio (over 12 ratios, some O.T.), 5/6 watts, 7/6. Stern's Heavy Duty Multi-ratio, all C/Tapped, handles 13 watts and suits P.X.4s, 616s, etc., 25/8. Roils Multi-ratio, 5/6 watts, 10/6.
L.F. Chokes, Midget 10 henry 250 ohm 40 mA., 3/6; 20 henry 250 ohm 60 mA., 6/6; 20 henry 300 ohm 100 mA 12/9; 5 henry 50 ohm 250 mA., 18/6; 20 henry 250 ohm 120 mA., 18/6; 9 henry 250 ohm 120 mA., 8/6.
Inter-Valve Transformer, Midget 1 1/4 in. x 1 1/4 in. ratio 3:1 (also ratio 5:1), 4/6 each. Varley "Niolet" ratio 4:1, 10/-; Heavy Duty, F/Pull Driver 3-1 each half, 40 mA., 8/-.
Aluminium Chassis, Substantially made of gauge 16 B.V.G. with four sides, 7in. x 4in. x 2in., 3/3; 9in. x 5in. x 2in., 4/-; 10in. x 6in. x 2in., 4/11; 10in. x 8in. x 2in., 5/6; 12in. x 9in. x 2in., 6/8; 14in. x 9in. x 2in., 6/11; 16in. x 8in. x 2in., 7/3; 16in. x 8in. x 3in., 8/6.
I.F. Transformer, 465 k/c. New well-known manufacturer's surplus 1 1/4 in. x 3/4 in. x 1 1/2 in. Iron Core, 9/- each, or size 1 1/2 in. x 2 in. capacity tuned, 13/9 pair. Denco Iron Core, 465 k/c, or 1.6 m/c, 1 in. x 1 1/4 in. x 3 1/2 in., 18/6 pair. Wearite Stand Cap, Tuned, 465 k/c, 20/- pr.
Meter Rectifiers, Westinghouse 250 micro/amp, 11/6, 1 mA, 10/6, 5 mA, 4/9.
Selenium Rectifiers, H.T. L. Wave, 250 v. 50 mA., 5/-; 200 v. 100 mA., 5/9; 250 v. 100 mA., 7/6. Bridge Rectifier 6 v. 1 1/2 amp, 11/3; 12 v. 1 1/2 amp, 12/6; 12 v. 3 amp, 19/8; 12 v. 5 amp, 25/-; 24 v. 3 amp, 23/6; Also L.T. 2/12 volt at 1/2 amp, max. 3/6.
Charger Transformer, Each has input of 230 volts. Output (a) 24 volt at 250 v., 9 v. and 4 v. at 3 amps, 21/6; (b) 30 volt at 15 v. and 9 v. at 3 amps, 22/-; (c) 15 volt at 9 v. at 3 amps, 14/3; (d) 12 volts, 1 1/2 amp, 11/3; (e) 15 volt at 9 v. at 6 amps, 19/9.
Valve Heater Auto Transformer, Step-up or down, 2 v., 4 v., 5 v., 6.3 v. at 3 amp., 9/6.
Filament Transformer, Input 230 volts, outputs 6.3 v. 1 1/2 amp., 7/6; 4 v. 1 1/2 amp., 7/6; Input 200/250 v., output 4 v. (C.T.) 1 1/2 amp., 4 v. 2 amp., 8.3 v. 2 amp. 17/6.
Denco Chassis Cutter, Adjustable between 1in. and 2 1/2 in. dia., used with Hand Brace, 7/6.
Surplus Components, Carbon Hand Mikes, with S/R switch, 2/11. Complete Set Moving Coil Headphones, and M/Coil Mike, 7/8. Bal. Armature Headphones, 1/9 (3/6 pr. with leads), Muirhead Precision Slow Motion Drive, ratio 60-1, 7/8. Midget Output Transf., 1 x 1 in. x 1 in., ratio 32-1, 3/-; 3 mfd. 5,000 volt Mainsbridge, 5/9. 1 mfd. 750 volt oil filled, 1/6. 1 mfd. 2,500 volt oil filled tubular, 2/6. 3 mfd. 2,000 v., 2/-; G.P.O. Telephone Hand and Bracket Set, complete, 12/6. 2 gang condenser, 0.0035 mfd., 4/-; M/Transf., new, input 110 v., 200 to 250 v. output, 235-0-235 v. 60 mA., 6.3 v. 3 amp., 5 v. 2 a., 19/6. 100 ohm w/vol. Volume Control with switch, 3/9.
WIRELESS AND ECONOMY
AMPLIFIER KITS AND CIRCUITS
All kits and Circuits show a practical component layout.
A Midget T.R.F. Battery Portable "Personal" Kit, a complete Kit of Parts to build a Midget 4-valve All-dry Battery Personal Set, consisting of Regenerative T.R.F. Circuit employing Flat Tuned Frame Aerial, with Denco Iron Dust Cored Coil, thereby ensuring maximum gain for Single-Tuned Stage covering medium Waveband.
Valve Line-up: 1T4 (R.F. Ampl.), 1T4 (Detector), 185 (1st A.F.), and 384 (output). Includes latest Roil 3in. Moving Coil Speaker, and a Chassis already drilled and shaped. A consumption of only 7 mA. ensures long battery life. The Kit is designed for a cabinet, minimum size 6 1/2 in. x 4 1/2 in. x 3 in. Detailed Building Instructions with Practical Layout and Circuit included with Kit make assembly easy.
Price for Complete Kit, £3/18/9 (plus 16/7 P.T.). Suitable unpainted Cabinet 6 1/2 in. x 4 1/2 in. x 3 in., 12/9. EverReady B114 Battery, 9/7. Building Instructions, Circuit, etc., supplied separately, 1/6.
"Wireless World" Midget A.C. Mains 2-Valve Receiver. We can supply all the components, including valves and M/Coil Speaker to build this set as specified in the March issue at a total cost of £3. Reprint of detailed assembly instructions and circuit supplied separately for 9d. A small complete outfit is now available to convert the 2-valve Receiver to the 2-Waveband, covering Medium and Long waves, 3-valve Receiver at a total cost of 33/6, including complete assembly instructions. (Supplied separately for 9d.).
We can supply all the Components, including Valves, M/Coil Speaker, etc., to build a Midget A.C./D.C. Mains T.R.F. 3-Valve (plus Metal Rectifier) Receiver as designed and specified by a popular Technical Magazine, at a total cost of £4/17/6. A reprint of the assembly instructions, and layout available for 9d.
An Entirely Complete 3-Valve Amplifier Kit of Parts, Operating on A.C. or D.C. Mains 200-250 volts. Has an output of max. 4 watts, with valve line-up 25A6, 6J7 and U31. A 6in. Moving Coil Speaker is supplied. Price, including Wiring Diagram, 75/-.
"Electronic" VALVE VOLTMETER. We can supply the COMPLETE KIT OF PARTS, including the Valve, Diode and Meter, etc., to build this instrument, as published in the January issue of "Electronic Engineering," complete with a reprint of the wiring diagram and assembly instructions (supplied separately for 9d.) at a total cost of £3/5/0.
TELEVISION !! The "Viewmaster" Telesior assembly Instructions showing Wiring Diagram and Practical Component layout, now available for 5/-. We have the specified Components, including the T.C.C.—Bulgin—Morzanite —W.R.—Westinghouse—Plessey—Colvern, etc., outfit in stock. Separate Components also available.
"Electronic" Telesior. Complete range of specified Components in Stock, instruction and explanatory booklet available for 2/6.
Denco Television Kit of Parts. We have the Complete Kit for both the 9in. and 12in. Telesiors in Stock. Price complete 9in. Kit, £41/7/11 (including C.R.T.). Price complete 12in. Kit, £47/16/8 (including C.R.T.). Prices include simple assembly instructions, with Circuit and Practical Layout (these can be supplied separately for 6/-).
*Send 2id. stamp for our Comprehensive Stock List. When ordering please cover packing and postage.
STERN RADIO LTD., 109 and 115 FLEET STREET, E.C.4.
Telephone: Central 5814 and 2380.

STERN RADIO LTD., 109 and 115 FLEET STREET, E.C.4.

Telephone: Central 5814 and 2380.

MORSE CODE TRAINING

There are Candler Morse Code Courses for:

BEGINNERS & OPERATORS

Send for this free

"Book of Facts"

it gives full details concerning all Courses.



JUNIOR Scientific Code Course for beginners. Teaches all the necessary code fundamentals scientifically.

ADVANCED High-speed Telegraphing for operators who want to increase their w.p.m. speed and improve their technique.

TELEGRAPH Touch Typewriting for those who wish to become expert in the use of the typewriter for recording messages and for general commercial uses.

Code Courses on Cash or Monthly Payment Terms

IRREFUTABLE EVIDENCE

of the value of the Candler System of Morse Code Training is given in the "Extracts from Students' letters," included with every "Book of Facts." Send for a copy now.

THE CANDLER SYSTEM CO.
(55.W) 121 Kingsway, London, W.C.2

Candler System Co., Denver, Colorado, U.S.A.

ATOM BOMBS AND ELECTIONS

may have you worried, but you can forget them if you possess a copy of the new, revised "HOME CONSTRUCTOR'S HANDBOOK" (now in its sixth edition!). This justly famous book is crammed full of many good things for ALL radio beginners, servicemen, dealers, experimenters, etc.

- Eight tested and guaranteed circuits, with full descriptions and parts lists.
- Feeder Units, Tuning Units and Superhets.
- Quality Amplifiers.
- Servicing and Constructional Hints and Tips.
- Resistance Colour Code, Charts, etc.
- Simple Formulae, etc.
- And many other interesting items.

We are proud to make the special offer once again of this useful book to "W.W." readers for 1/- ONLY. Send NOW for your copy of the new issue and catalogue. Letters of praise continue to reach us daily regarding the improved model 40 coil pack with CERAMIC switching for improved performance. These letters confirm our opinion that this unit has no equal anywhere even at double the price. P.S.H. of H.M.S. "Harrier" states: "I must add that your coil pack and IF's do everything you claim them to do."

The price is still unchanged at 42/- inclusive, or 47/- aligned and sealed for 465 kcs. I.F.

RODING LABORATORIES,
70 LORD AVENUE, ILFORD, ESSEX

COMPONENTS—SURPLUS AND SECONDHAND

CAR & GENERAL RADIO.—Components, materials and accessories at a saving! Prompt despatch (subject to being unsold); all goods guaranteed to their rating.

CABLES by famous makers: 7/044 single core, V.I.R., taped, varnished catlico taped, asbestos roved, cotton braided and varnished flameproof cable, 250 volt; colours green, yellow, red, blue, £9/18 per 100yd; 1/064 single core flameproof braided cable, 250 volt; colours red, black, green, yellow, red/black, blue/white, yellow/green, 32/- per 100yd; 3/035 single core, rubber insulated, taped, lead alloy sheathed, braided and fireproof compounded cable, 250 volt, £5/7 per 100yd; ditto 7/036 single core, £7/15 per 100yd.

CAPACITORS by famous makers (post-war manufacture) 50mf 50v dc peak waxed tubular electrolytics 3/ (32/- doz) 25mfd 25v dc working aluminium case tubular electrolytics, 2/2 (25/- per doz); solar metal box cased air-sealed non-inductive 0.1mfd 1000v dc working, 1/4 (14/- per doz); postage stamp moulded mica 0.001mfd 1000v dc working, 1/9 (18/- per doz); tubular rubber sealed non-inductive 1mfd 250v dc working 1/8 (18/- per doz); 0.5mfd auto suppressor condensers in sealed metal case with flying lead, 2/- (21/- per doz); ditto with heavy mounting lug, 2/4 (25/- per doz); tubular rubber sealed, non-inductive 0.1mfd 150v dc working, 8d (7/- per doz); waxed tubular non-inductive 0.005mfd 1000v dc working, 1/- (10/- per doz); waxed tubular 0.005mfd 800v ac working, 1/6 (15/- per doz); waxed tubular 0.001mfd 600v ac working, 1/2 (12/- per doz); the following waxed tubular 350v dc working 0.5mfd, 2/2 (21/- per doz); 0.25mfd 1/6 (16/- per doz); 0.1mfd, 1/2 (12/- per doz); 0.05mfd, 1/- (10/6 per doz); 0.02 and 0.01mfd, 10d (8/6 per doz); 0.005mfd 500v dc working, 10d (8/6 per doz); moulded mica capacitors 0.001mfd, 1/6 (15/- per doz); 300pf, 200pf, 100pf, 50pf, 10d (8/6 per doz).

ACCESSORIES: 1/4in diam. loud-hilling reflex horn speakers, 35/-; car radio, 6in extension loudspeakers in non-resonant baffle with adjustable mounting, 55/-; side mounting car radio two-section telescopic rod aerials, approx. 6ft 6in extended, 22/6 (carr. and packing 4/6 extra on less than 12/6).

RESISTORS: 1/4 watt, 3d each as follows: 1 meg, 1/4 meg; 1/2 watt, 3d each as follows: 560hm, 120hm, 150hm, 300hm, 3.3K, 3.9K, 11K, 27K, 47K, 51K, 62K, 68K, 100K, 250K, 750K, 1 meg; 1/2 watt, 4d each as follows: 15hm, 56hm, 62hm, 100hm, 120hm, 300hm, 1K, 3K, 4K, 5K, 5.1K.

SPECIAL quotations for quantities, dealers, wholesalers and manufacturers supplied; for further materials and components, etc., see our display advertisement in this issue; terms: c.w.o. (or c.o.d. inland over £1 on post goods only); please include sufficient to cover carriage and packing extra if under £2; overseas orders carriage and packing extra.

CAR & GENERAL RADIO. Attenbury Lane, Timperley, Cheshire. Tel. Sale (Manchester) 2214/5. Telegrams and Cables: "Motol" Altrincham. [4856]

MINIATURE output trans., 65-1, 104 each; condensers, 500pF x 50v, 9d; 1.1F x 1KV, 6d; W.W. pots, 10kd, long spindle, 1/-; 5000 meg spin, 9d; toggle switches, 6d; 4 gross 4BA x 1/4in bolts with nuts, and d'to 6BA, the lot, 4/3; valve holders, ceramic locals, 6d; int. octals, 4d; 465kc I.F. trans. iron core, 2/11.—Hatfield Radio, 78, Stroud Green Rd., N.4. [4866]

TELEKIT SUPPLY Co.—If its range you want, build the S.L.C.4 superhet television: S.L.C.4 W.D. receiver, complete with valve and wiring diagram and list of spare parts required, 45/-. S.L.C.4 Monitor unit, utilising 2 1/4-inch V.C.R.139, ideal oscilloscope cabinets, detachable top, hinged viewing hood, empty unblemished chassis, 8/-; with scanning components and valves, 15/-; complete with C.R.T., 27/6; moving coil microphone, as new, 1/6 each, 5/- pair, c.w.o.; post your requirements to: TELEKIT SUPPLY Co., 37, Station Approach, Hayes, Kent. [4874]

NO. 19 transmitter-receiver units.—Once again we have been fortunate to secure a limited number of these useful chassis. They were, in most cases, brand new, and of Canadian manufacture, but to conform to regulations were partially dismantled by the Ministry before release, and are sold by us for the many components, which include: 1 1/4-gang 0005 tuning condenser, 1 single 0005 tuning condenser, each fitted with slow motion dials, 3 I.F. transformers, approx. 15 valve holders, several Pots, Yaxley type switches, ceramic trimmers and several dozen condensers, resistors, etc. Special price is 12/6 carriage paid. We regret that when we last advertised these chassis the colossal demand exhausted all our stocks and we were forced to disappoint certain customers. If these customers will again apply, their orders will have preference.

POWER unit for the above works direct from a 12 or 24v battery and is actually 2 units in one (a rotary transformer and a vibrator unit), output 265v at 120 m/a and 540v at 26 m/a, brand new, Canadian manufacture; also contain fuses, indicator lamp, change-over switches, etc., a few only, at 49/6 carriage paid; we can also supply a rectifier unit Mallory type G634C for 10/- if ordered with this unit.

TELEVISION Enthusiasts!—Low loss Di-pole insulator, with heavy brass studs, for your own elements, to suit London or Birmingham, the basis of any ultra efficient aerial installation, only 5/- each; send s.a.e. for latest lists. **WALTON'S WIRELESS STORES**, 203, Staveley Rd., Wolverhampton (small orders); 48, Stafford St., Wolverhampton (callers only). [0061]

THESE ARE IN STOCK

Television Explained. By W. E. Miller. 5s. Postage 5d.

Practical Wireless Circuits. By F. J. Camm. 6s. Postage 5d.

Fundamentals of Radio-Valve Technique. By J. J. Dekker. 35s. Postage 1s.

Amateur Radio Receivers. By S. K. Lewer. 3s. 6d. Postage 2d.

Radio Valve Data Compiled by the "Wireless World." 3s. 6d. Postage 3d.

Basic Television. By Bernard Grob. 5s. 6d. Postage 1s.

Frequency Modulated Radar. By D. G. C. Luck. 34s. Postage 1s.

Amateur Radio Simple Transmitting Equipment. By W. H. Allen and J. W. Mathews. 2s. Postage 2d.

Recent Advances in Radio Receivers. By L. A. Moxon. 18s. Postage 6d.

The Radio Amateur's Handbook. By A.R.R.L. 15s. 6d. Postage 9d.

The Technique of Radio Design. By E. E. Zepher. 25s. Postage 9d.

A Home Built Televisor for Sutton Coldfield Reception. By W. I. Flack. 4s. 6d. Postage 3d.

Wireless Servicing Manual. By W. T. Cocking. 10s. 6d. Postage 5d.

We have the finest selection of British and American radio books. Complete list on application.

THE MODERN BOOK CO.

(Dept. W. 2)

19-23 PRAED STREET
LONDON, W.2

HAZLEHURST DESIGNS LTD.

R.F. E.H.T. EQUIPMENT

In order to meet the increasing demand for all types of our E.H.T. equipment, we have pleasure in announcing the purchase of a larger factory at the address given below, where both Office and Works are now situated. With the enormously increased facilities available, we are planning to increase the range of equipment offered and also to speed up deliveries. Enquiries welcomed for all equipment between 2,000 and 50,000 volts at currents up to 1 m.A.

**34, POTTERY LANE,
HOLLAND PARK, W.11.**

Phone number to be announced later

When Quality Counts



... the **HOMELAB** Signal Generator is a wise choice. But there is a snag—we cannot give immediate delivery. The fact is that the large demand for this instrument has, until recently, exceeded our manufacturing capacity. Some of our customers have had to wait longer than was anticipated, but we have now obtained additional premises for the production of the **HOMELAB** and are able to make lots more of them. During the next few weeks we will be able to get right up to date with orders. We offer our apologies to those who have patiently awaited delivery—but we gather from the letters we receive that the **HOMELAB** is well worth waiting for.

May we remind you that the **HOMELAB** Signal Generator has the following features:

- 100KCS. to 130 MCS.
- 30 per cent. MODULATION AT 400~ or
- UNMODULATED CARRIER
- PROVISION FOR EXTERNAL MODULATION
- OUTPUT IMPEDANCE 10Ω
- LOW EXTERNAL FIELD
- BUFFER STAGE
- VARIABLE 400~ OUTPUT
- ACCURACY OF CALIBRATION ±1 per cent.
- A.C. MAINS OPERATION ONLY.

PRICE £6:11:0 plus 5/- for packing, etc.

Please send S.A.E. for full technical details and enclose P.O. for 2/6 if circuit diagram required. The **HOMELAB** Signal Generator can be seen at our new showrooms—the address is **HOMELAB INSTRUMENTS**, 374, High Road, London, E.11—but orders can only be accepted by post and these, together with all enquiries should be addressed to:—

HELY-MANN
ELECTRONICS LABORATORIES
116, GROVE RD., LONDON, E.17.

COMPONENTS SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.P.1. Tel. Museum 9188. 20watt high fidelity amplifier kits for construction the McMurdo, 8-valve, AC/DC amplifier, low impedance input (suitable for moving coil mikes, etc.), by triple shielded trans to E.F.37. R.C. coupled to triode strapped stage (EF37). With switched bass and top cut provided, trans with output stage using four CL33's in parallel push pull, large O.P.T. matches to 10 or 15Ω rectifiers two UR3C's parallel, alternative high impedance input to second stage, for Xtal pick-ups, tuner units, etc., required inputs for full output, high imp. 0.5v r.m.s., low imp. 1millivolt. V.G. operates on both inputs, chassis isolated from mains, complete kit of first-class components (including Partridge trans), all valves, black crackle chassis (ready drilled), black crackle and chromium case (15½inX6½inX8in), circuit diagram, etc., everything required for the construction of a fine job, £15/3, carr. paid.

MANSBRIDGE Condensers, 4mf, 1,000v. WKG (4½inX4inX1¼in), 3/-; 6mf, 2,000v Test (5inX4inX1¼), 4/-; 3mf, 2,500v Test (6½inX3½inX2¼in), 2/6; 25mf (7inX3inX2in), inc. term, 8,000v Test, 3/6; 2mf, 2,500v WKG (6inX5½inX2¼in), 4/-, post extra.

PERSONAL receivers, 3-valve T.R.F. receivers, using I.T.4's, contained in handsome Bakelite case, with lift up lid, size 7inX6½inX5in with lid closed, plastic carrying handle, frame aerial in lid, these receivers cover the medium wave-band and operate from self-contained standard size, dry batteries, types W1435 and U2, output to a pair of lightweight high resistance 'phones, 2 gang conds with s.m.d., opening the lid switches on, supplied brand new in maker's carton, with valves, 'phones and batteries an ideal set for children, invalids, and many other purposes, these receivers are not Govt. surplus, and are offered, ready to play, £3/19/6 carr. paid; 360-0-360v 220ma, 4v 8A C.T., 4 3a. 3 3.5a, trans. input 210/250, 50c/s, new, 32/6 carr. paid. T.V. line transformer, 1000, 4/11, in all, with T.C. lead (used with PEN46), 11/6, chassis (steel), 5X5¼X1¼in, drilled 4 button base holes, 1/9; 5X9¼X1¼in, drilled 7 button base holes, 2/3; all 17X19¼X2¼in, drilled 7 int. oct. and square open-ends, 5/3; H.T. trans, 4kv 1ma, 2v Pr. 230/500, 29/6; rec. R. 1451 covers 65-68Mc/s, 10 valves (6.3v), tuning meter, 6in SM dial, circuit diagram, etc., brand new, in transit case, £4/4, carr. paid; personal receivers B.C.728c, 7 valve rec. using 1.4v valves, with 4 push buttons covering 2-6Mc/s, built in L/S, 2 valves, trans. new complete with valves (IT4, IR5, etc.), 2 and 12v VIB, 2v acc., telescope A.E., instruction book, etc., £8/19/6; auto trans., 200-250v-11v, 60W rating enclosed, 18/-; special line auto, 230/110v, 100W, 9/6; smoothing chokes 5H 120mA, 1400/, 3/6; 5H 200mA, 1000, 4/11; 200mA, 1000, 5/6; 5H, 250mA, 900, 7/6; electrolytics, 8mf, 150v, 1/3; 8/170v, 1/3; 8/450v, 2/3; 16/350v can, 2/3; 16+8 450v large can, 4/-; 16+24+8 450v can, 5/-; 24 450v large can, 2/9; 16+8 350v can, 3/6; 60+100 250v, 3/10; 32 250v, can, 2/3; 100mf 6v, 6d; 25/25v, 1/3; 100 25v, 1/6; 25/50v, 1/3; 16/350 can, 1/9; 24/350 can, 2/-; 8+24 350v can, 2/6; P.M. loudspeakers 5in less trans., 9/11; with trans. 4.500Ω, 11/6; 6½in less trans., 9/11; 10in with trans., 21/-; R.F. units type 124, 8/6; with valves, used in good condition, post 1/6 extra please; output trans. 2,000/2Ω, 2,500/2Ω, 2.750/Ω, 3,000/2Ω, 3/-; 4,500/2Ω, 7,000/4Ω, 3/6 3 ratio 7,000/3 5000/1,750/4Ω, 4/-; heavy duty 7,000, 2Ω 3/6; I.F. trans. 465 Kc/s small size, iron core, 7/6 pr.; 2 gang conds., .0005 ceramic ins., 1in standard spindle, 4/6; ceramic switches 2p., 3v. 1B, 2/-; 5p., 3v. 1B, 2/6; switches, standard size 2p., 4v. 1B (additional wafer with shorting plate), 2/6; 2p., 4v 3B, 2/6; 1p., 10v. 2B, 2/6; all have 3in spindles; resistors 100 assorted, 47 values ranging 180Ω ¼W-100K 3w, standard sizes, best makes, 10/6, post 6d; ceramic trimmers, 3/50pf, 3 cn a bar, 1/3; 1/15pf single, 4d; 3/30pf air spaced concentric, 6d; 3/25pf U.I.C. type, 3d; air spaced variable ¼in spindles 25v, 50pf, straight, 50pf diff. ceramic bases, 1/-; 35pf butterfly, 1/-; car radio vibrator packs with 12v 4 in VIB and OZ4 valve on chassis 5¼X3¼X1½in output 250v 65mA output brought out on 8ft screened lead, 17/6; meters mov'g coil, metal cased, 2in circular 0/500 microA, 7/6; 0/15-600v req. ext. res, 6/6; 0/20 or 0/40A with shunt, 5/-; Bakelite cased 2in square 01mA, 7/6; 0/5mA, 6/-; 0/50mA, 7/-; 0/300v series res, supplied 7/-; Bakelite cased 2½in circular, 0/500microA, 16/6; 0/30mA, 7/-; 0/50mA, 8/6; 0/100mA, 8/6; 0/200mA, 8/6; 0/15v type 1 line desk type, 15/-; visual indicators type 1 crossover needle, with 2 separate 60microA movements, 5/-; S.M. dials as on R.F.28, etc., 3/11; ex-Admiralty patt. 1257, 17in engraved 0-100, fast/slow (50-1), panel mounting, fits 1½in spin., 2/6; rotary power units type 104 12v D.C. input, outputs 250v 60mA 6.5v, 2 5mA P.M. rotary mounted on chassis with supp. 6/11; type 87 output as above but 24v input, 5/11; 10-valve receivers, R.28/ARC5, cover 100-150 Mc/s, brand new with valves (inc. 4-717 A.C. 42/6; Wilcox Gay V.F.O. covers 10 Mc/s, with 0-10 mA meter, supplied brand new in original carton, with 807 accessories (plugs, leads, etc.), and instruction book £5 carr. paid; Wilcox Gay Xtal multipliers 2-7 Mc/s, brand new, with 807, plugs, leads, instruction book, etc., in original cartons 40/- carr. paid; superhet coils 6X1¼in formers M.V. HF, AE, osc., L.V. HF, AE, osc., 1/6 per coil; I.F. traps iron cored 465 Kc/s 1/9, set of 6 coils and trap 9/6; 7 or 10 pin plugs and sockets with keyway 1/6 pr.; 8-way Jones p.ugs and sockets with cover, 1/6 pr.; V.C. carbon with sw. 2¼in spindle 5K, 25K, 50K, 100K, 250K, 4/-; 3 watt wire-wound no

(Continued on page 78)

MAINS TRANSFORMERS, FULLY INTERLEAVED, SCREENED AND IMPREGNATED. ALL PRIMARIES ARE 200/250 v.

Half Shrouded			
HS63.	Output 250/0/250v, 60 m/a.	6.3v. at 3 amps, 5v. at 2 amps	15/6
HS40.	Windings as above.	4v. at 4 amps, 4v. at 2 amps.	15/6
Output			
HS2.	250/0/250v.	80 m/a.	17/6
HS30.	300/0/300v.	80 m/a.	17/6
HS3.	350/0/350v.	80 m/a.	17/6
HS2X.	250/0/250v.	100 m/a.	19/6
HS30X.	300/0/300v.	100 m/a.	19/6
HS3X.	350/0/350v.	100 m/a.	19/6

Fully Shrouded			
Output			
FS2.	250/0/250v.	80 m/a.	19/6
FS30.	300/0/300v.	80 m/a.	19/6
FS3.	350/0/350v.	80 m/a.	19/6
FS2X.	250/0/250v.	100 m/a.	21/6
FS30X.	300/0/300v.	100 m/a.	21/6
FS3X.	350/0/350v.	100 m/a.	21/6

All the above have 6.3-4-0v. at 4 amps, 5-4-0v. at 2 amps.

FS43.	Output, 425/0/425v.	200 m/a.	6.3v, 4 amps. C.T. 6.3v, 4 amps. C.T. 5v. 3 amps. Fully shrouded.	42/6
FS50.	Output, 450/0/450v.	250 m/a.	6.3 v. 2 amps. C.T., 6.3v, 4 amps. C.T. 5v. 3 amps. Fully shrouded.	62/6
F30X.	Output, 300/0/300v.	80 m/a.	6.3 v. 7 amps. 5v. 2 amps. Framed, Flying leads.	26/6
FS5X.	Output, 350/0/350v.	250 m/a.	6.3v. 7 amps., 4v. 8 amps., 4v. 3 amps., 0-2-6.3v. 2 amps. Fully shrouded.	59/6

FILAMENT TRANSFORMERS

F4.	Output, 4v. 2 amps.	7/6
F6.	Output, 6.3v. 2 amps.	7/6
F12.	Output, 12.6v. tapped 6.3v. at 3 amps	15/6
F24.	Output 24v. tapped 12v. at 3 amps.	21/6
F12 and F24 framed with Flying Leads		
FU6.	Output, 0-2-4-5-6.3v. at 2 amps.	9/-
F19.	Output, 0-2-4-5-6.3 v. at 4 amps.	15/-
FU6 and F29 clamped with Flying Leads		
F5.	Output, 6-3v. at 10 amps., 5v. at 10 amps., 12.6v. at 5 amps., 10v. at 5 amps.	31/6
F6/4.	Output, four at 6.3v. tapped at 5v. at 5 amps. per winding, giving by suitable series and parallel connections 24v. at 5 amp.; 20v. at 5 amp.; 18v. at 5 amp.; 15v. at 5 amp.; 12.6v. at 10 amp.; 10v. at 10 amp.; 6.3v. at 20 amp.; 5v. at 20 amp.	47/6
F5 and F6/4 framed with Flying Leads		

OUTPUT TRANSFORMERS

MOPI.	Ratio 26,46, 56, 66, 90, 120-1, 50 m/a. max current, C.T. for Q.P.P. Class B, etc. Secondary 2¼ ohms. Top panel and clamped, each.	5/-
OPI.	Midget Power Pentode, ratios 30, 60, 90-1, 40 m/a., Secondary 2/3 ohms, each	3/2
OP1.	Midget Pentode, ratios 45-1, Secondary 2/3 ohms, 40 m/a. per doz.	33/-
OPI10.	10/15 watts output, 20 ratios on Full and Half primary.	16/3
OP30.	30 watts output, 20 ratios on Full and Half primary.	23/9
Williamson's O.P. Transformer to Author's specification.		£3/12/6
The following framed with Flying Leads:		
EHTU.	Tapped EHT, 1,500v, 2,000v., 2,500v., 3,000v. up to 5 m/a., 2-0-2v. at 1.5 amps., 4v. at 1.5 amps.	42/6
EHT.1.	1,000v. 5 m/a. 2-0-2v. 2 amps., 4v. 1.1 amps.	32/6
EHT.2.	2,000v. 5 m/a. 2-0-2v. 2 amps., 4v. 1.1 amps.	35/-
EHT.25.	2,500v. 5 m/a. 2-0-2v. 2 amps., 4v. 1.1 amps.	36/6

C.W.O. (add 1/- in £ for carriage), all orders over £2 carriage paid.

H. ASHWORTH
(Dept. W.W.)
676 GT. HORTON RD., BRADFORD, YORKS

AMC

TELEVISION

Manufactured to "Electronic Engineering" Telespecification.

MIDLAND T.V. Sound and Vision Panels fitted with formers and dust cores now available.

LINE OUTPUT TRANSFORMERS

NEW Improved SET OF GANTRIES COMPLETE

FOCUS COILS

LINE AND FRAME SCANNING COIL ASSEMBLIES

All Steel **CADMIUM PLATED POWER AND TIME BASE CHASSIS** valve-holders, 3 point and single socket and all necessary cut-outs.

SOUND PANEL CHASSIS ASSEMBLY, fitted with screens, valve-holders, formers and dust cores.

VISION PANEL CHASSIS ASSEMBLY, fitted with screens, valve-holders, formers and dust cores.

9" C.R. TUBE SUPPORT for mounting on top of Gantry Assembly.

9" CREAM MASKS.

5, SHAKESPEARE RD., FINCHLEY, N.3

Phone: FINchley 2188

PAPER DIELECTRIC CONDENSERS

Super quality, by a famous British manufacturer. In moulded Bakelite cases, Neoprene sealed ends, lin. diameter by 2½ in. long, plus terminal tags. Capacitance 0.01 µF. Working Voltage 5,000 D.C. at tropical temperature. Countless uses, including breakdown-free suppression, etc. Unused, and offered whilst stocks last at only 10/- per dozen, post paid. C.W.O. please, despatch at once. Enquiries invited for very large quantities. Don't miss these!

WIRELESS SUPPLIES UNLIMITED,
264-266 Old Christchurch Road, BOURNEMOUTH, Hants.

COMPONENTS—SURPLUS AND SECONDHAND

(Continued from page 77)

twin w/w 2.5a/2.5a, 2/b; 500/3001, 2/6; 50K; 50K, 3/-; twin carcon 1m/1m, 2/6; all. telescopic aerials, 15in closed 7ft 6in extended, 3/6; receivers type 76, 150/505 Kc/s, 3 valves ARTH2. VR53, VR32, 1 F, output 560 Kc/s, brand new, in transit case, 22/6, cart. paid.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. [0015

BRAND-new ex-R.A.F. power units contain- ing 0-1ma m/c meter, meter rectifier, 2 x 32 mid., 6000Ω condensers, 2 x 5000ms, 200 Henry 1.4 chokes, heavy duty mains transformer input 230 volts 50 cycles, output 350-0-350v at 300ma, 2 x 6.3v, 5v, 20-0-20v, 2 x EF50, EA50 5U4G. Condensers, resistances, thermal delay switches, fuses, etc. all in wooden packing case; bargain at £6/15, carriage paid.

TELEVISION—5000v rectifier V1907/960 4v fit; 6/-; conds. 0.25 1000v; 8/- doz; 0.03 2.5kv, 0.05 3.5kv; 1/- each; 0.1 6kv; 5/6 ea; 4mf 425v micropacks; 10/6 doz; condensers 0.01 1000; 3/- doz; 0.25 500; 3/6 doz; 0.25 1000; 6/6 doz; 4mf; 1/- ea; many other items, s.a.e. list.—Cross, Skerries Cross Lane, Grange, West Kirby, Cheshire. [4749

MOTORS, suitable for conversion to 230-volt a.c. mains. 5,000 to clear, space needed. Ideal for grinders, hand drills, etc.; 3 for 20/-; with instructions for conversion to approx. 1.5 mins; 2,000 Malloy vibrators, 12-volt, standard 4-pin, 12 for 20/-; 50,000 condensers, .001 to 32mf, ass., 200 for 20/-; 50,000 resistors, ass., 200 for 20/-; 20,000 volume controls, ass. with knobs, 50 for 20/-; 50,000 dimmer switches, rotary 50 for 20/-; 10,000 suppressor packs, 2 cond., 1 choke, 50 for 20/-; 100,000 standard G.P.O. telephone inserts, 25 for 20/-; 100,000 condensers, type 10C/8474, mica, 10 for 20/-.

GENERATORS samples all above, including motor 25/-, cart. paid. P.O. cash or cheque to—

UNIVERSAL TRADING SUPPLIES, St. Peters, Stamford, Lincs. [4855

TAYLOR 65B sig. generator, surplus, £10; 0-500u ampmmeters, 2in dia., 4/-; p.m. speakers, less trans. 10in Rola, £1; 6½in Plessey, 12/6; conical, 4in, 4/6; 455, 4/6; 44, trans. 11/-; 10-way keyed plugs and sockets, 1/7 pr; mains trans. 200-250v 50c, screened prim. 350-0-350v at 130ma, 6v at 4amp, 5v at 3amp, 22/-; min., carbon mikes with leads, 1/8; M/c h. phones, with m/c mike attached, 6/3; h. phone leads, 7 type with jack plug, 1/8; ball drives, ratio 6-1 1/8; S.W. condensers, or can be air spaced trimmers, 50 pf, ceramic ends, 1/-; resistances, ¼w 1/9 doz, ¼w 2/- doz, 1w 4/- doz; s.a.e. for enquiries; c.w.o. please, orders post, free over £1.—Rink, 10, Parkhill Rd., Bury, Lanes. [4844

VIBRATORS: 6 volt 4-pin; 3/6; ditto 12 2/6; old type telephones complete with bell, magneto, and handset, in wooden case, untested; to clear 10/-; coaxial plugs and sockets; 6d pair, 4/6 per doz; remote control units, U.S. make, complete with bell, hand generator, switches, transformer, etc. khaki finished steel case, new; only 17/6; meters: 0-300 volts voltmeters, new, boxed; 5/-; 0-100ma, scaled 0-300 ma; 3/6; 0-3.5 amps; 3/6; type 15/16 power unit (motor generator) 12-24 volt input, in original wooden transit case, easily converts to a power unit; motor only 15/-, BC966 IFF trans/receiver, 12 volt input, 13, 6 volt valves and motor generator, in good condition; 19/6; 6 volt vibrator power pack for the 21 w/s, 200 volts at 40-50 mills, will work on 240 v, 50 c., with jack plug, 2/-; complete with vibrator price 18/6.—Haynsons, 14, St. Mary's, Bedford. [0012

GENERAL ELECTRIC wire recorder, as new, £75; HRO receivers from £12/10; Hallcrafters, S27 SX24, R.C.A. models, AR38, AR88LF, AR77, German spot-wave receiver, ex-Arm, 107 received, 12/10; Eddystone 640, £22; rotary converters, all voltages and wattage, in stock; amplifiers, 50 cps, 200-250v, 20 watts, less valves, £4/10; valves for same, MH4, ML4, PPS/400, MU14, large selection of L.T. transformers from 6v to 50v; a large selection of meters, all ranges, mag. slips, in pairs, new, in cases, £3/5; small relays, 1,000Ω, 3/-; high-speed relays, 2,000Ω, 7/-; 522 transmitter chassis, less valves, 5/6 each, special offer meters, 5ma 6/3, 100ma 7/6; 5 thermo ampmmeters 5/6; 2in scale small motors, 12v, 24v, 9/6; ball and biscuit mikes, ex-Govt., £5; duo adaptors, new, in boxes, 12/6 each; Hammarlund super-pro receivers, with power unit, as new, £55 and £45; large energised speakers, Rolo G12, Magnavox 65; all prices exclude postage.

SERVICE RADIO SPARES, 4, Lisle St., London, W.C.2. Tel. Ger. 1734. [4876

JACK PORTER, Ltd. (Radio) new guaranteed components, midget relays 1/-; midget 1/-; chokes 2,000ohms, mu-metal and screened 1/-; television 8-way Amphenol terminal blocks 1/-; ceramic insulated 3-pole 4-way switches ¼in shaft 2/6; 2-pole 2-way wave switch ¼in shaft 1/-; U.S.A. 15mfds condensers, tapped 5, 5, 5, 400v d.c. 75c 4/-; oil condensers, 15mfid, 750v, tapped 4, 4, 4, 5/7/6; poited push-pull output transformers, load 10,000 plate to plate, 20watts, speech 150hms, weight 2½lb, 23/6; d-tted E.H.T. transformers, 4kv also 2 or 4v 55/-; driver transformers, split prim. and sec. 4/-; variable 30watt, 300ohm slider bias resistors 1/-; .01mfid mica condensers, wire ends 2/6 dozen; 300pf silver mica, wire ends 2/6 dozen; 004 mica, 400v 2/6 dozen; 100pf split-stator tuning condensers 1/6; BC433 flexible control drives, 6ft 3/9; U.S.A. chromax water immersion heaters, 200v, 750watts 7/6; R.F. thermo moving coil 150ma meters 3/6; cat 2,000mfid, 15v 2/6; Philco blowers 24v a.c./d.c. lamp, 6,000rpm, complete with fan and case 12/6; postage extra; lists free, with confirmation from—Jack Porter Ltd. (Radio), 30/31, College St., Worcester. [4757

WE DON'T

supply anything Ex-Government

ALL BRAND NEW GOODS

—fully guaranteed—

AUTO CHANGERS

GARRARD, RC65A. A.C./D.C. Mixed Records, £20/15/-.

GARRARD, RC65A. A.C. Mixed Records, £15/13/6.

E.M.I./MARCONI. A.C. Auto Changer non mix, Hi-Fi Head complete with Transformer, £10/10/8.

COLLARO, RC500. A.C. Auto Changer, Non Mix, Crystal or Hi-Fi Head, £10/15/-.

CABINETS, Unpolished, for all the above changers, Motor Boards ready cut to fit Plate, £3/10/-.

MOTOR AND TURNABLE with magnetic Pick-Up and Auto Stop. **COLLARO A.C.,** £9/13/6; **GARRARD, A.C./D.C.,** £12/9/2.

MOTOR AND TURNABLE ONLY— Induction Type. A.C., £5/18/4; A.C./D.C., £9/5/6.

TAYLOR TEST GEAR

The entire range by this famous maker is now available on Hire Purchase. S.A.E. for catalogue and terms.

ALL AVO TEST GEAR NOW IN STOCK

AVO 7, Leather cases, £2/2/6. We are the largest actual stockists of Avo Meters in England. S.A.E. for catalogue and price list.

All items can be supplied C.O.D. up to 15lb. In weight. Otherwise Cash with order, please.

Special attention to Overseas Orders, which are free of Purchase Tax.

MODERN ELECTRICS LTD.
164, Charing Cross Road, London, W.C.2.
Telephone: Temple Bar 7587.

COMPONENTS MATERIALS AND ACCESSORIES AT A SAVING!

PROMPT DESPATCH

(subject to being unsold)

ALL GOODS GUARANTEED TO THEIR RATING
LITZ WIRE, 8/48 D.W.A.S. Enamelled Copper 9/- per oz. 27/47 D.W.A.S. Enamelled Copper 15/6 per oz.

COLOR CODED WIRE. Single 92 S.W.G. Enamel, Cotton Reered and Glazed Paper Insulated. Colours: Brown, Brown/Blue, Blue, Red/Green, Red/Green, Black, Red/Brown, Blue/White, Orange, Red/Blue, Red, Green. 16 3 per 100 yds.

COMPONENTS ETC. G.T. Octal Valve Screens 8d. **Vibrator Earthing Clips,** 1/-, Plain Walnut Finish Bakelite Control Knobs, 1in. Diam. 6d. High Density 8in. P.M. Speaker Units, 3-4 ohm Coil 15/6. 4 Meg. Volume Controls with Switch (Heavy Duty) 6/6. 6 volt and 12 volt Non-Synchronous 4 pin Vibrators, 12/6. 6 volt Self Rectifying Vibrators, 15/3. Dial Lamp Holders 1/2. International Octal Chassis Valve Holders, 5d. Miniature 50 m/a Smoothing Chokes, 3/9. 3 Tag Terminal Strips, 4d. 2 Tag ditto, 3d. 2 Pye H.F. Chokes, 3/3. 4/40 pf. Mica Trimmers, 1/2. 40/80 pf. Ditto, 1/5. Valve Top Clips, 2/- per doz. Springs of Bostik Cement 2/2. Drum Drive Tension Stripes 3d. 5,000 ohm Auto Distributor Suppressors 1/3. Bulgin 5,000 ohm Wire Wound Heavy Duty Resistances on Ceramic Formers, Max. Disp. 20 Watts, 3/6. Palnton 25,000 ohm Wire Wound Resistors in Vitreous Enamel, Max. Disp. 10 Watts, 4/-, Zenith 6.4 ohm Wire Wound Resistors in Vitreous Enamel, Max. Disp. 30 Watts, 6/3. Simvic Type 2, 25 volt Thermal Delay Switches 12/6. Belling-Lee Shrouded 10 pin Connector Plugs 4/-. Sockets for same, chassis mounting, 2/-, 4-pin Chassis Mounting Valve Holders, 7d. 6-pin Ditto, 8d. 1½in. long, 20 Amp. Glass Cartridge Fuses, 4/- per doz. Dial lamps, 6/7 volt 15 Amp. M.E.S. 10 mm. 1/7.

SPECIAL QUOTATIONS FOR QUANTITIES

Dealers, Wholesalers and Manufacturers Supplied. For Further Lines of Cables, Capacitors, Resistors, etc., see our Advertisement in the Miscellaneous Columns. Terms: C.W.O. (or G.O.D. Inland). Over £1 on Post Goods Only. Please include sufficient to cover carriage and packing, extra if under £2. Overseas Orders, Carriage and Packing extra.

CAR & GENERAL RADIO

Attenuary Lane, Timperley, Cheshire.

Tel: SAE (Manchester) 2214/5. Grams and Cables: "Motol" Altrincham.

MAINS TRANSFORMERS

(Postage Extra)

As supplied to the Ministry of Supply, B.B.C., Education Authorities, etc. Interleaved and impregnated. Screened primaries tapped 200/250 v.

DROP THROUGH TYPE. TOP SHROUD.

(a) 250-0-250 v. 60 mA. 6.3 v. 3 a., 5 v. 2 a.	15/6
(b) 250-0-250 v. 60 mA., 4 v. 4 a., 4 v. 2 a.	15/6
Following types have Universal L.T. windings.	
6.3-4-0 v. 4 a. C.T., 5-4-0 v. 2 a.	
(c) 250-0-250 v. 80 mA.	17/6
(d) 300-0-300 v. 80 mA.	17/6
(e) 350-0-350 v. 80 mA.	17/6
(f) 250-0-250 v. 100 mA.	19/6
(g) 300-0-300 v. 100 mA.	19/6
(h) 350-0-350 v. 100 mA.	19/6

FULLY SHROUDED UPRIGHT TYPES.

(i) 350-0-350 v. 150 mA. 6.3 4-0 v. 6 a. C.T., 5-4-0 v. 3 a.	39/-
(j) 425-0-425 v. 180 mA., 6.3 v. 4 a. C.T., 6.3 v. 4 a. C.T., 5 v. 3 a.	42/6
(k) 425-0-425 v. 180 mA., 4 v. 8 a. C.T., 4 v. 4 a. C.T., 4 v. 4 a.	44/6
(l) 425-0-425 v. 180 mA., 6.3 v. 4 a. C.T., 4 v. 2 a. C.T., 4 v. 2 a. C.T., 5 v. 3 a.	47/-

Note.—Model (j) above is suitable for Williamson Amplifier.

WILLIAMSON OUTPUT TRANSFORMER.

Built to Author's specification. 1.75 secondaries £3 12 6

SMOOTHING CHOKES.

40 ma., 5/-; 60 mA., 6/6; 90 mA., 7/-; 100 mA., 12/6; 200 mA., 21/-; 250 mA., 25/-.

FEEDER UNITS.

High-class 110 feeder units with R.F. stage. Switched pick-up sockets. Glass scales. Completely aligned. MODEL A. Covers 16/50, 190/350 and 900/2,000 metres. Price, including P. Tax. £10 8 6
Set of 4 valves £22 11 3
MODEL B DE LUXE. Covers 45/145, 190/350, 900/2,000 metres and six ranges of band spread. Price, incl. P. Tax. £18 7 6
Set of 5 valves £3 2 6
Note.—Both feeder units illustrated in our catalogue

"VIEW MASTER" TELEVISION RECEIVER.

Designed in conjunction with prominent British Radio Manufacturers using new components—not surplus. CONSTRUCTOR'S ENVELOPE, containing full instructions, layouts, diagrams, etc., 5/4, post free.
W.B. Chassis and Speaker, etc. £6 5 0
T.C.C. Condensers £6 15 0
Westinghouse Rectifiers £3 2 6
Morganite Resistor Kit £1 6 9
Flessey Transformers, Focus Coils, etc. £5 12 6
Colvern Wire Wound Pot'meters. £9 3
Brelan Panels and Switches £2 6
Weatherite Coils and Chokes £1 2 0

B.V.A. AND TUNGSRAM VALVES.

Over 350 different types in stock, including difficult obsolete types. B.O.T. prices. Send for the valve you urgently require. C.O.D.

POLISHED ALUMINIUM CHASSIS, 16 S.W.G., 4 SIDES, 3 in. DEEP.

10in. x 6in., 10in. x 8in., 8/6; 12in. x 9in., 10/6; 14in. x 9in., 16in. x 8in., 11/6; 20in. x 8in., 12/6.

EDDYSTONE SHORT-WAVE COMPONENTS.

Full range stocked. Eddystone Illustrated catalogue, 6d.

HIGH FIDELITY LOUSPEAKERS.

Goodmans T2/1205, 12in. P.M. £6 15 0
Goodmans Axion, 12in. P.M., Twin Cone £8 8 0

INSTRUMENT WIRES.

Comprehensive range in enamelled, cotton and silk covered copper wires from 16 S.W.G. to 40 S.W.G.

EX-GOVT. SURPLUS.

A good range of equipment at bargain prices. S.T.C. Bull Microphones. List approx. £22 £4 15 0
Nine Detector Amplifiers. Containing three 1T4 valves in ceramic bases, condensers, resistors, etc. £1 2 6

SEND NOW 5d. in stamps for LATEST CATALOGUE.

Terms C.W.O. or C.O.D.

COULPHONE RADIO

"The Return of Post Mail Order Service"

53, BURSCOUGH STREET, ORMSKIRK, LANCs.

Phone 987

COMPONENTS—SURPLUS AND SECONDHAND

RECTIFIERS, 12v 1a 5/6, 12v 4a 12/6, 36v 4a 35/-, all sizes available; mains trans., 12v 3a, tapped every 2v. 15/-; mains units, 12v 16a d.c., 12v 50a a.c., £9/10; meters, 2-6in. at low prices; many types w/w. vitreous resistors, 250hm 1watt to 2,000hm 30watt from 3/- per doz.; tone vol. controls, 15,000 and 1meg. 11d.; crystal oven thermostats, 44 C to 47 C. 3/-; everything available, s.a.e. exact requirements. C. J. EMMS, 26a, Coleherne Mews, S.W.5. ^[4889] ^[4889]

RADIO UNLIMITED, Elm Rd., London, E.17. Tel. Key. 4815, offer the following spotless, guaranteed, surplus bargains; fresh stock condensers, 8mid, 450v. 3/-; 8X8, 450v. 3/3; 8X8X8, 450v. 3/6; 8X16, 450v. 4/6; 0.1, 500v. 3/- doz.; 2.2 meg pots. 1/1; p/pull hand mic w/switch, 5/6; mic trans 2/6; m/coil hand type mic w/switch, 3/6; alum., drilled chassis with valves 6/6, 6K7, 6K8, 6Q7, 5Z4, 37/6; A1134 battery amplifier, with valves, solled but O.K., 9/6; twin meter test panel, 12/6; m/iron 0-25 ammeter, 2/11; 0-40 m/coil ammeter, 4/6; 0-50volt 4/6; morse training units with wire, battery and microphone, 8/6; amplifier cabinet, black crackle finish, 15/-; toggle switches 1/3; bal/arm headphones with lead and plug, 4/6; m/coil phone & mic sets, 5/6; P.M. speaker with trans, 11/6; clockwork flasher device 10/-; carrying case battery cabinet for 10in speaker, 21/-; throat mics 2/3; A.C./D.C. 3v plus rec. amplifier, 105/-; headphone matching unit, high to low impedance, 3/6; multi-range output trans. 6/6; EF50 holders 6d; chrom 24v d.c. stand (folding) 29/-; high-grade m/coil mic. listed at 42/-, offered at 42/-; hundreds other lines: stamp list: mention W.W.

CARBON mike, 1/6; phones with combined throat mike, unused 3/6; morse key, flex, plug, 1/-; assorted resistors, 6/6 a 100; assorted condensers, 2/- doz.; r.f. chokes, 6d; new Coax plug and socket, 9d; telephone ringer, 4/-; Mallory 12v vibrators, 2/6; braided twin screened flex, 6d yd; 1mm sleeving, 3/- gross vds; 2mm, 4/- gross vds; 7/044 twin flat t.r.s. cable, £5 100 vds; octal valvoholder, 4d; 4-pin U.X. holders, 2/6 doz.; selenium rectifiers, 378v 1.2amps, h.w. 1/6; 550v 300 m.a., h.w. 6/6; 250v 75 m.a. i.f.w., 2/-; 180v 140 m.a. i.f.w., 2/-; insulated aerial wire, 8/6 100 yds; bulb holders, warning light type, black moulded case, red perspex top, uses cycle type bulb, 10d; 3-way multi color scale 1/1-1/4; chokes, 3/-; transformer, 230V 50c, input, 50W 11a output, can be adapted to 100v output, 25/-; assorted pots 12/- doz; assorted v/holders, 2/6 doz; rotary converter power supply unit, 24v d.c. input 12v and 200v d.c. output, contains relay, neon stabiliser, 5 chokes, 1 plus sockets, etc., brand new, 6/6; S.L.C.3 20 valves receiver, 2 r.f. stages, tunable local oscillator, 4 i.f.s. easily converted to T.V., 25/-; electric motor, 22v d.c., 2,000rpm, 1-30hp continuous rating, shunt wound, 5/-; R107 British Army Communications (reconditioned), Box 1069, 4XEB33, 1X6X5G 3-way valve 1-3 mcs, 2.8-7.25 mcs, 7-18 mcs, B.F.O., speaker, works from 12v d.c. or 100-250 v 50c, £10; B.T.H. Selsvn motors, 230v 50c, torque 45lb. ins. 2-speed geared handle, rubber moulded on metal base, £6.—Loken, Westalloy, Hitchin Herts. ^[4824]

WANTED, EXCHANGE, ETC.
FINE wires in large quantities only, must be new and perfect material

L. E. SIMMONDS, Ltd., 8a, Byron Rd., Harrow, Tel. Harrow 2524 and 0135. ^[3661]

WANTED, Magnetophone cons. B with spares (amplifier reconditioned).—Box 1069 ^[4882]

WANTED, quantity M.E.A. patt. 36 and 21 laminations in silcor I or radiometal.—Box 1503. ^[4882]

WANTED, "Wireless World," May 1940, and August, 1940.—Steffensen, Ehlersvej 8, Hellerup, Denmark. ^[4715]

WANTED, R.A.F. 1155N receivers, complete with valves and in good order.—Teleetric Co., 23 Regent Quay, Aberdeen. ^[4783]

WANTED, surplus relays and push-button units, any condition, large or small quantities; highest prices paid.—Box 8485. ^[3532]

WE pay top prices for used test equipment, all types.—University Radio, Ltd., 22, Lisle St., London, W.C.2. Tel. Ger. 4447 and Ger. 8582. ^[9892]

WANTED, AR88DS, SX28s, cash or part exchange; no objection slight repair.—P.C.A. Radio, Cambridge Grove, London, W.6. Tel. Riv. 3279. ^[0080]

WANTED, all kinds of laboratory test equipment, standard signal generators, bridges, oscilloscopes, "Q" meters, etc.; send price and details to: ^[0037]

HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779.

WE buy for cash, new, used, radio, electrical equipment all types; specially wanted: radios, radiograms, test equipment, motors, chargers, rewind and complete. If you want to sell at the maximum price call, write or phone to University Radio, Ltd., 22, Lisle St., Leicester Sq., W.C.2. Ger. 4447.

REPAIRS AND SERVICE
Mains transformers rewound, new transformers to any specification.
MOTOR rewinding and complete overhauls; first-class workmanship, fully guaranteed.

F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham, Est. 1917. Tel. 3855.

REWINDS and conversions to mains and output trans., pick-ups, fields, etc., from 4/6
N. L. Rewinds, 4, Brecknock Rd., N.7. ^[4593]

LOUNDSPEAKERS and transformers rewound, cones replaced, prompt service.—Dodds Radio Service, 34a, Bullingdon Rd., Oxford.

RADIOS and televisions repaired, trade discount; assistance to home builders.—E. W. Shackie, High St., Harlington Haves Middx.



THE "FLUXITE QUINS" AT WORK

"What's this? A procession?" cried OH.

Yelled the lads in reply "Oh no!

We've tried 10 times to-night

To fix up—and FLUXITE,

But it's snow us in this blessed snow!

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all Iron-mongers—in tins, 10d., 1/6 & 3/-.

TO CYCLISTS! Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 2/6, or filled, 3/6



ALL MECHANICS WILL HAVE

FLUXITE

IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT" SOLDERING and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d. each.

FLUXITE LTD.

(Dept. W.W.), Bermondsey Street, S.E.1

CABINETS AND COMPONENTS



Receiver cabinets as illustrated. Beautiful walnut veneer. Size 12 1/2" x 8 1/2" x 7 1/2" deep. 35/-. We can construct any type or quantity of cabinets to specification. Send full details.

All components to construct a T.R.F. or Superhet Receiver in above cabinet are available. Lists on request.



4 1/2 Watt A.C. Quality Amplifier with negative feedback. From £5.4.7d. 5 Watt Universal similar to above from £3.16.2d. 12 Watt Universal from £8.5.0d. Full details on request.

LEWIS RADIO CO. (Dept. W.3.)
322, High Road, Wood Green,
LONDON, N.22
Phone: BOWes Park 5997

OPPORTUNITIES
IN RADIO

Get this FREE Book! "ENGINEERING OPPORTUNITIES" reveals how you can become technically qualified at home for a highly-paid key-appointment in the vast Radio and Television Industry. In 176 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of TELEVISION and RADIO, A.M. Brit. I.R.E., A.M.I.E.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.

We definitely Guarantee
"NO PASS—NO FEE"

If you're earning less than £10 a week, this enlightening book is for you. Write for your copy today. It will be sent FREE and without obligation.

BRITISH INSTITUTE OF
ENGINEERING TECHNOLOGY
388B SHAKESPEARE HOUSE
17 1/2 STRATFORD PLACE, LONDON, W.1

BIET

REPAIRS AND SERVICE

LOUDSPEAKERS.—Sinclair Speakers. Service Dept. temporarily closed, due to removal.—All correspondence to 3 and 4, Manor Way, Braham Wood, Herts. [4792]

MAIN and output transformers rewound to pattern or specification, return post service.—H. Puzhe, Radio Rewind Service, Brithdir, Nr. Dolgellau, N. Waes. [3243]

MAJNS transformers rewound or constructed to any specification; prompt delivery.—Bede Transformer Co. Ltd., Bedesway Estate Trading Estate, Jarrow. [3198]

MAJNS transformers rewound or constructed to any specification, prompt deliveries.—Avon Transformer Co., 20, Heath Terrace, Leamington Spa, Warwick. [4498]

REPAIRS to moving coil speakers, cones. To coils fitted, field rewound or altered; speaker transformers clock coils rewound; guaranteed satisfaction, prompt service.

L.S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting London, S.W.17. Balham 2559.

ALL types of ammeters, voltmeters, Avos, etc., repaired; quick, efficient service, estimates free.—Donvin Instrument Co., 91, Princedale Rd., London, W.11. Tel. Park 4469. [0059]

AREWIND service which duplicates or modifies as required; transformers, loudspeakers, etc.; prompt returns.—Raidis Services, 49, Lr. Addiscombe Rd., Croydon, Cro. 6537.

ELECTRICAL measuring instruments of every make repaired and standardised.—The Electrical Instrument Repair Service, 329 Kilburn Lane, London, W.9. Tel. Lad. 4168. [3715]

REPAIRS—E.H.T., mains and O.P. Transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification; all work fully guaranteed.

WILLEDEN TRANSFORMER CO., Ltd., 781, Harrow Rd., N.W.10. Tel. No. Ladbroke 2846.

SERVICE with a smile.—Repairs of all types of British and American receivers; coil rewinds; American valves, spares, line cord.—F.R.I. Ltd., 22, Howland St. W.1. Museum 5675. [1575]

RADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs; armatures, E.H.T. motors, vac. units, portable tools etc.; good deliveries.—139, Goldhurst Terrace, N.W.6. Mal. 6133. [9925]

"STURDY" rewinds, mains transformers, chokes, and fields, first-class work, prompt deliveries and satisfaction guaranteed.—Sturdy Electric Co., Ltd., Dinton, Newcastle-on-Tyne. [2430]

A SECOND-to-none rewind service, reliable, neat, return of post service; your television requirements promptly executed, E.H.T. LHT and heater transformers; stamp for quotations.—R. E. F. 1374, Ashton Rd., Oldham. [3519]

24-HOUR service, 6 months' guarantee, any transformer rewind, mains outputs and i.f.s., etc.; all types of new transf., etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 130, Windham Rd., Bournemouth.

LT.P. rewind service, all rewinds are layer wound, vacuum impregnated, pressure tested at 2,000volts and guaranteed for three months, 48-hour service.—Enquiries, London Transformer Products, Ltd. L.T.P. Works, Cobbold Estate N.W.10. Tel. Willesden 6486.

METROPOLITAN RADIO SERVICE for rewinds, mains and E.H.T. transformers, chokes and field coils; delivery 3-5 days; new transformers designed and manufactured ready or in quantities.—Metropolitan Radio Service Company, 1021, Finchley Rd., London, N.W.11. Tel. Speedwell 3000.

REWINDS.—Send your "burn outs" to be rewound; no technical data wanted; post transformer, etc. labelled with your name, address, and marked "for rewind"; our windings are double wound, interleaved and impregnated.—Southern Trade Services, Ltd., 297-299, High St., Croydon. Tel. 4870. [3110]

WORK WANTED

WE make wireless and radiogram cabinets for home and export, immediate delivery.—Radiac, Ltd., 89/90, Caledonian Rd., London, N.1. Tel. Terminus 7447. [8025]

SPECIAL receivers, test gear, electronic apparatus, experimental and design work.—If you have a problem which needs expert handling, write in first instance to J. Mort, B.Sc., A.M.I.E.E., BCM/HFIDEL, London, W.C.1.

DRAGHTING, tracing, and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications, sub-contracting work of this nature undertaken.

DRAWING & TRACING, Ltd., 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 7406. [4183]

FIRST-CLASS transformers and chokes manufactured, stock lines available; also special manufacturers' components made to specifications; armatures and fields wound and motors assembled.—Avis & Baggs, Ltd., 40-141, Friar St., Reading, Berks. [2715]

MISCELLANEOUS


WALNUT radiogram and television cabinets, manf.'s samples; few only; stamp details.—Walters, 501, Hale End Rd., E.4. [4857]

WALNUT radiogram cabinets, £18; new 12in speakers, 45/-; stamp details.—Cabinetware, Summit Works, Heves St., Blackburn.

RADIO and television cabinets made to individual requirements.—Sketch and details to Burman's, 64, Reighton Rd., London, E.5. [4735]

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A. G. Engraving 19a, Windmill Rd., London, S.W.18. Brass, bronze, erinoid, perspex, dials; one knob repetition equally entertained. [0054]

ALLEN COMPONENTS LTD.

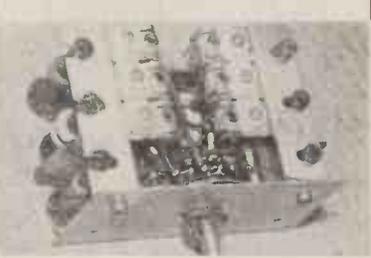

Type 300 3-wave band coil unit.

A reasonably priced assembly of exceptional performance consisting of switch, complete set of aerial and oscillator coils with all associated trimming and padding condensers. Improved aerial coupling system gives high sensitivity with exceptional discrimination against unwanted signals. A four position switch gives facilities for gramophone pick-up connection and RF muting. Suitable for use with any of the standard frequency changer valves and an IF frequency of 455Kc. Calibrated glass scale available.

Ranges: 16-50, 190-550, 800-2100 metres.
Type 300B: 11.0-26.0, 30-90, 190-550 metres.

Television: Scanning yokes, Focus coils, Line output transformers and EHT transformers approved for Electronic Engineering television.


ALLEN COMPONENTS LTD.

1, Shrewsbury Road, Stonebridge,
N.W.10

Telephone: Willesden 3675.

'Radiospares'
Quality Parts

**THE
SERVICE ENGINEER'S
FIRST CHOICE**

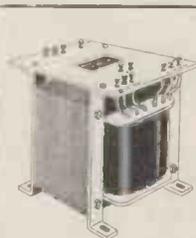

**HIGH-
CLASS
DESIGN.**

**VACUUM-
IMPREGNATED**


**TRANSFORMERS BY
MILLETT & HOLDEN LTD.,**
BIRCHAM WORKS, BIRCHAM ROAD,
SOUTHEND-on-SEA, Essex.
Southend 68409

BARKER AIMS AND ACHIEVEMENT

About this time last year we prepared to reduce our output and enter the back room for the summer recess; but to our confusion (and to our bank manager's joy) the plan had to be re-cast. Whether the financial results of Christmas were better than expected for many people; whether owners of 148As had invited many friends to hear Barker quality, or whether our January story was especially persuasive we shall never know. The fact remains that our postbag and sales shot up to new levels and have stayed there ever since.

One interesting point is that quite a fair proportion of our letters begin: "I am told . . ." or "I heard your 148A . . ." instead of "I read . . ." This means that our friends and our products are speaking for us as well as our advertisements and leaflets. Some of our friends are of course those enterprising dealers who realise that good quality sound is good business as well as an enlivening joy. Most, however, are owners of 148As who, like us, keep on getting thrills of pleasure at fresh revelations of what we aim at in

NATURAL SOUND REPRODUCTION

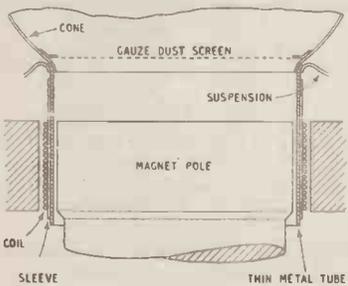

Let us re-state that aim at the start of a new year. It is to reproduce sound as naturally as possible by means of a simple and moderately priced electro-acoustic device. To that end we employ the exclusive patented Barker dual drive shown above, the special patented Barker cone with its logarithmically graded corrugations, high flux magnets, and lots of personal care at every operation from start to finish. We make every part we use except the magnet casting, nuts and bolts, and one disc suspension. Though we don't pay too much attention to spit and polish we do watch like hawks points affecting performance. Every Barker unit is a soundly made job and a precision acoustic reproducer. If your own ideals are in line with these, write for more information to:

**BCM/AADU
LONDON, W.C.1**

MISCELLANEOUS

REFLEX corner cabinets, Briggs design, 9 cubic ft. cement lined, density factor 5.—Particulars Hammonds, 97, Queens Rd., Nuneaton. Tel. Nuneaton 3007. [4891]

ALUMINIUM chassis and panels, any size manufactured quickly, holes punched for valve holders, etc., plain or cellulose finish.—E.A.D., 18, Broad Rd., Willingdon, Sussex.

ALUMINIUM alloy tubing all diameters, thicknesses and lengths, telescopic fitting, suitable television or radio masts; prices on application.—Bird, Surplus Stores, Milk St., B. [4814]

PE. exposure meter components.—Selenium light cell, 66; microamp meter movement, 10/6; Perspex case, 9/-; Ivorine conversion dials, 5/6; assembly instructions, 3/6; s.a.e. full details.

VACUUM and pressure impregnating plant (new), complete with 15in x 20in deep autoclave, vacuum pump, compressor, electric motors, tank, moisture traps, gauges, cocks, control gear, etc.—Box 1437. [4815]

FLUORESCENT lighting, 80 watt tapped brick choke, £10-24/0 a.c. with circuit, 17/9, or kit of parts less 5ft tube, 35/9; slim quick-start 40 watt ballast, 220-230V a.c. with holders, 47/6; list 1d s.a.e.—Malden Transformer Supplies, 200-202, Cambridge Rd., Nerriton, Surrey. [4038]

COPPER wires enamelled, tinned, Litz, cotton silk covered, all gauges; BA screws, nuts, washers, soldering tags, eyelets; ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod; headphones, flexes, etc.; latest radio publications, full range available; list s.a.e.; trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4. [1454]

3/6—For this modest sum we supply you with full constructional details for building our latest 10 watt quality amplifier with variable negative feedback; these constructional sheets are simplified so that the most inexperienced person may build and obtain first-class results. Complete Home Constructor's Handbook with circuit of this and many other sets, 1/- extra.—Supacols, Mail Order Office, 98, Greenway Ave., London, E.17. [4053]

BRITISH SOUND RECORDING ASSOCIATION—Membership is open to all professional and amateur recording engineers and high-quality reproduction enthusiasts. The official Journal, "Sound Recording," Vol. 5, Nos. 1-2-3 available at 2/8 post free. B.S.R.A. Diary for 1950 at 4/6 with eight pages of data on recording and reproducing topics, brochure and application form from Membership Secretary, Harrie J. King, 48, Mount View Rd., N. Chingford, London, E.4. [2119]

SITUATIONS VACANT
Vacancies advertised are restricted to persons or employments excepted from the provisions of the Control of Engagements Order, 1947.
CROWN Agents for the Colonies.

RADIO officer required by East Africa High Commission for Posts and Telegraphs Department for one tour of 48 months in the first instance; commencing salary according to age in scale £550, rising to £715 a year, gratuity of 13 1/4 per cent of total salary payable on satisfactory termination of contract; out of allowance £30; free messages; candidates, aged between 25 and 38, must possess Postmaster General's First Class Certificate of Competency in Radio Telegraphy, the equivalent certificate of the Air Ministry or the Ministry of Civil Aviation, or other equivalent Service qualifications, and have had considerable experience in the operation of medium and high-frequency radio stations; experience in the operation of modern radio and/or radar navigational aids and the day-to-day maintenance of modern radio equipment an advantage.—Apply at once by letter, stating age, whether married or single, and full particulars of qualifications and experience, and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M/N/25107 (3B) on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. [4786]

TESTERS, inspectors and faultfinders required: 5-day week, good prospects.
ACE RADIO, Ltd., Tower Works, Tower Rd., N.W.10, Willesden, 3304/5. [4774]

UNIVERSITY OF DURHAM, Medical School, King's College, Newcastle-upon-Tyne.

TECHNICIAN with practical experience in electronic engineering required for the laboratory of the department of surgery; applicants should be willing to work also in general biological research work; previous laboratory experience of this nature will be an advantage, but not essential as the necessary training could be provided; commencing salary within the range of £300 to £390 according to qualifications and experience; applications, together with the names of three persons to whom reference may be made, to be submitted to the undersigned not later than 15th February, 1950. [4635]

SERVICE engineers, radio, television, required by leading Bromley dealers; wages £6-£10 for qualified men.—Box 1472. [4848]

ENGLISH ELECTRIC VALVE Co., Chelmsford, require a young graduate engineer interested in micro-wave work on radio valves; interesting position with good prospects.—Write, giving full details, quoting Ref. 332, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., Westminster, S.W.1. [4821]

BAND SPREAD

by Armstrong
the **NEW**
EXP 119



This model has been produced after exhaustive investigation into the requirements of Overseas Listeners. Ease of operation on the short-wave bands high sensitivity and quality output have all been studied and incorporated in the EXP 119.

BRIEF SPECIFICATION

1. Designed specifically for the Overseas Listener.
2. 9 wave ranges. (6 bandspread and 3 general coverage) 11-570 metres.
3. High slope pentode R.F. stage.
4. 2 stages of I.F. amplification.
5. Variable selectivity.
6. Automatic noise limiter.
7. 10 watts push-pull output.
8. Separate A.C. power pack to facilitate operation from a vibrator if required.
9. 11 valve circuit (including cathode-ray tuning indicator).

Write now for fullest information.

Armstrong

THE CHASSIS PEOPLE

Armstrong Wireless & Television Co. Ltd.
Wariters Road, Holloway, London, N.7.
Telephone: NORTH 3213


SOLE BIRMINGHAM AGENT:

Hayes Company,
1 Alcester Rd., Moseley, Birmingham, 13.

SOLE AGENTS FOR

KENYA, UGANDA, TANGANYIKA & ZANZIBAR,
Messrs. Jennings & Fox (Mombasa) Ltd.
Kilindini Road, P.O. Box 56, Mombasa,
Kenya.

R.A.F. COMPUTER UNIT

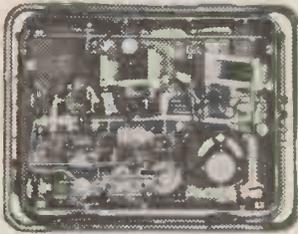

A WEALTH OF USEFUL PARTS FOR THE EXPERIMENTER AND MODEL BUILDER including GYRSCOPE, 2 x 27 VOLT MOTORS, 2 REV. COUNTERS, 25 GEAR WHEELS, WORM GEARS, RACK GEARS, etc., etc.

Carriage 5/- Extra.

50/-



4 - LIGHT FITTINGS
Adaptable for BED
WARMERS, FLOOD
LIGHTING, etc.

6/-

Send 1d. Stamp for Descriptive Leaflets
of this and other Bargains.
Large Range of Technical Books.

UNIVERSAL BAZAARS (M/c) Ltd.

8/10, Brown Street, Manchester 2. DEA 5009

ELECTRONIC & ELECTRO— MECHANICAL EQUIPMENT

developed for Industrial applications.
Reasonable charges.

SPENCER-WEST
QUAY WORKS, Gt. YARMOUTH

TRANSFORMERS & COILWINDERS

NEW AND REWINDS

All transformers interleaved & Impregnated
Tested for (1) Shorted turns. (2) Insulation
at 2 K.V. minimum. E.H.T. A SPECIALITY.
"E.E." MIDLAND SOUND & VISION COILS
19/6 SET. C.W.O.

J. E. THORNBUR & SONS

3 DEAN AVE. MANCHESTER 16

CHO 3849

EST. 1925

THE SOUND MAGNET TAPE RECORDERS

With the production of these wonder machines steadily
increasing, we are attacking the waiting list with all
possible vigour. Frankly admitting we are several
months behind our original schedules—the blame not
entirely ours—plans are now in operation to double
the weekly output, we thus hope to recover some of the
ground lost in 1949.

For information on this new method of Sound Recording
please write to Dept. S.M. Avoid telephone en-
quiries which result in lengthy descriptions, congest
our lines and delay our staffs in execution of their
all important duty of Production for Home and Export.
Printed literature will fully describe the SOUND
MAGNET RECORDERS.

GENERAL LAMINATION PRODUCTS LTD

"Winder House"

294 Broadway, Bexleyheath, Kent

SITUATIONS VACANT CROWN Agents for the Colonies.

WIRELESS station superintendent required by
Nigeria Government posts and telegraphs depart-
ment (for aeronautical wireless stations) for 18-
24 months with prospect of permanency; salary
according to age and experience in scale £660-
£850 a year (including expatriation pay); outfit
allowance £60; free passage; liberal leave; can-
didates must hold first-class radio-telegraph
operator's certificate, have had recent experience
in wireless operating and direction finding
apparatus, have thorough knowledge of trans-
mitters and receivers, and be capable of main-
taining (under an engineer's instructions) diesel
engine sets driving small generators.—Apply at
once by letter, stating age, whether married or
single, and full particulars of qualifications and
experience, and mentioning this paper, to the
Crown Agents for the Colonies, 4 Millbank,
London, S.W.1, quoting M.N/24044 (3B) on both
letter and envelope. The Crown Agents cannot
undertake to acknowledge all applications and
will communicate only with applicants selected
for further consideration. [4807]

THE UNITED LEEDS HOSPITALS

THE RADIOTHERAPY CENTRE at Leeds.
A TECHNICIAN with electronics experience is
required to assist in the construction and use
of apparatus for the measurement of the radio-
active content of the human body; the work is
being carried out on behalf of the Medical
Research Council, and the appointment will be
temporary in the first place; salary £350 p.a.;
application forms obtainable on written request
to the undersigned.

S. CLAYTON FREYERS, Secretary to the Board.
COSTING and progress clerk, with experience
of communication components, required.

WRITE to Managing Director giving experi-
ence, age and salary required.—Weymouth Radio
Mfg. Co., Ltd., Crescent St., Weymouth. [4797]

SERVICE mechanic required by leading deaf-
aid manufacturer.—Write in first instance,
giving details of experience and salary required
to Box 1534. [4899]

SERVICE engineer required with knowledge of
V.H.F.; must be capable of demonstrating
and servicing this type of equipment and free to
travel country with demonstration vehicle.

APPLY: Sales Dept., Eye Telecommunications,
Ltd., Newmarket Rd., Cambridge. [4805]

PILOT RADIO Ltd. requires immediately
fault finders and testers for radio and tele-
vision alignment; experienced in factory pro-
duction; five-day week with good rates of pay.
APPLY or write to Park Royal Rd., London,
N.W.10. [4517]

ENERGETIC progress man required for pur-
chasing department; experience essential
in radio and television.—Apply in person to
Scophony-Baird, Ltd., Lancelot Rd., Wembley,
Middlesex. [4827]

FERRANTI, Ltd., have vacancies in their radio
works, Moston, Manchester, for physicists
and engineers for research and development work
on vacuum and gas-filled electronic devices, as
follows:—

(a) SENIOR development engineers, qualifica-
tions include a good degree in physics or elec-
trical engineering and extensive experience in a
responsible capacity in the electronics field.

(b) DEVELOPMENT engineers; qualifications
include a good degree in physics or electrical
engineering or suitable extensive experience in
electronics.

SALARY on a liberal basis, according to qualifi-
cations and experience; the company has a
staff pension scheme.

APPLICATION forms from the Staff Manager,
Ferranti, Ltd., Hollinwood, Lancs. [4806]

APPOINTMENTS are invited for the following
appointments concerned with the build-up
of a new extension of the Research Laboratories
of the General Electric Co., Ltd., in the Stan-
more (Middlesex) area.

(a) SENIOR Mechanical Engineer, to take
charge of a Research Group in the field of special
mechanisms; experience in the theory and design
of servo devices, high efficiency gearing and
modern forms of light constructional methods is
essential; the applicant is expected to contribute
to the build-up of a mechanical laboratory,
which will be an important part of a new or-
ganisation to deal with a number of major pro-
jects.

(b) SENIOR Mathematician to take charge of
the mathematical work of the new laboratory;
a first-class mathematical background is required
together with experience in the theory of com-
puting and control systems involving both the
electrical and mechanical aspects.

(c) A NUMBER of Senior positions requiring ex-
perience in one or more of the following fields:
(i) microwave circuit design and measurements,
including wave guides and concentric lines; (ii)
the design of microwave aerial systems; (iii)
intermediate frequency amplifier design; (iv)
special engineering problems associated with
compact lightweight equipment.

(d) TWO Mathematicians, with good Honours
degrees and preferably with practical experience
of the application of mathematical methods to
electrical and mechanical problems.

(e) A NUMBER of vacancies for men qualified in
various electronic and mechanical fields includ-
ing (i) experimental work on and design of
microwave equipment; (ii) video frequency and
special waveform generating circuits; (iii) inter-
mediate frequency receiver design; (iv) servo-
control and computing circuits; (v) experimental
and design work on light mechanical engineering
problems.

APPLICATIONS should be sent to the Personnel
Officer, Research Laboratories of the General
Electric Co., Ltd., North Wembley, Middlesex,
and should contain full details of qualifications,
experience and age. [4802]

DUKE AND CO. OFFER THIS LOT FOR ONLY 7/6

CONDENSERS: 21 asstd.; paper tubular, 13 asstd.;
mica .18 asstd.; mica wax. 2 x 30 uuf (postage
stamp) trimming condensers, 9 concentric can (mainly
30 uuf), 1 splittater air cond.; and 2 two gang or 1
four gang variable cond. RESISTORS: 45 asstd.,
fixed, 5 variable potentiometers. R.F. COILS:
6 assorted. METER RECTIFIERS: 2.5 mA. TRANS-
FORMERS: 3 (465 kc/s) I.F. transformers, 1 output
trans.; 1 mica unit trans.;
OCTAL VALVE BASES: 13. VALVE CAPS: 5.
SLOW MOTION DRIVES: 2 (with 5" Ret Frequency
settings). CONTROL KNOBS: 5. SPRING LOADED
TERMINALS: 3 (insulated, 2 earthed). SWITCHES:
Yaxley type, 3 (2 rotary, 1 toggle). JACK PLUG
SOCKETS: 1. VARIABLE COIL VARIOMETER,
including rev.; counter coil and silver contacts. Com-
plete except for coil winding. Plus rack chassis and
case. This 22 set (TRANSMITTER RECEIVER) is
partly stripped, leaving the maximum of the above
good. THIS IS VALUE FOR MONEY.
SEND 7/6 and 2/- post and packing for this BARGAIN

OTHER BARGAINS. PRE-U.F. AMPLIFIER,
takes one EF30, is ideal for television or short-wave
rain stage, 2/6, post 6d. CONDENSER, 0005 mfd.
SLOW MOTION dial, complete, 3/-, post 6d. 0005
single, 2/2; 0005 two gang, 4/6; 3 gang, 2/6.
CRYSTAL SETS. Complete in bakelite cabinet, 7/6
each, post 6d.

VALVES All types in stock.
TELEVISION, 9in. white plastic escutchion, 2/6, post
6d.

HEADPHONES. New condition, low resistance,
2/6. High, 4/6.

INDUCTION MOTORS. 200/250 v. A.C. for milk shakes.
Complete with long spindle, runs smooth and silent,
small, 17/6, plus post 1/-.

NEW AND IMPROVED KIT. A 3-valve T.R.F.
2-wave band receiver. All parts including a smart
walnut, bakelite cabinet. Complete kit, £4/19/6.
Ivory cabinet available, 6/- extra.

TELEPHONES. Complete, dial system, G.P.O.
pattern, 15/- each, 25/- pair, plus 2/6 post.

Send stamps only for lists. TRADE ENQUIRIES INVITED,
219, Ilford Lane, Ilford, Essex. ILFord 0295.

EXPORT ENQUIRIES INVITED.

FOR DISPOSAL CATHODE RAY TUBES

Type 4/3 VCR 138

packed in each
original crate £1 Carriage Paid

The J. J. TRADING CO.,
Gatwick Airport, Horley, Surrey.

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE.
3,000 STANDARD STOCK SIZES


No Quantity too Small List on application

London: H. ROLLET & Co., Ltd. Liverpool:
6, Chesham Place. S.W.1. Kirkby Estate,
SLOane 3463 SIMONSWOOD 3271/3

ENGINEERS!

Whatever your age or experience, you must read
"ENGINEERING OPPORTUNITIES". Full details of
the easiest way to pass A.M.I.Mech.E., A.M.I.E.E.,
A.M.I.C.E., CITY & GUILDS, M.A.T.R.I.C., etc. on

176 PAGES
Free!

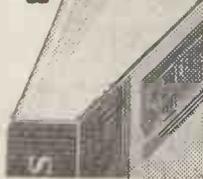

"NO PASS—NO FEE"
terms and details of
Courses in all branches
of Engineering—
Mechanical, Electrical,
Civil, Auto., Aero-
Radio, etc., Building,
etc. If you're earning
less than £10 a week, tell
us what interests you
and write for your copy
of "ENGINEERING
OPPORTUNITIES"
today—FREE!

B.I.E.T.
377, Shakespeare Hse.,
17-19, Stratford Place,
London, W.1.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

L.R.S.

**FOR
PROMPT & EFFICIENT SERVICE
CASH OR EASY TERMS**

When you purchase on L.R.S. Convenient Terms. Formalities are reduced to a Minimum and you deal direct with us from beginning to end.

ARMSTRONG ALL WAVE CHASSIS (incl. speaker and output transformer)

Model EXP/83/3. Cash price £18 17 1, or £4 12 0 with order and 12 monthly instalments of 26/-.

Model RF103/3. Cash price £26 10 0 or £4 12 0 with order and 12 monthly payments of £2 0 0.

All other Armstrong Chassis are available on similar terms.

Also available on Easy Terms

GOODSELL-WILLIAMSON

AMPLIFIER and TUNER UNITS

COLLARO RADIOGRAM UNITS and RECORD CHANGERS

LEAK TUNERS and AMPLIFIERS

GRAMPHON SOUND EQUIPMENT

SOUND SALES AMPLIFIERS and TUNERS

A.C. BARKER'S LOUDSPEAKERS

GOODMAN'S LOUDSPEAKERS

Axiom 12 and 22 also 12" Standard Unit

HARTLEY-TURNER LOUDSPEAKERS

WHARFEDALE LOUDSPEAKERS

ATLAS BATTERY CHARGERS

and most of the other High-Grade Equipment advertised in "Wireless World".

Also REMINGTON FOURSOME ELECTRIC SHAVERS

Please let us know your Radio requirements (enclosing 2/6 stamp) and we shall be pleased to quote.

Personal attention to all enquiries


THE LONDON RADIO SUPPLY CO.

Estd. 1925

BALCOMBE, SUSSEX

RELAYS

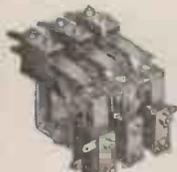for A.C. and D.C. 2VA Coil consumption from 2 to 600 volts and tested to 2000 volts. Aerial Changeover Relays, Mercury Relays, Measuring Relays and Time Delay Relays,



Midget Relay ML1C

Ask for leaflets RE/WV

LONDEX LTD

Manufacturers of Relays
07 ANERLEY ROAD, LONDON, S.E.20
SYDenham 6258

SITUATIONS VACANT

REQUIRED, a live man to be responsible for design and production of all types of radio interference components; full details of exp. etc. to—Box 1462. [4840]

APPPLICATION engineer required by H.F. induction heating equipment manufacturers. London area; duties consist in experimental work to be carried out in connection with customers' enquiries.—Write Box 1435. [4808]

APPPLICATIONS are invited from qualified television engineers to control central service station in executive capacity; must have good technical and administrative experience; write giving full details to—Box 1441. [4833]

TELEVISION/RADIO service engineer, fully experienced and able to drive; permanent position with excellent opportunities; full particulars and salary required to—W. J. Elliott, Ltd., Howardsgate, Welwyn Garden City, Herts. [4816]

DRAUGHTSMEN required by firm in Middlesex; experience in electrical circuits, telephony and light current apparatus essential.—Write particulars of age, experience and salary required Box 62, W. H. Smith & Son, 283, High St., Dorridge. [4816]

TELEVISION engineer required by sole Murphy dealer, Reading, also H.M.V., Pye, etc., must be to first-class technical standard, and have had pre-war experience of television.—Barnes & Avis, Ltd., 140/141, Fries St., Reading. [4822]

ELECTRONIC engineers required for interesting and progressive work in design and development; qualifications: degree or equivalent in electrical engineering or physics plus actual design experience in one of the following or allied fields:

- (1) Household appliances.
- (2) Small electric motors.
- (3) Power supply unit for airborne radio equipment.
- (4) Recording equipment (disc, film or tape).
- (5) Radio components and transformers.
- (6) UHF oscillator and aerial design.
- (7) Radar and television equipment.

APPPLICANTS should write, giving full details.—Personnel Department, M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. [4838]

RADIO engineer required for development of radio. U.H.F. communication receiver development and television components; apply giving full details of experience to—Personnel Department, E.M.I. Factories, Ltd., Blyth Rd., Hayes, Middx. [4838]

DRAUGHTSMEN required by company manufacturing radio communication equipment in S.W. London; experience in diagrams, mechanical design, etc. essential; good working conditions; remuneration up to £400 per annum, depending on experience or qualifications. [4791]

ENGINEERS required for servicing radar equipment; technical qualifications: Higher National certificate or degree, previous experience on electronic or radio equipment; commencing remuneration up to £400 per annum, depending on experience or qualifications.

APPLY Construction Department, The British Thomson-Houston Co., Ltd., Rugby. [4652]

Public A. engineer required, fully qualified and of smart appearance; experienced in installation and maintenance work; write stating age, experience and salary required to British Relay Wireless, Ltd., Public Address Department, 343/4 Weymouth Rd., London, S.E.17. [4778]

REPRESENTATIVE having really good connections with and at present selling to radio and electrical and/or motor traders, required by old-established electrical manufacturer to offer attractive non-competitive lines on liberal commission basis.—Box 1440. [4825]

MECHANIC required for the construction and servicing of industrial electronic apparatus, maintenance of mechanical transducers, etc.: West London area; forward full details of education, experience and salary required to—Box A.C.761, c/o Central News, 17, Moorgate, London, E.C.2. [4680]

FOREMAN with not less than 5 years of transformer winding and assembly experience for radio components, etc.; experience of A.I.D. specifications an advantage.—Write to Marketing Director, giving experience, age and salary required, Weymouth Radio Mfg. Co., Ltd., Crescent St., Weymouth. [4796]

CHIEF engineer required to take charge of small laboratory at radio manufacturers in N.E. London; must have good technical ability in design of R.F. test equipment and radio components.—Write, giving full particulars of qualifications and experience, stating age and salary required, Box 1410. [4827]

BEST engineers for high-grade communication equipment; should have experience of testing low power transmitters and/or H.F. and V.H.F. receivers and transmitter receivers; applicants should be prepared to work in East London area.—State full details, including age and salary required to Box 1456. [4813]

TELEVISION engineer required urgently; must be fully qualified and capable of dealing with television sales, installations and servicing; living accommodation available if desired, good wages and prospects for the right man.—Apply with particulars to Chas. J. Fox Plano Co., 16, Frenchgate, Doncaster. [4867]

WELL-KNOWN electrical manufacturing company requires sales representatives for Birmingham and London area; applicants, who must be electrical engineers, experienced on outside sales of industrial electronic or similar equipment, should write giving full particulars, quoting Ref. 727, to Box 1434. [4804]

WANTED, radio and television engineer qualified capable of controlling service dept., able to drive a car and willing to take Murphy Television course; organising ability necessary; permanent position and good prospects for suitable man.—Write, W. L. & F. M. Jones, Ltd., Cobham, Surrey. [4798]

GALPINS

ELECTRICAL STORES

408, HIGH ST., LEWISHAM, LONDON, S.E.13

Telephone Lee Green 0309. Near Lewisham Hospital

**TERMS: CASH WITH ORDER.
NO C.O.D.**

MAINS TRANSFORMERS, input 200/250 volts in steps of 10 volts, output 425/0/425, 150 mA., 6.3 volts 3 amp. twice, 5 volt 3 amp. (Williamson amplifier), 39/6 each. Another (Electronic Engineering) output 350/0/350 volts 300 mA., 4 volt 8 amp., 4 volt 4 amp., 6.3 volt 6 amp., 6.3 tapped 2 volt at 2 amps., 57/6 each. Another, 350/0/350 volts 180 mA., 5 volt 3 amps., 6.3 volts 4 amp., 4 volts 4 amp., 37/6 each. Another, 500/0/500 volts 150 mA., 4 volt 4 amp., 5 volt 3 amp., 6.3 volt 4 amp., 42/6 each.

EX-R.A.F. ROTARY CONVERTORS, 100 volts D.C. input, 50 or 100 volts, 500 cycles, 1 phase at 300 watts output, 82/6 each, carriage paid.

SWITCHBOARD AMPMETERS, 4 1/2 in. 0-14 amps. AC/DC, 25/- each.

ISENTHAL MAINS VARIABLE DIMMER RESISTANCES. W.W. control 60 ohms, max. 2 1/2 amps., as new, 27/6 each. Ditto Zenith slider variable resistances, protected type, 1,500 ohms to carry 0.45 amps., 32/6 each.

EX-R.A.F. CRYSTAL MONITERS, less crystal and valves. These units contain many useful parts, Transformers, Condensers, Resistances, etc., the basis of a Midget receiver all contained carrying case (new), to clear, 5/- each, carriage paid.

POWER TRANSFORMERS. Auto Wound Voltage changer tapped 0, 110, 150, 190, 230 v. to carry 1,600 watts, £5/5/-. Ditto, 2,000 watts, £6/5/-. Another of a 1,000-watt rating with a range of 32 various tappings from 5 to 230 v., including 110 v. All tappings at a 1,000-watt rating, £5/15/- each. Another 115 to 230 v. or vice versa at 1,000 watts, £4/15/-. Another, double wound, 4,000 watts, 130 to 250 v. or vice versa, weight 100lb., £10 each, carriage paid.

D.C. MOTORS 110/220 v. rated at 1/12th h.p. with laminated fields suitable when fields re-wound for A.C. Mains, 22/6 each. Another 110 v. approx. 1/4 h.p. D.C. only shunt wound, 10/- each. A.C. Motors name plate reads 230 v. 50 cys. 1 ph. 180 r.p.m. 5 output leads connections not known. Sold as rewinds, 50/- each.

MAINS TRANSFORMERS. 230 v. input 50/1 outputs 3 X 4 volt windings at 4/5 amps., 15/- each, post 1/-. Another 230 v. input with 2 X 6.5 volt windings at 5 amps., 15/- each. Another 230 v. input 12 v. at 12 amps. output, 30/- each.

MAINS TRANSFORMERS (Auto Wound). Voltage Changers tapped 10, 20, 25, 90, 130, 150, 190, 210 and 230 v., all at 1,000 watts, a combination of 24 voltages can be obtained from this transformer, new ex-Government Stock, £5/10/- each, carriage 5/-. Mains Booster Transformer, tapped 0, 6, 10, 19, 175, 200, 220, 225, 240 and 250 v. at 1,500 watts (new ex-Government), £5/5/- each, carriage 5/-. Another Auto Wound, tapped 0, 110, 150, 190, 210 and 230 v. at 1,500 watts, £6/10/- each, carriage 5/-. Ditto, 2,000 watts, £7/5/- each, carriage 5/-.

MAINS TRANSFORMERS, input 200-250 v., 50 cycles, in steps of 10 v. Output 450/0/450 v. 250 mA., 4 v. 4 a., 5 v. 4 a., 6.3 v. 8 a., 6.3 v. 8 a., 62/6. Ditto 450/0/450 v., 250 mA., 6.3 v. 4 a., 5 v. 4 a., 4 v. 8 a., 4 v. 8 a., 60/-.

Another 500/350/0/350 500 v. 250 mA., 6.3 v. 8 a., 0, 4, 5 v. 4 a. twice, 6.3 v. tapped at 2 v. 2 a., 67/6.

Another 350/0/350 v., 300 mA., 4 v. 8 a., 4 v. 4 a., 6.3 v. 4 a., 6.3 v. tapped 2 v. 2 a., 57/6.

Another 500/0/500 v. 300 mA., 6.3 v. 8 a., 6.3 v. 8 a., 6.3 v. 4 a., 4.4 a., 5 v. 4 a., 67/6.

PRE-PAYMENT 1/2-SLOT ELECTRIC LIGHT CHECK METERS, 200/250 volts 50 cys., 1 ph., 2 1/2 amp. load, 30/- each, carriage 3/6; 5 amp. load, 35/-, carriage 3/6. 10 amp. load, 42/6 each, carriage 3/6.

MAINS TRANSFORMERS. 230 v. input, 300 v. 150 mA. C.T. 6.3 v. 8 amp., 5 v. 2 amp., 15/- each.

ELECTRIC LIGHT CHECK METERS (watt hour type), all for 200/250 volt A.C. 50 cycles, all electrically guaranteed: 2 1/2 amp. load, 15/- each; 5 amp. load, 18/6 each; 10 amp., 21/-; 20 amp., 25/-; 30 amp., 30/-; 40 amp., 35/-; 50 amp., 42/6; 100 amp., 50/-. Carriage on all types 2/- extra.

B. & H. RADIO

BASS & TREBLE SEPARATOR
kit of parts £1 9 6

SCRATCH FILTER
Gives a marked reduction of scratch level without serious effect on treble response 15 0

VARIABLE SELECTIVITY I.F. TRANS.
465 kcs. Gives 3 degree of selectivity per pair £1 0 0

tone CONTROL UNIT
To connect to any equipment and gives independent control of bass and treble £4 10 0

MAINS FILTERS.
To eliminate mains borne interference. The four chokes are dust iron cored and the condensers are 1 KV. wkg. Cases are metal with inlet and outlet bushes 17 6

**B. & H. RADIO
EAST STREET,
DARLINGTON.**

TELEVISION CONSTRUCTORS!

E.E. Telesvisor Demonstrated Daily
MIDLAND CONSTRUCTORS ETC.
ARE INVITED TO SEND FOR OUR COMPLETE COMPONENT LIST AND TAKE ADVANTAGE OF OUR PROMPT POSTAL SERVICE

J. T. FILMER MAYPOLE ESTATE, BEXLEY, KENT. Tel. Bexleyheath 7267

LOCKWOOD

makers of
Fine Cabinets

and woodwork of every description for the Radio and allied trades

LOCKWOOD & COMPANY
Lowlan's Road Harrow, Middlesex. Byron 3704

WILCO ELECTRONICS

RACKS P.O. Standard 19in., with heavy angle iron base, 5ft. 60/-; 6ft. 70/-; 5ft. 6in. Lighter Type 50/-

POWER UNITS. 19in. Rack Mounting, panel 19in. x 10 1/2in., input 200-250 v., 50 cys., output 280-0-280 v. at 190 mA., 6.3 v. at 9A., 5 v. at 2A. Complete with choke, condensers, D.P. mains switch, indicator lamp, Bulgin connector, SU4G Rect. and Cover, £3/17/6.

RECEIVERS, TYPE W.5737. 1-10 M/c.s. 5 valves, less power pack, but complete with valves, £3 each.

WAVE-FORM GENERATORS, Type 37 complete with 6 valves, less power pack, 50/- each.

OPERATOR'S DESKS, rack mounting, standard 19 ins. 12 ins. deep, 15/- each.

CO-AX CABLE. 60-70 ohm, 10 1/2 d. per yd.

SPEAKERS P.M. 8in. Tannoy with trans., 21/- 5in. Rola less Trans., in case, 17/6.

CONDENSERS. Paper 8 m.f.d., 750 v. D.C. working, 10/6 each. 4 m.f.d. 750 v. D.C. working, 4/6 each.

Vibrators. Non Synch., 6 v. types, 5/6 each.
AMPLIFIERS. Push-pull. PX25s 15 watts output. Complete with Power Pack, less valves, Rack mounting, £6, carriage extra.

204 LOWER ADDISCOMBE ROAD, CROYDON
ADD. 2027

SITUATIONS VACANT

IN any grade or capacity there is usually a job for the right man at Sound Sales, Ltd.; applicants, who should be of British origin, should state age, details of experience, salary or wage required, by letter; testimonials should not be forwarded with inquiry; previous factory experience essential.

THE Managing Director, Sound Sales, Ltd., West St., Farnham, Surrey. [10054

INTERNATIONAL AERADIO, Ltd., have vacancies Bovingdon Airport for ground radar engineer at £450-£500 per annum and model shop fitter/mechanic, capable making tools and chassis at £358 per annum; single accommodation; travel, pensions fund.—Write: Senior Admin. Officer, 40, Park St., W.1. [4828

MECHANIC required to assist with the construction of scientific apparatus; bench work, fitting, assembly, drilling, turning etc., some electronic knowledge; age and salary £250-£350 according to age and experience; application with three references to—The Physician Superintendent, Crichton Royal Mental Hospital, Dumfries. [4829

LEADING radio manufacturers require technical assistant, London area; position may lead to assistant to service manager; experience in current radio practice, including car radio, familiarity with business methods, including correspondence, and a good academic background are the main qualifications; salary according to experience, which must be stated in full to Box 1438. [4817

PHYSICIST or engineer, age 23-28, required for interesting development work on gramophone pick ups and other radio experiments; qualifications: degree or equivalent plus actual design experience; experience on pick ups would be an advantage; write giving full particulars to—Personnel Department, E.M.I. Engineering Development, Ltd., Blyth Rd., Hayes, Middx. [4839

ENGLISH ELECTRIC require senior and junior instrument draughtsmen for interesting work at Stafford; work covers prototype design and layout of electric meters, instruments and similar devices.—Applicants should write, giving full details of training and experience, quoting Ref. 122, to Central Personnel Services, English Electric Co., Ltd., 24, Gillingham St., Westminster, S.W.1. [4855

MARCONI'S WIRELESS TELEGRAPH Co., Ltd., require research laboratories for Chelmsford, senior and junior research and development engineers for domestic television receivers; applicants, who must have had extensive experience in television receivers, should write giving full particulars quoting reference 266 to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [4851

SENIOR and junior development engineers and draughtsmen for radio, radar, electronics, etc.; service engineers, radio, television (London and Birmingham) radar, electronics, wiremen (skilled and semi-skilled), radio radar, etc.; H.F. repairers, testers, inspectors, assemblers for radio, television, radar, P.A.; numerous other senior and junior positions vacant.—Technical Employment Agency, 179, Clapham Rd., S.W.9 (Brixton 3487). [4858

MARCONI'S WIRELESS TELEGRAPH Co., Chelmsford, require a senior engineer to take charge domestic television receiver research and development; applicants with extensive experience in this class of work and with a capacity to lead a development team should write giving full details of previous experience, quoting Ref 286 to—Central Personnel Services, English Electric Co., Ltd., 24, Gillingham St., Westminster, S.W.1. [4826

APLICATIONS are invited for the position of lecturer in radio engineering at Marconi College, Chelmsford; applicants must be of degree standard either in engineering or physics, and preference will be given to those possessing a good radio background either in a technical or service capacity; write in confidence, giving full details of previous experience, quoting Ref. 260, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St. Westminster, S.W.1. [4858

AN assistant to the chief development engineer is required by large company manufacturing radio components and allied products; applicants must have technical education to B.Sc. in electrical engineering or physics and must have experience of development work in the radio field; a permanent and progressive position can be offered to an applicant with these qualifications and between the age of 30 and 35 years.—Kindly state fullest details in strict confidence to Box 1498. [4852

VACANCIES exist in the Nelson research laboratories of the English Electric Co., Ltd., Stafford, for senior and junior physicists and engineers for work in the vacuum physics laboratory; a degree in physics or engineering essential, and preference will be given to men experienced in electron optics and vacuum techniques.—Write giving full details, quoting Ref. 308, to Central Personnel Services, English Electric Co., Ltd., 24, Gillingham Street, Westminster S.W.1. [4854

THE south-western division of a leading radio company invite applications for the post of chief draughtsman; applicants should have qualifications to A.M.I. Mech. E. in electrical engineering or equivalent and have had not less than two years experience of senior responsibility in a drawing office concerned with layout and detailing of radar equipment, electronic apparatus and small mechanisms; salary will be commensurate with qualifications and experience, and housing accommodation can be made available to successful candidate; entry into pension scheme is offered after a period of service; full details in writing to be made within 7 days of the appearance of this advertisement.—Box 1439. [4820

**100 kcs.
QUARTZ
CRYSTAL
UNIT**
Type
Q5/100



for Secondary Frequency Standards

★ Accuracy better than 0.01% ★ Temperature coefficient 2 parts in a million per degree Centigrade temperature change. ★ Gold electrodes applied by cathodic sputtering direct to the faces of the crystal, giving permanence of calibration. ★ Simple single valve circuit gives strong harmonics at 100 kcs. intervals up to 20 Mcs. ★ Octal based mount of compact dimensions. PRICE 45/- Post Free

Full details of the Q5/100 including circuit are contained in our leaflet Q1. Send stamp to-day for your copy.

THE QUARTZ CRYSTAL Co., Ltd.

63-71 Kingdon Road,
NEW MALDEN, SURREY
Telephone: MALden 0334

**INSTRUMENT WIRE
ENAMELLED, D.C.C. SILK COVERED,
ETC.** All sizes from 10 s.w.g. to 42 s.w.g. in stock. **INSULATING MATERIALS,** Empire cloth, leatheroid, paroxin, sleeving etc.

Send S.A.E. for list to
STAN. HOLT,
349, HIGH ST. SMETHWICK, STAFFS
Telephone: WOODGATE 3789

**COPPER WIRE AND INSULATION
MATERIALS, ETC.**

Most gauges in stock, Leatheroid, Fibre, Mica, Varnish, etc. Also many other Radio, Electrical and Mechanical bargains at attractive prices. **ELECTRIC MOTORS FOR SALE, ALL AT BARGAIN PRICES.**

Send S.A.E. for List.
**L. C. NORTHALL, 18, Holly Road, Quinton,
Birmingham, 32. Telephone: WOO. 3166**

HILL & CHURCHILL LTD.

**BOOKSELLERS
SWANAGE, DORSET**

Available from stock

- "Radio Physics Course"—Ghirardi ... 37/6
- "Fields and Waves in Modern Radio"
—Whinnery 33/-
- "Radio Engineering"—Fink 42/-
- "Ultra-High Frequency Techniques"
—Brainerd 28/-
- "Inside the Vacuum Tube"—Rider ... 30/-
- "Radio Receivers and Transmitters"
—Amos & Kellaway 25/-
- "The Amplification and Distribution
of Sound"—Greenlees 16/-

Postage Extra

CATALOGUE ON APPLICATION

Pennine RADIO



AUDIO SIGNAL GENERATOR

- HIGH STABILITY
- WIDE RANGE 40-16000 C.P.S.
- LOW PRICE
- 3 WATTS OUTPUT

LIST PRICE **£9-9-0**

Write for Particulars
PENNINE AMPLIFIERS
 SOUTHGATE, ELLAND, YORKS, ENG.
 Tel.: Elland 2107

SOUTHERN RADIO'S WIRELESS BARGAINS

T.R. 1198. Six valve Super-hot Receivers. Complete with Circuit, 22/6.
CRYSTAL MONITORS. Complete in case, less Crystals, 6/-. With two crystals, 16/6.
CRYSTALS. American and British 2-pin types from 2040 kcs. to 38 mcs., 6/- each. Twelve assorted frequencies, 60/-.
SECTIONAL AERIALS. 8ft. interlocking, 3/6. Base for same, 2/6.
BENDIX COMMAND RECEIVERS. B.C. 454 (49-100 metres), B.C. 455 (33-49 metres). Complete with six valves, 35/-, plus 1/6 postage. A few only converted to 28-41 metres for television sound, 50/-.
CONTROL BOXES, for B.O. 453/4/5. Complete with slow motion dials, Volume Controls etc., 13/6.
TRANSMITTER-RECEIVERS. Type 38, Mark I. Complete in original cartons with Vibrator Pack, Batteries etc., £19.
R.A.F. BOMBIGHT COMPUTERS. Complete with Motors, Gyro, Gears, Blowers etc., etc., 55/-, plus 5/- carriage. The best component value ever offered.
INDICATOR UNITS. 299a. Complete with 7 valves C.R. Tube, 3BP1 and all components in metal case. Ideal for Oscilloscope conversion, 44/-, plus 5/- carriage.
CONTACTOR TIME SWITCHES, by Smith or Verner 10-hour movement with thermostatic control. Complete in sound proof case, 10/-, plus 1/4.
RADIO COMPASS INDICATORS, with Selayn motor, 3in. dial, 360 degrees, 13/6.
ROTOTHERM METERS. Chromium finish, 6/-.
BRAZING LAMPS. 5-pint size with extension hose and nozzle, 40/-.
ALDIS LAMPS. 6in. lens. Complete in transit case with spare bulbs, cable etc., 40/-, 8smaller size for signalling. Complete in metal case with tapper etc., 15/-.
DELCO HAND GENERATORS. 6 volts at 4 amps complete ready for use, 17/6.
LUGAS GENERATORS. 12 volt input to 480 volts D.C., 10/-.
SLEEVING. 1 mm. and 2 mm., 6/- gross yards. Minimum quantity one gross.
LUFBRA HOLE CUTTERS. Adjustable from 3in. to 3 1/2in. For use on wood, metal, plastic etc., 5/6.
WESTECTORS Wx5 and W12, 6/4 per dozen. Thousands of bargain lines for Gallers. All goods unconditionally guaranteed. Please send 2/4d. for full publication list.

Southern Radio Supply Limited
 46, LISLE STREET, LONDON, W.C.
 GERrard 6653

SITUATIONS VACANT
DRAUGHTSMEN required, to form the nucleus of a special section to produce ideas and design and develop small mechanisms and movements for mass production, associated with all phases of the radio, television and acoustic products of the company.—Reply, stating age, full details of experience and salary required, to Personnel Department, E.M.I. Ltd., 47th Rd., Hayes, Middx. [4784]

TECHNICAL assistant required in patent department of company engaged in the manufacture of precision instruments, radar, etc.; knowledge and experience of electronics and DHP technique required and experience of patent work according to qualifications and experience. Write stating age, experience, etc., to Personnel Manager, Sperry Gyroscope Co. Ltd., Great West Rd., Brentford, Middlesex.

VACANCIES exist at the Nelson Research Laboratories, English Electric Co., Ltd., Stafford, for draughtsmen. Applicants must have had experience of electronic circuit of similar work and preference will be given to those interested in electronic circuit development; salary in accordance with age, qualifications and experience.—Write giving full particulars, quoting reference 109, to Central Personnel Services, English Electric Co. Ltd., 24-30 Gillingham St., Westminster, S.W.1. [4654]

ENGLISH ELECTRIC invite applications from University-trained electronic engineers with radar experience covering centimetre aerials, wave guides and receivers; circuit and general electronic experience essential; interesting work near London for which a salary of £850 per annum upwards will be paid for a senior man according to qualifications and experience.—Write, giving full details, quoting Ref. 326, to Central Personnel Services, English Electric Co. Ltd., 24-30, Gillingham St., Westminster, S.W.1.

ENGLISH ELECTRIC invite applications from electrical engineers for appointments in the high voltage section of the Nelson Research Laboratories, Stafford; applicants should have a sound knowledge and experience of H.V. problems and heavy electrical equipment; a degree in electrical engineering is desirable and applicants must be interested in research and development.—Write, giving full particulars, quoting Ref. 229, to Central Personnel Services, English Electric Co. Ltd., 24-30, Gillingham St., Westminster, S.W.1. [4811]

ELECTRONICS Engineer.—Applications are invited for the position of Instrument Engineer (Electronics) in a large iron and steel works plant in this country. Candidates will be required to undertake the original design and development of electronic apparatus and its application to works problems. Previous steelworks experience is not essential but initiative and technical ability are considered of first importance. A substantial salary will be paid to the suitable applicant.—Replies giving details of experience to Box 1032. [4705]

ENGLISH ELECTRIC require a senior circuit engineer (electronics) for the Nelson Research Laboratories at Stafford. Applicants must hold a university degree or Associate Membership of the Institution of Electrical Engineers, have had two or three years' industrial experience, and be interested in the development of electronic circuits. The work will involve design of special circuits.—Write, giving full particulars, quoting reference 313, to Central Personnel Services, English Electric Co. Ltd., 24-30, Gillingham St., Westminster, S.W.1. [4650]

ELECTRICAL engineers for appointments at their Nelson Research Laboratories, Stafford; applicants should have a sound knowledge of heavy electrical engineering, and experience in the operation and maintenance of heavy electrical plant; a degree in electrical engineering is essential, and an interest in development desirable; successful candidates will be required for special duties in connection with short circuit testing.—Applicants should write, giving full information, quoting Ref. 299, to Central Personnel Services, English Electric Co. Ltd., 24-30, Gillingham St., Westminster, S.W.1. [4810]

CINEMA-TELEVISION, Ltd.—Applications are invited from television development engineers for positions in a new section now being formed; applicants should have several years television circuit development experience in one or more of the following fields: (a) timebase and scanning equipment, (b) vision and sound receivers, (c) high and low voltage power units; and preferably have commercial experience in designing equipment for production.—Apply in writing, giving age, qualifications, details of experience, salary required, etc., to the Personnel Department, Cinema-Television, Ltd., Worsley Bridge Rd., Lower Sydenham, S.E.26. [4846]

APPPLICATIONS are invited for the position of Assistant to senior mechanical engineer which exists within the organisation of a light engineering company; applicants must have technical qualifications equivalent to a good Degree in Engineering; experience must cover all phases of production engineering, including mechanical design of radio-communication and electronic equipment, design of press tools and planning and estimating; the salary which will be paid to the successful applicant will be up to £750 per annum, and the age range is from 30-45 years.—Applications, giving full details of qualifications, experience and salary required, should be addressed to Box 1426. [4789]

SITUATIONS WANTED
B.Sc. (second-class hon. in physics, pure and applied maths), grad. Brit. I.R.E., aged 24, industrial and teaching experience, seeks post in S.W. England.—Box 1499 [4862]
ADVERTISER.—20 years' experience television, radar and radio manufacture, sales and service, seeks post in Manchester area: own car.—Box 1532. [4894]

THE BRITISH NATIONAL RADIO SCHOOL

ESTD. 1940

A Prosperous New Year!

Our CONTRIBUTION, REDUCED FEES

Yours IMPROVED EFFICIENCY
 INDIVIDUAL COACHING BY POST


in
**RADIO, TELECOMMUNICATIONS,
 RADAR PHYSICS' MATHS.**

All examinations C. & G., P.M.G.
 Brit. I.R.E.

We can arrange for most examinations to be taken anywhere, aboard ship or furthestmost outpost. Free Booklet from

STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
 66, ADDISCOMBE ROAD, CROYDON
 Phone: Addiscombe 3341

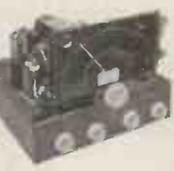-towards perfection- TUNER TYPE DT/4 by LOWTHER



The finest tuner unit in existence for quality reception (T.R.F. & Superhet). No complications in connecting to any well known amplifier.

Write for full descriptive folder to:—

THE LOWTHER MANUFACTURING CO.
 (The Laboratory Production Unit).

Lowther House, St. Mark's Road,
 Bromley, Kent RAV. 5225

TELEBOOSTERS

for long range Television reception. Super high gain single-stage pre-amplifier. 2 stage, 1 VR91 valve, slug tuned, London or Birmingham. Co-axial plugs and sockets, flying leads for High and Low tension, fully screened, low noise. Price £2/12/6. Power units for above £3/10/0.

S.A.E. for trade test report.

BOSCOMBE RADIO & ELECTRIC,
595, Christchurch Road, Boscombe,
Bournemouth. Phone: 36522

TELEVISION RECEIVERS SCANNING and FOCUS COILS TIME BASE COMPONENTS 7KV. EHT. RF. UNITS and TRANSFORMERS



Publications post free
HAYNES RADIO LTD.
Queensway, Enfield.

Our 1950 fully Illustrated
Catalogue is now Available
3? Post Free

BERRY'S
(SHORT WAVE) LTD.

25, HIGH HOLBORN, LONDON, W.C.1

BRIDISCO-MIDLANDS TELEVISION

A complete set of coils and chokes for sound and vision panels wound under strict laboratory supervision to "E.E." specification 19/6

TRF Coils, Long & Med. wave, a matched pair 5/9 TRF Coils, Long & Med. wave, with reaction 7/6 Superhet Coils, AER-OSC-HF Nos. 1-7, each 2/6 Miniature Coil Pack, 1 1/2 X 3 X 3 1/2 ins. Long, Med., Short, 3/7

From your local retailer, usual factor or:-

BRITISH DISTRIBUTING CO.,
66, HIGH ST., LONDON, N.8

(Send for literature)

YOU SHOULD HAVE A NEW TAYLOR

We can supply the latest Taylor Test-Equipment, and take your used Equipment in part exchange. Balance by cash or hire purchase.

Write, phone or send your gear along for inspection and offer.

UNIVERSITY RADIO LTD.
22 LISLE ST. Tel. GERRARD 4447 & 8582

SITUATIONS WANTED

ENGINEER, recently resigned four-figure post small enterprising company, versatile, active, experienced communications, radar. London area.—Box 1429. [4794]

TELECOMMUNICATIONS engineer, aged 37, seeks responsible executive post, small or medium-sized company, London area, wide experience research, development, general technical administration, radar and communications.—Box 1428. [4793]

BUSINESSES FOR SALE AND WANTED **FACTORY** possessing machine tools to the value of £1,000,000 is desirous of selling entire plant, either in bulk lots or as individual items, machines of all types offered; quick sale is essential for accommodation reasons; only enquiries for specific machines replied to.—Box 1174. [4775]

PATENTS

THE proprietor of British Patent No. 573313, entitled "Multiple section electronic tube and method of making it," offers same for licence or otherwise to ensure practical working in Great Britain.—Inquiries to Singer, Stern & Carlberg, 28, E. Jackson Boulevard, Chicago, 4, Illinois, U.S.A. [4825]

TECHNICAL TRAINING

A.M.I.E.E. City and Guilds etc., on "no pass, no fee" terms; over 95% successes. For full details of modern courses in all branches of electrical technology send for our 176-page handbook—free and post free.—B.I.E.T. (Dept. 388A), 17, Stratford Place, London, W.1. [6270]

TUITION

THE POLYTECHNIC, 309, Regent St., W.1.

ELECTRICAL Engineering Department. Head of Department: W. H. Date. B.Sc.(Eng.), M.I.E.E.

A SPECIAL course of four lectures on High-frequency Heating will be given by members of the research and design staff of Radion, Ltd., under the general direction of Captain J. A. L. Wharton, on Fridays at 6.30 p.m., commencing February 24th, 1950.

FEE for the course 10/-. A syllabus may be obtained on application to the undersigned [4799]

J. C. JONES, Director of Education, [4799]
RADIO training—P.M.G. exams, and I.E.E.

R Diploma; prospectus free.—Technical College Hull. [0611]

WIRELESS officer's attendance and "Radio-certs" postal course.—Apply Manager, The Wireless School, Manor Gdns, London, N.7.

WIRELESS, land, sea and air; students, both sexes, age 14 upwards, trained for interesting appointments in all branches of radio; low fees, boarders accepted; 2d stamp for pros.—Wireless College, Colwyn Bay. [0018]

WELL-PAID jobs await those trained in radio and television and other applications of electronics; our free booklet describes the wide range of postal and daytime courses, and the types of jobs awaiting those who have qualified themselves.—Write to:

E.M.I. Institutes, Dept. W.W., 10 Pembroke Square, Notting Hill Gate, London, W.2. Bayswater 5131-2. [01]

A.M.I.Mech.E., A.M.I.E.E. City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 176-page handbook—free.—B.I.E.T. (Dept. 387B), 17, Stratford Place, London, W.1.

TELEVISION postal course radio trades Examination Board's Diploma, also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence.—Apply British School of Television Ltd., 179, Clapham Rd., London, S.W.9. (40 years' experience in coaching students in wireless telegraphy and allied subjects.) [2586]

TELEVISION—The Gothic Television School specialises solely in training in television. All tutors possess university degrees and/or corporate membership of professional institutions and are appointed individually to postal course students to ensure complete and thorough training. Principals, M.B.E., B.Sc., M.Brit. I.R.E., education committee members, etc. Courses assume no previous television knowledge and provide guaranteed training for Brit.I.R.E. and R.T.E.B. examinations. Numerous well-known companies have adopted the School's Basic Television Course as standard television training for their staffs. Moderate fees. Details from Gothic Television School, 13, North Avenue, London, W.15. [0051]


BOOKS, INSTRUCTIONS, ETC.

VIEWMASTER TV construction, 8 full-size, stage-by-stage, assembly drawings with 32-page booklet. 5/-+6d post.

"EE" home-built television for Sutton Coldfield, 77-page book with wiring diagram, 4/6+4d post. Bernard's high definition TV manual, 5d-page book with details for a unit-built receiver, 3/6+3d post. Brimar radio valve and telerube manual, latest edition, 191 pages of valve data, including all the latest midget types, formulae and circuits. 4/-+6d post. Eddystone 145 Mc/s guide. 1/6+3d post.

LOUDSPEAKERS, The Why & How of Good Reproduction, 87-page book by G. A. Briggs of Wharfedale Speakers. 5/-+4d post. Sound reproduction, companion volume to Loudspeakers, 143 pages by the same author, 7/6+6d post. International Radio Tube Encyclopaedia, 410 pages, giving details and pin connections of 15,000 valves of every known type in the world made by 97 different makers. CV types are included, technical data is in 14 languages. 42/-post free.

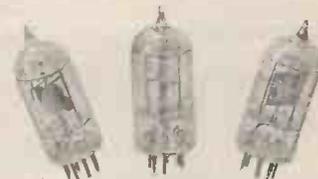FRITH RADIOCRAFT Ltd., Churchgate, Leicester. [0028]



TYPE G (87G BASE)

ENQUIRIES FOR ALL TYPES INVITED

BROOKES CRYSTALS LTD.

10 STOCKWELL STREET,
GREENWICH, LONDON, S.E.10.
PHONE GRE. 1828. CABLE. XTALS LONDON.

Globe-King MARVEL (REGD) IN MINIATURE SHORT-WAVE RADIO KIT

Probably the smallest one valve Short-Wave Radio receiver in the world using standard parts with Bandspread tuning device. "Magnificent performance"... vide testimonials British Isles and Abroad. Built and designed to precision standards, complete kit costs only 49/6—write today for descriptive catalogue.
JOHNSONS (RADIO) SPECIALISTS MACCLESFIELD
CHESHIRE (ENG)

Cutofeed SOLDERING IRON

Simple self-feed speeds up soldering. Better work. Saves solder. Write for leaflet 30.J.

RUNBAKEN-MANCHESTER I

YOUR METER DAMAGED ?

don't scrap it -
LET GLASER REPAIR IT

Leading Electrical Instrument Repairers to the Industry.

repairs by skilled craftsmen to all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Test meters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to

L. GLASER
SCIENTIFIC & ELECTRICAL INSTRUMENT REPAIRERS
341 CITY ROAD, E.C.1.
Tel. Terminus 2489

SPOTLESS SURPLUS BARGAINS

Offered by

RADIO UNLIMITED Elm Road, London, E.17.

TWIN METER TEST PANEL, containing M/coil 0-5 m/amp. meter and 0-20 Voltmeter, 3 Potentiometers, Variable resistance, Switches, etc., 12/6.

HEADPHONES, Bal/arm phones. (BA.5) Complete with lead and plug, 4/6 pair. Complete with Throat Microphone, 6/6. M/coil type, complete with hand Mic., 5/6 set.

P.M. SPEAKERS, New and Boxed. Covered by our guarantee of satisfaction. 5in. 10/-, 6 1/2in. 12/6, 10in. 16/6, 12in. 35/-.

M/COIL SUSPENSION TYPE MICROPHONE, 30 ohms. New/Boxed and Guaranteed. 35/- post free.

CABOT RADIO

R.C.A. H.T. TRANSFORMER. Input 190/260 v. (10 v. steps), 50 cps. sec. 2300, 1750, 0, 1750, 2300 v. (for nominal outputs 2000 v. or 1500 v. D.C. at 800 m/a). Wt. 97lbs. net. Size 9in. x 9in. x 7 1/2in. New in cases. £4 plus 7/6 carr.

R.C.A. MODULATION TRANSFORMER. Primary 10,000 ohms CT. Sec. 4000 ohms approx. (Push-pull 810's, 805's, TZ40's, etc., to any P.A. up to 1kW.) Wt. 67lb. net. Size 9in. x 9in. x 7 1/2in. New in cases. £3 plus 5/- carr.

SPECIAL OFFER. Both the above transformers together in one case. £6 10 0, plus 10/- carr.

SMOOTHING CHOKE. British made for 1131 cx. 15/20 H. 500 m/a, 80 ohms. Wt. 20lb. 25/-, plus 2/6 carr.

CONDENSERS. 4 + 4 mfd. 3KV wkg. 25/-, 4 mfd. 2KV wkg., 15/-, 4 mfd. 1,500 v. wkg., 10/- . All Carr. Paid.

TRANSMITTER. 1196 Phone and MCW 4.3-6.7 Mc/s. Easily modified for other frequencies. Complete with valves (EF50, OSC, TT1 PA, and EL32 Modulator) and circuit diagram. 27/6 plus 2/6 carr.

RECEIVER 1196, 6-valve Superhet, complete with valves (EF39RF, EK32FC, EF39IF, EF36AVC Amp, EBC33 Det, EF36AF Amp). 25/-, plus 2/6 carr. Also with circuit diagram.

CRYSTAL DIODES. CV101/11, suitable Xtal sets, F.S. meters, etc., 2/9 each, 8 for £1. Post free.

SOIL HEATING AND DEFROSTING TRANSFORMERS. (1) Primary 230 v. 50 cps. Secondary 11-13.5 v. (adj. Prim. tap). Service rated at 70 amps but O.K. for 150 amps. £4 10 0, carr. paid. New in Box. (2) Primary 230 v. 50 cps., sec. 6.75 + 6.75 v. 20A but O.K. for 40A. New. 50/- . Carr. Paid.

CABOT RADIO COMPANY LIMITED

28, BEDMINSTER PARADE, BRISTOL, 3.
Phone : 64314

BOOKS, INSTRUCTIONS, ETC.

"HOME Constructors' Handbook," the latest edition of this famous handbook containing circuits, radio construction and servicing hints and complete catalogue. is now available at only 1/-; mail order only.

SUPACOILS, 98, Greenway Ave., London, E.17.

WEBB'S 1948 radio map of world, new multi-colour printing, with up-to-date call signs and fresh information on heavy art paper. 4/6, post 6d; on linen on rollers 11/6, post 9d.—Webb's Radio, 1-4, Soho St., W.1. Gerrard 2089.

"PERSONAL Portables," the new book by E. N. Bradley, describes a whole range of tested loudspeaker-type personal sets. Build yours now for the holiday season, the circuits, layouts, drilling, constructional and wiring diagrams make it easy and interesting; 2/8 post free from Bradbooks, Sennen, Penzance, Cornwall. 14681

TESTSCOPE Mains Tester



For high & low voltage testing—:

1/30 & 100/850 volts A.C. or D.C. New popular model for 160/400 volts A.C. or D.C. — 12/6 Write for interesting booklet 90F.

RUNBAKEN MANCHESTER

TRANSFORMERS & COILS TO SPECIFICATION.

MANUFACTURED OR REWOUND

Filter Coils + 1% a Specialty.

JOHN FACTOR LTD.

9-11 EAST STREET, TORQUAY, DEVON.
Phone: Torquay 2162

ELECTRONICS DUPLEY LTD.

CRANMER AV. EALING. W 13.

Transformer and Coil Manufacturers to the Trade
Telephone: EALing 5688

POST RADIO SUPPLIES

OFFER EX-STOCK

COPPER INSTRUMENT WIRE.
ENAMELLED, TINNED, LITZ.
COTTON AND SILK COVERED.
Most gauges available.

B.A. SCREWS, NUTS, WASHERS,
soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS,
TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.

Latest Radio Publications.

Send stamped addressed envelope for comprehensive lists. Trade supplied.

POST RADIO SUPPLIES

33, Bourne Gardens, London, E.4.
Phone: CLIssold 4688

TAMSA

High Quality Tape Recording Components

RECORD HEADS	OSCILLATORS
PLAYBACK HEADS	AMPLIFIERS
ERASE HEADS	PRE-AMPLIFIERS

COMBINED RECORD-PLAYBACK HEADS
FREQUENCY CORRECTING NETWORKS
TAPE, Plastic Base, 600ft. 1,200ft., 3,250ft.
SPOOLS, 600ft., 1,200ft., 3,250ft.

Write for latest Price List, also for details of the NEW and REVOLUTIONARY TAMSA BEDLAMP.

AUDIGRAPH LTD.

Dept. MR3, 7, St. Peter's Place, Birmingham, 1

"You can rely on us"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES
IMMEDIATE DISPATCH

MIDGET SUPERHET COIL PACKS

MW/LV Size 2 1/2in. long, 1 1/2in. deep, 1 1/2in. high, Type "R"	25/-
MW/SV Size 2 1/2in. long, 1 1/2in. deep, 1 1/2in. high, Type "S"	25/8
SW/MW/LV Size 3in. long, 1 1/2in. deep, 1 1/2in. high, Type "O"	28/8

Comprising, iron-cored midget coil, wavechange switch, ceramic trimmers, neatly assembled for one hole fixing. The difficult part of a superhet overcome.

SPEAKER TRANSFORMERS

Super midget for "Personals" to match DL92, 884, etc.	4/8
Pentode output type 55: 1 at bargain price for quality	4/8
Midget mains output transformer	3/8

LOUDSPEAKERS

Celestion 2 1/2in. 25/8; 3 1/2in. 10/6; 5in. with dust cover 9/8; 6 1/2in. 12/6; with transformer, 17/6; 8in., 18/6; with transformer, 19/6; 10in., 21/-; 12in., 39/6; special lightweight 5in. small magnet, 10/6.

COILS

Warrant "P" Coils, 3/- each, full range stocked. Blue print with data supplied.

T.R.F. Matched pair, first quality, pair	7/6
MW Iron cored with reaction	3/8

FILAMENT TRANSFORMERS

Primary 200/240 v. Secondary 6.3 v. 1.5a.	8/6
Black crackle, small dimensions	12/6
Secondary 4 v. 3 a.	2/6

RESISTORS

1 watt, 3d.; 1/2 watt, 4d.; 1 watt, 8d. Large stock.

BARGAIN OFFER

Choke 70 m/a 150 ohms, super quality.
Boxed 5/-

VIEWMASTER TELEVISION

7 point to point circuits and booklet.
Post free 5/6
Components stocked.

HOT OF OTHER LINES.
Write, phone, or call for:
Price and Data folder containing Bargain List, 24d. Stamp.

RADIO SERVICING CO.

444, Wandsworth Road, London, S.W.8
Phone: MACaulay 4155.
77, 77A, Bus 28, Tram, Wandsworth Rd. S.R. Station.
Open till 6.30 p.m.

LABORATORY TEST EQUIPMENT

is of little use unless it is accurate. All equipment sold by HATFIELD INSTRUMENTS is GUARANTEED equal in every way to the makers' specifications. All instruments are either new or reconditioned as new.

Mr. R. H. Hatfield welcomes old and new friends to his new laboratories at Hanwell where Radio and communication test equipment may be inspected.

A selection of our stock is as follows:

Signal Generators.

- Type TF.144G by Marconi Instruments
- Type TF.517E by Marconi Instruments.
- Type TF.390G by Marconi Instruments.
- Type D.1. Advance.
- Type 52. Cossor.
- Type 106. Salford.

Oscilloscopes.

- Type 1035 by Cossor.
- Type 339 by Cossor.
- Type 11 Ultra.

Valve Voltmeters.

- Type TF.428A by Marconi Instruments.

Pulse Modulators.

- Type TF.675A by Marconi Instruments.

Also we have in stock wavemeters up to 1000 Mc/s. Variacs, constant voltage transformers, frequency meters, precision attenuators, etc.

Send for lists.

HATFIELD INSTRUMENTS

175, Uxbridge Road, Hanwell, W.7.
Telephone: EALing 0779.

SELENIUM RECTIFIERS

Chargers, Charger Kits.

NEW GOODS WITH FULL GUARANTEE
Sent Carefully Packed



FOOLPROOF CHARGER KITS, with full instructions. Standard Kit, 2v., 6v., 12v. at 3 amp., S.T.C., 12v. 3 amp. selenium rectifier, high grade 60 watt transformer, buretter, 45/6, post 1/4; ditto but 2 amp. rectifier, 37/8; or with special case, 49/6. Medium duty charger kit, 75 watt transformer, 12v. 4 amp. rectifier, ballast bulb, 52/6. Special case, terminals, screws, 17/8 for 3 amp. or 4 amp. 6v. kits as above, 2 amp., 33/-; 4 amp., 47/-; 1 amp., 30/-; 2v. 1 amp., 12/6. 12v. 6 amp. 95/-.

HEAVY DUTY CHARGER KITS, 120 watt trans., 12v. 6 amp. rectifier, slider resistance, high grade ammeter for 6v. 12v. charger, 24/15/-; ditto but 4 amp., 75/-, weight 15lb. Radio cell kit for 1 to 20 cells at 1.3 amp., 95/-, foolproof and will run continuously for years.

CHARGERS. Slider type, 4 amp. max. for 2v. to 12v., 22lb., 25/17/6, plus 12/6 crate and carr.; also 6v., 12v. 15 amp., 24/10/- . "Automat" Heavy Duty home charger, 9lb., 6v., 12v., 2 amp., 65/- or minor charger 6v., 2 amp./12v., 1 amp. 53/- or 12v. 1.5 amp. 53/- . E.772 12v. 3 amp. charger or E.776 6v. 3 amp./12v. 2 amp., 24/2/-, weight 12lb.; 12v. 6 amp. charger 27/5/-.

RECTIFIERS. S.T.C. selenium 12/15v. 3 amp., 18/6; 4 amp., 21/-; 5 amp., 25/-; giant fused 6 amp., 30/-; ditto 10 amp., 42/-; 6v. 4 amp., 17/6; 6v. 10 amp., 25/-; 24v. 2.5 amp., 28/-; 12v. 1 amp., 9/-; 6v. 0.5 amp., 4/10; 12v. 2 amp., 11/-, many others. E.T. Rectifiers 250v. 60 m/a., 7/-; 250v. 120 m/a. bridge, 12/8; 110v. 60 m/a., 6/-; 350-0-350v. 80 m/a., 9/8; all are small space selenium types. Crystall diodes in capsules, 3/6 each. M.B.3 instrument rectifiers, 3/6. Eliminator Kit with case 42/6, for 120v. 20 m/a.

CHAMPION PRODUCTS

43 Uplands Way, London, N.21
Phone: LAB 4457

INDEX TO ADVERTISERS

PAGE	PAGE	PAGE	PAGE
A.A. Tools	58	Frith Radiocraft, Ltd.	22
Acoustical Mfg. Co., Ltd.	10	Galpins	83
Aeru Electric Tool Mfg. Co., Ltd., The	16	Garland Radio	66
Adcola Products, Ltd.	88	Gee Bros. Radio, Ltd.	74
Advance Components, Ltd.	59	General Electric Co., Ltd.	21
Aerialite, Ltd.	52	General Lamination Products, Ltd.	82
Albert Mfg. Co.	78	Glaser, L.	86
Allan, Richard, Radio, Ltd.	14	Goodmans Industries, Ltd.	69
Allen Components, Ltd.	80	Goodsell, Ltd.	65
All-Power Transformers, Ltd.	56	Gramplan Reproducers, Ltd.	16
Alpha Accessories, Ltd.	20	Gray, Arthur, Ltd.	56
Ambassador Radio	33	Hallam, Sleigh & Cheston, Ltd.	34
Antiference, Ltd.	77	Hartley H. A. Co., Ltd.	72
Armstrong Wireless & Television Co., Ltd.	77	Hatfield Instruments	87
Ashworth, H.	24	Haynes Radio, Ltd.	86
Astor Eiselseller & Lawrence, Ltd.	87	Hazlehurst Designs, Ltd.	76
Audgraph, Ltd.	87	Hely-Mann Electronics Laboratories	77
Automatic Coil Winder & Electrical Equipmt. Co., Ltd., The	1	Henley's, W. T., Telegraph Works Co., Ltd.	74
B. & H. Radio	84	Henry's	62
Barker, A. C.	81	Hill & Churchill, Ltd.	84
Beethoven, Ltd.	70	Hivac, Ltd.	74
Belling & Lee, Ltd.	43	Holt, Stan	84
Berrys (Short Wave), Ltd.	86	Houghton & Osborne	32
Bird, S. S., & Sons, Ltd.	20	H.P. Radio Services, Ltd.	60
Birmingham Sound Reproducers, Ltd.	58	International Correspondence School, Ltd.	30
Booth, Jas., & Co., Ltd.	86	J.J. Trading Co., The	82
Boscombe Radio & Electric	86	Johnsons (Radio)	86
Brierley, J. H. (Gramophones & Recordings), Ltd.	58	Kershaw, S.	62
Britain, Chas. (Radio), Ltd.	54	Lasky's Radio	64
British Communications Corpn., Ltd.	56	Lawrence, G., & Co.	64
British Distributing Co.	86	Leak, H. J., & Co., Ltd.	49
British Institute of Engineering Technology	80, 82	Lewis Radio Co.	80
British Insulated Callender's Cables, Ltd.	Cover 11	Lockwood & Co.	84
British National Radio School	85	London, Ltd.	27
British N.S.F. Co., Ltd.	9	London Central Radio Stores	23
British Physical Laboratories	32, 67	London Radio Supply Co.	83
Brookes Crystals, Ltd.	86	London Television Co., Ltd., The	66
Brown, S. G., Ltd.	18	Lowther Mfg. Co.	85
Bulkin, A. F., & Co., Ltd.	87	Ludlow & Cole	68
Bullers, Ltd.	37	Lyons, Claude, Ltd.	74
Cabot Radio Co., Ltd.	75	Mail Order Supply Co.	55
Candle System Co.	78	Marconi Instruments, Ltd.	61
Car & General Radio	48	Marconi's Wireless Telegraph Co., Ltd.	65
Caxton Publishing Co., Ltd.	28	McMurdo Instrument Co., Ltd.	30
Celestion, Ltd.	87	Measuring Instruments (Pullin), Ltd.	57
Champion Products	36	Metro Pex, Ltd.	12
Charles Amplifiers, Ltd.	53	Metropolitan-Vickers Electrical Co., Ltd.	11
Cinema-Television, Ltd.	53	Midland Instrument Co.	66
Clydesdale Supply Co., Ltd.	58	Millett & Holden, Ltd.	80
Cohen, D.	22	Modern Book Co.	76
Collaro, Ltd.	42	Modern Electrics, Ltd.	78
Cosmocord, Ltd.	25	M.R. Supplies, Ltd.	24
Cossor, A. C., Ltd.	68	M.S.S. Recording Co., Ltd.	15, 40
Couploune Radio	79	Mullard Electronic Products, Ltd.	Cover 1v
Coventry Radio	68	Multicore Solders, Ltd.	18
Davis, Alec, Supplies, Ltd.	10	Murex, Ltd.	84
Dubilier Condenser Co. (1925), Ltd.	19	Northall, L. C.	84
Duke & Co.	82	Oliver Pell Control, Ltd.	88
Duple Electronics, Ltd.	87	Osmer Radio Products, Ltd.	60
Edison Swan Electric Co., Ltd.	44	Oxley Developments Co., Ltd.	64
Electradix Radios	73	Painton & Co., Ltd.	61
Electro Acoustic Developments	58	Park Radio, Ltd.	77
Electronic Instruments, Ltd.	20	Partridge Transformers, Ltd.	67
Electronic Precision Equipment	6, 7	P.C.A. Radio	70
E.M.I. Institutes	46, 48	Pennine Amplifiers	85
Enthoven, H. J., & Sons, Ltd.	28	Post Radio Supplies	87
Factor, J., Ltd.	87	Pratts Radio	64
Fielden (Electronics), Ltd.	84	Premier Radio Co.	4, 5
Flimer, J. T.	84		
Fluxite, Ltd.	79		
		Quartz Crystal Co., Ltd.	84
		Radio Exchange Co.	52
		Radio Servicing Co.	87
		Radiomenders, Ltd.	64
		Radiospares, Ltd.	88
		Radio Unlimited	86
		Redifon, Ltd.	63
		Reliance Mfg. Co. (Southwark), Ltd.	70
		Reproducers & Amplifiers, Ltd.	56
		Ring Lamp Co.	56
		Roding Laboratories	76
		Rogers Developments Co.	58
		Rollet, H., & Co., Ltd.	82
		Rothermel, R. A., Ltd.	36
		Ruco Products	26
		Runbaken Electrical Products	86, 87
		Salford Electrical Instruments, Ltd.	50
		Sangamo Weston, Ltd.	47
		Savage Transformers, Ltd.	66
		Scharf, Erwin	34
		Simmonds Aerocessories, Ltd.	14
		Simon Sound Service	33
		Smith, G. W. (Radio), Ltd.	70
		Sobell Industries, Ltd.	24
		Solartron Laboratory Instruments, Ltd.	37
		Sound Sales, Ltd.	46
		Southern Forge, Ltd.	85
		Southern Radio Supply, Ltd.	85
		Sower Transformers	70
		Sphere Radio, Ltd.	14
		Stability Radio Components, Ltd.	22
		Standard Telephones & Cables, Ltd.	41
		Stearlite & Porcelain Products, Ltd.	23
		Stera Radio, Ltd.	76
		Stratton & Co., Ltd.	35
		Sugden, A. R., & Co. (Engineers), Ltd.	28
		Supacoids	85
		Szymanski, S.	70
		T. & C. Radio College	70
		Taylor Electrical Instruments, Ltd.	34, 69
		Tele-Radio (1943), Ltd.	85
		Telegraph Condenser Co., Ltd.	Cover 111
		Telegraph Construction & Maintenance Co., Ltd., The	17, 52
		Thermionic Products, Ltd.	13
		Thornber, J. E., & Sons	82
		Transradio, Ltd.	46
		Trix Electrical Co., Ltd.	Edit. 75
		Truvox Eng. Co., Ltd.	5
		Universal Bazaars, Ltd.	82
		Universal Electrical Instruments Corpn.	54
		University Radio, Ltd.	51, 86
		Valradio	30
		Vitavox, Ltd.	31
		Voigt Patents, Ltd.	66
		Vortexion, Ltd.	45
		Webb's Radio	16
		West, Spencer	82
		Westinghouse Brake & Signal Co., Ltd.	63
		Weston Products (L'pool), Ltd.	68
		Wharfedale Wireless Works	32
		Whitley Electrical Radio Co., Ltd.	48
		Wilco Electronics	84
		Wilcox Electric Co.	2
		Wimbledon Eng. Co., Ltd.	26
		Wireless Instruments (Leeds), Ltd.	72
		Wireless Supplies Unlimited	78
		Woden Transformer Co., Ltd.	84
		Wolsey Television, Ltd.	35
		Wright & Weaire, Ltd.	62
		Young, C. H.	62



Products of
Quality & Reliability

MAINS TRANSFORMERS
A. F. TRANSFORMERS
THERMAL DELAY SWITCHES
SMOOTHING CHOKES
POWER RESISTANCES

Made by

OLIVER PELL CONTROL LTD

Telephone: WOOLWICH 1422-1426
CAMBRIDGE ROW · WOOLWICH · S.E.18

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark.



Designed for Wireless Assembly and Maintenance.

Working temperature reached in 1½ mins., consumption 25 watts, weight 2½ ozs.

Supplied in voltage ranges from 6/7v. to 230/250v.

⅜" diam. Copper Bit (standard model) 22/6. ½" diam. Copper Bit 25/-

Replacement Unit Bit Elements available.

British and Foreign patents.

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED
ALLIANCE HOUSE, CAXTON STREET, LONDON, S.W.1

Write or Phone: BR1xton 8075

MEET SOME OLD FRIENDS

THERE'S no friend like an old friend — and we have been making some of these friends since 1906: we lose sight of them very quickly, but we often hear about the long and reliable service they are giving. So — in case it is “out of sight — out of mind”, we take this opportunity of reminding you of their sterling qualities and wide range.

Rectangular Metal Cans.

Range: 250 to 30,000 v. D.C. working.

Capacitance: .01 to 10 Mfds.

The Moulded Mica types are also friends of long standing: they have been used in millions since their inception in pre-broadcasting days, and are regarded as the standard of condenser reliability.

Moulded stacked foil Mica.

Range: .00005 Mfds. at 350 v. D.C. working to .0025 Mfds. at 2500 v. D.C. working.



T.C.C. Condensers are exclusively specified in the View Master — the Television Set you build at home from standard parts. Constructor Envelopes (Model A, London or Model B, Sutton Coldfield) 5/- each from all Wireless Shops.

THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION: NORTH ACTON, LONDON, W.3 Telephone: ACORN 0061

RADIO FACTORIES ALL OVER THE WORLD

use ERSIN MULTICORE SOLDER



Philips Argentina S.A. Factory at Saavedra, Buenos Aires.



Sold MULTI 11



Radio factories of many world-wide organisations find that the use of British-made Ersin Multicore Solder effects great savings in material and labour costs. Here you can see Ersin Multicore Solder being used in a few of the factories where the famous Philips radio and television receivers are made. Ersin Multicore—with its 3-core construction, and efficient Ersin Flux—is the only solder which guarantees flux continuity, eliminating H.R. or 'dry' joints, and ensuring high speed precision soldering without waste. It will pay you to use only the Finest Cored Solder in the World—for economy with quality. Ersin Multicore Solder is supplied to manufacturers in 5 standard alloys, 9 gauges and 2 flux percentages. Service Engineers and Workshops are supplied with the handy Size 1 cartons in the specifications shown below.

Catalogue Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. length per carton	List Price per carton (subject) s. d.
C 16014	60/40	14	26 feet	5 0
C 16018	60/40	18	60 feet	5 0
C 14013	40/60	13	22 feet	5 0
C 14016	40/60	16	42 feet	5 0

MULTICORE SOLDERS LTD.

MELLIER HOUSE, ALBEMARLE ST., LONDON, W.1 • REGent 1411



X