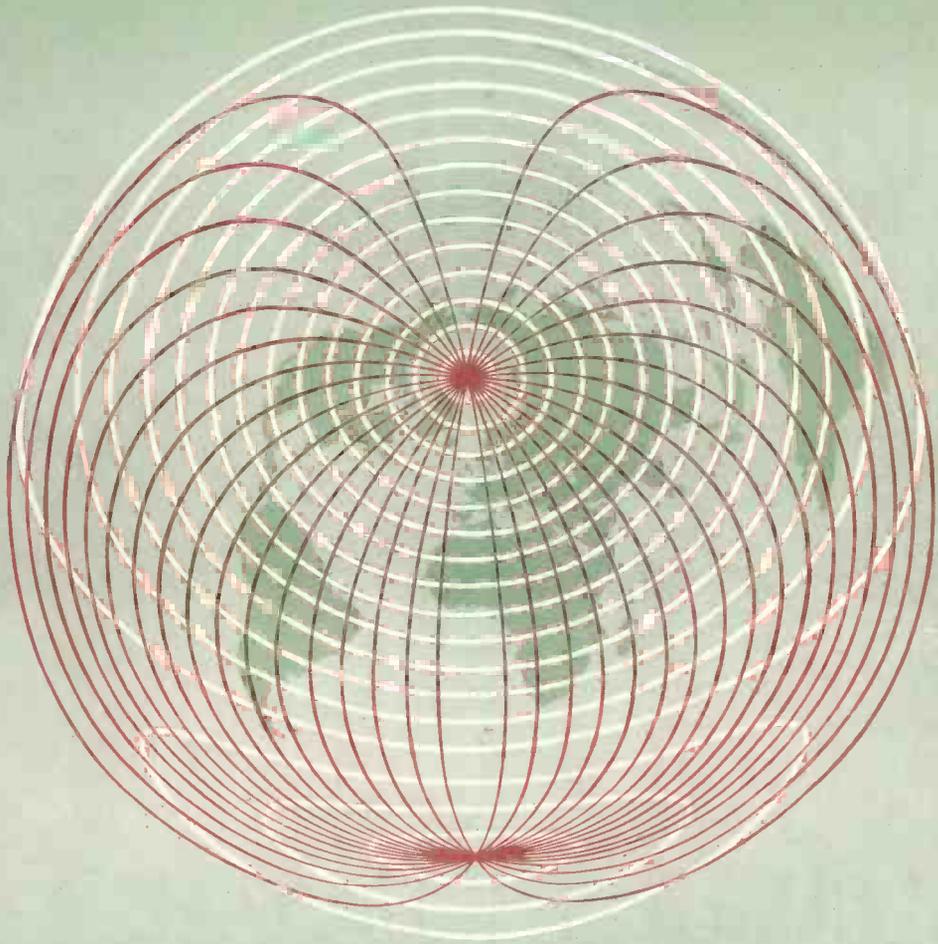


Wireless World

SEPTEMBER 1951 • TWO SHILLINGS



RADIO, TELEVISION AND ELECTRONICS

144 February



As the smallness of the ingeniously designed BICC Multicore Camera Trailing Cable is made possible by the use of solid conductors, this moulded-on coupler was developed mainly to overcome end breakage, which otherwise would be a serious problem with this type of cable. But the unique design of this coupler presents other advantages—it ensures reliable contact, adequate screening and great mechanical strength, leading to a long and trouble-free life.

BICC T/V Camera Cables with moulded-on couplers have satisfactorily withstood arduous service on BBC T/V Cameras.

BI
Callender's

**POLYPOLE
CABLE COUPLER**

BRITISH INSULATED CALLENDER'S CABLES LIMITED
NORFOLK HOUSE, NORFOLK STREET, LONDON, W.C.2

Wireless World

RADIO, TELEVISION
AND ELECTRONICS

41st YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.
Editor: H. F. SMITH

SEPTEMBER 1951

In This Issue

EDITORIAL COMMENT	337
A MODERN CRYSTAL SET. By <i>B. R. Bettridge</i>	338
MYSTERY BROADCASTING. By <i>Thomas Roddam</i>	341
RADIO TELEARCHICS	342
EFFICIENCY LINE-SCAN CIRCUITS—2. By <i>W. T. Cocking</i> ..	347
TENS OR TWOS? By “ <i>Cathode Ray</i> ”	351
RECORDING STUDIO DESIGN. By <i>P. A. Shears</i>	355
NATIONAL RADIO SHOW	361
LETTERS TO THE EDITOR	369
STEREOPHONY ON TELEVISION CHANNELS	371
WORLD OF WIRELESS	372
SHORT-WAVE CONDITIONS. By <i>T. W. Bennington</i>	375
MODIFYING “SURPLUS” METERS. By <i>W. H. Cazaly</i>	376
MANUFACTURERS’ PRODUCTS	379
RANDOM RADIATIONS. By “ <i>Diallist</i> ”	380
UNBIASED. By “ <i>Free Grid</i> ”	382

PUBLISHED MONTHLY: Price 2/- (last Tuesday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: “Ethaworld, Sedist, London.” *Annual Subscription:* Home and Overseas, £1 7s. 0d. U.S.A. \$4.50, Canada \$4.00. **BRANCH OFFICES:** Birmingham: King Edward House, New Street, 2. Coventry: 8-10, Corporation Street. Glasgow: 26B, Renfield Street, C.2. Manchester: 260, Deansgate, 3.

VALVES...and their Applications

MINIATURE BATTERY RANGE

OUTPUT PENTODES

Two output pentodes, DL92 and DL94, are available in the Mullard range of miniature battery valves. Both have centre-tapped filaments and can be operated with the two sections of the filament either in series when the L.T. drain is 0.05A at 2.8V, or in parallel when the drain is 0.1A at 1.4V. The filaments are, of course, suitable only for D.C. operation.

Type DL94 is designed for operation with equal voltages on screen and anode, and is the type recommended for normal domestic battery or A.B.C. receivers. Operated with the filament sections in parallel and with anode and screen potentials of 90V, this valve will give an output of 270mW with 7% total distortion for a drive voltage of 3.2 V.

Type DL92 may be operated with either equal or unequal voltages on screen and anode, and is primarily intended for use in miniature all-dry battery receivers, particular attention having been paid in its design to performance at anode and screen potentials of 67.5 V. Under these conditions an output of 160mW is obtainable with the series filament arrangement or 180mW with parallel filament arrangement, the drive voltage in either case being 5.5V.

Greater output can be obtained if the anode voltage is increased to 90V, the screen voltage remaining at 67.5V. In this case the output with series filament connection is 235mW and with parallel filament connection 270mW, again with a signal input of 5.5V.

Other valves in this range include:

DF91 Variable- μ pentode

DAF91 Short grid-base pentode with diode

DK92 Heptode frequency changer

OUTPUT PENTODES DL92 & DL94

RATINGS AND CHARACTERISTICS

	DL92	DL94
Filament		
Series connection		
V_f	2.8	2.8 V
I_f	0.05	0.05 A
Parallel connection		
V_f	1.4	1.4 V
I_f	0.1	0.1 A
Operating Conditions		
Series filament		
V_a	90	90 V
V_{g2}	67.5	90 V
V_{g1}	-7	-4.5 V
I_a	6.1	7.7 mA
I_{g2}	1.1	1.7 mA
g_m	1.4	2.0 mA/V
R_a	8	10 K Ω
$V_{in (r.m.s.)}$	5.5	3.2 V
P_{out}	235	240 mW
D_{tot}	13	7 %
Parallel filament		
V_a	90	90 V
V_{g2}	67.5	90 V
V_{g1}	-7	-4.5 V
I_a	7.4	9.5 mA
I_{g2}	1.4	2.1 mA
g_m	1.57	2.15 mA/V
R_a	8	10 K Ω
$V_{in (r.m.s.)}$	5.5	3.2 V
P_{out}	270	270 mW
D_{tot}	12	7 %
Limiting Values		
V_a max.	90	90 V
V_{g2} max.	90	90 V
I_k max.	12	* 12 mA

* 6mA for each 1.4-volt section of the filament.



Reprints of this article together with additional data may be obtained free of charge from the address below.

MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2.



SEPTEMBER 1951

VOL. LVII. No. 9.

National Radio Exhibition

IN this issue we publish, in semi-graphical form, a guide to the 18th National Radio Exhibition, which, it is hoped, will help not only readers who are actually visiting the show, but those who wish to keep informed of the current activities of those branches of the industry represented there. As will be seen, manufacturers of domestic broadcast and television receivers are very much to the fore; indeed, in this section the exhibition may be regarded as fully representative. The same cannot, unfortunately, be said of other branches of our art, though, as at the Castle Bromwich show last year, few are entirely without representation. Although the manufacturers' exhibits lean so heavily towards broadcasting, displays staged by Government departments and other non-commercial organizations are planned to show the visitor what is going forward in communications, electronics and many other applications of radio.

Television promises to be the greatest attraction, if only for the reason that the planned opening of two more B.B.C. stations during the next few months will go a long way towards providing complete coverage of the country.

New Broadcasting System?

WE suggested last month that there was little in the White Paper on the Beveridge Report to stimulate discussion on matters within our province. That opinion seems to have been justified, but, in the Parliamentary debate on the White Paper, the Postmaster General made a rather cryptic statement that, several weeks after the event, is still the subject of speculation in radio circles. Referring to v.h.f. broadcasting, the P.M.G. said, in effect, that an "entirely new" system of modulation had come to light, which might well supplant both f.m. and a.m.; this new system must be examined before any decision is made on a national system of v.h.f.

The natural reaction to this statement is "What is it?" and the P.M.G.'s reasons for failing to answer that simple question are singularly unconvincing.

There seems to be no good reason why we should not be given the facts, nor why the origin of the recommendation made to the Post Office should not be disclosed. As things are, there is a general feeling of uncertainty, mixed with a good deal of scepticism as to the real novelty of the mysterious system. The majority opinion inclines, naturally enough towards some form of pulse modulation, and this is the basis on which a contributor speculates elsewhere in this issue.

Wireless World has long urged that most careful thought should be given to the planning of our v.h.f. service, and, above all, that we should not be stamped into making a wrong choice of system. Every possible system should be examined, but the P.M.G.'s present smoke-screen tactics can only increase still farther the delay in coming to a decision.


Illegal Interference

CONTRARY to popular opinion, man-made interference with radio reception did not automatically become illegal on the passing of the Wireless Telegraphy Act, 1949. The anti-interference clauses of the Act remain ineffective until such time as the Postmaster General, acting on the advice of a duly appointed body, makes specific regulations.

The first real step towards outlawing avoidable interference has now been taken, and it may justly be regarded as a milestone. An advisory committee has been dealing with the question of radiation from the ignition systems of internal combustion engines and its effect on television reception. Specific recommendations have been made concerning the limitation of the radiated field of interference. The next step is for the P.M.G. to issue a statement on the action he proposes to take on the making of regulations. It is not until these regulations are actually made that interference will be, for the first time, legally preventable in Great Britain. At the present rate of progress, how long will it be before all forms of serious interference are outlawed?

Many other sources have yet to be dealt with.

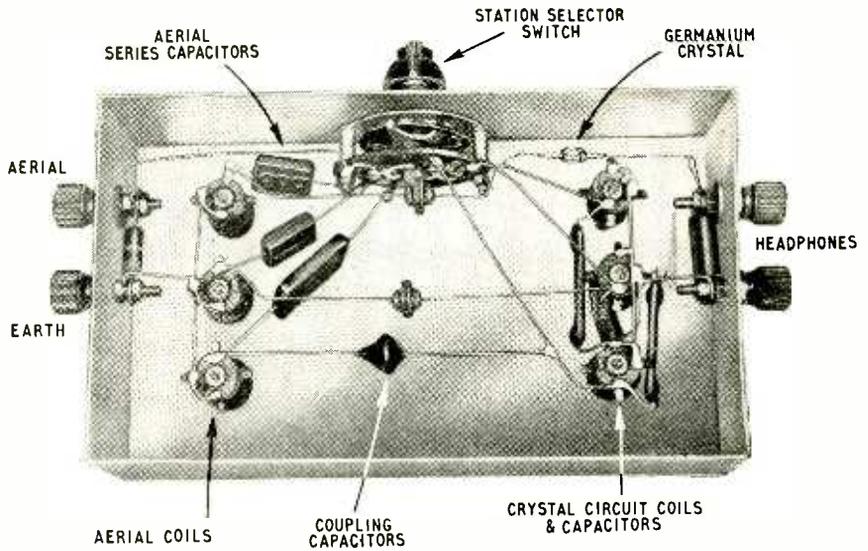Photograph of the underside of the chassis showing the position of all the parts. Terminals for aerial and earth leads are at one end and those for the headphones at the other. Nothing is mounted on top of the chassis.



A Modern Crystal Set

Pre-Selection of Three Stations to Suit Local Conditions

By B. R. BETTRIDGE*

THE advent of power cuts has forced many people to consider the crystal receiver as an alternative for programmes they particularly wish to hear, and the development of sensitive and robust permanent detectors has eliminated the nuisance of crystal adjustment. The crystal receiver is also gaining popularity as an alternative source of programmes for invalids and for children in bed.

The design of even so elementary a device as a crystal set is not so obvious as might be expected and there is room for wide divergencies of opinion as to what constitutes the best arrangement. The author was astonished at the amount of interest shown by colleagues and other friends with whom the matter was discussed and is grateful for their numerous suggestions.

A few basic requirements were taken as a starting point. They were: good performance on three programmes, moderate size, employment of standard components and simplicity of construction and operation. This meant that the possibly ideal arrangement for sheer performance, employing large diameter tapped coils wound with stranded wire could not be considered. It was also decided that the set should be primarily a fixed affair. The ability to take it from place to place and attach it to any aerial without adjustment was regarded as not worth the complication or sacrifice of performance which it would entail.

Most designs have a large element of compromise and this was no exception. As a general rule, however, when compromise had to be made the most important factor was deemed to be signal strength. This may seem strange considering the enormous increase in power of stations since the early days, but there are two other points to consider. The first is that people no longer look upon minute signals as acceptable and now demand what at one time would

have been regarded as very loud signals in the "phones on the table" category. The other, the inescapable fact that the only power available is that derived from the aerial and big aerials are out of fashion.

The question of good signal strength has particularly to be watched when meeting the need for reasonable selectivity since to some extent the two requirements are conflicting. The degree of selectivity needed varies according to area, but to suit the majority of users a two-circuit tuner is essential. This, without critical design or adjustment, gives considerably better station separation without undue sacrifice of strength than the most carefully designed single-circuit set. Incidentally, in assessing selectivity requirements account must be taken of various powerful stations situated about the country giving special services to Europe. No details of these transmissions appear to be

TABLE OF VALUES

Station	Aerial Circuit		Crystal Circuit		Coupling C in pF	
	Coil	Series C in pF	Parallel C in pF†	Coil		Parallel C in pF
L. W. Light (1,500m)	HH1	1,000	200	HH2	1,500	20-25
Third (464m)	HH2	300	150	HH3	350	10-15
Northern (434m)	HH2	300	100	HH3	300	10-15
Scottish (371m)	HH3	400	200	HH3	250	10-15
Wales (341m)	HH3	250	150	HH4A	1,000	15-20
London H. (330m)	HH3	200	150	HH4A	900	10-15
West (285m)	HH3	200	100	HH4A	700	10-15
Midland (276m)	HH3	150	100	HH4A	650	10-15
N. Ireland (261m)	HH3	150	80	HH4A	600	10-15
London L. (247m)	HH3	100	70	HH4A	500	10-15
West Local (206m)	HH3	70	50	HH4A	330	10-15
Third Local (194m)	HH3	70	40	HH4A	300	10-15

* Osram Valve & Electronics Dept., G.E.C.

† For modified circuit only.

generally available but they make their presence known in a very definite fashion in some areas. It is not anticipated that higher selectivity than that given by the standard arrangement will often be needed, but modifications will be mentioned for the benefit of those unfortunately placed.

The circuit finally adopted after numerous trials is shown in Fig. 1. It will be seen that station selection is by switching and that each station has its own pair of coils individually tuned and coupled. This arrangement has two distinct advantages besides extreme simplicity of operation. In the first place there is no ganged tuning to impose limitations on the circuit and in the second place optimum values may be chosen for each station instead of compromising between the requirements of different parts of the waveband. Thus instead of performance being sacrificed for the sake of simple operation it has in fact been improved.

Even if the design had not been started with commercial coils in mind this circuit would have made them almost essential, since six home-made coils of reasonable efficiency are apt to take up a lot of space. The coils used are wound with stranded wire and have adjustable dust iron cores. In spite of their small size they have "Q" values of over 100.

The aerial circuit is series tuned, an arrangement which is now uncommon in any but transmitting circuits but which gives greatest signal strength in the simplest way with the majority of aerials likely to be used for crystal reception. The modern method of aerial coupling widely used in valve receivers consisting of a high impedance aerial coil is quite unsuitable for crystal working because of its poor power-transfer efficiency. The other common form of coupling consisting of a low impedance coil or tap on the tuned circuit is better, but big deviations from optimum occur with different aerials unless several taps are provided. It will be noted that the coils used are actually h.f. transformers and the primary windings can be used for this form of coupling in special cases. Typical values of series capacitance are quoted but these may have to be modified for aerials differing greatly from that for which the set was designed. This slight disadvantage in setting-up procedure is amply compensated by the greater signal strength resulting from a correct matching.

Coupling between the circuits is by top capacitance. The value to be aimed at is the critical coupling which

gives maximum strength without double humping. It cannot be exactly specified since some of the factors affecting it vary from one set to another, in particular the aerial damping and the crystal load. A pre-set 0 to 30pF trimmer could be used by the meticulous but the typical values listed are unlikely to cause audible loss.

To feed the crystal a straightforward parallel tuned circuit is used. A tapped circuit might have been expected here, and indeed first experiments showed that with ordinary values, placing the crystal circuit across the whole of the coil produced so much damping as to cancel out most of the advantage of the double circuit tuner. To avoid having non-standard tapped coils made up, alternative means were explored such as a capacitance tap and a second crystal to complete the rectifier d.c. path. However, as often, the simplest means proved most effective and the equivalent of a matching tap was provided by lowering the impedance of the circuit by an unusually low L/C ratio. Thus a 390- μ H coil is used for 1,500 metres instead of the more usual one of 2,650 μ H, whilst the coil for the lower end of the broadcast band is 35 μ H instead of 178 μ H. A stranded wire version of the Weyrad HH4 coil, called the HH4A, is used here, this single minor departure from standard being preferable to the introduction of several tapped coils.

Germanium Crystal

The crystal used is one of the new germanium diodes which are already finding wide application in electronic gear generally. Many of the specialized types now available are selected for characteristics which are not important in a crystal receiver, and several of the standard types will give good performance in this set. For general purposes the G.E.C. type GEX35 will be found satisfactory, but where maximum sensitivity is desired a low level rectifier such as the GEX64 or GEX66 should be used. Where maximum selectivity is desired, a high impedance rectifier such as the GEX44/1 or GEX45/1 will give optimum performance.

Headphones of 4,000 ohms resistance can be fed direct or low-resistance ones can be operated via a suitable transformer, the impedance for matching purposes being taken as about 15,000 ohms. The precise value varies with signal so cannot be specified, but it is by no means

critical. While the quality of reproduction which may be obtained from a crystal receiver is extremely good, the cheaper patterns of diaphragm headphones have a restricted frequency response and marked resonances which colour the reproduction. This is particularly noticeable when signal strength is high. Where better quality

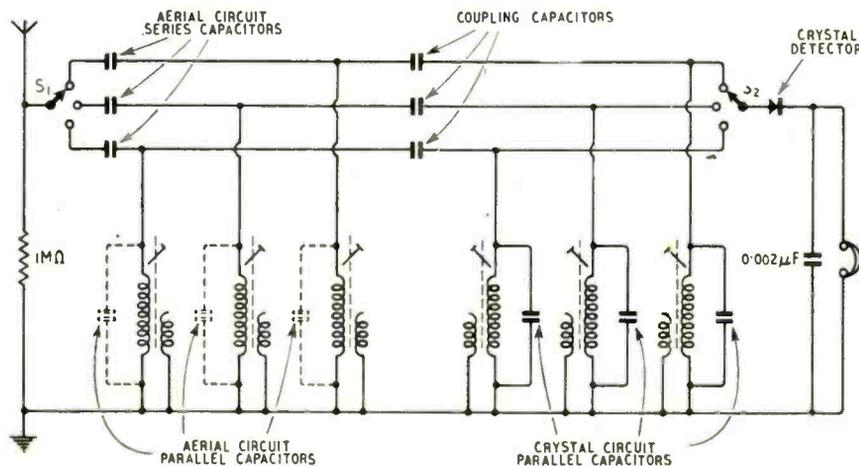


Fig. 1. Circuit diagram of the crystal set. Values of the series and parallel fixed capacitors depend on the three stations required and they are given in the table. The aerial circuit parallel capacitors (shown dotted) are required only under the conditions explained in the text.

is desired the moving coil type of headphone is advantageous. ☉

It is suggested that wherever possible an outdoor aerial should be used. This need not, however, be the elaborate affair of the old days, consisting of thick stranded wire and strings of heavy insulators. The main point is that it should be strong enough to withstand the weather. Within ten to twenty miles of a powerful station a loft aerial will give reasonable results, but it should be as long and as high as the house permits. Except in districts very near to a station the picture-rail type of aerial is quite certain to be disappointing. A 1-megohm resistor is shown connected between aerial and earth to avoid accumulation of static since the circuit provides no other direct path. Measurements show that a low resistance earth connection is really important, and a clip on a cold water pipe is one of the most satisfactory solutions.

The photograph shows how the set is made up. This construction was adopted so that it could be fixed permanently in an inconspicuous position such as under a window ledge with the phones hanging on a nearby hook. The chassis used is a readily obtainable standard size, but clearly a much smaller one could accommodate the components and could be used to suit individual tastes. The actual wiring is sufficiently obvious from the photograph of the underside of the chassis to need no detailed description. Type numbers of coils and values of capacitors for various stations are given in the table. The adjustable dust cores should give sufficient range to cope with the normal ± 20 per cent capacitor tolerance. As far as possible values have been chosen which are readily available, but in case of difficulty a value can, of course, be made up by connecting two or more in parallel.

The lining-up of the set is not difficult, but since tuning is fairly sharp some guidance may be helpful. The capacitance values given in the table are calculated to tune to the station required with the core near the mid position. Clipping the aerial temporarily on to the primary winding (green tag) of the crystal circuit and turning the set into a single circuit tuner is probably the quickest way of getting a tuning point on this coil. The aerial can then be transferred to its proper terminal and the aerial coil brought to resonance. After this the crystal coil should be re-trimmed. Should the aerial coil not peak a different value of series capacitance should be tried. The values listed are for an aerial about 80 ft long and 20 ft high; a larger one may require a smaller value and *vice versa*. In the case of very small aerials some parallel capacitance may have to be added across the coil to produce resonance, as shown in dotted lines in the circuit diagram Fig. 1. The process is repeated for each pair of coils, after which tuning from one station to another consists merely of rotating the switch.

The basic arrangement described above allows of certain variations which may be worth trying in some circumstances. The first is using the primary coil for aerial coupling. In this case parallel tuning of the aerial coil is necessary and appropriate values of capacitance are given in the table. An alternative is to couple these parallel-tuned coils to the aerial via a small capacitance, the actual value depending on circumstances. This constitutes a very flexible arrangement, especially useful for highly damped aerials, but in general severe loss of signal strength is


entailed. Yet another variation is to use the primary coil of the crystal circuit as a secondary to feed the crystal. This gives very low damping at considerable expense of signal strength. It is perhaps worth mentioning that those who require two programmes only need fit only the appropriate two pairs of coils, whilst those in London who wish to have the Light Programme available on both wavebands will easily find room for an additional pair of coils. This was in fact done in the prototype to facilitate checking its performance.

Tests were made at a number of places in the London and Midland areas, results being compared by taking readings on a micro-ammeter in series with the phones. Variations due to local conditions were greater than had been anticipated, and it was surprising to find that in some parts of London the 1,500-metre Light Programme provided a greater signal than the Brookmans Park transmission of the same programme. It is a matter of opinion as to what constitutes acceptable strength, but even $5 \mu\text{A}$ gives a signal that enables programmes to be followed perfectly in a quiet room. Probably the minimum comfortable level is about $20 \mu\text{A}$. Where readings above $100 \mu\text{A}$ are obtained programmes can be followed on a sensitive loudspeaker in quiet surroundings. One of the highest readings obtained was over $400 \mu\text{A}$ from an aerial on top of the *Wireless World* building, this figure being given by the Home Service.

A precise list of parts is not specified since, in general, constructors will wish to use components available locally. It is sufficient to mention the following points:—

The chassis measures $7\text{in} \times 4\text{in} \times 2\text{in}$; the switch is a 2-pole 3-way "Yaxley" type; the coils are Weyrad "H" type and the crystal is a G.E.C. germanium diode.

ACCESSIBILITY

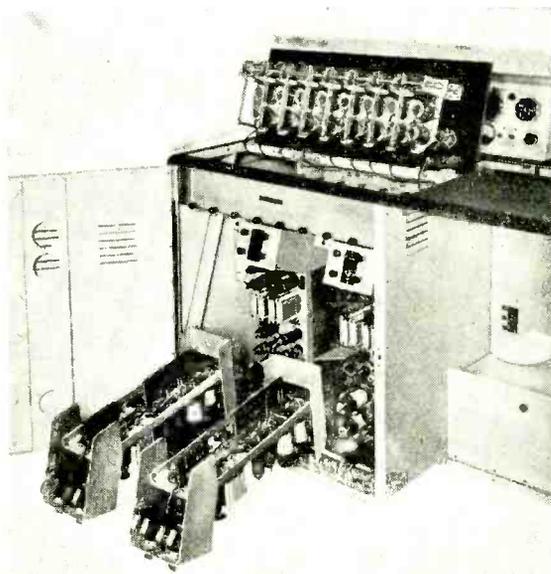

This view of the Ediswan 8-channel electro-encephalograph is an example of the growing tendency to design equipment with an eye to easy maintenance.

Mystery Broadcasting

THOMAS RODDAM Speculates on What the P.M.G. Meant

THE latest pronouncement on v.h.f. broadcasting appears to have been drafted by a student of the works of Franz Kafka and of Lewis Carroll. It lays down the future plans with all the precision of a charabanc poster advertising a mystery tour. Let us consider what the Postmaster-General said.

"Research has discovered an entirely new consequence, which completely sets aside all the reasons for giving favour to one or the other"* [a.m. or f.m.]. Can this possibly be true, in the engineering sense, not the political? If it is true, what can this "entirely new" thing be? I am, fortunately, in a position to reveal to readers of *Wireless World* a sensational possibility. In an article (July, 1945), "Radiophare" discussed telepathy and suggested that radio engineers would do well to conduct more experiments on the transfer of ideas. Shortly after this article appeared a lady, whose name I have unfortunately forgotten, got into communication with me and revealed that a certain Foreign Power was, in fact, well advanced in this field, and was engaged in putting ideas into people's heads, all unbeknownst. My own studies, carried out on a number of bathing beaches, showed that some individuals certainly possess a capacity to introduce a common idea into a number of independent heads.

I am afraid that this possibility, although no odder than some engineering proposals which have been studied at a high level, does not rank as Roddam's nap for to-day. If for one reason only, it must be eliminated: the Chancellor of the Exchequer would not be able to get his 15 per cent from telepathy. We must think again.

"Research has discovered . . .", and in a fortnight, too. That fortnight, like the thirteenth stroke of a crazy clock, casts doubt on all that has gone before. Not even a new system of colour television can be developed in a fortnight. My interpretation of this is that a gentleman from the Ministry has been reading departmental files and back numbers of *Wireless World*. He has worked back to February, 1947, when an obstinate scribe was advocating the use of pulse modulation, although Mr. Herbert Morrison had promised, in 1946,† "detailed plans for the establishment of f.m. stations . . . within a year or so." Yes, in 1946.

The case for frequency modulation was really that they have it in America, but that is in another country, and besides . . . The case against f.m. must now lay great stress on the financial side. We need completely new receivers for f.m. reception, and if we are to reap any real benefit from v.h.f. they must be good receivers. My guess is you will be lucky to get out

under £40 for a commercial f.m. receiver which gives that high-fidelity performance we are promised. A lot of money, a lot of design effort, a lot of components to be taken from the limited national supply for slightly improved entertainment. For the moment, amplitude modulation would let us have good reception with cheap convertors and our present receivers, and we could buy high-fidelity sets later.

This case against f.m. is a case against pulse modulation, too. I still believe that pulse modulation is the final answer to the v.h.f. broadcasting question, and I am afraid that I have converted the P.M.G. just at the moment when expediency makes me hesitate. And Mr. Ness Edwards is no Duke of Wellington, to say "expediency be damned."

Pulse modulation, for broadcasting purposes, will probably be pulse position modulation. A typical scheme would be one using 30,000 pulses per second, each pulse lasting 1 microsecond. A transmitter having a mean power of 1kW would then radiate 33kW during pulses and would be received as a 33kW transmitter. The modulation is applied to the pulse epoch: that is, the pulses are advanced or retarded slightly from the exact 33.3 μsec spacing, according to the modulation. They might, for example, be moved 1-2 μsec at 100 per cent. modulation. This would be an extravagant scheme in band-width, for it would need a 2-Mc/s band: band-width could be saved by using longer pulses, with a smaller duty ratio. When a second programme is provided, a new train of pulses is interlaced with the first, and a gate circuit in the video section of the receiver (they call it video in the pulse world) is used to select the wanted programme. A common r.f. and i.f. head can supply two video systems, so that you can have both programmes from one lot of v.h.f. receiver equipment. The advantage of the pulse system is that there is no tuning: the r.f. circuits can be pre-set and drift-proof. Pulse modulation offers a considerable gain in signal-to-noise ratio, and is better in this respect than f.m. Furthermore, an approximate calculation suggests that it will be much better under multi-path propagation conditions: you will not get unbearable distortion when the local gas-holder is full. But we must still buy a complete new receiver.

Perhaps I can at least dispel the mystery within the mystery of the P.M.G.'s statement. He cannot indicate the nature of the new development, because it has not been tested and proved. How on earth does he imagine a new broadcasting system can be tested in secret? And why? Security is becoming such an obsession in some quarters that we shall soon have our programmes scrambled. This blanket is debasing the idea of secrecy: everything, classified and unclassified, is becoming "fairly secret."

* Hansard 20 July 1951.

† Hansard 16 July 1946.



Preliminary trials on a 5-ft diesel-powered model (Electronic Developments) with which it is hoped to cross the Channel. This and many other radio-controlled models are at present on show at "The Model Engineer" Exhibition at the New Royal Horticultural Hall, Westminster, where radio telearchics is a prominent feature this year.

Radio Telearchics

Outlining Some of the Principal Systems

PROBABLY one of the earliest radio telearchic systems was that demonstrated at the Paris Exhibition of 1906, when Professor Branly, using his famous coherer, showed how apparatus could be switched on and off at a distance. This was about the limit of the simple wireless equipment of those days, but with the development of new radio techniques control systems have become more and more versatile, until now they can convey and reproduce at the receiving end almost any kind of manual operation. Flying an aircraft by remote control, for instance, has become quite a commonplace affair.

This seems to imply a bewildering variety of complex systems in use nowadays. From the functional point of view, however, there are only two basic types: *selecting systems*, which convey different orders, like "start" and "stop," and *positioning systems*, which convey the different degrees of an order, as necessary, say, for turning a rudder. Many of the systems met in practice, of course, are not just simple selecting or positioning systems but combinations of the two.

To begin with selecting systems, perhaps the most elementary kind is that in which the orders can only be given in a certain sequence. The orders are transmitted as impulses, and at the receiving end these are arranged to operate a selector or stepping switch

so that with each impulse the wiper moves on to a new contact and completes an associated control circuit. If the selector has a ring of, say, four fixed contacts, orders can only be given in the sequence 1, 2, 3, 4, 1, 2, 3, 4, 1, 2 . . . etc., so to get from, say, order 3 to order 2 it is necessary first to pass through orders 4 and 1.

Such a system has the great virtue of simplicity and, because the weight of apparatus at the receiving end can often be reduced to a matter of ounces, it is used very widely in radio-controlled models. The fundamental disadvantage of having to pass through a whole sequence of orders before getting to the right one does not always matter, as this can usually be done so quickly as to make little difference. A worse drawback is that the operator must always remember the last order given if he is to calculate the right number of impulses to the next one he wishes to give. This can become very confusing, so the system is really only suitable for handling a short sequence of orders which can be memorized easily.

With a slightly more complex version of the same system these inherent disadvantages can be avoided. For instance, the selector can be fitted with a homing device that will automatically return the wiper to the same initial position after the completion of each order. Then, each order is represented by a definite number of impulses and a code is formed. With this arrangement it is possible to use some device such as a telephone dial for generating impulses at the transmitter, as this can be made to send the right number automatically when the order is dialled. Another refinement can

be added to prevent the wiper from actuating all the intermediate control circuits as it travels to its final position. This can be a slugged relay, which operates to break the circuit of the wiper so long as impulses are being received and the wiper is travelling, then, when the impulses cease and the wiper comes to rest, falls back and so completes the required circuit.

Whatever form the sequential system may take, however, it is inherently rather slow in operation, and this makes it unsuitable for such uses as the control of high-speed

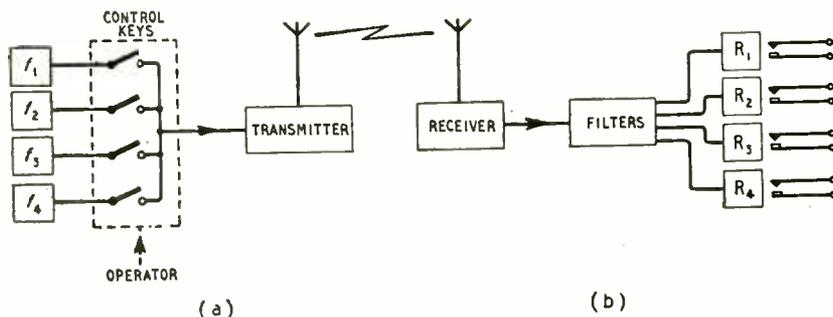



Fig. 1. Selecting system using modulating tones to provide the various control channels. At (a) the transmitter and (b) the receiver.

aircraft. For an almost instantaneous response probably the best system is the multi-channel type in which the orders are conveyed as different frequencies. In one form, the orders are transmitted as different radio frequencies and these are sorted out at the receiving end by means of r.f. tuned circuits and detectors, the outputs of which actuate relays. This, of course, amounts to a separate receiver for each order, but a modified scheme has been proposed requiring only one r.f. tuned circuit and detector. The tuned circuit has a variable tuning capacitor which is rotated continuously so that the incoming frequencies—whenever they are transmitted—are tuned in sequentially, or sampled, before passing to the detector. The resultant detector output voltages are then distributed to the correct relays by a rotary switch driven in synchronism with the capacitor.

Even with such modifications, selecting systems using different carrier frequencies tend to be unwieldy in design—and, of course, they occupy a great deal of space in the frequency spectrum. It is more convenient to use a single carrier frequency with a number of modulating tones to represent the orders, and this system is, in fact, very widely used for control purposes. Little explanation is necessary, for the mode of operation can be seen almost at a glance from Fig. 1. At the transmitting end (a) the modulating tones are generated by the oscillators f_1, f_2 , etc., and are selected for modulating the transmitter by a suitable switching arrangement. After being received and demodulated at (b) the tones are identified by a bank of filters; the output of each filter is then passed to a rectifier so that when the correct tone arrives it produces a d.c. voltage, which actuates a relay. A common practice is to include the relay in the anode circuit of a cut-off valve and apply the d.c. voltage to the grid in a positive sense to overcome the negative bias.

Besides being almost instantaneous in operation, the multi-channel system has the further advantage that several orders can be given at the same time. This feature is useful in another way. It means that the number of orders possible is not limited to the number of single tones available, since additional orders can be formed by combinations of tones. At the receiving end the contacts of the relays can then be interconnected in such a way that the transmission of tone combinations will bring into operation new circuits which are quite independent of the individual tones.

For installation in models, however, the receiving system in Fig. 1 usually proves too heavy and expensive, mainly because of the filters and the electronic apparatus necessary to work the relays. As an alternative, it is possible to use electromechanical frequency-responsive devices, which can be made much lighter than the equivalent electrical systems. A set of vibrating reeds, for instance, can be made to resonate with the various incoming frequencies by means of an energizing coil fed straight from the receiver. As each reed resonates it vibrates against a fixed contact and interrupts an external circuit, thereby generating impulses which can be made to charge a storage capacitor and so produce a steady voltage for operating a relay. Although it is the physical properties of the reeds which actually do the responding, improved selectivity can sometimes be obtained by electrically tuning the inductance of the energizing coil to the frequency band occupied by them. A device working on a very similar principle is the resonant relay.

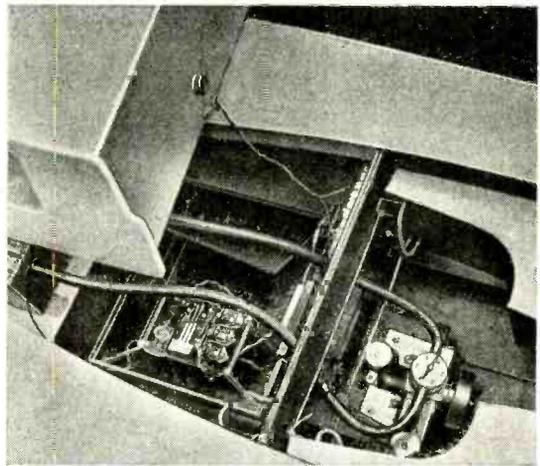

Interior of the 5-ft E.D. model. The 4-stage receiver (left) uses deaf-aid valves and drives a tuned-reed selecting system with three reeds working between 300 and 350 c/s. These switch the steering motor to port or starboard and sound a horn. The transmitter uses 100% square-wave modulation.

Here the armature is a permanent magnet held in position by a hair spring, and this oscillates backwards and forwards like the balance-wheel of a clock whenever the input to the energizing coil corresponds to the natural frequency of the mechanism.

Now to positioning systems. As mentioned before, these are for conveying different degrees of an order and enabling progressive adjustments to be made to a distant control mechanism. One of the simplest is that sometimes used for controlling the rudder movement of light craft, where very little mechanical power is needed. The actual driving mechanism is an electromagnetically-operated pawl and ratchet or an escapement, and this is stepped round by means of impulses from the transmitter.

With heavier craft, where considerable power is needed to apply helm, it becomes necessary to drive the rudder through reduction gearing from a rever-

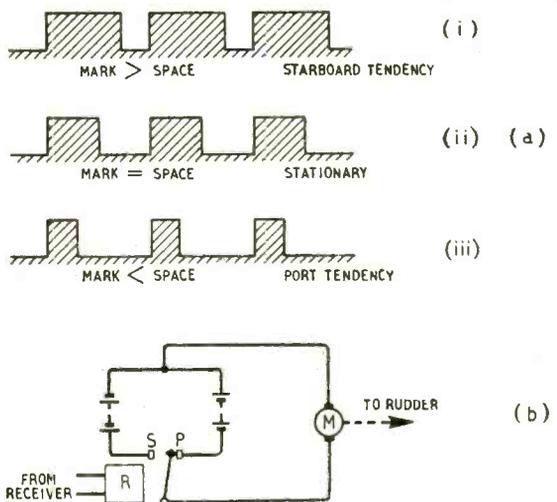



Fig. 2. Positioning system working on variations of pulse-width ratio, suitable for rudder control. The transmitted pulses (a) after being received are fed into the control mechanism (b).

sible electric motor—so that one order is needed for port helm and another for starboard helm. In its simplest form, however, this is not a very precise method of positioning, since the angle finally taken up by the rudder depends on the time the steering motor is running and so cannot be determined very accurately. There are, however, a number of improved versions of the basic idea and these provide the operator with a much better measure of control. One is a development of the time-switch principle in so far as the duration of the signal controlling the steering motor is adjusted automatically for the required rudder position—that is, not the duration of the signal in absolute time, but the ratio between the mark period and the space period in a train of square pulses. Fig. 2(a) shows how the pulse-width ratio is varied.


At the receiving end (b) this train of pulses is made to operate the relay R, which, as can be seen, determines the direction of the steering motor. During a mark the armature is pulled over to the contact S and the rudder moves to starboard; during a space the armature falls back on to the contact P and the rudder moves to port. Thus, if the mark/space ratio is 1:1 as in (ii), the rudder will move equal amounts in both directions and, if the reduction gearing between motor and rudder is sufficient and the pulse repetition frequency is great enough, it will remain stationary for all practical purposes. If broad pulses are transmitted as at (i) the rudder will progressively move to starboard, and if narrow pulses are transmitted as at (iii) it will move to port. And the greater the mark/space ratio the faster the rudder will move. To maintain the rudder in any particular position it is only necessary to revert to the 1:1 condition as at (ii). At the transmitting end the pulse generator can take the form of a vibrating relay, and there must, of course, be some means of continuously varying the pulse width.

The main disadvantage of the system is that the signal cannot be removed without sending the rudder to one extreme or the other. Moreover, the steering motor is necessarily consuming current all the time.

Another method of controlling the steering motor enables the operator to determine not merely the position of the rudder but the actual compass course that he wishes the craft to take. It involves a form of automatic pilot, controlled by a gyroscope, that maintains the craft on whatever course has been set. Referring to Fig. 3 (a), a constant-course heading is provided in the craft by a gyro-magnetic compass which maintains an electrical reference in the form of a pivoted contact arm, R. When the craft deviates from this heading, the gyro drives R into contact with one of the segments and thereby switches the steering

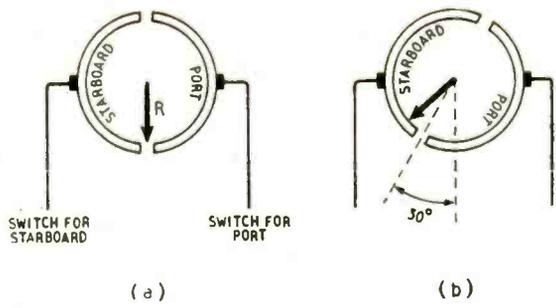

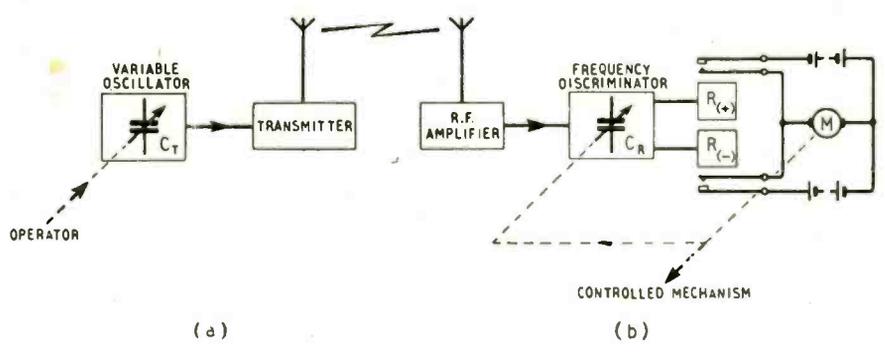Left: Fig. 3. Part of a device for rudder positioning making use of the automatic-pilot principle.



Below: Fig. 4. Servo positioning system working on variations of frequency: (a) the transmitter and (b) the receiver.

motor in the right direction to correct the deviation. When the craft has swung back on course again the reference arm R returns to the neutral position between the segments and so switches off the motor.


Steering is achieved by transmitting an order which deliberately rotates the segments the required number of degrees with respect to the arm R (30° to port in Fig. 3(b)). As the craft commences to turn the gyro swings with respect to it and so causes R to follow-up the rotation of the segments. When the craft has almost completed the order the gyro has swung through an equivalent angle but the gearing between it and R is arranged so that R has actually overtaken the neutral gap (Fig. 3(b)) and is now on the starboard segment. As a result the rudder begins to return to amidships, and the craft finally settles down on to its new course with R back in the neutral gap.

The initial rotation of the segments is achieved by a stepping mechanism which is operated by impulses from the transmitter—so many degrees being represented by each impulse.

From the description of the above system readers will no doubt recognize that a servo or follower principle is involved by the fact that "error-signals" are produced by deviations from course or by steering. These error-signals are of a mechanical nature and consist of deviations from a mechanical norm R that exists at the receiving end of the system. There are, however, other kinds of servo systems used in telearchics, and one of the most common and easily recognized is that where the error-signals are electrical deviations from an electric norm established at the transmitting end. In other words, a change deliberately introduced in the transmitted signal produces an error-signal at the receiver, and the servo or follow-up mechanism works by continuously and automatically adjusting itself so that this error-signal is balanced out. There are several ways of producing the continuously variable change required in the transmitted signal—by varying the frequency, amplitude or phase—but the final effect is the same whatever method is used.

Fig. 4 shows, for example, the essentials of a servo position control working on variations of frequency. The transmitter (a) includes a variable-frequency oscillator, the frequency of which is varied in accordance with the degree of the order by means of the variable capacitor C_T . At the receiving end (b) a similar variable capacitor is used for tuning, and the object of the servo or follow-up mechanism is to keep the system constantly in tune with the varying incoming frequency by rotating the variable capacitor C_R so that any movements of the rotating vane of C_T are followed faithfully by corresponding movements of the rotating vane of C_R .

The variable capacitor at the receiving end is actually part of a frequency discriminator of the well-known type which gives zero voltage output when it is tuned exactly to the incoming frequency and positive and negative voltages when the incoming frequency is too low and too high. Now assume that an operator at the transmitting end has decreased the capacitance of C_T and thereby increased the transmitted frequency. The discriminator then becomes off tune and produces a negative voltage error-signal which, after rectification, closes the relay $R_{(-)}$. As a result, power is applied to the reversible motor M , which drives the rotating vane of C_R in such a direction as to decrease the capacitance. By doing this, it progressively brings the discriminator into tune with the increased frequency; and when the circuit is exactly in tune the output of the discriminator falls to zero, relay $R_{(-)}$ opens, the motor stops and the moving vane remains stationary. The whole system is now restored to a balance condition. In the same way, if the operator increases the capacitance of C_T , relay $R_{(+)}$ will cause the motor to increase the capacitance of C_R correspondingly until once again the system is

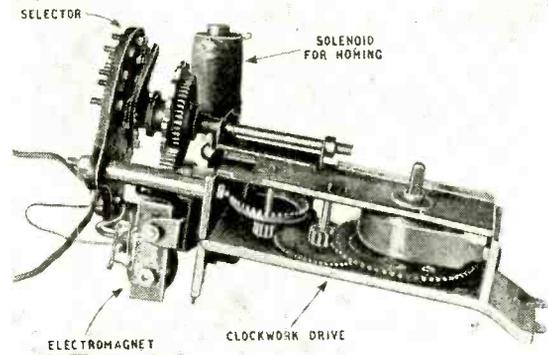


Sixteen-position selector operated by a clockwork-driven escapement which is tripped by an electromagnet. After each order, the selector is homed by a solenoid and slow-acting plunger; this operates fully when there is a pause after a series of actuating impulses. (Maker: N. A. Ough.)

restored to balance. It can be seen, then, that since the motor M is causing the rotating vane of C_R to follow closely every movement of the rotating vane of C_T , any mechanism driven by M will also follow the rotating vane of C_T —and any movements applied to C_T by an operator. The tuning control at the transmitting end can thus be calibrated in terms of mechanical displacement at the receiving end.


There are, of course, alternative methods of driving C_R . For instance, the incoming frequency can be keyed so that the discriminator will produce positive or negative pulses instead of d.c. voltages, these pulses being arranged at the correct frequency to drive a two-phase synchronous induction motor. Another ingenious system employs a simple series resonant circuit as the discriminator. Then, as the incoming frequency is varied above and below the resonant point, the phase of the current in the circuit either leads or lags with respect to the applied voltage, and these changes of phase constitute positive or negative error-signals which drive a two-phase motor in either direction. As in Fig. 4, the motor rotates a tuning element in the resonant circuit in such a direction as to bring the circuit back into tune with the incoming frequency and restore the system to balance.

The system working on variations of amplitude is similar in form. At the transmitting end the variable element is an attenuator, and a corresponding variable attenuator at the receiving end is kept in step with it by means of an amplitude-comparing circuit.

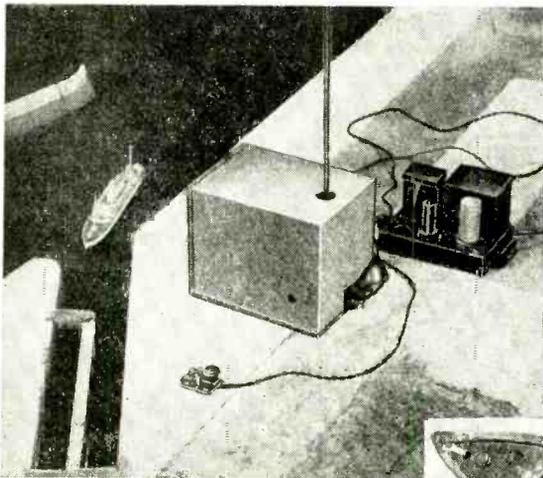Positioning by means of phase variations is a rather



Used by civil engineers (Sir Bruce White, Wolf, Barry and Partners) for testing scaled-down harbour installations (above), this model boat is only 11.8in long. Pulses of r.f. on 27 Mcs are transmitted to operate the receiver (right), a self-quenching super-regenerative type using an XFG1 subminiature gas triode. A sequential selecting system gives four rudder positions with the aid of a rubber-driven escapement and enables the motor to be started, stopped and reversed.

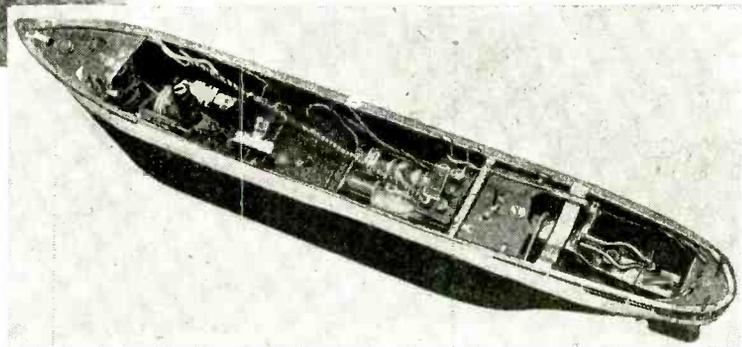

more complex matter, but an example of how it can be done is provided by a telearchic system developed by the General Electric Company for controlling high-speed aircraft in flight. Here, (Fig. 5), the conversion from mechanical movement into variations of phase is done by a phase shifter, PS_T , in the transmitter, and at the receiving end a servo system is arranged to drive a corresponding phase shifter PS_R such that the phase change initiated by PS_T is always reproduced by PS_R . Referring to (a), the frequency generator produces f_1 , one output of which provides the reference phase whilst the other output, after passing through PS_T , provides the controlling phase. These outputs — of the same frequency but different in phase — are then phase-modulated on to two separate sub-carrier frequencies, f_2 and f_3 , which, in turn, are amplitude modulated on to the carrier of the transmitter. At the receiving end (b) the sub-carriers f_2 and f_3 are filtered out and from them the two f_1 channels, differing in phase, are produced by demodulation in the phase discriminators. The f_1 control phase is now compared with the f_1 reference phase in a discriminator, after the latter has passed through PS_R . Any difference between them produces an error-signal in the form of a d.c. output which energizes the motor and so drives PS_R in such a direction as to eliminate the error signal. Looked at in another way, the balance condition of the servo is with f_1 (reference) in the same phase as f_1 (control); therefore PS_R works to neutralize exactly the phase difference introduced between the two at the transmitter and so moves through a corresponding angle to PS_T . The mechanical drive in (b) is then taken from the servo motor in the normal way.


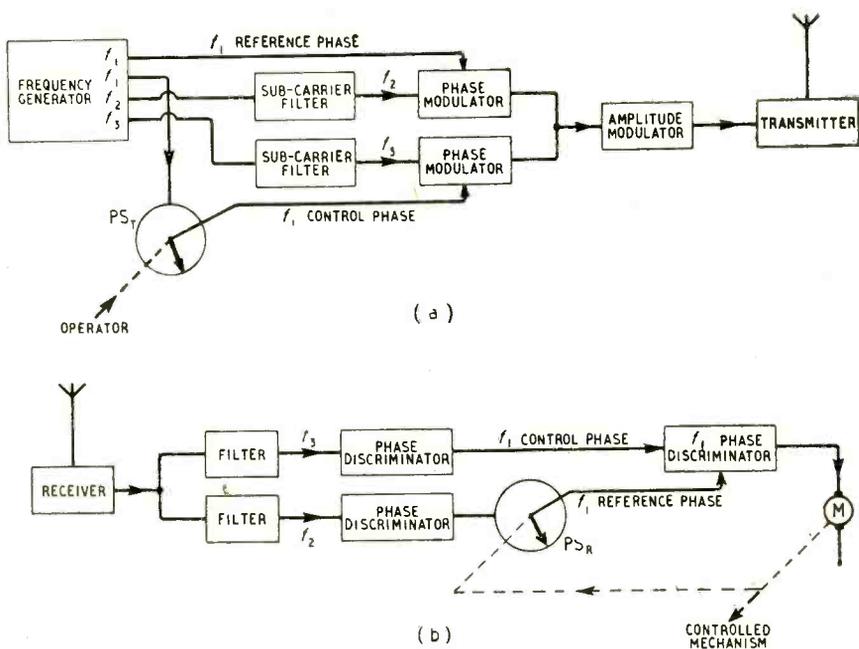
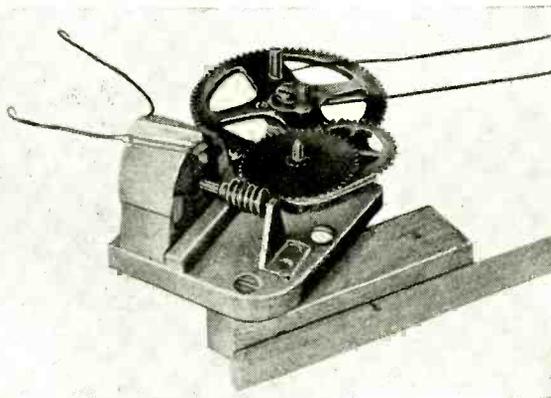


Fig. 5. Phase-shift servo positioning system in which a control phase is varied with respect to a reference phase: (a) the transmitter and (b) the receiver.

A feature of this system is that it enables a number of position-control channels to be operated on the one radio link. All that is necessary are additional pairs of phase shifters, corresponding to PS_T and PS_R , and additional sub-carriers (f_4, f_5, \dots etc.) to carry the new f_1 control phases. By using, say, two of these control channels for a single function it is possible to convey the information with great accuracy, as one control channel can be used as a kind of vernier on the other. The G.E.C. equipment actually contains seven control channels in all, together with the extra channel for the reference phase.

Finally, it goes without saying that combinations of the above basic systems can be used where a large number of different orders are required. One very convenient method is to provide a group of control channels by means of modulating tones, or sub-carriers, then each of these can be regarded as a radio link in its own right and used to carry a subsidiary system.

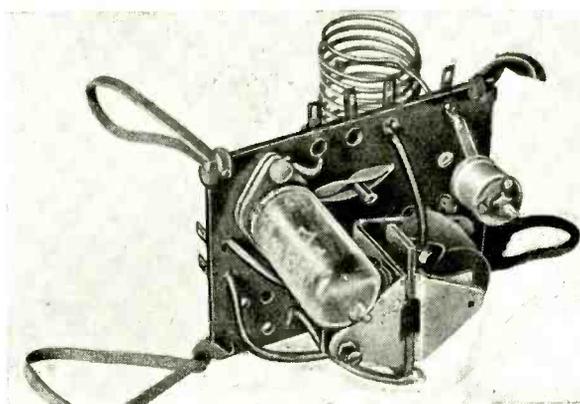Left: Commercially made receiver for radio-controlled models. Right: Steering mechanism driven by a reversible electric motor (maker, N. A. Ough). The wires on the right connect to a rudder-bar.



Efficiency Line-Scan Circuits

Part 2—Diode Conditions

By W. T. COCKING, M.I.E.E.

AS an example of conditions with a directly-fed deflector coil the following figures were derived in Part I for a valve having a peak-anode current of 200 mA with a minimum anode-cathode potential of 95 V: $L_L = 22.3$ mH, $C = 1160$ pF, $r_L = 44.6 \Omega$, $I_L = 360$ mA and overshoot $x = 0.8$. This results in $L_L I_L^2 = 2.9$ mH-A² and this is typical for a moderately efficient deflector coil with a 50° tube at 9 kV. The ideal mean valve currents were $i_a = 46.6$ mA and $i_c = 30$ mA but under practical conditions they are both likely to be 5–15 mA greater. This data all refers to the circuit of Fig. 1 which is repeated here for ease of reference.

The voltage and current waveforms are shown in Fig. 4. For the scan period τ_1 they have been calculated from the foregoing data, but for the fly-back period they have been estimated only. The voltage is shown with respect to the "cold" end of the deflector coil, point 1 in Fig. 1. Under the ideal operating conditions, which we are at first considering because they are the simplest, V_2 must be cut off except during the initial part of the scan, when the current is changing from -160 mA to zero. When it is cut off its anode potential must be negative with respect to its cathode, which means that the diode anode potential with respect to point 1 must be more negative than the voltages shown in Fig. 4.

Over the initial part of the scan, however, the anode voltage must vary in a particular way. The required voltage is easily computed if the voltage-current characteristic of the diode is available. From the curves of Fig. 4 take, say, four equal increments of time during the conductive period of the valve and read off the corresponding currents and voltages. From the valve characteristic determine the anode-cathode voltage for each current and add these voltages to those of the circuit, from Fig. 4.

With times of 16, 25.5, 35, 44.2 and 53.2 μ sec, we get currents of -160, -120, -80, -40, and 0 mA and voltages of -89, -91, -93, -95 and -97 V. At these currents the voltage drops across a typical diode are 14, 10.9, 8.2, 5 and 0 V and hence the anode voltage of the diode with respect to point 1 must be -75, -80.1, -84.8, -90 and -97 V.

This curve is plotted as a dotted line in Fig. 4 over the conductive period of V_2 . Outside this region the shape of the curve is unimportant as long as it lies below the voltage curve of the circuit.

This voltage is provided by the device A in conjunction with the $R_1 C_1$ circuit. Generally speaking, $R_1 C_1$ is an auto-bias circuit which under the influence of the mean diode current i_d builds up a constant voltage equal to the back e.m.f. across L_L . Thus

$$i_d R_1 = L_L I_L / \tau_1 = E_L$$

The current of V_1 [Fig. 3(c), Part 1] flows through A


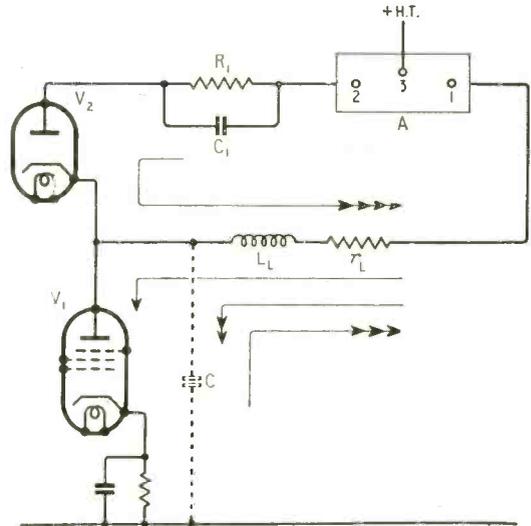


Fig. 1. The basic economy circuit with a directly-fed deflector coil. This diagram is repeated from Part I for easy reference.

Fig. 4. Calculated current and voltage curves for a peak current in V_1 of 200 mA and an overshoot, x , of 0.8. The dotted curve indicates the required anode voltage for the diode during its conductive period. At other times it must be more negative than the coil voltage.

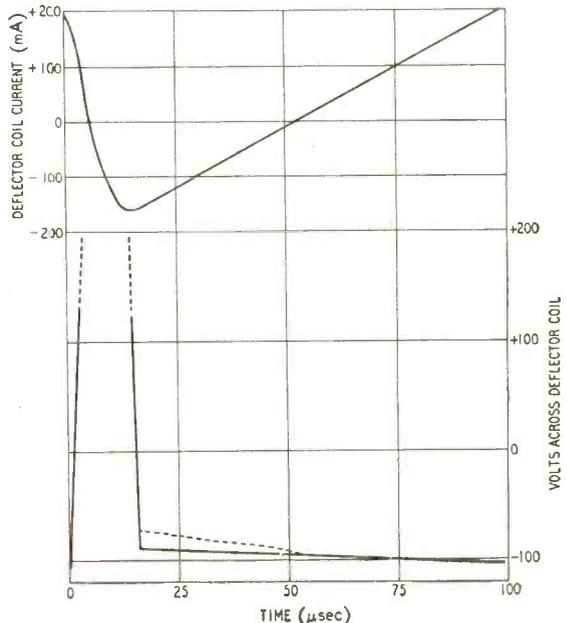

by terminals 1, 3; the current of V_2 [Fig. 3(b)] also flows through it by terminals 1, 2. Under the influence of these currents it must build up the required voltage waveform as just described between terminals 1, 2. It should do this with a minimum voltage drop between terminals 1, 3, since this voltage drop must be taken into account in assessing the h.t. voltage needed.


With the device A in the position shown in Fig. 1 the diode current flows through the whole impedance between 1, 2 and this is usually higher than the impedance between 1, 3 or 2, 3. It is usual to avoid this by a slight re-arrangement of the circuit which becomes as shown in Fig. 5. The current of V_1 still flows through A by terminals 1, 2, but the diode current by terminals 2, 3 while the diode control voltage is developed between 2, 3 instead of 1, 2.

Either circuit will work, but the network forming device A is not quite the same in the two cases. Usually, the position for A shown in Fig. 5 is the better and from now on we shall consider this.

The diode current flowing through the impedance between 2, 3 will set up a voltage drop in opposition to that needed. The voltage developed by the current of V_1 must therefore be sufficient to overcome this. Therefore, in general, the circuit must be of lower impedance between 2, 3 than between 1, 3 and there must be a phase reversal between the two. As a first approximation, therefore, the device A must be a transformer with a step-down turns ratio between 1, 3 and 2, 3.


It must be more than a simple transformer, however, for it has to produce a control voltage for the diode at a time when V_1 is non-conductive. It must, therefore, be of such a nature that it gives a response after the exciting current has ceased.

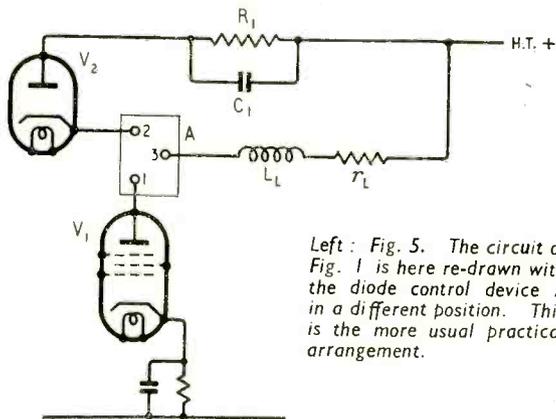The device A usually consists of a resonant circuit arranged to act as a tuned transformer and one form is shown in Fig. 6, which is numbered to correspond with Fig. 5. The anode current of V_1 [Fig. 3(c)] flows in at terminal 1 and the diode current of V_2 [Fig. 3(b)] enters at terminal 2. The result is the same as if the wave of Fig. 7(b) flowed in the simple



Left: Fig. 5. The circuit of Fig. 1 is here re-drawn with the diode control device A in a different position. This is the more usual practical arrangement.

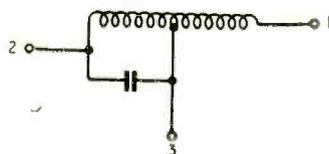Right: Fig. 6. One practical form of control element for the diode is shown here. In practice the inductance is variable.



tuned circuit of Fig. 7(a), this circuit being connected in series with the diode. Two cycles of the wave are shown. The first part of the cycle is the diode current itself and comprises the negative-going step followed by the positive-going linear section. The second part of the cycle—the negative-going linear part ending with the positive-going step—is a copy of the anode current of V_1 reversed in phase by the transformer action and increased in amplitude by the transformer ratio.

The effect of this current wave on the tuned circuit depends on the constants of the tuned circuit. If the damping is critical or greater the circuit is non-oscillatory. The main effect is produced by the steps in the wave at the beginning and end of fly-back and the linear intervening parts have relatively little effect and can be ignored in a first approximation.

The major current step at the end of the scan (A) Fig. 7(b) will produce a voltage wave across the circuit of the general form shown in Fig. 8, curve A. It is a form of saw-tooth and is roughly of the shape required. The second step (B) will produce the same waveform, but inverted and of smaller amplitude, and it will start after the first. The waveform produced by the two steps in succession will be the sum of the two individual waves.

Curve B shows the resultant waveform when the second step occurs at $t/2CR = 0.6$ and curve C when it occurs at $t/2CR = 1$ for the case when the second step has one-quarter of the amplitude of the first. The first, curve B, is more of the form required and leads to such practical values as $0.05 \mu\text{F}$ and 13.7 mH with a shunt damping resistor of 262Ω .

Diode Control Waveform

These curves are given only as an indication of the form of the results. Exact calculation is extremely difficult and the writer knows of no way of performing the inverse calculation for determining the required component values. The curves, too, are affected by the position of the damping resistor; it can be in shunt with L and C or in series with either, or it may be split and be partly in series with each.

In practice, it is necessary to determine the proper values by experiment, and it is normal to have the inductance continuously variable as a linearity control. In most final designs the proper damping is obtained by designing the coil to have the proper losses, but sometimes a fixed resistor is used. Instead of the transformer it is quite common to employ a single inductor with two capacitors as in Fig. 9, the step-down ratio being obtained by making the "secondary" capacitor larger than the "primary." This particular arrangement is unsuited to the circuit of Fig. 5 because it interrupts the h.t. supply.

When the conductive periods of the two valves overlap, as they do in practice, the diode current is different from the idealized case just discussed and the anode-voltage waveform required by it is also different. The diode current is greater and the control waveform must be modified to suit.

Simple calculation becomes impracticable because there is no obvious optimum amount of overlap. It becomes necessary to take the curvature of the valve characteristics into account and a graphical method must be adopted. In practice, the simplest course is usually to employ the simple idealized approach to determine suitable values of components for an initial experimental set-up. The precise conditions are then

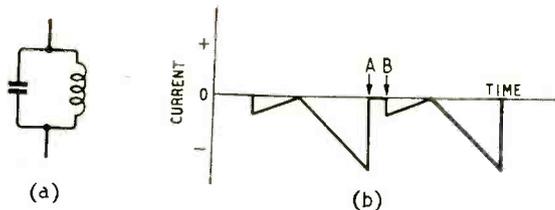


Fig. 7. The control element of Fig. 5 has the same effect as the single tuned circuit (a) fed with the current waveform (b).

found experimentally and consist mainly in finding the proper grid drive and bias for V_1 and the optimum values for the components in A.

This is a case where it is good engineering practice to design by a combination of approximate theory and experiment because it is much less laborious than a full theoretical solution.

The performance obtainable with all circuits of this nature and the values of components required are both very dependent upon the amount of over-shoot obtained in the oscillatory fly-back. If the valve V_1 is cut-off very quickly for the fly-back, as it should be, the overshoot is governed by the circuit losses and these occur mainly in the deflector coil. The magnitude of the overshoot is related to the Q of the circuit and, in fact,

$$x = e^{-\pi/2Q}$$

This relation is not of the highest importance at the moment for it is often as easy to measure x as Q, but when the transformer is introduced it becomes necessary.

In order to show the effect of the overshoot the

TABLE 1

x	Q	I_L (mA)	L_L (mH)	C (pF)	i_p (mA)	i_d (mA)	$i_p - i_d$ (mA)	E_L (V)	P (W)
0	—	200	72.5	359	84	0	0.42	176	14.8
0.4	1.71	280	37.1	700	60	9.6	0.18	125	7.5
0.6	3.1	320	28.4	915	52.5	18.9	0.1	110	5.8
0.8	7.05	360	22.3	1165	46.6	30	0.0467	96	4.56
1.0	∞	400	18.1	1140	42	42	0	87	3.65

circuit constants have been calculated for several values of x and are listed in Table 1. To those accustomed to work at radio-frequency the Q values will seem remarkably low. In fact, however, a Q of around unity is all that can be expected of a coil wound on a closed core of transformer stampings at some 32 kc/s—the natural frequency of the fly-back. The provision of an air-gap helps considerably and a deflector coil necessarily has a very large air-gap, but even then a Q much in excess of 10 is unlikely. With low-loss materials for the iron circuit much higher Q values are possible.

The figures in Table 1 are all for a valve delivering a peak current of 200 mA and a deflector coil of 2.9 mH-A². They are all for ideal conditions and in practice the mean anode current i_a of the driving valve V_1 is likely to be from 20 per cent to 50 per cent higher. The column headed P shows the product of E_L and i_a ; it is a part only of the total input power because it does not include the anode dissipation of the valves. The point of importance is the way in which it falls as the overshoot is increased. When h.t. boost can be used a part of this energy can be fed back and utilized; the power needed then decreases much more rapidly with increasing overshoot.

The case of $x = 0.8$ is a practical one. If the real anode current is 60 mA instead of the ideal 46.6 mA and the mean anode potential of V_1 is 95 V, the anode dissipation is 5.7 W. The circuit power is $0.06 \times 96 = 5.76$ and so the h.t. input power is about 11.5 W. Although much better than this can be done, it is an arrangement which demands no special materials and is free from many of the spurious oscillation troubles which are liable to occur when a transformer is introduced. With a deflector coil which is far from the most efficient the output is sufficient to scan a normal tube at 9 kV.

Uncontrolled Diode

Before we go on to consider the effect of the transformer it may be as well to say something about a circuit which is quite commonly used and which in its basic form is that of Fig. 1 but with the terminals 1, 2 and 3 of A connected together. In other words, it is the circuit of Fig. 1 without the control device A.

It is quite easy to show that in this arrangement both V_1 and V_2 must be conductive throughout the scan if the current in the deflector coil is to be linear. V_1 has to provide a peak-to-peak current of $I_L(1 + r_L/R)$ where R is the diode resistance; V_2 has to carry the current $I_L r_L/R$ in addition to the current resulting from the overshoot and the voltage developed across $R_1 C_1$ must equal the inductive back e.m.f. across L_L less the initial voltage drop at the start of the scan in r_L and R.

If i_p is the peak current in the deflector coil, the peak current in V_1 is $1 + r_L/R$ times as great and the

mean current is $\frac{1}{2} \cdot \frac{\tau_1}{\tau} \left(1 + \frac{r_L}{R}\right) i_p$. The basic efficiency

of the circuit is much lower than with a controlled diode and, unless r_L/R can be made quite small, it may well be poorer than that of the heavily damped circuit.

However, all the surplus current provided by V_1 flows through V_2 into the auto-bias circuit $R_1 C_1$ of this valve. This current is much greater than with the controlled diode and so a greater power is developed in R_1 . When a transformer is used, therefore, there is a

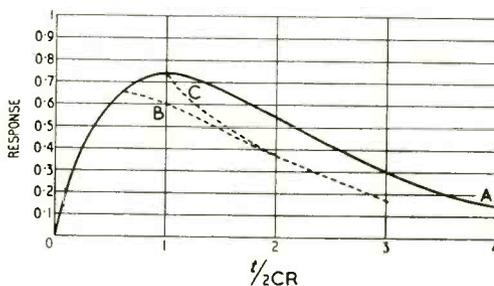


Fig. 8. Response of a critically damped circuit to a sudden change of current is shown by curve A. A second change of current in the opposite direction and of one-quarter the amplitude produces the total result shown by curves B & C for two different intervals between the two changes.

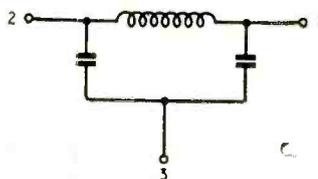


Fig. 9. A common practical form of control network for the diode is shown here. It is inapplicable to the particular circuit of Fig. 1 since it would interrupt the h.t. supply.

greater power available to be fed back as h.t. boost than with the controlled diode and this undoubtedly removes the basic disadvantage of the circuit.

Comparing the two, the controlled diode circuit is very efficient on a current basis and permits a moderate h.t. boost to be obtained. The uncontrolled diode circuit is very inefficient on a current basis, but permits a large h.t. boost. Although basically the less efficient, it may be practically the better circuit in a case where h.t. voltage is the main limitation and plenty of current is available.

In practice, too, it is not necessary to maintain a precisely linear current in the deflector coil. When non-linearity is permitted it is possible to obtain some "current-saving" in the driving valve and the efficiency can be increased appreciably.

So far, we have only considered in detail the directly-fed deflector coil and, as already mentioned, this is very rarely used. A transformer or auto-transformer feed is generally adopted. The next step, therefore, is to consider the effect of this component. Before doing so, however, it is necessary to point out one

practical difficulty that arises with both directly- and auto-transformer-fed coils. With both, the cathode of V_2 is at high potential to earth—up to about 1 kV with direct feed and possibly several kilovolts with an auto-transformer. The heater-cathode insulation of most valves is hardly adequate to withstand this and so the heater must be fed from a well-insulated winding on the mains transformer or, often more conveniently, from a small transformer between the normal heater supply and V_2 .

This is not only a nuisance but it rules out the possibility of d.c. operation of a receiver. It is, therefore, one reason why the use of a double-wound transformer for feeding the deflector coil is so popular. Because there can be a phase reversal between primary and secondary and the diode can be connected to the secondary, the diode cathode can be made earthy. However, diodes rated for heater-cathode peak voltages of as much as 3 kV are making their appearance, and the writer has used metal rectifiers with success. The difficulties of heater supply are thus not at all serious.

(To be continued.)

The Modulation Battle

More Advocacy of A.M. for British Broadcasting

THE long-standing arguments as to the relative merits of amplitude and frequency modulation for British broadcasting were continued at the 4th session of the Brit. I.R.E. Convention, held at Southampton, where J. R. Brinkley (Pye) read a paper entitled "V.H.F. Broadcasting: the case for Amplitude Modulation."

On the question of metre-wave broadcasting in general, the author contended the outstanding merit was its ability to provide multiple programmes, and this advantage should be exploited to the full. Many low-power stations were better than a few of high power, which were inherently inefficient, as attenuation increased rapidly beyond the limits of the optical path.

Mr. Brinkley based his case for a.m. on the twin factors of economics and availability of channels. He


contended that f.m. was inherently more costly; also that for the service he envisaged channels were available on a.m. but not on f.m. To equip the listeners of this country for reception of f.m. would cost about £60 million.

Cheap and satisfactory convertors for f.m. were a virtual impossibility, and the author was highly critical of such units as had already been produced. For amplitude modulation, on the other hand, he claimed the problem could be solved at a cost of about £5, and showed a small 3-valve experimental convertor with crystal control comprising an earth-grid triode as r.f. amplifier, an oscillator-multiplier and a triode mixer. The power requirements of this unit were so small that it could be fed from the supply system of the average receiver. With convertors of this type a.m. broadcasting on metre waves would be compatible

with the existing B.B.C. transmissions, and rapid growth of the metre-wave service might be expected. If the public had to buy completely new receivers, as for f.m., development would be too slow to be effective.

In the discussion that followed, the President of the Brit. I.R.E., Paul Adorian, seemed to express the general feeling by admitting that amplitude modulation had distinct attractions on a short-term basis, especially in view of the present economic situation of the country, but, as a matter of long-term policy and from the engineering aspect, he preferred frequency modulation. Earlier in the session Mr. Adorian had, in his opening address, expressed his belief that the B.B.C. f.m. plan could be justified. It would allow the majority of listeners to use cheap receivers; only those in fringe areas would need expensive sets.

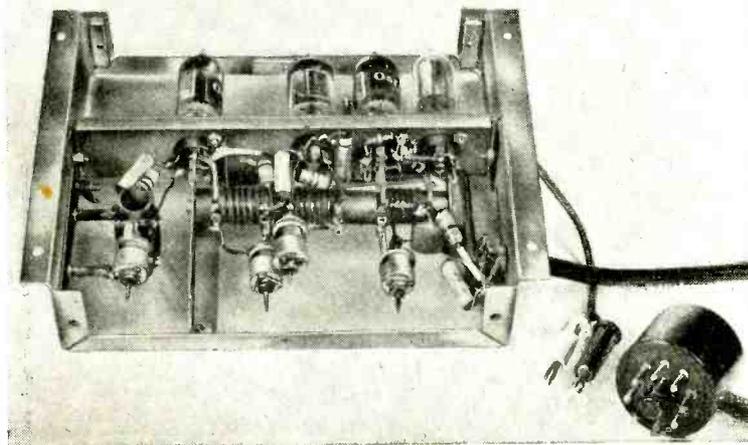Experimental a.m. converter with three triodes and crystal frequency control.



Tens or Twos?

Fingers and Thumbs Don't Count in Electronics

By "CATHODE RAY"

READERS who try to keep up with modern developments, such as electronic calculating machines (or computers) and the newer systems of communication, must surely have come across such terms as a "scale of two" (or some other number) or a "binary scale," and may have wondered what they meant. They may have noticed, too, that some of the best-known radio manufacturers now offer for sale not only such obvious products as receivers and amplifiers, but also mysterious things called "scalers." There are few words even in the English language that have so many meanings as "scale." In this particular context, however, one can hardly suppose that the devices in question are for the processing of fish or crocodiles or even for boiler reconditioning or dentistry. They might conceivably be used in the drawing office, or in the manufacture of measuring instruments, or perhaps be something to do with "scale distortion." But no; this kind of scale is a piece of valve circuitry used in electronic computers and atomic research—among other things. I don't propose to say anything about the circuitry, but will try to explain the rather important basic idea of "scale" itself.

Some time ago I referred to the debt we owe to our system of numerals which we take so much for granted, and how anybody who doubted it should try doing a little simple multiplication in Roman figures. We get so completely used to our system at such an early age that we tend to regard counting in tens almost as a law of nature, and are quite horrified when someone proposes that it would be better to count in twelves and make the sign "100" mean the number we now call 144. Yet there is no reason more binding than widespread custom for making ten the number at which to change from single to double figures, unless it be that most people's fingers and thumbs add up to ten. As the pioneer who invented the dozen probably realized, twelve is a better number than ten on which to base a system, because it is divisible by two, three, four, and six, instead of only two and five.

But that is by the way. The point is that although our familiar decimal (or scale-of-ten) system is used so universally that it has never occurred to most people that there could be any other, we are free to base a system on any number we like. If we adopted the duodecimal or scale-of-twelve system it would be necessary to have two new single figures to stand for ten and eleven, so that the first double figure (10) could mean twelve. On the other hand, a scale of fewer than ten puts some of our present figures out of a job. For the number of the scale is really the number of different values or levels that can be written in single figures. In the scale of ten there are ten: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9. The smallest scale that can be used is two, and it requires only two figures, 0 and 1. All the rest are superfluous.

Although it may be very proper and systematic to expound the nature of a system fully before going on to say how or why it is used, in practice it is very irritating to have to absorb a lot of new information before being able to find out whether it is going to be worth the effort; and in case my rather abstract talk about scales and numerals is engendering a "So what?" attitude among any readers who have not already given up, I had better provide some clue to where all this is leading.

Imagine you are starting to invent an electronic calculating machine. You are using valves so as to get quicker action than is possible with mechanical contrivances. For convenience in reading the answers you connect a milliammeter scaled in whole numbers from 0 to 9 in the anode circuit of the valve dealing with the "units," and similarly for tens, hundreds, etc. The valve is initially biased beyond cut-off, so that the milliammeter reads 0. By means of cunningly devised circuitry you arrange that when the pulses or other signals representing units arrive each one steps up the anode current by 1 mA, and directly 9 mA is exceeded the "units" valve flops back to the start and at the same time sends a signal to the "tens" valve to make it read 1. This is what mileage indicators and other counters do mechanically.

Before long you would probably decide that it might be a waste of time going any further in working out the details of such a system, because it would need a lot of setting up to make all the milliammeters read the whole numbers correctly all over their scales, and it would also be necessary to have all their supply voltages very effectively stabilized, otherwise the readings would go all haywire whenever the electricity people decided to start shedding voltage. And even then one could never be sure that the slope of at least one of the valves had not drifted half a milliamp or more—enough to raise a doubt as to which number was meant.

Twos are Better for Valves

For the really terrific calculations that justify the expense of electronic computing machines it just wouldn't do to have any risk of slipping a whole number here and there, perhaps in the billions column. A valve is all very well, but one is unwise to rely on it to click with mathematical precision and mechanical rigidity into ten different levels on its characteristic curve. The fact that it actually is curved and not straight is another difficulty. And it is taking a risk to expect the triggering action to distinguish infallibly between 9 mA and 10.

It is not, however, asking too much of a valve to expect it to distinguish between "off" and "on." The bias for "no current" can be made as negative as is necessary to ensure such a condition no matter how much the valve characteristics or the voltages are

off-centre; and so long as the current is large enough in the other condition to be recognizable as a current, it doesn't matter (within reason) how much more than the minimum it is. So non-linearity is of no account whatever, nor are drifting voltages or valve characteristics, so long as the valves can still pass any current at all. On this basis the whole thing is as reliable as it possibly can be. ●

And that is where the scale of two, or binary scale, comes in. Since it has only two varieties of figure, 0 and 1, its whole scale is fully represented by the two conditions "off" and "on." And yet the system can count up to any number, the only inconvenience (apart from its unfamiliarity) being the larger number of figures or digits, and hence valves.

Let us see how it works out. *Nought* is, of course, denoted by 0 everywhere. And *one* is denoted by 1. There is no such thing as "2," so adding another *one* means carrying to the next—the "twos"—column, where a 1 appears, and the 1 in the units column is cancelled. This procedure is exactly what we do in the decimal system when adding *one* to *nine*.

Let us see how it works out. *Nought* is, of course, denoted by 0 everywhere. And *one* is denoted by 1. There is no such thing as "2," so adding another *one* means carrying to the next—the "twos"—column, where a 1 appears, and the 1 in the units column is cancelled. This procedure is exactly what we do in the decimal system when adding *one* to *nine*.

Adding another *one* brings 1 back into the units column, so we have "11." (In the decimal system that symbol denotes one *ten* plus one *one*—eleven; in the binary system it denotes one *two* plus one *one*.) Adding the fourth *one* clears the units column again, as the *two* there is carried to the twos column; and as that makes two twos it also is cleared and carried to the next—the "fours" column. Result: 100 (to be read as "one—0—0"). And so on, like this:—

Ordinary or decimal number	Binary scale number
0	0
1	1
2	10
3	11
4	100
5	101
6	110
7	111
8	1000
9	1001
10	1010

By now you will probably have caught on to the thing enough to realize that the next column after the "fours" shows the absence or presence of an eight in the total; the next, a sixteen, and so on. For example: "1001101" in the binary notation would mean $(1 \times 2^6) + (0 \times 2^5) + (0 \times 2^4) + (1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) = (1 \times 64) + (0 \times 32) + (0 \times 16) + (1 \times 8) + (1 \times 4) + (0 \times 2) + (1 \times 1) = 64 + 8 + 4 + 1 = 77$. (Remember that any number to the power 0 is 1.)

Now, you may say, nobody except perhaps a music-hall "lightning calculator" could tell straight off that "1001101" was the number that in the decimal system is called seventy-seven. How can anybody be expected to know without working it out that the seventh figure from the right is a sixty-four, and so on for the others, and that the total comes to seventy-seven? On the decimal system one can see it straight off! Well, admittedly arithmetic in the binary system is less concise, owing to the larger number (though smaller variety) of figures needed; but the duodecimal system certainly wouldn't be open to this criticism, yet people would still complain that it would mean calculation with the twelve-times table to find that "77" meant the number that we call "ninety-one." They would say that with tens it is, of course, quite easy, because they are—well, tens!

Yet really it is just a matter of habit, and if we had

been brought up from infancy to count in twelves or thirteens or threes, with the symbols and names appropriate to the system, it would seem very odd to count in tens. It is really no easier (except as a result of practice) to tell that the number 534 is equal to five hundreds plus three tens plus four than to interpret it as five gross plus three dozens plus four. The difference we make is that we immediately start converting the latter into the decimal number, 760, because we have been accustomed to knowing how many "760" means, and would have difficulty in associating it with the figures "534."

Using Twos for Communication

Though it would be very muddling to introduce the duodecimal or binary or any other non-decimal scale of counting into everyday life, we have seen that the binary system (for example) has distinct advantages for special purposes such as electronic computing. The solution, if the advantages are worth it, is to translate or code the decimal notation into binary for the purposes required, and then back again into decimal when those purposes have been accomplished. After all, this is no more novel than translating the letters of the alphabet into dots and dashes for the purpose of long-distance communication, and then back again.

Originally the morse code was invented because at that time nobody had discovered how to send spoken words by wire in the form of the original sounds, so there was nothing for it but to translate them into signals. But seeing the obvious inconvenience of this indirect method, with its extra process at each end, one might suppose that now line and radio telephony have reached such an advanced state of development code telegraphs would be as obsolete as sending messages by lighting fires on the tops of hills. Nevertheless, the greater part of telecommunication other than domestic radio and telephone is done by telegraphy. Why?

You can appreciate one of the main reasons by considering the output stage in your broadcast receiver. Suppose it is capable of an output of 1 watt without serious distortion from overloading. And suppose you adjust the volume control until the announcer's voice is just reaching this limit at its peaks. Even if he is reading the news in his usual level tones, you might be surprised to know how little the *average* power is. I tried measuring it during sentences of speech (so as not to bring the average down by including the zero power between sentences) and found it to be about one-twelfth of what it would have been if the peak amplitude had been kept up all the time. And, of course, some sounds are reproduced at far less than the average—about one-seventieth in my experiment. I don't claim that these figures are highly accurate—in any case they depend a good deal on the speaker—but they probably represent typical conditions in the transmitter.

That may be all very well for broadcasting, where dozens or even hundreds of kilowatts are used to cover quite moderate distances, and millions of people are contributing all the time to pay for them. But for communication pure and simple the aim is certainty of reception under all conditions, at the minimum cost. The ultimate limiting factor is signal/noise ratio. In telegraphy the sender is either radiating at full power or not at all, and all the receiver has to do is tell which is which. But in telephony one has to provide for handling many times as much power

during the peaks in order to bring the quietest bits well above noise level. They have to be well above, because it is not just a matter of distinguishing between signal and no-signal but between, say, "m" and "n" sounds. Otherwise one is reduced to "m for monkey, n for nuts," etc., and progress is so slow that one might as well use morse and be done with it.

So telegraphy is much more economical and reliable than telephony. But the convenience of being able to speak into a sender and hear the voice come out of the receiver is so obvious that inventors have tried to combine it with the advantages of an on/off signalling system by devising automatic speech coding. The morse code, or any other based on letters and words rather than sounds, makes things very difficult because it necessitates a sort of robot shorthand-typist to translate the sounds of a voice into words; and even a human listener may find that difficult if the speaker comes from another part of the country! So the problem remains unsolved. A more practicable scheme is to make the signalling code mean sounds instead of letters, and this has actually and successfully been done in the Vocoder, which I described briefly some while ago.* The idea behind the Vocoder was not so much the improving of signal/noise ratio as the reduction of the frequency band required by the voice communication channel.

And that is rather a different story. Just now let us stick to the one idea of getting the best possible signal/noise ratio—and hence the longest range for the lowest power—by using simple on/off signals. How can the infinitely graduated amplitudes of speech waveforms, for example, be translated into such simple signals?

If you transmit the waveform of any sound, you can reproduce the sound. For example, if Fig. 1 represented a specimen of a sound waveform you could transmit it by causing the current in a telephone line to have the same waveform. Alternatively (though it would hardly be a practical proposition) you could plot a graph of the waveform on a long strip of paper, make a list of the ordinates (the heights of points on the graph above or below the baseline) at close enough intervals to enable the graph to be replotted at the receiving end, and send them there by telegraph. Taking the first half-cycle of Fig. 1, for example, you would wire the numbers 0, 19, 38, 60, 76, 83, 69, 52, 14, 10, 0, from which the recipient could replot that half cycle; and so on for the rest of the job. The sound could be reproduced from this graph in the same way as the sound track on a film.

This is where we join on to last month's story, which had got to showing how waveforms can be communicated by a series of pulses, sampling the waveform at intervals close enough to include at least two within the shortest wavelength present. In other words, the sampling frequency has to be more than twice the highest frequency to be transmitted. What this sampling amounts to is a particular method of signalling the graph ordinates: they are represented directly by the amplitude of the pulses. To signal the waveform with reasonable accuracy it would probably be necessary to detect amplitude variations down to 1 per cent of the highest peak. So for the smallest pulses to be distinguishable above the noise level it would be necessary for the largest to be 100 times greater in amplitude, or 10,000 times greater in

power, than would be necessary to override noise.

So this method of sampling shares the power-wasting characteristics of the original waveform. Theoretically the numbers could be signalled in morse, but seeing that for tolerable speech quality it would be necessary to send at least 10,000 double-figure numbers per second it might be rather difficult to decode them back again into waveforms! The decoding problem could be simplified if the wave amplitudes were represented by variation in pulse duration. With the 100-unit scale we are assuming that would be equivalent to having anything up to 100 of the shortest pulses side by side (Fig. 2(b)). If the sampling frequency were 10,000 per second, each sample would have to take place within 1/10,000th sec, or 100μ sec, so the shortest pulse could not at the outside be more than 1 μsec. That would necessitate a bandwidth of over 1 Mc/s right away, for rather poor quality sound, and for only one channel!

But we have already seen that in the binary scale a 7-digit group permits counting in units up to $1 + 2 + 4 + 8 + 16 + 32 + 64 = 127$, or rather better than the 100-unit scale we have been assuming as a necessity. So any one of 128 different amplitudes (including 0) can be signalled by a group of seven pulses or

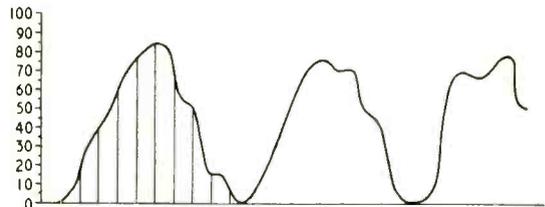


Fig. 1. If sound is transmitted electrically in its own waveform, its peak power must be many times greater than noise and interference, to ensure that the low-amplitude details are not lost.

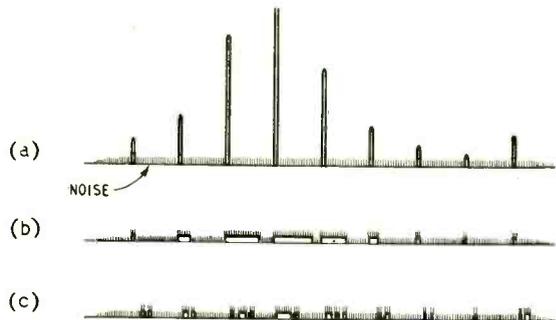


Fig. 2. When the waveform "plots" are signalled by the varying amplitude of pulses (a) it is still necessary to use a comparatively very high power to ensure that the smallest pulses are distinguishable from noise. If, to avoid this, pulse duration is varied (b) the large variations needed demand a very wide frequency band, to transmit the narrowest pulses. But in p.c.m (c) a 128-level range is compressed into a group of only seven equal-sized pulses or spaces.

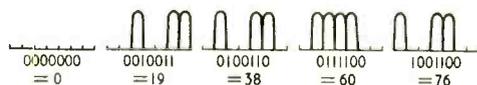


Fig. 3. A close-up of the Fig. 2.(c) type of binary-scale signals, being those necessary to communicate the first five points in the Fig. 1 waveform.

* "Channels of Communication," *Wireless World*, July, 1947.

no-pulses, as in Fig. 3, which represents the first five amplitudes in Fig. 1. Some signals of this type are also shown in Fig. 2(c) for comparison with (a) and (b). A method of decoding has been worked out, and a 12-channel telephone installation demonstrated successfully. • The system, which is called pulse code modulation (p.c.m.) was described in *Wireless World* by Thomas Roddam (March, 1949, p. 82).

What p.c.m. does is to obtain an enormous economy in power for a very moderate price in bandwidth. On the basis of our calculation (which admittedly is oversimplified, but gives the general idea) a sevenfold increase in pulse frequency and therefore of bandwidth allows a 127^2 or sixteen-thousand-fold saving in power. So long as the difference between signal and no-signal can be detected at all through noise and interference, there is no point in using any more power. And whereas frequent relaying of speech, etc., in the usual form causes noise to accumulate at each stage, the p.c.m. signals can be re-formed and cleared of noise and distortion at every stage in a long transmission. But, of course, a system of this kind would not be popular for broadcasting, because the automatic decoding gear would put up the cost of receivers. In a point-to-point system, with only one or two receivers, that is negligible compared with the saving in cost of the sender. Incidentally, there would seem to be nothing to prevent this p.c.m. system being applied to the special low-frequency signals of the Vocoder†.

As a matter of interest, let us find the general rela-

† *Journal I.E.E.*, Part III, Sept., 1948, p. 404 (8.2).

tionship between number of digits and number of numbers in a binary group. We have already found that a seven-digit group gives a choice of 128 numbers. That is because the first digit gives a choice of two numbers; for each of them the second digit gives a choice of two, making 2^2 in all; for each of them the third digit gives another choice of two, making 2^3 . And so on; D digits can count 2^D numbers, say N:

$$N = 2^D$$

Another way of writing this is $D = \log_2 N$.

Increasing D from 7 to 8, only about 14 per cent, increases N 100 per cent. And, as we have seen, N is bound up with the signal/noise ratio and minimum transmitter power. So it is very interesting that the Hartley Law ($M = kBT$) in its modern form makes $k = \log_2(R+1)$, where R is the signal/noise power ratio. It follows that the way in which information is organized for transmission by p.c.m. agrees in principle with the ideal. For example, you can theoretically divide the bandwidth (B) needed to transmit a given amount of information (M) in the seven-pulse groups shown in Fig. 3 by seven, by transmitting it in single pulses (Fig. 2(a)), but the single pulses have to be recognizable at 128 distinct amplitudes, so the signal/noise ratio must be vastly greater. In this way the maximum amount of information that can be communicated by an ideal system depends not only on bandwidth and time but also on signal/noise ratio. But as it is proportional to the logarithm of this ratio, a very large change in signal power is needed to make much difference in the rate of information.

High-Power Klystron

5 kW Output at 500 Mc/s

THE centre-piece in the accompanying illustration is an experimental high-power klystron amplifying valve developed by Varian Associates in collaboration with General Electric of America for use as the output stage in a high-power 500-Mc/s television transmitter. This valve is at present known as the Type Z-1891.


The theory of operation of the klystron is fairly well known, but a brief explanation of this particular valve may be of interest. It has three resonant cavities in cascade through which the electrons pass on their way from cathode to the catcher, or anode. Divergence of the beam is prevented by an external magnetic field.

When an r.f. input signal excites the resonant input cavity the electrons are "bunched," or velocity modulated, so that they travel in concentrations or groups. In passing through the following resonant cavities some power is extracted from these bunches, the operation being such that the power transferred to the output cavity is very much greater than that required to velocity-modulate the beam at the input cavity. Thus the valve behaves as an amplifier capable of very high gain at extremely high frequencies.

As a final broad-band amplifier in a vision transmitter, where the output response is required to be flat to within 1 db over a range of 5 Mc/s, a gain of 50 times is claimed, while in an accompanying sound transmitter, where a relatively narrow band suffices, gains of the order of 5,000 are said to be attainable. Under either condition of operation the output power is said to be 5 kW.

Modulation in the foregoing description means the "bunching" of the electrons; not modulation in the more generally accepted sense by sound or vision signals. This takes place in an earlier stage of the transmitter and the high-power klystron behaves as a linear amplifier.

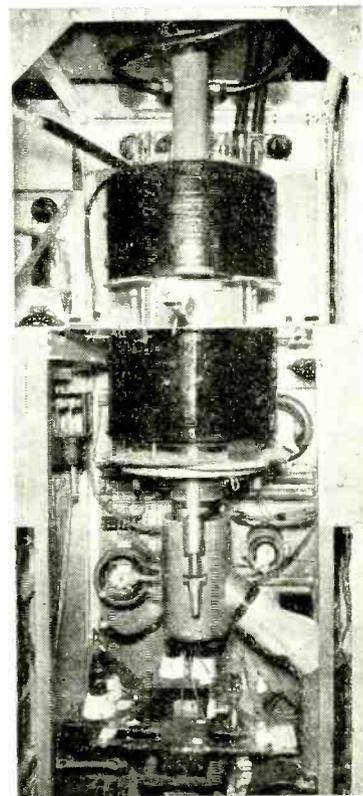Pure electron coupling exists in this valve with complete isolation of input and output circuits. The valve is water cooled.



Recording Studio Design

General Principles and Their Application to Small Rooms

By P. A. SHEARS

IN sound recording the studio provides the link between the matter to be recorded and the microphone. It is no less a part of the apparatus than the recording equipment, and equally can make or mar the overall performance; its contribution is therefore worth investigating.

Reproduction of sound over a microphone-loudspeaker system, whether or not recording is interposed, differs from direct listening in several respects. The most apparent of these is that a monaural—single-channel—system combines in the microphone the direct and reflected sound, so the listener cannot exercise his normal faculty of directivity and thus cannot distinguish between sound proceeding directly from the source and that reflected from the walls and objects in the studio. Once the direct and reflected sounds are combined they cannot be separated again; the final quality of the studio output thus depends greatly on the quality of the reflected sound, which appears as reverberation and as an apparent modification of frequency response.

Typical Defects

In practice, moreover, the reflected sound may be emphasized owing to a limited frequency range in the reproducing equipment. Suppose that a studio is bass-heavy due to excessive reverberation at low frequencies; while this defect might not be serious when observed on the relatively wide-range monitor loudspeaker of the recording equipment, when reproduced on an instrument limited to, say, 4 kc/s range, the excessive bass is no longer balanced by high frequencies and a recording may become unrecognisable. Some recording equipments have a bass-cut control which can alleviate this trouble. Frequently, the response of a device is peaked near the limits of its range to give an illusion of greater frequency range; this is done in the case of the ordinary radio loudspeaker and cheapens the whole set. However, if this method is adopted in recording to cover up studio defects, the result may sound quite different on different reproducers; a studio low-frequency resonance may coincide with a loudspeaker resonance on one reproducer and yet be cut off on another. The same applies to variations in high-frequency response. A high-quality loudspeaker in the recording room is of no help, since a response "cooked" to sound balanced over a wide range still is not necessarily balanced over the smaller range of a home reproducer on which a recording might be played.

However, even if the frequency response could be corrected, a bad studio will still introduce a distortion in time. In addition to reverberation prolonging sounds in general, standing waves may be set up in the air or in the structure of the studio which decay relatively slowly. If these or their harmonics coincide or beat with frequencies from the source of sound, a confusion

arises which, for example, makes certain pianos unusable in certain studios. Transients produced at the commencement of a note by the impact of the hammer on the strings may excite modes of oscillation in the room which are reproduced as dull thuds; also, harmonics may become changed in relative amplitude, thus changing the character of the sound.

These defects originate within the studio and can only be remedied in the studio itself. The studio characteristic is three dimensional—amplitude, frequency and time. If the studio is not to upset the balance of high and low frequencies it must clearly

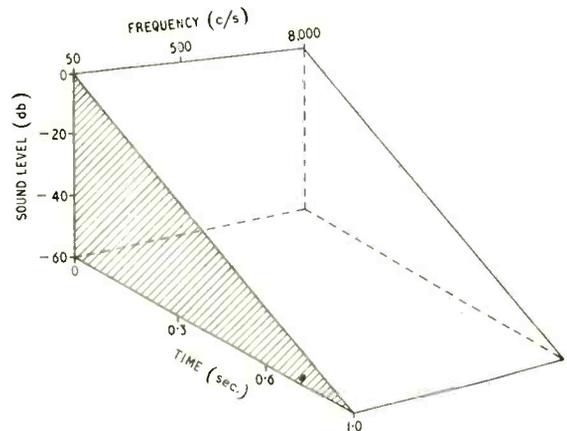


Fig. 1. Idealized reverberation characteristic of a studio.

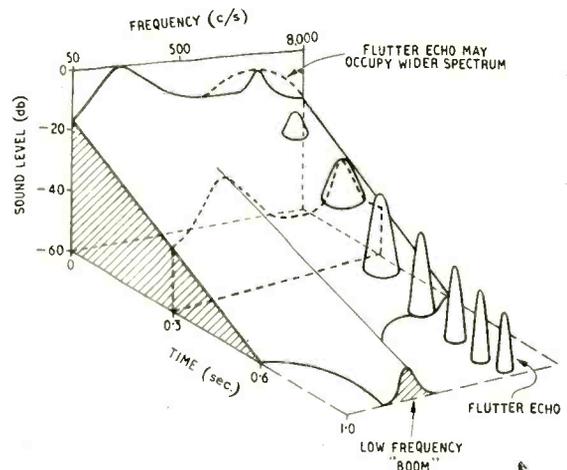


Fig. 2. Reverberation curve illustrating two typical defects in studios.

have a reverberation curve which remains flat throughout the period of decay of a sound. Fig. 1 shows a flat characteristic while Fig. 2 shows a typical pair of defects — an excessive reverberation time at a low frequency and a "flutter echo" due to high-frequency reflections.

The effect of these defects may be reduced somewhat by directional microphones. The ribbon microphone picks up some 6db less reflected sound at low and middle frequencies than the moving-coil type; but the latter also becomes directional to the extent of some 6db, above a few thousand c/s (Fig. 3). However, the fact that the ribbon microphone may


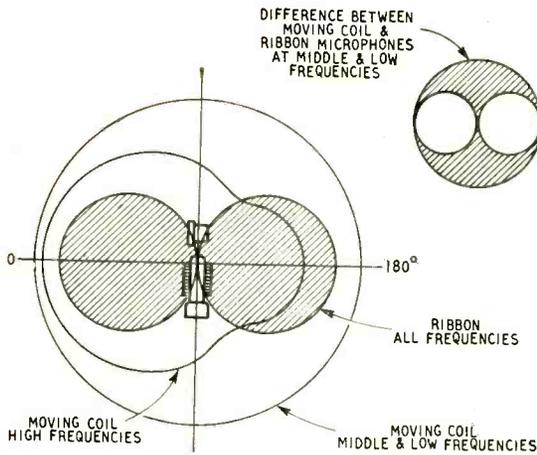


Fig. 3. Illustrating the directivity of ribbon and moving-coil microphones.

Fig. 4. Optimum reverberation time in terms of volume (based on figures given by Kirke and Howe, J.I.E.E. Vol. 78, p.404 1936).

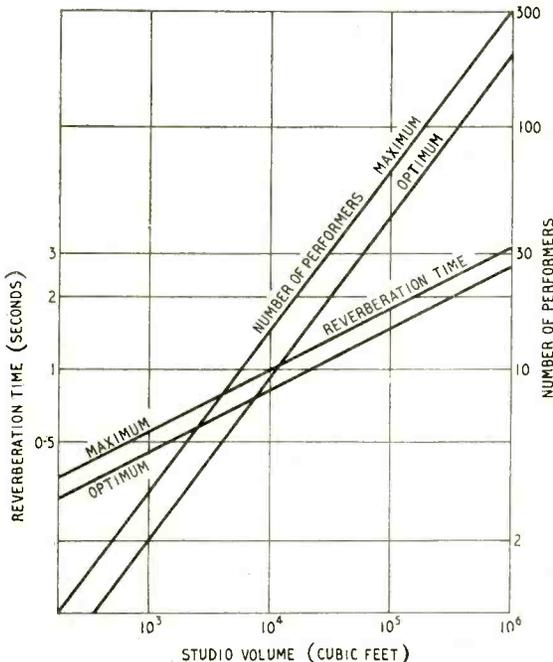

be positioned to avoid picking up from a certain direction, and its better frequency response, have resulted in its more general use.

Reverberation Time

A range of 50-8000 c/s, at any rate on the axis of the loudspeaker, is generally regarded as the minimum for good quality reproduction. The studio should therefore perform satisfactorily over this range, which means in practice (apart from echoes and other anomalies which must in any case be removed) that the reverberation time at any frequency within these limits should not exceed a certain value.

The optimum absolute value of the reverberation time, defined as the time taken for the sound to decay by 60db, depends on the size of the studio and the use to which it is to be put. Fig. 4 has been plotted as the average time for a number of successful concert halls, and extrapolated downwards gives a guide to studio times. Speech generally requires a shorter reverberation time than music; also studios require a shorter time than halls for live performances due to an apparent increase in reverberation time on account of monaural transmission—the ear cannot discriminate against reflected sound; and because the listener's room itself contributes some reverberation. Singers and violinists often prefer a room with a longer reverberation time than the optimum for recording since they can then judge their own tone by listening to the reflected sound. In a large hall this reflection, though too weak to interfere with recording, occurs long enough after the original sound to be audible to the performer. If the reverberation time of a small studio is increased to give a similar effect however, the loudness of the first reflections of sound at the microphone retains the characteristic quality of the sound as that from a small studio. A small studio cannot successfully be made to sound like a large one.

The reverberation time at any given frequency may be adjusted by the amount of sound absorbing material in the room, and may be calculated from Sabine's formula :

$$\text{Reverberation time } T = \frac{0.05 V}{S_1 x_1 + S_2 x_2 \text{ \& etc.}} \text{ seconds}$$

where V is volume of studio in ft^3

$S_1 S_2$, etc., are areas of absorption material in ft^2

$x_1 x_2$, etc., are coefficients of absorption of materials

For coefficients of absorption greater than 0.5 Eyring's version is to be preferred :—

$$T = \frac{0.05 V}{S_1 \log_e (1 - x_1) + S_2 \log_e (1 - x_2) \text{ etc.}}$$

This formula is independent of frequency and suggests that a uniform absorption is required over the frequency range to produce a level reverberation characteristic. However, although the absorption of high frequencies by the air can usually be neglected, at low frequencies standing waves may be set up in the studio, generally referred to as "eigentones." In large studios (10^5 ft^3) the fundamentals of these are of very low frequency but in small studios (3000 ft^3) objectionable modes may lie in the range 50-150 c/s. Their frequencies may be calculated precisely, but a rough guide can be found by regarding one half wave length as occupying the distance between opposite walls, or floor and ceiling. There are thus three fundamental modes corresponding to the length, breadth and height of the studio. These, together with any unpredictable structural resonances which may

occur make it desirable that, rather than have a level reverberation characteristic at low frequencies, these frequencies should be absorbed as much as possible.

The frequency of an eigentone may be calculated from :—

$$f = \frac{c}{2} \left(\frac{p^2}{l_1^2} + \frac{q^2}{l_2^2} + \frac{r^2}{l_3^2} \right)^{\frac{1}{2}}$$

where c = velocity of sound = 1130 feet/sec, p , q and r are integers from 0 upwards, and the fundamental mode in any one direction is given when the corresponding integer (p , q or r) is made unity. For example, the fundamental mode in say the l_1 direction is given then $p = 1$ and q and $r = 0$.

The formula then reduces to :—

$$f = \frac{c}{2l_1}; \text{ or } \frac{1130}{2l_1} \text{ (} l_1 \text{ being in feet).}$$

This mode corresponds to a half-wave lying in the l_1 direction in the studio, with pressure antinodes at the end walls. To find other modes the appropriate values of p , q and r are inserted and a hundred or so alternatives may well arise below 500 c/s.

The crux of the problem of small studios is that these low-order eigentones are within the audible range; for it is these that, because of their large dimensions in relation to the dimensions of the room, are most difficult to absorb or break up.

Provision of Absorption

The curves in Fig. 5 show that the textiles encountered in most living rooms absorb principally high frequencies. These can be used therefore for this purpose in studios, but they are liable to collect and produce dust which may be a nuisance, and professionally, specially made absorbent tiles which can be distempred are often preferred. However, some grades of ordinary insulating board absorb high frequencies to about one-third of the extent of these special absorbers and may suffice where a large enough area can be provided. Also this may be cheaper, if, as is frequently the case, panels of insulating board can be arranged simultaneously to absorb low frequencies by resonance. Resonant absorbers, though practically the only means of absorbing low frequencies, are cheap and simple to construct and may be painted without impairing performance. Basically these consist of a flexible panel mounted several inches from the wall, usually upon battens, thus enclosing an air space in which some absorbent material is provided. If absorption of low frequencies only is required the panel must be sufficiently heavy, and hard enough mechanically to reflect high frequencies; in electrical terms the impedance at the surface of the material must be high enough to reflect high-frequency sounds. At low

frequencies the panel must be flexible enough—i.e., of low enough mechanical impedance—to vibrate over an adequate area to couple the absorbent in the air space to the air in the studio. Part of the energy is dissipated here, and part in the internal damping of the panel material itself. The electrical analogy is a damped acceptor circuit, and the construction is shown in Fig. 6.

The panel may be of various materials from paper to building board, or insulation board, and rock wool may be used around the perimeter of the air space to provide damping. In the case of a panel of thick


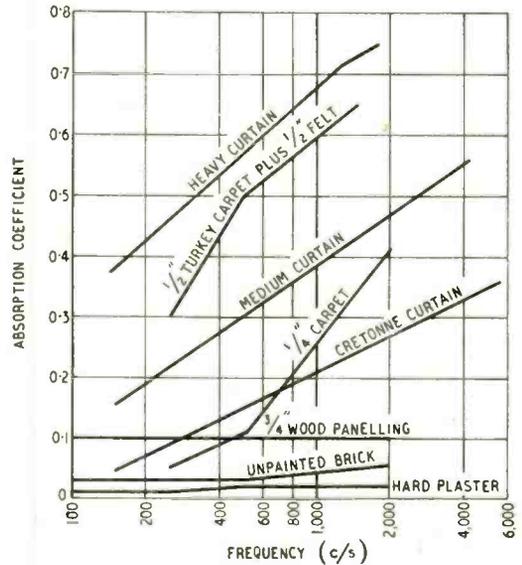


Fig. 5. Absorption coefficients of some typical materials (based on data from reference 5).

Fig. 6. Absorbent panels and their electrical equivalent circuits.

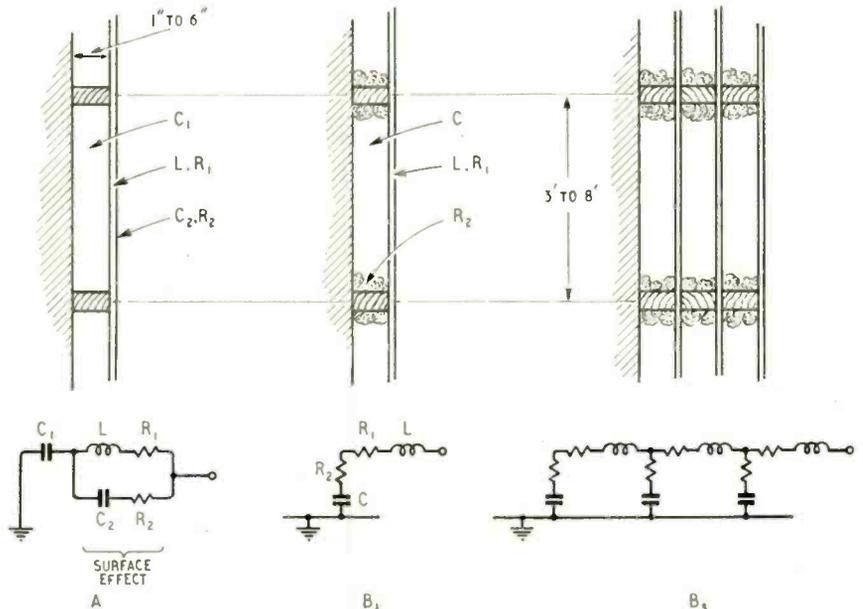


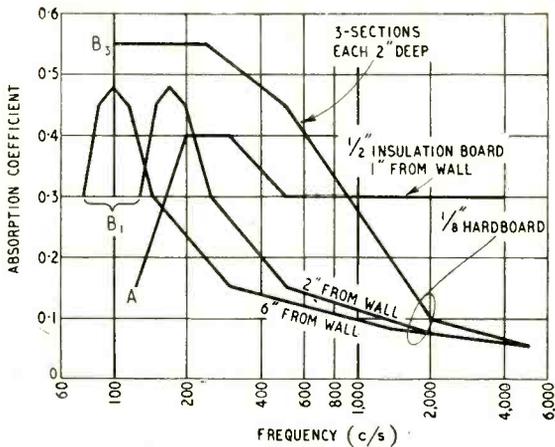
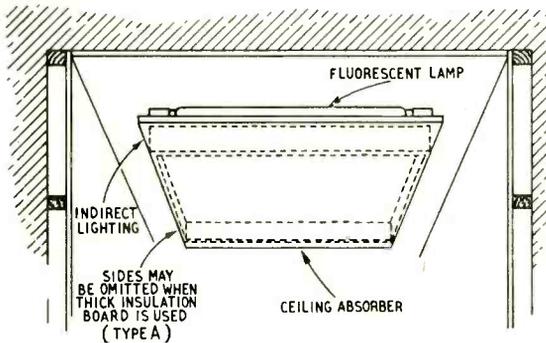


Fig. 7. Characteristics of some resonant absorbers (based on data from reference 5).

Below : Fig. 8. Ceiling absorption unit.

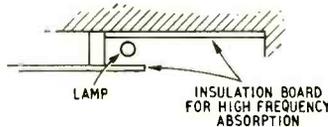

soft material this latter may be unnecessary owing to high internal damping in the panel.

Curves for typical absorbers are shown in Fig. 7. A is a curve obtainable with a $\frac{1}{2}$ in thick soft insulating board ; B₁ a curve for an $\frac{1}{8}$ in thick hard board ; and B₃ a 3-layer absorber of the same board as B₁ analogous to a 3-section filter incorrectly terminated. The difference in high-frequency absorption of the two materials is clear. The choice of panel material usually depends on the amount of high-frequency absorption required, the mounting and spacing from the wall controlling the low-frequency absorption.

The spacing from the wall is given by :—

$$d = \frac{29,900}{f^2 w}$$

when

d = distance of panel from wall in inches

w = weight of panel in lb/ft²

f = frequency of maximum absorption

Fixing centres of the battens must not be too close, otherwise the vibration of the panel will be interfered with, reducing the absorption coefficient at the resonant frequency. The centres should be varied

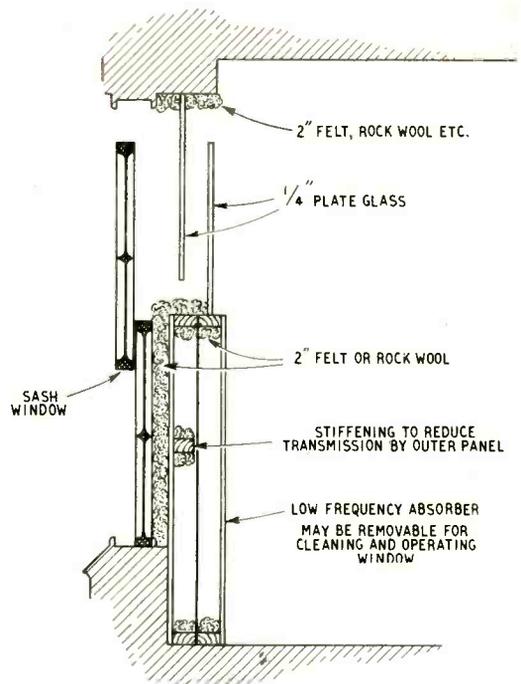


Fig. 9. Window treatment to admit light and air combined with low-frequency absorber. Sound insulation is about 40db closed and 25db open.

somewhat throughout the studio—3 to 8 feet is a suitable range.

In medium-sized studios such as that in the example in Fig. 10 the eigentone fundamental frequencies may be below 50 c/s, for which inconveniently large absorbers would be required. However, provided that the response of the recording equipment falls off fairly sharply outside the working frequency range these very low frequencies may be ignored. In magnetic recording the problem seems less important, but the author experienced one case in disc recording where a guitar band so strongly excited an eigentone of about 25 c/s that the resultant patterning of the disc prevented satisfactory playback.

Normally, the resonant panelling may be tuned to the lowest eigentone frequencies in the working range. The spacing from the wall will depend on the grade of board used and may be calculated from the formula given above, and will usually be between 1 and 6 inches depending on the frequencies to be absorbed.

Distribution of Absorption Material

In most cases of small studios it will be found necessary to cover the greater part of the interior surface of the studio with treatment. This is especially so when converting ordinary rooms to studios, since studios constructed as such generally have thin floors specifically for absorbing low frequencies. If the floor is concrete or heavy board some treatment must be applied to the ceiling.

This follows the general rule that absorbers are not effective for directions of propagation parallel to their surface. A floor-ceiling mode of resonance is scarcely affected by material on the walls. This

means that at any rate three surfaces, one in each plane, must be treated; and as absorption is only about 30 per cent it is desirable that all surfaces should carry some treatment.

It will usually be found that some of the low-frequency absorbers must reflect high frequencies if the high-frequency reverberation time is not to be reduced excessively. If this panelling is located on the live end—the lower half of the walls, furniture will help to disperse direct reflections between opposite sides. At a higher level—say about 4ft from the floor, hard reflecting surfaces should not face one another.


If these hard surfaces are grouped principally near one end of the studio—the “live” end—while curtains are provided at the other “dead” end, a useful variation in effects can be produced. Usually, however, the performers will occupy the live end and the microphone a position towards the dead end. If the floor is carpeted this should be arranged to roll back from the live end, but the ceiling above must carry some absorbent (Fig. 8).

Various sound insulating schemes will be found in textbooks to permit windows to be opened without admitting noise. Fig. 9 shows the type of arrangement. For the purpose of calculation the noise in the studio should not exceed 20 phons. The recording equipment must be in a separate room for monitoring and to avoid distracting performers, and a double window between may be found necessary to avoid acoustic feedback. A threshold condition of “singing” must be avoided at all costs as this modifies the frequency response. It is worth remembering that the least crack around a door or window transmits a considerable amount of sound and any insulating door or window must be made literally air-tight, with rubber or felt.

An Example

A room 20ft × 15ft × 12ft high with hard plastered walls and coconut matting over floorboards is to be converted to a studio.

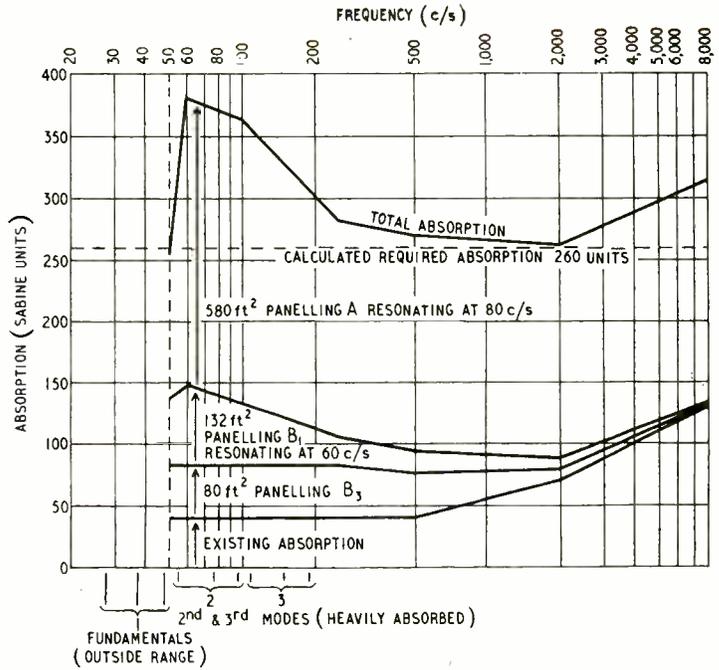1. Volume = 3600 ft³
From Fig. 4 reverberation time not to exceed 0.7 sec.



Above: Fig. 10. Absorption and reverberation calculations for the studio (Fig. 12) considered in the example.

Right: Fig. 11. Calculated reverberation frequency curve (1) from data of Fig. 10, (2) with alternative treatment of 660ft² of insulation board on 2-in battens.


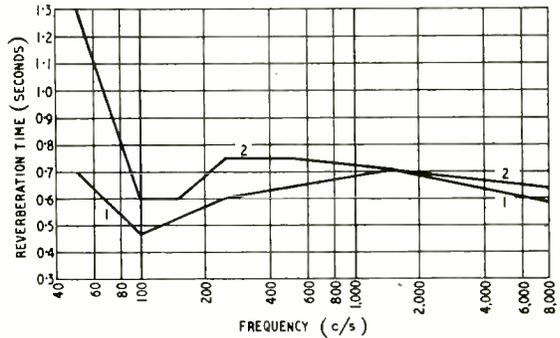


Fig. 12. Suggested layout of room 20ft × 15ft × 12ft treated according to calculations in the text.

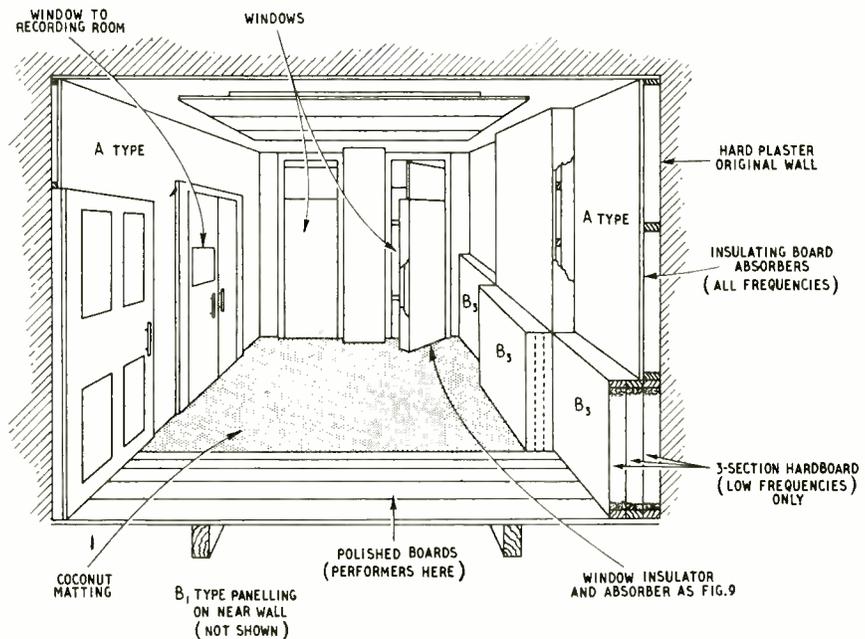

2. From $T = \frac{0.05 V}{S_x}$, $S_x = 260$ Sabine units

3. Calculate first eigentones :

$f = \frac{1130 \text{ c/s}}{2l}$, where l = length, width, height in feet respectively

TABLE
Absorption in Sabine Units.

Frequency (c/s)	50	60	100	250	500	2000	8000
Floor (300ft ²)	{ Coefficient ...	0.1	0.1	0.1	0.1	0.1	0.4
	{ Absorption ...	30	30	30	30	60	120
Doors (100ft ²)	{ Coefficient ...	0.1	0.1	0.1	0.1	0.1	0.1
	{ Absorption ...	10	10	10	10	10	10
Existing absorption (P) ...	40	40	40	40	40	70	130
Type B ₂ panelling (80ft ²)	{ Coefficient ...	0.55	0.55	0.55	0.55	0.45	0.1
	{ Absorption (Q) ...	44	44	44	44	36	8
Type B ₁ panelling (132ft ²)	{ Coeff. when resonating at 60 c/s	0.39	0.48	0.36	0.17	0.14	0.08
	{ Absorption (R) ...	52	63	48	22	19	10
Type A Insulation board (580ft ²)	{ Coeff. when resonating at 80 c/s	0.2	0.4	0.4	0.3	0.3	0.3
	{ Absorption (S) ...	116	232	232	174	174	174
Total absorption (P+Q+R+S) ...	252	379	364	280	269	262	313

4. Calculate absorption : (see Table above)

(1) Existing absorption.

Floor : $15 \times 20 = 300\text{ft}^2$

Absorption coefficient—below 200 c/s as for $\frac{3}{4}$ -in panelling (0.1), above 500 c/s estimated absorption of coconut matting half that of $\frac{1}{4}$ -in carpet (see Fig. 5).

Doors : 100ft^2 . Absorption coefficient 0.1.

(2) 3-section absorbers for a band of low frequencies. As these are bulky they must be

fitted into the room structure as convenient, and their area is thus predetermined, e.g., 80ft^2 , coefficient of absorption as Fig. 7.

(3) Panelling to absorb low frequencies only—Type B₁. The amount of this is chosen so that total absorptions at low and high frequencies are as nearly as possible equal. 132ft^2 was found to be a convenient area in the example.

(4) The remainder of the absorption is provided by insulation board which to some extent absorbs all frequencies, the low-frequency resonance being adjusted to absorb the respective eigentone of the wall concerned. This resonance is fairly broad and a uniform spacing from the various walls will often suffice and save cost (see Fig. 7).

(5) Plot total absorption and check final reverberation time.

Figs. 10 and 12 show the absorption provided in a fully treated studio. Fig. 11 shows (curve 2) the

rise in bass reverberation time resulting from the use of a cheaper arrangement of panelling—which does not fully absorb the low frequencies. Curve 1 corresponds to Fig. 10.

References.

1. Meyer, "Electroacoustics" (Bell).
2. Wood, "Acoustics" (Blackie).
3. Hope-Bagenal, "Practical Acoustics" (Methuen).
4. Cullum, "The Practical Application of Acoustic Principles" (Spon).
5. Constable and Constable, "Principles and Practice of Sound Insulation" (Pitman).
6. Moir, "Acoustics of Small Rooms," *Wireless World*, Dec. 1944.

NEW BOOK

The Testing of Hearing Aids (Booklet No. 490), by D. B. Fry and P. Denes. Pp. 39 with 11 illustrations. The National Institute for the Deaf, 105, Gower Street, London, W.C.1. Price 1s.

THE task of evaluating the performance of a hearing aid in general terms and on the basis of objective measurements is a formidable one. In view of the wide diversity of hearing defects and the range of age and aptitude in patients, one might be justified in thinking the difficulties insuperable. However, by limiting the problem to the transmission of intelligible speech and by carrying out large numbers of tests under carefully controlled conditions, workers both in this country and America have arrived at an optimum performance specification which appears to be independent of the particular type of deafness involved and which serves as a satisfactory basis for correlating subjective judgment with objective measurement.

In this book the authors give a well-reasoned argument, supported by references to the work of the Medical Research Council, the Harvard University report on hearing aids and others, for the validity of objective testing and describe in detail the apparatus used for the measurements upon which the National Institute for the Deaf will issue test reports on commercial hearing aids.

One assumes that the object of issuing this booklet is to inspire confidence in the reliability of these reports. By placing all their cards on the table and by showing

that those responsible for devising the tests have a rational and practical appreciation of the problem, they have not only succeeded well, but have also provided students of electro-acoustics with a well-written resumé of recent advances in the theory of hearing aids. F. L. D.

I.F. After Copenhagen

WHEN the B.B.C. moved on to its new Copenhagen Plan frequencies last year, unexpected whistles came into the homes of millions of listeners who were using superhet receivers. The reason was, of course, that the most commonly used i.f., 465 kc/s, was no longer suitable for the new frequencies and all kinds of heterodyne notes were being generated. This eventuality, predicted some time before the change*, has now been confirmed by the Broadcast Receiver I.F. Sub-Committee of B.R.E.M.A. in a report on a series of tests carried out by various B.R.E.M.A. member firms. Three i.f.s were under consideration, 422 kc/s, 465 kc/s and 470 kc/s, and the tests covered a total of 31 different sites. The main conclusions of the report are that 465 kc/s is, in fact, no longer satisfactory as a standard i.f. and that set manufacturers should confine their choice to either 422 kc/s or 470 kc/s. There is absolutely no hope of finding a single i.f. that will give freedom from whistles on all B.B.C. stations in all parts of the country.

* *Wireless World*, September, 1949, page 322.

18TH National Radio Exhibition



Classified Guide to the Principal Classes of Exhibits

Place: Earls Court, London, S.W.5
Date: 29th August to 8th September
Times: 11 a.m. to 10 p.m.
Admission: Adults 2s. 6d., Children 1s.

method of presentation gives a comprehensive view of the activities of the various exhibitors, and also enables the makers of any particular class of equipment, and their stand numbers, to be located quickly and easily. Those who are unable to visit the exhibition and depend on the pages of *Wireless World* will, it is believed, find this form of presentation a useful reference.


Lists of exhibitors are given both numerically by stand number and alphabetically under trade names or abridged company names.

Perhaps it need hardly be said that this year television will again be the centre of attraction. This is partly due to the imminent opening of the northern station, Holme Moss, which will bring a further 12 million people within the range of a station, and of the Scottish station at Kirk O'Shotts, and in part to a number of technical developments. In the 250-foot television viewing avenue, some 40 makes of receiver will be working.

THE Eighteenth National Radio Exhibition, organized by the Radio Industry Council and supported by 88 manufacturers and a number of non-commercial users of radio—such as the Armed Forces—will be opened by Earl Mountbatten at Earls Court, at 11.0, on August 29th. On the preceding day a pre-view of the exhibition has been arranged for overseas visitors and specially invited guests.

We have again prepared our guide to the exhibition in a classified and tabulated form as we believe this

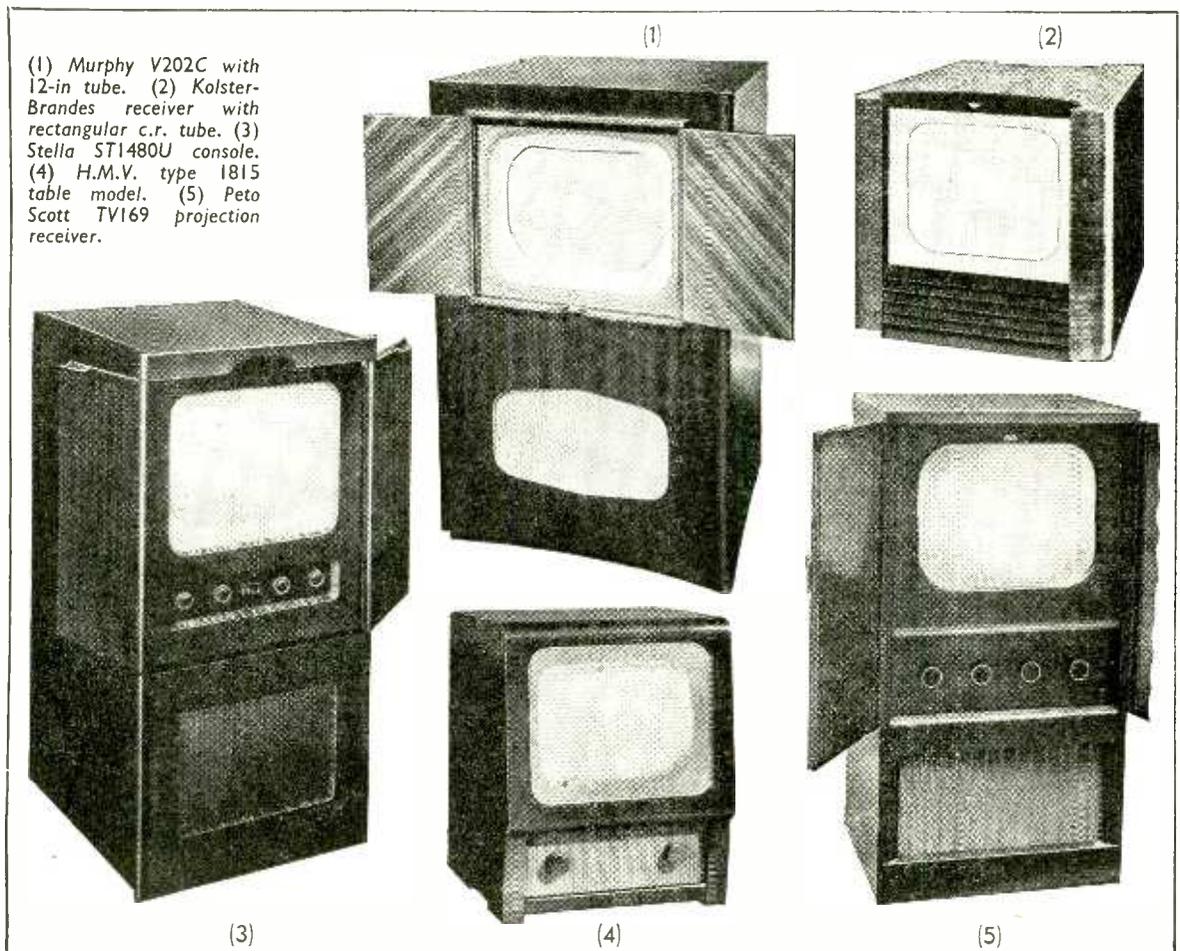(1) Murphy V202C with 12-in tube. (2) Kolster-Brandes receiver with rectangular c.r. tube. (3) Stella ST1480U console. (4) H.M.V. type 1815 table model. (5) Peto Scott TV169 projection receiver.



Larger and brighter pictures are the dominant feature of the new season's models and few sets have a c.r. tube smaller than 12in, while several makers are showing sets fitted with 15- or 16-in tubes. The introduction into television sets of the "flat-face" type of tube will, it is claimed, provide a wider viewing angle and produce the effect of a larger tube.

The present indications are that few changes, apart from cabinet designs, will be found in sound broadcast receivers. Portables and personal portables are becoming more popular and incidentally smaller.

In the field of sound reproduction the principal highlight is a more general use of two- and three-speed turntables in radio-grams and record players.

The tendency towards specialization in radio exhibitions is more than ever noticeable this year. It will be very apparent to the visitor that the national show is largely one of domestic radio equipment. A few component makers whose products are available on the retail market are showing, but the specialized firms catering for set makers only are far less prominent.

Rather surprisingly, fewer firms than had been expected are showing test apparatus and anything in the nature of fixed and mobile communications equipment is virtually non-existent, the special exhibits of the three Services excepted.

Our classified lists do not include the non-commer-

cial exhibits of the Government Departments, Forces, B.B.C., D.S.I.R., etc., and we must therefore deal with them briefly in this introduction. The B.B.C.'s participation is largely centred in the television studio in which programmes are to be rehearsed and broadcast. On their stand they invite visitors to "come and be televised"; for this they are using two 12-inch monitors. A 1:7 working model of one of the feeder switching towers at the B.B.C.'s short-wave station is demonstrated on the stand.


Each of the three Services has a stand. To deal with the senior service first; the Royal Navy's exhibit represents the bridge of a modern cruiser and the operations centre in which is simulated the action taken during an aerial attack on the ship. In addition to this live display the stand also exhibits the type of equipment issued by the Admiralty to members of the Royal Naval Volunteer Wireless Reserve for training in their own homes.

Both the Royal Corps of Signals and the Corps of Royal Electrical and Mechanical Engineers—the main users and the repairers of Army communication equipment—jointly man the War Office stand which depicts signalling systems through the ages and the equipment necessary for the maintenance of modern radio and radar gear.

The Royal Air Force exhibit consists mainly of
(Continued on page 364)

ALPHABETICAL LIST OF EXHIBITORS AND GUIDE TO THE STANDS

Name	Stand	Name	Stand	Name	Stand
A.R.B.M.	67	English Electric	58	Ossicaide	32
Ace	41	Etronic (Hale)	92	Peto Scott	73
Aerialite	47	Ever Ready	49	Petter	103T
Alba (Balcombe)	89	Ferguson	77	Philco	54
Ambassador (Fitton)	4	Ferranti	74	Phillips	83, 90
Amplion	114	G.E.C.	28, 51	Pilot	66
Antiference	94	G.P.O.	233	Plessey	8
Army	234	Gamma	15	Plus-a-Gram (Margolin)	25
Avimo	10	Garrard	68	Portogram	115
Avo (Automatic Coil Winder)	9	Goldring (Scharf)	35	"Practical Wireless"	30
B.B.C.	237	Goodmans	96	Pye	17, 65
Baird (Scophony)	50	Gramplan	110	R.A.F.	232
Barclays Bank	20	H.M.V.	84	R.G.D.	76
Belclere (Bell & Croyden)	22	Haynes	6	Regentone	88
Belling-Lee	64	Hobday	101T	Roberts	44
Bernards	104T	Hogg	106T	Rola-Celestion	39
Board of Trade	1	Hunt	95	S.T.C.	87
"British Radio & Television"	24	Imhof	93	Scott	18
British Railways	70	Invicta	78	Simon	13
Brown Brothers	107T	J.B. Cabinets	33	Skarsten	19
Bulgin	2	K.B.	52	Sobell	56
Burndept	40	Kerry's	102T	Stella	111
Bush	62	L. & P. Factors	105T	T.C.C.	97
Collaro	81	L.E.S.	109T	Taylor	38
Columbia	46	Lloyds Bank	42	Telerection	27
Connoisseur (Sugden)	12	M.C.A.	236	Television Society	36
Cossor	86	Magnavista (Metro Pex)	31	Trix	23
D.S.I.R.	235	Marconiphone	79	Ultra	53
Decca	82	Masteradio	80	Valradio	21
Defiant (Co-op)	91	McMichael	59	Vidor	55
Dibben	108T	Mullard	75	W.B. (Whiteley)	60
Dubiller	45	Multicore	48	Waveforms	34
Dynatron	71	Murphy	61	Wearite (Wright & Weaire)	112
E.M.I.	85	Nationa Provincial Bank	26	Westinghouse	43
Econasign	11	Navy	231	Westminster Bank	72
Eddystone (Stratton)	7	Newman	29	Winel (Elwin)	14
Ediswan	63			Winrad (Winter Trading)	99T
Eelex (Eastick)	100T			"Wireless & Electrical Trader"	3
Ekco	57			"Wireless World"	98
"Electrical & Radio Trading"	113			Wolsey	5
Electron (New London)	44A				
"Electronic Engineering"	37				
Elpico (Lee)	16				

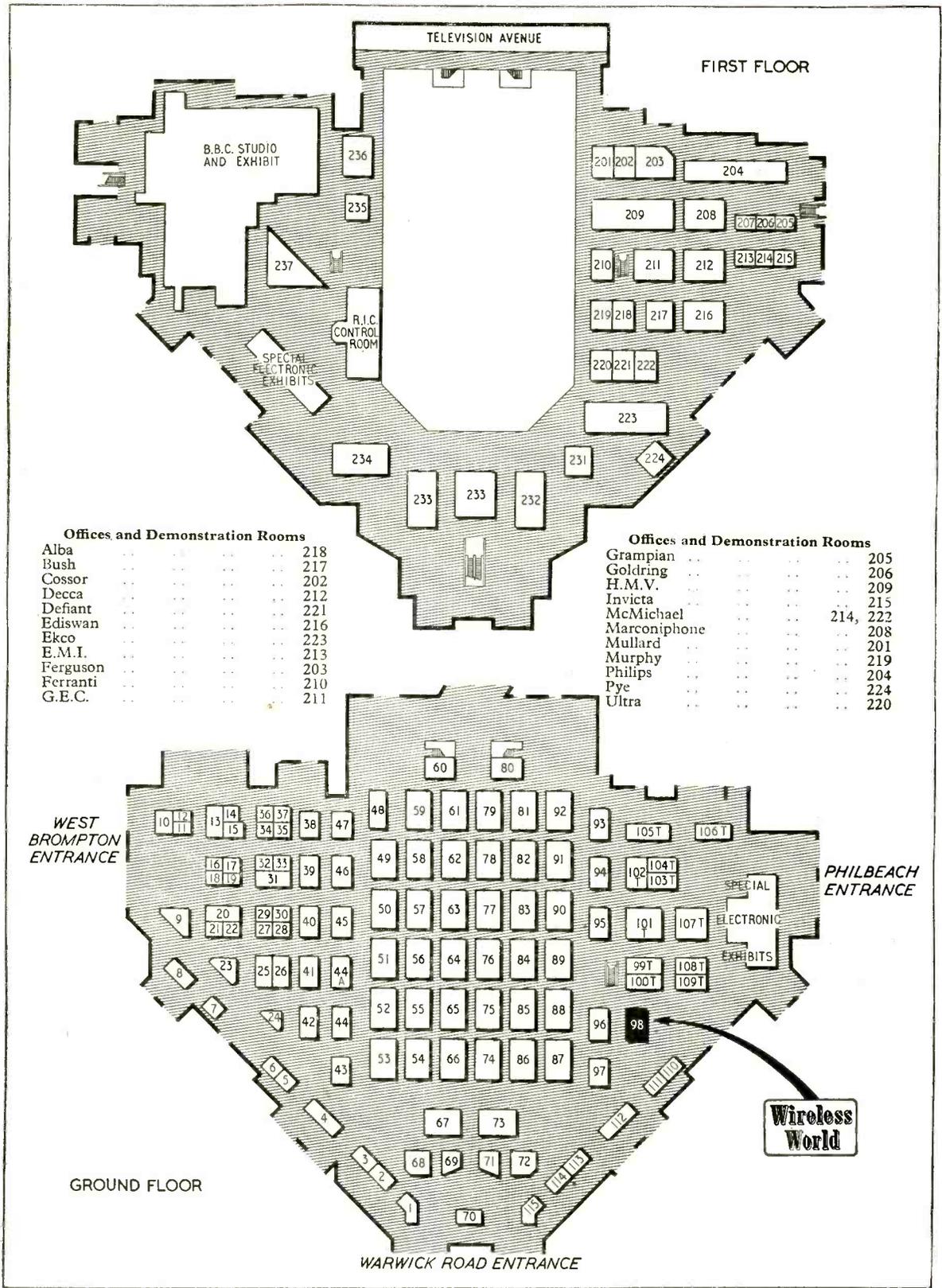

Offices and Demonstration Rooms

Alba	218
Bush	217
Cossor	202
Decca	212
Defiant	221
Ediswan	216
Ekco	223
E.M.I.	213
Ferguson	203
Ferranti	210
G.E.C.	211

Offices and Demonstration Rooms

Gramplan	205
Goldring	206
H.M.V.	209
Invicta	215
McMichael	214, 222
Marconiphone	208
Mullard	201
Murphy	219
Philips	204
Pye	224
Ultra	220

five pieces of radio and radar equipment, including a trainer (Type 102) which simulates the responses received in aircraft fitted with H2S blind bombing apparatus. Air interception gear, Rebecca, Gee and the transmitter-receiver TR1936 which is now standard communication equipment for bombers in the R.A.F.

The activities of the Post Office in the fields of radio and telecommunications generally, and the contributions made by its research engineers to improve the public services are illustrated on the two large stands occupied by the G.P.O.

The main feature of the Ministry of Civil Aviation exhibit is a scale model of London Airport as it will ultimately be, showing the radio and radar aids at present in use.

All the non-commercial users of radio so far mentioned make use of the ionospheric recordings of the Radio Research Directorate of the D.S.I.R. On the Department's stand a recorder, which continuously sounds the ionosphere with pulses in the frequency band 0.6 to 25 Mc/s is demonstrated. Variations in the service area of a television station due to meteorological variations is also illustrated. By using two television receivers on the stand, one tuned to Alexandra Palace and the other to Sutton Coldfield, it is hoped to demonstrate the varying signal strength from the latter (but not A.P.) during weather changes.


In conclusion, we will touch upon the technical services provided at the show for the distribution of sound and vision. Television will be distributed to the stands on the Sutton Coldfield carrier frequencies to avoid interference with the reception of the

Alexandra Palace transmissions. Three sources of programme will be available: (a) B.B.C. transmissions, for the reception of which a radio link working on 6,800 Mc/s will be used between Alexandra Palace and the exhibition; (b) films from a film scanner in the control room in the exhibition; and (c) programmes from the B.B.C. studio in the Hall. A small transmitter, installed in the exhibition control room, feeds the distribution amplifiers. The distributed signal, which has an average level of $1\text{mV} \pm 3\text{db}$ measured on Test Card "C," conforms in every way to standard B.B.C. practice.


A radio-frequency distribution system working on $1030\text{kc/s} \pm 150\text{c/s}$ is fed by co-axial cable to a number of demonstration rooms on the first floor of the exhibition for the operation of broadcast receivers. This signal will be modulated by magnetic-tape recordings. The signal level at each outlet is 300mV and the frequency response is within $\pm 2\text{db}$ from 20c/s to 14kc/s .

A second service, for the demonstration of audio equipment, is superimposed on the cables carrying the medium-wave r.f. signal. The overall frequency response from the Post Office line input to the a.f. outlet on the stands is within $\pm 3\text{db}$ from 20c/s to 16kc/s . There is, of course, the usual sound reproducing system for music and announcements throughout the show and a subsidiary amplification system for relaying the sound from the B.B.C. studio to the visitors looking through the glass-panelled walls.

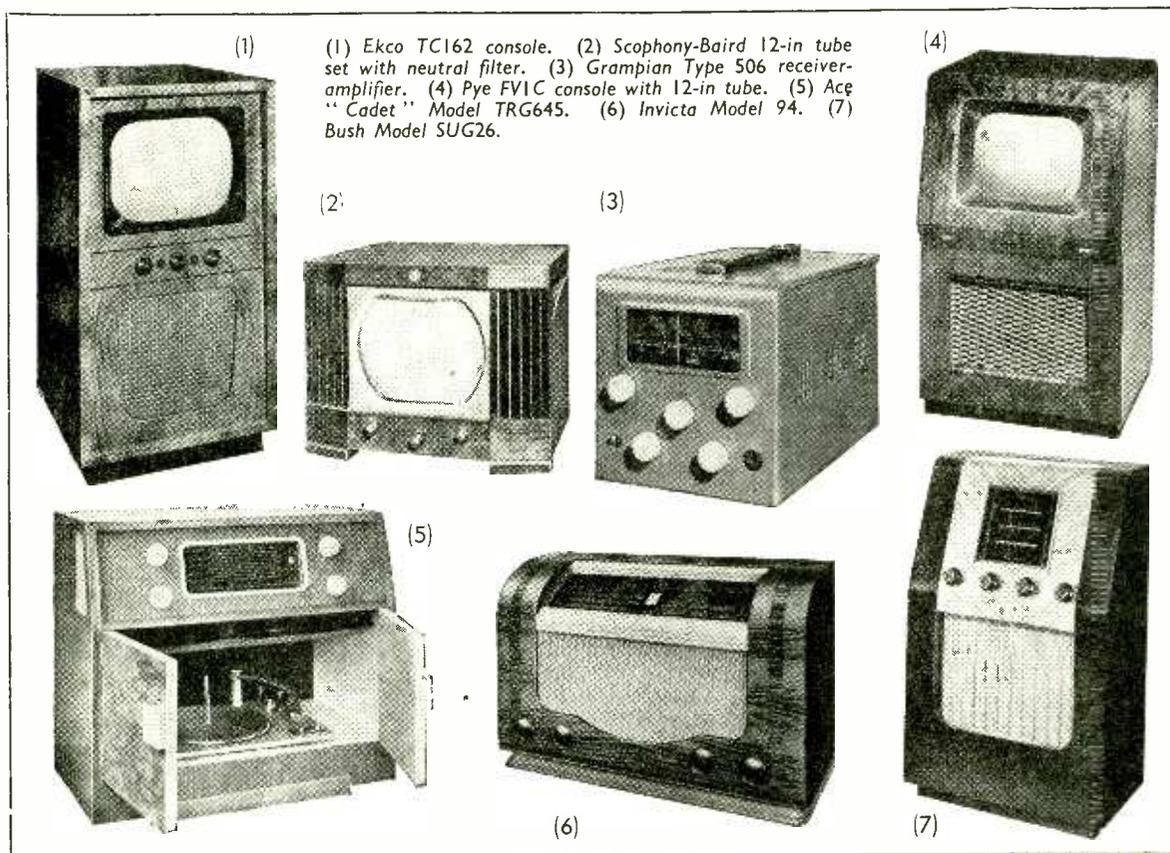The focal point of the technical services at the show is the R.I.C. glass-panelled control room situated on the first floor.



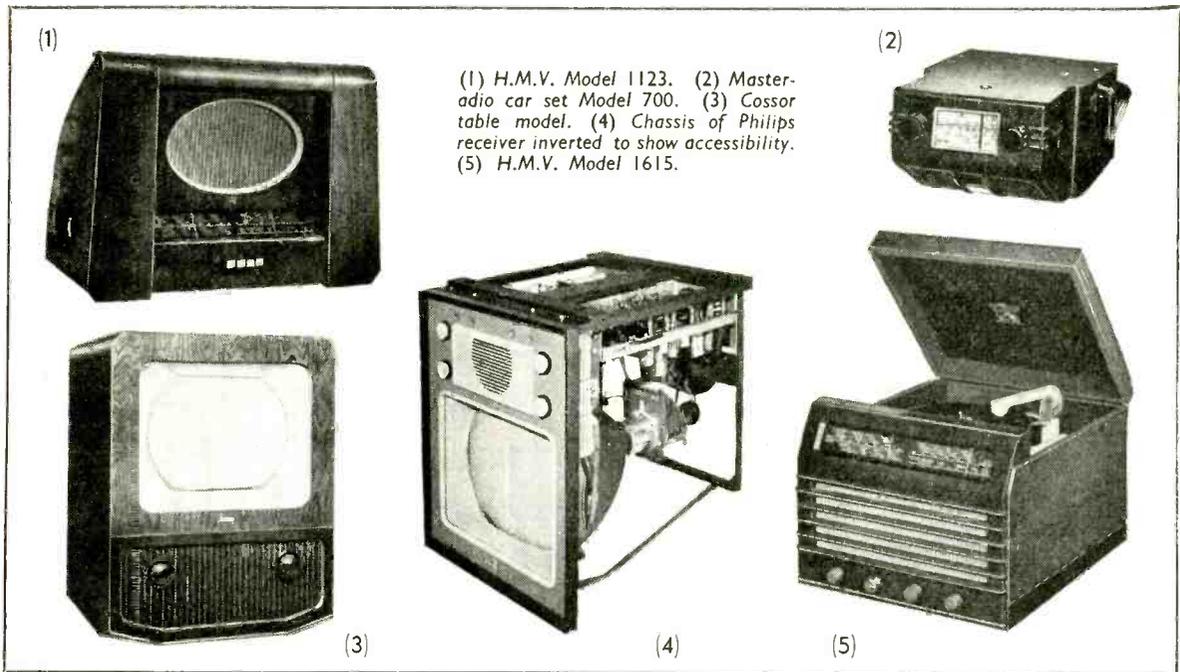(1) Ekco TC162 console. (2) Scophony-Baird 12-in tube set with neutral filter. (3) Gramplan Type 506 receiver-amplifier. (4) Pye FV1C console with 12-in tube. (5) Ace "Cadet" Model TRG645. (6) Invicta Model 94. (7) Bush Model SUG26.



(1) H.M.V. Model 1123. (2) Masteradio car set Model 700. (3) Cossor table model. (4) Chassis of Philips receiver inverted to show accessibility. (5) H.M.V. Model 1615.

RECEIVERS : Broadcast, Television, Communications and Special Purpose

FIRM	(Stand)	Broadcast							Television				V.H.F.	Communications	Schools	Trawler-band	Car		
		Mains	Battery	Mains/battery	Portable	Personal portable	Radio-gramophone	Chassis	Kits	Direct-viewing	Projection	Television-broadcast						Chassis	Kits
Ace	(41)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Alba	(89)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Ambassador	(4)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Baird	(50)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Burndept	(40)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Bush	(62)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Columbia	(46)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Cossor	(86)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Decca	(82)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Defiant	(91)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Dynatron	(71)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
E.M.I.	(85)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Eddystone	(7)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Ekco	(57)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Elpico	(16)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
English Electric	(58)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Etronic	(92)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Ever Ready	(49)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Ferguson	(77)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Ferranti	(74)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
G.E.C.	(28, 51)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Grampian	(110)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
H.M.V.	(84)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Haynes	(6)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Imhof	(93)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Invicta	(78)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
K.B.	(52)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
McMichael	(59)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Marconiphone	(79)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Masteradio	(80)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Murphy	(61)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Peto Scott	(73)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Philco	(54)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Philips	(83, 90)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Pilot	(66)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Portogram	(115)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Pye	(17, 65)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
R.G.D.	(76)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Regentone	(88)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Roberts	(44)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Sobell	(56)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Stella	(111)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Ultra	(53)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Vairadio	(21)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
Vidor	(55)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		
W.B.	(60)	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•	•		

ACCESSORIES : Including Materials, Valves and Non-electronic Rectifiers

FIRM	(Stand)	Aerials				Valves	C.R. tubes	Photocells	Metal rectifiers	Crystal valves	Batteries	Power units	Interference suppressors	Permanent magnets	Magnetic core materials	Magnetic recording tape or wire	Wire and cable	Insulants	Coil formers	Solder	Television pre-amplifiers	Television E.H.T. units	Television optical accessories	
		Broadcast	Television and E.H.F.	Anti-interference	Car																			
Aerialite	(47)	•	•	•	•																			
Amplion	(114)	•	•	•	•						•	•												
Antiference	(94)	•	•	•	•																			
Baird	(50)																							
Belling-Lee	(64)	•	•	•	•																			
Brown Bros.	(1077)																							
Bulgin	(2)																							
Burndept	(40)																							
Cossor	(86)					•	•																	
Dubilier	(45)																							
E.M.I.	(85)	•	•	•	•						•	•	•	•	•	•	•	•	•	•	•	•	•	•
Eddystone	(7)	•	•	•	•																			
Ediswan	(63)	•	•	•	•						•	•	•	•	•	•	•	•	•	•	•	•	•	•
Ekco	(57)																							
Electron	(44A)	•	•	•	•																			
Elpico	(16)	•	•	•	•																			
English Electric	(58)																							
Etronic	(92)																							
Ever Ready	(49)																							
Ferranti	(74)																							
G.E.C.	(28, 51)					•	•																	
Goldring	(35)																							
H.M.V.	(84)																							
Haynes	(6)																							
Magnavista	(31)																							
Marconiphone	(75)																							
McMichael	(59)																							
Mullard	(75)																							
Multicore	(48)																							
S.T.C.	(87)																							
Scott	(13)																							
T.C.C.	(97)																							
Telerection	(27)																							
Valradio	(21)																							
Vidor	(55)																							
W.B.	(60)																							
Wearite	(112)																							
Westinghouse	(43)																							
Wolsey	(5)																							

TEST AND MEASURING GEAR : Including Signal Generators and Test Sets

FIRM	(Stand)	Single-range pointer meters	Multi-range meters	Bridges and accessories	Valve voltmeters	Test sets	Signal sources	Television signal sources	Oscilloscopes	Test prods	
Avo	(9)										
Belclere	(22)										
Bulgin	(2)										
Cossor	(86)										
E.M.I.	(85)										
Eddystone	(7)										
Ediswan	(63)										
Goldring	(35)										
Hogg	106T										
Taylor	(38)										
W.B.	(60)										
Waveforms	(34)	•									

SCIENTIFIC, INDUSTRIAL AND MEDICAL APPARATUS

FIRM	(Stand)	Radio heaters	Electronic measuring instrs.	Counters	Medical apparatus	Hearing aids
Belclere	(22)					
Cossor	(86)					
Dynatron	(71)					
E.M.I.	(85)	•	•	•	•	•
Ediswan	(63)					
English Electric	(58)					
Ossicaide	(32)					
Taylor	(38)					

(1) Waveform's 5-channel television signal generator. (2) Dubilier e.h.t. capacitor in glazed ceramic tube. (3) Amplion "Activette" unit for reactivating dry batteries. (4) G.E.C. 12-in flat-faced television c.r. tube with aluminized screen. (5) T.C.C. "Plimoseal"-treated capacitors.


**SOUND REPRODUCING EQUIPMENT :
Audio-Amplifiers and Electro-Acoustic Apparatus**



(1) Goldring magnetic turnover pickup, Model No. 165.
 (2) Pye portable radio-gramophone Type P32QTG.
 (3) Goodmans "Axiom 90." (4) Collaro Model 3/514.
 (5) "Simphonic" Model 1A magnetic tape recorder.
 (6) Hunt's dual mica capacitor, Type L73, (7) Belling-Lee 18-way screened connector.


FIRM	(Stand)	Microphones	Pickups	Amplifiers	Loudspeakers	Gramophone motors	Record changers	Record players	Electric gramophones	Disc recorders	Magnetic recorders
Baird ... (50)											T
Belclere ... (22)											
Collaro ... (81)											
Connoisseur ... (12)											
Decca ... (82)											
Defiant ... (91)											
E.M.I. ... (85)											
Eddystone ... (7)											T
Ediswan ... (63)											
Ekco ... (57)											
Elpico ... (16)											
Etronic ... (92)											
G.E.C. ... (28, 31)											
Garrard ... (68)											
Goldring ... (35)											
Goodmans ... (96)											
Gramplan ... (110)											
H.M.V. ... (84)											
K.B. ... (52)											W
L. & P. Factors ... (105T)											
Marconiphone ... (79)											
Plus-a-Gram ... (25)											
Portogram ... (115)											
R.G.D. ... (76)											T
Rola-Celestion ... (39)											
Simon ... (13)											T
Trix ... (23)											
W.B. ... (60)											
Wearite ... (112)											T

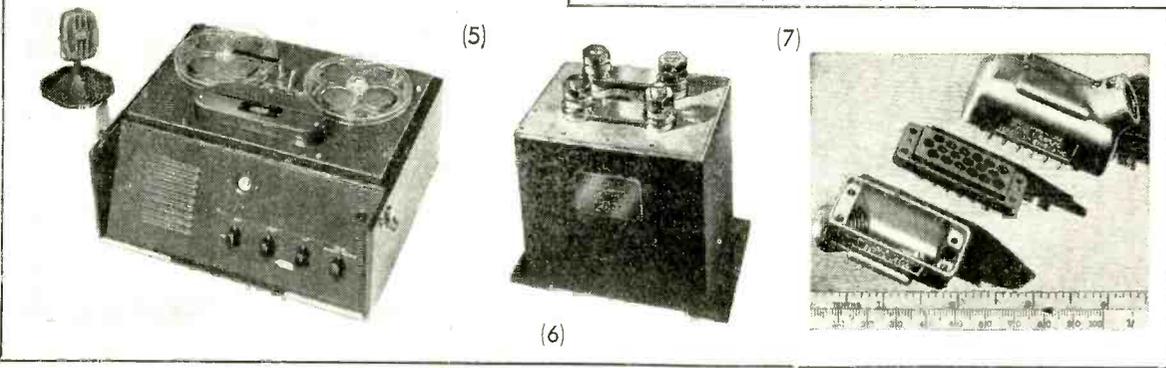D, domestic loudspeakers ; R, sound reinforcement loudspeakers ; T, tape recorders ; W, wire recorders.



COMPONENTS : Excluding Accessories and Sub-Assemblies

FIRM	(Stand)	Capacitors, fixed	Capacitors, variable	Trimmers	Resistors, fixed	Resistors, variable	Resistors, non-ohmic	Switches	Coils, R.F.	Transformers, mains	Transformers, audio	Chokes	Plugs, sockets, connectors	Chassis fittings	Cabinets, racks, chassis	Dials, drives, knobs	Vibrators	Scanning components	Focus and ion-trap magnets	
Aerialite ... (47)																				
Antiference ... (94)																				
Belclere ... (22)																				
Belling-Lee ... (64)																				
Bulgin ... (2)																				
Dubilier ... (45)																				
Eddystone ... (7)																				
Elpico ... (16)																				
Goldring ... (35)																				
Goodmans ... (96)																				
Haynes ... (6)																				
Hunt ... (95)																				
Imhof ... (93)																				
J.B. Cabinets ... (33)																				
Rola-Celestion ... (39)																				
S.T.C. ... (87)																				
T.C.C. ... (97)																				
Valradio ... (21)																				
W.B. ... (60)																				
Wearite ... (112)																				
Winrad ... (99T)																				

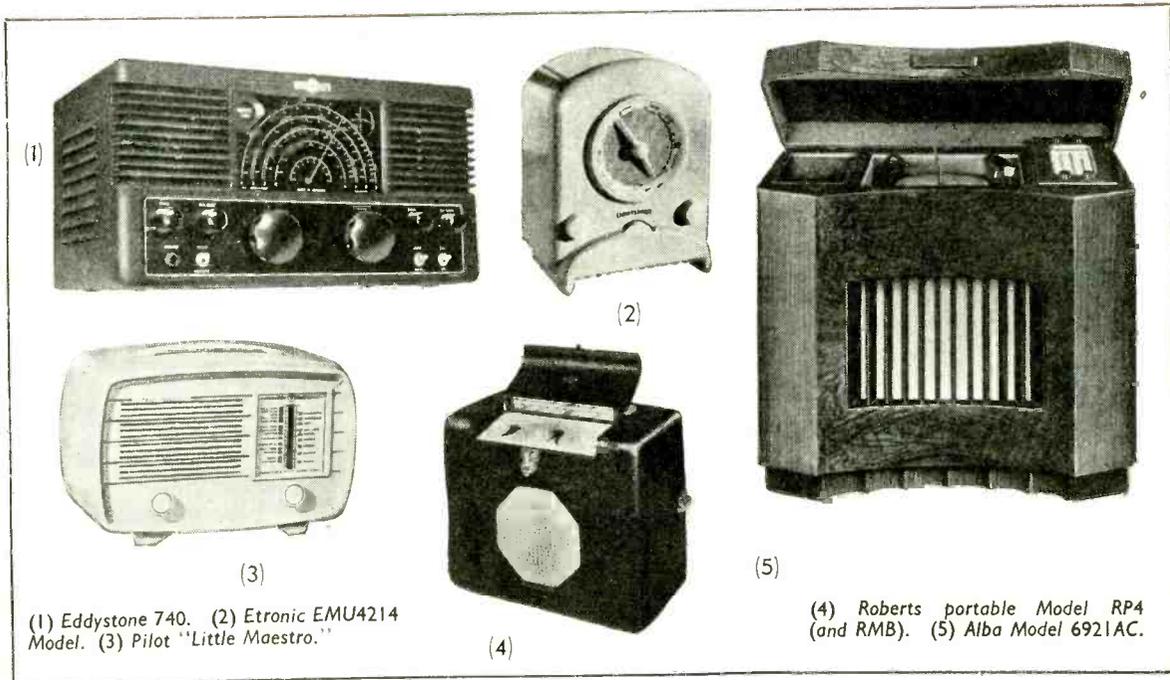

(1) Eddystone 740. (2) Etronic EMU4214 Model. (3) Pilot "Little Maestro."

(4) Roberts portable Model RP4 (and RMB). (5) Alba Model 6921AC.

NUMERICAL LIST OF STANDHOLDERS

- Board of Trade, Lacon House, Theobalds Rd., London, W.C.1.
- 2 A. F. Bulgin & Co., Rye-Pass Rd., Barking, Essex.
- 3 "Wireless & Electrical Trader," Dorset House, Stamford St., London, S.E.1.
- 4 E. N. Fitton, Princess Works, Pollard St., Brigg House, Yorks.
- 5 Wolsey Television, 75, Gresham Rd., London, S.W.9.
- 6 Haynes Radio, Queensway, Ponders End, Enfield, Middx.
- 7 Stratton & Co., Eddystone Works, Alvechurch Rd., West Heath, Birmingham, 31.
- 8 Plessey Co., Vicarage Lane, Hford, Essex.
- 9 Automatic Coil Winder Co., Winder House, Douglas St., London, S.W.1.
- 10 Avimo, Taunton, Somerset.
- 11 Econasign Co., 32, Victoria St., London, S.W.1.
- 12 A. R. Sugden & Co., Well Green Lane, Brighouse, Yorks.
- 13 Simon Sound Service, 48, George St., London, W.1.
- 14 Henry Elwin, Plumtree St., Nottingham.
- 15 Gamma Electronics, 518, Ipswich Rd., Trading Estate, Slough, Bucks.
- 16 Lee Products, 99, Great Eastern St., London, E.C.2.
- 17 Pye Radio Works, Cambridge.
- 18 Geo. L. Scott & Co., Cromwell Rd., Eillesmere Port, Cheshire.
- 19 Skarsten Mfg. Co., 21, Hyde Way, Welwyn Garden City, Herts.
- 20 Barclays Bank, 54, Lombard St., London, E.C.3.
- 21 Valradio, New Chapel Rd., Feltham, Middx.
- 22 John Bell & Croydin, 117, High St., Oxford.
- 23 Trix Electrical Co., 1-5, Maple Place, Tottenham Court Rd., London, W.1.
- 24 "British Radio & Television," 92, Fleet St., London, E.C.4.
- 25 J. & A. Marrolin, 112-116, Old St., London, E.C.1.
- 26 National Provincial Bank, 15, Bishopsgate, London, E.C.2.
- 27 Telecrown, 19, Suffolk Parade, Cheltenham, Glos.
- 28 General Electric Co., Magnet House, Kingsway, London, W.C.2.
- 29 J. & S. Newman, 100, Hampstead Rd., London, N.W.1.
- 30 "Practical Wireless," Tower House, Southampton St., London, W.C.2.
- 31 Metro Pex, 42A, Denmark Hill, London, S.E.5.
- 32 Ossicade, 1, Upper Richmond Rd., London, S.W.15.
- 33 J.B. Manufacturing (Cabinets) Co., 86, Palmerston Rd., London, E.17.
- 34 Waveforms, 26, Oakleigh Rd., London, N.11.
- 35 Erwin Scherl, 49, De Beauvoir Rd., London, N.1.
- 36 Television Society, 68, Compton Rd., London, N.21.
- 37 "Electronic Engineering," 28, Essex St., London, W.C.2.
- 38 Taylor Electrical Instruments, 419, Montrose Avenue, Slough, Bucks.
- 39 Rola Celestion, Ferry Works, Sumner Rd., Thames Diton, Surrey.
- 40 Buradep, West St., Erith, Kent.
- 41 Ace Radio, Tower Works, Tower Rd., Pound Lane, London, N.W.10.
- 42 Lloyds Bank, 71, Lombard St., London, E.C.3.
- 43 Westinghouse Brake & Signal Co., 82, York Way, London, N.1.
- 44 Roberts' Radio Co., Creek Rd., East Molesey, Surrey.
- 44A New London Electron Works, Boleyn Rd., London, E.6.
- 45 Dubilier Condenser Co., Ducon Works, Victoria Rd., London, W.3.
- 46 Columbia Graphophone Co., Hayes, Middx.
- 47 Aerialite, Castle Works, Stalybridge, Ches.
- 48 Multicore Solders, Mellier House, Albemarle St., London, W.1.
- 49 Ever Ready Co., Hercules Place, Holloway, London, N.7.
- 50 Scophony-Baird, Lancelot Rd., Wembley, Middx.
- 51 General Electric Co., Magnet House, Kingsway, London, W.C.2.
- 52 Kolster-Brandes, Footscray, Sidcup, Kent.
- 53 Ultra Electric, Western Avenue, London, W.3.
- 54 Philco (Overseas), Lion House, Red Lion St., Richmond, Surrey.
- 55 Vidor, West St., Erith, Kent.
- 56 Sobell Industries, Langley Park, Nr. Slough, Bucks.
- 57 E. K. Cole, Ekco Works, Southend-on-Sea, Essex.
- 58 English Electric Co., Queen's House, Kingsway, London, W.C.2.
- 59 McMichael Radio, 190, Strand, London, W.C.2.
- 60 Whiteley Electrical Radio Co., Victoria St., Mansfield, Notts.
- 61 Murphy Radio, Welwyn Garden City, Herts.
- 62 Bush Radio, Power Rd., Chiswick, London, W.4.
- 63 Edison Swan Electric Co., 155, Charing Cross Rd., London, W.C.2.
- 64 Bellink & Lee, Cambridge Arterial Rd., Enfield, Middx.
- 65 Pye Radio Works, Cambridge.
- 66 Pilot Radio, 31-37, Park Royal Rd., London, N.W.10.
- 67 Association of Radio Battery Manufacturers, 41, Gordon Square, London, W.C.1.
- 68 Garrard Engineering & Mfg. Co., Newcastle St., Swindon, Wilts.
- 69 British Railways, 222, Marylebone Rd., London, N.W.1.
- 70 Dynatron Radio, Perfecta Works, Ray Lea Rd., Maidenhead, Bucks.
- 71 Westminster Bank, 51, Threadneedle St., London, E.C.2.
- 72 Peto Scott Electrical Instruments, Adlestone Rd., Weybridge, Surrey.
- 73 Ferranti, Hollowood, Lancs.
- 74 Mullard, Century House, Shaftesbury Avenue, London, W.C.2.
- 75 Radio Gramophone Development Co., Pale Meadow Print Works, Bridgforth, Shropshire.
- 76 Ferguson Radio Corporation, 105, Judit St., London, W.C.1.
- 77 Inweta Radio, Parkhurst Rd., London, N.7.
- 78 Marconiphone Co., Hayes, Middx.
- 79 Masteradio, 10-20, Fitzroy Place, London, N.W.1.
- 80 Collaro, Ripple Works, Bye-Pass Rd., Barking, Essex.
- 81 Decca Record Co., 1-3, Brixton Rd., London, S.W.9.
- 82 Philips Electrical, Century House, Shaftesbury Ave., London, W.C.2.
- 83 Gramophone Co., Hayes, Middx.
- 84 E.M.I. Sales & Service, Hayes, Middx.
- 85 A. C. Cossor, Cossor House, Hightway Grove, London, N.5.
- 86 Standard Telephones & Cables, Footscray, Sidcup, Kent.
- 87 Regentone Products, New Factory, Eastern Ave., Romford, Essex.
- 88 A. J. Balcombe, 32, Tabernacle St., London, E.C.2.
- 89 Philips Electrical, Century House, Shaftesbury Ave., London, W.C.2.
- 90 Co-operative Wholesale Society, 1, Ballou St., Manchester, 4.
- 91 Hale Electric Co., Radio Works, Talbot Rd., London, W.13.
- 92 Alfred Imhof, 112, New Oxford St., London, W.C.1.
- 93 Antiference, 67, Brynston St., Marble Arch, London, W.1.
- 94 A. H. Hunt, Bendon Valley, Garratt Lane, London, S.W.18.
- 95 Goodmans Industries, Lancelot Rd., Wembley, Middx.
- 96 Telegraph Condenser Co., North Acton, London, W.3.
- 97 "Wireless World," Dorset House, Stamford St., London, S.E.1.
- 98 Winter Trading Co., 6, Harrow Rd., London, W.2.
- 99 J. J. Eastick & Sons, 12, Errol St., London, E.C.1.
- 100 Hobbay Bros., 21, Great Eastern St., London, E.C.2.
- 101 Kerry's, Warton Rd., London, E.15.
- 102 Petter Radio & Electrical Supplies, 201-9, Forest Rd., London, E.17.
- 103 The Bernards, The Grampians, Western Gate, London, W.6.
- 104 L.T.S. Distributors, 15, Alfred Place, London, W.C.1.
- 105 Gramplan Reproducers, Hanworth Trading Estate, Feltham, Middx.
- 106 Stella Radio & Television Co., 9-15, Oxford St., London, W.1.
- 107 Wright & Weaire, 138, Sloane St., London, S.W.1.
- 108 "Electrical & Radio Trading," 96, Long Acre, London, W.C.2.
- 109 Amphion, 230, Tottenham Court Rd., London, W.1.
- 110 Portogram Radio Electrical Industries, Prell Works, St. Rude St., London, S.W.1.
- 111 Admiralty, Whitehall, London, S.W.1.
- 112 Air Ministry, Parliament Square House, Parliament St., London, S.W.1.
- 113 General Post Office, Headquarters, London, E.C.1.
- 114 War Office, Whitehall, London, S.W.1.
- 115 Dept. of Scientific & Industrial Research, Charles House, 5-11, Regent St., London, S.W.1.
- 116 Ministry of Civil Aviation, Ariel House, Theobalds Rd., London, W.C.1.
- 117 British Broadcasting Corporation, Broadcasting House, London, W.1.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

B.B.C./G.P.O. Standards

C. R. WHITE'S letter in your July issue reveals a situation, if the facts are as stated, which is shocking. It is very regrettable that the B.B.C., which is obliged to publish an annual report to show what it does with our money, is not also obliged to declare annually its standard of technical achievement. All the hush-hushery which surrounds the quality of B.B.C. equipment and G.P.O. lines should be done away with before the possibility of spending £200,000 on even one v.h.f. station is given a moment's consideration.

B.B.C. quality as heard here in Edinburgh does seem to have improved in the last few months, but even so I can hear little difference in fidelity between live and recorded material, and what difference there is often in favour of the disc. Programmes originating in Scotland and broadcast in this region only do not seem to be of better technical quality than those which are piped from London, or, worse still, are piped down to London for control purposes and then piped back up again to the local transmitter. This suggests that the transmitter causes the main loss of quality.

A merely moderately good tape recording covering a frequency range of 100 to 7,000 cycles sounds to most people greatly superior to the average B.B.C. transmission, while speech over a good closed circuit often shakes them visibly. Film recording, involving electrical, chemical and physical processes can also be highly successful, to say nothing of the humble disc, slowly edging its way up to the 20,000-cycle mark. What prevents broadcasting from being *at least* as good?

Edinburgh, 9.

W. J. MACLEAN.

ON the evening of July 7 Droitwich was radiating a programme of dance music relayed from the Continent and between 11.00 and 11.15 p.m. this emanated from the German N.W.D.R. system in Hamburg.

From the moment the German transmission commenced the whole balance of the frequency characteristic was improved and there was no audible intermodulation buzz. Although I do not suggest that this was a perfect transmission I was so impressed that I waited to compare with it the ensuing programme from London. The instant the English announcer spoke, back came that intolerable harshness and transient buzzing effects that we have for so long had to tolerate on the majority, though not all, of our programmes.

Does this not demonstrate the important fact that the above-mentioned distortion does not originate in the B.B.C.'s main modulators, or even in the much maligned land lines, but in the microphones or early audio amplifiers at the studios? I feel somehow that it is bound up with the B.B.C. rising top characteristic (as we know, top lifting increases the harmonic content).

Wednesbury, Staffs.

A. A. COTTERELL.

YOUR correspondent C. R. White poses the question whether the B.B.C. has a different standard for the provinces than for London. As a Northern listener anxious to obtain the best quality I can afford and who has long suffered the vagaries of the Moorside Edge transmitters (Home 434 m and Light 247 m) I do not think there can be any doubt that the reply is in the affirmative. Indeed, it is not too much to say that the whole B.B.C. set-up for provincial broadcasting is such as to make a lower standard inevitable.

I had for some time been puzzled by the fact that the quality of broadcasts known to originate in local studios was noticeably poorer than that of programmes coming by landline from London. In February of this year I wrote to the B.B.C. on the matter. They stated that normally

all broadcasts of provincial origin, whether in Home or Light programmes are routed via London, which in the case of the Manchester studios must involve nearly 200 miles of landline instead of the 20-odd miles from Manchester to Moorside Edge. Poor quality is thus inevitable under present G.P.O. landline standards. The only apparent reason for this curious system is to give London direct control of provincial studio's output. It is significant of this that my original letter to the B.B.C. in Manchester, though concerned solely with Northern transmission quality, was acknowledged with the intimation that the complaint was a matter for London, and the ultimate reply came from the Engineering Information Department there.

It would seem that provincial listeners contemplating the purchase of high-fidelity equipment should ask themselves whether the substantial expenditure involved is worth while under current conditions, unless they are fortunate enough to be in the service area of the new Third Programme transmitter at Daventry, which, though about 100 miles distant, gives much better quality in the Manchester area than either of the local Home and Light medium-wave stations.

Manchester.

J. BRAMALL.

The Innocent Pentode

"DIALLIST," in your July issue, repeats an ancient libel on the innocent pentode. He charges it with producing high harmonics, amplifying high frequencies more than low, and even amplifying its own harmonics. Can these things be true?

Manifestly, the pentode does not amplify high frequencies more than low: the mutual conductance is constant. But if the load impedance rises, the gain will rise, and this effect is not offset in the pentode, as it is in the triode, by a high input capacitance.

When used at the same efficiency, the pentode produces less distortion than the triode. But it can be operated over almost the full anode voltage, and then it runs more sharply against end-stops, and the high harmonics rise. There is another source of distortion, and this may be in "Diallist's" mind when he states that the pentode amplifies its own harmonics. When the cathode is not decoupled, and the screen is at a.c. earth, and not at a.c. cathode, the screen current is in the feedback loop. The screen current, being a triode current, is severely distorted, and this feedback increases the distortion.

The bad reputation of the pentode is the result of careless circuit design: it is not the car which kills, but the driver. Feedback is used to make up for deficiencies in output transformer design and then, with such large phase shifts that the feedback is positive at high audio frequencies, the valve is blamed for the increased distortion. Instead of improving the design, the designer cries loudly that triodes were good enough for his father, and they are good enough for him: 10 per cent distortion was good enough for his father, too.

No, Sir: "Diallist" must suppress these reactionary thoughts and must be screened from the triodomaniacs. This is no time to lay down the slide-rule.

THOMAS RODDAM.

Bass Without Big Baffles

I MUST thank your correspondents G. A. Briggs and O. G. Kerslake (your August issue) for their generous remarks concerning the performance of my amplifier.

In case readers should be discouraged by Mr. Briggs' revelation that I use a "doctored" loudspeaker, perhaps I had better say a few words about this. The "operation" merely consisted of removing a pair of diametrically oppo-

site limbs of a four-limbed central spider with scissors.

The loudspeaker (with a cloth surround to the cone) had a specified fundamental resonance at 45 c/s, and, by thus increasing the compliance of the central spider, this figure was reduced to the region of 30 c/s. I believe that a really smooth bass response (in terms of the fundamental or of artificially produced harmonics) can only be obtained if a loudspeaker with a low natural resonance is used. However, my circuit was originally evolved round a cheap 10-inch speaker and a cabinet with a frontage of 2½ ft by 1½ ft, and gave excellent results. Dimensions such as those (or less) come into my category of "small baffles."

It may be that Mr. Briggs is under the impression that spurious harmonics at higher frequencies are removed in my amplifier by filtering. This is not so, since the filter precedes the distorting valve V_3 and limits frequencies admitted to V_3 to those lying below about 100 c/s. It is on the presence of a full range of harmonics appearing at the anode of V_3 that the effectiveness of the circuit is dependent.

There would seem, from personal correspondence which I have received, some demand among readers for information regarding suitable valve substitutes, etc. The following list of Osram equivalents (or near equivalents) should prove useful:—

For 6SF5 substitute Osram H63.

For 6J5 substitute Osram L63.

For EL33 substitute Osram KT61.

If the last-mentioned output valve is employed the value of the cathode bias resistor R_{16} should be altered to 90 ohms. Otherwise no circuit modifications need be made.

Regarding a suitable output transformer, I can recommend a Wharfedale W12, using tapings giving a ratio of 22:1 for the 15-ohm speech coil.

Snags in the form of instability are common with high-slope output valves such as those specified. Leads to and from the output transformer should be kept as short as possible, and leads at the input end of the amplifier should be screened. The small capacitor C_{10} was included in order to improve stability and its value may be varied accordingly. In some layouts this item may best be omitted altogether.

K. A. EXLEY.

Leeds, 6.

WHY all this talk about synthetic "bass"? Recently after hearing a concert in the Royal Festival Hall, seated where the volume level seemed comparable with that of a 10-W amplifier at close quarters, I certainly had no desire to go home and introduce abnormal bass emphasis. On the assumption that the experts who dealt with the acoustics of the Festival Hall were right, I found it necessary to return my bass lift circuit to "flat" on my Voigt equipment to approximate to what I was hearing at that concert.

E. R. VEATER.

Hayle, Cornwall.

Valve Priorities

ON page 166 of your April, 1951, issue, "Free Grid" asks whether de Forest devised a valve with grid in 1912 only, since a German named von Bronck had discovered high-frequency amplification already in 1911. "Free Grid" therefore assumes that the invention was made by de Forest before 1911.

It is correct that von Bronck discovered high-frequency amplification in 1911. (See German Patent 271,059.)

De Forest devised in 1907 the gas-containing Audion valve which had a grid, see U.S.A. Patent 879,532. This valve was, however, not intended to be an amplifier valve but a receiving detector valve and, at the time, could not hold its own against the crystal detector, since it had rather low sensitivity.

Knowledge of amplifier valves came to us in Europe through another inventor, R. von Lieben, who invented

the amplifier valve in 1910, see German Patent specification 249,142 (corresponding Austrian Patent 54,011).

Stuttgart, Germany. TELEFUNKEN G.m.b.H.

Diathermy Interference

IT would appear that a great many of the hospital diathermy equipments in use throughout the country are tuned to the same frequency as the Holme Moss television station.

In York and many West Riding towns, to my personal knowledge, radiation from these equipments is causing such serious interference that reception of the Holme Moss station will be impossible while they are operating. What action do the authorities concerned propose to take to eliminate this interference?

R. CUSSINS.

Cussins and Light, Ltd., York.

Intermodulation Tesis

I READ with interest the article in the July issue on "Intermodulation Distortion in Gramophone Pickups." Recently I have been making a series of intermodulation distortion measurements on various pickups (using a test set which I am confident avoids the pitfalls mentioned by Mr. Berth Jones in the June issue) and I am surprised at the emphasis placed by Mr. Kelly on the application of this particular form of measurement to checking the tracking capabilities of a pickup.

The minimum needle pressure required for a given pickup to track a given frequency recorded at a given level can be determined correct to at least ½ gram by the observation of waveform on an oscilloscope. The waveform produced by failure to track has a characteristic "spiked" appearance and a very small trace of this form of distortion is easily detectable.

The intermodulation distortion method can certainly be used to check the tracking capabilities of a pickup at the modulation frequency (although in my view it is an over-elaborate method). With the record discussed (JH138) this can be done at 60 c/s and 400 c/s for the maximum recording level at those frequencies; but this does not necessarily indicate the tracking capabilities of a pickup with a bass mechanical impedance resonance at 40 c/s, or worse still at 80 c/s. Further, in the case of a cantilever crystal pickup with a bass resonance at, say, 35 c/s and a treble resonance at, say, 10,000 c/s, the minimum needle pressure required may be determined by the impedance at the high-frequency resonance, i.e., although the pickup may track perfectly at 60 c/s (+8.6 db recorded level relative to 1 cm/sec) with a given needle pressure, a higher needle pressure will be required for perfect tracking at 10,000 c/s and the same recorded level (well below the maximum recording level at this frequency). The only answer would be a large number of intermodulation test records with a corresponding number of interchangeable filters in the test set! A relatively small number of high-level, single-frequency records (whose frequency can be varied by a variable speed turntable) and a reasonably good oscilloscope provide a far simpler method.

I suggest that the importance of intermodulation distortion measurement for pickups lies in that it is a sensitive and convenient way of measuring non-linearity when the pickup is actually tracing the record groove modulations satisfactorily. In this respect a small difference in intermodulation distortion between two pickups (as measured on the 400 c/s-4,000 c/s side of the record) is definitely detectable by ear when playing orchestral music records. In fact, within reasonable limits, intermodulation distortion measurements would appear to be as important as frequency range or response curve in judging the performance of a pickup. I have found so far that the critical unbiased listener will invariably express preference for lower intermodulation distortion rather than better frequency response.

L. J. ELLIOTT.

London, N.W.3.

Stereophony on Television Channels

Proposals for Binaural Broadcasting

WHEN the P.M.G. made his famous statement on a new system of broadcasting, was he, by any chance, referring to stereophony? Probably not, considering how many times the official wet blanket has been cast on the idea. Yet the fact remains many technical people still regard stereophonic broadcasting as *the* thing of the future. And, unlike the Chief Engineer of the B.B.C.,* they do not see overwhelming objections in the fact that two sound channels are necessary—especially in these days of multichannel radio links. The stereophonic broadcast staged in France last year did, certainly, require two complete chains of equipment from microphone to loudspeaker, and it was rather cumbersome—but then, after all, the B.B.C. used fundamentally impractical methods to show the world that a public television service was a practical possibility.

One of these devotees of stereophonic broadcasting, H. H. Olofsen, of Hilversum, Holland, has written to us expressing his faith in the idea and suggesting how an experimental system might be put into effect without too much trouble. He demolishes the main argument against the scheme—that we can't afford to set up duplicate systems because of the cost and the lack of space in the ether—by pointing out that we in Britain already have a system of duplicate transmitters and receivers standing idle for large parts of the day and just asking to be used. He has in mind the television system, with its vision and sound transmitters and corresponding dual arrangements in the receivers. Mr. Olofsen proposes, in fact, that the vision transmitter should be used for the second sound channel, so that in the television receiver it would only be a matter of switching the video output from the cathode ray tube to a second loudspeaker.

The scheme is simple and certainly worth a trial. Plenty of enthusiasts would be willing to convert their television receivers, but what about the B.B.C.? Unfortunately, its attitude can be predicted only too clearly from the fact that last year it rejected a proposal for radiating binaural programmes from the twin transmitters at Wrotham. Perhaps, too, its sense of economy would recoil at the suggestion of using a vision channel of 3-Mc/s bandwidth for a mere 15-kc/s sound spectrum. Certainly this would be wasteful. But here Mr. Olofsen comes forward again, with a proposal for utilizing this wide bandwidth to the full. He points out, in fact, that it would accommodate quite a large number of sound channels. So far from one stereophonic programme monopolizing two transmitters and receivers, he says, four stereophonic programmes could be radiated from a single transmitter and received on a single televisor.

A multiplexing system would, of course, be necessary to achieve this, and one which would utilize the existing vision transmitting and receiving circuitry to

the best advantage, with a minimum of alteration and change-over switching. Our correspondent suggests a time-division multiplexing system using pulse modulation. Each of the four programmes modulates a separate train of pulses and the trains are staggered so that they interlace to form a single, more closely packed pulse train. This is transmitted in place of the usual vision waveform. In the television receiver the individual pulse trains are selected by gate circuits—Mr. Olofsen thinks the time-base circuits could be adapted for this purpose—and so the four programmes are reconstituted. The operation of the gate-pulse generators is controlled by the original television sync. pulses, which are retained in the signal and separated in the usual way in the receiver. So far so good, but what about the two sound channels necessary for each programme? To accommodate these, Mr. Olofsen proposes to make the pulses in each train alternate in width and modulate one channel on to the narrow pulses and the other on to the wide ones. Then, in the receiver, a pulse-width discriminator separates them and so obtains the two channels. He adds that the system would be suitable for carrying "hyper-high-note" monaural programmes as a possible alternative experiment to the stereophony.

Incidentally, our correspondent makes the further suggestion that an extra channel could be provided by modulating the sync. pulses themselves. In fact, as "Cathode Ray" mentioned in "Sampling" last month, Pye have already tried a similar sort of scheme for carrying the sound of a television programme, the idea being, of course, to obviate the separate sound transmitter. "Cathode Ray" also posed the question: "Is it (sampling) the Answer to the Wavelength Problem?" Mr. Olofsen thinks that his multichannel scheme might well be. He suggests that all national and regional programmes could be distributed in this way, so that the medium waves would then be left free for such things as programme exchanges between countries. Thus our present sound broadcast receivers would become redundant and we should get all our programmes, television and sound, from the same box.

Undoubtedly this would be a welcome innovation to the average listener-viewer who at present must have either two separate sets or an equally expensive combined model. For the B.B.C., however, it would raise the new problem of how to share the available hours of the day between television and sound—and, until such time as the mounting pace of life forces us all to develop multichannel minds, it would need to be time division *without* multiplex. But at the moment, unless the B.B.C. has immediate plans for making television a 24-hour service, there would be no organizational difficulties in sharing the channels with stereophony, and, as Mr. Olofsen points out, it would give "full employment" to the transmitters.

* *Wireless World*, April, 1950, p. 158.

WORLD OF WIRELESS

Modulation Muddle ♦ I.T.U. Geneva Conference ♦ Record Radio Exports ♦ Audio Engineering Convention

A.M.-F.M. Controversy

A FURTHER complication in the a.m.-f.m. controversy has been caused by the United States' request that we in this country should, "in the interests of world standardization," reconsider the decision to use a.m. for our single-channel v.h.f. maritime radio services.

When asked in the House of Commons if he would give an assurance that he intended to maintain his declared policy on this question the P.M.G. stated that discussions with U.S. representatives had not yet taken place but, as matters stood, he proposed to support the case for amplitude modulation in any international discussions.

Reference was made to this question recently by C. O. Stanley, chairman of Pye, Ltd. He stated that during the three years since the decision was made to use a.m. for v.h.f. maritime telephone services the G.P.O. had "failed to equip a single British port with the necessary shore facilities" despite the fact that manufacturers had the equipment available. He added that the countries now pressing for a change in our policy "can point to substantial progress in this field, whereas Britain can point to none."

International Conference

SINCE the Atlantic City Conference in 1947 a number of meetings have been held in order to prepare plans for the allocation of frequencies to specific services or, as in the case of the Copenhagen Conference, to a service in a given area. Whilst some of these have had plenipotentiary powers, others have been purely investigatory. Now a conference is in progress in Geneva—it opened on August 16th—to confirm and, where necessary, modify the plans drawn up at these meetings for the allocation of frequencies between 14 kc/s and 27.5 Mc/s to the four main services. Where, as in the case of the Rapallo conference, a complete plan was not produced the present conference will be called upon to work out methods for drawing up new plans.

The conference has also to determine the role of the International Frequency Registration Board in the implementation of the new allocation tables.

The U.K. delegation, which will be led by Sir Robert Craigie, includes representatives of the Post Office, B.B.C., Armed Services, Foreign Office and Ministry of Civil Aviation.

Among the Post Office delegates are Col. A. H. Read (Director of Overseas Telecommunications), S. Horrocks (Telephone and Radio Branch), C. F. Booth (Radio Development Branch), E. Potts (U.K. representative on the Provisional Frequency Board) and R. M. Billington, whose main interest is in maritime mobile services in the U.K. The B.B.C. representative is W. J. Chalk.

Radio Exports

EXPORTS of radio equipment in the first six months of this year reached a record value of £10,195,333, which was 39.4 per cent more than the figure for the same period in 1950.

The biggest increase was in the export of receivers which rose by 74 per cent to £2,110,824. Loose components exported were valued at £3,387,892, of which approximately 10 per cent went to the U.S.A. and Canada. Exports of valves rose by 54 per cent to £1,817,171. Capital equipment (broadcast transmitters, communications equipment, navigational aids, etc., not including installations in ships and aircraft) increased by 12.6 per cent to £2,646,618.

According to the Radio Industry Council radio exports now form the highest single group among exports of the electrical industry.

Business Radio

WHEN questioned in the House of Commons on the Government's policy regarding the use and expansion of mobile radio services, the P.M.G. gave details of the number of licences in force at the end of July.

Taxis, hire cars, delivery vans, etc., head the list with 243 licences covering 222 fixed stations and 1,054 mobile stations. Police and fire services had 182 licences (428 fixed and 2,403 mobile stations); harbour and tug services, 65 (74 and 258); public utility services, 53 (61 and 221); ambulances, 19 (20 and 266); contractors, works, etc., 12 (8 and 62); and railways, 8 (7 and 41). This gives a total of 582 licences, 820 fixed stations and 4,305 mobile transmitters.

Audio Convention

THE sixth and last session of the Brit. I.R.E. Convention, which will be devoted to the subject of audio-frequency engineering and acoustics, will be held from September 4th to 6th in the Richmond Hall, Earls Court, during the period of the National Radio Exhibition.

Admission to the convention, which will be under the chairmanship of H. J. Leak, is by ticket obtainable from the secretary of the Institution, 9, Bedford Square,



HOLME MOSS. Medium-power stand-by transmitters (5kW vision, 2kW sound) installed by Marconi's at the B.B.C.'s northern television station which is to be opened by the P.M.G. on October 12th. The transmitters are similar to those originally ordered for the five secondary stations.

London, W.C.1. The registration fee for the session is 10s 6d.

Most of the fourteen papers to be read will include demonstrations, and the session will conclude with a discussion on high-fidelity reproduction in which both technicians and musicians will be invited to take part.

The papers are:—

- "The Royal Festival Hall: Acoustic Design and Testing," by P. H. Parkin, B.Sc. (D.S.I.R. Building Research Station).
- "Some Aspects of Magnetic Recording and Reproduction," by O. K. Kolb, Ph.D. (British Acoustic Films).
- "Problems in Magnetic Recording, with particular reference to Film Production," by N. Leever, B.Sc., A.C.G.I. (Leever Rich).
- "Microgroove Recording," by N. C. Mordant and E. D. Parchment (Decca).
- "Loudspeaker Baffles and Cabinets," by J. A. Youngmark, M.A. (Goodmans).
- "Stereophonic Reproduction using a 3-channel System," by J. Moir, M.I.E.E. (B.T.H.).
- "Intermodulation Distortion: Its Significance and Measurement," by E. Berth-Jones, B.Sc.(Eng.) (E.M.I. Studios).
- "Loudspeakers: Relations between Subjective and Objective Tests," by F. H. Brittain (Acoustics Division, G.E.C.).
- "The Mechanics of Hearing," by T. S. Littler, M.Sc., Ph.D. (Wernher Research Unit on Deafness).
- "The Loudspeaker in the Home," by P. J. Walker (Acoustical Manufacturing Co.).
- "Electrographic Organs," by L. E. A. Bourne (Compton Organ Co.).
- "Speech Input Systems for Broadcast Transmitters," by S. Hill, M.Sc. (Standard Telephones Cables).
- "Piezo-Electric Crystal Transducers," by S. Kelly (Cosmocord).
- "Objective Testing of Pickups and Loudspeakers," by K. R. McLachlan and R. Yorke, B.Eng., B.Sc. (University College, Southampton).

Broadcasting Station Guide

ALTHOUGH the Copenhagen Plan has now been in use for some eighteen months the situation in the l.w. and m.w. bands is still far from satisfactory. There is continuous jockeying among certain stations to get better positions. According to the latest available details there are nearly 200 stations operating on unauthorized frequencies; many of them sandwiched between the agreed channels.

The situation can best be visualized by perusing a copy of the latest edition (6th) of our 96-page book, "Guide to Broadcasting Stations," which includes operating details of some 360 authorized and 190 unauthorized long- and medium-wave transmitters in Europe. Details of some 1,400 short-wave broadcasting stations throughout the world are also given in the book, which is available from booksellers price 2s., or by post from our Publisher, price 2s 2d.

The substantial growth in the use of metre-wave broadcasting in Europe is shown by the increased number of stations listed; 46 as compared with 11 in the last edition. The contents also includes: European television stations, Consol and standard frequency transmitters, international call signs, standard time throughout the world and wave-length-frequency conversion tables.

Price Cutting and Service

WE reported in last month's issue the plea that the provision of "after-sales" service in such "technical" industries as radio and television called for some special dispensation in regard to the Government's proposed abolition of retail price maintenance.

The Board of Trade has now announced that special consideration is being given to "certain technical goods, such as motor cars, radio and television."



DR. D. C. ESPLY, O.B.E.
(See "Personalities")

Valve Making

IN his opening remarks as chairman of the valve session of the Brit. I.R.E. Convention, J. R. Hughes, who at short notice took the place of J. W. Ridgeway, spoke of the empiricism of valve making and of the difficulties of standardization in view of this. But, he asserted, "the main obstacle to standardization is the valve user."

There are, he pointed out, no second chances in valve making; it is a case of "one-shot" production—a valve is either usable or unusable. He also touched upon the present-day demands for miniaturization, smaller heater and filament current, operation at higher frequencies and reliability.

I.E.E. Awards

PREMIUMS have been awarded by the I.E.E. for twelve papers read before the Radio Section, or accepted for publication, during the 1950/51 session. In addition, the John Hopkinson Premium, which is not confined to a Section, is awarded to R. J. Clayton, Dr. D. C. Espley, G. W. S. Griffith and J. M. C. Pinkham for their paper "London-Birmingham Television Radio Relay Link," and the Heaviside Premium to Dr. G. G. Macfarlane and Mrs. A. M. Woodward for their paper "Small-signal Theory of Wave Propagation in a Uniform Electron Beam."

The Radio Section Duddell Premium is awarded to P. A. T.

Bevan and H. Page for their paper "Sutton Coldfield Television Broadcasting Station" and the Ambrose Fleming Premium to Dr. J. A. Saxton, G. W. Luscombe and G. H. Bazzard for their two papers on "Propagation of Meter Radio Waves between the Normal Horizon."

Extra premiums are awarded for the following papers:—

"The Vision Transmitter for the Sutton Coldfield Television Station" (E. A. Nind and E. McP. Leyton); "Low-Frequency Radio-Wave Propagation by the Ionosphere, with particular reference to Long-Distance Navigation" (Caradoc Williams); "Frequency Standardization" (Dr. L. Essen); "The Use of Saturable Reactors as Discharge Devices for Pulse Generators" (W. S. Melville); "Crystal Diodes" (R. W. Douglas and Dr. E. G. James); "An Automatic Monitoring of Broadcast Programmes" (H. B. Rantzen, F. A. Peachey and C. Gunn-Russell); "Factors Governing the Radiation Characteristics of Dielectric Tube Aerials" (D. G. Kiely); "Cheese Aerials for Marine Navigational Radar" (D. G. Kiely, Instr. Lieut. A. E. Collins, R.N., and G. S. Evans); and "Some Properties of Wave Guides with Periodic Structure" (Dr. A. W. Lines, G. R. Nicoll and Mrs. A. M. Woodward).

PERSONALITIES

D. C. Espley, O.B.E., D.Eng., the chairman of the I.E.E. Radio Section for the next session, has been in the Research Laboratories of the G.E.C., Wembley, since 1930. He is in charge of telecommunications research activities at the laboratory and was responsible for the design, development and installation of the London-Birmingham television radio-relay link.

J. A. Smale, B.Sc., who has been elected vice-chairman of the I.E.E. Radio Section, is chief engineer of Cable & Wireless, Ltd. He joined the Engineer-in-Chief's Dept. of C. & W. in 1932 and was responsible before the war for the development of long-



J. A. SMALE, B.Sc.

distance s.w. relay stations as a means of overcoming unfavourable propagation conditions. He also originated important development work on frequency-shift keying.

Dr. H. G. Booker, who went to the U.S.A. in 1949 as Professor of Electrical Engineering at Cornell University, was recently appointed chairman of the U.S.

Navy advisory board on aerials. He was at one time in charge of the Mathematics Section of the Telecommunications Research Establishment of the Ministry of Supply.

R. B. Dome, the engineer in the American General Electric Company's laboratories responsible for the development of the frequency-interlace system of colour television described in our December, 1950, issue, has been awarded the Morris Liebmann Memorial Prize by the American I.R.E. for "... his contributions to the inter-carrier sound system of television reception. . . ."

IN BRIEF

Broadcast Licences.—The increase in the number of "sound" receiving licences in the U.K. is counter-balanced by the withdrawals of "sound" for "vision" licences so that there is now a gradual decrease in the former. At the end of June the number of "sound" licences totalled 11,562,800 a decrease of 7,900 during the month. Vision licences increased by 27,800 to 897,000. The overall totals were May, 12,439,900; June, 12,459,800.

D.G. Radio Production.—The Government has decided to set up a Radio Advisory Council through which liaison between the Ministry of Supply and the radio industry can be maintained on matters affecting defence. When announcing this in the House the Minister of Supply stated that a Director-General of Radio Production would be appointed to act for the Ministry.

Unadvised!—The P.M.G., in reply to a question in the House, stated that the Television Advisory Committee, which was reconstituted on the appointment of the Beveridge Broadcasting Committee, had not met since November 4th, 1949.

Educational Opportunities.—Prospectuses covering both day and evening courses in telecommunications, television and radio theory, servicing and the amateur transmitter's examination, for the 1951-1952 session have been received from The Polytechnic, Regent Street, London, W.1; South East London Technical College, Lewisham, S.E.4; and Brentford Evening Institute, Brentford, Middlesex.

B.S.R.A. Officers.—C. E. Watts has been elected president of the British Sound Recording Association for the second year and M. J. L. Pulling and B. C. Sewell re-elected vice-presidents. H. Davies and H. J. Leak were also elected vice-presidents.

RECORDING ROOM, housing twelve disc and eight tape recorders, in the new headquarters of the Canadian Broadcasting Corporation. The control panel for each recorder is fitted with an automatic programme selector switch by means of which any one of 50 outlets from the Master Control Room can be recorded.



I.E.E. Council.—Among those elected to office on the Council of the Institution of Electrical Engineers for the ensuing year are the following members of the Radio Section:—Dr. W. G. Radley (G.P.O.) a vice-president; and Dr. J. L. Miller (B.I. Callender's Cables) and Prof. F. C. Williams (University, Manchester) ordinary members.

I.E.E. Radio Section.—The following have been elected to fill the vacancies occurring on the Radio Section Committee on September 30th:—Chairman, Dr. D. C. Espley (G.E.C.); vice-chairman, J. A. Smale (Cable and Wireless); ordinary members, G. Millington (Marconi's), Dr. E. L. C. White (E.M.I.) and W. E. Willshaw (G.E.C.).

R.S.G.B. Call Book.—The first edition of the R.S.G.B. Amateur Radio Call Book, which contains the names and addresses of some 6,000 amateur transmitters in the British Isles and the Irish Republic, is available by post from the Society at New Ruskin House, Little Russell Street, London, W.C.1, price 3s 9d, including postage.

Advice to potential viewers on such matters as size of screen, type of aerial and operation of a television set, is given in the illustrated 28-page booklet "What you need to know about TV" which is being issued free by Pye, Ltd., Cambridge.

B.I.F.—Next year's British Industries Fair will be held from May 5th to 16th in both London and Birmingham.

INDUSTRIAL NEWS

British transmitting and receiving gear has been chosen by the authorities in Bogota, Colombia, for their television service. Marconi's are supplying the 525-line transmitter and associated studio equipment whilst Ekco receivers will be available from the Municipality under a hire-purchase scheme.

Ekco.—To mark the silver jubilee of the formation of E.K. Cole, Ltd., the annual report and statement of account is issued as an illustrated brochure. It recalls that the company was formed in 1926 to market the Ekco battery eliminator.

Television Afloat.—Pye, Ltd., are operating through their subsidiary company Rees Mace Marine, Ltd., a service whereby ships lying in the Thames can be equipped with television receivers for the duration of their stay. The installation charge is 35/- and the rental 3/4 per day.

Wired Television.—A long-term agreement has been made between Broadcast Relay Service, Ltd., and Electric & Musical Industries, Ltd., to pool their wired television research and techniques. The arrangement envisages the participation of radio retailers in existing or new television relay services operated by B.R.S.

Pye (Canada), Ltd., of Ajax, Ontario, announce that their director, W. Jones, has been appointed Controller of Radar Production in the Electronics Division of the Department of Defence Production in Ottawa. He will retain his directorship of Pye (Canada), Ltd.

We are advised that J. H. Head, commercial manager of Sydney S. Bird & Sons, makers of Cyldon components, has joined Advance Components as general manager.

Burndep, Ltd., have opened a new factory at Erith, Kent, which is to house the company's Electronics Division.

Telerection, Ltd.—A new factory—Antenna Works, St. Pauls, Cheltenham, Glos.—has been acquired by Telerection, Ltd., whose offices will for the present remain at 12, Suffolk Parade, Cheltenham.

Valradio, Ltd., inform us that their projection television receiver has been accepted for inclusion in the South Bank Exhibition.

MEETINGS

British Sound Recording Association

Presidential address by C. E. Watts, at 7.0, on September 21st, at the I.E.E., Savoy Place, London, W.C.2.

Institution of Electronics

Southern Branch.—"Design Considerations for a Modern High-Fidelity Radiogram Receiver" by Lewis Williams (Electro Acoustic Developments) at 7.0 on September 5th in the Lecture Hall, Central Library, Portsmouth.

Television Society

Engineering Group.—"Slot Aerials" by H. Page (B.B.C. Research Dept.) at 7.0 on September 21st at the Cinema Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

Society of Relay Engineers

"Television Relay by Wire" at 2.30 on October 2nd at the E.M.I. Institute, 10, Pembroke Square, London, W.2.

British Institution of Radio Engineers

Annual general meeting at 6.30 on September 26th at the London School of Hygiene and Tropical Medicine, Keppel Street, London, W.C.1.

SHORT-WAVE CONDITIONS

July in Retrospect : Forecast for September

By T. W. BENNINGTON *

DURING July the average maximum usable frequencies for these latitudes decreased somewhat, both by day and night, as compared with those for June. Daytime working frequencies remained about the same as during the previous month, being higher than had been expected. 17 Mc/s was usually the best received daytime frequency for east/west paths, though those up to 22 Mc/s were frequently usable, and U.S.A. amateurs on 28 Mc/s were audible on at least one occasion. For north/south paths 22 Mc/s was about the highest regularly usable frequency, though here again higher frequencies were sometimes receivable. At night 11 Mc/s was usually workable till after midnight, and 9 Mc/s the night through.

Sporadic E was very prevalent, and a considerable amount of amateur communication on 28 Mc/s with certain European countries was noted as occurring by way of this medium.

The month was notable for the amount of v.h.f. reception which occurred by means of (presumably) tropospheric refraction. Dutch and German stations on 89-94 Mc/s were very frequently received, as also were French stations on 42 Mc/s.

Sunspot activity was, on the average, considerably lower than during the previous month.

Though several ionospheric storms occurred only one of these had really serious effects upon communications, namely, that which occurred during the period 1st-4th. The other disturbances occurred during 16th-18th, 22nd-23rd, and 16th-31st. Only one Dellinger fadeout has so far been reported, i.e., on 4th at 1255-1440 g.m.t.

Forecast: During September the daytime m.u.f. for these latitudes should increase considerably, and that for night-time decrease somewhat, as compared with con-

ditions during August. Daytime working frequencies for long-distance communication should increase generally, though 17 Mc/s will probably be about the highest regularly usable frequency for east/west circuits, with 21 Mc/s, or slightly higher frequencies, sometimes usable. Over north/south circuits frequencies up to 23 Mc/s should be regularly, and those up to 30 Mc/s sometimes, usable. At night 9 Mc/s should be regularly usable up to midnight, and 7 Mc/s thereafter over east/west circuits, whilst over north/south circuits 11 Mc/s should be regularly usable till midnight, and 9 Mc/s thereafter.

Sporadic E is likely to decrease somewhat in the frequency of its occurrence, though some medium-distance transmission on exceptionally high frequencies will probably be possible by way of this medium. Working frequencies for medium-distance communication by way of the regular layers will be somewhat lower than during August, both by day and by night, and such communication will take place by way of the E or F₁ layers for only a short period daily.

The curves indicate the highest frequencies likely to be usable over four long-distance circuits from this country during the month.



* Engineering Division, B.B.C.

Educational Filmstrips

THE 35-mm filmstrips on technical subjects produced by Mullard with the co-operation of the National Committee for Visual Aids in Education, have already been mentioned in *Wireless World*. There are now three additions to this series. "The Story of Radio," 35 frames in black and white, traces the history and development of radio and explains in simple terms how a broadcast programme (sound only) is transmitted and reproduced. It is suitable for pupils in the 11-16 age group and costs 10s. "The Cathode Ray Tube," however, occupies two filmstrips and is designed for older and perhaps more specialized audiences in technical schools and colleges. The first part, 29 frames in colour (price £1), is concerned with history, development and general principles, while the second part, 30 frames in black and white (price 10s), deals with construction and manufacture.

These three are distributed by Unicorn Head Visual Aids, Ltd., of Broadway Chambers, 40, Broadway, Westminster, London, S.W.1.

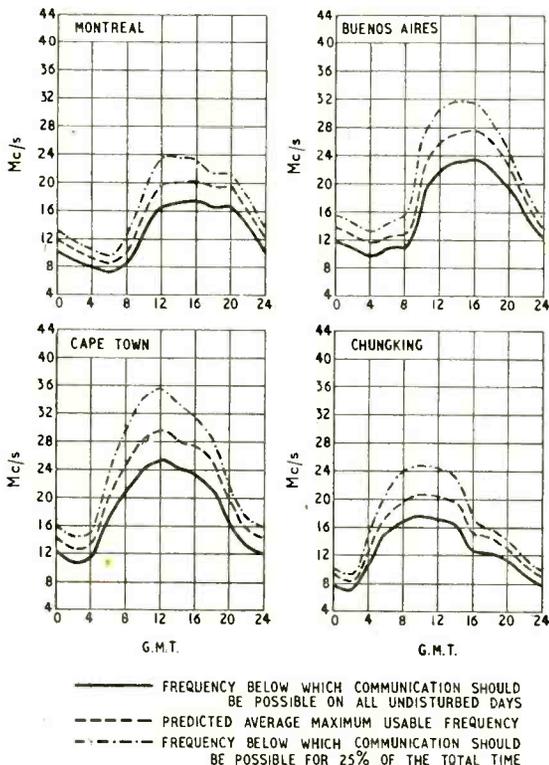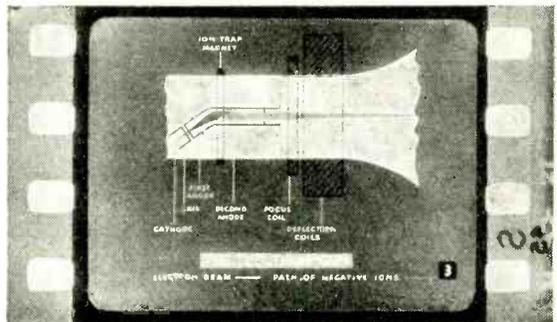
Typical frame from the filmstrip describing the history, development and general principles of the cathode ray tube.



Modifying "Surplus" Meters

Two Useful Instruments from an Ex-Government Indicator

By W. H. CAZALY

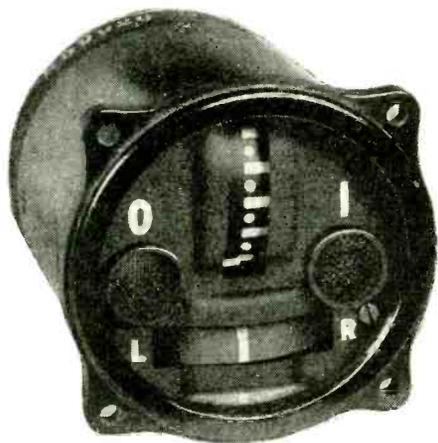

Visual Indicator Type 3 (10Q/4)

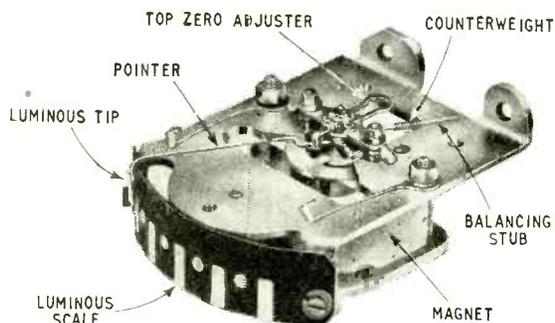


Fig. 1. Of the two movements in the indicator, this one has a linear characteristic and can be converted into a low-current meter.

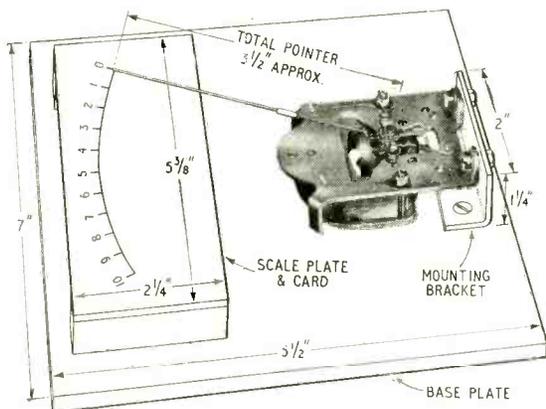


Fig. 2. Suggested form of construction for the modified meter.

CERTAIN instruments obtainable quite cheaply from Government "surplus" sources contain moving-coil movements which can be modified to provide linear-scale and centre-zero indicators of general utility. These movements are often very well made, and it seems a pity to regard them as "scrap."

As an example, the Visual Indicator Type 3 (10Q/4), obtainable for a few shillings at the time of writing, contains two moving-coil movements. Originally this was an aircraft instrument used in blind approach systems. One movement, the L-R, is a sensitive centre-zero indicator with flat pole faces, which can be used as a null indicator in bridge and other measuring circuits. Since the pole faces are flat, the characteristic is not linear, so that it is not very suitable as a "meter," but it makes a useful galvanometer with a deflection (when a new long pointer is added) of about 1½ in on either side of the central zero for about 30 μA. Currents of the order of 0.5 μA are quite detectable. It is heavily damped, and the working forces are so small that slight vibration (gentle tapping) is advisable to make the pointer return exactly to zero over the last ½ in adjacent to the zero mark. Its modification into a bench galvo is quite easy, on the lines which will be described in respect of the other movement.

The other movement (Fig. 1 shows how it appears when taken out of the instrument) has curved pole faces, with a linear characteristic over about 80°, so that it can be converted into a low-current meter such as a 0-750 μA or a 0-1 mA indicator.

It is proposed to outline, as a typical example, the conversion of this linear movement into a single-range 0-1 mA meter with a gratifyingly long scale (about 5 inches). If the principles of construction in this simple example are grasped, it should not be difficult for the experimenter to utilize these and similar movements in test instruments of various kinds.

First, a warning. Robust as moving-coil movements appear to be, it must always be borne in mind that the fine steel pivot points have considerable deforming pressure per unit area exerted on them if the pointer is not handled very gently indeed. Wood blocks should be at hand to rest the movement when it is taken out of the instrument and keep its weight off the pivot assembly; the pointer may be moved or steadied by means of a fine camel-hair artists' brush. All work done on the movement *must* be carried out on a clean surface scrupulously clear of dust, and the worker's hands must be clean; a good idea is to work on a large sheet of white paper pinned on a wooden table, with direct daylight as the illuminant. The equipment required other than the kind normally found in a small workshop comprises fine pointed tweezers, a sharp razor blade, sharp nail scissors, a camel-hair brush, a tube of Durofix (celluloid cement), and a scrap of Chatterton's compound, with a small solder-

ing iron for the melting of the compound. A jewellers' eyeglass is also a convenience, for close inspection of fine operations.

The first step consists of the construction of all the parts other than the actual movement, and assembling them ready to have the movement fitted. Ideas will vary about the form of the final instrument, but, assuming that a plain 0-1 mA meter is to be the final outcome, the author's suggestions illustrated in Fig. 2 may be useful. To outward appearances the meter will look like a shallow box made of non-magnetic material, as shown in Fig. 3. The top and sides form a removable cover, which can be taken off the base of the box, with a window over the scale, a zero adjuster, and the terminals. The base of the box constitutes the main base plate on which are mounted the scale plate, the movement, and the shunt. The cover, scale plate and base plate are carpentering jobs and should be constructed first, accurately and neatly. Plywood $\frac{1}{4}$ inch thick is quite suitable, but other materials, such as Paxolin, Bakelite, aluminium, etc., can be used, as long as they are non-magnetic. The movement mounting bracket is of stout brass or aluminium.

Next, a new pointer, which is to be added to the existing pointer of the movement, should be prepared. It consists of a thin, straight piece of hollow grass stalk, about $2\frac{1}{2}$ in long, gathered at the end of the autumn when Nature has turned it into a thin-walled, very light but remarkably strong, tube of cellulose fibre. Referring to Fig. 4, a short sleeve, about $\frac{1}{2}$ in long, made out of wider grass stalk, is slipped for about $\frac{1}{8}$ in over the butt end of the longer stalk, being secured with a tiny touch of Durofix. The open end of this sleeve will go in due course over the prepared end of the existing movement pointer, so the choice of stalks of suitable thickness should be carefully made after inspection of the movement pointer. When made, the new pointer is brushed with india ink and set aside to dry thoroughly for an hour in a warm place.

While it is drying, the scale card can be prepared. The total length of the modified pointer, from tip to pivot, can be fixed at $3\frac{1}{2}$ in, which will give a scale length of about 5 in. With this $3\frac{1}{2}$ in as radius, an arc is drawn to subtend an angle of 80° on a piece of Bristol board. The arc is then divided into ten parts (each 8°), and these divisions can each be further divided by eye into five sub-divisions. The ten divisions are then marked 0 to 10, from right to left, and the drawing is inked in. A light pencil line is drawn from the centre of the scale (the 5 mark) to the centre on which the arc was drawn, to assist later in placing the card in the correct position on the scale plate. The scale card is then cut to fit the scale plate with a small amount of play and stuck to the plate so that the central pencil line lies over the medial line of the base plate. Touches of glue at the four corners of the card will be sufficient to hold it without the buckling that might ensue if a lot of glue were used. The card must, of course, be dead flat.

Mounting the Movement

Now the movement can be dealt with. It is mounted on a non-magnetic metal bracket of fairly rigid construction (duralumin or hardened brass or aluminium $\frac{3}{32}$ in thick are suitable), in such a way that (a) the top assembly plate of the movement is level with or very slightly above the surface of the scale card and parallel with it; and (b) the pivot of the pointer is over the spot where the scale arc centre would be. Allow-


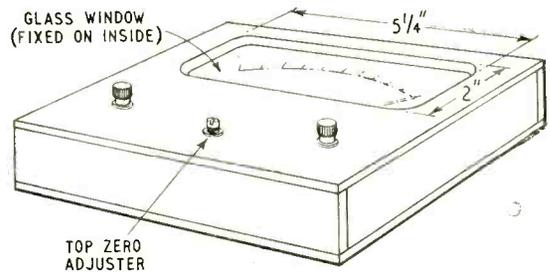


Fig. 3. The modified meter in its housing. The top and sides are made as a removable cover which fits on the base plate (Fig. 2).

Fig. 4. Detail of the movement, with the extended pointer and extra counterweight.

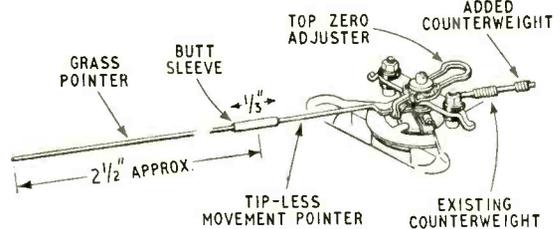

ing a slight amount of play in the bolt holes of the bracket will enable it and the movement to be positioned by eye with adequate accuracy.

The bent-over luminous tip of the existing pointer is snipped off with a really sharp pair of nail scissors, proceeding very cautiously in order to avoid strain on the pointer and steadying it with the camel-hair brush against jerking or violent swinging as it is cut. Next, the prepared grass pointer is added to the now tipless movement pointer by slipping the hollow butt sleeve over the existing pointer (with a trifle of Durofix inside the sleeve). If the choice of grass stalks has been intelligent, the sleeve should slip on quite easily but not too loosely. Grass is cheap and several experiments in making these grass pointers are worth while. Until the cement inside the butt sleeve has dried, the now long pointer should be supported about $\frac{1}{2}$ in above the scale card by suitable packing. When the Durofix is really dry (after about an hour), the packing can be removed and the new long pointer should then swing freely over the scale card, equidistant from its surface at all points. Slight final adjustment of the movement with the play in the bolt holes of the bracket will facilitate obtaining a nice parallel swing. The pointer should be moved by blowing it gently or pushing it with the brush. The pointer can be brought to the zero end of the scale (to the right, notice, not the left) by setting the top zero adjuster central and moving the bottom adjuster to bring the tip over the zero mark on the scale.

As soon as the assembly is tilted, the pointer, at this stage, will swing away from the zero mark, because it is not yet balanced by a counterweight on the balancing stub on the other side of the pivot. First the pointer is cut so that its tip just overlaps the scale arc (not projecting above the sub-division marks). This is done by steadying the pointer with the brush against the scale card and cutting off the required amount from the tip with a clean, chisel-like

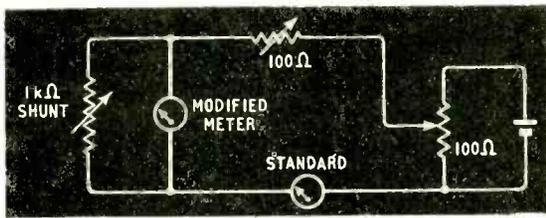


Fig. 5. Circuit for determining the shunt necessary to give full-scale deflection with 1 milliamp.

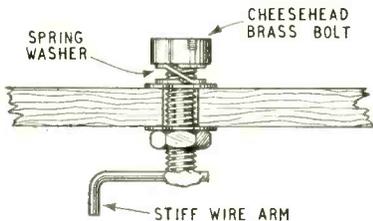


Fig. 6. Device made from a 2 B.A. bolt for external operation of the zero adjuster.

action of the razor blade. Unless the grass stalk is exceptionally thin and light, the pointer will be still unbalanced and will require added counterweight. The counterweight consists, in these instruments, of a fine helix of copper wire slipped over the balance stub. It is not advisable to try shifting the existing counterweight since this is fixed with cement, and there will be risk of damaging the movement while loosening it. A small helix of 36 or 34 s.w.g. copper wire is prepared by winding $\frac{1}{16}$ in along a darning needle. This additional counterweight is slipped over the free end of the balancing stub. A tiny touch of Chatterton's compound will fix it. Cement or glue

which dries is not very suitable, since the drying-out of moisture will upset the balance a little; the compound hardens by cooling. The small soldering iron is used to melt the compound. The added helix is shifted on the stub until its position is such that the pointer tip does not swing away from the zero mark by more than about $\frac{1}{16}$ in when the assembly is tilted sideways through a right angle.

The meter, as it can now be called, will show full-scale deflection of 80° with current between 600 and 700 μA passing through the coil. To make it show full-scale deflection with 1mA passing, a shunt is added. The circuit shown in Fig. 5 is employed for the purpose. A variable wire-wound resistor of $1\text{k}\Omega$ maximum is used temporarily as the shunt and its value is adjusted until the meter under construction shows full-scale deflection when 1mA is indicated on the instrument used as the standard. Then the shunt is accurately measured, and a fixed wire-wound resistor of small size is constructed to have exactly the same value and is wired permanently across the coil leads of the new meter.

Save for the connection of the movement leads to the terminals in the cover, and the fitting of some externally operable zero-adjusting device, the instrument is now complete. The simplest kind of zero-adjusting device would consist of a $\frac{1}{2}$ -in diameter hole in the cover, with a sliding lid, over the top zero adjuster of the movement, and something could be inserted through this hole to push the adjuster about. Details of a more elegant device, somewhat resembling the kind used in commercial moulded cases, is shown in Fig. 6. The position of this arrangement is such that the bent end of the stiff wire soldered to the end of the 2 B.A. bolt just engages in the slot of the zero adjuster without fouling the balance stub beneath it.

Standard Frequency Transmissions

Guaranteed Accuracy of B.B.C. Stations

THE B.B.C. radiates four broadcast transmissions that are guaranteed to have a frequency stability of ± 1 part in 10^6 . These standard frequency transmissions are the Light Programme transmission from Droitwich on 200 kc/s, which is broadcast daily from 0800-2300 G.M.T., GRO on 6.180 Mc/s in the 49-metre band, GSB on 9.510 Mc/s in the 31-metre band, and GSV on 17.810 Mc/s in the 16-metre band. Of these four, the 200-kc/s transmission is particularly useful for those in Europe requiring a guaranteed standard, for, owing to the wavelength used and the high power output of the transmitter, it can be received in most places. Although the frequency is guaranteed to be within 1 part in 10^6 of its nominal value, it is usually maintained to within ± 1 part in 10^7 , and can therefore be used with confidence for measurement or comparison to this high order of accuracy. For example, the B.B.C., in conjunction with the British Forces Network in Germany, uses this 200-kc/s transmission for maintaining the German transmitters precisely on their nominal frequency of 1214 kc/s, which they share with the B.B.C.'s Light Programme transmitters in the United Kingdom.

The 200-kc/s transmission is also used by the B.B.C. to control the carrier frequency of a number of low-power, unattended transmitters operating in the United Kingdom on the Third Programme channels of 647 and 1546 kc/s. Briefly, the method used is to pick up the signal from Droitwich on a t.r.f. receiver which is followed by a limiter and a chain of frequency dividers having an overall division ratio of 200:1. The 1-kc/s output from the dividers is compared with the transmitter frequency in a control

unit, which automatically adjusts the master oscillator frequency by an appropriate amount and in the right sense so as to correct any frequency error.

The frequencies of the standard transmissions on short waves (GRO, GSB, GSV) are maintained to well within ± 1 part in 10^6 of their nominal values. In view, however, of the Doppler effect, interference, and vagaries of the propagation path, it is not expected that these transmissions will be suitable for measurements requiring an accuracy better than ± 1 part in 10^6 . Unlike the 200-kc/s standard, these transmissions are not radiated according to a fixed schedule but at times which vary seasonally according to the requirements of the Overseas Service.

Apart from these standard transmissions, the frequencies of all the B.B.C.'s medium-wave stations are usually maintained to within ± 1 part in 10^7 of their nominal value. The short-term stability is generally better than ± 5 parts in 10^6 . Though no guarantee is given that this higher-order stability will be maintained, it is very unusual for the frequency to be outside these tolerances. Similarly, the frequencies of B.B.C. short-wave transmissions are accurate to ± 30 parts in 10^6 , as agreed at the Atlantic City Conference in 1947. In practice, however, it is rare for the frequency to exceed the limits of ± 10 parts in 10^6 , although such an accuracy is not guaranteed.

It may be noted that the 440-c/s tuning note radiated immediately before the opening of the B.B.C. Third Programme, and the 1,000-c/s note preceding the start of the Home Service and of the Light Programme are maintained to the same accuracy as that of the Droitwich 200-kc/s transmission.

Manufacturers' Products

New Equipment and Accessories for Radio and Electronics

Radio Tuner Unit

CONSTRUCTORS of high-quality amplifiers will be interested in the radio unit produced by C. T. Chapman (Reproducers), Ltd., of Riley Works, Riley Street, Chelsea, S.W.10. It has a four-stage superhet circuit (ECH42, EF41, EBF80) with two-position variable selectivity (7 kc/s and 10 kc/s) and amplified a.v.c. The makers claim very low noise and distortion and tell us that differential distortion is non-existent. The three controls are for tuning, wave range and selectivity—in addition to the normal medium- and long-wave bands there is a short-wave range of 16-50 metres. An output of approximately 250mV is available into 50-500 kΩ. External power supplies are needed for the heaters, which consume 1 A at 6.3 V, and h.t., which takes 20 mA at 250 V. Finished in stove enamelled silver lacquer and complete with an illuminated glass scale and bronze escutcheon, the tuner costs £12 plus £5 6s 8d Purchase Tax.

Electric Drill Suppressors

FOR eliminating the interference set up by their "Wolf Cub" drill, Wolf Electric Tools, Ltd., of Pioneer Works, Hanger Lane, London, W.5, have produced two suppressors, one for sound broadcast wavelengths and the other for television. The first, which costs 23s 6d,

is housed in an earthed metal case and is fitted at one end with a length of cable for connection to a three-pin mains plug, the other end being free to take the drill cable. The television suppressor, however, has to be fitted inside the drill body and drill owners are asked to send their machines to the nearest Wolf service depot where the job will be done for 8s 6d including return postage.

Ultrasonic Soldering Bath

TO permit the tinning of small and awkwardly shaped aluminium parts which cannot be handled by their ultrasonic soldering iron, Mullard, Ltd., of Century House, Shaftesbury Avenue, London, W.C.2, have introduced an ultrasonic soldering bath. It works on the same principle as the iron in so far as the oxide is removed by ultrasonic vibration coming from a magnetostriction transducer, but here the parts to be tinned are immersed in molten solder and the ultrasonic energy is applied through this. The bath consists of a container, $\frac{1}{2}$ in across and $\frac{1}{4}$ in deep, which is heated by a conventional resistance winding and agitated ultrasonically by a magnetostriction element composed of iron alloy laminations. It has been designed to operate from the same power unit as supplied with the iron—an amplifier which maintains a 20-kc/s oscillation by means of two coils on the magnetostriction element.


TRIX

Quality

SOUND EQUIPMENT

FOR

HIGH POWER INSTALLATIONS

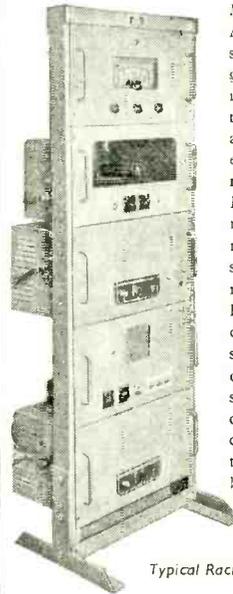

Typical Rack-Mounted Equipment

Most of the Trix Amplifiers and associated radio and gramophone units, mixers, remote control relays, etc., are designed to be easily adaptable to rack mounting. From the wide range of Trix equipment and accessories the requirements of any High Power installation can be met. We shall be pleased to outline a suitable scheme — without obligation — on receipt of details of the type of installation you need.



Reflex HORN SPEAKER


This is a heavy duty reflex type horn speaker suitable for both speech and music reproduction, having an air column 48in. in length, with flare diameter of 25in.

Full details of these and other models in the large Trix range of Sound Equipment available on request. Send for latest catalogue and price lists.

Meet us at
THE RADIO SHOW
EARLS COURT
LONDON Aug. 29-Sept. 8
X
STAND 23

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place, Tottenham Court Road,
London, W.1. Phone: MUSEum 5817
'Grams & Cables': "Trixadio, Wesdo, London."

AMPLIFIERS · MICROPHONES · LOUDSPEAKERS

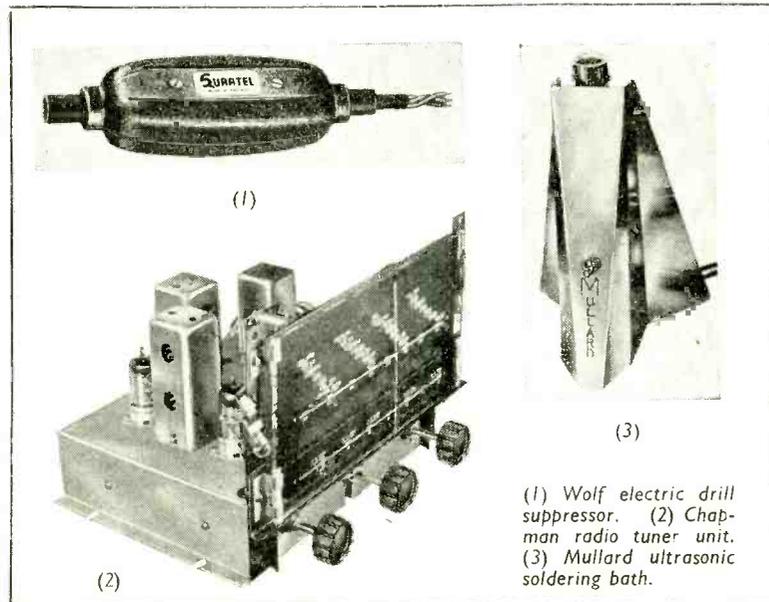

(1) Wolf electric drill suppressor. (2) Chapman radio tuner unit. (3) Mullard ultrasonic soldering bath.

RANDOM RADIATIONS

By "DIALLIST"

E.H.F. Mystery

AFTER THE LONG and thorough comparative trials of a.m. and f.m. from Wrotham, the Postmaster General's announcement in the House of Commons came as something of an anticlimax. The betting was on f.m., for the B.B.C. had made no secret of its own views and any who had had the chance of comparing the twin transmissions must have been in full agreement with them that for high-fidelity broadcasting on metre waves f.m. is the better of the two systems in fringe areas. The P.M.G. left us all rather gasping by his statement that he was advised that, in view of a certain recent development, it would be unwise to decide right away in favour of either system; he would say nothing of the new development, save that it had not yet been fully tried out. And there, at the moment of writing, we still are. The B.B.C. people professed no knowledge of it, so it must be something worked out by the Post Office engineers. One cannot believe that they would have given the P.M.G. the advice they did if they had not felt fairly sure that they had something rather good. What that something is is anybody's guess.

Acoustics

THE ACOUSTICS of the Royal Festival Hall, one reads, are so excellent that every sound is heard at its full value in any part of it. So far as broadcasts from the hall are concerned, I would say that one of its most striking acoustic features is the way in which it does justice—and more than justice—to the "ackin' corf." Clear through (or even over) loud musical passages come these bronchial barks; when the conductor stills the orchestra to a pianissimo passage, the coughs do not follow suit but continue their loud *obbligato*. Clearly, somebody ought to do something about it; but what? Tactful and charming attendants might move silently on rubber soles to administer lozenges. Alternatively, human gorillas, with bulging muscles, and also rubber-soled, might be employed to warn the persistent cougher: "One more cough out of you . . ." and then, if need be, to chuck him out. The experts of

the B.B.C. might invent a cough-filter for the microphone. Those who design our receivers would make sure of a terrific selling point could they devise a cough-eliminator which might be switched in when required. What an opportunity, if ever we come (which Heaven forbid) to the commercial programme, for the sponsors—"You have just been listening to barkless Bach: a cantata without a cough. Every member of the audience was supplied with Chisclers' Comforting Coughdrops for Chesty Chappies."

Sponsored Television

SPEAKING of sponsored programmes reminds me that I have had several letters recently from both Americans and Britons in the U.S.A. in which reference has been made to the programmes provided for viewers in the States. I gather that there is no little dissatisfaction with the matter provided by the advertisers responsible for the programmes. Some recent items have been, to say the least of it, not in the best of taste and I hear that one gave such widespread offence that a good many parents with children in their homes got rid of their receivers forthwith. Parenthetically, I would doubt whether that drastic step

achieved its object, for, if I know anything of "Junior" and his sister, they would make prompt arrangements to continue their viewing in the homes of young friends where television receivers were still *in situ*! Those who support the idea that we should go in for sponsored television might give a little thought to its not very pleasant possibilities.

That 15 Per Cent

WHEN THE GOVT. lightly gave as the reason for proposing to appropriate 15 per cent of the net licence fees that it was only just that the listener and the viewer should make some contribution to the general revenue in return for their entertainment, it must have been forgotten that both have made and continue to make substantial payments into the Government's kitty. When you buy your broadcast or television set you pay a considerable sum to the Treasury in the form of Purchase Tax. And whenever a new valve or c.r.t. is acquired, you pay your by no means small whack to the general revenue in the same way. Let's see how it works out in the form of annual contributions. Putting it on the low side, we might take the average P.T. on a wireless set at £7 10s. Give the set a life of five years and that represents £1 10s per annum. Tax on the renewals needed during that period won't be less than 5s a year—and may come to a great deal more. John Listener, then, is already putting at least £1 15s a year into the pool, in addition to the cost of his receiving licence. John Viewer starts



"WIRELESS WORLD" PUBLICATIONS

	Net Price	By post
FOUNDATIONS OF WIRELESS. M. G. Scroggie, B.Sc., M.I.E.E. Fifth Edition. (<i>Ready shortly</i>)	12/6	12/11
RADIO VALVE DATA: Characteristics of 2,000 Valves and C.R. Tubes. 2nd Edition.	3/6	3/10
TELEVISION RECEIVING EQUIPMENT. W. T. Cocking, M.I.E.E. 3rd Edition	18/-	18/8
SHORT-WAVE RADIO AND THE IONOSPHERE. T. W. Bennington. 2nd Edition	10/6	10/10
WIRELESS SERVICING MANUAL. W. T. Cocking, M.I.E.E. 8th Edition	12/6	12/11
RADIO LABORATORY HANDBOOK. M. G. Scroggie, B.Sc., M.I.E.E. 5th Edition	15/-	15/6
BASIC MATHEMATICS FOR RADIO STUDENTS. F. M. Colebrook, B.Sc., D.I.C., A.C.G.I. 2nd Edition	10/6	10/10
WILLIAMSON AMPLIFIER: Articles on Design of a High-quality Amplifier	3/6	3/9
RADIO DATA CHARTS. R. T. Beatty, M.A., B.E., D.Sc. 5th Edition—revised by J. McG. Sowerby, B.A., M.I.E.E.	7/6	7/11

A complete list of books is available on application

Obtainable from all leading booksellers or from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1.

with a much larger amount of P.T. when he buys a television set: about £20 would probably be a fair average—say £4 a year spread over the five years of his set's life. With his 15 to 20 valves and his c.r.t., I'd put the P.T. on his necessary replacements at not less than 12s 6d p.a.—and that gives an annual total per viewer of £4 12s 6d, again in addition to his licence fee. On the whole, I feel that our 11½ million listeners and our round about a million viewers are already contributing pretty well to the country's general revenue.

Problem Corner

IF ONE MAY JUDGE from the number of replies that each of them brings in, readers seem to like the little headaches that I offer them from time to time. Every one of them is founded on an actual experience. Here's a recent adventure. I was in the drawing room of a completely non-technical friend. The set, an up-to-date mains superhet of first-rate make, was switched on for the nine o'clock news. From moment to moment the announcer's words were blotted out by shattering volleys of *staccato* interference, sounding rather like the exhaust noises of an unsilenced motor bike travelling at great speed. The source of this interference was obviously something electrical in the room, for the house itself was completely detached from others and everything in other rooms was switched off. In this drawing room there were working at the time: diffused lighting from three concealed 80-watt fluorescent tubes of the kind-to-complexion type, an ordinary 2-kW electric fire (it was a chilly evening), a 600-W bowl fire, an electrically heated coffee pot and three 60-W lamp bulbs. Given that you had no measuring or other instruments available: (1) How would you have set about tracking down the interference? (2) Given that the bowl fire was guilty, what do you think was the cause of it? I warn you that it was something that I hadn't come across before.

GENERALLY speaking, the individual can do little in response to the majority of appeals made in the interest of national economy. But the salvage of waste paper is an exception; *everyone* can help. Of course, paper is *Wireless World's* raw material; equally, of course, we have an axe to grind, but we will not apologize for re-echoing the appeal being made by the Waste Paper Recovering Association for renewed salvage efforts.

PLUGS SOCKETS CROCODILE CLIPS SIGNAL LAMPS

SWITCHES

POTENTIOMETERS

RESISTORS

VALVE HOLDERS

T.V. SUPPRESSORS

TEST PRODS

KNOBS

JACKS

JACK PLUGS

FUSES

FUSE HOLDERS

THERMAL

FLASHER

UNITS

MICRO-SWITCHES, ETC., ETC.

FOR OVER



25 YEARS

'THE CHOICE OF CRITICS'

REGD. TRADE MARK

THE House of Bulgin extends a very warm welcome to all our Friends, to visit Stand No. 2 at the National Radio Show. For over a quarter of a century we have continued to give service, especially in times of difficulty, Technical advice when required, and unsurpassed quality of manufactures at all times.

With a range of over 2,000 different types of components which include 15,000 piece parts, an enthusiastic staff, and experience dating since the inception of Broadcasting we are sure Design and Production Engineers will find many new Bulgin Products displayed, and our Technical Engineers ready to give assistance on any problem of manufacture.

AUG. 29th to SEPT. 8th—VISIT STAND No. 2
NATIONAL RADIO SHOW, EARLS COURT

SEND FOR NEW CATALOGUE No. 190/W.W.
PRICE 1/- POST FREE

MANUFACTURERS OF RADIO & ELECTRONIC COMPONENTS

A.F. BULGIN & CO. LTD
BYE-PASS ROAD BARKING
TELEPHONE Rippleway 3474 (5 lines)

UNBIASED

By FREE GRID

Plea for Push Buttons

RADIO has had its fashions in receiver design just like women's clothes and some of them have been almost as silly, but on the whole there has been a sound reason for even the most ephemeral of wireless fashions. As an instance of this I would point to the popular reflex design of the early days of broadcasting. The high price of valves forced this compromise on us and great ingenuity was exercised in getting round some of its more glaring snags; how glaring they were was pointed out at the time by this journal under the apt title of "Rocks That Wreck Reflexing."

Other fashions, after a brief innings, have virtually disappeared only to return later in vastly improved form to become a permanent feature of design, the most outstanding instance of this being the superheterodyne. Push-button tuning threatens to become another instance of it. P.B.T. first made its appearance in pre-war years and, despite a lot of teething



A leaning towards the bar

troubles, it bade fair to become a permanency in all sets, but the war changed all that. It is, however, now starting to stage a comeback but a very cautious one so far. Nevertheless, I venture to prophesy that in its greatly improved and more stable form it will eventually sweep all other forms of tuning off the market. The sooner it does so the better, for it is, in my opinion, the only tuning system which is technically sound and at the same time completely womanproof.

If you pause for a moment to think instead of sitting down to write an indignant letter to the Editor, you will see why this is so. In the case of the ordinary system of variable tuning everything must of necessity be a compromise. If, for instance, the degree of aerial coupling and the LC ratio of the tuning circuits be just right for receiving a station at one end of the tuning scale, they certainly won't be just right at the other end;

the aerial coupling is, of course, set at a compromise value for all stations and the LC ratio varies from station to station with the tuning. Much the same thing applies to all the other possible "variables" in the receiver. But with pre-set P.B.T. a woman or other completely untechnical user can adjust a large number of "variables" simultaneously by simply pushing a button having the requisite large number of cams on the rod attached to it. Everything can, in fact, be made "optimum" for receiving a particular station.

My thoughts in this matter are, of course, far from original; they are just self-evident. But I do not doubt that those with a leaning towards the Bar can quickly work up a convincing set of counter-arguments to put before you who form the jury; in fact, I could do it myself.

National Radio Centre

THAT portion of the South Bank Exhibition which lies between the County Hall and Hungerford Bridge is, I believe, already earmarked for the erection of some sort of Government building, otherwise I would have suggested that a new and up-to-date Broadcasting House be erected there. Already, however, there is talk of clearing the unsightly mess on that portion of the south bank of the Thames which lies between Waterloo and Blackfriars bridges so that it may be made into a fitting counterpart of the Victoria embankment on the other side of the river.

So far only vague and tentative suggestions have been made as to the nature of the buildings to be erected there. But now that the National Concert Hall has been built and the Queen has laid the foundation stone of the National Theatre on the adjacent section of the river bank, it would surely be fitting for the whole of the south side of the Thames between Hungerford and Blackfriars bridges to be turned into a national entertainment centre. What more fitting than that the National Concert Hall and National Theatre should be flanked by a super radio and television centre which would make New York's Radio City look like a penny gaff. Next year, which sees the B.B.C.'s 30th birthday and also the 30th anniversary of the first radio exhibition at the Horticultural Hall, would be a fitting time to lay the foundation stone.

The site is ideal in every way even as to size, being not too big or too small. There would be ample room for spacious studios as well as public

listening and viewing halls. There would even be room for the administrative offices, although it would be preferable that they be left in the human rabbit warren at Portland Place and allowed to overflow into the present studios. The opportunity of acquiring such a magnificent position for broadcasting H.Q. is not likely to occur again for a thousand years.

Television Recording

IT is astonishing what a large number of "tape" recording and reproducing outfits—to say nothing of parts for making them—is available nowadays. The makers of some of them stress the fact that among their many uses is the bottling of broadcasting programmes for future consumption, but, so far as I know, none of them incorporates a time-switch so that you can pre-set the whole apparatus to can a programme which is due to go on the air at a time when you can't be at home to listen. Eventually, of course, as I've always demanded, every receiver will incorporate a recorder and time-switch as an integral part of it. At present, however, the expense of doing this would be too great, and the resultant set, complete with P.T., would be far beyond the means of all save dentists and others who earn their daily crust by the cold sweat on other people's brows.

Although, as I have already mentioned, recording units are now available in considerable numbers, I think I am correct in saying that nobody has yet made any attempt to produce one for the vision part of television programmes. I am not, of course, thinking of apparatus for recording television as actual pictures on cine film, but as modulated electrical impulses on disc or tape. Baird recorded vision on discs long years ago and there is no fundamental reason why the same broad principles should not be used for recording it on tape. It is no business of mine to take the bread out of the mouths of inventors and manufacturers by giving full technical details here and, therefore, much against my will, I refrain from doing so.



Cold sweat

The PERFECT TEST TEAM

See us at the
RADIO SHOW
 Stand No. **9**
EARLS COURT, LONDON
 Aug. 29—Sept. 8



The illustration depicts a set of modern "AVO" testgear being used to measure the "Q" of the secondary winding of the second I.F. transformer on a chassis of unknown characteristics—just one of many tests which can be performed by this combination of instruments.

A signal of predetermined frequency from the "AVO" Wide Range Signal Generator is being led into the Electronic Test Unit, where it is amplified and fed to the secondary winding of the transformer. The Electronic Testmeter is connected across the tuned circuit under test and, from the readings obtained and the controls of the Electronic Test Unit, the "Q" of the circuit can be determined.

The three instruments, shown as a team, cover a very wide field in measurement and form between them a complete set of laboratory testgear, ruggedly constructed to withstand hard usage.



ELECTRONIC TESTMETER

A 56-range instrument combining the sensitivity of a delicate galvanometer with the robustness and ease of handling of an ordinary multi-range meter. Consists basically of a highly stable D.C. Valve Millivoltmeter, free from mains variations and presenting negligible load on circuit under test.

Switched to measure:—
 D.C. Volts: 2.5mV to 10,000V.
 D.C. Current: .25 μ A to 1 Amp.
 A.C. Volts: up to 2 Mc/s. R.M.S.
 .1V to 250V R.M.S.
 up to 200 Mc/s.

A.C. Power Output: 5 mW to 5 Watts
 Decibels: -10db to +20db.
 Zero level 50 mW.
 Capacitance: .001 μ F to 50 μ F.
 Resistance: .2ohm to 10 Megohms
 Operates on 100-130v. and 200-260v.
 50-60 c/s A.C. mains



ELECTRONIC TEST UNIT

For measuring small values of A.C. voltage, inductance, capacity, and "Q" at radio frequencies. Although "Q" primarily for use with "AVO" instruments, it can be used with any suitable Signal Generator/Valve Voltmeter combination.

As a Wide Range Amplifier, it is capable of an amplification factor of 40 \pm 2-3db between 30c/s and 20Mc/s.

As a Capacity Meter, it covers measurements at radio frequency from .5pF to 1000pF in two distinctly calibrated ranges.

As an Inductance Meter it gives direct measurements from .5 μ F to 50mH in six ranges.
 As a "Q" Meter, it indicates R.F. coil and condenser losses at frequencies up to 20 Mc/s.
 Operates on 100-130 v. and 200-260 v.
 50-60 c/s A.C. mains.



WIDE RANGE SIGNAL GENERATOR

An instrument of wide range and accuracy for use with modern radio and television circuits. Turret coil switching, provides six frequency ranges covering 50 Kc/s to 80 Mc/s.

- Range 1. 50 Mc/s—150 Kc/s.
- " 2. 150 Kc/s—500 Kc/s.
- " 3. 500 Kc/s—1.5 Mc/s.
- " 4. 1.5 Mc/s—5.5 Mc/s.
- " 5. 5.5 Mc/s—80 Mc/s.
- " 6. 20 Mc/s—80 Mc/s.

Accuracy to within 1% of scale marking. Gives sensibly constant signal of good wave-form, modulated or unmodulated, over entire range. Minimum signal less than 1 μ V at 20 Mc/s and less than 3 μ V between 20 and 80 Mc/s. Gives calibrated output from 1 μ V to 50 mV.
 Operates on 100-130 v. and 200-260 v.
 50-60 c/s, A.C. Mains.
 Battery-operated model also available.

Sole Proprietors & Manufacturers:—

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
 WINDER HOUSE · DOUGLAS STREET · LONDON · S.W.1

Telephone: VICTORIA 3404-9

GOODSELL

RECEIVERS AND HIGH-FIDELITY AMPLIFIERS

NOTE THESE FEATURES

- ★ Impregnated grid coupling condensers.
- ★ Paper Condensers on the H.T. supply line.
- ★ Matched or close tolerance resistors, where balance is important.
- ★ Steel chassis.
- ★ Partridge Mains and Output Transformers.
- ★ Model D.P.S. with separate H.T. supply incorporated on the same chassis for use with multi-stage pre-amplifiers.

Williamson Amplifier Type K.T.66 D.P.S. to specification. Illustrated is the dual power supply model with Partridge transformers, large paper condensers and B.V.A. valves.

Price £32/10/-



● Four-Stage Tone-Control. Wide range four-stage tone-control and equalizer for L.P. and Standard records, with microphone and radio input.

Complete with engraved perspex panel £8/5/-.
Four-Station pre-set superheterodyne receiver with variable selectivity, from £8/15/- plus Tax.

Type E.L.37 D.P.S., illustrated, is a new model, using a special output transformer with sectionalized windings and having an extremely low leakage inductance, together with the latest Mullard B8a valves. 9 watts output. £22/-/-.



You need a GOODSELL for good reproduction

DEMONSTRATION ROOM AND SALES OFFICE

B.K. PARTNERS LTD., 229, 231 Regent Street, W.1. (Sole Distributors for United Kingdom)

STOCKISTS HOLLEYS RADIO 285 Camberwell Road, S.E.5

CLASSIC ELECTRICAL CO. LTD., Lower Addiscombe Road, Croydon

MANUFACTURED BY **GOODSELL LTD., 40 GARDNER STREET, BRIGHTON, 1**

H.P. TERMS—from L.R.S. COMPANY LTD., BALCOMBE, SUSSEX

Brighton 26735



..with a wide range of industrial applications

The Mullard range of electronic flash tubes is finding increasing use in industrial photography and in problems involving the analysis of motion in production processes. On account of their high luminous efficiency, low-triggering voltage, daylight colour quality, and short-flash duration, the Mullard flash tubes at present available offer wide possibilities in equipments used for applications varying from the motion-study of workers to the examination of high-speed machinery in operation. Brief technical details on these tubes are listed below. Fuller information will be supplied on request to the Communications and Industrial Valve Department.

TYPE	DESCRIPTION	MAXIMUM SINGLE DISCHARGE RATING (JOULES)	MAXIMUM OPERATING VOLTAGE (KV)
LSD2	Microsecond flash tube	35	10
LSD3	For operation in portable flash equipments	100	2.7
LSD3A			
LSD5	For studio flash equipments. Provision is made for a modelling lamp. This tube supersedes the LSD4	1000	2.7
LSD7	For higher power portable equipments	200	2.7
LSD8	Stroboscopic flash tube	30 watts dissipation	2.7
LSD9	Quartz tube for high-power or U.V. flash	1000	2.7

A full range of straight tubes is also available for those who require line source flash tubes.

STAND No. 75
THE RADIO SHOW
EARLS COURT





The **BROADCASTER** *Gliding*
SAPPHIRE GRAMOPHONE **NEEDLE**
Plays 5,000 times
without replacement

No. 1



TRAILER for use with heavy
Magnetic Pick-up or ordinary
Gramophones

No. 2



STRAIGHT for use with
Standard or Crystal Pick-up

No. 3



LIGHTWEIGHT for use with
Miniature Pick-up

AS USED FOR BROADCASTING

OBTAINABLE FROM ALL MUSIC & RADIO DEALERS

or direct from:


BROADCASTER RADIO SUPPLIES LTD., 112-114-116 Old Street, London, E.C.1

Telephone: CLERkenwell 2133-7

Telegrams: Plusagram, Cent, London



STANDARD ENCLOSED RACK UNITS

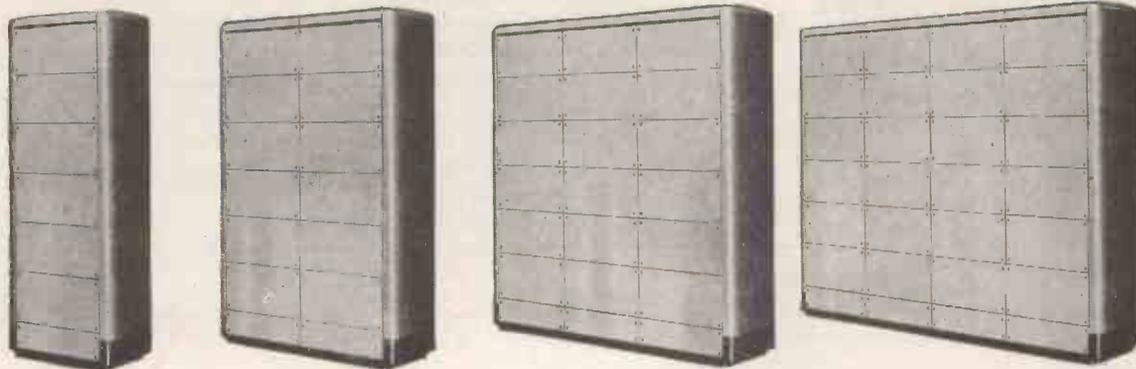

Imhof standard rack units are available as single units or multiple assemblies in small or large quantities. Units are made in 6ft. and 4ft. sizes to take standard 19in. panels and are 19in. deep. End and back panels are hung on lift-off hinges and back and top panels are louvred for ventilation. A range of standard accessories is available, including mobile base

unit, gram unit, desk unit, and panels, chassis, chassis runners and brackets, telescopic runners, handles, etc. Semi-Standard variations are units to take 22½in. panels and/or units 24in. in depth and racks with inner panel mounting frames. Special quotations can be given for non-standard variations. Write for illustrated leaflet on enclosed racks giving full details and prices.

IMHOF'S

ALFRED IMHOF LIMITED, 112-116, New Oxford St., London, W.C.1. Tel.: MUS. 7878

THE *New* WINDSOR Television **WOBBULATOR**



MODEL 260A

MODEL 260A TELEVISION WOBBULATOR • MODEL 260 A. TELEVISION WOBBULATOR MODEL 260A

The first self-contained electronic instrument providing visual alignment facilities for television receivers. Simple, compact and efficient—its use will save many hours of valuable time in the service department.

FEATURES

- ★ **CARRIER FREQUENCY** 5-70 Mc/s. 10-140 Mc/s (on 2nd harmonic).
- ★ **BANDWIDTH** 0-5 Mc/s total. 0-10 Mc/s (on 2nd harmonic).
- ★ **SWEEP FREQUENCY**. 50 c.p.s. sinusoidal, return trace blacked out automatically.
- ★ **OUTPUT**. Adjustable from 0-10 mV approx. Fixed and variable attenuators are fitted. Output impedance 75 ohms.

EARLY DELIVERY.

Please write for further details and information on other WINDSOR and TAYLOR products.

MODEL 260A TELEVISION WOBBULATOR • MODEL 260 A.



TAYLOR ELECTRICAL INSTRUMENTS LTD.
419/424 MONTROSE AVENUE, SLOUGH BUCKS., ENGLAND

Tel. SLOUGH 21381 (4 lines)
Grams. & Cables : TAYLINS, SLOUGH

'Let's have
"THE GONDOLIERS"
AGAIN!



Whatever your favourite piece of music, the Soundmirror will record it and play it back for you again and again. There is no end to the thrills which this new magic entertainer can bring. It will record the humorous patter of your favourite comedian, the art of the orator, the fun of a party or important family occasions like weddings. It will play them back with perfect fidelity immediately it is recorded and as often as you wish. Unwanted recordings are automatically erased as new ones are made and the magnetic tape used time and time again.

MODELS FROM £69. 10. 0 exclusive of microphone.

Manufactured under agreement with the Brush Development Co., of the U.S.A. Licensed under the Brush Development Co., the Brush Crystal Co., Magnetone Inc., and Thermionic Products Ltd. Patent No. 454595 and others; and patents pending in all the principal countries of the world.



Now available in England—the book "Magnetic Recording" by Dr. S. J. Begun. A comprehensive treatise. Price 25/-, postage 9d. extra.

Call on your local radio dealer and hear your own voice recorded or write for literature or a demonstration by appointment to the manufacturers.

THERMIONIC PRODUCTS LTD.

(Division SM/WW), Hythe, Southampton.

Phone: Hythe 3265

London Showrooms: **Morris House, Jermyn Street, S.W.1**

Telephone: Whitehall 6422 (5 line).

Sales and Service Centres: Manchester, Birmingham, Bristol, Leeds, Newcastle, Glasgow, etc.

ELECTRONICS CENTRE

of the
NORTH



**THE LARGEST STOCKISTS
OF ELECTRONIC INSTRUMENTS
IN THE NORTH**

Oscilloscopes, oscillators, signal generators, meters, radio and television test gear, tape recorders, resistance boxes, portable metal detectors, photoelectric apparatus, valve testers, high fidelity amplifiers, radiation monitors, E.H.T. units, electronic millisecond meters, constant voltage transformers and industrial electronic control apparatus of all kinds.

- **DISTRIBUTION** Suppliers and Stockists of all types of Electronic Instruments and equipment.
- **COMPLETE INSTALLATIONS ENGINEERED.** Metal Detection, Batch Counting, Electro-chemical Controls, Radiation Thickness Measurement.
- **DESIGN** of ANCILLARY EQUIPMENT
- **MAINTENANCE & SERVICE**

ADVANCE COMPONENTS LTD.

We are pleased to announce that we have been appointed sole distributors in Lancashire for Advance Components Ltd. Trade enquiries will receive immediate attention.

Write us to add your name to our mailing list for regular information on new instruments and development.


F. C. ROBINSON & PARTNERS LTD

287 DEANS GATE

MANCHESTER

DEAnsgate 6601

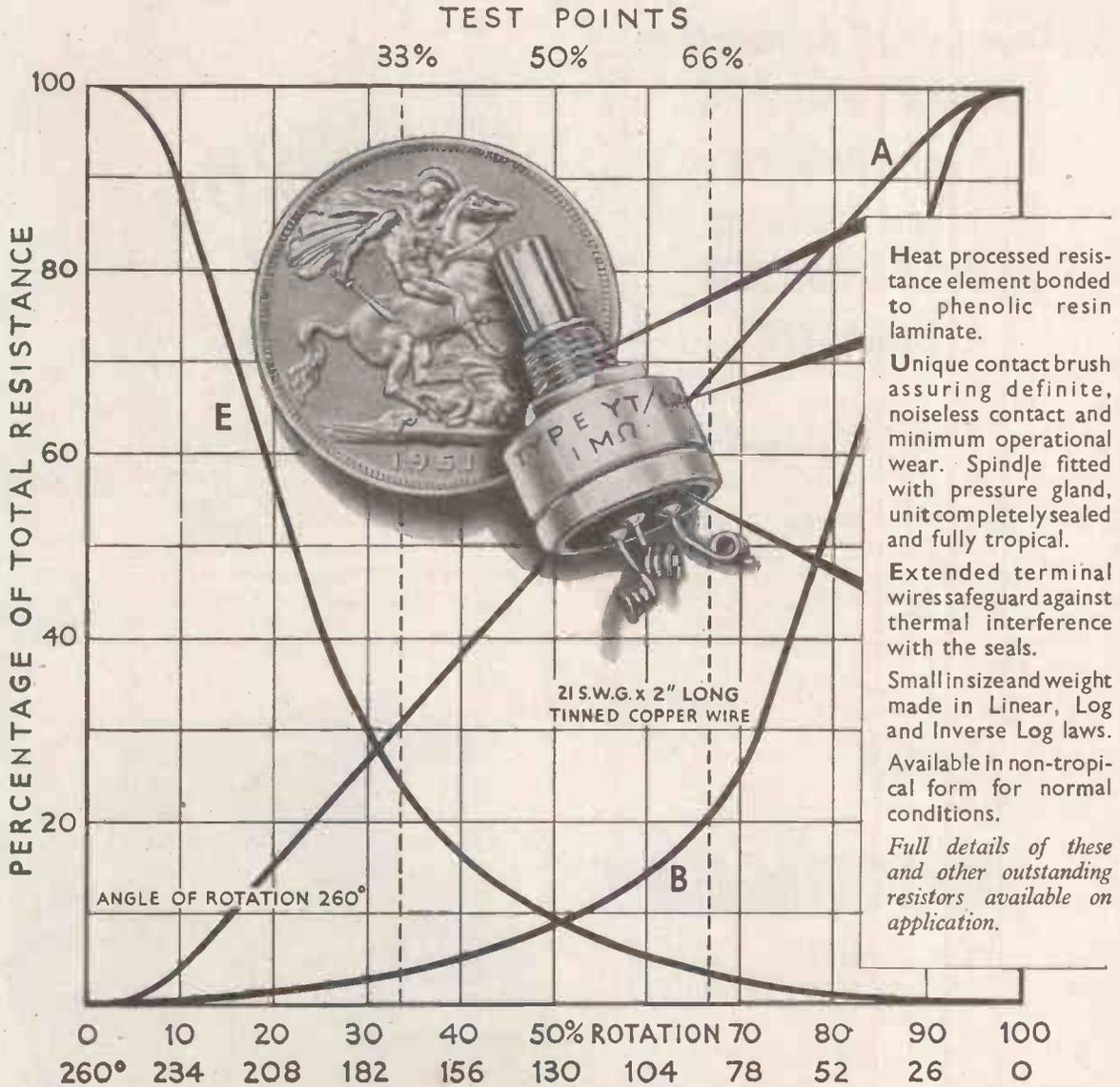DUBILIER *Miniature* VOLUME CONTROL TYPE Y



Heat processed resistance element bonded to phenolic resin laminate.

Unique contact brush assuring definite, noiseless contact and minimum operational wear. Spindle fitted with pressure gland, unit completely sealed and fully tropical.

Extended terminal wires safeguard against thermal interference with the seals.

Small in size and weight made in Linear, Log and Inverse Log laws.

Available in non-tropical form for normal conditions.

Full details of these and other outstanding resistors available on application.

A CROWN OF RESISTOR ENGINEERING ACHIEVEMENT

DUBILIER

RESISTORS

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, W.3.
 Telephone : Acorn 2241 (5 lines) Telegrams : Hivoltcon, Westphone, London
 Cables : Hivoltcon, London, Marconi International Code.

Recognised as the Most Reliable Valveholders

Now in full production
NOVAL and B7G
 Valveholders
 of all types in
NYLON LOADED
BAKELITE



B9A-NOVAL

B7G

We make all types of Valveholders

Wholesale Enquiries:—CYRIL FRENCH LTD., HIGH STREET, HAMPTON WICK, MIDDLESEX · KIN. 2240
 Manufacturers' Enquiries:—THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY ASHTEAD 3401

Presenting




GOODMANS

HIGH FIDELITY—12" P.M.
TWIN CONE AXIOM 150

This 12" high fidelity unit has a twin curvilinear diaphragm (Patent No. 451754). A carefully designed magnet assembly using anisotropic material provides a total flux of 158,000 maxwells on a 1 1/2" pole. The back centring device is a dustproof bakelised linen disc with concentric corrugations.

The combination of these features gives this precision-built instrument an outstandingly wide coverage from 40 to 15,000 c.p.s. free from base modulation effects.

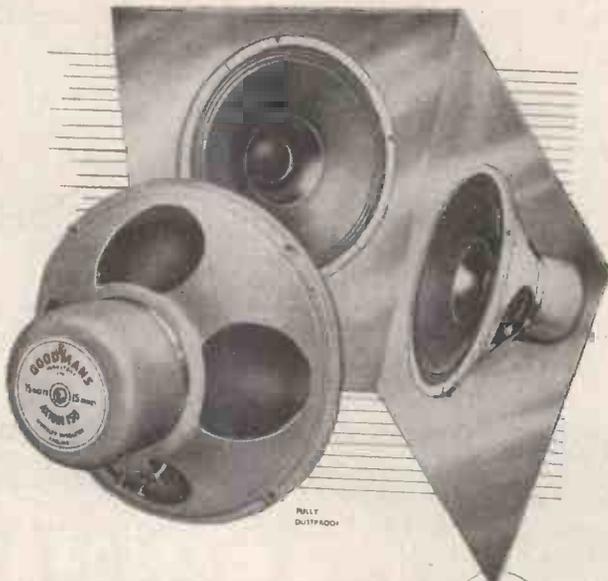An ideal high fidelity reproducer for the record enthusiast and the connoisseur of wide range musical reproduction, it gives exceptionally fine transient and frequency response.



WINGS
DAY
 SATURDAY SEPT. 15

Give for those who Gave

Meet us at the Radio Show—STAND 96

- Frequency Coverage 40/15,000 c.p.s.
- Overall Diameter 12 1/2"-31.3 cms.
- Overall Depth 6 1/8"-17.6 cms.
- Fundamental Resonance 55 c.p.s.
- Voice Coil Diameter 1 3/4"-4.4 cms.
- Voice Coil Impedance 15 ohms at 400 c.p.s.
- Maximum Power Capacity 15 Watts Peak A.C.
- Flux Density 14,000 gauss
- Net Weight 12 lbs. 13 oz.-5.8 kg.
- Finish Grey Rivelling Enamel

£10.5.6
 LIST




For use with this model we recommend Goodman's High Fidelity Heavy Duty Output Transformer Type H.4. Net Weight 5 lbs.—2.3 kg.



A Bass Reflex Cabinet measuring approximately 30"x23"x16" and a corner cabinet have been specially designed for this loudspeaker and working drawings are available

GOODMANS INDUSTRIES LIMITED
 Lancelot Road, Wembley, Middlesex. WEMbley 1200

Outstanding in its class...

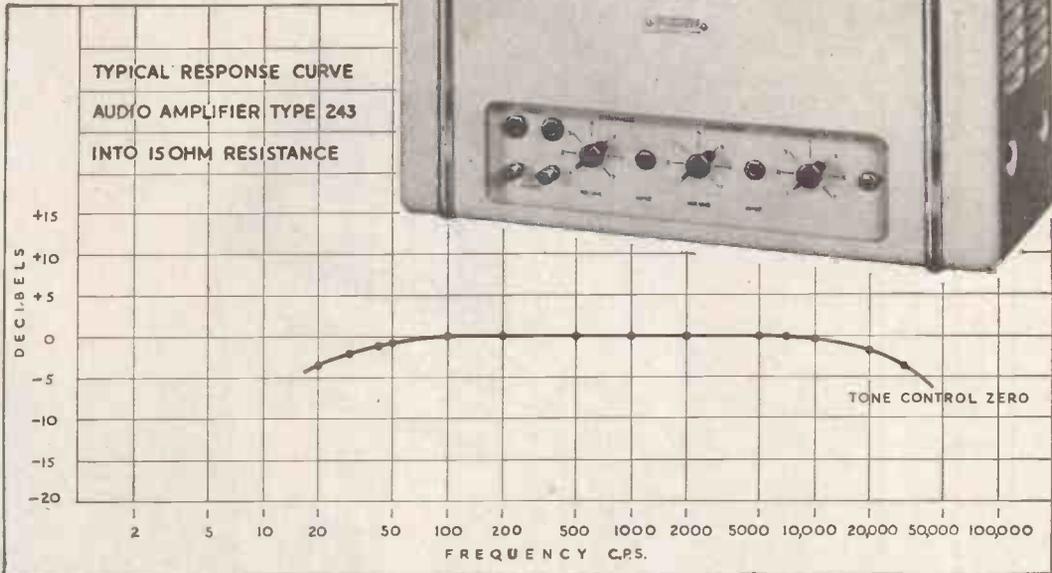

The METROVICK audio amplifier

TYPE 243

The type 243 amplifier is designed for use with high grade public address systems, for the connoisseur of quality and for industrial applications where faithful response over the audio range from 30 to 15,000 cycles is required. This Metrovick instrument is outstanding in its class and provides an output of 20 watts.

SPECIFICATION

Supply: 200/250V 50 c/s single-phase; consumption approximately 170 VA for full output.

Input: Gramophone not exceeding 0.2V for full output. Microphone not exceeding 0.02V for full output. The two circuits can be mixed as required.

Impedance: 7 ohms, 15 ohms and 45 ohms.

Output: 20 watts with negligible distortion.

Tone Control: Continuously variable.

Response: ± 1 db from 30 to 15,000 c/s at zero position of tone control.

Controls: These are recessed to avoid damage and are illuminated when in operation.

Dimensions: 18 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ ".

Weight: 60lb. net.

Finish: The instrument is housed in an attractive steel case, stove enamelled in cream or blue as desired. A leather carrying handle is fitted.

METROPOLITAN-VICKERS ELECTRICAL COMPANY, LIMITED, TRAFFORD PARK, MANCHESTER, 17

Member of the A.E.I. group of companies



METROVICK Applying Electronics to Industry

MAINS TRANSFORMERS, FULLY INTERLEAVED. SCREENED AND IMPREGNATED. ALL GUARANTEED. ALL PRIMARIES ARE 200/250 v. Half Shrouded.

MSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps.	18/-
MS63. Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps.	18/6
MS40. Windings as above. 4 v. at 4 amps., 4 v. at 2 amps.	18/6
Output	
HS2. 250-0-250 v. 80 m/a.	21/-
HS30. 300-0-300 v. 80 m/a.	21/-
HS3. 350-0-350 v. 80 m/a.	21/-
HS2X. 250-0-250 v. 100 m/a.	23/-
HS75. 275-0-275 v. 100 m/a.	23/-
HS30X. 300-0-300 v. 100 m/a.	23/-
HS3X. 350-0-350 v. 100 m/a.	23/-

Fully Shrouded

FSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps.	18/6
Output	
FS2. 250-0-250 v. 80 m/a.	23/-
FS30. 300-0-300 v. 80 m/a.	23/-
FS3. 350-0-350 v. 80 m/a.	23/-
FS2X. 250-0-250 v. 100 m/a.	25/9
FS75. 275-0-275 v. 100 m/a.	25/9
FS30X. 300-0-300 v. 100 m/a.	25/9
FS3X. 350-0-350 v. 100 m/a.	25/9

All the above have 6.3-4.0 v. at 4 amps., 5-4.0 v. at 2 amps.

FA43. Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded.	51/-
FS50. Output, 450-0-450 v. 250 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded.	75/-
F30X. Output, 300-0-300 v. 80 m/a., 6.3 v. 7 amps., 5 v. 2 amps. Framed. Flying leads.	31/9
F35X. Output, 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0.2-6.3 v. 2 amps. Fully shrouded.	71/6
FS160X. Output, 350-0-350 v. 160 m/a., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded.	45/-
FS43X. Output, 425-0-425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded.	69/-
HS6. Output, 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. For receiver R1355. Half shrouded.	29/3
HS150. Output, 350-0-350 v. 150 m/a., 6.3 v. 3 amps., C.T. 5 v. 3 amps. Half shrouded.	30/9
F36. Output, 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. Half shrouded.	30/9
FS120. Output, 350-0-350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 2 amps., C.T. 5 v. 3 amps. Fully shrouded.	33/-
FS256. Output, 250-0-250 v. 80 m/a., 6.3 v. at 6 amps., 5 v. at 3 amps. Fully shrouded.	30/9
PR1/1. Output 230 v. at 30 m/a., 6.3 v. at 1.5/2 amps.	23/-
FS150. 350-0-350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps.	34/9
FS150X. Output, 350-0-350 v. at 150 m/a., 6.3 v. at 2 amps., C.T. 6.3 v. at 2 amps., C.T. 5 v. at 3 amps. Fully shrouded.	34/9

The above have inputs of 200/250 v.

FILAMENT TRANSFORMERS

F4. Output, 4 v. 2 amps.	9/-
F6. Output, 6.3 v. 2 amps.	9/-
F6X. Output, 6.3 v. 0.3 amps.	6/-
F12X. Output, 12 v. at 1 amp.	9/-
F12. Output, 12.6 v. tapped 6.3 v. at 3 amps.	18/6
F24. Output, 24 v. tapped 12 v. at 3 amps.	26/-
F12 and F24 framed with Flying Leads.	
FU6. Output, 0.2-4-4-6.3 v. at 2 amps.	11/-
F29. Output, 0.2-4-5-6.3 v. at 4 amps.	20/9
FU6 and F29 clamped with Flying Leads.	
FS. Output, 6.3 v. at 10 amps. or 5 v. at 10 amps. or 12.6 v. at 5 amps. or 10 v. at 5 amps.	37/9
F6/4. Output, four at 6.3 v. tapped at 5 v. at 5 amps. per winding, giving by suitable series and parallel connections 24 v. at 5 amps., 20 v. at 5 amps., 18 v. at 5 amps., 15 v. at 5 amps., 12.6 v. at 10 amps., 10 v. at 10 amps., 6.3 v. at 20 amps., 5 v. at 20 amps.	57/-
F5 and F6/4 framed with Flying Leads.	
FU12. Output 0-4-6.3 v. 3 amps.	19/6
FU24. Output 0-12-24 v. 1 amp.	19/6

The above have inputs of 200/250 v.


OUTPUT TRANSFORMERS

MOPI. Ratios 26, 46, 56, 66, 90, 120-1 50 m/a. max. current. C.T. for Q.P.P. Class B., etc. Secondary 2/4 ohms. Top panel and clamped, each.	6/-
OPI. Midget Power Pentode, ratios 30, 60, 90-1, 40 m/a., Secondary 2/3 ohms, each.	4/-
OP2. Midget Pentode, ratios 45-1, Secondary 2/3 ohms, 40 m/a. per doz.	39/6
OPI0. 10/15 watts output. 20 ratios on Full and Half primary	19/9
OP30. 30 watts output, 20 ratios on Full and Half primary	28/6
Williamson's O.P. Transformer to Author's specification	£4/3/6
Chokes for Williamson's Amplifier. 30H. at 20 m/a.	15/6
10H. at 150 m/a.	35/6
Choke C4. 60 m/a., approx. 8 H., 350 ohms.	5/-
Choke C5. 40 m/a., approx. 5 H., 360 ohms.	4/-
Choke C6. 50 m/a., 50 H., 1,500 ohms.	22/-
C7. 90 m/a., 180 ohms, clamped.	6/3
C8. 360 Micro henries clamped.	5/3
Belling Lee Co-Axial Plugs. Type 642/F., each.	1/3
Belling Lee Co-Axial Sockets. Type 604/S, each.	1/3

Quotations etc.—stamped addressed envelope please.

C.W.O. (add 1/- in £ for carriage), all orders over £2 carriage paid. Trade and also Export enquiries invited

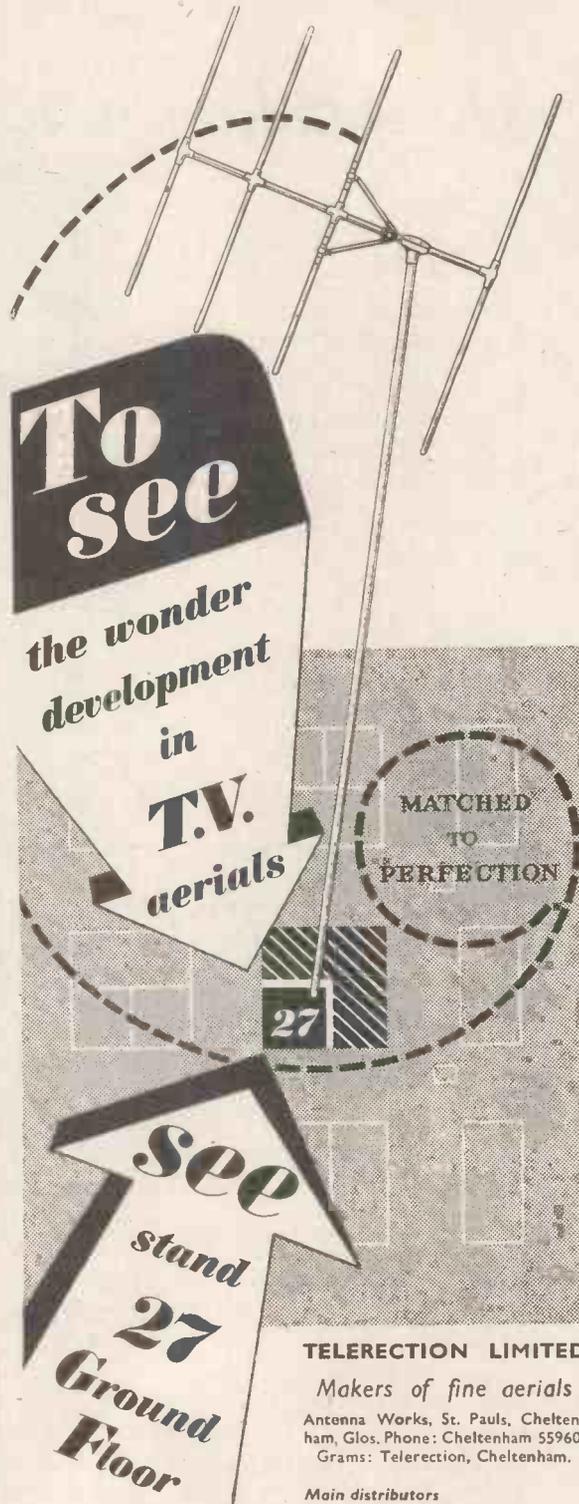**H. ASHWORTH (Dept. W.W.),
676, Gt. Horton Road, Bradford, Yorks.**



TELERECTION LIMITED

Makers of fine aerials
Antenna Works, St. Pauls, Cheltenham, Glos. Phone: Cheltenham 55960.
Grams: Telerection, Cheltenham.

Main distributors for Holme Moss Area


Messrs. Midland Auto Components, 58, Cambridge St. Birmingham.

PLEASE ASK FOR CATALOGUES SHOWING AERIALS COVERING EVERY REQUISITE

DEPTH PERSPECTIVE

The ability of a reproducer in separating the instruments of an orchestra is dependant among other factors upon the area from which the sound appears to emanate. Many experimenters will have found that a larger area appears to improve orchestral analysis but that it detracts from the realism of solo instruments and the human voice. In the Corner Ribbon Loudspeaker, the sound source is small and forward, but it radiates a proportion of sounds in nearly all directions, including upwards and to the rear. The sound pattern reproduced from solo instruments is very similar to that obtained in nature and it is probably the only loudspeaker which can be used in direct comparison laboratory tests to give a complete illusion of most instruments to a critical audience. With an orchestra, the larger microphone distances influence the acoustics of the recording so that the apparent sound source in the loudspeaker recedes. Reflections from the back radiation add to the area of sound so that it now appears to emanate from an opening of eight to ten square feet.

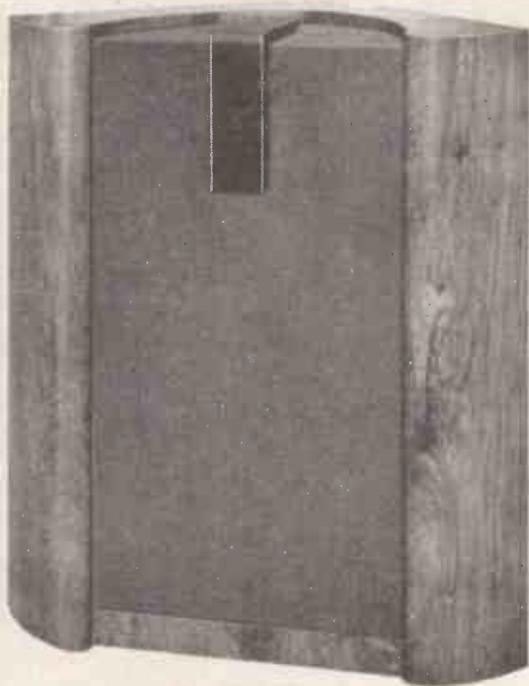The above is just one of the reasons why the Corner Ribbon Loudspeaker gives an analysis of sound in natural perspective.





THE
CORNER RIBBON
LOUDSPEAKER

£83

controlled sale

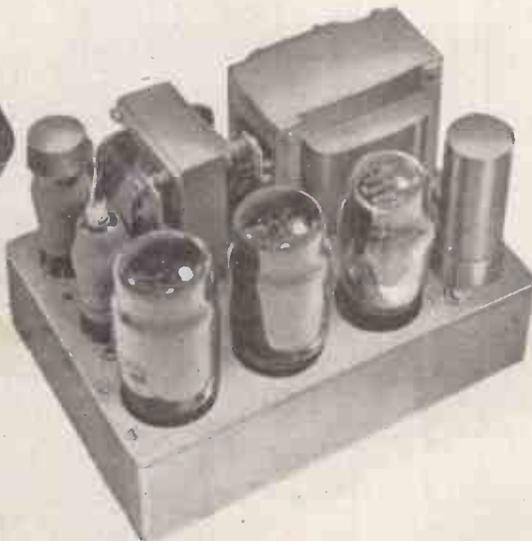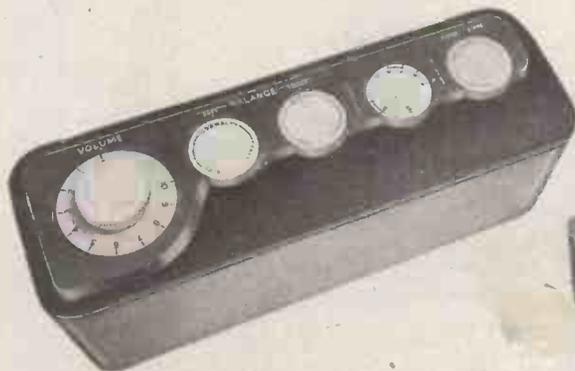A booklet describing the development of this loudspeaker is available on request



It is important to remember that a good loudspeaker will give you music, noise and distortion, all faithfully reproduced. The QUAD amplifier used with a good loudspeaker will give you the closest approach to the original sound.

THE Q.U.A.D. AMPLIFIER
in two units as illustrated

£35



HUNTINGDON · HUNTS · TEL: 866

AN AUDIO FREQUENCY RESPONSE CURVE

when plotted point by point is a tedious and lengthy operation. A bottleneck in production, it requires numerous instruments and operatives who could be used more profitably elsewhere.

The **MODEL 1900 AUDIO FREQUENCY RESPONSE CURVE TRACER** (see illustration) incorporates in the one instrument all the circuiting needed for taking a response curve. It automatically draws on the screen of a cathode ray tube a full and accurate curve once in **5 SECONDS** repeating it as often as desired.

The instrument's small size, portability and moderate price plus its high speed of operation, make it invaluable wherever a response curve must be taken.




Model 1900 A.F. Response
Curve Tracer

For details write to:—

INDUSTRIAL ELECTRONICS
Makers • of Industrial Controls and Precision Instruments
99, GRAYS INN ROAD, LONDON, W.C.1. Phone: HOLborn 9873/4

Ceramic stand-off Insulators

by
U.I.C.

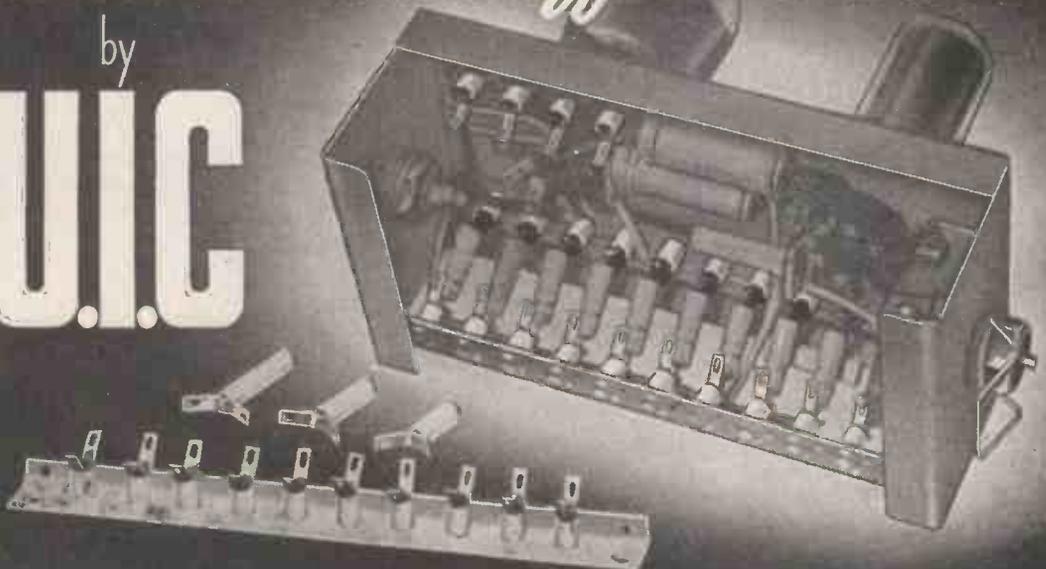

UNITED INSULATOR CO. LTD. OAKCROFT RD. TOLWORTH · SURBITON · SURREY
TELEPHONE: ELMBRIDGE 5241 CABLES: CALANEL, SURBITON



G.E.C.

Germanium Diodes


The photograph shows a G.E.C. germanium diode soldered between adjacent tags of an octal socket in a noise-suppression circuit. Standard half-watt and quarter-watt resistors provide an interesting comparison in size.

It is important to note that this photograph is of a G.E.C. production television sub-chassis into which the crystal is soldered without heat shunts and with the leads clipped to the required lengths.

For further information apply to Osram Valve & Electronics Dept.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2

EXACT EFFORTLESS TUNING

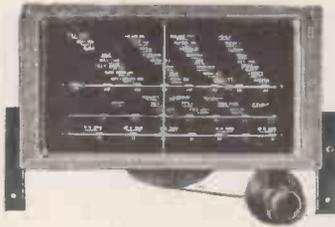

The S.L.8 Spin wheel drive gives easy control through a ratio 24-1. Fitted with constant velocity coupling, it eliminates strain on the Condenser, providing mechanical and electrical isolation from vibration and noise.

Complete with 3-band glass scale 9in. \times 4 $\frac{1}{2}$ in. Printed short, medium and long wavebands with station names. Scale length 7in. Supplied with florentine bronze escutcheon.

PRICE 27/6.

S.L.5, similar but fitted with reverse vernier drive, gives ratios of 18-1 search and 50-1 reverse vernier.

PRICE 26/6.

Replacement Scales calibrated to Copenhagen Plan now available for:

Airplane Drive	2/3 retail	Full Vision Drive	2/9 retail
Squareplane Drive	2/6 retail	S.L.8 or S.L.5 Drive	4/6 retail

PRECISION COMPONENTS BY



JACKSON

BROS. (LONDON) LIMITED
KINGSWAY · WADDON · SURREY

Telephone: Croydon 2754
Telegrams: Walfitco, Souphone, London



INCREASES YOUR PLEASURE

See the new models at the
RADIO EXHIBITION

STAND
No. 31

a product of

METROPEX LTD

42a DENMARK HILL, LONDON, S.E.5.

Television, Radio and Car Aerials by **AERIALITE**

STAND 47
THE RADIO SHOW

See these **NEW** Products at

AERIALITE have specialised in the design and manufacture of aerials of high performance and quality. For this reason you should visit **STAND 47** and see the comprehensive range of Television, Radio and Auto Aerial Equipment available.

AERIALITE also manufacture Coaxial Plugs and sockets, and Connector and Matching Boxes—for efficient television aerial installation.

A full range of cables including R.F. CABLES are exhibited.

It will pay you to pay us a visit.




MODEL 63A

For optimum results in "fringe" and difficult reception areas.




MODEL 69

A high gain double four element folded dipole. T/V aerial. Forward gain 14 db. Acceptance angle 50°. The ideal aerial for outer fringe reception or multiple receiver installations in local areas. Price £24 complete.

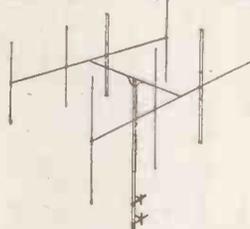


MODEL 74

A full flexible indoor loft-type T/V aerial with excellent signal gain. Suitable for locations up to 15-20 miles. Easy to instal and moderately priced at 13/6.

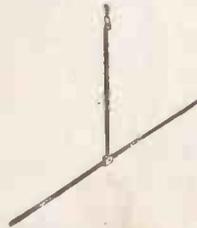


MODEL 17

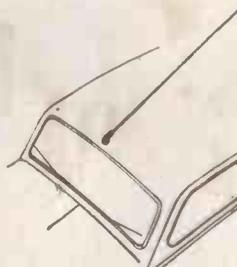
A car aerial for header bar mounting. It has a streamlined appearance and is finished in chromium. The aerial extends to 35 in. and is single hole fixing. Price 32/6d.



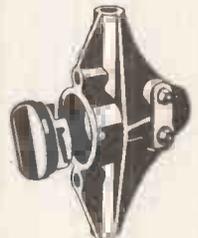
Bayonet Cap Fitting. Makes the Aerialite insulator even better. Quicker fitting and a single operation. To be fitted shortly as standard on the single and "H" aerial arrays.



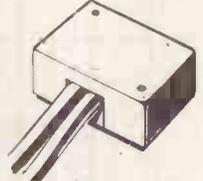Lightning Arrestor—provides effective protection for radio and television installations. Static charges are automatically discharged to earth. Size 1 3/4 x 1 3/8 x 3/4 in. deep. Completely waterproofed for outdoor windowsill mounting.



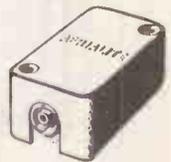
Coaxial Connector Box—(Part No. 153) for skirting board mounting. Finished in mottled brown. Easily fitted. Size 2 in. x 1 1/2 in. x 1 in. deep. Price 6/-.
Matching Box—(Part No. 153A) same size. Designed for multi-point television receiver installations. Price 10/-.




Universal Coaxial Plug (Part No. 155). To R.E.C.M.F. standard and provides a 100 per cent. efficient connection. Simple clamping method for braid and sheath. Price 10 1/2 d.



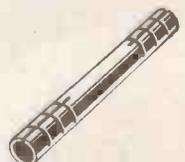Line Connector. (Part No. 154) for joining two coaxial feeders in an efficient and waterproof manner. Does not require soldering. Price 1/-.



IN STOCK

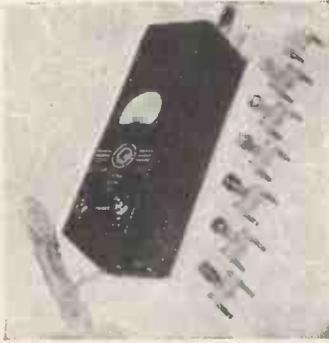

**"Q-MAX" MODEL G.D.O.I.
GRID DIP OSCILLATOR**

This is an extremely useful instrument which may be used for resonant frequency determination, tuning transmitters without application of power and for the determination of coil, mutual and stray inductances, fixed and stray capacitances. Includes built-in mains power pack. The frequency range of 1.5 to 300 Mc/s is covered by means of a series of eight plug-in coils.

9½ GNS (with one coil).
Extra coils 3/6 each.

CONNOISSEUR twin speed motor	£20 19 3
Pick-up with microgroove head	£5 14 8
Standard Head (extra)	£3 11 8
ACOS GP20	£3 11 8

AMPLIFIERS

BARKER Natural Sound Reproducers :	
Model 148a	£15 15 0
Model 150a	£18 18 0
GOODMANS "Audiom 60"	£8 12 6
15in.	£18 10 0
W.B. CONCENTRIC DUPLEX	
10in.	£7 7 0
12in.	£15 15 0
WHARFEDALE	
Super 5/CS/AL including baffle	£4 12 6
Super 8/CS/AL	£4 12 6
Golden 10in.	£4 17 6
W 10CS/B	£8 10 0
Super 12/CS/AL	£14 10 0
Choke Vol. Con.	£1 10 0
Microgroove Equal	£2 15 0
Crossover Unit	£3 9 6

SPEAKER

Williamson Amplifier components, including full range of precision resistors and capacitors.	
Output transformers by:	
VORTEXION (radiometalcore)	£7 7 0
(silcor 1 core)	£4 4 0
PARTRIDGE (unpotted)	£6 4 4
(potted)	£6 12 0
LEAK "Point One" Amplifier	£25 15 0
PC/PA/U Remote Control Pre-amp	£8 15 0
Radio Feeder Unit	£37 4 6
ACOUSTICAL "QUAD" Amplifier with tone control unit	£35 0 0
Radio Feeder Unit	£26 0 0
BERRY'S 10-watt Amplifier	£15 15 0

RECORDING EQUIPMENT

CLIFTON Tape Desk, 7½in. and 12in. p.s., 50-9,000 c.p.s., three motors	£25 0 0
BERRY'S Recording Amplifier. Record/playback. Mic/Radio inputs. Built-in bias/erase oscillator. Circuit and kit of parts	£12 3 0
Completely assembled and wired	£17 3 0
PHIDELITY and CLIFTON Recording Heads. All types from	£2 17 6
WODEN MT10IA Matching Transformers	£1 6 6
B.S.R. Motors	£1 18 0
Oscillator Coils, 45 or 65 kcs	10 0
TAPE . E.M.I. per 1,200 ft. spool	£1 5 0
G.E.C. High coercivity, 1,200ft. spool	£1 10 0
DUREX per 1,200ft. spool	£1 15 0

SEND THREE PENNY STAMPS FOR SPECIAL LIST OF RECORDING EQUIPMENT

BERRY'S
(SHORT WAVE) LTD.
25, HIGH HOLBORN, LONDON, W.C.1
TEL: HOLBORN 6231

REGULATED POWER SUPPLY




MODEL SRS. 151

D.C. OUTPUT : Continuously variable from 20-500 volts at 0-300 milliamperes. RIPPLE VOLTAGE : 8 millivolts maximum. INTERNAL RESISTANCE : 3 ohms. STABILISATION : 0.5% for a ± 10% change in mains voltage. TWO STABILISED NEGATIVE LINES : 0 to -170v variable, -170v fixed. Regulation 1% from no load to full load at maximum output voltage. TWO A.C. OUTPUTS : 6.3 volts at 5 amps, unregulated. Terminals identified for connection in series or parallel.

FREQUENCY RANGE : 25 c/s to 250 kc/s in four overlapping ranges. OUTPUT : 100 milliwatts into 600 ohms. INTERNAL IMPEDANCE : Less than 10 ohms. DISTORTION : Less than 1% from 25 c/s to 200 kc/s. HUM LEVEL : Less than 0.1% of maximum output voltage. STABILITY : Frequency drift ± 2% or 0.2 c/s including initial warming up period. With a mains voltage variation of ± 10% the frequency drift is less than ± 0.2% at 1kc/s. ACCURACY : 1% or 1 c/s. ATTENUATOR : 60 db in steps of 1db.

WIDE RANGE OSCILLATOR

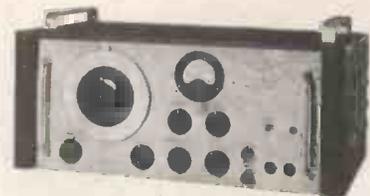

MODEL OS. 101

SOLARTRON LABORATORY INSTRUMENTS LTD
22 HIGH STREET, KINGSTON-ON-THAMES
KINGSTON 1787




QUALITY

ACCURACY

RELIABILITY

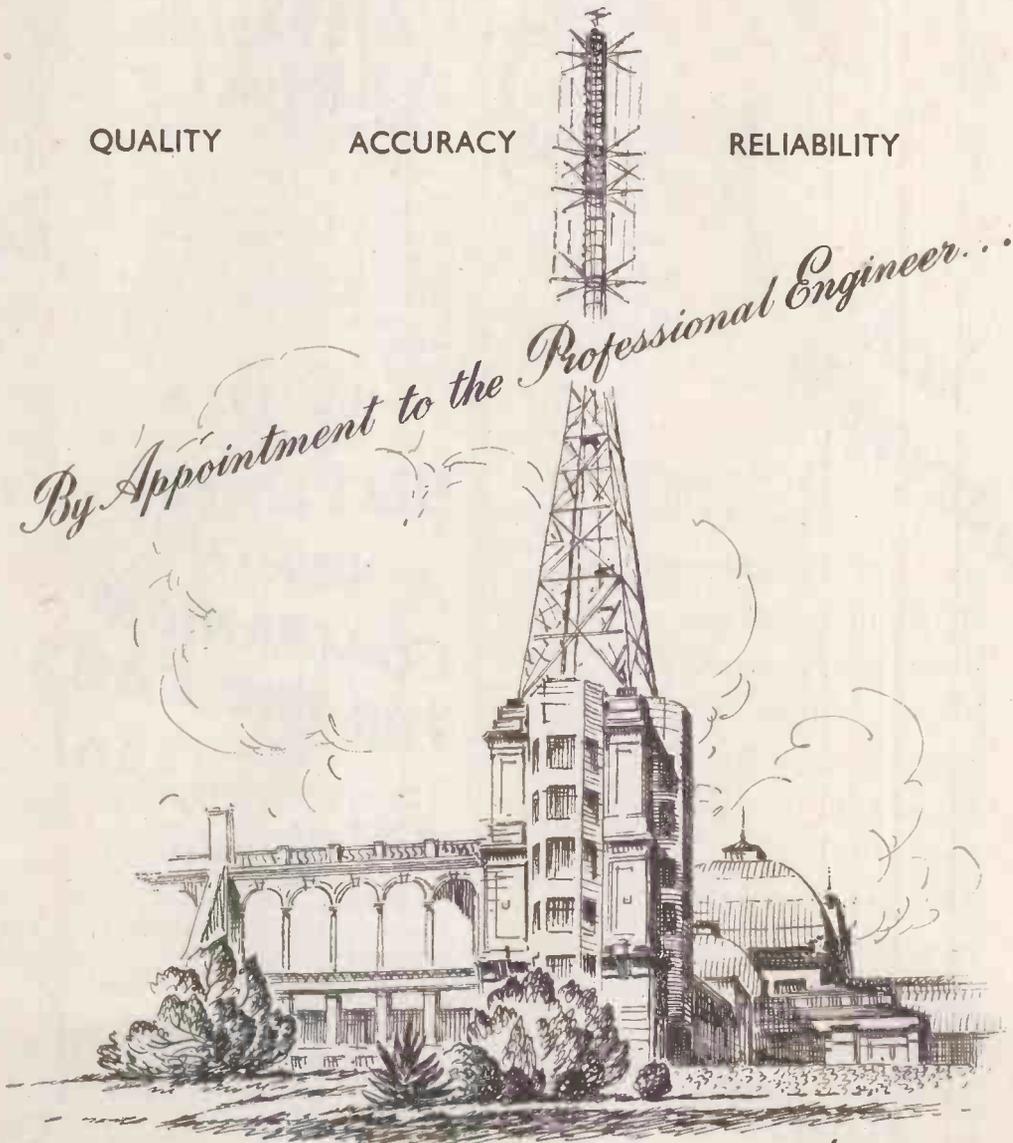By Appointment to the Professional Engineer...



ATTENUATORS • FADERS • SWITCHES • WIREWOUND POTENTIOMETERS • PLUGS
AND SOCKETS • WIREWOUND RESISTORS • HIGH STABILITY CARBON RESISTORS
KNOBS DIALS AND POINTERS • TERMINALS

PAINTON

Northampton England



**knocked out in the back
brought to**


...in any man's mind there's a single tissue of doubt. Suppose, just suppose, that something should fail when something should go right. One problem less, one more worry 'winged', lessens such moments of fear. The confidence of surprisingly many is based on Parmeko's single-minded skill, for they make only Transformers - and, by George, they make 'em well.

PARMEKO of LEICESTER

Makers of Transformers for the Electronic and Electrical Industries

.....it is **STILL THE BEST LONG-DISTANCE AERIAL!**

The FA22 maintains its superiority. Quite apart from its proven high sensitivity, its very sturdiness raises it well above any other TV aerial. Designed by engineers, its scientific construction enables it to withstand the rigours of the most exposed positions. A seamless Steel spreader, adjustable Steel Mast-head Clamp to fit masts from 1½ in. to 3 in. dia. Shock Absorber Reflector Mountings, and the general overall weatherproof method of construction ensures this unrivalled strength and durability.

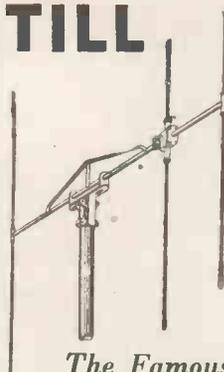


The Famous
FA 22

£5.12.6 Complete ALL CHANNELS
GUARANTEED FOR TWO YEARS

BUT—HERE IS A WORTHY COMPANION FOR THE FA22
The TS 50

STUDY THIS SPECIFICATION
The TS 50 retains the well known TELECRAFT DIPOLE FEEDER BOX ½" diameter Aluminium Alloy Tube COLLECTORS AND REFLECTORS New Type REFLECTOR ASSEMBLY Die-cast MAST-HEAD casting .15 Wave-length SEAMLESS STEEL SPREADER 7ft. SEAMLESS STEEL MAST STEEL LASHING with welded joints 12ft. 7-strand GALVANIZED LASHING-WIRE 3 CORNER-PLATES, "J" Bolts, "U" Bolts, ROPE GRIPS, THIMBLES, Etc.

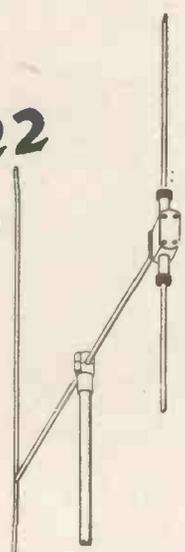

Complete
£4.12.6
ALL CHANNELS

Remember! Because of their fine construction TELECRAFT AERIALS ARE BETTER THAN ANY yet CHEAPER THAN MOST
All Stove Enamelled Throughout

Contact your Wholesaler and insist on



Send for Descriptive Literature

LIMITED
QUADRANT ROAD : THORNTON HEATH SURREY
Tel. : THORNTON Heath 1191-2-3

Depots:—BIRMINGHAM, BRISTOL, MANCHESTER, WORTHING, STOKE-ON-TRENT GLOUCESTER
SCOTTISH ENQUIRIES : LOUIS GRACE, 28, Langside Place, Glasgow, S.1 Langside 4633

proving
its name...



Taylor Tunnicliff
FISH-SPINE BEADS

The flexibility of fish-spine beads extends in dimensional as well as curvilinear aptitude; with a diameter of hole ranging from .056 to .500 there is practically no bare wire insulation problem beyond their capacity.

Each bead is complete in itself, providing for easy and rapid assembly, is accurately made to fine limits, capable of withstanding extremely high temperatures, and will resist severe thermal shock.

They are fine ceramics, finely made to the high standard for which all Taylor Tunnicliff Porcelains are world famous.

Our technical representatives are at your service to give you detailed information. Immediate delivery can be arranged.

• FOR BARE WIRE INSULATION

• *★ No gapping on the sharpest bend*



Taylor Tunnicliff (REFRACTORIES) **Ltd.**

Albion Works · Longton · Stoke on Trent

Telephone: Stoke on Trent 5272/4



From any angle
SRC
will stand the test

Production tests are carried out on each Silver Mica Capacitor and inspection tests are performed regularly on selected batches.

We use modern test equipment of high precision, and standards are frequently checked by official laboratories. A system of visual mica inspection has been evolved from long experience and enables us to select the best dielectric plates to ensure good stability of all capacitors.

STABILITY RADIO COMPONENTS LTD.
 COMMERCE ESTATE, WOODFORD AVENUE, LONDON, E.18.
 Telephone: BUCKhurst 6501/2

SIGNAL GENERATOR TYPE 10. 100 Kc/s-100 Mc/s
Price £7 . 10 . 0

As manufacturers engaged solely in the production of signal generators we confidently claim our New TYPE 10 to be the finest instrument value obtainable. Equally suitable for the testing of radio and television receivers, it is the ideal instrument for the service engineer or home constructor.

● 100 Kc/s to 100 Mc/s ● Modulated or unmodulated carrier ● Direct calibration ● Adjustable 400 c.p.s., AF signal ● Stable RF oscillator Large, easily read scale ● AC mains operation.

Obtainable only direct from the manufacturers. Send for full technical details or call at address below.

HOMELAB INSTRUMENTS
 68a, COBDEN ROAD, LONDON, E.11
 Telephone : LEY 5651

TO HAMS & DEALERS

WE GIVE TOP PRICES FOR THE FOLLOWING
 AMERICAN MADE GOVERNMENT SURPLUS EQUIPMENT
 IN NEW OR GOOD SECOND-HAND CONDITION

- TEST SETS, ALL KINDS
- TRANSMITTING TUBES
 Clystrons, Thyratrons
 Magnetrons, Xtal Diodes
- SIGNAL GENERATORS
- FREQUENCY METERS
- COMMUNICATION RECEIVERS
- All kinds of American made surplus
 Radio Components and Equipment

We are interested in any quantity from one upwards. Drop us a line and we will clinch the deal by return of post or send our representative to see you.

ALTHAM

**ALTHAM RADIO CO BRAZENNOSE ST
 MANCHESTER 2 Tel Deansgate 5387**

In Constant Demand

by **MUSIC LOVERS**
THE WORLD OVER



The **BAKERS 12"**
"TRIPLE CONE"
SPEAKER

Cone type.....	"Triple"
Effective cone dia.....	9in.
Suspension	Cloth
Voice coil dia.	1½ in.
Coil impedance (to order) Standard.....	15 ohms
Flux density	15,000 lines sq. cm.
Frequency range	20/15,000 c.p.s.
Natural resonance	35 c.p.s.
Max. peak input	10 watts

Price £8 : 5 : 0

This amazing Reproducer, known the world over, requires little introduction. The unique diaphragm assembly is comprised of three cones which, used in conjunction with an extremely powerful magnet system, control completely the brilliant upper register down to the lowest note of the organ, with perfect ease. This enables a class of reproduction to be obtained which will delight and thrill the heart of every music lover. If you are not fully conversant with all the ingenious constructional details of this High Grade Reproducer, you should write without delay for Descriptive Leaflets—or better still call for an audition of: "BAKERS" SPEAKERS, RECEIVERS and AMPLIFIERS, the combination of which offers the highest possible QUALITY REPRODUCTION obtainable.



EXPORT ENQUIRIES INVITED

A few Overseas Agencies still open.

Also Available :

12" Single Cone and 18" Duplex Speakers and High Class Amplifiers and Receivers for Home use and Public Address.

BAKERS
'Selhurst'
RADIO

EQUITABLE HOUSE, Dingwall Rd., CROYDON. Telephone : CROYDON 2271/2


Pioneer Manufacturers of Moving Coil Speakers since 1925

ULTRA GEN
No. 1

USING 1.4v VALVES—PROPERLY

The Ultra "Twin" is a portable for use on AC/DC mains, or on batteries. The four valves (plus metal rectifier) are 1.4v miniatures whose filament voltage is obtained from the smoothed HT supply. An important design requirement is that the filament voltage must be maintained substantially constant in the interest of the life

of the valves. This is much easier said than done. This difficulty could arise when the mains input to a normal rectifier circuit is changed from, say, 230v A.C. to 230v D.C. The HT voltage would decrease on the D.C. supply by as much as 25%. This change—added to the normal mains variation that has to be allowed for—is more than could be tolerated. To avoid the necessity for complicated switching to equalise the HT between A.C. and D.C. mains, the Ultra engineers have designed a circuit such that the rectifier efficiency on A.C. mains is adjusted to a value which compensates for the voltage drop which occurs when the set is used on D.C. mains. See resistance R in the diagram. In this way, the HT voltage and filament voltage is maintained substantially constant at the correct value when changing over from A.C. to D.C. mains without the need for switching. This is just one of the outstanding features of the Ultra "Twin" portable that has made it about the most popular receiver for many years past.

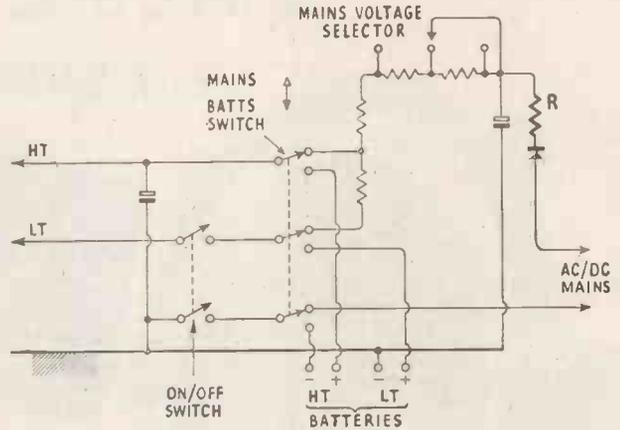

ULTRA ELECTRIC LIMITED
WESTERN AVENUE · ACTON · W.3

SWITCHES

SWITCHES
SWITCHES
SWITCHES!!

WE HAVE THEM!

○ A K—A B—N S F

TELE-RADIO (1943) LTD.

177 EDGWARE ROAD, LONDON, W.2

Phone : PAD 5606
PAD 6116


Shop Hours :
Mon. — Sat. 9 a.m. — 6 p.m.
Thursday 9 a.m. — 1 p.m.

BSR Induction Motors..

FOUR POLE MOTOR FP.10

A precision engineered well balanced motor, designed to give constant, trouble free performance indefinitely. This motor is used extensively in many wire and tape recorders, and gramophone units now manufactured.

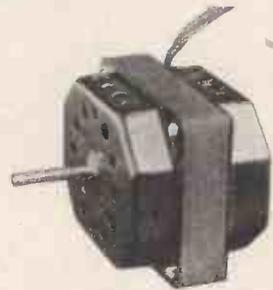Note these features :—Fully protected · Dual voltage range · Negligible external magnetic field · Oil impregnated self aligning bearings · Speed constancy and silent running.



Speed (light) 1400 r.p.m. Torque 3 inch ozs. Weight 1½ lbs.

TWO POLE MOTORS SRI & SR2.

A rugged and highly efficient motor that will stand heavy overloads, and for intermittent ratings is capable of giving up to twice the rated power. Used extensively in many motion displays, fans and gramophones now manufactured. SRI MODEL; Speed (light) 2750 r.p.m. Torque 3.0 inch ozs.—Weight 2.31 lbs. SR2 MODEL; Speed (light) 2750 r.p.m. Torque 2.0 inch ozs.—Weight 1.7 lbs.

.. Leaders in their field

Birmingham Sound Reproducers Ltd., Old Hill, Staffs. Tel. Cradley Heath 6212/3

There's a place for YOU



... in the

part-time

R.A.F

The Royal Air Force urgently needs a trained reserve it can count on in an emergency. And it is men and women like *you* who must form that reserve — people who are ready to give up a small part of their spare time to training: either to continuing to fly or to doing equally important jobs on the ground. Your close association with the Royal Air Force will bring you new experience and fresh companionship. Moreover, by volunteering now, you will be showing the world that you at least are ready to face up to whatever the future holds. Post the coupon below for full details.

TO: ROYAL AIR FORCE (W.D.69), VICTORY HOUSE, LONDON W.C.2


Please send particulars of part-time service with the R.A.F. (*Applicants from British Isles only.*)

NAME.....

ADDRESS.....

(If ex-R.A.F. or W.A.A.F. please give rank, trade and number)

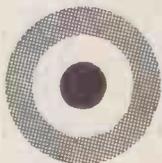★ If you are between 14 and 17 — and keen — join the Air Training Corps ★



37 TV manufacturers rely on the Murphy Pattern Generator

*How can it help with your
TV servicing problems?*

Skilled TV engineers are scarce and therefore expensive. You must use them to maximum advantage. Trainees cannot be expected to compute accurate results from indifferent equipment. Provide them with foolproof test gear.

The Murphy Pattern Generator is the answer. It saves the time of the skilled man and increases his output. It cannot give misleading results and is therefore easily understood by the trainee.

The Murphy Pattern Generator is completely reliable in use for it does not depend on the skill of the operator but gives visual proof which

requires no imagination or judgment. This pattern generator will positively *prove* whether or not a TV receiver will interlace.*

The full scope of this instrument must therefore be appreciated when considering price.

Nearly all TV receiver manufacturers rely on the Murphy Pattern Generator in their service departments and dealer instruction classes. The Murphy Pattern Generator is already saving thousands of pounds in TV servicing in all areas.

If in London for the radio show, visit Stand 106 for a demonstration.

* If a pattern generator does not give the correct frame sync. and $\frac{1}{2}$ line pulses, there is no proof whether a receiver is interlacing or not, and the pattern is unreliable in consequence.

For instance, if you apply a pattern not in accordance with the B.B.C. Standard Sync. Waveforms, a faulty receiver may appear to be working correctly, or vice versa. In these circumstances, only a transmission can prove that a job has been successfully completed, and the whole purpose of a pattern generator is therefore defeated.

The pattern of the Murphy Pattern Generator conforms to B.B.C. Standards and will give accurate results without any further check on transmissions.

F. LIVINGSTON HOGG

Specialists in high-grade instruments for the communications industry,

THE LABORATORY, 71 PRIORY RD. WEST HAMPSTEAD, N.W.6

Telephone: MAIDA VALE 3272



RADIO SHOW, 1951
Stand No. 6

NEW
3rd. Edition Now Ready

TELEVISION CIRCUITS

FOR THE GUIDANCE OF THE CONSTRUCTOR

Contents :-

Circuits cover, video receivers for upper and lower side bands, sound rejectors, video detectors and amplifiers, sync separators, line and frame time bases for normal and wide angle CR. tubes, H.T. boost, E.H.T. supplies by fly-back and R.F. oscillator, power unit, sound receivers, sound amplifier.

Coil construction and coil data charts.

A popular circuit reference book giving practical information. Not an extracted collection of published circuits but an up-to-date series developed and proved by repetitive production and especially applicable to the requirements of the constructor. 64 pages, 8½" x 5½", 2/6 post free.

All components for the making of Television Receivers, including the scanning of wide angle CR. tubes. Ask for list, post free.

HAYNES RADIO Ltd. QUEENSWAY,
ENFIELD, MIDDLESEX

on EXHIBITION at
MODERN ELECTRICS LTD.,

164, Charing Cross Road,
London, W.C.2

'phone TEMple Bar 7587

Immediate delivery from stock

Export enquiries welcomed.

TAPE RECORDERS		SOUNDMIRROR TAPE	
SOUNDMIRROR		E.M.I. Tape	£1 5 0
Table Model	£69 10 0	G.E.C. Grade A Tape	£1 10 0
Portable Model	£79 10 0	Durex MCI-III Tape... ..	£1 15 0
SIMPHONIC		E.M.I. & G.E.C. spools ..	4 0
Complete with Microphone	£60 0 0	Telephone Attachment, for all Tape Recorders	£3 3 0
SCOPHONY-BAIRD		MICROPHONES	
Complete with Microphone	£58 5 6	Acos Crystal	£6 16 6
		Moving Coil	£7 7 0
		'Magnetic Recording' by S. J. Begun, post free	£1 6 0
CONNOISSEUR		TEST GEAR	
2-speed Motors ...	£20. 19 3	Models, HR2, 7, 8 ...	£19 10 0
CONNOISSEUR. Pick-ups		D.C. Minor	£5 5 0
Standard and Micro-groove	£9 6 4	Uniminor	£10 10 0
Standard	£4 11 5	SIGNAL GEN.	
ACOS		Wide Band	£30 0 0
G.P.20 P/U	£3 11 5	Valve Tester	£50 0 0
ACOS		Electronic Test Meter	£40 0 0
LP and Std. Heads ...	£2 3 4	Univ Bridge	£26 0 0
DECCA. Pick-up ...	£3 15 4	TAYLOR	
DECCA. Motors		ALL TAYLOR TEST GEAR IN STOCK. Still available on H.P. Send S.A.E for catalogue and terms.	
33½ and 78 spd.	£3 14 4		
33½-45 & 78 spd.	£7 3 4		

Prompt attention to post orders

High Fidelity at a NEW PRICE LEVEL



THE REMARKABLE NEW FERGUSON '300' RG

Up to now, if you wished to enjoy high fidelity reproduction, you needed to be unusually rich or technically skilful—rich enough to afford one of the few really fine instruments on the market, or skilful enough to build one for yourself. The new Ferguson '300' RG changes all that. It brings really high quality within the reach of thousands of families.

The heart of the equipment is the new a.f. amplifier.

Here are some of its characteristics:

Total Harmonic Distortion ...

0.05% for 3 watts, 0.4% for 5 watts, 1.0% for 6 watts

Frequency Response referred to 1,000 c.p.s. ...

± .5 dB, 30—10,000 c.p.s.

Load Damping Factor ... 30

30 dB of negative feedback is applied overall with ample phase margin for stability. Continuously variable Bass and Treble tone controls are fitted. Specially matched to the amplifier is a new and exclusive 10" P.M. speaker, heavily damped to avoid resonances. And the result is outstandingly good—by any standards. At the price it is, we think, quite unrivalled.

MODEL '300' RG

88 GNS
TAX PAID

Brief Specification

6-valve 3 wave-band superhet. Negative feedback amplifier of 6 watts maximum output. High flux density 10" P.M. speaker. Interchangeable microcell crystal pick-up heads, with sapphire styli. Garrard 3-speed auto-changer for all types of records including L.P. Two-tone walnut cabinet with built-in record storage space.

Fine sets these FERGUSON'S

TOWARDS PERFECTION

LOWTHER'S cordially invite you to their showrooms (which are easily accessible by bus or train to Bromley South) for a demonstration of the most up-to-date range of sound and vision equipment.



**THE LOWTHER MANUFACTURING COMPANY,
Lowther House, St. Mark's Rd., Bromley, Kent**

Telephone : RAVensbourne 5225



HOME STUDY

**backs radio experience with
sound technical knowledge**

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following:

Complete Radio Engineering . Radio Service Engineers . Radio Service and Sales . Advanced Short-Wave Radio . Elementary Electronics, Radar and Radio Television Technology.

And the following R.D.'s Examinations

British Institution of Radio Engineers . P.M.G. Certificates for Wireless Operators . City and Guilds Telecommunications . Wireless Operators and Wireless Mechanics, R.A.F.

Students intending to sit for the above 1952 Examinations should enrol NOW for Courses in preparation.

Using a specially prepared study programme students will complete their Course, with time for revision, before the examination date, when they will sit with full confidence of success.


(I.C.S. Students are coached until successful)

Write today for our FREE "RADIO" booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need for and the means of instruction.

**GENEROUS DISCOUNT GRANTED TO ALL MEMBERS OF
H.M. FORCES.**

International
CORRESPONDENCE SCHOOLS

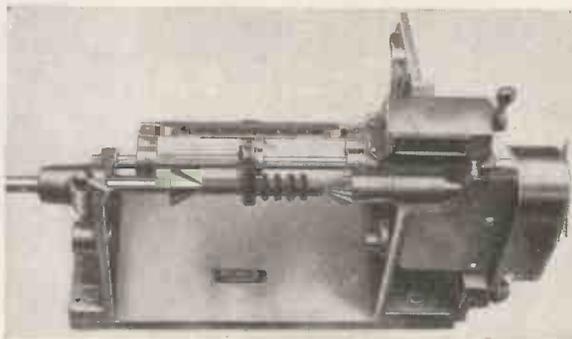Dept. W.L.26., International Buildings, Kingsway, London, W.C.2.



MODEL WX

AUTOMATIC COIL WINDING MACHINES AND HAND WINDING MACHINES

Wave winding machines for single or multiple coils of 1/16" to 3/4" wide for power drive.

SOLE AGENTS ABROAD


K. G. Khosla & Co., 22 School Lane, New Delhi, India.
Etablts Octave Houart, 14 Quai de l'Industrie, Sclessin-lez-Liege.
Hefty & Frogg, Oslo, Norway, Storgaten, 15.
R. H. Cunningham P.T.Y. Ltd., 62 Stanhope Street, Malvern, Victoria, Australia.

ETA TOOL CO

(LEICESTER) LTD.

29 a, WELFORD ROAD, LEICESTER

*Phone—5386

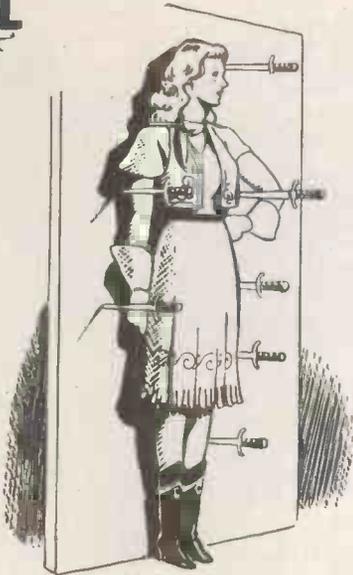

WHEN ACCURACY COUNTS

There are many times when a frequency source is required, the accuracy of which can be relied upon.

THE 'CINTEL' R.C. OSCILLATOR AND FREQUENCY MONITOR

provides any frequency in the range 10c/s to 100Kc/s with an accuracy of $\pm 0.005\% \pm 0.1c/s$ and indicates the exact value by means of an electronic monitor. This monitor samples the frequency every 5 seconds, measures it against a crystal and indicates the result on five panel meters each scaled 0 — 9. This operation continues automatically and thus the exact output frequency is always known. *Full technical details are available in publication No. RC1/1.*



CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

FOREMOST IN THE MANUFACTURE OF

• Counters & Chronometers • Metal Detectors • Oscilloscopes • Photo-Electric Cells • Cathode Ray Tubes • Geiger-Müller Tubes • Electronic Instruments

WORSLEY BRIDGE ROAD · LONDON · S·E·26

Telephone: H1Ther Green 4600

F. C. Robinson & Partners Ltd.,
287 Deansgate, Manchester, 3.

SALES AND SERVICING AGENTS:
Atkins, Robertson & Whiteford Ltd.,
100 Torrissdale Street, Glasgow, S.2.

H. Hawnt & Co. Ltd.,
59 Moor St., Birmingham, 4



REGISTERED TRADE MARK

YOU CAN MAGNETICALLY RECORD using your Gramophone Motor as a Drive




Necessary parts, also usable later for a more ambitious job, plans available, 1 Spool Diamond Magnetic Recording Tape and 1 take-up spool, 2 Corner Brackets, 1 Roller, 1 Record-playback Head Kit, 1 Friction Clutch, 1 Dual-purpose Supersonic Oscillator and Two-stage Preamplifier and your Radio Chassis. Set of parts £7.15.0 or items supplied separately.

Also Constructional Data for Wire and Tape Recorders 5s.

PARK RADIO OF MANOR PARK, 676/8, 783 Romford Road, London, E.12

ALL the A.C. power you require
from your D.C. supply

with a

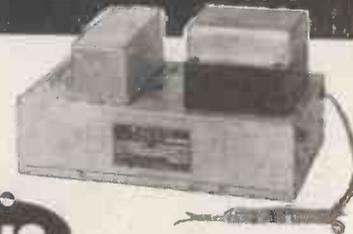

D.C./A.C. CONVERTER

Models for Electric Gramophones from £8, plus 10%

- Models for
- Radio-grams and Autochange Radio-grams (inc. 3-speed motors)
 - Radios
 - Televisions, etc.,
- from £10.15.0, plus 10%

**STAND 21
NATIONAL
RADIO SHOW**

Input, 6, 12, 24, 32, 50, 110 or 200/250V. D.C.
Output 230V. 50 or 60 c/s.



Descriptive literature W.W.7 from the manufacturers:-
NEW CHAPEL ROAD, HIGH STREET,
FELTHAM, MIDDXX.

Telephone: FELtham 4242

Overseas Enquiries to nearest E.M.I. Organisation Depot.

**1,000,000
EARN £18
PER WEEK**

WHY NOT YOU?

The demand for qualified technicians to fill well-paid industrial posts grows daily. Through the unique facilities offered by E.M.I. Institutes, you can train for a worthwhile job by means of our Home Study Courses. As part of the great E.M.I. Group (H.M.V., Marconiphone, etc.), we have first hand knowledge of the technical training required in modern industry. No other college can offer you such a practical background of industrial experience.

POST THIS COUPON NOW

E.M.I. INSTITUTES, Postal Division, Dept. 16,
43, GROVE PARK ROAD, CHISWICK, LONDON, W.4.

Please send, without obligation, your FREE BROCHURE. (I have marked the subjects which interest me.)

Mech. Eng. Elect. Eng. Draughtsmanship Radio
 Television Production Eng. Auto. Eng. Aero. Eng.
 Civil Service General Cert. of Education (Matric).
 Also Courses for A.M.I.Mech.E., A.M.I.C.E., A.M.Brit.I.R.E.,
 A.F.R.Ae.S., CITY and GUILDS EXAMS IN Mech. Eng.,
 Elect. Eng., Telecommunications, etc.

Other Subjects

NAME

ADDRESS



E.M.I. INSTITUTES — The College backed by an Industry

16 inch METAL C.R. TUBE

T. 901

British made by

'ENGLISH ELECTRIC'

FOR MANUFACTURERS AND CONSTRUCTORS

Introduced into this country by 'ENGLISH ELECTRIC', the Metal Cathode Ray Tube is one of the most significant television developments for many years.

It offers the following outstanding advantages:—

- ★ Magnetic focus and magnetic deflection
- ★ Short overall length 17 $\frac{1}{8}$ inches—suitable for shallow cabinets
- ★ Brilliant picture of uniform focus on an almost flat screen
- ★ Robust yet lightweight construction
- ★ An ion trap fitted to prevent ion burn discolouration and prolong tube life

PRICE **£24.6.5** TAX PAID




For full technical details and price for quantities write to

The ENGLISH ELECTRIC Company Limited

TELEVISION DEPARTMENT, QUEENS HOUSE, KINGSWAY, LONDON, W.C.2

**Three heads
are better
than one!**

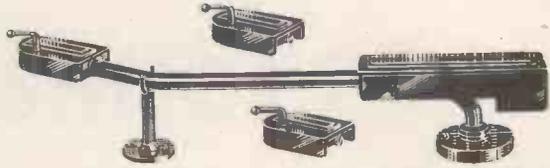

For Standard and Microgroove Recordings

- Green Spot with .001" radius sapphire for microgroove recordings.
- Red Spot with .0025" radius sapphire for modern standard recordings.
- Yellow Spot with .003" radius sapphire for older standard recordings.

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Armature mass 20 mg.

Extremely low mass at needle point (4/5 mg. only), allowing for reduction in downward pressure to 10/12 grams for standard recordings, and 5/7 grams for microgroove recordings.

Prices: With one head £4 10 0 plus £1 19 0 Purchase Tax. Extra heads each £2 10 0 plus £1 1 8 Purchase Tax. Spare armature system with sapphire 14/8 including tax.

Licensed under Letters Patent No. 586900 and/or 615424.

a **Connoisseur** *product*

Tel. : HALIFAX 69169. See STAND No. 12, Radio Show, Earls Court, August 29 to Sept. 8
Manufactured by A. R. SUGDEN & CO. (ENGINEERS) LTD., Well Green Lane, Brighouse, Yorks.

“WEYRAD”

Bandspread coil units for mixer input—Simplified construction with superlative performance.

In spite of the absence of an R.F. stage the sensitivity and image rejection characteristics of these units are very good. By their use the construction and alignment of bandspread receivers is simplified and the overall cost substantially reduced.

Standard types are available for early delivery.

TYPE B.S.4.—9 ranges.

13, 16, 19, 25, 31 and 41 metres bandspread.
15.7-43, 43-140 and 175-570 metres general coverages

TYPE B.S.6.—9 ranges.

13, 16, 19, 25, 31 and 41 metres bandspread.
43-140, 175-570 and 800-2,000 metres general coverage.

The special 2-section 2 gang tuning condenser supplied as an additional item together with a punched coverplate and octal valveholder.

Prices : Coil Unit 94/6 plus 40/10 P.T.
Coverplate, etc. 24/-
Tuning Scale 18/9

THE
**WEYMOUTH RADIO MANUFACTURING
CO., LTD.,**
CRESCENT WORKS, WEYMOUTH, DORSET

AMBASSADOR
OF GREAT BRITAIN

television

Clearly Unsurpassed




Your Ambassador dealer will be proud to show you a truly unique television receiver. Nowhere will you find anything to compare either in picture quality, cabinet style or price.

Ask to see the Ambassador T.V.5, 15" tube, 13½" x 10½" picture. Price £136. Literature on request.

Ambassador Radio, Princess Works, Brighouse, Yorks

SIGNAL GENERATORS • BRIDGES • VALVE VOLTMETERS • Q-METERS • OUTPUT METERS
 WAVEMETERS • FM • AM • TV • RADAR • TELECOMMUNICATIONS
 TELECOMMUNICATIONS • VALVE VOLTMETERS
 SIGNAL GENERATORS
 WAVEMETERS • FM
 TELECOMMUNICATIONS • VALVE VOLTMETERS
 SIGNAL GENERATORS
 WAVEMETERS • FM
 TELECOMMUNICATIONS
 SIGNAL GENERATORS
 WAVEMETERS • FM
 TELECOMMUNICATIONS
 SIGNAL GENERATORS
 WAVEMETERS • FM • AM
 TELECOMMUNICATIONS
 SIGNAL GENERATORS
 WAVEMETERS • FM • AM
 TELECOMMUNICATIONS
 WAVEMETERS • FM • AM • TV • TELECOMMUNICATIONS

REFER TO MARCONI . . .

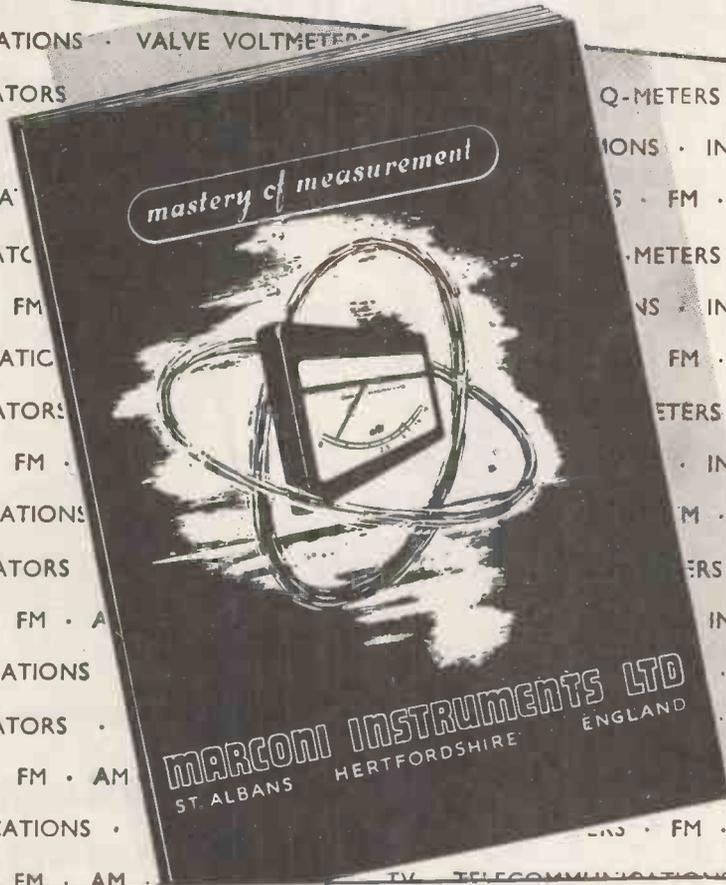

MASTERY OF MEASUREMENT

Marconi mastery of measurement is turned to account in a wide range of radio communication and allied measuring instruments. Embodying the skill born of years of experience, they nevertheless employ the latest techniques in circuits and contemporary styling. If you are professionally engaged in the radio communications field, write now for your copy of this 70 page, fully illustrated catalogue and find how the 30 preferred instruments can help you.

MARCONI instruments

MARCONI INSTRUMENTS LTD • ST ALBANS • HERTS • Phone: ST ALBANS 6161/7

London Office: Marconi House, Strand, W.C.2. Midland Office: 19 The Parade, Leamington Spa. Northern Office: 30 Albion Street, Hull.

ALL You Want for

QUALITY RECORDING!

The LANE PRECISION BUILT TAPE TABLE

- Heavy balanced flywheel gives extreme freedom from "wow" and "flutter."
- High fidelity Record/Play Back and Erase Heads in mumetal shields to ensure wide range response with correct amplifiers.
- Fast Re-wind.
- Very simple mechanical action—nothing to go wrong.
- Dimensions—11½ in. x 15½ in. x 7 in.
- 200 v.-250 v. A.C. only.

PRICE

£16.10.0

CARRIAGE AND PACKING 10/-

SOLE DISTRIBUTORS THROUGHOUT THE WORLD

VERDIK SALES LTD. 17 SHAFTESBURY AVE.

LONDON, W.I. Phone Gerrard 8266

The following components can be supplied separately:

COMPONENTS	
HIGH FIDELITY HEADS (complete with mumetal shield)	
VO Record/Play Back	£2 10 0
VR Super Record	£2 15 0
VF Super Play Back	£2 15 0
VE Erase	£2 2 0
OSCILLATOR UNIT Constructed on small chassis. Provides r.f. for Erase and Bias. Each unit checked for wave-form:	
Complete with valve	£3 10 0
TAPE New high coercive tape for high adlety recording at low speeds.	
DUREX 1,200 ft. reel	£1 15 0

Send for comprehensive lists.
Trade enquiries invited.



T.V.

FREQUENCY CONVERTER

Model HM2. 2-valve model, self-contained power unit, enables immediate change-over SUTTON COLDFIELD tuned receivers to HOLME MOSS reception, without ANY alteration to chassis, etc. Price £8.0.0.

T.V.

PRE-AMPLIFIERS

One-valve model, self-contained power unit, £5.17.6. TWO-valve model, self-contained power unit, for EXTREME fringe areas, £7.10.0. Extremely efficient. Many thousands in use.

Your dealer will be pleased to demonstrate.

Illustrated leaflets giving technical specification, etc., forwarded with pleasure, write: Manufacturers

**RAINBOW RADIO
MANUFACTURING CO. LTD.**
Mincing Lane, Blackburn, Lancashire

Drayton MOTOR UNITS

for

The Drayton R.Q. is a miniature capacitor induction type motor with a current consumption at 230 volts 50 cycles of 0.09 amps pf. 0.9. It is available:


R.Q.G. GEARLESS for running at 2700 r.p.m. continuously or intermittently in either direction or continuously reversed.

R.Q.R. GEARED for continuous running or reversing at speeds from 27 mins. per rev. to 600 revs. per min.

R.Q.H. GEARED for high final shaft speeds for continuous running, forward or reverse.

Send for List No. N.302-1

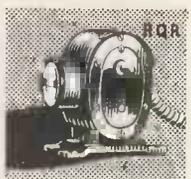actuating valves, dampers, rheostats, geneva movements, rocking baths, flashing signs, illuminated models, soldering and welding fixtures, rotating tables, automatic light strip feed, lubricating and other small pumps, small machines, animated displays, vibrators, developing baths, agitators, fans, aspirators and similar devices.



Drayton Regulator & Instrument Co. Ltd., West Drayton, Mdx. W. Drayton 2611

THE RECTIFIERS

for your particular
RADIO & TELEVISION APPLICATIONS

will be found at

STAND N° 43

at the **RADIO SHOW - EARLS COURT**

August 29th to September 8th

We cordially invite you to visit us at the above so that you can see for yourselves our newest rectifier developments. The type 36EHT rectifiers incorporating elements that withstand an extremely high peak inverse voltage are particularly suitable for E.H.T. supplies to television receivers and other electronic devices where current demands do not exceed 2 mA. D.C. Where a few extra milliamperes are required, we can offer the type 16HT double-voltage rectifier. New H.T. rectifiers constructed

with double-voltage elements will show a great reduction in size for any given output, and many well-known commercial television sets incorporate them. There, in their attractive new hammer grey finish, will be the "Westalite" battery chargers, with outputs that range from 72 to 2,400 watts.

And, of course, a copy of "THE ALL METAL WAY" will be available to all. A handy publication with much useful information on . . .

 **WESTINGHOUSE** 

RECTIFIERS

WESTINGHOUSE BRAKE & SIGNAL CO. LTD.

82, York Way, King's Cross, London, N.1.

Relevant Facts

on B.50 Series Microphones

The VITAVOX B.50 Series is most comprehensive and includes instruments to meet almost every requirement for a hand microphone. The series comprises Type B.50, incorporating a high-grade moving coil element; Type B.51 with crystal insert; and Type B.52, similar to Type B.50 but with a transformer for direct connection to amplifier or medium impedance line. The diagram indicates the wide range of switch circuits available with Types B.50 and B.51, and the different transformer ratios available with Type B.52 which has no switch. Additional versions can be supplied for special purposes when required in quantity.

NOTE: ALL DIAGRAMS SHOW THE SWITCH IN THE NORMAL POSITION i.e. BEFORE THE KNOB IS PRESSED.

					TYPE B50 [LOW IMPEDANCE DYNAMIC]	
CATALOGUE NUMBER CN 170 COLOUR CODE SILVER	CATALOGUE NUMBER CN 171 COLOUR CODE RED	CATALOGUE NUMBER CN 172 COLOUR CODE BLUE	CATALOGUE NUMBER CN 173 COLOUR CODE GREEN	CATALOGUE NUMBER CN 174 COLOUR CODE YELLOW		
NO SWITCH	MICROPHONE NORMALLY OPEN - CIRCUITED	MICROPHONE NORMALLY SHORT - CIRCUITED	MICROPHONE AND RELAY CONTACTS NORMALLY OPEN - CIRCUITED	MICROPHONE NORMALLY SHORT - CIRCUITED, RELAY CONTACTS NORMALLY OPEN - CIRCUITED		
						TYPE B51 [MEDIUM IMPEDANCE]
CATALOGUE NUMBER CN 175 COLOUR CODE SILVER	CATALOGUE NUMBER CN 176 COLOUR CODE RED	CATALOGUE NUMBER CN 177 COLOUR CODE BLUE	CATALOGUE NUMBER CN 178 COLOUR CODE GREEN	CATALOGUE NUMBER CN 179 COLOUR CODE YELLOW		
NO SWITCH	MICROPHONE NORMALLY OPEN - CIRCUITED	MICROPHONE NORMALLY SHORT - CIRCUITED	MICROPHONE AND RELAY CONTACTS NORMALLY OPEN - CIRCUITED	MICROPHONE NORMALLY SHORT - CIRCUITED, RELAY CONTACTS NORMALLY OPEN - CIRCUITED		
CATALOGUE NUMBER CN 180 COLOUR CODE SILVER	CATALOGUE NUMBER CN 181 COLOUR CODE RED	CATALOGUE NUMBER CN 182 COLOUR CODE BLUE				
IMPEDANCE 500 / 800 OHMS NO SWITCH	IMPEDANCE 10,000 OHMS NO SWITCH	IMPEDANCE 100,000 OHMS NO SWITCH				
TYPE B52 [HIGH IMPEDANCE DYNAMIC]						
IMPEDANCE 100,000 OHMS NO SWITCH						


VITAVOX LIMITED
Westmoreland Road, London, N.W.9.
Tel.: COLindale 8671.
Grams: Vitavox, Hyde, London,
Cables: Vitavox, London, England.

VITAVOX *Microphones*

5586

**Widney -
DORLEC**
CABINET SYSTEM

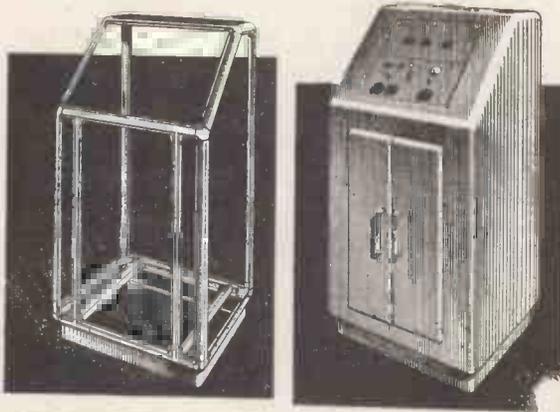Several of the scientific instruments displayed in the Festival of Britain exhibition are housed in Widney-Dorlec cabinets. If you do not already know about this unique cabinet system, write for details.



Technical Adviser: C. H. DAVIS
59 BROMPTON ROAD
LONDON, S.W.3



HALLAM, SLEIGH & CHESTON LTD
WIDNEY WORKS - BIRMINGHAM - 4

Phone: Aston Cross 0918, (4 Lines) - Grams: Superfine, Birmingham, 6.



To avoid radio ailments

EVERY GOOD RADIO DOCTOR PRESCRIBES OSMOR "Q" COILPACKS

As specified for conversion of the Type 25 unit of the TR.1196, Type 18 and Wartime Utility receivers, and others.



These mighty midget coilpacks will cure your radio troubles and ensure better performance in every way. Easy to assemble, with only five simple connections, the pre-aligned "Q" Coilpack saves hours of frustrated grappling with complicated circuits. All types available for mains and battery sets, complete with full instructions and circuit diagrams.

Send 5d. (stamps) for free circuits and new illustrated lists of Coils, Coilpacks, and all Radio Components.

OSMOR RADIO PRODUCTS LTD. (Dept. W.22)
BRIDGE VIEW WORKS, BOROUGHHILL, CROYDON, SURREY

Telephone: Croydon 1220

We've no
YES-MEN
at Keighley



...they're all
**KNOW-
MEN**

IT isn't always easy to resist the suggestion that price is the final consideration when selling in a competitive market. That is why we employ a team of knowledgeable, strong-willed "know-men" specially briefed to reject any compromise with quality.

We at Keighley are not satisfied by the knowledge that each switch we turn out will function correctly when it leaves our hands — we must also know that it will continue to do so throughout the life of the appliance it is designed to control.

Only then can our "know-men" feel satisfied that their job is well done. And—secure in the knowledge that fundamental simplicity of design, meticulous inspection at each production stage and rugged construction have provided a more than adequate margin of electrical and mechanical safety—they can then turn their attention to the unravelling of the next knotty problem.

And how much extra does the discriminating appliance manufacturer pay for this higher standard of quality? In a word — nothing. For the price he pays for his Cutler-Hammer Switches is immediately reflected in longer trouble-free service, reduced maintenance costs and enhanced goodwill for his product.



N.S.F. LIMITED
KEIGHLEY · YORKS

Phone: Keighley 4221/5 Grams: ENESEF, Keighley

LONDON OFFICE: 9 Stratford Place, W.1. Phone: Mayfair 4234

Licenses of Igranic Electric Co. Ltd. for the above products of Cutler-Hammer Inc. Milwaukee, U.S.A.

**"THE
SWITCH
PEOPLE"**



● Other N.S.F. Products include: 'OAK' Rotary, Push-button and Slider switches; Carbon and wire-wound potentiometers for Television and Radio applications.

'CLIFTON' Tape Recorders

Model M.Q.I. £52.10.0
(H.P. Deposit £13.2.6)

'CLIFTON' Playing Desks

With one reel Emitape £25
(H.P. Deposit £8.6.8)

Experientia docet!

Clifton products are backed by many years' research.

Hear the new models—Tape Speeds, 3½, 7½, 12, I.P.S.
High Fidelity Reproduction.

LONDON AGENTS: Will Day Ltd., 19 Lisle St., W.C.2
H. L. Smith & Co. Ltd., 287 Edgware Rd. W.2
EXPORT: Panrek, Suite 9, 140 Park Lane, W.1



Manufactured & Distributed by:—

BRISTOL CINE SERVICE

33, ALMA VALE ROAD, BRISTOL, 8. Tel: 33243



ONLY
25/6
POST FREE



**A
workshop
in your
pocket!**

THE TELEVISION AND
RADIO SERVICE ENGINEER'S
MASTER TRIMMER KIT

Contains:

- 1 End Trimmer.
- 1 Side Trimmer.
- 1 Yaxley Switch Contact Adjuster.
- 1 Low Capacity Trimmer.

- 1 Screwdriver.
- 1 Set of Feeler Gauges.
- 1 Set of six Box Spanners from 1 to 8 B.A.
- 1 Set of four Spanners from 0 to 8 B.A.

in durable black crackle finish metal case.

Export enquiries invited

SEND YOUR ORDER TO:

J. & S. NEWMAN LTD.

Meet us at
the Radio Show
—STAND 29
100 HAMPTSTEAD RD., N.W.1
Tel.: EUSton 5176/7

M.R. SUPPLIES Ltd

Offer from stock the following brand new (or otherwise perfect) material. Brief descriptions—fuller details if required, on request. All prices nett.

- IMMERSION THERMOMETERS.** Two models, 0/120 deg. C. and 40/140 deg. C., with Resistance Tube for 2½in. insertion and 2in. scaled meter (luminous), potential required 24 v. Tube and meter (please state which), 10/6 (des. 9d.).
- A.C. VOLT METERS,** rectifier m/coil, even scale, 2½in., 0/71 volts, 50/500 c/s, 12/6 (Des. 6d.).
- VACUO THERMOCOUPLES (S.T.C.)** 5mA (10 mA max.). Unmounted, with four leads. Vacuum tube 2in. x 1in., new, boxed, 3/6.
- JEWEL TIPPED PERMANENT GRAM-NEEDLES,** 2/6. Please state whether standard or miniature shank required.
- HIGH DUTY SELENIUM RECTIFIERS,** large range, new, under half nett price, from stock. Examples: 12 v. 50 amps, 34/- (des. 2/6), 60 v. 10 amps, 77/6 (des. 2/6), 30 v. 50 amps, pair £71/0/0 (des. 3/6), 240 v. 10 amps, 214 (des. 5/6). Please enquire for other ratings.
- EVERSHED BRIDGE MEGGERS (250 v.).** Ex-Govt. expertly overhauled. 0/50 megohms. Bridge 0.01/1 megohm, with carrying case, £17 (despatch 4/6).
- EVERSHED OHM-METERS.** Ex-Govt., expertly overhauled. Two scales, 0/1,000 and 0/200,000 ohms, with leads, probes and case (less flash battery), £5/10/0 (des. 1/6)
- SIMPSON OHM-METERS,** 0/1,000 ohms with internal 100/1 multiplier or 0/200,000 ohms. Uses ordinary U2 cell. 57/6 (des. 1/-).
- FLUXMETERS (Admiralty model WY p.n.23).** 500/4,000 Gauss in three scales, with probe, etc., in portable case, £5/10/0 (des. 2/6).
- VOLTAGE CHANGING TRANSFORMERS (portable).** 200/250 v.-110 v. (and vice versa) with selector switch and voltmeter, loading 1.25 kVA. £5/17/6 (des. 6/6).
- STEP-DOWN TRANSFORMERS (multi-purpose).** Prim. tapped 200-220-240 v. Sec. provides: 2, 3, 5, 7, 8, 9, 10, 15, 16, 17, 18, 20, 25, 27 and 30 v. 2 amps. Our usual reliable vacuum impregnated (fitted 2,000 v.) model, in great demand for important uses 29/6 (des. 1/6).
- P.V.C. STRIPPER PLIERS (S.T.C.).** Heated jaws remove all plastic insulation, from cables, cleanly and rapidly, with 200/250 v. transformer, 59/6 (des. 1/6).
- STUART CENTRIFUGAL PUMPS.** No. 21, fitted 220-250 v. 1 h.p. capacitor/induction motor (1,000 r.p.m.). 220 (des. 5/6).
- ROTARY VANE PUMPS.** Ex-Admiralty, all bronze, power required 1 h.p. (min.), 3,000 g.p.h. positive displacement, 26/15/0 (des. 4/6). **IMMERSION PUMPS,** self-priming (as R.A.F. German version). Can be immersed up to 30in. Approx 300 g.p.h. Rated for 24 volts D.C., suitable for 22 v. D.C. or short periods 15/24 v. A.C., 37/6 (des. 2/6).
- SHADED POLE INDUCTION MOTORS.** Hoover model SP201, 200-250 v. A.C., 950 r.p.m., silent, body 2½in. x 3½in., with ½in. shaft prof. 1in., 25/- (des. 1/-).
- EXTRACTOR FANS (Hoover).** 6½in. overall, inlet 1½in., outlet 2in., 24 volts A.C./D.C. suitable for under-deck, ceiling or wall mount, 17/6 (des. 1/6); also DELCO model, with 12in. impeller (14in. over ring). Fitted 200-250 v. induction motor, 25/17/6 (carr. paid). Also ex-Govt. (new, but soiled) fitted Brooks 1/6th h.p. cap./induction motor, 200-250 v. A.C., fitted 12in. impeller, dia. 17in. to four mounting centres. Reversible, 28/10/0 (des. 7/6).
- BANKS OF RELAYS.** All 150 ohms. (1) 1 bk. and 1 c.o., (2) 2 bk. and 1 c.o., (3) 1 bk. The three relays in metal housing approx. 4in. x 4in. x 2in., 9/6 (des. 9d.).
- KNIFE SWITCHES (G.E.C.).** 2-pole c.o., Q.M. & B., 30 amps., on paxolin base 8in. x 6in., 8/6 (des. 1/-).
- OVERLOAD AND SHORT CIRCUIT TRIPS.** In iron clad housing, 7in. x 4in. x 2½in. 200-250 v. A.C. 5-8 amps, 16/6; 15 amps, 19/6 (des. either 1/6).
- IMMERSION THERMOSTATS (Sunvic).** 90-190 deg. F., 15 amps., 200-250 v. A.C. Tube 10in. long, 25/6 (des. 1/-).

All goods for immediate delivery.

M.R. SUPPLIES Ltd., 68 New Oxford Street, London, W.C.1
Telephone: MUScum 2958

G.E.C.

QUARTZ CRYSTAL ACTIVITY TEST SET

UNSURPASSED AS A SIMPLE & ACCURATE INSTRUMENT FOR THE MEASUREMENT OF CRYSTAL PERFORMANCE



The G.E.C. Quartz Crystal Activity Test Set measures the equivalent parallel resistance of a quartz crystal when oscillating in a circuit having an input capacity of either 20 pF, 30 pF or 50 pF, the alternative capacities being selected by a switch.

The dial is calibrated and has a range of 4 kilohms to 130 kilohms and is direct reading. No calculation is necessary. Measurements can be made at any convenient amplitude of oscillation up to 10V. R.M.S. at the crystal terminals for crystals of normal activity.

The accuracy of the loss dial calibration is $\pm 2\%$.

WRITE FOR DESCRIPTIVE LEAFLET—

SALFORD ELECTRICAL INSTRUMENTS LTD.

PEEL WORKS : SILK STREET : SALFORD : LANCS.

Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND



THE LATEST MAGNETIC

Goldring Turnover Pick-up No. 165

FOR STANDARD AND LONG PLAYING RECORDS.

● **OTHER GOLDRING PRODUCTS**

THE THREE-WAY PICK-UP. No. 150. For standard and long playing records.

"THE HEADMASTER" interchangeable head pick-up, for every type of record.

THE BANTAM PICK-UP. The most popular replacement pick-up.

THE SUPER AUTO PICK-UP. For standard records, with built in Auto Stop.

Replacement Cartridges and Pick-Up Heads.
Sapphire Jewel Point Needles • Gramophone Needles
Radiogram and Gramophone Accessories.

Visit our stand No. 35. ALL PICK-UPS WILL BE DEMONSTRATED IN OUR DEMONSTRATION ROOM No. 206

ERWIN SCHARF

49-51a, DE BEAUVOIR ROAD,
LONDON, N.1.

TELEPHONE CLISSOLD 3434/6



THE SUPERFIDELITY
VARIABLE RELUCTANCE
"DUO STYLUS" CARTRIDGE
No. 200

For standard and long playing records.
The 2-speed record matching unit.



B.P.L. TEST SETS

NOW AVAILABLE

AT NET PRICES

B.P.L. UNIVERSAL TEST SET
£5 - 18 - 6

B.P.L. SUPER RANGER 1,000 Ω/v .
£13 - 10 - 0

B.P.L. SUPER RANGER 20,000 Ω/v .
£15 - 10 - 0

Prices include postage and packing
and are applicable to Home Market
only.

Send your order direct to:

BRITISH PHYSICAL LABORATORIES
HOUSEBOAT WORKS, RADLETT, HERTS

Tel.: Radlett 5674-5-6



RADIO TRANSMISSION

OF INTERNATIONAL 12 CHANNEL CARRIER GROUPS

Where telephone lines cannot be built or are too costly, this V.H.F. FM radio system will give C.C.I.F. transmission standards for 12 channel telephone groups over a single link up to 40-50 miles long. Radio relay stations are

available to extend links up to several hundred miles. Each main unit comprises a number of sub-units which are quickly replaced by spare sub-units when faults occur. The frequency ranges are from 40-90 Mc/s or 150-200 Mc/s.

AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

(Radio and Transmission Division)

STROWGER HOUSE · ARUNDEL STREET · LONDON · W.C.2
 Telephone: TEMple Bar 9262

Cablegrams: Strougerex, London




AT4161/B107

MYCALEX

(REGD. TRADE MARK)

THE INSULATOR


- Watertight assembly.
- Long leakage path.
- Element rods reinforced by the inserted metal tubes, at a point where fracture is liable to occur.
- Mycalex has high surface resistivity to moisture under damp conditions.
- Great physical strength due to nature of Mycalex which is a bond of Mica and Glass.
- Electrical connections easily accessible by means of removing the tough rubber end cap illustrated.

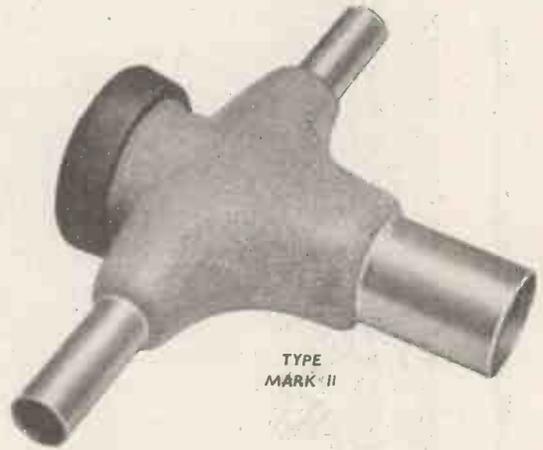

*Phone: CIRENCESTER 400 or send enquiries to

MYCALEX COMPANY LTD · ASHCROFT ROAD · CIRENCESTER GLOS

THE TALK OF MODERN BUSINESS

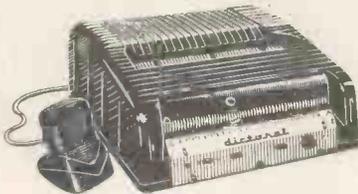

is the "DICTOREL"

This is the machine YOU have been waiting for—but you need wait no longer, because A.C.E.C. can supply you without delay. It is the last word in dictating machines, and has just the features every executive dreams of—unerring efficiency in "taking down" by a secretary who does not interrupt, catches every word and, by the flick of a switch, reads back exactly what you've said in the way you've said it! If you wish to correct your last sentence, you simply re-dictate the improvement you want, and the previous wording is automatically obliterated by recording the new.

Exclusive distribution in England and Wales by:

THE TREVOR-JOHNSTONE CO. LTD.,
169-174, SLOANE STREET, LONDON, S.W.1. Tel: SLO 6198 6199

Exclusive distribution in Scotland by:

LAND, SPEIGHT & CO., LTD.,
73, ROBERTSON STREET, Glasgow, C.2. Tel: Central 1082

**ATELIERS DE CONSTRUCTIONS
ELECTRIQUES DE CHARLEROI (Belgium)**



56, VICTORIA STREET, LONDON, S.W.1. Tel: VICTORIA 3662

Instruments  for Research and Industry

Model 44 SUBSTANDARD MULTI-RANGE METER

A self-contained precision instrument for general laboratory use and for calibrating first grade single or multi-range meters. The accuracy on the 44 range is **Substandard** on D.C. and within $\pm 0.5\%$ on A.C.



★ These meters are made with the greatest care and have been supplied for a number of years to the leading laboratories at home and abroad.

ELECTRONIC INSTRUMENTS LTD

17, PARADISE ROAD · RICHMOND · SURREY · ENGLAND



TAPE DECKS

TAPE RECORDERS

I.F. TRANSFORMERS


SWITCHES

VIBRATORS

COILS · COIL PACKS

A.F. HYPERLOY

TRANSFORMERS

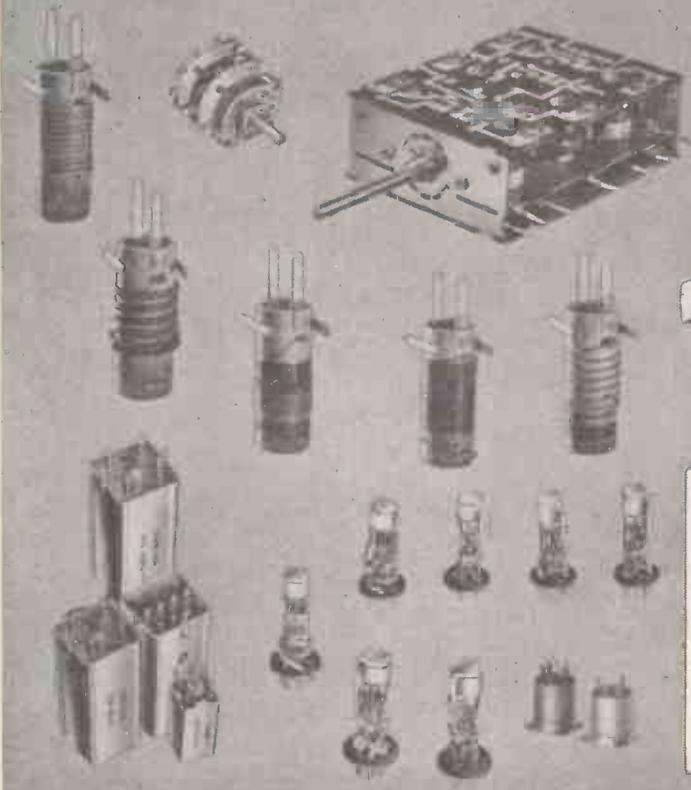

WRIGHT and WEAIRE
 LIMITED
 Manufacturers of Components for the
 Radio, Electronic and Sound
 Recording Industries
 138 SLOANE STREET, LONDON S.W.1
 Telephone: SLOane 2214-5
 Factory
 SOUTH SHIELDS, CO. DURHAM
 STAND No. 112 EARLS COURT
 AUG 29 - SEPT 8

test and adjust TELEVISION independent of B.B.C. transmissions



waveforms
PRODUCT

PRICE: £55 Net. Single Channel Model (London, Midland or Northern Frequency), £48 Net.

Meet us at the RADIO SHOW, EARLS COURT, London, Aug. 29th - Sept. 8th. Stand No. 34.

On ALL Frequencies with the new Radar "5 Channel" Video and Sync Generator

For Television engineers, whose services cover more than one transmission area, Waveforms Ltd., now introduce an instrument which provides a fully synchronized test pattern together with simultaneous sound on all B.B.C. frequencies. A three position attenuator is incorporated, giving outputs of 10 mV., 1 mV., and 100 Microvolts. equivalent to local, medium and distant signal conditions.

The inclusion of this inexpensive instrument in the servicing equipment of retailers service departments ensures a full eight hour working day for all engineers now handicapped by the inadequacy of the present B.B.C. test transmission periods. Send to-day for full technical details to:—



WAVEFORMS LIMITED, 26 Oakleigh Road, New Southgate, N.11. Phone: ENTerprise 5967

Get your share of EXTRA sales . . .

. . . with this NEW Gramplan Receiver Amplifier. A lower-output version of the well-known Gramplan Type 461, specially developed for applications where the higher output is not needed.

A superheterodyne Radio unit directly coupled to a L.F. amplifier with two output valves connected in parallel. Designed to meet the stringent requirements of Education Authorities, it is eminently suitable for small schools, being capable of feeding up to eight Loudspeakers at 1-watt each, or a larger number with a proportionately smaller output each.

Extend your sales to Clubs, Hotels, Works, etc.—they too will be interested in the Gramplan Type 506.

Gramplan Type 506. 8-watt A.C. Receiver Amplifier. 7½" wide x 13½" deep x 8½" high. Retail £32.10.0. P.T. £47.8.



STAND NO. 110
Radio Show, Earls Court
August 28—September 8

GRAMPLAN REPRODUCERS LTD

9 HANWORTH TRADING ESTATE, FELTHAM, MIDDX.
Phone: Feltham 2657 Grams: Reamp, Feltham

BRADMATIC LTD.

Offer the BRADMASTER Model 5 Tape Desk

- Built to professional standards.
- Two speeds—3½ and 7½ inches per second.
- Fast wind and rewind—full reel rewind in 1½ minutes.
- Heavy alloy flywheel. Freedom from "wow" and "flutter."
- Double servo brakes on each hub.
- Push Button control.
- Three heavy duty motors.
- Three shielded Bradmatic heads.
- Size: 13½in. x 15½in. x 6½in. deep.

Owing to the considerable rise in the cost of materials and etc., it has been necessary to increase the price of the model 5 tape desk. The new price, to take effect from 1st August, 1951, will be £41. This will include the price of the plugbox which is now fitted to all standard machines.

Hi-fidelity magnetic sound heads:	
type 5 R.P. (record/play head)	£3 5 0 each
type 5 E (erase head)	£3 5 0 "
Super fidelity magnetic sound head, type 6 R.P. (record/play head)	£3 15 0 "
Composite screening cans (constructed of steel and mumetal)	4 6 "
Oscillator coils	8 0 "
Tape on 7in. reels, 1,200ft.:	
Emtape, type 65	£1 5 0 "
G.E.C. Grade "A"	£1 10 0 "
Durex type, MC I—III	£1 15 0 "

Amplifiers and Microphones supplied.

Trade Supplied.


Send for Lists to the Sole Manufacturers:

BRADMATIC LIMITED

STATION RD. · ASTON · BIRMINGHAM 6

Phone: EAST 0574. Grams: Bradmatic, Birmingham

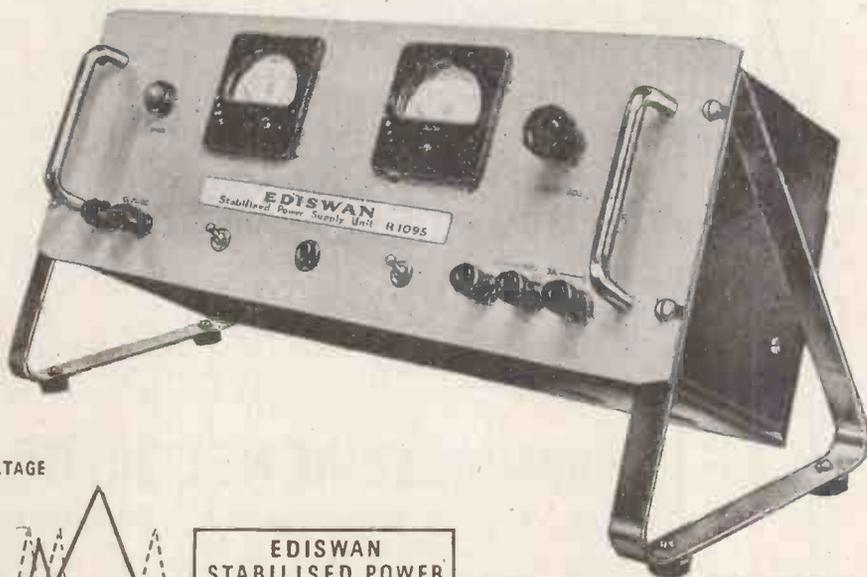
A new low-priced STABILIZED POWER SUPPLY UNIT



PRICE

Stabilized Power Supply Unit (metered) £23.2.6
 Stabilized Power Supply Unit (without meters) £18.18.6
 Plated Bench Stands £1.1.0

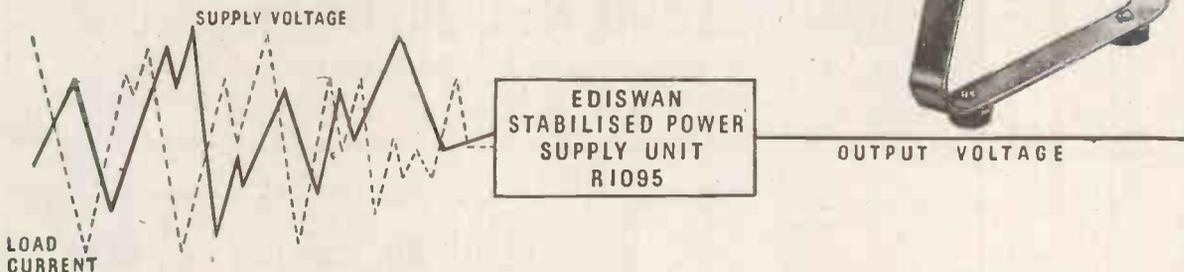EDISWAN
 STABILISED POWER
 SUPPLY UNIT
 R1095



Designed and developed as a result of many years experience in the design and use of Stabilized Power Supplies for research and test purposes, the Ediswan Stabilized Power Supply Unit R.1095 is an entirely new, low-priced constant voltage source.

Operating on 200-250 volts, 40-100 cycles A.C. supply it provides an adjustable 120-250 volts D.C. highly stabilized supply at 0.50 mA and a 6.3v C.T. 3 amp. A.C. unstabilized output for heater supply.

The stability is such that with mains change of 10v,

output change is less than 0.1v. With load change of 0.50 mA, output change is less than 0.1v.

Output resistance less than 2 ohms. Ripple approximately 2 mV.

The unit can be supplied with or without meters. Provision is made for the addition of meters at a later date. The unit is designed for standard 19" rack mounting or for bench use. Plated bench stands as illustrated are available if required.

Further details are available on request.

EDISWAN

THE EDISON SWAN ELECTRIC COMPANY, LTD.


Radio Division

155 CHARING CROSS ROAD, LONDON, W.C.2.

Member of the A.E.I. Group of Companies.

Telephone: Gerrard 8660.

Telegrams: Ediswan, Westcent, London.

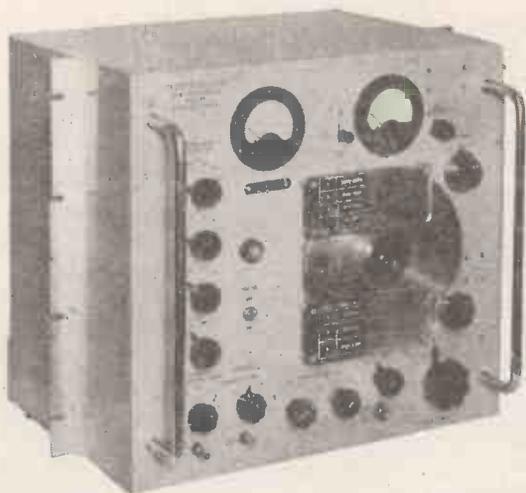

Power supplies :
200 — 250 Volt. 50 c/s

Range of measurements;
through levels + 10 db to - 61.5 db
or terminated levels + 10 db to - 81.5 db
referred to 1mW in 75 ohms

This is a precision instrument for measurements on multi-circuit coaxial cable carrier systems by means of a comparison with locally generated signals of known frequency and level.

Frequency coverage; 60 Kc/s—3 Mc/s in 7 ranges.

Calibration accuracy: below 0.2% or 2 Kc/s whichever is the greater.

BRITISH COMMUNICATIONS CORPORATION LTD.

GORDON AVENUE, STANMORE, MIDDX.

Telephone : GRIMSDYKE 2266

Cables : DISC, STANMORE

MICROGROOVE EQUIPMENT

Supplied from Stock

Turntables, with or without pickups, by BSR, Cosmocord, Decca, etc.

•
Also from Stock

Gramophone units and pickups for standard recordings.

•
Sound recorders and accessories—direct disc and magnetic tape.

•
Public address and internal telephone installations.

•
Send details of your requirements to

N. MIERS & CO. LTD.

115 Gower Street, London, W.C.1

'Phone: EUSton 7515. 'Grams: Miersco, Westcent

The "RD JUNIOR DE-LUXE" Amplifier (Improved Version)

NOW FITTED WITH KT66 PUSH-PULL OUTPUT STAGE,
GIVING 10 WATTS UNDISTORTED OUTPUT

New Specification: (Provisional)

Input Sensitivity P. U. 78 Standard
120m/V. P.U. 33 L.P.
80m/V. RADIO 200m/V.

Bass and Treble Controls ± 18 DB.

Response within ± .25 DB.
30-20,000 cps.

N.F.B. on all stages. Main loop
including output transformer 20 DB.

Distortion not exceeding .25% at
1,000 Kc/s.


PRICE £25.0.0 complete

Full details available on request.

Trade enquiries invited.

ROGERS DEVELOPMENTS CO.
"Rodevco House," 116 Blackheath Road,
GREENWICH, S.E.10.

Telephone: TIDeway 1723.

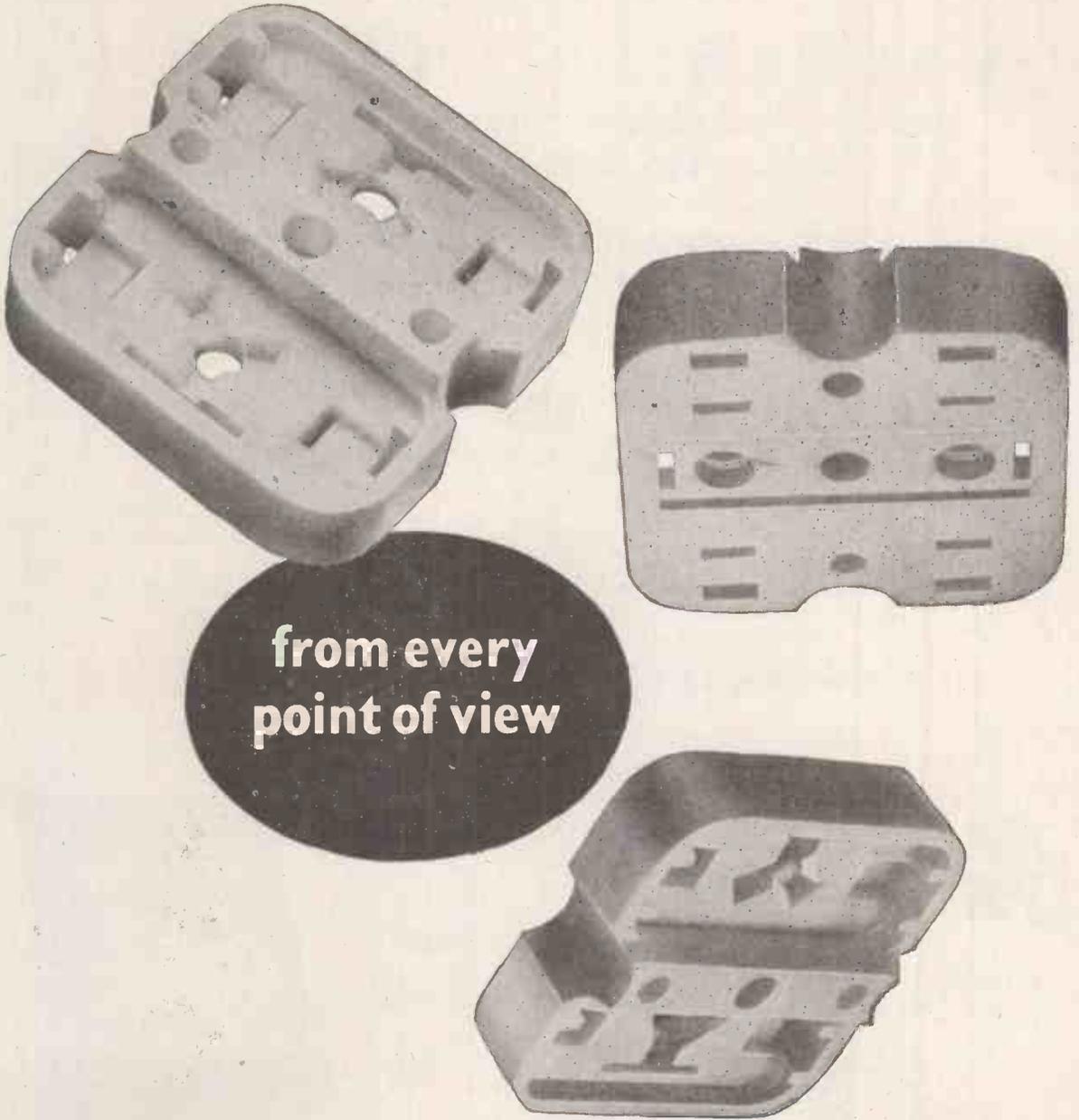

**from every
point of view**

“Frequentite” is the most suitable insulating material for all high frequency applications. Seventeen years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.

STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: Stourport-on-Severn, Worcestershire. Telephone: Stourport 111. Telegrams: Steatint, Stourport



VALVES!! TUBES!!

RECEIVING, TRANSMITTING, MAGNETRONS, KLYSTRONS,
CATHODE-RAY TUBES, PHOTOCELLS, ETC.

First Grade Quality - British and American Make - No Dollar Expenditure Involved

LARGE QUANTITIES & GREAT VARIETIES
IMMEDIATE DELIVERIES FROM STOCK

Write or Phone:-

S. Szymanski

(pronounced SHE-MAN-SKEE)

ELECTRONIC
ENGINEER & STOCKIST

95, STRODES CRESCENT, STAINES, MIDDLESEX

Telephone: STAINES 3971

Telegrams: "Shemanskee" Staines.

PROBABLY THE LARGEST ACTUAL STOCKIST IN ENGLAND

WHOLESALE & EXPORT ONLY

Only with **CO-AX**
R.F. **CABLES**

AIR-SPACED ARTICULATED

Patents Regd. Trade Mark

THE LOWEST-EVER
CAPACITANCE OR
ATTENUATION

**IMMEDIATE
DELIVERIES**

SPECIALISTS IN AIR-SPACED
ARTICULATED CABLES SINCE 1929

TRANSRADIO LTD.
CONTRACTORS TO H.M. GOVERNMENT
138A CROMWELL ROAD, LONDON S.W.2
ENGLAND

LOW WATTEN TYPES	IMPED. OHMS	ATTEN. db/100ft. at 100Mc.	LOADING %	OD. "
A 1	74	1.7	0.11	0.36
A 2	74	1.3	0.24	0.44
A 34	73	0.6	1.5	0.88
LOW CAPAC. TYPES	CAPAC. pF/ft.	IMPED. OHMS	ATTEN. db/100ft. at 100Mc.	OD. "
C 1	7.3	150	2.5	0.36
PC 1	10.2	132	3.1	0.36
C 11	6.3	173	3.2	0.36
C 2	6.3	171	2.15	0.44
C 22	5.5	184	2.8	0.44
C 3	5.4	197	1.9	0.64
C 33	4.8	220	2.4	0.64
C 44	4.1	222	2.1	1.03

HIGH POWER FLEXIBLE

PHOTOCCELL CABLE

VERY LOW CAPACITANCE



Precision
INSTRUMENTS



Thermo-couples are available, complete with 4 ft. compensating leads.

Portable PYROMETER

A high-grade, 3½" scale moving coil instrument, robust, accurate and speedy in response. Normally supplied with 2 scales, 0-200°C and 0-400°C, and 3 surface couples. Also supplied with ranges up to 1,600°C for all standard thermo-couples.


For details of this and other SIFAM instruments, write for new catalogue to:-

SIFAM ELECTRICAL INSTRUMENT CO. LTD.
LEIGH COURT, TORQUAY. Telephone: Torquay 4547-8



rectifiers

for the radio industry

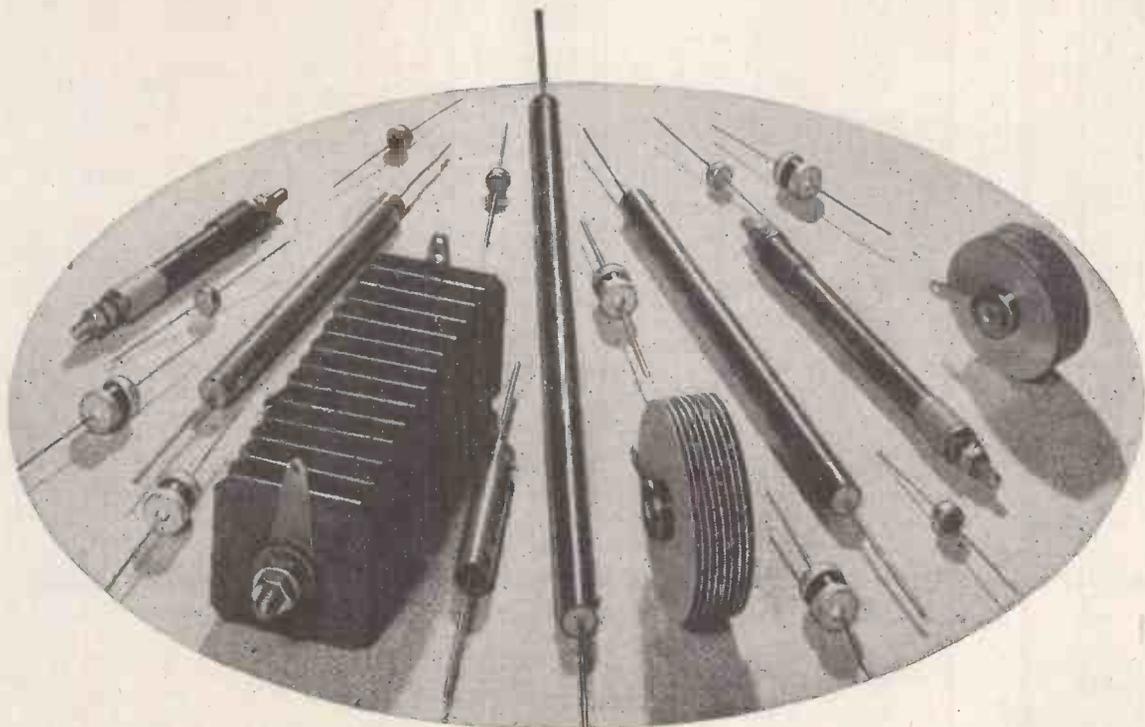

WHEREVER a radio or television diagram shows a rectifier operating at 0.5 Volts or higher, at a frequency below 5 mc/s there is almost certain to be a SenTerCel Selenium Rectifier which will do a better job because it:

Please write for leaflets **F/SRL9, 9a, 10 & 11**

- Saves space and weight
- Reduces wiring
- Withstands an unlimited instantaneous overload
- Reduces heat dissipation
- Needs no "warming-up" period
- Saves the cost of a valveholder
- Is practically indestructible in service
- Imposes no limit on the size of the reservoir capacitor
- Is low in cost


Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

See our Exhibits on
STAND No. 87
NATIONAL RADIO EXHIBITION
EARLS COURT

RECTIFIER DIVISION WARWICK ROAD, BOREHAM WOOD, HERTS.

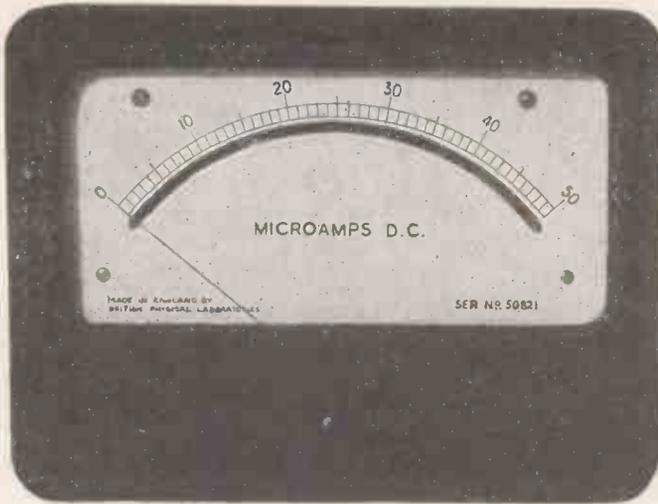Elstree 2401 Telegrams: Sentercel Borehamwood



SIZE	2½"	3½"	5"
RANGE	25μA	10μA	10μA
	to	to	to
	50A	50A	50A

(Prices on application)

S.50 type Microammeters are stocked by Messrs. M. R. Supplies at New Oxford Street, London, W.1.

All sizes available with
MIRROR SCALE
1st Grade Accuracy

SENSITIVE PANEL MOUNTING METERS

For particulars of these and our full range of measuring instruments write to :—

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone : RADlett 5674-5-6



ANOTHER BOOK

by G. A. BRIGGS *

FOR SOUND ENTHUSIASTS AND MUSIC LOVERS

190 pp., printed Fine Art paper, size 8½ x 5½, bound full rexine. 102 figures.
"This is a fascinating book excellently produced and richly illustrated: 192 pages packed with pleasure and profit for all who are interested in the pianoforte and the science of sound."—MUSIC TRADES REVIEW, June 1951.

"This book is as unusual as the title. It is a comprehensive study of the piano and contains a really fascinating chapter in which half-a-dozen internationally famous pianists answer a searching questionnaire. Mr. Briggs is always understandable, and he brightens the text with many an unexpected witicism."—YORKSHIRE OBSERVER, 4th July, 1951.

* Author of Two Practical Guides to Good Reproduction DOCUMENTED — AUTHORITATIVE — ILLUSTRATED

LOUDSPEAKERS by G. A. Briggs

The Why and How of Good Reproduction 3rd Edition (5th Impression). A standard reference book, written in the author's attractive style, it answers the numerous questions that arise in connection with the reproduction of sound via the Loudspeaker. 36 illustrations 89 pages, 5/-, (5/3 post free)

SOUND REPRODUCTION by G. A. Briggs

indispensable, both to the expert and to the amateur enthusiast, the second edition of this authoritative work provides full information and detailed guidance on a variety of subjects ranging from cabinet design to needles and grooves. 248 pages, 193 diagrams. Bound Full rexine 10/6 (11/- post free).



PUBLISHED BY—
WHARFEDALE WIRELESS WORKS TEL.: IDLE 461
BRADFORD RD., IDLE, BRADFORD, YORKS

Audix B.B. Ltd.

SCHOOL RADIO



PRICE INC. TAX £28.9.1

MOD. R.A.11.

- POWER OUTPUT 10 WATTS
- INPUT FOR GRAMOPHONE
- TUNING INDICATOR & MONITOR SPEAKER
- POLISHED OAK CABINET

HOCKERILL WORKS ● BISHOP'S STORTFORD
Tel : Bishop's Stortford 1394

PREMIER RADIO COMPANY

B. H. MORRIS & CO. (RADIO) LTD.

BRAND NEW R1155 RECEIVERS,
in original cases, complete with
10 valves, £12/10/-.

BRAND NEW R1355 RECEIVERS,
in original cases, as specified for the
"Inexpensive Telesor," complete
with 11 valves, £2/15/-.

**BALANCED ARMATURE LOW
RESISTANCE HEADPHONES,**
Type 2, 7/11 set.

**HIGH RESISTANCE HEAD-
PHONES,** 12/6 set.


MOVING COIL HEADPHONES,
Type 5, 8/11 set.

**TANNOY HAND MICRO-
PHONES,** with switch in handle,
4/11.

ACCUMULATORS by world-
famous maker, 2 volt 10 a., 4/11.

BURGOYNE SOLDER GUNS,
75/-.

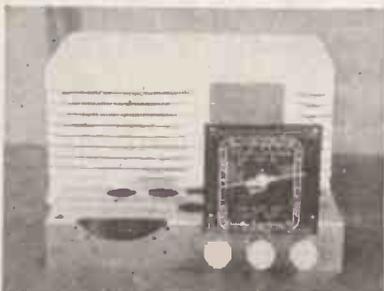T.R.F. COILS
180-550, 800-2,200 metres, pair 6/6



**GIVE YOUR HOME-BUILT RECEIVER
THAT PROFESSIONAL LOOK.**

We can supply all the parts to
help you. Bakelite Cabinet
(Brown or Ivory) 17/6
Punched Chassis
3 valve plus rectifier T.R.F. } 3/9
or 4 valve plus rectifier, Super-
het
Engraved Glass Dials
16-50 and 180-550 metres } 1/-
or 180-550 and 800-2,200 m. } each
or 16-50, 180-550 and 800-
2,200 m.
All with station names, new wavebands.

**P.M. MOVING COIL LOUD-
SPEAKERS (3 ohm voice coils)**

2½ in. Goodmans	15/-
3 in. Plessey	15/-
5 in. Plessey	12/6
5 in. Truevox	12/6
5 in. Rola	13/6
6 in. Truevox	12/6
8 in. Plessey	14/6
10 in. P.R.C.	35/-
12 in. Truevox	70/-

SUPERHET COILS
16-50, 180-550, 800-2,000 metres,
set 10/6

CIRCUIT DIAGRAMS
For T.R.F. or Superhet Receivers,
each 1/6

BRAND NEW CAR BATTERIES
Delco-Remy, in original cases
6 v. 100 a., £4/17/6, plus 7/6 carriage and
packing.
6 v. 140 a., £5/10/-, plus 7/6 carriage and
packing
12 v. 85 a., British made, £5/10/-, plus
7/6 carriage and packing.

OUR POSTAL SERVICE IS AGAIN IN OPERATION

Please Note: Our Only Address is

207 EDGWARE ROAD, W.2 Phone: AMBassador 4033


Open until 6 p.m. on Saturdays

**H.T. ELIMINATOR AND TRICKLE
CHARGER KIT**



All parts to construct an eliminator to give an
output of 120 volts at 20 m/a, and 2 volts to
charge an accumulator. Uses metal rectifier,
£2.

WILLIAMSON AMPLIFIER KIT

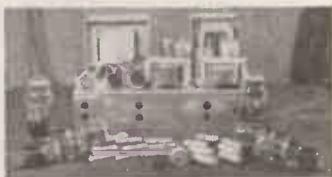

We can supply the Kit of Parts for the
latest version of this famous amplifier
complete in every detail for £10/10/-,
with valves, output and mains trans-
formers.



CORD DRIVE ACCESSORIES

Drum (2½ in. diam.)	1/-
Driving Head	1/-
Double Pointer	4d.
Spring	3d.
Nylon Cord (yard)	6d.
Dial Back Plate	2/6

**MAINS NOISE ELIMINATOR
KIT.** Two specially designed chokes
with three smoothing condensers with
circuit diagram. Cuts out all mains
noise. Can be assembled inside exist-
ing receiver, 6/- complete.

**T.V. WHITE RUBBER MASKS
(CORRECT ASPECT).** We can
supply a specially designed White
Rubber Mask for 6 in. C.R. tubes at
8/6 each.
9 in. White Masks, 9/6. 12 in. White
Masks, 16/11. Round or flat faced.


Please add 1/6 for post orders under 40/-,
1/- under 20/-. Cash with order or C.O.D.

CRYSTAL MICROPHONE

An entirely insulated crystal microphone which
can be safely used on A.C./D.C. amplifiers,
High impedance. No background noise, really
natural tone. The ideal Mike for tape, wire and
disc recording and sound projectors. Price
22/6.

SUPER QUALITY TELEVISION MAGNIFYING LENS.
To suit 5in., 6in., or 7in. Tubes. Increase picture size
considerably, 25/- each.

**GRAMOPHONE AMPLIFIER
KIT**

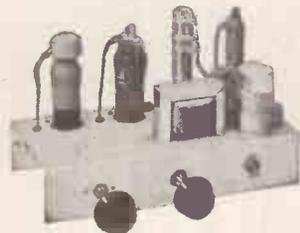

Consists of complete Kit of Parts for a
2½-watt Mains-operated 2-stage Ampli-
fier for use with any type of pick-up.
Volume and tone controls are in-
corporated. Output impedance is
3 ohms.
Cat. No. AMPI47. Price complete,
59/6. For 200-250 v. mains with valves
and diagrams.

RADIO VALVE DATA

Characteristics of 2,000 Valves and Cathode-ray Tubes

THE second edition of this reference—only just published—contains full details of over 2,000 types of British and American radio valves, and over 100 cathode-ray tubes. Eighteen British valve manufacturers alone are represented, all of whom have co-operated with WIRELESS WORLD in ensuring that the tabulated information given is accurate, comprehensive and up-to-date.

The main tables give the electrical characteristics of each valve, and separate tables show their base connections. Sub-divisions of the main tables further classify the valves into obsolete, replacement or current types as recommended by the makers. An index enables any valve to be found in the tables quickly and without trouble.



Obtainable at all good booksellers or direct by post from :

ILIFFE & SONS, DORSET HOUSE, STAMFORD ST., LONDON, S.E.1

The following classes of valves are shown: frequency-changers, screened tetrodes and pentodes, output valves, diodes, output valves and efficiency diodes for television line scan circuit, amplifier triodes, transmitting valves of various types up to 50 watts anode dissipation, valve rectifiers, E.H.T. rectifiers, tuning indicators, barretters, voltage stabilizers and thyratrons. In addition, non-thermionic diodes of the silicon, germanium and selenium types are listed, and also metal rectifiers. The cathode-ray tube section covers all British tubes for television receivers and oscilloscopes.

RADIO VALVE DATA must be considered an essential part of the equipment of every receiver designer, radio serviceman, dealer and experimenter.

3s. 6d. net. By Post 3s. 9d.

LOCKWOOD

makers of

Fine Cabinets

and specialists in
woodwork of every
description for the
Radio and allied trades.

LOCKWOOD & COMPANY


67, Lowlands Road, Harrow, Middx.

Telephone: BYRon 3704

BRIERLEY DIAMOND MICROARMATURE PICKUP

This new pick-up has many noteworthy characteristics, some of which are listed below:—

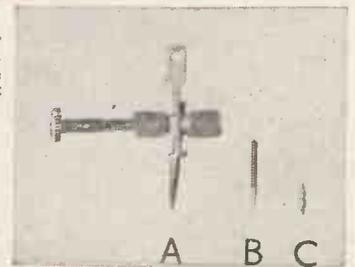1. The mass of the moving parts is less, we believe, than in any other pick-up of any type—other than our own Ribbon which is, of course, unique.
2. The output voltage—about 1/25th v.—is high enough to cause no trouble.
3. It is sufficiently robust to be used by any reasonably intelligent and careful family.
4. The use of a diamond point has, *inter alia*, the enormous advantage that a very large number of records may be played with negligible point wear. This results in a sustained "new" performance together with the elimination of that mental irritation at the gradual and perceptible "falling off" unavoidable with less wear-resistant points.
5. Organised production on a reasonable scale should give us a satisfactory



Photograph of A. Standard Needle, B. Miniature Needle and C. Brierley Microarmature.

production on a reasonable scale should give us a satisfactory "spares" and repair service and has enabled us to produce this pick-up at a price which many may at first have believed to be either a mistake or a printer's error.

Pick-ups, types JB/P/A/ID (78) and JB/P/A/IMD (LP) £6/0/0. Purchase Tax, £2/12/-.

Mumetal Coupling Transformer, type JB/T/A, £1/5/-.

Full details sent on request.

J. H. BRIERLEY (Gramophones and Recordings) LTD.
KIRKBY TRADING ESTATE · LIVERPOOL

MF, HF, and VHF transmitters, receivers, radio telephones, navigational aids, AF amplifying systems, flight simulators and other electronic devices are featured in the Redifon contribution to modern aviation. Enquiries for single units or complete networks, including aerials, masts, power supply, land line amplifiers, remote controls and other ancillary apparatus are welcome.



Redifon
WANDSWORTH, LONDON, S.W.18

TELCON LOW-LOSS TRANSMISSION LINES

<p>K.24.B 150-ohms nominal impedance, figure-8 section twin; capacitance 10.6 mmf/ft; Attenuation at 50 Mc/s, 2.1 db/100 ft; power rating at 100 Mc/s, 300 watts.</p>	<p>K.25.B 300-ohms nominal impedance, flat ribbon-type twin; capacitance 4.6 mmf/ft; attenuation at 50 Mc/s, 1.0db/100ft; power rating at 100 Mc/s 500 watts.</p>	<p>K.35.B 300-ohm tubular twin feeder with stable characteristics in varying weather conditions. Capacitance 4.0 mmf/ft; attenuation at 50 Mc/s 0.92 db/100ft; power rating at 100 Mc/s, 550 watts.</p>
--	--	--


THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO LTD

Head Office: 22, Old Broad Street, London, E.C.2
Enquiries to: Telcon Works, Greenwich, S.E.10

Telephone: LONDON Wall 7104
Telephone: GREENWICH 3291




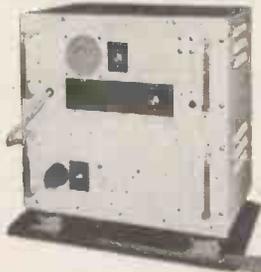ISOLATE that **VIBRATION** through **EQUIFLEX**



THE ALL-METAL SPRING MOUNTING

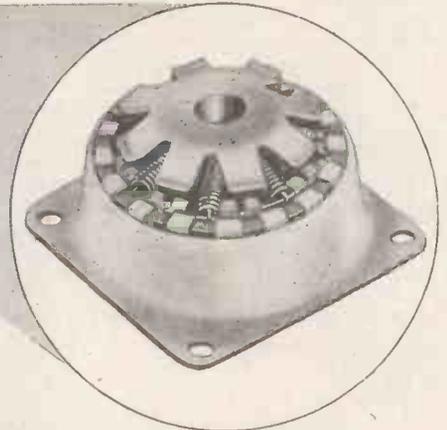- EQUAL FLEXIBILITY IN ALL DIRECTIONS
- CAN BE LOADED IN ANY DIRECTION
- UNAFFECTED BY CLIMATIC CONDITIONS
- VARIOUS TYPES FROM 1-35 lbs PER UNIT
- VIBRATION IS BOTH DANGEROUS AND COSTLY



Write for Catalogue and Price List to

A. WELLS & CO. LTD.
STIRLING R^d WALTHAMSTOW, LONDON E.17.

M.O.S. TYPE APPROVED. PATENT NO 571026
FOREIGN PATENTS GRANTED

FRITH RADIOCRAFT LTD for GRAM EQUIPMENT

These items available from stock :

B.S.R. MU-10-2-speed motors with 10in. turntable and rubber mat. A.C. only 100-250 v 50 c/s. Speed change from 33 to 78 effected by removing turntable and reversing drive pulley. Price £3/15/-.

B.S.R. MU-14 3-speed de Luxe version of above. "Rotacam" instant speed change from 33 to 45 and 78 r.p.m. Price £7/3/4.
COLLARO AC504. Radiogram units with auto stop. Complete with standard magnetic pick-up. Price £6/10/5.

RICHARD ALLAN portable case record player, incorporating Collaro 3/514 3-speed unit for 33, 45 and 78 r.p.m. Dual purpose ACOS GP27 crystal pick-up with sapphire. Auto stop, walnut finish cabinet. Price £21/5/4.

RICHARD ALLAN record player, incorporating Collaro 3RC/511 3-speed auto changer. Plays 10 7in., 10in. or 12in standard or microgroove records unmixd. Interchangeable Hi-Fi lightweight magnetic heads for standard or L.P. records. L.P. head fitted with sapphire. Complete in de Luxe walnut finish cabinet. Price £27/16/10.

CONNOISSEUR de Luxe two-speed motors as advertised. Speeds 33 and 78 r.p.m. Precision ground 12in turntable. Suitable for standard transcription and microgroove records. Price £20/19/3.

CONNOISSEUR super lightweight pick-ups. Twin interchangeable heads with sapphires. Matches the above motor. Price £9/6/4.

CHANCERY G33 epcyclic unit for playing L.P. records on standard 78 r.p.m. turntables. Price £3/12/6. Decca microgroove pick-up to match (A.C.O.S. cartridge with sapphire). Price £2/9/9.

GOLDRING lightweight magnetic pick-ups for standard records. Price £1/12/1.


MARCONI type 14 pick-ups, de Luxe lightweight type, complete with matching transformer. Price £2/8/4.

DECCA twin-head pick-ups incorporating turnover crystal cartridge and twin sapphires. Inside of PU head turns completely over for playing standard or L.P. records. Safety position at centre. Price £3/19/4.

ACOS GP20 pick-ups, limited supply. Price £3/11/5.
GP 19LP heads for microgroove records. Price £2/3/4.

FRITH RADIOCRAFT LTD

69-71 CHURCHGATE, LEICESTER. Phone 58927

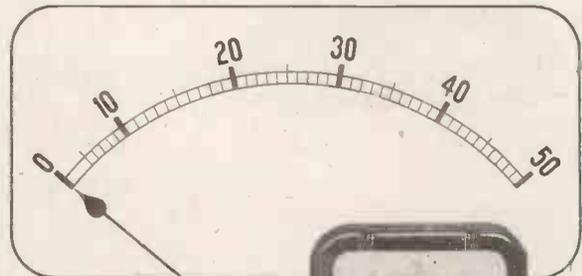

*Accuracy
is not enough*

The most accurate measuring instruments in the World are only of use if they can be read easily. A feature of the range of Pullin Rectangular instruments is the extreme legibility of their scales.


Available in all the standard ranges in sizes 3", 3½" and 6". Let us know your requirements and we shall be pleased to make recommendations regarding suitable instruments.

PULLIN RECTANGULAR
INSTRUMENTS



MEASURING INSTRUMENTS (PULLIN) LIMITED

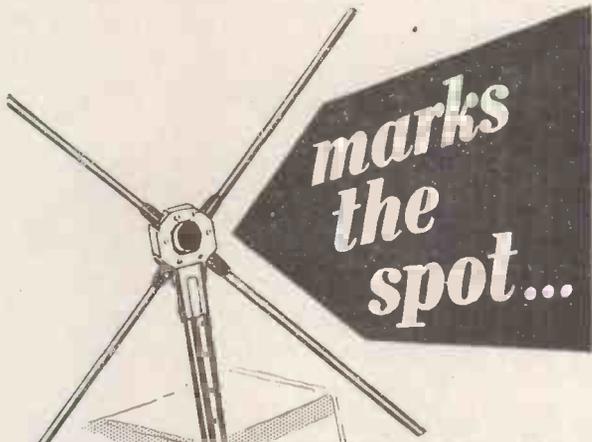Electrin Works, Winchester St., London, W.3. Phone: ACOrn 4651



..... where you can see the ANTEX AERIAL and the complete Antiference range of Radio and Television Aerials and Aerial equipment.

STAND N° 94

The
NATIONAL RADIO AND TELEVISION EXHIBITION

EARLS COURT
AUG 29th - SEPT 8th



ANTIFERENCE LIMITED
67 BRYANSTON ST. LONDON · W.1

Estd.

L.R.S.

1925

The
NEW SUPER REMINGTON CONTOUR 6

is now available for immediate delivery.

This latest American design is a considerable improvement on ALL previous shavers. We feel sure that once you have tried the new CONTOUR 6 you will never return to your present method of shaving and to convince you, our

TEN DAYS' FREE TRIAL
is available on receipt of deposit.

CONTOUR 6

AC/DC Model (200-250v.) Cash £8 19 5
or 50/- deposit with order and 7 monthly instalments of 20/-
(other voltages available).

Every Contour 6 Shaver is despatched in a superb presentation case by registered post.

Write for detailed Brochure which will be sent per return post by

THE REMINGTON SHAVER SPECIALISTS

ARMSTRONG ALL-WAVE CHASSIS

MODEL UNI 83/3. (AC/DC.) Cash £22/5/6 or £8 with order and 8 monthly instalments of 40/- (Delivery ex stock).
MODEL EXP 83/3. Cash £22/5/6 or £8 with order and 8 monthly instalments of 40/- (Delivery approx. 6 weeks).
MODEL RF 103/3. Cash £30/1/ or £10/10/- with order and 7 monthly instalments of 60/- (Delivery approx. 6 weeks).

All the above Chassis are supplied with Goodmans 10in. speaker with transformer.
Passenger Train 10/- extra (payable with deposit).

10" and 12" W.B. CONCENTRIC DUPLEX LOUDSPEAKERS also **GOODMAN'S AUDIOM 60 UNITS** are now in stock for immediate delivery.

CONNOISSEUR DUAL SPEED MOTORS

Cash £20/19/3 or £6/10/- with order and 8 monthly instalments of £2.

—Delivery from stock—


The **L.R. SUPPLY COMPANY** LTD.
(LONDON RADIO SUPPLY CO.)

BALCOMBE - - SUSSEX

Telephone : Balcombe 254.

1mV to 100,000mV

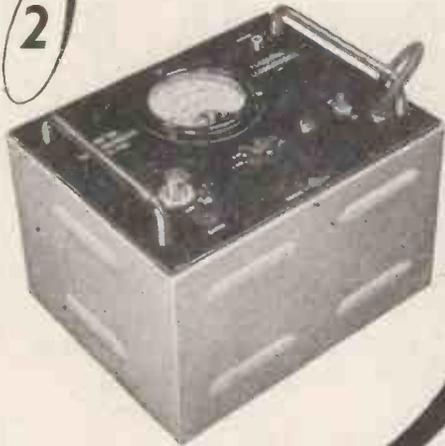Voltage measurements from 1mV to 100V within the frequency range of 10c/s to 500Kc/s can be made with this Sensitive Valve Voltmeter. The logarithmic scale shape of the meter enables an accuracy of $\pm 5\%$ at all points to be achieved.



Furzehill

FURZEHILL LABORATORIES LIMITED
BOREHAM WOOD, HERTS. ELSree 3940

AIDS TO EFFICIENCY



Type "K"

S. G. BROWN Type "K" Moving Coil Headphones meet every requirement of those engaged on laboratory and DX work, monitoring, etc. Accuracy is assured by their High Quality reproduction.

D.C. Resistance 47 ohms. Impedance 52 ohms at 1,000 c.p.s.



Type "F"

S. G. BROWN Type "F" (Featherweight) Headphones derive their popularity with the world's radio enthusiasts, experimenters and servicemen because of their High Sensitivity, Durability and lightness of weight.

D.C. Resistance 4,000 ohms.
Impedance 14,000 ohms at 1,000 c.p.s.
Weight 9 ozs.

Send for Brochure "W," it gives details of all types of S. G. Brown headphones.

S. G. Brown, Ltd.

SHAKESPEARE STREET, WATFORD, HERTS.


Telephone: Watford 7241.

FOR HIGH SPEED PRECISION SOLDERING



DU BOIS TRI-SOL
Activated
RESIN-CORED SOLDER

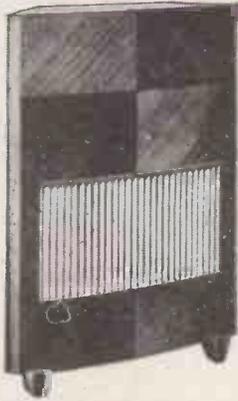Write for generous free sample and descriptive literature
THE DU BOIS CO. LTD., 15 BRITANNIA ST.,
KING'S CROSS, LONDON, W.C.1. TERminus 6624



"Prestige" Extension Loudspeaker. Walnut £14/19/6



Standard "Bafflette" Extension Loudspeaker. Walnut or Mahogany £4/12/6



Model N.C. Autochange Record Player. £22/9/8 (tax paid)



Major £3/15/-

Minor. £3/3/-

Baby £2/7/6

Supplies are difficult — but the Richard Allan Baffle Extension Speaker is again on show, maintaining its firmly established reputation for first-class workmanship, high quality materials and unique baffle design. Be sure to take advantage of this reliable service by placing your orders early.

Richard Allan

RADIO LTD · BAFFLETTE HOUSE · BATLEY · YORKSHIRE

Your first move . . . **FOR BETTER INSULATION**

CONSULT

Bullers


Makers of Low Loss Ceramics

Made in Three Principal Materials—

FREQUELEX An insulating material of Low Dielectric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

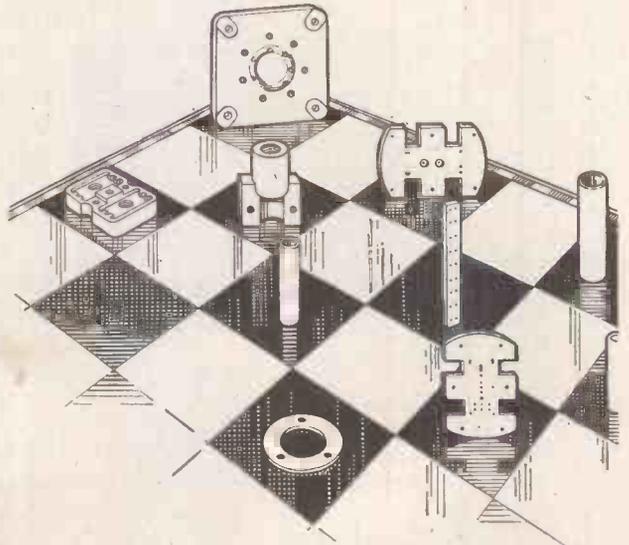TEMPLEX A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.



BULLERS LIMITED

6 Laurence Pountney Hill, London, E.C.4. Phone: Mansion House 9971 (3 lines) Grams: "Bullers, Cannon, London"



BLSB

LUXURY RADIOS

G.E.C. OVERSEAS 10 valve 5 waveband, push pull output of 12 watts, twin speakers, really "hot" on 10 metres, full range 10-2000 metres including trawler band. Bandsread scale. Variable sensitivity and separate bass and treble tone controls. This is the most sensitive and powerful set on the market. The large table cabinet is finished in a new ultra modern style. Present day price about £70. We offer six sets at only £30 each. 100-260 v. A.C. mains.

MARCONI DE LUXE 8 valve motor tuned press button all wave table radio. Super output of 8 watts from 6L6 and high gain pick-up input for use with the latest high fidelity types together with a host of push button stations makes this a most useful receiver. You can cruise round the dial on the motor tuning. This type of set is not available on the Home Market. Complete, of course, with makers instructions book. Six only at **£28 each.**

PX25 AMPLIFIERS. A superb push pull 15 watt model with all the latest refinements, extended tone control range. 3in. moving coil panel meter for current and distortion checks, oil filled condensers, fuses in circuits, two smoothing chokes and although in a steel case the front panel extends to fit on a 19in. standard rack. The high gain circuit in latest design will give full volumes from the smallest input. 500 ohm output, £12; 2/15 ohm output, **£13.10.0**; steel racks **£2.10.0.**

COMPLETE WAREHOUSE OF
Reconditioned

PHILCO RADIOS
ONE THIRD PRICE

125/- Large table model in light walnut large circular dial. Very selective.

147/- De Luxe Model with Bronze speaker grill.

189/- All Wave de luxe table model, large circular dial. Two speed tuning. Takes normal or dipole aerial.

120/- Cathedral model in light or dark oak. Receives all British and European stations with great clarity.

95/- Standard table model, square cabinet in light or medium oak. An absolute gift. Very few of these available.

ALL TYPES

have 5 valves despatched anywhere have pick up sockets take extension speakers cover voltages 200-260 v. are tested before despatch supplied in A.C. or A.C./D.C. current

WALKIE-TALKIE (Transmitter and Receiver) **CHASSIS** Type 38 Mk. II. Range 7.4-9 Mc/s. A superb Amateur Superhet receiver with an RF stage for Field Work. The speech modulated transmitter utilises a VFO with doubler and alternate sockets are provided for large or short aerials. Complete with 5 valves, throat microphone, phones and circuit.

Each set Air Tested, **£3.8.6**
Postage and Packing 2/6.

An Exceptional Offer!
CHEVROLET CAR RADIO RECEIVERS.

9 valves, 5 wavebands, 6 volt. This product of General Motors is exceptional value. Size 14in. wide x 9in. deep x 9in. high, graduating to 5in. at back. Carr. and packing 7/6.

£18.10.0

NATIONAL 1-10

This famous receiver covering the bands 1-10 metres carries the famous NATIONAL dial, has an RF stage, will work PM speaker or phones. Covers 144 mcs, Wrotham FM, Police, Fire services, Aviation etc. Complete with valves, Air Tested.

£9.10.0


Power Pack extra 75/-.

23, LISLE ST. (Telephone **LONDON CENTRAL** GERrard 2969) **LONDON, W.C.2**
RADIO STORES
Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m.—6 p.m.

The BIJOU

This ever popular Wharfedale speaker combines attractive appearance, handy size and moderate price. Fitted with the Standard 8" Unit. Handles 3 watts.

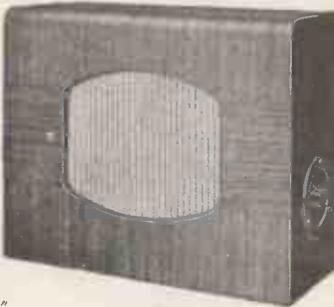Hand polished Walnut and fitted with volume control and 5' of P.V.C. flex. Weight 5½ lbs. Size: 12½" x 10" x 5½".



AN EVER POPULAR
SPEAKER FROM


85/-

Wharfedale
WIRELESS WORKS

BRADFORD RD., IDLE, BRADFORD, YORKS

Telephone: 'DLE 461

TUNERS

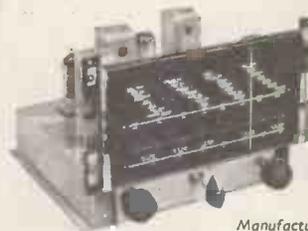

Our Type S4 is the Ideal Quality Tuner for your high-quality amplifier. This four-valve Super-Het Unit has a lively performance with very low distortion. Fitted variable selectivity 7K.C. and 10K.C. Wave-band coverage 16-50m., 195-550m., 900 2 000m. Using latest Mullard valves ECH42, 2xEF41, EB91.

£17.6.8
TAX PAID

Manufacturers of Vortex Cabinets.

C. T. CHAPMAN (Reproducers) Ltd. 4577/8
RILEY WORKS, RILEY STREET, CHELSEA, S.W.10
Daily Demonstrations at Webb's Radio

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark



Reg. Design, 860302

Designed for Wireless Assembly and Maintenance.

SUPPLIED FOR ALL VOLT RANGES FROM 6/7v to 230/50v.

The three Adcola Models cover the requirements of the Television, Telecommunication and Radar Engineers and assure thorough jointing.

- ½ in. dia. Bit. Standard Model— 22/6
- ½ in. dia. Bit. Standard Model— 25/-
- ½ in. dia. Detachable Bit — 30/-

Patented in England and Abroad.

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED
General Offices & Works: CRANMER COURT, CLAPHAM HIGH STREET, LONDON, S.W.4. Tel.: MACaulay 4272.



A NEW development in

**...reduced power factor by 50%
...increased R.F. loading 100%**

- TYPE M20 13" x 6 1/2" R.F. loading 140 kVA.
5000-10000 pf. 10 kV. Pk. Wkg.
1000-3000 pf. 15 kV. Pk. Wkg.
- TYPE M10 6 1/2" x 6 1/2" R.F. loading 70 kVA.
500-2000 pf. 15 kV. Pk. Wkg.
- TYPE M5 6 1/2" x 3 1/4" R.F. loading 35 kVA.
150-500 pf. 15 kV. Pk. Wkg.

R.F. loading ratings are at room temperature (15-20°C.)

Intensive development of electrodes, dielectric and processing now provides a new and greatly improved Hunt-Ingram Capacitor—the MARK 51.

In this latest type, the power factor has been reduced to a limit not exceeding 0.1%; as a result the R.F. loadings can be increased by approximately 100%.

Among the many applications are HF. Heating (blocking and bypass); High Altitude Airborne Service; Delay Networks in Pulse Circuits; Radio Transmission; Voltage Dividers and Stabilising Units. They are particularly useful in High Voltage and Power R.F. equipment.

Full information is freely available and enquiries are invited from designers.

Meet us at
Stand No. 95
THE RADIO SHOW
EARLS COURT
AUG. 29 - SEPT. 8




THE TRADE MARK OF RELIABILITY

A. H. HUNT LTD - WANDSWORTH - ENGLAND
Telephone: BAttersea 3131 Established 1901

*12 1/2 mA
Subminiature
Output
Tetrode*

XFY21

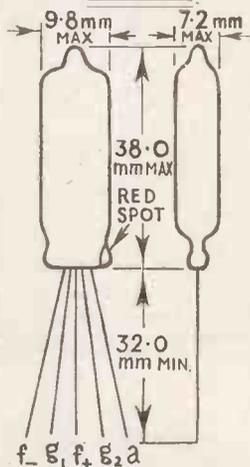

The XFY21 is a sub-miniature output valve now being made in the high-efficiency beam tetrode construction.

It is a robust, reliable valve suitable for the output stages of hearing aids. The output is sufficient for magnetic as well as crystal receivers.

The XFY21 has other applications in small instruments.

TYPICAL OPERATION

Filament Voltage	1.25v
Filament Current	12 1/2 mA
Anode Voltage	22 1/2 v
Average Anode Current	0.25 mA
Power Output	1.75 mW

HIVAC
THE SCIENTIFIC VALVE
BRITISH MADE
GREENHILL CRESCENT
HARROW-ON-THE-HILL, MIDDLESEX
Telephone: HARrow 2655

PROFFITTS of BOLTON

The leading suppliers of tape and wire recorders

MAGNETIC RECORDING—comparatively unknown to most amateurs in pre-war days, magnetic recording has now achieved amazing popularity due to the foresight of leading manufacturers, and really first-class instruments can be purchased for a modest outlay (see details of our Terms below), giving a performance very comparable with the modern gramophone record. As one of the leading distributors in the Country, we stock only recorders which have been thoroughly vetted and approved by us before offering for general sale, and you therefore may approach us with confidence with the assurance that over 25 years in the trade has developed an organisation competent to deal with all mail order queries however technical.



British enterprise gives you this marvel of Magnetic Tape Recording. Made in England by Messrs. Thermionic Products, Ltd., The Soundmirror opens up enormous fields in the development of mobile or static recording and reproducing. The Soundmirror uses paper coated tape, giving 30 minutes of high fidelity continuous recording, and moreover the recording is permanent and can be used indefinitely without total loss of quality.

Note these outstanding features:—

- ONE single-tip control provides for play-record rewind (2 positions) or fast forward requirements.
- Automatic erasure as each recording is made.
- Perfect fidelity without scratch or other extraneous noises.
- Frequency response 80–8000 output 3½ watts in push-pull.
- 8 inch P.M. speaker.
- CRYSTAL OMNIDIRECTIONAL MIKE.
- Magic eye modulation level indicator.
- Input channels for Mike, Gram and Radio.
- Power supply 200–250 volts A.C., etc., etc.

PRICES. Standard Model in polished wood cabinet—a distinctive piece of furniture £76/6/6 or deposit £15/5/3 balance 24 months.

Portable Model, case finished in crocodile skin £86/6/6 or £17/5/3 deposit, balance 24 months. ALL PRICES INCLUDE TAPE AND MICROPHONE.

SCOPHONY-BAIRD HOME RECORDER. A self-contained portable recording instrument of British manufacture using plastic coated tape.

Note these special features:—

- Simplicity of operation—fast rewind, stop and forward drive Operated from one control—simplified threading.
- Time indicator shows number of minutes already played and permits rapid selection of any part of recording.
- PORTABILITY—Equipment contained in neatly designed carrying case with provision for storage of mike and mains lead.
- Records from mike, gram, pick-up or radio—frequency response 50–5000 C.P.S. at 7½ in. per second.
- Output 10 watts in push-pull.
- Distortion less than 2 per cent at maximum level.
- Weight 30lb.
- Power supply 200–250V. A.C.
- Modulation level indicator, etc. Price, inclusive of M.C. Mike and Tape £58/5/6 or £11/13/- deposit, balance 24 months.

TAPE. We are also stockists of Wirek, Simon, etc., Descriptive leaflets with pleasure. EMI Plastic 25/6; G.E.C. High Coercive 30/6; Soundmirror paper 25/6—all prices are for 1 reel of 1,200ft. post paid. "MAGNETIC RECORDING" BY BEGUN. At last a comprehensive technical book on recording written by the chief designer of BRUSH CRYSTAL CO., of America. Price 25/6 inc. post. Limited supplies—order your copy NOW!

EASY TERMS

We offer the most generous terms in the trade. The above recorder may be yours for only 1/5th deposit, and the balance can be paid over 12, 18 or 24 months. Details and proposal forms on request.

R. W. PROFFITT LIMITED

(Main Suppliers of Recorders, Cine and Photographic Equipment)
49/51, KNOWSLEY STREET, BOLTON, LANCs.

'Phone: Bolton 4422.

Grams: Electra, Bolton.

URGENTLY REQUIRED

THE FOLLOWING EQUIPMENT
IN ANY CONDITION:—

SIGNAL GENERATORS Type TF.144G, TF.390F or G, TF.517, 605B and 804B. Ex-Govt. types 30, 31, 51, 52, 52A, 53, 56, 57, 101, 103, 106 and others.

FREQUENCY METERS Type BC221, TS.174/U, TS.175, TS.69AP, and other types.

CRYSTALS FOR BC.221 FREQUENCY METERS.

RECEIVERS Type S27, SX28, AR88 and others.

ALSO:—IMPEDANCE OR UNIVERSAL BRIDGES, OSCILLOSCOPES, "Q" METERS, VARIACS, OUTPUT METERS, ETC.

Please write, call or phone:—


OAK ELECTRIC CO.,
175, UXBRIDGE RD., HANWELL, W.7

EALing 0779

THE CLIP THAT GETS TO GRIPS WITH VIBRATION



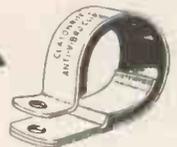The Clatonrite rubber-lined dual-purpose clips absorb vibration and provide an efficient method of securing pipes, conduits and cables. Plain Clip type A/9373 assures electrical insulation. Conducting or Earthing type A/9381 assures electrical contact through a metal tongue.



We shall be pleased to send literature and prices.

HOWARD CLAYTON-WRIGHT LTD., Wellesbourne, Warwickshire
Phone: Wellesbourne 316/7/8 Grams & Cables: 'Clatonrite', W'bourne

CONDENSERS
CRYSTALS
HEADPHONES
METERS
PLUG & SOCKETS
RESISTORS
VOLUME CONTROLS

Silver Mica · Tubular · Mansbridge
American · British
High and Low Impedance
Thermo · Moving Coil · Moving Iron
All Types
Carbon and wire wound
Carbon and wire wound

We hold large and comprehensive stocks of new components and units, both Government and Manufacturers' Surplus


No. 19 Set, Equipment Available.

Wholesale and Export Only.

ANDERS RADIO LTD.


167, HAMPSTEAD ROAD, LONDON, N.W.1
EUS. t. 1639 EST. 1928

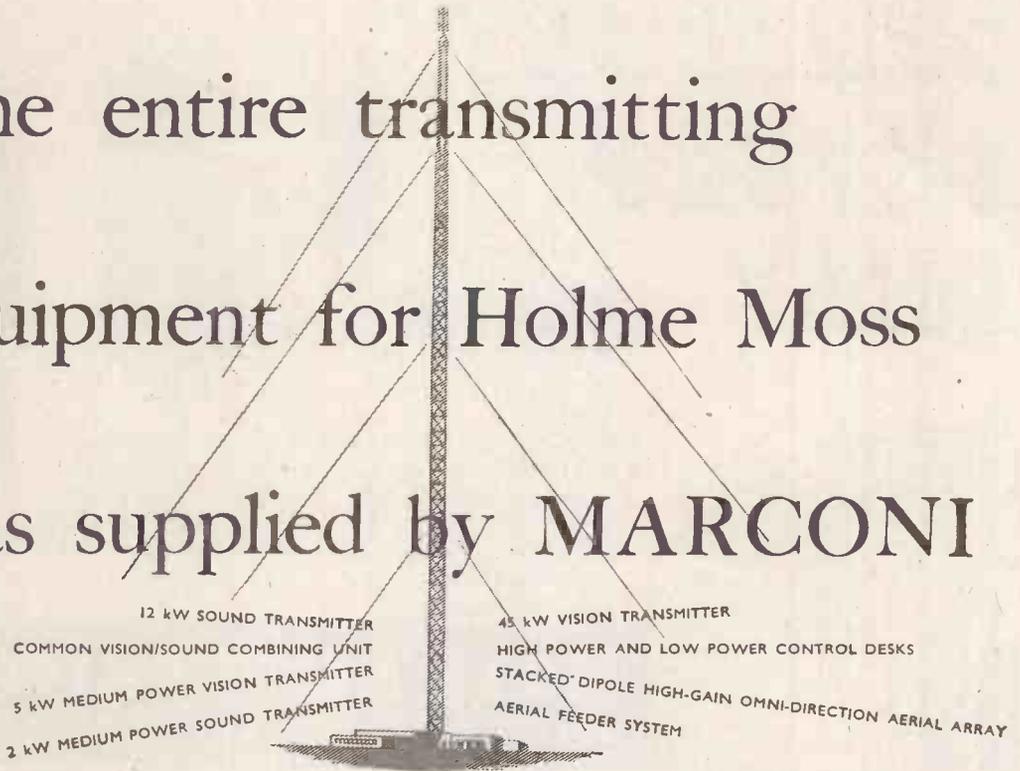The entire transmitting
 equipment for Holme Moss
 was supplied by **MARCONI**



MARCONI'S WIRELESS TELEGRAPH COMPANY LTD · MARCONI HOUSE · CHELMSFORD · ESSEX

External Field

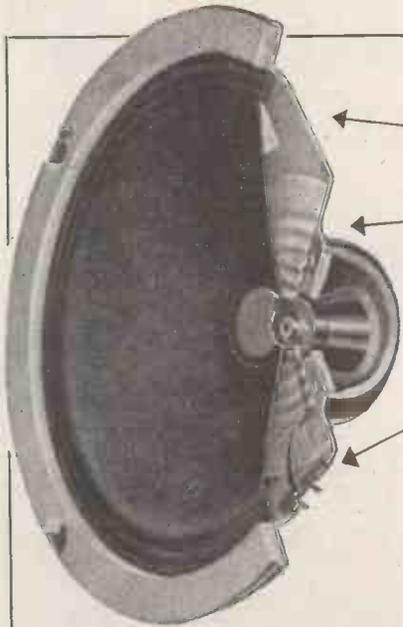

ZERO

Any loud-speaker with a ring magnet has a strong external field. This is unimportant in a radio set, but it matters a great deal in television, particularly in compact designs.

With centre-pole construction, as designed by R. & A., and total enclosure of the magnet system, much of the flux leakage is confined within the pot-shell itself. Using aluminium instead of mild steel for the chassis also helps, though at the expense of strength and rigidity.

But these are only palliatives, so we developed (and patented) a simple and effective method whereby, after assembly and magnetising, all external flux is eliminated without reducing the flux in the gap.


This method enables us to make—and support—our claim of 'Zero External Field', and accounts in part for the growing popularity of R. & A. Reproducers among leading television manufacturers.

REPRODUCERS AND AMPLIFIERS LIMITED
WOLVERHAMPTON · ENGLAND

Telephone : Wolverhampton 22241 (5 lines). Telegrams : Audio, Wolverhampton



STRICTLY EXPORT ONLY

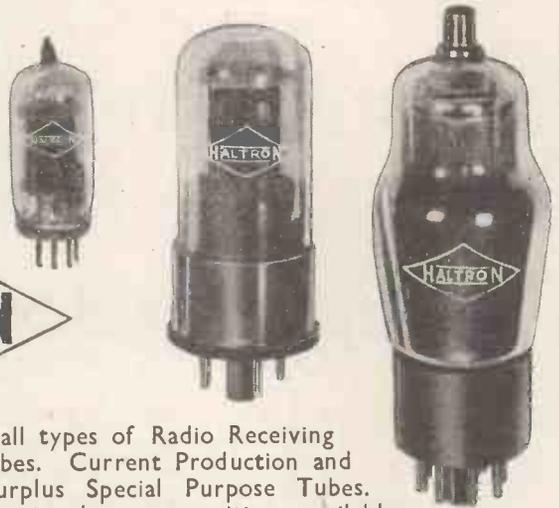

Leading Exporters of all types of Radio Receiving and Transmitting Tubes. Current Production and Ex-Government Surplus Special Purpose Tubes. Over 400 types in large quantities, available Ex-Stock. Suppliers to Foreign Governments, Airlines, etc.

HALL ELECTRIC LTD

89, CHARLOTTE ST., LONDON, W.I.

Phones: MUSEUM 9661 (5 lines)
Cables: HALLECTRIC, LONDON

“You’re **CERTAIN** to get it at **ARTHURS!**”

★ **VALVES** : We have probably the largest stock of valves in the country. Send your enquiries.

AVO METERS IN STOCK

Avo Model 7	£19 10 0
Avo Model 8, high resistance	£19 10 0
Avo Model 40	£17 10 0
Heavy Duty	£13 13 0
Avo Minor, AC/DC model	£10 10 0
Electronic Test Meter	£40 0 0
Signal Generator	£30 0 0
Valve Characteristic Meter	£50 0 0
Universal Bridge	£26 0 0

★ **Cossor Oscillograph Model 1035** £85.00

VALVE MANUALS

Mullard - - - 5/- ea
Mazda : Part 1, 1/- Part 2, 2/-
Brimar Teletube and Radio Valve Replaces Mullard Valve Replaces Mullard Guide 1933-43, 2/6 Post 6d. each extra. Send for catalogue.

TAYLORS METERS. List on request.

DECCA PICK-UPS	£3 15 5
DECCA HEAD	£2 19 2
ADAPTOR for Garrard	3 8

All goods offered subject to price alterations and being unsold.

LONDON'S OLDEST LEADING RADIO DEALERS

Arthur's EST. 1919
PROPS: ARTHUR GRAY, LTD. Terms C.O.D. or cash with order

Our Only Address. **Gray House, 150/152 Charing Cross Rd., London, W.C.2** TEMple Bar 5833/4 and 4765
ELECTRICAL, TELEVISION & RADIO ENGINEERS

NEON TEST PROD

Suitable for testing up to 250 V. supplies. Will indicate polarity and detect leakage. Housed in moulded rubber black case. Totally shockproof and safe.

Tests on **A.C. & D.C.**



A.F. BULGIN & CO., LTD.,
BYE PASS RD., BARKING, ESSEX

RADIO DEALERS AND SERVICE ENGINEERS

WE HAVE WHAT YOU WANT to service your Radio & Television Receivers. Stock Lines all Types of Condensers—Mains Transformers—Chokes—Coils—Potentiometers—Resistors—Loud Speakers, and many other attractive items at low prices.

SEND FOR OUR MONTHLY BULLETIN which includes special bargain lines.

— TRADE ONLY SUPPLIED —

HOME and OVERSEAS

V. E. S. WHOLESALE SERVICES LTD.
11, GUNNERSBURY LANE, WEST ACTON, W.3
Phone: ACORn 5027

FOR OVER THIRTY YEARS!

"Expert" hand-made products have enjoyed a name and reputation for high quality record and radio reproduction that has never been surpassed, or even equalled. Many readers of the "Wireless World" may also be readers of the "Gramophone," and to those who are, we need no introduction. Ever since the first issue of the "Gramophone" over twenty-five years ago, our name and reputation for high quality reproduction has been known and respected by critics and music lovers in every corner of the world.

We are fully aware that the "Gramophone" appeals mostly to the music lover, but we feel quite sure that "Expert" productions will have an equal appeal to the more technical minded readers of the "Wireless World," who will have a special interest in the test report by the National Physical Laboratory on the 15-watt New Master Amplifier (a special three-piece outfit); from this report you will see that this amplifier, like the latest edition of the "Expert" Master Speaker, is "in a class by itself."

The purpose of this advertisement is to put our theory to the test.

If you are really interested in the highest quality reproduction it is possible to obtain, irrespective of all other considerations, then you will ask us to send you full details of our work, and we will be very pleased to do so.


"EXPERT"

GRAMOPHONES LTD

"INGERTHORPE" · GREAT NORTH ROAD · LONDON · N:2

DEMONSTRATIONS AT ANY TIME, DAY OR EVENING BY APPOINTMENT

Phone MOUNTVIEW 6875

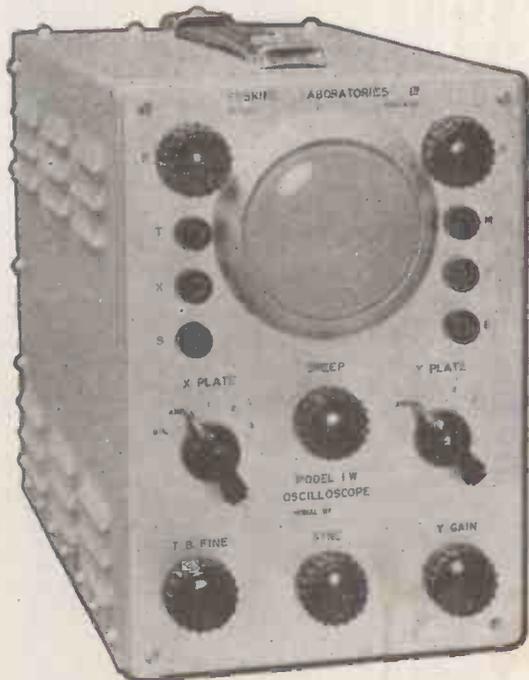

TELEVISION & RADAR

SQUARE WAVES

THIS OSCILLOSCOPE HAS A STEPPED Y-AMPLIFIER GAIN CONTROL COMPENSATED, ON EACH STEP OF APPROXIMATELY 6 DB., TO ENSURE ACCURATE REPRODUCTION OF SQUARE WAVES

OTHER FEATURES

BUILT-IN WOBBULATOR
 TIME-BASE 10-250,000 c/s
 BRILLIANCE MODULATION
 SHIFT CONTROLS, etc. etc.


PRICE **£25** MODEL 11W

WRITE FOR DETAILS

HIRER PURCHASE TERMS AVAILABLE

ERSKINE LABORATORIES LTD., SCALBY, SCARBOROUGH, YORKS.

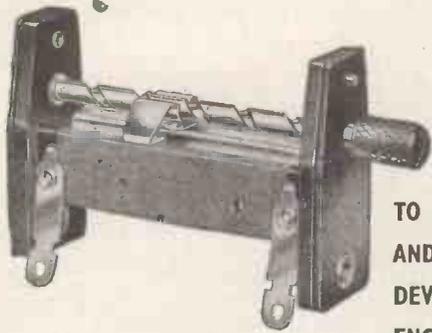(THE DEVELOPERS and MANUFACTURERS OF THE NOW FAMOUS TYPE 13 FOR THE SERVICES)



TO RADIO
AND T/V
DEVELOPMENT
ENGINEERS

This mid-set pre-set variable resistor with new double-slider gives greater stability and makes accurate adjustment easier. Designed for panel or chassis mounting: available in any value from 10 to 25,000 ohms.

EGEN
ELECTRIC LTD

Charfleet Industrial Estate, Canvey Island, Essex. Phone: Canvey 691

1 KW TELEGRAPH TRANSMITTERS. Two HF 300's output. Operation 3.5 mc to 16 mc.

HALLICRAFTERS BC 610's. Complete with speech amplifier, antenna tuning unit; exciter units and coils for all bands.

RCA TRANSMITTERS. Type ET-4336. Complete with matched speech amplifier, crystal multiplier and VFO units. Brand new.

LM-300 TRANSMITTERS (U.S.A.). 140 kc to 400 kc and 650 kc to 1,600 kc. 300 watt output.

No. 12 TRANSMITTERS. With coupling units, remote control etc.

AR-77's NC 200, NC 45.

AUTOMATIC HIGH SPEED TELEGRAPH EQUIPMENT. "BOEHME" (U.S.A.). Up to 400 signs per minute on line and wireless.

NAVY MODEL TBY-8 TRANSMITTING-RECEIVING EQUIPMENT. Output 0.75 watts on M.C.W. telegraphy and 0.5 watts on telephony. Frequency range 28-80 mc.

SKYRIDER DIVERSITY HALLICRAFTERS RECEIVERS. Complete with console, power units and loudspeaker.

All above items in excellent working condition.

Working demonstration upon request.

TX VALVES 805, 807, 813, 814, 861, 866A, DET-16 and many others.

Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken.

P.C.A. RADIO

Transmitter Division:—

The Arches, Cambridge Grove,
London, W.6, Tel. RIV 3279

Receiver Division:—

170 Goldhawk Road,
London, W.12,
Tel. SHE 4946

ALEC **Davis**
SUPPLIES Ltd.

Dept. W.W.

18 TOTTENHAM
COURT ROAD,
LONDON, W.1

Tel.: MUSeum 2453/4539

Shop hours: Monday - Friday 9-5.30
FULL MAIL ORDER FACILITIES.

Saturday 9-1
Please add postage


RELAYS (EX-MINISTRY)

D.C. COIL RESISTANCE

3,000 TYPES: 1.9Ω to 80,000Ω
600 TYPES: 0.4Ω to 9,200Ω

ALSO LARGE STOCKS OF
DOUBLE & TRIPLE-WOUND
AND SLUGGED COILS.

600 or 3,000
TYPE

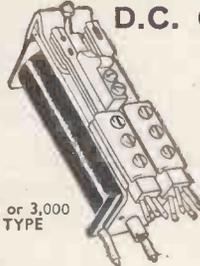

CONTACTS

3,000 TYPES: up to 8 sets.
600 TYPES: up to 4 sets.


3,000 TYPES: Make (M), Break (B), in Twin-silver, Twin-platinum, Dome-silver (2 amp.), Tungsten (5 amp.), and Flat-silver (8 amp.). Change-Over (C), in all but Tungsten: Make-Before-Break (K), in Twin-silver and Twin-platinum.

600 TYPES: (M), (B) and (C), in Twin-silver and Twin-platinum.

SPECIAL

3,000 type Relays with 80,000Ω coils operating on approx. 600 μA. with up to four sets of contacts.

SIEMENS H/S
TYPE

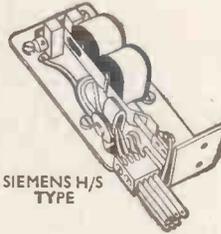

COILS • COILS • COILS

T.R.F. • SUPERHET • FILTERS • PACKS
TELEVISION COILS • I.F. TRANSFORMERS

FOR DEPENDABLE COMPONENTS
CONTACT

OLYMPIC RADIO COMPONENTS

COIL WINDING SPECIALISTS & MANUFACTURERS
224, HORNSEY RD., N.7. NORTH 2914

**RADIO DEALERS & SERVICE ENGS. ONLY
EXPORT AND IN THE U.K.**

Invited to write for our 1951 Complete Price List.

Full details of A.W.F. speaker cone assemblies give you fast, cheap, speaker repairs in your own workshops. A.W.F. Transformers and chokes for almost all replacements. A.W.F. Repair Department for repairs to speakers, transformers, Gram. motors, Vac. motors, etc., Current stocks of Tungram Valves, T.C.C. and Dubilier capacitors. Erie Resistors and pots, Components and Cabinets for "View Master" and "E.E." Televisors, and hundreds of other lines.

ENCLOSE POSTAGE 3d. inland, 2/- Overseas Air Mail:

A.W.F. RADIO PRODUCTS
TATLER CHAMBERS • THORNTON ROAD
BRADFORD • YORKS

TEL: 24008

GRAMS. & CABLES: "TESTPROD"

Announcement!

We are pleased to announce the **SIMPHONIC 1A**, an addition to our range of portable recorders. The new model has an impressive specification and offers long playing times coupled with ample output power and high quality. Features include:—

- 3½ and 7½ ins/secs. with **CONSTANT SPEED CAPSTAN**
- **TWIN TRACKS** ● Finger tip **MONO-MASTER** control
- **PUSH-PULL** output—8 watts ● **RESPONSE** 50-10000 c/s
- Independent **BASS** and **TREBLE** controls

The well-known **SIMPHONIC Model 2B**, is still available for all applications where simplicity, reliability and moderate cost are important considerations.

See the 2B and our **NEW MODEL 1A** at the **RADIO SHOW Stand 13** or write for details.



MODEL 2B



Recorder House, 48-50 George Street, Portman Square, London, W.1, England

Telephone: Welbeck 2371 (4 lines)

Telegrams: Simsale, Wesdo, London.

Cables: Simsale, London

AN ULTRASONIC SOLDERING IRON


Can be used for soldering aluminium, and other metals that form refractory oxides

THE problem of soldering metals that form refractory oxides has now been overcome.


A new soldering iron, developed by Mullard Ltd., destroys oxide film by ultrasonic stimulation and provides a "clean" metallic surface.

This means that perfect soldering of aluminium, and other metals, can now be achieved without scraping or brushing molten metals. Standard soft solders can be used. And no flux is needed.

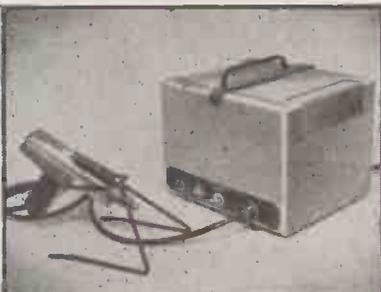A small electronic amplifier supplies the ultrasonic power. Two controls, a mains and a trigger switch, ensure simplicity of operation. Unskilled workers can use the apparatus without discomfort, since the ultrasonic frequency used is inaudible to the human ear. Full information about the Mullard Ultrasonic Soldering Iron—the only commercial model in the world—is available on request.



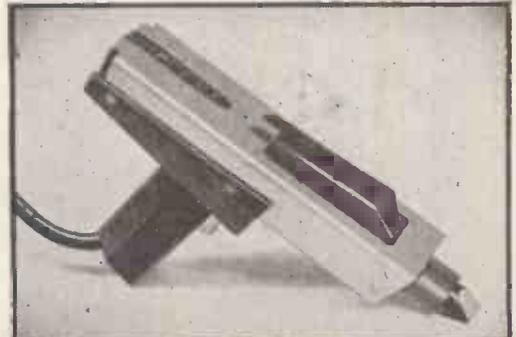The Mullard Ultrasonic Soldering Iron and Amplifier. The unit operates from A.C. mains and is robustly made to suit workshop conditions.



The soldering iron has a nickel silver bit driven by a magnetostriction transducer. The transducer is arranged to run at its natural resonant frequency by a feed-back system. A conventional low voltage winding heats the soldering bit.

Mullard

CONDUCTIVITY EQUIPMENT • POTENTIOMETRIC TITRATION APPARATUS • ELECTRONIC POLAROGRAPHY • TEMPERATURE CONTROLLERS • UNIVERSAL MEASURING BRIDGES • VALVE VOLTMETERS
F.M. SIGNAL GENERATORS • OSCILLOSCOPES


NORTHERN AGENT: F. C. Robinson & Partners, Ltd., 287, Deansgate, Manchester, 3.
MIDLAND AGENT: Hadley Sound Equipments, 72, Cape Hill, Smethwick.
SCOTTISH AGENT: Land, Speight & Co. Ltd., 73, Robertson Street, Glasgow, C.2.
Mullard Ltd., Equipment Division, Century House, Shaftesbury Avenue,
London, W.C.2. Telephone: GERrard 7777



Hear these amplifiers first . . .


PORTABLE BATTERY MAINS BM40

An attractive appearance and unique construction combined with first-rate performance give this instrument a hall-mark of distinction. Peak power 40 watts, 30 watts undistorted. Designed for both A.C. Mains and 12-volt battery operation. Provision for independent electronic mixing of two microphones and one gramophone channel. Built-in vibrator. Special tone control and treble boost and cut. These and many other features make the BM40 the most up-to-date amplifier available.
List price £50.

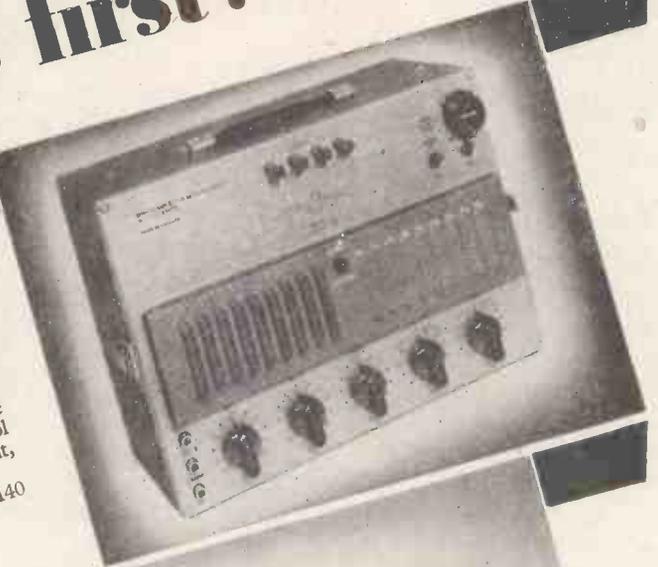

MOBILE CAMPAIGN OUTFIT MA15

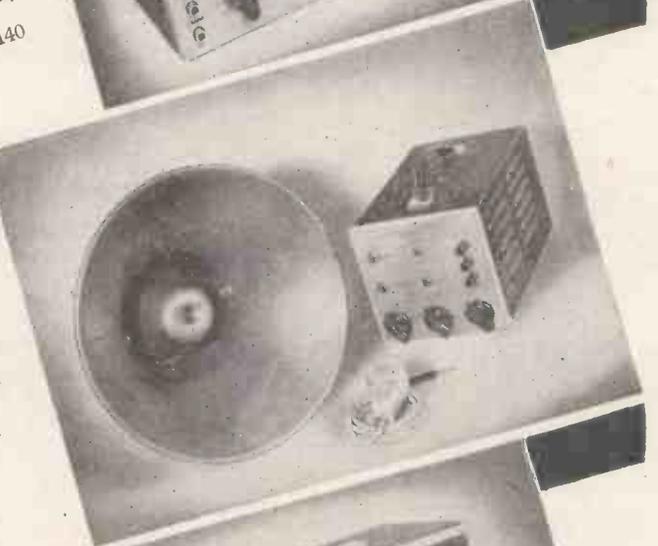An ideal equipment for mobile applications, giving crisp, clear messages. The outfit comprises: 15 watt amplifier for either 6 volts or 12 volts operation; and microphone type M.C.B., and co-axial weatherproof loudspeaker. A gramophone input and battery-saver switch are incorporated.
List price £48 10s.



30 WATT PORTABLE PA 30/B

A 30 watt amplifier for public address men. Inputs for moving coil or ribbon microphones and gramophone. Tone control. Illuminated panel and output signal level indicator. Outputs: 7.5, 15 ohms and 100 volt line. Operates from 200/250 volts A.C. mains, or 12-volt battery when used with battery adaptor unit type LT30. An ideal equipment for P.A. vans, general installations and outdoor requirements. Supplied in a handsome portable case.
List price: PA30/B Amplifier, £40.
LT30 Battery Adaptor, £14



BIRMINGHAM SOUND REPRODUCERS' LIMITED
CLAREMONT WORKS, OLD HILL, STAFFS. TEL.: CRADLEY HEATH 6212/3



Wireless World

RADIO, TELEVISION
AND ELECTRONICS

41st YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.

Editor: H. F. SMITH

SEPTEMBER 1951

In This Issue

EDITORIAL COMMENT	337
A MODERN CRYSTAL SET. By <i>B. R. Bettridge</i>	338
MYSTERY BROADCASTING. By <i>Thomas Roddam</i>	341
RADIO TELEARCHICS	342
EFFICIENCY LINE-SCAN CIRCUITS—2. By <i>W. T. Cocking</i> ..	347
TENS OR TWOS? By " <i>Cathode Ray</i> "	351
RECORDING STUDIO DESIGN. By <i>P. A. Shears</i>	355
NATIONAL RADIO SHOW	361
LETTERS TO THE EDITOR	369
STEREOPHONY ON TELEVISION CHANNELS	371
WORLD OF WIRELESS	372
SHORT-WAVE CONDITIONS. By <i>T. W. Bennington</i> ..	375
MODIFYING "SURPLUS" METERS. By <i>W. H. Cazaly</i> ..	376
MANUFACTURERS' PRODUCTS	379
RANDOM RADIATIONS. By " <i>Diallist</i> "	380
UNBIASED. By " <i>Free Grid</i> "	382

PUBLISHED MONTHLY: Price 2/- (last Tuesday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Ethaworld, Sedist, London." *Annual Subscription:* Home and Overseas, £1 7s. 0d. U.S.A. \$4.50, Canada \$4.00. **BRANCH OFFICES:** Birmingham: King Edward House, New Street, 2. Coventry: 8-10, Corporation Street. Glasgow: 26b, Renfield Street, C.2. Manchester: 260, Deansgate, 3.

VALVES...and their Applications

MINIATURE BATTERY RANGE

OUTPUT PENTODES

Two output pentodes, DL92 and DL94, are available in the Mullard range of miniature battery valves. Both have centre-tapped filaments and can be operated with the two sections of the filament either in series when the L.T. drain is 0.05A at 2.8V, or in parallel when the drain is 0.1A at 1.4V. The filaments are, of course, suitable only for D.C. operation.

Type DL94 is designed for operation with equal voltages on screen and anode, and is the type recommended for normal domestic battery or A.B.C. receivers. Operated with the filament sections in parallel and with anode and screen potentials of 90V, this valve will give an output of 270mW with 7% total distortion for a drive voltage of 3.2 V.

Type DL92 may be operated with either equal or unequal voltages on screen and anode, and is primarily intended for use in miniature all-dry battery receivers, particular attention having been paid in its design to performance at anode and screen potentials of 67.5 V. Under these conditions an output of 160mW is obtainable with the series filament arrangement or 180mW with parallel filament arrangement, the drive voltage in either case being 5.5V.

Greater output can be obtained if the anode voltage is increased to 90V, the screen voltage remaining at 67.5V. In this case the output with series filament connection is 235mW and with parallel filament connection 270mW, again with a signal input of 5.5V.

Other valves in this range include:

DF91 Variable- μ pentode

DAF91 Short grid-base pentode with diode

DK92 Heptode frequency changer

OUTPUT PENTODES DL92 & DL94

RATINGS AND CHARACTERISTICS

	DL92	DL94
Filament		
Series connection		
V_f	2.8	2.8 V
I_f	0.05	0.05 A
Parallel connection		
V_f	1.4	1.4 V
I_f	0.1	0.1 A
Operating Conditions		
Series filament		
V_a	90	90 V
V_{g2}	67.5	90 V
V_{k1}	-7	-4.5 V
I_a	6.1	7.7 mA
I_{g2}	1.1	1.7 mA
g_m	1.4	2.0 mA/V
R_a	8	10 K Ω
V_{in} (r.m.s.)	5.5	3.2 V
P_{out}	235	240 mW
D_{tot}	13	7 %
Parallel filament		
V_a	90	90 V
V_{g2}	67.5	90 V
V_{k1}	-7	-4.5 V
I_a	7.4	9.5 mA
I_{g2}	1.4	2.1 mA
g_m	1.57	2.15 mA/V
R_a	8	10 K Ω
V_{in} (r.m.s.)	5.5	3.2 V
P_{out}	270	270 mW
D_{tot}	12	7 %
Limiting Values		
V_a max.	90	90 V
V_{g2} max.	90	90 V
I_k max.	12	* 12 mA

* 6mA for each 1.4-volt section of the filament.



Reprints of this article together with additional data may be obtained free of charge from the address below.

MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2.



ON LAND



BRIMAR



IN THE AIR



BRIMAR



ON THE SEA



BRIMAR



EVEN UNDER THE SEA



BRIMAR

BRIMAR

VALVES are proving that there's no substitute for *EXPERIENCE*

Brimar experience and Brimar techniques have produced one of the world's finest ranges of replacement valves.

PERFORMANCE PROVED in actual circuits

For Industry . . . the Services . . . for all whose work demands a guaranteed minimum life and complete reliability—


NOW is the time to BRIMARIZE!

Standard Telephones and Cables Limited FOOTSCRAY, KENT



high fidelity MICROPHONES

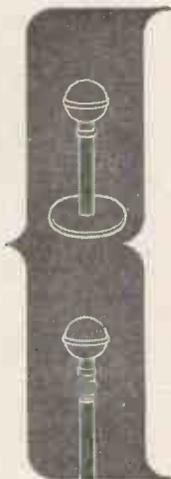FOR PUBLIC ADDRESS : RECORDING : AMATEUR RADIO



TYPE MIC 22

This model incorporates the famous Acos "Filtercel" insert giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 cps. The microphone is vibration and shock proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head:

MIC 22-2 is supplied as a complete unit incorporating an attractive desk stand with cable side entry.

MIC 22-1 is for fitting to any British or American type standard floor stand and can also be used as a hand microphone.

PRICE £6 · 6. (Either Model)


TYPE MIC 16

Incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 cps. Performance is unaffected by vibration or shock and low frequency wind noises. As in the case of the MIC 22, two alternative mountings for the MIC 16 head are available:

MIC 16-2 is a complete desk stand unit with side cable entry.

MIC 16-1 is ready for fixing to either British or American type floor stands by means of a knurled ring.

PRICE £12 · 12. (Either Model)

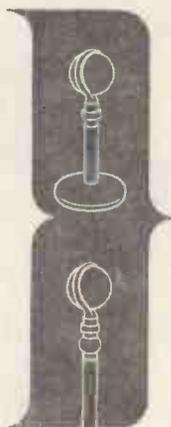

COSMOCORD LIMITED


ENFIELD, MIDDX.

P.S. As you probably know, we make good pick-ups too, in large numbers. But even larger numbers of people want them. Although, therefore, we expect to be producing still more and still better pick-ups soon, just now we don't advertise pick-ups at all.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

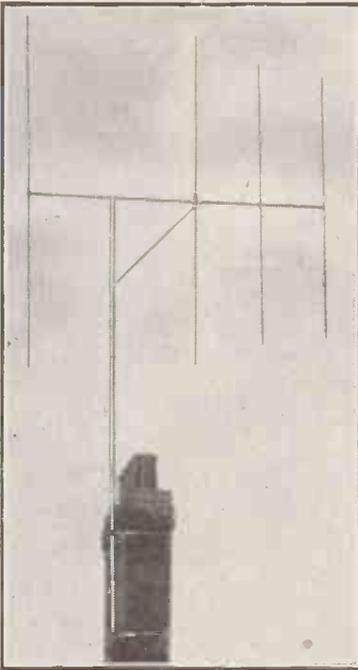General Characteristics of Parasitic Element Arrays in Relation to Television Aerials.



"Belling-Lee" "Multirod" mounted on a 14' mast.

Theoretical considerations of the action of parasitic elements in increasing the gain of a dipole may be summarised as follows:—

- (1) There is no known aerial array or system (theoretical or practical), for a given compactness, which can give a gain or directional response comparable to the simple parasitic element array as typified by our "H" and "Multirod" models.
- (2) The maximum gain can only be secured at one frequency, and the closer one designs for that maximum, the more critical is the response on either side of the design frequency.
- (3) The maximum gain will be obtained with close spacing (around $1/10$ wavelength) and a parasitic element shorter than the fed dipole, and which acts as a director instead of a reflector.
- (4) Under these conditions the performance will fall rapidly on either side of the design frequency. If the design

frequency is centred on a Television channel the response on the sound channel (which is always lower in frequency) will be much worse than if the channels were reversed.

- (5) Under the conditions stated in (3) impedance matching problems are raised. The impedance at resonance is low (15 ohms and less) and the impedance becomes very reactive slightly off tune. Thus, what one gains by optimising the dimensions may readily be lost in the process of matching, particularly when the load impedance (any make of T.V. set) is not standardised and varies considerably from model to model.
- (6) Under the conditions stated in (3) the aerial elements must be very rigid or considerable picture flutter will occur in gusty winds.
- (7) Under the conditions stated in (3) manufacturing and assembly tolerances must be closer and may result in a higher proportion of material rejects.

The conclusion which must be drawn and which we must reiterate is that the general problems arising out of manufacture and subsequent use will be least when wide spacing ($\frac{1}{4}$ wave) is employed. As compared with close spaced parasitic elements they are:

- (a) Easier to match and fairly tolerant of fortuitous mismatch.
- (b) Comparable in gain on both sound and vision channels.
- (c) Less susceptible to gust flutter.
- (d) Less susceptible to proximate conductors.
- (e) Easier to manufacture.

A strong case for closely spaced parasitic arrays might be made for single channel (CW) working where all the variables are under the designer's control, e.g., mast, material, type of feeder, proximity of other conductors, receiver input impedance, etc.

"Winrod" Aerial.

This was designed to be fitted on a window-sill. We have heard of people fitting them on the gutter board to take advantage of extra height, but lately, again from a coastal town, we learn that a considerable number have been fitted to chimney stacks.

Our first query was "How does the bracket stand it?" but appar-

ently it does, and the wind really blows on the coast. Let us hasten to add that we do not exactly recommend the practice, as the aerial is just not designed for it, and we certainly could not be held responsible for accidents.


Rain Static?

Precipitation Static?

"Coronette" Static Discharger

Yes, this is a hardy annual. We had a visit from a member of a prominent Scarborough firm who volunteered the information that his company never installed a "Belling-Lee" "Skyrod" vertical aerial without fitting one of these dischargers. They really do work in that area. We have heard the same thing from one of the best known dealers in the Bristol area and, perhaps with less emphasis, from most parts of the country. In fact, to our knowledge, there are not many districts where they will not justify their use; one of these is in the North-West, round Whitehaven.

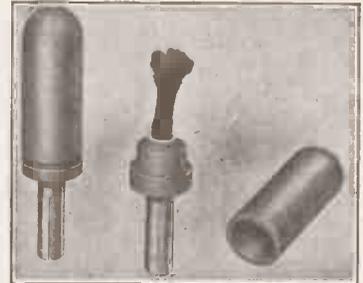We claim that the fitting of a "Coronette" will reduce noise by about 40 db. The residual noise may even then, in certain circumstances, be sufficient to spoil the programme.



"Coronette" Corona Discharge Limiter.


In controlled experiments carried out by our Research Department at Enfield, the programme from the Brookmans Park Transmitter has been completely blotted out by this form of interference, but on switching to an aerial fitted with a "Coronette" no interference was apparent. This does not mean that reception from a more distant station would necessarily be satisfactory in similar conditions.

We would welcome correspondence on this subject as we feel there is a lot to be learned.

See our announcement on Page 72.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDD., ENGLAND

A QUESTION FOR DESIGNERS

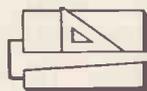

**How will
tomorrow's
battery radio
be different?**



Circuits progress ; new cases will evolve from new materials and techniques — but the one outstanding feature of tomorrow's battery radio is here today —

V E N N E R *Lightweight Accumulators*

One third the weight and half the size of standard accumulators of comparable capacity, these revolutionary miniature storage batteries maintain a steady 1.5 volt output on load throughout their discharge period.

Thus they eliminate the need for constant replacement due to voltage drop, which is the failing of all other conventional L.T. batteries.

In addition, Venner Lightweight Accumulators are completely non-spillable, are unharmed by high charge and discharge rates and may be left in discharged condition without damage.

The services of our technical department are freely at your disposal in investigating the many operational advantages of these accumulators.

For full technical data please write for leaflet VAO11/WW

VENNER

ACCUMULATORS LTD

Distributors for London and Home Counties :—
DAVID & SOLF LTD., 173, SLOANE STREET, S.W.1. Tel. : SLOane 8532

KINGSTON-BY-PASS, NEW MALDEN, SURREY. Telephone: MALden 2442 (6 lines)

3-WAY MIXER & peak programme meter

for recording and large
sound installations etc.



One milliwatt output on 600 ohm line (.775 V) for an input of 30 microvolts on 7.5—30 ohm balanced input. Output balanced or unbalanced by internal switch. The meter reading is obtained by a valve voltmeter with 1 second time constant, which reads programme level, and responds to transient peaks.

Calibration in 2 db steps, to plus 12 db and minus 20 db referred to zero level. Special low field internal power packs supplies 8 valves including stabilising and selenium rectifier, consumption 23 watts.

Manufactured by:

VORTEXION LIMITED

257-263, THE BROADWAY, WIMBLEDON,
LONDON, S.W.19

Telephones : LIBerty 2814 & 6242-3

Telegrams : " Vortexion, Wimble, London."



TERMINALS
insulated, sealed and glass seal.

FUSES & FUSEHOLDERS
baseboard, panel, neon indicating and miniature.

PLUGS & SOCKETS
single, coaxial, multi-sealed and high tension.

SCREENECTOR
range of 1-2-3-way screened plugs and sockets.

INTER-CHASSIS CONNECTORS
(Unitors).

VALVEHOLDERS
(B7G, B8A, B9G, B9A, D.I. Diode) and High Voltage.

INTERFERENCE Suppressors
to meet the Wireless Telegraphy Bill.

PREVIEW OF "BELLING-LEE"

STAND No. 64 AT THE NATIONAL RADIO EXHIBITION

Readers of the "Belling-Lee" page who are visiting the National Radio Show will find us on Stand No. 64 in the centre of the hall. The "Multirod" surmounting the section of a "Skytower," which reaches up from the centre of the stand, offers an easy landmark.


A brief mention of some of the exhibits is made below:—



VALVE HOLDERS

Both the B7G (Belling-Lee L.718) and the B9A (L.720) are made with fixing flanges or skirts to take the standard screening cans. They are intended to fill the gap between the cheaper types and the very expensive P.T.F.E. holders but are likely to prove too expensive for cheaper commercial receivers. The insulators are moulded from high-quality nylon filled powder, and a new flat-type screen is incorporated giving the desired screening between contacts; this may be cut down if necessary for application where space is limited.

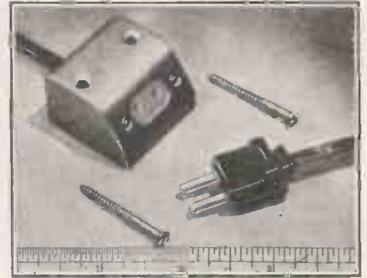The contacts are made of silver-plated beryllium copper differentially hardened to obtain the best possible contact pressure. The solder tags remain annealed and are tin dipped for ease of soldering. Other types exhibited will be the B8A (L.620), B9G (L.500), high voltage, duodecal, etc. . . .



PLUGS AND SOCKETS

A very comprehensive range will be exhibited including such items as single, coaxial, multi and sealed connectors, also a special range of screened 1, 2 and 3 pole connectors, together with aerial outlet boxes such as the one illustrated above. This is the "Belling-Lee" L.739, which was produced for use with plug L.733/P, also illustrated, a new inexpensive plug, specifically designed for unscreened balanced twin feeder as used for television or shortwave reception. The twin feeder (L.336) is loaded simply by pinching the wires in the spills provided and the ingenious black polythene moulding folds into shape where it is held together by means of the two ball-headed studs.

We are also showing the newly developed coaxial plug L.734/P. This replaces 3 others, and accepts coaxial cables of outside diameters from $\frac{5}{16}$ " to $\frac{3}{8}$ " including 50 ohm.

OTHER ITEMS OF INTEREST INCLUDING TELEVISION AERIALS

A particularly interesting section is devoted to radio interference suppressors, both industrial and domestic, together with motor vehicle ignition suppressors, a windscreen wiper suppressor designed for use on public transport vehicles using 24-volt electrical systems.

One of our mobile research units will be available for inspection in the electronic attractions section. These vehicles enable us to carry out on-the-spot investigations into the behaviour of television aerials,

speedily and efficiently.

We will be showing an extensive range of television aerials, both outdoor and indoor types. These include the "Multirod" 4-element array for "fringe" area reception, the well-known "Viewrod" 'H' and simple dipole types with a variety of mountings, "Doorod" and "Viewflex" indoor models, and the "Veerod" loft mounting aerial. Our Sales engineers, who are familiar with the possibilities and peculiarities of your location, will be available to assist you in your

problems and answer your queries. Amongst the broadcast aerials on view will be the "Skyrod," an 18ft. vertical aerial with or without "Eliminoise" anti-interference matching transformers, the "Winrod" an easy-to-fix window-sill aerial, and the "Carod," a telescopic, rattle-free motor-car aerial for scuttle mounting.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDLESEX, ENGLAND

CHOOSE RADIO & TELEVISION
WITH THE WORLD'S FINEST
TECHNICAL BACKGROUND . . .

When you choose a Marconiphone you choose a set with a real 'pedigree' going back to the very beginning of Radio. So if you want to be sure of reliable, high standard reception, you can always confidently choose *Marconiphone.*




Model VC. 56DA (London)
 Model VC. 76DA (Midlands)
 Model VC. 86DA (Northern)
 Corner Console with 12" tube.
 £93. 15. 0 (Tax Paid)



Model VT. 56DA (London)
 Model VT. 76DA (Midlands)
 Model VT. 86DA (Northern)
 Table Model with 12" tube.
 £79. 15. 0 (Tax Paid)



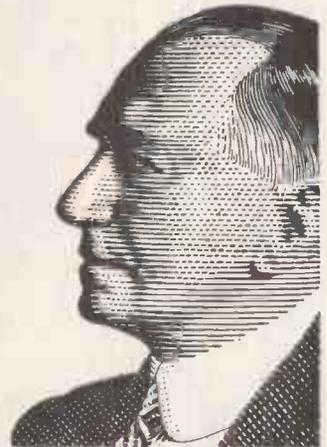
Model T. 29A
 5-valve, 3-waveband Table
 Receiver for AC mains.
 Price on application.



MARCONIPHONE

THE GREATEST NAME IN RADIO —

G. Marconi

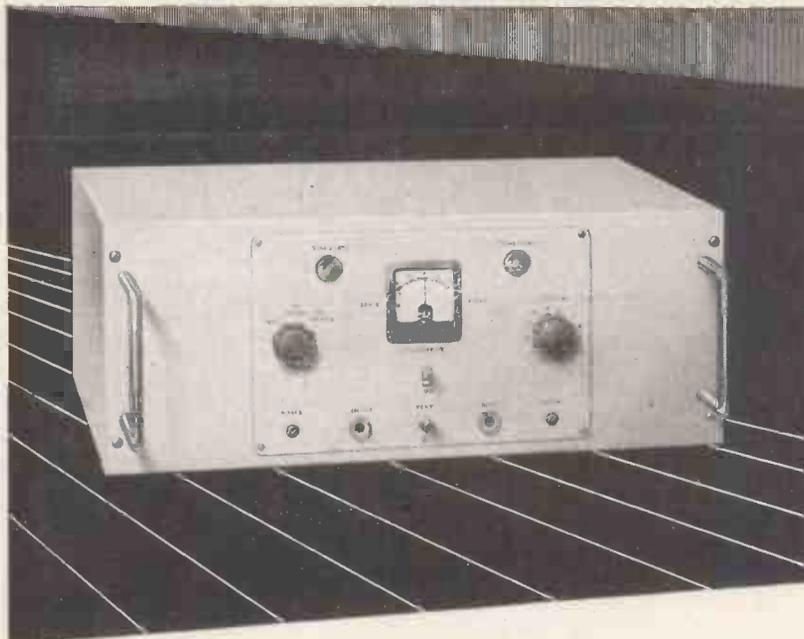

RECORDING UNIT (HU. 11)

- ▶ For use with any normal communications receiver.
- ▶ Accepts Frequency Shift or On/Off telegraphy signals.
- ▶ Visual tuning indicator for Frequency Shift reception.
- ▶ Outputs: Double current into high or low resistance.
- ▶ Supplies: 110 or 200-250 volts, 50 c/s mains, 75 watts consumption.

MARCONI COMMUNICATION SYSTEMS

SURVEYED • PLANNED • INSTALLED • MAINTAINED

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD • MARCONI HOUSE • CHELMSFORD • ESSEX



ROLA SPEAKERS

DESIGNERS USE THEM . . .
DEALERS CHOOSE THEM . . .


*Because the CUSTOMER
Wants the Best!*



ROLA

Manufacturers' Enquiries to :—
ROLA CELESTION LTD.
FERRY WORKS, SUMMER ROAD, THAMES DITTON, SURREY
(Emberbrook 3402-6)

SEE US AT EARLS COURT—**STAND 39**

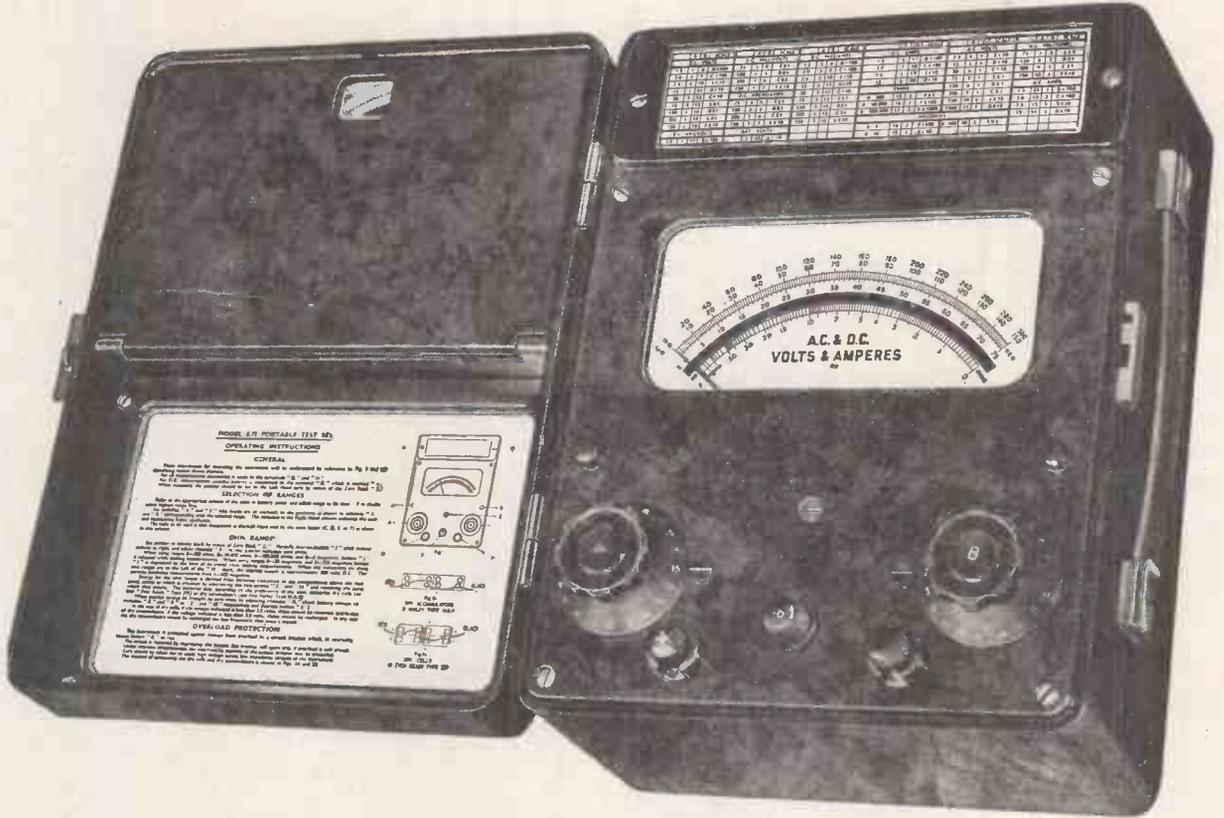

The
WESTON
S.75
 Multi-Range
 Test Set

53 Ranges with Rotary Switch Selection

This uniquely comprehensive Test Set has 53 ranges for measuring A.C. and D.C. current and voltage, resistance and insulation. It is completely self-contained with internal batteries to provide power for the ohms ranges and self-contained power pack for insulation measurement at 500v. Selection is carried out by two 20-position switches. A fully-protective safety device is fitted and is operative for forward or reverse overload. The 150-division 6in. scale is uniformly divided and is fitted with an anti-parallax mirror. The set is enclosed in a handsome bakelite case and fully complies with B.S.S. No. 89, covering first-grade instruments. Full details of the ranges covered, and of the complete specification, will gladly be supplied on request.

SANGAMO WESTON LIMITED
ENFIELD, MIDDLESEX

TELEPHONE: ENFIELD 3434 (6 LINES) AND 1242 (4 LINES)
 TELEGRAMS: SANWEST, ENFIELD

BRANCHES: .

Glasgow, Manchester, Newcastle-on-Tyne, Leeds,
 Liverpool, Wolverhampton, Nottingham, Bristol,
 Southampton and Brighton.

On with the Show!

COME...

Come and see us at the Radio Show. You'll find us at Stand 60, ready to welcome old friends and new. (If this is not possible, we shall be happy to send you descriptive literature on any of our products in which you may be interested).

SEE...

See the complete range of Stentorian extension speakers and chassis units and other famous Whiteley components.

HEAR...

Hear the celebrated Concentric-Duplex High Fidelity Reproducer, combining exceptionally high quality with great power handling capacity.



See and hear the "VIEW MASTER"—the Television set that anyone can build

Stentorian


SEE YOU AT
STAND 60

EXTENSION SPEAKERS

WHITELEY ELECTRICAL RADIO CO, LTD · MANSFIELD · NOTTS

The Greatest Advance towards Perfect Reproduction The NEW "TONE COLOUR" UNIT Plus the

AMAZING

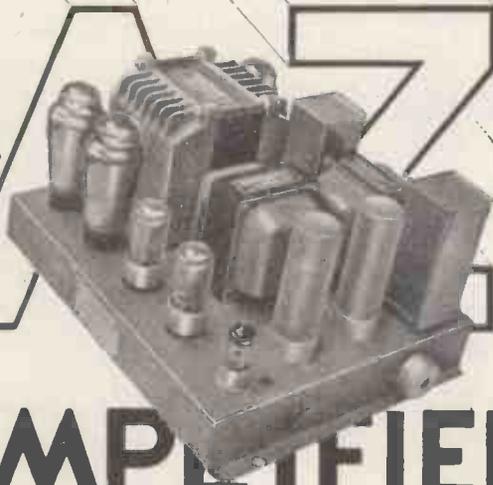

TYPE A-Z

£32.10.0
Complete

AMPLIFIER

SOUND SALES LIMITED

DEMONSTRATIONS at our London Showroom:


LLOYDS BANK CHAMBERS, 125 OXFORD STREET, W.1 (ENTRANCE IN WARDOUR ST.) Telephone: GERrard 8782
(Works: West Street, Farnham, Surrey Telephone: Farnham 6461)

CRAFTSMANSHIP

'I can most certainly say at this stage that the workmanship and finish are of a quality which I have never before encountered in the radio industry, despite the fact that my association with the industry in one capacity or another extends back over 27 years. I think you are to be congratulated all the more on this achievement in view of the increasing tendency nowadays towards inferior workmanship and design.'

Part of a letter from a purchaser who is a very well-known engineer and whose identity is known to the Editor of "Wireless World."

"POINT ONE" AMPLIFIERS

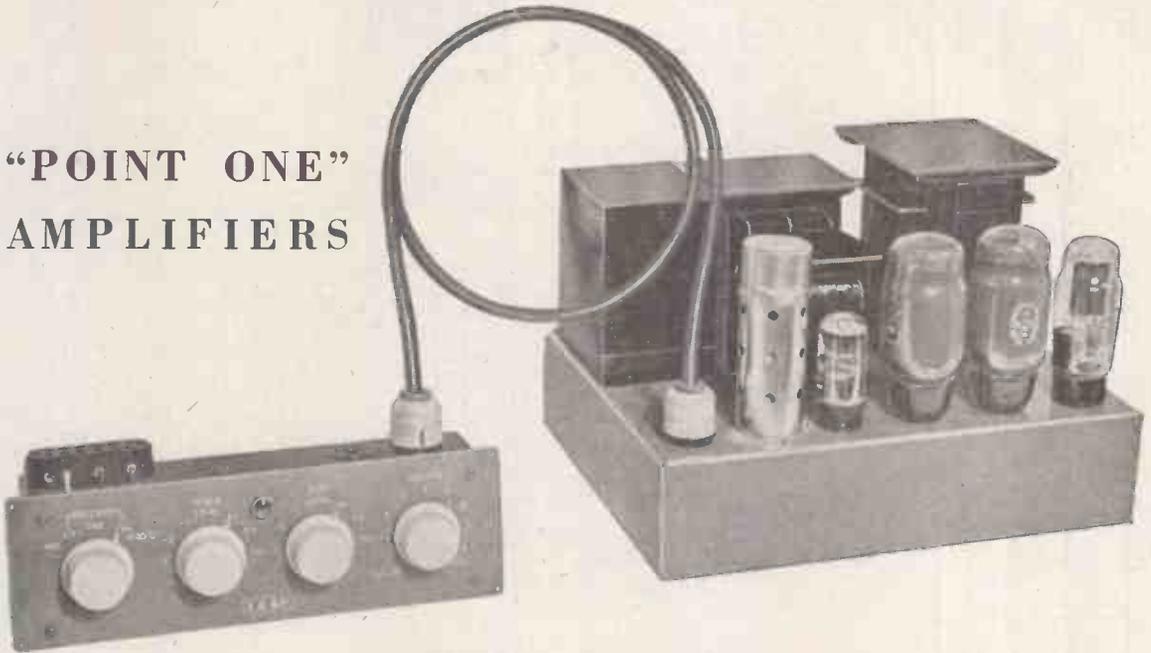

**NEW RC/PA/U
REMOTE CONTROL PRE-AMPLIFIER**
PRICE : 9 GUINEAS

**"POINT ONE" TL/12 12 WATT
TRIPLE LOOP FEEDBACK AMPLIFIER**
PRICE : 27 GUINEAS

APPLICATIONS

1. For laboratory use as a stabilised-gain audio-frequency power amplifier.
2. For the highest possible standard of disk recording.
3. For the highest possible quality of reproduction from Pickup, Radio, Microphone, Film and Magnetic Tape.
4. For use as a driver amplifier in the speech modulator chain of broadcast transmitters.
5. Used with the RC/PA/U pre-amplifier and the best available complementary equipment the TL/12 power amplifier gives to the music-lover a quality of reproduction unsurpassed by any equipment at any price. It is designed in a form so that the power amplifier can be housed in the base of a cabinet and the small pre-amplifier mounted in a position best suited to the user.
6. The pre-amplifier and the power amplifier are drilled for bolting together to make a single transportable unit. A cover with a carrying handle is available for this unit, and assembled in this form the equipment is particularly suitable for lecturers and for Public Address work where very high quality of reproduction is essential.

The New B.B.C. Monitor loudspeaker uses a Leak TL/12 amplifier. 731 TL/12 amplifiers were ordered by broadcasting authorities during 1950, including :—

The British Broadcasting Corporation.

The South African Broadcasting Corporation.

The Swedish Broadcasting Corporation.

The Swiss Broadcasting Corporation.

The Italian Broadcasting Corporation.

The "POINT ONE" TL/12 and RC/PA/U AMPLIFIERS are built to a tropical specification and they are distributed throughout the world. During 1951 to date (May, 1951) orders totalling over 2,000 have been received from the U.S.A. for RC/PA/U and TL/12 amplifiers for high quality radiogramophone reproducers for the home.

FOR COMPLETE DETAILS APPLY TO YOUR LOCAL DEALER OR WRITE TO DEPT. W.

H. J. LEAK & CO. LTD. (Est. 1934)


BRUNEL ROAD · WESTWAY FACTORY ESTATE · ACTON, W.3

Phone : SHEpherds Bush 1173, 1174.

Telegrams : Sinusoidal, Ealux, London.

Foreign : Sinusoidal, London.

ELPREQ PAGES

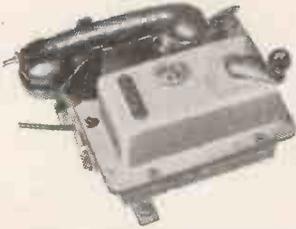


EX-ROYAL NAVY SOUND POWERED TELEPHONE

These require no batteries, and will go for long periods without attention. Complete with generator and sounder which gives a high pitched note, easily heard above any other noise. Also fitted with an indicator lamp which in quiet situations can be used instead of the sounder, or where several phones are used together will indicate which one is being called. Size 7½ in. × 9 in. × 7½ in., wall mounting, designed for ships' use, but equally suitable for home, office, warehouse, factory, garage, etc. Price 37/6 each, plus 3/6 carriage.

TRIP SWITCHES




In addition to the many industrial uses, these trip switches are useful additions to your laboratory and workshops. Fitted into the power circuit like a normal switch they can in the first place be used to control the power outlets and when as often happens a short circuit occurs, instead of the fuses blowing, the switch will simply trip and will not close again until the short is cleared. The actual current at which the switch trips can be adjusted. Price 12/6.

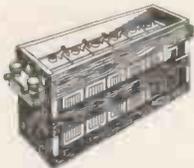

12-CELL ACCUMULATOR

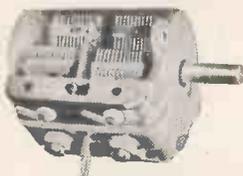This accumulator can be coupled up to give 24 v. with all cells connected in series or 12, 6 or 2 volts by series parallel arrangements. They were originally made for the Admiralty by a leading manufacturer, have never been filled, and are in excellent condition. Each is contained in a wooden crate as illustrated. Price 27/6 each. Postage and insurance 5/-.



2-GANG .00035 TUNING CONDENSER


Complete with perspex dust cover and built-in trimmers. Super job for tuning personal receivers, 8.6 each.

MAINS/BATTERY PORTABLE

Ultra modern cabinet, highly suitable for making up an all-mains and/or all-dry battery receiver. Cabinet dimensions, 7½ in. deep and 10½ in. high × 12 in. wide. Imitation crocodile cabinet with back and wooden platform, battery dividers, inner front drilled for three controls, and handle, 22/6 complete.

Ivory Fret with Perspex Window, loud speaker louvres and turning scale, 5/6. Frame Aerial wired for long and medium wave with plug board and tag strip, 5/6. Unwired, 2/6. Metal Chassis punched out and with loudspeaker cut out, 5/6. Assembly for holding dial and lamps, 1/9. Matched Knobs, set of 3, 2/-.

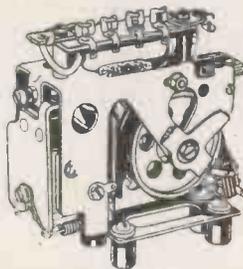Or all items unwired frame aerial, 38/6; wired frame aerial, 42/6. Wiring diagram and constructional details, 2/6. All components available (total cost of set should not exceed £7/10/-). For details, see constructional data.



REMOTE CONTROL

With only one pair of wires and a simple push button you can select any one of four stations without leaving your armchair. This is just one of the many applications of our impulse relay, the price of which is only 3/9. There are many other purposes to which it can be put we will supply a booklet of circuits for 1/9 post free. The action of the impulse relay is as follows:—current to the solenoid causes the ratchet wheel to rotate one notch per impulse, a built in automatic switch keeps the impulses coming in until they are switched off by secondary contacts which operate

four times per complete revolution. Shorting the secondary contacts starts the impulses again. Attached to the ratchet wheel is a four way single pole switch. We are sure that there are many new applications for this relay and we offer prizes for new ideas.

TIMED SWITCH MECHANISM

This comprises a beautifully made 8 day jewelled miniature clock or watch movement, which operates two 2 amp contact switches. These switches also are quite suitable for mains use. There are two calibrated dials, one contact adjusts in ¼ hour intervals up to 6 hours, the other one in one hour intervals up to 36 hours. The whole is really precision made to stringent M.O.S. specification. The size of the complete switch mechanism is 3½ in. long and 2½ in. across. Or if you wish, the miniature clock movement can be removed completely and this then measures only 1½ in. × ½ in. The price of the complete timed switch is 27/6. These are brand new still in the manufacturers original sealed boxes.



SPECIAL PERSONAL SET OFFER

Resulting from the changeover of a famous manufacturer to important work, we are able to offer practically all the parts for the really neat personal radio illustrated.

The most important thing of course, is the cabinet and for this we can offer a complete kit of parts, which includes cream plastic lid, base and escutcheon, cracked metal body and all accessories such as knobs, hinges, lid arm and clips, etc.

Price 22/6, but remember this brings the complete cabinet size 7 × 4 × 3½ in. Other items available are:—

Metal Chassis. Five-part assembly comprises the main chassis and sections for holding the batteries and the loudspeaker. Price 4/6. Ditto with four B7G valve holders already riveted in their correct positions. Price 7/-.

Frame Aerial, 3/6.

Oscillator Coil, 3/6.

I.F. Transformers, Wearlite Midget type 400B, 15/- pair.

Volume Control, 1 meg. Midget, 3/6.

Speaker, Midget Plessey 3 in., 14/6.

Output Transformer to match, 5/-.

On/Off Switch, lid operated, 1/6.

Resistors, miscellaneous, total 8, 4/-.



Condensers, miscellaneous, total 9, 4/6.

B7G Amphenol Valve Holders, 8d. each.

Tuning Condenser, 8/6.

Assembly Instructions, including wiring diagram and alignment data 2/6.

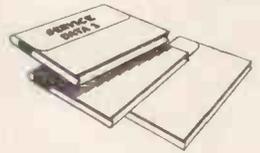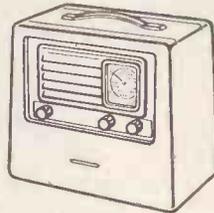Note.—All these parts are offered separately. Valves required are IR5, IT4, IS5, 3S4 or 3V4, all available at low prices, send for our current valve list.




SERVICE DATA

100 service sheets, covering British receivers which have been sold in big quantities, and which every service engineer is ultimately bound to meet. The following makers are included: Aerodyne, Alba, Bush, Cossor, Ekco, Ever-Ready, Ferguson, Ferranti, G.E.C., H.M.V., Kolster Brandes, Lissen, McMichael, Marconi, Mullard, Murphy, Philco, Phillips, Pye, Ultra. Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price £1 for the complete folder.

Our folder No. 2 consists of 100 data sheets covering most of the popular American T.R.F. and superhet receivers "all dry" etc., which have been imported into this Country. Names include Sparton, Emmerson, Admiral, Crossley, R.C.A. Victor, etc. Each sheet gives circuit diagrams and component values, alignment procedure, etc., etc. Price for the folder of 100 sheets is £1. Post free.

MISCELLANEOUS BOOKLETS

These give circuit diagrams and details of Ex-Government receivers and equipment. In practically all cases the information has been extracted from official publications. Separate booklets for each piece of equipment. Booklets available covering the following:—R1155, R208, R109, TR1196, TR18, BC348, BC312, R1116, R107, R103, BC221, BC342, Pre-Amp. from RF27, Pre-Amp. from Unit 208A, T.V. Receiver from 14-metre superhet for London or Birmingham, T.V. receiver from 3170, etc. T.V. receiver from 194 strip. Dual band T.V. receiver. Price of any of these booklets is 1/6 each—all post free.

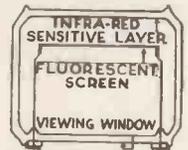

"SNIPERSCOPE"

Famous wartime "cats eye" used in conjunction with a lens system and h.t. for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. It follows that as light from an ordinary lamp is rich in infra-red these cells will work: burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Here then is a golden opportunity for some interesting experiments price 9/6 each, or six for 52/6. Data will be supplied with cells if requested.

HIGH VOLTAGE CONDENSERS

We have many types in stock, one special one at a low price is .01 mfd. 5 k.v. in 5 in. All-can, 2/6.


TWO-VOLT ACCUMULATORS

Made for the Forces by one of the most famous firms in the world. 15 amp.-hour size approx. 6in. x 1 1/2in. square in ebonite case, pre-charged, only need filling with acid, 5/9 each, plus 9d. post and insurance. Six or more post free.



LAMP HOLDERS

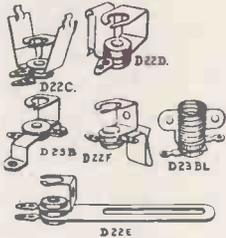We carry a large assortment of dial lamp holders. Price 6d. each. Order by list numbers.



15 AMP. DOUBLE POLE ROTARY SWITCH

Made by the famous Diamond H Company, it is complete with pointer knob. Price 5/6.



ALUMINIUM TUBE (CONDUIT)

1/2in.—ideal for all lighting work and for making T.V. aerials, etc. Price 1/6 per foot.




AERIAL STRAINERS

Brass body, price 1/6 each.




EXTENSION SPEAKER IN METAL CABINET

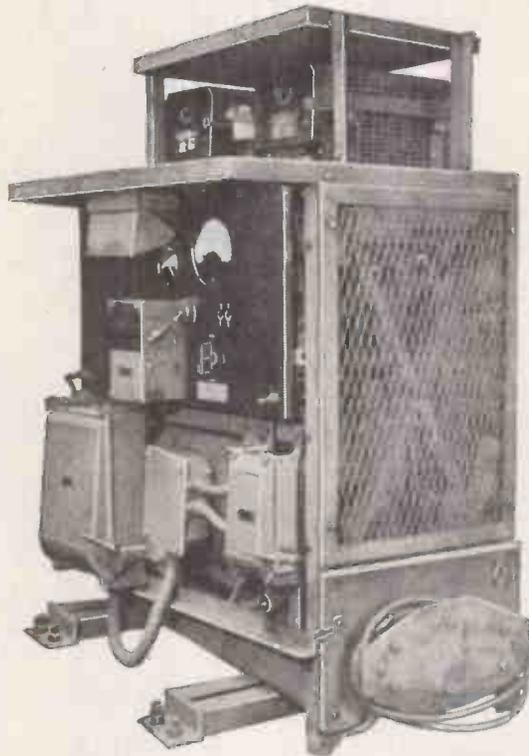This has a 6in. P.M. Goodman's Speaker, heavy magnet type, complete with an output transformer. It is fitted in grey steel case with perforated front and back, ideal for P.A. work in canteens, clubs, etc., 27/6 each.



10 kVA ALTERNATOR SETS

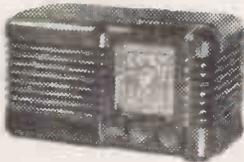Complete electrically with all switch gear, voltage regulators, frequency meters, etc., etc. These have two circuits, one giving 10kVA. at 230 v. 50 cycles, the other giving 1 1/2 kVA. 230 v. 500 cycles. Complete with 'Vee' belt pulley. Can be driven by lorry engine, oil engine, etc., the speed of which is not important. Unused but somewhat storage soiled. Price £65, carriage extra.



"OCCASIONAL 4 CABINET"

Attractive bakelite cabinet, size 12in. x 5in. x 6in., suitable for making a T.R.F. or superhet receiver. Price with back 17/6, in walnut, green or ivory. Post and insurance 2/6.

PUNCHED METAL CHASSIS T.R.F. for three valves and rectifier, 5/6. **ENGRAVED GLASS DIALS** 16-50 and 180-550 metres, 2/6. 180-550 and 800-2,200 m., 2/6. Dial back plate, 2/6. **COILS T.R.F.** 180-550, 800-2,200, 5/6 per pair. Superhet 16-50, 180-550, 800-2,200 metres, 10/6 per set. **CORD DRIVE ACCESSORIES** Drum 2 1/2in. dia., 1/6. Driving head, 1/6. Double Pointer, 4d. Spring, 3d. Nylon Cord, 6d. per yard. A set can be built into this cabinet for less than £6, constructional data, 1/6.


6-VOLT AMERICAN HEAVY-DUTY BATTERIES

Made by one or other of the most famous American battery companies. For reliability and long service between charges these are in a class of their own. Capacity rating is 140 amp.-hour. We have a limited quantity of these batteries available, unused—in fact they have never been filled with acid, and the price is £5/10/-, carriage extra at cost depending upon your locality.



SPRAY GUN

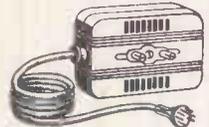Hand operated, ideal to put the finish on a good chassis, and for respraying valves, etc. (completes the perfect job). Price 15/6, complete with instructions, plus 9d. postage.



POWER PACK FOR ALL-DRY RECEIVERS

Output 90 v. H.T. and 7.5 v. L.T. using metal rectifiers. Fitted into bakelite case, size only 3 1/2 x 2 1/2 x 1 1/2, complete with flex and mains input plug. Suitable for A.C. or D.C. mains. Price 19/6

BREAK-DOWN UNIT

At present-day prices the spares in this unit would cost at least £5. Here is a list of the main contents:

- 3 two metre coils;
 - 3 tuning condensers, split-stator type;
 - 4 two-watt carbon resistors, useful values;
 - 1 tapped 20 watt resistor, vitreous covered;
 - 6 paper condensers, .05 mf. 1,000 v. working.
 - 3 paper condensers, .1 mf. 1,000 v. working;
 - 2 H.F. chokes;
 - 4 paper condensers, .1 mf. 450 v. working;
 - 2 paper condensers, .15 mf.
 - 5 bakelite moulded mica condensers .001;
 - 1 paper condenser, .01 mf. 3,000 v. working;
 - 24 rubber grommets, assorted sizes;
 - 6 resistors, 1 watt, all useful values;
 - 6 resistors, 1/2 watt, all useful values;
 - 40 resistors, 1/4 watt, all useful values;
 - 40 silver mica condensers assorted values, including: 10, 15, 20, 40, 50, 100, 150, 300, and 500 pf. types;
 - 4 English octal valve holders;
 - 2 English 5-pin valve holders
 - 1 E.F.50 type valve holder;
 - 3 diode valve holders;
 - 1 louvered casing, size 12 x 7 x 4in.;
 - 1 heavy metal chassis size 12 x 7 x 2in.;
 - 8 condenser clips, assorted sizes.
- Also an assortment of nuts, bolts P.K., self-threading screws, tag boards, chassis mounting tag connectors, screened grid caps, plain grid caps, levers, rollers connecting rods, output sockets, etc., etc. **ALL THIS COLLECTION OF PARTS FOR 6/6** only plus 1/9 postage and packing.

CLEAR PERSPEX PANELS Size 5 1/2in. long, 3 1/2in. wide, and a little over a 1/2in. thick. Price 1/6 per panel.

Orders under £2 add 1/6, under £1 add 1/- Postable items can be sent C.O.D., additional charge approx. 1/- . List 6d. All post orders to Ruislip. Early closing days: Wednesday, Ruislip; Saturday, City. Telephone: Ruislip 5780.




PRECISION EQUIPMENT (2)

152-153 FLEET STREET, E.C.4.

42-46 WINDMILL HILL, RUISLIP MANOR, MDX.


ELPREQ PAGES

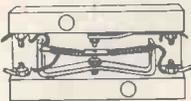

REPLACING THE U.U.8


You can overcome the shortage of high current indirectly heated rectifiers by using a Thermal Delay Switch. You simply connect this across the heaters of a directly heated rectifier such as FW 4/500 and the H.T. will not be switched on until the other valves have had ample time to warm up. The delay switch is as illustrated, with the addition of a protective cover, with the heater voltage is 4, but of course this can be used on higher voltages with a limiting resistor.

RELAYS


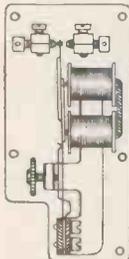


Extra light weight extra sensitive for high speed or radio control work, weight only 1 1/2 oz., closes on 2 mA., solid, platinum change-over contacts, adjustable pressure. Price 13/6.

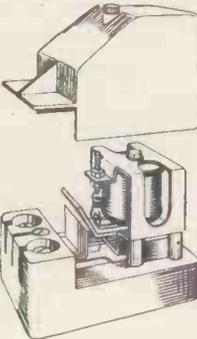Totally enclosed in bakelite, this relay has a 24 v. coil but can of course be rewound for mains operation. Its contacts are suitable for breaking 20 amps. Price, 4/6, 48/- doz.



Post Office types. Upright mounting, prices as follows: sensitive types with coil resistances of 2,000 ohms and over with 1 pr. of contacts 7/6, with 2 pr. of contacts, 8/- then 6d. extra per pair of contacts. Medium sensitivity type 1,000 ohms and over with 1 pr. of contacts, 4/6, extra contact as above. Low voltage types coil resistances of 100 ohms and over with 1 pr. of contacts, 3/6, extra contacts as above.

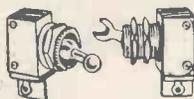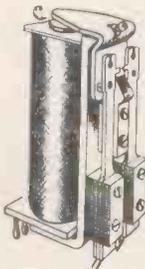


TOGGLE SWITCHES

Meta! body standard size, made by our leading maker. Available with round dolly or with special V cut dolly. State which type when ordering. Price while stocks last only 1/6 each.

PLUGS & SOCKETS

SOCKET STRIPS. Paxolin mounted.

Two socket engraved L.S. 6d. each. Bin C16B.
Two socket engraved A.E. 6d. each. Bin C18A.
Two socket engraved P.U. 6d. each. Bin C19A.
Two socket engraved Dipole 6d. each. Bin C19B.
Two socket plain. 5d. each. Bin C18B.
Three socket engraved DIP and E. 9d. each. Bin C16D.
Three socket engraved A1, A2 and E. 9d. each. Bin C19D.
Four socket engraved A.E. Pickup, 9d. each. Bin C19E.
Four socket engraved P.U. Ext. L.S. 9d. each. Bin C16E.
Five socket plain. 9d. each. Bin C16C.

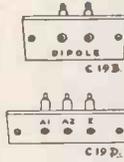

3 PIN PLUG AND SOCKET

Very useful for connecting up gramophone pick-ups, extension loudspeakers, etc. We can offer this at a really knock-out price, namely 8d. per pair.




TELEPHONE JACKS AND PLUGS

Jack Plugs, bakelite, 7d. each. Bin D31A.



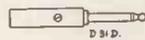Jack Socket for D31A. 10d. ea. Bin D31B. Jack Plugs thin type fibre insulated. 1/3 each. Bin D31D.



Jack socket for D31D, one hole fixing for mounting on metal panels, complete with insulating and spacing washers, 1/3 each. Bin D31C.



B7G PLUG

With hard rubber body, fits into standard B7G valve holders, ideal for joining small chassis, etc., 1/4 each.



Seven way brass cased plug ideal for portable apparatus. Price 2/3 each half, Bin D33BR & D33BL.

WANDER PLUGS

Insulated split-pin type, blue 3d. each. Bin D31F.
Insulated split-pin type, red, 3d. each. Bin D32E.
Larger banana type, black, 6d. each. Bin D32D.
Lockable wander plug, can't fall out 9d. each. Bin D30A.



MINIATURE FLEX CONNECTORS.

Plug and socket complete, ebonite, non-reversible. Ideal for toys, razors, etc., 2 amp rating, 9d. pair. Bin D32B.



CO-AXIAL PLUGS AND SOCKETS.

Suitable for car radios as well as T.V. for mic. leads, etc. Plugs 6d. each. Bin D32AR. Sockets 7d. each. Bin D32AL.



TERMINALS. Screw and Spade.

Spades, red or black, for L.T. Batteries. 3d. each. Bin C18E.

Spades, heavy duty, fit ex-Government car batteries, 9d. each. Bin C20A.

Screw Earthing terminals, flat bottom plate for flush mounting, with soldering tag. 4d. each. Bin C19C.

Earthing screw terminals, 2BA, also used for connecting two spades (as C20A) together. 9d. each. Bin C20C.

Screw down terminal 4 B.A. with plain insulated head. 5d. each. Bin C80F.

Screw down terminal all metal, 6 B.A. 4d. each. Bin C21C.




TAG STRIPS. Paxolin mounted.
Two lugs, one earthed, 3d. each. Bin C17A.

Three lugs, centre earthed, 4d. each. Bin C17B.

Four lugs, one end earthed, 5d. each. Bin C17C.

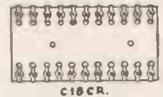Six lugs, two ends earthed, 6d. each. Bin C17E.



GROUP PANELS. Paxolin mounted.

5 components (10 lugs), 7d. each. Bin C18CL.


6 components (12 lugs), 8d. each. Bin C18CC.

11 components (22 lugs), 1/- each. Bin C18CR.

THERMOSTAT




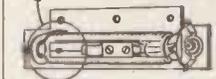These are sealed in a glass tube and break contact at 31°C. (88°F.). Variations of this operational temperature can be achieved by re-



moving the thermostat, from its glass case and altering the contact screw. No precise figures can be quoted, but we estimate that the limits by adjusting the screw would be from about 20°C. to about 200°C. Price 3/6 each.

INDUCTANCE TYPE ATTENUATORS

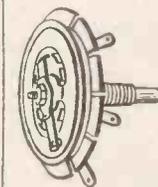

High fidelity enthusiasts will confirm that an ordinary wire wound volume control in series with a speech coil introduces distortion. We have some inductance type attenuators

wound in a very compact manner with heavy stud contacts giving reactance tappings as follows: off 42, 34, 23, 13, 7.9, 4.3, 1.7 0 ohms. You will see that these tappings have been chosen to enable the control to be calibrated in decibels. Price 4/6 each.



SHEET PAXOLIN

Invaluable for when you are experimenting. Size 6in. x 6in., 1/- Size 12in x 8in., 2/- Size 12in x 12in., 3/6. Size 24in. x 12in., 6/-.

CABLE CLIPS

These cable clips are carefully made for the Navy and are designed so that the edge of the clip cannot cut into the insulation of the cable. In addition to their use for holding cables, these clips are also suitable for fixing back conduit, for fixing T.V. aerial masts to poles or window frames, etc. —




Depth of Saddle (inches)	Across Saddle (inches)	Admiralty No.	Price each
2	7 1/2	7,000	9 1/2 d.
	7 3/4	7,087	8 d.
	3 1/2	3,350	7 d.
1 1/2	6 1/2	7,001	8 d.
	3 1/2	7,086	6 d.
	8 1/2	7,005	10 1/2 d.
1 1/4	8 1/2	7,003	10 1/2 d.
	6 1/2	7,002	8 d.
	6	7,091	8 d.
	3 1/2	3,354	5 d.
	3	7,090	5 d.
1 1/8	5 1/2	7,004	6 d.
	3 1/2	7,088	5 d.
1 1/4	5	7,095	6 d.
	2 1/2	7,094	3 d.
	1 1/2	7,083	2 d.
1 1/4	6 1/2	7,008	8 d.
	5 1/2	7,099	4 d.
	2 1/2	7,006	3 d.
1	4 1/2	7,013	5 d.
	3 1/2	7,016	4 d.
	3	7,101	4 1/2 d.
3/4	1 1/2	1,100	2 1/2 d.
	5 1/2	7,106	6 d.
	4 1/2	7,102	5 d.
	3 1/2	6,105	5 d.
	2 1/2	7,104	3 d.
	1 1/2	7,103	2 d.
	1 1/4	7,107	2 d.
	4	7,111	5 d.
	3	7,110	3 d.
		3,488	2 d.
		7,112	1 1/2 d.

Special quotations to quantity users.

A MILLIBAR BAROMETER

If you are interested in meteorology, or if you think a good barometer would help you to explain some tricky radio problem, then you will be interested to know that an article appeared in one of the leading meteorological journals, showing how the Ex-R.A.F. Sensitive Altimeter can become a first-class highly sensitive yet robust aneroid barometer. We offer the sensitive altimeters in good condition with instructions at 17/6 plus 1/- postage.

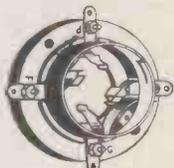

JUMBO VALVE BASES
Ceramic 4-pin for transmitting valves. Price 3/6 each. We have all other types and sorts of valve holders in stock at competitive prices.

LITTLE COMPANION CABINET

This modern design bakelite cabinet in ivory, blue or brown is ideal for an all mains receiver complete with back, 19/6 postage and insurance 2/6. Metal Chassis, punched out with speaker cut out, 5/6. Metal Assembly for holding dial and pilot lights, complete with long and medium wave dial, 2/6. Moulded Perspex Window, 1/9. Marched knobs, set of three, 2/-. A complete T.R.F. Receiver can be built into this cabinet for under £6. Constructional data 1/6.




GUESS WHAT FOR £5



We have done something to the valve as photographed, but what we have done has not altered its performance in our T.R.F. circuit. We invite you to state the type number of the valve, and to the first three correct solutions opened, we offer prizes to the value of £5 to the first, £3 to the second and £2 to the third. Final date for entries, first post September 29th. The actual valve can be seen in our window at Fleet Street.

CHARGING SWITCHBOARD

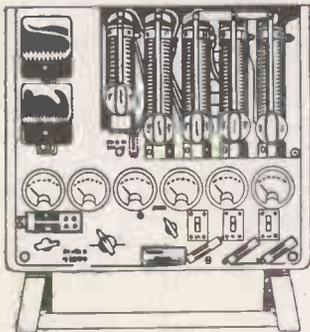


This 550 watt 18 volts charging board is fitted into a steel case with doors and it comprises, three reverse current relays (cut-outs) one voltmeter, one main ammeter, two secondary ammeters, and three variable resistances for controlling load circuit—brand new in original cases £6/10/- carriage 10/- extra.

Note: Illustration is of 1250 watt model which is very similar. All our stocks of these have been cleared.

EQUIP YOUR LABORATORY

You many times have felt the need of a device which would enable you to put resistance or capacity or a combination of these two quickly into a circuit. We have a small quantity of resistance capacity boxes which, by the simple manipulation of plugs, will enable you to do this. With these boxes you can put in 1 ohm, 2 ohms, 3 ohms, 4 ohms, and so on, in steps of 1 ohm, right up to 6,000 ohms. In a similar way capacity can be put into circuit by small amounts, thus making it simple for you to find optimum working conditions. These boxes made for Government Laboratories are available while they last at 19/6 each, plus 1/6 post and packing. Don't delay—order by return.

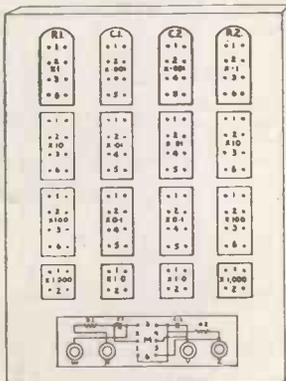

ELECTRICAL INSTALLATION MATERIALS.

In addition to our large range of radio accessories, we also carry a good stock of electrical wiring accessories, details of a few of these and of cables can be found below:—
T.R.S. CABLES, 250 v. CLASS
3/029 twin flat, 1/4 yd.
3/029 3-core flat, 2/- yd.
3/029 twin, with earth, 1/8 yd.
7/036 twin flat, 2/9 yd.
7/029 twin flat, 2/- yd.
3/036 3-core flat, 2/8 yd.
7/029 twin, with earth, 2/4 yd.
7/064 twin flat, 4/9 yd.

LEAD COVERED CABLES, 250 v. CLASS

3/029 3-core, 2/3 yd.
3/036 3-core, 3/8 yd.
7/044 twin, 3/3 yd.
3/036 twin, 2/- yd.
7/099 twin, 2/9 yd.
7/064 twin, 5/- yd.

WAR EMERGENCY TYPE CABLES 250 v. CLASS


These are P.V.C. or rubber insulated, laid flat then braided with cotton and compounded:
7/029 3-core flat, 2/- yd.
7/044 twin flat, 2/- yd.
7/064 twin flat, 3/3 yd.

FLEXIBLES

Maroon gauge cotton covered:
23/36 twin twisted, at 6/- doz. yds.
P.V.C. 14/36 twin twisted, at 4/- doz. yds.
Twin flat P.V.C. for clocks, etc., 4/6 doz. yds.

MULTICORED FLEXIBLES

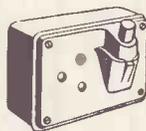All are suitable for mains work as the separate conductors are very well insulated, then they are covered overall either with hard rubber, plastic or waterproofed braiding:—
10 core, at 2/6 per yd.
7 core, at 2/- per yd.
5 core, at 1/- per yd.



CLIX 15 AMP. FOOT SWITCH PLUG
Made to B.S.S. specification, shuttered in moulded bakelite case, 8/6 each.



SLIDELOCK FUSES
15 amp., very latest pattern for mounting on the front of instrument panels, etc. Price 1/6 each.

"CRABTREE" SURFACE SWITCHES

Lincoln all brown No. 3000 one way. Price 1/11 each. Standard 1 way, brown on white No. 3010, 2/6. Standard 1 way double pole, brown on white, No. 3230, 4/-.



Orders under £2 add 1/6, under £1 add 1/-. Postable items can be sent C.O.D., additional charge approx. 1/-. List 6d. All post orders to Ruislip. Early closing days: Wednesday, Ruislip; Saturday, City. Telephone: Ruislip 5780.

152-153 FLEET STREET, E.C.4.

42-46 WINDMILL HILL, RUISLIP MANOR, MDX.

MAINS TRANSFORMERS

These transformers are all famous radio manufacturers' surplus and are fully interleaved, impregnated and guaranteed.

Primary 200-250 v. P. & P. on each 1/6 extra

300-0-300, 100 mA, 6 volt, 3 amp, 5 volt, 2 amp, 17/6.

320-0-320, 100 mA, 6 volt, 3 amp, 5 volt, 2 amp, 17/6.

320-0-320, 120 mA, 6 volt, 4 amp, 5 volt 2 amp, 25/-.

Heater Transformer. 4 volt 3 amp, 4 volt 3 amp, 4 volt 3 amp, 2 volt 2 amp, 7/6.

250-0-250, 100 mA, 6 v. 3 amp, 4 v. 3 amp, 4 v. 3 amp, 17/6.

250-0-250, 60 mA, 6 v. 4 amp (to be used on common heater chain with 6x5 rectifier), 13/6.

280-0-280, 80 mA, 6 v. 3 amp, 4 v. 2 amp, drop-through, 14/-.

Drop thro, 350-0-350 v, 70 mA, 6 v. 2.5 amp, 5 v. 2 amp, 14/6.

Semi-shrouded, drop-thro' or upright mounting 280-0-280 80 mA, 4 v. 6 amp, 4 v 2 amp, 12/6.

Auto-wound H.T. 280 volts at 360 mA, 4 v. 3 amp, 2 v. 3 amp, or 6 v. 3 amp Separate 4v. 3 amp rectifier winding (upright or drop-thro'), 10/6.

350-0-350 v, 120 mA, 4 v. 6 amp, 4 v. 3 amp, drop-through, 21/-.

Auto-transformer, various combinations of voltages including 110 v. 70 watt, and 3/4 volts windings at 1 amp, 2 volt 1 amp, drop-through or upright mounting, 10/6.

Heater Transformer Pri 200-250 v., 6 v. 1 1/2 amp, 6/- P. & P. each 9d.

ELECTROLYTIC CONDENSERS

16 + 16 mfd. 450 v. wkg., 5/6.

50 mfd. 50 wkg., 1/9.

100 mfd. 12 v. wkg., 1/3.

50 mfd. 12 v. wkg., 1/-.

25 mfd. 25 v. wkg., 1/2.

16 x 8 mfd., 450 wkg., 4/-.

8 mfd 450 v. wkg., 2/6.

250 mfd. 12 v. wkg., 1/3.

16 mfd. 500 v., 4/-.

8 mfd. 500 v., 3/-.

8 x 8 mfd. 450 wkg., 3/6.

32 mfd., 350 wkg., 2/6.

32 + 32 mfd, small tube tag ends 200 v. wkg., 2/-.

16 + 8 mfd, 350 wkg; miniature tag end, 3/-.

P.M. SPEAKERS

with less trans. trans.

3 1/2 in. 11/6

5 in. 15/- 12/6

6 1/2 in. 14/6 11/6

8 in. 17/- 14/6

5 in. Energised 750 ohm field with O.P. trans., 13/6.

P. & P. on each of the above 1/- extra.

D. COHEN

RADIO & TELEVISION COMPONENTS

TELEVISION COMPONENTS

by famous manufacturer, name supplied on request



FOCUS COIL.....9/6



LINE & FRAME COILS

Complete with mounting bracket (removed from chassis). Guaranteed...6/6



MOUNTING BRACKET

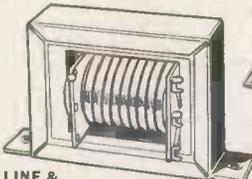
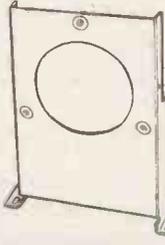
For use with the above coils 6 1/2" x 4 1/2" x 1 1/2" price.....2/-



LINE & E.H.T. TRANSFORMER 5 Kv. (removed from chassis). Guaranteed9/6

HEATER TRANSFORMER

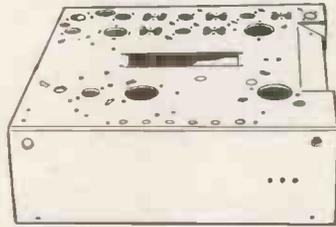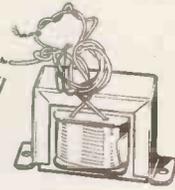Primary 230-250v Secondary 2v, 2.5 amp.....5/-



CHASSIS—could be adapted for use with the above components. Size 9 1/2" x 9 1/2" x 3 1/2".....3/-


FRAME BLOCKING OSCILLATOR TRANSFORMER

Price4/6



SMOOTHING CHOKE

2 Henry 200mA Price..3/6

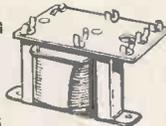

COIL PACK. 3 wave band, 16-50 metres, 180-550 metres, 1,000-2,000 metres. Iron cored coils, I.F. frequency 465 kc. Size 1 1/2" high x 2 1/2" wide x 2 1/2" deep, complete with circuit diagram, tax paid 24/-. Post paid.

MINIATURE BUTTON NEON INDICATOR. Complete with brass batten holder 200/250 v., 2/-.

MAINS or BATTERY PORTABLE COILS. Comprlsng medium wave frame aerial and long wave loading coil, used as aerial coils. Midget iron cored screened L/M osc. coils, complete with circuit I.F. frequency 465 Kc., 9/6.

6 IRON CORED LONG, MEDIUM and SHORT WAVE COILS coupling winding on all bands, 13.5-50, 180-550, 1,000-2,000 metres, complete with circuit, 8/6.

METAL RECTIFIERS, 250 v. 60 mA, latest midget Selenium type, 7/-.

WALNUT BAKELITE CABINET. Size 12 in. long x 7 1/2 in. high x 6 1/2 in. deep, scale aperture 3 1/2 in. x 4 in., louvred front, complete with 3 wave-band scale, back plate, 5-valve superhet chassis and back, 19/6. Post and packing, 2/-.

OUTPUT TRANSFORMERS. Standard type 5,000 ohms imp., 2 ohms speech coil, 4/9; Push-Pull 6 v. 6 matching 10 watt 2 ohms speech coil, 6/9. Miniature type to suit IS5, 5/-.

SET OF 3 BROWN KNOBS marked "wave change," "tuning," and "volume," 1/6.

TELEVISION MASKS

White Rubber. 9 in. with glass, 10/6. White Rubber. 12 in. with glass, 15/-. 15 in. white rubber mask, soiled, 12/6, plus 1/- P. & P.

Midget Components. Twin gang 3/4 in. diameter, 3/4 in. long. (The dimensions of this gang are slightly deeper than a standard volume control.) Pair Medium and Long iron cored T.R.F. Coils 3/4 in. long X 3/4 in. wide complete with a 4-valve all dry circuit, tuning scale and pointer knob. All the items 10/- post paid.

All Dry A.C. Mains Supply Unit, size 3 1/2 in. long x 2 1/2 in. wide x 1 1/2 in. deep. We can supply a complete all-dry circuit, using the above Midget Components to incorporate the above Power-Unit, 19/6, post paid with circuit.

Midget Bakelite Cabinet. 7 in. x 5 1/2 in. x 5 in. c/w 5-valve 5/H. chassis med./long wave scale and back (takes std. twin gang condenser and 3 1/2 in. speaker), 15/- P. & P 1/6.

Line and Frame Coil Assembly. Frame coils wound but not fitted (full instructions supplied). High impedance frame; low impedance line, matching 5-1, 8/6.

Wave Change Switches. 6-pole 3-way, 2/-; 3-pole 2-way, 1/2; 4-pole 3-way, 1/9; 5-pole 2-way matched, 1/9. P. & P. 3d. each.

Pre-Aligned Midget 465 Kc. Q. 120, 9/- per pair, post 6d. **Miniature 465 Kc. I.F.s. Q.120,** per pair, 10/-.

465 Kc. Midget I.F.s. Q.120, size 1 1/2 in. long, 1 in. wide, 3/4 in. deep, by very famous manufacturer. Pre-aligned adjustable iron dust cores, per pair, 12/6.

Iron Cored 465 Kc. Whistle Filter, screened, each 2/6.

Valve Holders. Paxolin international octal, 4d. each. Moulded international octal, 7d. each. EF50 ceramic, 7d. each. Moulded B7G slightly soiled, 6d. each.

Line Cord. 3-way 0.3 amp., 180 ohm per yard. 1/3 per yard. **Ceramic P.F.S.** 3 each of the following: 330, 220, 180 and 82, 2/6.

Trimmers. 5-40 pf., 5d.; 10-110, 10-250, 10-450 pf., 6d.

Twin Gang .0005 Tuning Condenser, 5/-. With trimmers, 7/6. Post and packing 6d.

Twin Gang Midget .00037 with perspex dust cover and trimmers, 8/6. Post and packing 6d.

Mains Droppers. 0.3 amp, 460 ohms, tapped 280 and 410, 1/6; 0.2 amp. 717 ohms, tapped at 100 ohms, vitreous, 1/6; 0.3 amp. 950 ohms, tapped 700 and 825, 2/6; 0.2 amp. 1,000 ohm, vitreous, tapped, 2/6. P. & P. on each, 3d.

Volume Controls by famous manufacturer. Long spindle and switch, 1/2, 1 and 2 meg., 4/- each; 20, 25 and 50 k., 3/6 each. Post and packing 3d. each.

Volume Controls, by famous manufacturer. Long spindle less switch, 5 k., 50 k., 500 k., 1 meg., 2/6 each. P. & P. 3d. each.

Terms of business:—Cash with order. Where post and packing charge is not stated please add 1/- up to £1 and 1/6 up to £2. Write for LIST. All enquiries must be accompanied by stamped addressed envelope.

PLEASE NOTE—Regret no orders accepted from outside United Kingdom.

NEW ADDRESS

23, HIGH STREET (Opposite Granada Cinema) ACTON, W.3

Hours of Business : Saturdays 9-6 p.m. Wednesdays 9-1 p.m. Other days 9-4.30 p.m.

MAGNETIC RECORDING EQUIPMENT

We carry extensive stocks of parts used for recording, some of which are shown here, and offer clients an advisory service on their problems with this equipment.

BSR INDUCTION MOTORS

- TYPE FP 10
4-Pole, 1,400 r.p.m., weight 1½ lb. Torque, 3in. oz., minimum stray magnetic field 38/- each
- TYPE SR 2
A medium power motor suitable for take-up spool drive where fast forward facilities are not required 25/- each
- TYPE SR 1
A motor of the same power as the renowned FP10, suitable for feed spool operation, giving fast rewind. Suitable also for take-up spool when fast forward facilities are required. Due to its higher stray magnetic field, this motor is not recommended for capstan drive..... 32/- each
All the above motors are suitable for A.C. mains.

"TAMSA" MAGNETIC RECORDING HEADS

These recording/playback heads give outstanding performance and first-class frequency response when used with good quality recording tape, e.g. Durex.

In addition to being a neat and attractive assembly they permit **TWIN TRACK RECORDING**, so effecting a considerable saving in tape cost. The gap of the Record/Playback head is set to finer limits than normal, and it is through this that extended high frequency response is attained.

A unique method of mounting allows perfect alignment of the face of the head to the tape, thus ensuring a high transfer efficiency.

Being **HIGH IMPEDANCE**, no transformers are required to couple these heads to the amplifiers, and one source of hum pick-up is therefore completely eliminated.

- "TAMSA" RECORD/PLAYBACK £2/19/6 each
- "TAMSA" ERASE HEAD £2/19/6 each

ELECTRIC SHAVERS

- PHILISHAVER £6 6 0
 - ARVIN CONSORT £2 19 7
 - ARVIN DE LUXE £4 0 0
 - REMINGTON FIVESOME DUAL VOLTAGE £9 15 8
 - " FIVESOME £8 17 7
 - " CONTOUR 6 £8 19 5
- Seven days free trial on CASH deposit. H.P. terms available.

2 VALVE MORSE TRAINER

A morse oscillator of high quality. A five-position switch selects the desired note and controls the output level. A jack is provided for superimposing interference over the C.W. note. Complete, 15/- Carr. pkg., 1/6 extra. 12 months guarantee on valves.

FOR RELIABILITY plus EFFICIENCY the "BURGOYNE" AERIAL CONNECTOR

This is the ONE and ONLY unit available which enables a really efficient and reliable weatherproof connection to be made between a dipole and its feeder. Why continue to worry about your dipole? Come gale or hail, rain in drops or by the bucket, this connector will never let you down. Brand new in original cartons. **18/6** Postage 8d.

R1355. I.F. TRANSFORMERS
Replacement I.F. transformers, for the R1355. Fully screened and guaranteed.
4 for 5/- post paid.

BOSTIK CEMENT

Handy pocket-size tubes. The ideal, waterproof sealing compound. Will stick or seal almost anything. Single tubes, 1/-. Six tubes for 5/- (please add postage).



The "BURGOYNE" 7 second **SOLDER GUN** **79/6**

A.C. ONLY 200-250v.

Post free

Two spare bits supplied with each gun. No current used unless actually making a joint; cold when not in use; no element to burn out; heats up in 7 seconds; no risk from touching the "wrong end." No constant re-tinning. Spare soldering bits, 10 for 7/6. Two years guarantee.

FLUX DENSITY METERS WY0023

With 3 ranges, calibrated —

Complete with Polarity Indicator and probe	500/1000	} Gauss
Brand new in Portable case 12" x 9" x 6".	1000/2000	
	2000/4000	

£15-0-0

COMPONENT BARGAINS

- Matched set of 3 walnut fluted **KNOBS** with brass insert ½in. spindle 2/6 per set (postage 3d.)
- Set of TRF coils M.W./L.W. boxed with circuit diagram... 6/- per set (postage 7d.)
- 3in. Plessey lightweight P.M. speaker 11/- (P. & P. 1/-)
- Remote control magnetic switch complete with relay and rectifier, 1 pole 2 way lin. break. For use on 230 v. 50 c/s. A.C. 12/6 (P. & P. 2/-)

DUREX MAGNETIC RECORDING TAPE

- TYPE MCI-III. Medium coercivity tape, ensuring extended frequency response, high sensitivity and ease of erase. 35/0
- Low noise level, 1,200ft. reel 25/0
- EMITAPE, type 65, 1,200ft. reel 25/0

"TAMSA" OSCILLATOR COILS

Designed for use in a single valve circuit, using a 6V6 valve, this coil unit will produce sufficient output to erase high coercivity tapes. The output is of good wave form, leaving the tape perfectly silent. Complete with circuit diagram and fixed tuning condensers.


Please note that this coil is only suitable for use with TAMSA high impedance heads 10/6 each

HI-FI

AMPLIFIER A1

For A.C. 200-250 v. only. Kit, incl. valves, for gramophone amplifier giving high quality reproduction. Simple instructions with many illustrations enable even those without previous experience to construct this amplifier. Kit complete in every detail down to solder tags and solder. Pre-drilled chassis, group board with all resistors, condensers, etc.

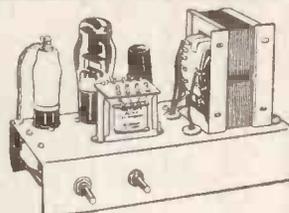Complete kit with instruction manual, £4/12/6. Instruction manual only, 3/6. Tone control kit, 5/-.



GRAMOPHONE EQUIPMENT

- DECCA 37A Playing Units £12 1 6
- CHANCERY G33 Adaptor: Obtain 33½ r.p.m. from your existing 78 r.p.m. turntable £3 12 6
- Or complete with DECCA pick-up £6 3 6
- COLLARO AC504MB Motors £5 18 6
- DECCA MU14 3-speed motors (33½-45-78) with turntable, A.C. mains £7 3 4
- DECCA Crystal Pick-up FFRR £3 15 4
- DECCA Playing Unit, 33A £9 9 0
- DECCA Playing Unit, 33B, or 37A £12 1 6
- CONRAD RUA Motors, 33½ r.p.m. £3 8 2
- ACOS GP20 Pick-ups £3 11 5
- GP19 L.P. Head £2 3 4
- CONNOISSEUR Dual Speed Gram. Motors £20 19 3
- CONNOISSEUR Pick-ups for above with one head ... £5 14 8
- Extra heads £3 11 8

AMERICAN TYPE LONG BEAM FOCUSING TORCHES

Again available—our imported torches are ideal for the motorist or cyclist, and for all-year-round use in home or workshop.

All solid brass, nickel-plated construction with adjustable ring focus head. Pullout carrying loop in base with spare bulb container. All torches are **FULLY GUARANTEED**. Supplied ready for use, complete with batteries. Illustration shows Type B, with range of 400ft., using 2 U2 batteries. Other types available: Type Beam Batteries Focusing Head Price A 700ft. Three U2 Ring 3½ dia. 18/6 C 300ft. Two U2 Ring 2 dia. 11/6



TYPE B
400ft
BEAM
15/6
post free

HS30 HEADSETS

U.S.A. miniature headphones, high impedance. New and complete with lead and jack plug. **17/6 post free**

AMPLIFIER Type A2 for A.C./D.C. 200-250 v.

Same fundamental circuit as A1. First-class reproduction. Kit complete with instructions. **65/-**. Instruction manual only 3/-.

AVOMETERS ON H.P.

		12 monthly	Cash	Payments of
Avo model 7, 8 or 40	£19/10/0	£6	£1/5/6	
Avo Universal Avominor	£10/10/0	£3/10/0	14/-	
Avo Signal Generator	£30	£10	£1/17/6	
Avo Universal Bridge	£26	£9	£1/12/0	
Avo Electronic Test Meter	£40	£12	£2/12/6	

These are some examples of our hire purchase facilities which we can offer on practically all proprietary equipment advertised in this journal. Send for details, specifying goods required.

BRITISH AND AMERICAN VALVES

We are now able to offer any type of valve required at B.V.A. prices. We will dispatch by C.O.D. post upon receipt of your order.

BERNARDS RADIO MANUALS

An extensive range of these popular Manuals is still available.

LARGE STOCKS OF RADIO AND TELEVISION RECEIVERS STILL AVAILABLE AT PRE-BUDGET PRICES.

M.O.S

MAIL ORDER SUPPLY CO., The Radio Centre,

(DEPT. W.W.9)

33 Tottenham Crt. Road, London, W.1. Museum 6667



"TELEVISION"

CONSOLE CABINETS

DE LUXE BEAUTIFUL WALNUT VENEER

TELEVISION SOUND AND VISION ON ONE

CHASSIS Size 10in. x 4½in. x 1in.

MADE POSSIBLE BY USING MINIATURE VALVES. LONDON FREQUENCY.



These units are not ex-Government, but are brand new manufacturer's surplus. They may be used with any type time base and c.r. tube, are fully assembled and wired. Voltages required—L.T. 6.3 volt 3 amps, H.T. 270 volts 80 ma. Valve line-up:—5 6AM6's R.F. amplifiers sound and vision, one common to both. 2 6AL5's sound and vision detectors. 6AM6 video amplifier, 6AM6 sync. sep., 6AM6 sound output. **LASKY'S PRICE** Send 6d. for a copy of the full data, circuits (less valves) **95/-** and photographs dealing with this unit. Carriage and packing 3/6 extra.

For 9, 10 or 12in. cathode ray tubes. Beautiful figured medium walnut finish, with high polish. Fitted with shelf for receiver, glass, speaker baffle and fret, and castors for easy movement. Undrilled. Suitable for use with the Viewmaster. "Electronic Engineering," "Practical Television," "Practical Wireless," and "Wireless World" televisions

LASKY'S PRICE
£8.10.0

Carriage 12/6 extra.

Outside dimensions of cabinet: 17½in. x 16½in. x 32in. high.

Why not convert your table receiver to a console?



CATHODE RAY TUBE MASKS. For 12in. tubes. Black, 10/6; soiled white, 10/-; White, complete with fitted armour plate glass, 21/-; Brand new white, 19/6; New White, special for flat face c.r. tubes, 22/- Postage 1/- per item extra.

PLIERS. Soiled, assorted types, round and flat nosed, long and short, etc. **LASKY'S PRICE** 1/6 Per pair Post extra.

CATHODE RAY TUBES. TYPE 3BP1. 3in. American tubes. Brand new in original cartons. **LASKY'S PRICE** 25/- Carriage and packing 2/6 extra.

TYPE VCR97. 6in. Electrostatic. Suitable for television. Brand new and unused. **LASKY'S PRICE** 35/- Carriage and packing 5/- extra.

FRAME BLOCKING OSCILLATOR TRANSFORMERS. **LASKY'S PRICE** 6/6 each. Post 4d. extra.

T.V. SCAN COILS FOR LINE AND FRAME. Brand new, manufacturer's surplus. For 9in. or 12in. c.r. tubes. **LASKY'S PRICE** 19/6 Post 1/-.

SAFETY FIRST. Fused test prods. Fully insulated pencil type with retractable point. Contact is only made when desired by pressing top. Each prod contains a cartridge type fuse and spring. **LASKY'S PRICE** 4/11 per pair (one red, one black). Post 6d. extra.

P.M. TELEVISION FOCUS MAGNETS Suitable for any type of cathode ray tube. Tetrode. **LASKY'S PRICE** 15/- Triode. **LASKY'S PRICE** 16/11 Postage 1/- extra.

BRAND NEW AND UNUSED. CATHODE RAY TUBES. COSSOR 108K. 10in. Magnetic tube. Uses a special ion trap which prevents screen burn. **LASKY'S PRE-BUDGET PRICE** £12.12.0 Carriage and insurance 22/6 extra.

T.C.C. HIGH VOLTAGE CONDENSERS. .1 mfd. 4 Kv. Price 3/11 each. .1 mfd. x .1 mfd. 3.5 Kv. Price 7/11 each. All post extra.

THE VIEWMASTER

Every component sold separately.

Plessey. Line E.H.T. Trans., 24/6. Focus Ring, 22/6. Line width coil, 10/- Boost, 5/9.

Westinghouse Rectifiers. 14A86, 18/6. 14D36, 10/6. 36EHT100, 26/8. Westectors, 3/5 each.

CARBON POT/METERS. All with long spindle. ½, 1 and 2 meg. **LASKY'S PRICE**, less switch 3/3 each. With switch 4/3 each. All post extra.

SPEAKERS. BRAND NEW MOVING COIL. P.M. All less o/trans.

10in.	29/6	9in.	16/11
8in.	14/6	6½in.	13/6
5in.	12/6	3½in.	14/6
2½in.	13/11		

Postage 1/6 per speaker extra. **BEST MAKES.**

PHOTOCELLS. Type VA26. Requires 100 volts D.C. or peak A.C. to function. Cathode area 15 sq. cms. **LASKY'S PRICE** 12/6 Post 1/6 extra.

LONG AND MEDIUM T.R.F. COILS. With reaction. **LASKY'S PRICE** 6/9 Per pair. Post 6d. extra.

SELENIUM METAL RECTIFIERS. 12 volts 6 amps., 27/6, post 9d. extra. 12 volts 1 amp., 7/9, post 9d. extra. 12 volts ½ amp., 3/11, post 6d. extra. 350 volts 80 M/a., 7/11, post 6d. extra. 250 volts 60 M/a., 6/6, post 6d. extra. Meter Rectifiers 5 M/a., 6/6, post 6d. extra. 800 Volts at 5 M/a. and 1,200 volts on pulse circuits. Manufactured by S.T.C. **LASKY'S PRICE** 9/11 each. Post 1/-.

VALVES AND CATHODE RAY TUBES There is no shortage at Lasky's.

GERMANIUM CRYSTALS. No. 1. Lasky's Price 4/3 each. No. 2. Lasky's Price 3/9 each. Silicon Crystals. Lasky's Price 3/- each. All post extra.

SPARES FOR OUR £25 T.V. RECEIVERS. All now available from stock. Prices on request.

MAINS TRANSFORMERS. All 200-250 volt 50 c.p.s. primary. Finest quality, fully guaranteed.

MBA/3. 350-0-350 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans. . . . Price 20/-

MBA/4. 270-0-270 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a. Semi-shrouded, black finish. . . . Price 16/11

MBA/5. 350-0-350 v. 125 m/a., 6.3 v. 4 a., 5 v. 3 a. With mains tapping board. . . . Price 37/6

MBA/6. 350-0-350 v. 100 m/a., 6.3 v. 3 a., 5 v. 2 a. With mains tapping board. . . . Price 27/6

Postage 1/6 extra per transformer.

FILAMENT TRANSFORMERS. Primary 230 volts 50 c.p.s.

FIL/2, 6.3 v. 1.5 a. Price 7/6

FIL/3, 6.3 v. 3 a. Price 12/6

FIL/4, 2 v. 2 a. Price 5/11

Special Transformer. 30 volts at 2 amps, with the following tappings:—3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volts. . . . Price 19/6

All fil. tapers 1/- extra per item postage.

MAINS SMOOTHING CHOKES. All 10-20 Henrys.

40 m/a.	3/6	80 m/a.	4/11
100 m/a.	6/11	120 m/a.	7/6
150 m/a.	10/6	250 m/a.	15/6



Special Choke Type SCRI. 2,000 ohms, 150 H. at 75 m/a. Price 8/6

Postage 6d. per choke extra.

CONDENSERS. ALL BRAND NEW. 8 mfd. 500 v.w., 3/6. 8 mfd. 450 v.w., 3/3. 16 mfd. 500 v.w., 4/6. 16 x 16 mfd. 450 v.w., 25 mfd. 25 v.w., 1/11. 5/6. 8 x 16 mfd. 500 v.w., 60 x 100 mfd. 350 v.w., 5/6. 8/6. 64 mfd. 500 v.w., 6/6. Postage extra.

EX-A.M. COMMUNICATION RECEIVER TYPE R1155. BRAND NEW IN WOOD TRANSIT CASE. Aerial - tested before despatch. Supplied complete with 10 valves. Circuit: B.F.O., A.V.C., R.F. Amp., two I.F. stages, magic eye, etc. 5 frequency ranges: 18.5-7.5 Mc/s.; 7.5-3.0 Mc/s.; 1,500-600 kc/s.; 500-200 kc/s.; 200-75 kc/s. **LASKY'S PRICE** £12.10.0 Carriage (in wood case) 7/6 extra. Full modification data and circuit details supplied.

"AMPLIFIERS" AT THE LOWEST EVER PRICES

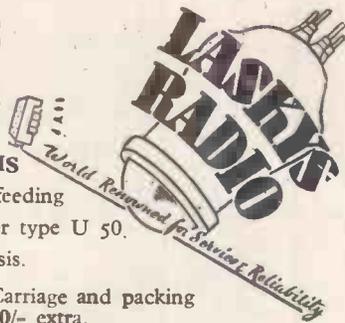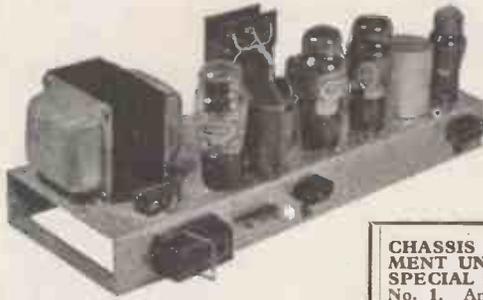

J/RA/2. 10-12 WATT CHASSIS AMPLIFIER. Uses an L63 feeding 2 KT61s in push-pull. Rectifier type U 50. Size: 6in x 17in. on 2in. chassis.
LASKY'S £7.19.6 Carriage and packing 10/- extra.

L.S.L. PORTABLE VALVE AND CIRCUIT ANALYSER. Brand new and unused. Limited quantity still available.

LASKY'S PRICE £10.19.6
 Plus 10/- carriage
 Further details of this unit available on request.

EX. A.M. RADAR INDICATOR UNIT TYPE 62. Unused but soiled. Containing 20 valves and a 6in. C.R. tube type VCR97. Valve line-up:—16 SP61; 2 EA50; 2 EB34. Dozens of components, resistances, coils, condensers, 117 Mc/s crystal, pot. meters, etc. Totally enclosed in metal case. Size: 18in. x 9in. x 11in. Weight 40 lb. Enamelled grey or black with coloured control knobs.

LASKY'S PRICE 69/6
 Carriage 10/- extra.

TYPE 6 INDICATOR UNITS. BRAND NEW AND UNUSED. In makers' original cartons. Contains a 6in. c.r. tube type VCR97 and 7 valves:—4 EF50, 3 EB34. Also 12 pot/meters, and hundreds of assorted components, resistances, etc. In metal case, grey enamelled, size:—18in. x 8in. x 7in.

LASKY'S PRICE 79/6
 Carriage 7/6 extra.

RF. UNITS FOR USE WITH THE R1355 RECEIVER.

Type 24.
LASKY'S PRICE 17/6 Carriage 2/6 extra.

Type 25. Suitable for London T.V.
LASKY'S PRICE 25/- Carriage 2/6 extra.

The above units are supplied complete with 3 SP61 valves.

TANNOY HAND-POWERED MICROPHONE AND HEADPHONES (M/C).
LASKY'S PRICE 12/6 per set
 Post Free.

RADAR INDICATOR UNITS TYPE 162C. BRAND NEW IN MAKER'S ORIGINAL WOOD CASE. Contains 2 cathode ray tubes, one 6in. VCR517 and one 3in. VCR139. Also the following valves: three SP61, one 6J5, three EA50, one D1. Dozens of components, coils, resistances, condensers, seven pot. meters, etc. Enclosed in metal case, size 12in. x 9in. x 19in. Weight 40 lb.

LASKY'S PRICE 79/6 Carriage 7/6 extra.

TABLE MICROPHONE STAND. Two sections, chrome plated. Crackle finished base. **LASKY'S PRICE 21/-** Post, packing 2/6 extra.

CHASSIS BARGAINS, EX GOVERNMENT UNITS STRIPPED OF VALVES. SPECIAL PRICES TO CLEAR.

No. 1. American Air Corps unit. Size:—12in. x 7in. x 7in. high. Contains 10 ceramic int. octal valve holders, 2 panel mounting fuse holders, on/off switch, relay, 6' pot/meters, condensers, resistances, etc. In metal case, black crackle finished.
LASKY'S PRICE 10/- Carriage 3/6 extra.

No. 2. The TX. section of the SCR522. Size:—15in. x 6in. x 7in. With 3 ceramic valve holders, a tuning condenser (2 gang) with auto tuning, a small selection of other components. Ideal for experimental work.
LASKY'S PRICE 7/6 Carriage 3/6 extra.

No. 3. I.F.F. Receiver 3108. Size:—10in. x 12in. x 8in. In double deck chassis. Contains 8 valve holders int. octal, condensers, switches, etc. Also motor generator, 24 volts in 480 volts out.
LASKY'S PRICE 12/6 Carriage 3/6 extra.

No. 4. Receiver Type 25. Rx. section of TR1196 equpt. Size:—8in. x 6in. x 6in. Contains 6 int. octal valve holders, condensers, coils, tuning etc. Ideal for conversion to an all wave receiver. In black metal case.
LASKY'S PRICE 8/6 Carriage 3/6 extra.

No. 5. V.H.F. Receiver Units. Size:—7in. x 11in. x 6in. Contains 8 int. octal valve holders, also hosts of components, auto switch tuning. This is a superhet unit with an RF. stage and three I.F.'s. Frequency covers 124 Mc/s.
LASKY'S PRICE 4/6 Carriage 2/6 extra.

COIL PACKS. ALL AT PRE-BUDGET PRICES.

By Weymouth. No. 1. Standard long, medium and short wave coverage. Simple single hole fixing. For use with 465 Kc/s I.F.'s. Size:—3in. x 2in. x 4in. Price 35/-. Postage 1/6 extra. No. 2. As above, but of miniature dimensions, as follows:—3in. x 1in. x 2in. Price 44/-. Postage 1/6 extra.

By Osmor. Type Q Packs. Superhet for 465 Kc/s I.F.'s. These packs are aligned and tested in actual receivers. Medium, short, Price 45/10. Long, medium and trawler band, Price 45/10. Postage 1/6 extra. All coil packs are supplied with full circuit.

ALL OTHER TYPES AVAILABLE.

ANTENNA ROD SECTIONS. Each section is steel heavily copper plated, 12in. long and 1/4in. in diameter. Any number of sections can be fitted together. **LASKY'S PRICE 2/6** per doz.; 6/- for 3 doz.; 11/- per half gross; 20/- per gross. Post extra.

CARBON HAND MICROPHONES. Heavy case, chrome plated. Complete with screened cable.

LASKY'S PRICE 39/6 Postage and packing 3/6.

MATCHING TRANSFORMERS. Type T268A. Price now reduced to 12/6 each.

TYPE J/RA/1. 30 watts. HEAVY DUTY AMPLIFIER. Rack mounting, grey crackle finished. Uses KT263 and L63, feeding 2 KT66s in push-pull. Rectifier type U52. Meter and switch for checking all current readings. Panel light, bass brilliance and gain controls. Size: 19in. x 12in. x 12in. on a chassis 4in. high.
LASKY'S PRICE £13.19.6
 Carriage and Packing 25/- extra.

6-VOLT VIBRATOR PACKS. BRAND NEW, IN ORIGINAL CARTONS. By Masteradio. Output 200 volts, 80 M/A. Supplied with 4-pin non-synchronous vibrator and OZ4 rectifier. Completely enclosed in metal case, grey enamel finish. Size:—9in. x 4in. x 6in.

LASKY'S PRICE 29/6
 Postage 2/6 extra.

VIBRATOR PACKS. For use with the P.C.R. Philips Communications Receiver. 12 volt input. Supplied complete with vibrator and metal rectifiers, etc.
LASKY'S PRICE 39/6
 Carriage 5/- extra.

OLON SOLDERING IRONS. For 230 volts. All 65 watts. Price; Straight bit, 19/-; Pencil bit, 21/-. Postage 1/6 per iron extra.

RESISTANCES. ALL VALUES, ALL SIZES. 5 ohms to 50 meg. ohms. Send us your order. Prices:—1/2 and 1/10 watt, 7d. each; 1/4 and 1/4 watt, 4d. each; 1 watt, 8d. each.

CO-AXIAL CABLE. Suitable for television. 80 ohm. Single, 1/- per yard; twin 1/3 per yard. Twin feeder at 7d. per yard.

RADAR RECEIVER UNITS TYPE R3584. BRAND NEW AND UNUSED. IN ORIGINAL WOOD TRANSIT CASE. Contains 23 valves:—15 EF50; 2 VR65; 3 EB34; 1 VR55; 1 EA50; 1 VR53. Also a removable 45 Mc/s I.F. strip (Receiver Unit 153). Hundreds of components, resistances, condensers, 12 pot/meters, etc. Relays, amphenol and ceramic valve holders. Totally enclosed in metal case, size 7 1/2 in. x 13in. x 21in.
LASKY'S PRICE 119/6
 Carriage 7/6 extra.

LASKY'S RADIO

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital)

Telephones: CUNningham 1979 and 7214

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs. half day 1 p.m. Send a 2d. stamp with your name and address (in block letters please) for a copy of our current stock list giving details of our supplies of new manufacturers' surplus equipment and ex-Government radio, radar and valves, etc.

BUILD A PROFESSIONAL RADIO OR AMPLIFIER AT LESS THAN HALF TODAY'S PRICE


A MAINS OR BATTERY PORTABLE KIT



A Midget 4-valve Superhet Portable Set covering medium and long wavebands. Designed to operate on A.C. mains 200/240 volts, or by an "Alldry" battery. The set is so designed, that the mains section is supplied as a separate unit which may be added at any time. The Kit therefore can be supplied either as an "Alldry" Battery Personal Set, or as a Midget Portable for combined Battery/Mains operation. Circuit incorporates delayed A.V.C. and Pre-selective Audio Feedback. Kit is complete in every detail and includes ready wound frame aerials, fully aligned I.F. Transf., and drilled chassis, etc. Overall size of assembled chassis 8in. x 4in. x 2 1/2in.

We can supply the set either as a complete Kit of Parts for £8/16/9 (incl. P.T.) (less Cabinet and Mains Unit), or by supplying the components separately. The complete Assembly Instructions, which include full price details (including prices of individual components), Circuit and Component Layout, etc., are available for 1/8 incl. postage.

A T.R.F. BATTERY "PERSONAL" KIT

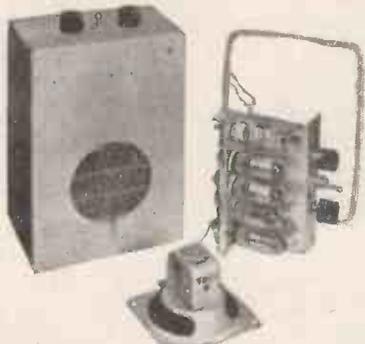

A complete Kit of Parts to build a Midget 4-valve Alldry Battery Portable Set, covering medium waveband. Consists of Regenerative T.R.F. circuit, employing Flat Tuned Frame Aerial with Decca Iron Dust Coiled Coil. Valve line up, two I.T.4's (R.F. Ampl. and Det.), 1S5 and 3S4 output.

Kit is complete in every respect and includes drilled chassis, and latest type Rola 3in. P.M. speaker. Overall size of assembled chassis 4 1/2in. x 2 1/2in. x 2 1/2in. We can supply the Complete Kit (less cabinet) for £6 4/8 (inc. P.T.) or by supplying the components separately. The Complete Assembly Instructions, including individual component prices, Circuit and Component Layout, etc., is available for 1/-, incl. post.

A KIT OF PARTS

Complete in every detail, to build a 3-valve Amplifier for A.C./D.C. mains 200-250 volts. Has an output of 3 watts, and incorporates a Tone Control. Valve line up, 2S6, 6J7, U31. Our price of £4/12/6 for complete kit, includes a matched 6 1/2in. P.M. speaker. This Amplifier can also be supplied assembled and ready for use for £5/12/6.

You're SURE to get it at STERN'S ESTABLISHED 25 YEARS

A MIDGET 4-STATION "PRE-SET" RECEIVER

A complete Kit to build a 4-Station "Pre-Set" Superhet Receiver for A.C. mains operation.

The Set is designed to receive any three stations on medium waveband and one on long waves, each station being received by the turn of a Rotary Switch—No Tuning being necessary.

It is of midget size, being 8 1/2in. x 4 1/2in. x 7in. high, and has the performance of a far more expensive ready made set, but can be built for half the price.



Price of complete Kit of Parts (including aligned I.F. Transf. and drilled chassis, etc.), £9/2/6 (incl. P.T.) (plus Cabinet 25/6), or the components can be purchased separately. The complete Assembly Instructions including Individual Component Price List, Circuit and Component Layout, etc., is available for 1/8.

Purchase Tax is ONLY charged on Complete Wireless KITS of PARTS.

It is NOT chargeable on
WIRELESS COMPONENTS or
AMPLIFIER KITS

THE WIRELESS WORLD MIDGET A.C. MAINS 2-VALVE RECEIVER

We can supply all the components to build this set, as published in the March issue, including Valves and Moving Coil Speaker for £3/10/-, including Designer's complete building instructions (these are available separately for 9d.)

THE "SUMMER ALLDRY" BATTERY PORTABLE

As published in June issue of "Practical Wireless." We can supply, from stock, all the components to build this Midget 3-valve Portable for £2/19/6 (less valves). This also includes dials, top panel and a/v. sheet for chassis. The complete article and circuit, including practical Layout and Price List, is available for 9d.

A complete Kit of Parts to build the Valve Voltmeter specified in the "Electronic Engineering." This Meter has fine voltage ranges, 1.5-25-100 and 250 volts. For use on A.C./D.C. mains. Price (less case), £3/19/6. A reprint of complete Assembly Instructions available for 9d.

ALL KITS INCLUDE "EASY TO FOLLOW" POINT-TO-POINT WORKING DIAGRAMS

THE WIRELESS WORLD 3-VALVE SET



A Midget 3-valve T.R.F. Receiver for operation on A.C. mains, covering long and medium wavebands.


We are able to supply all of the components to build this set, as designed, and specified in the Feb. 1950 issue, including the drilled chassis, valves, and moving coil speaker, etc., at the following prices:—

To construct complete chassis, less dial and drive assembly, £4/17/8. Ditto, including dial and drive assembly, £5/12/8.

To construct the complete Set, including dial and drive assembly and cabinet, £6/14/3.

Overall size of cabinet is 7 1/2in. x 6 1/2in. x 1 1/2in. A reprint of the designer's article, giving Circuit and Assembly Instructions (this is available separately for 9d.), together with a Practical Component Layout is included with each of above assemblies.

BATTERY CHARGER KITS

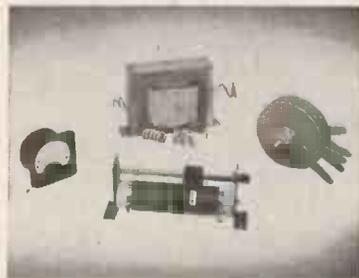

All Kits incorporate Metal Rectifiers, and are for use on A.C. mains 220-250 volts. All Kits include an easily followed Wiring Diagram.

For charging 6 v. battery at 1 1/2 amps., £1/2/6. For charging 6 volt. battery at 1 1/2 amps., with Variable Resistor and Meter, £2/2/6.

For charging 12-volt battery at 1 1/2 amps., £1/8/-.

For charging 12 volt battery at 1 1/2 amps., with Variable Resistor and Meter, £2/5/3.

For charging 6 or 12 volt battery at 3 amps., £1/18/-.

For charging 6 or 12 volt battery at 3 amps., with Variable Resistor and Meter, £2/19/-.

The Decca 3-speed Gram. Motor, complete with turntable and "turnover head" type lightweight pick-up, £11/2/6; or less pick-up, £7/3/4.

PICK-UPS:

Cosmocer "G.P.20." for standard records, £3/11/5; interchangeable (G.P.19) Head for L.P. records, £2/3/4.

Decca lightweight "turnover head" type, for L.P. and standard records, £3/19/6.

Marconi, Standard, lightweight Magnetic, 35/10. Marconi Matching Transformer, 7/6.


Goldring, Standard, lightweight, Magnetic, 32/6.

★ Send 6d. P.O. for our STOCK LIST, it shows "hundreds" of Wireless. When ordering please include

STERN RADIO LTD., 109


Tel: CENTRAL

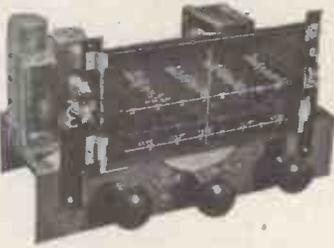AN A.C. MAINS "ALL-WAVE SUPERHET" CHASSIS



A completely assembled chassis for A.C. mains 200-250 volts, designed for good selective and quality reproduction, and serves as an ideal replacement chassis for that "old radiogram, etc." It incorporates in addition to the three controls shown above, a Tone Control and a Radio-gram Switch. These two are left on "floating leads" to enable them to be placed in any position on cabinet. The set employs a modern 5-valve line up, and covers three wavebands, 16-50, 190-550 and 800-2,000 metres. Fly-wheel tuning is incorporated. Overall size of assembled chassis, 13 1/4 in. x 6 in. x 8 1/4 in. High. Dial size 9 in. x 4 1/4 in.; an attractive Dial Escutcheon Plate is supplied. Price of complete chassis, wired and ready for use £14/19/6.

A QUALITY "PUSH PULL" AMPLIFIER KIT

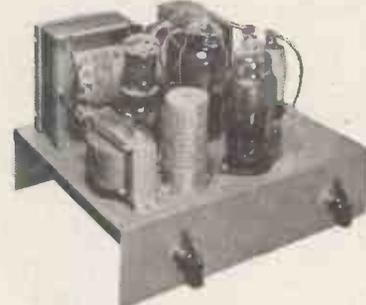

A Kit of Parts to build a 6-8-watt Push-Pull Amplifier for operation on A.C. mains 200-250 volts. Incorporates a simple arrangement to enable either a magnetic, crystal, or light-weight pick-up to be used. A 10-watt Output Transformer is designed to match from 2 to 15 ohm speakers. Tone control is incorporated. The overall size of the assembled chassis is: 10 1/2 in. x 8 in. x 7 1/4 in. high. Price of kit, complete in every detail, including drilled chassis and valves, £8/5/-. Component layout is supplied. Price of assembled chassis, supplied ready for use, £7/10/-.

"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "All Day" Battery Eliminator, giving approx. 60 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltages as above, or approx. to 60 volts.




The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4 1/2 in. x 1 1/2 in. x 3 1/2 in. Price of complete kit, with easy to follow assembly instructions 42/6.

Trickle Charger, for A/D/C mains, charges 2 volts at max. 1 1/2 amps.. 37/6.

You're SURE to get it at
STERN'S
ESTABLISHED 25 YEARS

A NEW AND ULTRA MIDGET SUPERHET COIL TURRET FOR 4 PRE-SET STATIONS

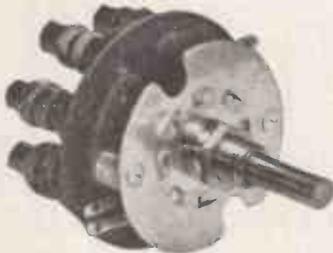Designed on the Rotary Turret principle from which any three stations on medium waveband plus one on long waveband can be received by a turn of the Turret Switch.



The outstanding advantages this has over other similar units can be readily seen, the main points being—

- (a) Neat and compact, the overall size being only 2 1/4 in. dia. x 1 1/4 in. deep.
 - (b) Easily accommodated, having one hole fixing and requiring only four connections.
 - (c) The Rotary Turret design switches the actual coils on to positive contacts, thereby reducing stray capacities to the absolute minimum.
 - (d) For use with Superhet circuits employing 465 K/c. I.F. Transformers.
- Selected stations are "set" by means of variable dust cored coils, which give excellent sensitivity and selectivity with use of small traller aerial.

Price 39/6
A complete receiver circuit is supplied with each unit.

THE FAMOUS W.B. "STENTORIAN" RANGE OF P.M. SPEAKERS.

Size	Impedance	Watts	Price
2 1/4 in.	2-3 ohms	1	17/3
3 1/4 in.	"	2	18/6
5 in.	"	2 1/2	19/6
6 in.	"	3	23/6
7 in.	"	3 1/2	23/6
8 in.	"	5	26/9
9 in.	"	7	33/-
10 in.	"	10	41/9
12 in.	15	15	£8/3/6

New Mrs. Surplus Speakers. All 2 1/2 ohms. 2 1/4 in. 15/-, 3 1/4 in. 14/6, 5 in. 14/6, 6 1/4 in. 15/6, 8 in. 16/9, 10 in. 19/6, 12 in. 47/6. New Type Rola. 3 in. 21/-, 4 in. 22/6.

Output Transl. Midget 60-1 (or 90-1) 1 1/2 in. x 1 in. x 1 1/2 in. 3/6. 5-watt, Multi-ratio, 12 tapings between 24-1 and 114-1 (some C.T.). 8/8. Wharfedale, 12 watt, push-pull, multi-ratio, 23/6. P/pull, 20 watt, multi-ratio, 37/6, and many others.

Ext. Speaker Volume Control, 2/6. New Electrolytic Condensers. Not Ex-Govt. All 450/500 volts, 8 mfd. (1 1/2 in. x 1 in. dia.), 3/-, 8-8 mfd. (1 1/2 in. x 1 in.) 4/8, 16-8 mfd. (1 1/2 in. x 1 in. dia.), 16-16 mfd. (1 1/2 in. x 1 1/2 in. dia.), 32 mfd. (1 1/2 in. x 1 1/2 in. dia.), 5/9. Card-board Tubular, 4 mfd. 500 v. 3/6, 8 mfd. 500 v. 4/-, 16 mfd. 500 v. 5/9. Can. Standard size, all 500 volt, 4 mfd. 3/6, 8 mfd. 4/3, 8-8 mfd. 5/9, 16 mfd. 5/6, 16-16 mfd. 7/9, 32 mfd. 6/9.

Denco I.F. Liners, for accurately lining 465 K/c. and 1.6 m/c. I.F. channels, and associate circuits. Battery operated, small and completely self-contained, 47/6.

Potentiometers. New, not Ex-Govt. 2K, 5K, 10K, 25K, 50K, 100K, 250K, 1/2 and 2 meg. Price, less switch, 3/9. Price with 8/Pole switch, 5/9. Price with D/Pole switch, 6/6.

Surplus Potentiometers. All standard with extended splines, 5K, 10K, 15K, 20K, 25K, 50K, 100K, 1/2 and 1 meg., 2/- each.

Ex-Govt. complete set of Moving Coil Headphones and Microphone, with headgear, 10/6.

Coils, Denco "Maxi Q," midget size, Litz wound on Polystyrene Formers, with adjustable iron cores. Available for Aerial, H.F. and Oscillator 465 K/c. or 1.6 M/c. 3/9, each, or with reaction winding 4/9. Denco Matched pair T.E.F. Coils for long and medium waves, 6/6 pr. Weymouth matched pairs of coils, for T.R.F. covering long and medium waves, 10/6 pr., or for Superhet covering Long, Medium and Short waves, 11/6 pr. All types of Wearite "P" coils in stock at 3/- ea.

Coil Packs, Ormor Midget Coil Pack, Size 3 1/2 in. x 2 1/4 in. x 1 1/4 in. covering S. M. and L. waves. Coils wound on Polystyrene Formers with adjustable iron cores, ensure efficient performance. Factory wired and aligned. Price including full circuits for Superhet 465 K/c. Unit 52/- (incl. P.T.). This Ormor Coil Pack is also available for Midget Superhet BATTERY Portable sets including a matched ready wound Frame Aerial. Price 54/2 (incl. P.T.). Weymouth Midget 3 1/2 x 2 1/4 in. covering S.M.L. w/bands, for 465 K/c., employing Matched Iron Cored Coils on each w/band, 51/6.

Wearite Pack, 4 1/2 x 3 1/2 x 1 1/4 in., Type 706 covers two short w/bands and medium w/band and Type 706 covers short-medium-long waves. Both for 465 K/c. Incorporates gram. position, and employs adjustable cored coils, 53/4.

All of the above Coil Packs include Switching, Padding and Trimmer Condensers.

L.F. Chokes, Midget 10 Henry 250 ohms 40 mA., 3/6; 20 Henry 250 ohm 60 mA., 6/6; 20 Henry 30 ohm 100 mA., 12/9; 5 Henry 60 ohm 250 mA., 28/6; 20 Henry 250 ohm 120 mA., 15/-; 9 Henry 250 ohm 120 mA., 8/6, 18 Henry, 200 ohm, 250 mA., 25/6.

I.F. Transformer, 465 K/c. New well-known manufacturer's surplus 1/2 in. x 1/2 in. x 1 1/4 in. Iron Core, 9/- each. Denco Iron Core, 465 K/c. or 1.6 m/c., 1 1/2 in. x 1 1/2 in. x 3 1/4 in., 16/6 pair. Wearite Stand Cap. Tuner, 45 K/c., 20/- pr. New Surplus 465 K/c. Iron Core, 4 in. x 1 1/2 in. sq., 10/- pair.

Transformers. (a) Input 230 volt, output 200 volts 25 mA. and 6.3 v., 9 amp., 11/-; (b) Input 230 volts, output 250 volts 30 mA. and 6.3 volts 1 amp., 13/9.

E.H.T. Transformer. Prim. 230 v. Sec. 5 Kv. and 4 volt, tapped 2 volt, 59/6. Do. but 4 Kv., 54/-.

Hester Auto Transformers. (a) tapped 2 v., 4 v., 5 v., 5 v., and 6.3 volts 3 amp., 9/6; (b) 4 v., 3 amp. to 5 v., 2 amp. Reversible, 6/6; (c) 4 v., 3 amp. to 6.3 v., 2 amp. Reversible, 6/6.

NEW SURPLUS !! FOSTER TRANSFORMERS. Primary 230 volts, Secondary 12 volts 9 amp., 21/-.

Filament Transformer. Input 230 volts, output 6.3 v. 1 1/2 amp., 8/3; 4 v. 1 1/2 amp., 7/6; Input 200/250 v., output 4 v. (C.T.), 1 1/2 amp., 4 v., 2 amp., 6.3 v., 2 amp., 19/6. Input 230 v. output 6.3 v. (C.T.) 4 amp., 17/6.

Metal Chassis, substantially made with four sides, 7 in. x 4 in. x 2 in. 3/11, 9 x 5 x 2 1/2 5/3, 10 x 6 x 2 1/2 6/-, 10 x 7 x 2 1/2 6/3, 12 x 9 x 2 1/2 7/8, 14 x 9 x 2 1/2 8/3, 16 x 8 x 2 1/2 9/-.

Mains Transformers. All New Stock with Primaries tapped for 200-250 volts. Secondaries (a) 250-0-250 volt, 80 mA., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., 18/6 (also available with 350-0-350 volt at 18/6). Stern's 350-0-350 volt, 150 mA., 6.3 v. (tapped 4 v.), 4 amp. and 5 v. (tapped 4 v.) 2 amp., 41/6; (c) 350-0-350 v., 250 mA., 4 volt, 8 amp., 4 v., 3 amp., 6.3 v. (tapped 2 v.) 2 amp. and 6.3 v., 6 amp., 79/6, and many other ratings.

Westinghouse Rectifiers. (a) H.T. 51. Rated 350-0-350 volts, 100 mA., 35/-; (b) H.T. 52. Rated 350-0-350 v., 200 mA., 37/6; (c) H.T. 53. Rated 500-0-500 v., 200 mA., 50/-; (d) Type 16H.T.56, 179/; (e) Type 36E.H.T.25, 11/9; (f) Type 36E.H.T.35. Rated 2.5 kv., 1 mA., 17/6; (g) Type 36E.H.T.100. Pulse rating 5/6 kv., 100 mA.

F/V Wave Bridge Rectifiers. For charging 2, 4 or 6 volt at 1 1/2 amps. 9/6 For charging 6 or 12 volt at 1 1/2 amps. 11/9 For charging 6 or 12 volts at 5 amps. 16/9 For charging 6 or 12 volts at 5 amps. 25/- For charging 12 or 24 volts at 5 amps. 29/6 A Variable Resistor for control of Charging Equipment (Model) up to 3 amps., 13/6; or up to 6 amps., 17/9.

Suitable Charger Meter, max. 4 amps., 7/6.

Meter Rectifiers. Westinghouse 250 micro/amp., 11/6; 1 mA., 10/6; 5 mA., 6/6.

Selenium Rectifiers. H.T./H. wave. 250 v. 50 mA., 5/6; 250 v. 100 mA., 7/6; 250 v. 170 mA., 13/9.

Charger Transformers. Suitable for use with preceding Rectifiers. Each has input of 230 volts. Outputs (a) 24 volts tapped 15 v. v. and 4 v. at 3 amps., 23/9; (b) 30 volts tapped 15 v. and 9 v. at 3 amps., 25/9; (c) 15 volts tapped 9 v. at 3 amps., 17/9; (d) 12 volts 1 1/2 amps., 11/9; (e) 15 volts tapped 9 v. at 6 amps., 23/-; 15 volts tapped 9 v. at 1 1/2 amps., 14/3; 12 volts 1 amp., 7/6.

A Battery Charger Wiring Diagram is included with purchase of Charger Transformer and Rectifier.

Adjustable Mains Droppers. 1 1/2 in. dia. x 2 1/4 in. (a) 15 amp., 1,500 ohms, 5/-; (b) 2 amp., 1,000 ohms, 4/3; (c) 3 amp. 600 ohms, 5/-.

Television. We keep a very comprehensive range of T.V. components. The Viewmaster T.V. Assembly Instructions showing Practical Layout and Price List is in stock price 5/6 (incl. post). We can supply all the specified components for the T.V. ex stock, either by way of individual components or by the published stages.

Maxi "Q" Chassis Cutters. The quickest and most simple method of chassis cutting, consists of a die, punch, and Allen screw.

To cut 1/2 in. dia. (B70)	10/6
To cut 1/2 in. dia. (B8a)	10/6
To cut 1/2 in. dia. (Octal)	13/6
To cut 1/2 in. dia. (English)	13/6
To cut 1/2 in. dia. (EP50)	14/6
Key for any of above	1/-
Adjustable Chassis Cutter for holes from 1/2 in. to 2 1/2 in. dia. (used with hand brace), 7/6.	

The "Handy-Utility" 1/2 in. Portable Electric Drill for use on A.C. or D.C. mains. A powerful and robust drill that will drill wood, metal, and almost anything, can also be used for grinding, buffing and wire brushing, etc. Employs instant release trigger switch. Price £6/10/-. Descriptive leaflet is available.

The New Pyrobit Soldering Iron, with instrument type bit, for use on A.C. or D.C. mains, 22/-. Spare elements and bits always in stock.

Components and many KITS OF PARTS for both Sets and Battery Chargers.

Approx. cost of Post & Packing.

115 FLEET STREET, E.C.4

5814 and 2280

UNIVERSITY RADIO

Offer Guaranteed Used Equipment at Attractive Prices

M.C.R.I., complete with coils, power pack, phones etc., as new	£8 0 0
Eversheds, 500 volt wee megger, in leather case, as new	£9 10 0
Garrard R.C.65, Record Changer as new	£16 10 0
Valradio Converter, 200/250 Volt D.C. = 200/50 Volts A.C. 300 watts, 75 cycles, works overhauled, as new	£11 10 0
E.D.C. Rotary Converter, 230 D.C. to 230 A.C., 200 watts with filter unit and silencing cabinet, perfect	£15 0 0
Avo 1948 Signal Generator, as new	£12 0 0
Avo Valve Testers, 1948/9, with roller panel as new	£12 0 0

Advance E.I. Signal Generator, as new	£17 0 0
Taylor 90 A. A.C./D.C. Test Meter, as new	£9 10 0
Taylor 120 AC/DC Test Meter, as new	£7 0 0
Avo Minor AC/DC, as new	£7 10 0
Pullen series 100 AC/DC Test Meter, as new	£8 10 0
Avo Model 7 as new	£14 10 0
Avo Model 40, as new	£12 0 0
Eddystone 640, as new	£22 0 0
Eddystone 504, as new	£36 0 0
B.S.R. Ribbon Mike, as new	£7 0 0
Hunts Bridge Model C.R.B. as new	£10 10 0
Avo 1949 Capacity and Resistance bridge as new	£8 0 0

Cossor Impedance Bridge Model 3389, as new	£19 10 0
Cossor Ganging Oscillator, Model 343, as new	£20 0 0
Pye workshop test rack, Ref. No. 940020 as new	£37 10 0
B.S.R. Latest Model Disc recording unit in portable case including playback, pick-up, and speaker, less amplifier as new cost £145	£75 0 0
C.D.P. Disc recording unit, less amplifier, with play-back, pick-up, latest model, as new	£27 10 0
Recording motor and 12 inch heavy turntable, 200/50 A.C. Perfect	£9 0 0

**WE NEED GOOD USED EQUIPMENT URGENTLY
PLEASE SEND, BRING OR PHONE FOR OFFER**

E.D.C. Rotary Converter, 12 volt D.C. to 230 A.C. 100 watts, 1 phase 50 cycles as new	£7 10 0
Ward Rotary Converter, 100/110 D.C. to 230 volts A.C., 250 watts, 1 phase 50 cycles, with built in filter unit, perfect as new	£17 10 0
As above, 230 D.C. to 230 A.C.	£17 10 0
Mico 5 watt amplifier, latest model M/C mike, and gram inputs in attractive metal sprayed case, complete with valves, as new	£10 10 0
Cossor double beam 'scope Model 339, as new	£45 0 0
Cossor as above, Model 3339	£36 10 0

Latest Model Avo Valve characteristic meter, complete as new	£40 0 0
"Hambander" Complete with valve as new	£12 10 0
"Legg" 2 Circuit Model F, 36/3 72 volts at 3 amps 72 volts as 2 amps, complete and perfect	£22 0 0
Charles latest model K.I. Amplifier, complete with valves, as new	£12 10 0
Trixette Portable Auto Change Record Player, with built in amplifier in portable rexine case, as new	£26 0 0

Decca portable Auto Change Record Player, containing Garrard R.C. 65 mixer changer with Decca lightweight head, as new	£21 0 0
Pam 25 Watt Amplifier, 2 Pam 8 Watt speakers in cabinets, Pam mike and floor stand, A.C. 200/50 as new	£35 0 0
We can supply Pam 12 volt car battery adaptor, for mobile use at	£10 0 0
Eddystone Model 740, perfect as new	£32 10 0
Eddystone Marine Receiver, 659/670, perfect, as new	£42 10 0

**WE NEED AR 88's - BC 221's - 348's - 342's ALSO
COSSOR DB'SCOPIES 339A OR 3339 ETC. WE WILL
PAY WITHIN £2.0.0 OF THE MARKET PRICE**

Latest Model Grampian 50 watt Amplifier, Type 476, 4 M/C. Mike inputs, Gram and radio inputs complete and as new with line transformers	£45 0 0
Triplet Combination Tester, Model 1183-SC complete with leads etc., as new	£13 10 0
U.H.F. Signal Generator, Type T.F./517 E, by Marconi Instruments, as new	£27 10 0
U.S.A. Signal Generator, in metal case, Ranges 100-32000 K.C. as new A.C./110/250 A.C.	£18 10 0
Taylor Valve Tester, Model 47A several extra valve adaptors, charts etc. complete and perfect as new	£20 0 0

Barker 150 Speaker in Barker Phase inverter cabinet as new	£28 10 0
Labgear Electronic Fault Tracer. Type B.525.C complete and as new	£19 10 0
B.C. 342, as new unconverted-complete with valves	£21 0 0
B.C. 348 as above	£21 0 0
Eversheds Bridge Megger, 500 volts built in resistance box as new and perfect	£25 0 0
12 inch Heavy Recording Turntable, new	£4 0 0
R.107 with built in S. Meter complete and as new	£14 0 0
Decca "Decallion" non Auto Record Player, with built-in amplifier perfect, as new	£19 0 0

Vitavox K12.20, as new	£8 0 0
As above K/12.10	£5 5 0
Goodmans "Audiom 60" as new	£5 0 0
Goodmans "Audiom 150" as new	£7 0 0
Wharfedale W.10.C/S, 3 or 15 ohms.	£6 0 0
Latest Model Avo Wide Range Slg. Gen. as new	£23 0 0
Weston E.772, 20.00 O.P.V. as new	£16 0 0
As above, Weston 1000 O.P.V.	£13 0 0
Taylor 65B Signal Generator, as new	£12 0 0
Pye Audio Oscillator, Type No. 940173 as new	£25 0 0

SPECIAL!

On receipt of 12 penny stamps we will send you our list of current goods for 13 weeks. This includes equipment which arrives daily and is not normally included in our advertisements.

THESE ITEMS ARE ONLY A SMALL SELECTION FROM OUR STOCK OF EQUIPMENT. YOUR ENQUIRIES FOR ANYTHING THAT YOU MAY NEED WILL BE WELCOME WE HAVE OTHER EQUIPMENT ARRIVING DAILY!

Stamped addressed envelope, please.

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE EXTRA.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

OUR BRANCH AT 39a (opposite) IS OPEN ALL DAY THURSDAY

Phone: GERRARD 4447, 8582 and 5507. Hours 9 to 6. Thursdays 9 to 1.

GARLAND BROS

AMPLIFIER ACIII. Further deliveries enable us to offer a limited number of kits for this popular amplifier. Specification : 7 valves (including rectifier). 10 watts push-pull output to 3 ohm or 15 ohm speaker. Supply available for tuner unit, etc. High and low gain inputs. Separate Bass and Treble controls. Negative Feedback. Varley mains and output transformers. Complete kit, with circuits and instructions, including circuit of suitable local-station quality tuner, £8/19/6, plus carriage 5/-.

TAPE DECK AMPLIFIER UE6. A six-valve record-playback amplifier suitable for use with high or low impedance heads. Features include variable bass and treble lift, recording level indicator and built-in oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes. Supplied in kit form, with punched chassis, all valves, components, circuits and full instructions. £10/10/-, plus carriage 5/-.

TAPE DECK AMPLIFIER HNES. A five-valve record-playback amplifier suitable for use with high impedance heads. With built-in oscillator supplying h.f. bias and erase. Supplied in kit form, with punched chassis, all valves and components, circuits and full instructions. £7/10/-, plus 5/- carriage.

MODIFICATION KIT UE2. Enabling the use of Amplifier ACIII as a high-quality tape record-playback amplifier, for use with high or low impedance heads. Incorporating pre-amplifier, oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes and recording level indicator. In kit form, with all valves, components, punched chassis, circuits and full instructions £4/4/-, plus 5/- carriage.

LANE PRECISION BUILT TAPE TABLE. High fidelity high impedance record-playback and erase heads in mumetal shields. Heavy balanced flywheel giving freedom from "wow" and "flutter." Fast rewind. Heads are half-track, giving one hour's playing time with 1,200-foot reel of tape. £16/10/-, plus carriage, etc., 10/-.

MAGNETIC RECORDING TAPE. Emitape, 600ft., 15/- ; 1,200ft., 25/- . Durex, 1,200ft., 35/-.

SPARE TAPE REELS. 7in. (1,200ft.) plastic, 4/- each.

MAGNETIC RECORDING HEADS. High impedance half track heads, in mumetal shields. Record-playback, £2/10/- . Erase, £2/2/-.

AMPLIFIER II/66. An improved version of our Amplifier ACII, for those who desire good quality reproduction at low cost. Valve line-up is 6J5-6J5-KT66-5Z4. Output 5 watts. Volume, tone and variable feedback controls. High grade output transformer. Chassis completely isolated from mains. Complete kit, including punched chassis, all valves and components, with circuits and instructions, £5/2/6. Amplifier wired and tested, £6/2/6.

DECCA THREE-SPEED GRAM MOTORS. For 33 $\frac{1}{2}$, 45 and 78 r.p.m. Instant single-lever speed selection. For A.C. only, 100-250 v. 50 cycle operation. Price (incl. P.T.), £7/3/4. (Please note manufacture of two-speed model now discontinued.)

DECCA TURNOVER PICKUP. A high fidelity crystal pickup with turnover head (two sapphires) for use on the above or other multi-speed motors. Price (incl. P.T.), £3/19/4.

CHANCERY LONG-PLAYING ATTACHMENT. Enables you to use long-playing 33 $\frac{1}{2}$ r.p.m. records on your existing record-player. Easily fitted. Price £3/12/6.

GERMANIUM DIODES. Latest sub-miniature wire-ended glass-enclosed type, by a leading manufacturer. Minimum life 10,000 hours, low shunt capacity, no heater supply required. Special offer at 5/6 each, or £3 per dozen.

METAL RECTIFIERS TYPE RM2. The latest type rectifier. 125 v. at up to 100 mA. (depending on temperature). Dimensions : 1 $\frac{1}{2}$ in. (diam.) x $\frac{3}{8}$ in. Two of these in series required for mains voltage. Price 4/- each.

HIGH-CAPACITY PRECISION MICA CONDENSERS. By leading manufacturers. Accuracy plus or minus 0.5 (point five) per cent. of stated value. Pure mica and copper foil.
(c) 0.035020 μ F, 1/6 ; (d) 0.040710 μ F, 1/6 ; (f) 0.065350 μ F, 1/6 ; (f1) 0.082910 μ F, 1/6 ; (g) 0.087460 μ F, 1/6 ; (h) 0.108435 μ F, 1/9 ; (i) 0.123750 μ F, 1/9 ; (j) 0.147000 μ F, 1/9 ; (k) 0.205276 μ F, 2/-.
No further stocks (a), (b), (b1) or (e). Many close tolerance standard values may be made up by parallel or other combinations of above, e.g., 4J+2K=1 μ F ; 2k+g=0.5 μ F ; c+f=0.1 μ F. (A table of over 150 series, and parallel combinations of these condensers, invaluable on calculating filter networks, etc., is available on receipt of 2 $\frac{1}{2}$ d. stamp.)

CLOSE TOLERANCE SILVER-MICA CONDENSERS. 10,000 pF (0.01 μ F) plus or minus 2%. Ideal for service bridges, etc., 1/- each, 9/- per doz., £4/10/- per gross.

JUNERO ENGRAVING TOOL. Engraves steel and other metals plastics, wood, etc. By the makers of the famous Junero Multi-Purpose Tool. For A.C. mains, 200-240 v. Complete, ready to plug in. 12/6.

TWO-GANG CONDENSERS. .0005 μ F, with fixing feet. Size 2 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. Spindle diameter $\frac{1}{16}$ in, spindle length lin. 7/9 each. Midget two-gang condensers 0.005 μ F with trimmers. Size 1 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. Spindle diameter $\frac{1}{16}$ in., spindle length lin. 8/6 each.

STABILIVOLTS. Type NS1. Voltage stabiliser and divider. Operating voltages 280 v., 210 v., 140 v., 70 v. ; max. electrode current, 80 mA. Each 10/-.

STABILIVOLT TYPE VS68. Similar to STV280/40. Operating voltages 280, 210, 140, 70 v. Max. electrode current 60 mA., 7/6 each or 78/- per doz.

CATHODE RAY TUBES. 5CP1, Electrostatic Intensifier-type C.R.T., diameter 5in. max. second anode voltage 2 kv., max. intensifier anode voltage 4 kv., medium persistence screen. Brand new in original crate or carton, 22/6 each.

AERIAL RODS. Copper plated steel. Fit into each other to make up any length aerial. Per doz., 2/- ; per gross, 18/- ; per thousand, £4/10/-.

HEATER TRANSFORMERS. Pri. 230 v., Sec. 6.3 v. 1.5 a., 7/6 ; Pri. 230 v. Sec. 12 v. 1 a., 7/6.

BAKELITE-CASED IGNITION SWITCHES. Type SC7547 Willswitch substantial currents at low voltage ; many useful applications. 1/3 each, 13/- per dozen, £6/10/- per gross.

VALVEHOLDERS. Ceramic : UX5 (807, etc.), 1/- each, 10/- doz ; UX7 medium (1625, RK34, etc.), 1/- each, 10/- doz. ; B9G (EF50, etc.), 9d. each, 7/6 doz. Amphenol : Int. Octal, 9d. each, 7/6 doz. ; Br. 7p, 9d. each, 7/6 doz. ; Br. 5p, 9d. each, 7/6 doz. ; UX7 med., 9d. each, 7/6 doz. ; UX5, 9d. each, 7/6 doz. Paxolin : Br. 5, Br. 7, UX4, UX5, UX6, UX7, 6d. each.

PULLIN MOTORS. Type A/3R. For 24 v. D.C. 3 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. x 2in., 8/6 each

METAL CUTTING SHEARS. A robust tool, one-inch blades, will cut up to 16 s.w.g. aluminium. Per pair, 2/- ; per doz. pairs, 21/-, per gross pairs, £11.

I.F. TRANSFORMERS. 465 kc., standard size, capacity-tuned. Made for us by a leading manufacturer. Per pair, 12/6.

CONDENSERS (pFs). 2, 4, 10, 15, 20, 25, 50, 75, 100, 160, 200, 6d. each, 5/6 per doz. 220, 300, 330, 500, 1,000, 5,000, 9d. each, 7/6 doz.

METAL-CASED CONDENSERS. 0.01/1,000 v. wkg., 9d. each, 7/6 per doz. 0.1/350 v. wkg., 9d. each, 7/6 per doz. Ditto, but screw-fixing and with long insulated leads, 9d. each, 7/6 per doz.

SMALL-SIZE PAPER CONDENSERS. 2 μ F 100 v. wkg., dimensions 1 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. x $\frac{3}{8}$ in. Ideal for cross-over networks, etc., 4/6 per doz., 45/- per gross, £14/10/- per thousand.

PAPER CONDENSERS. 1 μ F 500 v. wkg., 2 $\frac{1}{2}$ in. x 2in. x $\frac{3}{8}$ in. Inverted mounting, 1/- each, 9/- per doz., £3/12/- per gross. 1 μ F 600 v. wkg., 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. x 1in. Upright mounting, 1/6 each, 15/- per doz., £7 per gross.

TUNING CONDENSERS. 160 pF. (0.00016 μ F) maximum. Upright mounting, with four fixing feet, spindle $\frac{1}{16}$ in. diam., length 1 $\frac{1}{2}$ in. Ideal for the short-wave enthusiasts. 2/3 each, 24/- per doz., £12 per gross.

PLUGS AND SOCKETS. Pye angle, 1/- ; Pye straight, 1/3 ; B. & L. 5-pin, 1/6 ; B. & L. 7-pin, 1/9 ; Jones 6-way, 1/6 ; Jones 8-way, 1/9 ; E.H.T. Single, 1/- . The above prices include plug and socket in all cases. Pye T-pieces, 9d. Pye connectors, 9d. Pye Angle P. & S. to fit $\frac{1}{16}$ in. cable, 1/3 complete.

SPECIAL PURPOSE VALVES. VR116, 5/- ; VT501 (TT11), 6/6 ; CV73, 4/- ; 9003, 5/- ; 954, 3/- ; CV1141, 6/6 ; CV66, 6/6 ; VR136 (EF54), 7/6 ; VR137 (EC52), 7/6 ; VU111, 5/- ; VU133, 3/6 ; CV54, 3/6 ; E1148, 3/6.

FOR CALLERS ONLY. Emiscope Type 4/1 3in. Electrostatic C.R. Tube, as used in "Wireless World" Cathode Ray Oscilloscope with Wobblulator (December 1948 issue). Complete with holder, 12/6 each. (Reprints of above article available 7d. each) **Bomb Computers** : as widely advertised, contain 3 motors, hundreds of gears, aneers, etc., etc., 39/6 each (bring your car!). PT25H. High Output Pentode, 4 v. and 400 v., 5-pin British ceramic base. Also successfully used, strapped as replacement for 4 v. triodes in quality amplifiers. 7/6 for two

SLEEVING. 2 mm. oiled silk, etc., 3/6 per 24 nominal yard lengths, assorted colours, 33/- per two gross ditto

ALL GOODS NEW AND UNUSED OTHERWISE STATED. GOODS SHOWN AS EX-EQUIPMENT HAVE BEEN FULLY TESTED AND ARE IN GOOD WORKING ORDER. PLEASE ADD POST OR CARRIAGE ON ALL ITEMS. KINDLY PRINT NAME AND ADDRESS. POST ORDERS TO OUR DEPTFORD ADDRESS. EARLY CLOSING THURSDAY, OPEN ALL DAY SATURDAY.

GARLAND BROS

GARLAND RADIO

CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8

TELEPHONE : TIDEWAY 4412/3

ALLEN & GOULD

5 OBELISK PARADE, LEWISHAM, S.E.13

TELEPHONE : LEE GREEN 4038

R.1155 COMMUNICATIONS RECEIVER. The famous ex-R.A.F. Bomber Command set. Covers 5 wave ranges, 18.5-7.5 mcs., 7.5-3.0 mcs., 1,500-600 kcs., 500-200 kcs., 200-75 kcs., and is easily and simply modified for normal mains use, full details being supplied. These sets have had some use, but are all guaranteed tested and working before despatch, and are offered at ONLY £7/19/6 (carriage and packing 10/-). A factory-made-power pack with output stage, which operates the R1155 immediately, can be supplied for £5/5/-.

CLASS D WAVEMETER. Another small quantity has become available since our "sell out" a few months ago, and intending purchasers should act quickly. This is a really first-class crystal controlled wavemeter, which has been repeatedly reviewed and recommended in the "R.S.G.B." Bulletin. Covers 1.9-8 mcs., and is complete with 100/1,000 kc/s. crystal, 2 valves ARTH2, two 6-volt vibrators, and instruction manual. Designed for 6 v. D.C. operation, but modification data for A.C. supplied. BRAND NEW IN MAKER'S TRANSIT CASES. ONLY £5/19/6 (carriage, etc., 3/6). Transformer for A.C. modification, 7/6.

CHASSIS OF INDICATOR TYPE 96. A "snip" not to be missed. Contains 9 v-holders, 14 potentiometers, C.R.T. holder, high voltage condensers, and hundreds of resistors and normal condensers. Size 18 x 8 x 8 in. and contained in metal case. BRAND NEW. ONLY 12/6 (carriage, etc., 2/6).

SECTIONAL TELESCOPIC AERIAL, comprising 16 sections each 16 in. in length, and colour coded for easy assembly. Complete in web case. BRAND NEW. ONLY 9/6 (postage 1/-).

WALKIE-TALKIE CHASSIS TYPE 38. This beautifully made 6-valve chassis is offered as a summer "snip." Ideal for the enthusiast. As used by the Forces, with the exception of certain transmitting parts and crystals removed by the Ministry of Supply (no valves). ONLY 9/6 (postage 1/6).

PACKARD BELL PRE-AMPLIFIER. A first-class American job designed to increase the output of low gain microphones and pick ups. Most efficient. Contains two double valves, push-pull input and push-pull output transformers a relay, a choke, etc., etc. BRAND NEW IN MAKER'S CARTONS. ONLY 14/6 (postage 1/6), or with 2 spare valves, 22/6 (postage 1/6).

3½ in. 0-1 m/A. PANEL METER. Flush fitting with 50 division scale. BRAND NEW IN MAKER'S CARTONS. ONLY 15/- (postage 1/-).

PLESSEY P.M. SPEAKERS. 6½ in. with trans., 14/6; 8 in. less trans., 14/6 (postage 1/6). BRAND NEW.

CHOKES. 20 H. 80/120 mA., 6/6; 5 H. 200/300 mA., 6/- (postage 1/-).

GERMANIUM CRYSTAL DIODES. 5/-.

VR91 (EF50) ex New Equipment, and tested, 6/6; American Red Sylvanias, 8/6.

MAINS TRANSFORMERS. Standard primaries. Universal mounting, 350-0-350 v. 80 mA., 0-4-6.3 v. 4 a., and 0-4-5 v. 2 a., 18/6. Upright mounting, fully shrouded 250-0-250 v. 100 mA., 6.3 v. 6 a., 5 v. 3 a., 27/6 (postage 1/6 either trans.).

TRAIN TRANSFORMER. 200/240 v. Input, Output 30 v. 2 a. tapped 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v. 12 v., 15 v., 18 v., 20 v., 24 v., 19/6 (postage 1/6).

EHT TRANSFORMER for VCR97 tube, with 4 v. for tube heater, and 4 v. tapped 2 v. for EHT rectifier, 32/6 (postage 1/6).

6 in. MAGNIFYING LENS for VCR97 TUBE. First grade oil filled. ONLY 25/- (POSTAGE 1/6).

Cash with order please, and print name and address clearly. Amounts given for carriage refer to inland only.

U.E.I. CORPORATION
Radio Corner, 138 Gray's Inn Road,
London, W.C.I. Phone: TERMINUS 7937.

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

LAWRENCES

NEW SPECIAL PURPOSE AND TRANSMITTING VALVES. At 2/6. VR92, CV1116, CV1135, LD210, LP220, VR116, VR135, V872, 954, 7193. At 3/6. 2C26, 28D7, VR65A, VR66. At 5/- . VT135, VT288, VT133, 713A, 1619, 9004, 9006, AUS, CV66, VR137, VR136, VT51, VU111, VU133. At 6/6. VT65, VT90, VT94, 7C7, 7N7, VT268, VT209, 32, 955, CV1106, CV303, CV1124. At 7/6. 2X2, 3B26, 6AG5, 1G6GT, VT65G, VT69, VT134, CV925, 717A, 1625, VT162, VR56, NGT1. At 8/6. VT210, VT179, VR91, VR53, VT152, VT133. At 10/- . VT173, VT112, VT244, VT112, VT93, VT86, VT86A, VT96, VT107, VT92, VT229, CV2941, GTIC, CV1503, NR77, VR150/30. At 12/6. VT115, VT231. At 15/- . 721A, 724B. At 17/6. 866A. At 20/- . 805. At 25/- . 8025. At 30/- . 3BP1. At 60/- . 725A. At 85/- . 723A/B. Two or more valves post free, otherwise add 6d. All fully guaranteed. Quantity quotations upon request.

NEW GAS DISCHARGE TRIODES. Argon-filled. Type GTIC. Heater 4 v. 1.3 a. Anode 500 v. peak. 300 mA. peak. Control ratio 27. 10/- each. Also type NGT1. Heater 4 v. 1.75 a. Anode 350 v. peak, 1,000 mA. peak, average 200 mA. Tube voltage drop 20 v. Control ratio 40. 7/6 each.

BRAND NEW G.E.C. "MINISCOPE" M861B MINIATURE CATHODE RAY OSCILLOSCOPES. Self-contained, includes a 1½ in. C.R. tube, time base, sig. amp. and attenuator. Achieves max. versatility, compatible with min. of space. Operated from either 110 v. A.C. 50/100 c/s., 180 v. A.C. 500 c/s. or 200-250 v. A.C. 50/100 c/s. The tube employed gives exceedingly clear wave traces. Hard valve time base is employed with range about 10 c/s to 50,000 c/s., continuously variable steps. The amplifier embodied consists of resistance-capacitance coupled miniature valves with negative feedback. Overall gain approx. 150 with freq. range 50-30,000 cps. Three sig. in-put sockets for 10, 70 and 500 v. peak input with panel attenuator control. Panel controls for T.B. Off, T.B. Coarse, T.B. Fine, Sync., Y. Shift, X. Shift, Gain, Brill and Focus. Panel Terminals: Y. Plate, Sig. Out, T.B. Out, X. Plate, Sync. Out, Sync. In, Grid, Flyback black out. Dimensions 8½ x 6½ x 2½ in. Nett weight, 7½ lbs. Special unrepeatable bargain price, inc. leatherette covered carrying case, sockets, plugs, leads and instruction manual. Only £13/10/0 each, carriage paid. In sealed maker's cartons.

SPECIAL OFFER R.F. PENTODE VALVES, TYPE CV303. Heater 6.3 v. 2 a., V.A. 250 v., I.A. 6 mA., V.G.2 100 v., I.G2 1.7 mA., V.G1—2.5 v. RK 325 ohms. RA 1.2 meg., GM 2200. This modern versatile tube is of metal-cased construction similar to VR91, etc., only B8G base. Brand new in maker's cartons. Price 6/6 each. Special quotations for large quantities.

EDDYSTONE COMMUNICATION RECEIVER, TYPE 504. Wonderful performance on all bands up to 30 mcs. Features 2 RF amplifiers, "S" meter, Crystal Gate, V.F.O., Noise Limiter, etc., etc. Very slightly used, but as brand new in maker's carton with manual and speaker. £27/10/0.

GARRARD Model E RADIOGRAM UNIT. A.C. mains operated, fitted with magnetic pick-up and excellent quality motor or 200-250 v. A.C. As brand new in maker's carton. Only £7.

NEW AMERICAN 14ft. WHIP AERIALS. Superior pattern. 3 sections screw joints. Price 9/6 each.

NEW ROTARY ALTERNATORS. Input 24 v. D.C. Output 230 v. A.C. 50 c/s. Automatic voltage stabilization. Control panel is fitted with A.C. meter, fuses, etc. Suitable for operating radio, TV sets or PA eqpt. from accumulators or emergency use during power cuts. £5/10/0 each.

BRAND NEW RADAR P.P.I. UNITS, Type R7/AP52. Large eqpt., incredibly intricate construction, contains 42 valuable valves, including eight matched 6L6, also 6SN7, 6AC7, 5U4G, VR150/30, etc., tubes 5FP7, 2AP1, and innumerable quality parts. Good basis for amateur TV transmission work. In maker's cases at less than value of valves alone. £17/10/0 each.

NEW P.A. PARMEKO SPEAKERS. Superb quality, short horn, re-entrant type. Absolutely weatherproof. Fitted with matching transformer and three position tone switch voice-coil impedance 15 ohms. A fraction of cost at 48/6 each. Also alternative model as above, but twin-horn unit, 57/6. All in maker's cartons.

EXPERIENCED EXPORT SHIPPERS

*All prices include U.K. carriage. Terms C.W.O.
Satisfaction guaranteed or money immediately refunded*

LAWRENCES
61 BYROM ST., LIVERPOOL, 3
Telephone Central 4430

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

S-440-B V.H.F. TRANSMITTER CHASSIS

Partly stripped by the M.o.S., less valves, tuning coils and crystal but otherwise fairly intact. A fine basis for VHF Tx. or 144 mcs. rig. Original frequencies 85-98 mcs. valve types 3/RK34, 2/6N7 6V6. Housed in louvered case finished grey crackle. Dim. 14 x 8 x 7in.

CLYDESDALE'S PRICE ONLY **27/6** POST PAID
Circuit of S-440-B available at 1/3.

P.40 RECEIVER UNIT

With valves 4/EF34, EC52, 2/EF39, EB36, 6J5, 6V6, complete unit less crystal in grey louvered case 11½ x 5½ x 4½in.

CLYDESDALE'S PRICE ONLY **£3. 19. 6** POST PAID

S-451-B POWER UNIT

The Power Pack for the P.40 Receiver. Input 200/250 v. A.C. 40/60 c/s. Outputs 175 v. D.C. 60 mA. 12.5 v. Fully smoothed and rectified in grey louvered metal case 11½ x 5½ x 4½in.

CLYDESDALE'S PRICE ONLY **£1. 19. 6** CARRIAGE PAID

Circuit of P.40 and S-451-B available at 1/3.

6 way cable socket for P.40, @ 3/6 each.
5 pin chassis plug of same type, @ 1/- each.

COMMAND TRANSMITTER CHASSIS

Partly stripped by the M.o.S., less valves, coil winding, crystal and dynamotor, but otherwise fairly intact.

A fine basis for ideas in V.F.O. or Tx. Models BC-457 to BC-459 components identical, valve types 2/1625, 1626, 1629. Conversion suggestions and circuits supplied. In aluminium case dim. —7½ x 6 x 8½in. Wgt. 8½ lbs.

CLYDESDALE'S PRICE ONLY **15/-** POST PAID
Conversion suggestions and circuits available at 2/6

SPEECH MODULATOR BC-456

Command Modulator unit with valves, 1625, 1235, VR150/30 less dynamotor, otherwise complete in metal case 10½ x 7½ x 4½in. chassis depth 2½in.

CLYDESDALE'S PRICE ONLY **19/6** CARRIAGE PAID

Circuit for the BC-456 available at 1/3.

TEST EQUIPMENT IE-65-A

Command series Test Gear with 3 Antennas, 3 Test Units, Mod. BC-456-B (or E) with dynamotor, Antenna Relay, 2 Radio Control Boxes, 2 Racks, 6 Mountings, 1F Shunt Unit, Control Unit MC-237, and 17 Cable Assembly.

CLYDESDALE'S PRICE ONLY **£22. 10. 0** CARRIAGE PAID

MICROPHONET-17B

Made by Shore Bros. of Chicago, U.S.A.

Carbon handset mic. with press-to-talk switch, stowing hook, cord and jack plug as used with Command series, etc.

CLYDESDALE'S PRICE ONLY **30/-** POST PAID

CANADIAN No. 9 SET, MK. I.

with Power Supply Unit.

An eleven valve (7/ARF3, 2/128C7, 12Y4, 024), superb Receiver, with built-in calibrator, 1,000, 100 and 10 Kc/s. frequency range, 2 to 5 mcs., two slow motion pre-set channels, switched HT and "S" meter, RF and LF gain, B.F.O., etc., etc. Separate Power Unit operated from 12 v. D.C., 115 v. A.C. or 230 v. A.C., with spare kit, all valves, Aerial, Insulators. Headphones, all packed in wood case, 24 x 22 x 32ins.

CLYDESDALE'S PRICE ONLY **£10. 0. 0** CARRIAGE PAID

MORSE KEY U.S.A. PATT. TYPE C.J.B.

Made by J. H. Bunnell & Co. enclosed contact type, as used in American aircraft. Finish black crackle. Complete with contact and tension adjustments and capable of speeds up to 25 v.p.m. Dim. 2½ x 1½ x 2in.

CLYDESDALE'S PRICE ONLY **12/6** POST PAID

DINGHY TELESCOPIC MAST

A lightweight (4 oz.) mast for many uses, Car Aerial, Camera, Tripod, Fishing Rod, etc. Made of aluminium, 7 sections Closed 14½in. Extended 7ft. 6in. Diam. base ½in. top 7/16in.

CLYDESDALE'S PRICE ONLY **6/-** POST PAID

AERIAL INSULATORS LOA/1275

Black plastic chain insulators, 3 links, each 3½in. long 1½in. wide. Total length 7½in.

CLYDESDALE'S PRICE ONLY **1/6** per pair POST PAID

HAND GENERATOR 10 watt Mk. II

Designed for W8.48 and W8.18, driven by two handles, complete with operators seat. Speed should be 50/70 r.p.m. Smoothed outputs 162 v. 60 ma., 3.1 v. 3 A. and 12 v. Generator Dim. —5½ x 5½ x 6½in. wgt. 13 lbs. Leg w/seat dim. —33 x 6 x 2½in. wgt. 5½ lbs. Legs (2) dim. —20 x 4½in.

CLYDESDALE'S PRICE ONLY **45/-** CARRIAGE PAID

FLUXMETER WY.0023



Designed to calibrate the field of Magnets within the range of 500 to 4,000 gauss and to determine their polarity. Complete with probe unit and contained in a hard wood case with hinged lid and handle. Instructions on lid. Dim.: 12½ x 9 x 6in.

CLYDESDALE'S PRICE ONLY **£5** CARRIAGE PAID

ELECTRONIC IGNITION TESTER

Type V.E.D. Patt. 563562, made by English Electric.

A Cathode Ray Tester employing an entirely new technique in ignition testing of internal combustion engines. Enables the electrical performance of the entire ignition system to be observed on the screen of the Cathode Ray tube, while the engine is running. Will operate from 6, 12 and 24 volts D.C. or 230 v. A.C. Built into a black crackle case, with hinged front and carrying handle, dim.: 15½ x 8½ x 11½in.

CLYDESDALE'S PRICE ONLY **£35** CARRIAGE PAID

INDICATOR UNIT TYPE 217A

Containing 100 microamp fsd. 2½in. flush mtg. meter, dial calibrated in yards; vol. controls, toggle sw. etc., in metal case 6 x 4½ x 2in.

CLYDESDALE'S PRICE ONLY **25/-** POST PAID

CRYSTAL OVEN

Brand new, extremely sensitive with adjustable thermostat control and thermometer. Built into a cork lined metal box 12 x 6½ x 8½in. Wgt. 5½ lbs.

CLYDESDALE'S PRICE ONLY **£3. 19. 6** POST PAID

PUMP DESSICATOR ADM. PATT. 12128 FOR TELESCOPES AND BINOCULARS

Hand operated complete with spare gel cell and conn. tubes, 31-cc cap 480 ccs. fitted humidity gauge, reads 10-100% vacuum gauge 0/30in. In wood transit case 19½in. x 12in. x 9in.

CLYDESDALE'S PRICE ONLY **£5. 10. 0** CARRIAGE PAID

COOLANT PUMP. By Packard U.S.A.

A turbine type pump, directly driven from semi-ball point splined socket (by motor not supplied) clockwise rotation, with safety valve, sludge vent, etc. Dia. of turbine 6in. dia. of pump chamber, 8½in. depth 2in. Inlet and outlet dia. 1½in. Overall dim.: 11½ x 7½ x 13in.

CLYDESDALE'S PRICE ONLY **49/6** CARRIAGE PAID

FEATHERING PUMP 5U/402

Driven by 24 v. D.C. motor type C2801, through 2.1 reduction gear, fluid moved by two 12 tooth wheels. Safety valve fitted. Overall dimensions 12½ x 6 x 6in. Pumping rate: lubricating oil 2 gals. per min. approx. Air pressure: 4½lb. per sq. in. Oil pressure: over 100 lbs. per sq. in. Inlet ½in. Outlet ½in.

CLYDESDALE'S PRICE ONLY **£2. 10. 0** CARRIAGE PAID

MULTICORE CABLE

8 core, metal braided and PVC covered, 1/8 per yard. 6 core, metal braided and PVC covered 1/6 per yard. 2 core, metal braided 6d. per yard. Metal braided sleeved 3 mm. 1 yard long 3 for 1/-.

FOR EXPORT ONLY. WIRELESS SET No. 38 Mk. 2. BRAND NEW

A haversack type Transceiver range up to 5 miles. Frequencies 6-9 mcs. 5 valves: 4ARF12, ATP4, complete with Headphones, Throat Microphones, Aerials, Junction Box, Spares, Satchels and instruction card. 4 complete units packed in wood case 57½ x 14 x 14in. PRICE ON APPLICATION.

JEFFERSON-TRAVIS UF-2 TRANSCIEVER CHASSIS

Partly stripped by the M.o.S., less valves, tuning inductances, osc. connections, but otherwise fairly intact. A fine basis for a transportable type two way radio. Original frequencies 60-75 mcs. Valve types 2/4Y7, 12B5. The unit comprises two chassis, with controls and speaker mounted on chrome plated etched steel panels, housed in cabinet finished black crackle, dim.: 15½ x 18½ x 8½in.

CLYDESDALE'S PRICE **£2. 10. 0** CARRIAGE PAID
Circuit of UF-2 available at 1/9.

JEFFERSON TRAVIS UF-1 POWER SUPPLY

Complete self contained vibrator, Input 12 volts. Outputs 120/150 v. D.C. 30/50 ma. Choke capacity smoothed and 2 L.T. taps. Unused but vibrator contacts stuck due to long storage. Complete with synchronous vibrator, smoothing cond. etc., in metal case dim.: —7 x 3 x 4in.

CLYDESDALE'S PRICE ONLY **19/6** CARRIAGE PAID

12 VOLT MOBILE AMPLIFIER UNIT

Made by Parmeko, uses EF36, EC31 and 2 EL33 in Class AB1 push pull. Dynamotor powered, controls, combined Mic/Gram gain, separate H.T. and L.T. switches, built in metal case finished grey. Dim. 12 x 9½ x 10½in.

CLYDESDALE'S PRICE ONLY **£9. 9. 0** CARRIAGE PAID

AMPLIFIER A1271 10U/549



A one valve (VR56 = EG36) Amplifier Chassis, with 400 ohm, 4M 2B relay, 2 transformers, vol. control, cond., and resistors, mounted on rubber in a black finished metal case, 5 x 5 x 4½in. All conn. brought to 4, 6 and 12 p. plugs. CLYDESDALE'S PRICE ONLY **10/6** POST PAID

Order direct from:—

CLYDESDALE SUPPLY 2 BRIDGE STREET

CO. LTD. GLASGOW - C5

Phone: South 2706/9 Branches in Scotland, England and Northern Ireland.

RADIO SUPPLY CO.

15, WELLINGTON STREET, LEEDS, 1.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/2 charged on orders under £2. Open to callers 9 a.m. to 5.30 p.m., Sats., until 1.0 p.m.

R.S.C. MAINS TRANSFORMERS

Fully Guaranteed, Interleaved, and Impregnated. Primaries 200-230-250v., 50 c/s. Screened.

DROP THROUGH TYPES WITH TOP SHROUD	
260-0-260 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.	12/11
350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.	14/11
350-0-350 v. 80 ma., 0-4-6.3 v. 2 a., 0-4-5 v. 2 a.	18/9
260-0-260 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a.	19/9
350-0-350 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a.	19/9
250-0-250 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a.	21/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion	23/11
350-0-350 v. 100 ma., 6.3 v. 4 v. 4 a. C.T. 0-4-5 v. 3 a.	21/11
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a.	25/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a.	27/11
FULLY SHROUDED UPRIGHT MOUNTING	
250-0-250 v. 60 ma., 6.3 v. 2 a., 5 v. 2 a., Midget type 24-3-3in.	16/9
350-0-350 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.	18/9
350-0-350 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a., 0-4-5 v. 3 a.	23/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for 1355 Conversion	26/9
300-0-300 v. 100 ma., 6.9 v. 4 v. 4 a. C.T., 0-4-5 v. 3 a.	23/9
350-0-350 v. 100 ma., 6.3 v. 4 v. 4 a. C.T., 0-4-5 v. 3 a.	23/9
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a.	27/9
350-0-350 v. 150 ma., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a.	29/11
350-0-350 v. 250 ma., 6.3 v. 6 a., 4 v. 8 a., 0-2-6 v. 2 a., 4 v. 3 a., for Electronic Eng. Televisor	63/-
425-0-425 v. 200 ma., 6.3 v. 4 v. 4 a. C.T., 6.3 v. 4 v. 4 a. C.T., 0-4-5 v. 3 a., suitable Williamson Amplifier	47/6
325-0-325 v. 20 ma., 6.3 v. 0.6 a., 6.3 v. 1.5 a., for Williamson Preamplifier	17/6

FILAMENT TRANSFORMERS	
All with 200-250 v. 50 c/s. primaries: 6.3 v. 2 a., 7/6; 0-4-6.3 v. 2 a., 7/9; 12 v. 1 a., 7/11; 6.3 v. 3 a., 10/11; 6.3 v. 6 a., 16/9; 0-2-4-5-6.3 v. 4 a., 16/9; 12 v. 3 a. or 24 v. 1.5 a.	16/9
CHARGER TRANSFORMERS	
All with 200-230-250 v. 50 c/s. Primaries: 0-9-15 v. 1.5 a., 12/9; 0-9-15 v. 3 a., 15/9; 0-9-15 v. 6 a., 21/9; 0-4-9-15-24 v. 3 a., 21/9; 0-9-15-30 v. 3 a.	22/9
SMOOTHING CHOKES	
200 ma. 5 h. 100 ohms	7/6
100 ma. 10 h. 100 ohms	7/6
90 ma. 10 h. 100 ohms	7/6
80 ma. 10 h. 350 ohms	5/6
50 ma. 50 h. 1500 ohms. For Williamson Amp.	8/6
AUTO TRANSFORMERS	
100 watts 110-200-230-250 v.	19/9
FILAMENT AUTO TRANSFORMERS	
6.3 v. to 4 v. 3 a. or 4 v. to 6.3 v. 3 a.	7/11
ELIMINATOR TRANSFORMERS	
200-250 v. 50 c/s input, 120 v. 40 ma. output	7/9
OUTPUT TRANSFORMERS	
Midget Battery, Pentode 66: 1 for 354, etc.	3/6
Standard Pentode 8,000 ohms to 3 ohms	4/9
Multi ratio 40 ma., 30: 1, 45: 1, 60: 1.	5/3
90: 1 Class B Push-Pull	9/11
Push-Pull 8 watt 6V6 to 3 ohms	9/11
Push-Pull 10-12 watts 6V6 to 3 or 15 ohms	15/11
Push-Pull 10-12 watt to match 6L6, PX4, 6V6, etc., to 3-5-8 or 15 ohm speaker	15/11
Push-Pull 15-18 watt to match 6L6, etc., to 3 or 15 ohm speaker	21/9
Williamson type exact to author's spec.	72/-
SPEAKERS P.M. 5in. 2-3ohms.	14/9
M.E. 8in. 2-3 ohms. (Field 600 ohms.)	12/9

RECEIVER CHASSIS, 16 s.w.g., Aluminium: 10-51-2in., 3/3; 11-6-2in., 3/9; 12-8-2in., 4/6; 16-8-2in., 5/8; 20-8-2in., 7/6

AMPLIFIER CHASSIS, 16 s.w.g., Aluminium: 12-8-2in., 6/6; 16-8-2in., 7/11; 20-8-2in., 10/6

MISC. ITEMS, T.V. Masks, 12in., White, 12/9. Ex Govt. Chokes, 100 ma., 10 h., 100 ohms., tropicalised 4/3 each, 45/- doz. Ex-Govt. Selenium Rects. (Ex-New Equip.), 120 v. 40 ma., H.W. 3/6 each; 250/500 v. 100 ma., 6/11. Ex-Govt. Receiver Units, type 71, less valves, 7/6. Vol. Controls 200K less Sw. long spindle 1/6. Sectional Aerial Rods, Copperised steel lft. in length, in. diameter, 1/11 doz., 15/- gross; 0.1 mid., 1,000 v. Tubs, 5/6 doz.

BAKELITE CABINETS. Premier type 12-61-5in. (Supplied complete with back). Brown or ivory 18/6. Following parts sold only with cabinets: Fully punched T.R.F. chassis 4/6. Ditto Superhet 4/9. L and M, 3 colour glass dials 1/11, L, M and S, 2/3. Back Plates and Brackets 1/3 set. S.M. Drum Drives 2/3.

SPECIAL OFFERS
Mains Transformers, 230 v. input 320 v. 70 ma. auto output and 6.3 v. 3 a. 8/6, 200-250 v. primary Secs. 300-0-300 v. 80 ma. 4 v. 4 a., 4 v. 3 a. 11/11. 230 v. primary 6.3 v. 1.5 a. sec. 5/9. Smoothing chokes 80 ma. 40 h. 250 ohms. 4/6. Electrolytics 8 mfd. 350 v. 1/11.

FULL RANGE OF STANDARD COMPONENTS AVAILABLE AT KEEN PRICES. ALL GOODS GUARANTEED AND NEW, UNLESS OTHERWISE STATED. WE CAN QUOTE FOR ANY TYPE OF CHOKE OR TRANSFORMER. (EXCEPT E.H.T.). S.A.E. PLEASE WITH ALL ENQUIRIES. FULL STOCK LIST, 4d. SPECIAL LIST FOR TRADE, 4d.

TRANSMITTERS 1154 3 band in transit case, £7/10/-, carriage paid.

RECEIVERS, TYPE 1155, £12, carriage paid.

SPEECH AMPLIFIER (British made) for Transmitter R.C.A. ET4336, complete with all valves, £26 ea.

BENDIX FREQ.-METERS TYPE BC221, complete £30 ea.

AR88 RECEIVERS (LF), £50 each.

TUNING UNITS FOR BC375E TRANSMITTER. TUS-6-7-8-9-10 and 26B, 22/- each.

IDEAL 25-WATT TRANSMITTER, Army Type No. 12. Frequency coverage 1-17.5 Mc/s. in your switched bands, C.W. and phone, built-in modulator. Operated from A.C. mains 100-250 volts, complete with all tubes and delivered, £25 each.

WAVEMETER CLASS D, No. 1 (for use with VS19 and 22). 2 bands 1900 kc/s—4000 kc/s. and 4000 kc/s.—8000 kc/s. Also 1 Mc/s Check points. Operates from 6 volt D.C. supply. £7/10/- each. Carriage paid.

BC610 FUSES. Edison screw fitting, 1/6 ea.

HALLICRAFTER MAINS TRANSFORMERS, for S20 Receivers, 32/6.

HALLICRAFTER OUTPUT TRANSFORMERS, for S27 Receivers, 22/6.

LORD MOUNTINGS (Rubber to steel shock absorbers), set of four 1/6. Enquiries for large quantities invited.

McELROY-ADAMS MFG. GROUP LTD.

(Sole concessionaires, U.K. for Halli-crafter communication equipment,

46 GREYHOUND ROAD, LONDON, W.6.

Cables: Halli-crafter, London.

Phone: FULham 1802.

EX GOVT. & SURPLUS GOODS

Aerials, 3-4ft. sections make good fishing rods	...6/6 each
10-way Spanners for large or small nuts1/0 "
Goggles with case, for motor cycle or welding2/6 "
8 mfd. Paper Electrolytic Condensers. NEW	...3/6 "
8 x 8 mfd. Metal Electrolytic Condensers. NEW	4/6 "
5-inch Speakers, Plessey15/6 "
6½-inch Speaker, R. & A.15/6 "
Speaker Transformers, Tapped5/0 "
2-volt Accumulators, small capacity4/6 "
½-meg. Vol. Controls, small, with switch5/0 "
Small White Knobs7/0 doz.

CASH WITH ORDER. INCLUDE 1/- postage under £1.

MAYCO ELECTRIC,

43, ROSEBERY AVENUE, LONDON, E.C.1

PRATTS RADIO

1070 Harrow Road, London, N.W.10
(N. SCRUBBS LANE)




MODEL AC10E 99/15/-

31, LADBROKE 1734
AMPLIFIERS. College general purpose units. MODEL AC10E. 4 valve 10 watts. Neg. feedback. £9/15/- MODEL AC10BE, 6 valve; 16½ watt P/P output. Feedback over 3 stages. £14/14/- MODEL AC32E, 32 watts P/P output. Feedback over 3 stages. £17/17/- MODEL U10E, for DC/AC mains, 6 valve 10 watt P/P output. Feedback over 3 stages. £12/12/- All are complete with cases and chrome handles. They have a separate microphone stage. Separate inputs for mike and gram., allowing individual mixing, etc. Output match 3, 8 or 15 ohm speakers. Max. input volts required for full stated output average Mike .003, Gram. .3 v. MODEL AC8C, 5 valve P/P 8-10 watt unit for records, radio, etc. Feedback over 3 stages. Output to 3, 8, 15 ohms. £9/13/6. MODEL AC4C, 3 valve record/radio amplifier, 4 watts to 3 ohms. £5/5/- Ditto U4C for DC/AC mains. £5/5/- Stamp for list. Full range of accessories available, including: Rothermel Crystal Mikes, 105/-; Goodman's 12in. P.M. speaker, £6/15/-; Coliario A.O. Record Players, rim drive, magnetic model, £6/8/-; Crystal, £6/15/-; Jack plug 1/6 each extra. Nearest Station: Kensal Green.

Recognised as the Most Reliable Valveholders

Sub-Miniature Valveholders

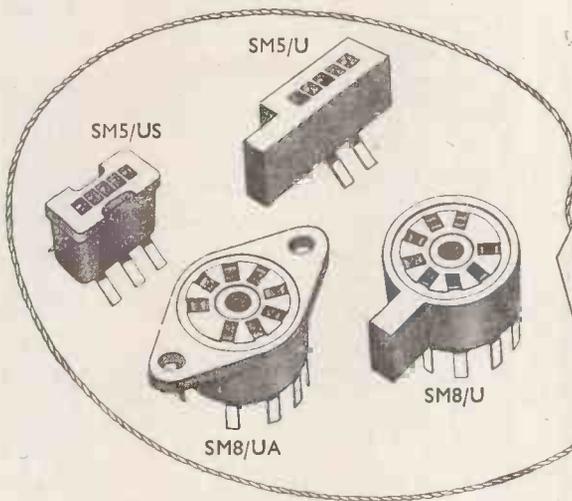

All Moulded in Silica-loaded Polystyrene

- B5A TYPES
 - SM5/U. Panel Mounting
 - SM5/US. Chassis Mounting
- B8D TYPES
 - SM8/U. Panel Mounting
 - SM8/UA. Chassis Mounting

Wholesale Enquiries:—CYRIL FRENCH LTD., HIGH STREET, HAMPTON WICK, MIDDLESEX · KIN. 2240
 Manufacturers' Enquiries:—THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY ASHTEAD 3401

GALPIN'S ELECTRICAL STORES

408 High Street, Lewisham, London, S.E.13

Telephone: Lee Green 0309

Near Lewisham Hospital

Terms:

CASH WITH ORDER. NO C.O.D.

EARLY CLOSING DAY THURSDAY

ALL GOODS SENT ON 7 DAYS; APPROVAL AGAINST CASH

ALTERNATORS. 2.7 kilowatts, 110 volts, 50 cycles, 3-phase, complete with exciter generator and switchboard, £25 each, carriage forward.
EX-RADAR MAINS TRANSFORMERS. 230 volts, input 50 cycles, 1 phase. Output 4,500-5,500 volts approx., 30 m/amps., 6.3 volts 2 amps., 4 volts 1½ amps., 2 volts 2 amps.; these transformers are new, immersed in oil. Can be taken out of the oil and used as television transformers, giving an output of 10 m/amps.; overall size of transformers, separately, 5½ x 4½ x 4in. and 3 x 3 x 2½in., price £3/10/- each, carriage paid.
EX-RADAR TYPE 101 R.F. UNITS (new). Containing 6 valves, including grounded grid triode F.H.P., 24 volt universal motor, numerous resistances and condensers, etc., 35/- each, carriage 3/6.
RECTIFIERS (new). D.C. A.C. Input 50 cycles, 1 phase. Output to match the required voltage for the rectifier, £15 per set., carriage 10/-.
VORTEXION 15-WATT AMPLIFIERS (portable, new). Mains 200-250 volts A.C. or stand-by voltage of 12 volts D.C., suitably matched for either M.I. or Crystal pickup and microphone. Outputs matched for 7½ or 15 ohm speakers, £17/10/- each, carriage 7/6.
MAINS TRANSFORMERS (new). Suitable for spot welding, input 200-250 volts, in steps of 10 volts. Output suitably tapped for a combination of either 2-4-6-8-10 or 12 volts at 50-70 amps., 87/6 each, carriage 7/6.
EX-NAVAL ROTARY CONVERTERS. Input 110 volts D.C. Output 230 volts A.C., 50 cycles 1 phase, 800 watts, capable of 50 per cent. overload as new, crated weight 2½ cwt., price £25 each, carriage forward. Another ex-naval type 110 volts D.C. input. Output 230 volts A.C., 50 cycles, 1 phase, 250 watts, capable of 50% overload, weight 100 lb., price £10/10/- each, carriage forward.
MAINS TRANSFORMERS (New). Input 200/250 volts in steps of 10 volts Output 350-0-350 volts, 300 m/amps., 6.3 volts 8 amps. twice, 4 volts 4 amps., 5 volts 4 amps., 65/- each, carriage 3/6. Ditto, 450-0-450 volts 250 m/amps., 6.3 volts 8 amps. twice, 4 volts 4 amps., 5 volts 4 amps., 65/- each, carriage 3/6. Another input as above. Output 500-0-500 volts 250 m/amps., 6.3 volts 8 amps. twice, 6.3 volts 4 amps., 4 volts 4 amps., 5 volts 4 amps., 70/-, carriage 3/6. Another, wound to (electronic) specifications, 350-0-350 volts 250 m/amps., 4 volts 8 amps., 4 volts 4 amps., 6.3 volts 8 amps., 0-2-6.3 volts 2 amps., 63/6 each, carriage paid. Another, input as above. Output 500-350-0-350-500 volts 250 m/amps., 6.3 volts 6 amps., 0-2-6.3 volts 2 amps., 0-4-5 volts 4 amps. twice, 67/6 each, carriage 3/6.
PRE-PAYMENT I/- SLOT METERS. 200-250 volts A.C., 50 cycles, 1 phase, set at 3d. per unit, 60/- each, carriage 5/-. Ditto for D.C. mains, 45/- each, carriage 5/- (all 20 amp. load).
SWITCHBOARD METERS. 4in. scale Moving coil (D.C.) only, 0 to 14 amps., 17/6 each, post 1/6. Ditto, A.C./D.C., 22/6 each, post 1/6. Another 0 to 30 amps., A.C./D.C., 25/-, post 1/6.
MAINS TRANSFORMERS (new). Input 200-250 volts in steps of 10 volts, output 350-0-350 volts 180 m/amps., 4 volts 4 amps., 5 volts 3 amps., 6.3 volts 4 amps., 39/6 each, post 1/6. Another 350-0-350

volts 180 m/amps., 6.3 volts 8 amps., 0-4-5 volts 4 amps., 39/6 each, post-1/6. Another 500-0-500 volts 150 m/a., 4 volts 4 amps. C.T., 6.3 volts 4 amps., C.T., 5 volts 3 amps., 42/6 each, post 1/6. Another 425-0-425 volts 160 m/amps., 6.3 volts 4 amps., C.T. twice, 5 v. 3 amps., 42/6 each, post 1/6.
ELECTRIC LIGHT QUARTERLY TYPE CHECK METERS. All for 200-250 volts A.C., 50 cycles, 1 phase, 5 amp. load, 17/6 each, post 1/6; 10 amp., 21/- each, post 1/6; 20 amp. load, 25/- each, post 1/6.
SLIDER VARIABLE RESISTANCES. 14 ohms, 1 to 4 amps., 12/6 each, post 1/-. Another 0.4 ohms 25 amps., 10/- each, post 1/6. Another 90 ohms 4 amps., twin bar type, 30/- each, carriage 3/6. Another 1925 ohms 0.3 amps., 25/- each. Post 1/6.
MAINS TRANSFORMERS (new). 200-250 volts input, in steps of 10 volts. Output 0, 6, 12, 24 volts 6 amps., 37/6 each, post 1/6. Another as above, but 10-12 amps., 48/6 each, post 1/6. Another, as above, but 25-30 amps., 70/- each, carriage 3/6. Another input as above, output 0, 18, 30, 36 volts 6 amps., 42/6 each, post 1/6.
FIRST GRADE MOVING COIL METERS (switchboard). 6in. scale, 0 to 10 volts, 25/- each, post 1/6; 0 to 75 volts, 27/6 each, post 1/6; 0 to 200 volts, 27/6 each, post 1/6.
ELECTRIC MOTORS, FAN TYPE. 110 volts D.C., 7/6 each, post 1/6.
RELAYS, small type, 1,200 ohm coils, platinum points, 2 M. and B., 8/6 each.
ROTARY CONVERTORS. 24-28 volts D.C. input, 1,200 volts 70 m/amps. D.C. Output 10/- each, P.F.
AUTO WOUND VOLTAGE CHANGER TRANSFORMERS. Tapped 0-110-200-230 volts 350 watts, 48/6 each, post 1/6. As above but 500 watts, 62/6 each, carriage 3/6. As above 200 watts, 35/- each, post 1/6. 1,600 watts, tapped 0-110-150-190-230 volts, £5/5/- each, carriage 5/-.
DU-COIN VARIABLE TARIFF 1/- — 1d. SLOT METERS. 200-250 volts A.C., 50 cycles, 1 phase, 5 amp. load. Tariff can be varied from ½d. to 1/3d. per unit. Data sheet supplied, 45/- each, carriage 3/6.
DOUBLE WOUND VOLTAGE CHANGER TRANSFORMERS. 3,000 watts, 110 to 240 volts or vice versa, weight 100 lb., £10/10/- each, carriage 10/-.
BOOSTER TRANSFORMER. Auto-wound tapped 0-6-10-19-175-200-225-250 volts 1,500 watts, £5/5/- each, carriage 5/-.
EX-W.D. SURPLUS METERS. 2in. scale 0 to 20 volts, 6/6 each, post 6d.; 0 to 40 volts, 7/6 each, post 6d. (both moving coil). Thermo coupled, 0 to 350 m/amp., 7/6 each, post 6d.
SWITCHBOARD. 4in. scale Amp. meters, moving coil meters, 100 to 250 amps., complete with shunt, 30/- each, post 1/6.
EX-W.D. CHARGER UNIT 110-125 volts A.C., 50 cycles, 1 phase input, output 24 volts 50 amps. D.C., £30, carriage forward.

Henry's

RADIO COMPONENTS
ELECTRONIC
& TELEPHONE
EQUIPMENT

RECEIVER TYPE 25. The receiver portion of the T/R 1196. Covers 4.3-6.7 Mc/s, and makes an ideal basis for an all-wave receiver, as per *Practical Wireless*, August, 1949, issue. Complete with valves type EF36 (2), EF39 (2), EK32 and EBC33. Supplied complete with necessary conversion data for home use, 35/-, new condition. Chassis only 8/6.

PLESSEY. 3in. P.M. Speaker with miniature O/Trans., 17/6. W.B. 2 1/2in. P.M. 3 ohms, 1/trans., 15/-.

R.3515 I.F. STRIP. A complete I.F. Unit comprising 6 SP61 I.F. Stages, tuned to 13.5 Mc/s., 1 EASO diode detector and 1 EF36 or EF39 output or video stage. A few modifications only are required to adapt this unit, which will give pictures of extremely good quality. Price, complete with valves and foolproof modification instructions is 45/-, plus 5/- carriage and packing. Limited quantity only.

5CPI C.R. TUBES. Brand new and boxed, 25/-, carriage paid.

3 BPI C.R. TUBE, complete with base and shield in holder with leads, 30/-, Brand new.

3547-RECEIVERS. Absolutely brand new, in sealed manufacturers' packing cases. Incorporating 15 valves type EF50, 2 of SP61, EF36, EBC33, 3 of EB34. Complete 45 Mc/s. I.F. Strip, motor dial and drive, pots, etc., etc., £6 only, plus 10/- packing and carriage. Whilst they last!

TYPE 25 R.F. UNIT. Brand new, converted from new R.F.24, 19/6 (carriage and packing, 1/6).

This unit can now also be supplied modified to cover R.F.26 frequency (for Midlands T/V), brand new, at 25/-.

MIDGET .0005 mfd. TWO-GANG TUNING CONDENSER. Size only 2 1/2in. x 1 1/2in. x 1 1/2in. Capacity guaranteed, standard length 1/2in. spindle, complete with mounting bracket, less trimmers, 6/6, or complete with "built-in" trimmers, 7/6, each, plus 6d. post.

GERMANIUM CRYSTALS, complete with circuit diagram, 4/6.

MIDGET TWO-GANG .0005 WITH 4 W. PUSH BUTTON, 8/6.

5 mA. METER RECT., 6/-. W.6 and WX6, 1/6.

RECEIVER R.1355 as specified for "Inexpensive Television." Complete with 8 valves VR65, and 1 ea. 5U4G, VU120, VR92, and a copy of "Inexpensive TV." ONLY 55/- (carriage, etc., 7/6).

RECEIVER TYPE 21. The receiver portion of the W/S 21 operating from 4.2-7.5 Mc/s. Double superhet from 18-30 Mc/s. Incorporating B.F.O. and crash limiter. Valve line-up 7-ARPI2 (VP23) and 2-AR8 (HL23DD). Absolutely brand new, complete with circuit. Only 45/- complete. Vibrator power unit for above, brand new, 17/6 only.

No. 38 "WALKIE-TALKIE" TRANS/RECEIVER. Complete with throat Mike, 'phones, junction box and aerial rods in canvas bag. Freq. range 7.4 to 9 Mc/s. All units are new and tested before despatch. As supplied to Overseas Police Forces, £4/19/6, carriage 2/6.

EF50 (VR91) BRAND NEW RED SYLVANIAN. 10/-, original boxes. British Types boxed, 8/6. Unboxed British Types, 6/-.

I.F. TRANSFORMERS. Manufacturers' surplus, Iron-cored, 465 kc/s. Size 4in. x 1 1/2in. x 1 1/2in. Per pair, 8/6, whilst they last.

INDICATOR TYPE 6. These units are brand new, in excellent condition and are all fitted with a VCR97 CRT, the tube which many constructors have put to T.V. use. Valves include 4/VR9 (EF50), 3/VR54 (EB34), plus a host of potentiometers and H.V. condensers, etc. The complete unit is enclosed in a metal box 18 x 8 1/2 x 7 1/2in. Price only £3/19/6, post paid.

VIBRATOR POWER UNITS, 2 volt. As for Canadian 58 set. Completely smoothed, output 1.5 v. L.T. and 90 v. and 180 v. H.T. at 35 mA. Complete in grey metal box. Size 8 x 3 1/2 x 4 1/2. 50/- only.

METAL RECTIFIERS. S.T.C. 300 volts 75 mA., 6/-. G.E.C., 6 volts 1 amp., 4/-. Westinghouse, 12 volts 2 amp., 12/6. Pencil Type E.H.T., 600 v. 1 mA., 4/7; 1,000 v. 1 mA., 6/-; 2,400 v. 3 mA., 15/-; 150, 500 v. 2 mA., 7/6.

FILAMENT TRANSFORMERS. All input 200/50 A.C. 6.3 v., 1.5 amp., 7/6; 1granic 6.3 v. 2 1/2 amp., 10/-; 6 v. or 12 v. 3 amp., 15/-; 6.3 v. 12 amp., 37/6.

MAINS TRANS. 250-0-250, 90 mA., 6.3 v. 3 amp., 5 v. 2 amp. Input 110/250, 20/-. Min. Mains Trans. 3 1/2 high by 3 by 2 1/2, fully shrouded. 250-0-250, 60 mA., 6.3 v. 3 amp., 5 v. 2 amp., 21/-.

Send stamp for current Component List—
Probably the most comprehensive in the trade

5, HARROW ROAD, LONDON, W.2

PADddington 1008/9 and 0401

G2AK This Month's Bargains G2AK

C.R. TUBES Type 5CPI brand new in cartons 17/6 each, plus 1/6 postage.

MOVING COIL HEADPHONES with moving coil microphone. Price 6/-. Post 1/-. Transformer to match 2/-. High resistance headphones, 4,000 ohms, 8/6 per pair. Post 1/-.

CABLE. 10ft. length flexible T.R.S. 3-core. Fitted with 3 position switch and plug. 1/6 post free.

TWIN RIBBON FEEDER. Heavy duty 300 ohm 5d. per yd. Standard K25 300 ohm ribbon, 9d. per yd. Co-ax. cable, 1/2in. dia. 70 ohm., 8d. per yd. 1/2in. dia., 1/- per yd. 7ft. length 1/2in. dia. Co-ax. with Pye plug one end, 1/6, post free. All other Co-ax., and feeder, plus 1/6 post any length.

POTENTIOMETERS. 5 watt wire-wound 20 k., 25 k., 2/- Carbon Type Potentiometers, 50 k., 100 k., 1 meg., 2 meg., 1/6.

TRANSMITTING TUBES. Type 807, 10/- ea. Type 813 New and Boxed £3/10 each. 723 A/B Klystron £3 ea. Type 866A 17/6 each. Few only.

METERS. 2 1/2in. Flush mounting M.C. 100 mA., 500 mA., and 20 mA. 12/6 each. 2in. Flush M.C. 500 Microamp, 10/-, 5 mA., 7/6. 2 0.5 Amp. Thermo, 5/- Special Offer 2 1/2in. Flush 0—1 mA. Rectifier meter, scaled 0—10 volts, 22/6 each. Few only.

STATION LOG BOOKS. 200 pages printed one side only. Size 8 1/2in. x 11in. First class paper and bound with heavy cover. Price 17/6.

Carriage paid on all orders over £1 except where stated. Please include small amount for orders under £1.

Please print your name and address.

CHAS. H. YOUNG, G2AK

All Callers to 110 DALE END, BIRMINGHAM

Phone: CENTRAL 1635.

Mail Orders to 102 HOLLOWAY HEAD, BIRMINGHAM

Phone: MIDLAND 3254.

THE FIDELIA

Features include variable selectivity, infinite impedance detector, electronic bass and treble controls, push-pull triode output stage; 3 wavebands 18-50, 190-550 and 1,000-2,000 metres. Audio amplifier response 30-18,000 cycles; bass, treble and volume controls operate on grammo, suitable for lightweight p.u. Price £25 5s. Also 8 valve, £24 5s., 7 valve, £21 15s., 5 valve £15 15s. Data sheets on request.

9 VALVE
DELUXE
R/GRAM
CHASSIS



ELECTRO Acoustic DEVELOPMENTS-
18 Broad Rd., Willington Eastbourne, Sussex.

TELEVISION DIPOLE AERIALS!

We are pleased to announce that we are again able to offer a limited number of T.V. Aerials. MIDLAND FREQUENCY 15/- plus 2/6 Carriage. HOLME MOSS FREQUENCY 17/6 plus 2/6 Carriage. High grade Insulators with 3/8in. dia. strong tubing.

The following lines previously advertised are still available:—
Dipole Insulators with brass stubs, to fit your own tubing 5/- plus 1/6 post.
Sectional Masts, in 5ft. 6in. sections. 11ft. (2 sections) 12/6 Plus 2/6 Carr. 22ft. (4 sections) 22/6 Plus 3/6 Carr.

WALTON'S WIRELESS STORES,
48, STAFFORD STREET, WOLVERHAMPTON
HUNDREDS OF SPECIAL BARGAINS FOR CALLERS.

OUR 16th YEAR. MONEY SAVING OFFERS.

AVIATION AND RADIO BARGAINS.

SPERRY GYRO HORIZONS. Mk. Ic. R.A.F. No. 6A/1649. Sperry Part No. 650412. Absolutely Brand New and Unused. In original shockproof packing. 460 available. Price On Application. Can be supplied ARB approved if desired.

AIRCRAFT GENERATORS. Brand New. 12 v. 500 watts. Clockwise Rotarian. Convenient short spindle. Ideal for car, lorry or building a lighting set. Cost £15 each. We have 250 at the bargain price of 21/- each, carr. 6/-.

AIRCRAFT CAMERAS. Telescopic Lens, f/7.7. Gun Style. Type G28. Takes Standard 120 Film. Amazing Pictures from Great Distances. Illuminated Graticule. Brand New, £6 each, carr. 10/- Perfect in every respect

MAGAZINE ASSEMBLY for Aircraft Camera, Type K-24. Brand New in Cartons. 260 available. 10/- each, carr. 1/6.

AIRCRAFT LOADMETERS. These are for weighing and checking balance of aircraft. 15,000 lbs. Black and Decker Manufacture. Brand New in Cases: 2 only. £75 each.

SWAGING MACHINE. Large Collection of Dollies and Mandrels. (For tubes and pipes. Not cables.). Brand New, £25.

AIRCRAFT INSTRUMENTS. Approx. 200 instruments. Various types. For sale in one lot. Buyer to inspect. Sorry no lists. To clear, £25 the lot.

1143A Complete. Airworthiness Certificate. £40.
SCR522 TRANSMITTER AND RECEIVER. 65-86 mcs. 2 units. With Valves. In one Black Crackle Case. £15 each. 6 available.

Ex R.A.F. 1154 Transmitters. With Valves. Used but good condition, £5 each.

H.R.O. RECEIVER. With 230 v. A.C. Power Pack incorporating LS. ALL for Rack mounting. Perfect Order and Condition. £30, carr. paid.

EDDYSTONE 640. As New, £22. BC348. 28 v. Perfect, £30.
1155 RECEIVERS. With Valves. As Brand New. In Transit Cases. 10 gns, carr. per pass. train 7/6.

RECEIVER TYPE 25 (TR1196). Easily Converted to allwave superhet, see "Practical Wireless" May 1951. 6 valves. EF36 (2), EF39 (2), EK32, EBC33. We also supply full conversion details. Probably the last lot in the country. Stocks now down to 70 sets. Price 39/6. New Condition. Carr. 1/6.

TELEVISION PRE AMPLIFIERS. Single EF50 valve. Makes an amazing improvement in all fringe areas. Length 4in. width 3½in. overall depth to top of valve 4½in. Coax. input and output sockets. Power requirements 6.3 v. LT. 200/275 v. HT. Connection diagram supplied. 2,000 sold to date. Suitable for Birmingham, London or Holme Moss. Tested and Guaranteed. 15/- each, carr. 1/-.

AIRCRAFT MAGNETOS. Type C2E145/1. Brand New and Perfect. For 14 cylinder engines. 4 only. £25 the lot.

1155 AC POWER PACK AND OUTPUT STAGE. This is fitted in a neat black crackle case, size 12in. x 8in. x 5in. Has U50 and KT61. 5in. Loudspeaker and finest quality components. 200-250 v. A.C. Connections terminate in a Jones Plug which simply plugs into your 1155 and the set is immediately all mains operated. No modifications whatever required. Specially made by us. Matches 1155 in appearance. Price £6/10/-, carr. 3/6. Owing to enormous demand delivery 2/3 weeks.

FREQUENCY METERS. American Type 906D. Brand New in Cases. 150-225 mcs. Valve VT172. Complete with charts and circuit. 4 gns., carr. 5/-. Last few.

VOLTAGE CONTROL UNIT TYPE C3. Except' onally efficient noise filter circuit. Brand new. Size 12in. x 9in. x 8in., 12/6, carr. 2/6.

CONTROL UNIT 454A. 8½in. x 6½in. x 4in. ervice No. 10LB/6272. Fitted with 0-1 ma. meter. 3 pots. DP Toggle Switch. 3 jewel light jacks. G.P.O. type 2 pole switch. Yaxley 5 pole switch, etc. Ideal for conversion to first grade test meter. 30/-, carr. 1/6.

SECTIONAL AERIAL MASTS. Approx. 30t. Seasoned Timber. 10 metal sleeved sections. Store soiled but abtely sound. 50/- each, carr. 5/-.

MOVING COIL HEADPHONES WITH MOVING COIL MICROPHONE. 50 ohms. New condition. 5/- per set.

AMERICAN THROAT MICROPHONES. Carbon. Very Sensitive. 250 used available. £6/5/- the lot. Ditto, brand new and in makers cartons, 5/- per set.

PAMPHONIC PA LOUDSPEAKERS. 10in. high flux unit Handsome Maroon Cellulose Cabinet. 20in. x 9in. x 13in. impedance 3 ohms. Limited Supplies. Less Than Half Price. Brand New, 55/-, carr. paid.

TYPE 87 ROTARY POWER UNITS. Input 24 v. Output 250 v. 65 ma. and 6-5 v. 2.5 amps. Elaborately smoothed output. Neat Black Case. Size 8½in. x 7in. x 4½in. Brand New. 10/- each, carr. 1/6.

TERMINAL BLOCKS. 5c/719 and 5c/463. 6/- dozen.
TUBULAR CONDENSERS. .25 mfd. 500 v. 5/- dozen.
VOLUME CONTROLS. 10K. Twin Wire Wound. 1/- each. 10/- dozen.

AMPLION CRYSTAL PICKUPS. High Fidelity. Brand New in Cartons. Outstanding value, 26/9, post paid.

SELECTOR DRIVE IMPULSE RELAYS TYPE No. 10D/373. With ratchet mechanism. 1 notch rotation per impulse. Brand New in Sealed Cartons. 3/9, post 10d.

AMPLIFIER A1271. Brand New. Size 5in. cube. Fitted VR56 (EF36), DPDT relay. 2 mfd. condenser. Potmeter. 2 transformers. Fine job. 15/-, post 1/6.

VALVES. Type 8012. 10/- each. post 6d.

H. P. RADIO SERVICES LTD., 55, COUNTY ROAD, WALTON, 4. And at SPEKE AIRPORT, LIVERPOOL. Estab. : 1935. Tel. : Aintree 1445.

For Quality Bargains Always
—Best Buy at Britain's

COMMUNICATION RECEIVER TYPE R1155. A first-rate superhet communication receiver already well known to most short-wave enthusiasts, home and overseas. As an introduction we suggest the new revised and enlarged "Wireless World" leaflet which gives circuit data and all relevant information. We can supply this at 1/3 post paid.

The receivers are in brand new condition and in perfect working order and very moderately priced at £11.19.6. We believe that this will be the last release of these famous receivers, so buy now. Carriage and packing in original transit cases 10/6.

We have a few of these receivers slightly soiled but in perfect working order at reduced prices for personal shoppers only. Any set gladly demonstrated to callers.

R1155 Power Pack and Output Stage. Enables this receiver to be operated direct from A.C. mains, just plug in and connect low impedance speaker. (Note : speaker NOT supplied.) £3/19/6, carriage paid. This unit is manufactured by ourselves from new components and valves and assembled in a neat black A.M. case, size 8½in. x 6½in. x 4in. All necessary connecting leads and plugs are supplied and included in the price.

Simpson Dual Range Ohmmeter. Brand new American instrument. Incorporates 2½in. moving coil meter, ranges 0-2000 ohms and 0-200,000 ohms. 52/6, post free.

Mains Transformers. Three types, all standard primaries Universal mounting. (1) 350-0-350 v. 80 mA., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a. (2) 250-0-250 v. 80 mA., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a. (3) 30 v. 2 a. tapped at 3 v., 5 v., 6 v., 8, 9, 10 v., 12 v., 15 v., 18 v., 20 v., 24 v. All these transformers are brand new and boxed, fully guaranteed and prices at 18/6 each, plus 9d. postage.

Special offer of manufacturers' surplus transformers—standard tapped primary. 375-0-375 v. at 200 mA., 6.3 v. 8 a., 5 v. 3 a., 4 v. 2 a., 4 v. 2 a. Size 4½in. x 4in. x 5in. Semi-shrouded, drop through chassis mounting. A bargain offer at only 39/6, plus 1/6 post and packing.

Mansbridge Condensers. 10 mfd. 1,000 v. test. Size 3½in. x 3in. x 2in. Will work at 600 v. D.C. Price 3 for 10/6, post paid. These are brand new and boxed.

Ex-R.A.F. U.H.F. Antenna. This consists of an EA50 untuned detector stage mounted on a moulded streamlined base. The copper antenna measures 22.5 cm. All connections are brought out to a 3-pin screened connector. These units are brand new and boxed. Only 5/-, post paid.

Battery Chargers. Contained in a black crackle case size 6in. x 7in. x 12in. Includes a heavy duty transformer, metal rectifier, 0-5 ammeter on/off mains switch and 2 slydlock fuses. 230 v. 50 cycles input, output 4 amp. 6 or 12 v. battery. The transformer, etc., is conservatively rated, and the whole unit is of sturdy construction and super quality. Made to a very stringent specification, this equipment is well worth the price of £4/19/6, plus 5/- carriage and packing. In brand new unused condition. All post orders executed in strict rotation, so please order early.

Portable Testing Instruments. These multimeters are perfect, brand new and contained in manufacturer's original box. The instrument is a moving coil volt ohm milliammeter, complete in an attractive carrying case with handle. The dial is calibrated for readings of 0-1.5 v., 0-3 v., 0-60 mA. and 0-5000 ohms. Further ranges may be added as desired. A range switch is also incorporated and the basic movement is 6 mA. 250 ohms resistance. Our price 15/-, plus 1/6 post and packing.

Metal Rectifiers. 12 v. 2 a. full wave bridge, 12/6, plus 6d. post. Miniature H.T. rectifiers, type RM2—125 v. 100 mA., 4/3 each, or 2 for 8/-. RM3—125 v. 120 mA., 5/- each, or 2 for 9/6, plus 6d. post for one or two.

Electrolytic Condensers. 8 mfd. 600 v. working, 700 v. surge, three or 10/-, post paid. 16 mfd. 500 v. working 600 v. surge, three for 11/6, post paid. These condensers are tall can type single hole fixing. Minimum quantity supplied by post is three.

Multiple Block Condensers. Electrolytic, 8 x 16 x 4 x 4 x 6 mfd., all for 450 v. wkg. 4/9, plus 9d. post or two for 10/-, post paid.

Block Condensers. Electrolytic, 8 mfd. 500 v. wkg. Three for 9/-, post paid.

We have the largest stock of competitively priced radio and television components and valves in London. Come and see for yourselves—one minute from Leicester Square Tube Station and from Lisle Street.



CHARLES BRITAIN (Radio) Ltd.
11, UPPER SAINT MARTIN'S LANE
LONDON, W.C.2. TEM 0545

3 minutes from Leicester Square Station (up Cranbon Street)
Shop Hours: 9-6 p.m. (9-1 p.m. Thursday) Open all day Saturday

RADIO EXCHANGE CO.

BRAND NEW ACCUMULATORS. Multiplate, in transparent non-spillable plastic cases. 7 A.H. 2 v., 6/6. 21 A.H. 2 v (ex 58 set), with built-in hydrometers, 15/-.

H.T. BATTERIES. 60 v. 5/- each, 8/11 for two ; 75 v. (layer), plus 1.5 v., 6/6.

RECEIVER P.40. Complete with valves, covering 85-95 Mc/s., this is ideal for Wrotham, or converting for "2." Contains 4 EF54s (RF, mixer, Xtal multipliers), EC32 (Xtal oscillator), 2 EF39s (2.9 Mc/s IFs), EB34 (det.), 6J5 and 6V6 (audio). Housed in attractive grey cases. Only 69/6, in original cartons.

POWER UNIT S441B. Separate individually controlled H.T. and L.T. transformers, jewelled indicator lights, attractive appearance and modest size (14in. x 7½in.) x 7in. Output from 200/250 v. 50 cps., is 300 v. at 200 mA, 12 v. at 3 a. and 5 v. D.C. ONLY 65/- (5/- carr.) in original cartons.

TRANSMITTER 21. Sending C.W., M.C.W., or speech on frequencies of 4.2-7.5 or 18-31 Mc/s, these are complete with valves, key, control box and front panel. Relays and wire from P.A. coils (formers are intact) have been stripped by the M.O.S., but may easily be replaced with the circuit and data supplied by us. In excellent condition, 25/- (5/- carr.)

RECEIVER 1225. Complete with 5 EF50s, 2 EF39s and 1 EB34, these operate on four pre-set frequencies, L.O. being crystal controlled, and are ideal for two metres. ONLY 39/6 (1/6 post).

POWER UNIT 5532. Containing 5Z4 rectifier, SU2150 (5KV) EHT rectifier, choke, relay, condensers, transformers, etc. Complete with our 50 cps. EHT and H.T. conversion data, 17/6 (2/3 post).

VIBRATOR UNIT 21. 6 v. input, approx. 160 v. at 40 mA., D.C. smoothed output. Designed to supply the Trans/Rec. 21. ONLY 15/6.

AMPLIFIER 1135A. With ERC33, EK32 and EL32, our conversion data permits construction of a really fine little amplifier with inputs for mike and gram, 16/6 (2/3 carr.).

POWER PACK KIT. Suitable for use with the above, providing approx. 200 v. at 30 mA. and 18 v. at .2 a.; complete with Instructions, 16/6 (1/6 post).

THE NEW 1355 CONVERSION data for all five TV channels, 3/-.

9 CAULDWELL STREET, BEDFORD

Phone 5568.

OUTSTANDING OFFERS FOR EXPORT ONLY

U.S.A. RADIO EQUIPMENT

RCA TRANSMITTERS Type ET 4338-H
Westinghouse AIRCRAFT TRANSMITTERS, Navy Model G.O.9
TRANSMITTERS/RECEIVERS SCR-536
TEST EQUIPMENT iE-46 (I.F.F. Test)

U.S.A. RADAR EQUIPMENT

Mk. 26 (Models 3 and 4) APS-3, 4 and 6 units and spares
BM-Units AN/UPM-1B
BN-Units VF-Units SO-13

SPARES (RADIO & RADAR — U.S.A.)

(ET.4336, SCR-522, ATC, BRC, RU, Aircraft Radio Altdmeter Equip. AN/APN, BC-840, BC 463/4/5 APX, TPX, ABK, BM, BN, SO-1, 2, 13, BL, SK, SL, SA-2, etc. Full range of spares for A.C.U. of SO-Series of Naval Radar Equipment :

Gisholt Balancing Metering Units
Operation Centre—Model AN/TTQ-1

COMPONENTS

Large quantity of all types of U.S.A. and British Condensers—Transformers—Chokes—Coils—Potentiometers—Resistors—Relays—Crystals—Dynamotors, etc.

POWER UNITS PE-99 (7½ KVA) PE-117 and PE-120 (50 of each) Large quantity of Aircraft Instruments and Accessories (A.R.B. and A.I.D. release upon request).

Individual Test Certificates and A.I.D. Certificates can be supplied upon request.

ENQUIRIES TO

BRITISH SAROZAL LTD.

(Export Branch)

1, BRISTOL HOUSE, SOUTHAMPTON ROW, LONDON, W.C.1
Telephone : HOLborn 6763/4/5 Cables : Sarozal, London

OVERSEAS BUYERS ARE CORDIALLY INVITED TO VISIT OUR WAREHOUSES, SHOWROOMS AND LABORATORY

Come to HOLLEY'S RADIO SHOW

of High Fidelity Equipment

at

285 GAMBERWELL ROAD, S.E.5

and hear

NEW ACOUSTICAL Q.U.A.D. RADIO TUNER AND AMPLIFIER

LEAK T12 AMPLIFIER RCPU/U PRE-AMP. and SUPER-HET. RADIO TUNER

WILLIAMSON AMPLIFIER PRE-AMP. and TUNER by GOODSSELL Ltd.

SOUND SALES A-Z AMPLIFIER, TONE COLOUR UNIT AND DX RADIO TUNER UNITS

FELICITY L.P. JUNIOR AMPLIFIER AND TUNER

AMPLIFIERS BY ROGERS DEVELOPMENT CO. AND VORTEXION

NEW McMICHAEL HIGH FIDELITY RECEIVERS

Recommended SPEAKERS:

VOIGT DOMESTIC CORNER

TANNOY " DUAL CONCENTRIC "

WHARFEDALE NEW FIVE AND CORNER BARKER 148a and 150 UNITS

GOODMANS AXIOM 150 and AUDIOM 60

DECCA CORNER SPEAKER AND LONG

PLAYING RECORD EQUIPMENT


TWO-SPEED MOTORS AND L.P. PICK-UPS

RADIO AND CORNER SPEAKER CABINETS

Oper. all day Saturday Callers only

Phone : ROD 4988

POTENTIOMETERS

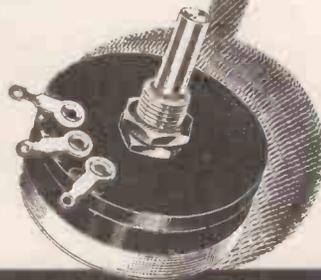

Wire-wound and Composition types. Single, Ganged, Tandem Units. Characteristics: linear, log., semi-log., non-inductive, etc. Full details on request.

RELIANCE

RELIANCE MFG., CO. (SOUTHWARK), LTD.

SUTHERLAND ROAD, HIGHAM HILL,

WALTHAMSTOW, E.17.

Telephone : Larkwood 3245

THE HOUSE FOR QUICK DELIVERY

The following Goods Ex-Stock.

Cash with Order, or C.O.D.

LEAK TL/12-Watt Loop Feedback Amplifier £25 15 0

LEAK RC/PAU Pre-amplifier.....£8 15 0

PLESSEY Single-speed Record Player, complete with Pickup. Limited quantity £6 16 2

DECCA 3-speed Motors with turntable ready for mounting..... £7 3 4

CHANCERY special Turntable for converting from 78 to 33½ for L.P. records complete with pick-up..... £6 2 3

ROMAC 25-watt Amplifier A.C. mains, Mic. and gram. inputs. Brand new. A REAL BARGAIN..... £18 15 0

ROMAC Record Player, A.C. mains, complete with all connectors in special metal case with carrying handle. Garrard S unit fitted..... £9 15 0

ACOS G.P.20, complete with standard or L.P. head..... £3 11 5

ACOS Pick-up Heads, standard or L.P., each..... £2 3 4

Send me your order for all your —

Wharfedale speakers. Test meters—Avo, Taylor, Advance. Valves. Components.

Please note : These prices are subject to any increases by the makers due to rises in costs.

A. ERNEST BUCHAN

(M.O. Dept.)

28, BELMONT ST., ABERDEEN

Telephone 23579

Wireless World Classified Advertisements

Rate 7/- for 2 lines or less and 3/6 for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World" Dorset House, Stamford St., London, S.E.1.) Trade discount details available on application. Press Day: October 1951 issue, Thursday, August 30th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS BERNARD'S.—New address (see below).

BERNARD'S, manufacturers of television, radio and amplifying equipment, can now offer rapid deliveries of hand-built equipment; let us quote you and save yourself £££££ by buying direct from actual manufacturers; 12 months' written guarantee; we supply complete television receivers; time-bases, vision strips, amplifiers; 5-1,000 watts, radio receivers; quotations by return post. BERNARD'S, 12, St. Stephens House, Westminster Bridge, London, S.W.1. (0097)

UNIVERSAL ELECTRONIC PRODUCTS, 36, Marylebone High St., London, W.1. Weirbeck.

SPECIALISTS in the design and manufacture of high fidelity reproducing equipment; from 5-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.E.57) with independent bass and treble outputs, provides the most satisfying standard of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.), and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements.

12-watt high quality amplifiers, bass and treble boost; £12/15; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. (10065)

WILLIAMSON amplifier from 15gns; amplifiers, tone controls, tuners, etc., of highest quality at lowest prices.—For details and demonstration write or phone A. S. Colman, 1, St. Stephens Gdns., W.2. Bay. 3661 after 7 p.m. (7311)

MIDLAND RADIO COIL PRODUCTS offer a service for the production of high quality amplifiers and radio equipment to specification; list of standard products is available; suppliers of audio and radio equipment to the Northamptonshire Education Authority.—Enquiries to 26, Winstanly Rd., Wellingborough. (6336)

SCRAP that old radiogram chassis, our 5-valve all-wave superhet replacement chassis is just the job, easy to fit, simple to operate, aerial tested and aligned ready for installation, fully illuminated glass dial, 8in or 10in P.M. speaker; 2/4d stamp for illustrated leaflet, price, etc.; trade enquiries invited.—Bayly Bros., 46, Pavilion Drive, Leitch-on-Sea, Essex. (7187)

C.J.B. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Hubert St., Birmingham, 6 (Aston Cross 2440), the Midlands specialist manufacturers of high fidelity sound reproduction equipment, for the world-famous Williamson amplifier and associated accessories including tone control stages, loudspeaker crossover units, distortionless contrast expanders and radio feeders; send for details and prices. (10105)

TELRAD ELECTRONICS, 70, Church Rd., Upper Norwood, London, S.E.19.—Designers and manufacturers of Telrad quality amplifiers; established as the most outstanding value in high-quality amplifiers, thanks to faithful reproduction at unrivalled price, these unique amplifiers are the first choice of the enthusiast; built to satisfy the discriminating ear; bass and treble independent controls, providing widest possible variation to suit all recordings and varying acoustic properties of one room with another; full details on request.—Write, call or phone Livingstone 4879 (10019)

CONNOSSEUR'S receiver, acclaimed by its users as the finest receiver for the enthusiast and the only one with the following facilities: 9-1,500-metre, world-wide results on highly sensitive 10-valve receiver, comparable with any good communication set, or by change of switch maximum fidelity reception of local stations on non-superhet receiver with high quality 2-PX4 push-pull amplifier incorporating all refinements bass and treble tone control (boost to cut) whistle filter and gram input, etc.; basis rebuilt. R155 write for details or call for demonstration FEEDER units as above, for use with external high-quality amplifiers; R155 specialists, receivers repaired and re-aligned, also modified as above, or to your requirements; R155 circuit and values 2/- post free.—R.T.S., Ltd., 5, Chadstone Rd., Wimbledon, S.W.19. Tel. Lib. 3303



Partridge News

PRECISION TRANSFORMERS (5VA to 100kVA)

100 TYPES available for early delivery

This extended range also includes all components for the

WILLIAMSON AMPLIFIER

The transformer illustrated provides the widest possible audio range, the lowest possible distortion and an output of 20 watts . . . it is built to the strict demands of the designer of this famous amplifier—it embodies the finest technical skill and craftsmanship available


De Luxe Model

PRICE £6 - 4 - 0

Or Potted as shown

PRICE £6 - 12 - 0

Technical data available on request.

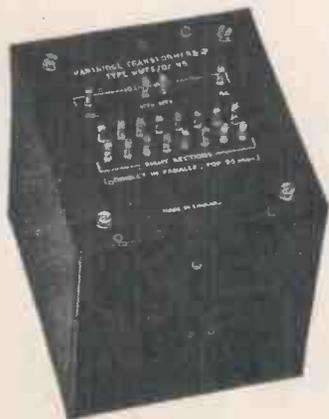

PARTRIDGE TRANSFORMERS LTD

ROEBUCK ROAD, KINGSTON BY-PASS
TOLWORTH SURREY
Telephone: ELMbridge 6737-8

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND

TELEVISION, English Electric, 15in screen, perfect order, practically new; nearest offer: £90.—Box 3228. (7253)

R.1294, handbook mains p.p. continuously tunable 500-3,000mc/s, £15; R.1132A p.p. type 3, £6/10.—Box 3296. (7281)

B.C.348, £19; Vitavox 10w M.F. unit, £4; X-over unit, 35/-; Collaro 3-speed auto-change, £21; all in brand new condition.—Box 3299. (7298)

H.R.O. Rx's and coils in stock, also AR88, BC348R, CR100 etc.—Requirements please to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. (10053)

FOR sale, Hallcraft 5x24 Defiant, built-in power pack, 5" meter, B.F.O., crystal, etc., £22; also Simon sound service disc recorder, motor and tracking gear, £25, with 15 ohm cutting head.—Harwill Recorders, Norsy Rd., Billericay. Tel. 625. (7310)

NEW war surplus H.R.O. Senior, table model black cracked, X'tal, S. Meter, N. C'es, laboratory N.L. power pack, coils, G.C. & handspread, 80, 40, 20, 10; £45; any trial tubes collect.—Weston Radio, 103, Claybrook Rd., London, W.6. (7259)

LOUDSPEAKERS—SURPLUS AND SECONDHAND

AXIOM 150 boxed as new; £8.—Rodmell, 6, Chatham Ave., Manvers St., Hull. (7266)

FOLDED bass corner horn (Klipsch) (Telefunken 12in unit), 40in high x 36in wide, polished finish; £19.—Tel. Pro. 4563. (7293)

REFLEX-RE-ENTRANT PA speakers, v/coil, 7 ohm, unused, brand new condition, 45/-; sound power head and breast sets, unused, brand new condition, 10/- set; ex-R.N. sound power telephone wall fitting, 55/- each; all goods brand new condition.—J. Wells, 118, Lake Rd., Portsmouth. (7295)

TEST EQUIPMENT—SURPLUS AND SECONDHAND

AVO 7 perfect, leather case, £15; Evershed bridge megger, 500v, Varley tests, etc., pointer damaged in transit; best offer secured.—Bolton, Suffolk Rd., Sheringham, Nrk. (7251)

BRIDGE meggers by E. & V., Ltd., .01 ohm to 50 megohms, self-contained, 250v, accuracy tested, each in leather case; £15.—P. B. Crawshaw, 166, Fixmore Way, Letchworth, Herts. (7149)

SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your enquiries are invited.—Requirements to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986.

DAWE wide-range rc. osc., 0.1 to 1,000cps, built-in CRO type 400, 4 new offers; Evershed bridge-megger, 500volt, 4-dial res. box, £16; Cambridge Grassott fluxmeter, as new, £17; Cambridge LX in-pivot Galvo, thermal scale, with 4 thermo-couples, £11.—Box 2803. (7313)

TRANSMITTING EQUIPMENT

MAGSLIP transmitters from 10/-, ideal for remote radio control, including Antenna direction indicator; stamp for details. ENGINEERING FACILITIES, Ltd., 29, Rea St., Birmingham, 5. (6982)

CANADIAN C43 transmitter, 17 valves, P.A.2.8135, 350 watts, phone MCW/C.V., voice controlled carrier 2 VFOs, new; exchange for Wearite or other good quality tape recording apparatus; seen London.—Box 3227. (7247)

NEW DYNAMOS, MOTORS, ETC.

400-, 500-, 800-cycle alternators or motor generators wanted, all ratings, voltages and makes, any quantity.—Wilho Products, 216-226, Gorbals St., Glasgow, C.5. Tel. South 2385. (7209)

BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C.; any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. (10122)

ALL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engine generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.

DIESEL Electric generating plants, 3kva, 230v with push-button remote control, starting equipment, ready for use, £228.

ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 300v d.c., permanent magnet field, 20/-; ditto, input 28v d.c. and 1,200v 70ma d.c. output; energised field, 35/-; ditto, input 12v d.c., output 500v, 90ma d.c., energised field, 35/-.

CHAS. F. WARD, Lordcroft Works, Haverhill, Suffolk, Tel. 253 (10039)

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

VALRADIO converter Type 2F0/200, in new condition, cost £15/15; what offers?—Box 3231. (7259)



PRELUDE TO A NEW SEASON

The Hartley-Turner Selected Record Catalogue has won many new friends in the past month or two. It was the first critical record guide of the world. As we were the pioneers of high-fidelity (1927) so were we the pioneers of telling you which were the best records, to enable you to enjoy your high-fidelity equipment to the full.

Today the Selected Record Catalogue is still unique. Here are its own particular attributes:—

Being loose-leaf it will always be up-to-date.

(Being concerned only with records of outstanding performance and recording quality, it gives you only the best. Nothing else is good enough for you.

Compilation followed listening tests on Hartley-Turner equipment of the very highest quality. Thus, no defect on any record was unobserved.

Price 25/- (Listings to July 1951)

And what is the Hartley-Turner equipment?

Our catalogue is now ready and a copy will be sent free on request.

During the period of the Radio Show we shall have a special display, with demonstrations, at our headquarters. Only a short distance from Earl's Court.

H. A. HARTLEY CO. LTD.

152, HAMMERSMITH ROAD,
LONDON, W.6.

Telephone: RIV. 7387

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

ROTARY converter "Janette" 210/220 D.C. 220 A.C. 250 watts, with radio filter; £14. or offer.—Corcoran, 7, Ranelagh Ave., S.W. 17292

D.C.-A.C. converter: Laurence Scott 5 KVA 230 D.C. input 230v s.p. and 3 ph. 50 cycle output with starter, new, sacrifice at £40; cost treble; weight approximately 5cwt, suitable for cinema, works or showmen.—George Hill, Electrical Engineers, Tadcaster. 17286

DIESEL alternator plant, 230/1/50 3 kva, belt driven by Petters latest type diesel A.V.I. engine, alternator self-energised, automatic voltage control, press-button and remote control, 1 press-button start and stop unit supplied complete with H. duty Eddie starter battery and charger for starter battery, full load 4½-5 hrs. on 1 gallon of cheap fuel; engine covered by Petters inspection service; delivered ready for use; £215 or packed f.o.b. London Docks £220; fullest descriptive literature on request.

ALTERNATORS, 110/1/60 and 230/1/50, 3, also 6 kva, 1,500 rpm 50 cycles, 1,800 rpm 60 cycles, self-energised, automatic voltage control by winding on stator, with d.c. output of 32v 15amp for charging 24v starter battery which can be used for lighting when main plant is not in use, press-button start, state direction of rotation when ordering, fullest descriptive literature on request; 3 kva £61, 6 kva £81 delivered; 3kva £66, 6 kva £87/10 f.o.b. London Docks.

THE above two items are new current products of well-known British manufacturers. 24v d.c. 230/1/50 rot. converter, switch, steel case, 7½/- del.; H. duty double rubber covered starter cable, 100 amp, over 1 cwt per 100 yds, £12 del.

6v BATTERIES, 85 amp-hr 70/-, 120-140 amp-hr £5. 200 amp-hr 150/- del.; Douglas twin, air-cooled petrol engine driving alternator, 100/1/60, 1.25 kva, automatic voltage control, voltmeter, main switch and fuses, £35 del.; also some d.c. sets, small, economical to run.

PLEASE do not ask for catalogues; see displayed advert, page 106 for S.T.C. selenium rectifiers; terms c.w.o., pro-forma invoice, c.o.d. (post goods only).

PEARCE, 66, Great Percy St., W.C.1 (near Angel). 0014

NEW GRAMOPHONE AND SOUND EQUIPMENT

MAGNETIC recording and "Play-back" amplifiers, complete, Mic. inputs, built in Mic. transformer, complete, £15/15.

E. & M. DEVELOPMENTS, 176, Grove Lane, Handsworth, Birmingham, 21. 17212

TAPE recorder motors, 230v a.c., powerful, quiet, brand new, 13/11; post, etc., 1/1.—K. W. Logan, Westalley, Hitchin, Herts. 16469

MAGNETIC tape new high coercivity Emi-tape 55/- 1,200ft, Type 65 25/- 1,200ft; blank recording discs 10in d/sided 3/- from stock; full trade terms.

SOUND DISCS (SUPPLIES), Ltd., 178, Bispham Rd., Southport, Lancs. Tel. 82153. 5353

SCOPHONY-BAIRD definitely the best complete home recorder, latest model, complete hi-fi mike and Emitape, £58, ex stock.—N.R.S., 16, Kings College Rd., London, N.W.3. 17273

MAGNETIC sound recording wire, stainless steel, temporary wooden spools, approx. 1½ hours' running time at 2ft per sec.; 14/- per spool.—A Smart, 40 Grange Rd., Halesowen 16491

TAPE recording, qualtape decks, standard amplifiers to match; converter preamp units; components for suggested circuits.—In stock at Lathbury's, 3, Saracen's Head, Newark, Notts. 17244

CINE-VOX disc recording equipments, type C7J for high-quality recordings from existing microphone equipment, price from 28gns; also available as a complete channel inclusive of mic. amplifier and playback equipment, price 70gns; type C7, for highest quality professional requirements—recorder mechanism at 48gns, or complete channel at 110gns; demonstrations arranged in London.

PLEASE write for details to K.T.S., Ltd., 60, Aylward Rd London, S.W.20. (Liberty 2426.) Callers by appointment only. 16724

"**M**AGNETIC Tape Recorder Construction" (28 1/2 pages, 7/6), gives full details and drawings, mechanical arrangement simple but effective. Reader's letters say: "... the most interesting and comprehensive book; and I have bought and devoured them all!" "... a lucid and most interesting thesis." Precision castings, spindles, guides, supplied; reducing your mechanical problems to drilling and mounting.—GM6LS, 15, Corstorphine Hill Rd., Edinburgh. 17226

FRITH RADIOCRAFT, Ltd., recommend and can give immediate delivery from stock of the Scophony Baird magnetic tape recorder; completely portable and self-contained and weighing only 30 lbs. This instrument has a frequency response of 50-5,000 c/s at 7½in per second and push-pull output of 10 watts, a.c. only 200-250v 50 c/s; price complete in handsome case with mike, tape and spare reel, £58/5/6; carriage paid in U.K.; H.P. terms available.

TAPE and spools also available from stock; E.M.I., 65A, 25/-; G.E.C., 30/-; Durex (Scotch Box), 35/-; all per 1,200ft reel; spare reels 5/- each.

RECORDING motors, BSR, SR1 32/-, SR2 25/-, FP10 38/-.

MEICO transverse current microphones; price £2/10 each.

RCA ribbon microphones on desk stand with switch, price £6/8; matching transformers to suit, 21/- each.

FRITH RADIOCRAFT, Ltd., 69-71, Church Gate, Tealester. Tel. 58927. 10024

PITMAN Radio Books



AC/DC Test Meters

By W. H. Cazaly and Thomas Roddam. Describes the principles, circuit design and construction of multi-range test instruments of workshop grade used for measuring voltage, current, resistance and capacitance, and low power at audio frequencies. With 112 illustrations. 18/- net.

Radio Upkeep and Repairs

By Alfred T. Witters, A.M.I.E.E., A practical handbook on the location and correction of faults, invaluable for potential service engineers and keen amateurs. Sixth Edition 7/6 net.

Echo Sounding at Sea

By H. Galway. A guide to basic principles and present-day techniques, with a detailed account of the Hughes and Marconi types of equipment. Illustrated. 35/- net.

PITMAN

Parker Street, Kingsway, London, W.C.2

"You can rely on us"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

IMMEDIATE DISPATCH

MIDGET COIL-PACKS

These are an ideal miniature Coil-Pack especially suited where space is limited. They consist of iron-cored miniature coils for both Aerial and Oscillator stages, built-in Wavechange switch and midget trimmers. They are intended for an I.F. of 465 Kc/s, and I.F. Transformers type RS/GB 465 (12/6d. per pair) are the ideal companions for a trouble-free superhet.

TYPE "R"
MW/LW/GRAM. Ranges: 200-550 metres, 800-2,000 metres.

SIZE: Length 2½in. Width 1½in. Depth 1½in.

TYPE "S"
MW/SW/GRAM. Ranges: 200-550 metres, 17-50 metres.

SIZE: As Type "R."

TYPE "C"
LW/MW/SW. Ranges: 800-2,000 metres, 200-550 metres, 17-50 metres.

SIZE: Length 3½in. Width 1½in. Depth 1½in.

TYPE "R" and "S" each 28/-. TYPE "C" each 32/6. Post 6d.

All coils enclosed—all iron-dust cores adjustable. Completely wired, only five connections needed to external circuit.

Catalogue with Data, 6d.

AERIAL FILTERS 465 K/c/s 6/3 Post 3d.

RADIO SERVICING Co.

444, Wandsworth Road, London, S.W.8

Phone: MAcaulay 4155.

77, 77A, Bus: 28, Tram, Wandsworth Rd, S.R. Station
Open till 6.30 p.m.

NEW GRAMOPHONE AND SOUND EQUIPMENT

MAGNETAPE recording panels, designed for the connoisseur, 2 speeds, 7.5 and 15 i.p.s., selected by 2-position switch, automatic braking, rewind, tape lifting and tensioning mechanism all interlocked to 3-position switch, simple to operate, no tape spills, no unclenching of tape for rewind, tape can be inched or shuttled in either direction with instantaneous stop and start for easy editing and cueing; erase and hi-fidelity record/play heads using full width track for low noise recording; frequency range 30 to over 12,000 c/s, panel size 19in x 12in in black perspex and is symmetrical in layout, heads and mechanism enclosed in moulded perspex cover; price £28. Stamp for details to Electromechs, Euston Chambers, Morecambe, Lancs. [7284]

GRAMOPHONE AND SOUND EQUIPMENT - SURPLUS AND SECONDHAND

CONNOISSEUR pick-up, red spot, as brand new, unused, £4; Garrard a.c./d.c. motor, dropper, 12in turntable, £4.—Box 3240. [7271]

QUANTITY Mu, metal boxes, approx. 3 1/2in square, also strip metal (new).—E. & M. Developments, 176, Grove Lane, Handsworth, Birmingham. [7213]

DECCA playing desk, incorporating Garrard R.C. 65 auto change mixer unit, perfect, £16; Leak RC/PA pre-amplifier, perfect, £4.—Ashworth, 6, New Barn Lane, Rochdale. [7252]

LAATEST pattern Wearite, tape deck, complete with special components, nine reels O.E.C. tape, all unused and boxed; sell for retail price, £60.—82, East St., Epsom, Surrey. Epsom 2057. [7279]

DISC recorder, H.M.V. portable, complete in three leather-faced carrying cases, including Monitor speaker and ribbon microphone, condition as new; £200 or near offer.—Box 3308. [7310]

WIREK Model B2. Wire Recorder, fitted with special time switch, pick-up, microphone; in showroom condition; £38, or offers; B. & H. recording wire (spooled) 30/- per spool.—Palmer's, 114, Waterloo Rd., Middlesbrough. [7237]

NEW COMPONENTS

HANNEY OF BATH, offers:—
EDDYSTONE 740 receiver, limited number, ex-stock, £35/10.
ACOS GP20 pick-ups, standard or LP, £3/11/5 tax paid; heads only, 43/4.
WB STENTORIAN speakers, complete range as advertised, 24/1n to 10in.
OSMOR "Q" collpacs, type HO 52/-; HF stage, 21/8.
WEARITE type 705 packs, 37/10; Wearite "P" coils, all ranges, 3/- each; Denco type "C" TRF coils, 6/6 pair.
WILLIAMSON amplifier, 25 resistors and pots, for main amplifier, 33/9; 9 ditto fig. 13, 9/6; 23 ditto fig. 12, ditto fig. 19, 37/-; 6 condensers for fig. 13, 15/-; 15 ditto fig. 15, 47/-; 33 ditto fig. 19, 54/6; the above kits contain 1st-class components only by the best makers and are exactly to specification.
W.W. TV S'het. Receiver, coils are now available for all 5 channels; our TV list contains items for W.W., P.T.T., E.E., and Viewmaster Televisors.
SEND 3d stamp for our comprehensive lists, new goods only; no surplus; c.w.o. or c.o.d. (no c.o.d. under £1).
L. F. HANNEY, 77, Lower Bristol Rd., Bath, Tel. 3911. [7189]

CRYSTAL microphone inserts (Cosmocord Mic-6), guaranteed brand new; 15/6, post free.
RADIO-AID, Ltd. (Retail Dept.), 29, Market St., Watford. [0036]

TELEVISION.—Many items for the "Wireless World" long range, superhet, televisor, prices still the same; lists available; trade enquiries invited.
TELEVISION.—Iron-cored polyesterene coil-formers, various types 6mm and 8mm, 7d and 10d list; also latest 1/4in canned cored formers, undrilled, set, 1/10; W.W., E.E., P.W., view/mast.
TV coilsets.—Wobblur coilset, 7/6; 9kc/s, 20mH coils, 7/6; recorder oscillator coils, 12/6; set 3-band 1/4in s-het coils, 6 pieces, with cct., 9/-; double wound Minicoils, s-het, AE HF osc., poly cored former, boxed, tagged, coded, ea. 3/6.
WILLIAMSON type tuner coils, m.w. and l.w., 7/6 pair; to your station choice, 9/- pair.
BEL, Manufacturing Radio Engineers, Marlborough Yard, London Archway, N.19. Arc. 5078. [0183]

3/6 only.—Complete simplified set of instructions for building any one of the following sets: 5-valve a.c.; 5-valve a.c./d.c.; 6-valve a.c.; 3-waveband superhet feeder unit; 3-waveband superhet feeder unit with R.F. stage and high fidelity switching; 10watt quality push-pull amplifier; or any two sets of these instructions, 6/-.
RANGE of high quality components in stock, including the popular Supacoils at 3/- each; Model 30 coil pack at 53/4; Model 40 coil pack at 90/2; I.F. transformers at 16/6 pair; see also our display advertisement in this issue.
HOME Constructor's Handbook, send 2/- now for the latest edition of this popular handbook, which includes 11 tested circuits, complete resistance colour code, servicing and constructional information.
SUPACOILS, 98, Greenway Ave., London, E.17. [0133]

EVERYTHING for home constructor, chassis, condensers, coils, valves, resistors, gram units, speakers, test gear, Viewmaster kits, etc., cash or H.P.; stamp for lists; quick service, no Govt. surplus offered.—BCM/EDHWA, London, W.C.1. [6227]



A WINDOW WORTH LOOKING INTO

Television. Type 208a, 2 Valve Amplifier complete with 2 E.F.50 valves and instructions 14/6 each.

Meters. Brand New and Boxed. 0-1 1/2 M/A. 2in. Round Flush Mounting, 6/6 each.

Rectifiers. L.T. 24 volt Full Wave 5 amp. rate, Brand New, 32/6 each.

P.O. Type Indicator Lamps. 6d. each. Large quantity available.

Midget Jones Plugs, 6 way Female, 1/3 each. Feed Through Ceramic Insulators, Heavy type, length 5in., 1/3 each.

Special Offer. Control Units type 488, containing 2.5 meg., 1 50 K., 1 100 K., High Voltage pots, Toggle and Yaxley Switches, Slow motion Drives, Resistors and condensers. Offered at the very low price of 5/6 each, boxed new.

Battery Amplifiers. Type 1369, complete Battery intercom. amplifier complete with driver valve and Q.P.P. output valve. Brand New, 12/6 each.

Television Coil Formers, with Iron Dust Cores, 1in. x 1/2in. single hole fixing, Polystyrene. 6d. each.

Rectifiers. L.T. 12 volt 5 amp., full wave, 17/6 each.

Meters. Brand New Boxed. 0-350 M/A. R/F. 2in. Round Flush mounting, 5/6 each.

Condensers, Block Type. 16 mid. x 16 mid. x 16 mid. at 450 volt Electrolytic Size 2in. x 2in. x 4 1/4in. Really first-class condensers, 3/6 each.

Button Base Ceramic Holders. 87G with bottom screen 1/2 each. Large number available.

Television. 7ft. telescopic Aerials, in Dural, ideal for Television Aerials, collapse to 15in., only 4/6 each.

Midget Jones 18 Way Plugs and Sockets in Polystyrene, 1 1/2in. x 1/2in., 4/6 per pair.

12 Volt Rotary Packs. Fully Smoothed Outputs 260 volt 60 M/as, completely screened and suppressed, 17/6 each.

Television. .1 mid. High Voltage Condensers, Mansbridge type, 5,000 volt working, the most reliable condenser to fit. Special price 2/- each. Limited number only.

25 pt. 2 Gang Short Wave Condensers, 2/6. Ditto, Single Gang spindle each end, 1/6 each.

Pots. 5 K. Heavy Duty Wire Wound 2in. dia., 4/6 each. 1 meg. midget pots, 1/6 each. Midget I.F.s, 465 K/cs, 12/- per pair.

Condensers. Mansbridge types. 25 mid. 6,000 volt, 3/6 each, 5 mid. 3,500 volt, 3/6 each, 1 mid. 1,500 volt, 2/6 each.

Transformers. 100/250 volt A.C. 150 watts, 19/6 each. Ditto, 100 watts, 15/6 each.

Micro Switches. Several types available. Large stocks. 2/9 each.

G. W. SMITH & CO.

Open all day Saturday

(RADIO) LTD.

3, LISLE STREET, LONDON, W.C.2

Telephone: GERrard 8204

AUTUMN JOYS AHEAD



Memories of a grand summer are now with us all, and we look forward to the times we shall spend with our radio, records and television during the coming evenings.

Many friends have asked us why we are not at the Radio Show. Our specialised activities, confined entirely to making a limited number of really fine sound units for those who seek the very best and most natural results, appeal to few of the many people who throng the exhibition. We are always busy, even in the summer months, and the time off for preparing a stand and spending a fortnight away from the lab. would cost us many units of output which we need to fulfil orders. So that's that!

Now for business. We continue our 148a and 150 Sound Units

because so far there is no major change which justifies a new model. Several detail improvements have come in during the year, chiefly linked with the new die-cast frame and cone suspension. Both models have benefited

Keeping prices unchanged is a struggle. As far as we can see, we shall manage until the end of the year, but then—? Supplies of our 501 cabinet have been very limited, and will continue so. It has made many new friends by its clean performance and good looks.

IF YOU SEEK GOOD SOUND, ACT NOW. BARKER UNITS ARE UNIQUE FOR CLARITY OF DETAIL, WIDE FREQUENCY RANGE, SMOOTHNESS AND THE POWER OF GIVING LIFE TO SOUND REPRODUCTION.

Send for details to

BARKER NATURAL REPRODUCERS

BCM/AADU

LONDON, W.C.1

SUCCESSFUL SALES! **SATISFIED CUSTOMERS!**

Pennine RADIO

THE ALL SEASON SENSATION. ACCLAIMED THE COUNTRY OVER. THE INTIMATE RECEIVER WHICH COMBINES APPEARANCE AND PERFORMANCE. HOUSED IN A BEAUTIFUL WALNUT CABINET. EACH SET FULLY GUARANTEED.

HEIGHT 10", WIDTH 12", DEPTH 5 1/2"
4 Valve SUPERHET

THE SET THAT SELLS ITSELF!

UNBEATABLE VALUE
£15 0 2
INC. TAX.



"THE ROVER"

SUPPLIED ONLY THROUGH SELECTED WHOLESALE. ILLUSTRATED LEAFLETS AND ATTRACTIVE DISPLAY CARDS.

PENNINE AMPLIFIERS
ELLAND YORKS ENGLAND
TEL. ELLAND 2107

NEW COMPONENTS

PALMERS of Middlesbrough—for best selection of quality components in the North: s.a.e. for current list from Palmers, 114, Waterloo Rd., Middlesbrough. [7236]

EHT Transformers, mains transformers, output transformers and chokes; open or potted types; transformers designed to individual specifications: singles or in quantity.

WILLEDEN TRANSFORMER COMPANY, Ltd., 20a, Church Lane Church Road. N.W.10. (Tel. Willeden 7095. [0075]

YOU are bound to try an Osmor "Q" Coil-pack eventually and be delighted with the results; why not save time and money now? Send a stamp for free circuits and latest lists of coils, coilpacks, dials, etc., etc.

OSMOR RADIO PRODUCTS, Ltd. (Dept. W.C.A.), Borough Hill, Croydon, Surrey. [0046, Croydon 1220]

MIDGET TRF 3-station coilpack kits, 15/-; Midget relays, 5,000 ohm coil, weight loc. 10/-; "Viewmaster" TV pre-amp kits, inc. valve, 42/-; "High C" TRF coil, LW and MW with reaction, inc. circuits, 5/-; replacement P.U. bobbins, 4,000 ohms, 7/6, other values to order; 465KC I.F. rejectors, midget size, wire-wound, 3/-; deliveries by return; all c.w.o.—A. P. Cretton (W), 349, Copnor Rd., Portsmouth. [7045]

COMPONENTS—SURPLUS AND SECONDHAND

C. J. EMMS, Ltd.

RECTIFIERS, full wave bridge type, as follows: 1 amp, 12 or 6v, 5/6; 3 amp, 12 or 6v, 12/6; 5 amp, 12 or 6v, 15/-; 5 amp, 12 or 6v, 17/6; 7 amp, 6 or 12v, 22/6; 24v 1 amp, 11/-; 24v 3 amp, 25/-; 24v 4 amp, 30/-.

NEW sliding resistance sets from 1 to 4 amp 14 Ω to 12 amp 1Ω, 7 in all, 30/- per carton. 25a, Colborne Mews, London, S.W.10. [0201, Fremantle 8941]

RADIO CLEARANCE, Ltd.

TELEVISION! Set of 3 components, comprising line output trans., with E.H.T. winding to give 7 kv, using EY51 (heater winding for EY51 also included), and fitted with width control, scanning coils, low impedance line and frame, focus coil (res. 10,000), current approx. 20 mA); the set of 3 for 42/- plus 1/6 post, diagram of line trans. supplied, scanning coils, as "Viewmaster," low imp. line and frame, 12/6 plus 9d; **M**INIATURE iron cored coils, former size 1 1/2 x 3/4 in adjustable core, set of 4 coils, M.W., AE and OSC, S.W., AE and OSC, 5/11, post 6d; main dropping resistors for 15a valve, 920Ω, tapped at 850 and 700Ω, small size (3in x 1/2in), 2/3.


A.C./D.C. amplifiers, complete kit for construction of 20w, 8v amplifier, by McMurdo, all first-class components by Farridge, Gardner, etc., valves 6XCL33, 2XU37, 2XU3C, 2XU3B, crackle, chassis and case, isolated from mains, and drilled, circuit diagram supplied, everything complete, £10/10/6, carr. paid; television focus coils, for 9 or 12in mag. tubes, res. 10,000Ω, average current 20mA, 7/6.

PERSONAL receivers, 3 valve T.R.F. using IT4s, contained in handsome bakelite case with lift-up lid, size 7x6 1/2 x 5 1/2 in with lid closed, plastic carrying handle, fram AE in lid, these receivers cover the medium waveband and operate from self-contained dry cells, standard types W1435 and U2, output to a pair of lightweight 'phones (H.R.) controls, SM tuning and reaction, opening lid switches on, supplied brand new, with valves, batteries, 'phones, an ideal set for invalids, hosp. patients, etc., these receivers are not Gov. surplus and are offered ready to play; carr. paid £4/4.

CHASSIS steel 5 1/2 x 5 1/2 x 1 1/2 in drilled 3 button base holes 1/8, 5 x 9 x 1 1/2 drilled 5 button base holes, 2/3, all 17 x 9 x 2 1/2 drilled 7 int. octal and square open ends 3/-, all 14 1/2 x 10 x 2 1/2, 10-BBA, 5 int. octal, ex. T.V. 4/3, 4/3, 0-110-210/240v 50c/s, secs 300-0-300v 80ma, 4v 2a, 6.5v 2.5a, 15/6, heater trans., auto. wound 200/250v 50c/s to 6.5v 3a, 8/-; smoothing chokes 20H, 30ma 350Ω 6/11, 5H, 30ma 100Ω 5/6, 8H 250ma 50Ω size 4x5x5 potted 10/6 post paid; electrolytics 32mf 350v card 2/-, 32-350v can 2/6, 25-50v w/e 1/3, 100-12 1/3, 16-450v can 2/6, 8+4 450v can small 2/9, 8+4 275v 2/-, 2-450v 1/6; switches standard Yaxley type, 2p 4w 1b with shortins wafer 2/-; superhet coils 1 1/2 x 1 1/2, formers M, wave H.F., AE, Osc. L, wave H.F., AE, Osc. 1/9 per coil; I.F. trans. 465kc/s 1 1/2 x 1 1/2 x 4 1/2 in iron cored 8/- pair; meters 2in square bakelite cased, 0/5ma 6/6, 0/5ma 7/6, 0/300v d.c. with series res, 7/6, bakelite cased 2 1/2 in circular 0/200ma 9/6; 100 power units type 104, p.m. rotary mounted on chassis with supp. input 12v d.c. output, 250v 60ma, 6.5v 2.5a d.c. 7/-, type 87 24v input, outputs as 104 6/6 post paid; plugs and sockets, bakelite with keyway 5, 7, 1/6 pair; extension speaker controls 100 wire wound, 1/2 in spindle 9d; "Pye Strips" the well-known 45mc/s vision strips, brand new, less EF50s, with EA50, perfect condition, 39/6, plus 1/6 post; focus coils, low res., 200Ω, standard TV 8/6, can be had as alternative with kit, required; 6 1/2 in loudspeakers, p.m. less trans. boxed, 12/6 post paid; Mansbridge conds., 4mf 1,000v wkg. 3/-; v.c. with sp switch long spindle 25k, 50k, 100k, 2m 4/-.

SMALL size iron cored I.F.s, 465kc/s, size 1in x 1 1/2 in x 2 1/2 in, 8/6 pair; frame aerials for personal sets, etc., medium wave, rectangular winding, size 6 1/2 x 4 1/2 x 1 in, wound round 4 wooden bobbins mounted at the corners of an all. plate, tabs for connections 2/6 post paid; output trans., 5,000Ω, 750, 2/11; valveholders, Amphenol, 88A 7d, int. octal 7d, ceramic int. octal, 10d. **R**ADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. [0015]

OPPORTUNITIES IN RADIO

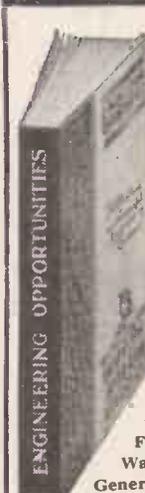

Get this FREE Book!

'ENGINEERING OPPORTUNITIES' reveals how you can become technically qualified at home for a highly paid key-appointment in the vast Radio and Television Industry. In 144 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of **TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.** We definitely Guarantee

"NO PASS—NO FEE"

If you're earning less than £12 a week this enlightening book is for you. Write for your copy today. It will be sent FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
388 SHAKESPEARE HOUSE,
17/19 STRATFORD PLACE, LONDON, W1



MAGNETIC TAPE

Recording Equipments and Components

OSCILLATOR UNIT. Constructed on small chassis, suitable for sub-assembly, provides r.f. for erase and bias at 45 kc/s. Requires 250 v. h.t. and 6.3 v. for operation. Complete with 6V6 valve, £3.

OSCILLATOR COIL ASSEMBLY. Comprises high "Q" coil and condenser tuned to 45 kc/s. Specially designed to provide highly symmetrical sine wave output for low tape noise, 10/6.

RECORD/REPRODUCE HEAD. Impedance: 100 ohms at 1 kc/s. High quality response. Totally enclosed. Gap length 1 mil., £2/2/-.

REPRODUCE HEAD. As above, but gap length 0.5 mil. (suitable for 2-head systems), £2/2/-.

ERASE HEAD. Capable of erasing new high coercive force tape when used with oscillator unit above, £2/2/-.

TAPE. New high coercive force tape suitable for high fidelity recording at slow speeds. 7in. (1,200ft.) reels, £1/10/-. Spare reels, 7in., 4/6 each. 11in. (1,000 metre) reels also available.

INPUT TRANSFORMER. Ratio 1/40. Frequency response: ± 2 db. 50 c.p.s.—20 kc/s. Suitable for head to grid step up. Mumetal core, 17/6.


TRANSFORMER. As above, but fitted in 16 S.W.G. mumetal screening can, 30/-. Send for further details including circuits. Trade and export enquiries invited

CABOT RADIO COMPANY LIMITED

Electronic Equipment Manufacturers
28, BEDMINSTER PARADE, BRISTOL, 3.
Telephone 64314

New!

THE HAYES RG/135 RADIOGRAM CHASSIS

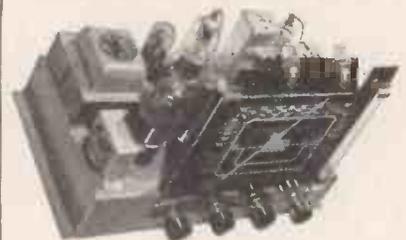

★ 7 VALVES

★ 6 WATTS OUTPUT

★ £18.0.0 Complete

also, constructed to the same high standard, our popular RG/120 5 valve chassis at £14.10.0. Write for full details of these chassis, which will be gladly sent by return of post.

1951 RADIO EXHIBITION During the period Aug. 28th—Sept. 8th we are extending our normal hours, and our showroom will be open from 10 a.m. to 9 p.m. each day. Both the above chassis will be on demonstration, together with the full range of new Armstrong chassis.

THE HAYES COMPANY

1 Alcester Road, Birmingham 13

Telephone South 0202

Sole B'ham Agents for Armstrong chassis.

Surplus BARGAINS

MANUFACTURERS' & BANKRUPT STOCKS LIMITED SUPPLIES ONLY

PRICES ARE RISING SUPPLIES ARE GETTING SHORT

-BUY NOW-

ALWAYS SOMETHING NEW VISIT OUR SHOWROOM We can offer for immediate delivery

SPECIAL OFFER NOW AVAILABLE

-DIRECT FROM M.O.S.



STORAGE AND STARTER BATTERIES

- 6 volt. 72 Amp. "ESE"
- 6 volt. 90 Amp. 15 plate "Reading" U.S.
- 6 volt. 100 Amp. 15 plate "Delco Remy"
- 6 volt. 140 Amp. 21 plate "Delco Remy"
- 12 volt. 9 plate.
- 12 volt. 14 Amp. In METAL CARRYING CASE.


All Brand New in original cases.

Receivers: R1155, 1355 and 184 Brand New in original cases. Dinghy Radio Transmitter SCR 578.

EX-W.D.

AERIALS CAN ALSO BE USED AS FISHING RODS

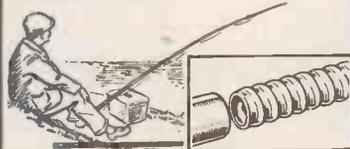12ft. Light Steel Aerials in 3 screw-in sections of 4ft.



Charging Control Boards with Auto. cut out, 3 amp. 220 v.

Yaxley Type Switches, Mainsbridge Condensers (Oil filled and Jelly), Burgoyne Solder Guns, Tannoy Handmikes, Dinghy Transmitter Sets. Adhesive Tape, Coaxial Cable, Magnifying Lenses, Rubber Masks, Speakers, Coaxial Plugs and Sockets, Belling Plugs and Sockets, Vibrators, Belling Fuseholders, Meters, Mica Condensers, Electrolytic Condensers, Volume Controls, Valve Holders, Output Transformers, Mains Transformers, Chokes, Headphones, Valves Type CV 101, etc., etc.

Your enquiries are invited

WHOLESALE AND EXPORT ONLY

For further bargains call at our Counter or write for NEW bulletin

RADIO MERCHANDISE COMPANY LIMITED

65, Farringdon Road, London, E.C.1 Telephone: HOLborn 6377 Quote Dept. W.W.

COMPONENTS—SURPLUS AND SECONDHAND

TELEVISION Dipole Insulators.

HIGH grade ex-Government Polyethylene Insulators with Brass Stubs, need two pieces of 3/4in 1/4 Tubing only to form a highly efficient Dipole or H aerial, for all areas; our special price 5/- each, post, etc. 1/6.

TELEVISION Masts. STEEL a few 2in o/d steel masts in 5ft 6in sections; wonderful value; 11ft (2 sections), 12/6 each, carr. 2/6; 22ft (4 sections), 22/6 each, carr. 3/6.

NOW is the time to alter and obtain full efficiency from your aerial system; obtainable only from the Midland Television Specialists. WALTON'S Wireless Stores, 48, Stafford St., Wolverhampton. [0061

BENDIX BC.221 frequency meters complete. £30.

S.D.R. 522 frequency 100-156 mcs complete transmitter/receiver, in new condition, with all tubes; £30.

EIMAC 100th transmitting valves; 55/-.

TAYLOR T200 transmitting valves; £6.

THROAT microphones new and boxed; 4/6

PLUG and key assembly No. 3 with send/rec. switch; 5/6.

LEACH relay heavy duty 24 VDC, res. 250 ohms; 7/6.

CLARKE keying relays; 17/6.

PAPER condenser, 4mid 300v wkg., 6/6; paper condenser, 0.25mid 1,200v wkg., 4/-; paper condenser, 0.05 plus 0.05, 2,000v 4/-.

SMALL porcelain jumbo, 4-pin bases; 4/- each

LARGE porcelain jumbo, 4-pin bases; 6/6 each.

MCLEIROY-ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., Fulham, W.6. Tel. Fulham 1802.

Cables: Hallcraft, London. [0196

MEISSNER de Luxe signal shifter. £20; Hallcraft Skydier Model 25, perfect.

EDDYSTONE 640, 1145, transmitters, communication receivers in stock. Hammerlung Super Pro. H.R.O. Seniors, C.R.100, A.R.88D., A.R.88L.F., etc., all in perfect order; R.1155 receivers in new condition; your enquiries are invited for rotary converting and electric motors.

most sizes and types available from stock; motor alternators, 110v d.c., input 230v a.c., 50 cycles, 250 watt output, £8; special clearance of F.H.P. electric motors, 35/-, 110v-250v a.c.

UNIVERSAL a.c./d.c. motors, suitable for sewing machines, 40/- each; 12v-15v a.c./d.c. motors with extended spindle, suitable for models, etc. 9/3; 20 watt P.A. rack mounting amplifier, new and complete, with heavy duty a.c. power pack, 200/250v, PX25 P.P. output, £4/10, less valves; new moving coil microphones, hand type, heavy duty and complete with 12yd screened cable, £3/15; 20ft telescopic tubular T/V mast, 18/6 each; large selection of test equipment; multi-range meters, valve testers, signal generators, oscilloscopes, bridge meggers and meggers, etc., all at reasonable prices; hand bearing prismatic compasses with provision for battery in handle, perfect, 40/- each; very large stocks of transmitting valves, Klystron, of all types, send us your requirements; special offer of new, not ex-W.D., mains transformer, semi-shrouded, 200/250v tapped primary, 250-0-250, 100ma, 5v 5amp, 6v 5amp, 20v each; large stocks of L.T. transformers, special sizes and ratings wound to specification; auto-record changers in stock from £10/15; switchboard mounting voltmeters, ampeters, various ranges a.c. and d.c. available at cheap prices to clear; large stocks of enamelled wire, 28 s.w.g., 18 and 20 w.g., D.S.G. No. 15 U.X. base, American valves available. Special offer: H.R.O. coils, 48-96 m/c and 180-430 k/c. 45/- each; quantity of 11tz and nickel chrome wire available; type 74 indicator units, complete with tube, as new, £5 each; Fluxmeters, model WY-0023, complete, new, £5/10, prices do not include postage; American Dinghy transmitter, type SCR578, 500 k/c M.C.W.; large stock electric exhaust fans, most types; Hallcraft Super Skydier 5X26 and S27CA in stock. Evershed bridge megger, 500v, 1 1/2 kw, d.c. rotary converted, £20 d.c./250 a.c., complete with Igranite starter, £28

Large selection of American Pyranich high-voltage working condensers; 0-50m/a meter rectifiers 6/3 ea.

SERVICE RADIO SPARES 4, Lisle St., W.C.2 Gerrard 1734. [0188

MAGSLIPS at 1/10 to 1/20 of list prices.

huge stocks, please state requirements.

K. LOGAN, Westaley, Hitchin, Herts. [6369


TERRYS Anglepols lamps, brand new, 35/- each, cash with order.—Passinghams', 19, Leeds Rd., Bradford, Yorks. [6991

C. A. RYALL, "Utopia," Mayfield Rd., Herne Bay, Kent, offer post-free barkalms:

meters, 2 1/4in, 3 1/4in overall, 0.30ma circular, bush, bolting through front flange, bakelite cased, 6/9 each, or best known make 8/9, or 2 1/2in best make 8/9, also 2 1/2in square front best make 0-5ma 6/9, and 2 1/2in square front 0-300v, 5ma, separate series resistance, price 6/9; metal boxes, size 3 1/4x 7 1/4, four fixing lugs, bench or wall fixing, paxolin lid, 1/4in exact, 6/9 complete; paxolin panels, 12x12, 1/4in, 4/10, or slightly soiled or marked, two for 5/10; miniature instrument switches, S.B., 2-b. 6-way, 1/6 each; standard size Yaxley type 9w S.B. 2-b. 1/6 each; ditto 2-b. single-pole 6-way, 1/6 each; smaller type, 3-bank, 2-pole, 6-way, total five poles, only 2/- each; none soldered; one type switch, soldered with leads, 2-bank, 4-way, with five poles total, one double bank, 1/6 each; ditto 2-b., 3-p., 3-way, total six poles, with bakelite pointed knob, 1/6 each; all switches single-hole fixing. Headphones, high resistance, with good class carbon microphone, padded double headband, with sponge type earcups, all wired with first-class cords into large four-cleft plug, R.A.F. type, unused, as new, 8/10 per set. [0205

Armstrong

THE CHASSIS PEOPLE

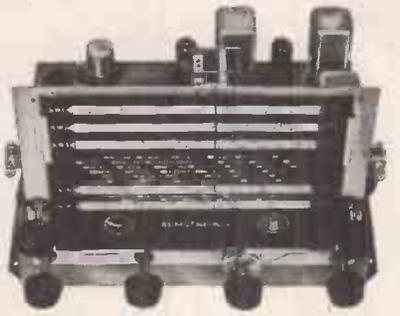

The prestige of Armstrong chassis is firmly based upon many years of constant endeavour to produce reliable and efficient receivers at an economical price. Our present range of chassis will even further advance the already high reputation enjoyed by our receivers. We are delighted to give demonstrations in our showroom and our illustrated catalogue will be sent on request.

MODEL EXP 125/3 14-VALVE ALL-WAVE RADIOGRAM CHASSIS

5 Wave Bands covering from 10.9 to 550m and 800 to 2,000m. R.F. Pre-Amplifier. Two I.F. Stages with Variable Selectivity. Bass and Treble Controls. 15-Watt Push-Pull Output. For A.C. Mains. £36.15.0. plus P.T.

MODEL RF 104 10-VALVE ALL-WAVE RADIO CHASSIS

4 Wave Bands. R.F. Pre-Amplifier. Two I.F. Stages with Variable Selectivity. 10-Watt Push-Pull Output. For A.C. Mains. £24.0.0. plus P.T

MODEL EXP 73 8-STAGE ALL-WAVE RADIO CHASSIS

3 Wave Bands. Variable Selectivity. Fly-Wheel Tuning. 8-Watt Push-Pull Output with Negative Feed Back. For A.C. Mains. £17.15.0. plus P.T.

EXPORT MARKET

Overseas customers are cordially invited to write for details of Models BS 125 and EXP 119. Both these chassis have been designed in consultation with engineers from many parts of the world to ensure maximum performance under adverse conditions.

Sole Agents for:—

KENYA, UGANDA, TANGANYIKA, ZANZIBAR Jennings & Fox (Mombasa) Ltd., Kilindini Road, P.O. Box 56, Mombasa, Kenya.

EGYPT Emmanuel Cokkinos & Co., P.O. Box 1720, Cairo.

URUGUAY Arbesa, S.A., Jaime Zudanez 2713, Montevideo.

ARMSTRONG WIRELESS & TELEVISION CO. LTD. WALTERS ROAD, HOLLOWAY, LONDON, N.7

Telephone: NORTH 3213

A FINE NEW AMPLIFIER

Of the amplifier designs sponsored by the technical press we give first place to that of "The Gramophone." Performance is exceptional by any standards, the more attractive at such a reasonable cost.

THE GRAMOPHONE AMPLIFIER

has an excellent response from 30-20,000 c.p.s., only 0.15% harmonic at 8V output, full negative feedback, push-pull output, 5 all-glass valves, input 0.1v. Pre-amplifier, single valve, gives full tone control for "78" or L.P. records, input 50mV.

Send now for full constructional details and diagrams, 1/6 post paid.

Also available assembled and tested.

AMPLIFIER 16 Gns. PRE-AMP. 4 Gns.

ACOS GP20 Pick-up	£3 11 5
Long Playing Head	£2 3 4
DECCA Hi-Fi Crystal pick-up, two cartridges for "78" or L.P.	£4 4 6
With single cartridge	£2 13 0
CAPACITORS, wax tubular, new. 0.1, 500V.	10d., 8/6 doz.
"Sound Reproduction" by G. A. Briggs	11/- post free
WHARFEDALE W 10/cs, 3 or 15 ohm	£8 10 0
Chancery Long Playing Attachment	£3 12 6
THREE SPEED Decca Gram. Motors	£7 3 4
LECTRONA 10In. High Flux Speaker, 3 ohm	£1 12 6
W.B. Stentorian 10In., 3 ohm	£2 1 9

For Satisfaction.

Mail Orders Only to

QUALITY MART

110 VILLIERS ROAD, WATFORD

COMPONENTS—SURPLUS AND SECONDHAND

SUPREME RADIO, 746b, Romford Rd., Manor Park, London, E.12, Tel. III. 1260. Est. 17 years.

THIS month's "Supreme" bargains:—
28-WAY tag strips, break it as required, 1/- ea.; moulded B7G valve holders, 10d ea.
L.T. heater trans. 0-200v-230v-6.3v, 1.5amp, our price 6/9; Westinghouse type metal rectifiers, 250V R.M.S., 65mA., 5/6 ea.; C.V.102 crystal diodes, 3/- ea.; flat type mains dropper, tapped for 200-250v 630ohm, 0.2amp, 1/6 ea.; PF/S, 100pf, 70, 65, 50, 40, 307, 530, 570, 1,800. all at 2/6 doz. or ass. doz.

TRIMMER panels with 2 500f and 2 350f trimmers, 30 ea.; Dole suppressor units, consisting of 2 0.1mfd cond. and iron-cored choke, 6d ea.; panels with 6 resistors and 5 cond. or with 6 resistors, WX6, and P/F cond., all handy values either panel 1/6 ea.

ELECTROLYTIC cond., 16+16mfd, 450v, tub cardboard clip mounting, 2/9 ea.; 16mfd 450v, 2/- ea.; 8mfd 350v, wire end, tub. cardboard, 2/6 ea.; bias cond., 50mfd 50v or 25mfd 25v, 1/3 ea.

PERMANENT magnet focus units, for triode or tetrode tubes, also high flux type, 16/6 ea.; drop thro' type mains trans., primary tapped, 0-250v on voltage panel, sec. 275-0-275v 80mA., 6.3v 3amp, 5v 2amp, with screen, 15/11 ea.

GLASS dials, 8 1/2x4 1/2x1/4 in. L.M.S. wave station name for the new wavelengths, in 3 colours, 3/6 ea.; metal escutcheon for same, 2/6 ea.; pointer, 10/6d.

2-POLE 2-way small switches, 8d ea.; 5mA. meter rectifiers, bridge type, 5/- ea.
CARBON vol./controls, all less switch, 0.25 megohm, 2/- ea.; 1meg and 1/2 meg, 2/9 ea.; 3meg, 1/2 ea.; 100K ohms, 1/3 ea.; 5K ohms, 1/- ea.

ENQUIRIES welcomed on all types of radio and television component parts; terms, c.w.o., no c.o.d.; send 6d extra for postage orders under 25/-, 2/6 ea. and all over, as listed. 10021

SEND for 1951 bargain Radio-TV lists, component Sents.—Jack Porter, Ltd., 30-31, College St., Worcester. [7210]

G.E.C. double pole change-over relays, platinum contacts, coil resistance, 2,500 ohms; price 13/6 each.

15amp Mercury switches, fitted with saddle and clip, 4/6 each; post paid.
S.T.C. wire-wound resistance bobbins, 1/4 in diam., 1/4 in deep, 2 1/2% accurate, values 25, 100, 200, 400 and 1,000 ohms; price 4/6 per set; post paid; special quotation for larger quantities.

ADMIRALTY pattern heavy-duty L.T. transformers, primary 230v a.c. 50 cycles 9amp, secondary 18v centre tapped 10amp; £12/10 each; carr. 20/-.

LONDEX relays, type 220, ref. No. 10F/494, two heavy brass contacts, 24v, fitted in metal cases 4x4x2 1/2 in; 8/6 each.

STAINLESS steel aerial wire in 1.650t reels, gauge 7/015; 38/- per reel; post paid.
STEP down transformers, input 230v a.c. 50 cycle, output 6.3-0-6.3v 19amp; £2/12/6 each; carriage 5/-.

MAINS transformers, 230 v.a.c., output 250v 90ma-2.7v 8amp; price 17/6 each; post paid.

L.T. transformers, input 200-250v 50 cycles, output 12-25v 250va, in metal cases; price £2/15 each.

METAL rectifiers, output 180v 3 1/2 amp; price £3/5 each.

RECTIFIER units, a.c. to d.c., input 200-250 v.a.c. 50 cycles 1 phase, output 160-200 v.d.c. 45mA., price 4/6 each; post paid.

WESTINGHOUSE rectifier sets, style 288 G.P.O., input 200-250v a.c. 50 cycles, output 50v d.c. 1 1/2 amp; £3/10 each; carriage 10/-; ditto rectifying sets, output 50v d.c. 5amp; £2/10 each; carriage 5/-; we have a large stock of G.P.O. type 3000 and 600 relays, assorted contacts and coils and Siemens high-speed relays.

NEW Uniselector spares, comprising of banks, wipers, coils, etc., price on application.

A LARGE assortment of various ex-W.D. radar and radio equipment, relays power packs, oscillograph units, gears, photographic apparatus; s.a.e. for lists.

H. FRANKS, 58 New Oxford St., London, W.C.2. Tel. Museum, 9594. [0057]

SOUTHERN RADIO SUPPLY, Ltd., 11 Little St., Newcut, London, W.C.2. See our displayed advertisement page 109. [0016]

LARGE selection of Govt. surplus technical equipment of all types; your enquiries welcome from 20 tons to one condenser; restricted to post orders only at the present.—J. Wells, 118, Lake Rd., Portsmouth. Callers welcome. [7296]

VOLTAGE control units, with metal rectifier voltage regulator, panel light, switch, 8 mfd. paper, mains noise filter (this alone advertised elsewhere at 21/-), fuses, etc., brand new; 9/6 carr. paid.—K. W. Logan, Westalby, Hitchin, Herts. [7147]

MIKES, 40/50, 9d; mike trans. VOR97 holders, 1/-; 7193, 1/9; VT501, 3/-; 2B6, 2A6, 3/6; iron cores, 1/3 doz.; sleeping, 2d; SW coils, 6d; 20K potms. 6d; 015kV, 9d; 8/275, 1/6; 64/150, 9d; crystals, 3d; s.a.e. lists before ordering.—Annakin, 25, Ashfield Place, Otley, Yorks. [7291]

230/115v step-down transformers, 75-watt, 230/6/6; heavy duty output transformers, weight 3 1/2 lb., primary 230v, one centre tapped and one secondary 4 taps, these can also be used as small mains transformers, delivering 150-0-150v at 100ma and 10-20-30-40v all at 65mA, 230v input only, 4/6, one only Sophony Baird Tape Recorder with microphone and guarantee, used only for demonstration, £45.—Haynsons, 14, St. Mary's Bedford, Tel. 5568.

"AUTOMAT" HOME CHARGERS, SELENIUM RECTIFIERS, CHARGER KITS

All New Goods with Full Guarantee



"AUTOMAT" HEAVY DUTY HOME CHARGER, for car or radio cells. Virtually unbreakable. Selenium rectification. Impregnated transformer of large size. Fine workmanship and appearance. 12 months guarantee. For A.C. mains only. Standard model 6 v./12 v. 2 amp. output, 8 1/2 lbs. wt., 59/6, post 2/-. Minor 1 amp. model, wt. 7 lbs., 50/-, post 2/-. 5 amp. truck or large car model, £6, carr. 5/-. Minor model for 6 v. only at 2 amp., 52/6, post 2/-. CHARGER KITS, standard model kit, 45 watt trans., triple tapped, 12 v. 2 amp, selenium rectifier, ballast bulb, for 2 v. 6 v. 12 v. charger, simple and foolproof, 38/6, post 1/4. Handsome steel case with screws and grommets, 13/- extra. Kit 6 v. 2 amp. only, 34/-, extra 13/-, Larger kit, 60 watt trans., 12 v. 3 amp. Westalby rectifier, ballast bulb for 2 v., 6 v., 12 v. charger, 46/-, post 1/8, or 70 watt trans., 12 v. 4 amp. S.T.C. rectifier ballast bulb for 2 v., 6 v., 12 v., 54/- Heavy duty kit for 6 v./12 v. 6 amps. 120 watt trans., 12 v. 6 amp. rect., slider resistance, ammeter, £4/12/6, wt. 17 lbs. Carr. 3/-. Ditto kit to charge 1 to 9 cells at 4 amps. or up to 18 at 2 amps., £4/18/-, carr. 3/-. 2 v. trickle rectifier with transformer 12/6, post 8d. SELENIUM RECTIFIERS, new stocks not surplus, £2/6, 32 v. 1 amp., 13/-; 12 v. 2.5 amp., 18/6; 12 v. 4 amp., 22/-; 6 v. 2 amp., 9/-; 24 v. 4 amp., 48/-; Giant finned type, 12 v. 6 amp., 32/-; 24 v. 6 amp., 63/-; trickle charger type 2 v./6 v. 1 amp., 4/10; 6 v. 1 amp., 6/10, post 6d.; 12 v. 1 amp., 9/-; Selenium H.T. rectifiers, small space type, 260 v., 60 ma., 7/6 ea., post 4d.; 250 v. 100 mA. bridge, 13/6, post 6d.; for U.S. midgets 110 v. 60 mA., 6/6. Eliminator type, 130 v. 30 mA., 6/6; 24 v. 40 ma., for relay operation, 2/10.

ELIMINATOR KIT. Transformer, selenium h.t. rect., l.t. rect., 2x15 mfd. condensers for 120 v. 30/30 mA. eliminator with trickle charger, 35/-, or with handsome steel case, 43/-, post 1/2.

"RENEWBAT" battery desulphator and conditioner car size, 3/-, post 4d.

CHAMPION PRODUCTS

43 Uplands Way, London, N.21. Phone LAB 4457

NEW ELECTRONIC SUPPLIES Co. 281 LEEDS ROAD, FAGLEY, BRADFORD, YORKS.

MAIL ORDER ONLY

Primaries 200/250. Varnish impregnated. New goods only. S = drop through. F = fully shrouded. W.F. = skeleton finish, upright. Special quotes 48 hours. Stamp, please. C.W.O. carriage paid.

S261. 250-0-250 v. 75 m/a., 6.3 v. 3 a., 5 v.	18/11
2 a.	21/3
*S350. 350-0-350 v. 90 m/a.	23/11
*S250. 250-0-250 v. 110 m/a.	23/11
*S300. 300-0-300 v. 110 m/a.	24/11
*S351. 350-0-350 v. 110 m/a.	26/11
Above marked * have L.T.s 0-4-6.3 v. 4 a. 0-4-6 v. 2 a.	
S315. 350-0-350 v. 160 m/a., 6.3 v. 3 a. C.T., 5 v. 3 a.	29/11
F315. 350-0-350 v. 160 m/a., 6.3 v. 6 a., 6.3 v. 3 a. 5 v. 3 a.	43/9
*F350. 350-0-350 v. 90 m/a.	23/3
*F250. 250-0-250 v. 110 m/a.	24/11
*F300. 300-0-300 v. 110 m/a.	25/11
*F350. 350-0-350 v. 110 m/a.	27/11
Above marked * L.T.s 0-4-6.3 v. 4 a., 0-4-6 v. 2 a.	
W.F.S. 260-0-260 v. 90 m/a.	19/11
W.F.B. 350-0-350 v. 90 m/a.	20/11
Above 2 L.T.s, 6.3 v. 3 a., 5 v. 2 a.	
S3515. 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	29/6
F3515. 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	32/9
S205. 250-0-250 100 m/a., 6.3 v. 6 a., 5 v. 3 a.	27/9
F205. 250-0-250 100 m/a., 6.3 v. 6 a., 5 v. 3 a.	29/11
Williamsons mains F.425. 425-0-425 v. 200 m/a., 6.3 v. 4 a. C.T., 6.3 v. 4 a. C.T., 5 v. 3 a.	52/11
Williamsons Amplifier Components below — Pre-amp, Mains, F.320-0-325, 20 m/a., 6.3 v. 1.5 a., 6.3 v. 0.6 a.	
C.E.8. 50 H. 50 m/a., 1,500 ohm	21/11
C.E.9. 10 H. 150 m/a.	29/11
C.E.10. 30 H. 20 m/a.	18/-
W.F.C.11. 8 H. 110 m/a.	14/11
All above very heavy jobs, generous design.	
5in. Speakers	19/8
6in. Speakers	22/8
8in. Speakers	25/8
10in. Speakers	33/8
All above less Transformer.	
Chassis Type 2 to 4 ohm Speech Coil Transformers can be supplied.	
1lb. bobbin silk covered 7/0048 Wire (suitable coil winding) 2/6 per bobbin.	

Cabinets of Distinction

2 1/2d. stamp for Catalogue.

Chassis

A.C., 5 valve 3 w/b Superhet Radiogram chassis. Absolutely complete kit of parts including wiring diagram . . . £10. 10. 0

Or fully wired and tested £12. 5. 0

Amplifiers

Four to fifteen watts output. Wired or in kit form from £3. 19. 6

Full details of above available on request.

LEWIS RADIO CO.

All correspondence to:— (DEPT. 951), 322 HIGH ROAD, WOOD GREEN, LONDON, N.22.

Callers to:— 120, GREEN LANES, PALMERS GREEN, LONDON, N.13. Telephone: BOWes Park 7148 & 5997.

JOHN FARMER

inc. The Mail Order Dept. of the
MIDLAND INSTRUMENT CO.

MAINS TRANSFORMERS, input 200-220-240 v., 50 cycles, 1 phase, tapped secondary giving 3-4.5-6-8-9-10-12-15-18-20-24 and 30 v. at 2 amps. With all terminal data, brand new, boxed, 22/6, post 1/3. **RADIO TRANSFORMERS**, drop through shrouded type, input 110-225-245 v., output 250-0-250 v. at 90 mA., 5 v. 2 amp., 6.3 v. 3 amp., screen. A first-class trouble-free transformer, manufacturers' surplus, brand new, boxed, 20/-, post 1/3.

PARMEKO L.F. CHOKES (potted), 2 types: (a) 100-H at 10 mA., new, boxed, 5/6, post 10d.; (b) 3.6 to 4.2-H at 150 mA., 20-H at no D.C., unused, 5/6, post 1/-.

GERMANIUM CRYSTAL RECTIFIERS, wire ends, brand new, 4/6 each, post 3d., 48/- doz., post 3d. **ANTENNA RODS** (Whip Aerials), 3 4ft. tubular steel heavily copper-plated sections that screw into each other, total length 12ft., weight 11 oz., base 3/4 in. dia., tapering to 1/4 in. dia. Ideal for T.V. and car radios. Brand new in water-proofed cardboard containers, 7/6, carriage 1/-, 3 for 20/-. Carriage 1/6, 72/- doz., carriage 2/6. **VOLTMETERS**, 0-100 v. A.C., moving coil, internal rectifier, 1 mA., scale 0-20-40-60-80-100 with 1/10th sub-divisions, 2 1/2 in. scale, flush panel mounting, new, 20/-, post 6d. **AMMETERS**, hot wire, 0-9 amps. A.C./D.C., 3 1/4 in. dia., 2 1/2 in. scale, fit 2 1/2 in. dia. hole, flush panel mounting. Brand new, boxed, 10/-, post 6d., 96/- doz., post 1/6.

ALTIMETERS containing high-grade aneroid movement, suitable as ordinary barometers, brand new, 7/6, post 8d., 72/- doz., carriage 2/-. **VEEDER COUNTERS**, 0-9999, last digit is 1/10th. Direct operated side shaft 1/2 in. dia., 5/-, post 3d., 48/- doz., post 8d. **BOWDEN DRIVE CABLE**, very fine stranded steel, for radio tuning drives, etc., packets of 10ft., 2/6, post 3d., 24/- doz., post 4d. **"PYE" 45-Mc/s I.F. STRIPS**. A ready-made vision unit for the London frequency, complete with 7 valves (EF50 (6) and EA50). New, unused, 60/-, post 1/6. **RU-19 DUAL COIL SETS**, low range "Q" and high range "M", 540-830 and 5200-7700 kc/s., 5 coil sets, 5-gang switch, trimmers, etc., new, unused, 1/6, post 1/-.

PACKARD BELL PRE-AMPLIFIERS. Contain 2 valves (6SL7/GT and 28D7), input and output transformers, relay, resistors and condensers, etc., operates from single 24/28 v. 4 amp. battery source, low impedance input and output, will raise moving coil or carbon mike on input to loudspeaker level on output. In very smart metal cases, size 5in. x 4 1/2 in. x 3 1/2 in., complete with accessories and instructions, brand new, 20/-, post 1/-. **LONDEX RELAYS**, Type 452, 9-12 v. operation, 150 ohm coil, 2-pole contacts, size overall 2 1/2 in. x 1 1/2 in. x 1/2 in., new, 2/6, post 4d., 24/- doz., post 1/-. **MOTOR ALTERNATORS**, 230 v. 50 cycle 1 phase, .64 amp. cont., rating 2,880 r.p.m. capacitor motor. Fitted enclosed reduction drive gearbox, final drive approx. 60 r.p.m. Motor is coupled to generator 250 v. 1,250 cycles 24 amp., flexcitation 24 v. 4 amp., cont. rating. Size approx. 14 1/2 in. long, 6in. dia. Standard base mounting with external wiring diagram. Perfect condition, 70/-, carriage 7/6. **DIMMER SWITCHES**, variable wire wound resistors, approx. 50 ohms at 1/2 amp., new, boxed, 1/6, post 3d., 15/- doz., post 1/-. **TOGGLE SWITCHES**. Single hole panel mounting, 250 v. 2 amp. S.P. On/Off, brand new, 9d. each, post 3d., 7/6 doz., post 6d., 72/- gross, post 1/6. **MODULATOR UNITS**, TYPE 169. Contain CV-67 Klystron, 5U4G, EF50, 3 neon stabilisers, also 84101 valve, two 250 v. 100 mA. selenium rectifiers, small motor with reduction gearing, 2 large transformers, various oil and paper condensers, pots, resistors and other incidentals, in metal cases, size 18in. x 8 1/2 in. x 7 1/2 in., brand new condition, in wood cases; a real bargain offer, 40/-, carriage 7/6.

The above are a few items from our May Catalogue and June Supplement, obtainable direct from:

JOHN FARMER (DEPT. A.1.)
194 HARBORNE PARK RD.,
HARBORNE, B'HAM 17

Tel.: HARBORNE 1309

COMPONENTS-SURPLUS AND SECONDHAND

LITTLEWOODS, North London's best selection of radio and television components; pay us a visit or phone your enquiries; no lists. **LITTLEWOOD & GRUNER**, Ltd., 27, Ballards Lane, Finchley, N.3. Fin. 3060. 10055

ENQUIRIES invited for home or export use for large or small quantities of tropically sealed, metal-cased tubular capacitors, paper dielectric; also waxed ceramic disc capacitors, 10pf, 20pf, 25pf, 30pf, at £1 per gross or £5 per thousand; mica, .01mf wire ends, 10/- per dozen; CV65 triggered spark gap valves, £5 per dozen, unboxed and unused—Ward, 9, West Cliff, Dawlish, Devon. Tel. 2135. [7297]

MAINS transformers. Surplus to requirements of leading manufacturer. 350-0-350, 6v 3a, 5v 2a, 100 mA, standard voltage, with adjust panel, 23/-, post 2/-; fresh stock conds. 8mf 450v 2/6, 16/450 3/3 8x16/450 3/9, 25/25 1/6, 50/50 2/-; 1/500 7/6 doz; co-ax cable, 80 ohms 12/6 doz yds; P.M. speakers 2 1/2 in 13/6, 3in 11/6, 3 1/2 in heavy 12/6, 3 1/2 in light 14/6, 5in 13/6, 8in 15/6; out/trans. 3/6; h/duty 5/9; v/holders, 10/10c, amp 6/- doz. BGG 3/6 doz. component list available; stamp please—Radio Unlimited, Elm Rd., London, E.17. Key 4813. 10062

NOTICES

BRITISH SOUND RECORDING ASSOCIATION. MEMBERSHIP of the Association is essential to all actively engaged or keenly interested in high quality sound recording and reproduction. Additions have again been made to the publications of the Association. There are also the very special test discs. Full information is contained in the latest Publications List P.104. This, together with the new brochure giving full information of the work of the Association and the benefits conferred by membership; with a Membership Application, may be obtained from the Membership Secretary, Harrie J. King, 48, Mount View Rd., North Chingford, London, E.4. 10119

IN excess of present requirements, stock of new British valves for disposal in one lot, 350, mainly relative to sets pre-1945, suitable for leading makes.—Kingstone, Ltd., 39-43, Bedford St., Leicester. 17299

WANTED, EXCHANGE, ETC.
WANTED, Magnetophon Toms B, with spares (amplifier not required)—Box 2665, 10198

WANTED, dynamometer, a.c. test set, also oscilloscope type 339A, also L050A oscillator.

LESLEE DIXON & Co., 214 Queenstown Rd., Battersea, S.W.8. Maudslayi 2159.
WANTED 8-way slide contact valveholders: quantity, price and sample to B. E. P., Ltd., Rugeley, Staffs. 17223

EX-GOVERNMENT aircraft and radio equipment, metal, wood, any quantity.—Ball, 60, Heath Row, Bishop's Cleeve, Herts. 16969

WANTED, HRO coils, Rx's, etc. AR88s BC348s, S27s, etc.—Details to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. 10163

WANTED, laboratory test equipment, including standard signal generator, watt meter, oscilloscope, bridges, recorders; send price and details to: **HATFIELD INSTRUMENTS**, 175, Uxbridge Rd., Hanwell, W.7, Tel. Ealing 7719. 10037

WANTED, all types of radio equipment, test instruments, radio receivers, personal sets, television, components, etc., etc.; call, write, send or phone.

MILLER'S RADIO, 38a, Newport Court, Charing Cross Rd., London, W.C.2. 10037

WANTED, set manufacturers' or ex-Government radio equipment, large or small quantities of valves, electrolytics, speakers, meters, also components. 10081

LOWE BROS., 199, Mile End Rd., London, E.1. Ste. 2579. 16554

WANTED, RCA speech amplifiers, type MI-11220 J or K.—Offers, stating quantity and price, to PCA Radio, The Arches, Cambridge Grove, W.6. 10081

VALVES surplus, following types wanted for cash, any quantity:—6K8, 6Q7, 6V6, 5Z4, EF39, EF36, EL32, or equivalents.—N. R. S., 16, Kings College Rd., London, N.W.3. 17242

WANTED, Antenna tuning units type BC-939-A and T-50 microphones and junction boxes JB-70-A—PCA Radio, The Arches, Cambridge Grove, W.6. Tel. Riv. 3279. 10080

WANTED, BC-610 Hallicrafters transmitter, SX-28, AR-88, S-27; HRO receiver and spare parts for above; best price—Write Box 6664, c/o Spicers Service, 69, Fleet St., London, E.C.4. 10167

CLEAN copies "Wireless Engineer," May, '43, Index abstracts for '45, '48, '49; offer "W.E." for Jan., '49; Dec., '48; Nov., '45; April to Dec., 1938.—Brown, 29, Camborne, W.312, Morden, Surrey. 17312

WANTED, AN/APR-4 receiver, any units; any other good quality U.S. surplus radio and radar, tubes, test sets; laboratory equipment, etc.; give condition and price in first letter.—Littell, Farhills, Box 26, Dayton 9, Ohio, U.S.A. 16346

REPAIRS AND SERVICE

BERNARD'S—New address (see below).

TELEVISION, radio and amplifier repairs, conversions and modifications; home-built receivers aligned; commercial radios rebuilt; send equipment with full instructions for quotation by return post; 12 months' guarantee on all work done.

BERNARD'S, 12, St. Stephens House, Westminster Bridge, London, S.W.1. 10099



"DEMOBBED VALVES" MANUAL

2/9 POST FREE

giving equivalents of British and American Service and Cross Reference of Commercial types, with an appendix of B.V.A. Equivalents and comprehensive Price List. We have still some valves left at PRE-BUDGET rates which actually sold at the old price.

There is a space free for YOU on our mailing list. EXPORT to all parts of the Commonwealth and beyond—safely packed, fully insured (no C.O.D.) and free of tax.

SPEAKER MATCHING TRANSFORMERS, Ex-Gov. Surplus, guaranteed, 2/- post 6d.

MORSE BUZZER OUTFITS. Consisting of a buzzer, a morse key and a battery compartment, all mounted on a polished baseboard. All parts high grade ex-Air Ministry. An excellent gift for a boy. 6/- post free.

NEW BOOKS.

"Wireless World" Radio VALVE Data, characteristics of 2,000 Valves and C.R. Tubes, 3/9.

"Radio Data Book for Constructor, Amateur and Engineer," 1/9.

"Using Ex-Service Radio Apparatus," 2/9.
"Modern Valve Comparison Manual," 3/3.
"A Comprehensive Radio Valve Guide," 5/3.

SPECIAL PURPOSE VALVES: VR92 = EA50 2/9 post 9d. VT137 = 1626 7/6; 1904 Barretter 4 pin 7/6; 1616 West ngouse 21/-; 304H 25/-; 813 45/-; Test Prods. Superior Quality, the pair 4/-; Easter Rods, 3/6; Post 1/-. Sapphire Gram needles (6,000 playings) 6/6.

CONDENSER TESTERS and Rectifier Units. Plugs straight into A.C. mains 200/240 v. and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete 39/6. Post 1/-

AMPLION TEST METER. 1,800 ohm per volt on all D.C. and A.C. ranges, 10 v., 100 v., and 500 v. D.C. and A.C., 50mA and 500 mA. D.C. Resistance up to 200,000 ohm. (3,000 ohm centre scale), with self-contained battery, 5,000 volt range with a separate H.T. test prod (9/6 extra). Supplied with test prods. Multi-colour scale easily readable. £5.

SERVICE SHEETS, the one you require enclosed if available in a dozen our choice 10/6.



Engraving as a profitable spare-time Business at Home with our **VIBRO TOOL**.

ENGRAVE on anything, even the hardest Metal, Plastic, Glass, Wood, Leather, Jewellery, etc. Operates off A.C. mains, plugs into light socket. 10,000 users enthusiastic. 26 pp. illus. instruction manual FREE. Guaranteed. Remit cross P.O., M.O., Cheque or C.O.D. 52/6. (Old price.)

SPECIAL OFFER: JUNEERO Complete Workshop in a Box sent on 7 days APPROVAL with Money Back Guarantee. Complete only 45/- Post 1/6.

(Kindly mark envelope W.W.9.)

RADIO BULLS VALVES
246, HIGH ST., HARLESDEN NW10



RACK MOUNTING CABINET FOR 19" PANEL

CABINET to accommodate one 19" x 10 1/2" x 14 G. Steel Rack Panel with 17" x 12" x 2 1/2" Chassis and Angle Brackets in 18G Steel; Panel secured by four Chromium Plated Screws. Approximate overall dimensions 21" x 12 1/2" x 11 1/2" high, Louvered on Back, having radussed front corners and Rubber Feet..... £4 2 6

Less Panel Chassis and Angle Brackets..... £3 11 6

Recessed Lid 17 1/2" x 8" in top. EXTRA 11 0
Finishes; Black, Grey or Brown Wrinkle Enamel. Parc Carriage and Packing (on orders under £5)..... 5 0


Please note that all List Prices have been increased 10% from 31st March, 1951.

ILLUSTRATED LISTS AND TRADE TERMS ON APPLICATION.

REOSOUND ENGINEERING & ELECTRICAL COMPANY, "REOSOUND WORKS," COLESHILL ROAD, SUTTON COLDFIELD

Tel.: SUT. 4855. Grams: Reosound, Sutton Coldfield

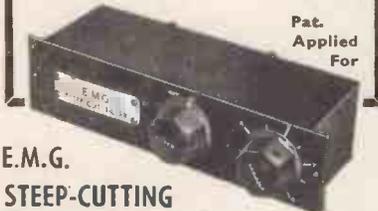A REMARKABLE ACHIEVEMENT IN FILTER DESIGN



E.M.G. STEEP-CUTTING INFINITELY VARIABLE FILTER

- Cuts at any selected frequency between 4,000 and 8,000 c.p.s.
- Average steepness of cut 30 db. per octave.
- Connects between secondary of output transformer and speaker (16 ohms. rated impedance).
- Specially valuable for use with new microgroove records.
- Greatly reduces needle-hiss on ordinary records with minimum high note loss, and suppresses high pitched interferences on radio.
- No distortion, and no appreciable loss of volume.
- Leadset available from the manufacturers.
- Novel circuit, patents pending.

£4 - 10 - 0

Trade Enquiries Invited

E.M.G. HANDMADE GRAMOPHONES, LTD.
6 Newman St., Oxford St., W.1.
Telephone: Museum 9971-2-3

REPAIRS AND SERVICE
M AINS transformers rewound, new transformers to any specification.
MOTOR rewinds and complete overhauls; first-class workmanship, fully guaranteed.
F. M. ELECTRIC Co. Ltd., Potters Bldgs., Warser Gate, Nottingham, Est. 1917. Tel. 3855.
L OUDSPEAKERS repaired promptly.—Model Loudspeaker Service, 34a, Bullingdon Rd., Oxford.

S PEAKER repairs, cones fitted, fields and clock coils wound, prompt service, guaranteed satisfaction.
L. S. REPAIR SERVICE, Pluckley, Ashford, Kent. [0130]

M AINS transformers rewound or constructed to any specification; prompt delivery.—Bede Transformer Co., Ltd., Bedesway, Bede Trading Estate, Jarrow. [3198]

R EPAIRS.—E.H.T., mains and O.P. transformers field coils and chokes; also armatures and motors; new transformers designed to any specification; all work fully guaranteed.
WILLESDEN TRANSFORMER Co., Ltd., 20a, Church Lane, Church Rd., N.W.10. Tel. Willesden 7093.

R ADIO MAINTENANCE SERVICE for guaranteed rewinds and repairs; armatures, F.H.P. motors, vac. units, portable tools, etc.; good deliveries.—139, Goldhurst Terrace, N.W.6. Mal. 6133. [5925]

"SERVICE with a smile"—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cord.—F.R.I. Ltd., 22, Howland St., W.1. Museum 5675. [0112]

R EWINDS, special service. Specialists of all standard and non-standard range, repairs and standardised; prompt attention.—The Electrical Instrument Repair Service, 329, Kilburn Lane, London, W.9. Tel. Lad. 4168. [3715]

A ISH REWINDS, no delay transformers. Mains, T.V. output, chokes, also to your specification, vacuum impregnation, interleaving, new tag panels; our aim—your satisfaction.—Aish & Co., Ltd., Vanguard Works, Poole, Dorset. [7065]

24-HOUR service, 6 months' guarantee, any transformer rewound, mains outputs and i.f.s., etc.; all types of new transf., etc. supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 100 Windham Rd., Bournemouth. [6520]

M ETROPOLITAN RADIO SERVICE for rewinds, windings, mains, E.H.T. transformers, chokes and field coils; new transformers designed and manufactured singly or in quantities.—Metropolitan Radio Service Company, 75, Kilburn Lane, London, W.10. Tel. Ladbrooke 3120. [0130]

WORK WANTED

TOROIDAL coils, manually wound to close inductance limits, precision wavewinding, on Govt. lists.
BEL, Marlborough Yard, London, N.19. Arc. 5078. [0165]

K IT radio sets, amplifiers and pre-amps built up, 7/- per valve stage; send kit and circuit for immediate attention; special price to trade.—R. E. Hope, Television Engineer, Bealington, Herts. [7287]

D RAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications; sub-contracting work of this nature undertaken.
DRAWING & TRACING, Ltd., 456a, Ewell Rd., Tolworth, Surbiton, Tel. Elmbridge 7406. [5975]

J. MORT, M.Sc., A.M.I.E.E., offers to the J. trade and amateur a service of technical advice, design and construction of special test gear, receivers and other apparatus, including correction of faults in home-built apparatus.—J. Mort, 18, Heath St., Golborne, Lancs. [5752]

MISCELLANEOUS

M ETALWORK; all types cabinets, chassis, racks, etc., to your own specifications.
PHILPOTTS METAL WORKS, Ltd. (G4B1), Chapman St., Loughborough. [0208]

W ALNUT radiogram cabinets, stamp leaflets.—Cabinetware, 1a, Heyes St., Blackburn.
W ALNUT radiogram cabinet; stamp details.—E. Wisker, 501, Hale End Rd., Highams Park, E.4. [6942]

80 ft. coaxial cable, 1/- yard; 800 balanced line, 7/4d yard; please add postage.—Fon Radio, 7, Station Approach, Slough, Bucks. [7219]

FLEX—Super quality aero intercom. leads containing 4 lengths, two screened, tot. approx. 24ft, 2/3 each. Buy for 10/- post free.—L.T.S., Ltd., Bromhurst, Barton Rd., Urmston. [7166]

E NGRAVING, amateurs and trade could take full advantage of the opportunity of engraving problems in the future by getting in touch with A. G. Engraving, 15a, Windmill Rd., London, S.W.18. Brass, bronze, erinoid, Perspex dials; one knob or repetition equally entertained. [0034]

A LLSCREWS, Ltd., for B.A. screws, nuts, washers, studding, grub-screws, bolts, soldering tags, woodscrews, etc., plain or nickel or cadmium plated, one-cross packets or large quantities; stamp for lists.—270a, King St., Hammersmith, W.6. Riv. 7762. [5426]

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges; B.A. screws, nuts, washers, soldering tags, eyelets, ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod; headphones, flexes, etc.; latest radio publications, full range available; list, s.a.g., trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4. [0138]

NORTHERN TRANSFORMERS CO.

TRANSFORMER HOUSE,
215, BARKEREND RD., BRADFORD,
YORKS.

All Transformers guaranteed against faulty workmanship

ALL PRIMARIES ARE TAPPED 200/250 v. INPUT

MAINS TRANSFORMERS

DT/150, 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	35/8	
MF/150, 350-0-350 v. 150 m/a., 6.3 v. 4 a. C.T., 5 v. 3 a.	37/9	
DT/100, 350-0-350 v. 100 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	25/6	
MF/100, 350-0-350 v. 100 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	27/8	
DT/80, 350-0-350 v. 80 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	24/3	
MF/80, 350-0-350 v. 80 m/a., 0-4-6.3 v. 3 a., 0-4-5 v. 3 a.	26/6	
DT/33, 350-0-350 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	22/6	
MF/350, 350-0-350 v. 250 m/a., 6.3 v. 6 a., 4 v. 2 a., 0-2-6.3 v. 2 a., 4 v. 3 a.	68/6	
MF/180, 350-0-350 v. 180 m/a., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a.	44/6	
MF/120, 350-0-350 v. 120 m/a., 6.3 v. 4 a., 5 v. 3 a.	34/6	
DT/120, 350-0-350 v. 120 m/a., 6.3 v. 4 a., 5 v. 3 a.	33/9	
DT/M2, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	20/6	
DT/80, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	21/6	
MF/M2, 250-0-250 v. 80 m/a., 6.3 v. 3 a., 5 v. 2 a.	22/9	
Williamson O.P. Transformer	87/8	
Williamson Mains Transformer	425-0-425, 6.3 v. 4 a. C.T., 5 v. 3 a., 6.3 v. 4 a. C.T.	57/6
Williamson Choke, 30 H., 20 m/a., shrouded	22/3	
Williamson Choke, 50 H., 50 m/a., shrouded	24/9	
Williamson Choke, 10 H., 150 m/a., shrouded	33/6	
Williamson Free Amplifier Transformer	23/9	

WE HAVE A SPECIALS DEPARTMENT WHICH DEALS SOLELY WITH WINDINGS TO ANY SPECIFICATION.

DT = Drop Through Type. MF = Fully shrouded type. DT/M = Smaller Drop-through type. MF/M = Smaller fully shrouded type.

WILCO ELECTRONICS

SIGNAL AND NOISE GENERATOR.
This Test Set Type 210 has a Range of 20-88 Mc/s in 4 Bands. Output 10M/V. approx. Modulated or unmodulated, Noise generator output 5 Microvolts with attenuator, Crystal controlled, 2 Crystals, Vernier adjustment. Brand new. Input 80 and 115 volts 1,000 cycles. £20. Or 230 volts 50 cycles £25.
CONDENSERS. Block type, 8 Mfd. 750 v. D.C., 10/6 ea.; 10 Mfd. 1,000 v. D.C. 15/- ea.; 10 Mfd. 1,500 v. D.C., 23/- ea.; 1.5 mfd. 4,000 v. D.C., 25/- each.
0/50 MICROAMMETER 2 1/2 in. Flush type contained in Test Set 28. A very sensitive meter only 50/-.

GERMANIUM CRYSTAL DIODES.
Midget size wire ends, 4/6 each.
VR91 (EF50). Brand new, Red, American make 9/6 each guaranteed. British 8/6 each. Ceramic V/holders for same 9d. ea. 7/6 doz.
AIRCRAFT CLOCKS with splendid 8-day jewelled movement. Flange type, made to stringent Govt. specification. Brand new, guaranteed. Ideal for car, study, bedroom, etc., Special offer, 65/- each. Post free.
SLOW MOTION DRIVE. Muirhead, Ratio 50-1. 8/6, Post 1/-.

SLOW MOTION DIAL with Vernier, 200-1 Reduction, front of panel mounting 6in. dia., calibrated 0-100, 5/6 each, post 1/-.
POWER UNITS. With standard mains transformer, 350-0-350 volts, 80 m/a., 6.3 volt 1 a., 6.3 volt .5 a., 5 volt 2 a., 5Z4G valve, etc. Brand new £2/10/- carr and pkg. 2/6.
AMPLIFIERS. 50 watt "Tannoy" Rack mounting, less valves, only £8/10/- to clear. The transformers and chokes are guaranteed O.K. but some small components may require replacing, and wiring renewed. 4 amplifiers on one P.O. Rack for £25.

AMPLIFIERS. 15 watts, Marconi Type 6, using 2-PX25, MHL4, rack mounting, complete with power pack, 200 to 250 volts, 50 cycles, meter, carriage, with valves, £8/10/-, less valves, £6. Catter 7/6.
204 LOWER ADDISCOMBE ROAD, CROYDON.

THE MODERN BOOK CO.

Theory and Design of Television Receivers. By S. Deutsch. 55s. 6d. Postage Free.

Radio Valve Data. By "Wireless World." 2nd edition. 3s. 6d. Postage 3d.

Call Book: Radio Amateur Stations of the United Kingdom. 4s. 3d. Postage 3d.

Radio Amateur Stations of the World (exclusive of the U.S.A.). 8s. 6d. Postage 6d.

Radio Servicing, Theory and Practice. By A. Marcus. 35s. 0d. Postage 1/-.

Radio Amateur's Handbook. By the "A.R.R.L." 28th edition 22s. 6d. Postage 1/-.

Time Bases (Scanning Generators). By O. S. Puckle. 2nd revised edition. 30s. Postage 9d.

Radio Servicing Equipment. By E. J. G. Lewis. 25s. 0d. Postage 9d.

Fundamentals of Automatic Control. By G. H. Farrington. 30s. Postage 6d.

Radio Handbook. By "Editors and Engineers." 13th edition. 48s. Postage 1/-.

Wireless Servicing Manual. By W. T. Cocking. 8th edition. 12s. 6d. Postage 4d.

Radio Engineering. By F. E. Terman. 3rd edition 50s. Postage Free

Radio Circuits. By W. E. Miller. 3rd edition. 5s. Postage 4d.


We have the finest selection of British and American radio books in the Country. Complete list on application.

19-23 PRAED STREET

(Dept. W.9)

LONDON, W.2.

PADddington 4185

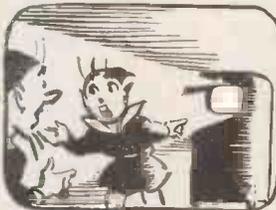

THE "FLUXITE QUINS" AT WORK

"The light in our TV's gone out.

It needs overhauling, no doubt.

"Till we get some FLUXITE

And just for w-night

I've borrowed your headlight, old scout."

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all Ironmongers—in tins from 1/- upwards

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire AND SOLDER. It's simple—with FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by simple pressure. Price 2/6, or filled, 3/6.

FLUXITE
SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT Soldering and for leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1d. ea.

FLUXITE LTD. (Dept. WW), BERMONDSEY STREET, LONDON, S.E.1.

MISCELLANEOUS

TELEVISION camera data as used in amateur demonstrations, 15/-.—G2DUS/T, 40, Regent St., Stotford, Beds. [7256

WALNUT radiogram and television cabinets. Specially constructed, stamp details.—R. Shaw, 69, Fairlop Rd., Leytonstone, E.11. [7248

CABINETS.—We manufacture radio and television cabinets to private or trade order singly or in quantities; trade enquiries for special and exclusive designs invited; also, we supply drawings and instructions for home construction of cabinets, including radiogram, radiogram/TV, 9in table and 12in console TV (both suitable for Viewmaster, etc.); send for illustrated catalogue and price list, etc. CHAFFY-CONSOLE, 6, Setton Rd., Petts Wood, Kent. [7171

FLUORESCENT 80w tapped choke, 22/6; twin 40w ballast, 230v, complete with 2 bi-pin holders, glow starters, circuit, 15/9; glow starter lamps, S.B.C., 2/6; battery chargers, 6-12v, 2 1/2 amps, 47/6; selenium metal rectifiers, F/w, 12v, 2 1/2 amps, 8/9; Colvern wirewound pots, 50 ohm, 1in spindle, 3/-; transformers, suitable for carbon arc welding, 230v, will weld your car mudguards nicely, 45/-; 1/4hp electric motors, 230v a.c., 80/-.—Malden Transformer Supplies, 200, Cambridge Rd., Kingston. [0038

SITUATIONS VACANT

ADMIRALTY.
APPLICATIONS are invited from engineering, electrical and ship draughtsmen for temporary service in Admiralty Departments at Bath. CANDIDATES must be British subjects of 21 years of age and upwards, who have had practical workshop and drawing office experience. SALARY will be assessed according to age, qualifications and experience within the range £320-£545 per annum. APPLICATIONS, giving age and details of technical qualifications, apprenticeship (or equivalents), workshop and drawing office experience, should be sent to Admiralty (C.E. II, Room 83), Empire Hotel, Bath. Candidates required for interview will be advised within two weeks of receipt of application. [6952

CROWN AGENTS FOR THE COLONIES.
(A) DIESEL-ELECTRIC mechanic and (B) WIRELESS operator mechanic required for the Falkland Islands Dependencies Survey for one tour of 18 or 30 months in the first instance. Salary according to qualifications and experience in scale £250 rising to £400 a year. Duty allowance £50 a year. Quarters, subsistence, clothing and routine canteen stores are provided free of charge while serving in Dependencies. Liberal leave on full salary. For both posts candidates should preferably be single. For post (A) they must possess a general working knowledge of electricity, and be capable of running and maintaining small diesel generating sets with associated switchboards, accumulators, etc. For post (B) candidates must be able to transmit and receive Morse at 25 words a minute (plain language or code) and be capable of elementary maintenance of wireless transmitting and receiving equipment.—Apply at once by letter, stating age, full names in block letters, and full particulars of qualifications and experience and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting for post (A) M.28666.B and for post (B) M.28666.B on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. [7305

CROWN AGENTS FOR THE COLONIES.
DIESEL-ELECTRIC Mechanic required by the Falkland Islands Dependencies Administration for service in South Georgia for one tour of 30 months in the first instance. Salary £310 rising to £370 a year. Free furnished quarters, light, water and fuel. Free passages and liberal leave on full salary. Candidates must possess a sound knowledge of the general principles of electricity and have had experience of the running and maintenance of small diesel-driven A.C. and D.C. plants with associated switchboards and of the charging and maintenance of lead acid accumulators. They should also be capable of undertaking the maintenance of Redifon and Marconi transmitters (of 500 to 800 watt output) and receivers, Creed Automatic Transmitter equipment and automatic distress signalling equipment. Apply at once by letter, stating age, full names in block letters, and full particulars of qualifications and experience, and mentioning this paper to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M.28624.B on both letter and envelope. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. [7254

NORTHERN POLYTECHNIC, Holloway, London, N.7.
THE Governing body invite immediate applications for appointment as Head of the Department of Radio & Musical Instrument Technology; the salary will be in accordance with the Burnham Scale for Heads of Departments—Grade III, £1,150X£25X£1,500, plus London Allowance; duties to commence on January 1st, 1952.—Application form, together with full particulars will be forwarded on receipt of a stamped, addressed foolscap envelope. R. H. Currell, Clerk. [7301

RADIO-T/V service engineers required N.W. London, only 1st class men apply please, preference given to drivers.—Write Greystone T/V Service, Ltd., 256, Bishopsgate, E.C.2. [7294

NUSOUND PRODUCTS

136 WARDOUR STREET, LONDON, W.1

(Oxford Street end)

Tel: GERrard 8845

WE ARE NOW ABLE TO SUPPLY DECCA, ETC., L.P. RECORDS BY RETURN OF POST. Decca L.P. Catalogue 1/8, post free.

A NEW AMPLIFIER, 10 watts—All triode line-up PX4 output, Neg. feedback etc. Available October, Price £26. (Send stamp for full information. Trade Enquiries invited.)

NUSOUND QUALITY AMPLIFIERS.
81-WATT OUTPUT.—PP 8V8s—Independent bass and treble boost and cut—switch for L.P. records—neg. feedback—provision for radio feeder unit—freq. response 23 to 20,000 c.p.s. ± 1 d.b.—hum 80 d.b. down at 6.5 watts—feedback 14 d.b.—sensitivity .05 volt. Price only £15/17/6. Also available with remote control unit. Price £17/10/-.

41-WATT OUTPUT.—Independent bass and treble boost pre-amp.—provision radio feeder unit. £11/10/-.

PRE-SET T.R.F.—Home, Light and Third with gram-position—air spaced trimmers for stability of tuning. £7/12/6, inc. constructional booklet, 1/8, post free.
Pre-set 8/12c.—Home, Light and Third—choice of M.W. and L.W. Light—Gram. position. £2/18/- inc. VARIABLE RADIO TUNER UNIT.—M.W. and L.W. Bands—8/Het. of small dimensions—R/gram. switch etc. Out latest model. Price £11/5/- inc. All-wave model. £12/2/6.

NUSOUND REMOTE CONTROL AND PRE-AMP. UNIT.—Bass boost—Treble boost and cut—V/C, and switch—L.P. correction switch—Gives a gain of 10:1 in voltage—Ideal for Williamson and W.W. Amplifiers. Price £5/7/6.

NUSOUND REFLEX CABINETS.—For Wharfedale speakers—10in. £9/9/-—12in. £10/10/-.

Veneered polish finish mahogany or oak.

GRAMOPHONE EQUIPMENT.—Connoisseur P/pups Standard L/weight, £3/10/-; Trans., 13/-; Super L/weight, one head, £5/14/8; Micro-groove head, £3/11/8; Trans. 15/-; Fibre P/pup, £4/3/-; Special Trans., 25/-; Garrard plug-in heads, standard, 25/-; Miniature, 49/7; Hi Fi, 53/6; Adaptor, 6/6. Decca Mag. Heads, L.P. and 78, 59/2. Chancery L.P. Attachment G.33, £3/12/6, with Decca L.P. Xial P/pup, £6/2/3.

Decca three-speed motor, £7/3/4; Connoisseur two-speed motor, £20/19/3; Decca Xtal P/pup 53/-; second Acos insert for L.P., 31/6 (similar to GP20); Decca Turnover Xtal P/pup, L.P. or 78, £3/19/4.

COLLARO AC/DC MOTOR, 12in. turntable, £12/2/7
Garrard AC6 Motor (speed controlled), £6/15/10
COLLARO A.C. 514 MB—A.C. motor and Mg. P/pup—Auto Stop, £6/10/5, with Xtal P/pup, £6/16/11; Decca 3-speed Player, Hi Fi Mag. P/pup, L.P. and 78, £19/19/-.

We stock a full range of Wharfedale speakers and all types of components, etc. LATEST ARRIVALS—Super 2XS/AL £14/10/-; Super 5 £4/12/6; Grosver unit 55/-; T.V. & Gram List 4d. (Please add Postage).

B. & H. RADIO EAST STREET, DARLINGTON

BASS & TREBLE SEPARATOR
Enables the use of separate speakers for Bass and Treble. Permits adjustment of treble and matches up speakers of different impedance. Kit of Parts £1 13 6

SCRATCH FILTER
Easily fitted to pick-up and gives marked reduction of scratch 17 6

WHISTLE FILTER
Is very simply installed in speaker wiring and completely eliminates 9 Kc/s. whistle £1 15 0

A.F. and R.F. COILS rewound or wound to specification.

**THE
BRITISH NATIONAL
RADIO SCHOOL**

ESTD. 1940

NOW IN OUR TWELFTH
YEAR AND STILL

**NO B.N.R.S. STUDENT
HAS EVER FAILED**

to pass his examination(s) after completing our appropriate study course.

NOTHING SUCCEEDS LIKE SUCCESS and what we have done a thousand times already, for others, we can do again, for YOU!

**A.M.Brit.I.R.E. and
CITY and GUILDS Radio and
Telecommunications Exams, etc., etc.**

Six months' trial period without obligation to continue.

Please mention this advt. and send for free booklet to:—

**STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
66, ADDISCOMBE ROAD, CROYDON**
Phone: Addiscombe 3341

NEW S.T.C. SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products. **NOT SURPLUS.** E.H.T. H4/200 W.V. Teleserv. Replaced by N2/100, 17/-; for VR97, N2/50 12/-, post 6d.

NOTE REVISED PRICES 1st JUNE, 1951

HALF WAVE RECTIFIERS. 16 v. 2 a., 9/8; 1 a., 10/8; 2 a., 12/2; 3 a., 18/3, all post 6d. 4 a., 19/3; 6 a., 27/-, post 1ld. 30 v. 1 a., 14/8; 2 a., 18/-; 4 a., 31/-; 6 a., 45/6; 48 v. 1 a., 19/6; 2 a., 24/3; 4 a., 44/6; 6 a., 64/-; 100 v. 2 a., 43/-; 4 a., 80/-; 6 a., 116/-, all post 1/1.

HALF WAVE HEAVY DUTY 7½in. SQUARE COOLING FINS. 16 v. 5 a., 26/-; 10 a., 29/-; 16 a., 53/-; 30 v. 5 a., 41/6; 8 a., 47/-; 48 v. 2.5 a., 31/-; 5 a., 56/-; 8 a., 65/-; all post 1/1.

BRIDGE CONNECTED FULL WAVE. 17 v. 1.25 a., 14/2; 1.7 a., 22/9; 2.5 a., 25/-; 3 a., 26/-; 4 a., 30/-; 5 a., 32/6 all post free. 33 v. 7 a., 21/-; 1 a., 24/3; 1.5 a., 39/-; 2 a., 44/-; 3 a., 45/-; 4 a., 54/-; 5 a., 58/- all post 1ld. 54 v. 1 a., 33/6; 1.5 a., 54/-; 2 a., 60/-; 3 a., 61/-; 5 a., 81/-; 72 v. 1.5 a., 68/-; 2 a., 79/-; 3 a., 80/-; 5 a., 106/-; 100 v. 1.5 a., 97/-; 2 a., 112/-; 5 a., 152/- all post 1/1.

BRIDGE CONNECTED HEAVY DUTY 7½in. SQUARE COOLING FINS. 17 v. 6 a., 43/-; 10 a., 49/- post 1/6.

BRIDGE CONNECTED HEAVY DUTY FUNNEL COOLED, also 7½in. SQUARE COOLING FINS. Revised price, same both types. 17 v. 12 a., 88/-; 20 a., 102/-; 30 a., 142/-; 50 a., 211; 33 v. 6 a., 79/-; 10 a., 91/-; 12 a., 146/-; 20 a., 164/-; 54 v. 6 a., 104/-; 10 a., 124/-; 72 v. 6 a., 134/-; 10 a., 154/-; 100 v. 6 a., 192/-; 10 a., 211 all post 1/8.

Special price Funnel Rects. BRIDGE. D.C. Output, 120 v. 20 a., £15/10, delivered.

SLOW DELIVERY OF SOME RECTS., WILL DO OUR BEST!

Wholesale & Retail
T. W. PEARCE (Est. 19 yrs.)
66 GREAT PERCY STREET, LONDON, W.C.1
On Pentonville R.I. Between King's Cross and Angel

SITUATIONS VACANT

COMMONWEALTH Technical Co-operative Scheme.
APPLICATIONS are invited by the Commonwealth Relations Office for the post of expert radar technician for a radar wind finding station in Colombo under the Government of Ceylon, at a salary of £1,000 to £1,200 per annum; an allowance will be paid to cover board and lodgings, and free medical attention will be available; return passage of the person appointed will be paid together with cost of local travel on duty; arrangements for leave and the passage of dependants by negotiation; applicants preferably between the ages of 35 and 45, should have a Higher National Certificate or be of R.T.C.B. and City and Guilds standard; they must have considerable servicing and maintenance experience of radio and radar and preferably a knowledge of G.L.III sets; the selected applicant will be responsible to the Director, Department of Meteorology, and will be expected to take over and maintain the station equipment and train local staff on routine maintenance; the duration of appointment is approximately three years.—Forms of application may be obtained from the Ministry of Labour and National Service, Technical and Scientific Register (K) York House, Kingsway, W.C.2, quoting D324/51/O/A. [7218]

THE PLESSEY Co., Ltd., Ilford, requires the following staff:—
TEST gear design and development engineers, with sound theoretical knowledge and experience in the development of test gear for radio, television and other electronic equipment.
FIRST-CLASS estimator/ratefixer with production planning experience of communications and radar equipment—early promotion to production engineer is envisaged for successful applicant.

SENIOR draughtsman for communications section of the drawing offices with experience of communications equipment.
DRAUGHTSMAN for test gear department with experience of radio or light electrical engineering.
RADIO mechanics with experience of installation and maintenance of test gear—Service or civilian.
ALL positions carry the right to participate in the pension fund and life assurance scheme after the usual trial period; state full particulars to personnel manager. [7300]

TELEVISION service engineer wanted, new London, 5-day week, good position offered to capable experienced man.—Box 3229. [7257]

ILFORD LIMITED engineering research and development department have vacancies for draughtsmen in the following categories:—

(1) **ELECTRICAL.**—Drawing office and workshop experience of power and lighting layouts is essential.
(2) **SERVICES.**—Experience in practical schemes for boiler plant, refrigeration and air conditioning is necessary.

(3) **MECHANICAL DESIGN.**—A wide experience with mechanisms of all types is required.
PERMANENT and well-paid positions in good working conditions will be offered to competent men.—Write fully to: Ilford Limited, P.O. Box No. 10, Romford, Essex. [6984]

TELECOMMUNICATIONS ENGINEERS, experienced design and development engineer required.—Write to: Telephone Rentals, Ltd., Kent House, Knightsbridge, S.W.7. [7278]

RADIO and television engineer with qualifications and experience also driving ability required by Messrs. Vallance & Davison Ltd., 11, Briggate, Leeds, 1. [7261]

RADIO mechanics are required for service in the Air Ministry ocean weather ships; voyages are of 27 days at sea followed by 15 days in port at Great Britain.

APPLICANTS must possess a sound knowledge of the principles of radio and radar up to the standard of third year City Guilds telecommunications engineering; they should have a general knowledge and practical experience in the maintenance of ground radio transmitting receivers, D.F. systems, and radar installations; duties will include operation of radar equipment; suitably qualified and experienced ex-service radio mechanics will be given preference.
SUCCESSFUL candidates will be engaged on a non-pensionable basis; the weekly scales of pay on appointment at age 25 and over are 135s. rising by annual increments of 5s to a maximum of 165s; entrants aged 21 years and over but under 25 will receive slightly lower rates according to their age; an allowance at the rate of £50 a year is payable to compensate for any excess hours of duty required; food and accommodation is provided free on board ship; not less than six days leave may be granted between voyages.
APPLICATIONS, stating age, qualifications and experience, should be addressed to Air Ministry, S.5 (g), Cornwall House, Stamford St., S.E.1. [7215]

RADIO and television service manager urgently required, good references essential.—Write, W. L. & F. M. Jones, Ltd., High St., Cobham, Surrey. [7285]

TELEVISION aerial erectors, fully experienced. All makes: London area: clean driving licence: first-class men only: salary, bonus and overtime.—Box 3226. [7235]

RADIO engineer wanted, conversant with all types of radios; wages 3/6 to 4/- per hour, according to experience. Write to Cadman's, 115 City Arcade, Hanley, S.O.T. [7307]

SKYWAYS, Ltd., Stansted Airport, Essex, have vacancies for aircraft radio mechanics: basic week of 44 hours; holidays with pay; good prospects.—Apply: Personnel Manager. [7275]

BOYD, Ltd., require radio & T.V. engineers for their central service depot, 18, Crown Place, N.W.5, top wages, own car an advantage.—Apply Service Supervisor, 256, Edgware Rd., W.2. [7262]



SAVAGE TRANSFORMERS LTD
Nursted Road · Devizes · Wilt
Tel: Devizes 536

Good Investments

Dynamos, 12 volt 10/15 amp. D.C. 1,400 r.p.m., easily adapted for windmill work, 50/- carr. 5/- Small hand dynamos, 6 volts 5 amp. 100 r.p.m. through gearing in handle, 25/-
Motor Alternator, 230 volts 50 cy. S.P. input 230 volts 60 watts 1,250 cycles output with control box fitted starter, 4-med. condensers, 2 24 volt Rectifier Voltmeter, and wire wound Pot., £35, carr. extra. Rotary Converter 22/29 volts D.C. input 80 volts 240 watts S.P. 1,600 cycles output 8,000 r.p.m.
D.C./A.C. Rotary Converters, 50 cycle output. 110 volts D.C. input 230 volts 200 watts output, £10. 24 volts D.C. input 230 volts 100 watts output, £3/10/- Send for Rotary Converter List. Rectifiers. Selenium ½-wave 500 volts 40 m.a., new, 7/6.

Photographic Glazing Machines by Velox, 230 volt A.C. motor, speed control, Heaters, Switches, Glazing Drum, etc., all in first class condition. Cheap. Neutral Binocular Filters, new and wrapped, 5/-
Sterilisers. G.E.C. 1 and 2 K.W. sizes 230 volts A.C. with tray for medical instruments, good condition.

Show Card Machine. No. 9, cold press Masson Seeley with 11 sets type, 5 sets figures, guillotine, beveller and other accessories, cheap.
Motor Pumps. Stuart Turner No. 10 230 volts A.C. or 12 volts D.C. lift 3ft. head 10ft. capacity 100 g.p.h., £6/10/- Foot valve and strainer, 25/-, delivery ex stock.

Motor Blowers. 24 volts D.C. for valve cooling or conversion to hair dryer, 21/-
Thermostats, small, fit test tube, operate 0 degrees cent., easily altered and suitable for fish tank, new in makers box, 6/6, post 6d.
Heater Elements 24 volts 75 watts flat copper plate with insulated connector fitted one end, 4in. x 2in. x ½in., new, useful for soil heating, etc., 1/6 ea. Special prices for quantity.

ELECTRADIX RADIOS
214 Queenstown Road, London, S.W.8
Telephone: MACaulay 2159

NOW AVAILABLE!!

**A Special Candler Course
for all desiring to pass the
G.P.O. MORSE CODE TEST
for securing an Amateur
Transmitting Licence**

The Course includes all essential training to enable the average student to be successful. The fee is reasonable too.

Please send for the

CANDLER

"BOOK OF FACTS"

stating which of the following courses you are interested in:—

- (1) Special Course for G.P.O. Morse Code test for Amateur Transmitting Licence.
- (2) Candler Senior Course for Beginners.
- (3) Candler Advanced Course for Operators, who desire to increase their speed and accuracy.

THE CANDLER SYSTEM CO.,
(55W) 52b, ABINGDON RD., LONDON, W.8.
Candler System Company, Denver, Colorado, U.S.A.

DUKE & CO.

BESIDE RADIO KIT. In walnut bakelite cabinet, 4 valve T.M.E. Universal or A.C. For only 25/12/6. Ivory or pale green 6/- extra. Assembled 35/- extra. New and improved circuits. The ONLY set now available at this price. (Cabinet approx. 12in. x 5 1/2in x 7in.). Post and packing 2/6.

TYPE 25/196 SUPERHET RECEIVER. New purchase makes it possible to again offer a limited number of these bargains. Note price 12/6 only, with free drawings. These convert easily to A.C., Universal or Battery. All-wave receivers, 465's I.F.'s, 4 tuning condensers, 28 fixed coils, 32 resist., trans., switches and v/controls. Valve holders, and all the usual parts less valves. Post 1/6.

NEW 1124 RECEIVER CHASSIS. A few hundred only, containing—30 fixed condensers, 36 resistors, 24 trimmers (ceramic). 3 I.F.'s, 3 tuning coils, Xaley 8 way switches, v/control, v/caps, 2 trans., (QF and IV). If made to work set tunes, Television, Police, F.M., etc. Contents not guaranteed. 9/6, plus 1/6 post.

T.V. LENSES, made by reputable firm, 8in., 9in. or 10in., 55/-; or 12in., 75/-. Post and pack 1/8.

AERIALS, ex W.D., on winch, 30ft., 2/9, plus 10d. post.

AERIALS, 12ft., tubular copper plated steel, 3-4ft. tapered sections, 8/6, plus 2/- carr.

AERIAL BASE. Rubber with fitting to take 12ft. aerial. 1/6, plus 10d. post.

CRYSTAL SETS, in bakelite cabinet, very attractive, 9/6, or luxury type in oblong cabinet, 16/6. Post 10d.

CRYSTAL DETECTORS. Semi-permanent, 2/6.

HEADPHONES. Single headset 1/9, twin headset 3/9, used but all tested.

COMFORTABLE SEATS. Covered in hide or moquette, 34x16x4in. thick, backs 19in. high. Complete seats 45/- and 50/- . Seats only in hide 22/6. Carr. extra.

DINGHIES. Boat shape, 13ft., ex Military. NEW in 2 shoulder packs with all accessories, 6 gns., plus carr.

Money back guarantee. Cash With Order please, or C.O.D. Stamps ONLY for lists.

621, ROMFORD ROAD, MANOR PARK, E.12
Grangewood 6677

Retail trade: 219, ILFORD LANE, ILFORD
ESSEX I.L.F. 0295

SITUATIONS VACANT

FERRANTI, Ltd., Moston Works, Manchester, have staff vacancies in connection with long-term development work on an important radio tele-control project.

(I) SENIOR engineers or scientists to take charge of research and development sections. Qualifications include a good degree in physics or electrical engineering and extensive past experience in charge of development work. Salary according to qualifications and experience in the range of £1,000-£1,500 per annum. Please quote reference R.S.E.

(II) ENGINEERS and scientists for research and development work in the following fields: Radar, radio and electronic circuits, micro waves, high power centimetric valves, vacuum and/or high voltage techniques, servo control and electro-mechanical devices. Qualifications include a good degree in physics or electrical engineering or mechanical science, or equivalent qualifications. Previous experience is an advantage but is not essential. Salary according to qualifications and experience in the range £420-£1,000 per annum. Please quote reference R.T.E.

(III) TECHNICAL assistants for experimental work in the fields listed in (II) above. Qualifications required: A degree or Higher National Certificate in electrical or mechanical engineering or equivalent qualifications. Salary in the range of £250-£550, according to age and experience. Please quote reference R.T.A. THE company has a staff pension scheme, and will give housing assistance in special cases.—Application forms from Mr. R. J. Hebbert, Staff Manager, Ferranti, Ltd., Hollinwood, Lancs. [7097]

LANCASHIRE AIRCRAFT CORPORATION require radio mechanics.—Apply with details of experience to Technical Manager, Bovington Airport, nr. Hemel Hempstead, Herts. [6998]

Pye, Ltd., Cambridge, have vacancies for radio men and draughtsmen for development of domestic radio.—Apply Personnel Manager, Pye, Ltd., St. Andrew's Rd., Cambridge. [7222]

CAPABLE man of high intelligence and integrity as personal assistant to owner-manager of soundly established London retail radio and electrical business, state age and full details of career.—Box 3230. [7258]

FERRANTI, Ltd., Moston Works, Manchester, have staff vacancies in connection with special electronic valve development and manufacture in association with an important radio tele-control project.

(I) SENIOR valve engineers to take charge of research and development work. QUALIFICATIONS include a good degree in physics or electrical engineering and extensive experience in charge of development work. SALARY according to qualifications and experience in the range of £1,100-£1,600 per annum; please quote Ref. S.V.E.

THE company has a staff pension scheme, and will give housing assistance in special cases.—Application forms from Mr. R. J. Hebbert, Staff Manager, Ferranti, Ltd., Hollinwood, Lancs. [7227]

TEST engineers required for electronic instrument testing; Higher National Certificate in electrical engineering preferred.—Solartron Laboratory Instruments, Ltd., 22, High Street, Kingston-on-Thames. [7277]

INTERNATIONAL AERADIO, Ltd., requires radar engineer/instructors, Karachi, up to £1,200 p.a., quarters free, pension scheme.—Write quoting RAD, Senior Admin. Officer, 40, Park St., London, W.1. [7269]

TECHNICAL writers for radio and television equipment urgently required. Must be over 26 years of age, salary in accordance with capabilities and experience. Write to Personnel Department, Pye, Ltd., St. Andrew's Rd., Cambridge. [7129]

ELECTRONIC engineer with practical experience in sound recording equipment required for testing and servicing magnetic recording equipment.—Apply in writing, giving age, previous experience and salary required to Box 3297. [7282]

RADIO mechanic required for radio service work at S. Smith & Sons (England), Ltd., Great West Road Factory, Brentford, experience essential, high starting wage.—Apply in person to Personnel Manager, or phone Baling 8071, Ext. 25. [7191]

TELEVISION engineer with original ideas wanted for novel application in important defence project in special laboratory within 40 miles of London starting salary £700-£1,000 p.a., according to qualifications.—Write quoting ref. 1AH to Box 3232. [7268]

A SENIOR draughtsman required with experience precision mechanical or electro mechanical apparatus; also senior draughtsman with experience of radio and electronic instruments; salary up to £11 per week.—Reply, giving fullest details, to Box 3211. [7221]

SENIOR designer draughtsman required with experience of design and development of radar and electronic apparatus to service requirements, S.E. London area; applicants are asked to state age and salary required and details of experience, to Box 3213. [7228]

JUNIOR draughtsman required for interesting work on electro-mechanical apparatus in connection with radar and electronic, S.E. London area; applicants are asked to state age and salary required, and details of experience and qualifications, to: Box 3214. [7223]

SUPACOILS

**SPECIAL OFFER
MAKE YOUR OWN
COIL PACK
for 18/- only**

For this modest sum we will provide you with all the components you require to make a high-efficiency two waveband superhet coil pack (Long and Medium plus gram position). The parts supplied for this pack include specially wound variable iron dust-cored coils, three position rotary switch, padders, trimmers, mounting plate, wire, sleeving, solder, etc., together with detailed wiring and assembly instructions. Also included is a circuit diagram showing a typical superhet in which the coil pack can be used.

Trade and overseas enquiries invited.

We still, of course, supply our normal range of constructors' parts, including:

- **COILS.** A complete series of High Q variable iron dust-cored coils (as recommended for the P.W. 9-valver) in wave-lengths 10-30, 16-50, 30-75, 75-200, 190-550 and 800-2,000 metres; Aerial, H.F. or Oscillator at the remarkable price of 3/- each.
- **I.F. TRANSFORMERS.** Our famous iron dust-cored, permeability tuned, high stability I.F. Transformers, already aligned to 465 kc/s are still available at the extremely reasonable price of 16/6 pair.
- **DIALS.** Attractive metal dial—three wavebands in three colours... 5/- J.B. Dials and assemblies—full range stocked including the well-known SL8 at 27/6
- **CONDENSERS**—Two-gangs 14/- Three-gangs 18/3 Silver micas (all sizes) 9 Tubulars 1/- Electrolytics from 2/9
- **COIL PACKS** and Tuning Units in stock—we specially recommend the famous 30 and 40 series and 6-band Communications.
- **HOME CONSTRUCTOR'S HANDBOOK.** This valuable booklet contains tested circuits of Feeder Units, Superhets, Amplifiers, etc. Constructional and Servicing information, Resistance Colour Code, and many illustrations of sets you can build with ease. It also carries our latest priced stocklist and is available for 2/- only, or a copy will be given free with any order for £1 or more.

SUPACOILS MAIL ORDER OFFICE
98, Greenway Ave., London, E.17

CRYSTALS

TYPE "M"
Range 8 to 17 mc/s
Hermetically sealed metal can 0.75" high under pins, 0.75" wide, 0.375" thick, with 3/8" diameter pins at 0.490" centres.



BROOKES CRYSTALS LTD.
10, Stockwell St., Greenwich, London, S.E.10
Phone: GREENWICH 1028. Cables: Xtals, London. Grams: Xtals Green, London.

WANTED

End equipment, tubes and component parts.

Will pay highest prices.

END EQUIPMENT

APN-9	HS-23
ARC-1	T-17D
APN-4	American made ARC-3
SCR-522	R-5A/ARN-7
BC-640	BC-453
ART-13	SCR-720
BC-639	APR-4
BC-221	AT-4/ARN-I Antenna
RTA-1B	TN-16, 17, 18, 19 and 54
HS-33	

TEST EQUIPMENT

TS-13	TS-174
TS-34	TS-182
TS-35	TS-203
TS-45	TS-235
TS-70	TS-251
TS-89	TS-270
TS-118	TS-263
TS-120	TS-268
TS-142	IE-19

ARROW SALES, INC.

1712 S. MICHIGAN AVENUE,
CHICAGO 16, ILL., U.S.A.

Phone: WEbster 9-7454

LYONS RADIO Ltd.

RADIO EXHIBITION. During the period of the Exhibition we are holding a **SPECIAL SALE**. We are only a little over a mile from Earls Court so if in town why not call in and inspect a fine selection of R.x., T.x., Test Gear, Components, etc., all at clearance prices. **EXAMPLES:** Eddystone Communications receivers at 25, Bendix Transmitters from 30/-; Meters from 3/- and dozens of other bargains. The Sale is for callers only. Shop hours 9 a.m. to 6 p.m. Thursdays 1 p.m.

TRANSMITTERS TYPE T.1403A. This Tx. provides an output of 40 w. on W/T, or 10 w. on R/T, over the frequency range of 2 to 7 Mc/crystal or MO. operation. Circuit comprises a Pierce Co. (VR55), tuned buffer (EL33), PA. (607), Mod. (EL33), contained in a handsome metal case with hinged lid at top with all controls, clearly marked, on the front, twin metered, pen. Meters indicate amplifier and aerial current. Overall dimensions approx. 19x15x14in. Power requirements are H.T. approx. 600 v. D.C. at 200 mA. and L.T. 6.3 v. at 3 A. Supplied in new unused condition with circuit diagram and operating instructions. **PRICE £12, carriage £1 (10/- returnable on crate).**

RECEIVERS TYPE R3515. Adaptable for reception of Television sound or vision details of which are given in the May issue of Short Wave Listener. Fitted with 10 VR55s, 1 VR92, 5 VR56s, 3 VR55s, 1 VR64, 1 VR53, 13 M/c. I.F. strip and a wealth of useful components. In good condition. **PRICE complete with valves £31/7/6, or less valves 30/-, carriage 7/6.**

AERIAL MASTS. Consist of 4 sections of stout all-weather resisting paxolin tubing each section approx. 7ft. long. Max. dia. 3 1/4in. Min. dia. 1 1/4in. x 3/4in. wall. Each section fits together with metal ferrules forming a mast 28ft. high. Very light weight and can easily be raised by one man. Guy ropes, etc., are not supplied. **PRICE £2/-, carriage 4/-, or top two sections only to form a mast 14ft. high. PRICE 18/6, carriage 2/6.**

L.T. MAINS TRANSFORMERS. PRIMARY 200 to 250 v. 50 c.p.s. SECONDARIES: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 v. at 2 amp. total loading. Brand new and fully guaranteed. PRICE 18/6, post 1/6.

**3 GOLDHAWK ROAD, (Dept. M.W.)
SHEPHERDS BUSH, LONDON, W.12**

Telephone: Shepherds Bush 1729

SITUATIONS VACANT

ADMIRALTY.—Vacancies exist for Electrical and/or Mechanical Engineering Draughtsmen in Admiralty Research and Development Establishments located in the vicinity of Weymouth, Portsmouth, Teddington (Middlesex) and Baldock, Herts.

DRAUGHTSMEN experienced in light current, electro-mechanical, precision mechanical and electronic equipment are particularly needed. **CANDIDATES** must be British subjects of 21 years of age and upwards, who have had practical workshop experience (preferably an apprenticeship), together with drawing office experience.

APPOINTMENTS will be in an unestablished capacity, but opportunities may occur for qualified staff to compete for established posts. **THE** salaries offered, depending on age, experience, ability and place of duty, will be within the range £520—£560 p.a. **HOSTEL** accommodation is available at some Establishments.

APPLICATIONS, stating age and details of technical qualifications, apprenticeship (or equivalents), workshop and drawing office experience, should be sent to Admiralty (C.E.T. Room 88), Empire Hotel, Brompton, quoting DM/R.D. Original testimonials should not be forwarded with application. Candidates required for interview (at London or Bath, which ever is nearer) will be advised within two weeks of receipt of application. [7109]

REQUIRED. West London area, several skilled and semi-skilled wiremen for assembly and wiring audio and electronic equipment. Good conditions and variety of high-grade work on small batch production.—State age, experience and salary required, Box 2606. [7124]

EXPERIENCED electronic wiremen required immediately for top priority Government contracts, excellent wages, working conditions and prospects for the right type of applicant.—Apply, Peto Scott Electrical Instruments, Addlestone Rd., Weybridge, Surrey. [7265]

CIRCUIT draughtsman or tracer required, able to work from sketches and produce equipment in electronic section: A.E.S.D. rates; 5-day week, canteen, pension scheme.—Apply, stating experience, etc., to Redifon Ltd., Broomhill Rd., Wandsworth, S.W.18. [7249]

JUNIOR draughtsman required for interesting detail work on electro-mechanical apparatus in connection with radar and electronics. S.E. London area; applicants to state age and salary required and details of experience and qualifications to Box 2618. [7153]

SENIOR designer draughtsman required with experience of design and development of radar and electronic apparatus to service requirements S.E. London area; applicants to state age and salary required and details of experience and qualifications to Box 2612. [7262]

A NUMBER of senior and junior vacancies for radio, radar electronic, television, etc., development, service engineers, draughtsmen, wiremen, testers, inspectors, etc.; urgently required 30 television service engineers.—Write in confidence, Technical Employment Agency, Clapham Rd., S.W.9. (Bristol 3487) [10103]

DRAUGHTSMAN required for the design and development of domestic radio and television equipment; payment in accordance with A.E.S.D. rates.—Write, giving full particulars of experience and qualifications, to Regentone Products Ltd., Eastern Ave., Romford, Essex. [7245]

RADIO engineer required by North London manufacturer's service department; sound education and adequate technical training essential.—Applicants should give fullest information of general and technical education, experience, age and salary required to Box [7119]

TECHNICAL development engineers required, senior, intermediate and junior, for interesting work in electronics, including defence contracts; excellent salaries for suitable applicants.—Apply to Technical Director, All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7240]

SENIOR and junior electronic development engineers required, H.N.C. and degree standard, experience in U.H.F. and centrimetric work an advantage.—Apply by letter, stating experience, nationality and salary required, to E.M.I. Engineering Development Ltd., Penleigh Works, Wells. [7027]

A WELL-KNOWN company undertaking interesting radar development work in the London area has vacancies for the following: 1. **SENIOR** electronic engineer who must be fully experienced in the design of radar equipment; degree desirable; salary about £800 p.a. (Ref. IBA.)

2. **MECHANICAL** engineer conversant with Naval radar installation and control systems; degree desirable; salary according to qualifications and experience. (Ref. IBA.)

3. **DESIGNER** draughtsman, H.N.C. desirable, should be capable of working on own initiative and doing all necessary calculations, and draughtsmen with general electronic and/or mechanical experience; salary according to qualification and experience. (Ref. AEP.)

APPLICANTS should write, quoting appropriate reference, to Box 3305. [7306]

SENIOR and Junior Electronic Development Engineers required for work of high priority; degree or Inter-B.Sc. desirable; salary £400-£750 p.a. according to qualification and experience.—Write, stating full details, to Personnel Manager, The McMurdo Instrument Co. Ltd., Ashstead, Surrey. [6924]

QUARTZ CRYSTAL UNITS



For— **AIRCRAFT, MARINE AND COMMERCIAL USE** are available in the complete range from 35 kilocycles to 15 megacycles.

Alternative mountings in standard two-pin A.M. pattern 10X, International octal, and miniature type FT243, can be supplied for most frequencies.

Prices are fully competitive, and we specialise in prompt deliveries for urgent requirements.

WE WELCOME YOUR ENQUIRIES.

THE QUARTZ CRYSTAL Co., Ltd.

63-71 Kingston Road,
NEW MALDEN, SURREY

Telephone: MALden 0334

TAMSA

TAPE & WIRE RECORDING COMPONENTS

Write for the latest price list of the following:—

RECORD, PLAYBACK & ERASE HEADS. THE NEW TAMSA HEAD RANGE ARE NOW AVAILABLE. RECORD PLAYBACK AMPLIFIERS OSCILLATOR COILS & UNITS.

TAPE E.M.I.
G.E.C.
DUREX

WIRE On standard
1/2, 1, and 1 1/2
Spools.

5", 7", 11" Spools.

Constructor's Envelopes. Books on Tape Rec'd'g.

Manufactured by

AUDIGRAPH LTD.

Dept. MR.3, 74, Great Hampton Street,
HOCKLEY, BIRMINGHAM 18

HOLME MOSS CONVERSION

Type AC/4 Converter unit for use with Sutton Goldfield receivers. Optimum picture detail and sound reception without retuning or alterations. Incorporates power supply unit, R.F. stage and the highly successful double mixer stage ensuring freedom from noise and correct reception of the new single side band transmitters.

Delivery at present ex-stock. Price complete with 5 valves etc., 15 gns. On approval 7 days C.O.D. if desired or by arrangement through your own Dealer. Holme Moss models of the type AC/3 neutralized triode Pre-Amplifier are also available ex-stock. A well designed and proved unit giving the best possible results for Fringe viewers. Our confidence in the unit is revealed by our 7 days approval offer. C.O.D. if desired or by arrangement through your Dealer. Illustrated leaflets and details etc. available on request.

SPENCER WEST
Quay Works, Gt. Yarmouth

SOUTHERN RADIO'S WIRELESS BARGAINS

WALKIE - TALKIE (TRANSMITTER-RECEIVER). Type 38 Mark II. Complete with 5 valves, Throat Microphone, Headphones and Aerial. 7 mcs Amateur Band suitable for field use. Powerful Superhet Receiver. Modulated Transmitter. Guaranteed ready for the Air, less batteries, £3/10/-.

R.315 TELEVISION UNITS. Complete with 21 valves. 6 Stage 14 mcs I.F. Strip. Ideal for T.V. Conversion. Brand new in original wooden cases, £3/10/-.

RECEIVERS B.C. 454 (49-100 Metres) B.C. 455 (39-49 Metres). BRAND NEW COMPLETE WITH 6 VALVES. BLACK CRACKLE FINISH, £3/10/-. 1.5-3 Megs., £4/-.

LUFBRA HOLE CUTTERS. Adjustable from 1/16 to 3/16 in. for use on Wood, Metal, Plastic, etc., 5/9. **LUFBRA FLY CUTTERS**, 14/6.

LIONEL "BUG" KEYS. Genuine U.S.A. Automatic Morse Key, Type J36. Few only, £3/7/6.

THROAT MICROPHONES. Magnetic type complete with long lead and plug, 4/6.

CONTROL CABLES for COMMAND RECEIVERS. B.C. 453/4/5, 14ft. with adaptors, 9/6. **CONDENSERS**. 100 assorted tubular and mica all new useful sizes to 2 Mfd. 15/- 100.

RESISTANCES. 100 assorted new to 3 watts, 12/6 100.

HAND GENERATORS. 6 volts at 5 amps. With Crank, 21/-.

SPEAKERS. Celestion 2 1/2 inch. P.M. Moving Coil 3 to 5 ohms, 17/6.

PLASTIC TRANSPARENT MAP CASES. 14 inches by 10 1/2 inches. Ideal for Maps, Charts, Display, Photographs, etc., 5/6.

STAR IDENTIFIERS. With Hydrographic Office Modifications A-N Type I. Complete in case, 5/6.

MOVING COIL D/C METERS. Brand new, 2in. 0.2 mA., 0.5 mA., 0.30 mA., 0.20 volts, 9/6 each.

WESTECTORS. Type WX6 and W112, 1/- ea., 11/- doz. Full List of Radio Publications, 2/6.

SOUTHERN RADIO SUPPLY, LTD.
11, Little Newport St., London, W.C.2.

(Gerard 6653)

amc
TELEVISION
Manufactured to
"ELECTRONIC ENGINEERING"
TELEVISION SPECIFICATION
LINE OUTPUT TRANSFORMERS

FOCUS COILS

P.M. Focus Ring R.17. (all Mullard Tubes).
P.M. Focus Ring R.20 & R.25. (all other tubes).

LINE AND FRAME SCANNING COIL ASSEMBLIES

All Steel Cadmium Plated Power and Time Base Chassis valve-holders, 3-point and single socket and all necessary cut-outs. Sound Panel Chassis Assembly, fitted with Screens, valve-holders, formers and dust cores. Vision Panel Chassis Assembly, fitted with screens, valve-holders, formers and dust cores 9in. and 12in. C.R. Tube Support for mounting on top of Gantry assembly. Smoothing Choke (Ch. 9) 5 H., 250 mA. 5-valve Superhet Radio Chassis. Drilled and fitted with 5 Amphelox Octal valve holders, aerial, earth and gramophone sockets, necessary cut-outs for all control mountings, mains transformer and tuning gang condenser. Complete with 2 steel fixing feet. Cadmium plated.

Full Vision Drive Assembly. Fitted with unbreakable Perspex 3-coloured scale for long, medium and short wave-bands. Calibrated in metres, kilocycles and station names. I.F. Transformers High Q 465 k/c/s.

ALBERT MANUFACTURING CO.
5 SHAKESPEARE ROAD, FINCHLEY, N.3
Telephone: Finchley 2188

SITUATIONS VACANT
EXPERIENCED television aerial riggers required for all London areas, Maidstone and Chatham; current driving licence and working knowledge of radio essential; good wages and prospects.—Write, stating age and wages required. Antiferne Installations, Ltd., Watford Way, N.W.7. [7234]

WORKSHOP and office juniors are required by radio company in North London district; opportunity for boys with interest in radio to progress in service or technical correspondence sections after a period of general duties.—Apply, giving full details of education and age, to Box 2603. [7120]

WEBB'S RADIO require senior engineer for specialised service department, must be conversant with the overhaul and alignment of communication receivers, including the provision of test and factory precision.—Write to the Manager, Webb's Radio, 14, Soho St., London, W.1. [7283]

TELEVISION and radio engineer, fully experienced, qualified and passed exams, permanent position, progressive, very good salary; also assistant 2nd engineer required, some experience preferred and willing to learn; West Middlesex area, in both cases state age, experience, qualifications, and salary required.—Box 3212. [7224]

VACANCIES exist in a rapidly expanding department of a large engineering organisation in the London area, for graduates in physics and electrical engineering or equivalent, the work involves the development of quartz crystals together with the associated circuits.—Apply stating age, experience and salary expected to Box 3298. [7287]

A VACANCY exists for a senior wireless engineer to control a team engaged on research, development, and engineering of new low-power equipments in the 400-600 megacycle band; salaries up to £1,200 per annum offered to suitable candidates.—Please write giving full details and quoting ref. HHE to Box 2729. [7182]

PRODUCTION testers and assembly inspectors for radio, radar and nucleonic equipment required for Government contract, work of utmost importance; rates of pay will be in accordance with ability and experience.—Applicants should send full details in writing to Personnel Manager, E. K. Cole, Ltd., Malmesbury, Wilts. [6954]

TELEVISION field service engineers required by E. London firm with all leading agencies; applicants should have extensive experience, ability and initiative, and will work with 1st-class team of engineers; salary £8-£9 p.w. or according to aptitude and experience.—Apply to "L.B. Leytonia Radio, 828, High Rd., Leyton, E.10 [6978]

TESTING personnel required by large firm. S.E. London, for work on radio and radar equipment; should be capable of fault-finding and dealing with both transmitter and display equipment; applicants should have had 2-3 years' previous experience on this type of work.—Apply, stating age, previous experience, and salary expected, to Box 3225. [7232]

MCMICHAEL RADIO, Ltd., require qualified draughtsman with experience in the mechanical design of radio and electronic instruments for the Government services; salary will be commensurate with ability.—Write, stating age, training, experience and salary required, to the Chief Engineer, Equipment Division, McMichael Radio, Ltd., Slough, Bucks. [7103]

E. K. COLE, Ltd., have vacancies in their Electronic Department at Malmesbury, Wilts. for Senior and Intermediate Draughtsmen in the Development Drawing Office, for work on radar, communications and electronic projects; previous experience in this field desirable, but not essential.—Apply in writing to the Personnel Manager, Ekco Works, Malmesbury, Wilts. [7001]

ELECTRONIC engineer.—Applications are invited for the post of development engineer (West London area), experience on radar, television or similar pulse techniques would be an advantage, and special consideration will be given to applicants with B.Sc. degree or H.N.C.; salary would be determined by qualifications and experience.—Apply to Chief Engineer, Box 2683. [7176]

DEVELOPMENT engineer required by electrical component manufacturers situated in N.W. London; applicants must be experienced in mechanical and electrical engineering, and it is desirable to have experience in model shop or design-development work; minimum qualification Inter-B.S. or equivalent.—Write, giving full details and stating salary required, to Box 3306. [7308]

TECHNICAL laboratory assistants, with some experience preferably in the electronic experimental field, are required by the Research Laboratories of the General Electric Co., Ltd., East Lane, Nth. Wembley, Middx.; good education essential; beyond Matriculation standard desirable.—Apply in writing to the Personnel Officer (Ref. GBIC/G/727), quoting age and record. [7036]

ELECTRONIC engineers required by large firm S.E. London for the development of radio and radar equipment; applicants should have had 2-5 years' previous experience in similar work and qualifications either to degree or H.N.C. standard; this work is of high National importance.—Apply, giving full details of previous experience, qualifications and salary expected, to Box 3224. [7231]

"DEFINITELY IN STOCK NOW"

COLLARO AC/514 3-speed Gram. Units, with Pick-up taking 2 Acos GP27 plug-in heads for Std. and L.P. Fitted autostop. Price complete £14/8/9 and carr. 2/6. Above mounted in de Luxe rexine covered portable case, 17 gns., plus carr. 2/6.

GARRARD VDIS SPECIAL QUALITY A.C. GRAM. UNITS (78 r.p.m.) comprising robust centre drive induction motor with variable speed and full 12in. turntable, counter poised pick-up arm and autostop. Whole unit floats on anti-microphony springs. Above quality unit offered at special price of £7/5/-. Pick-up heads to suit: Standard Magnetic 35/-; Miniature Lightweight (takes silent stylus or sapphire), with adaptor, 65/-.

DECCA THREE-SPEED GRAM. MOTOR and substantial turntable, fitted precision switch, giving 33 1/3, 45 and 78 r.p.m. Our special offer, £7/3/9, plus 2/6 post.

DECCA LIGHTWEIGHT PICK-UP to match, complete with Acos GP19 (78) and GP19LP (33 1/3) plug-in cartridges with permanent sapphires, £4/4/6, or with either one head only, £2/13/0, post 1/6. Spare heads 32/6.

ABOVE MOTOR AND PICK-UP with 2 heads fitted in de Luxe leatherette-covered portable case, 15 gns.

GP20 PICK-UP with standard or micro-groove head, £3/11/5, post 1/6. Either head separately, 43/4, post 8d.

SYMPHONY NO. 1 (AMPLIFIER) by N.R.S. Independent control of Bass, Middle and Top, separate Scratch Cut, negative feedback. For A.C. 200-250 v., input for magnetic crystal and hi-fi pick-ups, also Tuner. 5-watt output. Price: 3 ohm model, 9 1/2 gns.; 15 ohm model, £10/7/6, carriage 5/-.

SYMPHONY NO. 2, MARK II. New model with 10 watts push-pull triode output, distortion at 1,000 c.p.s. less than .5%, hum level negligible—90 db down. Woden mains transformer, choke and output transformer for 3, 7.5 and 15 ohms input for ordinary and hi-fidelity pick-ups. Tone control system same as No. 1. A truly magnificent instrument for only 15 gns., carriage 5/-.

NO. 2 PUBLIC ADDRESS AMPLIFIER. Same chassis and power parts as No. 2 Symphony but simple one knob tone control. 15 watts push-pull output, 2 inputs with separate volume controls for fading mike and gram. Complete kit 10 gns. Ready built, £11/19/6.

RECORD PLAYER CASES, well made, measure 16 1/2 x 13 1/2 x 7in., beautifully covered in brown leatherette, fitted hinged lid, clasp and sprung carrying handle. Price, complete with uncut motorboard, 57/6.

BASS-REFLEX CABINET KITS give superb bass response and top (3in. patent speaker). Full instructions supplied. 8in. timber model 2ft. 6in. high x 1ft. 3in. x 1ft. deep. Price 85/-; 10in. speaker model, 97/6; 12in. speaker model, 107/6. Any of above ready built for 7/6 extra. Carr. 7/6.

Send 5d. for latest bargain catalogue and supplement, indispensable to all Quality Enthusiasts. TERMS c.w.o. or c.o.d. Callers welcome. Demonstrations Monday to Saturday (inclusive), 9 a.m. to 6 p.m.

NORTHERN RADIO SERVICES,
16 Kings College Road, London, N.W.3
Phone: PRImrose 8314.

PARALEX ADJUSTABLE HOLE CUTTER

Selected for the

FESTIVAL of BRITAIN 1951



A PRECISION TOOL
Capacity 1 1/2 to 4"
Vernier adjustment

1/4" High Speed 18% Tungsten Toolbit

P.L. round shank.....16/- each
P.L.S. square tap shank 17/- each (incl. post)

Liberal Trade Discount.
Wholesale and Export Enquiries invited.
LUDFRY LTD.
189, Wardour Street, London, W.1.

G.E.C.

GERMANIUM CRYSTAL DIODES

LATEST, SMALLEST,
SUPREME CRYSTAL DETECTOR
Midget Size, 5/16in. x 3/16in.
Wire Ends for Easy Fixing.
4/6 each, postage 2½d.

Technical Details and Selected Types available.

SILICON DIODES, 3/6. Postage 2½d.
Fixing Brackets, 3d. pair.

COPPER INSTRUMENT WIRE
ENAMELLED, TINNED, LITZ,
COTTON AND SILK COVERED
Most gauges available.
B.A. SCREWS, NUTS, WASHERS,
soldering tags, eyelets and rivets.

**EBONITE AND BAKELITE PANELS,
TUFNOL ROD, PAXOLIN TYPE COIL
FORMERS AND TUBES, ALL DIAMETERS.**

*Latest Radio Publications.
SEND STAMP FOR LIST.
TRADE SUPPLIED.

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4

IMMEDIATE DELIVERY OF TAPE RECORDERS

Scophony Baird	55½ gns.
Simon Simphonic	£60
Magnograph Twin Track	£59
Tape Decks	from £13.13
E.M.I. Tape	£1.5

List by return

w. w. ALFRED ROSE, A.I.R.E.
134-136 LEWISHAM WAY, S.E.14
Tel.: TIDeway 3696

Come to

SMITH'S of EDGWARE ROAD, the friendly shop, for all radio components

We stock everything the constructor needs—our 25 years' experience of handling radio parts and accessories enables us to select the best of the regular lines and the more useful items from the surplus markets in:—

Loudspeakers & Phones	Capacitors & Resistors
Transformers & Chokes	Coils & Formers
Meters & Test Equipment	Plugs & Sockets
Pickups & Turntables	Aerials & Insulators
Switches & Dials	Motors & Generators
Metalwork & Bakelite	Wires & Cables
Books & Tools	Panel Lighis & Fuses
Valve Holders & Cans	Sleeving, Nuts & Bolts,
Metal Rectifiers	Tags, Clips, Grommets &
Cabinets & Cases	all other bits and pieces

NOTHING TOO LARGE—NOTHING TOO SMALL
We have one of the largest stocks of B.V.A. Valves & C.R.T.'s
(No general catalogue available.)

H. L. SMITH & CO. LTD.

287, 9, EDGWARE ROAD, LONDON, W.2
Tel. Paddington 5891. Hours 9 to 6 (Thursday 1 o'clock)
Near Edgware Road Station, Metropolitan and Bakerloo

SITUATIONS VACANT
ELECTRONIC instrument manufacturers require development engineer for pressure pick-ups and electro-mechanical transducers, candidates should have degree in mechanical or electrical engineering and an interest in both fields.—Southern Instruments, Ltd., Fernhill Hawley, Camberley, Surrey. [7260]

TECHNICAL assistant required to take charge of small-scale production of electronic valves for specialised equipment; previous similar experience desirable and education up to Inter-B.Sc. advantageous.—Apply, giving age, details of education and experience, together with salary required, to Personnel Department (GR.T), E.M.I. Factories, Ltd., Hayes, Middx. [7250]

RADIO testers and fault finders required for work of national importance; men with experience of domestic radio, television or V.H.F. communications, can be offered attractive posts according to their ability.—Applicants, who must be prepared to reside in the Midlands area, should write giving full details of experience and present salary, to the Personnel Officer, Ref. (Radio Test) Box 3233. [7270]

A COMPANY manufacturing domestic appliances and television receivers in North West England requires the services of a qualified production engineer familiar with the latest American and British techniques in the manufacture of decorative name plates, control knobs, handles, trim, etc. from metals, plastics and wood.—Please write, giving full details quoting Ref. 1B.J, to Box 3241. [7274]

BRITISH OVERSEAS AIRWAYS CORPORATION have vacancies for radio mechanics experienced in radio maintenance and/or overhaul; rates of pay 10 per hour plus 40 per hour provision of bonus; attractive proficiency pay up to 3d per hour; 5-day, 44-hour week; possible shift work; good pension, sick pay and holiday facilities.—Write or call, Staff Manager, Hut 29, London Airport. [7315]

DYNATRON RADIO, Ltd., require experienced foreman to take charge of their wiring and assembly shop, applicants must be fully conversant with high-class radio and television assembly, and have good knowledge of coil winding; good salary offered with excellent prospects for the right man.—Write giving age, previous experience and salary required to the Personnel Manager, Ray Lea Rd., Maidenhead, Berks. [7262]

E. K. COLE (Electronics Division) offers excellent opportunities for young draughtsmen of Ordinary National standard to gain experience in the development of radar, communications and nucleonic equipments. Also a limited number of vacancies for senior draughtsmen with experience of this type of work.—Apply, giving details of experience, to Personnel Manager, E. K. Cole, Ltd., Maimesbury, Wilts. [7094]

SCOTSMAN with television servicing experience required as instructor for Glasgow area, in addition to taking charge of short practical television courses, this instructor should be able to lecture to City & Guilds Radio III level; commencing salary depends on experience and qualifications, and will be in range of £450—£650 per annum.—Apply to the Principal, E.M.I. Institutes, 10, Pembroke Square, London, W.2. [7302]

SENIOR electronic engineer required by large firm in S.E. London for development work in connection with radio and radar equipment, a good knowledge of pulse and C.R.T. display technique is essential; this work is of particular interest, as it deals both with research and production aspects, and is of high National importance.—Apply, giving full details of previous experience, qualifications and salary expected, to Box 3223. [7230]


BRITISH European Airways have vacancies for instrument mechanics, radio mechanics, electricians, sheet metal workers, airframe and engine fitters; hourly rates 2/10 plus 4d. provisional bonus, plus up to 3d. proficiency; opportunity for good bonus earnings; pension, insurance and sick pay schemes; 2 weeks' paid holiday a year; air travel concessions.—Apply Personnel Officer, B.E.A., Northolt Base, Ruislip, Middlesex. [7272]

ENGLISH ELECTRIC require junior and senior electronic engineers for radio, radar, servo-mechanism and analogue computer design and development, starting salaries up to £1,200 per annum, according to qualifications and experience; location, Bedfordshire; applications, giving full details of qualifications and experience, quoting ref. S.A.7, should be addressed to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., London, S.W.1. [7288]

A HOUSE (married accommodation) is available for senior electronics or radar engineers, required to organise a ground radar system including development of certain control and monitoring and supervisory circuits and displays, special circuit engineers already available; location in special laboratory for important defence project within 30 miles of London; salary up to £1,200 per annum for suitable candidate.—Apply quoting ref. DEF to Box 2678. [7168]

THE GENERAL POST OFFICE has vacancies for radio operators at its coast radio stations and applications are invited from men between 21 and 28 years of age who hold the Postmaster General's First or Second Class Certificate of Proficiency in Radiotelegraphy, selected candidates who hold or obtain the First Class Certificate will be considered later for permanent pensionable posts.—Early application should be made to the Inspector of Wireless Telegraphy, G.P.O. Headquarters, London, E.C.1, who will supply particulars. [7290]

This UNIQUE BENDER

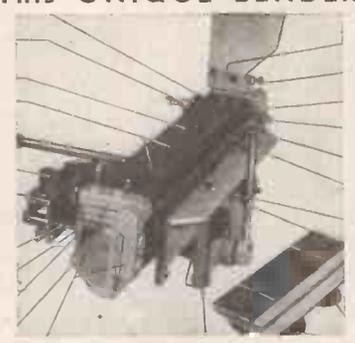

Quickly and Accurately Forms
Angles, Channels, Sections, Boxes, Liris, Trays, Tanks, Chassis Brackets, Clamps, Clips, Shrouds.
Chemical, Electronic and Electro Medical apparatus.
Used by leading Radio Manufacturers. Invaluable to Servicing Engineers, Hospitals, Universities and Research Workers.


For 6 page Folder write to:—
A. A. TOOLS
179a Whitesacre Rd., Ashton-u-Lyne



HIFI LTD., 150, HIGH STREET, LYE,
STOURBRIDGE, WORCS. Telephone: LYE 2/1

ODDIE FASTENERS

PAT 507249

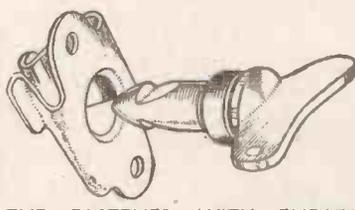

THE FASTENER WITH ENDLESS APPLICATIONS—SIMPLE—POSITIVE SELF-LOCKING. MADE IN A VARIETY OF TYPES AND SIZES.
SPECIAL FASTENERS TO SUIT CUSTOMERS REQUIREMENTS.
WIDELY USED IN THE RADIO INDUSTRY

Illustrated brochures and other information will be gladly sent on request.

Oddie, Bradbury & Cull Ltd., Southampton
Tel.: 55883 Cables: Fasteners, Southampton

★

'Radiospares'

Quality Parts

**The
Service Engineer's
First Choice**

★

The VOIGT Loudspeaker is still ahead of all others. P.M. Unit with 23,000 line gap flux £40 ex works.
Corner Horns (in the white) £19.10.0 or £47.10.0 ex works.

VOIGT PATENTS LTD.
Sydenham, S.E.26 SYD6666
Sole makers of VOIGT Products

**MAGNETIC TAPE RECORDERS
and COMPONENTS**

from

WILL DAY, LIMITED

19 Lisie Street, London, W.C.2.
GERrard 7105 and 4476

SEND 14d. STAMP FOR LIST — SENT BY RETURN

ENGINEERS!

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES". Full detail of the easiest way to pass A.M.I.Mech.E., A.M.I.C.E., CITY & GUILDS (Electrical, etc.), MATRIC., etc., on "NO PASS—NO FEE" terms and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc. If you're earning less than £12 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE!

B.I.E.T.

387 Shakespeare Hse.,
17-19 Stratford Place,
London, W.1.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

THREE in ONE

TRANSFORMER 6' each

Post 1/-

- Use as Push/Pull Modulation Transformer Push/Pull 211's to single 211-100 watts. Makes ideal Output Transformer P/p 6L6 or 807 to match High Impedance Relay Speakers And as,
- 230 volts 50 cycles Input 150-0-150 at 100 m/A. Output Useful for H.T. Eliminators and Low Voltage Power Supply. Can also be used 300 volts Half-Wave at Lower Current. And as,
- 230-115 volt AUTO Step/Up or Step/Down Mains Transformer 75 watts rating. U.S.A. Manufacture—Fully Shrouded. SIMPLE : EFFICIENT : GUARANTEED.

NORMAN H. FIELD
68 HURST STREET, BIRMINGHAM 5
Mail Order Dept.
64-65 CHURCH LANE, WOLVERHAMPTON

SITUATIONS VACANT

CHIEF OF FOREIGN WIRE RELATIONS required by large British telephone company in Brazil to negotiate and prepare the execution of general agreements with other utility companies; review estimates for protection, electrolysis and power interference considerations; investigate electrical accidents to plant; prepare studies and make recommendations regarding protection of toll and local networks from interference from lightning, HV power lines, radio transmission and damage to plant due to electrolysis; assist in preparation of testing programmes for the analysis of interference and electrolysis problems.

APPLICANTS holding B.Sc. (Eng.) degree or equivalent, aged 30 to 40 and preferably single, having about 10 years' experience with manufacturing or operating company, with experience in design, operation and maintenance of telephone plant including carrier systems preferred. Knowledge of power generation and distribution systems an advantage. Practical and theoretical experience in inductive co-ordination, electrical protection and electrolysis problems as applied to telephone plant together with methods of protecting telephone plant from lightning and low frequency induction would be added advantage.

IT is intended that the position will be permanent, but in the first instance the engagement will be for three years, 1st Class fares paid. Salary commensurate with living costs in Brazil. Pension and provident plan in effect. Applications should be received within the next 14 days, and should include detailed particulars of the applicant, his qualifications and experience.—Write Box W.W.215, at 191, Gresham House, E.C.2. [7255]

ELECTRONIC design and development engineers are required by Canadian Aviation Electronics, Ltd., Montreal, Canada. The work covers communication equipment, both ground and airborne, radar, television receivers, commercial receivers, also field installation work, antennas and systems. Senior project engineers must have seven to ten years' experience, be capable of handling projects through development, manufacture and installation, with minimum supervision; salary \$4,500 to \$5,700 per annum. Junior project engineers must have four to seven years' experience and be capable of handling projects under supervision of senior engineers; salary \$3,500 to \$4,800 per annum; 5-day week. Selected applicants will be interviewed in England. Please give full particulars in letter.—Box 5318. [7314]

DIRECTOR of engineering required to take charge of a highly technical research and development company in the Greater London area (a subsidiary of a large engineering Public company); applicants must possess a first-class honours degree and must have specialised in electronics, considerable experience is essential in the direction and management of research establishments, and the ability to guide and supervise teams of project engineers, design offices and model shops; position carries a high salary, the possibility of an exceptional house and excellent long-term prospects with pension facilities; all replies will be treated in full confidence; write giving full details of qualifications, past experience and salary required to the Managing Director.—Box 2142. [7079]

THE GENERAL ELECTRIC Co. Ltd. Radio and Television Works, Coventry, have vacancies for development engineers, senior development engineers, mechanical and electronic, for their development laboratories on commercial and Government work of national importance, fields include microwave and pulse applications; salary range £400—£1,250 per annum; vacancies also exist for specialist engineers in component design, valve applications, electro-mechanical devices and small mechanisms; the company's laboratories provide excellent working conditions with social and welfare facilities, superannuation scheme; assistance with housing in special cases.—Apply by letter, stating age and experience, to The Personnel Manager (Ref. CHC). [7217]

PERSONNEL experienced in the maintenance and repair of electronic control equipment and radar equipment as applied to anti-aircraft guns are required for employment as civilians in the following areas, Guildford, Portsmouth, Southampton, Bristol, Gloucester, Andover, Central Dorset and Bournemouth; the standard required is that of armament artificer R.E.M.E.; salary £30.00 to £40.00 with increments to the age of 26, one increment deducted for each year below 26 years and up to two increments added over 26 years; opportunities exist for promotion to higher grades.—Replies, giving full details of age, experience, technical qualifications, and salary links to £200 to £400, should be sent to A.D.M.E., H.Q., 2 A.A. (Gro), Barrrosa Barracks, Stanhope Lines, Aldershot, Hants. [7225]

APPLICATIONS are invited for radio mechanic vacancies at various Air Ministry establishments in the United Kingdom and Northern Ireland; duties include maintenance and repair of ground and airborne radio/radar equipment; knowledge of basic radio theory essential; rate of pay on appointment in Provinces as Class II mechanic at age 25 or over £6/4 a week, rising by annual increments of 5/- to £7/4 for 44-hour week; slightly lower rates for entrants between 21 and 25 years; Class I mechanic at age 25 £6/15 a week, rising by 5/- to £8/5; annual leave 16 working days, with 1 day for 5-day week in addition to usual public holidays; favourable sick leave conditions and promotion prospects.—Applications should be addressed to the Air Officer Commanding-in-Chief, Headquarters, Maintenance Command, Royal Air Force, Andover, Hampshire. [7246]

YOUR METER DAMAGED?

don't scrap it—
LET GLASER REPAIR IT

Leading Electrical Instrument Repairers to the Industry.

Repairs by skilled craftsmen to all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Test meters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to:—

L. GLASER
Electrical Instrument Repairers
341 CITY ROAD, E.C.1
Tel. Terminus 2489

TELECRAFT

AERIALS ENSURE THE BEST TELEVISION

TRY ONE AND SEE FOR YOURSELF

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE,
3,000 STANDARD STOCK SIZES

No Quantity too Small. List on application.
London: **H. ROLLET & Co. Ltd.** Liverpool: 6, Chesham Place, S.W.1 Kirby Estate, SLOane 3463. SIMONSWOOD 3271/3

STOCK AND EQUIPMENT SALE

Bandpass filters, 15 only, VF rack mtg. 100/120 cs. Bandwidth, Mid freqs.:—2,220, 1,980, 1,740, 1,500, 1,260, 1,020, etc.

Wound Toroids, about 1,000 in 5 sizes, mostly 2 1/2 in. dia., inductances:—2.4, 1.6, 1.5, 1.4, 1.26, .79, .67, .35, .3, .28, .25, .2, .15, .1, .05 Hys., easily stripped to lower values.

Permalloy ring cores, taped and tested ready for winding, about 1,000 in 5 sizes.

500 Transformers, potted, 110v/240v/100v, also mic/grld.

1,000 Silver-mica filter condensers from .003 to .155 mf., most 1% tol. wire ends.

Full lists, tech. information, etc., available. Offers for lot or parts.

Box 2802, c/o Wireless World.

TRANSFORMERS

**FOR ALL PURPOSES
SINGLY OR IN QUANTITIES
FROM OUR STANDARD RANGE
OR TO YOUR SPECIFICATIONS**

**GOOD DELIVERIES
REASONABLE PRICES**

We have also a department for rewinds giving you a 24 hour service and a better job. Please label all burnt-outs with your name and address when despatching.

P. HOWORTH

51 POLLARD LANE · BRADFORD
Tel.: 37030

SITUATIONS VACANT

JUNIOR Engineers to assist in the design construction and test of laboratory models of special electronic circuits, with several years' experience of similar work. A knowledge of radar circuit designs and operations would be an advantage. Salary in the range of £600 per annum. Location, special laboratory in Bedfordshire. Please write giving full details and quoting ref. 815B to Central Personnel Services, English Electric Co., Ltd., 24/30, Gillingham St., Westminster, S.W.1. [7152]

THERE are a number of vacancies suitable for Honours Graduates in Physics, electrical or mechanical engineering or mathematics, or a good general Degree covering two or more of these subjects, for both research and development work in the following fields: radio and line communications, radar, electronic instrumentation, microwaves, ultrasonics, vacuum techniques and electromechanical devices; salary according to qualifications and experience, consistent with general present-day levels; there are vacancies for which considerable post-graduate experience is required and others for which previous experience is not necessary; consideration will be given to students taking finals during the current academic year; prospects of promotion are good, and the posts all fall within the Mullard Company's Superannuation Scheme.—Apply Personnel Officer, Mullard Electronic Research Laboratory, Salfords, Nr. Redhill, Surrey. [6883]

SITUATIONS WANTED

AMBITIOUS young man, aged 37, 15 years' exp. in radio, plus 5 years in television, 3 languages, desires progressive post, home or overseas.—Box 3507. [7309]

TELEMETRY engineer, 30, with extensive experience of various radio telemetering systems, both in laboratory and field applications; min. starting salary £700 p.a.—Box 3504, [7504]

APPOINTMENT wanted in electronics/telecommunications engineering in India, Burma or Ceylon, B.Sc. (Eng.) London University, over one year's works training in wireless and mechanical engineering in U.K.—Write A. P. Singh, P.O. Bakshi Bazaar, Monghyr, India. [7280]

Wanted
Binoculars - Prisms - Lenses - Optical Goods.
Any quantity.
BOX NO. 3270
"WIRELESS WORLD," DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

RADIO G200 OFFERS
Type 9B. Rectifiers. 400-415-440 Volts 3P. 50~ input to 36 Volts 50 Amp D.C. output.
Price £35.0.0
TRADE & OVERSEAS ENQUIRIES INVITED
ARTHUR HOILE 55 UNION STREET, MAIDSTONE, KENT Phone 2812

Enquiries invited for ELECTRONIC DEVELOPMENT WORK, MODIFICATION OF ELECTRONIC INSTRUMENTS, REWINDING, TESTING, CALIBRATION and SMALL BATCH PRODUCTION.
ROBERT PRINGLE & SONS (London) Limited
36-42 Clerkenwell Road LONDON, E.C.1
CLerkenwell 2341 (5 lines)

ELECTRONICS DUPLEY LTD.
CRANMER AV. EALING, W.13.
Transformer and Coil Manufacturers to the Trade
Telephone: EALing 6688

BUSINESS OPPORTUNITIES

SOUTH AFRICAN company director now in England wishes to contact British and Continental manufacturers of radar and marine radio and electronic equipment with a view to arranging service and sales facilities in South and East Africa.—Box 3505. [7305]

TECHNICAL TRAINING

E.M.I. gave the world electronic television. E.M.I. is now giving the finest home study television courses; moderate terms—facilities for easy payment; free brochure giving full details on application to the Registrar, Dept. WW7.—E.M.I. Institutes, 10, Pemberton Sq., London, W.2, Baywater, 531-2. [6179]

CITY & Guilds (Electrical, etc.), on "No Pass—No Fees" terms. Over 85% successes. For full details of modern courses in all branches of Electrical Technology send for our 176-page handbook, free and post free.—B.I.E.T. (Dept. 368A), 17, Stratford Place, London, W.1. [6179]

PAINTS, CELLULOSE, ETC.

PAINT spraying handbook 5/6, post free; cellulose and synthetic paints and all spraying requisites supplied; catalogue free.—Leonard Brooks, 53, Harold Wood, Romford. [6207]

TUITION

THE Polytechnic, 309, Regent Street, W.1. A COURSE of six lectures on "Radio Wave Propagation at the Ionosphere" will be given by Mr. L. Precher (Engineer in Division, B.C.C.), on Tuesday evenings, from 6.30 to 8, commencing 16th October, 1951.

A DETAILED Syllabus is available. Application to attend this course should be made as soon as possible to the Head of the Department of Mathematics and Physics, BOROUGH Polytechnic, Borough Road, S.E.1. [7276]

A COURSE of 14 lectures by specialist lecturers on Application of Electronic Instruments to Engineering Problems and Measurements, to be held on Monday evenings at 7 p.m. will begin on Monday October 1st, 1951.

FURTHER particulars and forms of application for enrolment may be obtained from the Secretary. [7214]

MIDDLESEX County Council. Education Committee. **SOUTHALL** Technical College, Beaconsfield Road, Southall.

SPECIAL courses each of 20 weeks duration will be held in Pulse Technique (Thursdays, 7-9 p.m., commencing on 11th October) and Electronic Acoustical Transducers (Mondays, 7-9 p.m., commencing on 8th October). Intending students, who should possess a Higher National Certificate or an equivalent qualification, should enroll before 1st October. The fee is £1 for each course. [7264]

RADIO training.—P.M.G. exams, and I.E.E. Diploma; prospectus free.—Technical College, Hull. [6111]

WIRELESS operating; attendance and postal courses.—Stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7. [6111]

NOTHING succeeds like success! What we have done a thousand times we can do again, for you.—See the B.N.R.S. advt. page 106. [6172]

SEE the world, 600 Radio Officers required; send 2d stamp for prospectus to Britain's leading college; we train most, in shortest period, at lowest cost.—Wireless College, Colwyn Bay.

SAMSONS SURPLUS STORES

38ft. AERIAL MASTS R.H.F. Type 60 Complete kit. Consists of 9 Tubular Sections, Length 4ft. Dia. 2in. Set of pickets. Top plate. Guys and all fittings. Brand New, in canvas carrying case £8/10/-, Carr. 7/6.

SPECIAL OFFER. BRAND NEW TELEPHONE CABLE. Type D3 Single on mille drums 55/-, carr. 5/-.

ALKALINE CELLS. 2.5 v. 21 AH 12/6, carr. 1/6; 2.5 v. 10 AH 10/6, carr. 1/-.

A.M. HEAVY DUTY TRANSFORMERS. Prim. 200-240 v. 50 cy. Sec. 14-20 v. 20 A. 45/-, carr. 2/6. Prim. 100-240 v. 50 cy. Sec. 23, 29, 30, 31 v. 21 A. Prim. 180 v. 240 v. 50 cy. Sec. 4.2 + 4.2 v. 10 A. 25/-, carr. 2/-.

Fl. Transformers. Prim. 200-240 v. 50 cy. Sec. 6.3 v. 15 A. 17/6, carr. 1/6. Prim. 200-240 v. 50 cy. Sec. 6.3 v. 6 A. 5 v. 3 A. 15/-, carr. 1/6. Prim. 200-240 v. 50 cy. Sec. 5.75, 10 v. 5 A. 17/6, carr. 1/6.

30ft. LENGTHS COILS CO-AXIAL CABLE with Pye Sockets on each end 8/6, carr. 1/-.

BRAND NEW 6 mfd. 1500 v. Condensers 5/6, carr. 9d.

169/171 Edgware Road
London, W.2. Tel. PAD. 7851
125 Tottenham Court Road, W.1
Tel. EUS. 4982

All orders and enquiries to our Edgware Road branch, please. Open all day Saturday at the Edgware Road Branch.

TUITION

A.M.I. Mech. E., A.M. Brit. I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% success. For details of examination courses in all branches of engineering, building, etc., write for 176-page handbook—free.—B.I.E.T. (Dept. 367B), 17, Stratford Place, London, W.1. [6118]

NORWOOD Technical College, W. Norwood, London, S.E.27.—Full-time, part-time day and evening courses in radio and television (technology and servicing), radar and line; preparation for following examinations, C. & G., Full Technological, R.T.E.B., Amateur Transmitting Licence, P.M.G.; free telecomm. prospects (A) from the secretary; (170). [6601]

TELEVISION postal course for radio trades Examination Board's diploma; also postal courses for P.M.G. 2nd and 1st class Certificates and Amateur Radio Transmitting licence.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd. London, S.W.9. (40 years' experience in coaching students in wireless telegraphy and allied subjects.) [6124]

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade; enrolments limited, fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [6088]

TYPEWRITING

EXPERT service for all kinds of typewriting and duplicating; highly experienced technical terminology.—Miss Stone, 447, Strand, W.C.2. Term. 5984. [7048]

BOOKS, INSTRUCTIONS, ETC.

I.P.R.E. Technical Publications; 5,000 alignment peaks for superheterodynes, 4/9 post free; The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free; membership and examination data 1/- post free.—Secretary, I.P.R.E., 20, Fairfield Rd. London, N.8. [6089]

SIGNAL AND NOISE GENERATOR.

This Test Set Type 210 has a Range of 20-88 Mc/s in 4 Bands. Output 10M/V, approx. Modulated or unmodulated, Noise generator output 5 Microvolts with attenuator, Crystal controlled, 2 Crystals, Vernier adjustment. Brand new, Input 80 and 115 volts £20, or 230 volts 50 cycles £25.

SIGNAL GENERATORS. I.721, Ex-U.S.A., range 100kc. to 32 Mc/s. In five ranges, 400 cycle modulation, output, 30,000 microvolts for 110-125 volts. A.C. operation. Brand new unused, £19/10/0.

RELAYS

P.O. TYPE 3.000 SIEMENS HIGH SPEED CONTACTS up to 6 changeover. COILS up to 20,000 ohms. Large stocks held. Also: TELEPHONE HANDSETS, JACK SOCKETS, KEY SWITCHES, SLYDLOK FUSES, CONDENSERS Etc. Wholesale only.

L. WILKINSON

19, LANSDOWNE RD., CROYDON, SURREY

YOU READ MUSIC ?

Then how about making yourself an electronic organ. Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 43 valves. With its variable attack you can play Classics and Swing.

Write now for free booklet to: **C. S. Co.,** 10 Duke Street, Darlington, Durham

AUTOMATIC SWITCHES

(RECONDITIONED)
ELECTRIC CLOCKWORK
1 to 100 AMPS. 7 to 35 DAYS
From 35/- EACH
All guaranteed for a year.
Write for illustrated lists:
DONOHUE'S (Timers), 6/2, GEORGE ST., NORTH SHIELDS, NORTHUMBERLAND.

TANNOY PRODUCTS
SOUND EQUIPMENT
clearly the best for all occasions
WEST NORWOOD S.E.27. Tel. GIPsy Hill 1131 (7 lines)



INDEX TO ADVERTISERS

	PAGE		PAGE		PAGE
A.A. Tools	110	Galpins	93	Post Radio Supplies	110
Acoustical Mfg. Co. Ltd.	11	Garland Bros	89	Pratts Radio	92
Adcola Products, Ltd.	56	General Electric Co., Ltd.	13	Premier Radio Co.	49
Aerialite, Ltd.	15	Glaser, L.	112	Pringle, R. & Sons (London), Ltd.	113
Albert Manufacturing Co.	109	Goodmans Industries, Ltd.	8	Profitt, R. W., Ltd.	58
Allan, Richard, Radio, Ltd.	20	Goodsell, Ltd.	2		
Alkham Radio Co.	30	Gramplan Reproducers, Ltd.	42	Quality Mart	102
Ambassador Radio	58	Gray, Arthur, Ltd.	60	Quartz Crystal Co., Ltd.	108
Anders Radio, Ltd.	53				
Antiference, Ltd.	53	Hall Electric, Ltd.	60	Radio Exchange Co.	96
Armstrong Wireless & Television Co., Ltd.	101	Hallam, Seigh & Cheston, Ltd.	34	Radio Merchandise Co., Ltd.	101
Arrow Sales Inc.	103	Harley, H. A., Co., Ltd.	98	Radio Servicing Co.	98
Ashworth, H.	10	Hayes Co., The	100	Radio Supply Co.	92
Ateliers de Constructions Electriques de Charleroi (Belgium)	40	Haynes Radio, Ltd.	24	Radiomenders, Ltd.	114
Audigraph, Ltd.	108	Henley's, W. T., Telegraph Works Co., Ltd.	111	Radiopares, Ltd.	32
Audix, B. B., Ltd.	48	Henry's	94	Rainbow Radio Mfg. Co., Ltd.	51
Automatic Coil Winder & Electrical Equip. Co., Ltd.	1	Hifi, Ltd.	90	Reddon, Ltd.	46
Automatic Telephone & Electric Co., Ltd.	39	Hivac, Ltd.	57	Reliance Mfg. Co. (Southwark), Ltd.	96
A.W.F. Radio Products	62	Hogg, F. Livingston	24	Resound Engineering & Electrical Co. Reproducers & Amplifiers, Ltd.	104
		Holle, Arthur	113	Robinson, F. C., & Partners, Ltd.	59
E. & H. Radio	105	Holley's Radio Stores	96	Rogers Development Co.	8
Bakers "Selhurst" Radio	21	Homelab Instruments	20	Rola Celestion, Ltd.	74
Barker, A. C.	99	Howorth, P.	112	Rollet, H., & Co., Ltd.	112
Belling & Lee, Ltd.	69, 72	H.P. Radio Services, Ltd.	95	Rose, A.	110
Berry's (Short Wave), Ltd.	16	Hunt, A. H., Ltd.	57	Royal Air Force, The	23
Birmingham Sound Reproducers, Ltd.	22, 64				
Bradmatic, Ltd.	42	Iliffe & Sons Ltd.	50	Salford Electrical Instruments, Ltd.	37
Brierley, J. H. (Gramophone & Recordings), Ltd.	50	Imhof, Alfred, Ltd.	4	Samsons Surplus Stores	113
Bristol Cine Service	36	Industrial Electronics	12	Sangamo Weston, Ltd.	75
Britain, Chas. (Radio), Ltd.	95	International Correspondence School, Ltd.	26	Savage Transformers, Ltd.	106
British Communications Corp., Ltd.	44	Jackson Bros. (London), Ltd.	14	Scharf, Erwin	38
British Institute of Engineering Technology	100, 112			Sifan Electrical Instrument Co., Ltd.	46
British Insulated Callenders' Cables, Ltd.	Cover ii	Lasky's Radio	84, 85	Simon Sound Service	63
		Lawces, Liverpool, Ltd.	90	Smith, G. W. (Radio), Ltd.	99
British National Radio School	106	Leak, H. J. & Co., Ltd.	77	Smith, H. L. & Co., Ltd.	110
British Sarozal, Ltd.	98	Lewis Radio, Co.	102	Solartron Laboratory Instruments, Ltd.	16
British Physical Laboratories	38, 48	Lockwood & Co.	50	Sound Rentals, Ltd.	112
Broadcaster Radio Supplies, Ltd.	4	London Central Radio Stores	56	Southern Radio Supply, Ltd.	109
Brookes Crystals, Ltd.	107	Lowther, Mfg. Co.	26	Spencer West	108
Brown, S. G., Ltd.	54	L.R. Supply Company, Ltd.	109	Stability Radio Components, Ltd.	20
Buchan, A. E.	96	Ludfry, Ltd.	108	Standard Telephones & Cables, Ltd.	47, 67
Bulgin, A. F. & Co., Ltd.	60, Edit.	Lyons Radio	108	Stearite & Porcelain Products, Ltd.	45
Bull, J. & Sons	103			Stern Radio, Ltd.	86, 87
Bullers, Ltd.	55	Mail Order Supply Co.	85	Sugden, A. R., & Co. (Engineers), Ltd.	30
Cabot Radio Co., Ltd.	100	Marconi Instruments, Ltd.	34	Suzacols	107
Candler System Co.	107	Marconi's Wireless Telegraph Co., Ltd.	59, 74	Szymanski, S.	46
Champion Products	102	Marconiphone Co., Ltd., The	73		
Chapman, C. T. (Reproducers), Ltd.	56	Mayco Electric	92	Taylor Electrical Instruments, Ltd.	5
Cinema-Television, Ltd.	27	McElroy-Adams Mfg. Group, Ltd.	8, 95	Taylor, Tunnelliff (Refractories), Ltd.	19
Clayton-Wright, Howard, Ltd.	58	McMurdo Instruments Co., Ltd.	53	Telecraft, Ltd.	18, 112
Clydesdale Supply Co., Ltd.	91	Measuring Instruments (Pullin), Ltd.	52	Telegraph Condenser Co., Ltd.	Cover iii
Cohen, D.	82	Metro Pex, Ltd.	14	Telegraph Construction & Maintenance Co., Ltd., The	51
Cosmocond, Ltd.	68	Metropolitan-Vickers Electrical Co., Ltd.	9	Tele-Radio (1943), Ltd.	22
C.S. Company	113	Midland Instrument Co.	103	Telection, Ltd.	10
Davis, Alec, Supplies, Ltd.	62, 111	Miers, N. & Co., Ltd.	44	Thermonic Products Ltd.	6
Davis, Jack (Relays), Ltd.	114	Modern Book Co.	105	Thorn Electrical Industries, Ltd.	25
Day, Will, Ltd.	114	Modern Electrics, Ltd.	24	Transradio, Ltd.	46
Donohoe's (Timers)	113	M.R. Supplies, Ltd.	36	Trix Electrical Co., Ltd.	Edit. 379
Drayton Regulator & Instrument Co., Ltd.	32	Mullard, Ltd.	3, 65, 66		
Du Bois Co., Ltd., The	54	Multicore Solders, Ltd.	Cover iv	Ultra Electric, Ltd.	22
Dubiller Condenser Co. (1925), Ltd.	7	Mycalex, Ltd.	40	United Insulator Co., Ltd.	10
Duke & Co.	107			Universal Electrical Instruments Corp.	92
Duple Electronics, Ltd.	113	New Electronic Supplies Co.	102	University Radio, Ltd.	88
Edison Swan Electric Co., Ltd.	43	Newman, J. & S., Ltd.	36		
Egen Electric, Ltd.	62	Northern Polytechnic	111	Valradio, Ltd.	28
Electradix Radios	106	Northern Radio Services	109	Venner Accumulators, Ltd.	70
Electro Acoustic Developments	94	Northern Transformers Co.	104	Verdik Sales, Ltd.	32
Electro Technical Assemblies	38	N.S.F. Ltd.	35	V.E.S. Wholesale Services, Ltd.	60
Electronic Instruments, Ltd.	40	Nusound Products	105	Vitavox, Ltd.	34
Electronic Precision Equipment	78, 79, 80	Oak Electric Co.	58	Voigt Patents, Ltd.	112
E.M.G. Handmade Gramophones, Ltd.	104	Odde, Bradbury & Cull, Ltd.	52	Vortexion, Ltd.	71
E.M.I. Institutes	28	Olympic Components	92		
English Electric Co., Ltd., The	29	Osmor Radio Products, Ltd.	34	Walton's Wireless Stores	94
Erskine Laboratories, Ltd.	61	Painton & Co., Ltd.	17	Waveforms, Ltd.	42
Eta Tool Co. (Leicester), Ltd.	26	Park Radio, Ltd.	28	Wells, A. & Co., Ltd.	59
Expert Gramophones, Ltd.	61	Parmeko, Ltd.	28	Westinghouse Brake & Signal Co., Ltd.	50
Farmer, John	103	Partridge Transformers, Ltd.	18	Weymouth Radio Mfg. Co., Ltd., The	30
Field, Norman H.	112	Pearce, T. W.	97	Wharfedale Wireless Works	48, 56
Fluxite, Ltd.	105	Pennine Amplifiers	106	Whiteley Electrical Radio Co., Ltd.	76
Frith Radiocraft, Ltd.	52	Pitman, Sir Isaac & Sons, Ltd.	100	Wilco Electronics	104
Furzehill Laboratories, Ltd.	54	Porchester Electrical Supply Co., Ltd.	111	Wilkinson, I.	113
				Wright & Weaire, Ltd.	41
				Young, C. H.	94



RELAYS AND KEY SWITCHES

LARGEST EX-GOVT. STOCK IN GT. BRITAIN

Types 600-3000 Relays — Siemens High Speed
Also A.C. 400 volts 50 cycles

Unselector Switches, Telephone Switch-boards, Telephone Components
Plugs, Jacks, Handsets — Government Contractors.

JACK DAVIS (RELAYS) LTD. (DEPT. W.)
36 PERCY STREET, LONDON, W. 1

Phones: MUSEum 7960 LANgham 4821

RADIOMENDERS LIMITED

FOR SPECIAL TRANSFORMERS AND REWINDS

We specialize in


AMATEURS' WINDINGS, TRANSFORMERS
ALL TYPES, CHOKES, PICK-UP COILS,
INSTRUMENT COILS, Etc.

Highest Workmanship ★ Good Delivery

RADIOMENDERS LTD.,
Television and Radio Apparatus, Transformer and Coilwinders,
123-5-7 Parchmore Road,
THORNTON HEATH, SURREY.
LIV 2261. Trade enquiries invited. Established 16 years.

Condenser leadership -from the inside!

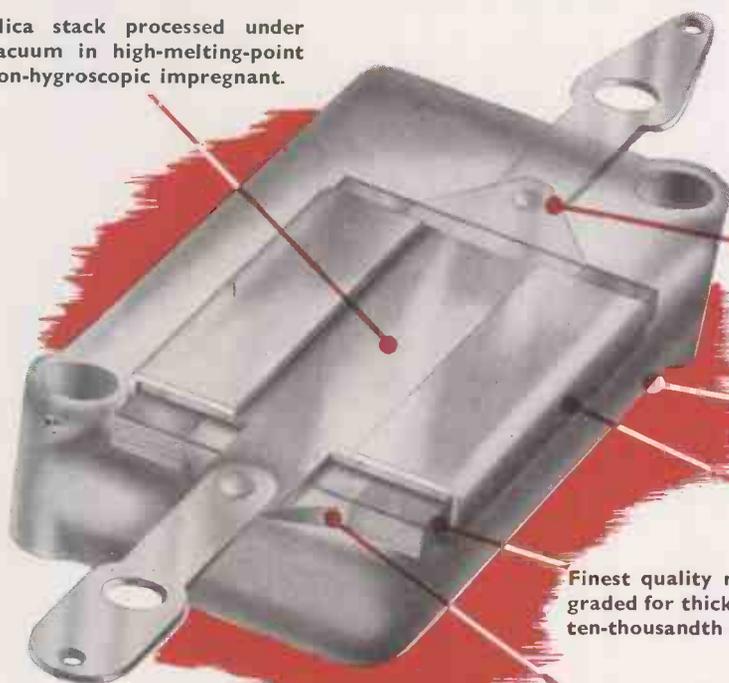Mica stack processed under vacuum in high-melting-point non-hygroscopic impregnant.



Hot tinned soldering tags, positively spot welded to electrodes.

Moulding of high grade low-loss material.

Robust steel clamping plate to maintain stability.

Finest quality mica blades graded for thickness to one ten-thousandth of an inch.

Precision laid electrodes of heavy gauge material providing ample current rating and mechanical strength.



THE original T.C.C. 'M' Type moulded mica condensers — known the world over since the earliest days of radio — are now available in a wide range of capacities from .00005 μ F to .01 μ F and voltages from 350v. DC to 2,500v. DC working. Their construction ensures low power factor and high insulation resistance.

Their ample current rating renders them ideally suitable for low power R.F. conditions such as are encountered in Signal Generators, Portable Transmitters, R.F. Measuring Instruments, etc.

As an alternative to the tag terminations shown, the complete range is available with wires $1\frac{1}{2}$ " long.

Temperature range -40° C. to $+71^{\circ}$ C.




STACKED FOIL MOULDED MICA CONDENSERS

MEET US ON STAND 97
at the RADIO SHOW

THE TELEGRAPH CONDENSER CO. LTD · RADIO DIVISION · LONDON · W.3 · Tel: Acorn 0061 (9 lines)

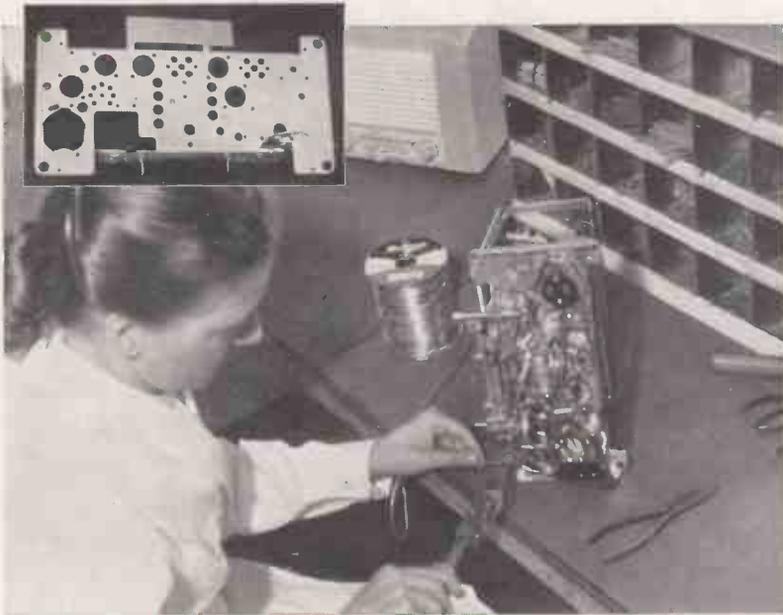The *first* radio receiver assembled, soldered & tested at a National Radio Show



Probably the largest working exhibit and certainly one of the most remarkable displays ever seen at a Radio Show attracted thousands of interested spectators to the Ersin Multicore Stand at Earls Court. They saw staff from E. K. Cole Ltd.'s Southend-on-Sea Works *actually manufacturing* EKCO Radio Sets from the assembly of the parts to the installation of the completed chassis in the cabinet.

The speed and precision with which these skilled operatives soldered every joint was one of the outstanding features of the display—and a practical demonstration of the wisdom of E. K. Cole Ltd.'s choice of solder for the job—ERSIN MULTICORE—the finest cored solder in the world.

From start to finish, every stage in the manufacture of EKCO Radio Sets was watched with great interest by visitors to the Ersin Multicore Solder Stand.

These three factors influenced E. K. Cole Ltd. and other leading television and radio manufacturers throughout the world to choose ERSIN MULTICORE SOLDER :

- Its 3-core construction, ensuring quicker melting, guaranteed flux continuity and speedier soldering without waste.
- The flux contained in the three cores—Ersin, a high-grade rosin specially activated to prevent oxidation and to remove oxides from metal surfaces.
- The fact that every joint made with Ersin Multicore is a perfect electrical connection and will remain sound and free from corrosion during the life of the equipment.

Ersin Multicore Solder

The Finest Cored Solder in the World

SIZE 1 CARTONS 5/- RETAIL

Catalogue Ref. No.	Alloy Tin/Lead	S.W.G.	Approximate length per carton
C 16014	60/40	14	13 feet
C 16018	60/40	18	37 feet
C 14013	40/60	13	13 feet
C 14016	40/60	16	26 feet



MULTICORE SOLDERS LTD., MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1 • REGent 1411